

TELEVISION


SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

316
(17½ new pence)

JANUARY
1971

HOLOGRAPHY

3-DIMENSIONAL DISPLAY

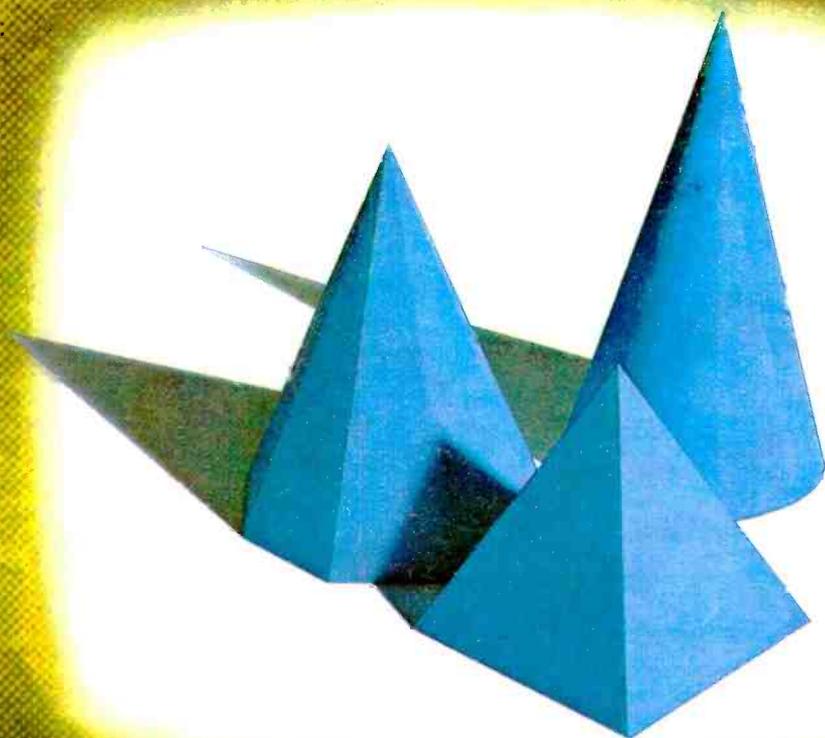

also SYNCHRONOUS DETECTORS • BAND III PREAMP
SERVICING THE BAIRD 620-640 SERIES

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone 01-722 9090

0A2	0-30	6B1H6	0-43	68A7GT	12AV6	0-28	30L1	0-32	7193	0-53	DK95	0-37	EC189	0-48	EL86	0-40	1W4/350	0-38	PCL82	0-37	0-83	UY85	0-29	
0B2	0-30	6B1J6	0-43	68A7GT	12AX7	0-28	30L15	0-64	7475	0-70	DL92	0-35	EC28040-58	EL91	0-23	KT74	0-63	1W4/500	0-38	PCL84	0-38	0-83	U10	0-45
0Z4	0-23	6BQ5	0-28	68A7M	12AY7	0-88	30L17	0-78	A1834	1-00	DL92	0-32	EC28071-35	EL95	0-35	KT76	0-63			PCL86	0-38	0-83	U12/14	0-38
1A3	0-23	6BQ7A	0-38	68C7GT	12BA6	0-30	30P4MR		A2134	0-98	DL94	0-29	EC28080-33	EM80	0-38	KT78	1-70			PCL88	0-43	0-83	U16	0-75
1A5	0-25	6BR7	0-79		12BB6	0-30			A3042	0-75	DL96	0-37	EC28082-33	EM81	0-42	KT44	1-00			PEN45	0-35	0-83	U17	0-35
1A7GT	0-37	6BR8	0-83	68G7GT	12BH7	0-40	30P12	0-89	AC044	1-18	DM70	0-30	EC28084-10	EM87	0-38	KTW620-50				PEN45DD	R20	0-59	U22	0-89
1D5	0-38	6BW7	0-79		12K1	0-85	30P19/30P4		AC2/PEN/		DM71	0-38	EC28042-10	EM87	0-38	KTW630-50				PEN45DD	R20	0-59	U25	0-65
1D6	0-48	6BW6	0-72	68H7	0-53	12K15	0-50		DD	0-98	DW4/350	0-38	EC2811-63	EY51	0-37	MR162	0-83			PF1200-59	UARC80	0-83	U49	0-59
1FD1	0-35	6BW7	0-85	68J7	0-35	12K17GT			DD	0-98	DW5/300	0-38	EC2813-63	EY81	0-35	M14000-74				PL33	0-38	0-83	U50	0-28
1FD9	0-22	6BZ6	0-33	68K7GT		12Q7GT	0-34		DD	0-98	DW5/300	0-38	EC2814-63	EY83	0-55	MHL4	0-75			PL36	0-48	0-83	U76	0-24
1H5GT	0-35	6C6	0-19		12Q7GT		0-28		AC6/PEN/		DY84/7	0-28	EC2818-63	EY84	0-50	MHL16				PL81	0-48	0-83	U82	0-28
1L4	0-13	6C9	0-73	68Q7GT		12R7GT	0-28		AC/PEN(7)	0-38	DY84/7	0-28	EC2819-63	EY88	0-43	N78	2-02			PL82	0-33	0-83	U87	0-22
1LD5	0-30	6CD9G	1-15		12S7GT	0-28	12S7GT	0-28	30PL14	0-75	EM87	1-20	EC2820-35	EY91	0-53	N108	1-40			PL83	0-33	0-83	U91	0-63
1LN5	0-40	6C1H6	0-38	6UJ4GT	0-60				35A5	0-50	EM87	1-20	EC2821-35	EY91	0-53	N108	1-40			PL84	0-33	0-83	U92	0-63
1N5GT	0-39	6CL6	0-43	6U7G	0-53	12S7GT	0-28		35A5	0-75	EM87	1-20	EC2822-35	EY91	0-53	N108	1-40			PL85	0-33	0-83	U93	0-63
1R5	0-28	6CV4	0-83	6V6G	0-18	12S7GT	0-28		35D5	0-70	EM87	1-20	EC2823-35	EY91	0-53	N108	1-40			PL86	0-33	0-83	U94	0-63
184	0-24	6D6	0-15	6V6GT	0-33	12S7GT	0-28		35L8GT		EM87	1-20	EC2824-35	EY91	0-53	N108	1-40			PL87	0-33	0-83	U95	0-63
185	0-22	6F1	0-63	6X4	0-22	12S7GT	0-28			0-44	EM87	1-20	EC2825-35	EY91	0-53	N108	1-40			PL88	0-33	0-83	U96	0-63
1U4	0-28	6F6	0-63	6X5GT	0-25	12S7GT	0-28			0-44	EM87	1-20	EC2826-35	EY91	0-53	N108	1-40			PL89	0-33	0-83	U97	0-63
1U5	0-48	6F6G	0-25	6Y6G	0-55	12S7GT	0-28			0-44	EM87	1-20	EC2827-35	EY91	0-53	N108	1-40			PL90	0-33	0-83	U98	0-63
2D21	0-35	6F12	0-17	6Y7G	0-63		0-50			0-50	EM87	1-20	EC2828-35	EY91	0-53	N108	1-40			PL91	0-33	0-83	U99	0-63
2A4	0-20	6F13	0-33	7B6	0-58	14H7	0-48			0-24	EM87	1-20	EC2829-35	EY91	0-53	N108	1-40			PL92	0-33	0-83	U100	0-63
2A5	1-00	6F15	0-85	7B7	0-35	14H7	1-15			35Z5GT	EM87	1-20	EC2830-35	EY91	0-53	N108	1-40			PL93	0-33	0-83	U101	0-63
3B7	0-25	6F18	0-45	7C6	0-30	19A5	0-24			0-30	EM87	1-20	EC2831-35	EY91	0-53	N108	1-40			PL94	0-33	0-83	U102	0-63
3D6	0-19	6F23	0-72	7F8	0-63	19H1	2-00			0-30	EM87	1-20	EC2832-35	EY91	0-53	N108	1-40			PL95	0-33	0-83	U103	0-63
3Q4	0-38	6F24	0-88	7H7	0-28	20D1	0-55			0-30	EM87	1-20	EC2833-35	EY91	0-53	N108	1-40			PL96	0-33	0-83	U104	0-63
3Q5GT	0-35	6F25	0-85	7H7	0-28	20D1	0-55			0-30	EM87	1-20	EC2834-35	EY91	0-53	N108	1-40			PL97	0-33	0-83	U105	0-63
3S4	0-28	6F28	0-70	7H7	0-28	20D1	0-55			0-30	EM87	1-20	EC2835-35	EY91	0-53	N108	1-40			PL98	0-33	0-83	U106	0-63
3V4	0-32	6F32	0-15	9B5W6	0-50	20L1	0-98			0-30	EM87	1-20	EC2836-35	EY91	0-53	N108	1-40			PL99	0-33	0-83	U107	0-63
5R4Y	0-53	6H6GT	0-15	9I7	0-78	20P1	0-88			0-30	EM87	1-20	EC2837-35	EY91	0-53	N108	1-40			PL100	0-33	0-83	U108	0-63
5V4G	0-38	6J5G	0-19	10C1	1-25	20P3	0-90			0-30	EM87	1-20	EC2838-35	EY91	0-53	N108	1-40			PL101	0-33	0-83	U109	0-63
5Y3GT	0-28	6J6	0-18	10C2	0-50	20P4	0-72			0-30	EM87	1-20	EC2839-35	EY91	0-53	N108	1-40			PL102	0-33	0-83	U110	0-63
6Z3	0-45	6J7G	0-24	10D1	0-56	20P5	1-00			0-30	EM87	1-20	EC2840-35	EY91	0-53	N108	1-40			PL103	0-33	0-83	U111	0-63
6Z4G	0-35	6L8GT	0-58	10R2	0-74	25A5GT	0-28			0-30	EM87	1-20	EC2841-35	EY91	0-53	N108	1-40			PL104	0-33	0-83	U112	0-63
6S0L2	0-58	6K7G	0-10	10F1	0-75	25L6G	0-28			0-30	EM87	1-20	EC2842-35	EY91	0-53	N108	1-40			PL105	0-33	0-83	U113	0-63
6A8G	0-33	6K7GT	0-23	10F9	0-45	25V5	0-38			0-30	EM87	1-20	EC2843-35	EY91	0-53	N108	1-40			PL106	0-33	0-83	U114	0-63
6AC7	0-15	6K8G	0-20	10F18	0-35	25V5G	0-43			0-30	EM87	1-20	EC2844-35	EY91	0-53	N108	1-40			PL107	0-33	0-83	U115	0-63
6AG5	0-25	6L1	0-98	10L11	0-53	25Z4G	0-30			0-30	EM87	1-20	EC2845-35	EY91	0-53	N108	1-40			PL108	0-33	0-83	U116	0-63
6AK5	0-25	6L6GT	0-38	10P13	0-85	25Z5	0-40			0-30	EM87	1-20	EC2846-35	EY91	0-53	N108	1-40			PL109	0-33	0-83	U117	0-63
6AK6	0-30	6L7GT	0-38	10P14	1-10	25Z6G	0-43			0-30	EM87	1-20	EC2847-35	EY91	0-53	N108	1-40			PL110	0-33	0-83	U118	0-63
6AM6	0-17	6L8	0-45	10P18	0-33	30C1	0-30			0-30	EM87	1-20	EC2848-35	EY91	0-53	N108	1-40			PL111	0-33	0-83	U119	0-63
6AQ5	0-23	6L19	0-38	12A6	0-63	30C15	0-65			0-30	EM87	1-20	EC2849-35	EY91	0-53	N108	1-40			PL112	0-33	0-83	U120	0-63
6AR6	1-00	6L20	0-48	12AC6	0-40	30C17	0-80			0-30	EM87	1-20	EC2850-35	EY91	0-53	N108	1-40			PL113	0-33	0-83	U121	0-63
6AT6	0-20	6N7GT	0-40	12AD6	0-40	30C18	0-64			0-30	EM87	1-20	EC2851-35	EY91	0-53	N108	1-40			PL114	0-33	0-83	U122	0-63
6AU6	0-25	6P28	1-25	12AE8	0-48	30F5	0-80			0-30	EM87	1-20	EC2852-35	EY91	0-53	N108	1-40			PL115	0-33	0-83	U123	0-63
6AV6	0-30	6Q7	0-43	12AT6	0-23	30PL1	0-64			0-30	EM87	1-20	EC2853-35	EY91	0-53	N108	1-40			PL116	0-33	0-83	U124	0-63
6B8C	0-13	6Q7G	0-30	12AT7	0-19	30PL2	0-75			0-30	EM87	1-20	EC2854-35	EY91	0-53	N108	1-40			PL117	0-33	0-83	U125	0-63
6BA6	0-23	6R7	0-55	12AU6	0-24	30PL12	0-80			0-30	EM87	1-20	EC2855-35	EY91	0-53	N108	1-40			PL118	0-33	0-83	U126	0-63
6BE6	0-24	6R7G	0-35	12AU7	0-23	30PL14	0-73			0-30	EM87	1-20	EC2856-35	EY91	0-53	N108	1-40			PL119	0-33	0-83	U127	0-63

EC33	1-58	EL32	0-18	1W4/350		PCL82	0-37	0-83	UY85	0-29
EC40	0-60	EL34	0-52			PCL83	0-52		U10	0-45
EC41	0-19	EL37	0-97	1W4/500		PCL84	0-38		U12/14	0-38
EC82	0-23	EL41	0-55			PCL803/85			R11	0-98
EC83	0-23	EL42	0-53	KT2	0-25		0-45		R16	1-75
EC84	0-30	EL81	0-50	KT8	1-73	PCL86	0-43		R17	0-88
EC85	0-28	EL83	0-38	KT41	0-98	PCL88	0-78		R18	0-50
EC86	0-40	EL84	0-24	KT44	1-00	PEN45	0-35		R19	0-33
EC88	0-35	EL85	0-40	KT63	0-25	PEN45DD			R20	0-59
EC189	0-48	EL86	0-40	KT66	0-83		0-75		R22	0-38
EC28040-58	EL91	0-23	KT74	0-63		PEN46	0-20		RK34	0-38
EC28071-35	EL95	0-35	KT76	0-63		PEN45DD			SP42	0-75
EC28080-33	EM80	0-38	KT78	1-70			0-88		SP61	0-33
EC28082-33	EM81	0-42	KT44	1-00		PEN45	0-35		TH48	0-50
EC28084-10	EM87	0-38	KTW620-50			PENDD			TH233	0-98
EC2811-63	EY51	0-37	MR162	0-83			4020	0-88	TP260	0-88
EC2813-63	EY81	0-35	M14000-74			PF1200-59			UARC80	0-83
EC2814-63	EY83	0-55	MHL4	0-75		PL33	0-38		U50	



MAKES 4 DIFFERENT RADIOS + AMPLIFIER Limited Quantity **39/6**

Amazing Radio Construction set! Become a radio expert for 39/6. A complete Home Radio Course. No experience needed. Parts including instructions for each design. Step-by-step plan, all Transistors, loud speaker, personal 'phone, knobs, screws, etc., all you need. Presentation box size 14" x 10" x 2" 5/8 extra (parts available separately). Send only 39/6 + 4/6 P. & P. Money back guaranteed.


REAL WORKING ELECTRONIC ORGAN



Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorized—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas," play "Silent Night," play "Auld Lang Syne," play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13 1/2" x 10" x 2 1/4".

Uses standard battery. You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER.** No soldering necessary. Anyone from nine years upwards can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low, low price. **ONLY 55/- + 4/6 P. & P.** for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformers, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone Money back guarantee.

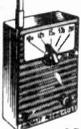EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS. JUST OUT V.H.F. AIRCRAFT BAND CONVERTER only 47/6



Countless thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JET PLANES. Eavesdrop on exciting cross-talk between pilots, ground approach, ground control, airport tower. Hear for yourself the disciplined voices hiding tensions on talk-downs. Be with them when they have to take nerve-ripping decisions in emergencies—Tune in to the international distress frequency. Covers the whole aircraft frequency band including **HEATHROW - GATWICK, LUTON, BINGWAY, PRESTWICK ETC. ETC. CLEAR AS A BELL.** This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worked instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/4". All you do is extend rod aerial, place close to any ordinary medium-wave radio—even six transistor portables) **NO CONNECTIONS WHATSOEVER NEEDED.** Use indoors or outdoors. **THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW. ONLY 47/6** for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately). Money back guarantee.

CONCORD ELECTRONICS LTD. (TV11) 8 Westbourne Grove London W.2. (Nr. Bayswater tube) • Callers Wel. 9-6 inc. Sat.

Available now!



175 Naval Apprenticeships

Every six months the Navy needs 175 hand-picked men to train as its future top technicians. You could be one of the next 175. But apply early. Send now for the free booklet, all about Artificer Apprenticeships. It tells you how the Navy gives you one of the finest engineering trainings in the world.

And look what it means: You become the man in charge of advanced modern equipment in ships, submarines and helicopters—like electronic systems, computers, radar, missiles, gas and steam turbines.

The Navy gives you a full 4-year apprenticeship at its own technical schools. There are plenty of sports and hobbies too. And, during training, you get nine weeks' holiday a year.



Full union status and O.N.C. ensure you a secure, well-paid job for life—in the Navy or out.

You enjoy a life of action—exciting and adventurous, with the chance to see something of the world while you're young.

FIND OUT MORE. To enter the Navy as an Artificer Apprentice you must be 15 1/2-17 1/2 and pass an entry exam. (With 'O' level or C.S.E. Grade 1 in Maths plus one Science subject or English Language, you are exempt from the written part.) If you're 17 1/2-23 you can apply for a Mechanician Apprenticeship. Post the coupon.



In your early twenties you can be a Chief Petty Officer earning over £2,000 a year. And there are very good chances of becoming a commissioned officer.

REBUILT TELEVISION TUBES

STANDARD TYPES:

- 17" £5- 0-0 21" £6- 0-0
- 19" £5-10-0 23" £6-10-0

'PANORAMA' & 'RIMGUARD' TYPES:

- 19" £7- 0-0 23" £9- 0-0

TWIN PANEL or BONDED FACE TYPES:

- 19" £7-10-0 23" £9-10-0

- ★ Complete new gun fitted to every tube.
- ★ Two years' guarantee.
- ★ **Free delivery** by our own transport within 250 miles of London. Over this distance 15/- extra for carriage and insurance (Passenger Train).

We have been rebuilding tubes for the past 12 years and can supply any type including 11", 12", 13", 16", etc. and colour tubes. Trade enquiries invited.

N.G.T. ELECTRONICS LTD.,
22 Anerley Station Road,
London, S.E.20
Telephone: 01-778 9178

Send for free book.

Royal Naval Careers Service (Apprenticeships) (R20GW 1), Old Admiralty Building, London, S.W.1. Please send me full details without obligation.

Name _____
 Address _____

 Date of birth _____
 (Enquiries from U.K. residents only)



STEPHENS

ELECTRONICS,
P.O. BOX 26,
AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded.

GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE

1 YEAR'S GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS

AZ31	10/-	ECF80/2	9/6	EL809	17/-	PC085	8/6	PY83	10/-	UL41	11/6	6AR5	6/6	6EH7	6/6	6G7	6/6	6H7	6/6	12B86	6/6	30P18	7/-
AZ50	12/-	ECF86	11/-	EL821	11/-	PC088	14/-	PY88	8/6	UL84	11/6	6AR6	6/6	6EJ7	7/-	6H7	6/6	6H7	6/6	12B87	6/6	30P19	15/6
CB1L	10/-	ECH35	13/6	EL830	15/-	PC089	12/3	PY500	20/0	UM80/4	9/-	6AR5	7/-	6EW6	12/-	6H7	6/6	6H7	6/6	12B87	10/0	30P21	15/6
CB1S1	17/-	ECM42	13/6	EM34	16/0	PC0189	12/3	PZ30	16/0	UY41	8/-	6AR7G	16/0	6F1	14/-	6H7GT	6/6	6H7	6/6	12K5	10/0	30P13	18/6
CY31	7/-	ECM81	10/3	EM71	12/6	PCF80	10/3	QV02-6	42/-	UY85	6/0	6AT6	6/0	6F5	8/-	6H7GT	6/0	6H7GT	7/0	12K7GT	7/0	30P14	17/0
DAF91	8/3	ECM83	8/3	EM80	8/3	PCF82	10/3	QV03-10	U25	15/-	6A06	5/9	6F9G	5/9	6H7	8/3	6H7	8/3	13Q7G	8/3	35A3	10/0	
DAF96	8/3	ECM84	9/6	EM81	7/6	PCF84	9/6	U25	15/-	6A06	5/9	6F9G	5/9	6H7	8/3	6H7	8/3	13Q7G	8/3	35A3	10/0	35A4	11/0
DF91	9/-	ECL80	8/-	EM84	7/6	PCF86	12/3	QV03-12	13/-	U191	14/6	6BA5	6/6	6F12	4/6	6H7	6/6	6H7	6/6	12M7	7/0	35B6	18/0
DF96	9/-	ECL82	9/6	EM87	11/6	PCF200/1	16/3	R19	13/0	U193	8/3	6BE6	12/3	6F13	7/0	6U4GT	12/6	12M7	7/0	12M7	5/0	35C5	7/0
DK91	11/6	ECL83	11/6	EN91	6/6	PCF801	12/3	R20	15/0	U301	17/0	6BH6	6/6	6F14	12/0	6U8	7/0	12M7	5/0	12M7	5/0	35D5	13/0
DK96	11/6	ECL86	9/6	EY61	6/6	PCF802	12/3	SU2150A	15/0	W729	11/0	6BJ6	8/6	6F15	11/0	6V8GT	6/6	12M7	5/0	12M7	5/0	35L6GT	9/0
DL92	7/6	ECL L800	30/0	EY80	9/0	PCF805	13/0	TT21	48/0	Z769	24/6	6BK7A	10/0	6F18	8/0	6X4	5/0	12M7	5/0	12M7	5/0	35W4	5/0
DL94	7/6	EF39	10/6	EY81	9/0	PCF806	12/3	TT22	50/0	0A2	6/0	6BL8	7/0	6F22	6/6	6X5GT	5/6	12M7	5/0	12M7	5/0	35Z3	11/0
DL96	9/6	EF60	8/0	EY83	11/0	PCF808	13/6	U18/20	13/6	0A3	5/0	6BN5	8/6	6F23	15/6	6X8	11/0	12M7	5/0	12M7	5/0	35Z4	11/0
DM70	6/6	EF83	10/0	EY86	8/0	PCF820	14/0	U20	13/6	0B2	6/6	6BN6	8/0	6F24	15/6	6Y8G	12/0	12M7	5/0	12M7	5/0	35Z6GT	7/6
DY86/7	8/0	EF85	8/8	EY87	8/6	PCL82	10/3	U25	15/0	0B3	10/0	6BQ5	5/0	6F25	15/0	7Y4	12/0	1487	16/0	50A5	13/0		
DY802	8/6	EF86	13/3	EY88	8/6	PCL83	12/3	U26	15/0	0C3	7/0	6BR7	15/0	6F26	14/0	9B6	6/6	20D1	9/0	50B5	7/0		
E55L	55/-	EF89	8/0	EZ35	5/6	PCL84	10/3	U31	9/0	OD3	6/6	6BR8	10/0	6F28	14/0	10C2	10/0	20L1	20/0	50C5	7/0		
E88CC	8/0	EF91	8/6	EZ40	9/0	PCL85	10/6	U37	30/0	3Q4	7/0	6BW6	16/6	6F29	6/0	10D1	8/0	20P1	10/0	50L6GT	3/0		
E130L	90/-	EF92	10/0	EZ41	9/0	PCL86	10/6	U60	6/0	384	8/0	6B37	13/0	6F30	7/0	10D2	8/0	20P3	12/0	83A1	18/0		
E130F	19/0	EF93	10/0	EZ60	6/6	PCF600	30/6	U62	6/0	3V4	6/0	6BX6	5/0	6J4	9/6	10F14	20/0	30A5	8/0	812A	60/0		
EABC80	10/6	EF94	15/6	EZ61	6/6	PL200	14/0	U78	6/6	6BAGY	11/0	6B26	6/6	6J5GT	6/6	10F9	10/0	20P6	20/0	90A9	45/0		
EAF42	10/6	EF95	12/6	EZ90	5/0	PL36	12/6	U78	5/0	5U4G	6/0	6C4	6/0	6J7	6/0	10F18	8/0	25C6	9/0	90C1	12/0		
EBC33	11/0	EF183	11/3	GB10C	100/0	PL38	18/0	U191	15/0	5U4GB	7/6	6C5GT	7/0	6K6GT	10/0	10L1	8/0	25L6GT	7/6	90CV	25/0		
EBC41	9/6	EF184	7/6	GY501	10/3	PL81	10/3	U201	7/0	5V4G	8/6	6C6GT	28/0	6K7	6/0	10LD11	11/0	25Z4G	6/0	807	9/6		
EBC81	6/6	E280F	42/0	GZ30	7/6	PL81A	12/6	U281	8/0	5Y3GT	6/0	6CA4	5/6	6K8G	6/0	10P13	11/0	25Z8GT	10/0	811A	30/0		
EBC80	9/6	EF800	20/0	GZ31	6/6	PL82	7/6	U282	8/0	5Z3	6/0	6CA7	10/6	6K23	10/0	10P14	20/0	30A5	8/0	812A	60/0		
EBF80	6/6	EF804	20/0	GZ32	9/6	PL83	10/6	U301	11/6	5Z4GT	6/0	6CB3	6/0	6K2C	6/0	12A3B	3/0	30A3	8/0	813	7/6		
EBF83	8/0	EF811	15/0	GZ33	11/6	PL84	8/3	U403	10/0	6/80L2	15/0	6CD6GA	23/0	6L6GT	9/0	12AC8	7/6	30C15	15/0	866A	14/0		
EBF89	8/0	EL34	10/6	GZ34	11/0	PL500	16/6	U404	7/6	6AB4	6/6	6CG7	9/0	6L7	6/0	12AD6	7/6	30C17	16/0	5542	12/0		
EB91	5/3	EL36	9/6	HK90	6/0	PL504	17/0	U801	20/0	6AP4A	9/6	6CH6	11/0	6L18	8/0	12A15	8/0	30C18	15/0	6180	27/6		
EC53	10/0	EL41	11/0	HL92	7/0	PL505	29/0	UABC80	10/6	6AG7	7/6	6CL6	10/0	6LD20	6/6	12AQ5	3/0	30F5	17/0	6400	30/6		
EC86	12/0	EL42	11/6	HL94	8/0	PL608	20/0	UBF99	8/0	6A16	10/0	6CW4	12/6	6N7GT	7/0	12AT6	5/0	30FL1	15/0	6146B	47/6		
EC86	12/0	EL51	10/0	KT86	27/6	PL569	30/6	U301	11/6	6A18	6/0	6F1	6/0	6P1	6/0	12AV6	21/0	30FL2	18/6	6860	25/6		
EC90	6/0	EL83	8/3	KT88	27/6	PL502	17/6	UC85	9/3	6A15	6/0	6C77	12/0	6P25	21/0	12AV6	6/0	30FL2	18/6	6860	25/6		
EC92	6/6	EL85	8/6	N78	21/0	PL805	17/6	UCH42	13/6	6A16	11/6	6D3	8/0	6P28	18/6	12AV7	9/0	30FL13	10/0	6939	42/0		
EC93	9/6	EL86	8/6	PABC80	8/0	FY33	12/6	UCH81	10/0	6A13	8/6	6DC6	13/6	6Q7	7/6	12AX7	6/0	30FL14	15/6	7199	15/0		
ECC81	8/0	EL90	6/6	PC86/8	10/3	FY80	6/6	UCL82	10/3	6A15	8/3	6DK6	8/6	6R7G	7/0	12AY7	12/6	30L1	7/0	7360	26/0		
ECC82/3	8/6	EL91	5/6	PC95	7/3	FY81	3/3	UCL83	12/3	6AM5	5/6	6DQ6B	12/6	6S2	8/0	12B44	10/0	30L15	17/0	7586	25/0		
ECC84/5	8/6	EL95	7/0	PC97	8/3	FY800	3/3	UF41/2	11/0	6AM6	4/6	6DQ6	6/6	6B94	15/0	12BA6	6/6	30L17	17/0	9002	6/6		
EC85	11/0	EL96	7/0	PC97	8/3	FY801	3/3	UF80/5	6/6	6A15	6/6	6DQ6	6/6	6B94	15/0	12BA7	6/6	30P12	16/0	9003	10/0		
E88CC	12/6	EL360	23/0	PC084	9/3	PY82	7/0	UF89	5/3	6A16	10/0	6EA8	11/0	6BA7	7/6	12BA7	6/6	30P12	16/0	9003	10/0		

SEMICONDUCTORS

BRAND NEW · MANUFACTURERS' MARKINGS · NO REMARKED DEVICES

2N388A	12/6	2N2193A	10/0	2N3055	15/0	2N3854	5/6	2N5176	9/0	40315	9/6	AF106	8/6	BC117	7/8	BCY54	6/6	BF238	6/6	B8X20	3/6
2N404	4/6	2N2194A	4/6	2N3133	6/0	2N384A	5/6	2N5232A	6/0	40316	12/6	AF114	5/0	BC118	6/6	BCY58	4/6	BF257	9/6	B8X21	7/6
2N696	4/0	2N2217	5/6	2N3184	6/0	2N3856	5/6	2N5246	12/6	40317	9/6	AF115	6/0	BC121	4/0	BCY69	4/6	BF22A	9/6	B8X26	9/0
2N697	4/0	2N2218	6/6	2N3185	5/6	2N3855A	6/0	2N5246	12/6	40318	18/6	AF116	5/0	BC122	4/0	BCY69	10/6	BFX12	4/6	B8X27	9/6
2N698	5/0	2N2219	6/6	2N3186	5/6	2N3855	6/0	2N5249	13/6	40320	9/6	AF117	5/0	BC125	11/0	12CV70	4/0	BFX13	4/6	B8X28	6/6
2N699	12/6	2N2220	5/0	2N3340	19/6	2N3856A	7/0	2N5249A	13/6	40323	8/6	AF118	12/0	BC126	11/0	BCY71	8/6	BFX29	7/0	B8X60	16/6
2N706	2/6	2N2221	5/0	2N3349	28/0	2N3858	5/0	2N5265	6/0	40324	11/6	AF119	4/0	BC134	11/6	BCY72	3/6	BFX43	7/6	B8X61	12/6
2N706A	2/6	2N2222	6/0	2N3390	7/6	2N3856A	6/0	2N5266	5/0	40326	11/6	AF124	4/0	BC140	7/6	BY210	5/6	BFX44	7/6	B8X76	4/6
2N708	3/0	2N2287	21/6	2N3391	4/0	2N3859	5/6	2N5287	5/6	40329	7/0	AF125	4/0	BC147	3/0	BCZ11	7/6	BFX48	18/6	B8X77	5/6
2N709	12/6	2N2287	6/0	2N3391A	6/0	2N3859A	6/6	2N5287	5/6	40344	7/0	AF126	4/0	BC148	3/0	BD116	22/6	BFX54	6/0	B8X78	5/6
2N718	5/0	2N2386	3/6	2N3392	4/0	2N3860	6/0	2N5306	8/0	40347	8/6	AF127	3/6	BC149	3/6	BD121	13/0	BFX55	7/0	B8X10	5/6
2N718A	6/0	2N2389	3/6	2N3393	4/0	2N3866	30/0	2N5307	7/6	40348	12/6	AF139	7/6	BC152	3/6	BD123	16/6	BFX56	6/0	B8V11	5/6
2N726	6/0	2N2369A	4/0	2N3394	4/0	2N3877	8/0	2N5308	7/6	40360	11/0	AF178	9/0	BC157	4/0	BD124	12/0	BFX87	6/0	B8Y24	3/0
2N727	6/0	2N2410	8/6	2N3402	4/6	2N3877A	8/0	2N5309	12/6	40361	12/6	AF179	9/0	BC158	3/6	BD131	19/6	BFX88	8/0	BY225	3/0
2N914	3/6	2N2483	5/6	2N3403	4/6	2N3900	7/6	2N5310	8/6	40362	18/6	AF180	10/6	BC159	4/0	BD132	19/6	BFX89	18/6	BY226	3/6
2N916	3/6	2N2484	6/6	2N3404	7/6	2N3900A	8/0	2N5354	5/6	40370	7/6	AF181	8/6	BC160	12/6	BDY10	37/6	BFY10	6/6	BY227	3/6
2N918	6/0	2N2539	4/6																		

SEMICONDUCTORS

continued

GET873	2/6	NKT773	5/-
GET880	6/-	NKT781	6/-
GET887	4/-	NKT10389	9/6
GET889	4/6	NKT10419	6/-
GET890	4/6	NKT10439	7/6
GET896	4/6	NKT10519	6/6
GET897	4/6	NKT20329	9/6
GET898	4/6	NKT80111	
MAT100	6/-		15/6
MAT101	6/-	NKT80113	
MAT120			19/6
MAT121	6/-	NKT80113	
MJ400	21/6		22/6
MJ420	22/6		18/6
MJ421	22/6		18/6
MJ430	20/6	NKT80212	
MJ440	19/-		18/6
MJ480	18/6	NKT80213	
MJ481	25/-		18/6
MJ490	20/-	NKT80214	
MJ491	27/6		18/6
MJ1800	48/6	NKT80215	
MJE340	18/6		18/6
MJE320	17/6	NKT80216	
MJE321	17/6		18/6
MPP102	5/6	OC20	15/-
MPP103	7/6	OC22	10/-
MPP104	7/6	OC23	10/-
MPP105	7/6	OC24	11/6
MPS3058	6/6	OC25	10/-
NKT10013	6/6	OC26	6/6
NKT124	8/6	OC28	12/6
NKT125	5/6	OC29	15/-
NKT126	5/6	OC35	8/-
NKT128	5/6	OC36	12/6
NKT135	5/6	OC41	4/6
NKT137	6/6	OC42	5/-
NKT210	6/-	OC44	4/-
NKT211	6/-	OC45	2/6
NKT212	6/-	OC46	3/-
NKT213	6/-	OC70	2/-
NKT214	4/6	OC71	2/6
NKT215	4/6	OC72	2/6
NKT216	7/6	OC74	6/6
NKT217	5/6	OC75	4/6
NKT219	6/-	OC78	4/6
NKT223	5/6	OC77	5/6
NKT224	5/-	OC78	5/-
NKT225	4/6	OC81	4/-
NKT229	6/-	OC81D	4/-
NKT237	7/-	OC83	5/-
NKT238	6/-	OC84	5/-
NKT240	5/6	OC139	6/6
NKT241	5/6	OC140	6/6
NKT242	4/-	OC189	4/6
NKT243	12/6	OC170	6/-
NKT244	3/6	OC171	6/-
NKT245	4/-	OC200	6/6
NKT261	4/-	OC301	9/6
NKT264	6/-	OC202	9/6
NKT271	4/-	OC203	6/6
NKT272	4/-	OC204	8/6
NKT274	4/-	OC205	8/6
NKT276	4/-	OC207	12/6
NKT281	4/-	OC271	8/6
NKT401	17/6	P346A	4/6
NKT402	18/-	T1834	12/6
NKT403	15/-	T1843	9/-
NKT404	12/6	T1844	2/6
NKT405	15/-	T1845	3/6
NKT406	12/6	T1846	3/6
NKT451	12/6	T1847	3/6
NKT462	12/6	T1848	3/6
NKT453	9/6	T1849	3/6
NKT603F	6/6	T1850	4/6
NKT613F	6/6	T1851	3/6
NKT674F	6/-	T1852	3/6
NKT677F	6/-	T1853	6/-
NKT713	6/-	T1860	6/-
NKT717	6/6	T1861	9/-
NKT734	8/6	T1P29A	12/6
NKT736	7/-	T1P30A	15/-
		T1P31A	16/6

STYLI

ACOS

Sapphire Diamond

GP59	2/6	7/6
GP65	2/6	7/6
GP67	2/6	7/6
GP73-1	6/6	9/6
GP73-2	6/6	9/6
GP79	2/6	7/6
GP81-1	2/6	7/6
GP91-1	6/6	9/6
GP91-2	6/6	9/6
GP91-3	6/6	9/6
GP91-1Sc	6/6	9/6
GP91-3Sc	6/6	9/6
HGP37	2/6	7/6

B.S.R.

BSR CI (ST3)	6/6	9/6
BSR TC8H	2/6	7/6
BSR TC8M	2/6	7/6
BSR ST8	6/6	9/6
BSR ST9	6/6	9/6
BSR ST10	9/-	9/-
BSR X1M	6/6	9/6
BSR X1H	6/6	9/6
BSR X3M	6/6	9/6
BSR X3H	6/6	9/6
BSR X4H	6/6	9/6
BSR X5H	6/6	9/6

COLLARO

Collaro Studio 'O'	2/6	7/6
Collaro-Ronett TX88	2/6	7/6
Collif SK1	2/6	7/6
Dual CDS2/CDS3 (DN2)	6/6	9/6
Dual CDS3/320 (DN3)	6/6	9/6
ELAC KST9 (PE10)	6/6	9/6
ELAC KST9 (PE1B)	6/6	9/6
ER5MB	6/6	9/6
ER5M X	2/6	7/6
ER5 SB	6/6	9/6
ER60 Stereo	6/6	9/6

GARRARD

Sapphire Diamond

EV26 Stereo	2/6	7/6
GC2	2/6	7/6
GC8	2/6	7/6
GCE12	2/6	7/6
GCS10/1	2/6	7/6
GCS10/2	2/6	7/6
S 1-2-3	6/6	9/6
TS1	6/6	9/6
TS2	6/6	9/6
TS3	6/6	9/6

GOLDRING

CM50	2/6	7/6
CM60	2/6	7/6
MX1	2/6	7/6
MX2	2/6	7/6
Stereo CS80	2/6	7/6

PERPETUUM EBNER

PE188	6/6	9/6
-------	-----	-----

PHILIPS

AG3016	2/6	7/6
AG3063	2/6	7/6
AG3306	6/6	9/6
AG3310/3306	6/6	9/6
AG3400	2/6	7/6

RONETTE BINOFLUID

BF40	2/6	7/6
DC284	2/6	7/6

SONOTONE

2T	6/6	9/6
3T	6/6	9/6
8T4A	6/6	9/6
9TA	6/6	9/6
9TA/HC	6/6	9/6
19T	2/6	7/6
20T	2/6	7/6

The Diamond Tip is .007 in. radius, thus making it compatible to play stereo records on mono equipment without damage to the record; and of course full stereo.
BRITISH MADE
EXPORT ENQUIRIES WELCOMED

CARTRIDGES

ACOS

Inc. P.T. each

GP79	12/6
GP91-1SC	21/-
2-11	17/9
12-49	15/6
50-500	13/6
GP91-2SC	As above
GP91-3SC	As above
Suitable to replace TC8, etc.	
GP92	26/5
GP93-1	24/9
GP94-1	31/-
GP94-5	36/-
GP95	24/9
GP96	31/6
Acos 104	41/10
11-25	39/9
25-50	38/3
51-499	35/5

B.S.R.

Inc. P.T. each

X3M	S/S	27/9
X3H	S/S	27/9
X5M	S/S	27/9
X5H	S/S	27/9
SX5M	S/S	36/3
SX5H	S/S	36/3
SX5M	D/S	39/11
SX5H	D/S	39/11
X4N	D/S	27/3

RONETTE

105	S/S	19/10
106	S/S	19/10
DC400	S/S	14/-
DC400SC	S/S	14/-
105	D/S	22/4
106	D/S	22/4
DC400	D/S	16/9
DC400SC	D/S	16/9

SONOTONE

8TA	D/S	25/-
9TA	D/S	35/10
9TAHC	D/S	35/10

CATHODE RAY TUBES

New and Budget tubes made by the leading British manufacturers. Guaranteed for 2 years. In the event of failure under guarantee, replacement is made without the usual time wasting forms and postage expense.

Type	New	Budget	Type	New	Budget
	£	£		£	£
MW36-20		4/10/-	A60-120W/R	10/17/-	
MW36-21		4/10/-	AW63-80	8/18/8	6/5/-
MW43-80Z	6/18/-	4/12/8	AW63-88	8/18/8	6/5/-
MW43-80Z	6/18/-	4/12/8	AW69-80	9/11/8	7/4/-
AW43-80Z	6/18/-	4/12/8	A69-15W		
	6/12/-	4/12/8			
	6/12/-	4/12/8	A69-11W		
	6/12/-	4/12/8	A69-13W	18/18/-	10/19/6
AW43-80	6/12/-	4/12/8	A69-16W	13/18/-	10/19/6
AW47-90	6/12/-	4/12/8	A69-23W	18/18/-	10/19/6
AW47-91	7/18/4	5/7/8	A69-28W/R	18/18/-	10/19/6
A47 14W	CME1901	7/18/4	PORTABLE SET TUBES		
	CME1902	7/18/4	TSD217		6/15/-
	CME1903	7/18/4	TSD282		6/15/-
	C19AH	7/18/4	A28-14W	9/8/4	Not supplied
A47 13W	CME1906	10/6/8			
A47-11W	CME1905	8/17/8			
A47-26W	CME1905	8/17/8			
A47-26W/R	CME1913R	9/6/8			

A discount of 10% is also given for the purchase of 3 or more New tubes at any one time. All types of tubes in stock. Carriage and Insurance 15/-.

TRANSISTORISED UHF TUNER UNITS NEW AND GUARANTEED FOR 3 MONTHS

Complete with Aerial Socket and wires for Radio and Allied TV sets but can be used for most makes. Continuous Tuning, 90/-; Push Button, 100/-.

PLUGS

Jack Plugs and Sockets	8/10	Co-Axial Plugs	
Standard Plugs	8/10	Belling Lee (or similar type)	1/8
Standard Sockets	2/6	Add 5d. per doz. p. & p.	

DE BANKS MAGNETIC RECORDING TAPES

POLYBSTER	Spool Size in.	Price
Length		
Standard Play		
600 ft.	5	10/-
850 ft.	5	12/6
1200 ft.	7	14/-
Long Play		
210 ft.	3	5/6
450 ft.	4	8/6
900 ft.	5	14/-
1800 ft.	5	17/-
1800 ft.	5 1/2	17/-
Double Play		
1200 ft.	5	17/6
1800 ft.	5 1/2	22/-
2400 ft.	7	28/-

EMPTY TAPE REELS

CASSETTES

8 in. 1/6	Boxed in Plastic Library Packs
4 in. 1/10	C60 10/6
6 in. 2/8	C90 12/6
5 1/2 in. 2/6	C120 17/6
7 in. 2/7	

P. & P. 1/6 on all orders.

WILLOW VALE ELECTRONICS LIMITED

The Service Department Wholesalers

Compare our prices

e.g. NEW 19" C.R.T's . . . OUR PRICE £5.19.0 Plus 12/6 carriage

Please note: Components are sold in packs, quantities per pack are shown under each heading. Prices are per piece of each value.

TUBULAR CAPACITORS

(3's)			
-001	400v.	9d.	
-0022	600v.	9d.	
-0033	600/1500v.	9d.	
-0047	600/1500v.	9d.	
-01	400v.	10d.	
-022	600v.	11d.	
-033	600v.	11d.	
-047	600v.	11d.	
-1	600v.	1/0d.	
-22	600v.	2/0d.	
-47	600v.	2/10d.	
-01	1000v.	1/1d.	
-022	1000v.	1/1d.	
-047	1000v.	1/8d.	
-1	1000v.	1/8d.	
-22	1000v.	2/8d.	
-47	1000v.	3/8d.	
-001	1500v.	1/6d.	

WIRE-WOUND RESISTORS

(3's)			
10	Ohm	1/9d.	
10	Ohms	1/9d.	
13	"	1/9d.	
25	"	1/9d.	
33	"	1/9d.	
50	"	1/9d.	
87	"	1/9d.	
100	"	1/9d.	
150	"	1/9d.	
220	"	1/9d.	
330	"	1/9d.	
1K	"	1/9d.	
2.2K	"	1/9d.	
3.3K	"	1/9d.	
4.7K	"	1/9d.	

PULSE CERAMICS (3's) 12KV

100pf	22pf	1/1d.
120pf	47pf	1/1d.
180pf	68pf	1/1d.
250pf		1/1d.

Tubular type for use in Scan correction circuits and Line Outputs.

CERAMICS (6's)

500pf	22pf	8d.
680pf	47pf	8d.
820pf	68pf	8d.
1000pf	100pf	8d.
1500pf	120pf	8d.
3000pf	180pf	8d.
5000pf		8d.

BIAS ELECTROLYTICS (3's)

25mfd	25v.	1/6d.
50mfd	25v.	1/8d.
100mfd	25v.	1/11d.
250mfd	25v.	3/0d.
500mfd	25v.	3/8d.
1000mfd	12v.	6/0d.
1000mfd	30v.	5/9d.
2000mfd	25v.	7/0d.
2500mfd	30v.	9/0d.
3000mfd	30v.	9/6d.
5000mfd	30v.	10/0d.
25mfd	50v.	1/8d.
50mfd	50v.	2/0d.
100mfd	50v.	2/6d.
250mfd	50v.	3/8d.
500mfd	50v.	4/6d.
2000mfd	50v.	9/0d.
2500mfd	50v.	10/6d.

SMOOTHING ELECTROLYTICS

Wire ended, 450v. working.		
1mfd		1/6d.
2mfd		1/6d.
4mfd		2/3d.
8mfd		2/6d.
16mfd		3/0d.
32mfd		4/6d.
50mfd		5/0d.
8/8mfd		4/0d.
8/16mfd		5/0d.
16/16mfd		5/0d.
16/32mfd		5/0d.
32/32mfd		5/0d.
50/50mfd		8/0d.
50/50/50mfd		10/0d.

CANNED ELECTROLYTICS

100/200mfd		12/6d.
100/400mfd		16/6d.
200/200mfd		16/0d.
200/200/100mfd		18/6d.
200/400/32mfd		18/6d.
100/300/100/16		18/6d.
100/400/32mfd		18/6d.
100/400/64/16		21/0d.

SKELETON PRE-SETS (3's)

25K	Vertical	1/4d.
50K	"	1/4d.
100K	"	1/4d.
250K	"	1/4d.
500K	"	1/4d.
1 meg	"	1/4d.
2 meg	"	1/4d.
500K	Horizontal	1/4d.
680V	"	1/4d.
1 meg	"	1/4d.

SUB-MINIATURE ELECTROLYTICS (3's)

1mfd	18v.	1/8d.
2mfd	18v.	1/8d.
4mfd	18v.	1/8d.
5mfd	18v.	1/8d.
8mfd	18v.	1/8d.
10mfd	18v.	1/8d.
16mfd	18v.	1/8d.
25mfd	18v.	1/8d.
32mfd	18v.	1/10d.
50mfd	18v.	1/10d.
100mfd	18v.	1/10d.
200mfd	18v.	2/3d.

THERMISTORS (3's)

Miniature	1/6d.
THI	2/4d.

RECTIFIERS

Silicon Mains (3's)		
Westinghouse S10AR2	6/6d.	
BY127 Mullard	5/3d.	
BY105 Mazda	7/0d.	
BY327	5/6d.	

CONTACT COOLED FULL WAVE

75ma	12/8d.
100ma	13/8d.
150ma	16/8d.

CO-AXIAL PLUGS

Bakelite top	10d.
Egen metal	1/4d.
Single point (car radio)	2/0d.

SLIDER PRE-SETS (3's)

100K	1/6d.
1 Meg	1/6d.
2.2 Meg	1/6d.

JACK PLUGS

Chrome standard	4/0d.
Standard	3/0d.
3.5mm. metal	3/0d.

DIN PLUGS (3's)

3-pin	1/10d.
5-pin	2/2d.
Sockets	1/0d.

DOUBLE DIODE RECTIFIERS

(3's)		
Bush/Murphy/BRC, etc.		
Line/frame timebases etc.		
3 leg	6/3d.	
4 leg	6/3d.	
5 leg	6/3d.	

RADIO/TV GLASS

FUSES		
1 amp, 1.5 amp, 2 amp, 3 amp.		
Per dozen		3/0d.

MAINS FUSES

2 amp, 3 amp, 5 amp, 13 amp.		
Per dozen		5/0d.

TERMINAL STRIPS

2 amp	2/3d.
5 amp.	2/10d.
15 amp	5/9d.

CARBON FILM RESISTORS

1/2 watt and 1 watt.
The following values are packed in cartons of six of each value. Price 2/6d. per carton.

10 ohm	1.2K	150K
12 "	1.5K	180K
15 "	1.8K	220K
18 "	2.2K	270K
22 "	2.7K	330K
27 "	3.3K	390K
33 "	3.9K	430K
39 "	4.3K	470K
43 "	4.7K	560K
47 "	5.6K	680K
56 "	6.8K	820K
68 "	8.2K	1M
82 "	10K	1.2M
100 "	12K	1.5M
120 "	15K	1.8M
150 "	18K	2.2M
180 "	22K	2.7M
220 "	27K	3.3M
270 "	33K	3.9M
330 "	39K	4.3M
390 "	43K	4.7M
430 "	47K	5.6M
470 "	56K	6.8M
560 "	68K	8.2M
680 "	82K	10M
820 "	100K	12M
1K "	120K	15M

All the above values are available in both 1/2 watt and 1 watt versions.
*Special for Philips TV's:
8.2M 2-watt, 4/6d. per pack.

VOLUME CONTROLS

Standard spindle with flat.		
Double pole switch		4/7d.
Without switch		3/6d.
(One per pack)		
5K, 10K, 25K, 50K, 100K, 250K, 500K,		1 meg, 2 meg.

RECORD PLAYER CARTRIDGES

ACOS: GP67/2g. High gain general purpose Mono
GP91/3C. Stereo-compatible replacement
GP91/3SC. High gain version of above
GP94/1SS. Stereo cartridge

GENERAL PURPOSE REPLACEMENT FOR TC8's etc.
High gain, plenty of output (Jap.)
Stereo version

16/8d.
22/0d.
22/0d.
37/9d.
19/10d.
37/9d.

SERVISOL AND ELECTROLUBE

PRODUCTS (Nect trade)
Servisol aerosol can
Electrolube ZAX aerosol
Servisol Freezit
Electrolube No. 1 Snorkel
Electrolube 2GX Grease
Servisol Aero-Clene for tape heads
Servisol Aero-Duster

12/6d. nett
14/0d. nett
9/6d. nett
18/0d. nett
8/4d. nett
10/6d. nett
10/6d. nett

REPLACEMENT SYLLI

TC8 4/6d.
GC8 4/6d.

REBUILT AND NEW TUBES—TWO YEARS' GUARANTEE

REBUILT	BRAND NEW	A FEW SAMPLE TYPES, REMEMBER WE STOCK EVERY TUBE
17" @ £4 14 6	£5 10 0	CME1702, AW43-80, CRM173, MW43-80, MW43-69*, CRM172*, AW43-88, AW43-89, CME1705, CME1703, C17AF, C17SM, etc.
19" @ £4 17 6	£5 19 0	CME1903, CME1902, CME1901, AW47-90, AW47-91, A47-14W, C19AH, C19AF, C19A.
21" @ £7 5 0	£8 10 0	CME2101, AW53-88, AW53-89, CRM211*, CRM212*, MW53-20*, MW53-80*.
23" @ £7 5 0	£8 19 0	CME2303, CME2301, AW59-90, AW59-91.
COLOUR TUBES IN STOCK. PRICES ON APPLICATION		*NEW ONLY. NO REBUILDS
ALL PRICES ARE NETT		
	TWIN PANELS 19" CME1906 A47-13W } £10 1 0	23" CME2306 A59/13W } £16 1 0
EVERY TUBE IN STOCK INCLUDING 12", 16" PORTABLES, PANORAMA & RINGUARDS. TERMS: CASH WITH ORDER. CARRIAGE ANYWHERE IN GT. BRITAIN 12/6 per Tube		

HOT-LINE ORDERS
Tel: 01-567 5400/2971
TRADE ONLY

e.g. New VALVES . . . **33 $\frac{1}{3}$** plus **13%** plus quantity discounts **6%**

RADIO AND TELEVISION VALVES SMALL SELECTION

British made valves normally supplied. EVERY TYPE IN STOCK

DY86/7	10/-	EY86/7	10/-	PCL86	11/4
DY802	9/1	EZ80	10/10	PD500	31/7
EABC80	12/8	EZ81	8/2	PFL200	15/9
EB91	8/2	EZ90	9/3	PL36	16/4
EB90	10/10	GZ34	13/7	PL81	13/7
EBF80	10/10	GY501	15/9	PL81A	14/6
EBF89	10/10	PC86	14/6	PL82	10/10
ECC81	10/0	PC88	14/6	PL83	13/8
ECC82	10/0	PC97	10/10	PL84	12/8
ECC83	10/0	PC900	12/8	PL302	13/7
ECC804	15/4	PCC84	10/0	PL504	20/-
ECH81	14/6	PCC88	16/8	PL508	20/4
ECH84	12/8	PCC89	13/7	PL509	31/7
ECL80	9/6	PCC189	13/7	PY33	12/2
ECL82	12/8	PCC806	15/9	PY81	10/10
ECL83	13/4	PCF80	11/4	PY800	10/10
ECL84	11/4	PCF86	13/7	PY801	10/10
ECL86	12/8	PCF87	18/1	PY82	8/4
EF80	9/6	PCF801	13/7	PY83	13/7
EF85	12/8	PCF802	13/7	PY500	20/4
EF86	16/4	PCF805	14/11	UABC80	13/7
EF89	10/10	PCF806	13/7	UCH81	13/7
EF183	12/8	PCF808	14/11	UCL82	12/8
EF184	12/8	PCL82	11/4	UCL83	14/6
EH90	13/7	PCL83	13/4	UL41	14/6
EL34	10/0	PCL84	13/7	UL84	12/8
EY51	13/7	PCL85	13/7	UY85	9/0

ALL MAZDA/BRIMAR TYPES IN STOCK.

TRADE & SERVICE ENGINEERS ONLY SUPPLIED

Cash with order. 10% MAY BE DEDUCTED FROM THE ADVERTISED PRICES EXCEPT FOR NETT ITEMS, C.O.D., OR TUBES

All orders must exceed £5 in value otherwise postage and packing will be charged at 5/0d. per invoice. Components must be ordered in multiples as packed.

COMPREHENSIVE CATALOGUE listing valves, tubes, L.O.P.T.'s components, transistors, including HUGE VALVE EQUIVALENTS LIST. 2/6 in loose stamps, please.

L.O.P.T.'s

LINE OUTPUT
TRANSFORMERS

ALL MAKES SUPPLIED

EXCHANGE UNITS AND NEW REPLACEMENTS

EVERY MAKE SUPPLIED
(EXCEPT MURPHY OIL-FILLED)

REWIND SERVICE FOR OBSOLETE MODELS

FRAME OUTPUT, SOUND OUTPUT AND
MAINS TRANSFORMERS REWOUND

REMEMBER . . . We are the Service department Wholesalers and supply only the Service Engineers' requirements and can therefore carry large stocks, and also we know and understand your problems regarding getting the right spares QUICKLY and the RIGHT PRICE.
HOT-LINE ORDERS: LONDON 01-567 5400-2971. 01-579-3582. SOMERSET 045-84-2597

4 & 5 THE BROADWAY, HANWELL, LONDON, W.7

Telephones: 01-567 5400 01-567 2971 01-579 3582

and at 42 WEST END STREET, SOMERSET 045-84 2597



who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

In only **4 weeks** you're in – and only the incredible **Eduputer** can make it possible.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

Who created Eduputer? The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

Jobs galore! The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

Telephone: (01) 437 9906 NOW!

Or post the coupon today for full details FREE and without obligation.



London Computer Operators Training Centre,
B74 Oxford House, 9/15 Oxford Street, London W.1.
Telephone: (01) 437 9906.
127/131 The Piazza, Dept. B74, Piccadilly Plaza, Manchester 1.
Telephone: (061) 236 2935.

Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name _____ P.P. _____

Address _____

Tel: _____



PADGETTS RADIO STORES

OLD TOWN HALL, LIVERSEGE
YORKS.

Telephone: HECKMONDWIKE 4285

Amplifier Units Type A1413. Complete with 5Z4 and 6V6GT Valves 230/250 Volt 50 cycles Transformer Clean Condition. Untested 25/-. Carriage B.R.S. 15/-.

Airmileage Units. Complete with 24 Volt Motor and Gears, etc. Less Relay. Clean condition. Untested 15/-. Carriage B.R.S. 15/-. **Panel with Two Miniature Relays** and One Carpenter Relay with Base. Ex Units 7/6 post paid.

Panels of Resistors and Condensers. Ex Equipment 8/- per doz. post paid.

AW 43/80 Tubes. Reclaimed with 6 month guarantee 25/-. Carriage 15/-.

AW 43/88 Tube. Reclaimed with 6 month guarantee £2. Plus carriage 15/-. **MW 43/69 30/-.** Plus carriage 15/-.

Speakers P.M. All 3 Ohm perfect condition ex T.V. Sets. Postage and packing on any Speaker 4/-. 5" Round 3/-. 6 x 4 3/-. 7 x 4 5/-. Slot Speaker 8 x 2 1/2 3/-.

Special Offer. Bush 17" T.V. Sets Series 75. 12 Channel. Complete and Tested with good tube £6/10/0. Plus carriage and insurance passenger train G.B. only 35/-. Cabinet condition fair. Complete untested 17" T.V. Sets 12 Channel 50/-. Carriage £1.

Top Grade Mylar Tapes. 7" Long Play 14/-. 7" Standard 11/6. 5" Long Play 10/-. 5" Standard 7/9. Post and packing on any Tape 1/9.

VALVE LIST EX EQUIPMENT 3 months' guarantee. Single Valves.

ARPI2	1/6	PCC84	2/-	PL36	5/-	688	1/6
EB91	9d.	PCF80	2/-	PL81	4/-	68W7	2/6
EBF89	3/-	PCC89	3/-	PY81	1/6	6U4	4/-
ECC82	3/-	PCL85	5/-	PY800	3/6	20D1	3/-
ECL80	1/6	PCL84	4/-	PY82	1/6	20P1	5/-
EF183	3/-	PCL82	4/-	PY33	5/-	20P3	2/6
EF184	3/-	PCF86	4/-	U191	4/-	30PL1	5/-
EY86	4/-	PCL83	3/-	6F23	4/-	30P12	4/6
						30F5	2/9

★ **IMPORTANT NEW DEVELOPMENT FOR THE COLOUR T.V. INDUSTRY**

THE FISHER/B.B.C.

'color-trak'

DEVELOPED IN CONJUNCTION WITH THE B.B.C. THIS NEW COLOUR TELEVISION REFERENCE SOURCE FILLS AN URGENT NEED FOR A HIGHLY PORTABLE, TOUGH, SCIENTIFICALLY DESIGNED INSTRUMENT AT A LOW ENOUGH COST TO ENABLE EVERY SERVICE ENGINEER TO CARRY ONE.

TAKES THE GUESSWORK OUT OF GREY-SCALE TRACKING

THE COLOR-TRAK ENSURES AS-TRANSMITTED PICTURES SATISFIED CUSTOMERS REDUCTIONS IN EXPENSIVE CALL BACKS USED NOW BY MOST UK BROADCASTERS AS REFERENCE SOURCE FOR MONITORS.

ILLUMINATE: D6500°
PEAK WHITE: 21 FT. LAMBERTS
VOLTAGE: 200/250 OR 110V 50/60 HZ

THE AGREED INTERNATIONAL STANDARDS FOR COLOUR

£12 PLUS 5/- P.P. FROM

FISHER CONTROLS LTD.
BREARLEY WORKS,
LUDDENFOOT,
HALIFAX, YORKSHIRE.

OR YOUR RADIO STOCKIST

TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

VOL 21 No 3
ISSUE 243

JANUARY 1971

EXPLANATIONS

This is the first TELEVISION to appear since our November issue was published on October 23rd last, so we must start with an apology to our readers—and also our advertisers and regular contributors—for the loss of the December issue and the very late appearance of this one—on the date when normally our February issue would have been published. Most of the features in the present issue are those which would have appeared in the lost December issue, and all series are being resumed where they left off, so readers will find no editorial gaps in the contents of the current volume. The industrial dispute that led to the loss of the December issue and the late appearance of this one followed the closure of Fleetway Printers' Sumner Street works where TELEVISION had been set for the last two years or so: we are glad to say that agreement has now been reached by all the parties concerned. We shall however have to ask our readers to bear with us a little while longer while we try to get back to our normal monthly publishing date.

This month we welcome to our columns a regular cartoon. Ed Pullin's ideas and drawings have amused us greatly and we hope that readers will find them equally entertaining.

With the publication this month of an article on *Synchronous Detectors* we conclude a group of three articles—the others were *PAL Chroma Detection* in the November issue and *PAL Switching Techniques* in the October one—which between them have looked in detail at the techniques used in the colour signal processing sections of a PAL colour receiver. The aim has been to examine the circuits found in practice in this crucial part of a colour TV set to find out exactly what goes on.

Lastly we regret that due to space difficulties with this issue we have had to hold over the second part of our feature on *Flashover Protection*. This will appear in the February issue which we hope to publish in about three weeks' time.

W. N. STEVENS, *Editor*

THIS MONTH

Teletopics		104
Holography	<i>by I. R. Sinclair</i>	106
The Lighter Side	<i>Ed Pullin</i>	111
Synchronous Detectors	<i>by S. George</i>	112
Versatile IC 'Scope Preamplifier—Part 2	<i>by Martin L. Michaelis, M.A.</i>	116
Servicing Television Receivers—Baird 620-640 Series	<i>by L. Lawry-Johns</i>	119
DX Amateur TV on the 70 cm. Band		122
Colour Receiver Circuits—IF Stages	<i>by Gordon J. King</i>	123
International Broadcasting Convention 1970	<i>by J. I. Sim</i>	126
Band III Aerial Preamplifier	<i>by Roger Bunney</i>	128
DX-TV	<i>by Charles Rafarel</i>	130
Your Problems Solved		134
Test Case 97		138

**THE NEXT ISSUE DATED FEBRUARY
WILL BE PUBLISHED FEBRUARY 12**


TELETOPICS



APPROACH OF videocassettes

As the time approaches when video recordings in cassette form will be available to the public more firms are releasing information on their plans and competing systems. Rank-Bush-Murphy have now demonstrated—ahead of their original development schedule—their colour EVR video cartridge player. Full production of these players at the RBM Plymouth factory is expected to be in operation by April and the price will be around the £350 mark. The cartridges—one hour black-and-white ones and, later, colour ones—will cost between £20 and £40 and will also be available for hiring at 30/- upwards.

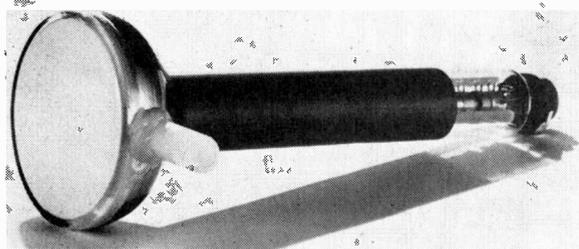A key component in the RBM teleplayer, the scanning light source which illuminates the film and does away with the need for a pull-down sprocket system, is the Brimar flying-spot scanner tube type Q8-100AA. This is a high-precision 3in. c.r.t. which has been specially developed for the application by



The Brimar Q8-100AA 3in. flying-spot scanner tube developed for use with EVR teleplayers.

Brimar in conjunction with the EVR Partnership. The tube is available to the maintenance trade at a recommended trade price of £30.

A colour videocassette system using magnetic tape has also now been demonstrated by Sony. The system is at present designed for use with the US NTSC system but Sony intend to make their equipment compatible with the videocassette standard being established by Philips for use with the European colour television system. The Sony colour videocassette playback units are expected to cost about £200 and an adaptor to enable off-air recordings to be made will be about £50. The tape is expected to cost about £1 a minute's playing time. The Sony player can be connected to any standard television set without the need for modifications to the set and as it is fully compatible it can also be used with black-and-white sets. The videocassette has two sound channels, holding out the possibility of stereo sound. The system is expected to be available to the Japanese public this autumn and will later be available for export.

In addition the US videotape recorder giant Ampex has joined forces with a leading Japanese consumer electronics firm Toshiba to enter this market with a magnetic tape videocassette system called the "Instavision" system. The recorder/player is claimed to be the smallest to date and there will be a choice of players or recorder/players operating on batteries or mains supplies and in colour or black-and-white. Standard $\frac{1}{2}$ in. tape in a small circular plastic cartridge 4.6in. in diameter and 0.7in. thick is used and this is compatible with all other conventional reel-type recorders using the international type one standard of the Japanese EIA. Instavision equipment should be available in the US in mid-1971 and in Europe by the end of 1971. Prices will be approximately £333 for a monochrome player, £385 for a monochrome recorder/player or colour player and £416 for a colour recorder/player.

Thorn have announced that they intend to make videocassette players to the standards established by Philips.

The EVR Partnership have concluded licence agreements with the Japanese firms Mitsubishi Electric and Hitachi Ltd. for the manufacture and distribution of EVR teleplayers.

NEW SETS

Several new monochrome models have been introduced in the **Marconiphone** range. These are the single standard 20in. Model 4807 at £71.14.0d., the 17in. Model 4803 at £61.1.0d. and the 24in. Model 4808 at £79.13.0d. Dual-standard versions are the 20in. Model 4649 at £83.7.0d., the 17in. Model 4661 at £77.3.0d. and the 24in. Model 4668 at £90.17.0d.

A 22in. **Korting** colour model, the 51675, is being imported by Europa Electronics Ltd., Howard Place, Shelton, Stoke-on-Trent ST1 4NW. This model, which has a recommended price of £309.19.0d., features a six push-button tuner, slider controls for colour tone and intensity, brilliance and contrast, and 4.5W audio output. **Telefusion** are also to market this set under the name "Carnival".

A new battery/mains 13in. portable model from **Hitachi** sells at £82. A 26in. colour model has been added to the Bang and Olufsen range. This, the **Beovision** Model 3200SJ, has recommended prices of £428 with teak finish and £434.10.0d. with rosewood finish.

Colour receiver deliveries rose to 48,000 last September, bringing the total for the first nine months of the year to 306,000. Monochrome set deliveries also increased in September to 169,000. For October the figures were 56,000 (colour) and 185,000 (monochrome). US set sales were down 27.2% (colour) and 10.2% (monochrome) during the first six months of last year.

HITACHI GET PAL LICENCE

The Japanese Hitachi company has successfully completed negotiations with the West German AEG-Telefunken company—the PAL patent holders—for a licence to manufacture PAL colour sets and is planning to enter the UK market later this year.

TRANSMITTER NEWS

BBC-1 programmes are now being transmitted at u.h.f. from four more stations. These are **Tacolneston** on channel 62 with horizontal polarisation (aerial group C), **Reigate** on channel 57 with vertical polarisation (aerial group C), **Guildford** on channel 40 with vertical polarisation (aerial group B) and **Brighton** on channel 57 with vertical polarisation (aerial group C). BBC-2 transmissions have now started from **Blaenplwyf** for West Wales on channel 27 with horizontal polarisation (aerial group A) and **Malvern** on channel 62 with vertical polarisation (aerial group D).

The ITA's **Sudbury** transmitter is now in operation on channel 41 with horizontal polarisation carrying Anglia TV (aerial group B).

The French government has decided to create a third state-run television channel. It is intended that the third channel, in colour, will start in 1972 and reach all France by 1975.

The ITA has issued a convenient new fold-out publication titled "ITA Transmitters—A Pocket Guide" which provides full data on the ITA Band III and Band IV/V networks. Copies are available on request from the ITA Engineering Information Service, 70 Brompton Road, London, SW3.

US TV LOSES CHANNELS


The US Federal Communications Commission (FCC) has announced that due to the expansion of two-way radiotelephone services the Band 806-947MHz is to be allocated exclusively to these services. The Band previously included TV channels 70-83 (806-890MHz). These TV channels are at present occupied by low-power translators (1kW and less) but it was expected that high-power TV transmitters would open using these frequencies when the lower channels became too crowded. As radiotelephone equipment for these frequencies is not at present available and will take some time to develop, however, the FCC has authorised as a short-term solution the sharing by these services of two lower TV channels—channels 14 (473-5MHz) and 20 (509-5MHz). This will mean changing TV station channel allocations in some areas.

NEW PRODUCTS

The English Electric Valve Co. Ltd. has introduced a new vidicon camera tube type 7262A for closed-circuit television systems. This is a short (5.18in.) 1in. vidicon for use in compact monochrome or colour systems.

Mullard have released three new npn silicon planar transistors for use in TV receiver video output stages. They have high collector current and voltage ratings making them suitable for use in large-screen colour or monochrome receivers and can also be used as line output stage drivers. Small heatsinks are required. The BF336, BF337 and BF338 have maximum collector-emitter voltages of 180V, 200V and 225V respectively and use TO-39 encapsulation.

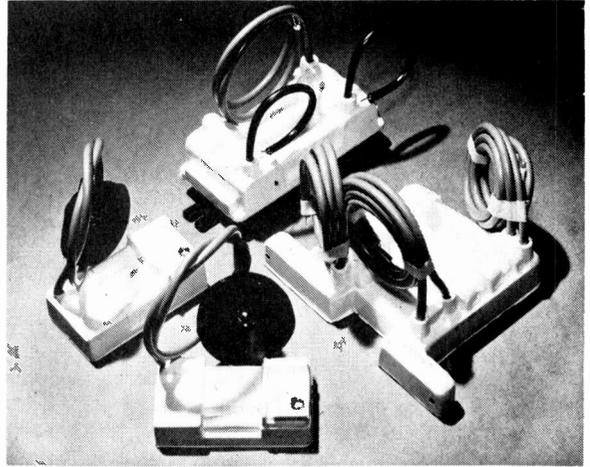Clayridge Electronics Ltd. (2 Stoke Newington High Street, London, N16) are now able to supply



A selection of the replacement e.h.t. rectifier trays available from Clayridge Electronics Ltd.

from stock replacement e.h.t. rectifier trays for sets using semiconductor e.h.t. multiplier circuits. These are mainly Thorn/BRC sets and colour sets by the GEC, Pye and Rank-Bush-Murphy groups.

AERIALS

Antiference have introduced a new high-gain u.h.f. aerial which they claim combines the performance of a 2x18 broadside Yagi array with the advantages of single-boom mounting. The new aerial, called the Hi-Gain, has a double director chain with the pairs of directors mounted in the same plane: the idea is to avoid the "cross-polarisation effects" which Antiference say can be troublesome with some multi-director designs because of the mixture of horizontal and vertical polarisation used in the UK. The director chain is matched into a patented "Trucolour" dipole and the array is completed by a six-element angled reflector. The aerial has been designed to give even response, and accurate matching with optimum directional characteristics throughout the channel groups—group A, B and CD versions are available. Recommended retail price is £6. Further details from Antiference Ltd., Aylesbury, Bucks.

Also now available from Antiference is a new set-top aerial, the Super Set-Top. This is a Yagi array with reflector, dipole and three directors and is available for the aerial groups A, B or CD.

The BBC Engineering Information Service (BBC, Broadcasting House, London, W1A 1AA) has issued an information sheet, No. 4006(2), giving a useful summary of the facts of u.h.f. TV reception and aerial requirements and installation.

APOLOGIES TO MCGRAW-HILL

We have been asked by the McGraw-Hill Publishing Co. Ltd. to make clear that the author of their recently published book *Colour Television Theory: PAL-System Principles and Receiver Circuitry* which was advertised in our last issue, dated November, 1970, is by Geoffrey H. Hutson. The author's name appeared incorrectly spelt in our advertisement.

NEW INDEPENDENT TV COMPANY

The new company resulting from the merger of Yorkshire Television and Tyne Tees Television will be known as Trident Television. The Chairman will be Sir Richard Graham.

3-DIMENSIONAL DISPLAY

HOLOGRAPHY

I. R. SINCLAIR

HOLOGRAPHY is a term that has suddenly become very prominent, though the basic idea has been around for some time. The attractions of holography lie in the possibilities of storing optical images in a very compressed form, a form of photography without the use of lenses, and true three-dimensional effects without the need for viewing spectacles, split screens or any of the other optical devices which we have previously associated with 3-D.

A hologram is a recording of an image—as is a photograph—but the appearance of a hologram is totally different from the appearance of a photograph just as the appearance of a piece of videotape is totally unlike the images which may be recorded on it. A hologram is a coded form of an image and it is this which makes it of such interest to workers in TV, because TV is basically concerned with methods of coding images. This is indeed what the process of scanning is.

The production of holograms has now become associated with the use of lasers, but the idea of holography goes back to before the invention of the laser and holography using sound waves has been also recently described.

Interference of Waves

Before we can begin to understand holography we must know something of the waves which produce the effect, remembering first that the only difference between the light waves used in holography and the radio waves with which we may be more familiar is the difference of wavelength: the waves of light are of a much shorter wavelength. We can therefore take the information which we know about one type of wave and apply it to the other, the only differences being ones of size.

When waves of the same frequency meet each other the effect produced depends on the relative phase of the waves. To make this clearer consider Fig. 1. In Fig. 1(a), the two sets of waves coincide, the peaks of one wave occurring at exactly the same time

as the peaks of the other. The total effect on any receiver—whether it be the eye for light or a radio set for its own brand of wave—is of one wave of double the amplitude, for the amplitudes of waves at any point in space add simply. In Fig. 1 (b) the two sets of waves are exactly half a wave out of step, the peak of one in the positive direction corresponding with the peak of the other in the negative direction. If the waves are of the same amplitude we can add the two together at any point in space to produce zero amplitude.

When two waves of the same frequency combine then, the resulting amplitude can vary all the way from the sum of the amplitudes to the difference between them depending on the relative phase or position of one wave as compared to the other. If the two waves have the same amplitude the resulting amplitude can be anywhere between twice the amplitude of one down to zero, depending on phase. This effect takes place with all waves, whether electromagnetic (radio, light, X-rays etc.) or mechanical (sound, ultrasonics) but cannot always easily be observed, particularly with the very short wavelengths.

Assuming that we can observe the effect though we would find that when an object is placed near a source of waves and a receiver, as shown in Fig. 2(a), so that waves can travel directly from source to receiver and indirectly to the receiver by being reflected from the object, the amplitude observed at the receiver will vary as the object is moved. This is the principle of the Doppler radar system used by the police for detecting the speed of cars, for the rise and fall in amplitude of the received wave takes place at a speed which depends on the speed of the object. Old timers may remember the "Luxembourg Effect" which was caused by Radio Luxembourg transmissions arriving here along with a reflection from the Heaviside layer in the upper atmosphere: movements of the layer caused periods of complete fadeout when the reflected wave was completely out of phase with the normally received one.

Much more important for our purposes is the effect shown in Fig. 2(b) where the detector is moved from side to side. As this is done different amplitudes are detected, because the distance travelled by one wave compared with the distance covered by the other is changing. The important quantity is the difference in path length, preferably written as a number of wavelengths, since we can easily calculate from this the phase difference between the two signals. We can then draw a "map" of these amplitudes in the region around the detector, and this is called an *interference pattern* because it represents the amount

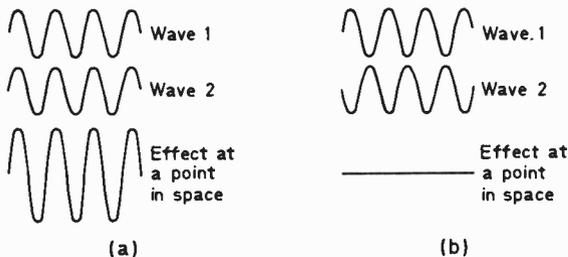


Fig. 1: Addition of waves.

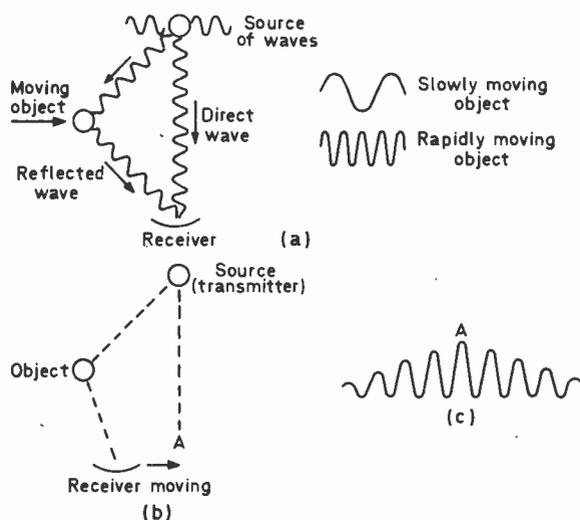


Fig. 2: (a) A moving object gives an interference signal which varies with time—it is in fact a sinewave. (b) Fixed object but moving receiver. (c) Pattern of waves picked up by the receiver. The peak amplitude is usually at the point where the receiver and transmitter are closest.

of interference between the waves—constructive interference where the waves add in amplitude, destructive where they subtract. Fig. 2(c) shows the type of pattern which can be obtained using radio waves. Incidentally this type of pattern can be used as a means of measuring distance very accurately if the distance between two receivers whose signals are then combined is known. This process is called *radio interferometry* and is of very great use to astronomers.

Demonstrating Interference Effects

Interference patterns can also be heard. If a stereo outfit is available the existence of interference can be convincingly heard if the channels are combined by switching to mono and a single note such as a tuning signal is fed to both speakers. As the listener's head moves from place to place, the sound becomes alternately louder and softer because of


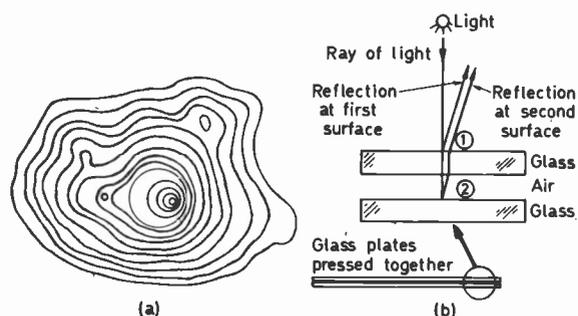


Fig. 3: Newton's rings. (a) Typical pattern seen between glass plates. (b) The two reflected waves have travelled different distances and their phase will depend on the spacing between the plates, which are never truly flat. Perfectly flat plates would show no pattern. Each space between rings represents a change of air gap of 50 millionths of a centimetre.

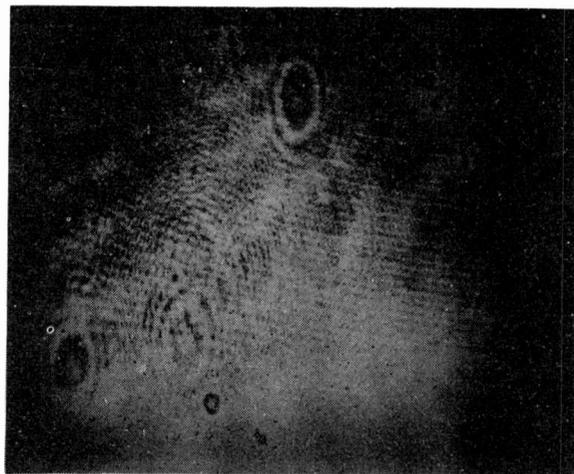

Appearance of a hologram produced by a set-up as shown in Fig. 4 when viewed in daylight. (Photo courtesy The Marconi Company Ltd.)

interference between the two sets of sound waves. Another feature of interference patterns can also be observed from this simple experiment. If the note used is of high pitch (short wavelength) the distance which the head has to move from a loud point to the next soft point is small; if the note is of low pitch (long wavelength) the distance between the loud and soft parts of the interference pattern is large. This indicates that there is more difficulty in detecting the interference patterns made with short wavelengths because of the very small distance between the high-amplitude points and the low-amplitude points.

This does not mean that the patterns cannot be observed with light but it does mean that the circumstances in which we can expect to find interference patterns may be more limited. One of these circumstances is well known to photographers. If colour slides are being made up by pressing the film between two plates a pattern of closed loops looking at first sight like a giant fingerprint is seen. The same pattern, called Newton's Rings (Fig. 3), can also be seen when the flat glass pieces are pressed together without the film. The pattern varies as the glasses are pressed together, because the glass is bending and thus varying the distance which the reflected light ray has to move. Its visibility is greatly increased if it is viewed in the light of a single colour such as the light from a sodium lamp. This effect again has many applications in the measurement of very small distances.

Forming Holograms

Holography, first suggested by Professor D. Gabor of Imperial College London, is a reversible process of forming an interference pattern of an object. The process involves using a light source and a recording medium, such as a photographic plate, to form the hologram, which can then be reconverted to an image by viewing, either directly or by the use of a screen. The difference between this process and conventional photography is that no lenses are used and that the pattern on the photographic plate bears absolutely no resemblance at all to the object which has been holographed. Also unless the light source used has certain features not

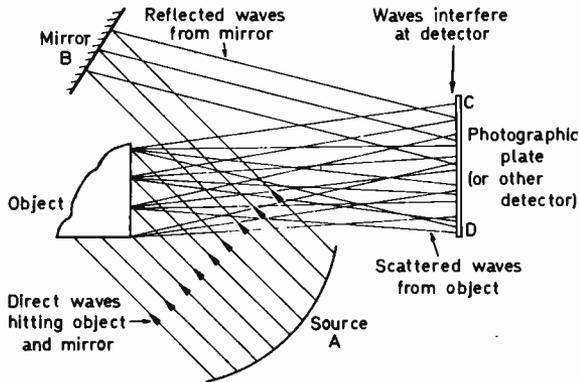


Fig. 4: Creating a hologram.

generally found in conventional sources of light the pattern is neither obtained nor reconvered. Incidentally it is interesting to note that Professor Gabor first suggested the process as a lensless method of recording images so that better X-ray images could be obtained since we know no way of focusing X-rays, lenses being useless at the short wavelengths of X-rays.

The basic set-up for creating a hologram is shown in Fig. 4. An object is illuminated by waves from the source A and the waves are reflected from the object on to the photographic plate CD. At the same time waves are also reflected from the mirror B towards the photographic plate. If the source of the waves is very small there will be two distinct wave rays reaching every point on the photographic plate, one reflected from the object and one reflected from the mirror. These waves will interfere so that the amplitude of the wave reaching the plate at any point depends in a complicated way on the shape of the object.

The shape of the hologram is totally unlike that of a photograph. In a photograph, light from a point on an object is focused by a lens so that it reaches a point on the photographic plate, and each point of the object focuses to a *corresponding* point on the plate. In making a hologram, each point on the object reflects (more properly, *scatters*) waves to *all* points on the photographic plate, where they interfere with a "reference wave" coming in a definite fixed direction from the mirror.

When we look at a hologram in the normal way we cannot see the image of the object but only a complicated pattern which might be a giant fingerprint or an entry at an art exhibition. The reason for this is that the "reference wave" which plays such an important part in forming the hologram is missing. A good comparison is with a single-sideband, suppressed-carrier radio transmission (or the suppressed-subcarrier colour TV chroma signal). To receive these correctly we have to supply the missing carrier in the correct phase and then detect. Similarly before we can detect a hologram with our eyes it is necessary to supply the missing "carrier" wave at the correct frequency and phase. We shall discuss some of the problems of doing this later.

Characteristics of Holograms

Because each part of the hologram carries information about all portions of the object, a hologram can be broken up into a number of parts each of

which can still be used to reconstruct the object. Something must of course be lost and in this case it is the resolution, but the difference between hologram and photograph is evident. Another striking difference is that the hologram contains information about the distance of each part of the object from the photographic plate and not merely information about the object's length and breadth so that holograms are three-dimensional in nature.

In photography we can create this 3-D effect only by taking two photographs from slightly different positions and arranging that each eye of the viewer sees a different image. This is a clumsy process compared with the holographic method where instead of different viewpoints a reference beam is directed on the hologram and, as shown in Fig. 5, the image can be viewed in the normal

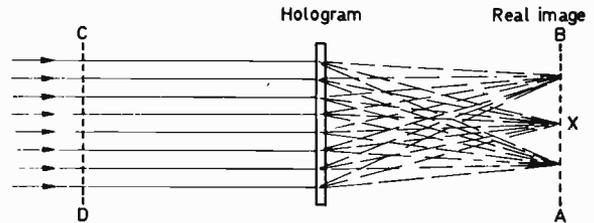




Fig. 5: If the hologram is held in a parallel beam of suitable waves the interference of these waves caused by the hologram forms a real image which can be projected on to a screen at position AB. If instead an observer's eye is at position X he will see the image at position CD.

manner. Further if with a hologram we change the angle between our direction of viewing and the reference beam, for example by moving our position, it is as if we actually change the angle at which we viewed the original object, the image appearing to us as if we had been able to turn it. It is in fact possible to make a hologram which contains all information on all sides of an object so that rotating the angle of the reference beam enables us to view all sides of the image in turn. It is almost like the dream situation of seeing a photograph of a house and then without moving looking behind it to see what the garden is like! Another point about holograms is that the difference between positive and negative images is unimportant since one can be converted into the other by adjusting the phase of the reference wave.

It all sounds too good to be true. Take the lens away from the old Box Brownie, arrange your scene with a mirror to provide a reference beam, get a hologram which does not need printing to a positive and project your image so that moving the projector's light position enables you to see the picture at a different angle! In addition, no distorting lenses and it doesn't matter if the dog eats half the picture! It sounds too good to be true and it is, but the reasons for the impossibility of the scene just imagined are rather complicated.

Practical Problems

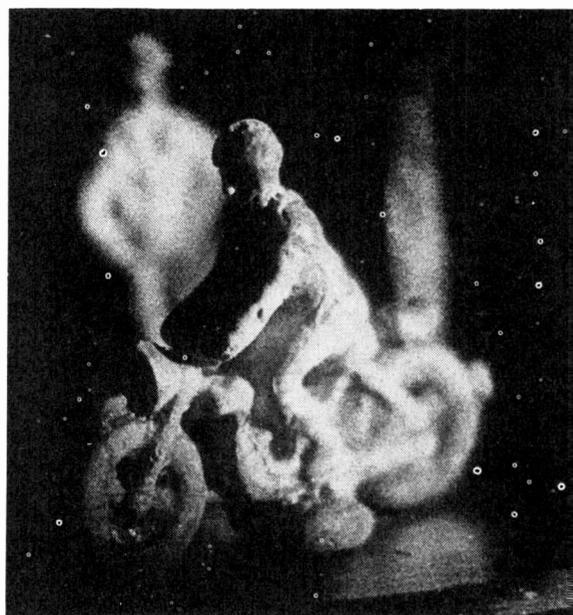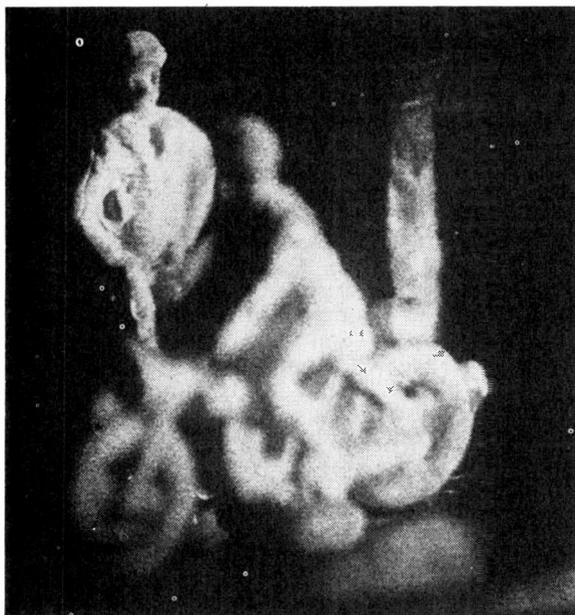Holography indeed was not a practical proposition when it was first suggested and is still not practicable with most light sources. This is the case with most inventions—the means of making them work not being available when the idea first occurs. With holography the snags are the wave sources and



Showing the 3-D nature of a holographic display. The display of a hologram of model soldiers was photographed using a camera with a small depth of focus, the left-hand photo being made with the camera focused on to the rear plane of the display and the right-hand photo with the camera focused on the front plane of the display. (Photos courtesy The Marconi Company Ltd.)

the detection of the waves. Since we are going to combine two sets of waves at the detector it is important that the sources of the waves should keep in step. It is equally important that we should be able to detect the holographic pattern over a reasonably large area, for though each small area contains all the information needed the resolution suffers if the area is too small while if the area is comparable in dimensions to the wavelength of the waves being used no hologram can be formed at all.

One method which seems obviously easy is to use light waves and record on a photographic plate. For reasons which we shall discuss shortly this has been possible only recently. Radio waves can be used, but we cannot conveniently "photograph" radio waves and it would be tedious to move a receiver over a large area, noting the wave amplitude and plotting it at various points, even if we took the sensible step of using short wavelengths such as 3cm. microwaves.

Quanta and Coherence

The apparatus shown in Fig. 6(a) does not produce any interference effects with light, the apparatus shown in Fig. 6(b) does. Early physicists were puzzled by this difference but accepted that interference effects could be demonstrated only if a single beam of light was split into two parts, one being taken along a slightly longer path than the other before being recombined to give *interference fringes* as they are called. The difference in length between the paths has to be very small, only a few (up to 50 or so) wavelengths of light. As the wavelength of light is only 50 *millionths* of a centimetre this means that interference effects of light have to be demonstrated using very small distances indeed, and this accounts for the usefulness of interference in

the measurement of small distances. Once again early physicists were puzzled by this: they could not see why interference effects could not be obtained using longer path lengths, and their problem was not solved until much later.

At one time, one reason for the difficulty of obtaining interference effects from two light sources was thought to be the bandwidth of the light. White light consists of a very wide band radiation extending from around 100 million MHz to 250 million MHz—the bandwidth of about 150 *million* MHz makes the frequency response of your video amplifier look a bit tame and should increase your respect for the human eye. It is asking rather a lot that this huge range of frequencies from two different light sources should interfere simultaneously, so it would seem reasonable to try the experiments of Fig. 6 again with light of a more limited bandwidth or, as it is more familiarly known, light of a single colour. When we do this we find that the fringes produced by the method shown in Fig. 6(b) are very much more distinct and have a more "focused"

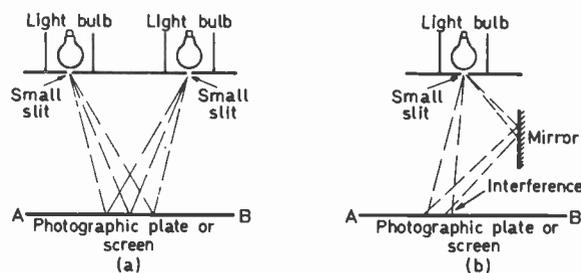


Fig. 6: Interference is seen only when one light beam is split into two sections one of which travels farther than the other. (a) There are no interference effects seen with this set up. (b) With one bulb and one slit, interference effects are seen.

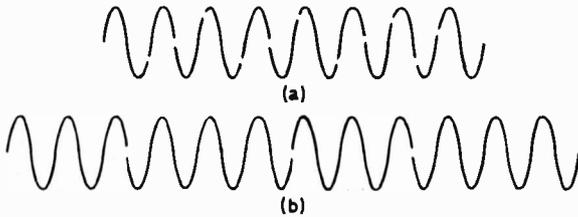


Fig. 7: (a) Diagrammatic representation of "quanta" or "wave packets". Note that the phase usually changes after each break. (b) Effect of quantum breaks at longer wavelengths (not to scale).

appearance, but the method shown in Fig. 6(a) still does not work. Thus another effect must be present. Though limiting the light bandwidth is not the answer to the problem it does indicate that our holograms might have to be made with light of a single colour if we are to have good resolution of fine detail.

The "other effect" was not discovered until the end of the last century. It forms the basis of the Quantum Theory of Max Planck and is probably the most far-reaching theory in all physics. What it boils down to is that no oscillation is truly continuous. Instead oscillations stop and start, giving a broken train of waves as illustrated in Fig. 7. It may seem odd that this effect was not noticed earlier, but the breaks are very small and cannot be observed directly though the effects which we have mentioned are the consequences of these breaks.

For long waves the gaps are very small compared to a wavelength and occur between a large number of wavelengths; for short wavelengths the gaps may occur several times in the course of a single wavelength. In the first case we can observe the wavelength but we cannot see the gaps because they are so small and infrequent. In the second case we cannot observe the waves either because we have no means of doing so. In each case however Planck's Theory predicts that the product of the energy of the wave and the time between the gaps is a constant (small) quantity now called Planck's Constant. This can be measured in a variety of different ways and appears always to have the same value.

We can now see why it is not possible to produce interference between two separate light sources. Each source is producing pieces of waves (quanta) and there is no way of ensuring that the phase of one quantum is the same as the phase of the next—in fact it is almost certain that there will be some difference. For long waves this should be less of a problem since as the gaps are so very small compared to the wavelength the phase differences must also be small.

The ability of any wave source to produce quanta whose phase is constant or at least does not vary too much from one wavelength to another is called *coherence*. The longer a wavelength the easier it is to produce coherent waves and the easier it is to maintain that coherence over long distances because these distances represent only a few waves. For this reason it is easy to demonstrate interference with two loudspeakers, for sound waves are coherent over long distances. On the other hand it is almost impossible to show coherence in normally-produced light waves because coherence extending over a few light wavelengths means that we should be reduced to an impossibly close spacing of our apparatus.

Enter the Laser

One of the properties unique to the *laser* as a generator of light waves is that these are coherent over an enormous number of wavelengths amounting to a distance of several metres. This is because of the way in which the laser generates light. In an incandescent lamp of the normal type groups of atoms are oscillating due to the electrical energy with which the lamp is being fed. There is nothing to keep the individual oscillators in step, so it is not surprising that the light is not coherent. In a laser however the energy fed in (electrical, chemical or in the form of other light) is used to raise the electrons of each atom to a higher energy level. When an electron then returns to its normal energy level the light emitted can trigger the other electrons so that the portions of wave are kept in step and the light emitted is coherent. Because of this the laser is the ideal source of light for holography.

Applications

Until recently the main applications of laser holography have been in the realms of metrology, the science of exact measurement. Suppose we have a manufactured object which has to be made to very close limits. By using a laser in a holographic set-up we can make a hologram on film which is a coded representation of the object. If we keep the object and its hologram in position and rearrange the laser and the mirror so that we produce an image of the object in exactly the same place as the object, then when image and object coincide exactly nothing unusual is seen. If however a slight change has occurred in the object, for example expansion due to a tiny temperature change, then the image and object are no longer identical and the object has interference bands across it. The spacing of the interference bands indicates the difference in dimensions between the object when it was holographed and when it was imaged, close spacing meaning large differences and wide spacing small differences. The words large and small here mean in comparison to a wavelength of the light used.

Using this idea we can measure very small changes in dimensions such as occur when metals are magnetised, and we can make these measurements without any physical contact with the object. We can also very rapidly check the dimensions of a copy of the object since any deviation from the dimensions of the one used to form the hologram will show up. Laser holography is in this way of enormous value to industries producing items to very fine tolerances.

RCA Selectavision System

Recently an application of laser holography to TV was announced. RCA have shown the first prototypes of their colour TV recording system which uses the holographic principle as a convenient way of coding an image. RCA claim that reproduction of the image can be carried out by a player whose cost is estimated at about \$400 (£170) and which plugs into the aerial terminal of an ordinary colour TV receiver. This compares very favourably with even a black-and-white magnetic videotape player and the amount of tape required for a given length of programme seems to be smaller.

Few details have been released of the Selectavision

system—as it is called—at the time of writing but the whole process starts with the production of a holographic tape. A colour programme, which may be live or from tape or telecine, is used in the form of a video signal. This video signal is recorded on conventional photographic film by means of an electron-beam recorder, shown in diagrammatic form in Fig. 8. The electron beam is obtained from a conventional cathode-ray tube gun but in place of a screen there is a carrier which winds the film past the scanning beam in a vacuum. In scanning

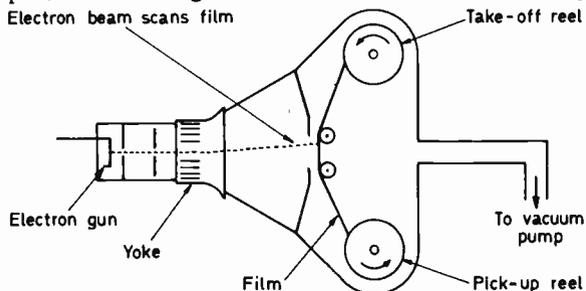



Fig. 8: Basic outline of an electron-beam recorder.

the film the beam exposes it with an intensity proportional to the amplitude of the signal. If a light beam scans the developed film the video signal can be recreated in conjunction with a photocell. The brightness, hue and saturation information are contained in this video signal and the tube used for recording needs only one gun and no shadowmask.

The film of the video signal could be used directly as the recording but film is expensive to copy. If this were not so it would be cheaper to film the original programme and sell copies of the film. Instead it is necessary to turn the film into a form which can be copied cheaply. To do so a hologram film is made, using the now-familiar holographic recording set-up. This hologram is made not on ordinary film but on a plastic tape coated with photoresist—the material used in the production of printed and integrated circuits. This material hardens when exposed to light but can be easily washed off where it has not been exposed. When the hologram has been made the film is washed to remove the unexposed portions.

Imagine the appearance of this film. The pattern on it is that of the typical hologram—loops and lines in perplexing order—but the loops and lines are raised portions of hard material. We have thus converted from a light-and-shade image into a high-and-low hologram in one operation. This is the holographic master tape and can be reproduced using the same techniques as used for LP records which also consist of patterns cut in a suitable material. The master tape is electroplated with nickel and the nickel carrying the exact shape of the holograms on the master tape is next stripped off. The nickel tape can then be laid on a transparent vinyl tape and the two passed between heated rollers resulting in a pressed out copy of the original. Since this is a printing process and can be made continuous, can operate at high speeds and needs no chemical processing it is relatively cheap. RCA estimated that the cost of a 30-minute tape would be about £4 which is very much less than a colour film copy would cost even in 8mm. stock. Just as with LP records thousands of copies can be made from one master.

THE LIGHTER SIDE . . .

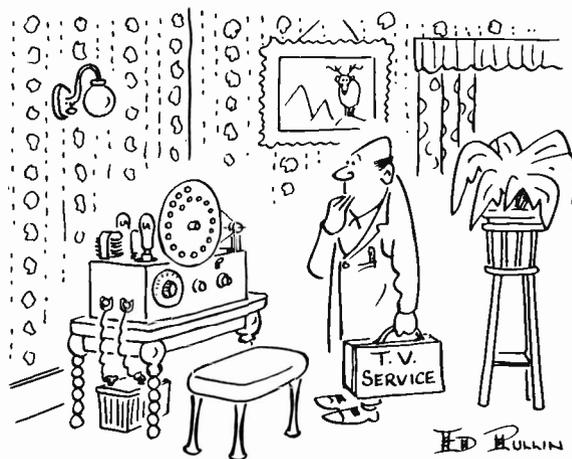

The problem now is to convert from the hologram tape to the video signal and this is the part of the process about which least has been revealed. If the tape is reeled past a laser and a mirror in the standard arrangement for reproducing a hologram, the image which can be detected will consist of the original recorded image, that is of light and shade corresponding to the amplitude of a colour video signal. If the reproducing beams are arranged to interfere at the photocathode of a photomultiplier then the light and shade signals will produce an electrical signal—the video signal which we want.


This video signal will contain all the information required to operate a colour TV set, including the sync and colour-burst signals, but it will be usable only if the rate at which it is played back is equal to the rate at which it is recorded. The playback system must therefore wind the tape at a reasonably constant speed equal to the speed with which the original recording was made, though this requirement is not so stringent as that for a videotape recorder since the hologram is tolerant of mispositioning.

More important is the scanning of the tape. If the laser beam can be scanned the light can be focused straight into a photomultiplier, as has been assumed in this description. If the laser beam is not scanned the scanning must be done by the pick-up tube, which would presumably be of the form of the old-time Farnsworth image dissector (see *Early TV Camera Tubes*, PRACTICAL TELEVISION, June 1969). In either case some form of sync signal would be necessary so that the scanning keeps in step with the rate used at the recorder, but again we would expect this process to be very tolerant of errors.

The video signal is then amplified and modulated on to a suitable r.f. carrier so that it can be fed directly to a colour TV set aerial input socket.

This has not been the only announced application of lasers to TV. Others include large-screen colour TV and also 3-D TV. The Selectavision system however seems to be the most advanced application of lasers to TV practice and is certainly the only application so far of holographic recording. It is certain that we shall see other applications of this remarkable method of image coding and decoding.

SYNCHRONOUS DETECTORS

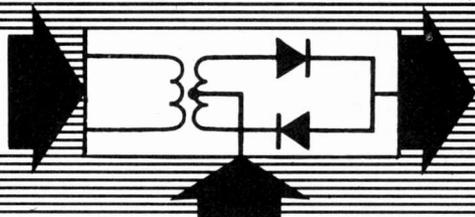

S GEORGE

MOST colour receivers incorporate four synchronous demodulators, one to detect the R-Y colour-difference signal, one to detect the B-Y colour-difference signal, one to detect the burst signal and one as a.f.c. discriminator in a flywheel line sync circuit. Thus the first thing to note is that synchronous demodulators are not something completely new, though the synchronous detector circuits used in colour television receiver decoders are rather different from the familiar line sync discriminator circuits. The Philips G6 single- and dual-standard chassis use in addition a further synchronous demodulator as automatic chrominance control rectifier.

Phase-sensitive Detectors

An alternative name for synchronous demodulators is *phase-sensitive rectifier* and this brings out the important feature of synchronous detectors, that they provide an output which is proportional not only to the amplitude of the signal to be detected but also its phase at the instant of detection. This means that unlike a simple diode detector a synchronous detector will provide either a positive- or negative-going output depending on the phase of the signal being demodulated at the instant of detection—or, more accurately, to the phase relationship between the signal being demodulated and the reference signal also fed to the synchronous detector, synchronous detectors requiring as we shall see two inputs.

This phase-sensitive action is illustrated in Fig. 1. A sine-wave signal is shown at (a) and a simple diode detector would pass either the positive or negative-going signal excursions depending on which way round it was connected. If a synchronous detector conducts at instants A during each cycle of the sine-wave it will provide an output as shown at (b), while if it conducts at the instants marked B it will provide an output as shown at (c). These outputs of course assume that there is no load capacitance in the detector circuit.

Timed Rectifiers

We have emphasised the instant of conduction. This is because synchronous detectors are “timed”, that is unlike a simple diode detector which conducts on alternate half-cycles of the signal for a certain time a synchronous detector conducts, as illustrated in Fig. 1, for a brief, set instant each cycle or half-cycle (depending on the type of circuit). As a result of this instead of getting an output which is always either positive- or negative-going, the output of a synchronous detector is positive- or negative-going as shown in Fig. 1(b) and (c), depending on the phase of the signal

at the instant conduction. Thus a synchronous detector rectifies either the positive- or negative-going signal excursions depending on the point during the reference signal cycle at which it conducts, the reference signal providing the timing action. Fig. 1 (d) shows a synchronous detector in block schematic form: the reference signal switches the synchronous detector on once or twice each cycle to obtain the required output.

Need for Synchronous Detectors

But why is a phase-sensitive detector necessary for demodulating the chroma signal, that is for R-Y and B-Y colour-difference signal demodulation?


It will be recalled that in colour television the *amplitude* of the chroma signal denotes the *strength* or *saturation* of the colour—whether for example it is pale pink or deep red—while the *phase* of the chroma signal denotes the actual colour—red, green, blue and so on. So in demodulating the chroma signal we need to extract information on its amplitude and phase—which a synchronous demodulator does.

To take an example, Fig. 2 (a) shows the basic B-Y colour-difference signal for the standard colour-bar test pattern while Fig. 2 (b) shows this signal after modulation on to its subcarrier. If (b) is demodulated by a simple diode detector we get the signal shown in Fig. 1 (a)!. And this is because the output of a simple diode detector tells us nothing about the phase of the chroma signal.

The important difference between Fig. 1 (a) and (c) is one of polarity. In Fig. 1 (a) bars 1, 3 and 5 are negative-going while bars 2, 4 and 6 are positive-going. In (c) they are all positive-going—which would give us, to take the first colour bar (we are ignoring the white and black bars of the actual test pattern since there are of course no colour-difference signals during these bars) a blue signal (compare with bar 6) on the yellow bar when the blue gun of the tube should actually be cut off, yellow resulting from a combination of red and green in colour television.

Colour Signal Modulation

Now the modulation system used for the colour-difference signals indicates to the receiver whether the detector output should be positive- or negative-going. This is done by modulating the chroma subcarrier in both phase and amplitude, phase as previously mentioned indicating the particular colour and amplitude its saturation. The “colour clock” diagram shown in Fig. 3 makes this clear. The chroma signal can vary in

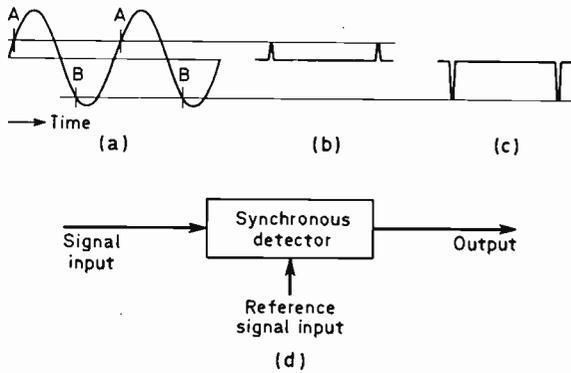

phase from 0° , representing red, at the top, right round to red again, the various phase positions in between ($360^\circ =$ one cycle of the subcarrier) representing different colours. Thus a signal at A, 10° away from R, would consist of red with a small amount of blue added, i.e. a variation away from pure red towards magenta. A signal 225° away from the reference 0° point brings us into the $-B$ and $-R$ regions, i.e. here the blue and red guns of the tube are biased back to give us a yellowish green colour. At C we've a mixture of equal red and blue giving magenta while at D we have blue but R is in the negative region giving us a cyan shade—shown in this case as being of low amplitude to bring out the saturation/signal amplitude aspect.

To go back to Fig. 2(b), it will be appreciated that the phase of the signal on bars 1, 3 and 5 is such that the signal moves in the $-B$ region of the "colour clock" while on bars 2, 4 and 6 the phase of the signal is over on the right-hand side of the colour clock.

It will be clear now why a phase-sensitive detector is needed to get (a) instead of (c) in Fig. 2: if our chroma detector tells us something about the phase of the signal as well as its amplitude, then we shall be able to recover (a). And this is where the second, reference signal input to the synchronous detector comes in. This input is used to switch on the synchronous detector briefly once or twice (depending on circuit configuration) each subcarrier cycle to sample the amplitude and phase of the signal at that

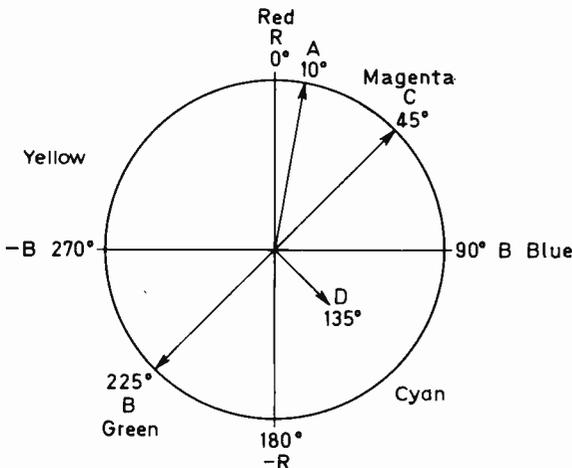


Fig. 3: The "colour clock": the phase of the chroma subcarrier varies to indicate different colours.

Fig. 1 (left): Operation of a phase-sensitive rectifier. The rectifier will produce an output as shown in (b) if switched on at the points marked A during the sine-wave input; if switched on at the points marked B it will produce an output as shown at (c). The polarity of the output thus depends on the instant at which the rectifier conducts during the input waveform. In (d) a block diagram of a synchronous detector is shown: the reference signal input is used to switch on the synchronous detector which then samples the signal input providing an output which depends on the phase and amplitude of the signal.

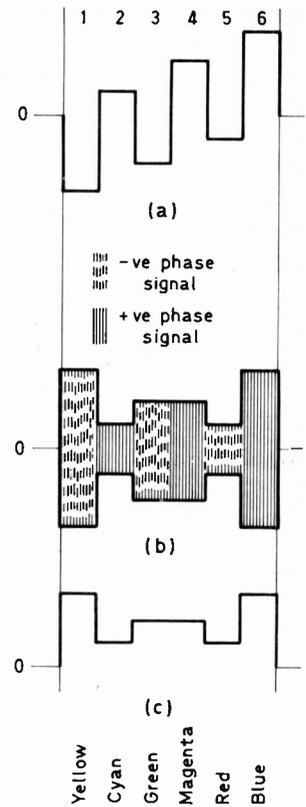


Fig. 2 (right): (a) The B-Y colour-difference signal for the standard colour-bar test pattern. (b) The signal shown at (a) modulated on to its subcarrier. (c) Output derived from (b) by a simple diode detector.

instant, the output then being of the correct amplitude and polarity. For this action to be accurate of course the transmitter subcarrier and receiver reference oscillator must be synchronised and for this purpose the colour burst is transmitted once each line.

To return to the B-Y colour-bar signal shown in Fig. 2 (a), to obtain correct reproduction we need to know during each bar the polarity and amplitude of the signal as indicated by the phase and amplitude of the modulation. So what we do is to arrange for our B-Y synchronous detector to conduct briefly at the 90° , or 90° and 270° points, in Fig. 3, i.e. on the B-Y axis. It will then tell us once or twice each subcarrier cycle the amplitude of the B-Y signal at that point and whether it is of negative or positive polarity. If we switch it on on every half-cycle we must of course invert the output on alternate half-cycles to get a consistent signal.

Practical Circuits

There are many variations in detail in synchronous detector design but all those so far used in colour sets in this country fall into one of four categories: series-diode bridge, series-diode pair, shunt-diode pair and triode valve. The series-diode bridge has till now been most frequently used and was briefly introduced last month. It is shown again in Fig. 4 (a). When the diodes are non-conducting the chroma signal is isolated from the load resistor R_L and its associated capacitor C_L . A reference signal at subcarrier frequency is also however fed to the bridge, via T1. Once each cycle the junction of diodes 1 and 2 will be sufficiently positive for them to conduct

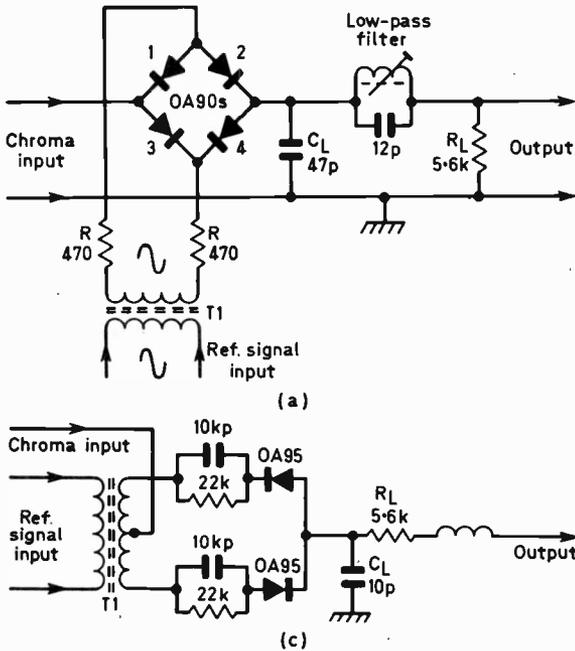



Fig. 4: Four types of synchronous detector: (a) series diode bridge; (b) shunt diode pair; (c) series diode pair; (d) triode valve.

and, 180° later, the junction of diodes 3 and 4 will be sufficiently negative for them to conduct. During these occasions CL charges to the chroma signal amplitude—positive or negative with respect to earth. The diodes are in opposite polarity on alternate half-cycles, giving the required signal inversion.

The bridge must of course conduct only briefly on each occasion—on the negative and positive tips of the subcarrier signal. With a peak chroma signal of about 1V a 5-7V reference signal is necessary and the resistors R ensure that the diodes conduct only on the peaks of the reference signal input. The reference signal itself is not wanted of course and is filtered from the output by the low-pass filter.

Quadrature Detection

Now if there is no chroma signal, or the chroma signal is 90° out of phase with the reference signal, there is no output: the reference signal is filtered out while if the chroma signal is 90° out of phase with the reference signal it will be at zero at the instant when the diodes conduct. This latter feature enables the detector to discriminate against unwanted cross-talk between the R-Y and B-Y colour-difference signals. Although these are separated in the PAL system in the delay-line circuitry, nevertheless slight unbalance in circuit tolerances may lead to some B-Y information being present at the input to the R-Y detector and vice versa. As the R-Y and B-Y signals are 90° out of phase however unwanted cross-colour components will be ignored by the detectors since the reference signals fed to them are in quadrature— 90° apart in phase—and synchronised with the transmitter's subcarrier so that the R-Y detector operates on the correct R-Y axis and the B-Y detector operates on the correct B-Y axis. A 90° phase shift network is generally incor-

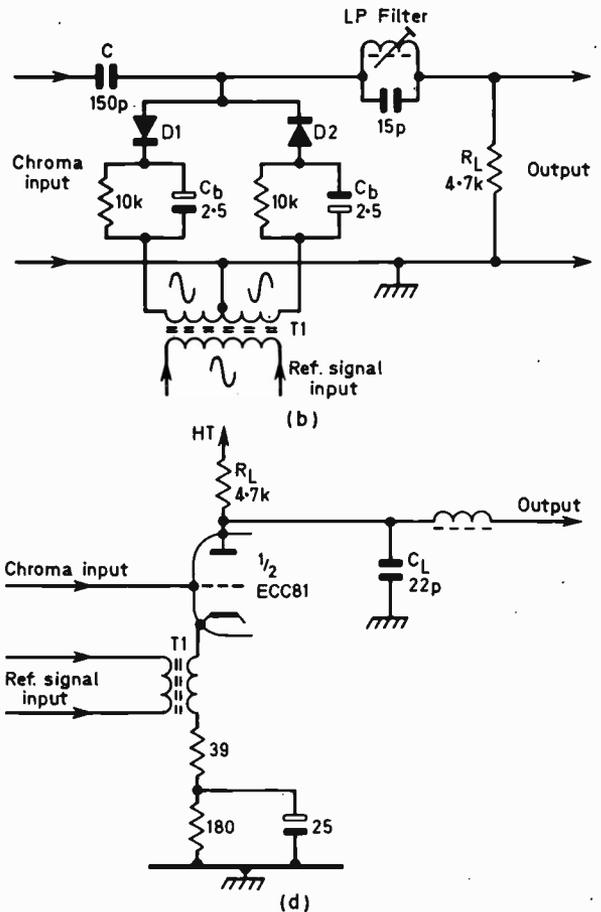

porated in the reference oscillator feed to the B-Y detector in order to achieve the correct 90° phase displacement between the instants of conduction of the two colour-difference synchronous detectors.

R-Y Switching

With the R-Y signal we have of course the further complication that its phase is alternated 180° from line to line in the PAL system. It will be appreciated however that this can be adjusted in the receiver either by shifting the R-Y signal back again in phase on alternate lines or by inverting on alternate lines the phase of the reference oscillator feed to the R-Y synchronous detector.

Dual-diode Detectors

A shunt-diode pair synchronous demodulator is shown in Fig. 4(b). Here the previous system has been re-arranged, the capacitor being in series with the signal instead of shunting the output while the active elements are in shunt instead of in series with the chroma signal. The two diodes form a bridge with the centre-tapped secondary of T1. The inset waveforms show that the two diodes conduct together once each reference signal cycle—when the signal at D1 cathode is negative-going and that at D2 anode positive-going. The whole bridge is effectively at earth potential when the diodes conduct, and the capacitor then charges to the signal voltage presented

to it, subsequently discharging via R_L . The bias capacitors C_b charge up so that the diodes conduct only on the tips of the reference signal.

Clamp Detector

It will be noticed that the basic circuit shown here is identical to one form of d.c. clamping circuit, and in fact this circuit is sometimes referred to as a clamp detector. The difference is purely one of frequency of operation. A black-level clamp is switched on at line frequency, i.e. once each line or 15,625 times a second, whilst a synchronous detector is switched by the reference signal at 4.43MHz. The effect is much the same: in the clamp circuit the coupling capacitor charges to the sync tip amplitude every time the clamp conducts while with the synchronous demodulator the capacitor charges to the varying chroma signal amplitude each time the detector diodes conduct.

Series-diode Circuit

A series-diode pair synchronous detector—as used in the Philips G6 chassis—is shown in Fig. 4(c). As in the circuit shown in (a) the diodes isolate the chroma signal from CL . The diodes conduct once each reference signal cycle and CL is then charged by the chroma signal. The capacitors in the bridge ensure that the diodes conduct only on the reference signal tips.

Triode Synchronous Detector

For the sake of completeness Fig. 4 (d) shows the triode synchronous detector used in early Baird colour chassis and in many US models. The cathode circuit is controlled by the reference signal and incorporates a bias network so that the triode conducts briefly on the tip of the reference signal waveform, CL then being charged by the chroma signal.

Burst and Flywheel Sync Detectors

To turn finally to the burst and line a.f.c. discriminators, these of course have in common the fact that they both provide an output to control the frequency of an oscillator—the decoder reference oscillator in the former case and the line oscillator in the latter. The principle of operation is similar to that already described. In the case of the burst detector the burst signal (the 10 cycles of subcarrier transmitted during the sync pulse back porch period) is one input and the reference oscillator output the other, an output being obtained only when both signals are applied to the detector. The output is positive- or negative-going depending on whether the oscillator leads or lags the burst signal in phase, and is used after smoothing as a control potential to control the reference oscillator frequency. In the case of a flywheel sync circuit the inputs to the discriminator are of course the sync pulses and a reference waveform tapped from the line oscillator (rarely) or the line output transformer. The control action is the same as in the case of the decoder reference oscillator. We will give examples of burst phase detector circuits in a later article when we consider the entire burst gating and amplifying circuitry and the a.p.c. loop. ■

NEXT MONTH IN

TELEVISION

SIMPLE EHT METER

With the increasing use of transistorised line output stages and semiconductor e.h.t. tripler circuits the days of spark testing for e.h.t. are fast disappearing and there is consequently the need for a means of simply metering the e.h.t. supply. Next month we provide details of a simple, safe meter to meet this requirement.

IMPROVE YOUR TV AUDIO

Few modern sets do anything like justice to the quality of the TV sound signal transmitted. One solution might be the use of a separate hi-fi amplifier and loudspeaker. There are however problems in making safe electrical connections to a TV set with its a.c./d.c. techniques. An alternative approach presented next month is to build a good-quality audio circuit into your set: this can be used to drive a separate hi-fi loudspeaker if required. The amplifier is based on the Mullard 3-3 circuit, using only two valves, so can be easily built into any set.

VIDEO LF RESPONSE

The video circuits should have ideally a response down to d.c. but there are certain conflicting requirements. A lot of attention in design detail goes into shaping the response of the video amplifier at this end of the video spectrum and we shall be taking a close look at the techniques used in modern sets.

SHF RECEPTION

After v.h.f. and u.h.f., what next? The answer may be a move into the s.h.f. bands. Experiments are already being carried out and next month we shall be reporting on the results of these and the problems of producing a suitable converter for use with a standard TV set.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW

TO.....
(Name of Newsagent)

Please reserve/deliver the FEBRUARY issue of TELEVISION (3/6, 17½p), on sale FEBRUARY 12, and continue every month until further notice.

NAME.....

ADDRESS.....

versatile IC 'SCOPE PREAMPLIFIER

PART 2

MARTIN L. MICHAELIS, M.A.

THE output at Sk4 should be connected to the oscilloscope with any convenient length of coaxial cable not exceeding about two yards. Special alignment for a particular length as for an input signal probe is not necessary here. The acceptable cable length and capacitance tolerance at Sk5 are even greater since the bandwidth restricting capacitor C17 already imposes a high basic capacitive load. Resistors R33, R34 and R32 restrict the possible currents at the respective outputs so that even prolonged short-circuits with full drive cannot damage the preamplifier. Both outputs—Sk4 and Sk5—are suitable for driving headphones of any impedance from 50Ω to 4kΩ directly. As shown in Fig. 2 last month the preamplifier may be used in this manner as a sensitive r.f., i.f., a.f. signal tracer on its own.

With the oscilloscope connected to Sk4 headphones (or any ordinary monitor amplifier with loudspeaker) may be simultaneously connected to Sk5. Alternatively, with the oscilloscope connected to Sk4 the i.c. millivoltmeter described in the Oct. issue may be connected simultaneously to Sk5. Always connect to the 5V f.s.d. range of the i.c. millivoltmeter, never to any other range, when using the instrument in this manner. The voltmeter reads according to its normal $\pm 5V$ f.s.d. scale when the coarse gain switch of the preamplifier is in the centre position 2 and the 10:1 signal probe is used at input Sk1. In switch position 1 the meter then reads $\pm 25V$ f.s.d. and in position 3 it reads $\pm 2.5V$ f.s.d. with corresponding deflection sensitivities on the oscilloscope in each position.

The vernier gain control of the Videoscope MV3 allows for 10:1 ratio maximum discrepancy between the d.c. and a.c. components of a signal whilst remaining within the linear ranges of the equipment. Switch S2 must of course be set to d.c. whenever meter and scope displays are required simultaneously.

If during a series of tests through a piece of equipment the odd test point carries an excessive d.c. potential temporarily move S2 to a.c. for such test points to mute the meter. Provided the 10:1 signal probe is always used for dual meter-and-scope readings there are no significant meter offset shifts with different source impedances at the test points touched with the signal probe.

To set up connect the signal probe, preamplifier, i.c. millivoltmeter and oscilloscope as shown in Fig. 2 and switch on the i.c. millivoltmeter *first*. After adjusting its set zero control switch on the preamplifier and then adjust its d.c. shift control to re-zero the meter. Do not touch the zero control of the i.c. millivoltmeter again. Any zero corrections of the meter are subsequently always made with the zero shift control of the preamplifier. Set the polarity switch on the i.c. millivoltmeter as required. It is equally permissible to readjust the preamplifier d.c. shift control for centre zero meter reading if repeatedly changing d.c. component polarities are encountered at successive test points. This does not affect the a.c. component display on the oscilloscope.

If the strobe-trigger timebase unit is also included in the equipment set-up always connect the preamplifier between the signal source and the strobe-trigger timebase unit, not between the latter and the oscilloscope. There are no restrictions in the logically available functional combinations and the i.c. millivoltmeter or headphones may be connected simultaneously to the second output of the preamplifier.

First Stage

The gain factor is determined in the normal manner for an operational amplifier as the ratio of the negative feedback resistor R13 to the total \bar{IP} source resistance $R6 + R4 + R5 = 420k\Omega$. This ratio is evidently 5. The output lag capacitor C11 and the input frequency compensation C8, R14 have been given corresponding fixed values.

As usual \bar{IP} is a voltage node point (virtual chassis short-circuit) with the heavy applied negative feedback via R13 so that for input signals coming via R2 or R3, R6 behaves as if it were in parallel with R4 and R5, presenting a net impedance of roughly 100kΩ between the bottom end of C3 and chassis. It is not practicable to obtain a higher impedance value here by using proportionately higher values for R4 to R6 because this would demand impossibly large values for R13 to maintain the required gain factor. The author has satisfactorily used values of up to 15MΩ in the equivalent position R13 for mathematical operations (we shall meet an example in a subsequent operational amplifier article featuring a frequency meter) where large capacitances are in parallel therewith to provide the integrator function, but the system is prone to severe instability and excessive noise if values much greater than 2MΩ are used in a.c. amplifier applications.

We are using conventional \bar{IP} -side voltage offset balance with VR1 to set the d.c. operating point right through both stages. To maintain reasonable offset current symmetry and thus keep the class A operating point on the track of VR1 even in the maximum gain setting of S3 it is necessary to satisfy the usual condition that the source impedances at \bar{IP} and \bar{IP} should not differ too greatly. Hence the large value

of R7 to match R4 to R6, which R8 alone cannot match.

We mentioned last month the fact that a differential amplifier generates at least twice as much thermal input noise as a single-ended stage because being random the noise components at IP and \bar{IP} do not cancel but add quadratically and there is a current division noise contribution. C7 mitigates this additional noise by reducing the IP source impedance drastically for a.c. signals, leaving only R8 as surge safety resistor in this branch.


The value of R7 has been chosen sufficiently smaller than the sum of R4 to R6 to bring the class A operating point (zero d.c. voltage at outputs with inputs open-circuit) near the positive end of VR1 track in the maximum gain setting of S3. This provides class AB, B and C operating points too within the range of VR1.

Check as follows: The class A operating point (voltmeter at Sk5 reads zero) should lie about 30% of the track of VR1 from the right-hand stop with S3 in position 3. The class B operating point (amplifier just cutting off) should lie about 30% of the track of VR1 from the left-hand stop. The grass on the Videoscope MV3 at maximum gain setting, S3 in position 3, vanishes abruptly at this point leaving only the undisturbed timebase trace for all settings of VR1 further to the left. Alternatively check with headphones at Sk5; the weak background hiss vanishes abruptly at the class B point.

If the class A and class B points do not lie reasonably close to the specified settings of VR1, judiciously adjust the values of R9 and R10 after first making sure that the trouble is not due to grossly unequal voltages of the two batteries. Apart from the need of two stages for proper positioning of the gain switch and for no net inversion of signal polarity, the two-stage arrangement preserves absolutely symmetrical current drain from the two batteries regardless of d.c. operating point because when one stage is driven up the other is driven down and vice versa. Thus the total current drain is 3.5mA per fresh battery irrespective of the operating point set by the d.c. component of a signal or with VR1, and the two batteries will discharge symmetrically.

This is why the input IP has been used as signal input for both stages even though impedance problems would have been much simpler with the IP inputs and correct signal polarity would have been given just as well. If however the IP inputs had been used as signal inputs any operating point other than class A would have produced grossly unequal battery loading and consequent early exhaustion of only one battery. The resulting confusion regarding battery renewals effectively shortens the service life of a pair of batteries to less than 20 hours whereas with the guaranteed symmetrical discharge at least 48 hours non-stop operation without a rest are obtainable with any operating point, or 60 to 80 hours intermittent.

Always replace the batteries as a pair, not individually, and as far as possible use two batteries from the same batch as replacements. It is then safe to assume that the batteries will always discharge symmetrically giving optimum service life as long as they are not defective. It is not necessary to be unduly apprehensive about battery life by switching on for only brief measurements. It is normally

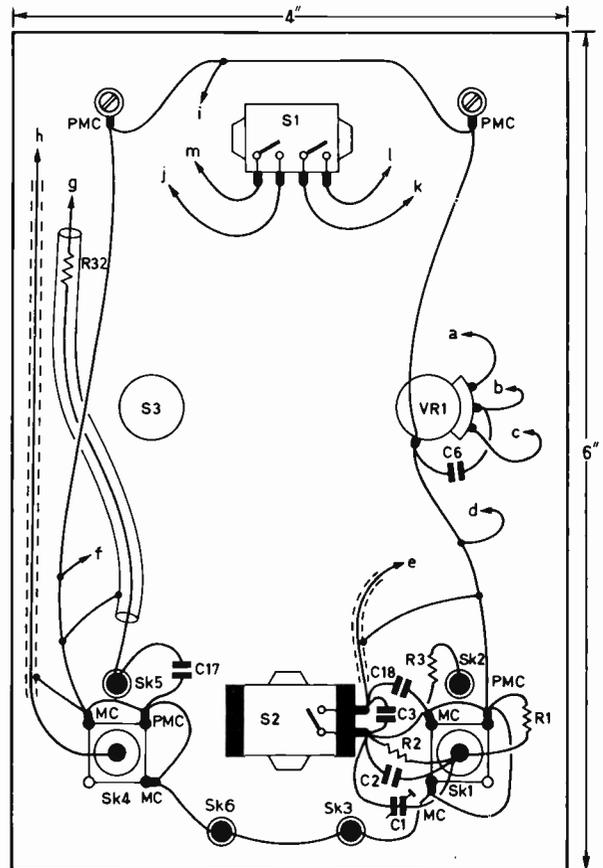

MC Chassis soldering tag under fixing bolt for coaxial socket
PMC Chassis soldering tag under fixing bolt for coaxial socket and printed circuit board

Network MC/PMC bare tinned copper wire
Lead g/R32/Sk5 insulated wire and resistor, insulated sleeving, outside shield braid sleeving
S3 attached to printed circuit board

Fig. 3: Wiring on rear of front panel.

quite economical to switch on at the start of a working session of several hours and to switch off only at the end of work—but remember to switch off before leaving the workshop!

Class B and C Operating Points

There are several very important applications of these features. To mention only two, better output swing exploitation in relation to d.c. components is obtainable with a class B or just AB operating point for highly asymmetrical pulse waveforms. If strobe or trigger is required with waveforms possessing much large-amplitude detail between the dominant pulse sections, e.g. with composite video and sync waveforms, improved stability is possible by selecting a class C operating point to effect sync pulse separation. The correct setting of VR1 for this purpose can be observed by first connecting the preamplifier output to the oscilloscope Y-input and then transferring to the external sync input.

Further consideration of non-class A operating points will be left to a following article introducing mathematical operations with the MC1709CG and featuring a frequency meter. The present preampli-

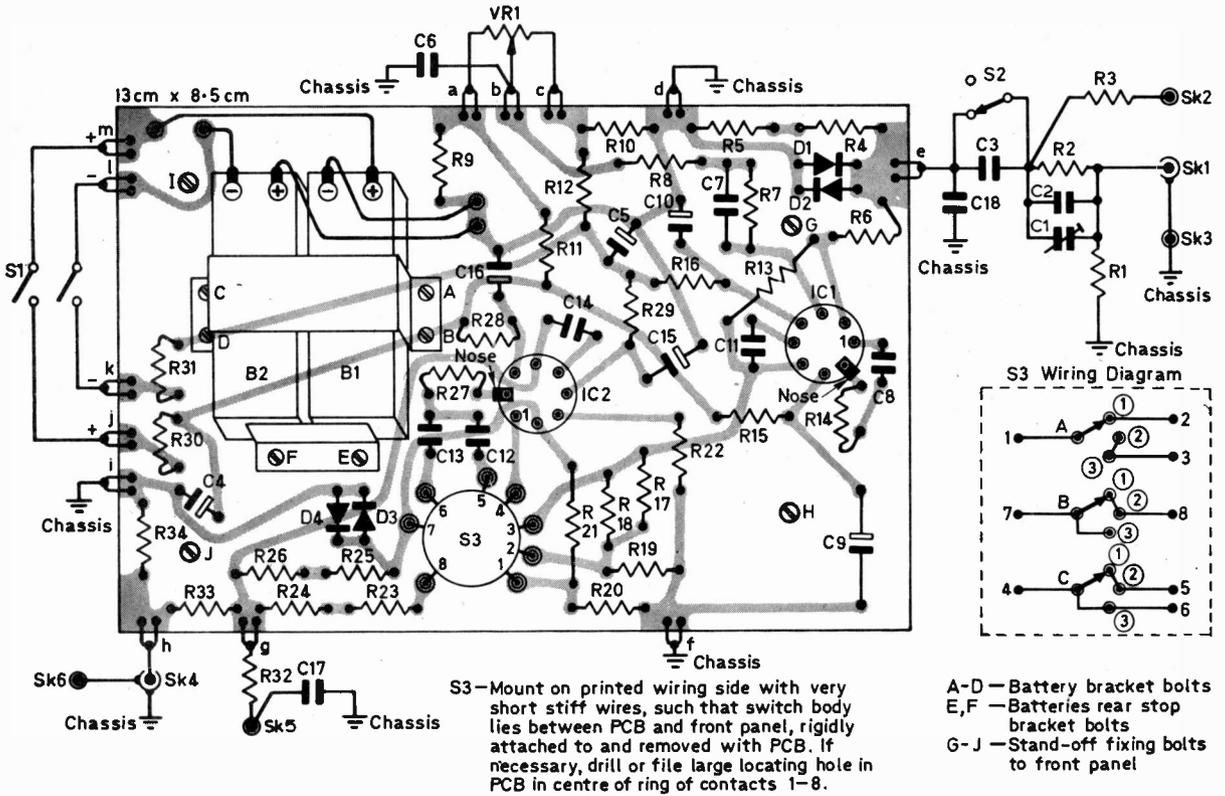


Fig. 4: Layout of the printed board, viewed from the component side.

fier is envisaged as drive preamplifier for this frequency meter, with threshold selection facilities similar to the sync separator function of a television receiver.

Second Stage

The gain factor is here the ratio of R23+R24 (or R25+R26) to R21 plus R19 in setting 1 of S3A or plus the output impedance (about 150Ω) of IC1 in settings 2 and 3 of S3A. The IP source impedance is thus very nearly 2.5kΩ in all settings of S3A. S3B, switching the negative feedback resistors, establishes nominal gain factors of 20 or 40. A common output lag value for C14 suffices for this small range of gain variation, but the input frequency compensation must be switched with S3C. R22 provides the same source impedance for IP as for IP to cancel offset current. This stage possesses no offset voltage compensation of its own since by virtue of the d.c. coupling VR1 serves to control the offset for both stages and thus saves more than half a milliamp of battery current because only one bleeder network is necessary.

Adjustments

The various series or parallel combinations of two resistors serve for alignment by selection. Equivalent preset potentiometers may be used if desired.


With a signal of about 5kHz fed to Sk2 select a slightly different value for R4 or R5 (if necessary) to make the output voltage at pin 6 of IC1 exactly five

times the input voltage fed to Sk2 (use oscilloscope with signal probe touched to respective points). Now select a different value for R17 (if necessary) to make the signal voltage across R19 exactly the same as the input voltage fed to Sk2. Next with S3 in position 1 select a different value for R23 (if necessary) to make the voltage at Sk4 ten times as great as that fed to Sk2. Finally switch S3 to position 3 and select R26 to make the voltage at Sk4 ten times as great as a signal voltage fed to Sk1.

Bandwidth

Inject a squarewave of a few kHz repetition frequency to Sk1 via the 10:1 signal probe (see Fig. 2) after this signal probe has already had its own trimmer capacitor adjusted for dead-beat squarewave display when connected directly to the Video-scope MV3. Now adjust C1 for dead-beat squarewave flanks, without rounding-off or overshoot noses. The resulting bandwidth is as specified in Table 1 with the 6dB point lying at 350kHz for the W input and output combination if C1 is adjusted for dead-beat squarewaves. If C1 is adjusted to give about 10 to 20% overshoot noses on the squarewave display the bandwidth is boosted to approach 1MHz. This may be useful for some applications involving quasi-sinusoidal signals rather than pulse signals, but for general television work it is generally preferable to use the dead-beat pulse display alignment. A bandwidth of 350kHz is normally quite adequate at high deflection sensitivity and it is usual to restrict bandwidth when boosting deflection sensitivity.

—continued on page 129

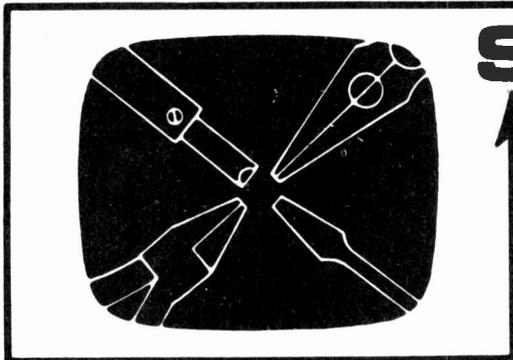

SERVICING television receivers

L. LAWRY-JOHNS

BAIRD 620-640 SERIES

cabinet should for obvious reasons be resisted.

THIS group of models was developed from the 600 series which had many similar features. Some of these notes will therefore be found to apply to this previous series but the correct service information should be used if any involved servicing is undertaken on these earlier models.

These are quite reliable receivers, suffering mainly from width circuit problems or trouble with the u.h.f. tuning drive. The latter trouble takes the form of distortion of the drum on which the nylon drive cord is wound or breakage of the drum at the centre boss. Modified drums were used during production and the serial number of the set should be quoted when ordering replacements. The diagrams which accompany this article should render further comment on restringing unnecessary.

Width Modification

Modification was also made to the width circuit to increase the range of the control. This it undoubtedly did but it also resulted in the possibility of quite a nasty burn-out, as with the modified arrangement the control was connected directly from the boost line to chassis. The absence of a series resistor means that as the control changes value (which they do) the current increases to a point where the control burns out with the possibility of damage to the panel or nearby components. It is the writer's practice to include a $1M\Omega$ resistor from the low end of the replacement control to chassis to prevent a recurrence of the trouble.

Access

Whilst servicing the main deck is quite easy since it swings down when the two top side screws are removed (support the chassis when removing the screws or it may swing down quicker than you want it to!) access to the tuners is not so easy in some models as the space is very limited.

The top fixing screws of the side assembly are obvious but the two bottom ones are situated in a very restricted space requiring the use of a long screwdriver or a very small coal miner. The front knobs pull off—even if they do not appear to—as far as the tuners are concerned, but the volume and brightness knobs may have grub screws. Some models have a small cover at the bottom of the cabinet: this allows the v.h.f. turret contacts to be cleaned easily, an operation which is necessary when v.h.f. switching becomes troublesome.

Servicing of the larger and rather handsome 23in. models with folding doors is much easier but the temptation to lift these by the top overhang of the

Common Faults

Mention has already been made of the boost line supply to the width control where some trouble can be expected. Attention is also directed to the boost line supply to the tube first anode and field oscillator. From the circuit it will be seen that this is a common supply point from the top of the focus control R103, the other end of which connects to chassis. As with the width control, so with the focus control: it can and does change value. As it does so the height of the picture is reduced with a perhaps not so obvious darkening of the picture as the first anode voltage at pin 3 of the tube base also falls.

It is not always necessary to replace the focus control if the value has only fallen to say $1M\Omega$ or thereabouts. The optimum position of the slider is usually at the top end and therefore the introduction of a $1M\Omega$ resistor between the bottom end and chassis will often restore normal conditions with no further change of working value. This type of improvisation may cause a frown to appear upon the brow of some engineers who are used to the cosy confines of a workshop, but when one is out in the depths of the Yukon on a cold wet night it has a certain appeal!

Field Timebase

Quite often the symptoms of lack of height are due to a failing PCL85 (PCL805) and this is the valve to change when one is faced with a reduced scan, no vertical scan at all, vertical hold troubles or a jittery picture. If a new valve does not clear the trouble or new troubles present themselves try another new one (not all new valves are good).

In the event of lack of height, after this try checking the value of R195 ($820k\Omega$) and C238 for leakage. Then check R187 and R188 if necessary.

In the event of bottom compression check C234 by shunting a $100\mu F$ capacitor across it and see that the colours of R178 are bright and clear. This 330Ω resistor does not often change value in this model but it can be damaged by a faulty PCL85.

If field roll is the trouble note whether the control is at one end of its travel or not. If it is check R183 and C235 and also the control itself (remember that the PCL85 has already been checked). If the rolling is up or down with no secure locking point try squeezing the M3 interlace diode X10 with a pair of pliers (to improve the internal contact) before measuring its back-to-front resistance. If the fault is not due to the interlace diode check back to the sync separator screen feed resistor (R78) $100k\Omega$ and the video cath-


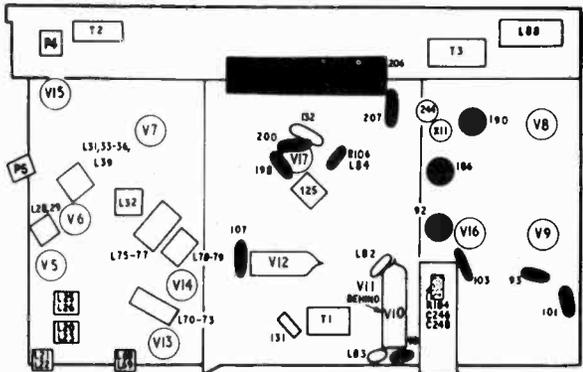
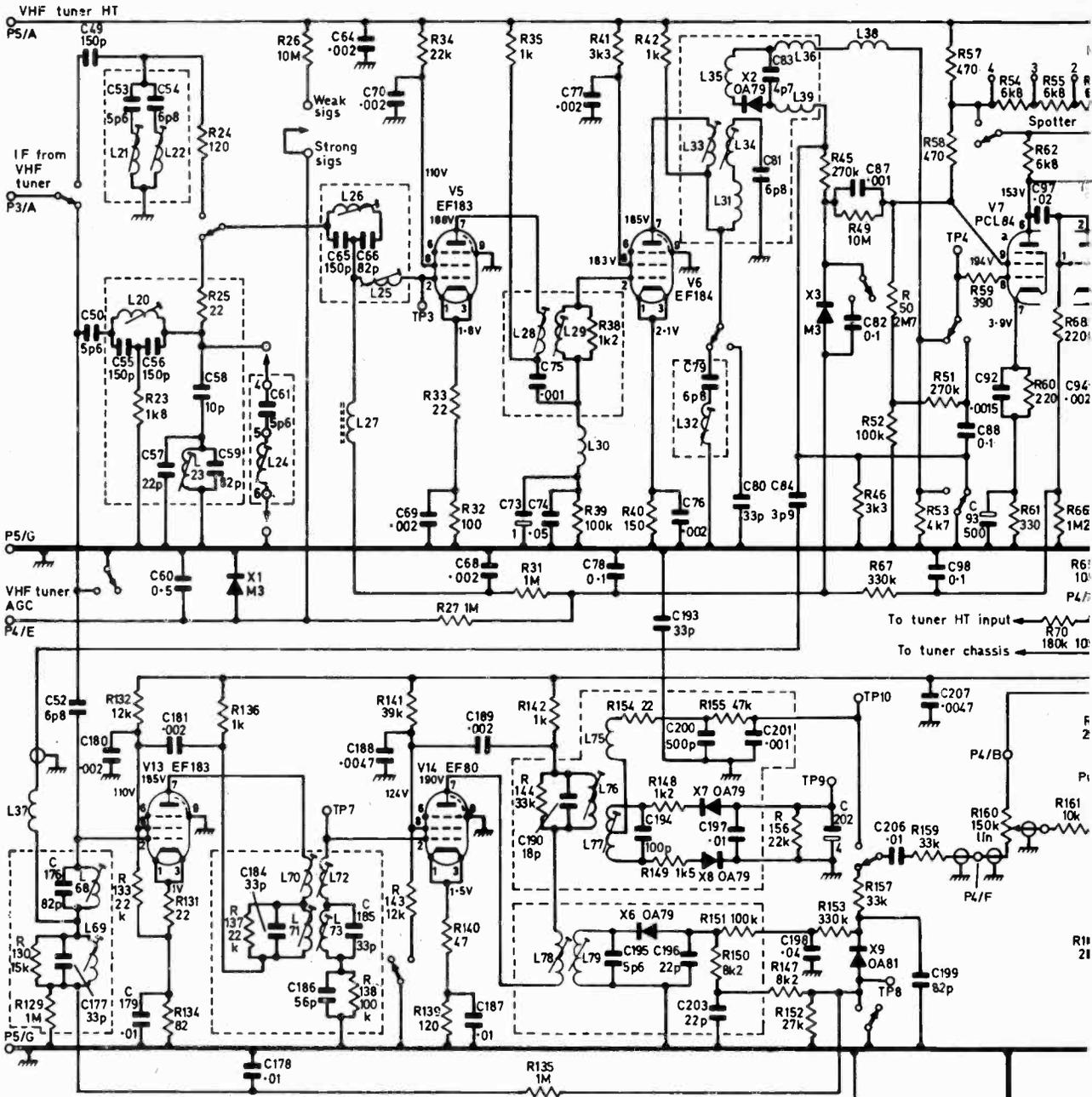



Fig. 1: Circuit of the main chassis, Baird 620-640 series.

Fig. 2 (left): Rear chassis view.

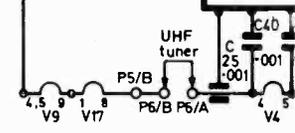

ode 500µF electrolytic C93 which may be open-circuit.

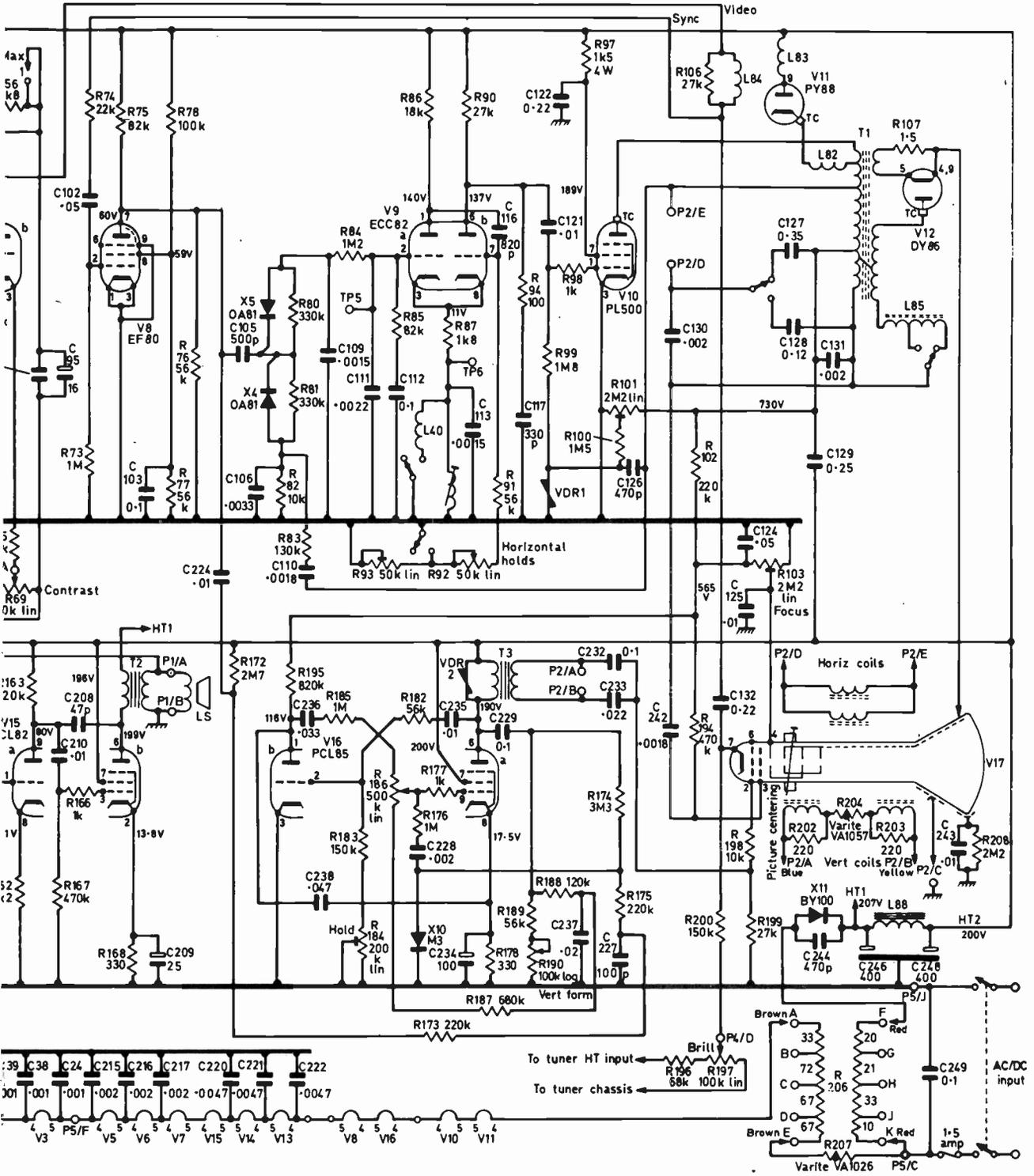On occasions the symptom of no scan at all will present itself—evidenced by a narrow line across the screen. If the PCL85 is not responsible (it nearly always is) it will be necessary to check the voltages at the base. If there is no voltage at pin 6 but pin 7 shows normal h.t. this will generally indicate an open-circuit in the primary winding of the field output



transformer (the v.d.r. will allow a little voltage to appear at pin 6 but not a lot).

The Video Stage

The PCL84 video amplifier stage can be the source of a few troubles, some obvious and some not so obvious. The obvious troubles cause loss of picture content, leaving a blank raster, a weak picture lack-

ing in contrast or what appears to be a normal picture with very poor sync.

Probably the fault which gives most trouble is when the PCL84 develops an internal short and the set is being used on 405. On this system the vision detector diode X2 is directly connected to the PCL84 control grid and the sudden appearance of h.t. at this point ruins the diode. On 625 there is a series

capacitor C88 which blocks the d.c. and saves the diode. So the lesson here is that if there is a cook-up in the video stage necessitating replacement of the PCL84 and some resistors (check the screen, grid and cathode resistors) and the set was being used on 405 lines the detector diode will also have suffered and a picture will not be obtained until this is replaced.

The video cathode capacitor C93 has a habit of going open-circuit. This leads to weak sync and a slightly smeared picture. Check by bridging another electrolytic across it.

The writer keeps a multisection electrolytic to hand with a pair of flyleads. One lead is permanently clipped to the common negative tag and is terminated in a crocodile clip. The other can be clipped to any other tag and terminates in a probe. Since the capacitor is rated at 275V and has 100, 300 and 16 μ F sections it provides a quick method of checking capacitors suspected of being open-circuit in most situations, be they h.t. electrolytics or low-voltage bias capacitors.

When checking for various faults in the video or any other section always ensure that the system switch contacts are making where they should. This is more

or less a visual examination and any adjustment is mechanical requiring no explanation.

The Audio-output Stage

A PCL82 is used in the audio stage. The fault most often encountered is weak and distorted output. This is most often due to a faulty valve but other points should be checked as these may have contributed to the valve's failure.

C210 can have leakage which will cause the valve to draw excess current with the possibility of damage to the bias resistor R168. Therefore a check on this stage should include voltage readings at the cathode pin 2 and the control grid pin 3. The latter should record no voltage and the former about 14V. The presence of a voltage at pin 3 and a higher voltage than 14V at pin 2 will indicate a faulty PCL82 or a leaky C210.

Another worthwhile check is on the value of R163 (220k Ω). This can go high-resistance, resulting in low and distorted sound.

CONTINUED NEXT MONTH

DX AMATEUR TV ON THE 70cm. BAND



Transmission from GW6JGA/T Prestatyn received portable by GD6FDZ/T on the Isle of Man, path 79 miles.



John Lawrence GW6JGA/T at Prestatyn (Photo: Rhyl Journal).

FOLLOWING a series of local /T tests between John Lawrence GW6JGA/T Prestatyn and Derek Whitehead GW6FDZ/T Llandudno and after obtaining the necessary special permission from the Ministry of Posts and Telecommunications, Derek Whitehead went /T portable to the Isle of Man for the first GD-GW Amateur Television QSO. The crossing from Liverpool was made on Tuesday 15th of September and by 17.30 hours two-way 'phone contact was established followed by two-way video.

The first video signals were around strength 2 (British Amateur Television Club TV Signal Strength Reporting System) but after some tweaking at both stations this improved to strength 3-4 and very good pictures were received in each direction. The weather conditions were good but unfortunately there was very little lift in propagation conditions.

The following day an almost continuous series of tests were made to evaluate the performance of various parts of the gear. Some lift was noticeable shortly after 12.00 hours but weather conditions deteriorated rapidly during the afternoon with dense low cloud and rainstorms. During this time very deep slow fading was experienced.

Valuable help was received from Jack Elliott, David Williams, Alan Antley GW3UTG and George Moorfield GW3DIX who kindly loaned the Honda generator used.

Location	Prestatyn N. Wales	Nr. Laxley Isle of Man
Call	GW6JGA/T	GD6FDZ/T GW6FDZ/T/A (GD)
Height a.s.l.	350ft.	1000ft.
Signal source	Vidicon camera 405 line	Vidicon camera 405 line
Tx	QQVO6/40 Grid mod. by 6CL6	QQVO6/40 Grid mod. by 5763
Rx	40W pk white BF180 converter and Ekco Model TMB272	40W pk white BF180 r.f. TV tuner and Sony TV receiver
Aerial	J-Beam 70/MBM46	J-Beam 70/MBM46
Distance		79 miles

COLOUR RECEIVER CIRCUITS

I.F. CHANNEL—1

The tuner(s) provide sound and vision i.f. outputs and on colour of course the vision signal also embodies the chroma subchannel components. Dual-standard sets not only have the complication of two tuners but also that of vision i.f. channel response switching. Usually the vision i.f. passband is fundamentally tailored to suit the 625-line signal, filters being switched in on the 405-line standard to narrow the response and to provide the necessary rejector characteristics. Sets of this kind generally employ the mixer stage of the v.h.f. tuner as an extra i.f. amplifier stage on the 625-line standard. This is achieved by taking the i.f. output of the u.h.f. tuner not to the i.f. channel direct but to the input of the v.h.f. mixer stage. To some extent this simplifies the system switching as it means that the output of the v.h.f. tuner can be permanently coupled to the dual-standard i.f. channel. Filter switching commonly takes place at the input of the i.f. channel.

The extra i.f. amplifier stage provided by the v.h.f. tuner mixer on the 625-line standard is useful in making good the gain lost in the u.h.f. tuner, for the overall gain of a u.h.f. tuner is generally below that of a v.h.f. tuner. Single-standard sets have therefore to be designed with a greater i.f. channel gain than dual-standard models and the trend is to provide this by using a cascode stage in the i.f. channel. Pye and Rank-Bush-Murphy sets are two examples which adopt this scheme (see PRACTICAL TELEVISION July 1970, pages 438-440).

Dual-standard sets also have to feature a sound i.f. channel which will respond to both the 405-line i.f. signal and the 6MHz intercarrier signal on the 625-line standard. This is achieved by the use of dual transformers and filters in the channel, one lot responding to the sound i.f. on 405 lines and the other to the 6MHz intercarrier signal on 625 lines. Owing to the substantial difference between the 405-line sound and the 625-line intercarrier frequencies, filter and transformer switching is not necessary. It is of course necessary to switch at the input from the sound i.f. takeoff on 405 lines to the intercarrier take-off on 625 lines and to incorporate audio switching to change from the 405-line a.m. detector output to the 625-line f.m. detector output.

Carrier Positions

Figure 1 shows the video-frequency spectrum of a 625-line PAL colour television signal. It can be seen that the chroma subcarrier is approximately 4.43MHz and the sound carrier 6MHz from the vision carrier. The u.h.f. tuner delivers this spectrum at i.f. and the placement of the three carriers on the i.f. response curve in a typical receiver is shown in Fig. 2. Typical alignment frequencies

GORDON J. KING

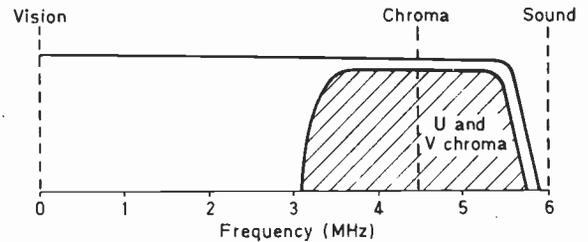


Fig. 1: Video frequency spectrum of the PAL colour television signal.

are vision i.f. 39.5MHz, 625 sound i.f. 33.5MHz and chroma i.f. about 35.07MHz. For correct vestigial-sideband detection the vision carrier normally has to fall about 6dB down the response curve. It is also common for the chroma subcarrier response to be a little down—on the other side of the response curve—by an amount depending on the design of the receiver's i.f. channel and chroma bandpass amplifier.

The chroma subchannel uses double-sideband suppressed-carrier modulation. This means that—depending on the position of the chroma subcarrier on the i.f. response characteristic—one chroma sideband could be amplified more than the other and thus result in chroma distortion. In some designs this is compensated by purposely introduced 'roll-off' or asymmetry in the chroma bandpass amplifier response characteristic. The chroma channel input high-pass filter alone may provide the necessary compensation in some designs while in others the alignment of the chroma bandpass amplifier is

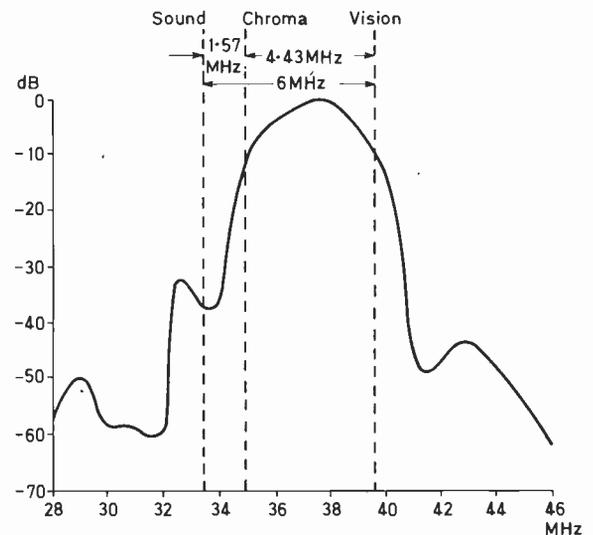


Fig. 2: Typical colour receiver response curve.

geared to that of the i.f. channel. Most of this however concerns the chroma bandpass amplifier which I shall be investigating in subsequent articles.

Returning now to Fig. 2 it will be seen that the sound carrier coincides with a rejector trough approaching -40dB . This corresponds to the 625-line sound attenuator found in all dual-standard and single-standard sets of the 625-line variety. It will be recalled that the vision i.f. channel on this standard passes the f.m. sound signal as well as the vision information and that the non-linear characteristic of the vision detector results in a beat frequency equal to the difference between the vision and sound carriers being produced. This is of course the intercarrier signal at 6MHz which carries the f.m. sound information. The vision a.m. signal which it may also carry is mostly limited in the intercarrier channel either by the amplifier stages or the ratio detector (or both).

Sound-chroma Beat

A point worth noting at this juncture is the beat between the sound and chroma signals. Fig. 2 shows that this works out to about 1.57MHz. The design of the i.f./detector channel has to take this into account so that the beat signal amplitude is kept as low as possible. Clearly, as the vision detector produces the intercarrier signal it will by exactly the same process also give rise to a 1.57MHz sound-chroma beat signal and if this is allowed into the luminance channel the picture display can be badly affected by herring-bone pattern interference. Some designers solve the problem by using separate sound and vision detectors. The sound detector must of course receive both the vision and sound i.f. signals to yield the intercarrier signal, but when two detectors are employed that dealing with the vision signal need only receive the vision i.f. signal, meaning that a rejector can be included at this point to delete the sound i.f. signal and hence also the chroma-sound beat signal.

There is hardly any point in this series in delving too deeply into the signals appropriate to the 405-line standard since these are now very well known. On this standard we have seen that the vision and sound signals are handled by separate i.f. channels. The intercarrier sound system cannot be adopted of course because the sound signal is amplitude-modulated the same as the vision signal. To clear the vision i.f. channel of sound signal, rejectors resonated to the sound i.f. are incorporated and one of these is employed to extract the sound i.f. signal from an early stage. These rejectors are not quite the same as those used in the i.f. channel on the 625-line standard for the plan in this latter case is not to delete the sound signal altogether but merely to reduce its amplitude to a rather critical lowish value to ensure the best intercarrier sound performance and the least intercarrier buzz in the sound channel.

If the rejector which puts the trough at the sound i.f. in the response curve shown in Fig. 2 is incorrectly tuned for example the sound signal will not be properly attenuated and the vision detector will receive more sound signal than required for correct intercarrier operation. The symptom is commonly that of buzz on sound caused by the interaction of the vision signal—this is generally called "intercarrier buzz". The rejector dip could also if mistuned lie

somewhere in the vision passband and on colour this could severely affect both the amplification and the phasing of the chroma subchannel signal.

Phase Aspects

So far we have considered mainly the amplitude/frequency characteristic of the i.f. channel, sometimes loosely referred to as its "frequency response". There is another equally important characteristic, the delay/frequency characteristic. This characteristic is indeed of major importance in colour receivers since if the signal delay through the i.f. channel varies over the frequency spectrum the various components of the vision signal will fail to pass through the channel at the same rate. This means that some frequency components will arrive at the output before others. On monochrome this produces the typical "echo" effects, giving overshoot symptoms like black-after-white etc., but on colour the effect can be even more severe owing to the phase-sensitive nature of the chroma signal. With the PAL system however, the phase sensitivity is significantly diminished, but if the chroma phasing is badly distorted there will be a reduction in colour saturation if not in hue error.

Thus the design of the i.f. channel in a colour set has to take into consideration the delay/frequency characteristic more critically than a monochrome set does. The switched i.f. channel of a dual-standard set can certainly aggravate the problems involved, and all told it is rather amazing that such good results on colour are achieved from most receivers of this kind. Happily the design problems are eased by the recent single-standard approach. From the circuit point of view one may not be aware of the detailed attention that has been paid to the delay/frequency characteristic since this is related mainly to the design of the tuned circuits and rejectors and to the overall alignment of these circuits.

Circuit Analysis

Now let us have a look at a representative circuit. The complete i.f./detector channel of the dual-standard Rank-Bush-Murphy CTV25-CV2510 is shown in Fig. 3. The vision i.f. stages consist of transistors Tr1, Tr2 and Tr3 and the i.f. signal from the tuner is directed to the base of Tr1 via the input filters. The sections of switch 2S1 are involved with standard changing and are all shown in the 625-line position.

The first 2S1a merely introduces an extra filter on 405 lines to assist with the tailoring of the 405 response in the manner already explained. On the 625-line standard the filter is inactive of course. The bandpass transformer in Tr1 collector circuit couples the signal to Tr2 via a rejector. Alternative bandpass coupling circuits on 405 and 625 selected by 2S1b and 2S1d link the signal from Tr2 to Tr3 base. On 625 the output from a bandpass transformer is by way of a tapping on the secondary and a capacitor to 2S1d and then to Tr3 base.

The collector of this transistor feeds two detectors. The top one D1 provides the intercarrier signal only. Here the signal is tuned by a 6MHz transformer and extracted from a tapping on the secondary. It is then conveyed through a screened lead and fed to the base of Tr10 via 2S1h. The bottom

INTERNATIONAL BROADCASTING CONVENTION IBC-70

J.I.SIM

THE International Broadcasting Convention combined a large broadcasting exhibition with a programme of technical sessions covering techniques and developments since the last Convention—in 1968. It was opened by Christopher Chataway who made it clear to the Broadcasting authorities that they had a duty to supply a television service to every person who wanted it: those living in the remote areas of Wales, Scotland, the Lake District and the South West must be considered and not all engineering resources channelled into the u.h.f. duplication of services. However, the cost per viewer of giving a television service to the really remote areas of the United Kingdom is so enormous that had it been the prime aim the u.h.f. programmes might never have started. The answer perhaps lies with satellite transmission.

The problems of coverage were also brought up by Howard Steele, Chief Engineer of the ITA, in the opening technical session. "In 1969 alone we in the Authority installed more r.f. transmitter power than in all our fourteen previous years taken together. Today we have in operation twelve main u.h.f. transmitters with a total e.r.p. of over 7MW and over 500kW of r.f. power." Mr. Steele went on to say that the ITA's v.h.f. coverage of 98.7% of the population of the UK was achieved with 47 transmitting stations including low-power relays. The BBC have nearly twice as many v.h.f. transmitting stations to obtain their higher percentage coverage. "For u.h.f. the BBC and ourselves speak hopefully of providing roughly comparable coverage with perhaps 60 main stations and 500 relays. We must be clear that to attempt full national coverage on Bands IV and V even in a country as compact as the UK will be a truly Herculean task. And not only is it going to be difficult, it's going to be damned expensive."

Technical Sessions

Automation of equipment was a predominant topic of both opening addresses and the technical sessions during the week: automation of transmitter operations, of measurements of standard parameters, of trade test transmissions, of videotape editing and so on. These things may not appear of much significance but in fact will result in programme pictures of more consistent quality. As Howard Steele put it, "They (*automation and digitalisation*) are probably the most important words at this Convention and those that will follow. From knob twiddling we went to 'hands-off'. We are now progressing to feet-up operation. Digital, or no-go, go, no-go techniques mean that we are gradually moving away from the era of graduated colour quality towards an era of either perfect quality or a totally unrecognisable blur."

Automation in the programme chains overcomes some of the deficiencies of the human operator and permits manpower reductions which with the training of television staff becoming more and more expensive is increasingly important. Unmanned stations are becoming the rule rather than the exception and whereas three years ago only a relay station was unattended now even the largest stations can be made reliably automatic. The big-

gest example is the new 1MW unattended u.h.f. ITA station at Crystal Palace. But to control the wide number of unattended stations a network of fourteen regional colour control centres has been set up at existing ITA v.h.f. manned stations: a fault at an unattended site monitored by one of these centres results in a maintenance team being sent out. Naturally with more unattended stations more members are required on the mobile maintenance teams and the installations of these stations will therefore result in some increase in transmitter personnel. A great deal of cooperation has always existed between the engineering staffs of the BBC and the ITA—sometimes very unofficially—and it is therefore rather surprising that no official arrangements have been suggested for the staff of one authority to engineer equipment of the other authority, even if only under emergency fault conditions.

Other technical sessions at the Convention included papers on developments in colour cameras, colour coders and telecines in the origination sector; on videotape copying by thermal contact and colour-film operations in the recording and films section; and on developments in the distribution of signals and in transmitting and transposing equipment.

Most of the technical sessions were fairly well balanced in their content and it was generally felt that the Programme Committee had made the best choice of papers possible. In the session on receivers however only four papers were offered. Three of these dealt with the broadcast-quality receivers used for pick-up of transmissions intended for rebroadcasting at a different frequency—as at a relay station—with the minimum possible distortion. The only paper directly about receivers was that by T. L. Harcombe of Glamorgan Polytechnic who described a hybrid, thick-film, capacitance diode tuned u.h.f. tuner for receivers. Mr. Harcombe's tuner adopts the present-day view that tuning should be independent of mechanical intricacies. He therefore follows the trend towards the use of varicaps as the tuning capacitors—the capacitance being simply controlled by a d.c. bias from a preset potentiometer.

The tuner is constructed on a substrate with the transmission (lecher) lines laid by solder dipped palladium silver. Mr. Harcombe explained that the problem of oscillator drift was more severe on a varicap tuned system because of the dependence of frequency on supply rail voltage and temperature. The former is easily solved with the use of a zener diode stabilising the supply rail voltage. The zener is thermally bonded on to the tuner substrate so that it is all at the same temperature.

Temperature compensation was considered by Mr. Harcombe in two alternative ways—either by heating the substrate with a thick-film heating element controlled by a bi-metallic strip or by using a power transistor as the heating element driven by an amplified reference voltage derived from across the zener. Both systems therefore depend on the substrate operating at above ambient temperature. The second method is to be preferred because the heating control is smooth and continuous and not an on-off mode as provided by the first method. It was rather unclear as to how long it would take in either case for the substrate to reach its operating temperature: it was also unclear whether the tuner described would meet the rather severe image-frequency rejection specification suggested by BREMA.

Apart from the mechanical simplification of the tuner the use of varicaps has a secondary advantage which is not immediately obvious: as the tuner frequency depends on a d.c. control potential a great deal of the circuitry necessary for a.f.c. in a conventional tuner is made redundant.

This paper then was the only one connected directly with the commercial receiver and this was rather surprising. After all, whatever skill goes into the production of television programmes and their provision and transmission by engineering expertise the final link is the most important one—the receiver. Bernard Rogers of Rank-Bush-Murphy was to have presented a paper reviewing

colour television receiver trends but this paper very unfortunately missed the closing deadline. This paper might have broken the unhealthy view held by the majority of the television manufacturers that their work is top-secret. This viewpoint is outdated. Sufficient details of new developments could quite happily be released to give the industry an idea of the direction in which progress lies without giving away "secret" details of particular circuits or manufacturing techniques. Perhaps it would shake up the manufacturers to know that those who really want to find out do so anyway.

One of the papers on professional receivers—by F. H. Wise of the ITA—did however touch on an area which might be of future interest in the commercial receiver. Present receivers use diode envelope detectors for video and because of the nature of the vestigial sideband transmissions this results in a form of distortion known as *quadrature distortion*. This shows up as a narrowing or expanding of horizontal picture detail. The professional receiver is now beginning to use synchronous detectors (a similar arrangement to that used for detection of the U and V signals in a colour receiver) and this overcomes quadrature distortion. A secondary advantage is found to be an inherently linear detection characteristic which cannot be obtained with an envelope detector.

The Exhibition

A complete review of the exhibits at IBC-70 would take up a not inconsiderable space. We must therefore confine ourselves to the new, the novel and the exhibits of most interest to the majority of readers.

Both the BBC and the ITA had stands at IBC-70. Members of the ITA's Engineering Information Service handled a large number of enquiries on ITV engineering and the stand relayed a special programme of colour television throughout the Convention. The BBC showed off their mobile colour demonstration unit which has toured Great Britain showing quality colour pictures to the general public. Both authorities also illustrated on their stands some of the engineering work taking place; from the proposed colour distortion correction unit developed by London Weekend Television's engineering subsidiary—Dynamic Technology Ltd.—to the automatic monitoring and control systems developed by the BBC for its u.h.f. transmitting stations.

New Colour Cameras

Two completely new colour cameras were shown for the first time at the Convention. The one to attract most attention was the Marconi Mark VIII camera channel. The Mark VIII is a three-tube camera as is the new EMI camera channel type 2005. So after years of arguments between the supporters of the three-tube and those of the four-tube colour camera all the suppliers to the British market—EMI, Pye and Marconi—are now producing three-tube cameras.

The Marconi Mark VIII is described as "the world's first automatic colour television camera". And automatic it is—at least in the engineering sense—with a unique sequential line-up system which starts with a push-button. A special line-up pattern is displayed and the camera sets up its channel gains to give similar outputs on red, green and blue, aligns the three electron guns in the Plumbicon tubes and then automatically registers one upon the other. With the dioscope pattern switched off the colour balance then sets itself up to give accurate white from the scene being transmitted.

Automation is taken a stage further by the use of an automatic test display allowing diagnostic checks to be made on the camera throughout the video channels and in the power supplies and scanning sections. The display is made on a monochrome picture monitor and the absence of a white patch in the display pattern indicates a fault in the appropriate section of the camera. The implications of time saving are enormous not only for the time saved in an operator lining up each channel manually

but by the fact that one unskilled operator can simultaneously start the line-up sequence on any number of cameras without assistance. There is also the extra ease afforded by the channel in outside broadcast use and the known repeatable quality of camera pictures.

The flexibility and size of the cable connecting the camera to the camera control unit has always been a problem because of the very large number of signals passed. Both Marconi and EMI use time-division multiplex to code signals together for cable passage and have been able to reduce the size of the camera cable to the same proportions as those used for monochrome cameras.

The EMI 2005 colour camera seemed not to attract the same engineering attention as the Marconi camera and this was perhaps reflected best in the announced EMI orders, the majority of which were for the existing EMI 2001, already established as a camera capable of giving superb colour pictures.

Videotape Recorders

One of the great difficulties over the years in the use of videotape recorders has been their relatively slow lock-up time—the time needed for the machine picture to lock to the local source of line and field sync pulses and sub-carrier in both frequency and phase. This is necessary if the machine is to produce pictures capable of being faded, superimposed or inlayed with others. This time delay has resulted in having to cue a VTR at least three seconds, normally more, before it is required. Ampex showed their latest videotape recorder—the AVR-1—which gives a lock-up in 200 milliseconds (1/5th second). This is more or less the time needed to come off the back-stop of a video fader so that the AVR-1 can be programme cued instantaneously. To achieve this remarkable lock-up Ampex have had to improve the speed of tape run-up, reduce the tension on the tape to prevent stretch and considerably speed up the electronic servos. The result is a space-age looking machine with an amount of logic circuitry that is quite frightening.

The only contender to Ampex in the British market is RCA. This year they showed their latest TR70-C machine with its improved colour performance over previous models. During the show it was announced that Westward Television had ordered two such machines for the start of their colour operations next April.

It has often been said by VTR engineers that the helical-scan machine will never achieve broadcast standard requirements. Those who support that view must have been sorely disappointed to see the International Video Corporation's IVC-900 machine which offers really superb colour performance at a price of about a fifth that of a quadruplex machine.

Whilst in the area of videotape recordings, the FAM system (see page 4, October, 1970, TELEVISION) was seen demonstrated by a German firm, Vitronic, in use on a Sony ½ in. videotape recorder. The colour pictures from this rather narrow-bandwidth machine were quite acceptable from a closed-circuit viewpoint. The video disc from Teldec (Telefunken-Decca) was again on show and it is hoped to examine this in more detail in an article in TELEVISION at a later date.

The Unusual

Probably the smallest IBC exhibit was a cassette audio recorder by Data-Vision. This single-track machine is fitted with synchronous drive and end-of-tape and broken-tape sensing. The smallest stand was that of Plymouth Polytechnic, but an enormous amount of interest was shown in its Television Engineering courses. The largest stand was the EMI one—they built a small studio on the floor of the exhibition hall. The most fascinating demonstration—shared between Thorn with their Q-File memory lighting system and Michael Cox Electronics with their three-level colour caption synthesisers—was the production of three coloured captions from a monochrome

—continued on page 133


ROGER BUNNEY



DESPITE the ever-expanding u.h.f. network in the UK there are still many areas that are unable to obtain a satisfactory colour service from all three networks. Consequently in parts of the country viewers will have to rely on the existing v.h.f. services for some years yet. Generally the Band III service is less favourably received over long distances than Band I and the amplifier described here may prove useful in such areas. The DXer will also find this amplifier of interest.

Circuit

The unit itself is a simple basic circuit covering Band III with a relatively flat response and having an average minimum gain of 12–14dB. The input signal is coupled to the emitter of the BF180 via C1, L1 serving as a static discharge path and as a bypass for any m.f. and h.f. radio breakthrough from any strong local transmissions. Emitter bias is via R1 and a ferrite bead is fitted at the signal end of the resistor. The use of this bead is optional. The base

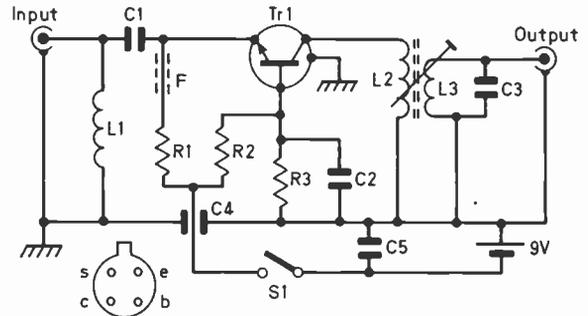

BF180 base viewed from underneath

Fig. 1: Circuit of the Band III preamplifier.

is biased by R2 and R3, decoupled to r.f. by C2.

The collector load L2 develops the appropriate signals across it, these being coupled to the output by the secondary tuned circuit L3, C3. The dust core on this coil former is a high-Q type available from Home Radio Ltd., Mitcham, listed in their catalogue under catalogue number Z82A, iron dust slug, high-Q (50-300 MHz). Circular tagrings to fit the coil former will facilitate construction.

Construction

The amplifier is mounted on a tin subchassis within an Eddystone diecast box, though any other metal container will suffice. Most of the com-

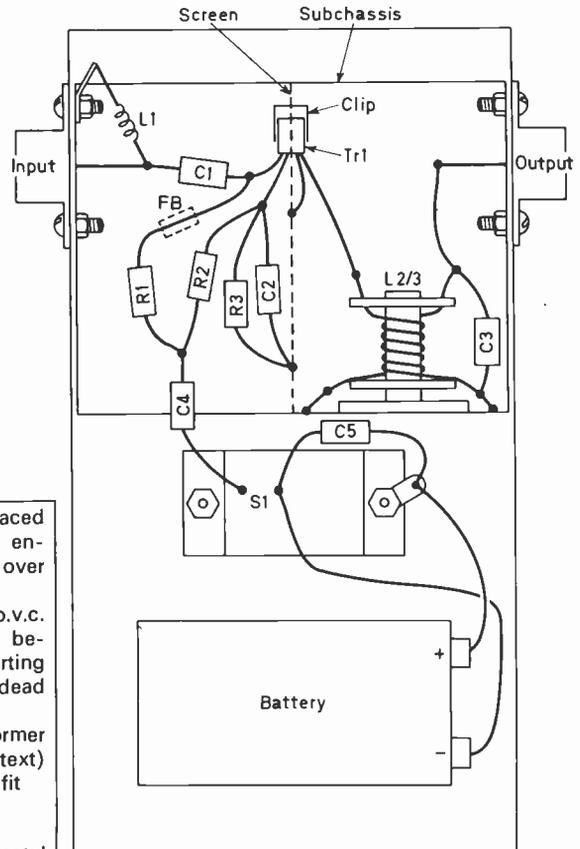


Fig. 2: Physical layout.

components list

Capacitors:			$\frac{1}{8}$ in. diameter close spaced	
C1	39pF	Silver mica 20%	L2	5 turns. 20 s.w.g. enamelled wire spaced over $\frac{1}{2}$ in.
C2	820pF	Silver mica 20%	L3	2 turns. 26 s.w.g. p.v.c. covered wire wound between L2 turns, starting one turn in from "dead end"
C3	10pF	Silver mica 5%		
C4	1,000pF	Feedthrough		
C5	820pF	Silver mica 20%		

Resistors:

R1	1k Ω
R2	3.3k Ω
R3	10k Ω
All 5% $\frac{1}{2}$ W	

Other components:


Tr1	BF180
L1	V.H.F. choke. 12 turns. Two coaxial sockets, metal 26 s.w.g. enamelled wire case, etc.
F	Ferrite bead
S1	S.P.S.T. slide switch

ponent wiring was completed on the subchassis which is secured in the case by the nuts and bolts holding the input and output sockets.

The transistor was the last component fitted on the subchassis before it was mounted in the case. As usual the normal precautions should be taken when soldering the transistor into circuit and all wiring should be kept to the minimum length possible. In the interests of stability the emitter and base circuits should be screened from the collector circuit and for this purpose the transistor is mounted on the chassis with a clip and a metal screen is inserted between the above mentioned connections.

The response of this amplifier is extremely broad and therefore the alignment is extremely simple. The receiver should be tuned to a mid-frequency in Band III and the dust core then adjusted to give maximum performance. It should be noticed that only a slight peaking effect occurs. Check the unit on other weak signals to ensure correct performance. The amplifier should be completely stable either loaded or unloaded at the input or output. If instability is found at any point over the band a slight adjustment to the dust core should overcome this.

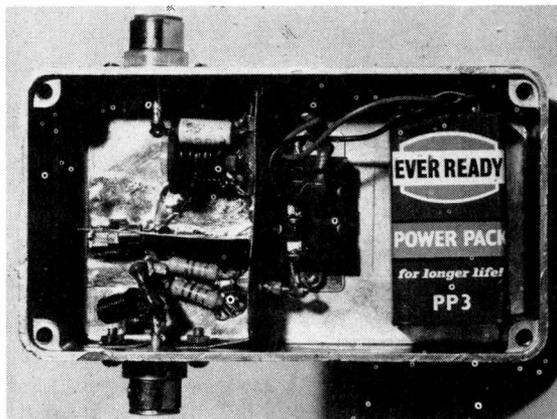The Mullard npn silicon transistor type BF180 has a quoted gain of 24dB at 200MHz and a typical noise figure of 4.5dB. With the wide bandwidth of



Inside view of the Band III preamplifier.

this amplifier the gain obviously drops but should be about 12-14dB. In practical terms the amplifier can lift a weak Cherbourg signal on channel F12 from weak traces of line sync pulses to a locked, noisy picture (212.85MHz).

The current consumption is approximately 2.5mA. Transistor voltages relative to the chassis (positive side of the supply) are as follows: collector 0V; base 7V; emitter 7.7V.

IC 'SCOPE PREAMPLIFIER

—continued from page 118

The frequency compensation components C8, R14 and the network on S3C, which are necessary to stabilise the operational amplifiers, inherently restrict the maximum bandwidth to about 1MHz. These reasonably priced operational amplifiers are normally incapable of giving significantly greater bandwidth.

Conclusion

We may conclude this feature by pausing a moment to consider why the vast majority of ordinary oscilloscopes provide maximum Y-input sensitivities of some 50 to 100mV/cm., occasionally as high as 20mV/cm., but seldom more. The detailed discussion of this preamplifier, which has been presented so as to illustrate the general principles involved, has shown that any attempts to boost deflection sensitivity to a value greater than 20mV/cm. must be accompanied by careful consideration of the bandwidth-impedance product.

There is a tendency for grass to grow on the timebase trace at higher deflection sensitivities unless bandwidth and/or impedance are restricted below the figures commonly found in general-purpose oscilloscopes. This means that the actual input ratings become ambiguous, depending on the type of signal source. A general-purpose oscilloscope is no longer feasible under these conditions because it would be producing an unnecessarily large amplitude of grass for many applications where much lower input impedances and smaller bandwidths would suffice with greatly superior signal-to-noise ratio.

Our approach to this problem has been to provide a logical selection of input/output combinations on our preamplifier. We make no claim to have taken the noise performance to its ultimate, indeed certain

sacrifices in noise performance have been deliberately made in favour of other outstanding advantages of using i.c. operational amplifiers. Practical circuits are readily realisable with very much greater deflection sensitivities if we drastically restrict both bandwidth and impedance.

For example, the basic thermal noise level in 200 Ω with a 20kHz bandwidth is about 0.6 μ V peak-peak. An optimum noise-matched amplifier input stage readily achieves a noise figure of 6dB so that the actual peak-peak equivalent input noise level would be some 1.2 μ V. If once again we choose to tolerate a maximum grass amplitude of 2mm. on the oscilloscope screen we could use this system for deflection sensitivities as high as 6 μ V/cm. This is nearly a hundred times greater than the maximum available deflection sensitivity with our preamplifier—but only for signal sources whose impedance is 200 Ω or less, which is such a serious restriction that it does not merit further consideration except for special requirements which individual readers may encounter. The maximum audio signal resolution of 50 μ V r.m.s. from source impedances up to 100k Ω provided with our general-purpose preamplifier is considered to be of more general appeal.

One final remark: if the noise source is truly white, which implies quite uniform spectral energy distribution throughout all frequency ranges of interest, the thermal noise voltage generated in a given impedance is independent of frequency. In other words the noise voltage is the same for a band from zero to 20kHz a.f. and for a bandwidth of 20kHz around any h.f. carrier. Practical circuits are not always strictly white noise sources throughout all the frequency bands up to and including u.h.f., but they may be treated as such to a first approximation. Thus we have to face an inevitable thermal noise level of about 5 μ V peak-peak in a 60 Ω television feeder line with 5MHz channel bandwidth.

DX-TV

CHARLES RAFAREL

As a result of our losing the December issue we have two months to report on this time. For most of September we have reports from Roger Bunney and Maurice Opie, since I was on holiday during this period. My September log covers only 1-4/9/70 and 29-30/9/70, and as expected the SpE activity was not very good:

- 1/9/70 Austria E2a, Pol/MT test card Poland or Hungary R1.
 - 2/9/70 USSR R1, Czechoslovakia R1.
 - 3/9/70 Czechoslovakia R1, Pol/MT test card Poland or Hungary R1.
 - 4/9/70 USSR R1, Pol/MT test card Poland or Hungary R1, Austria E2a.
 - 29/9/70 Pol/MT test card Poland or Hungary R1, Sweden E2.
 - 30/9/70 USSR R1.
- Roger Bunney reports as follows:
- 5/9/70 Czechoslovakia R1, Spain E3.
 - 6/9/70 USSR R1 and R2, Hungary R1.
 - 7/9/70 Sweden E2, Italy IB.
 - 8/9/70 East Germany E4, Italy IA and IB.
 - 10/9/70 USSR R1, Poland R1.
 - 11/9/70 West Germany E4.
 - 12/9/70 Italy IA.
 - 13/9/70 East Germany E4, Norway E2 and E4, Sweden E2, Italy IB.
 - 14/9/70 West Germany E4, Italy IB.
 - 15/9/70 Poland R1, Czechoslovakia R1.
 - 16/9/70 Italy IB.
 - 26/9/70 East Germany E4, Italy IB.
 - 27/9/70 Czechoslovakia R1, West Germany E4, Sweden E2.

His m.s. (meteor-shower reflection) experiments were rewarded with Austria E5 on the 12th, nice work!

Maurice Opie too managed some SpE:

- 8/9/70 Czechoslovakia R1, USSR R1 and R2, Austria E2a, and the old type "Telefunken" test card on R1 (this is a mystery).
- 9/9/70 Poland R1.
- 17/9/70 Spain E4.

You will recall that we published details recently of the possibilities of m.s. (meteor-shower reflection) in Band III as well as in Band I. This idea appealed to me but I must confess that after only limited success by R. Bunney and myself I felt that when we asked other DXers to cooperate I was not too hopeful that any startling reports would come in. I was a little too pessimistic however. It can be done and Dennis Boniface has done it in a big way. I quote from his letter:

"SpE and Trops are 'old hat' for me now, the thing with me is m.s. on Band III. On August 10 at

11.00 I switched on and the log speaks for itself: E5 Sweden test card at 12.40 and Denmark test card at 12.44. On the 11th I tried E6 and joy of joys E6 Denmark on test card at 12.14 then E6 Sweden on test card at 12.33. Back to E5 for the 12th August—E5 Sweden test card at 11.20 and E5 Denmark test card at 11.26. Sweden E5 was seen again at 12.15, 13.00, 13.04, 13.30 and 13.40. Then on August 13th E5 EBU test card at 09.55 ? location, E5 Sweden test card at 10.09, E5 Denmark test card at 10.09."

He goes on to say that having tried two different TV receivers he concluded that a narrow bandwidth set gave the better results—his old 3.5MHz Bush TV56 was better than a more modern 5.5MHz set, so now you know! His aerial was an 11-element array at 20ft. with a three-transistor preamplifier. R. Bunney suggests, quite correctly I feel, that Dennis might do even better if he canted his array upwards between 5° and 20°. This achievement is magnificent and we wish him every success with his future m.s. efforts.

Whilst on holiday I saw Gibraltar E6 on test card. It is test card G with no other lettering. The opening caption is "GBC" in white letters for Gibraltar Broadcasting Co. We went to Gibraltar for the day via the back door from Tangier as the Spanish frontier is of course closed. The 200kW transmitter is high on the Rock, on E6, and I can't help wondering if there is after all just a chance of reception here by m.s. after what has already been achieved.

Once back in France again I had the opportunity of taking a closer look at SECAM colour TV and after having seen a lot of PAL here I would say that the differences in the results of the two systems are only marginal. But SECAM sets really are very expensive. Having duly noted this we took the plunge on our return and got a Decca CS2520 25in. colour set. So watch out you CDXers, all I want now are some good Trop u.h.f. openings! I have had the u.h.f. Mendip Forest station in colour already at some 90 odd miles.

OCTOBER REPORT

During October the SpE activity declined to an even lower level than in previous months. This does not mean that there is no SpE DX about: it means that we must double our efforts, be even more patient than previously and above all be prepared to accept short-duration bursts of signals. This short-duration reception was very evident during October and a further point noticed is that the direction of reception has been East-West rather than North-South. Now for the log for the period 1-31/10/70:

- 1/10/70 USSR R1, Spain E2.
- 2/10/70 Spain E2.
- 3/10/70 Sweden E2.
- 4/10/70 Spain E2, Sweden E2.
- 5/10/70 Spain E2.
- 6/10/70 USSR R1, Poland R1.
- 7/10/70 USSR R1, Czechoslovakia R1, Poland R1.
- 8/10/70 USSR R1, Poland R1, Austria E2a.
- 9/10/70 USSR R1.
- 10/10/70 USSR R1, Czechoslovakia R1.
- 11/10/70 USSR R1.
- 12/10/70 Czechoslovakia R1, Austria E2a.
- 13/10/70 USSR R1, Czechoslovakia R1, Spain E2.
- 14/10/70 USSR R1, Poland R1.
- 15/10/70 USSR R1, Poland R1.
- 16/10/70 Czechoslovakia R1.

**Still waiting for spares Tom ?
You should have phoned 01-567 5400
01 567 2971**



Every time you need spares, don't be like Tom, contact the No.1 wholesaler to the service engineer. For quality, price & availability you must try....

'WILLOW VALE'

4 & 5 The Broadway, Cherington Road, Hanwell, London, W.7.
also at 42 West End, Street, Somerset. & Scotland

By Return Despatch

Valves, Tubes, LOPTs, Transistors,
Components, Scan Coils Etc.

LAWSON BRAND NEW TELEVISION TUBES



SPECIFICATION: The Lawson range of new television tubes are designed to give superb performance, coupled with maximum reliability and very long life. All tubes are the products of Britain's major C.R.T. manufacturers, and each tube is an exact replacement. Tubes are produced to the original specifications but incorporate the very latest design improvements such as: High Brightness Maximum Contrast Silver Activated Screens, Micro-Fine Aluminising, Precision Aligned Gun jiggling, together with Ultra Hard R.F. High Vacuum Techniques.

DIRECT REPLACEMENTS FOR MULLARD-MAZDA BRIMAR GEC, ETC.

A47-11W (P)	MW52/20 (M)	C21/AA (M)	CME2104 (M)	7504A (M)
A47-13W (T)	MW53/80 (M)	C21/AF (M)	CME2301 (M)	7601A (M)
A47-14W (M)	AW47-97 (M)	C21/KM (M)	CME2302 (M)	7701A (M)
A47-17W (P)	AW53-80 (M)	C21/SM (M)	CME2303 (M)	CRM121 (M)
A47-18W (P)	AW53-88 (M)	C23/7A (M)	CME2305 (P)	MW31-74 (M)
A59-11W (P)	AW53-89 (M)	C23/10A (M)	CME2306 (T)	A50-120W/R (P)
A59-12W (P)	AW59-90 (M)	C23/AK (M)	CME2308 (M)	
A59-13W (T)	AW59-91 (M)	C23/AKT (T)	CRM173 (M)	
A59-14W (T)	C17/1A (M)	CME1402 (M)	CRM212 (M)	
A59-15W (M)	C17/5A (M)	CME1702 (M)	CRM211 (M)	
A59-16W (T)	C17/7A (M)	CME1703 (M)	23SP4 (M)	
AW36-80 (M)	C17/AA (M)	CME1705 (M)	171K (M)	
AW43/80 (M)	C17/AF (M)	CME1706 (M)	172K (M)	
AW43-88 (M)	C17/FM (M)	CME1901 (M)	173K (M)	
AW43-89 (M)	C17/5M (M)	CME1902 (M)	212K (M)	
AW47-90 (M)	MW/53-80 (M)	CME1903 (M)	7205A (M)	
AW47-91 (M)	C19/10AP (T)	CME1905 (P)	7405A (M)	
MW43-69 (M)	C19/AK (M)	CME1906 (T)	7406A (M)	
MW43-64 (M)	C21/1A (M)	CME1908 (M)	7502A (M)	
MW43-80 (M)	C21/7A (M)	CME2101 (M)	7503A (M)	

REBUILT TUBES

LAWSON "RED LABEL" CRTs are particularly useful where cost is a vital factor, such as in older sets or rental use. Lawson "Red Label" CRTs are completely rebuilt from selected glass, are direct replacements and guaranteed for two years.

	Brand New Tubes	Red Label Rebuilt	Carr. Ins.
12-14" mono (M)	£4.10.0	£4.0.0	10/-
16-17" " "	£5.19.0	£4.12.6	12/6
19" " "	£6.19.0	£4.17.6	"
21" " "	£7.19.0	£6.10.0	15/-
23" " "	£9.10.0	£6.12.6	15/-
19" Panorama (P)	£8.10.0	"	15/-
23" Panorama (P)	£11.10.0	"	"
19" Twin Panel (T)	£9.17.6	"	"
23" Twin Panel (T)	£13.10.0	"	"
20" Panorama (P)	£10.15.0	"	"

LAWSON TUBES

18 CHURCHDOWN ROAD,
MALVERN, WORCS.
Malvern 2100

2 YEARS' GUARANTEE FULL TUBE FITTING INSTRUCTIONS

Tubes are despatched passenger train, road or goods taking far too long for customer satisfaction.

Learn at home... First Class Radio and TV Courses



After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how. **FREE GUIDE**

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.S.E. (Elec.). Guide also gives details of range of certificate courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable terms of

Satisfaction or refund of fee
Write now for your copy of this valuable publication. It may well prove to be the turning point in your career.

Founded 1885 Over 150,000 successes
CHAMBERS COLLEGE
(Incorp. National Inst. of Engineering)
(Dept. 844V) Aldermaston Court, Reading, RG7 4PF

NEW VALVES

Guaranteed and Tested
24 HOUR SERVICE

1B5 5/6	ECC81 8/6	PCF802 8/9
1B5 4/8	ECC82 4/-	PCF805 12/9
1T4 2/9	ECC83 4/9	PCF806 11/-
3B4 5/9	ECF80 5/9	PCL82 6/9
3V4 6/6	ECF82 5/9	PCL83 10/6
6/30L2 11/8	ECH35 6/6	PCL84 7/-
6AQ5 5/-	ECH81 5/9	PCL85 8/6
6F25 12/-	ECL80 7/-	PCL85 + 8/-
25L8GT 4/6	ECL82 6/8	PFL200 11/8
30C18 12/8	ECL86 7/6	PL86 9/8
30FL1 12/8	EP89 4/6	PL81 9/8
30L15 12/8	EP80 4/6	PL82 5/9
30P4 12/-	EP85 5/9	PL83 6/8
30P19 12/-	EP86 6/8	PL84 6/-
30PL1 12/3	EP89 4/9	PL800 12/9
30PL13 14/-	EP91 2/6	PL804 13/-
30PL14 13/6	EP183 5/6	PY32 10/-
35Z4GT 4/6	EP184 6/-	PY33 10/-
COH85 13/-	EH90 7/3	PY81 5/-
DAC32 6/9	EL33 9/8	PY82 5/-
DAF91 4/3	EL84 4/9	PY85 6/6
DAF96 7/-	EM34 13/9	PY800 7/-
DF33 7/6	EY51 7/-	PY801 7/-
DF91 2/9	EY86 6/8	R19 6/8
DF96 7/-	EZ80 4/8	U25 12/9
DK32 6/9	EZ81 4/8	U26 11/6
DK61 5/8	KT61 9/8	U191 12/-
DK92 6/8	KT66 18/6	U251 14/-
DK96 7/8	N78 17/-	U329 14/-
DL35 4/9	PC86 9/9	UABC80 6/8
DL92 5/9	PC88 9/9	UBF89 6/8
DL94 6/6	PC97 7/6	UCC85 7/8
DL96 7/8	PC90 7/-	UCH81 6/6
DY86 5/8	PC84 6/8	UCL89 6/9
DY87 5/8	PC89 9/8	UF89 6/8
EABC80 6/3	PC189 9/8	UL84 6/8
EB91 2/-	PCF80 5/11	UY41 7/-
EBC33 7/9	PCF86 9/-	UY85 5/8
EBF89 6/-	PCF801 6/6	Z77 8/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

NEW RANGE U.H.F. - TV - AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays: 7 element, 45/-; 11 element, 52/6; 14 element, 60/-; 18 element, 70/-; Wall Mounting with Cranked Arm: 7 element, 65/-; 11 element, 75/-; 14 element, 82/6; 18 element, 90/-; Chimney Mounting Arrays, Complete: 7 element, 80/-; 11 element, 87/6; 14 element, 95/-; 18 element, 105/-; Complete assembly instructions with every aerial. Low loss co-axial cable, 1/8 yd. King Teleboosters - Labgear U.H.F. Boosters from 75/-; Belling Lee 'Concord' all Band V.H.F./U.H.F. mains operated pre-amp., £7.10.0. State clearly channel number required on all orders. P.P.: Aerials, 8/-; accessories, 3/-; C.W.O. or C.O.D.

BBC - ITV - FM AERIALS



BBC (Band 1): Loft, 25/-; wall S/D, 32/6; 'H' array, 60/-; ITV (Band 3): 5 element loft array, 45/-; 7 element, 55/-; wall mounting, 5 element, 65/-; Combined BBC/ITV: Loft 1+5, 55/-; 1+7, 67/6; wall mounting 1+5, 77/6; chimney mounting 1+5, 90/-; Pre-amps from 75/-; Combined BBC/ITV/BBC2 Aerials: 1+5+9, 80/-; 1+5+14, 90/-; 1+7+14, 100/-; Available loft only.

FM Radio: Loft S/D, 19/6; 'H', 38/6; 3 element array, 57/6. Standard co-axial cable, 1/- yd. Co-ax plugs, 1/8. Outlet boxes, 6/-; Diplexer crossover boxes, 17/6. P.P.: Aerials, 8/-; accessories, 3/-; C.W.O. or C.O.D. (min. C.O.D charge 3/6). 1/- for fully illustrated lists.

CALLERS WELCOMED.
OPEN ALL DAY SATURDAY.

K.V.A. ELECTRONICS (Dept. P.T.)
40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

17/10/70 Poland R1.
 18/10/70 USSR R1.
 19/10/70 Czechoslovakia R1.
 20/10/70 Czechoslovakia R1.
 21/10/70 USSR R1.
 22/10/70 Czechoslovakia R1, Hungary R1, Austria E2a, Spain E2.
 23/10/70 Sweden E2.
 24/10/70 USSR R1, Austria E2a.
 25/10/70 Czechoslovakia R1.
 26/10/70 Poland R1, Spain E2.
 27/10/70 Austria E2a.
 28/10/70 Poland R1, Sweden E2.
 29/10/70 USSR R1.
 30/10/70 Czechoslovakia R1.
 31/10/70 Czechoslovakia R1.

I have been receiving bursts of the EBU bar on several occasions on Ch. R1 during the past month and have not as yet been able to identify its source. The only suggestion I can offer is that Bacau Rumania R1 has increased its power. This seems to be very much a shot in the dark, has anybody any other ideas?

The Tropes have been pretty poor with only a moderate opening to France on 17/10/70. There was however a big Trop opening on 20-26/9/70. Roger Bunney had eight new West German stations and Ian Beckett had "a whale of a time". In addition to W. Germany Rimberg Ch.39, Hohen Meissen Ch.53 and Lingen Ch.59 as new ones identified on caption he had France Sarrebourg? Ch.53 and Limoges? Ch.50 and it appears that Bands III and u.h.f. were wide open to W. and E. Germany during this period. The best effort however was by M. Bluck of Scarborough—brought to my notice by D. Boniface—who had Czechoslovakia Prague Ch.24 on test card on 18/6/70 and received their confirmation. His communication with Czechoslovakian TV brought the following list of u.h.f. stations: Prague Ch.24

70kW H; Bratislava Ch.27 15kW H; Ostrava Ch.31 14kW H; Brno Ch.35 25kW H. In view of this we may all have a chance given some good Trop conditions.

I am delighted to report further Meteor Shower success, further confirming its possibilities. We have received confirmation from an old DX friend Frank Smales of Pontefract, Yorks. His meteor-shower report for August 1970 is:

10/8/70 Poland R7 at 21.10 on caption.
 11/8/70 Sweden E6 at 10.15 on test card.
 Sweden E5 at 12.35 on test card.
 Poland R7 at 14.10 on test card.
 Denmark E5 at 18.52 on test pattern.
 12/8/70 Sweden E6 at 12.15 on test card.
 Poland R7 at 12.24 on test card.
 Denmark E6 at 19.27 on test card.

The receiver used was an American 23in. model converted to CCIR standards. He also has an excellent Trop log for the September opening. In Band III he had Austria E5 and Luxembourg E7. Amongst the multitude of u.h.f. stations he received (getting like Band III now!) he got Austria on Chs. 21, 22, 23 and 24 on 25/9/70. He thought at first these were W. Germany but as the signals improved he recognised the ORF test card and later the test pattern with the word "Oesterreicher" on it. He also had (reverting to Band III) East Germany Brocken E6, Marlow E8, Leipzig E9 and Schwerin E11 (very good).

These results should encourage us all. With the "new" meteor shower possibilities now proved and some good future Trop openings in Band III and u.h.f. the future does not seem so black after all, even during the winter SpE lull. I for one am embarking on a reorganisation. Since the arrival of the Decca colour TV set there has been a general rearrangement of sets and in future the DX ones will be on shorter coaxial leads which should help a lot.

IBC-70

—continued from page 127

camera. The biggest possible money-spinner was the Gates automated radio equipment, allowing virtually automatic programming and transmission of radio—a great possibility for commercial local radio stations.

Summary

If prizes were to be given we would have to award Ampex a gold medal for their development of the AVR-1 videotape recorder and another gold to D. A. Tilsley of Granada Television who in describing his company's new colour outside broadcast unit made what could have been a very boring description into a presentation to be remembered. With a slickness of slides, his Northern humour dominated all the delegates. Mr. Tilsley has what it takes to make a star comedian. A gold medal too to Marconi Communications Systems for their beautifully engineered one valve f.m. broadcast transmitter.

Silver medals should go firstly to Dr. Boris Townsend of Thames Television for his kindly good naturedness to all and sundry (including yours truly) during the week and his unique blandishment when he was either chairman or one of the rapporteurs at the technical sessions, and secondly to the poor girl who danced herself to a perspired globule day after day in front of the new Marconi colour camera.


Some of the booby prizes must go to those technical papers which had no place at IBC-70 either because of their complete lack of technical content or because they were rehashes of papers already published by the same authors or because they were nominally presented by

persons *under whom* the work was undertaken and not *by whom*. Fortunately these papers were few in number. Although we have congratulated Ampex on the AVR-1 we must also criticise them on their closed-circuit stand where the colour-capable helical-scan VTRs they were to demonstrate were non-operational for a good portion of the week.

IBC must be the success it is for a variety of reasons. By no means unimportant is the opportunity it gives for a relatively small network of people to meet again and to meet new faces. The exhibition is undoubtedly important—not so much in terms of direct sales for the exhibiting companies but as an enlightening opportunity for making comparisons, for having arguments which one might not care to start on ones own premises, and for meeting the designers rather than just the salesmen.

Most of all though IBC-70 was the time for broadcasting engineers to assess the results of PAL colour and its major introduction into transmission. Certainly a large proportion of the US engineers who attended must have gone home wondering whether it was too late for them to change to PAL. It was a great pity therefore that some of the exhibitors did not wave the flag both for PAL and themselves by having their colour monitors set up properly. Only one Bloclight (BBC/Fisher Bloclight for setting up Illuminant D and grey scale) was seen in use and that was on the BBC stand.

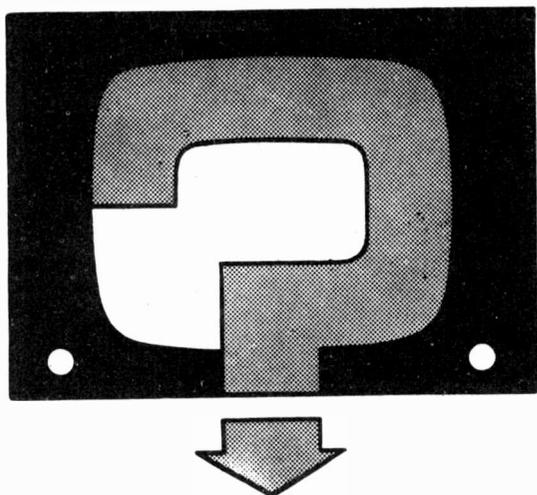IBC-70 was a resounding success for all. If the odd *faux pas* has been noted by the organising sponsors the Fourth Convention in 1972 should be even better. But it will be difficult over two years to remember the name that goes with the face and who owes who that drink!



YOUR PROBLEMS SOLVED

★ Requests for advice in dealing with servicing problems must be accompanied by a 2s. postal order (made out to IPC Magazines Ltd.) the query coupon from page 138 and a stamped, addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets or answer queries over the telephone.

MASTERADIO 4018

There was picture rolling and the vertical hold control could not be adjusted to cure this. R102 in series with the hold control was increased in value and this temporarily corrected the fault. The fault occurred again, so the PCL85 was replaced and R102 further increased to 1M Ω . The trouble now is that there is a series of white lines across the top of the picture, which is also $\frac{1}{2}$ in. short at the bottom. These faults occur on 405, 625 line operation being perfect.—G. Wainwright (Dorchester).

First check the 0.05 μ F capacitor C156 in the field sync feed circuit. Then check C147 (field charging capacitor) and the two capacitors C150 and C148 to the grid of the triode section of the field timebase valve. If necessary replace C151 and C155 (both 0.01 μ F) in the field linearity feedback circuit and check P8 the field linearity control.

BUSH TV148U

The trouble is buzz of varying intensity on BBC-2, depending on picture content. This buzz is worse when the picture is darkened by adjusting the contrast control. It is only when the contrast control setting is reduced to an unacceptable level that the buzzing stops. The detector balance control has been carefully adjusted and the coils tuned. The picture itself is very good and the correct aerial is installed.—E. N. Paynter (St. Austell).

No amount of detector balance control adjustment will tune out the buzz if the OA79 detector diodes are not matched. So check the back-to-front resistance of these (2MR2 and 2MR3) and replace as necessary. Also check the 5 μ F capacitor 2C46.

FERGUSON 3602

The PL36, U193, PCL85 and ECC82 valves have been replaced, also the width control and boost reservoir capacitor, but still there is insufficient width—it is about $\frac{1}{2}$ in. short at each side. Do you think the width stabilising varistor is at fault?—N. Ratcliffe (Birmingham).

The varistor Z1 is not likely to be at fault but the high-value resistors in the width circuit are inclined to change value. Check R100 1.8M Ω and R101 2.2M Ω .

DECCA DM45

When the gain is set at minimum a full field can be held but the picture is washy. When the gain is increased by moving the aerial or adjusting the sensitivity control the field blinks rapidly, alternating from a full field to a thin white horizontal line about twice a second. There is at the same time a loud synchronous clicking. The PL84 field output valve has been replaced.—F. McLaughlin (Devonport).

In Decca receivers of this vintage a novel control called the interlace control was fitted. On the DM45 it is situated immediately below the mains tag panel. The setting of this control is often overlooked and leads to hours of wasted time. To set it, rotate fully anti-clockwise then rotate the field hold control to the fully anti-clockwise position. Lock the field with the interlace control, if necessary slightly adjusting the hold control. Then adjust both controls for good interlace over the complete range of locked field and so that there is no field folding at the bottom of the picture.

COSSOR CT1700U

There is reduced picture size all round with this 17in. receiver and the sound is very soft and distorted.—A. G. Chambers (Gt. Yarmouth).

First check the h.t. voltage. If low check both PY82 rectifiers and the a.c. input to pin 9 at both bases. If the h.t. is not low check the PL81 and PY81 valves and the value of the focus control (2M Ω), and also the value of the 2.7M Ω triode audio amplifier anode load resistor (to pin 1) which on these models is fed from the boost rail.

MURPHY V149U

The trouble is field slip. This is very bad on 625, and the field slips once or twice an evening on 405. The signal strength is as good on each system and I have fitted a new PCL85 and PFL200.—L. R. Harris (Portsmouth).

Your problem could be due to aerial trouble or a faulty sync diode block 3MR1-2-3 to the right of the system switch on the timebase unit.

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1R5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 18/6. DAF96, DF96, DK96, DL96, 4 for 29/-.

1A9GT 7/6	25U4GT11/6	DL94 6/9	EM34 14/6	PCL85 9/-	UBF80 5/9
1B6GT 7/3	30C1 6/8	DL96 7/3	EM80 8/3	PCL86 8/3	UBF89 6/9
1N5GT 7/9	30C15 13/-	DL98 5/9	EM81 8/3	PCL88 14/6	UCC84 7/-
1R5 5/9	30C17 16/-	DY87 5/9	EM84 6/9	PCL80015/6	UCC85 7/3
1R5 4/3	30C18 13/6	EABC80 6/6	EM87 7/6	PENA4 8/6	UCF80 7/3
1T4 2/9	30F5 15/9	EAF42 10/-	EY61 7/3	PFL20011/9	UCH42 12/6
384 5/9	30FL1 12/9	EB91 2/3	EY86 6/6	PL36 9/9	UCH81 6/6
3V4 6/9	30FL12 14/6	EBC33 8/-	EZ40 8/-	PL81 9/3	UCL82 7/-
5Y9GT 6/9	30FL14 14/6	EBC41 10/6	EZ41 8/-	PL81A 10/3	UCL83 11/-
5Z4G 7/6	30L1 6/8	EBF80 6/9	EZ50 8/-	PL82 6/-	UF41 10/6
6/30L2 12/-	30L15 13/-	EBF89 6/3	EZ81 4/9	PL83 6/6	UF85 6/9
12A8H 45/-	30L17 15/6	ECC81 3/9	GZ32 8/9	PL84 6/6	UF89 6/9
6AL5 2/3	30P4 13/-	ECC82 4/9	GZ34 9/9	PL800 13/6	UL41 12/6
6AM6 2/9	30P12 13/9	ECC83 7/-	KT41 15/6	PL604 13/6	UL44 30/-
6AQ5 5/3	30P19 13/-	ECC85 5/9	KT81 9/9	PL508 23/6	UL84 7/-
6AT6 4/6	30P11 12/9	ECC89 12/-	KT86 16/9	PM84 7/6	UM80 5/6
6BA6 4/6	30PL13 14/6	ECP80 6/-	LN329 15/6	PX25 23/6	UM84 4/6
6BE6 4/9	30PL14 14/-	ECP82 6/-	N78 17/6	PY32 10/-	UY41 7/6
6BJ6 8/6	35L6GT 8/9	ECH35 6/-	P61 10/-	PY33 10/-	UY85 5/9
6CG6 4/9	35W4 4/6	ECH42 12/9	PABC80 7/-	PY81 5/3	VP48 15/6
6CD6G 22/-	35Z4GT 5/-	ECH81 5/9	PC86 10/3	PY82 5/3	W119 7/-
6F14 9/-	807 9/9	ECH83 8/3	PC88 10/3	PY83 5/9	Z77 4/6
6F23 14/3	6083 12/6	ECH84 7/6	PC89 8/6	PY88 8/9	
6F25 12/6	AC/VP2 15/6	ECL80 6/-	PC97 8/-	PY800 7/6	
6K7G 3/6	AZ31 9/6	ECL82 6/9	PC900 7/6	PY801 7/6	
6KR6 3/-	B349 13/-	ECL86 8/-	PCC84 6/6	R19 6/6	
6N7GT 4/3	B729 12/6	EF37A 6/6	PCC85 6/-	R20 12/-	
6V9G 3/3	CCH35 13/6	EF39 4/9	PCC88 9/-	SU2150A	
6V9GT 6/6	CL33 18/6	EF41 11/9	PCC89 9/6	U25 12/6	
6Y4 4/9	CR21 6/9	EF80 4/6	PCC189 9/9	U36 18/-	
6X5GT 5/9	DAC92 7/3	EF86 6/3	PC805 13/6	U47 13/6	
10F18 7/-	DAF91 4/3	EF86 6/3	PCF80 6/6	U49 12/-	
10F18 12/-	DAF96 7/3	EF89 5/3	PCF82 6/6	U78 4/9	
12AT7 3/9	DF33 7/9	EF91 2/9	PCF86 9/6	U191 12/6	
12AU7 4/9	DF91 2/9	EF183 5/9	PCF800 13/6	U193 8/6	
12AX7 4/9	DF96 7/3	EF184 6/6	PCF801 6/9	U251 14/6	
12K8GT 7/3	DH77 4/6	EH90 8/6	PCF802 9/-	U301 10/6	
19B9G617/6	DK32 7/6	EL33 9/9	PCF805 13/6	U329 14/6	
150B2 13/6	DK91 5/9	EL34 9/6	PCF806 11/3	U801 19/6	
20F2 13/6	DK92 8/6	EL41 11/-	PCF808 14/6	UABC80 6/6	
20P3 11/9	DK96 7/3	KL84 4/9	PCL82 7/3	UAF42 10/3	
20P4 12/6	DL35 5/-	EL90 5/3	PCL83 10/9	UBC41 10/6	
25L6GT 5/-	DL92 5/9	EL600 12/6	PCL84 7/6		

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

NEW TELEVISION TUBES

FULLY GUARANTEED

TRADE LIST

17".....	£5.10.0	19".....	£ 5.17.0
20".....	£9.15.0	21".....	£ 7. 0.0
23".....	£8.10.0	24".....	£13.10.0
19" Twin Panel	£9.15.0	23" Twin Panel	£13. 5.0
19" Rimguard	£8.10.0	23" Rimguard	£11.10.0

PLUS New Colour Tubes at LOW Prices.

Send for full lists. Full Range of High Quality Low Cost Rebuilds available from £4.0.0.

Carriage 12/6 per Tube.

VACUONICS LIMITED

Newtown St., Cradley Heath, Warley, Worcs.
Telephone: Cradley Heath 69138

“NO



I'D RATHER HAVE A MINITEST™

The SEI MINITEST has made a remarkable impact in the pocket-sized multi-range meter market, by making itself a firm favourite with discerning people in the industry. Let's look into the reasons why.

First, the appearance. Diminutive, neat, wipe-clean cyclocac case with shock and magnetic field proof steel liner. Controls are simple and easy to use.

Second, the range. The Minitest measures a.c. and d.c. voltages d.c. current and resistance over 20 ranges to a sensitivity of 20,000 and 2,000 ohms per volt d.c. and a.c. respectively. Third, high voltage probes. These extend the range to 25 or 30kV d.c. Little wonder the Minitest is preferred!



SALFORD ELECTRICAL INSTRUMENTS LTD
Peel Works, Barton Lane, Eccles, Manchester M30 0HL
Telephone 061-789 5081 Telex 667 711
A Member Company of GEC Electrical Components Ltd.

NEW LINE OUTPUT TRANSFORMERS

ALBA 655, 656, 717, 721 **75/-**, 890-895, 1090, 1135, 1195, 1235, 1395, 1435 **118/-**.
BAIRD. Prices on request. From model 600 quote part no. normally found on TX base plate.
BUSH TV53 to TUG69 **40/-**. TV91 to TV139 **95/-**. (From Model TV123 an alternative Square Tag Panel was fitted on Main Bobbin, please state if required.) TV141 to TV176 Rewind **90/-**.
COSSOR 904 to 957 Rewind **90/-**. CT1700U to CT2378A **118/-**.
DECCA DM1, DM3C, (90°) **78/-**, DM4C (70°) **78/-**, DR1, DR2, DR121 **90/-**.
DEFIANT 7P20 to 7609. Prices on request.
DYNATRON TV30, TV35 **55/6**, TV36, TV37, TV38, TV39, TV40, TV41, etc. **80/-**.
EKCO T231, T284, TC267, T283, T293, T311, T326, T327, T330 **55/6**, TMB272 **68/6**, T344, T344F, T345, TP347, T348, T348F, TC347, TC349, TC356, T368, T370, TC369, T371, T372, TP373, TC374, T377A, T393, T394, 433, 434, 435, 436, 437 all at **80/-**, 503, 504, 505, 506 **95/-**.
FERGUSON 306T, 308T **55/6** each, 406T, 408T, 416, 436, 438, 506, 508, 516, 518, 536, 546, 604, 606, 608, 616, 619, 636, 646, 648, 725, 726, 727, 3600, 3601, 3602, 3604, 3611, 3612, 3614, 3617, 3618, 3619, 3620, 3621, 3622, 3623, 3624, 3625, 3626, 3627, 3629 **80/-**. Jelly Pots, please state colour: red, black or white.
FERRANTI T1001, T1002, T1002/1, T1004, T1005 **55/-**, T1023, T1024, T1027, T1027F, TP1026, T1071, T1072, T1121, TC1122, TC1124, T1125, TC1126 **80/-**, 1154, 1155 **95/-**.
G.E.C. BT302, BT342 **62/6**, BT454DST-456DST, 2010, 2013, 2014, 2012, 2000DS, 2001DS, 2002DS **85/-**.
H.M.V. 1865, 1869 **55/6**, 1870, 1872, 1874, 1876, 1890, 1892, 1894, 1896 **80/-**.
KB OV30, NF70, NV40, PV40, QV10, QV30, RV10, RV20, RV30, PVP20 **90/-**. Featherlight **90/-**. Chassis No. VC1-VC2-VC3-VC4 **90/-**.
MASTERADIO 4013 DST, D500 DST, D507 DST **85/-**.
MARCONI VT153, VT155, VT156 **55/6**, VT157, VT159, VT161, VT163, VT165, VT170, 4611, 4800, 4801, 4803, 4615 **80/-**.
PAM 600S to 822F **80/-**.
PETO SCOTT. Prices on request.
PHILCO 1019, 1020, 2021 **82/6**, 1029, 1030, 1035, 1036, 1040, 1050, 1060 **82/6**.
PHILIPS 11TG190 to 24T301 **118/-**, 1768U to 2196U Rewind **95/-** (old unit required).
PILOT PT450, 452, 455, 650, PT651, P60A, P61 **80/-**.
PYE V200, V400, 200LB, 210, 220, 300F, 300S, 310, 210S, 410, 510, 530, 600, 620, 630, 700 A or D, 710 A or D, 830 A or D or LBA **80/-**, 11U Series, 11U-P/NO, AL21003, 21F to 61. Part Nos. must be given when ordering Pye LOPTS **80/-**.
REGENTONE 197-198, 298, TV402, TV401, TV501, TV502 **90/-**.
R.G.D. 626, 627, 628, 726, RV202, RV302 **90/-**.
SOBELL 1000DS, 1002DS, 1005DS, 1010DST, 1012, 1013, 1014, 1018, 1019, 1020, 1021, 1032, 1033, 1038, 1039 **85/-**.
STELLA T1011U to 2149A **118/-**.
ULTRA 1770, 2170, 1772, 1782, 2172, 1771, 2171, 1775, 2175, 1774, 2174, 1773, 2137, 1980c, 1984c, 100c, 200c, 2380, 2384, 1984, 1985, 1986, 1980, 1980a, 1780, 2180, 2181, 2183, 2182, 1871, 1783, 6600, 6625, 6626, 6628, 6632, 6642 Etc. **80/-**.
 We can rewind most LOPT **95/-**.

Post and Package 4/6. C.O.D. 6/- extra.

LINE OUTPUT TRANSFORMER INSERTS ONLY

BUSH TV92-TV93, TV94-TV95-TV96-TV97, TV98, TV100, TV101, TV103, TV104, TV105, TV106, TV108, TV109, TV110, TV113, TV115, TV115R, TV115c, 123, 125, 128, **55/-**. Complete with heater windings. TV75, TV85 **55/-**.
DECCA DR95, DR101, DR202, DR303, DR404, DR505, DR606 **55/-**.
EMERSON E700, E701, E704, E707, E709, E710, E711, Portarama **37/6**.
FERGUSON 204T, 205T, 206T, 214T, 235T, 236T, 244T, 245T, 246T **40/-**.
FERRANTI 14T2, 14TC, 14T3F, 14T4, 14T4F, 14T5, 14T6, 17K3, 17K3F, 17T3, 17T3F, 17K4F, 17K6, 17SK6, 17T4, 17T4F, 17T5, 17T6, 21K6, 21K6V **37/6**.
INVICTA T118, T119, T120 **50/-**.
KB PV40, MV100, OF100, PV100, NV40, NF70, OV30, QV10, QV30 **40/-** pair.
PETO SCOTT 1416, 1418, 1419, 1422, 1423, 1716, 1719, 1720, 1722, 1723, 1724, 1725 **29/6**.
PYE V4, VT7, CTM4, TCM7 **50/-**.
REGENTONE 10-4, 10-6, 1021, 17-18, 10-12 **35/-**, T176, TT7, 191, 192 **37/6**.
R.G.D. Deep 17, The 17, 590, 600, 606, 611, 710, 723 **35/-**.
 Guarantee. Post and Package 4/6. C.O.D. 6/- extra.

NEW REPLACEMENT L/OP/TX

MURPHY 118/- 4/6 P.P.
V310 TO 789

REPLACEMENT DROPPERS

Philips Type 30+125+2.85 **12/6 P.P. 1/-**.
 Ferguson, H.M.V., Marconi, Ultra 800 & 850 Series (Convertible) 37+31+97+26+168. **12/6 P.P. 1/-**.
 As above 850 Series (Dual Standard) 14+26+97+173 **12/6 each P.P. 1/-**.

HIGH VOLTAGE PULSE CERAMICS

10, 15, 22, 33, 68, 82, 100, 120, 140, 155, 180, 220, 250pf. **1/6 P.P. 6d.**

T.V. CANNED ELECTROLYTICS

64-100. 450v. **22/6 each P.P. 2/6**.
 100-200. 275v. **18/- each P.P. 2/6**.

T.V. CANNED ELECTROLYTICS

100-200. 350v. 22/6 each 2 P.P. 6.	150-100-100-100-150.
100-200-60.	320v. 39/9 each P.P. 2/6.
300v. 22/6 each P.P. 2/6.	200. 350v. 15/- each P.P. 2/6.
100-300-100-16.	200-200-100.
275v. 27/- each P.P. 2/6.	350v. 31/6 each P.P. 2/6.
100-400 275v. 19/- each P.P. 2/6.	300-300. 300v. 37/9 each P.P. 2/6.
100-400-16.	125+200+100+32-275v. 28/- .
275v. 26/- each P.P. 2/6.	400+400-350v. 44/3.

POWER RESISTOR SECTIONS

These wirewound sections enable you to build up any Mains Dropper to your requirements. A central 2BA hole is provided for mounting.

Ohms 7, 9, 10, 12, 14, 17.5, 20. All at -7A	3/10 each.
Ohms 22, 25, 28, 30, 33, 36. All at -7A	4/9 each.
Ohms 40, 47, 52, 56, 60, 63, 66, 75, 87, 100 at -3A	3/10 each.
Ohms 120, 140, 160, 180, 200, 220, 250, 270 at -3A	4/9 each.
Ohms 300, 350, 400, 470, 560, all at 12A	3/10 each.
Ohms 726 at -15A	4/9 each.
K Ohms, 1 K ohm at -1A	3/10 each.
K Ohms, 2 (-07A)	4/9 each.

Postage each section 6d.

WE CAN STILL SUPPLY PARTS FOR THE CONSTRUCTOR 625 RECEIVER. S.A.E. FOR REQUIREMENTS

CALLERS WELCOME. But to avoid disappointment please phone to check that the items you require are in stock. All new components inserts are guaranteed for three months from the date of invoice subject to the breakdown being due to faulty manufacture or materials. S.A.E. all enquiries.

Dept. "R" D. & B. TELEVISION (Wimbledon) LTD. **80 MERTON HIGH STREET, S.W.19**
01-540 3513 01-540 3955

BUSH TV139U

The picture flicks from a normal to a slightly fainter one, this occurring roughly every three minutes. The tube and video amplifier have been replaced.—G. H. Clapperton (Colchester).

The "set A.G.C. 405" control could be at fault and often is. In fact the setting of the preset controls can be very critical on these models, including the bottom left-hand 15V transistor voltage adjustment. We suggest you set the 405 preset contrast control and take voltage readings in the i.f. strip.

EKCO T344

The timebase valves and the c.r.t. have been replaced on this set, also R59, R66, R68 and C51. However when either the contrast or brilliance are increased the picture swells and then disappears, leaving a blank screen.—H. J. Bennett (Marlow).

Your symptoms could be due to inadequate e.h.t. rectifier heater voltage. This is often caused by a faulty 2V winding on the line output transformer. This can be readily rewound using a length of coaxial cable inner conductor.

GEC BT302

The picture suddenly lost all brilliance and is almost non-existent, being only dimly discernible in a dark room. The raster is otherwise quite normally bright but has flyback lines superimposed.—S. Newcombe (Lincoln).

The usual cause of a large loss of contrast on the picture together with superimposed flyback lines is the ageing of the video amplifier valve. This is V6, Z339. Also check the D77 interference limiter and 120k Ω resistor in the feed to the c.r.t. cathode.

BUSH TV148U

The width is inadequate although the height and sound are OK. Replacing the PL504 and PY800 had little effect, but reducing the brilliance control increases the width though unfortunately this introduces a circular area in the centre of the picture which is fainter than the rest.—R. A. Crawford (Ayr).

We feel that the problem is in the line set stabilising circuit. Check the 750k Ω feed resistor 3R24, the 680k Ω resistor 3R21 to the slider and the 1.8M Ω grid resistor 3R20. Also check the line set stabilisation control itself.

405-625 CONVERSION

I am about to convert a 17in. KB Royal Star receiver to 625-line operation and plan to use as a basis the "Constructor's 625-line Receiver" circuit along with a surplus transistorised i.f. strip and tuner unit. As I shall be using only seven valves plus the c.r.t. in the circuit, what will the value of the mains dropper R90, at present 130 Ω , need to be changed to?—J. N. Brown (Edinburgh).

The dropper resistor R90 in your Royal Star model will have to be increased to about 200 Ω —then check that the heater current on test is about 300mA.

BUSH TV77

The spacing between the lines of the raster varies continually, giving the effect of the picture stretching and shrinking all the time. I have changed the valves and most of the components in the field timebase without effecting a cure.—S. A. Blyth (Watford).

Check that the values of the smoothing resistors behind the voltage adjustment panel are correct—it is quite often that they are replaced with ones of incorrect value and if the value is too low the smoothing efficiency is reduced—it is poor smoothing that is causing your trouble. If the smoothing resistors are of the correct value, change the main smoothing capacitor block.

PYE V700D

The fault is that the picture creeps up from the bottom after about half an hour leaving a 2in. gap which cannot be opened out. The PCL85 field timebase valve and 200 μ F cathode decoupler have been replaced.—S. W. Naylor (Bridgewater).

Check the 100 μ F decoupler in the h.t. feed to the field timebase—this is part of the main smoothing block. Then check the 0.1 μ F capacitor coupling the triode blocking oscillator section (pin 1) of the valve to the pentode output section.

EKCO T344

The picture is difficult to keep steady. There is a pulsing to and fro movement accompanied by a sympathetic note as this occurs from the line output transformer. On increasing the contrast this stops and the picture steadies but goes negative, whilst on reducing the contrast again the picture is momentarily perfect but then resumes its pulsing.—A. L. Brown (Bolton).

Check the value of the 27k Ω stabilising resistor connected between the h.t. line and the cathode of the 30FL1 video amplifier valve. This resistor often changes value to give the symptoms you describe.

PHILCO 1021

There are about four to five white vertical columns consisting of diagonal lines about $\frac{1}{2}$ in. long in the centre of the screen. Sometimes these multiply to the left of the screen making this half much lighter than the other.—J. Brook (Wakefield).

The line output transformer is fixed in position on a grooved carriage, the contacts being made by bow-springs underneath. Check the contact of these springs and clean them. Then check the 1k Ω resistor across the line linearity coil. Check the scan coils plug and socket and all connections to the line output transformer.

RANK TV154

The field hold control setting is very critical and there is an annoying bounce at times. There is also sound-on-vision.—F. Samuels (Botley).

This set is fitted with the same chassis as the Bush TV161 series. For the field fault we suggest you change the interlace diode 3MR3 and check the associated components. For the sound-on-vision adjust the preset a.g.c. control 2RV1.

FERGUSON 406T

The scanning is satisfactory when first switched on but after about a quarter of an hour begins to slip at the top and bottom. The picture can be locked by adjusting the hold control but eventually the control is at the end of its range. Finally the picture is about 7-8in. high. The height and linearity controls work satisfactorily and the field timebase valves have been changed. Also the picture is of rather poor quality with what appears to be line smearing.—E. A. Trowse (Brighton).

The field timebase trouble is almost certainly caused by the field oscillator cross-coupling capacitor C101 (0.01 μ F) from pin 2 of the PCL84 to pin 1 of the PCL82 becoming leaky. Also check R112 (220k Ω) which is in series with the field hold control. The poor picture quality is probably due to a component defect in the video amplifier stage. Check the stabilising resistor R51 (47k Ω) connected between pins 9 and 7. All the components in this circuit however should be checked, including the 0.1 μ F coupler (C61) to the c.r.t.

McMICHAEL MP17

There is no sound or vision on BBC! or ITA on this 17in. portable model. All I get is white lines across the screen on switching on. The valves have been replaced.—I. Hannay (Woking).

A frequent cause of the trouble you describe with these receivers is the failure of the 10k Ω 1W resistor under the tuner unit (across the PCF80 valvebase)—the grid resistor of the triode oscillator section. The original colours, brown black and orange, will be found faded.

MARCONIPHONE 4619B

There is a 3in. black band at the bottom of the screen and the height control only makes the picture roll. As the top of the picture is good I've not checked the PCL85.—C. Lethbridge (Preston).

The PCL85 may well be the cause of the trouble and should be replaced. If this does not cure the fault check the 0.01 μ F capacitor C88 in the field linearity feedback loop.

BUSH TV161GU

The fault is hum on video, a dark bar going up or sometimes down the screen and distorting the picture. This is very pronounced on 625 and at the same time there is intermittent field judder and the hold control setting becomes critical. I have checked by substitution the PFL200 and PCL85, and the smoothing electrolytics.—S. Hale (Battersea).

We have always found that the smaller electrolytics associated with the PFL200 are at fault when this type of trouble is experienced. The 8 μ F screen decoupler 2C48 of the sync separator section should in particular be checked.

QUERIES COUPON

This coupon is available until February 12, 1970, and must accompany all Queries sent in accordance with the notice on page 134. Don't forget the 2/- postal order!

TELEVISION, JANUARY, 1971

TEST CASE**97**

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

? A Bush CTV25 colour set exhibited a gradual reduction in colour intensity with increasing temperature from switch-on. Tests in the colour-difference stages indicated that all was well here and that the fault must lie in the chroma parts of the circuit. Subsequent tests however proved that the chroma amplifier gain remained fairly steady during the condition of the symptom. A clue was provided by the saturation returning to normal after readjustment of the line lock control, but such readjustment was not necessary from the point of view of the line lock which remained solid at all times.

What was the most likely cause of this symptom and why could it be corrected by readjusting the line lock control even though this was not necessary for correct line synchronising? See next month's TELEVISION for the solution to this problem and for a further item in the Test Case series.

SOLUTION TO TEST CASE 96

Page 90 (November 1970)

Since there was no distortion on the 405-line sound trouble in the audio amplifier could be discounted. Moreover the accompanying effect of intercarrier buzz almost always indicates poor a.m. rejection in the f.m. detector, assuming that the intercarrier channel and the appropriate rejectors in the vision i.f. channel are in correct alignment.

The service technician should have concentrated a little longer on the f.m. detector, for apart from making sure that the diodes are in good condition a check should also have been made to establish the d.c. conditions. The set in question employs a small preset potentiometer for balancing the ratio detector (adjusted for the least a.m. breakthrough and intercarrier buzz) and it was subsequently discovered that the slider connection to the track was impaired.

TELEVISION CLASSIFIED ADVERTISEMENTS

The pre-paid rate for classified advertisements is 4/- per line (minimum order 12/-), box number 1/- extra. Semi-display setting £2 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to TELEVISION and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, TELEVISION IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4, for insertion in the next available issue.

EDUCATIONAL

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for *FREE prospectus and find out how ICS can help you in your career.*

ICS, DEPT. 560, INTERTEXT
HOUSE, STEWARTS ROAD,
LONDON S.W.8.

RADIO AND TV Exams and Courses by Britain's finest home study School, Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Certificate, etc. Free brochure from British National Radio School, Russel Street, Reading.

COLOUR TV SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV engineer technician, and approved by leading manufacturer. Full details from ICS (D.562), Intertext, House, London SW8, or 'phone 01-720-1983

R.T.E.B. Certs., City & Guilds, Colour TV, Radio, Computers, Radio Amateurs' Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—*FREE*. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 172K, Aldermaston Court, Reading RG7 4PF.

HUNDREDS OF top paid jobs in Engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful *FREE* book. B.I.E.T., Department 153K, Aldermaston Court, Reading RG7 4PF.

BECOME "Technically Qualified" in your spare time, guaranteed certificate and exam Home Study courses in Radio, TV, servicing and maintenance, R.T.E.B., City & Guilds, etc., highly informative *FREE* Guide.—Chambers College (Dept. 858K), Aldermaston Court, Reading, RG7 4PF.

FOR SALE

LARGE QUANTITIES of used TV spares for both modern and obsolete models. Lopts, Tuners if strips, scan coils, frame and sound transformers, etc., etc. S.a.e. for quotations, C.W.O. to TV Dismantlers, Foxhole Whitstone, Holsworthy, Devon.

FOR SALE

UHF 12 Element Aerial, 36/-, p & p Free. State Channels. Lawton, 1 Tower Square, Stoke, Staffs, ST5AA.

625/405 VHF/UHF IF Panels. B.R.C. 850 series. Ideal for components, IF transformers and switching, P/C Valve bases or repairs to this Thorn receiver. 35/- each plus 4/6 p.p. WILLOW VALE, 4 The Broadway, Hanwell, W.7.

TV CAMERA (closed circuit), N.E.V. Icon., complete with lens, etc. Brand new, cost £110, £30. Danbury 2011 (Essex).

BULK PURCHASE of ex-Rental TVs. 23" from £6/10/0, 19" and 21" from £4/0/0, 17" from £2/10/0. Others available for spares from £1. Tel. Nottingham 240403.

B.R.C. COLOUR chassis with Teak cabinet, only requires Tube, £100, 17 Ashfield Road, Norton, Bury St. Edmunds, Suffolk.

VALVES ex TV boxed, tested, from 1/-, 6d. postage: speakers from 7/6d., postage 2/-, Globe Electrics, 151a. Brighton Road, Surbiton, Surrey. 01-399-7333.

HEATHKIT 5" Oscilloscope, new, unused, built and tested, specification as published, £30. D. Harrod, "Almaur", 20 Butts Road, Horspath, Oxford, OX9 1RH.

MISCELLANEOUS

ENAMELLED COPPER WIRE
S.W.G. Per lb. reel Per 1 lb. reel
18-22 11/3d 16/6d
23-30 11/9d 17/6d
31-35 12/3d 18/6d
36-40 15/0d 24/2d
41-44 17/9d 29/6d
Orders despatched by return of post. Please add 1/2 per item P. & P.

Supplied by:
BANNER TRANSFORMERS
Brooks Street, Higher Hillgate
Stockport, Cheshire
TRADE ENQUIRIES INVITED

SERVICE SHEETS

SERVICE SHEETS

(1925-1970) for Radios, Televisions, Transistors, Radiograms, Car Radios, Tape Recorders, Record Players, etc.
By return post with

FREE FAULT FINDING GUIDE

PRICES FROM 1/-

Over 8,000 models available.
Catalogue 2/6.

Please send stamped addressed envelope with all orders and enquiries.

Hamilton Radio

54 London Road, Bexhill, Sussex

SERVICE SHEETS (continued)

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES

LIMITED

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From

Address

enclose remittance of

(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (November T)

RADIO, TELEVISION, over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Road, London, W.6. SHE 8441.

SERVICE SHEETS. Radio, TV, etc. 8,000 models. List 2/-, S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS with Free Fault Finding Chart, 4/6, S.A.E. Lesmar, 15 Conholt Rd., Andover, Hants. (Mail only).

WANTED

TOP PRICES PAID

for new valves, popular
TV & Radio Types

KENSINGTON SUPPLIES

(A), 367 Kensington Street
Bradford 8, Yorks

CASH PAID for New Valves. Payment by return, WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

WANTED (continued)

SERVICE SHEETS purchased, HAMILTON RADIO, 54 London Road, Bexhill.

WANTED. Service Sheet English Electric for 16T18F £1. Offered. S. FOSTER, 18 Lytton Road, Bournemouth, Hants.

WANTED. Bulk Purchase of scrap and redundant TVs. CASH ON COLLECTION. Immediate Clearance. G. A. Morley, T.V. Disposal Co., 61B Shakespeare Road, Telephone Bedford 61876.

NEWNES "Radio and T.V. Servicing" 1959-65 inclusive. State price/condition. LEAKE, 6 Triangle, Ilkeston, Derbys.

WANTED! New valves especially TV types. Cash waiting. Bearman, 6 Potters Road, New Barnet, Herts. Tel. 449/1934.

LADDERS

VARNISHED TIMBER LADDERS from manufacturer, **LOWEST PRICES** anywhere. 15½ ft. ext., £5 10s.; 17 ft. ext., £5 15s.; 20 ft. ext., £6 5s.; 21½ ft. ext., £7; 24½ ft. ext., £8 2s.; 29 ft. ext., £9 5s. 3½ ft. Triple ext., £11 2s. 6d.; 36 ft. Triple ext., £14 10s. Carr. 13/6. Free Lists. Also Aluminium Ext. & Loft Ladders. CALLERS WELCOME. Dept. PTT HOME SALES, Baldwin Road, Stourport, Worcs. Phone Stourport 2574.

AERIALS

BAKER AND BAINES
UHF Aerials BBC and ITV 625 Colour
10 ele 42/-, 14 ele 47/-, 18 ele 65/-, 22 ele 75/-, Double 22 ele 160/-.
BBC Aerials: Dipole 35/-, X 43/-, H 48/-.
ITA Aerials: 5 ele 39/-, 8 ele 54/-, 11 ele 66/-, double 5 array 98/-.
Combination Aerials: Dipole plus 5 54/-, H plus 5 82/-, X plus 5 90/-. Special Loft Dipole plus 5 42/-.
Diplexers — Triplexers — Matched Diplexers UHF — VHF.
Poles, Lashings, Clamps, Couplers, etc. Co-Ax 1/3 and 2/3.
Postage paid inland on Aerials only. Please state channels when ordering. SAE for full lists.

11 Dale Cres., Tupton, Chesterfield

AERIALS

UHF: Set Tops 42/-. Outside: 9 ele 25/-, 10 ele 38/-, 11 ele 50/-, 12 ele 51/-, 18 ele 65/-, 20 ele 70/-. Multibeam 46 and Supremes 110/-.

All aerials supplied with clamps.

ANTIGHOST: Troubleshooters/Log-beams 100/-.

FM/VHF: H 45/-, 3 ele 65/-, 4 ele 75/-, Stereo 6 ele 120/-.

Motorized Units: Semi Auto £20, Auto £20.

All Aerials by either, "AERIALITE", J BEAM, ANTIFERANCE, PREMIER, MAXVIEW.

ACCESSORIES: Sockets, Plugs, Dips, Splitters, Masts, Lashings, etc., etc.

EAGLE PRODUCTS:

All that's best in Electronics: Head-phones, Amps, Speakers, Meters, etc. Send 5/- for Catalogue.

COAXIALE: Standard 100 Mtrs 90/-, Low Loss 140/-, or per Mtr.

State channels for all TV Aerials/Amps. FM state wide band or channelized. TERMS: CWO, COD, P & P 6/6. Send 6d. stamps for lists. Callers Welcome.

JEFFRIES SERVICES

31 Hambrook St., Portsmouth, Tel. 28354

BELLING-LEE TV Aerials. Band I, III, Combined Band I & III types. Less than half price. Aluminium rod, tubing, insulators, clamps, etc. Price List. Cook, 90 Ewhurst Road, Crawley (23885), Sussex.

AERIALS

AERIAL KITS. Coaxial Cable—VHF 1/- and UHF 2/- per yard. CO-AX Plugs, 1/3d. UHF Aerials for BBC2, ITA and Colour—10 Element, 32/-; 14 Element, 37/-, 18 Element with support boom, 45/- . All aerials have four reflectors and tilt and roll brackets for up to 2" masts. Double 18 with support cradle, junction box and bracket. 110/- . All aerials post paid mainland. Please state channel required when ordering. Every type of lashing kit, wall or chimney bracket, clamp, etc., available. We can also supply a wide range of VHF/UHF Diplexers, Triplexers, Co-Ax outlet boxes, crossover switched boxes, coupling units, poles and other aerial accessories. Postage extra on Co-Ax and accessories. S.a.e. for illustrated list and prices.

TRADE ENQUIRIES INVITED.

48 ESSEX ROAD,
MALDON, ESSEX

SETS & COMPONENTS

WITWORTH TRANSFORMERS LTD.

Dept. P.T., 26 All Saints Road,
North Kensington, W11. 1HQ
Telephone: 01-229 9071. 9 a.m. till 5 p.m.

TELEVISION LINE OUTPUT TRANSFORMERS

PRACTICALLY ANY MAKE OR MODEL SUPPLIED OR REWOUND

EKCO, FERRANTI, DYNATRON
Replacement cases £1-0-0d. each, please state model.

S.A.E. for return of post quotation. TERMS: Cash with order or C.O.D., please add 4s. for postage.

C.O.D. orders will be charged 6s. Transformers fully guaranteed. (98)

R & R RADIO

51 Burnley Road, Rawtenstall
Rossendale, Lancs.
Tel.: Rossendale 3152

VALVES BOXED, TESTED & GUARANTEED

EF80	3/-	PCC84	3/-	PY82	3/-
EBF89	3/6	PCF80	3/6	UI91	4/6
ECC82	3/6	PCF82	3/6	30F5	2/6
ECL80	3/6	PCL82	4/-	30L15	5/-
EF80	1/6	PCL83	4/-	30P12	4/6
EF85	3/6	PL36	5/-	30C15	5/-
EY86	4/6	PL83	4/-		
EZ40	4/6	PY33	5/-		
EBC41	4/6	PY81	3/6		

POST: ONE VALVE 9d. TWO TO SIX 6d. OVER SIX POST PAID.

VALVES, VALVES, VALVES

Any ten of your choice 14/6., post 1/-, 100 £5 10s. 0d., post paid.

EF85, EF80, EB91, EBF89, ECL80, EF183, EY86, PCF80, PCC84, PL36, PY81, PCL82, PCL83, PCC89, PY33, PY82, PY800, PY801, PY88, PCL84, 30F5, 6BW7, PY801.

BOB'S,

2 St. James Street, Rawtenstall
Rossendale, Lancs.
Mail order ONLY.

SETS & COMPONENTS

(continued)

TELEVISION TUBE SHOP

BRAND NEW TUBES AT REDUCED PRICES

A28-14W	£11. 0.0
A31-18W	£12.10.0
A47-11W	£9.19.6
A47-13W	£11.15.0
A47-14W	£7.12.6
A47-26W	£10.15.0
A50-120WR	£12.10.0
A59-11W	£12.19.6
A59-13W	£15.10.0
A59-15W	£9.19.6
A59-16W	£14.15.0
A59-23W	£14.15.0
A61-120WR	£15.10.0
AW21-11	£10.10.0
AW36-20, 21	£5.12.6
AW36-80	£5. 7.6
AW43-80	£6.17.6
AW43-88, 43-89	£6.12.6
AW47-90, 91	£7.10.0
AW53-80	£8.17.6
AW53-88, 53-89	£8. 5.0
AW59-90, 59-91	£9.10.0
C17LM, PM, SM	£6.12.6
CME1201	£12.10.0
CME1101	£11.19.6
CME1601	£10. 5.0
CME1602	£12. 0.0
CME1702, 1703	£6.12.6
CME1705	£7.12.6
CME1901, 1903	£7.10.0
CME2013	£12.10.0
CME2101, 2104	£8. 5.0
CME2301, 2302	£8.15.0
CME2306	£15.10.0
CME 2413	£15.10.0
CRM93	£5.10.0
CRM124	£5.10.0
CRM141, 2, 3, 4	£5.12.6
CRM171, 2, 3	£6. 7.6
CRM211, 212	£8.17.6
MW36-24, 44	£5. 2.6
MW43-64, 69	£6. 7.6
MW43-80	£6.17.6
MW53-20	£8.17.6
MW53-80	£8.17.6
7405A	£6.12.6
TSD217, 282	£14. 0.0

All tubes tested before despatch and guaranteed for 12 months.

Fully rebuilt tubes available—prices on request.

CARRIAGE & INSURANCE 15/-

COLOUR TUBES

(Carriage & Insurance 40/-)

A49-11X, A49-191X	£66. 0.0
A56-120X	£72. 0.0
A63-11X	£77. 0.0

TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD
LONDON, S.W.11. BAT 6859

WE GIVE GREEN SHIELD STAMPS

COLOUR TELEVISION

tubes by Mullard, R.C.A., and Mazda some at half price, i.e. R.C.A. 21" with scan coil and convergence unit, £45/0/0. Time-base units, £12/0/0, etc. Write stating wants to

RADIO SALES,

11a Roe Green Lane,
Hatfield, Herts.

SPARES

available from second-hand TVs. Transformers, Valves, etc. S.A.E. over enquiries. Complete 19-in. TVs, untested, from £5 plus 30/- carriage.

LINAVAL RADIO LTD.,

48 Hoe St., London, E.17.
01-520-7546.

COLOUR TV COMPONENTS. All parts for Home Constructed Colour Receivers. S.A.E. to FORGESTONE COMPONENTS, Ketteringham, Wymondham, Norfolk.

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous +20 watt, 15/- Post Free. **WHITSAM ELECTRICAL**, 33 Drayton Green Road, West Ealing, London, W.13.

COLOUR TV MONITOR P.C. Panels, ex-production, would make ideal basis for Professional Quality Colour Receiver. Panels supplied in groups with diagrams. R.G.B. Video Chain, 5 P.C.'s at £5 plus 4/6 post. Timebase Panels include Line osc/drive, Field T.B., Sync., etc., at £5 plus 4/6 post. Also Convergence Units and Mains TX's. Details, FORGESTONE COMPONENTS, Ketteringham, Wymondham, Norfolk.

£5 TELEVISIONS £5

Delivered anywhere in Great Britain

17" 12 channel. Complete & tested. Excellent condition
Carriage and ins. \$1

17" Untested T.V.s 12 channel. 30/- Carriage £1. All makes

TUBES! TUBES!

Guaranteed 6 months

17" & 19" All makes..... 30/-
23"..... 50/-
19" Bonded..... 70/-
23" Bonded..... 90/-

Plus 10/- carriage

VALVES EX EQUIPMENT

Guaranteed 6 months

APR12 1/-	PCC84 1/6	PL36 4/6	688 1/-
EB91 3d.	PCF80 1/6	PL81 3/6	68W7 2/-
EBP89 2/6	PCC89 2/6	PY81 1/-	6U4 3/6
ECC82 2/6	PCL85 4/6	PY800 3/-	20D1 2/6
ECL80 1/-	PCL84 3/6	PY82 1/-	20P1 4/6
EF183 2/6	PCL82 3/6	PY33 4/6	20P3 2/-
EF184 2/6	PCF86 3/6	U191 3/6	20PL1 4/6
EY86 3/6	PCL83 2/6	6F23 3/6	30PI2 4/-
			30P5 2/3

On 2 valves or more 6d. postage & packing

UHF TUNERS TO SUIT MOST MODELS

i.e. FERGUSON 850 900 Chassis
K.B. G.E.C. etc. 50/- P. & P. 10/-

VHF TUNERS MOST MAKES

30/- delivered. (Discount for quantity)

Dept. T.S.

THORNBURY TRADE DISPOSALS

Thornbury Roundabout, Leeds Rd., Bradford. Tel. 66570

SOUTHERN VALVE COMPANY

NEW! (Mostly BVA Valves)

DY86/7	7/6	PCF80 (BVA)	8/-	PY800/1	7/-	30L15	14/6
DY802	9/-	PCF86	10/6	U25	12/6	30L17	14/6
EB91	3/-	PCF801/2	9/9	U26	11/6	30P12	12/6
ECC82	7/6	PCF805	10/-	U191	12/6	30PL1	12/6
ECL80	7/6	PCF808	12/6	U193	7/6	30P4MR	17/-
EF80	5/-	PCL82/4	7/6	U251	12/6	30P19	12/-
EF183/4	7/6	PCL83	10/6	6/30L2	11/6	30PL13	14/6
EH90	9/-	PCL85	9/-	6BW7	12/6	30PL14	14/6
EY51	7/-	PCL805	9/-	6CD6G	19/-		NOTE
EY86/7	7/6	PL36	10/6	6F23	13/6	BY127 (BY100)	
PC86/8	10/-	PL81	9/-	20L1	19/-	whm 33 ohm res	
PC97	8/-	PL84	10/-	20P4	15/-	10 watt is 3/11 !	
PCC84	6/9	PL500/4	13/-	30C15	12/-	Valve data books	
PCF80 (large)	6/6	PY81	7/-	30FL1/2	12/-	4/-	

POSTAGE 6d. per valve, £3 and over, post free.

44 Earls Court Road, London, W.8. (Mail order only)

T.V. SPARES

OIL FILLED MURPHY LOPT's U26 type. Model number not known. 25/- each plus 4/6 p.p.

PUSH BUTTON V.H.F. TUNERS—FERGUSON Piano key type. Less valves PC97 and PCC89. 50/- each plus 4/6 p.p.

BAIRD V.H.F. TUNERS. Uses PC97 and 30C18 valves. Fits 620 to 650 series models, complete with all coils, supplied less valves. 55/- each plus 4/6 p.p.

U.H.F. TUNERS. Few only, to clear. Supplied less slow motion drive and mounting brackets and valves PC86, PC88 type. 35/- each plus 4/6 p.p.

BRC 850 SERIES TIME BASE PANELS. Complete and unused in maker's unopened cartons. 45/- each plus 4/6 p.p.

FERGUSON/EKCO PLUG IN MAINS LEADS. Moulded two-pin connector type. 6 for 50/- plus 4/6 p.p.

G.E.C./SOBELL 196, 197, 1000, 1014, etc. Dual Standard 405/625 I.F. Panels, complete with switching for direct replacement in this popular Radio and Allied receiver. 90/- plus 4/6 p.p. Fits all 1000 and 2000 series.

LINE TIMEBASE PANELS for above series, complete and for direct replacement, 55/- plus 4/6 p.p.

TIMEBASE PANELS to fit Sobell 195, 282, 283, 284, 285, 286, 287, 288 (and DS models), McMichael MT762, 763, 765, P405. Complete and new for direct replacement, 55/- each plus 4/6 p.p.

V.H.F. ROTARY TUNER UNITS to fit McMichael, Sobell, G.E.C. 1000 series. New and unused. 55/- each plus 4/6 p.p.

MULLARD COLOUR SCAN COILS. Complete with plug in leads. 110/- each plus 4/6 p.p.

FERGUSON 800/850 series TIMEBASE PANELS, complete and unused in original packing. 45/- each plus 4/6 p.p.

Terms: Cash with order or C.O.D. 3/6 extra. S.A.E. all enquiries. Catalogue of valves, CRT's, LOPT's, components, etc., 2/6.

WILLOW VALE ELECTRONICS LTD.

4 & 5 The Broadway
Hanwell, London, W.7

Tel: 01-567 2971 and 5400

01-579 3582

Terms cash with order or C.O.D. 4/6 extra
S.A.E. all enquiries. Catalogue 2/6

TELEVISION SALES. 77-79 Victoria Road, Warminster, Wilts., Phone Warminster 8156. Valves, boxed, tested and guaranteed. PCF80, PCC84, PL81, PY81, EY86, EF80, 30F5, EB91, ECC82, PCL83, 30FL1, ECL80, PCL82, PY82, PCL84, 6-30-L2, you select 8 for 20/-, p. & p. 2/- S.A.E., other types, several CRT's cheap, tested, for callers only.

TOWERBY LTD

For Line Outputs and Deflector Coils

We have the Country's largest stock of Manufacturer's Original (or Authorised Replacement) Line Output Transformers for many "difficult" makes, including Ambassador, Baird, Cosor, Decca, Dynatron, Ekco, Ferguson, G.E.C., H.M.V., K.B., Masteraid, Peto-Scott, Philips, Regentone, RGD, Sobell, Ultra, etc. Also deflector coils output and oscillator transformers, inc. Alba, Bush, Murphy, Examples: L.O.P.T. Murphy 350/410/540/659/759, 147/-; Bush, TV80, TV95, TV96, 147/-; Cosor 950, 77/6; Ferguson 306/308, 79/6; Philips 1768U L.O.P.T. assembly, 135/-; Ultra 1984-200C, 101/3. Rewind most L.O.P.T., 90/-.

SPECIAL OFFER

Ekco improved type for Models T221, 231, 310, all at 45/-; Ferranti 1474 series inserts, 25/-; Philco 1019/1021, 52/6. Terms: C.V.V.O. or C.O.D. (3/6), post/packing 6/-; 2 or more L.O.P.T.s. post/packing free. All enquiries answered but regret no lists available. Same day delivery on most types.

TOWERBY LTD

MAIL ORDER DIVISION OF T.C.S. LTD.
70 STREATHAM HILL, LONDON, SW2
Tel: 01-674 2185.

GARRARD 1000 Mono, £6/15/0 + pp. 7/6. BSR/Phillips, Mono, £6/15/0 + pp. 7/6. BSR/Phillips Stereo, diamond, £8/10/10 + pp. 7/6. Record player cabinets, Phillips, £4/10/0 + pp. 7/6. Steel TV legs with fittings 19" or 23", 25/-, pp. 4/6. Pye 40F IF, panels damaged, complete, 15/-, pp. 2/- EHT EY/DY 86 valve base, 4/6 + pp. 1/- Ekco channel change knobs, 418 series, 4/6, pp. 1/- New C19/10AP Cathodean 19" twin panel tubes, £9/15/0, pp. 10/- 405 line output transformers, No. T748856, 50/-, pp. 3/- 23" clear implosion masks, 35/-, pp. 3/- Scanning coils No. 782742, 30/-, pp. 4/6. Pye 625 line chassis, complete less L.O.P.T. Hundreds of new components, £3/10/0, pp. 15/- UHF tuner units with geared drive unit, less valves, 50/-, pp. 4/6. TV cabinets, 19" and 23" in Pye assorted models, 50/-, pp. 10/- UHF integrated transistor 6 push button tuner with I.F. panel, £10, pp. 5/- To fit 40F chassis and constructor 625, as in PRACTICAL TV, March/October 1970. Transistor Ltd., 82 Junction Road, Edmonton, N.9.

EX N.E.V. C.C.T.V. Camera and Monitor Circuits, S.A.E. for list. LOWE, 29 Vanner Point, Hackney, London, E.9. 5AX.

TELEVISION SPARES. All makes and models, new and used. Send S.A.E. for your enquiries. Used Tested Valves 4/- each, postage 6d. Thriftys, Green Lane Farm, Green Lane, Chessington, Surrey.

SETS & COMPONENTS (continued)

AERIAL BOOSTERS 59/- EACH

We make four types of transistorized aerial pre-amplifiers. These take only seconds to install.

1. L45 625 TELEVISION (U.H.F.).
2. L12 405 TELEVISION (V.H.F.).
Please state channel numbers.
3. L11 V.H.F. F.M. RADIO.
4. L10 WIDEBAND RADIO.
This covers M/W and S/W to 20 MHz.

PRICE EACH
L45, L12 and L11 59/-; L10 39/-.

S.A.E. FOR DETAILS
MONEY BACK GUARANTEE

VELCO ELECTRONICS

62 Bridge Street, Ramsbottom, Bury, Lancs. Tel. 3036

VALVE BARGAINS

Any 1-2/-, 5-9/-, 10-14/-.

EB91, EBF89, ECC82, EY86, ECL80, EF80, EF85, EF183, EF184, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF800, PCL82, PC483, PCL84, PCL85, PL36, PL81, PL83, PY32, PY33, PY81, PY82, PY800, PY801, 30FL1, 30F5, 30L15, 30C15, 6F23, 6-30LZ.

TESTED, WITH 3 MONTH GUARANTEE VALVES
4/- EACH

BY100 TYPE RECTIFIERS with Surge-resistor on bracket, 2/6 each.

NEW BVA VALVES | Huge range by return postal service well known to the trade. Brief list of television types herewith, full list S.A.E. All types ex stock!

DY86/7	8/-	PCF86	12/3	PY82	7/-	20L1	19/6
EB91	5/-	PCF801/2	12/3	PY800/1	8/3	20P4	20/-
ECC82	8/6	PCF805	13/-	R19	13/-	30C15	13/9
ECL80	8/-	PCF808	13/6	U25	15/-	30C17	15/9
EF80	8/-	PCL82	10/3	U26	15/-	30F5	16/6
EF85	8/3	PCL83	12/3	U37	15/-	30FL1	12/9
EF183/4	11/3	PCL84	10/3	U191	14/6	30L15	15/3
EH90	10/3	PCL805/85	11/6	U193	8/3	30L17	14/6
EY51	7/6	PCL86	10/3	U251	17/3	30P12	15/6
EY86/7	7/9	PL36/8	12/9	U301	17/-	30PL1	12/9
PC86/8	10/3	PL81	11/6	U801	24/-	30P4MR	20/-
PC97	8/3	PL83	10/3	6/30L2	15/6	30P19	12/9
PC900	10/3	PL84	12/-	6AT6	9/9	30PL13	18/6
PC84	9/3	PL500	16/6	6BW7	13/9	20PL14	18/6
PCC89	12/3	PL504	17/-	6CD6G	28/-		
PCF80	10/3	PY81	8/3	6F23	15/6		

etc. Trade prices

POST FREE OVER £3—LATEST BY100/127 type and 33 ohm 10 watt res, 4/- !

Imported PCF80 6/6 ! Note. Ask for separate components lists.

LOOK! Nearly every type in stock now ! !

NEW TELEVISION TUBES!

TWO YEAR FULL REPLACEMENT GUARANTEE

SEE THE DIFFERENCE A NEW TUBE CAN MAKE TO YOUR VIEWING—LATEST SCREENING TECHNIQUES INCLUDING TINTED SCREENS ON MOST 19" and 23" TYPES

Large stocks by Cathodeon and other leading manufacturers so why buy ordinary rebuilds?
Colour 25" £45! -

Special offer! 19" rebuilds, 2 year guarantee £5 10s. 23" £7 10s.

12" £3 (not 110°) 20" Mullard. 14" to 16" (not 110°) £4 15s.

17" £5 17s. 6d. A50/120W £10 10s. 19" 1901 and 19AH £7 10s.

Other 19" mono tubes—all £6 17s. 6d. Carriage all 12s. All 21" mono tubes—£7 17s. 6d.,

23" mono tubes £9 10s. Carriage 15s.

RIMBANDS, 19" £8 10s.; 23" £11 10s.

TWIN PANELS, 19" £10 2s. 6d.; 23" £15. Carriage 20s.

Bulk enquiries welcomed, special terms

PAY BY GIRO. Our No. 34.361.4006.

PHILIP H. BEARMAN


(Suppliers to H.M. Govt. etc.)

6 POTTERS ROAD, NEW BARNET, HERTS.

Closed Thurs & Sat afternoons

TEL. 449/1934 & 1935
(Robophone)

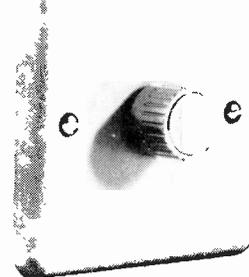Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescents at mains voltages from 200-250 V, 50 Hz. The DIMMASWITCH has built-in radio interference suppression. Price: £3. 4. 0d plus 1/6d post and packing Kit Form: £2. 14. 0d plus 1/6d post and packing Please send C.W.O. to:-

DEXTER & COMPANY

1 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH. Tel: 0244-25883.
As supplied to H.M. Government Departments,
Hospitals, Local Authorities, etc.

Write now for your

FREE CATALOGUE

containing

THOUSANDS OF COMPONENTS

ALL NEW QUALITY

COMPONENTS

From:

W.E.C. LIMITED (JTV)

74 THE STREET,
ASHTEAD, SURREY

Please mention

TELEVISION

when replying to

ADVERTISEMENTS

BI-PAK SEMICONDUCTORS

NEW LOW PRICED TESTED S.C.R.'s.

	1A	3A	7A	16A	30A
	(TO-5)	(TO-6)	(TO-48)	(TO-48)	(TO-48)
	case)	case)	case)	case)	case)
PIV each	each	each	each	each	each
50	4/6	5/-	9/6	10/6	25 20/-
100	5/-	6/6	10/6	12/6	50 23/-
200	7/-	7/6	11/6	15/-	100 28/-
400	8/6	9/6	13/6	18/6	200 32/-
600	10/6	11/6	15/6	25/-	400 35/-
800	12/6	14/-	18/-	30/-	800 80/-

PRINTED CIRCUITS EX-COMPUTOR

Packed with semiconductors and components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- p. & p.

TRANSISTOR EQUIVALENT BOOK

A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 6/- ea.

Sil. trans. suitable for P.E. Organ, Metal TO-18 Eqv't. ZTX 300 1/- each. Any Qty.

120VCB NIXIE DRIVER TRANSISTOR. Sim. BSN21 & C407. 2N1893. FULLY TESTED AND CODED NDI20. 1-24, 3/8 each. TO-5 NPN 25 up 3/- each.

MULLARD I.C. AMPLIFIERS

TAA243, Operational amplifier, 70/- each. TAA263, Linear AF amplifier, 18/6 each. TAA293, General purpose amplifier, 21/- each.

CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS

Audio Power Amplifier, 30/- each.

SIL. RECTS. TESTED

PIV	750mA	3A	10A	30A
50	1/-	2/9	4/3	9/6
100	1/3	3/3	4/6	15/-
200	1/9	4/-	4/9	20/-
300	2/3	4/6	6/6	22/-
400	2/6	5/6	7/6	25/-
500	3/-	6/-	8/6	30/-
600	3/6	6/9	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/3	12/6	50/-
1200	6/6	11/6	15/-	

TRIACS.

VBOM 2A	6A	10A
(TO-1)	(TO-66)	(TO-88)
100	14/-	15/-
200	17/6	20/-
400	20/-	25/-

2N3055 115 WATT SIL. POWER. NPN. OUR PRICE 12/6 EACH

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-18V 400mW (DO-7 Case) 2/6 ea. 1-5W (T op-Hat) 3/8 ea. 10W. (SO-10 Stud) 5/- ea. All fully tested 5% tol. and marked. Base voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS Code and Guaranteed. PAK No. EQVT T1 8 2G371A OC71 T2 8 2G374 OC75 T3 8 2G374A OC81D T4 8 2G381A OC81 T5 8 2G382T OC82 T6 8 2G344A OC44 T7 8 2G345A OC45 T8 8 2G378 OC78 T9 8 2G399A 2N1302 T10 8 2G417 AF117 All 10/- each pack

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and quality Satisfaction GUARANTEED in Every Pak, or money back.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	30 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	18 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV	10/-
U17	30 Germanium PNP AP Transistors TO-5 like ACY17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	25 Silicon NPN Transistors like BC108	10/-
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors 2G300 Ser. & OC71	10/-
U23	30 Mut's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-nin	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1-amp SCR's TO85 can up to 600 PIV CR51/25-600	20/-
U31	20 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mW DO7 case mixed Volts. 3-18	10/-
U33	15 Plastic case 1 amp Silicon Rectifiers IN4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28392/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY 50/51/52	10/-
U37	30 Bil. alloy trans. SO-2 PNP, OC200 2S322	10/-
U38	20 Fast Switching Sil. trans. NPN. 400 Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1308/5 TO-5	10/-
U40	10 Dual Trans. 6 lead TO-5 2N2060	10/-
U41	25 RF Germ. trans. TO-1 OC45 NKT2	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

AD161 NPN
AD162 PNP
MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS For mains driven output stages of Amplifiers and Radio receivers.
OUR LOWEST PRICE OF 12/6 PER PAIR.

UNIUNION
UT46, Eqv't. 2N2646
Eqvt. TIS43, BEN3000
5/6 EACH
25-99 5/- 100 UP 4/-

NPN SILICON PLANAR BC107/18/9 2/- each 50-99, 1/10, 100 up, 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

AF219 PNP GERM. Siemens VHF transistors. RF Mixer & osc. up to 900 MHz. Uses as replacement for AHT139-AF186 & 100's of other uses in VHF. Our special low price: 1-24 7/6 25-99 6/9 each, 100 + 6/- each.

CADMIUM CELLS
ORP 12 8/6
ORP60, ORP61 8/-

PHOTO TRANS
OC771 type 8/6

EX-EQUIPMENT MULLARD
AF117 transistors large can 4 lead type. Leads cut short but still usable, real value at 15 for 10/-.

FET'S
2N 3819 7/-
2N 3820 18/6
MPF 105 8/-

BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.

BI-PAK Order No.	SIM-TYPE. Description	Prices and qty. prices		
		1-24	25-99	100 up
BP00 7400N	Quad 2-Input NAND GATE	6/6	5/6	4/8
BP01 7401N	Quad 2-Input NAND Gate—OPEN COLLECTOR	6/6	5/6	4/8
BP04 7404N	HEX INVERTER	6/6	5/6	4/8
BP10 7410N	Triple 3-Input NAND GATE	6/6	5/6	4/8
BP20 7420N	Dual 4-Input NAND GATE	6/6	5/6	4/8
BP30 7430N	Single 8-Input NAND GATE	6/6	5/6	4/8
BP40 7440N	Dual 4-Input BUFFER GATE	6/6	5/6	4/8
BP41 7441AN	BCD to decimal decoder and NIT Driver	22/8	20/-	17/8
BP42 7442N	BCD to decimal decode (TTL 9/1)	22/8	20/-	17/8
BP50 7450N	Dual 2-Input AND/OR/NOT GATE—expandable	6/6	5/6	4/8
BP53 7453N	Single 8-Input AND/OR/NOT GATE—expandable	6/6	5/6	4/8
BP60 7460N	Dual 4-Input—expandable	6/6	5/6	4/8
BP70 7470N	Single JK Flip-flop—edge triggered	9/-	8/-	7/-
BP72 7472N	Single Master Slave JK Flip-flop	9/-	8/-	7/-
BP73 7473N	Dual Master Slave JK Flip-flop	10/-	9/-	8/8
BP74 7474N	Dual D Flip-flop	10/-	9/-	8/8
BP75 7475N	Quad Bistable Latch	11/-	10/-	9/8
BP76 7476N	Dual Master Slave Flip-flop with pre-set and clear	11/-	10/-	9/8
BP83 7483N	Four Bit Binary Adder	28/-	22/6	20/-
BP90 7490N	BCD Decade Counter	22/6	20/-	17/8
BP92 7492N	Divide by 12 4 Bit binary counter	22/6	20/-	17/8
BP93 7493N	Divide by 16 4 Bit binary counter	22/6	20/-	17/8
BP94 7494N	Dual Entry 4 Bit Shift Register	22/6	20/-	17/8
BP95 7495N	4 Bit Up-Down Shift Register	22/6	20/-	17/8
BP96 7496N	5 Bit Shift Register	24/-	21/-	18/8

Data is available for the above Series of Integrated circuits in booklet form, price 2/6

BRAND NEW FULL TO MANUFACTURERS' SPECIFICATION

BP709 Operational Amplifier, dual-in-line 14 pin package—age—SN7209 and similar to MIC709 and ZLD709C 10/8 9/- 8/-
This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rugged specifications. Ideal for learning about I.C.'s and experimental work, on testing some will be found perfect.

PAK No.	PAK No.	PAK No.
UIC00 = 5 x 7400N . 10/-	UIC42 = 5 x 7442N . 10/-	UIC80 = 5 x 7480N . 10/-
UIC01 = 5 x 7401N . 10/-	UIC50 = 5 x 7450N . 10/-	UIC82 = 5 x 7482N . 10/-
UIC02 = 5 x 7402N . 10/-	UIC51 = 5 x 7451N . 10/-	UIC83 = 5 x 7483N . 10/-
UIC03 = 5 x 7403N . 10/-	UIC60 = 5 x 7460N . 10/-	UIC85 = 5 x 7485N . 10/-
UIC04 = 5 x 7404N . 10/-	UIC70 = 5 x 7470N . 10/-	UIC90 = 5 x 7490N . 10/-
UIC05 = 5 x 7405N . 10/-	UIC72 = 5 x 7472N . 10/-	UIC92 = 5 x 7492N . 10/-
UIC10 = 5 x 7410N . 10/-	UIC73 = 5 x 7473N . 10/-	UIC93 = 5 x 7493N . 10/-
UIC20 = 5 x 7420N . 10/-	UIC74 = 5 x 7474N . 10/-	UIC94 = 5 x 7494N . 10/-
UIC40 = 5 x 7440N . 10/-	UIC75 = 5 x 7475N . 10/-	UIC95 = 5 x 7495N . 10/-
UIC41 = 5 x 7441AN . 10/-	UIC76 = 5 x 7476N . 10/-	UICX1 = 20 ass'd 74's 30/-

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UIC1. Every PAK carries our BI-PAK Satisfaction of money back GUARANTEE.

DUAL-IN-LINE LOW PROFILE SOCKETS

14 AND 16 Lead Sockets for use with Dual-in-Line Integrated Circuits.

Order No.	Description	Price each		
		1-24	25-99	100 up
TSO14	14 pin type	7/6	8/6	5/3
TSO16	16 pin type	10/-	8/6	7/9

RTL. FAIRCHILD (U.S.A.) I.C's

RTL Micrologic Circuits
Epoxy case To-5 temp range 15°C to 55°C. Qty. prices each
μL 900 Buffer 1-11 12/- 24 25/99 100 + 8/- 7/- 6/8 5/8
μL 914 Dual two-input GATE 8/- 7/- 6/8 5/8
μL 923 J-K Flip-flop 10/8 10/- 9/8 9/-
Full data and circuits for ICS in Booklet form price 1/8 each.
μA703E Linear RF-IF AMPLIFIER 11/- 10/- 9/- 8/3
PLASTIC CASE To-5 9 lead up to 100 m/c/s.

DTL. DIGITAL I.C's

DTL dual in-line package
Type MC844P expandable dual 4-input NAND Power Gate 10/- each
Type MC845F Clocked Flip-flop 15/- each
Type 862 Triple 3-input NAND/NOR Gate 10/- each
FULL DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

BI-PAK SEMICONDUCTORS

DEPT. T, P.O. BOX 6, WARE, HERTS

Postage and packing add 1/- Overseas add extra for Airmail. Minimum order 10/- Cash with order please.

SPECIAL OFFER!

RE-CONDITIONED GUARANTEED TUBES FROM STOCK:

12" — £4-0-0 17" — £4-5-0 19" TWIN PANEL £9-10-0
 14" — £4-0-0 19" — £6-0-0 21" MONO £6-10-0
 23" MONO £6-10-0 23" TWIN PANEL £10-0-0

ANY TYPE OF NEW TUBE SUPPLIED... PRICES ON APPLICATION
 CARRIAGE ON ALL TUBES 12/6 EACH

TELEVISION VALVES:—

DY86	8/-	ECL80	7/-	GY501	15/-	PCC89	10/6	PCF802	9/9	PD500	28/-	PL802	16/6	PY801	9/6	6CD6G	24/-	30FL1	16/-
DY47	6/6	EF80	4/9	GZ22	10/-	PCC189	10/6	PCF806	13/6	PL200	14/-	PY32	10/9	R19	7/9	6F23	18/-	30L15	17/-
DYN02	12/6	EF85	6/6	KT61	22/6	PCF80	6/9	PCH200	12/6	PL36	10/9	PY33	10/9	U25	15/6	6F25	28/6	30L17	17/-
EB91	3/-	EF91	3/6	PC86	11/6	PCF86	9/-	PCL82	7/9	PL81	9/6	PY81	15/9	U26	18/6	6X4	4/6	30P4	22/6
ECC81	6/-	EF183	6/6	PC88	11/6	PCF200	16/-	PCL83	10/3	PL82	8/6	PY82	6/3	U191	13/9	10F1	14/9	30P19	15/-
ECC82	5/9	EF184	7/-	PC97	8/9	PCF201	15/6	PCL84	8/6	PL84	7/-	PY83	7/-	U801	23/6	30C15	15/-	30PL1	16/-
ECC83	6/3	EY51	7/8	PC900	8/6	PCF800	15/-	PCL85	9/3	PL508	29/-	PY500	18/6	U78	21/-	30C17	16/-	30PL13	18/6
ECC85	5/-	EY86	7/8	PCC84	6/6	PCF801	9/9	PCL86	9/3	PL509	29/-	PY800	9/6	6/30L2	15/-	30F5	17/-	30PL14	18/-

Postage per valve first class 9d. Orders over £5 post free.

TELEVISION TRANSISTORS:—

2N698	8/6	28034	12/6	AF178	9/6	BC107	2/6	BC116	8/-	BC154	7/6	BF154	8/-	BF180	7/6	BFY50	4/6	BZY86	3/6
2N3703	2/6	AC127	5/-	AF180	10/6	BC108	2/6	BC118	7/6	BC187	5/6	BF158	8/-	BF481	7/6	BFY51	4/-	Series	3/6
2N3705	3/-	AC128	5/-	AF186	8/-	BC113	5/-	BC134	7/6	BD124	12/6	BF167	5/-	BF184	3/6	BY100	3/6	OA47	2/-
2N3710	2/6	AC153	4/-	BA102	5/-	BC115	6/6	BC148	2/6	BD115	5/-	BF173	6/-	BF194	3/6	BY126	3/-	OA79	2/-

Postage free on all Transistors.

ALL VALVES AND TRANSISTORS BRAND NEW AND FULLY GUARANTEED.

SEND S.A.E. FOR LISTS OF VALVES, TUBES, TRANSISTORS. 6000 TYPES LISTED.

OPEN DAILY TO CALLERS MON.—FRI. 9 A.M.—5.30 P.M. SAT. 9 A.M.—1 P.M., 2.30 P.M.—5 P.M.

RST 16 WELLFIELD ROAD, LONDON, S.W. 16 PHONE 01-769 0199

2 NEW "TELEBOOSTERS"



**THE M4
 DUAL BAND
 V.H.F. UNIT
 KING . . .**
 the name you
 can depend on.

- * Boosts all Band III and any specified Band I Channel simultaneously.
 - * Still higher gain . . . nominally 17-18 d.B. both Bands.
 - * Very low noise third generation passivated transistor.
 - * Fitted fly lead . . . installed in seconds.
 - * Quality Case 3 1/4" x 3 1/4" x 1 1/2" Cork base.
- Specify Band I channel when ordering.

THE NEW UM4 UHF "COLOURBOOSTER"
 Channels: Group "A" Red Spot. "B" Yellow Spot, "C" Green Spot. Prices: Both types—75/- Battery Model OR £5.17.6 Self Contained Mains Model. P/P 2/6d.

TRANSISTOR DEVICES LIMITED
 Bridge House, NEWTON ABBOT, Devon.
 Literature on request.

UHF, COLOUR AND TELEVISION SPARES

COLOUR Leading Brit. makers surplus LUMINANCE/CHROM PANELS 20/- p.p. 4/6. SCAN COILS 70/- p.p. 6/6. CONV COILS 65/- p.p. 4/6. INTEGRATED TRANSMITTER. DECODER UNIT including circuits 27/- p.p. 2/6.
 UHF/625 conversion kits and tuners at reduced prices. Lists available.
 UHF integrated transist. 6 position push button tuners, leading Brit. maker surplus £4.10.0 p.p. 4/6. TRANS. IF PANELS (SALVAGED) £2.10.0 p.p. 4/6.
 MURPHY 600/700 series UHF conversion kits in cabinet plinth assy., can be used as separate UHF receiver £7.10.0 p.p. 10/6. 625 IF amplifier incl. 5 valves and circuit 58/6 p.p. 6/6.
 SOBELL/GEC dual 405/625 IF amp. and o/p chassis incl. circuit 32/6. ULTRA 1980C to 2384 625 IF amp. chassis and switch incl. circuits 25/- p.p. 4/6.
 UHF TUNERS transist. incl. 5/M drive or P.B. £5.5.0 p.p. 4/6.
 TV SIGNAL BOOSTER UNITS Latest PVE/LABGEAR all station UHF/VHF transist. "feedback" mains operated £7.15.0. UHF Masthead £5.5.0 p.p. 4/6.
 FIREBALL TUNERS. Ferr. HMV, Marconi new 37/6, others salvaged 18/6.
 PUSH BUTTON. Plessey, Ekco incl. valves 58/6, RGD612 (used) 30/- p.p. 4/6.
 TURRET TUNERS PETO SCOTT 960, COSSOR 1064, DECCA DE 95, 101/606 38/6. CYLON C 20/- AB dual standard suitable Ferguson, K.B. Baird, etc. 25/- Pyc CTM 17 25/- p.p. 4/6. Large selection ch. colls.
 LINE OUTPUT TRANSF. Popular types available, brand new replacements fully gum. A selection which can be supplied, p.p. 4/6, C.O.D. 3/6.
 PHILIPS 17TG100 range, STELLA 1011/1029 70/-
 BUSH TV33 to 69, 40/- 95 to 135 90/-
 EKCO 221 to 331 (U25 or U26 types) 42/6
 FERRANTI 1001 to 1019 (U25 or U26 types) 85/-
 EKCO 342 to 394 FERRANTI 1021 to 1065 75/-
 EKCO/FERRANTI 418, 1093, etc. 70/-
 DECCA DM17, 3, 4 (70") DR95, 101/606 78/6
 FERG 305 to 436, 505 to 727 75/-
 FERG HMV MARCONI ULTRA PHILCO 3600, 2600, 4600, 6600, 1100 ranges, Jellypot 75/-
 KB QVP20, QV20/1 to SV20 55/-
 KB PVP 20 VC1 to VC11 78/-
 MARCONI VT157 to 172 75/-
 GSC 302 to 345, 45/-; 448 series 85/-
 HMV 1065/9, 1070, 1092 78/-
 PVE CTM/CW series (print circuit) 17/21
 17/8, 110 to 510, 700, 830, 11U to 40F 70/-
 PAM INVICTA equiv. LOFTS to above PVE 70/-
 PETO SCOTT 1419 to 1725, 35/-; 733 to 738 50/-
 SOBELL/MEMICH TP8173, 180, T23, 24, 178, 278, SC24, 270, MP17, 18, M72, 74 45/-
 TP8781, T279, SC34, 370, MP27, M73, 76, 93 45/-
 195, 282, 762 series 65/-
 PHILCO 1010 to 1021 45/-
 ULTRA 1770 to 2384, PILOT PT450 to 650 72/6
 LOFT Inserts p.p. 2/-
 Alba 655, 656 35/-
 Bush TV32, 46, 43 45/-
 Cosmor 933 to 950 35/-
 Ekco TP308 35/-
 Emerson 700 range 35/-
 Ferguson 203 to 246 35/-
 Ferranti 1475 to 21K6 35/-
 KB, NF70, OV30, PV40, 35/-
 PVP20, QV10, 20, 30 35/-
 KB/RGD Featherlight 50/-
 KB/RGD VCL 2, 3, 4 35/-
 PETO SCOTT 733/738 35/-
 Philco 1961, 1030 series 35/-
 Philips 17TG100 range 35/-
 Pyc, VT4, VTT 42/6
 RGD D17, 690 to 619 35/-
 REG 10-4, 10-17 to 192 35/-
 Ultra 1770, 1780 range 35/-

MANOR SUPPLIES
 172 WEST END LANE, LONDON, N.W.6
 (Near W. Hampstead tube stn; 28, 59, 159 Bus Routes) 01-794 5751
 MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering ...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship*

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Construction

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T., and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D258, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



BIET

POST THIS COUPON TODAY

To: B.I.E.T., Dept D257 Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name..... Age.....

Address.....

Occupation.....

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE