


JULY 1979

Australia 95c; Malaysia \$2.75; New Zealand 98c

55p

TELEVISION

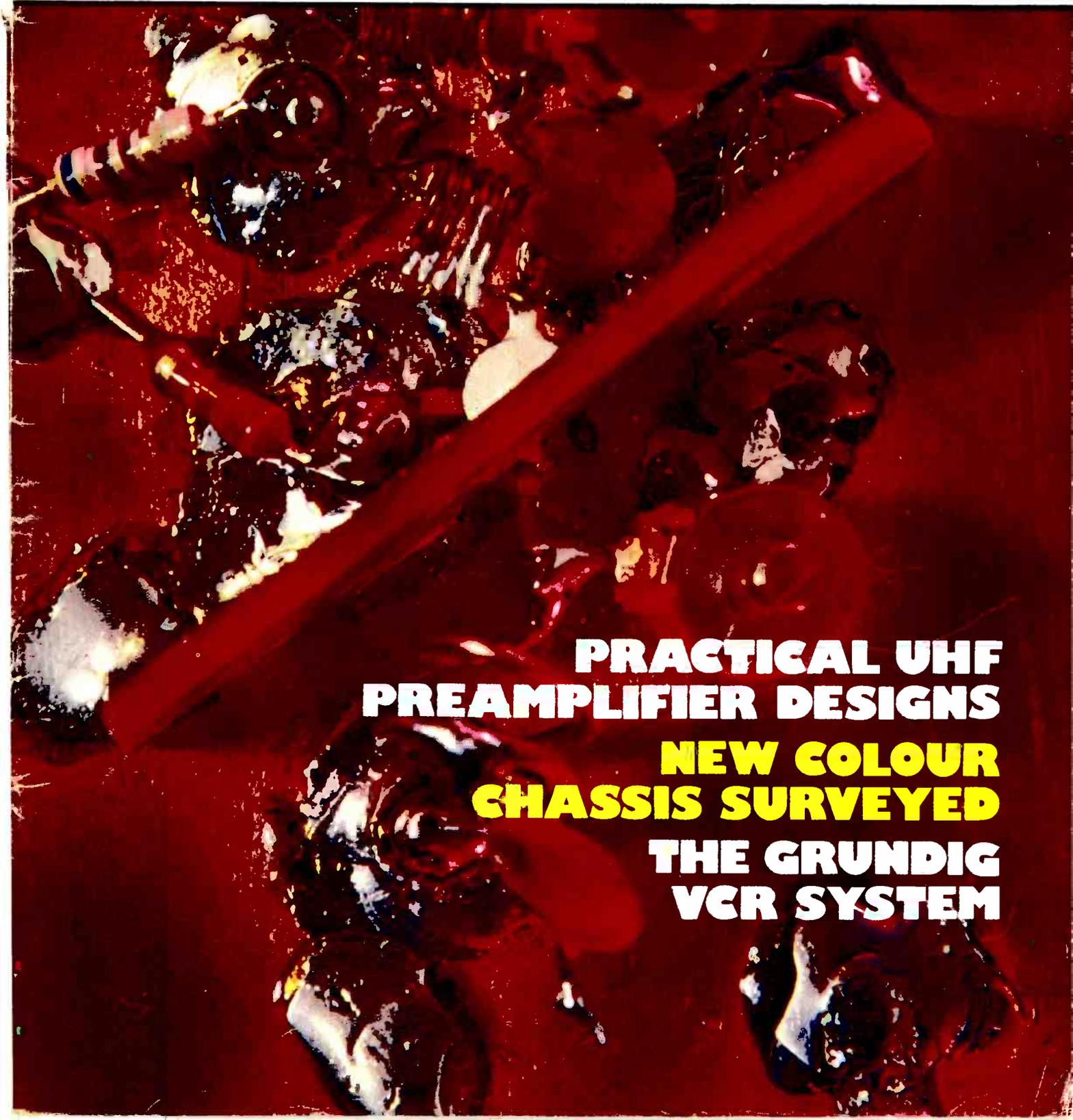SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS



**PRACTICAL UHF
PREAMPLIFIER DESIGNS**

**NEW COLOUR
CHASSIS SURVEYED**

**THE GRUNDIG
VCR SYSTEM**


PHD COMPONENTS

RADIO & TV COMPONENT DISTRIBUTORS
 UNIT 7 CENTENARY ESTATE
 JEFFRIES RD ENFIELD MIDDX
 MAIL ORDER ONLY TELEX 261295

ALL COMPONENTS OFFERED SUBJECT TO AVAILABILITY. WE RESERVE THE RIGHT TO SUBSTITUTE REPLACEMENTS SHOULD THE ORIGINAL PART BE OUT OF STOCK OR UNAVAILABLE!
 PLEASE ADD 0.35p per parcel post and packing.

SEMICONDUCTORS

AA113	0.16	BC117	0.20	BU208/02	3.00
AA116	0.16	BC118	0.20	BU326S	1.50
AA117	0.16	BC119	0.20	BU406	2.00
AA119	0.16	BC125	0.20	BU406D	2.50
OA91	0.12	BC126	0.20	BU407	2.50
OA95	0.12	BC136	0.20	BU407D	2.50
OA202	0.18	BC137	0.20	R2008B	2.50
BA100	0.18	BC138	0.40	R2010F	2.50
BA102	0.10	BC139	0.40	R2540	3.00
BA130	0.15	BC140	0.40	ME402	0.20
BA154	0.10	BC142	0.40	ME412	0.20
BA155	0.10	BC143	0.40	ME4003	0.15
BA164	0.12	BC147	0.15	ME6002	0.20
BAX13	0.16	BC148	0.10	ME8001	0.20
BAX15	0.16	BC149	0.15	MJE2995	1.50
BAX16	0.08	BC153	0.15	MJE3005	1.30
BY206	0.20	BC154	0.15	MPR113	1.00
IN4148	0.04	BC157	0.15	MPS505	1.20
BY126	0.20	BC158	0.15	MPS155	1.20
BY127	0.15	BC160	0.40	TIP295E	1.30
BY133	0.22	BC161	0.40	TIP305S	1.30
BY194	0.50	BC170	0.15	TIS90M	0.60
SK82/08	1.00	BC171	0.15	TIS91M	0.50
BY236	0.15	BC172	0.20	2N2904	0.50
BYX10	0.18	BC177	0.20	2N2905A	0.50
IN4001	0.10	BC178	0.20	2N2906	0.50
IN4002	0.10	BC179	0.20	2N3053	0.50
IN4003	0.12	BC182A	0.15	2N3703	0.20
IN4004	0.12	BC183L	0.15	2N3705	0.20
IN4005	0.12	BC184L	0.15	2N3710	0.20
IN4006	0.14	BC184LC	0.15	2N3055H	0.75
IN4007	0.16	BC186	0.30	TAA350	0.80
IN5407	0.33	BC187	0.30	TAA550	0.60
BR100	0.50	BC203	0.15	TAA570	1.80
BR101	0.50	BC204	0.15	TAA611	1.75
BR102	0.50	BC205	0.15	TAA630S	2.50
BR103	0.50	BC206	0.15	TAA661B	2.00
BR104	0.50	BC207	0.15	TN76540N	1.50
BR105	0.50	BC208	0.15	TAD100	0.50
BR106	0.50	BC209	0.15	TBA120AS	1.50
BR107	0.50	BC210	0.15	TBA231	1.20
BR108	0.50	BC211	0.15	TBA4800	2.00
BR109	0.50	BC212	0.15	TBA5200	2.00
BR110	0.50	BC213	0.15	TBA530	2.00
BR111	0.50	BC214	0.15	TBA5300	2.00
BR112	0.50	BC215	0.15	TBA540	2.20
BR113	0.50	BC216	0.15	TBA540Q	2.20
BR114	0.50	BC217	0.15	TBA550	3.00
BR115	0.50	BC218	0.15	TBA550Q	3.00
BR116	0.50	BC219	0.15	TBA560C	2.00
BR117	0.50	BC220	0.15	TBA560CC	2.20
BR118	0.50	BC221	0.15	TBA570	2.50
BR119	0.50	BC222	0.15	TBA5700	3.00
BR120	0.50	BC223	0.15	TBA619X	3.00
BR121	0.50	BC224	0.15	TBA641B11	4.00
BR122	0.50	BC225	0.15	TBA651	3.50
BR123	0.50	BC226	0.15	TBA720A	1.50
BR124	0.50	BC227	0.15	TBA730	1.50
BR125	0.50	BC228	0.15	TBA750	2.00
BR126	0.50	BC229	0.15	TBA7500	2.00
BR127	0.50	BC230	0.15	TBA800	1.50
BR128	0.50	BC231	0.15	TBA810S	1.50
BR129	0.50	BC232	0.15	TBA820	1.50
BR130	0.50	BC233	0.15	TBA8200	2.00
BR131	0.50	BC234	0.15	TBA920	2.00
BR132	0.50	BC235	0.15	TBA9200	2.00
BR133	0.50	BC236	0.15	TBA990	0.80
BR134	0.50	BC237	0.15	TBA9900	2.00
BR135	0.50	BC238	0.15	TC2705A	3.00
BR136	0.50	BC239	0.15	TC2705B	3.00
BR137	0.50	BC240	0.15	TC2705C	3.00
BR138	0.50	BC241	0.15	TC2705D	3.00
BR139	0.50	BC242	0.15	TC2705E	3.00
BR140	0.50	BC243	0.15	TC2705F	3.00
BR141	0.50	BC244	0.15	TC2705G	3.00
BR142	0.50	BC245	0.15	TC2705H	3.00
BR143	0.50	BC246	0.15	TC2705I	3.00
BR144	0.50	BC247	0.15	TC2705J	3.00
BR145	0.50	BC248	0.15	TC2705K	3.00
BR146	0.50	BC249	0.15	TC2705L	3.00
BR147	0.50	BC250	0.15	TC2705M	3.00
BR148	0.50	BC251	0.15	TC2705N	3.00
BR149	0.50	BC252	0.15	TC2705O	3.00
BR150	0.50	BC253	0.15	TC2705P	3.00
BR151	0.50	BC254	0.15	TC2705Q	3.00
BR152	0.50	BC255	0.15	TC2705R	3.00
BR153	0.50	BC256	0.15	TC2705S	3.00
BR154	0.50	BC257	0.15	TC2705T	3.00
BR155	0.50	BC258	0.15	TC2705U	3.00
BR156	0.50	BC259	0.15	TC2705V	3.00
BR157	0.50	BC260	0.15	TC2705W	3.00
BR158	0.50	BC261	0.15	TC2705X	3.00
BR159	0.50	BC262	0.15	TC2705Y	3.00
BR160	0.50	BC263	0.15	TC2705Z	3.00
BR161	0.50	BC264	0.15	TC2705AA	3.00
BR162	0.50	BC265	0.15	TC2705AB	3.00
BR163	0.50	BC266	0.15	TC2705AC	3.00
BR164	0.50	BC267	0.15	TC2705AD	3.00
BR165	0.50	BC268	0.15	TC2705AE	3.00
BR166	0.50	BC269	0.15	TC2705AF	3.00
BR167	0.50	BC270	0.15	TC2705AG	3.00
BR168	0.50	BC271	0.15	TC2705AH	3.00
BR169	0.50	BC272	0.15	TC2705AI	3.00
BR170	0.50	BC273	0.15	TC2705AJ	3.00
BR171	0.50	BC274	0.15	TC2705AK	3.00
BR172	0.50	BC275	0.15	TC2705AL	3.00
BR173	0.50	BC276	0.15	TC2705AM	3.00
BR174	0.50	BC277	0.15	TC2705AN	3.00
BR175	0.50	BC278	0.15	TC2705AO	3.00
BR176	0.50	BC279	0.15	TC2705AP	3.00
BR177	0.50	BC280	0.15	TC2705AQ	3.00
BR178	0.50	BC281	0.15	TC2705AR	3.00
BR179	0.50	BC282	0.15	TC2705AS	3.00
BR180	0.50	BC283	0.15	TC2705AT	3.00
BR181	0.50	BC284	0.15	TC2705AU	3.00
BR182	0.50	BC285	0.15	TC2705AV	3.00
BR183	0.50	BC286	0.15	TC2705AW	3.00
BR184	0.50	BC287	0.15	TC2705AX	3.00
BR185	0.50	BC288	0.15	TC2705AY	3.00
BR186	0.50	BC289	0.15	TC2705AZ	3.00
BR187	0.50	BC290	0.15	TC2705BA	3.00
BR188	0.50	BC291	0.15	TC2705BB	3.00
BR189	0.50	BC292	0.15	TC2705BC	3.00
BR190	0.50	BC293	0.15	TC2705BD	3.00
BR191	0.50	BC294	0.15	TC2705BE	3.00
BR192	0.50	BC295	0.15	TC2705BF	3.00
BR193	0.50	BC296	0.15	TC2705BG	3.00
BR194	0.50	BC297	0.15	TC2705BH	3.00
BR195	0.50	BC298	0.15	TC2705BI	3.00
BR196	0.50	BC299	0.15	TC2705BJ	3.00
BR197	0.50	BC300	0.15	TC2705BK	3.00
BR198	0.50	BC301	0.15	TC2705BL	3.00
BR199	0.50	BC302	0.15	TC2705BM	3.00
BR200	0.50	BC303	0.15	TC2705BN	3.00
BR201	0.50	BC304	0.15	TC2705BO	3.00
BR202	0.50	BC305	0.15	TC2705BP	3.00
BR203	0.50	BC306	0.15	TC2705BQ	3.00
BR204	0.50	BC307	0.15	TC2705BR	3.00
BR205	0.50	BC308	0.15	TC2705BS	3.00
BR206	0.50	BC309	0.15	TC2705BT	3.00
BR207	0.50	BC310	0.15	TC2705BU	3.00
BR208	0.50	BC311	0.15	TC2705BV	3.00
BR209	0.50	BC312	0.15	TC2705BW	3.00
BR210	0.50	BC313	0.15	TC2705BX	3.00
BR211	0.50	BC314	0.15	TC2705BY	3.00
BR212	0.50	BC315	0.15	TC2705BZ	3.00
BR213	0.50	BC316	0.15	TC2705CA	3.00
BR214	0.50	BC317	0.15	TC2705CB	3.00
BR215	0.50	BC318	0.15	TC2705CC	3.00
BR216	0.50	BC319	0.15	TC2705CD	3.00
BR217	0.50	BC320	0.15	TC2705CE	3.00
BR218	0.50	BC321	0.15	TC2705CF	3.00
BR219	0.50	BC322	0.15	TC2705CG	3.00
BR220	0.50	BC323	0.15	TC2705CH	3.00
BR221	0.50	BC324	0.15	TC2705CI	3.00
BR222	0.50	BC325	0.15	TC2705CJ	3.00
BR223	0.50	BC326	0.15	TC2705CK	3.00
BR224	0.50	BC327	0.15	TC2705CL	3.00
BR225	0.50	BC328	0.15	TC2705CM	3.00
BR226	0.50	BC329	0.15	TC2705CN	3.00
BR227	0.50	BC330	0.15	TC2705CO	3.00
BR228	0.50	BC331	0.15	TC2705CP	3.00
BR229	0.50	BC332	0.15	TC2705CQ	3.00
BR230	0.50	BC333	0.15	TC2705CR	3.00
BR231	0.50	BC334	0.15	TC2705CS	3.00
BR232	0.50	BC335	0.15	TC2705CT	3.00
BR233	0.50	BC336	0.15	TC2705CU	3.00
BR234	0.50	BC337	0.15	TC2705CV	3.00
BR235	0.50	BC338	0.15	TC2705CW	3.00
BR236	0.50	BC339	0.15	TC2705CX	3.00
BR237	0.50	BC340	0.15	TC2705CY	3.00
BR238	0.50	BC341	0.15	TC2705CZ	3.00
BR239	0.50	BC342	0.15	TC2705DA	3.00
BR240	0.50	BC343	0.15	TC2705DB	3.00
BR241	0.50	BC344	0.15	TC2705DC	3.00
BR242	0.50	BC345	0.15	TC2705DD	3.00
BR243	0.50	BC346	0.15	TC2705DE	3.00
BR244	0.50	BC347	0.15	TC2705DF	3.00
BR245	0.50	BC348	0.15	TC2705DG	3.00
BR246	0.50	BC349	0.15	TC2705DH	3.00
BR247	0.50	BC350	0.15	TC2705DI	3.00
BR248	0.50	BC351	0.15	TC2705DJ	3.00
BR249	0.50	BC352	0.15	TC2705DK	3.00
BR250	0.50	BC353	0.15	TC2705DL	3.00
BR251	0.50	BC354	0.15	TC2705DM	3.00
BR252	0.50	BC355	0.15	TC2705DN	3.00
BR253	0.50	BC356	0.15	TC2705DO	3.00
BR254	0.50	BC357	0.15	TC2705DP	3.00
BR255	0.50	BC358	0.15	TC2705DQ	3.00
BR256	0.50	BC359	0.15	TC2705DR	3.00
BR257	0.50	BC360	0.15	TC2705DS	3.00
BR258	0.50	BC361	0.15	TC2705DT	3.00
BR259	0.50	BC362	0.15	TC2705DU	3.00
BR260	0.50	BC363	0.15	TC2705DV	3.00
BR261	0.50	BC364	0.15	TC2705DW	3.00
BR262	0.50	BC365	0.15	TC2705DX	3.00
BR263	0.50	BC366	0.15	TC2705DY	3.00
BR264	0.50	BC367	0.15	TC2705DZ	3.00
BR265	0.50	BC368	0.15	TC2705EA	3.00
BR266					

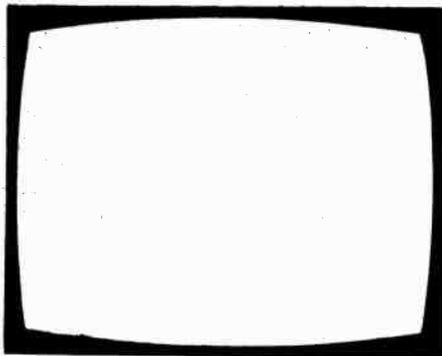

TELEVISION

July
1979

Vol. 29, No. 9
Issue 345

COPYRIGHT

© IPC Magazines Limited, 1979. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

SUBSCRIPTIONS

An annual subscription costs £9.50 in the UK, £10.50 overseas (\$21 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£2.85) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 70p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Your Problems Solved". Send to the address given above (see "correspondence").

this month

- 455 **Leader**
- 456 **Teletopics**
News, comment and developments.
- 458 **Letters**
- 462 **Practical UHF Preamplifiers** *by Roger Bunney*
A low-noise design using a silicon pnp transistor. The wideband version is intended for use in areas with poor or difficult signal conditions, the narrow-band version for use in obtaining regular reception of an extra, non-local channel.
- 464 **Only in Dreams . . .** *by Les Lawry-Johns*
During the day there are problems with recalcitrant sets, customers and dogs, but during the night the real battles have to be fought and won.
- 466 **The New Colour Chassis**
During the past year, most UK setmakers have introduced new colour chassis, primarily intended to drive the smaller size, 90° tubes. The technical features of the ITT CVC40 and CVC45/1, the Pye/Philips KT3, the Decca 70 series and Thom TX9 chassis are summarised.
- 470 **Test Report: New Dimension TV TR500 CRT Tester/Reactivator** *by J. H. Starling*
An assessment of the usefulness of this device in field servicing.
- 471 **Renovating Körting Hybrid Colour Receivers, Part 2** *by Mike Phelan*
This concluding instalment includes setting up and decoder alignment instructions.
- 474 **Long-Distance Television** *by Roger Bunney*
Reports on DX reception and conditions, and news from abroad. Also a look at the satellite TV situation in N. America.
- 478 **Service Notebook** *by George Wilding*
Notes on faults and how to tackle them.
- 479 **Teletext Decoder Update, Part 2** *by Steve A. Money, T.Eng.(C.E.I.)*
Continuing the account of the circuitry on the extra board.
- 481 **The Grundig SVR VCR System** *by D. K. Matthewson, B.Sc., Ph.D.*
While based on the same cassette format as the Philips system, there are considerable differences in other aspects of the Grundig Super Video VCR.
- 483 **Next Month in Television**
- 484 **TV Servicing: Beginners Start Here . . . Part 22** *by S. Simon*
The most useful aid the service engineer has is his multimeter. Its selection and use in practical servicing are considered.
- 487 **Readers' PCB Service**
- 488 **Colour Pattern Generator, Part 3** *by Malcolm Burrell*
Constructing the analogue board, testing and setting up the entire generator, and suggestions for fault finding. With board layout details and full components list.
- 493 **Your Problems Solved**
- 495 **Test Case 199**

OUR NEXT ISSUE DATED AUGUST WILL BE
PUBLISHED ON JULY 16

THE UNBEATABLE BRIARWOOD SERVICE

EX-EQUIPMENT SPARES

MISC. S/Output Trans.
£1 + VAT + £1 P&P
F/Output Trans.
£1.25 + VAT + £1 P&P.
Scancoils £1.50 + VAT
+ £1 P&P. Other
spares available, please
write or phone for details.

MONO TUBES (tested)

19" Ringuard £3.00
23" Ringuard £4.00
20" Ringuard £5.00
24" Ringuard £6.00
+ £4.00 P.&P.

MONO TUNERS

6-button integrated all
at £6.00
U.H.F. P/Button D/S
£4.50. U.H.F. P/Button
S/S £4.50. Rotary £3.00
+ £1 P&P.

MONO LOPTS

All D/Standard Lopts
at £4.00 + £1 P.&P.
All S/Standard at
£4.00 + £1 P.&P.

MONO PANELS

i.e. Philips, Bush etc.
£3.50 + £1 P.&P.
Quotations for
complete
S/hand chassis if
required. (Diff. prices)

PLEASE ADD 12½% V.A.T.
TO ALL ITEMS AND
OVERSEAS AT COST.
CASH WITH ALL ORDERS.

VALVES (MONO & COLOUR)

PCL82	0.10	PCF802	0.10	PCC86	0.10	EY86/7	0.10	30PL1	0.25	PL509	1.00
PCL83	0.25	PCF805	0.25	PC97	0.20	EY8/7	0.10	30PL13/4	0.10	PY500	1.00
PCL84	0.10	PCF806	0.10	PC900	0.10	DY802	0.10	30P12	0.10	GY501	1.00
PCL85	0.10	PCF808	0.25	EF80	0.10	PY800/1	0.10	30FL1/2	0.25	PL508	0.50
PCL86	0.10	PCF80	0.10	EF85	0.10	PL36	0.25	ECC82	0.10	PCH200	0.50
PFL200	0.10	PCC189	0.10	EF183	0.10	PL504	0.25	ECC81	0.10	PCF200	0.50
PCF801	0.10	PCC86	0.10	EF184	0.10	PL81	0.10	ECH81	0.10	CEY51	0.15
30C1	0.10	30C15	0.10	6BW7	0.10	6/30L2	0.10	ECL80	0.10		
30C17	0.10	30C18	0.25	ECC85	0.10	U26	0.10	ECL82	0.10		
PL83	0.10	PL84	0.10	EH90	0.10						

Please note there is 25p Postage and Packing per order.

WE DO NOT SELL RUBBISH
AT BRIARWOOD TV

D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUTPUT	POWER	L/TB	F/TB
Bush/Murphy	6.50	6.50	6.50	—	—	6.50	1.50	6.50	—	—
GEC/Sobell	6.50	7.50	—	—	—	6.50	—	—	—	7.50
Philips	6.50	9.50	—	—	—	7.50	—	—	—	6.50
Decca	6.50	12.50	12.50	—	—	6.50	—	8.00	—	6.00
Thorn 2000	6.50	7.50	7.50	6.50	6.50	7.00	—	8.00	15.00	6.50
Pye	7.50	7.50	9.50	—	—	6.50	—	—	—	7.50
Baird	6.50	8.50	8.50	—	—	6.50	—	—	—	6.00

Postage & Packing £1.25

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	20.00	—	8.00	6.00	15.00	—
GEC Hybrid	9.50	9.50	15.00	—	6.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	9.00	—	—	10.00
Thorn 3000	10.00	9.00	18.00	10.00	6.00	20.00	20.00	10.00
Pye 691/693	8.00	7.50	12.00	—	8.00	—	15.00	7.50
Thorn 3500	10.00	9.00	12.00	10.00	7.50	20.00	20.50	7.50

Korting and other foreign
panels available on request.

Postage & Packing £1.25

COLOUR TUBES

19" £18.00
19" A49, 192 £20.00
20" £20.00
22" £22.00
25" £18.00
26" £28.00

Plus P&P £4.

NEW
Rebuilt tubes
available on request.

COLOUR TUNERS

Bush £6.50
GEC £6.50
Philips G6 S/S £6.50
Thorn 3000 £6.50
Pye 691/697 £7.50
Some new tuners in stock,
can supply on request. Many
Foreign Tuners also available
on request. Plus P&P £1.

COLOUR LOPTS

Most Lopts available
from £7.00. Both
British & Foreign
makes. Please ring
or write.
P&P per Lopt £1.

MISC.

S/Output transformer
from £1.50.
F/Output from £1.25.
Scancoils from £5.00.
P&P £1.
Other spares available on
request.

G8 PANELS

SPECIAL OFFER
CHROMA £12.00

THORN 1500 TUNERS

NEW SPECIAL OFFER
AT £8.00

Postage & Packing £1.00

MAIL ORDER T.V.s. IN GOOD WORKING ORDER

COLOUR				MONO					
Pye	19"	£60.00	22"	£65.00	26"	£75.00	20" & 24" S/S	£16.00	Pye, GEC, Bush etc.
GEC	19"	£60.00	22"	£65.00	26"	£75.00	20" & 24" D/S	£14.00	Pye, GEC, Bush etc.
Bush	19"	£80.00	22"	£80.00	26"	£90.00	19" & 23" D/S	P/button £12.00	Pye, GEC, Bush etc.
Philips	G6	—	22"	£63.00	26"	£70.00	19" & 23" D/S	Rotary £8.00	Pye, GEC, Bush etc.

Many other makes & models available.
Please ring or write for information.

**PERSONAL CALLERS
WELCOME.**

Please note there is 12½% V.A.T. on all the above prices.
Plus £8 P&P. England, Wales & Scotland for colour T.V.'s.
Inland N. & S. Ireland P&P £15. P&P £5 for mono T.V.'s
to England, Wales & Scotland. Inland N. & S. Ireland £7
per set.

Briarwood T.V. Limited
Britain's Mail Order
T.V. Specialists

BRIARWOOD

THE PROFESSIONAL CHOICE. NATIONWIDE

NEW SPARES

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	DIODES	E.H.T. TRAYS MONO		
AC107	0.20	AF170	0.25	BC172	0.08	BD222/T1P31A	0.24	BF260	0.24	OC45	0.20	1N4001	0.04	950 MK2 1400	2.00
AC113	0.17	AF172	0.20	BC173	0.12		0.37	BF262	0.28	OC46	0.35	1N4002	0.04	1500 18" 19" stick	
AC115	0.17	AF178	0.49	BC177	0.12	BD225/T1P31A	0.25	BF263	0.25	OC70	0.22	1N4003	0.06		2.37
AC117	0.24	AF180	0.60	BC178	0.12		0.39	BF271	0.20	OC71	0.28	1N4004	0.07	1500 24" 5 stick	2.48
AC125	0.20	AF181	0.30	BC179	0.12	BD234	0.34	BF273	0.12	OC72	0.35	1N4005	0.07	Single stick Thorn TV	
AC126	0.18	AF186	0.29	BC182L	0.09	BD222	0.73	BF336	0.27	OC74	0.35	1N4006	0.08	11.16K 70V	0.75
AC127	0.19	AF239	0.43	BC183L	0.09	BDX22	0.73	BF337	0.24	OC75	0.35	1N4007	0.08	TV20 2 MT	0.75
AC128	0.17	AU113	1.29	BC184L	0.09	BDX32	1.98	BF338	0.29	OC76	0.35	1N4148	0.03	TV20 16K 18V	0.75
AC131	0.13			BC186	0.18	BDY18	0.75	BF42	0.26	OC77	0.50	1N4751A	0.11		
AC141	0.23	BA130	0.08	BC187	0.18	BDY60	0.80	BF43	0.24	OC78	0.13	1N5401	0.12		
AC142	0.19	BA145	0.14	BC209	0.11	BF115	0.24	BFX84	0.27	OC81	0.20	1N5404	0.12		
AC141K	0.29	BA148	0.17	BC212	0.09	BF121	0.21	BFX85	0.27	OC810	0.14	1N5406	0.13		
AC142K	0.29	BA155	0.08	BC213L	0.09	BF154	0.12	BFX88	0.24	OC82	0.20	1N5408	0.16		
AC151	0.17	BAX13	0.05	BC214L	0.09	BF15B	0.19	BFY37	0.22	OC820	0.13				
AC165	0.16	BAX16	0.08	BC237	0.07	BF159	0.24	BFY50	0.15	OC83	0.22				
AC166	0.16	BC107	0.10	BC240	0.31	BF160	0.23	BFY51	0.15	OC84	0.28	VALVES			
AC168	0.17	BC108	0.10	BC281	0.24	BF163	0.23	BFY52	0.15	OC85	0.13	DY87	0.52	TBA341	0.97
AC176	0.17	BC109	0.10	BC262	0.18	BF164	0.17	BFY53	0.27	OC123	0.20	DY802	0.64	TBA520Q	1.10
AC176K	0.28	BC113	0.09	BC263B	0.20	BF167	0.23	BFY55	0.27	OC169	0.20	ECC82	0.52	TBA530Q	1.10
AC178	0.16	BC114	0.12	BC267	0.19	BF173	0.21	BHA0002	1.90	OC170	0.22	EF80	0.40	TBA540Q	1.45
AC186	0.26	BC115	0.10	BC301	0.22	BF177	0.26	BR100	0.20	OC171	0.27	EF183	0.60	TBA550Q	1.40
AC187	0.21	BC116	0.10	BC302	0.30	BF178	0.24	BSX20	0.23	OA91	0.05	EF184	0.60	TBA560CQ	1.50
AC188	0.20	BC117	0.11	BC307	0.10	BF179	0.28	BSX76	0.23	R2008B	1.50	EH90	0.60	TBA570Q	1.00
AC187K	0.30	BC119	0.22	BC337	0.11	BF180	0.30	BSY84	0.36	R2010B	1.50	PC86	0.76	TBA800	1.00
AC188K	0.30	BC125	0.12	BC338	0.09	BF181	0.34	BT106	1.18	R2305	0.38	PC88	0.76	TBA810	1.50
AD130	0.50	BC126	0.09	BC307A	0.10	BF182	0.30	BT108	1.23	R2305/BD222		PCC89	0.65	TBA920Q	1.50
AD140	0.65	BC136	0.12	BC308A	0.12	BF183	0.29	BT109	1.09	SCR957	0.65	PCF80	0.70	TBA990Q	1.50
AD142	0.73	BC137	0.12	BC309	0.14	BF184	0.23	BT116	1.23	TIP31A	0.38	PCF80	0.68	TCA270SQ	1.45
AD143	0.70	BC138	0.21	BC547	0.09	BF185	0.29	BT120	1.23	TIP32A	0.36	PCF81	0.70	TCA270SA	1.45
AD145	0.70	BC139	0.21	BC548	0.11	BF186	0.30	BU105/02	1.50	TIP3055	0.53	PCF82	0.74	TCA1327B	1.00
AD149	0.64	BC140	0.24	BC549	0.11	BF194	0.09	BU105/04	2.00	T1590	0.19	PCL82	0.67		
AD161	0.40	BC141	0.22	BC557	0.11	BF195	0.09	BU126	1.40	T1591	0.19	PCL84	0.75	E.H.T. TRAYS COLOUR	
AD162	0.40	BC142	0.19	BD112	0.39	BF196	0.12	BU205	1.20	TV106	1.09	PCL86	0.78	Pye 731	5.20
AD161	1.00	BC143	0.19	BD113	0.65	BF197	0.10	BU208	1.60			PCL87	0.75	Pye 691/693	4.50
AD162	1.00	BC147	0.07	BD115	0.30	BF198	0.11	BY126	0.09			PCL805	0.75	Decca (large screen)	
AF106	0.42	BC148	0.07	BD116	0.47	BF199	0.14					PLF200	1.00	CS2030/2232/2630/	
AF114	0.23	BC149	0.07	BD124	1.30	BF200	0.28					PL36	0.90	2632/2230/2233/	
AF115	0.22	BC153	0.12	BD131	0.32	BF216	0.12					PL84	0.74	2631	5.00
AF116	0.22	BC154	0.12	BD132	0.34	BF217	0.12	OC22	1.10			PL504	1.10	Philips G8 520/40	5.30
AF117	0.30	BC157	0.10	BD133	0.37	BF218	0.12	OC23	1.30	SPECIAL OFFER		PL509	2.45	Philips 550	5.30
AF118	0.40	BC158	0.11	BD135	0.26	BF219	0.12	OC24	1.30	SL901B	3.50	PY88	0.63	GEC C2110	5.50
AF121	0.33	BC159	0.11	BD136	0.26	BF220	0.12	OC25	1.00	SL917B	5.00	PY500A	1.60	GEC Hybrid CTV	5.10
AF124	0.33	BC160	0.22	BD137	0.26	BF222	0.12	OC26	1.00			PY81/800	0.57	Thorn 3000/3500	5.00
AF125	0.29	BC161	0.22	BD138	0.26	BF221	0.21	OC28	1.00					Thorn 8000	2.42
AF126	0.29	BC167	0.09	BD139	0.40	BF224	0.12	OC35	1.00					Thorn 8500	4.75
AF127	0.29	BC168	0.09	BD140	0.28	BF256	0.37	OC36	0.90					Thorn 9000	5.50
AF139	0.39	BC169C	0.09	BD144	1.39	BF258	0.27	OC38	0.90					GEC TVM 25	2.50
AF151	0.24	BC171	0.08	BD145	0.50	BF259	0.27	OC42	0.45					ITT/KB CVC 5/7/8/9	5.10
								OC44	0.20					RRI (RBM) A823	5.00

All transistors, IC's, offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc. Please add 12 1/2% VAT to all items and overseas at cost P & P U.K. 25p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

TELEVISION SALE DISCOUNT FOR QUANTITY

Please note all mono sets sold as 100% comp. No broken masks, no broken panels etc. Colour sets sold with good c.r.t.s and 100% comp.

Working Mono £3.00 extra. Working Colour £15.00 extra. Supplied in 1's or 100's.

MONO Rotaries 19" & 23"

GEC	£3.00
Thorn 950 etc.	3.00
K.B.	3.00
Pye	3.00
Thorn 1400	4.50

D/S P/B 19" 23"

Thorn 1400	7.00
Bush 161 etc.	7.00
Baird 660 etc.	7.00
Philips 210 etc.	7.00
Pye Olympic etc.	7.00

D/S P/B 20" 24"

Bush	10.00
GEC	10.00
Philips	10.00
Pye	10.00
Thorn	10.00

S/S 20" 24"

Bush 313 etc.	£12.00
Pye 169 chassis	12.00
Thorn 1500	12.00
GEC series 1 & 2	12.00
Decca MS series	12.00

S/S COLOUR

	19"	20"	22"	25"	26"
	£	£	£	£	£
GEC	40	40	40	40	40
Philips	—	—	40	40	40
Thorn	55	—	60	45	65
Korting	—	—	55	—	60
Pye Mechanical	40	—	40	40	40
Pye Varicap	45	—	45	45	45

MAINS DROPPERS

Mono	
Bush 161	60p
Philips 210 30+125+2K85	50p
Philips 210 118R+148R	48p
Thorn 1400	75p
GEC 2018	58p

Decca 2K5+90+100	72p
+167+5	70p
Thorn 1500	

Colour	
Bush A823	72p
Pye 723 27Ω+56Ω	57p
GEC 2110-41Ω	45p
GEC 2110-12R5+12R5	47p
GEC2110-27R5	45p
Thorn 3500	58p
Thorn 8000	58p
Thorn 8500	54p
Philips G8 47R	30p
Philips G8 2.2+68	42p

All plus VAT at 12 1/2%.

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED.

EXPORT COLOUR & MONO T.V.s AVAILABLE READY FOR USE OVERSEAS


TELEVISION

Briarwood House Preston Street
Bradford West Yorkshire BD7 1NS
Tel. Bradford 306018 (STD code 0274)


OTV

If you deal in used Colour TV's and haven't yet paid us a visit, you are missing out on a new development in the trade. We are currently disposing of large regular quantities of *GENUINE PART EXCHANGED TV'S*. Our TV's are not ex-rental and are superior to anything previously available. Whether buying 2 or 200 you will be dazzled by the quality and variety of stock. Our prices are low – we are open all day Monday to Saturday – S/S C TV's tube tested from £30.

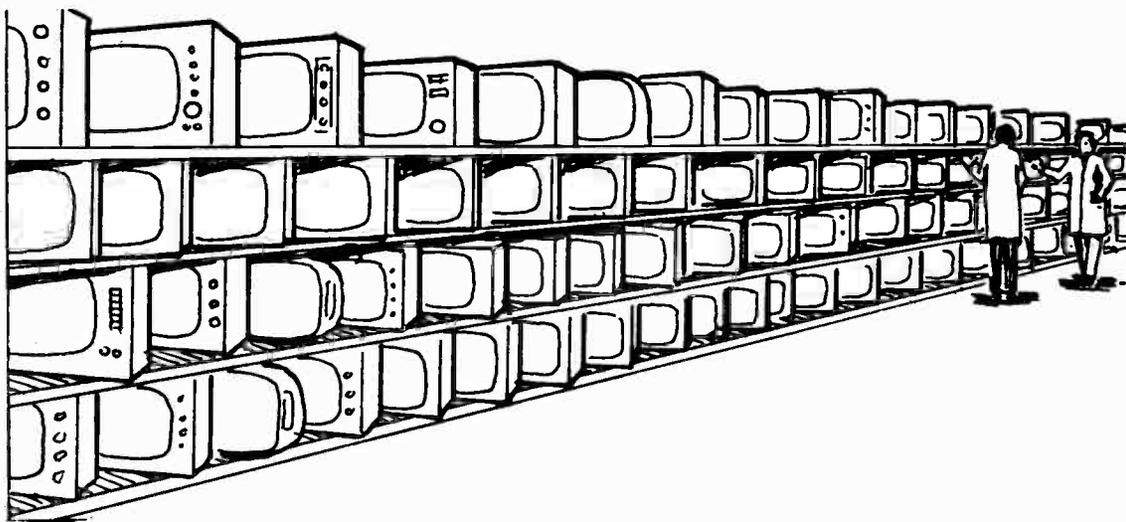**You owe it to yourself to Phone us on 01-985 6111 –
or better still come and see us – YOU WON'T BE
DISAPPOINTED. YOU WILL BE DELIGHTED**



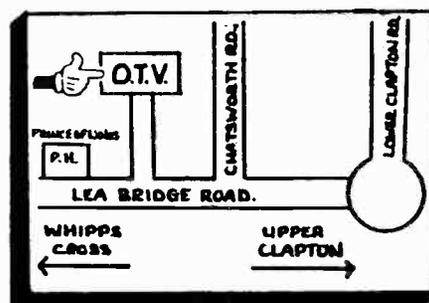**OTV TELEVISION LTD,
144A Lea Bridge Rd, London E5 9RB.
Tel: 01-985 6111/8687 We specialise in Export**



ARE YOU IN THE DARK? ..ABOUT OUR



COLOUR T.V. PANEL EXCHANGE REPAIR SERVICE

FULL RANGE OF
THORN · RBM · PHILIPS
PYE · INVICTA · GEC
DECCA · TELPRO
AND MANY OTHER MAKES

90 DAY GUARANTEE ON ALL REPAIRS
SAME DAY POSTAL SERVICE

We employ a large skilled Staff, who utilise some of the most sophisticated Test equipment available, inclusive of AUTOMATIC FAULT FINDING COMPUTERS together with specially designed SERVICING JIGS which in short means to you --

HIGH QUALITY REPAIRS - AT LOW COST



ONE OFF
OR



100 OFF · NO ORDER TOO
LARGE OR SMALL

SEND FOR PRICE LIST

SEND FOR CATALOGUE

BLOCK DISCOUNTS FOR TRADE CONTRACTS

TO

Campbell Electronics Ltd.

Factory Unit E5, Halesfield 23, Telford Shropshire TF7 4QX
Telephone: Telford (0952) 584373. Ext. 2. Telex 35191 Chamcon


S & R. BREWSTER

LIMITED Ref:TV

86-88 UNION ST.
PLYMOUTH

TELEPHONE
0752-65011

Manufacturers of

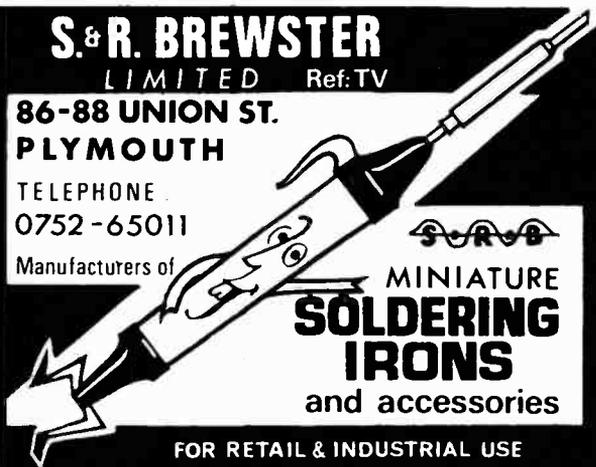

MINIATURE
**SOLDERING
IRONS**
and accessories

FOR RETAIL & INDUSTRIAL USE

QUALITY USED TV'S AT GIVE AWAY PRICES

S.S. MONO FROM £12
D.S. MONO FROM £5
S.S. COLOUR FROM £40
PRICES PLUS V.A.T.

ALL WORKERS, FRESH STOCKS WEEKLY,
QUANTITY DISCOUNTS, DELIVERY ARRANGED.
TRY US YOU WILL NOT BE DISAPPOINTED.

TELETRADERS

We have moved to our new Warehouse where we have much bigger stocks.

St. Leonard's Warehouse, St. Leonard's Road,
Newton Abbott, Devon.
Telephone (0626) 60154

Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs - and they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

City and Guilds Certificates:-

Telecommunications Technicians,
Radio, TV and Electronics Technicians,
Electrical Installation Work,
Technical Communications,
Radio Amateur,
MPT General Radio Communications
Certificate

Diploma Courses:-

Electronic Engineering,
Electrical Engineering,
Computer Engineering,
Radio, TV, Audio Engineering, Servicing and
Maintenance. (inc. Colour TV)
New Self-Build Radio Courses with Free Kits

Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful - at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name

Address.....

..... Phone No:

ICS International Correspondence Schools,
Dept. J285, Intertext House,
LONDON SW8 4UJ. Tel 622 9911


(all hours)

TRANSISTORS, ETC.

Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.48	AU103	2.40	BC192	0.66	BC377	0.29	BD234	0.68	BF222	0.51	BRX29	1.82	MPSU05	0.66
AC117	0.38	AU107	2.76	BC204	0.39	BC394	0.39	BD235	0.63	BF224 & J	0.22	BR101	0.83	MPSU06	0.76
AC126	0.36	AU110	2.40	BC205*	0.39	BC440	0.59	BD236	0.63	BF240	0.32	BR103	0.84	MPSU55	1.26
AC127	0.44	AU113	2.60	BC206*	0.37	BC441	0.59	BD237	0.68	BF241	0.31	BR303	1.06	MPSU56	1.32
AC128	0.46	BC107*	0.16	BC207*	0.39	BC461	0.78	BD238	0.68	BF244*	0.51	BR4443	1.76	MPSU60	0.82
AC128K	0.16	BC108*	0.16	BC208*	0.37	BC477	0.30	BD253	1.58	BF245*	0.43	BRY39	0.60	MPU131	10.59
AC141	0.68	BC109*	0.16	BC209*	0.39	BC478	0.25	BD410	1.65	BF254	0.48	BRYS6	10.44	OC26	1.90
AC141K	0.70	BC113	10.22	BC211*	0.36	BC479	0.33	BD433	0.66	BF255	0.58	BS527	0.92	OC28	1.49
AC142	0.60	BC114	10.22	BC212*	0.17	BC547*	10.13	BD435	0.70	BF256*	0.49	BT106	1.80	OC29	1.60
AC142K	0.65	BC115	10.24	BC212L*	0.17	BC548*	10.13	BD436	0.71	BF257	0.44	BT109	1.99	OC35	1.25
AC151	0.31	BC116*	10.26	BC213*	0.16	BC549*	10.16	BD437	0.74	BF258	0.52	BT116	1.45	OC36	1.25
AC152	0.36	BC117	10.30	BC213L*	0.16	BC550	10.24	BD438	0.75	BF259	0.54	BT119	1.52	OC42	0.90
AC153	0.42	BC118	10.24	BC214*	0.18	BC556	10.23	BD439	0.88	BF262	0.73	BU105	11.80	OC44	0.68
AC153K	0.82	BC119	10.34	BC214L*	0.18	BC557	10.18	BD440	0.88	BF263	0.65	BU105/02	11.85	OC45	0.63
AC154	0.41	BC125*	10.30	BC225*	0.16	BC559*	0.17	BD000	1.23	BF270	0.47	BU108	12.98	OC46	0.63
AC176	0.45	BC126	10.30	BC227*	0.16	BC559*	0.17	BD063BR	0.86	BF272A	0.80	BU126	12.91	OC47	0.73
AC178	0.51	BC132	10.20	BC229*	0.22	BCY30A	1.06	BDX18	1.55	BF273	10.33	BU204	12.60	OC81D	0.95
AC178K	0.51	BC135	10.22	BC238*	0.16	BCY32A	1.19	BDX32	2.95	BF274	10.34	BU205	12.60	OC139	1.30
AC187	0.56	BC135	10.22	BC239*	0.22	BCY34A	1.02	BDY16A	0.63	BF336	0.63	BU206	13.09	OC140	1.35
AC187K	0.65	BC136	10.22	BC252*	0.26	BCY42	1.07	BDY18	1.55	BF337	0.65	BU208	14.88	OC170	0.80
AC188	0.52	BC137	10.30	BC253*	0.38	BCY72	1.02	BDY20	2.29	BF338	0.68	BU407	11.38	OC210	0.80
AC188K	0.61	BC138	10.35	BC261A*	0.28	BD115	1.35	BDY22	2.29	BF339	0.68	BU407	11.38	OC211	0.82
AC193K	0.70	BC140	0.36	BC262A*	0.28	BD123	1.50	BDY28	1.38	BF355	1.07	BU77	2.50	OC270	3.90
AC194K	0.74	BC141	0.44	BC263*	0.26	BD124	1.85	BF115	0.48	BF362	1.04	C106D	0.43	OC271	3.95
ACV17	1.20	BC142	0.35	BC267*	0.20	BD130Y	1.56	BF117	0.45	BF363	1.04	C106F	0.43	OC272	2.40
ACV19	0.95	BC143	0.38	BC268	0.28	BD131	0.58	BF120	0.56	BF367	1.02	C111E	10.46	OC273	2.95
ACV28	0.98	BC147*	10.12	BC268	0.40	BD132	0.68	BF121	0.85	BF451	0.43	D40N1	0.84	OC275	3.95
ACV39	2.02	BC148*	10.12	BC287	0.49	BD133	0.70	BF123	0.48	BF457	0.46	E1222	0.47	OC276	1.98
AD140	1.79	BC149*	10.13	BC291	0.27	BD135	10.37	BF125	0.68	BF458	0.49	E5024	10.19	DN236A	0.94
AD142	1.90	BC152	10.42	BC294	10.37	BD136	10.38	BF127	0.61	BF459	0.52	GTB72	0.46	R2008B	2.92
AD143	1.78	BC153	10.38	BC297	0.36	BD137	0.40	BF137F	0.78	BF594	10.16	MC140	10.36	R2010B	12.79
AD149	1.92	BC154	10.41	BC300	0.62	BD138	0.42	BF152	0.19	BF596	10.17	ME0402	10.18	R2322	10.75
AD161	0.66	BC157*	10.13	BC301	0.38	BD139	0.46	BF158	10.25	BF597	10.27	MF0404/02	10.18	R2323	10.85
AD162	0.71	BC159*	10.12	BC302	0.86	BD140	0.50	BF159	10.26	BF599	10.27	ME6001	10.18	ST2110	0.48
AF114	0.35	BC160	0.62	BC303	0.64	BD144	2.24	BF160	10.20	BF600	10.29	ME6002	10.18	TC140	10.25
AF115	0.35	BC161	0.58	BC304	0.44	BD145	2.76	BF161	10.20	BF601	10.29	MJ2955	1.30	TC141	10.25
AF116	0.41	BC167B	10.15	BC305*	0.17	BD150A*	10.51	BF163	10.63	BF602	10.29	MJ2955	1.30	TC142	10.25
AF117	0.42	BC168B	10.15	BC308*	0.18	BD151	10.90	BF164	10.65	BF603	10.29	MJ3000	1.58	TC143	10.25
AF118	0.38	BC169C	10.15	BC317*	0.15	BD158	0.75	BF167	0.38	BF604	10.29	MJ3000	1.58	TC144	10.25
AF121	0.68	BC170*	10.15	BC318*	0.15	BD159	0.68	BF173	0.35	BF605	10.29	MJE341	0.72	TC145	10.25
AF124	0.38	BC171*	10.15	BC319*	0.19	BD160	2.69	BF177	0.36	BF606	10.29	MJE341	0.72	TC146	10.25
AF125	0.38	BC172*	10.14	BC320	10.17	BD163	0.67	BF178	0.46	BF607	10.29	MJE341	0.72	TC147	10.25
AF126	0.36	BC173*	10.22	BC321A & B	10.18	BD165	0.66	BF179	0.58	BF608	10.29	MJE520	0.85	TC148	10.25
AF127	0.66	BC174A & B	10.28	BC322	10.28	BD166	0.88	BF180	0.63	BF609	10.29	MJE520	0.85	TC149	10.25
AF139	0.58	BC175	10.26	BC323	1.15	BD175	0.90	BF181	0.53	BF613	0.55	MJE520	0.85	TC150	10.25
AF147	0.52	BC176	0.22	BC327	1.16	BD177	0.58	BF182	0.44	BF614	1.02	MJE520	0.85	TC151	10.25
AF149	0.45	BC177*	0.20	BC328	1.18	BD178	0.92	BF183	0.52	BF615	1.02	MJE520	0.85	TC152	10.25
AF178	1.35	BC178*	0.22	BC337	1.17	BD181	1.94	BF184	0.52	BF616	1.02	MJE520	0.85	TC153	10.25
AF179	1.36	BC179*	0.25	BC338	1.17	BD182	2.10	BF185	0.42	BF617	1.02	MJE520	0.85	TC154	10.25
AF180	1.35	BC182L*	10.15	BC340	0.19	BD183	1.34	BF186	0.42	BF618	1.02	MJE520	0.85	TC155	10.25
AF181	1.35	BC182L*	10.15	BC347*	0.17	BD184	2.30	BF194*	0.14	BF619	1.02	MJE520	0.85	TC156	10.25
AF186	1.48	BC183*	10.14	BC348A & B	10.14	BD187	1.20	BF195*	0.13	BF620	1.02	MJE520	0.85	TC157	10.25
AF202	0.27	BC183L*	10.14	BC349B	10.17	BD188	1.25	BF196	0.14	BF621	1.02	MJE520	0.85	TC158	10.25
AF239	0.73	BC184*	10.15	BC350	10.24	BD189	0.91	BF197	10.15	BF622	1.02	MJE520	0.85	TC159	10.25
AF240	1.40	BC184L*	10.15	BC351*	10.22	BD190	0.91	BF198	10.15	BF623	1.02	MJE520	0.85	TC160	10.25
AF279S	0.91	BC185	0.36	BC352A*	10.22	BD225	0.91	BF199	10.29	BF624	1.02	MJE520	0.85	TC161	10.25
AL100	1.30	BC186	0.25	BC360	0.59	BD233	0.62	BF218	10.42	BF625	1.62	MJE520	0.85	TC162	10.25
AL103	1.58	BC187	0.27												

Alternative gain versions available on items marked * For matched pairs add 20p per pair.

LINEAR IC's		DIODES		VDR's, etc. (t)		VALVES (t)		RESISTORS	
Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Carbon Film (%) (t)	Mixes of a minimum of 10pcs of any value:
BRC1330	0.93	AA113	0.17	E295Z	0.60	DY86/87	0.76	1W 5.0-330K (E12)	100pc 1.48
CAB1005	2.44	AA129	0.28	/01	0.28	DY802	0.75	1W 100-10M (E24)	3pc 95p
CA3021	1.45	AA143	0.18	/02	0.28	ECC81	0.78	1W 100-10M (E12)	5pc 45p
CA3014	2.23	AA230	0.28	E298GD	0.25	ECC82	0.95	2W 100-10M (E6)	9pc 90p
CA3018	0.71	AA215	0.42	/A25B	0.25	EF80	0.78		
CA3020	1.89	AA217	0.42	/A25C	0.25	EF80B	0.78		
CA3028A	0.80	AA218	0.42	/A25D	0.25	EF80C	0.78		
CA3028B	1.09	AA219	0.42	/A25E	0.25	EF80D	0.78		
CA3045	2.15	AA220	0.42	/A25F	0.25	EF80E	0.78		
CA3048	0.70	AA221	0.42	/A25G	0.25	EF80F	0.78		
CA3065	1.74	AA222	0.42	/A25H	0.25	EF80G	0.78		
CA3068	1.90	AA223	0.42	/A25I	0.25	EF80H	0.78		
CA3130S	1.57	AA224	0.42	/A25J	0.25	EF80I	0.78		
FC1161	12.40	AA225	0.42	/A25K	0.25	EF80J	0.78		
FCJ101	13.32	AA226	0.42	/A25L	0.25	EF80K	0.78		
LM309K	1.98	AA227	0.42	/A25M	0.25	EF80L	0.78		
LM380N-14	1.65	AA228	0.42	/A25N	0.25	EF80M	0.78		
LM1303N	3.08	AA229	0.42	/A25O	0.25	EF80N	0.78		
MC1307P	11.82	AA230	0.42	/A25P	0.25	EF80P	0.78		
MC1310P*	11.94	AA231	0.42	/A25Q	0.25	EF80Q	0.78		
MC1312P	2.34								

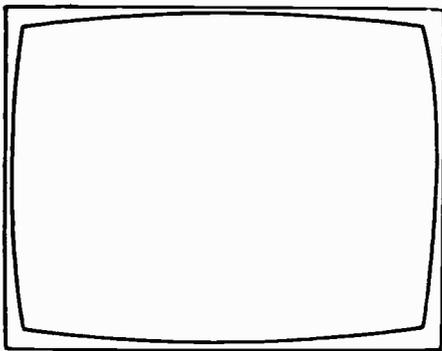

TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTS MANAGER

Roy Smith 01-261 6671

CLASSIFIED ADVERTS

Colin R. Brown 01-261 5762

A Set for the 80s

The UK's largest TV setmaker, Thorn, has a long history of engineering innovation. It's the only major setmaker never to have produced a hybrid colour chassis for a start. With the commencement of colour transmissions in the UK in 1967, Thorn introduced the 2000 chassis, the world's first all solid-state colour chassis. It used a pair of line output transistors that had been developed for radar purposes, another similar transistor for e.h.t. generation, and three jelly-pot transformers. There were separate regulators for the field and line timebase supplies, and an effective excess current trip. It must have been an expensive beast to produce, but was a major step forward when there weren't any large-screen monochrome solid-state sets either.

Single-standard operation came in 1969, when all three networks started transmissions at u.h.f., and from Thorn came the much simpler 3000 chassis. But again there was a major innovation, in the introduction for the first time of a switch-mode power supply in a TV receiver. Service engineers were worried about the strange idea of the chopper, with its variable mark-space ratio drive, chopping away at line frequency and feeding an inductive reservoir. But the system itself behaved very well.

It was not long before Thorn was back on the innovation trail again. June 1971 saw the introduction of the entirely new 17in. (to start with) 8000 series chassis, designed to break through the £200 price barrier for colour TV sets. Thorn had managed once again to reduce circuit complexity substantially. Three i.c.s appeared on the signals panel, a thyristor did the regulating, and out went the tripler, to be replaced by a carefully worked out transformer/half-wave rectifier combination.

In 1974 Thorn introduced the 4000 chassis, with a 110° delta-gun tube. This was intended mainly as an export model, with a decidedly up-market specification. The technical innovations included ultrasonic remote control, touch-tuning with a MOS i.c., and the use of a number of thick-film modules.

The next chassis for the popular market, the 9000, came in 1975. Once again important technical developments put in an appearance. There was the 90° PIL tube with its in-line guns, and the famed Syclops circuit in which a single transistor acts as switch-mode power supply chopper and line output transistor, driving two transformers. It's larger-screen brother, the first European set to use a 26in., 110° PIL tube, followed two years later.

Which brings us to 1979 – and the TX9 chassis just announced by Thorn. It's designed to drive 90° PIL tubes in all sizes from 14 to 20in., and the whole concept has been based on an assessment of what is likely to be a truly competitive chassis internationally in the early 1980s, bearing in mind the intensifying competition from an increasing number of countries. Innovations include the use of a single-chip decoder, a world first so far as PAL decoding is concerned, but the emphasis has been on getting the basic product right rather than on radically new technical departures.

What does this involve? First a neat and compact layout. The importance of this is not for cosmetic reasons, but because it simplifies manufacture, minimises the problems that can arise due to distribution hazards, and makes any servicing required during the life of the set easy to carry out. Thorn's achievement in this respect is quite remarkable, as the photograph on a later page shows – a whole colour chassis on a board measuring only about 10in. by 15in., with a small daughter board for the i.f. strip. This also minimises interconnections and the problems they give rise to. The second basic requirement is good shopping – getting good performance at the right price with assured reliability, on the basis of carefully drawn up specifications.

The TX9 certainly seems to match up to these requirements, and it's interesting to know the origin of "TX9" – 9 for 90°, X because current tubes have an X in their type numbers, and T because the remarkable success of the Model T Ford was kept firmly in mind! The reasoning was that if Ford could produce a reliable product that provided good performance and, at one time, accounted for about half the cars in the world, here was something worth emulating.

There's more to such a success story than getting the product right of course. It has to be sold, and when it comes to exporting today, well, there are few countries indeed with such open and well developed trading conditions as the UK. Getting the product right is nevertheless the essential first step and at a time when it's fashionable, with some justification, to discount much of the UK's manufacturing industry, it's heartening that Thorn have come up with something as fundamentally sound as the TX9. The UK's TV industry at any rate is alive and kicking in these difficult times.

Teletopics

1979 TRADE SHOWS

The main item of TV interest in this year's radio and television trade shows was the introduction of various new chassis, mainly small-screen ones. Some of these are discussed elsewhere in this issue. The new Mullard 20in. tube, the AX51, has put in an appearance in some new Thorn releases using a new version of the 9000 chassis (9900 chassis). Another new tube to appear is the Philips/Mullard 30AX, which Grundig are using in their new Super Colour 80 chassis. The tube has improved focus performance and simplified setting up compared to the 20AX, while the deflection system consumes less power. The small N. Ireland setmaker MAM is understood to be considering the introduction of a 30AX set shortly. One of the few large Japanese setmakers not previously represented in the UK, NEC (Nippon Electric), has appointed a distributor, Laltex and Co., 1 Canal Street, Manchester: the range includes 12, 14, 18 and 20in. colour sets, a 12in. monochrome portable, a 5in. portable with combined a.m./f.m. radio, and a 5½in. portable with a.m./f.m. radio plus cassette tape recorder. Remote control systems were present in abundance, the trend here being towards infra-red systems. A surprise was the re-emergence of projection TV systems for domestic use – at least three are available (Grundig, Mitsubishi, Panasonic) at prices from just under £2,000 to just under £4,000.

Grundig's new modular chassis is unusual in that almost all the components are housed in a group of modules. These have metal casings to provide screening and protection, and have a lead seal which will indicate whether they have received the attention of what Grundig refer to as "unauthorised amateur engineers". To make sure that the authorised, professional engineer does not have too difficult a time however each module incorporates a l.e.d. to indicate whether it is functioning . . . Another purpose of the metal casings is to provide additional large cooling surfaces, the air gaps in them being designed to give a chimney effect.

Another unusual set was shown by Toshiba – the smallest colour set at the shows, the 6in. portable Model C690B. This is 10in. wide, 6½in. high and 12¾in. deep, weighs 15lb, and has a suggested VAT inclusive price of £349.50.

The aim of Philips in introducing their 22in. Model 666 is to bring teletext within the reach of the 600,000 consumers expected to purchase replacement TV sets this year.

THE INTERNATIONAL SCENE

All these new small-screen chassis have not a little to do with the fact that the PAL licensing system expires this October. That will remove all restrictions on the production of PAL colour receivers. A consequence of this is that TV setmakers will be forced to think in terms of international markets. We all know about Japanese competition, but there's more to it than that. Japan is not a cheap country for production purposes, a fact that is reflected in the relatively high price of Japanese sets. In fact Japanese setmakers compete on reliability rather than price. The cheap sets come from elsewhere, from Taiwan, Singapore and South Korea for example.

There are some surprising facts when you come to look into this. For example South Korea, which is expected to produce some 1.3 million colour sets this year, has no colour service (it's expected to start in a couple of years' time). The sets have to go somewhere, which means abroad. This mainly means the USA, but the US government has imposed a quota of 300,000 sets a year. The result of this is excessive stocks – of both monochrome and colour sets – with prices at rock bottom. Yet more Korean firms are planning to enter the field. More countries too for that matter. A TV industry is being established in the Philippines, and plans are being laid to start production in the Argentine. One thing is certain: the TV industry is not going to be a very cosy place in the next decade.

It's one thing to be able to assemble TV chassis however, another to be able to make and check all that goes into them. Here the established manufacturing nations still have the advantage of know-how and technological back-up services. This is one reason why it's always been regarded as essential for the UK to retain its own tube manufacturing capacity.

THE 30AX TUBE

Now that the new Philips/Mullard 30AX tube has put in an appearance, some details can be filled in. The new tube has been developed from the 20AX, which has been in production since 1974, but brings with it several important advances. First, no dynamic convergence, static convergence, purity or raster correction adjustments are necessary. Secondly the new yoke design gives improved deflection sensitivity, a straight NS raster, and reduced EW raster distortion. Due to the close mechanical tolerances and the inclusion of positioning bosses on the tube bowl, the tube and yoke can be aligned simply by being pushed together – any 30AX yoke will automatically match any 30AX tube of the appropriate size. Thirdly the newly designed electron gun gives a sharper spot, with greater focus uniformity over the screen area. An internal magnetic ring is used to give correct purity and static beam convergence, in place of the multipole unit used in previous in-line gun tube designs. This results in a strikingly compact assembly. The automatic yoke/tube alignment does away with the need for preset mechanical tilt and shift adjustments which, Philips point out, correct one error by introducing another. The new tube is being produced in the 26, 22 and 20in. screen sizes. The power consumption of a set fitted with the 30AX is typically 100W compared to 120W with the 20AX system, at 1.2mA beam current and with an e.h.t. of 25kV. This compares with 88W for a set fitted with a 90° narrow-neck tube and hybrid yoke, under the same conditions.

3-D AND HI-FI VIDEO

Philips have been carrying out "considerable research and development" into three-dimensional colour TV at their Eindhoven research laboratories. The practical introduction of such a system is considered to be at least ten years away however. Research is also being carried out on high-definition TV using an increased number of lines. Neither development could be introduced without an agreed change

in broadcasting standards, which seems a rather remote likelihood at present. The capability to produce high-definition equipment is with us now, but Philips point out that it's necessary to be "very careful not to overload the consumer with technology." TCE's director of engineering recently commented that he sees a 1,000-line TV service with stereo sound as a possible development.

NOTIFICATION OF TV SET DISPOSALS

The Television Licensing Organisation, Bristol BS98 1TL, has issued a new simplified version of form BRL1192 which is used by dealers to notify TV set disposals, whether by purchase or rental, to the organisation. The amending regulations authorising use of the new form come into operation on August 1st. The organisation stresses the importance of including the customer's post code on the form - this helps its computer.

STATION OPENINGS

The following relay transmitters are now in operation:

Chingford (East London) BBC-2 ch. 50, Thames/London Weekend Television ch. 52, BBC-1 ch. 56. Receiving aerial group C/D.

Craigellachie (Scotland) BBC-1 ch. 57, Grampian Television ch. 60, BBC-2 ch. 63. Receiving aerial group C/D.

Hasland (Derbyshire) BBC-1 ch. 57, Yorkshire Television ch. 60, BBC-2 ch. 63. Receiving aerial group C/D.

Hemel Hempstead (Herts) BBC-1 ch. 58, Thames/London Weekend Television ch. 61, BBC-2 ch. 64. Receiving aerial group C/D.

Llanwrtyd Wells (Powys) BBC Wales ch. 21, HTV Wales ch. 24, BBC-2 ch. 27. Receiving aerial group A.

Little Stretton (Salop) BBC-1 ch. 57, ATV ch. 60, BBC-2 ch. 63. Receiving aerial group C/D.

All the above transmissions are vertically polarised.

DOMESTIC COLOUR PROJECTION TV

The Panasonic Cinema-Vision colour projection TV system mentioned last month is a one-piece unit - the output from the projection unit, which is in the base of the equipment, is reflected back on to the screen - with a five-foot screen (diagonal measurement). The suggested price is £3,995 including VAT. Two rival systems have since been introduced. The Mitsubishi VS500 is similarly a single-piece unit, with a 50in. screen and a suggested price of around £3,500. The Grundig Cinema 9000 on the other hand has a separate projection unit, a 5ft. screen, and a suggested price of "a little under £2,000". All these sets feature remote control, and both the Grundig and Panasonic models can be used with VCRs and other video sources.

AEROSOL SPRAY REMOVES SCREEN REFLECTIONS

Teleflex have introduced an aerosol spray which can be applied to c.r.t. screens to avoid reflections. The treatment gives the screen a matt finish. There are two cans, one for applying the finish and the other for polishing the glass before and afterwards.

VIDEO EQUIPMENT

Two products of interest have emerged from the JVC factory recently. The HR3330 VHS-format VCR is an improved version of the HR3300. The two look very similar externally, but the new version features a remote pause unit, an eight-day timer and a u.h.f. signal generator to make the tuning of the TV set to the VCR's output easier. The timer

can also be set to record say six thirty-minute editions of a daily serial on consecutive days, on a three-hour cassette.

The other item is a portable VCR system, incorporating the HR4100 VCR, AAP41 mains power unit/battery charger, TU41 timer/tuner unit and a choice of colour cameras, the GC4100 or GY71. The VCR itself is conventional, but has some neat protection arrangements, including excess moisture and low battery warning lights. With the TU41 added, the system can be used as a normal domestic VCR for recording off-air programmes. The GC4100 is a two-tube (one for colour, one for luminance) camera with a 6:1 zoom lens, auto iris control and electronic viewfinder. Colour temperature compensation is available to match the camera to a range of light sources, while additional controls provide for simple white and colour balancing. Extra amplification can be switched in to enable recording to be made at illumination levels as low as 100 lux. The GY71 is a single-tube colour camera which is somewhat cheaper but also incorporates the 6:1 zoom lens, auto iris control and electronic viewfinder. Another version, the G31, has a fixed focus lens and optical viewfinder and sells for around £600. The GS1000 monochrome camera can also be used with the system.

Thorn have now entered the video field, and are marketing the above VCRs under the Ferguson brand name. The basic VCR is known as the Videostar Model 3V00, and the portable version the 3V01. The monochrome camera is type 3V04 and the colour camera type 3V06.

Panasonic have also introduced colour cameras for use with their VHS type VCRs. There are two versions, the WV3310E which has an optical viewfinder, 25mm fixed focus lens and is expected to retail at about £575 excluding VAT, and the WV3300E which has an electronic viewfinder, a 6:1 zoom lens and a price tag of around £770. Both prices include the a.c. adaptor which connects the camera with the recorder.

A new version of the Philips VCR, Model N1702, has been introduced. The new machine is outwardly very similar to the N1700, but features a ten-day timer and a four-digit tape counter to give faster and more accurate access to the recorded material. The new machine will be marketed alongside the existing version. Philips point out that internal developments have resulted in improved picture quality.

Another Philips introduction is the G7000 Videopac Computer. This is a programmable video games unit which in addition has a full alphanumeric keyboard. Some 11 Videopacs are already available, and in addition to quite sophisticated games include a basic course in computing and other instructional material. The G7000 has a suggested price of around £150, with the Videopacs at about £11 each.

SOLUS EXTEND ACTIVITIES

Solus (Electronics) Ltd., well known for their TV picture tubes, have started to distribute discrete active and passive components as well. A well laid out, 48-page catalogue showing the complete range of components, valves and c.r.t.s has been published and is available free of charge to all service departments. There are some 1,500 items, covering the majority of servicing needs. Attractive quantity discounts are offered, the discounts being clearly shown against every part number. There's a nation-wide service, with no delivery or minimum order charges, and twelve representatives have been appointed to call on retail and rental outlets. For a free copy of the catalogue, contact Sheila Roberts at Cambridge (0223) 51502, or write to Solus (Electronics) Ltd., Kirkwood Road, Cambridge, CB4 2PF.

Letters

The subject of green tinting and an intermittently wholly green screen on the ITT hybrid colour chassis has come up in your columns from time to time. On a recent occasion I traced this to a break in the copper track pad at the junction of the green output transistor's collector load resistor R179 and the associated peaking coil L63, resulting in partial disconnection of the transistor. A spot of solder permanently reunited the components and cleared the fault.

G.R. Kay, Epsom, Surrey.

FAULT ROUND-UP

I've recently encountered several TV faults which might be worth setting down for the benefit of other readers of *Television*.

First, the Decca 80 series solid-state colour chassis. A couple of these came to us with the "dead set" symptom and the mains fuse blown. Tests proved that the fuse failure was due to excessive current demand from the power supply circuit, and in both cases this turned out to be the result of a burn up of the print between pins 3 and 4 of socket PLA on the line output panel.

Another Decca solid-state colour set, this time fitted with the 100 chassis, suffered from ringing of the verticals over the top third of the screen. The condition was intermittent and turned out to be due to C310 (4.7 μ F) in the TBA920 line oscillator circuit. Another line oscillator fault on this chassis is failure of the wire-wound resistor R317 in the start-up circuit. When this goes open-circuit, the set appears to be dead.

Sound problems on these sets are generally due to the plug and socket connections (PTU C, to the volume control) on the side of the main chassis. On several occasions I've encountered poor connections between the wires and the pins, causing either no sound, noisy sound or full volume, depending on which wire is affected.

Another chassis I have a fair amount to do with is the Pye solid-state 731 series chassis. One came in because of no results and on examination it was found that whilst a.c. was present at the input to the thyristor mains rectifier there was no d.c. output. An oscilloscope check showed that there were no drive pulses at its gate. This was eventually traced to D901, which had gone short-circuit. This diode is in the pulse timing circuit, and is included to ensure that the negative-going excursions of the mains waveform do not affect the operation of the circuit.

A peculiar effect occurs on these sets when the h.t. reservoir capacitor C880 goes open-circuit. The following smoothing resistor R973 (56 Ω) gets very hot, presumably because of the increased a.c. ripple flowing through it. The fault caused confusion when we first encountered it, as an overload elsewhere in the set was suspected.

I had the same problem with a set fitted with the Rank Z179 chassis - in this case the set was dead, as the resistor (4R104, 27 Ω) had disintegrated. The h.t. reservoir capacitor 4C72 was completely open-circuit. In neither the Pye nor the Rank chassis was there any sign of leakage from these capacitors incidentally.

Returning to the Pye chassis, on another of these sets the thermal link on R555 would open for no apparent reason. This resistor forms part of the smoothing network for the 28V supply, which is obtained from the line output transformer. The cause of the trouble was broken print

around the associated smoothing capacitor C554 (4,700 μ F). On yet another of these sets crackles and pops on the sound were due to both the BD131 audio output transistors.

A Thorn set fitted with the 8800 chassis suffered from intermittent field collapse. The condition was very erratic however and couldn't be brought on by either freezing or heating. It was eventually found that W421/2 were the culprits, though they read all right on a static test. They form part of the discharge path for the field charging capacitor C446 (earlier versions of the chassis use a single diode in this position).

The problem with an ASA Model CT6000A 110° colour set was lack of height with slight field foldover. Any attempt to increase the height would result in severe bottom fold up. This was eventually traced to the 7W feed resistor Rg45 which supplies the field output stage: it had increased in value from 2.7 Ω to 3 Ω . The supply (28.6V) is obtained from the input/commutating transformer in the thyristor line output stage.

Distorted sound was the problem with a Telefunken colour set fitted with the 710 hybrid chassis. It was found that the supply to the audio output transistors was very low, due to the feed resistor R244 reading open-circuit instead of 4.7 Ω . There was no sign of physical damage to this resistor, but replacing it completely cured the trouble.

A favourite fault on the subsequent solid-state 711 chassis is severe blue misconvergence. This often occurs after the set has been moved. The cause is the core dropping out of the sawtooth transformer Tr564.

The later 712 20AX chassis seems to be very reliable. The only problem I've come across is failure of the BU208 line output transistor. A complete new line output panel was fitted, but a few days later the customer complained of a loud bang after which the set went dead. The loud bang was found to be due to C567 (10 μ F) on the line output stage panel exploding. It's connected between the h.t. (163V) input and chassis. A thyristor is used to provide the stabilised 163V rail, and on monitoring this supply we found a steady increase as the set warmed up. A replacement thyristor cured the trouble.

A Telefunken set fitted with the Decca 30 chassis suffered from top compression with a white line across the picture, about a third of the way down the screen. The cause was the PL508 field output valve's cathode bias resistor R413 (560 Ω) going completely open-circuit (there's a d.c. path to chassis via the field convergence circuit).

Mick Dutton, Heath Hayes, Nr. Cannock, Staffs.

DARK SCREEN


We encountered a mysterious fault recently on a NordMende 110° colour receiver (F VI chassis). A normal picture was obtained when the set was switched on, but after about five minutes the screen became dark. The first step of course was to check the c.r.t.'s cathode voltages, which were found to increase from 155V to 198V when the fault condition occurred. The tube base socket was removed and the measurement confirmed, indicating that the fault was in the drive circuitry rather than the tube.

Checking back under the fault condition revealed complete absence of voltage at the bases of the RGB output transistors (the lower ones in these class AB circuits). The drive comes from a TBA530 matrixing i.c., which next came under suspicion. A check at the luminance input pin revealed 2V instead of 1.3V however. Operating the service switch produced a horizontal white line of normal brightness, while the voltage at the TBA530's luminance in-

MANOR SUPPLIES

COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

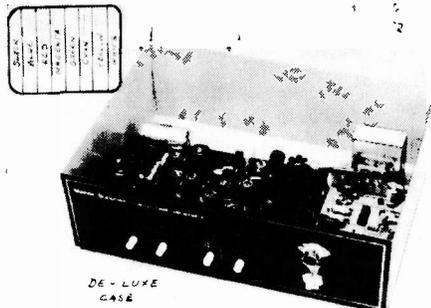

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £37.80 + £1.00 P/Packing. DE-LUXE CASE £5.20. ALUMINIUM CASE £2.80, BATT HOLDERS £1.62, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.20.

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £27.00 + £1.00 p.p. CASE EXTRA £1.70. BATT. HOLDERS £1.62.


- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed.

MK4 DE LUXE (BATTERY) BUILT & TESTED £62.25 + £1.20 P/Packing.

VHF MODULATOR (CH1 to 4) FOR OVERSEAS £3.78
INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.
 (ABOVE PRICES INCLUDE 8% VAT)

MANOR SUPPLIES TELETEXT KIT (incl TEXAS DECODER). Wide range of facilities in colour. External unit. AE input to set. Write or call for further information. See working demonstration model! Easy to build and results guaranteed for every completed unit.

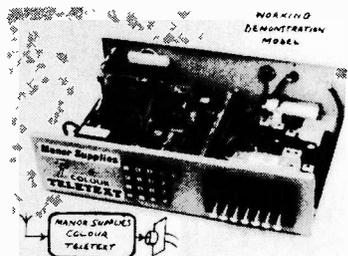Texas XM11 Decoder £146.25 p.p. £1.00.
 Auxiliary Units. £99.00 p.p. £1.50
 De-Luxe Case £16.65 p.p. £1.00.
 Add 12% VAT.
 Prices include 12% VAT
 Separate Price List for Individual Units available.



Changes from "Teletext to picture without switching aeriels.

Armchair control of Teletext and T.V. stations.



15 1/4" x 10" x 3 1/4"

Now available ex stock **NEW MULLARD TELETEXT DECODER MODULE 6101 VML**, complete and tested. Details on request.

COLOUR, UHF & TELEVISION SPARES

NEW 'TELEVISION' COLOUR RECEIVER PROJECT PARTS BEING SUPPLIED. POWER, SIGNAL & TIMEBASE. SEND OR PHONE FOR LIST. WORKING DEMONSTRATION SET NOW ON SHOW.

NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.00 p.p. £1.00.

T.V. PORTABLE PROJECT PARTS AVAILABLE. SEND OR PHONE FOR LIST. WORKING MODEL AT 172 WEST END LANE, NW6.

TV TEST GENERATOR UHF MODULATOR £3.78 p.p. 35p.

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET

£11.88 + 45p. p.p. (ALUM CASE £2.16 p.p. 75p.). COMPLETE TESTED UNITS, READY FOR USE (DE LUXE CASE) £23.54 p.p. £1.00.

ADDITIONAL GREY SCALE KIT £3.13 p.p. 30p.

STAB MAINS POWER SUPPLY FOR ABOVE £5.18 p.p. 75p.

UHF SIGNAL STRENGTH METER KIT £18.14 (ALSO VHF VERSION ALUM CASE £1.65, DE-LUXE CASE £5.18 p.p. £1.00.)

CRT TESTER & REACTIVATOR PROJECT KIT £22.46 p.p. £1.30

"TELEVISION" COLOUR SET PROJECT (1974) SPARE PARTS STILL AVAILABLE. ALTERNATIVE IF COMPL. & TESTED £18.90 p.p. £1.00.

STABILISER UNITS, "add on" kit for either 40V or 20V. £3.15 p.p. 35p.

PHILIPS 210 or 300 Series IF Panels £2.85 p.p. £1.00.

PHILIPS 210, 300 Series Frame T.B. Panels £1.12 p.p. 65p.

PHILIPS 19TG 170 Series Timebase Panels £2.85 p.p. 90p.

BUSH A823 (A807) Decoder Panel £8.45 p.p. £1.00.

BUSH A823 SCAN CONTROL PANEL £2.85 p.p. 75p.

BUSH A823 IF PANEL (EXPORT VERSION) £3.15 p.p. 85p.

BUSH BC6100 IF PANEL (EXPORT VERSION) £5.65 p.p. 75p.

BUSH A816 IF PANEL (SURPLUS) £2.80 p.p. 75p.

BUSH 161 TIMEBASE PANEL A634 £4.28 p.p. 90p.

GEC 2010 SERIES TIMEBASE PANEL £1.12 p.p. 85p.

GEC 2040 Surplus Panels, ex-rental. Decoder £5.65 p.p. 90p.

GEC 2040 Convergence Control Panel £2.80 p.p. 90p.

DECCA CTV25 Single Stand. IF Panel £4.28 p.p. 65p.

DECCA Colour T.V. Thyristor Power Supply. HT, LT etc. £4.28 p.p. 95p.

BUSH TV 300 portable Panel incl. circuit £5.65 p.p. 95p.

BUSH TV 312 IF Panel (Single I.C.) incl. circuit £5.65 p.p. 65p.

BUSH Mains Stabilised Power Supply Unit 6V & 9V. £5.40 p.p. 85p.

BUSH TV Portable Eleven Volt Stab. Power Supply Unit £4.28 p.p. £1.00.

PYE 697 Line T.B. P.C.B. for spares, £1.70 p.p. £1.00.

MULLARD AT1022 Colour Scan Coils £6.75 p.p. £1.20. AT1023/05 Convergence Yoke £2.85 p.p. 85p. AT1025/06 Blue Lat. 85p p.p. 35p. Delay Lines. DL1E £1.00, DL20, DL50 £4.00 p.p. 75p.

PHILIPS G6 single standard convergence panel, inc. 16 controls, switches etc., and circuits £4.25 p.p. 85p. or incl. yoke, £5.65. G8 Decoder panels salvaged £4.25. Decoder panels for spares £2.00 p.p. 85p.

VARICAP, Mullard ELC1043/05 UHF tuner £6.20, G.I. type (equiv. 1043/05) £3.95 p.p. 35p. Control units, 3PSN £1.35, 4PSN £1.70, 5PSN £2.00, Special offer 6PSN £1.70, p.p. 35p. TAA 550 56p p.p. 15p. Salv. UHF varicap tuners £1.70 p.p. 35p.

BUSH "Touch Tune" assembly, incl. circuit £5.65 p.p. 75p.

VARICAP UHF-VHF ELC 2000S £9.60 p.p. 65p.

UHF/625 Tuners, many different types in stock. UHF tuners transisted. incl. s/m drive, £3.20; Mullard 4 position push button £2.80, 6 position push-button £5.00 p.p. 90p. AEISOL 56p p.p. 20p.

TRANSISTORISED 625 IF for T.V., sound, tested, £7.65 p.p. 65p.

PHILIPS 625 IF Panel incl. circuit 56p p.p. 65p.

HELICAL POTS, 100K, 4 for £1.35 p.p. 20p.

RBM 774 250R Mains Droppers, four for £1.12 p.p. 35p.

LINE OUTPUT TRANSFORMERS. New guar. p.p. 85p.

BUSH 145 to 186SS series £7.85

BUSH, MURPHY A816 series £9.60

DECCA DR 121/123,

20/24, MS1 700, 2001, 2401 £7.65

DECCA MS2000, 2400 £6.50

FERG., HMV, MARCONI,

ULTRA 900, 950, Mk. 1 £6.65

950II, 1400, 1500, 1580 £6.65

GEC 2000, 2047 series, etc. £7.65

INDESIT 20/24EGB £7.65

ITT/KB VC2 to 53, 100, 200, 300 £7.65

MURPHY 1910 to 2417 series £7.85

PHILIPS 19TG170, 210, 300 £7.65

PYE 368, 169, 769 series £7.65

PYE 40, 67 series (36 to 55) £7.65

PAM, INVICTA, EKCO,

FERRANTI equivalents as above.

SOBELL 1000 series £7.65

STELLA 1043/2149 £7.65

SPECIAL OFFERS

BUSH TV125 to 139 £3.15

GEC 448/452 £1.70

THORN 1590/1591 £5.40

KB VCI, VCII (003) £3.15

MURPHY 849 to 939 £3.15

COLOUR LOPTS p.p. £1.00.

BUSH CTV 25 Mk3 £9.25

BUSH 182 to 1122 etc. £11.00

MURPHY Equivalents £11.00

DECCA "Bradford"

(state Model No. etc.)... £9.90

GEC 2110 Series £12.00

ITT CVC 5 to 9 £7.65

PYE 691, 693, 697 £20.00

PHILIPS G6 SS or DS £20.00

PHILIPS G8 £9.90

THORN 8500 £12.20

THORN MONO SCAN COILS (850 to 1500) £3.15 p.p. 85p.

THORN 850 Time Base Panel. Dual Standard 56p p.p. 80p.

THORN 950 3 Stick Tray £2.25 p.p. 50p. Others Available.

6-3V CRT Boost Transformers £3.60 p.p. 75p., Auto type £2.00 p.p. 45p.

CALLERS WELCOME AT SHOP PREMISES (Tel: 01-794-8751)

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE NOT NORMALLY ADVERTISED

MANOR SUPPLIES
172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Bakerloo & Jubilee)
 W. Hampstead British Rail Stn. (Richmond, Broad St., Barking)
 (St. Pancras, Bedford) Bus Routes 28, 159

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.
 ALL PRICES INCLUDE VAT AT 8% OR 12%

**QUARTZ LCD
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

**QUARTZ LCD
7 Function**

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOP WATCH.

£9.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M2

**QUARTZ LCD
11 Function SLIM CHRONO**

6 digit, 11 functions. Hours, mins., secs., day, date, week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£12.65 Thousands sold!

Guaranteed same day despatch.



M3

**QUARTZ LCD
ALARM 6 Function**

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

**QUARTZ LCD
ALARM 7 Function**

Hours, mins., secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

£15.95

Guaranteed same day despatch.



M5

QUARTZ LCD Alarm Chronograph with Dual Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£22.65



M6

SOLAR QUARTZ LCD Chronograph with Alarm Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£25.65



SOL M7

QUARTZ LCD Alarm Chrono

22 function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

£22.65

Guaranteed same day despatch.

METAC ★ PRICE



M8

SOLAR QUARTZ LCD Chronograph

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins. Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

£13.95



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass. List Price £130.00

**METAC PRICE
£105.00**



M10

SEIKO Chronograph

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap time. Back light, stainless steel water resistant, HARDLEX glass. List Price £85.00

**METAC PRICE
£68.00**



M11

SOLAR QUARTZ LCD 5 Function

Genuine Solar. Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.


£8.95

Guaranteed same day despatch.



M12

**HANIMEX
Electronic
LED Alarm Clock**

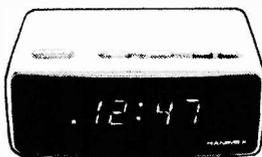

Features and Specification. Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatably 9 minute snooze. Display bright/dim modes control. Size 5 15" x 3 93" x 2 36" (131mm x 111mm x 60mm) Weight 1.43 lbs (0.65 kg). AC power 220V.

£9.65 Thousands sold!

Guaranteed same day despatch.

M13

QUARTZ LCD Ladies Slim Bracelet

5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£15.95

Guaranteed same day despatch.



M14

QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.


£9.95

Guaranteed same day despatch.



M15

DIGITAL LED CLOCK

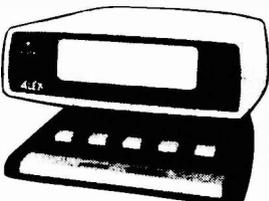

Automatic brightness control. Weekend alarm cancel.

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on-off control. Display flashing for power loss indicator. Repeatably 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

£10.95

Guaranteed same day despatch.

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT

Trade enquiries: Send for a complete list of trade prices - minimum order value £100.
Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.

CALLERS WELCOME
Shops open 9.30 - 6.00.

Metac ELECTRONICS & TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

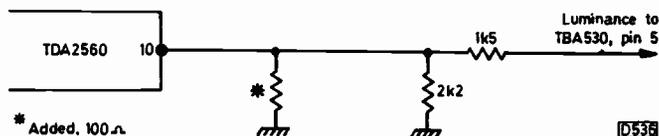


Fig. 1: Dr. Karailiev's method of stabilising the luminance output from the TDA2560 i.c.

put pin fell to 1.4V. So it was back to the TDA2560 luminance/chrominance signal processing i.c. The luminance input to this i.c. comes from an emitter-follower and was found to be correct, so the remaining thing to do was to try a replacement TDA2560. This is not available here at present however, so instead we decided to try connecting a 100Ω resistor from its luminance output pin (10) to chassis (see Fig. 1). This resulted in a first class picture.

Dr. A.M. Karailiev, Senior Lecturer, College of Science and Technology, Port Harcourt, Nigeria.

Editorial note: The NordMende F VI chassis is also used in the Ferguson 3787 14in. portable. The output from pin 10 of the TDA2560 comes from an integrated emitter-follower. The added 100Ω resistor will increase the emitter-follower's collector current, a dodge that can work when the trouble is due to a leaky transistor.

FUSIBLES AND SUCHLIKE

How is Les getting on with Mr. and Mrs. Black (April issue)? You see, the sequence of events leading to all three RGB output stage collector load resistors springing open is (1) the h.t. rises (check 8R6, the diac 8D3 and thyristor 8THY1), (2) the e.h.t. rises and the line timebase is shut down by the overvoltage trip, removing the clamp pulse so that the RGB output transistors are bottomed, when (3) the load resistors go ping, ping, ping.

Another odd 'un on this chassis is when the 600mA h.t. fuse 8F3 is found open-circuit but only normal current is drawn when the fuse is bridged by the Avo meter on its 1A range. The giveaway here is to look for flyback lines, which indicate faults in 4VT1/2 on the c.r.t. base panel. The cause is no beam limiter action, with 8F3 opening on a peak white raster.

Finally a fuse fault on the newer Rank T20/22 chassis. This time when the mains fuse 7FS2 is found blackened and the set dead. Again the meter shows that all is well, but in fact the posistor 7TH1 in the degaussing circuit goes short-circuit intermittently. Replacement is the only cure.

I could think of many more oddities on Rank chassis, like low height (1½in.) on the Z718 chassis, all diodes in the field timebase measure o.k. when checked cold, but one is faulty. Or the flyback blanking diode (on the signal panel) which produces a picture edge like the Himalayas though the raster is o.k.

Tony Thompson, Coventry.

MAINS FILTER CAPACITORS

As a self-confessed chopper-out of mains filter capacitors I would like to comment on the letter in the March issue. My reason for not fitting replacements is quite simply that I've never been able to find capacitors that are sufficiently reliable when used in this position - 1kV d.c. working seems to be the highest voltage rating available. In my experience these are quite inadequate, surviving at best only a month or two. If one's conscience shrinks from actually omitting the filter capacitor, I've found that using a lower-value replacement is often successful.

Regarding 13A plugs and 3kW heaters (*Teletopics*, March), I've never been able to find 13A plugs and sockets

which are able to supply 3kW for any length of time without overheating - many indeed are hard pressed at 2kW. A light smear of silicone grease on the plug pins is helpful however. W.G. Williamson, Yell, Shetland.

Editorial comment: Polypropylene capacitors of suitable value rated at 1.25kV d.c., 400V a.c., are available, for example in the RS Components range, and are recommended as replacement mains filter capacitors.

PURITY PROBLEM

We had purity trouble on a Hitachi Model CAP160 and eventually discovered that this was due to lack of degaussing as a result of the somewhat unusual mains switching system employed. When the power on/off switch is switched on, the c.r.t. is preheated to give an instant picture once the pull on/push off switch associated with the volume control is operated. It's worth noting that the degaussing circuit operates when the receiver is switched off, but that this action does not occur if the mains supply is completely removed by the power on/off (or wall) switch. A dramatically improved picture has been obtained since we realised that for the degaussing action to occur the mains must be left connected after the push-pull switch has been operated.

H. Gregory, Blackpool, Lancashire.

COLOUR RECEIVER RENOVATIONS

In reply to the letters in the April issue commenting on my article on renovating colour receivers, Mr. Charles is quite correct in pointing out that there is another path for the PL802's control grid current on the Pye hybrid colour chassis other than via the 4.7MΩ resistor R352. This was an oversight on my part. The case for reducing the value of the PCL84 colour-difference output valves' grid leak resistors still applies however - it's been proved to increase the reliability of the CDA stages in both the Pye and GEC hybrids we've modified in this way.

Regarding Mr. Coles' remarks on the G6 colour-killer, there are actually two a.c.c. systems on this chassis. One works in the conventional way, using a single diode to rectify the burst, producing a negative voltage which is applied to the control grid of the EF183 first chroma amplifier valve. The other system employs a phase detector circuit which is similar to the burst phase detector except that it produces a positive output when the reference oscillator is phase locked to the burst. This positive voltage is amplified by one section of the PCC85 double-triode valve, the resulting negative-going output being again applied to the control grid of the EF183.

I've always found it easier to pull out the PCC85, and indeed to anyone unfamiliar with the chassis this is easier than locating other components on the layout diagram. Only the phase-dependent a.c.c. is disabled by this action - the burst amplitude is at maximum, and cannot be increased by turning down the colour control. If there are no faults present, this should give a slightly over-saturated display. I've never found this a disadvantage when setting up the a.p.c. loop, particularly as the a.c.c. system that's been disabled comes into action only when the reference oscillator has been finally locked.

Also, when the delay line output is shorted out (simple PAL) the saturation is reduced by half. The G6's valve chroma amplifiers are very linear, so that if the blinds on a very saturated display are cancelled out the adjustment still holds good at normal saturation levels. Most G6 decoders are in such a state of misalignment that they can only be improved.

Mike Phelan, Holmfirth, Yorkshire.

Practical UHF Preamplifiers

Roger Bunney

THE UK's u.h.f. transmitter network has grown dramatically in recent years. Phase I, in which all communities of more than 1,000 people are within the service area of a main or a relay transmitter, is now nearing completion, and Phase II, in which communities of 500-1,000 will be similarly served, has now been started. There are nevertheless still vast numbers of sites in fringe areas or where reception is inferior due to screening by local obstructions (hills, valley locations, etc.) even though they are within an accepted service area. There is a continuing need therefore for medium-gain, low-noise signal preamplifiers to improve the reception quality under such conditions, and in fact a steady stream of enquiries for details of such amplifiers is received by the magazine.

The needs of such viewers were the first consideration behind the present article, leading to a wideband amplifier design. For many readers however the main requirement is an alternative programme source on a specific channel, usually from a neighbouring ITV area. For this application a narrow-band amplifier is required, and the basic design was modified accordingly.

Selected Transistor

The transistor selected was the SGS/ATES BF679S, a silicon planar pnp device which is supplied in a T-plastic package. It's a low-current device featuring a low-noise performance with a relatively high stage gain. The SGS/ATES data sheet quotes a typical power gain of 15dB at 800MHz,

and a typical noise figure at the same frequency of 3.5dB. Optimum gain is obtained when the collector current is in the range 2.5-4mA.

Wideband Circuit

The wideband circuit adopted is shown in Fig. 1. The transistor is operated in the common-base mode, the base being biased by the potential divider R3/R2, decoupled at r.f. by C5, while the emitter is biased by R1, decoupled by C4, L1 being a stand-off choke. The signal is coupled to the emitter of Tr1 by C1, with C2 providing a degree of noise matching. L2 forms the collector load, with the supply end decoupled by C6. The signal is tapped off to the 75Ω output by C3, which is soldered close to the earthy end of L2.

With the 9V supply, the current consumption of both versions of the amplifier is 3mA.


The wideband circuit was built up and once the adjustment of the output coil L2 was completed a good gain/bandwidth performance was obtained. For group A operation, 2½ turns were sufficient for L2, which was tapped at half a turn from the dead end. The coil was made using the single inner conductor from low-loss coaxial cable. To adjust for optimum frequency coverage, spread or compress the turns. This adjustment must be done with care in order to avoid damaging the transistor's lead-out connection. For group B/C, 1¼ turns should be sufficient, adjusted as before.

The value of the input noise matching capacitor C2 should be below 5pF, typically 3pF. The optimum value can be found by experiment. A low-loss miniature preset could be used, provided the lead inductance can be severely minimised.

Single-channel Version

For the narrow-band (single-channel) version the basic circuit was modified to that shown in Fig. 2. The transistor's biasing conditions remain the same, but bandpass tuning is used at the input and output. The input tuned circuit consists of L3 and the trimmer C7 – with L3 actually the inner conductor of the input coaxial socket. Noise matching is again provided by C2, which in the ch. 23 prototype was found to have an optimum value of 3.9pF. The transistor's collector circuit is tuned to resonance by the trimmer C8, and the channel peaking adjustment of this is extremely sharp.

Both C7 and C8 have to be adjusted to set up the amplifier. The tuning of C7 is rather flat, whereas C8 is by comparison critically sharp. Alignment is best carried out using a field strength meter. Alternatively a TV set can be used, but the a.g.c. action must be minimised in order to reduce the masking effect of the a.g.c. on the signal displayed on the screen. If a strong local signal is present on an adjacent channel, correct alignment on the weak wanted signal should discriminate against breakthrough by the local one. With incorrect peaking under these conditions, you are

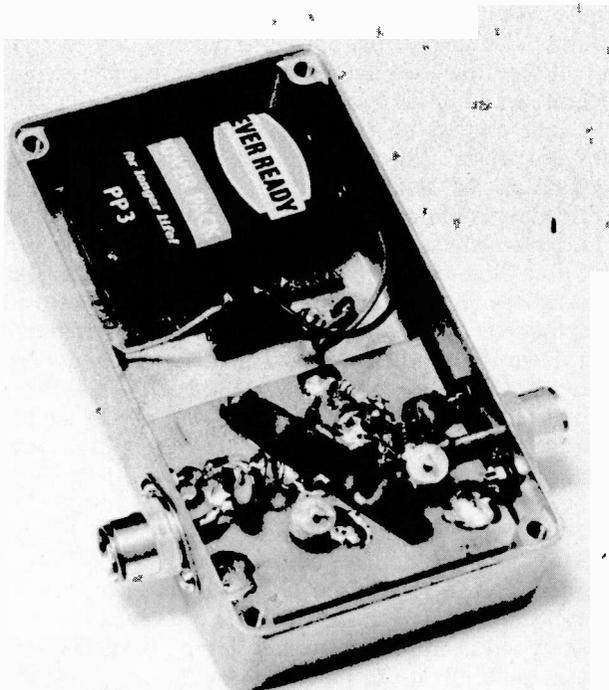

Internal view of the narrow band version of the preamplifier.

Only in Dreams . . .

Les Lawry-Johns

WEARILY I clambered up the graceful curve of the Spit's port mainplane, once again to wedge myself in the tiny cockpit, to clunk-click the straps, and to prepare for the ordeal to come. I looked down on the strained and anxious faces of my faithful fitter and rigger, Fred and Reg, who had kept the Spit serviceable through the long months to enable this one plane, with its one pilot, to hold off the entire enemy air force by night and by day. I was feeling a bit groggy, after six months without sleep . . . Alone to keep the skies clear until replacements could be built and pilots trained to take my place.

"Be careful sir" shouted Fred. "They'll be coming at you out of the moon." My haggard face managed a ghost of a smile as I pulled up the side of the cockpit cover and pressed the starter. The sharp bark of the Koffman cartridge preceded the clatter of the Merlin as it burst into life in the early morning air, and the March Hares sat up in silence around the airfield perimeter, sole witnesses to what could well be the last act of the drama, their ears providing V signs of encouragement.

"Chocks away chaps."

"Chocks away sir, and good hunting. Oh God. He can't, he just can't. But of course . . . he must".

My headphones crackled into life. Dorniers over Dover, Junkers over Jarrow, Messerschmitts over Manchester. I pushed the throttle forward and the tiny aircraft raced across the grass. Make sure the guns are working. I gave the eight Brownings a quick burst, and the Vs disappeared from the March Hares' heads. No more for them the battle's noise. The engine screamed and the tail lifted . . . Screamed.

"Wake up, wake up. You're tearing the bed to bits. What dream is it this time?"

This was to be my reward then. To be rudely awakened by an unsympathetic spouse who knew and cared nothing about my valiant efforts to save our blessed island home.

I lay there reflecting for a while, the battle of the skies receding as I remembered what I'd done the previous day to my precious test cassettes, all carefully recorded. Correction. They had been carefully recorded until I'd left that open-wound transformer next to them while testing some audio stuff. For the life of me I couldn't find the reason for the loss of playback on the next cassette to be tested. I really must learn to be careful and logical like all those other chaps are . . .

Came the Day

Some outside calls to make. Mrs. Acorn was first.

"I'm on the third floor, this end. The lift's at the far end."

Might just as well nip up the stairs at this end rather than drag all the way along to the lift carrying this lot and then drag all the way back again once I get up there and repeat the process on the way back.

So we danced up the first flight and then up the next to the first floor. Nip smartly up the next flight and round up the next to the second floor. Funny, it says first floor on the board. The first two flights had been up to the ground floor . . . Plod up the next two flights to the second floor. The boxes now weighed a ton and my legs felt a bit rubbery. Stagger up the next flight

and then the final seven steps which seemed like seventy. It was worse than this when we climbed Everest the first time though. But not a lot worse. At least we (the boxes and I) arrived at No. 49.

Mrs. Acorn was the chatty, worrying type, always thinking up reasons for doom and disaster and discussing them at great length to no real purpose.

"The set's in here. Do you think it's finished? I've had it only a couple of years. It should last longer than that, shouldn't it? Doesn't seem fair. The vacuum cleaner was the same. It all happens at once, and I do miss the telly. Half way through Cross Roads. I'm frightened to touch it myself. Always have been afraid of electricity, but I don't suppose you are. Neither was my husband, and he's dead."

By this time I'd reached the set. A 20in. monochrome one with a solid wood case. Unfamiliar. Unitra. Oh dear.

Back off, juice on and present at h.t. points. No heaters alight. Where's the dropper? Swing down chassis. Thermistor and large wirewound behind the e.h.t. compartment, upper right side.

Wirewound intact. Chase along to PY800. Open-circuit. Should have been a PY88 (PY800 19V heater, PY88 30V heater). Fit new PY88.

Heaters now alight, hissy sound. Aerial out of wall socket. Insert plug. No better. Redress plugs at both ends. Sound clear, but no raster yet.

Narrow picture slowly expanding after extended wait. Lazy PL504. Fit new one. Full picture now, but expanding when brilliance advanced. DY802 e.h.t. rectifier glowing o.k., but suspect low emission. DY802 not a DY802 but an EY86, with four turns on the heater winding. Look in vain for an EY86. Refit old one and promise to return later with replacement.

"Can I use it? It won't blow up, will it? Perhaps I'd better not have it on, but it's all I have and I do want to see the World at One."

"It's all right Mrs. Acorn. It's just that the picture gets bigger when it's bright, and I'll be back later anyway to stop that caper."

"All right, I'll get my little radio out, and you can do that for me, as well when you come back, and perhaps you could have a quick look at the cleaner as well."

I fled.

Ekco, Ekco

They never come in singles, and it's a constant source of surprise that if you get a fault on one type of set the next one will be identical. After this you may go months before encountering the same fault again, even though the same type of set is met regularly but with different defects.

Next we had a 26in. Ekco colour set (Pye group hybrid chassis) which was a little too big for the customer to bring in. Symptom: sound, no picture. No valves heating. Whip out the PY500: open-circuit heater. Whip out the PL509: open-circuit heater. Check for shorts, none until PY500 refitted — it had a heater-cathode short of course, and since the PY500 is the second valve in the heater chain the first heater (PL509) is

also dealt a mortal blow. Extract new valves from spares box, fit, and ensure that all is well before departing. The following call required exactly the same performance, with the result that we are now out of PL504s and PY500s.

And of Course

The last call was a little way out in the sticks. Ringing the door bell produced a loud barking by way of response. The door was opened by a friendly lady and the largest Old English Sheepdog I have ever seen. As far as his face was concerned, all that could be seen other than fur was a black nose. His feet were the size of dinner plates. More like a Yeti than a dog. He was friendly though. Even though he had no tail to wag, his rear end sort of undulated to show his pleasure.

"Get out of the way Saxon, you big slob" said Mrs. Norman.

We made our way to where the sick set stood. A large Philips G6. I was suddenly aware of what was not in the spares box.

I put the tool box down and grappled with the G6 to move it out. At the same time Saxon decided to sit on the tool box and I think he looked at me although I couldn't be sure. I then had to grapple with him to get him off the box, and he thought this was great fun and was in no hurry to give up his seat. Eventually I grabbed the box and got out the 4BA nut spinner to remove the rear cover of the set. Saxon was a great help, and did his best to distribute all the tools on the floor just in case I needed them.

With the set on, all the valves glowed and there was h.t. to the top caps of the PL509 and PY500 but no pulse voltage, the PL509 remaining cool. Check its screen feed resistor. Easier said than done on these sets. It proved to be open-circuit. The spares were out in the van.

"I'm going out to get a couple of bits and pieces. Are you coming?" I asked Saxon. He didn't need second asking and was ahead of me to the front door. Out we went to get the wirewound and the iron. Saxon jumped into the van and settled down comfortably.

"Come out you daft bugger, we haven't repaired the set yet." He didn't argue, and amiably followed me back into the house.

Now putting a new wirewound under the PL509 and PY500 valve bases is no joke, and as I wasn't inclined to put the set on its side I had to adopt a rather uncomfortable posture in order to solder the thing in. The trouble was that Saxon wanted to see what was going on as well, which made our heads too close for comfort, particularly since his was twice the size of mine and took up far too much space. Mrs. Norman came to my aid and dragged away my helper.


Eventually the resistor was in, and as there were no shorts present we tried the set, desperately hoping the PL509 was not going to play tricks. The resultant picture was quite pleasant, but rather soft and tinted due to the age of the tube precluding an accurate grey scale. I prepared to depart and the final pleasantries were being exchanged.

"The picture's gone off" said Mrs. Norman. Back to square one, with the wirewound overheating sufficient to melt the solder. The PL509 was faulty after all.

"Sorry Mrs. Norman, I'll have to pop back later. It needs something I had when I started out but haven't got now. See you later Saxon."

Visit from a Reader

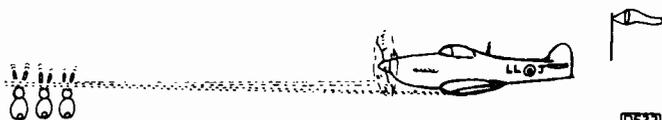Back at the ranch we had a few bits and pieces to clear up before we could return to the scene of the uncompleted jobs. I'd just accidentally managed to short the base and collector



0532

A quick burst from the Brownings . . .

of a regulator transistor in a reel-to-reel tape recorder, thereby returning us to exactly the same condition as when we had started (worse, as we now had no MJE3055: the last one had been the last one), when a couple of very nice people came into the shop to make themselves known as regular readers (she as well as he). As I say they were very nice people, but there was one odd thing: he was wearing a fur collar, not her.

"We thought we'd pop in to say hullo and just to make sure that you really do have a dog and a cat that do funny things."

"Oh yes. They're here all right. There's Spock, and the nose round the corner is Ben."

At that moment I took another look at the fur collar and it yawned at me. It was a dog. "She was getting tired you see." The dog was elegantly draped around his neck and for all the world looked like a fur collar. What a lovely lot of daft readers we do have.

Came the Night

We had discharged our responsibilities to the letter, and had recharged our batteries at Harold's hostelry before retiring for the night, the better to slumber rather than lie fretting into the early hours . . .

It was a freezing cold morning as day dawned. The lone Swordfish stood, ungainly as ever, freshly loaded with its single torpedo, and only one occupant instead of three.

Lt.-Commander Prangham-Wright nodded to me briefly as I clambered up the lower port mainplane, the starting handle in my icy hand.

"The entire enemy fleet is proceeding up through the straits — two carriers, two battleships, four cruisers and ten destroyers. They must not be allowed to get through, or all is lost. Not one. I must press home my attack with the utmost despatch."

"But this is our last aircraft sir, and that's the last torpedo" I stammered, at a loss to see how he could sink the lot in one go.

"No one knows that better than I" said the intrepid naval officer. "I've had the armourers up all night specially hardening the warhead so that it'll penetrate anything up to nineteen ships and explode on impact with the last — just in case they have a supply ship tucked away. All I've got to do is to get 'em in line and dive the old stringbag at 100 knots at the first one and the lot will go down *wham!*" What a wonderful man. What ingenuity. What courage. No wonder he had the D.S.O. and scar.

"Right Les, wind her up and we'll get going."

Standing on the leading edge of the mainplane, I inserted the handle into the socket behind the engine and commenced the winding up process. Slowly my frozen hands rotated the handle to get the flywheel moving, then faster and ever faster until the flywheel was up to speed. "Switches on." "Switches on." I removed the handle and pulled the ring which would bring the spinning flywheel into marriage with the engine. Clatter, clatter, clatter. The big three-bladed airscrew turned and stopped as the engine coughed and died.

"You bloody fool, you didn't get her up to speed. Do it again" bawled Prangham-Wright. "And this time put some backbone into it."

Wearily I reinserted the handle, and with aching muscles started to wind her up again. Faster and faster, faster and faster. The flywheel was screaming, screaming . . .

The New Colour Chassis

It has not for many years been such an interesting time in the TV receiver industry. All of a sudden, every setmaker has introduced a new colour receiver chassis. There are two basic reasons for this. First, an expected substantial increase in the sales of smaller-screen colour receivers, and secondly a more settled situation in the tube field. The latter is of interest, since it seems not so long since that a growing number of incompatible tube systems were being offered to setmakers. The present situation is that the 110° PIL and 20AX tubes have come to be accepted for use in larger-screen (22 and 26in.) models, while for use in smaller-screen (14-20in.) sets the 90° PIL type of tube has been generally adopted. So we find that every setmaker now feels it necessary to have a smaller-screen chassis designed to drive a tube of the 90° PIL variety. Amongst the new chassis are the ITT CVC40 and CVC45/1, the Decca 70 series chassis, the Pye/Philips KT3 chassis and the Thorn TX9 chassis. The purpose of this article is to survey the technical features of these new chassis.

You might think that given a common requirement, to drive a 90° thin-grid tube using a saddle-toroidal (line/field) deflection yoke, setmakers would come up with much the same solutions. After all, car manufacturers seem to come up with remarkably similar products for various sections of the market. The TV industry never seems to have worked in this way however, and the new chassis present some interesting contrasts in design approach. In fact there are only three circuit features common to all these chassis, the use of a bridge rectifier in the mains input circuit, the use of the Mullard U321 tuner unit, and the use of a TDA2540 in the i.f. strip. The latter device incorporates a three-stage i.f. amplifier with a.g.c. applied to each stage, synchronous vision and a.f.c. demodulators, a gated a.g.c. system, a white-spot inverter and video preamplifier. Areas of contrast include whether or not to use a switch-mode power supply linked to the line timebase, the extent to which i.c.s have been adopted, and whether to use single chassis or modular construction.

ITT CVC40 and CVC45/1 Chassis

The first of these chassis to come along, the ITT CVC40, was introduced late last year. The original version was fitted with a 16in. tube and the power consumption under normal operating conditions was down to 65W. The subsequent CVC45/1 is fitted with a 20in. tube and has the same average consumption though a slightly higher consumption (90W) at maximum brightness. The figure of 90W compares very favourably with the 150W consumption of the previous CVC20 chassis at maximum beam current.

The CVC40 was evolved from the CVC20, using the same modular chassis approach and the same Mullard three-chip decoder (TBA560C/TBA540/TCA800) with class A RGB output stages. There are substantial differences elsewhere however.

First, the switch-mode power supply also drives the BU208 line output transistor. The idea is shown in Fig. 1. A series chopper transistor is used, and the line output transistor obtains its base drive from a secondary winding

on the chopper's inductive reservoir. The line oscillator is contained within the well-established TBA920 sync/line generator i.c., the line drive from this being fed to a relatively simple discrete component switch-mode power supply control circuit. A feature of the line output stage is the use of a diode-split line output transformer to provide the e.h.t. while the EW modulator drives a transducer which is connected in series with the line scan coils. The field timebase uses discrete circuitry throughout, with a class B output stage.

On the signals side, the TDA2540 i.f. i.c. is preceded by a surface acoustic wave filter (SAWF) which forms the i.f. bandpass response. This is in turn preceded by a two-stage wideband transistor amplifier to make up for the SAWF's insertion loss. There are separate intercarrier sound (TBA120U) and audio (TDA2611A) i.c.s.

The main difference between the CVC40 and the CVC45/1 is that the latter employs a conventional line output transformer with a separate tripler to provide the e.h.t.

Pye/Philips KT3 Chassis

The Pye/Philips KT3 chassis has some things in common with the ITT chassis, in particular the use of modular construction. Perhaps we should put this down to the continental approach to TV receiver design. There's also a series chopper which again also provides the drive to the line output transistor. At this point however a couple of rather interesting i.c.s come into the picture, the TDA2581 and TDA2571, which are designed as a matched pair for switch-mode driven line deflection circuits. Each i.c. contains an oscillator, the TDA2571's oscillator operating at twice line frequency (31.250kHz) while the TDA2581's oscillator operates at 15.625kHz. The idea is that the TDA2571 provides timebase synchronisation while the TDA2581 controls the switch-mode power supply. The block diagrams (Fig. 2 and 3) indicate the functions of each. The TDA2571 is particularly interesting in containing a 625:1 divider to obtain a field sync pulse from the line sync pulses. It incorporates a field sync pulse separator as well,

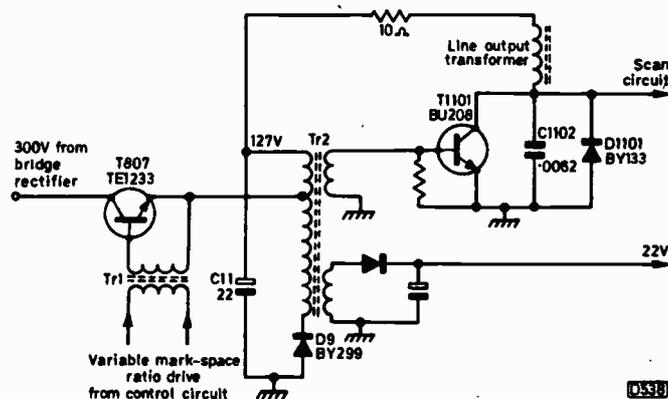


Fig. 1: Simplified circuit showing the way in which the line output transistor obtains its drive from the switch-mode power supply in the ITT CVC40 chassis.

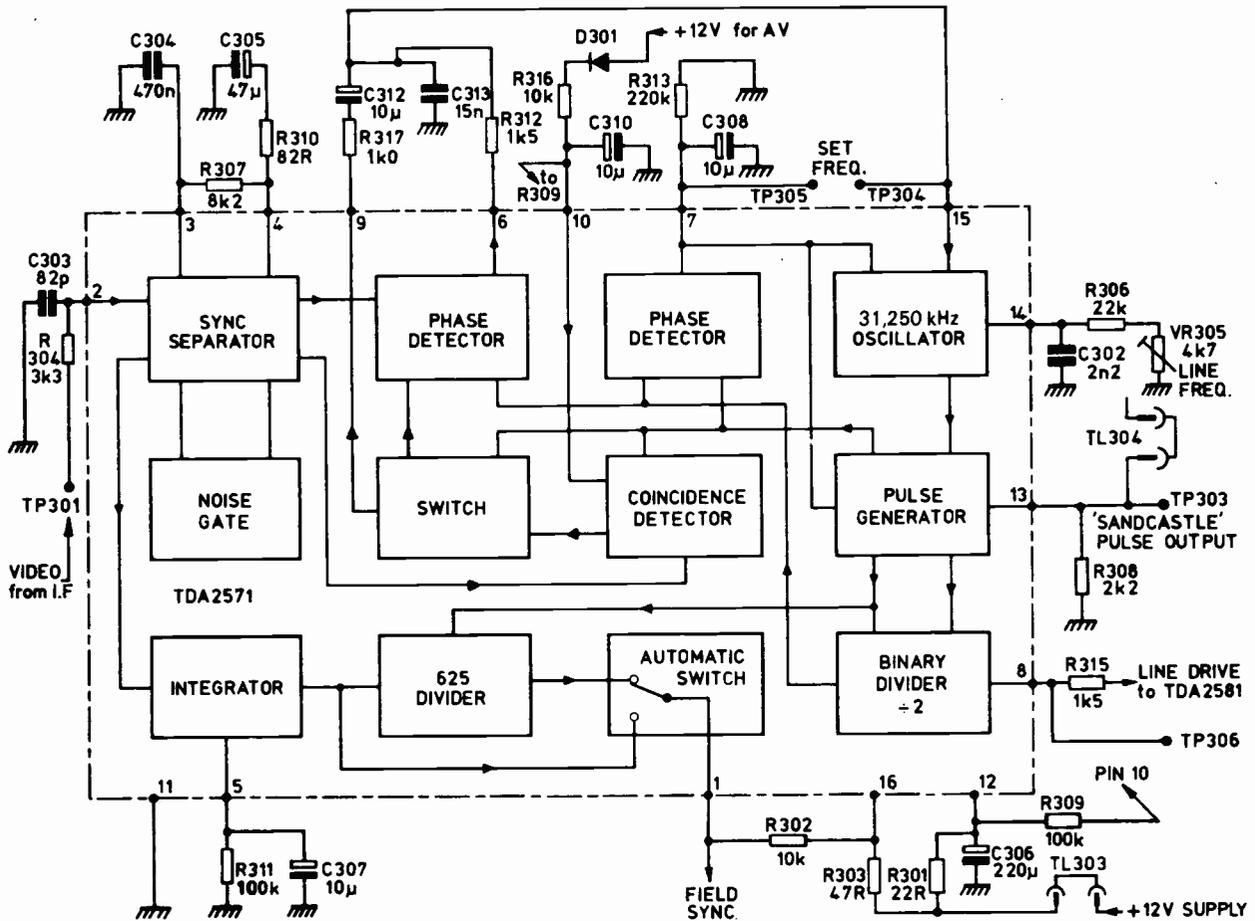


Fig. 2: Block diagram of the TDA2571 i.c., which combines the sync and line oscillator functions. The oscillator operates at twice line frequency, and with a standard signal input the field sync pulses are obtained from line frequency pulses by means of a 625:1 divider. There are three control loops within the i.c., each with its own phase detector. Peripheral components as used in the Decca 70 series chassis.

with automatic switching between direct field sync and sync pulses obtained by counting down. This provides for VCR use.

The KT3's timebase circuitry is otherwise conventional, with a diode modulator for EW correction, a tripler to provide the e.h.t., and a discrete component field timebase with class B output stage.

On the signals side, conventional LC filter networks form the i.f. response prior to the TDA2540 i.f. strip. The sound section is similar to the CVC40, with a TBA120AS intercarrier i.c. and TDA2611AQ audio i.c. There are two chips in the decoder, a TDA2560 luminance and chrominance signal control i.c. and a TDA2522 reference oscillator/chrominance demodulator/PAL switch i.c. A discrete resistor network is used for matrixing to obtain the RGB signals, which are fed, via emitter-followers, to class AB output stages.

14, 16 and 20in. models using the KT3 chassis have been announced, and the average power consumption is quoted as 65-70W depending on screen size.

Decca 70 Series Chassis

14 and 16in. models have so far been announced using the Decca 70 series chassis, which is quoted as having an average power consumption of 60W. Most of the circuitry is contained on a single panel, with two daughter boards, one for the i.f. strip and the other a decoder sub-panel. The switch-mode power supply/line output stage arrangements look similar to those of the KT3 chassis, but there are some important differences. While the TDA2581/TDA2571

combination again puts in an appearance, a parallel chopper circuit using a BUW81A Darlington device is used. By this means the switch-mode power supply can be used to provide mains isolation. There's also a rather neat touch in the start-up arrangements. To get the set going, the TDA2581 requires a start-up supply. This can be obtained from a zener diode fed via a suitable resistor from the rectified mains supply, but the zener's feed resistor will continuously dissipate several watts. The arrangement used in the 70 series chassis is shown in Fig. 4. At switch on, Tr601 is forward biased and the TDA2581 receives its supply via R627, Tr601 and D603. Once the switch-mode power supply comes into operation, D604 and Tr602 switch on and Tr601 switches off. There is thus no further dissipation in R627.

The line output stage uses a BU500 transistor with a tripler to provide the e.h.t. There's an unusual looking diode connected between the base of the BU500 and the pulse winding on the line output transformer. The purpose of this is to apply a negative-going 10V pulse to the base of the transistor to ensure that it remains switched off during the flyback period. EW correction is by means of a driven transducer in series with the line scan coils, as in the CVC40 chassis.

The field timebase consists of a TDA1170 i.c. as in the Decca 80 and 88 series chassis. This includes a class B output stage. A TDA1190Z i.c. is used as the intercarrier sound strip and audio amplifier. There's a TDA2560 and TDA2522 in the decoder, as in the KT3 chassis, but matrixing is carried out in a TDA2530. Class AB RGB output stages are used.

A SAWF with differential input forms the i.f. bandpass response ahead of the TDA2540 i.f. i.c. A Plessey SL1430 i.c. provides i.f. preamplification to make good the insertion loss introduced by the SAWF.

Thorn TX9 Chassis


Moving finally to the Thorn TX9 chassis, we find a simple main panel with an ultra-low component count, achieved by the extensive use of i.c.s, and a single daughter board for the i.f. strip. Keeping the i.f. strip on a separate board simplifies production in enabling boards for different TV systems to be easily substituted. The main board is also drilled ready for accepting the addition of a v.h.f. tuner. One of the most intriguing technical features however is that Thorn, who pioneered the use of switch-mode power supplies in TV sets, have this time decided to use a thyristor instead for voltage regulation and to keep the power supply and line timebase separate. The chassis is designed to drive all tube sizes in the range 14-20in., and the consumption under normal viewing conditions is only 55W – 40W at back level.

The i.f. strip follows the same pattern as the Decca 70 series chassis – an SL1430 providing differential drive to a SAWF followed by a TDA2540, and again a single chip (TDA1035S) takes care of all the sound circuitry. Another similarity is in the field timebase, though this time the slightly different TDA1170S is employed while the use of close-tolerance, high-stability components in conjunction with the stable oscillator in the i.c. has enabled the field hold control to be dispensed with.

A particularly interesting technical feature is that the decoder consists of a single i.c. driving class A RGB output stages. The chip is the NEC type UPC1365C, and the story behind this is a tale in itself. Thorn had heard of the extraordinary reputation for reliability of NEC's NTSC single-chip decoder, and entered into a joint operation to develop a version for PAL decoding. The result is a complete decoder in a 28-pin chip, a low-consumption device and a considerable contribution to achieving a single board layout.

Thyristor regulated power supplies have been widely used but have been disliked technically because the current drawn from the mains supply has consisted of narrow, large-amplitude pulses – typically 6-20A when operating at 50Hz. This current pulse produces considerable r.f. interference and, due to its high r.m.s. value, causes dissipation problems in the thyristor and the series limiting components. Using a bridge rectifier to give operation at 100Hz helps and is not new, but the significant feature of the TX9's thyristor power supply is the use of a large value choke (typically 0.3H) to spread the thyristor's conduction time to about 5msec. This, in conjunction with the low receiver power consumption, limits the current pulse to approximately 0.6A, greatly reducing r.f. interference and enhancing the reliability of the circuit.

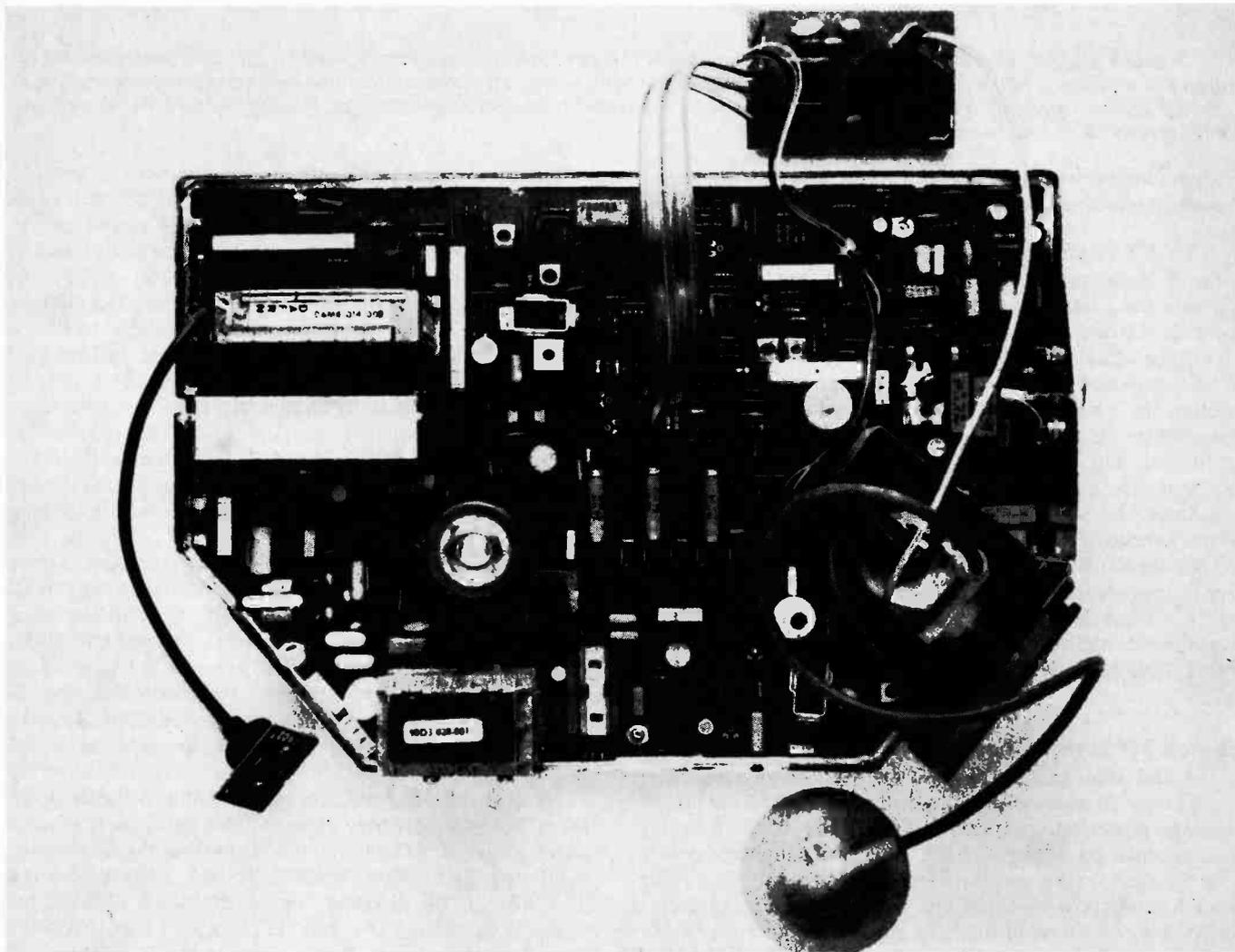The thyristor's control circuit includes a time delay which results in a wait period of about 1sec at initial switch on. This ensures that the degaussing operation is completed before the field scan starts. The power supply then goes through a soft-start cycle, with the h.t. rail rising relatively



The Thorn TX9 chassis.

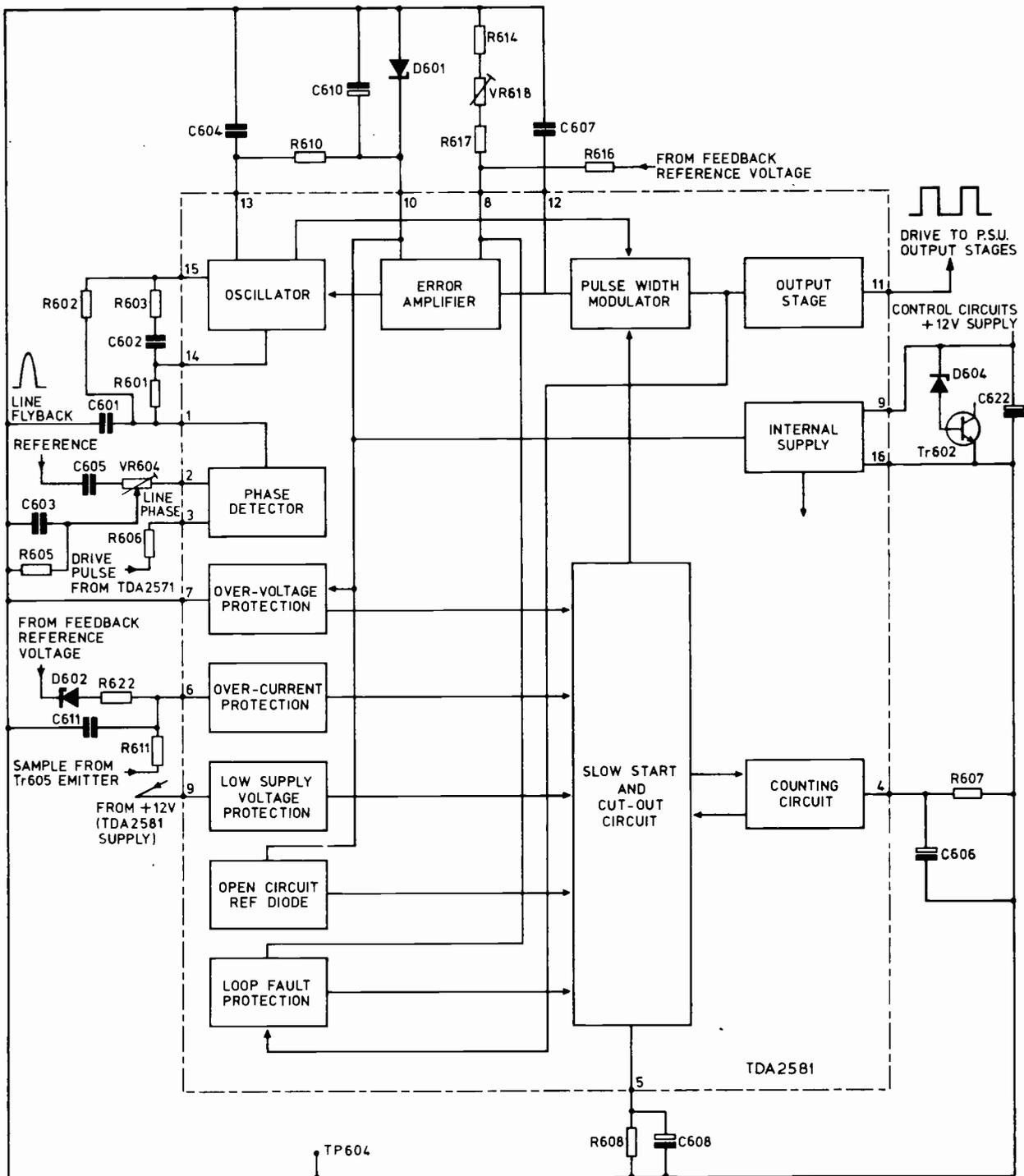


Fig. 3: Block diagram of the TDA2581 switch-mode power supply control i.c., which is designed to operate in conjunction with the TDA2571. Component numbering as used in the Decca 70 series chassis.

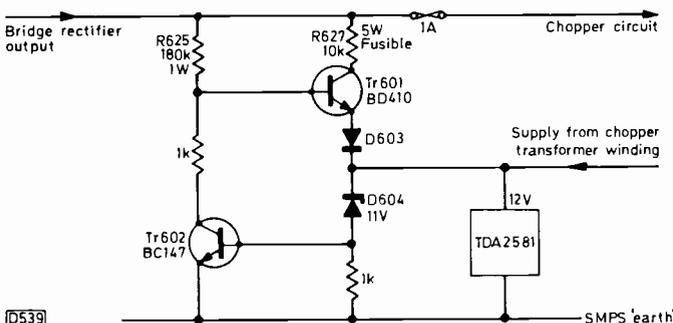


Fig. 4: The TDA2581 start-up circuit used in the Decca 70 series chassis.

slowly to eliminate supply rail overshoot and minimise mains input current surges.

The e.h.t. is obtained from a diode-split line output transformer with integral focus unit. The transformer's output impedance is improved by the use of an external, damped tuned circuit. This interacts with the transformer's inherent harmonic tuning, giving an output impedance of about 1.6MΩ. The tuned circuit requires no adjustment for different transformers of the same type, and no adjustment is necessary when replacing a transformer. The significance of this low output impedance is in improved e.h.t. regulation of course.

The line oscillator and sync circuits are contained in a TDA9053 i.c., while a diode modulator is used to provide

EW correction.

Some final points worth noting about the TX9. In comparison with the 9000 chassis, which it replaces, the component count is 410 against 618. This also reduces the number of soldered joints, the number of interconnecting plugs and sockets, and the amount of wire – there are around 400 fewer soldered joints than in the 9000 chassis, and there's 15m less wire! There's a 35% reduction in the number of setting up adjustments in comparison with the 9000 chassis – the use of the single-chip decoder has reduced the number of adjustments in this area from 12 to 8. The power consumption is halved compared to the 9000 chassis.

All this doesn't come cheaply: Thorn have made a massive investment in new capital plant – roughly £10

million is being spent on new machinery for the production of the TX9 chassis, much of it under sophisticated computer control.

The first set to be fitted with the TX9 chassis is the 14in. Model 3755. An optional inverter unit to enable the set to be operated from a 12V or 24V battery is available for use with this model. It fits inside the cabinet, on the left-hand side. Current consumption with a normal picture is approximately 5A from a 12V battery.

To sum up, these new chassis offer good performance and efficient operation, exploiting the latest technology. Black matrix tubes offering high brightness with good focus performance are used. The aim is products that compare favourably with those from any other source. ■

Test Report: New Dimension TV TR500 CRT Tester/Rejuvenator

J. H. Starling

BEING a full-time field service technician, most of my time is spent looking after various rental and maintenance contract TV sets. The majority of these date from the TV boom years of 1972-4, so their tubes are by now getting rather tired. This means that some means of checking and reactivating them is an almost essential item of servicing gear. There's quite an elaborate tube tester in the workshop, but it's too expensive to spend most of its time under the seat in the service van. Most build-it-yourself reactivators on the other hand don't include a meter amongst the transformers, pygmy bulbs and whatnots. The presence of a meter is most important so far as I am concerned: it can be used for before-and-after checks on the effectiveness of tube reactivation, can forestall attempts to jack-up a perfectly good tube when the fault lies elsewhere in the set, and also allows you to let the anxious customer see for himself the condition of his tube.

CRT reactivation can be likened to Russian Roulette – perhaps sudden death may ensue, or maybe a reprieve for months or years. Life is full of surprises! The game is usually played in a dark corner of the customer's lounge, where the victim sits surmounted by assorted pot plants, souvenirs of last year's package holiday on the Costa del Whatsit and a photo of Aunt Flo, skirt at half-mast, taking her annual paddle at Blackpool. Squatting behind all this paraphernalia, cup of tea in one hand and the reactivator in the other, I usually suggest to the customer that he leaves the room. Often, with a sense of impending doom, he'll hover outside the door . . .

So to the subject of this test report, the New Dimension Television TR500 "universal tube tester". It's a pocket-sized instrument in a plastic case measuring 11 x 7 x 4.5cm. CRT emission is indicated on a small panel meter whose scale is divided into "low" and "good" segments. The heater of the tube being tested is supplied with 8V from the mains transformer within the TR500, and during reactivation a positive voltage is applied between the selected grid and cathode, the resulting current flow being sufficient to remove the resistive layer of oxides from the cathode. The degree of removal is determined by the instrument's current limiting properties. A neon indicator shows the level of reactivation current, and is fully lit when the reactivation process is complete.

The TR500 comes with no tube base fitted, just a 6-core

colour-coded cable. I found it most convenient to wire this into B8H and B14G sockets mounted on the faces of a small box – plastic for preference, since the wires to the c.r.t. base can become live if the tester is incorrectly wired to the mains. The latter condition, also the absence of an earth connection, prevents the neon indicator in the TR500 working, thus drawing attention to the error.

I quickly got to know what meter readings to expect during emission tests of tubes of varying degrees of decrepitude. Although the meter scale is small, the readings are clear and reliable. A first-class tube drives the meter just to f.s.d., with tubes of lesser virtue giving proportionally lower readings.

Regarding the efficacy of the reactivation process, I found that the TR500 is well capable of "jacking" most c.r.t.s encountered. A colour tube with all guns low emission and maybe six or more year's use behind it is not a good prospect however, and of course the same applies to tubes which have been "squirted" before. As with any tube tester, sometimes a tube appears to have been successfully reactivated but then goes downhill during the next day or two. I find the best proposition for reactivation is a colour tube with one gun low in emission, or one in which all three guns have deteriorated over four years or less.

Conclusion

Since I've had the TR500, it's probably paid for itself several times over by saving recalls with the workshop machine. A session with the TR500 quickly establishes whether a set needs carrying off to the workshop, and I've seldom found the more elaborate workshop machine able to reactivate a tube on which the TR500 had failed.

It cannot be denied that the "live chassis" technique used on the instrument, and the necessity for an earth connection, is sometimes inconvenient in the field. But nobody is more used to working with a live chassis than the field service technician!

I've no doubt that this small and compact instrument is reasonable value for its price tag of £25 or so, and very useful to a busy field technician. It's available from New Dimension Television, 12 Buxton Row, Heavily, Stockport, Cheshire. ■

Renovating Körting Colour Receivers

Part 2

Mike Phelan

LAST month we covered the power supplies and timebases, also the tuner unit. In this concluding instalment we will be covering the remaining signal stages and also providing setting up notes.

The i.f. module, designated Z, is very reliable. It follows the now almost universal practice of having the bandpass filtering at the front, followed by a broad-band amplifier. In this chassis there's also extensive filtering after the final i.f. amplifier stage, before the final vision and sound detector diodes (D102 and D101 respectively). By this means the 33.5MHz sound carrier is almost entirely eliminated from the input to the vision detector, so that there is no trace of sound/chroma beat.

The i.f. module also contains the video/chroma distribution amplifier (T105), the gated a.g.c. stage (T106), and the a.g.c. phase-splitter (T107 – the tuner requires a.g.c. of the opposite polarity to that of the controlled i.f. stage).

The i.f. strip does not cause many problems. Most of those that do occur are in the a.g.c. circuit. If the a.g.c. locks out when the line timebase starts operating, C142 (33 μ F) will be found open-circuit. C144 (0.47 μ F) can cause low gain if open-circuit and lockout if short-circuit.

The preset contrast control R135 can become intermittent, and should be adjusted with a non-metallic tool to avoid shorting the wiper to ground. This also applies to the presets on the decoder.

Overloading when the brightness is turned up is caused not by an i.f. fault but by the print to the earth connection on the line output transformer being open-circuit. This also causes certain of the convergence controls to vary the i.f. gain (yes!).

Finally, the usual warning about not twiddling cores. The Körting i.f. strip is more difficult to align than most, so beware! Test points (the base connections of each stage) are available through holes in the screen. The habit of C149 shorting to blow the 24V supply fuse Si6 was mentioned last month.

After leaving the i.f. strip, the luminance signal passes through the luminance delay line and then goes to the Y board. This contains the luminance preamplifier T201, a switchable notch filter (L201), the beam current limiter (T204-5), and the sync separator (T206). The preamplifier is an emitter-follower, with the contrast control connected between its emitter and a potential divider. The transistor and its load resistor thus form one arm of a bridge, which is balanced by setting the transistor's collector current (R203), so that the contrast control does not alter the black level. The notch filter is tuned to 6MHz, but on receipt of a chroma signal a voltage from the colour-killer circuit forward biases the switching diode D201, putting an extra capacitor across the tuned circuit and reducing its resonant frequency to 4.43MHz.

The beam current limiter (see Fig. 4) monitors the PL509 line output valve's cathode voltage, as is usual in hybrid colour sets. It's a two-stage amplifier, thus giving a very sharp cut-off. This allows the c.r.t. to run right up to its

maximum beam current (1.5mA). This is necessary, otherwise the beam limiter would be working in opposition to the fast-acting e.h.t. stabiliser. The sync separator is entirely conventional.

T201 sometimes goes open-circuit, giving no luminance, but this symptom is often due to a dry-joint on the filter coil L201. Use a small, very hot iron for removal. The signal can be traced with a meter from the vision detector to the c.r.t., as the entire luminance channel is d.c. coupled. The sync separator transistor and its load resistor R233 (680k Ω) occasionally fail, giving weak sync or no sync at all. Either of the beam limiter transistors can give rise to no raster, which will be restored by pulling off the red and white lead next to the contrast control plug.

There are three versions of the audio panel. The earliest one used a discrete transistor output stage which gave good results from the twin-cone speaker. It used a TAA640 as the intercarrier sound channel. This panel gives little trouble. Later ones use a TBA800 audio i.c., with either a TBA480 or TBA120S intercarrier sound i.c. The audio from these is good, though not quite up to that of the original panel. The TBA800 fails fairly often, giving intermittent or no sound. There are facilities for fitting an extension speaker, in the form of extra pins on the panel above the mains transformer.

As mentioned before, the c.r.t. base panel houses the luminance output transistors T150/T151 (see Fig. 4). The input from the contrast control is at a very low impedance, and the final stage T151 is an emitter-follower. The tube's input capacitance and that of the wiring make little difference to the h.f. response therefore. This, coupled with the fact that the stages in question are mounted on the c.r.t. base, means that the definition is better than average. The transistors get very hot however, and frequently become dry-jointed. Replace with BF337s and use heatsink grease. Later models use BF459s which do not seem to suffer from this problem.

If T151 goes open-circuit emitter-to-base, the 47k Ω resistor in the c.r.t.'s final anode cap will emit much smoke, hopefully before the demise of the tripler! R160/161 going open-circuit will cause severe ringing, as will a faulty delay line. Burning of any of the c.r.t.'s 1.5k Ω cathode resistors means a heater-cathode short in that gun: see notes about this earlier.

Blanking board A gives little trouble. H.T. smoothing blocks, forget them! Transductor, ditto. R464 (12 Ω) occasionally goes open-circuit to give slight pincushion distortion, and the blanking transistor T302 and diode D302 sometimes fail. The three 1M Ω resistors R465-7 feeding the c.r.t.'s first anodes sometimes increase in value.

The controls on the convergence panel are fairly high in value (mostly 250 Ω) and don't give as much trouble as those of lower value used on other chassis. Severe trapezium distortion means that the wire link behind the line symmetry coil L940 has become disconnected (it's located on top of the scan coils). The three controls for radial static convergence should be set to mid-position first, and coarse adjustment carried out with the magnets.

Setting Up

Before attempting any adjustments on the set, ensure that the 24V rail is correct; adjust if necessary. The c.r.t. first anodes should be set at 500-550V. Set the preset contrast control for a signal of 130V peak-to-peak at the tube cathodes, with the front contrast control at maximum. Adjust R203 so that the black level remains constant at all contrast settings. Inability to do so means an emitter-base

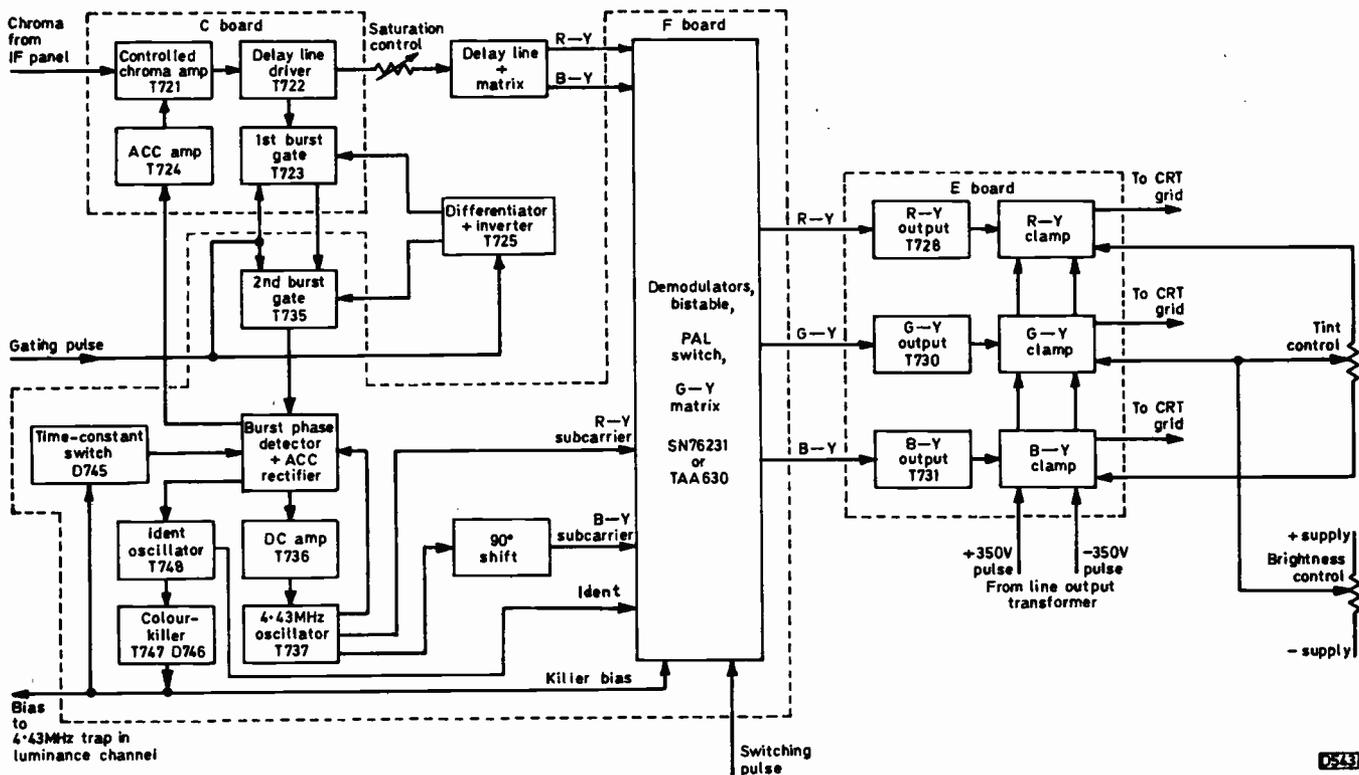


Fig. 6: Block diagram of the decoder.

short in T201, or that R206 (220Ω) or R207 (390Ω) have altered value. Turn the brightness control to maximum, and the beam limiter potentiometer R223 likewise, then set the preset brightness control R361 so that the black bar of a grey-scale wedge is just illuminated. Finally turn the beam limiter control R223 slowly until the black bar just starts to darken.

The Decoder

The decoder is arranged on three printed boards, with a number of components on the main board. The block diagram (see Fig. 6) shows what is where. As this part of the set has a few unconventional features, a brief description will not be amiss. The unusual stages are the burst gate and the ident oscillator.

Composite chroma is fed to T723 (see Fig. 7) and then to T735, both of which are without a fixed forward bias. A large-amplitude positive-going line flyback pulse is clipped to 24V by D731, giving a wide, square pulse extending from the flyback until after the burst. This drives the two gates T723 and T735 into conduction. The pulse also goes to the base of T725, through the differentiating network C747/R759 which form a positive spike followed by a negative one. As T725 is normally saturated, the positive spike cuts it off, producing a negative pulse at its collector. This is integrated by R761/C749 and fed to the bases of the two burst gates, thus cancelling out the first part of the gating pulse. This really is a most ingenious way of doing it! C733 sets the burst amplitude, and via the a.c.c. the chroma level.

The ident stage (Fig. 8) is an RC sinewave oscillator (T748) which is synchronised by the 7.8kHz ripple from the burst phase detector. The output is rectified by D746 to give a killer turn-on bias. When no burst is present, pin 10 of the TAA630 demodulator/matrix i.c. is taken down to 0.1V, causing the outputs to go high, so that the colour-difference output stages are saturated. The time-constant of the d.c.

amplifier circuit in the reference oscillator control loop is also altered to give a greater pull-in range for a short period on switching from monochrome to colour.

Many chroma problems are due to incorrect adjustment of the ident/killer circuit. A scope, or at least a diode probe, is essential. The complete decoder setting up procedure is given later.

There seem to be few recurring decoder faults. Transistors fail occasionally, particularly T725, which will cause weak chroma. To over-ride the killer, simply turn R876 fully clockwise. C747 (27pF - see Fig. 7) on the main board goes open-circuit sometimes, removing the burst. Reluctance of the oscillator to lock may be due to a faulty crystal or to the a.c.c. diode (D732 OA90) being leaky. Weak locking accompanied by excessive chroma, usually intermittent, can be because C749 (100pF) is going open-circuit. No chroma when the killer is disabled may be a stopped oscillator (check capacitors and T737), one of the capacitors in the input filter (near the two coils on the main board), or the TAA630 i.c.

Faults on the CDA board are usually defective transistors, which will give loss of one colour-difference signal, or leaky clamp diodes, giving lack of or excess of one primary colour. These must be replaced in pairs of the same type, e.g. BA148, BA158, BY206 or any other suitable fast soft-recovery type.

To set up the decoder, turn the colour-killer threshold control R876 clockwise and use a bar or test card signal. First set the d.c. levels of the colour-difference signal output stages by adjusting R847, R844 and R845 for 140V, 70V, and 120V at the collectors of the B-Y, G-Y and R-Y output transistors. Always set the blue first. Short the base of T735 to earth to remove the burst, and set the reference oscillator to zero beat with R817. Remove the short.

A peculiarity of this chassis is that if the ident phase control R887 is in need of adjustment the result on the screen looks similar to the reference oscillator being off frequency. Adjust L802 for minimum chroma, either visually or with a

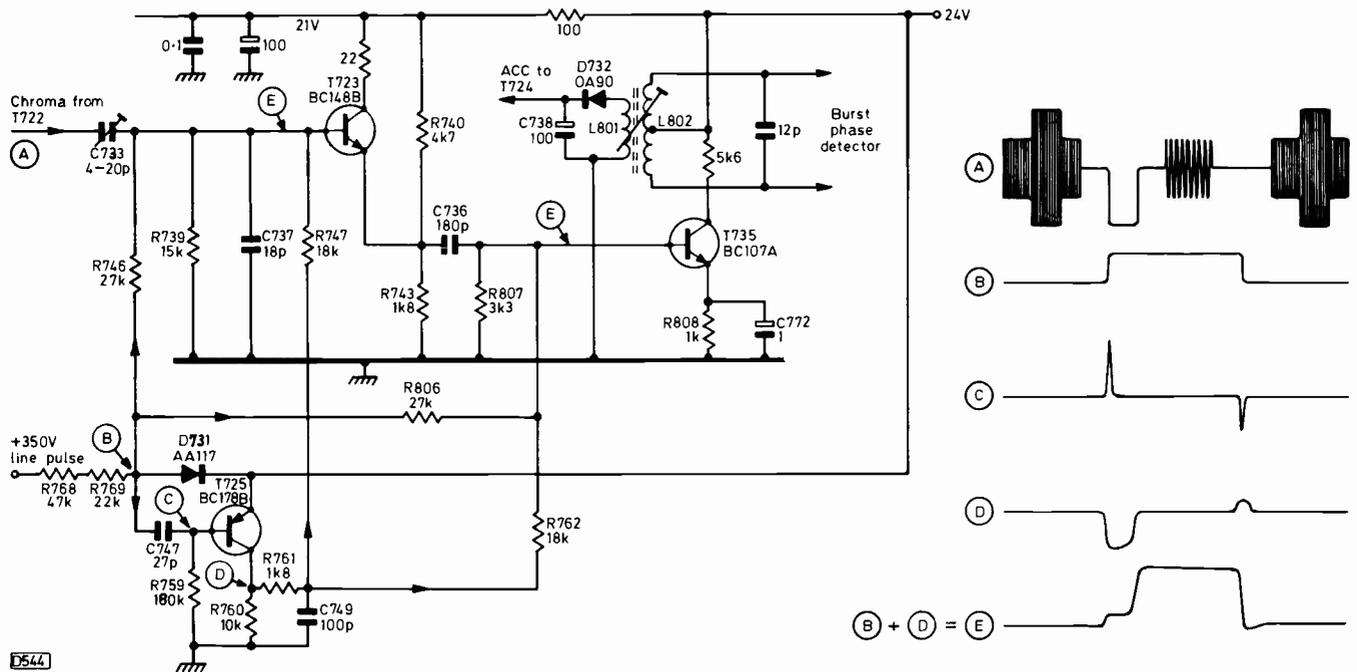


Fig. 7: Both transistors (T723 and T735) in the burst channel are gated. T725 provides pulse inversion.

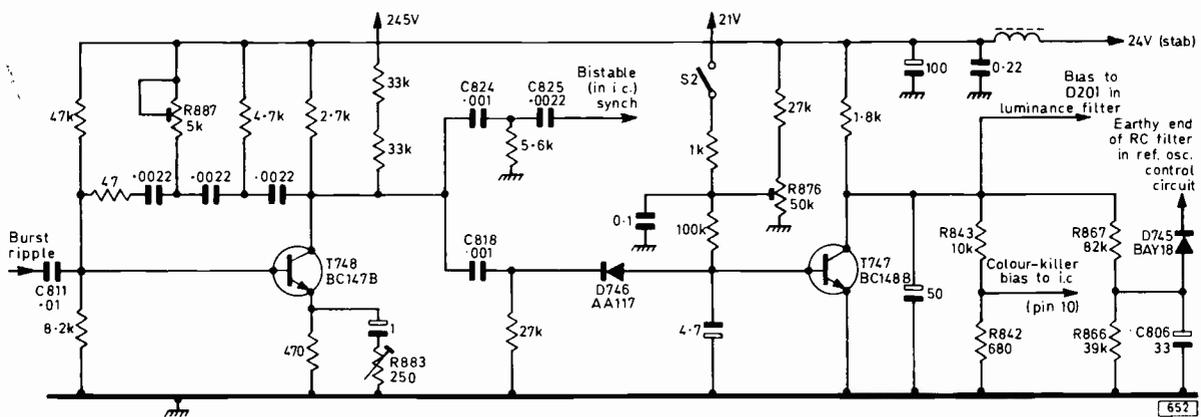


Fig. 8: The ident oscillator and colour-killer circuits.

scope on point M34 (the pin at the top of board C). Note that the tuning of this coil is very flat. With the scope on pin 8 of the decoder edge connector, set R887 for maximum sinewave, then set R883 (ident amplitude) for 18V peak-to-peak. Repeat both adjustments several times. If a dual-trace scope is available, a better way of setting R887 is to display one line of video, from the luminance delay line for example, and with the other trace display two consecutive lines of ident sinewave, so that they overlap: two lines of ident is, of course, one complete cycle. R887 can then be set so that the crossing over of the ident coincides with the line sync pulse on the video waveform. Now to set the killer threshold control R876, reduce the ident to 6V peak-to-peak with R883, then turn R876 slowly anti-clockwise until the colour goes off. Reset the ident to 18V. For those without access to a scope, reasonable results can be had with a diode probe and meter, but haphazard twiddling will not work with this circuit.

The subcarrier phase coils L721 and L731 can be easily set by converting to simple PAL. This is done by placing a shorting clip across pins 14 and 15 of the edge connector. Any blinds present are due to phase errors, and can be removed by adjusting the two coils. Remove the short, then remove remaining blinds with the delay line amplitude control R896.

On early models there was also a delay line phase control (L705). In this case a better method of alignment is to set only *one* of the subcarrier phases, then deliberately misalign the other one so that severe blinds appear on that signal, say R-Y. Then adjust the delay line potentiometer for minimum blinds (easier with a scope) on R-Y *only*. Set the R-Y phase coil by the simple PAL method, and finally adjust the delay phase coil.

There's an R-Y amplitude control (R754) which can be used to obtain correct flesh tones on the test card. C733, as mentioned before, acts as a preset colour control.

Front Controls

The rotary front controls don't seem to give any problems, but the slider controls become noisy. They are repairable if dismantled carefully. The trouble is mainly the metal strip that forms the common connection becoming tarnished. A rub with metal polish and all is well. Don't use switch cleaner. Reassemble carefully, with special attention to the plastic strip as this keeps the dust out.

In conclusion, though many faults have been mentioned, few will be experienced on any one set. An ex-rental set in good condition should give long and trouble free service. Spares are readily available.

Long-Distance Television

Roger Bunney

APRIL, often a quiet time before the opening of the Sporadic E season in May, ran pretty well to form this year, with little reception via any mode of long-distance signal propagation. Even the usual MS (meteor shower) signals were lacking here at Romsey during the early part of the month, though there was an improvement towards the end. I've seen little of importance unfortunately, though there are rumours that RTVE (Spain) may be using a new test pattern. Details are awaited.

On both the 11th and 16th I logged F2/TE signals from a southerly direction during the early evening period. On the 11th there was a vertical pattern at 1825, followed by a caption at 1844, the station announcer at 1845 and then news, the signal fading completely at 1846 (all times BST). True to form the signal was very fuzzy during the caption and announcer time, making positive identification impossible. The weak signal information on the 16th came from the same direction at a similar time but didn't give a recognisable image.

Kevin Jackson (Leeds) reports an aurora just after midnight on the 4th, producing we think for the second time transatlantic, auroral TV signals on ch. A2 – non-locking, with rolling and the sound carrier some 4MHz higher than the vision one (the system M sound/vision spacing is 4.2MHz). The signal went off the air at 0101 GMT, which Kevin suggests is perhaps too early for a North American station, though certainly no European transmitters are on-air at that hour. There have been suggestions that the signal could well be from an AFRTS ch. A2 outlet in perhaps the Faroes, Iceland or even Greenland, though there are no listings anywhere of any such outlets. It suggests to me that the transmitter could perhaps be located in a more rural part of the Canadian N.E. seaboard. Any comments on this unusual sighting would be welcome. Meanwhile, congratulations to Kevin on this reception. A daytime check with a TVP (Poland) MS signal enabled Kevin to confirm the ch. A2 position in relation to the Polish ch. R2 frequency.

Though F2 reception above 40MHz has been generally absent in the UK and W. Europe, reports from Australia indicate that there's been F2 activity there. Bob Copeman (Sydney) reports reception of two floating chessboard patterns on March 31st, probably originating from Nanking and Lanchow (ch. R1). Deutsche Welle harmonics were present on 38.4/46.8MHz, several Russian communications channels at up to 43MHz, and another Asian TV channel on the ch. E2 video frequency. Bob confirms incidentally that ATV0 will move to ch. 10 this year, though the TVQ0 move may be delayed. A thousand miles to the west, Anthony Mann reports a massive TE opening from 1850 till 0015 on March 20th, with Chinese, Malaysian and suspected Indonesian test cards, East Malaysia in at "tremendous strength" on ch. E2 with programme material, Korean ch. A2 signals, and Russian and Chinese ch. R2 signals adding to the general confusion.


Ian Roberts reports from Pretoria, South Africa, that a new amateur radio record was established recently with a series of three contacts, two using c.w. (i.e. morse) and the other s.s.b. (single sideband), between a Greek (Athens)

radio amateur and the South African amateur ZS6DN in Pretoria, using the 2 metre (144MHz) band. The signal was weak but resolvable, strange characteristics being a 15 μ sec delay over the signal path – theoretically the delay should have been only 5 μ sec – and that the reception in Greece was at an optimum with an aerial elevation angle of 20° from horizontal. Ian confirmed reception during March of BBC stations up to the ch. B4 sound frequency (at 10.37p.m. on the 12th), also RTE (Eire) ch. B and on the 12th signals up to the ch. E4 vision frequency till approaching midnight locally. All very exciting, but for us UK enthusiasts I fear that the F2/TE signals are falling in the south of France!

Further news on the reception last July 30th by myself and three other DXers of unknown system M ch. A2 signals via Sp.E. The ch. A2 transmitter we all received (two of us also received ch. A3 vision) has still not been positively identified, but my cassette recording of the ch. A2 sound was sent to WTFDA member John Combs in Orlando, Florida who is familiar with the various American accents. He's been able to resolve part of the identification that had been incorrectly deciphered by myself. TFL has not been explained, but at the end of the identification the signal continues "... at 10.30, Ottawa Rough Riders meet the Edmonton Eskimos." This is apparently a plug for a Canadian football league game that was replayed during the evening on July 30th, and Canadian members of the WTFDA active in the broadcasting field are checking old schedules to find out who carried the game at 10.30 and the possible ch. A2 transmitters. It's hoped to be able to single out a specific one through the promotional music and content. More news is hoped for soon.

The New Antiference Aerial

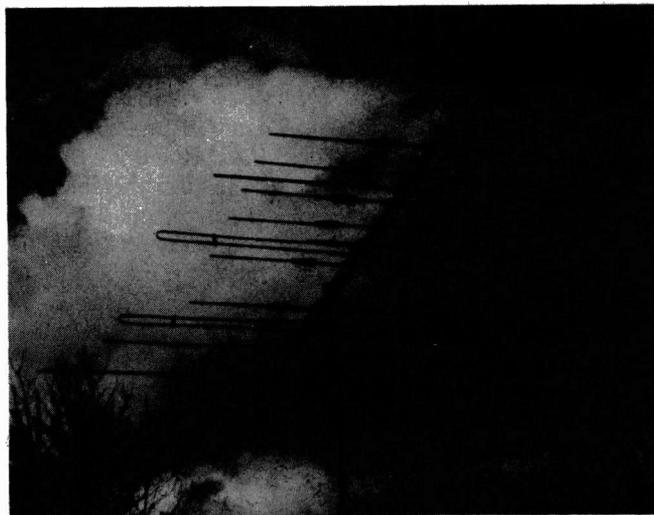During the Easter break I laboured to instal the Antiference wideband aerial described last month. As anticipated, it was not an easy system to rig. Problems arose



The Antiference MH473 wideband (Band I/III) aerial, with its colinear elements.

due to a slight wind at 30ft. above ground level, as a result of which the elements were blown against the mast, meshing with the latticework. . . The 10ft boom and weight in excess of 8kg means that installation should be carefully planned – preferably on a mast without guywires!

Once installed, Lopik ch. E3 was immediately resolved. Band III has been more difficult to assess, due to the extremely poor tropospheric conditions recently, but Belgium chs. E8/10 are present (just) at times. I was surprised at the directional performance of the system in Band III, and the pickup from beneath the main forward lobe is a noticeable improvement on earlier systems (i.e. less pickup of unwanted signals/interference). Not surprisingly, the system is expensive, and anyone interested should contact accredited suppliers for delivery dates. Since this is an export array in batch rather than continuous production, delays may be experienced. I hope to report further on the system following a longer period of evaluation.

The recommended retail price of the MH473 array is £47. Other aerials in the Antiference range include the H1010 at £14, the MH308 at £22 and the MH311 at £25. The prices do not include VAT (12½%).

News Items

Saudi Arabia: Aramco TV (HZ22), previously on system M (525 lines), has confirmed the change to system B with PAL colour. The e.r.p. has not been increased.

Qatar: There's been a report that an English language TV service is to start in the near future, at u.h.f.

Belgium: The RTB service's PM5544 pattern generator was destroyed during a fire. The pattern subsequently radiated consisted of colour bars with the identification "RTBF" or "RTBFbis".

USA: Amongst the proposals the FCC will be making at the World Administrative Radio Conference are the extension of the MW broadcast band to 1860kHz, the extension being on a shared basis but with 1800-1860 exclusive to broadcasting, the use of the 470-890MHz band exclusively for TV broadcasting rather than on a shared basis as at present, and also the allocation of the 12/14GHz bands similarly for broadcasting from satellites.

Spain: The projected Catalonian TV service has been rejected.

France: New EBU listing – Brest TF1 1,000kW e.r.p., horizontal.

From our Correspondents . . .

Andrew Tett is using a Murphy V849 receiver fed from a horizontal Band I dipole "with Band III attachments" in the loft, pointing to Europe. Despite this difficult arrangement, Andrew resolved Holland ch. E4 and Belgium chs. E3, E8 and E10 last November via tropospherics. He's anxious to hear from any other local DXers who can assist him in improving the gain of his receiver – the address is 109 Ronelean Rd., Tolworth, Surrey.

Gareth Price (Lowestoft) has had the benefit of assistance from Clive Athowe and has successfully resolved a vast number of v.h.f. and u.h.f. signals, using a Premier wideband Band I aerial and Fuba XC391 u.h.f. array. The receivers in use are a Philips with the 210 chassis and an added G8 selectivity panel, and a 5½in. JVC v.h.f./u.h.f. set. The latter is apparently a high performance receiver and, being a mains/battery portable, can be carried around the house for monitoring anywhere. Amongst the signals received on this set are Gwelo, Rhodesia ch. E2 and many MS signals. It seems that prior to Lopik ch.E4 coming on

**CONTINENTAL AERIAL SPECIALISTS, RETAIL AND TRADE.
GOLDEN ANODISED, WEATHER PROTECTED, SUPERB ARRAYS.
GUARANTEED BY US FOR FIVE YEARS.
GOLDEN QUALITY IN A PLASTIC AGE.
AERIALS EXCHANGEABLE FOR 7 DAYS.
10% DISCOUNT OFF AERIALS**

For new glossy, highly graphic lists & brochures send 40p & stamp only. 40p credit on 1st order.

AGENTS FOR
FUBA & PLEMI

Stockists of the finest aerials available in Britain:

STOLLE FM aerials (W.Ger.)
FUBA TV & FM aerials (W.Ger.)
PLEMI TV aerials (Hol.)
UKW FM aerials (E.Ger.)
ANTIFERENGE TV & FM aerials (U.K.)



The fabulous golden anodised FUBA XC391

We specialise in
Rotator & DX work.
Bands I & III stocked.

ASTRA (GOLDEN D.I.Y.) AERIALS

A friendly family firm. Now Established 24 years

D.I.Y. AERIAL SPECIALISTS FOR ALL DOMESTIC TV & FM RECEPTION
Weather exposed part of U.K.? Scotland, Wales, West Country etc. Gales, salt air corrosion problems? Want to install your aerial and forget it?

The continental aerial range from Germany and Holland having proved so fantastically successful, we are in future recommending continental aerials (especially Fuba) as our first choice for customers. In short we offer quality in a plastic age. Anodised against corrosion, guaranteed for five years, robust, high gain, easy to assemble, eye-catching superb aerials, what else, in truth could we recommend?

SPECIAL PROMOTION OFFER

15% + DISCOUNT ON PLEMI RANGE

Over 3,000 aerials stocks: All Bands: Masts: Lashings: Wall Brackets: Rotators: Televertas: Diplexers and Triplexers: You can now mix Band 4 and Band 5, or lower Band 5 with higher Band 5, or mix FM with either, 1.5db loss approx.: Padded outlets: Directional splitters: Coax, white or brown: 300 ohm cable.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Gloster Pub & Garage Tel: 01-684 4300
Open 9.00-5.30 MON-SAT. 01-684 5262
Closed 12.30-1.30 But Open ALL day Sat. 24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY

LOOK! Phone: LUTON,
BEDS. 38716

OPPORTUNITIES TRADE SALES

START AT £25 INC. VAT!!

FOR D/S COLOUR TV's

G.E.C., Philips, Murphy, Decca, Ferguson

S/S COLOUR TV's

Philips, G.E.C., Telefunken, Decca, Ferguson

FROM £40 INC. VAT!!

MONO TV's, all makes from
£5 INC. VAT

SQUARE SCREEN, all models
£12 INC. VAT!!

Deliveries arranged if necessary.


**HUNDREDS OF SETS EACH WEEK TO BE
DISPOSED OF AT GIVE-AWAY PRICES.**

OPPERTUNITIES

9A, Chapel Street, Luton, Beds.

LUTON 38716

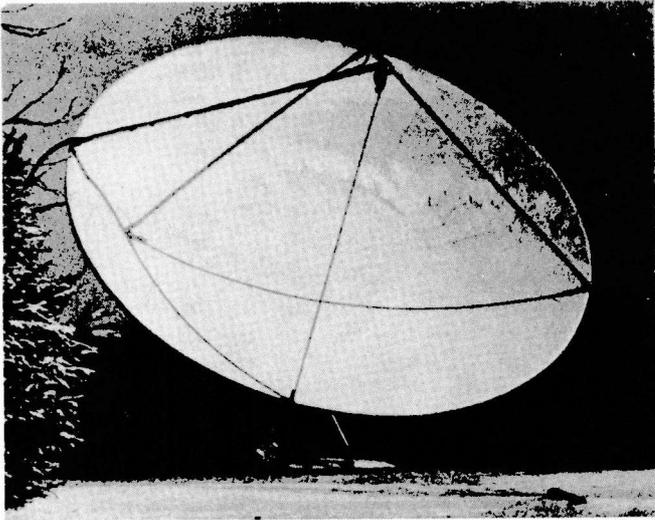9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.



A 6-metre USTC (United States Tower and Fabrication Company) dish aerial for satellite reception.

air certain oil rig communications have been heard. I'm wondering whether this is due to cross-modulation, since this is an allocated broadcast band.

Hugh Cocks has been carrying out tests with a Wolsey Colour King and a Jaybeam JBX21 array at his East Sussex location. He's noticed that the signals from the two aerials at their different heights can vary considerably. The Colour King is at 38ft. and the JBX somewhat lower, but at times fading will give a stronger signal from the lower aerial and vice versa.

N. American Satellite TV

It's unfortunate that with the OTS-2 satellite in use at present to conduct tests into 12GHz propagation and receiver techniques no commercial receiving equipment is available. There's the further point that with an established terrestrial network, the advent of satellite TV broadcasting to the UK is likely to be some way into the future. Things seem to be more lively in the USA however.

In recent months Bob Cooper, from the CATA organisation at Oklahoma City, has been sending me copies of their journal CATJ, which is devoted to describing progress and developments in the cable TV field. It's all too obvious from this that enthusiasm for advances in communications and entertainment is rather more dramatic there than we experience in the UK and W. Europe. Satellite engineering and the associated receiving apparatus seem to have become something of a growth industry in the US, with emphasis in particular on improved, low-cost amplifiers and other spin-offs which will be to the advantage of consumers.

Satellite TV is already a benefit to both cable TV operators and TV station operators in the states, enabling the former to offer their subscribers a much wider choice of material ob-

tained from the latter. For example, WTCG Atlanta ch. 17's programmes are now (as at October 1978) linked via the Satcom-2 satellite to some 250 cable systems serving 1.3 million households. WTCG pioneered satellite TV programme distribution of this type. Its success has been followed by other stations across the USA, and by what are called programme facility houses, all leasing relay transmitters (transponders) on a variety of satellites (or "birds" as they are coming to be known as in CATV circles).

From 99°W to 135°W a series of synchronous satellites operating in the 3.7-4.2GHz band is providing coverage over the greater part of N. America (with spot beams to the USA's 50th state, Hawaii). The numerous programme sources are transmitted to the satellites from ground stations operating in the 6GHz band. Three of the satellites (Anik 1, 2 and 3) are used primarily by the Canadian government and the CBC to provide links with conventional transmitters which reradiate the programmes. Included in the transmissions are 12GHz signals for the CTS experiment. The five satellites operating in the USA are Westar 1 and 2 (Western Union), Comstar, and two RCA owned satellites.

Western Union's satellites have 12 channels each, within a 500MHz bandwidth, each channel being 40MHz wide with a 40MHz separation between channels. The RCA satellites similarly have 40MHz channels, but the 20MHz separation provides 24 channels within the total bandwidth. This is made possible by using cross-polarisation — vertical polarisation is used for twelve of the channels and horizontal polarisation for the other twelve.

Certain guidelines on the performance of the receiving terminals are laid down by the FCC, and potential users have to present their proposed specifications for approval. Since the field strengths produced by the various satellites vary over the landmass, it follows that the design of receiving terminals varies.

Once the terminal has received FCC approval, the operator can turn to a large number of suppliers of the specialised equipment required. Negotiations with programme originators continue during the installation of the terminal. Many TV stations now feed their output to satellites, from San Francisco in the West to Las Vegas, Chicago, Atlanta and Virginia Beach in the east: the programme facility houses often provide exclusive reshowings of movies on current release, and shows. Once contracts are concluded, the cable operator hooks up his system to the satellite and the extra programmes are added to those (often in double figures) already available to his subscribers.

The parabolic reflector aerials used vary in diameter from 11 metres down to 4.5 metres. The feeder system may be of the prime focus type (r.f. extracted at the focal point of the dish) or the Cassegrain type (r.f. extracted at the dish centre, after reflection from the focal point). The heart of the system, determining the performance of the terminal, is the low-noise amplifier. It's perhaps in this area that most original research has been done, in an effort to achieve very low noise figures without recourse to the use of the rather larger parametric

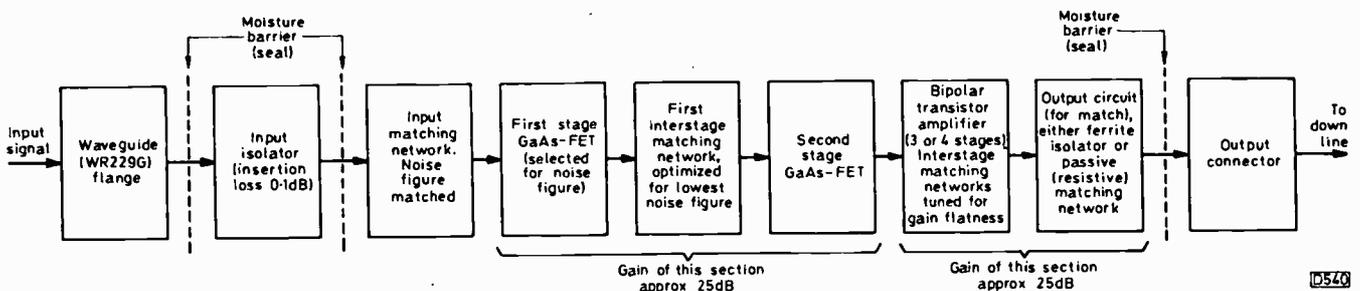



Fig 1: Block diagram of a high-gain low-noise amplifier for satellite reception in the 4GHz band.

amplifier. The gallium-arsenide f.e.t. seems to have revolutionised LNA manufacture, making it possible to achieve a noise figure of under 2dB at 4GHz with a gain of 25dB. The Hewlett Packard HFET-2201 has noise figures of 1.2dB, 2.4dB and 3.1dB at 4, 10 and 14GHz respectively. These devices are expensive, currently around \$300 for one off. Higher noise devices such as the HFET-1102 (1.7dB at 4GHz) sell for correspondingly less – \$150. Delivery is slow, due in part to the small quantity production, with each device being individually selected and processed. The LNA is mounted at the r.f. extraction head, with the signals fed to the main receiver via low-loss coaxial cable which can be up to an inch thick. The receiver itself may be a single-channel type, a 12- or 24-channel type, or tunable over the 500MHz bandwidth. The prices are high – up to \$4,000 for a single-channel unit, up to \$7,500 for a multi-channel type. The output from this is remodulated and fed to the cable distribution system.

There is increasing interest in the US amongst private operators thinking of setting up their own backyard terminals and hooking up to the programmes now available via satellite. If this develops, we may see manufacturers producing smaller dishes – 10ft. and below, possibly using fibreglass in view of the increasing cost of aluminium.

In practice terminals are constructed for use with alternative satellites, calling for a high degree of mechanical engineering precision to obtain both accuracy of aerial aim and rigidity during service. Some operators prefer to employ separate aerials for different satellites.

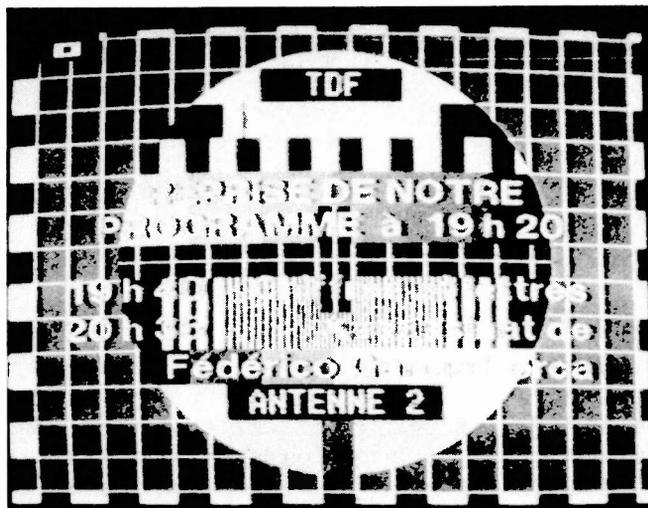That very simply is a summary of the present state of satellite TV in the USA. No direct transmissions to domestic installations are planned at present, though one manufacturer has been awarded a contract to undertake



An impressive shot of the TDF A2 test card received by Steve Birkhill at 12GHz from the OTS-2 satellite.

research into and develop a low-cost 12GHz "domestic quality" terminal using a small, say 3ft., dish.

The N. American satellites unfortunately can't be received in W. Europe – even if any reasonably priced 4GHz equipment was available (if anyone knows of a source, let me know!). There are other satellites operating in this band however, such as the Intelsat series. If you're thinking of trying to construct a terminal, you'd be well advised to check with the Home Office at Waterloo Bridge House, London – such activities are likely to be restricted to an experimental basis only.

My thanks to Bob Cooper for his help with information and illustrations.

★ NEW ★ COLOUR BAR GENERATOR

U.H.F. AERIAL INPUT PATTERN GENERATOR CPG6-RF

All Facilities of our PG6RF



PLUS COLOUR BARS.

Produces 7 invaluable patterns.

**Robust, Battery Powered, Pocket Sized Unit,
Plugs Straight into Aerial Socket.**

W H I T E	Y E L L O W	C Y A N	G R E E N	M A G E N T A	R E D	B L U E	B L A C K
-----------------------	----------------------------	------------------	-----------------------	---------------------------------	-------------	------------------	-----------------------

FEATURES:

- ★ CROSSHATCH GRID
- ★ DOT MATRIX
- ★ VERTICALS
- ★ PLUS PAL COLOUR BARS;
ONLY 3 SIMPLE ADJUSTMENTS.
- ★ PG6RF OWNERS; Buy Add-On 'C6' Unit!
- ★ HORIZONTALS
- ★ WHITE RASTER
- ★ GREYSCALE

ORDER NOW!

PG6RF KIT £24.30 BUILT £31.32 – As per TV Review, Jan. 1979

C6 KIT £17.82 BUILT £24.84 – Add-on Colour to PG6RF

CPG6RF KIT £39.96 BUILT £59.40 – Both above combined.

These prices INCLUDE P & P and 8% VAT. Export VHF versions available.

ALSO AVAILABLE:

TECS: TECHNALOGICS EXPANDABLE COMPUTER SYSTEM.

Full Colour Teletext; full facility Microprocessor-based, Aerial Input Decoder with extensive computing facilities. The most versatile decoder on the market. Expandable from a simple teletext decoder to a full professional computer/information centre. Send large S.A.E. for details.

**SEND ALL ORDERS OR ENQUIRIES TO TECHNALOGICS LTD. (DEPT. TV)
8 EGERTON STREET, LIVERPOOL L8 7LY.**

In response to demand we have produced an add-on Colour Bar unit C6 to upgrade the PG6RF to PAL COLOUR. A MUST for TV construction or servicing! Available as a KIT or BUILT & TESTED. Kit includes all components and ready built modulator etc.

Full 12 month guarantee on built units.

MAIL ORDER

ONLY

Quantity Discount
on application

ACCESS

ORDERS

WELCOME

Service Notebook

George Wilding

Poor Picture

A GEC hybrid colour set was brought to us with the complaint "poor picture with white lines". The white lines were field flyback lines, which were being emphasised because the brightness control couldn't reduce the d.c. level of the picture sufficiently. We also noticed that the focus was well away from optimum, while the line scan was short by about three-quarters of an inch at the right-hand side of the screen. The owner commented that the picture took a long time to reach this size.

Since the width deficiency was at the right-hand side, the first main suspect was naturally the PL509 line output valve. A replacement brought no improvement however, but on changing the PY500 efficiency diode the warm-up time returned to normal, the raster gap disappeared, and the tube had a much healthier appearance – doubtless due to the increased e.h.t. Readjusting the first anode presets enabled the brightness control to be adjusted to give the correct black level, removing the flyback lines, while adjusting the focus control removed the final defect and gave a very good picture.

More on EW Tinting

In the March issue I mentioned EW tinting on a Pye hybrid colour receiver, with the trouble vanishing when the first anode switches were turned off and on again one at a time. This brought a very interesting letter from Bill Thorpe of Southampton, who has come across the trouble on several occasions. The first time, Bill found that on the following day the trouble had returned. After making some inconclusive tests, he decided to try some resistance measurements. On making comparative tests from the anodes of the colour-difference output pentodes to chassis, he found that although readings were obtained from the R – Y and G – Y valves there was no reading from the B – Y valve, due it turned out to its 12k Ω anode load resistor being open-circuit – though surprisingly he was able to obtain a voltage reading at pin 6 (anode) of the valve. Possibly current was getting across the break in the resistor. Anyway, replacing the resistor completely cured the trouble – on this and later occasions. Bill comments that it's been the B – Y stage every time.

Lack of Width with Field Bounce

The width on a Bush colour set fitted with the A823 chassis was in slightly at the right-hand side of the screen, while a few minutes after switching on the raster would bounce up and down erratically by about a quarter of an inch. Now field judder due to a defect in the power supply (the thyristor or, less often, the trigger diac) is quite common on these sets, but this intermittent and pronounced bounce was quite different. Correct h.t. voltage is vital to the operation of a transistor line output stage of course, so our first move was to measure this. There was only about 187V at the h.t. fuse 8F3, so we advanced the set e.h.t. control 8RV1 to obtain

just under 200V. This might seem a little on the low side to some, but we find that the h.t. voltage often tends to creep up as the set gets really warm: adjusting it slightly on the low side to start off with reduces the risk of trouble in the line output stage. Anyway, this gave us correct width and also completely cured the field bounce. After readjusting the focus control and the static convergence magnets, a really good picture was obtained – it never fails to amaze the professional service engineer how viewers accept the performance of a set that's gradually drifted away from its original standard.

Intermittent Purple Picture

A hybrid ITT colour receiver fitted with the CVC8 chassis gave a good picture which went purple intermittently for brief periods, i.e. there was intermittent loss of green. On arriving at the owner's house, we found that a monochrome set was being temporarily used as a replacement. Even without an aerial, the colour set gave a surprisingly good picture, but on plugging the aerial in the picture, raster and sound completely vanished. Oh dear! On top of the green trouble, we'd apparently given ourselves another fault simply by plugging in the aerial.

Off came the back, and all fuses were found to be intact. Bearing in mind the importance of the stabilising zener D11, which stabilises the tuning voltage supply as well as providing the reference voltage for the l.t. supply series regulator circuit, we first checked the voltage across it. This turned out to be only 11V, while the diode's metal casing was quite hot. It was clearly defective, and a good picture with normal sound was obtained on fitting a replacement. The raster had gone due to the lack of drive to the RGB output circuit incidentally, leaving the c.r.t.'s cathodes at h.t. The fault occurred during the freak cold weather this winter, and we assume that the failure of the diode so soon after switching the set on, coincidentally with plugging the aerial in, must have been as much due to a sudden thermal change as to an electrical breakdown.

Within minutes, the intermittent total loss of green developed, and we found that the fault could usually be cured or instigated by panel tapping. All the soldering in the green channel appeared to be perfect, so as the RGB output transistors are BD115s, which have given us trouble in the past, we tended to suspect the green one (T26). A simpler course to start with however was to try a new TDA1327A colour demodulator i.c., since on this particular chassis it's a plug-in arrangement – changing a video output transistor on its heatsink can be time consuming. Unfortunately however the fault persisted.

The RGB channels are extremely simple, consisting of a pnp emitter-follower driving the output transistor, with d.c. coupling throughout. We decided to see whether we could pin-point the fault by finding out which voltages altered when the green was not present. It didn't take long to establish that the output transistor's base voltage disappeared, though the correct voltage was still present at the emitter of the driver transistor, clearly pointing to intermittency in the 180 Ω series resistor R177. The resistor is secured to a pair of short mounting pillars and, due to their close positioning, the leadout wires have to be bent at right angles almost at the ends of the casing. This had evidently put some internal mechanical strain where one of the leadout wires joined the resistive composition, with the result that light tapping caused this apparently – perfect resistor to go open-circuit intermittently. Anyway, a new resistor cured the trouble, and after readjusting the focus control and the first anode presets a perfect picture was obtained.

Teletext Decoder Update

Adding colour and other options to the Television teletext decoder

Part 2

Steve A. Money, T.Eng. (C.E.I.)

LAST month we saw how the colour control commands are decoded, and how the corresponding luminance signal is generated. In order to produce colour on the screen however we also have to create a pair of colour subcarrier signals which, when added to the luminance component, will produce a PAL compatible video signal.

The chrominance subcarriers are derived from a pair of chrominance signals representing R-Y and B-Y respectively. We shall start by examining the B-Y signal, since it's much easier to generate than R-Y.

The B-Y Signal

Some simple arithmetic with the equation for Y shows that the B-Y signal is made up from the following mixture of R, G and B components:

$$B-Y = 0.886B - 0.299R - 0.587G.$$

This can readily be generated, in much the same way as the luminance, by adding together appropriate proportions of the R, G and B logic signals in a resistor network (R19-21, see Fig. 1 last month). To cope with the minus signs, the logic signals for R and G are inverted. Thus if all three logic signals are at 1, corresponding to white, the R and G components together will cancel out the B component, giving a B-Y signal of zero.

At the start of every line of the signal a reference colour burst must be inserted. This burst, which occurs just after the trailing edge of the line sync pulse and lasts for about 2.25µsec, is used to synchronise the colour demodulator circuits in the receiver.

The burst pulse is produced by a monostable (IC17) which is triggered from the trailing edge of the line sync pulses. The B-Y burst pulse amplitude is adjusted to -0.5B by using the negative-going pulse from the monostable, feeding it to the matrix via R22. Adding the burst signal causes a bias at the B-Y output, so a further resistor (R23) to chassis is included in the matrix to compensate for this bias component.

At the output of the matrix, the B-Y signal swings positively and negatively about a mean level of some +2.5V. The positive swings produce a blue display whilst the negative swings produce the complementary yellow colour. Note that if B is off whilst R and G are both on, the result will be yellow. B combined with either R or G gives a lower level blue output, as required for magenta or cyan displays.

PAL Switching

An extra complication arises when we start to consider the R-Y signal. In the PAL system, the phase of the R-Y component of the colour subcarrier signal is reversed on alternate lines in order to reduce colour errors due to phase shifts during transmission.

To achieve this phase reversal requirement, we need a control signal which switches state on alternate lines. This is

obtained by using a 7474 D-type flip-flop (IC9) as a divide-by-two counter, driven from the line sync pulses.

Originally this divide-by-two counter was driven from the combined sync signal that comes into the options board. It was found however that although the divide-by-two circuit appeared to be running correctly the resultant signal would not unlock the colour-killer circuit in many receivers. As a result, there was erratic colour or no colour at all. The effect was apparently due to the divide-by-two circuit responding to the half-line period pulses in the field sync interval, and was solved by using a monostable to effectively filter out these half-line period pulses. The monostable IC16 has a time period of roughly 0.75 of a line scan period, and once triggered it will not respond to any pulses occurring during this time. The output from this monostable provides the clock drive for the divide-by-two circuit, which then produces the PAL phase switching control signal.

The R-Y Signal

Like the B-Y signal, the R-Y signal can be built up from R, G and B components which in this case come out as:

$$R-Y = 0.701R - 0.587G - 0.114B.$$

Once again a resistor network (R16-18) is used to produce the required proportions of the three input logic signals, but here the phase of the three signals must be reversed on alternate lines.

This phase switching is carried out by means of exclusive-or type gates (IC18). In a two-input gate of this type, when one input is held at 0 the signals at the other input simply pass through to the output. If one input is at 1 however the signals from the other input still pass to the output but this time they are inverted. By applying the PAL switching signal to one of the inputs of each exclusive-or gate and the colour drive signal to its other input, the required phase switched output signals can be produced for application to the resistor matrix.

The R signal gate is controlled by the \bar{Q} output of the divide-by-two stage, whilst the B and G gates are fed from its Q output. They always have the opposite phase to the R component therefore, as required by the R-Y equation.

A phase-switched burst pulse in the same phase as R is produced in a further exclusive-or gate and added to the matrix. To compensate for the bias effect produced by the burst pulse, a component from the Q output of the divide-by-two counter must also be applied to the R-Y matrix. This is fed in via R14.

The R-Y matrix produces a signal at a mean level of about +2.5V. In this case positive-going signals produce red on the screen whilst the negative swings produce green. The proportions of R, G and B have in fact been modified from the correct values to give a higher R drive and smaller B drive. This gives improved saturation of the red parts of the display.

When combined with the B-Y burst, the R-Y burst

signal produces a resultant burst signal which swings $\pm 45^\circ$ about the -B phase on alternate lines.

Subcarrier Generation

Having generated the B-Y and R-Y signals, we must use these to modulate a 4.43MHz colour subcarrier. What we require is a double-sideband suppressed-carrier chrominance signal. This involves the use of a 4.43MHz oscillator and a pair of double balanced modulator circuits.

We've used the National Semiconductors LM1889 i.c. (IC19) to perform this operation. This integrated circuit was originally made for use with TV games providing colour displays, and is designed to produce colour signals to the American NTSC standard. It contains a subcarrier oscillator intended to operate at the 3.83MHz NTSC subcarrier frequency, but it was found to work quite happily at the PAL 4.43MHz subcarrier frequency. There are two double balanced modulators for the R-Y and B-Y signals, and these are also suitable for use with PAL signals. In addition the device has a pair of v.h.f. oscillators and modulators for generating Band I signals, but these are not required for our application.

The oscillator is designed to generate two subcarrier signals which are phased 90° relative to one another. This is achieved by using two external RC phase-shift circuits, one producing a 45° lead and the other a 45° lag. The oscillator frequency is primarily controlled by the 4.43MHz external crystal XL1, whilst a trimmer capacitor (C11) is used for fine tuning and to adjust the phase of the feedback network to ensure proper oscillation.

The inputs to the two balanced modulators are fed in at pins 2 and 4, whilst a common reference bias voltage is fed to both modulators via pin 3. The subcarrier inputs to the two modulators are connected internally.

With a supply of +12V the modulator reference input should ideally be set at +6V, but for convenience we have used the +5V logic supply rail as a reference supply.

The R-Y and B-Y drive signals must now be arranged so that they swing positively and negatively about a nominal +5V level. Since the matrix outputs are at around +2.5V, a d.c. voltage shift is required. This is provided by feeding each signal through an emitter-follower (Tr2 and Tr3) and then tapping the drives for the LM1889 down the emitter load resistors. To allow the bias levels of the R-Y and B-Y signals to be adjusted for proper colour output, a preset potentiometer has been fitted in each emitter load (VR2, VR3).

A subcarrier output signal is produced at pin 12 of the LM1889. This pin is also one of the inputs to the v.h.f. modulator, whose other input goes to pin 13. To balance the internal circuits of the LM1889, pins 12 and 13 have been connected together. The chrominance signal from pin 12 is fed through an emitter-follower buffer stage (Tr4) and is then coupled via a small capacitor (C12) to the luminance signal output line where it's combined with the luminance and sync signals to form the composite video output signal.

Flashing Symbols

Symbols can be made to flash on and off if a flash control command is received. This effect is sometimes used to highlight a particular item on the page. A typical use can be seen on the Ceefax page 190, where an index of news pages is shown. Here the page number of the latest item to have been added to the magazine is flashed on and off. To restore the display to a steady state, a steady command may be sent. The following symbols in the row will then be

displayed normally again.

The flash and steady codes each produce a pulse at the 0 output of the 7442 decoder chip IC6. This signal is used as a clock pulse for a D-type flip-flop (lower IC8) which controls the flash operation. The D input of this flip-flop is fed from the delayed bit 1 signal to avoid timing problems at the start of the row of text.

When a flash command is received, the flash control flip-flop will be reset, since bit 1 is at 0, and its Q output will go to the 1 state. This output is used to open a 7400 gate (IC1, pin 9). The flashing rate of the symbols is set by a free-running oscillator, using the 555 timer device IC14. The rate is set at about one cycle per second. The signal from this oscillator is also fed to the 7400 gate (pin 10). Thus when flash is selected the output from the gate will switch at about one hertz. The output from this gate passes through a 7408 AND gate where it's combined with the reveal control signal, and then goes on to another 7408 gate where it switches the dot video input signal to the colour gate.

Thus when flash is selected the dot video signals will switch on and off at about one hertz, producing flashing symbols on the screen. The background colour is not affected by the flash pulses, and when a symbol is blanked by the flash signal its space will be displayed in the background colour.

When a steady command is received, the flash control flip-flop will preset. Its output will go to 0, closing the 7400 gate and forcing its output to a steady 1 state. This in turn allows the dot video signal to pass through unaffected and give normal display symbols. Only those symbols which are supposed to flash during a text row will be blanked by the one hertz flash clock signal.

At the start of each row of text it's automatically assumed that the display will be in the normal steady state. To ensure this condition, the line sync pulse presets the flash control flip-flop to its steady state at the start of each scan line.

Reveal-Conceal

When a conceal command is detected it will cause the 4 output line of the 7442 (pin 5) to produce a pulse. This in turn clocks the conceal control flip-flop IC9. The D input of this flip-flop is driven by a delayed bit 1 signal, and as a result the flip-flop goes to its reset, or conceal state, when bit 1 is at 0.

The output signal from the conceal flip-flop passes first through a 7408 gate, where it's combined with the flash blanking signal, and then on to a second 7408 gate where it controls the dot video signal which produces the displayed symbols. Those symbols following the conceal code will now be blanked out on the display.

Although part of the display on the screen may be concealed, the data for the blanked out symbols will still be retained in the page memory. In order to display concealed parts of the display therefore all we have to do is to override the conceal control flip-flop by forcing it into its normal reveal state. This can be done by means of a viewer operated switch on the front panel of the decoder. This switch is used to hold the reveal input line to the options card at 0V, which in turn forces the preset input of the conceal flip-flop low, causing the flip-flop to return to its reveal state. The dot video gate will now be released, allowing the symbols that were blanked out to appear on the screen.

It will be seen from the code table (Table 1 last month) that a contiguous graphics command will also produce a pulse at the 4 output of the 7442, and will therefore also

clock the conceal flip-flop. In fact it will produce the same effect as a reveal command. In practice it's unlikely that this command code will occur within a concealed portion of the display, since in most cases the concealed symbols are text, while the contiguous graphics code is rarely used anyway. This condition could have been avoided by using a more complex decoding scheme for conceal commands. It was felt however that the simplified decoding scheme used would be acceptable, though on a few rare occasions incorrect operation of conceal may occur.

It will be seen that there is in fact no separate code for reveal, though clearly it's desirable that only a part of a display row may be concealed. Careful study of the teletext specification shows that an alternative scheme has been provided for restoring the revealed display after a conceal command has been received in a text row. This is achieved by using any of the colour change commands to reset the conceal state. In our decoder this is implemented simply by routing the colour change clock pulse to the preset input of the conceal control flip-flop. Thus any colour code for alpha

or graphics will restore the display to the normal revealed state.

At the start of each text row the display is assumed to be in the revealed state. To ensure this, the line sync is coupled to the preset input of the conceal control flip-flop, forcing it to the reveal state at the start of each line.

The reveal switch on the front panel of the unit can be either a toggle type or a simple push-button according to the preference of the individual constructor. A push-button switch has some attraction here since it ensures that the concealed parts of the page will normally be blanked out until the viewer presses the reveal button to take a look at the answers to the quiz or whatever else may have been concealed on the page.

Correction

R21 in the B-Y matrix circuit should have been shown as 12k Ω instead of 15k Ω in the circuit diagram (Fig.1) shown in Part 1 last month.

The Grundig SVR VCR System

David K. Matthewson, B.Sc., Ph.D.

THE Grundig Super Video SVR4004GB is the latest in a long line of Philips' format based VCRs designed for sale to domestic users. Although the mechanics are designed around the Philips cassette with its concentric reels, this VCR will operate only with the special Grundig standard SVC (Super Video Cassette). The crafty inclusion in the VCR of an extra microswitch which engages in a lug in the plastic cassette housing ensures this. Grundig say that this is done because only specially well machined and assembled cassettes will give the consistently high standard of reproduction claimed for the machine. Rumours have it however that any recently produced Philips type cassette will work in the machine if the microswitch is, um, fixed. Note however that the specification of the oxide coat on the tape in the SVC cassette is considerably higher than that of the standard Philips type.

The SVR uses the two-head, slant azimuth, helical-scan recording/playback system which has become standard for domestic VCRs. In this system there's no guard band between adjacent tracks. Instead, the slant azimuth mounting of the heads is relied upon, the resultant recorded signals on adjacent tracks being out-of-phase with one another. This gives an acceptable level of cross-talk between tracks.

The tape speed is 3.95cm/sec, giving a recording time of four hours. This compares with a speed of 14.29cm/sec for the original Philips' one-hour format. Grundig had hoped to introduce a five-hour tape during 1979, but plans for this seem to have been delayed. The present SVR gives the longest playing time of any domestic VCR, but this is likely to be overtaken by the four hours per side Philips V2000 machine before too long. It's certainly a fast moving field! Trying to find an SVR4004 - or an ITT 240 (same machine, different sticky label) - to review turned out to be rather tricky - Grundig said there were only about 70 of them in the UK at the time.

When one eventually arrived in our workshop it turned out to be quite an attractive machine. Though it has few features which can be said to be truly unique, it gives a general impression of being well built, somewhat up-market from the Philips N1700. For a start, all the tape transport controls are solenoid operated, from a series of touch-buttons on the front panel or an optional remote control unit

The TV tuning section is very neat, incorporating a self-seeking unit and covering the v.h.f. Bands I and III as well as the u.h.f. Bands IV and V. The circuitry used is similar to that employed in some of the more expensive Barco colour television receivers, and an eight-channel preselector and l.e.d. display of the selected channel are incorporated.

As is standard practice on domestic VCRs, the machine incorporates a digital clock to enable unattended recordings to be made. The main advantage of the Grundig system over its rivals is that a delay of up to ten days can be selected between setting the machine and the recording taking place.

A picture crispener circuit is incorporated. This effectively enhances the horizontal definition on playback. An unusual feature is the large customer control, on the top, to adjust the degree of crispener (do some people really prefer a softer picture?).

A few neat features include the use of the front panel meter to display the approximate frequency of the selected TV channel, and also to give an indication of the tracking error in the playback mode. Tracking is a measure of how closely the alignment of the video heads with the video tracks corresponds to that during the recording process: the better the match, the better the picture. As previously mentioned, the SVC cassette incorporates an extra lug to activate a microswitch - a small l.e.d. on the front panel indicates whether you are trying to put a non-SVC cassette into the VCR! Another l.e.d. flashes on and off if the cassette breaks or becomes jammed.

The most common version of the VCR is the SVR4004GB. For about £30 more however you can buy the SVR4004GB-AV, which incorporates colour video in and out facilities as well as audio in and out. The basic machine has a microphone input socket only. Both versions have u.h.f. in and out sockets. The specifications of the three VCR formats based on the Philips cassette are compared in Table 1.

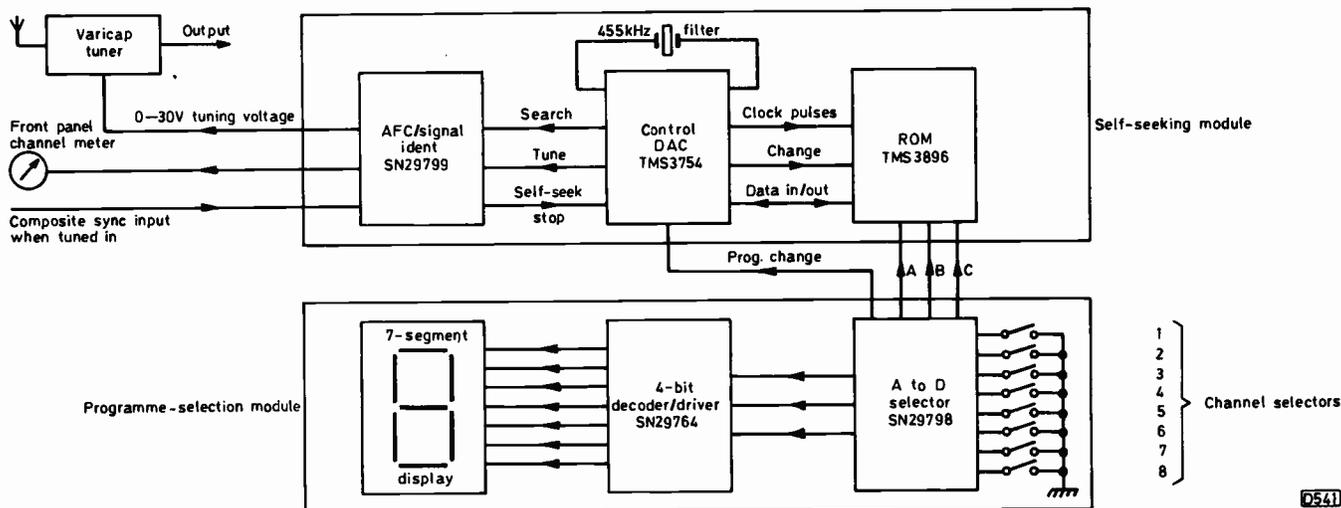


Fig. 1: Block diagram of the tuning arrangements used in the Grundig SVR4004 videocassette recorder. There are three basic modules, the tuner itself, the programme-selection module and the self-seeking tuning section.

Grundig have gone to considerable lengths to ensure that the Philips' format cassette is treated as gently as possible. In addition to the solenoid-operated controls and logic circuitry interlocks, there are various tape speed and tension sensors to protect the tape and the machine. Five separate motors drive the rewind, fast forward, play, cassette lace-up and head-disc functions.

Following this general outline of the VCR, we'll take a more detailed look at some of the specifications and the circuitry used.

The video heads are made of a glass impregnated ferrite material, which should be very resistant to wear but unfortunately has the property of being rather brittle. Video heads have never been the most robust of items however!

The use of side-by-side, out-of-phase video tracks improves the information packing density and thus tape costs, but the penalty is some increase in the luminance and chrominance signal cross talk. By tilting one video head 15° with respect to the other the luminance cross talk is reduced to an acceptable level, but this procedure is not sufficient to produce acceptable chrominance signals. To overcome this problem, alternate pairs of lines of chroma information from alternate fields are inverted and, on playback, compared in a comb filter. This results in cancellation of errors due to cross talk, giving an acceptable picture. As usual, the chroma information is recorded on the tape using a "colour under" system - the chroma carrier frequency is 562.5kHz.

Upon taking the lid off the machine, one is greeted by a very tidy layout. Most of the active components are mounted on plug-in boards which are attached to a mother

board. Unlike the Philips N1700 however, which uses the modular and mother board system, the Grundig units are not enclosed in small metal boxes and are not intended as non-repairable items. Indeed Grundig produce three adaptor cards which plug into the mother board and into which the module under test can be plugged. Not only do these adaptors allow the module to be removed from the depths of the VCR to be worked on, they also allow currents to be measured without the need to desolder components etc. Incidentally the set of adaptors fits not only the SVR4004 but also the older BK3000, VCR3500, and VCR4000.

Function Control Module

Although it might seem logical to start an examination of the circuitry at the tuner unit, I will instead look first at the function control module. This is the heart of the VCR, and is analogous to the Syscon module found in the Sony U-matic and Betamax VCRs. It accepts signals from the tape transport selectors (fast forward, rewind, etc.) as well as from the tape sensors, time clock, threading motor and microswitches which check the cassette compartment and cassette identification. The motor speeds are also checked by the Syscon module. A single 28-pin i.c. correlates this information, and will allow only permissible options to be performed. Checks are made to ensure that nothing goes wrong during operation - i.e. if the tape breaks during rewind, the signals from the rewind motor will alter and the function control module will stop the tape transport system and unthread the cassette. The beginning and end of the cassette are marked by conductive metal foil strips.

A neat touch is that when an unattended recording comes to the end the tape rewinds to the beginning and then stops, leaving the programme ready to watch.

Tuning System

When we turn to the tuner, the care which Grundig have lavished on this VCR again becomes rapidly apparent. The tuning arrangement consists of three modules: the varicap tuner itself, the programme-selection module, and the self-seeking unit. The assembly covers all the u.h.f. and v.h.f. bands used in Europe, on 625 lines only. The varicap tuner is quite conventional and needs no further explanation. The programme-selection and self-seeking modules are of more interest, as they rely extensively on digital integrated circuits. These i.c.s have been custom made for Grundig by

Table 1: VCR system specifications

System	VCR	LVC	SVR
Tape speed (cm/sec)	14.29	6.56	3.95
Writing speed (m/sec)*	8.1	8.1	8.2
Video track width (μm)	130	85	51
Guard track width (μm)	57	none	none
Video head inclination	0°	±15°	±15°
Maximum playing time (minutes) with VC60	60	130	220
Maximum playing time (minutes) (VC80)	80	180	300
		(LVC180)	(SVR5)

*The writing speed takes into account both the linear tape speed and the rotation of the video heads.

Texas Instruments, and two of them are closely related to microprocessor i.c.s. Fig. 1 shows in block diagram form the functional relationships of the component parts of the tuning assembly.

The programme-selector unit houses eight channel-selector buttons, an encoding i.c., and the seven-segment display and decoder/driver i.c. to indicate the selected channel. The output of the SN29798 encoding i.c. is fed to the TMS3896 programme memory i.c. in the self-seeking module. This is a microprocessor family i.c., and is of the ROM type (Read Only Memory). This i.c. stores in its memory the coded information corresponding to the eight selected channels and enables this to be recalled at any time when the appropriate channel selection button is operated. The main i.c. on this panel is the TMS3754, which controls both the programme memory and the automatic frequency control i.c. The TMS3754 operates as a type of digital-to-analogue convertor, taking from the ROM i.c. the coded pulses corresponding to say BBC-1 and converting them into a control voltage for the varicap tuner unit. Thus the ROM can be envisaged as a store of digital codes which correspond to certain tuning voltages. There are also facilities for manually adjusting the fine tuning of the picture.

The self-seeking unit scans the wavebands by producing a slowly increasing voltage which is fed to the varicap tuner. When an active TV channel is located, the sync pulses are detected and used to stop the scanning system. If the user wishes to retain this channel, he simply presses the store button and the digital code for that channel will be stored. The self-seeking board also provides an output to drive the front panel frequency meter, which gives an approximate indication of the channel selected.

All in all a very sophisticated tuning system – and one that calls for a good read of the instruction book before you try to use it! Incidentally, the channel frequency information stays stored in the memory i.c. even when the power is switched off.

Other Modules

The i.f. module has a single transistor plus two i.c.s. It's interesting to see that the various i.f. coils are etched on to the board, again showing the manufacturer's thoughts concerning ease of maintenance and factory setting up. I.C.s are also used in the sound module, which resembles that found in audio tape recorders and is quite conventional.

The other circuits, including the servo, u.h.f. modulator and audio/visual in/out board (found only in the AV version) are all straightforward and neatly designed.


Performance

Some of the test results obtained from the machine are interesting, especially when you consider the very slow tape speed. The audio response was measured as 85Hz-8kHz \pm 1dB, and to 10kHz \pm 4dB. (The audio response of the Philips N1700 is 100Hz-10kHz \pm 8dB.) The resolution was quite acceptable – the 2.5MHz bars on the test card were clearly resolved. With a pulse and bar test, the uppermost limit was found to be around 3.5MHz.

To sum up, a very well designed machine making the best of the concentric reel design of the Philips cassette. Grundig have obviously put a lot of thought and money into its design and production, but with new VCR formats springing up almost every month one can only wonder whether the SVR has any chance of lasting success. ■

next month in

TELEVISION

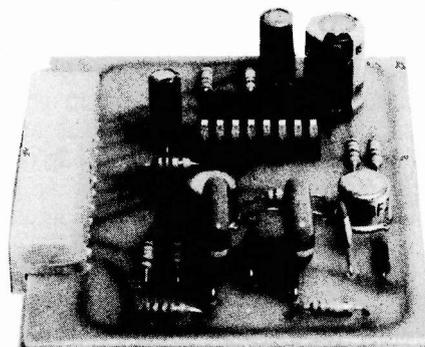

● MONOCHROME MONITOR CONVERSION

A monochrome set which can be picked up second-hand for only a few pounds can form the basis of a quality monitor. In this monitor conversion the i.f. strip and video output stage are replaced by an i.c. video preamplifier and a class AB output stage built on a single PCB measuring only 80 x 62mm. The circuit uses d.c. brightness and contrast controls and provides excellent picture quality. Suggested circuits for improved sync and sound will be included.

● TV IC FAULTS

I.C.s can be responsible for some puzzling faults in TV sets. They've been around long enough however for some fault patterns to have emerged. John Coombes summarises various i.c. troubles and comments on servicing techniques.

● SIMPLE SPG

The simplest way of generating sync pulses is to use a ZNA134 i.c. It's an expensive device however and some people may prefer a cheaper solution. Malcolm Burrell's circuit uses a couple of 555 timer i.c.s and some simple logic circuitry to provide a random-interlace unit at a very modest cost.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO (Name of Newsagent)

Please reserve/deliver the AUGUST issue of TELEVISION (55p), on sale July 16th, and continue every month until further notice.

NAME

ADDRESS

.....

.....

TV Servicing: Beginners Start Here . . .

Part 22

S. Simon

WE'VE spent some time discussing the various sections of a TV receiver and what goes wrong with them, mentioning expected meter readings and even the effect of the meter upon some circuits. It's been pointed out to us however that many readers are in some doubt as to the basic use of a voltmeter, ammeter or ohmmeter. Now long drawn out explanations can be pretty dreary reading, so we'll liven things up a bit by taking some actual practical examples of the use of a multimeter (one which performs most of the required functions), with the "hows" and "whys" included so as not to leave anyone out.

Let's assume first that you don't have a meter and are about to purchase one. What do you want?

Voltage and Current Ranges

The first basic requirement is that you need to be able to measure voltages from zero up to say 1,000V with a fair degree of accuracy. Bearing in mind the low voltages involved in transistor and integrated circuit operation, it's essential to be able to read these low voltages accurately and without too much eye strain. This is where the digital meter scores, as the read out shows the actual figures and only these, the size of the read out not being too important. Most will choose the traditional needle and scale type however, as these have certain advantages which may not be immediately obvious. Here the size of the scale and the ease with which it can be read are most important - it's of little advantage to have good accuracy if the measurement cannot be read accurately. Thus on the lowest scale the needle should deflect from zero to say 2.5V or 3V, showing each division between clearly, so that the difference between say 0.5V and 0.7V can be read without difficulty.

This requirement rules out the choice of a pocket meter of the lowest price. In addition, such a meter would have a pretty low sensitivity, which means that a lot of current is required to move the pointer. Since this current is drawn from the circuit to be tested, this disadvantage is too obvious to require comment - the current taken distorts the circuit's operation.

So the main voltage requirements are accuracy, nicely spread (easily read) scales, and low loading on the circuits to be tested. This latter requirement dictates a "goodness or sensitivity" factor of not less than 20k Ω /V, and the specification of the meter will state whether this requirement is met.

As well as the low voltage range already mentioned, full scale readings of say 10V, 25V, 100V, 250V and 1,000V are necessary, at least on the d.c. ranges. The a.c. ranges are less essential, but we will again need to be able to read up to 250V.

It's also essential to know how much current is passing through a particular circuit. For example, we've already seen that simply removing a fuse and connecting a meter in

its place will record the current being drawn by the circuit protected by that fuse. Thus when the meter is switched to the current ranges (amps, milliamps, microamps) it should be capable of recording the amount of current expected. If a meter is designed to pass only 500 mA say, it can't be used to measure for example the total current (l.t.) taken by a mains-battery portable TV set - the l.t. current (not the mains) could in this case well be some 1.5A. So one has also to look at this aspect or limitation of the proposed "best friend" of the service engineer.

Resistance Measurements

The other prime requirement is a good ohms range, since we may need to know the resistance of various items varying from say 0.5 Ω to several million ohms. We need at least three ohms ranges therefore to stand a dog's chance of getting an accurate reading, not forgetting that the high resistance ranges can also be used for a rough check on capacitors, recording their ability to charge up from the ohmmeter's internal battery. The low resistance range will also enable one to check loudspeakers. When the meter is applied to the loudspeaker's tags, a click should be heard if the coil is intact, the meter then indicating for all practical purposes the impedance of the coil - say 3 Ω , 8 Ω or 15 Ω - thus confirming or not its suitability for use in the circuit if the speaker is unmarked.

Earlier in the series we outlined the checks that could be made on transistors and diodes with the ohmmeter. Couple this with continuity checks on printed panels, leads and fuses etc. and one sees the importance of the ohmmeter, matched only by the voltmeter. The ability to measure current is secondary, since current consumption can be gauged by the voltmeter when it's applied across a resistor of known value (voltage divided by the resistance gives the current flowing, as you already know of course from Ohm's Law).

Meter Protection

There are several other factors to bear in mind. Among the most important is provision against overloads, which can occur due to incorrect connection of the meter or wrong range selection. Such things happen far more often than they should, to even the most careful. Whilst a fuse may be fitted there's an inevitable delay before this fails, and during this time the meter movement may be damaged. A fast-acting cutout is a most desirable feature therefore.

Add all these features together, and the choice of the cheapest meter must be the wrong one.

Getting Used to the Meter

Having obtained a meter and fitted the batteries

necessary to operate the ohms ranges, check these ranges to ensure that the pointer deflects fully when the test prods are touched together. Do this on each ohms range, so that the control provided (perhaps one for each range) can be set to indicate zero. Failure to obtain a full deflection (zero ohms) probably means that the batteries supplied are less than fresh.

Having happily zeroed the ohms ranges, one can sort out a few resistors of various values (known) in order to get used to the scale readings, and then go on to check transistors and diodes to see the different readings obtained by reversing the leads – remembering the fact that most meters have the positive side of the batteries brought out to the “negative” (black) terminal. This means that the “negative” prod will have to be applied to the anode (unmarked) of a diode in order to cause it to conduct, with the “positive” (red) prod applied to the cathode (marked).

Similarly, if one wishes to check an electrolytic capacitor it's the black probe that should be applied to the capacitor's positive terminal in order to polarise it correctly. When this is done and the highest resistance range is selected, the pointer will move over as the capacitor charges, and then settle back to a high reading. The deflection will depend upon the value of the capacitor. The capacitor will remain charged for a short time, and this charge can be read if the meter leads are removed, the meter switched to a low voltage range, and the leads are again applied but reversed (positive to positive this time).

Try these things to find out, but do start by making sure that the test capacitor is not still holding a charge from its last employment (if any). Do this by shorting the capacitor's positive and negative terminals together with a lead or a screwdriver blade – or, if the capacitor is known to have been recently connected in a fairly high-voltage circuit, use a low-value resistor to short the terminals (in order to limit the current flow – otherwise you could take up welding as a hobby).

You can of course check your own resistance with the meter switched to the high ohms range, holding one prod in each hand. You will probably record some 50k Ω if your skin isn't too thick, which explains why you can often check a transistor with the meter applied to its collector and emitter and your finger applied between the collector and base – provided you get the polarity right for the type of transistor, as outlined in more detail in a previous article.

Trying the Voltage Ranges

To get used to the voltage ranges, check any spare batteries which may be around. A one-cell type such as an SP2 (HP11 or HP7 for example) should record 1.5V according to its condition, and for this we would switch to the d.c. voltage 2.5V or 3V range in order to get something like a mid-scale reading. A battery such as a PP9 should record 9V approximately on the 10V or higher range, and the rule is to select the highest voltage range before applying the test prods if there is any doubt at all about the voltage likely to be present. If no satisfactory reading can be obtained from a known good source, the meter is probably switched to a.c. instead of d.c.

Checking the Mains Input Circuit

Having got used to the behaviour of the meter, we can now employ it to trace faults on a TV receiver.

The normal household has a single-phase supply consisting of a live and a neutral cable with a difference of

240V between them (r.m.s. value, since it's constantly rising and falling at 50Hz). There's also a connection to true earth made on the premises, and all appliances with an exposed metal surface must be bonded to this. The average TV receiver is adequately covered by plastic or wood, and does not have an earth connection.

When part of the cover is removed to expose the receiver's working parts, it must first be established that the main frame metalwork is not live. This may sound “old hat” to most of you, but we have to put safety first and cater for all. If the supply cable is connected to the supply source via a three-pin plug which is fused, the brown lead (old red) must be connected to the fused pin, which should be the live connection if the household wiring has been properly carried out. There's no guarantee that it has. In addition, all too often the supply plug is of the two-contact type, which is reversible.

There's always the possibility therefore that the metal parts of the chassis may be connected to the live side of the mains supply, or that the receiver is designed so that the “chassis” is always live with respect to true earth. It must be treated accordingly, and nothing which has an earth connection (this includes the aerial plug) must be allowed to make direct contact with it.

Your best friend is a neon screwdriver which is known to be working. It should glow clearly when applied to the live mains. If it also glows when applied to the receiver's chassis, either the mains connection is wrong (join in the lead?), the on/off switch is defective, or there is some other reason why the neutral return is not being made (break in the lead?) – or perhaps the receiver is of recent design, with a floating chassis due to the use of a bridge rectifier connected direct to the mains.

If a receiver shows no signs of life when plugged into the mains, it must not be assumed that the set is not live at some point or points. Indeed it must be assumed that the set *is* live until proved otherwise. Having proved that the *chassis* is not live, one then goes on to prove certain other points – the set's input fuse, the on/off switch or, if there's a dropper resistor in a convenient position, the tags of this. If there are still no signs of life, remove the supply plug from the mains and check the continuity of the supply lead with the ohmmeter.

Now let's go over that again, this time using the voltmeter. If the chassis is not live (neon check), clip the common (black) lead of the meter to the chassis (assuming that the set is an average table model, and not a mains/battery portable with an isolating transformer, in which case the only connection to the mains would be through the primary winding of this) and, with the meter set to 250V a.c. or higher, apply the red lead's probe to the set's fuse, the on/off switch's live contacts, or to any other point which should be at full mains potential. If no reading can be obtained, locate the ends (brown and blue usually) of the mains lead and apply the meter to these lead ends. If there's still no reading, remove the mains plug from the supply source and prove the continuity of the leads with the ohmmeter switched to the low ohms range. If the plug fuse is intact, the break is likely to be where the lead is captured under the point of entry to the plug. The fractured lead would have to be the live one (or both), since the neon check would have shown the presence of mains at the receiver if the neutral lead only had been open-circuit.

Defective Switch

The receiver's on/off switch is a suspect item, and can be checked with the ohmmeter if the supply is not connected or

with the voltmeter if it is. The on/off switch has four contacts, one pair to break the live mains connection, the other to break the neutral one. It's common to find one pair defective.

Blown Fuse

If the voltmeter or neon shows that the mains input fuse has blown, its condition will often give a clue as to the cause. If the fuse is severely blackened, it's likely that either the mains filter capacitor has shorted, thus making a direct connection between live and neutral, or that the h.t. rectifier diode has suffered a similar fate, the almost direct path from live to neutral in this case being through the surge limiting resistor, the diode and then its reservoir electrolytic capacitor which presents a dead short-circuit to a.c.

If the overload that blew the fuse is "farther in" the set, it would not normally have such a severe effect due to resistive paths. Thus the fuse, although open, would not present such a blackened appearance.

So if the fuse is blackened one would first locate the h.t. rectifier diode and check this with the ohmmeter on the low range. A reading of some 30Ω should be recorded with the prods applied one way, and a much higher reading when they are reversed. A low reading both ways indicates that the diode is shorted, or possibly that the small protection capacitor wired across it is defective — this is far less likely however. If the diode reads all right, find the mains filter capacitor — probably near the fuse or the on/off switch — and suspect this even if the meter shows no direct short when applied across it. If in doubt, unhook it and see if a replacement fuse holds. Do not leave the set working without a filter capacitor, as it has the job of absorbing high peak "spikes" on the mains waveform.

Heaters not Alight

If the mains voltage is known to be present at the fuse etc. but the valves are not heating there are several ways of tackling the problem. We have seen previously that the valve heaters are connected in series in the average type of set likely to be encountered — much like a string of fairy lights. The start of the chain is the mains supply live side, and of course there must be a return to neutral. Adding up the various valve heater voltage ratings will not produce a figure anything like 240V, so the difference must be dropped by something or some things. The something could be a single large wirewound resistor, the value of which can be calculated by dividing the voltage that has to be dropped by the heater current, which is normally 0.3A (300mA).

If for example we need to drop 80V, assuming that the valve heater chain total requirement is say 160V, as it may be if lots of valves are used, the resistor would need to be about 266Ω and its wattage rating would be 0.3A times 80V which is 24W — 30W would be an adequate rating.

This assumes that the heater current is raw a.c. It doesn't have to be. If there are fewer valves, as in most sets (perhaps only four or five), instead of using a very large resistor dissipating a lot of heat we can insert a diode in the chain. This will lop off half the a.c. waveform, providing a rippled d.c. supply. As a result, the voltage to be dropped will be somewhat smaller (not half, as may be thought, more like 30%). In such a design there will be a dropper resistor of about 160Ω (in the Thorn 1500 chassis for example it's 148Ω), and a diode of the BY126 variety.

In addition to the dropper resistor there may well be a thermistor to limit the current at switch on, when the valve heaters are cold.

There follows the heater chain itself. The first heater is usually the efficiency diode, say pin 4, with pin 5 leading off to the line output valve and so on through to the tube. The final heater connection may go either direct to chassis or through a network to provide a transistor supply line.

If the heaters do not light up but the supply is present at the supply fuse, the first suspect must be the dropper resistor — if for no better reason than that it's the most convenient point to check on most sets. It's essential of course to establish which section of the mains dropper resistor is used in the heater line — there are likely to be several sections, each performing different functions, and it's easy to be misled.

If there's doubt, start at the valve base of the efficiency diode and establish whether or not there is a high voltage at pin 4 or 5. If not, follow the relevant track or lead back to one of the dropper sections and see what's present at the other end of this section. Full voltage will probably be found here, proving that there's a fracture in this section.

If full voltage is present at both ends, carefully follow the circuit to the first valve heater as it's possible that there is a break in this feed line.

If the full voltage is present at the first heater pin, check at the next pin (4 or 5) to see whether this valve's heater is open-circuit. Then if necessary check through the chain until the point of no reading is obtained. This can be done with a d.c. voltmeter (250V range minimum) if there's a diode in the circuit, or switched to a.c. if there's no diode (GEC 2038 and back for example), or simply with a neon screwdriver.

No HT Supply

Another common symptom is that the set is quite lifeless except for the fact that the heaters are glowing. Here one would switch to 250V d.c. or more, again with the negative probe to chassis, and apply the positive probe to any convenient point which is known to be at h.t. potential when the set is working properly. Examples are the tags of the main electrolytic smoothing block, pin 9 of the PY801 (PY88 etc.), or the cathode of the h.t. rectifier diode.

One has to use a little caution here. It's possible for the diode to be working (a.c. applied to its anode and its cathode at full h.t.), thus charging the reservoir capacitor section of the main electrolytic block, but if the h.t. smoothing resistor (perhaps part of the dropper) is open-circuit there will be lack of h.t. elsewhere. The point about this is that even after the set has been switched off the reservoir capacitor will still be fully charged and will still indicate full h.t. when the meter is applied to it. This means that it has to be discharged before being handled. Since the fault is an open-circuit resistor, one can either bridge the suspect with a wirewound resistor of the correct resistance value and wattage rating, or discharge the capacitor to chassis using any convenient fairly low-value resistor. This is before getting down to fitting the correct replacement (don't leave a defective wirewound bridged as it may remake contact when hot, thus upsetting the operation of the circuit).

On the other hand it's quite likely that no h.t. voltage will be found at all. This suggests that the anode of the h.t. rectifier diode is not receiving its a.c. supply, due to the surge limiting resistor becoming open-circuit. This is a very common fault indeed, as the surge limiter leads a very hard life. A typical value for this item is 10Ω — higher in some cases, lower in others. If it's open-circuit, a.c. voltage will be recorded at one end only. Once again this resistor may form part of the mains dropper. If you use a neon tester for this check, you might expect it to glow fully when applied to one

end and not glow at all at the other because there's no through circuit. This is not always so however, and in fact the neon may glow at the "dead" end, albeit a subdued glow. This can be misleading to the uninitiated, and serves to demonstrate the more precise results obtained by using a multimeter.

Some other Checks

Whilst most checks are carried out with the negative probe connected to chassis, thus reading positive voltages at various points with respect to chassis and comparing them with those shown on the service sheet, it must be remembered that many receivers have lines which are negative with respect to chassis. In addition, readings obtained in this way may be meaningless or may actually interfere with the correct operation of the circuit. In such cases the voltage drop across a particular resistor may be more relevant, and many circuit diagrams show this sort of reading.


The meter itself can alter the working conditions of a circuit, since it requires current to operate it – more if it is of low sensitivity. This factor can often be used to our advantage. If the voltmeter is connected across a resistor, it forms a parallel resistive path or shunt of value depending on the meter's sensitivity and the range to which it's switched (so many ohms per volt, as specified). As a result, if a resistor is suspected of being "high", application of the test prods

across it will often produce a visual effect on the screen of a working set. We get this clue in addition to the voltage reading obtained on the meter. Obviously we're not talking about resistors with a value of a few thousand ohms or less. We're talking in terms of say $1M\Omega$ or more. Such resistors are often used in a.g.c., height and width circuits for example.

In the latter case there may be several resistors with values of well over $1M\Omega$, and there may be some doubt as to which is the cause of say severe loss of width. Whilst they can be checked "cold" separately, using the ohmmeter switched to the highest resistance range, it's often more convenient to leave the set on and apply the meter (switched to a high voltage range) across each suspect resistor in turn, noting the effect. There will be an effect if the suspect is good, due to the shunting effect of the meter. We would not be looking for small variations however.


Caution is needed here as there will probably be high boost line voltages (say 1kV) present across certain resistors, plus pulse voltages. It's imperative therefore to have the meter on the highest range. In addition the meter should not be left connected in the circuit for long – its presence may result in the line output stage being over driven (excessive width), with consequent risk of breakdown in the line output transformer.

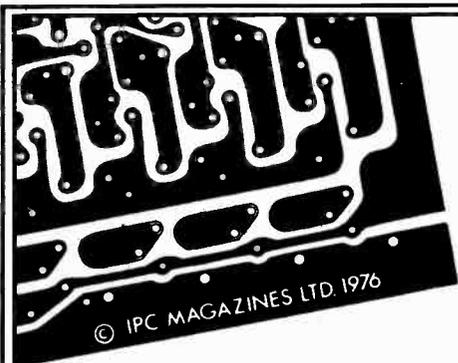The secrets of nearly all electrical circuits can be unravelled by judicious use of a voltmeter when the equipment is powered and an ohmmeter when it is not.



All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

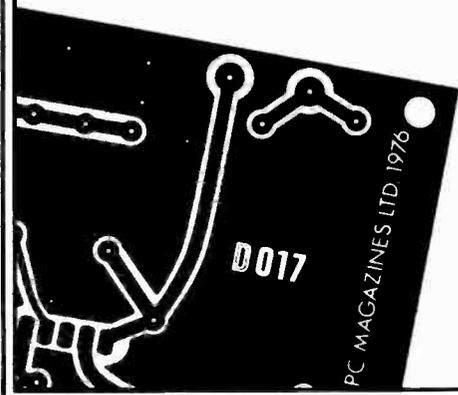Any correspondence concerning this service must be addressed to **READERS' PCB SERVICES LTD**, and not to the Editorial offices.



TELEVISION READERS PCB SERVICE

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£2.95 per set
December 1976	IC Sound Circuits for the Constructor	D009	£1.25
		D017	£1.25
March 1977	Teletext Decoder Power Supply	D022	£2.95
May 1977	Teletext Decoder Input Logic	D011	£9.80
May 1977	Single-chip SPG	D030	£3.00
June 1977	Wideband Signal Injector	D031	£0.65
June 1977	Teletext Decoder Memory	D012	£7.90
July/Aug 1977	Teletext Decoder Display	D013	£8.00
August 1977	Logic State Checker	D038	£1.50
September 1977	Teletext Decoder Switch Board	D021	£1.25
September 1977	Teletext Decoder Mother Board	D027	£4.00
October 1977	Teletext Decoder IF Board	D041	£6.00
Feb/March 1978	On-Screen Clock	D045	£6.50
April/May 1978	CRT Rejuvenator	D046	£2.50
May/June 1978	Test-Pattern Generator	D048	£8.50
Aug/Sept 1978	Diagnostic Pattern Generator	D051	£8.00
October 1978	Colour Receiver PSU Board	D052	£3.50
January 1979	Colour Receiver Signals Board	D053	£10.00
February 1979	Commander-8 Remote Control System	D054/5	£5.00 per set
March 1979	Colour Receiver Timebase Board	D049	£16.00
July 1979	Colour Pattern Generator	D062	£12.50
		D063	£8.50

To:— Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____

ADDRESS _____

Post Code _____

Colour Pattern Generator

Part 3

Malcolm Burrell

LAST month we described the analogue board and dealt with construction of the logic board. This time a brief note on constructing the analogue board, followed by suggestions for testing and setting up.

Constructing the Analogue Board

The analogue board is also used for the power supply components, except for the mains transformer. First, drill two holes in the heatsink. These serve the dual purpose of clamping the regulator i.c.s down and holding the assembly on the board. Use 6BA or similar nuts and bolts. It's prudent to smear a little heatsink compound on the components before finally tightening them down. If you are working to a tight budget, the heatsink can be omitted and the regulators fixed directly to the case metalwork: it will be necessary to lengthen their leads however, and will make fault-finding more difficult.

Having mounted the power supply components, make temporary connections to the mains transformer and measure the two supply rails to ensure that both 12V and 5V are present and correct – a simple precaution, which could prevent most of the i.c.s being damaged if the 5V rail is too high due to a fault.

Next fit the single wire link to the board, following this with the small components and a couple of sixteen-pin i.c. holders (or Soldercons). Finally fit coil L1 and the modulator. Check that all joints are secure, that there are no shorts, and that the right parts are in the correct places.

Testing and Setting Up

The analogue board is designed to sit on top of the logic board when everything is complete. While testing and setting up however it's probably better to lay them side by side. Tune in a monitor TV set (between channels 35-40) to lock in the pattern.

Although a scope has its uses, a monitor TV set is better for adjusting VR1 and VR2. A very good one would be something like an old Thorn 900 or 950 series dual-standard monochrome chassis (non-flywheel sync version) as this permits the line hold to be slipped, producing a side lock. The edges of the pattern can then be seen at the centre of the screen, on either side of the line blanking pulses. Failing this, try to reduce the scan amplitude so that the extreme edges of the pattern can be examined.

Adjust VR1 so that an equal amount of castellation is visible at each side of the pattern. There is not much doubt about this. Incorrect setting gives either a large, stretched pattern with one side missing or two patterns side by side.

Next slip the field hold to obtain a false lock, or reduce the height. Adjust VR2 for equal amounts of castellation at the top and bottom, without any white parts intruding between the pattern and the blanking pulse. Adjustment of this control moves the entire pattern up or down. Adjustment of neither of these controls is tricky however, and there's just sufficient range to allow for component tolerances.

Having obtained a satisfactory monochrome display, plug the unit into a colour set – with the a.f.c. disabled if fitted. With an insulated trimming tool, rotate C9 until the colour locks in. It's just like adjusting the reference oscillator in a colour set. Attenuate the signal input with say an 18dB attenuator, and trim if necessary for a more critical lock.

The whole unit can then be assembled, and any minor adjustments made after it's warm. There's a hole in the analogue board to gain access to VR1.

The coder is not perfect. If it overloads some sets, especially older ones, a green cast may be seen. It may be necessary to reduce the value of R8 (220 Ω). A 5,000pF ceramic capacitor to decouple pin 4 of the modulator may also be helpful if it's fitted as close to it as possible, with short leads. If there's insufficient colour, add capacitance (C18) across R13 in steps of 100pF until the correct level is found.

Since the modulators may vary, the value of R13 may need altering slightly to compensate. Should the frequency coincide with a local channel, the loop of wire over the BF197 in the modulator can be bent *slightly*, although some trial and error will be needed since it's necessary to remove the can for this, and subsequent refitting will of course shift the frequency again.

Fault Finding

After many hours of painstaking construction, the dreaded moment arrives and with bated breath the constructor switches on. The fact that perhaps nothing happens or the result is a jumble will probably be a disappointed relief. Dry-joints and other mistakes are quite easy to see on the analogue board. The logic board is where the fun begins! You could sit and look at it for hours – you *might* see something but, if you'll forgive the pun, you must adopt a logical approach.

If a locked raster is obtained on the monitor, the sync generator and modulator can be assumed to be in order. Glance at the board for missing through links and dry-joints, particularly with the top soldering.

Check that the 5V supply is present on all the i.c.s by measuring between their supply pins (pins 7 and 14 in most cases).

If a scope is handy you can proceed with that. You might however find it easier to locate faults by using the monitor itself, since by this means you can observe the relative

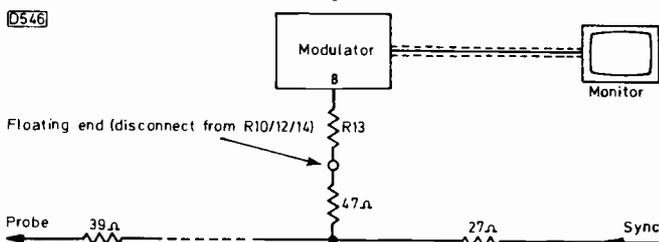


Fig. 6: Probe to enable a monitor to be used for fault-finding in the logic circuitry.

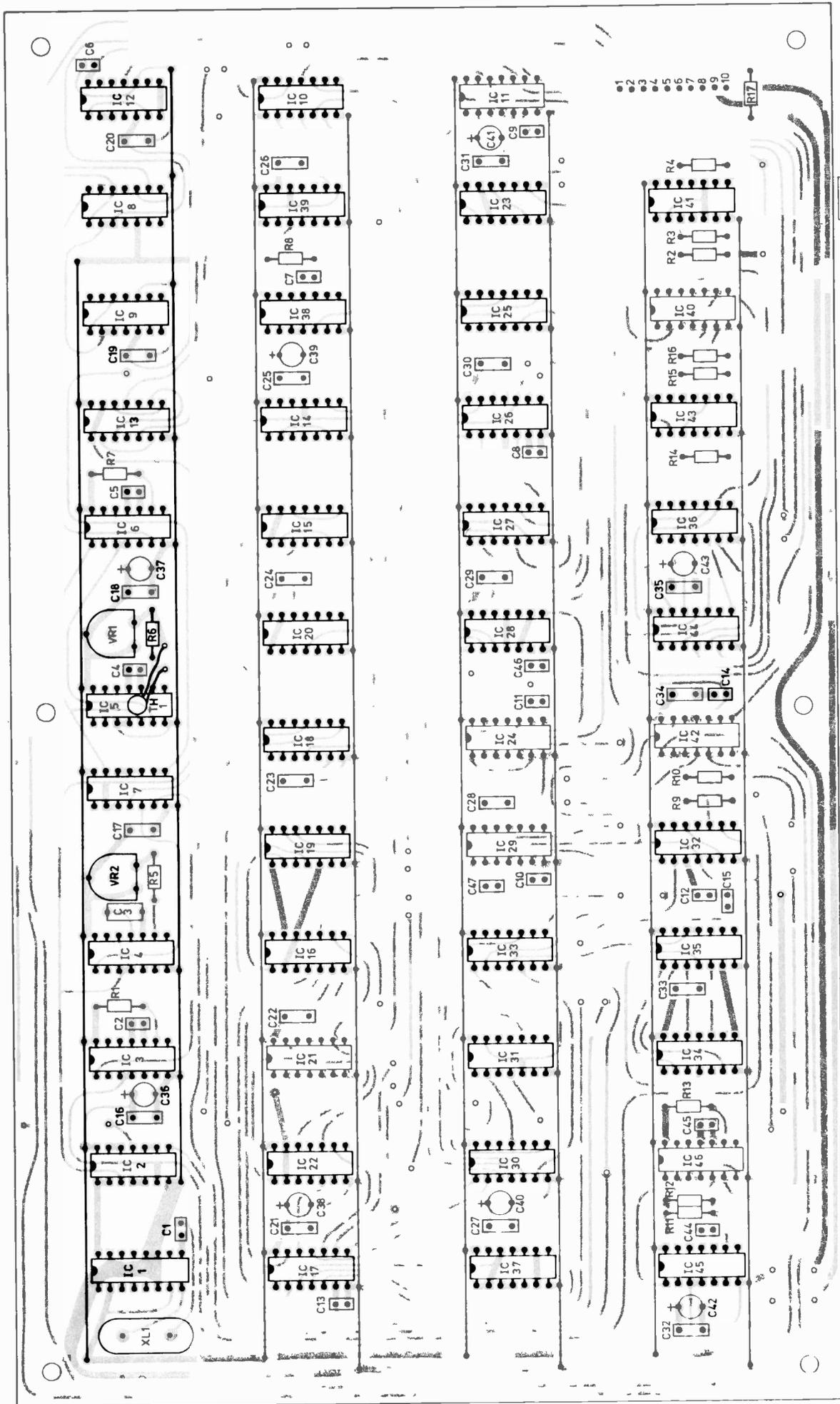


Fig. 7: Layout of the logic printed board. Note that there are print patterns on both sides of the board. Actual size is $7 \times 11 \frac{3}{4}$ in.

★ Components List

Analogue Board

Resistors:

R1	10k
R2	33k
R3	47k
R4	1k2
R5	220k
R6	1k
R7	560
R8	220
R9	8k2
R10	39
R11	100k
R12	27
R13	220
R14	68
R15	47
R16	100k
R17	1k
R18	220
R19	270
R20	1k
R21	220
R22	270
R23	6k8
R24	2k7
R25	1k2
R26	560
R27	47

All 0.25W, 5% carbon film

Capacitors:

C1	1n ceramic
C2	1n ceramic
C3	10n ceramic
C4	22p ceramic
C5	100n polyester
C6	82p ceramic
C7	10n ceramic
C8	47n polyester
C9	2-60p trimmer
C10	18p ceramic
C11	220p ceramic
C12	1/35 tantalum bead
C13	1/35 tantalum bead
C14	4700/25 electrolytic
C15	470n polyester
C16	220n polyester
C17	470n polyester
C18	220p ceramic
C19	10/16 tantalum bead
C20	22p ceramic

Semiconductors:

IC1	TBA540
IC2	TBA520
IC3	7812
IC4	7805
Tr1	BC212L
Tr2	BC212L
Tr3	BC212L
BR1	KBL02 (or RS Components type 262-113)

Miscellaneous:

L1: GEC C2110 series reference oscillator coil, part no. L420016
 Heatsink for IC3 and IC4: RS Components type 401-497
 UHF modulator: From Manor Supplies
 Coaxial cable
 XL1: 4.43MHz crystal
 Mains transformer: Secondary 15V, 3A. RS Components type 207-267 with the secondaries in parallel
 PCB D063

Logic Board

Resistors:

R1	5k6
R2	560
R3	220
R4	47
R5	560
R6	1k
R7	1k
R8	10k
R9	100
R10	100
R11	10k
R12	47k
R13	1k2
R14	100
R15	270
R16	560
R17	27

All 0.25W, 5% carbon film

VR1 4k7
 VR2 4k7
 Subminiature Horizontal mounting

Capacitors:

C1	22p ceramic
C2	2n2 ceramic
C3	470n polyester
C4	22p ceramic
C5	22p ceramic
C6	330p ceramic
C7	22p ceramic
C8	1n ceramic
C9	1n ceramic
C10	470p ceramic
C11	2n2 ceramic
C12	3n3 ceramic
C13	1n ceramic
C14	1n ceramic
C15	1n ceramic
C16-	
C35	100n ceramic for decoupling

C36-	10/35V tantalum bead, for decoupling
C43	
C44	1n ceramic
C45	1n ceramic
C46	1n ceramic
C47	3n3 ceramic

Semiconductors:

IC1	ZNA134
IC2	7408
IC3	74121
IC4	74121
IC5	74121
IC6	74121
IC7	7401
IC8	7493
IC9	7493
IC10	7404
IC11	7408
IC12	7490
IC13	7474
IC14	7474
IC15	7474
IC16	7421
IC17	7408
IC18	7432
IC19	7421
IC20	7421
IC21	7421
IC22	7421
IC23	7400
IC24	7432
IC25	7408
IC26	7432
IC27	7408
IC28	7411
IC29	7411
IC30	7432
IC31	7408
IC32	7408
IC33	7404
IC34	7404
IC35	7430
IC36	7411
IC37	7400
IC38	74121
IC39	7474
IC40	7408
IC41	7408
IC42	7410
IC43	7432
IC44	7404
IC45	74121
IC46	74121

Miscellaneous:

TH1 G23 or GL23
 XL1 2.5625MHz crystal from Senator Crystals, 36 Valleyfield Road, London SW16 2HR.
 PCB D062

Corrections: C20 was omitted from the analogue board circuit (Fig. 5). It's connected from pin 15 of IC1 to chassis. C11 was shown as 200pF in error. On the digital board circuit (Fig. 2) IC27 should be shown as type 7408 and C7 as 22pF. C47 (not shown) is between pin 8 of IC26 and the supply line.

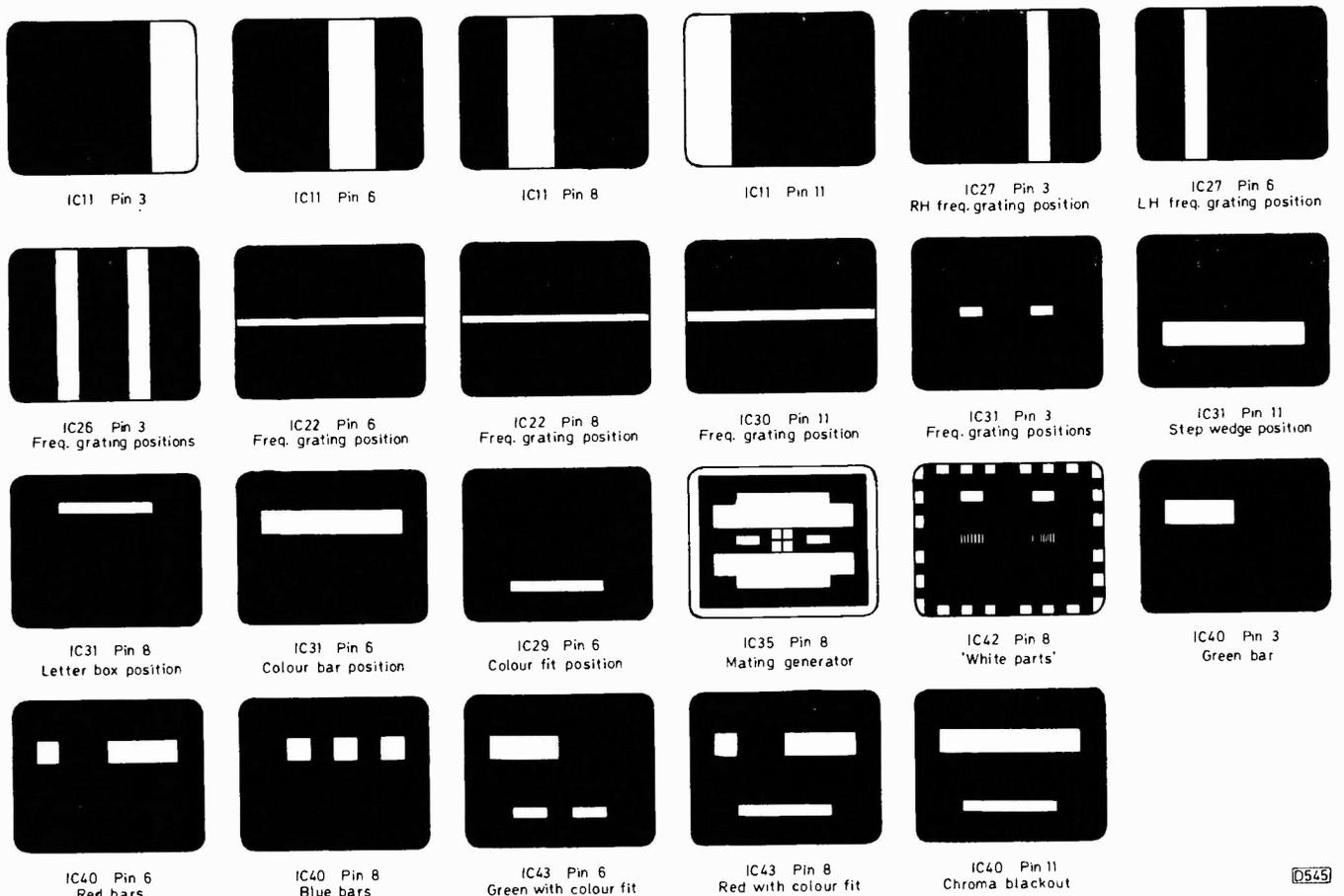


Fig. 8: Patterns which should be obtained at various points, using a probe and monitor.

positions of each shape in both the horizontal and vertical directions.

To do this, unhook R13 (see Fig. 6) from its junction with R10, R12, R14 (see Fig. 5). Unhook R14 from its printed link to the plug/socket at the end of the analogue board. Connect a 27 Ω resistor to this connection and fit a 47 Ω resistor in series with it. Connect the other end of this 47 Ω resistor to the floating end of R13. We now have a sync feed to the modulator, but no video. Take a short piece of wire to use as a probe, and fit a 39 Ω resistor to its end. Connect the wire to the junction of the added 27 Ω and 47 Ω resistors.

With careful tuning, it should be possible to monitor the outputs of most of the gates. Since there's no blanking signal however, there may be some pulling of the picture at times. An attenuator in the aerial output lead may help. Beware of stray pickup with this approach, since this will cause vertical lines on the picture and can be misleading.

TTL chips are very robust, and it's very unlikely that this method of fault-finding will cause any damage. Try to stay clear of the ZNA134 however – it's too expensive to take risks with.

Systematic Checks

Using the diagrams and tables in Part 1, together with the circuit description, first check the presence of waveforms 1 to 7. On a TV screen, they will show as vertical stripes. If these are OK, check the outputs from IC11. These should be as shown in Fig. 8: bear in mind that VR1 will affect their formation. Some examples of the waveforms and shapes to be expected from the frequency grating generator have been shown in detail. Other diagrams show the various complete shapes for the patterns. If they are not present, it will be necessary to trace back along the chain of gates until

an abnormality is found. Waveforms 8 to 12 may be tricky to hold on the screen, since they may disturb vertical locking, but subsequent shapes at the gate outputs should not present too many problems.



These are digital i.c.s and the outputs are always either on or off. White areas are therefore logic 1, black areas logic 0. This is an unusual approach to checking but it certainly works, especially if you can't afford an oscilloscope.

If the output from a gate is missing or incorrect when the correct inputs are apparently present, either there's a short circuit to the 0V rail or between the pins of the next chip it feeds. Faults in gates themselves are not as common as badly soldered joints. Chips incorporating bistables, such as the 7474 and 7490, are a little more prone to failure, but even here the above comments still apply.

Conclusion

Provided you are familiar with TV engineering and fault-finding, this circuit should not prove too difficult to construct, even if you've never handled digital i.c.s before. We have attempted to produce a cheap solution to the engineer's problem of lack of a test pattern at crucial times. Since individual requirements vary, it's possible that some readers will modify the circuit. We will be pleased to hear of any suggestions and modifications which may be made, and hope shortly to publish a short article on extending the range of the unit to utilise some of the waveforms to generate other patterns. For those who find the price of the ZNA134 i.c. daunting, we've produced a simple alternative in the form of a cheap, random-interlace s.p.g. Details will follow next month.

Analogue board details overpage

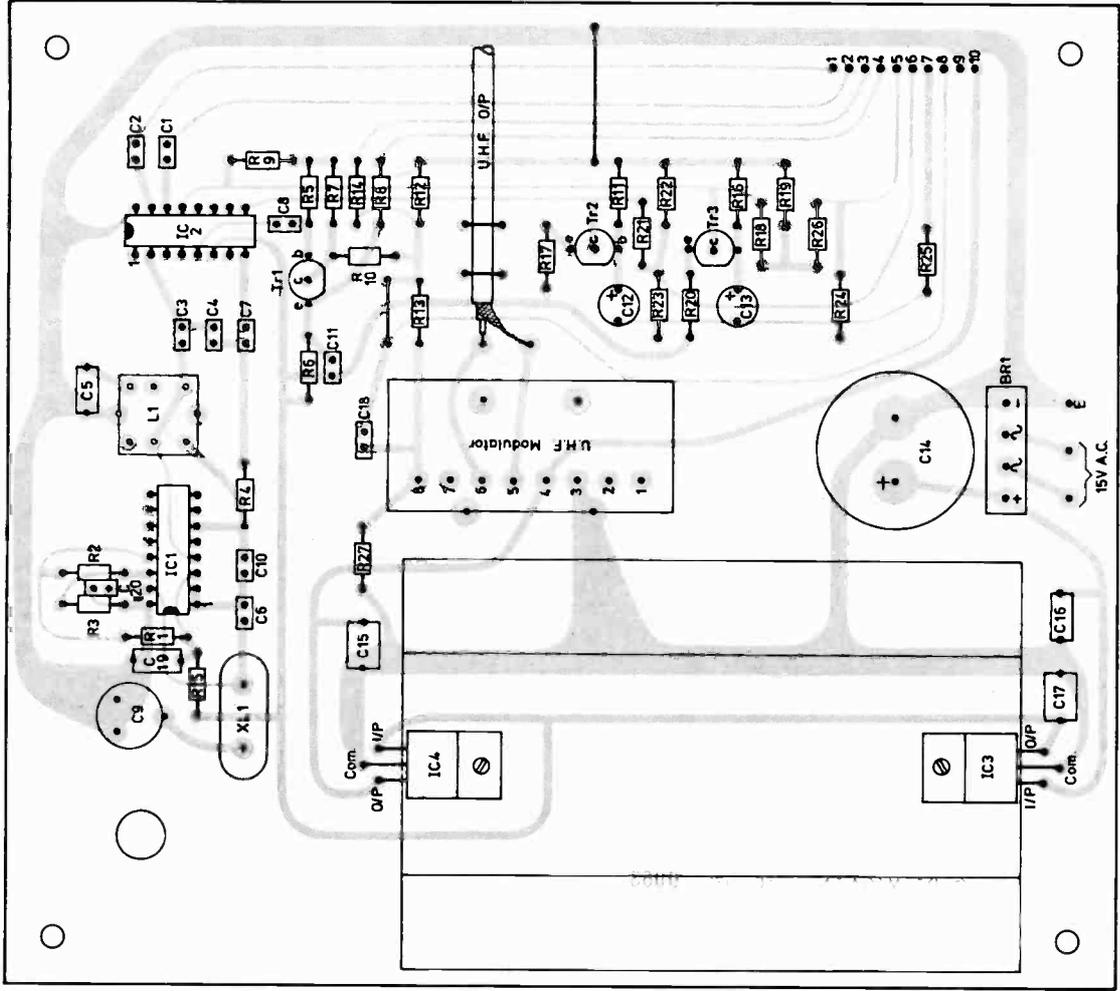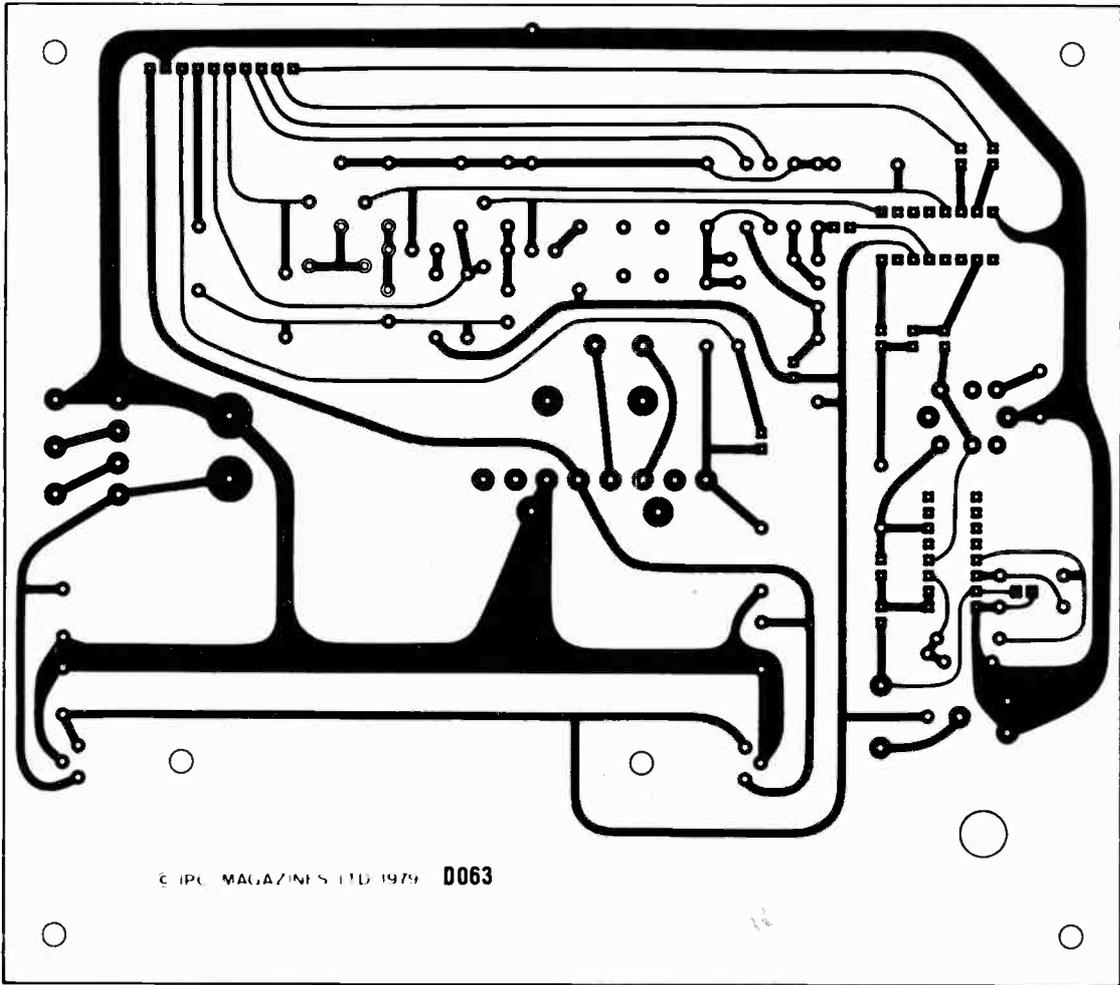

IMEEST

Fig. 9: Layout of the analogue board (right) and print pattern (left). The actual board dimensions are 7 × 6½ in.

Your PROBLEMS solved

Requests for advice in dealing with servicing problems must be accompanied by a 50p postal order (made out to IPC Magazines Ltd.), the query coupon from page 495 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

PYE 693 CHASSIS

The screen lights up two-three minutes after the set is switched on, but for the next nine-ten minutes the picture is very blurred. It then becomes sharp. Also, there's a loud crack and a flash from the line timebase area during warm up, when changing channels, or when the brightness is lowered.

The trouble is undoubtedly in the VDR from which the focus voltage is obtained. If one end connection has become loose, you may be able to repair it by bonding with wire. Be careful though, there's 25kV on one end!

DECCA 100 CHASSIS

There are two intermittent faults on this set. First, red patches appear at the centre edges of the screen. They are most noticeable in white areas of a monochrome picture, though they can be seen on some colour pictures. They don't vary when the colour control is adjusted. The purity has been adjusted, improving matters, but the fault is still visible. The tube has also been degaussed. Secondly, patches of green and black vertical lines appear even more erratically. They are visible on black backgrounds only, and only one patch at a time appears.

The patch problems are certainly due to impurity, and are a function of the shadowmask temperature. This accounts for their intermittency. The two remedies which we find seldom fail are to readjust the purity when the set has been running for some time, and to run the set at lower brightness and contrast levels. This will keep the mask cooler and also provide a much better picture.

RANK A774 CHASSIS

The line and field sync are very weak, the picture pulling over to the left and rolling every minute or so. The fault disappears when the printed board is flexed, but no breaks can be found in the tracks. The symptoms also disappear after the set has been on for about an hour.

The trouble is due to poor contact between the tags of the vertical struts on the main frame, at either side of the tube neck. These tags protrude through the panel in about four places, from top to bottom. First remove the solder from those earthing points to expose the tags. Clean the tags thoroughly (you'll probably notice that the solder never "bit" into them all in the first place) and tin them. Then resolder, and run a lead from the top to the bottom to ensure that the earthing is good even without the efficient contact of one or more of the tags. Solder each lead in four places in order to back up the vertical metal strips.

BRUNSWICK CSB2206

I've been unable to identify this 22in. hybrid colour set. The fault is no raster, though the e.h.t. is present and correct.

The set is probably basically the same as the Decca 20 series chassis. As there is no screen illumination though the e.h.t. is normal, check the c.r.t.'s first anode voltages (should be over 400V) and its cathode voltages (should be under 200V). High cathode voltages would suggest a low-emission PL802 luminance output valve or incorrect operation of this stage.

RANK A816 CHASSIS

The sound is o.k. on this set, but the tube heaters don't light up and there's no spark from the final anode of the c.r.t. I've checked the c.r.t. heaters, which are in order.

Since the sound is normal and the l.t. supplies are obtained from the line output transformer, it would appear that the line output stage is working. The TV20 e.h.t. rectifier stick could be open-circuit, removing the e.h.t., while 3R114, which is in series with the c.r.t. heaters, could be open-circuit to remove the heater supply.

SANYO CTP 5101

The trouble is arcing from the flyback transformer T904, where the lead goes to the e.h.t. rectifier. Does this mean that the e.h.t. is too high for some reason, and how do I go about testing when the arcing starts immediately the set is switched on?

This is a fairly common fault on these sets, and is due to the insulation breaking down around the high-voltage connector. The only cure for the problem is to fit a new transformer.

BUSH TV125

There's a fuzzy dark patch, about 4in. in diameter, in the centre of the screen. Also the picture is split, e.g. with a newsreader the right-hand half is on the left and vice versa. With more than one object on the screen, nothing can be seen properly.

First get the line hold right. If the line hold control 3RV5 can be adjusted so that one complete picture hovers on the screen (without actually locking), replace the flywheel sync discriminator diodes (top right side). If you cannot manage to resolve one picture, check the PCF80 line oscillator valve 3V3 by substitution and the setting of the preset line hold control 3RV3. Once a steady picture has been obtained, check the DY86 e.h.t. rectifier valve or, if the picture is of insufficient width, the PL36 line output valve.

TELETON C18BS

There's no sound or raster, though the five fuses are intact and voltages are present at the mains transformer secondaries. The tube heaters, also the channel lights, glow. The touch-type channel selectors work, but channel one does not appear automatically when the on/off switch is operated.

The touch-tune system depends on a voltage feed from the line timebase, which is clearly not working, cutting off the rest of the set. Check whether the 120V line is present at the output of the series regulator transistor TR708, and that it's reaching the collector of the line output transistor TR304. If not, check TR708, R414 (10Ω), L403 etc. If power is reaching TR304, suspect loss of line drive – there should be 89V at the collector of the line driver transistor TR303.

INTEL BPT12 PORTABLE

This portable, made by Amerex, has a damaged tuner unit. I've been unable to find any source of spares however. Any suggestions for alternatives?

The JVC 3020 uses a similar tuner to that in the Amerex set. The mechanical fitting differs however, and you may have to redrill the fixing holes. Most other Japanese tuners incorporate a built-in i.f. preamplifier, which would complicate adaption.

THORN 3500 CHASSIS

The line output transistor was replaced (had been found short-circuit) and the set e.h.t. control was then adjusted for minimum e.h.t. consistent with sufficient width (h.t. at 60V, I can't measure the e.h.t. itself). The set was o.k. for a time, then on switching on the final anode kept arcing loudly to the metal shield. I cleaned around the anode connector and the insulated metalwork, and reduced the h.t. slightly (width still adequate) but there's bad frying to the outer tube coating, so the e.h.t. is obviously too high – increasing the h.t. above 58V makes it worse. The tripler has been replaced and the preset controls set up. The voltage across R907 in the beam limiter circuit is slightly high at 1.7V.

We feel that it's essential to be able to check the actual e.h.t. voltage. If this is not in excess of 25.5kV, cleaning and polishing the appropriate areas of the c.r.t. bowl should be sufficient. If the e.h.t. is excessive, suspect the flyback tuning capacitor C518 (0.028 μ F). Note that there are alternative line output stage transformer connections and that these affect the width – details are given on card 9 in the service manual.

PYE 693 CHASSIS

The set gives excellent results but there appears to be an intermittent power supply fault. The mains lead, plug etc. are free of physical defects, but when the set is switched on from cold the raster and sound collapse then return within a split second – as though there was a momentary power supply interruption. This happens up to a dozen times, after which the set operates normally.

The trouble sounds like a thermistor with a dry-jointed end. The one to suspect is the surge limiter R305 (VA1104) in the h.t. supply, on the panel behind the e.h.t. box. A disturbance test should show a spark at the offending end.

TELETON TH14

There's a very strong "shadow", or second image, to the right of the pictures on the screen. Sometimes however the display changes, the entire picture becoming negative.

The double-image effect could be due to the set being operated from its own loop aerial or a badly sighted outdoor aerial. The entire picture becoming negative suggests a worn tube however, the weakness possibly being accentuated by over-advanced contrast and/or brightness control settings. Reduced tube emission would also make it difficult to see the picture in bright daylight, with silvery highlights and a tendency to defocus at the edges. If the tube is at fault, the picture should return from negative to normal when the contrast/brightness levels are reduced. It would also be worth ensuring that the 1X28 e.h.t. rectifier is in good condition.

If the negative picture can't be restored to normal when the contrast/brightness levels are reduced, the fault could be a video one, probably the SE7010 (or 2SC686) video output transistor TR205 itself. In this case, compare the

working voltages in the video output stage under normal conditions and when the picture is negative.

The fact that the picture goes negative only on occasions could be due to different signal strengths on the channels available. Variations in a.g.c. level could also produce a negative picture if the tube is weak, but this should be accompanied by sound level variations and possibly a tendency to cross-modulation (vision on sound or vice versa).

Note the effect (if any) the contrast control has when the negative picture develops – there could be an intermittent short in the 100 μ F electrolytic (C235) connected from its slider to chassis. If the tube gives a bright picture, free from the silvery effect, change this anyway to be on the safe side. Also check that the peaking coil in the video output transistor's collector circuit is not intermittently open-circuit.

ITT CVC8

The trouble with this set is pincushion distortion, which is most pronounced at the top. Adjusting the associated controls R362 and L125 has no effect on the picture geometry at all.

First check for dry-joints (under the transducer, and on the print connection to pin 1 of the line output transformer). R362 or R364, which are in series across the transducer, could be open-circuit, or the transducer itself defective. Once the cause of the trouble has been put right, adjust R362 and L125 for optimum picture geometry.

ITT CVC9

The tube is blanked out at the centre, and to avoid damage the tripler must be disconnected. The RGB output transistors are all switched hard on – only 15V at their collectors. There's 15V at the RGB output pins of the TDA1327A colour demodulator/matrixing i.c. instead of 6V. Removing the i.c. results in the voltages at the collectors of the RGB output transistors rising, but fitting a replacement does not cure the fault.

The d.c. levels at the RGB output pins of the TDA1327A i.c. are under the control of the voltage at pin 3 (luminance input). You'll probably find this wildly incorrect. If so, check the beam limiter transistor T24, the voltage at the cathode (pin 9, sensed to give the beam limiting action) of the PL509 line output valve, and the presence of 15.8V at the top of the preset brightness control R90. If these points are in order, check the black-level clamp diodes D21 and D22.

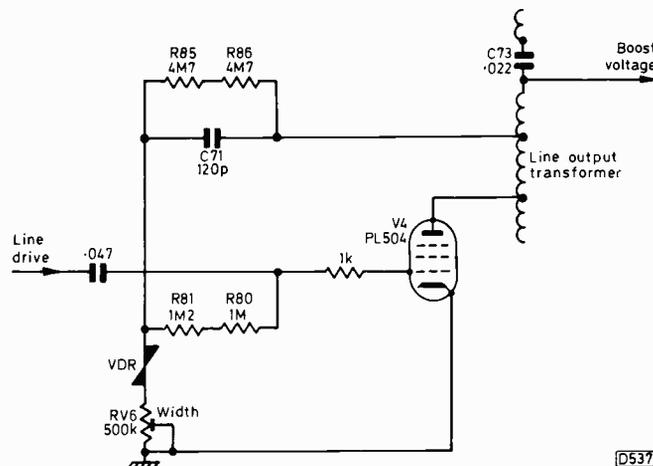


Fig. 1: Width control circuit, Pye 169 chassis.

PHILIPS G6 CHASSIS

Two coloured bands, blue and green, move slowly up and down the screen. They are also present on a monochrome display.

The problem is hum on the signal. First check the PCF200 colour-difference output/clamp valves for heater-cathode leakage – preferably by substitution. If the trouble persists, the most likely cause is hum on the l.t. lines, probably due to C1019/20/21. Make sure they are properly earthed before replacing them.

TEST CASE

199

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

A Pye colour set fitted with the 691 hybrid chassis suffered from a change of colour from one side of the screen to the other. This became increasingly apparent the longer the set remained in operation. The symptom was present even with the colour control turned right down, so it was concluded that the fault had something to do with the tube's d.c. conditions.

It was decided to look first at the control grid circuitry, since this chassis uses colour-difference drive, i.e. the three control grids are driven by the three separate colour-difference signals while the luminance signal is applied to the cathodes. There are three PCL84 valves on the colour-difference amplifier panel, one each to drive the red, green and blue grids of the tube. In each case the pentode is the output section of the valve, a.c. coupled to the tube, the triode section acting as a driven clamp, i.e. it's switched on once each line by a drive pulse applied to its grid. The purpose of the clamp is to hold the d.c. conditions steady during the line scan. The symptom gave the impression that the d.c. conditions were changing during each line scan, so the first line of attack was to check the clamp valves and associated components.

To isolate the stage responsible for the colour drift, the three c.r.t. guns were switched on individually. The blue raster (red and green guns off) showed up the symptom far more dramatically, so the blue PCL84 was replaced. This failed to provide any improvement, so as a further check on the valves all three were interchanged. Once again the fault remained the same.

The technician then consulted the circuit diagram and noted the high-value (8.2M Ω) anode load resistors in each clamp stage. Such resistors tend to change value, but on checking their values all three were found to be within the tolerance range. The one in the blue circuit was nevertheless changed, to be on the safe side, but again the fault came up as before. It was next decided to make sure that the clamps were actually operating, by checking that the drive pulses were pre-

sent. Connecting the oscilloscope up proved that everything was in order in this part of the circuit.

After making further checks in the blue colour-difference amplifier circuit, the technician resolved the problem by replacing one small component. What is the most likely suspect? See next month for the solution and a further item in the series.

SOLUTION TO TEST CASE 198

–Page 439 last month–

There are two basic width control arrangements used in conjunction with valve line output stage width/e.h.t. stabilisation circuits. Usually the width control is connected in a resistive chain between the boost rail and chassis, its slider being connected via a high-value resistor to the line output valve's grid bias network. The alternative arrangement, used in the chassis in question and a number of others, is to connect the control between the VDR and chassis – see Fig. 1. In this particular circuit C71 couples flyback pulses to the VDR, which rectifies them to produce on the capacitor a d.c. bias voltage proportional to the flyback pulse amplitude and hence the e.h.t. To enable the width control to be used to set up the circuit, a d.c. path is also necessary. This is provided by the two high-value resistors R85 and R86, which are effectively connected from the boost rail to chassis via the VDR and the width control.

There's a high d.c. voltage across R85 and R86 therefore, and in addition they are subjected to the high-amplitude flyback pulses. Now resistors are not too happy when subjected to high-voltage stress, and tend to change value – usually going high and tending towards open-circuit. With a pair of resistors in series, as here, the stress will be divided between them. This helps, but the trouble is still one to bear in mind. The technician concerned was aware of this, and the reliable and swift method of checking he adopted to prove the goodness or otherwise of the suspect resistors was to use the meter itself as a shunt resistor.

The meter reading obtained is of little significance, but when making shunt checks while watching the display any change brought about by the checks is immediately apparent.

A 20k Ω /V meter switched to the 240V f.s.d. range has a terminal resistance of 4.8M Ω – just right for shunting 4.7M Ω resistors! The test proved of course that the first resistor tested, R85, was abnormally high in value. The slight overscan produced was due to the fact that the resistor was not completely open-circuit – the net resistance present was less than 4.7M Ω therefore. Replacing the resistor resolved the fault without further ado.

QUERY COUPON

Available until 18th June 1979. One coupon, plus a 50p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 493.

TELEVISION JULY 1979

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R 0NE. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £9.50, Overseas £10.50 per annum payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Manufacturers Surplus Components FIT THE RIGHT PART

300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt resistors £1.50
 150 mixed 1 and 2 watt resistors £1.50
 300 mixed **Capacitors**, improved pack, most types £3.75
 100 mixed **Electrolytics** £2.20
 300 mixed **Printed Circuit** mounting **Components** for various TVs, resistors, caps etc. £1.50
 300 printed circuit **Resistors** $\frac{1}{2}$ to 4 watt £1.00
 100 **High Wattage** TV resistors, **Wirewound** etc. £2.75
 100 mixed miniature Ceramic and Plate Caps £1.50
 100 mixed polystyrene capacitors £2.20
 25 mixed **Pots and Presets** £1.20
 25 mixed **TV Presets** £1.00
 20 assorted **TV VDRs** and **Thermistors** £1.20
 10 assorted **TV Convergence Pots** £1.00
 20 assorted **TV knobs**, includes push button, chrome, control types etc. Mostly Thorn and ITT £1.00
 10 assorted **Valve Bases**, B9A, ceramic, EHT, etc. £1.00
 20 assorted **Sync Diodes** blocks for various TVs £1.00
 25 assorted **Pulse Caps** high voltage £1.25
 10 **Spark Gaps** £1.00
 20 assorted **Zener Diodes** 1 watt and 400MW £1.50
 100 **Mixed Diodes**, includes zener, power, bridge, varicap, germanium, silicon etc. All full spec. £4.95

NEW
 4-433 C.T.V. Crystals
 Long Leads £1.00 each
 3 for £2.50

New Improved Transistor Packs
 100 **New and Marked Transistors** including: BC148, BC154, BF274, BC212L, BF200 and lots of others only £4.95

200 **Transistors** as above and including 2N3055, AC12B, BD131, BFY50, BC238, BC184L only £9.95

Why Buy Expensive Triplers!
 Repair your old 5 and 3 sticks at a Fraction of the Cost.
 10 Replacement Rectifier Sticks (Thorn). £1.00

Special TV Bargain Parcels

Lots of useful parts including damaged panels, tuners, components etc. 10lb for £7.50
Hardware Pack
 Includes BA nuts and bolts, nylon, posidrive, self-tapping "P" clips, cable markers, clamps, fuse holders etc. £1 per lb.

THORN SURPLUS

3500 Series **Scan Coils**, new and boxed, complete with convergence yoke, purity assembly, static controls, leads and sockets £5.25
 3500 **Focus** units with metrosil £1.50
 8500 **L.O.P.T.** windings £2 pair
 1500 **Multi Cap. Replacement**. £1
 3500 "625" line **VHF Kit** for wired systems £9.50
 4 **Knobs** black with chrome caps to fit ITT, Thorn, GEC and most small diam. shafts 60p per set
 1500 **bias caps** 160 μ F 25V 10 for £1.00
 950 rotary transistor tuner with leads and slow motion drive £3.00
 950 bottom panel complete with i.f.'s switch etc. £3.00
 950 line transformer (not Jellypot) £2.50
Convergence Pots with knobs. 5 Ω , 10 Ω , 20 Ω , 30 Ω . 8 of 1 type £1.00. 8 of each £3.50

SAVE THAT TUBE.
 Fit our **C.R.T. Isolating Transformer**. Ideal for HTR./Cath. Shorts. 200-220-240 inputs. 750-900 MA outputs with thermal cutout. Made for **Thorn 4000 C.T.V.** but works O.K. on other sets.
 £2.00 each 3 for £5.00

MISCELLANEOUS

Bush CTV 25 Quadrupler Remo type Q25B. equiv. to ITT. TU25 30K. with mounting brackets. £4.25 each. 3 for £10

GEC single standard, hybrid chassis. convergence panel. Brand new, complete with plugs and leads **Focus unit** with lead, £2.50

for above chassis £1.50
ITT Featherlight Super. Side Chassis, with controls, V. Cap Tuning Panel, Regulator, P/Button Switches, Bridge

Rec. etc., etc. £4.95
 I.C. for above £1.00

Hitachi Miniature Transistor Tuner, spindle fixing. As fitted to various portables, ITT, Mentor, etc. £6.30

SPECIAL OFFER

GEC transistor rotary tuners with 147 Ω + 260 Ω 50p 3 for £1.00
 2010 Series £2.50

KB VC3 transistor tuner £1.50

ITT VC200 transistor tuner (Philips type) £1.50

ITT CVC5 power panel. New but five resistors never fitted £1.50

Pye 697 line and power panels, damaged or some bits missing but invaluable for spares £2.00

Pye mono mains droppers with fusible link. 147 Ω + 260 Ω 50p 3 for £1.00

Decca "Bradford" C.T.V. triplers 25KV £3.00 each 4 for £10

Portable TV EHT Sticks "Siemens TV 18 KV". Fit most portables 50p each 3 for £1.00

Pye 18" CT200 V. Cap P/B Assembly with leads and plug £1.20

Luminance Delay line. 7 $\frac{1}{2}$ ". R.B.M. etc. £1.00

EMO. On/off switch £1.00

EMO Convergence Panels untested, ex. T.V. £3.00

G.E.C. S/S Hybrid Focus Assembly with lead £1.50

2 x **Coax Sockets** on plates suitable for various T.V.s £1.00

White Ceramic TV Resistors 20 Ω 16W, 180 Ω 11W, 13 Ω 11W. 10 of any one type £1.20
 10 of each type £3.00

2.2k fusible, vertical mounting **Screen Feed** resistors 9 watt 8 for £1.00

0.47 Ω $\frac{1}{2}$ watt emitter resistors 40 for £1.00
 10 μ F 400V modern Small Type 8 for £1.00

4.7 μ F 63V 20 for £1.00

1000 μ F 16V 10 for £1.00

Bias Caps 330 μ F 25v 10 for £1.00

470 μ F 25V 10 for £1.00

160 μ F 16V 10 for £1.00

Avoid Lethal Shocks
 Buy our specially designed

EHT Probe, removes high voltage charges from tubes, caps, etc. Heavily insulated with lead and earth connector 80p each

B9A P.C. valve bases 20 for £1.00

EY87/DY87 EHT bases 10 for £1.00

PL509/PY500 ceramic bases 10 for £1.00

20mm Antisurge Fuses. 800MA, 1A, 1.25A, 1.6A. 12 for £1.00

2A, 2.5A, 3 15A 100 for £7.00

TH1 thermistors 6 for £1.00

TH3 thermistors 10 for £1.50

Aluminium **Coax Plugs** 8 for £1.00

Metal Coax Couplers 8 for £1.00

200V 1A Diodes 10D2 (equivalent to 1N4003) 20 for £1.00

Miniature "Terry" clips ideal for screwdrivers and small tools etc. 40 for £1.00

Low profile 14 pin quill **I.C. Sockets** (to fit most "Q" series I.C.) 12 for £1.00

Cassette Motors self regulating, 9V, make unknown type 9FM 90p

Rediffusion/Doric Mk 13 5 stick Triplers can be modified for other sets £1.00

Portable T.V. Batt. Leads with Croc Clips and flat 2 pin socket £1.20

KB, VC3 etc. new **VHF Tuner** with valves £2.50

Miniature Level/Batt. Meters as fitted to many cassette recorders 90p

ZENERS

400MW. 4.3V, 4.7, 6.8, 7.5, 30V, 10 of one type 80p

1.3W. 12V, 13V, 18V, 10 of each type £3.00

10 of one type £1.00

10 of each type £2.50

Gen. Purpose Diodes

IN4000 30 for £1.00 IN4003/10D2 20 for £1.00
 IN4002 25 for £1.00 IN4148 20 for £1.00

ULTRASONIC TRANSDUCERS

Transmitter and receiver. 40 kHz 14 mm diam. £4.25 pair

LOUDSPEAKERS

2" Round 8 Ω 60p

2 $\frac{1}{4}$ " Round 8 Ω 70p

2 $\frac{1}{4}$ " Round 20 Ω 90p

2 $\frac{1}{2}$ " Round 8 Ω 80p

6" x 4" Elliptical 8 Ω £1.25

5" x 3" Elliptical 12.5 Ω £1.00

4 $\frac{1}{4}$ " x 2 $\frac{3}{4}$ " Elliptical 8 Ω for R.B.M. £1.00

5 $\frac{1}{4}$ " x 2 $\frac{3}{4}$ " Elliptical 3 Ω £1.30

Mono T.V. £1.30

PROTECT YOUR PROPERTY

Buy a "SENTINEL" **Smoke and Gas Detector**. Uses TGS105 plug in sensor, housed in 3 $\frac{1}{2}$ " diameter diecast box. 24V. Convertible to 12V. Will activate lamp or relay.

With Data and Circuit £16.95

Suitable 24V Relay £1.00

De Luxe Fibre Glass Printed Circuit Etching kits

Includes 150 sq. ins. copper clad F/G. board. 1 lb ferric chloride 1 dalo etch resist pen. Abrasive cleaner. Etch tray plus instructions.

Special Price £4.95.

1 lb F.E. C1 To mil. spec. £1.25

5 lb F.E. C1. To mil. spec. £5.00

150 sq. in. **Single sided** board £2.00

150 sq. in. **Double sided** board £3.00

500 Watt

Dimmer Switch

Toroidal mains suppression, fused with satin aluminium knob, white.

ONLY

£4.25.

Send **40p P. & P.** on all above items; send Cheque or P.O. with order to:-

SENTINEL SUPPLY DEPT. TV

149a Brookmill Rd., Deptford, London SE8

(Mail Order address only. Callers by appointment)
 Trade enquiries for quantity welcome.

Surplus stocks purchased for cash.

TELEVISION ELECTRONIC DISTRIBUTION (SPARES) LTD.

412a Hanworth Road, Hounslow, Middlesex
Telephone: 01-572 4668

PANEL REPAIR/EXCHANGE SERVICE TRADE ONLY

BERRYVISION 510

EMO

THORN 2000 Series, 3000/3500 Series,
8000/8500/8800/9000 Series.

GEC Solid State 2110 Series.

PHILIPS G8 G9

RBM A802/823 AV (Ultrasonic)

DECCA Solid State 80 Series/Hybrid 30 Series.

GRUNDIG 5010/6010 GB

PYE 691, 697, 713, 723, 731

SONY 1800UB

TRADE REPAIRS ON ALL SONY COLOUR T.V.'s
VERY COMPETITIVE PRICES.

3 MONTHS WARRANTY ON PANELS FROM
DATE OF OUR INVOICE.

DISCOUNT FOR BULK PANEL ORDERS.
CATALOGUE AVAILABLE ON REQUEST.

TV LINE OUTPUT TRANSFORMERS

ALL MAKES SUPPLIED
PROMPTLY by our

**RETURN OF POST
MAIL ORDER SERVICE**

All Mono Lopts at the one price

£6.75
BONA FIDE
TRADE

£7.30 RETAIL

(V.A.T. INCLUDED AT 12½%)

Postage and Packing 70p

All Lopts NEW and GUARANTEED
for SIX MONTHS

WE ALSO SUPPLY SEPARATE WINDINGS FOR
THE FOLLOWING COLOUR L.O.P.T.S
Pye 691 or 697 Chassis.

Bush CTV25 Mk. 1-2-or 3

Decca CTV 25 Non-Tripler Version.

Philips G.6 Single or Dual (Overwind for this Model
on Exchange Basis Only).

Philips K.70 Underwind Only.

EMO90°

COMPLETE L.O.P.T.S

Philips G.8, ITT C.V.C. 5-9 and Decca Bradford.

Prices for the above Colour L.O.P.T.S and
Windings on application.

S.A.E. all enquiries All offers subject to availability.

PAPWORTH TRANSFORMERS

80 MERTON HIGH STREET,
LONDON S.W.19

01-540 3955

COLOUR TUBES STANDARD TUBES

METAL BAND TUBES

Rebuilt with new Electron
Guns to British Standard
415/1972. Clause 18.2.


SUFFOLK TUBES LIMITED

214, PURLEY WAY
CROYDON, SURREY
01-686 7951

Britain's Largest Independent
TV Tube Rebuilder



A NEW APPROACH TO T.V. TESTING

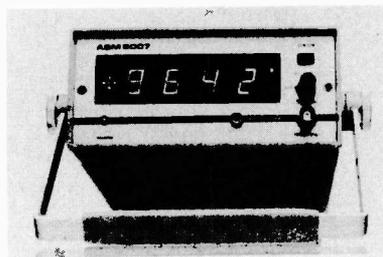

**50kV PROOF + AUTO RANGE +
MEMORY DISPLAY**
Withstands EHT mistakes!

VOLTS DC

9.999 99.99 999.9V ± 0.08% ± 1 digit

VOLTS AC

9.999 99.99 999.9V ± 1% ± 1 digit to 20KHz

OHMS

9.999 99.99 999.9K ± 0.02% 9999K ± 1%

FREQUENCY

9.999 99.99 999.9KHz

Tone indication of new reading. Sample + Hold facility.
High brilliance 16mm display. 220/110V 50/60Hz 10W.
Fast Reading 12/sec.

See us at TESTMEX EXHIBITION WEMBLEY
19, 20, 21 JUNE '79 STAND M9.



ADRETTA LTD,
NORTH STREET
WELLINGTON, SOMERSET

TEL (082 347)
3535

VIEW WELL WITH WELLVIEW TV TUBE REBUILDS

Exchange Mono

	our price	+VAT	total price
CME 1601-1602	£9.30	£1.16	£10.46
A44/120WR	£9.30	£1.16	£10.46
A50/120WR	£9.30	£1.16	£10.46
AW59/23W	£11.00	£1.37	£12.37
A61/120WR	£11.00	£1.37	£12.37

Exchange Colour

	our price	+VAT	total price
A44/270X-271X	£27.00	£3.37	£30.37
A47/342X-343X	£27.00	£3.37	£30.37
A49/120X	£27.00	£3.37	£30.37
A51/110X	£27.00	£3.37	£30.37
A55/14X	£32.00	£4.00	£36.00
A56/120X	£32.00	£4.00	£36.00
A63/120X	£36.00	£4.50	£40.50
A66/120X	£36.00	£4.50	£40.50
A67/120X	£36.00	£4.50	£40.50
A67/200X	£36.00	£4.50	£40.50

18 month full guarantee (Established ten
years).

Send cash or cheque together with
old tube with your order.

Carriage=£3.75 including VAT

ALSO YOUR VALVE SUPPLIER
NEW AND BOXED
(inclusive of VAT)

DY802=72p	ECC82=59p	EF183=63p
EF184=63p	PCC89=70p	PCF802=96p
PCC82=77p	PCL84=90p	PCL805=94p
PFL200=£1.12	PL36=£1.00	PL504=£1.35
PFL509=£2.75	PL519=£2.86	PY88=69p
		PY500a=£1.50

Postage and Packing 10p per valve. All
orders over £10 Free of charge.

WELLVIEW TUBES LTD.,

Unit 7, KING ROAD,
CHARFLEET INDUSTRIAL ESTATE,
CANVEY ISLAND,
ESSEX
TELEPHONE 65372

TV'S TV'S TV'S

THOUSANDS OF MONO TV'S IN STOCK

All makes - all sizes from £1.12½. Square screens from £6.75. Clearance of 25" D/STD CTV'S (Philips 500 and GEC 2028 only). Checked complete £15.75 each, add £8 p/pkg. Earlier model S/STD (Philips 511, GEC 2040, Pye Hybrid etc) Singles tested tube & checked complete £38.25.

Quantities from £27 each
Singles working £47.25 each
Add £6 p/pkg

More recent S/STD CTV'S always in stock (Pye Varicaps, Bush Integrated, Thorn 3500/8000, Decca Bradford, GEC 2100, Korting, Grundig, Luxor, Japanese etc). Sold with tube tested from £45, working from £63.

Ring for quotations

EX-TV SPARES

RANK BUSH MURPHY 184 SERIES ETC

Decoder (Single IC) or Line Board £13.50
I.F. Panel or Power Panel £9.00
Convergence Panel £6.75
Tuners £6.75
Complete EHT Stack £20.25

GEC HYBRID 2040/1 SERIES AND PYE HYBRID CHASSIS

Decoder or DCA (Inc. Valves) £13.50
I.F. Panel or Convergence Panel £9.00
Line Panel £15.75
Tuners £6.75

PHILIPS 511

I.F. Panel £9.00
Tuners £6.75
Lopt £9.00

Any above add £1.60 postage & packing

RING FOR QUOTATIONS ON OTHER SPARES

COLOUR TUBES

(fully tested)
25" £18.00
19" £20.25
22" £24.75
26" £29.25
Plus £4.00 p/pkg.

MONO PANELS/TUNERS

Most types £3.37
£1 p/pkg.

VEGA MONOCHROME TUBES

(Brand new USSR Manufacture in Maker's Box with 12 months Guarantee)
20" Size £15.18
24" Size £17.44
Add £2.50 p/pkg.
Discounts for orders over five.

MULLARD COLOUREX/MAZDA NEW LIFE TUBE REBUILDS

(Callers only)
One year guarantee.
Any size only £30.00 plus old glass.

SPECIAL OFFER

20"/24" Single/STD PYE/EKCO/PHILIPS TYPE 230 (Plastic back) Re-furnished with good cabinet and brand new USSR tube (12 month guarantee).
20" Model £31.50
24" Model £33.75
Add £4.00 p/pkg.

ALL PRICES ARE INCLUSIVE OF VAT.

NORTHERN
Thornbury
Roundabout
Leeds Road
Bradford 3.
Tel: (0274) 665670

SCOTLAND
Peacock Cross
Industrial Estate,
Burnbank Road
Hamilton.
Tel: (0698) 282141

LONDON
Kingsley House
Off Avonmore Rd.
(Opp Olympia)
Hammersmith Rd.
LONDON W14.
Tel: (01) 602 2882

TRITEL GROUP

WEST
Unit 4a
Bulwark Industrial
Estate, Choptow,
Nr. Bristol.
Tel: Choptow
(02912) 6652

MIDLAND
48/52 Pershore
Street,
Birmingham 5.
Tel: (021) 622 1023

SOUTHERN
Wading Street
Heckcliffe, North
Ounstable (on A5)
Tel: Heckcliffe
(052521) 768

MAIL ORDER SEND CWO (CHEQUES OR UNCROSSED PO'S) TO ANY BRANCH

FOR EX RENTAL COLOUR AND MONO TELEVISIONS

Why not call in and see us - a relaxed friendly atmosphere, together with a choice of hundreds of sets at low, low prices. Colour from £15, Mono from £2. Also stands, spares etc. Send an S.A.E. or phone for our current price lists and area map showing how to find us.

Export enquires welcome

West Midlands TV Trade Sales Ltd.
92 High Street, Kings Heath, Birmingham B14 7JZ.
021-444 6464

N.G.T. COLOUR TUBES

First Independent Rebuilder with
B.S.I. CERTIFICATION
(Certificate No. 004)

12 month's guarantee: 4 year option

Tubes are processed using high temperature pumping schedules giving high definition and long life. They are then fitted with an implosion safety system approved by the British Standards Institution.

N.G.T. ELECTRONICS LTD.,
120, SELHURST ROAD., LONDON S.E.25
Phone: 01-771 3535.

20 years experience in television tube rebuilding.

ARE YOU

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "**How to Deal Successfully in Used Colour Televisions**" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have "pooled" their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail - for both televisions **and new/used spares**. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular updating service.**

You can start tomorrow - but you'll need our guide. The latest big illustrated edition is out now, and costs just £4.95 - a small price to pay for financial independence!


SAME DAY SERVICE

CITY PUBLISHING, HAYWORTH ROAD, SANDIACRE, NOTTINGHAM NG10 5LL

To: City Publishing, Hayworth Road, Sandiacre, Nottingham NG10 5LL.
Please send by return post "How to Deal Successfully in Used Colour Televisions".
I enclose cheque/p.o. for £4.95.

NAME.....
ADDRESS.....
.....

**BIG NEW EDITION
OUT NOW!**

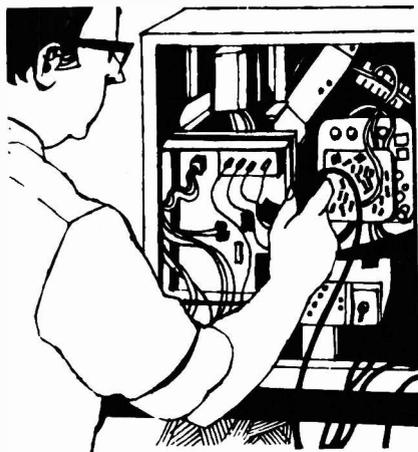

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

SETS & COMPONENTS

URGENT TRADE NOTICE

Large quantities of good quality mono and colour TV receivers for sale, at competitive prices.

WHY not come to us where your custom will be welcomed and appreciated.

WE supply receivers to all parts of the UK, and to EIRE. All export enquiries welcomed.

TV WHOLESALE SUPPLIES

35 Shipston Road, Stratford-on-Avon.
TEL: 0789 4424

RE-BUILT COLOUR TUBES

19" £29.50 MONO 20" £30.50
22" £32.50 20" 24" 25" £34.50
26" £38.50 £16

One Year Guarantee.
MATRIX TV LTD.,

112 Essex Road, London N1. Tel: 226 1111

TELEVISIONS to the Trade. Large quantities of Mono from £2.00; Square Screen from £6.00. Colour T.V.s Working from £65. R.B.M. GEC, Pye, Thorn etc. Phone Scarborough 0723-68087-65451. Scarborough T.V. Trading, Ridings House, Depot Lane, Seamer Road, (A64) Scarborough.

TELEVISION AERIALS

The full range of quality BASIC aerials, amplifiers, lashing kits, cables, masts, rotators and accessories can be supplied at extremely competitive prices, normally from stock. Representative examples are shown. For quotations on specific items, or general and technical application queries, please write enclosing (S.A.E.) Lists on request.

Teleng Supervertor Upconverter £27-52
Labgear CM7025 High Gain UHF amplifier 29dB in Group 'A' £15-60
Jaybeam 'Super-Fringe' FM9S F.M. Aerial £28-87
Jaybeam JBX21 High Gain UHF Aerial £38-06

All prices include VAT and post and packing. We are happy to advise on specific installations and associated problems. An improved version of the high performance UHF amplifier (JULY Television) incorporating dual input switching is currently under development, providing a 2nd ITV channel in most areas. Details to be announced shortly.

BASIC: Aerialite, Antiference, Jaybeam, Maxview, Wolsey Premier Industries.

SOUTH WEST AERIAL SYSTEMS

10 Old Boundary Road, Shaftesbury, Dorset. Tel. 0747 4370

SMALL ADS

The prepaid rate for classified advertisements is 18p per word (minimum 12 words), box number 60p extra. Semi-display setting £3.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

VALVE LIST

ALL VALVES FULLY TESTED

Five valves or over postage paid
Under five valves postage 6p each

DY86/87 15p	PC900 8p	PCL85/805 20p
EB91 12p	PCC84 8p	PL36 20p
ECC82 10p	PCC85 20p	PL504 25p
ECL80 8p	PCC89 8p	PY32/33 15p
EF80 8p	PCC189 8p	PY81/800 15p
EF85 8p	PCC805 15p	PY801 20p
EF183 10p	PCF80 8p	U191 15p
EF184 10p	PCF86 15p	6F23 15p
EH90 13p	PCF805 20p	6/30L2 15p
EY86/87 13p	PCL82 15p	30F5 10p
PC86 15p	PCL83 15p	30FL1 20p
PC88 15p	PCL84 15p	30PL14 15p

AND MANY MORE AVAILABLE

S. W. ELECTRONICS

114 Burnley Road, Rawtenstall, Rossendale, Lancs.

REBUILT COLOUR AND MONO TUBES IN

South Wales

All tubes are guaranteed for 12 months. Colour tube guarantee extendable to 4 years.

Colour	Price examples
18", 19"	£31.00
20", 22"	£33.00
25"	£35.00
26"	£36.00

20AX and P.I.L. tube prices available on application.

Mono	Price examples
20"	£11.00
24"	£12.00

Add V.A.T. @ 12½% to all the above prices.

Prices are based on a sound tube for tube exchange.

For further details, contact:

C.R.T. Services

Telephone: Newport (0633) 412112
And Llanwern 2112

COLOUR PANEL EXCHANGE SERVICE

BRC 3000 - 3500 8000 - 8500
Philips G8 and GEC 2110 series.

Free delivery in London area on Exchange Panels. Large stock of BRC 3500 series spares. New and S/H BRC Panels for sale. Immediate exchange on repairable panels.

Catalogue available on request.

KAY JAY TV SERVICE

34, Clauson Avenue, Northolt. Phone 864 0350.

PL802/T TOP QUALITY SOLID STATE REPLACEMENT VALVE

£2.40 each C.W.O.

LLOYD ELECTRONICS

63 North Parade, Grantham, Lincs.

Solid State C.D.A. Panel for Pye 203/205 + £19.

B7127 5 for 60p	BU208	£1-60
BT106 85p	B0X32	£1-60
TV106 £1-30	BF459	45p
2N4443 70p	MPSA42 300v NPN	30p
2N4444 85p	2SC 1520 250v	
R2010B £1-20	Power	30p
R2008B £1-40	BF394 (BF194)	5 for 60p
BU105 £1-60	BC184	5 for 60p

TV CONDENSERS

PYE 200+300/ 350v	£2.00
THORN 3K 175/ 400v+ 100+ 100-350v	£2.00
THORN 3K 1,000/ 70v	75p
12VA CHOKES SUITABLE FOR THYRISTOR OR LOW VOLTAGE SMOOTHING	65p
PHILIPS/BUSH/GEC 600/ 300v	£1-80

ADD 20p P/P ORDERS UNDER £10 QUANTITY DISCOUNTS.

SECAM TELEVISIONS Available for French Reception. Also Mono Sets. DXTV Receivers made to order. Overseas enquiries Welcome. Hugh Cocks, Bre Cottage, Staplecross, Robertsbridge, E. Sussex. Tel: 058083-317.

COLOUR TUBES

Rebuilt with new electron gun, to British Standard. High temperature pumping.

Here is what you pay.

17-18-19 inch.....	£29.00
20 inch.....	£30.00
22 inch.....	£32.00
25 inch.....	£34.00
26 inch.....	£38.00

Guarantee 2 years.

Exchange basis.

Prices negotiable for contracts.

Old Colour tubes purchased.

Carriage £5.00.

TELESTAR TUBES

575c Moseley Road, Birmingham B12 9BS.
Tel: 021-440 5712.

20 AX & P.I.L. TUBE

Colour Tubes.....	from £25
20 AX all sizes.....	from £25
Toshiba P.I.L. All Sizes.....	from £25
S/S COLOUR SETS.....	from £60
S/S & D/S MONO.....	from £5

RING: JEFFRIES 01-845 2036

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

VALVE BARGAINS

ANY 1-20p, 5-80p, 10-£1.25, 50-£5.50

ECC82, ECH84, EH90, PFL200, EF80, EF183, EF184, PCF80, PCF802, PCL82, PCL84, PCL85/805, PY81, PY800, PY88, PL36, PL504, 6F28, 30PL14.

COLOUR VALVES 50p EACH

PY500/A, PL508, PL509, PL519.

Postage & Packing 30p, no VAT

VELCO ELECTRONICS

9 Mandeville Terrace, Hawshaw, Via Bury, Lancs.

QUALITY REBUILT TUBES

HIGH TEMPERATURE PUMPING
Colour (2 year guarantee) from £30
Mono (including thin necks) from £10

Send or phone for full list and terms
OPEN SATURDAYS
WELTECH PICTURE TUBES

5 Masons Avenue, Wealdstone, Harrow, Middx.
01-427 5063.

P. V. TUBES

12 months guarantee

Colour tubes supplied on a 'glass for glass' basis
Callers ring to arrange to bring your glass for on the spot exchange from our stocks
Lancashire/W. Yorks deliveries by arrangement
Carrage costs per tube: Portables £1.80; Mono £3.50; Colour £4.50; incl. VAT

REBUILT MONO	REBUILT COLOUR		NEW MONO	
A28-14W 11" (Pencil)	17" 18" 19" 20"	£28	A31/510 12"	£17
A31-410W 12"	22"	£30	Replaces A31/120	} Mullard 2 year warranty
A31-120W 12" (Pencil)	25" 26"	£34	A31/410	
A31-18W 12"	26" 110"	£36		
A31-100W 14" (Pencil)			A34/510 14"	£18 50
A38-160W 15" (Pencil)			Replaces A34/100	
A44-120WR 17"			A50/120WR 20"	£12 50
A59 23W 23"			A61/120WR 24"	£13 50
A50-120WR 20"			All tube prices subject to 12 1/2% VAT	
A61-120WR 24"				

Glass is required for portable rebuilt mono please

No minimum order limit - you may order as you please

Cash with order please - any excess refunded

Cash with order please

SAE all enquiries please

Immediate despatch

Many more 'TV' series valves in stock

NEW VALVES

Type	Price	Valve prices include 12 1/2% VAT	Type	Price
30FL1/2	£1 25		PL36	90p
OY802	67p		PL81	50p
OY86/7	58p		PL84	65p
ECC81	52p		PL95	£1 00
ECC82/3	62p		PL504	£1 33
ECC85	50p		PL508	£2 00
ECC88	72p		PL509	£2 52
ECC80	85p		PL519	£3 00
ECC82	85p		PL802	£2 22
ECH81	55p		PY81	89p
ECH84	£1 00		PY88	80p
ECL80	60p		PY500A	£1 60
ECL82	80p		PY800/1	69p
ECL86	75p		UCH81	65p
ECC86	80p		UCH82	75p
EF80	40p		UCH83	£1 00
EF85	40p		U26	50p
EF86	60p		U191	50p
EF183	64p			

ALL VALVES ARE UNUSED - BOXED - AND GUARANTEED

Post & Packing charges 14p for 1 valve - 7p for each
Additional valve - 2p extra for large valves - max. 80p.
Post free orders over £20 - any parcel insured extra 10p.

P. V. TUBES

38A Water Street, Accrington, Lancashire. BB5 6PX
V.A.T. No. 291-1937-45.

EX RENTAL TV

19" UHF 625 £4.50
23" UHF 625 £6.00
Colour from £40.00

EDWARDS & SONS
103 Goldhawk Road, London W12
Tel: 01-743 6996

COLOUR TV's

Many working for disposal, trade only.
All sizes and makes available.
Mono sets also available.

Ingertone (London)

24 Dames Road, Forest Gate,
London E7. Tel: 01-555 5569

Ingertone (Bristol)

28 St. Thomas St., Bristol 1.
Tel: 0272 211179

PLEASE MENTION TELEVISION
WHEN REPLYING TO
ADVERTISEMENTS.

T.V. SPARES, PANELS AND MANUALS

PHILIPS · GRUNDIG
TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

MAINS DROPPERS AND CAN CONDENSERS

Philips G8 47!	40p
Philips G8 2-2-68!	60p
Philips 210 118 148-Loop!	60p
Philips 210 30-125 2K85!	70p
Philips GT23 6-124-84!	70p
Thorn 3500	70p
Thorn 1500 350-20-148-1500-317!	85p
Thorn 1400	75p
Thorn 8000 56-1K-47 12!	85p
Pye 725 27-56!	60p
R B M. TV 161 250 14 156!	65p
GEC 2010 8-15-17 70 63 188!	85p
2010 Covers 2013 2014 2017 & Sobell 1010 10A 13 & 1014	
Bush EV165 166 171 175 176-178	65p
Murphy V 1910 1913-1914 2014 2310 2311 2312 2314	60p
Bush A823 68-56!	85p
TV Condensers. 200 - 200 + 100 mfd 300V	42p each
150-100-100-100 150M 325V	£1.90
150-150-100M 300V	£1.50
175M 400V 100-100M 350V	£1.95
400-400M 350V	£2.50
All 2500-2500m 30V	75p
Can 4700m 25V	80p
Cond 2200m 40V	60p
BDX32	£1.98
100-300-100-16m 300V	£1.60
Post Free, Cash with order, VAT paid.	

Durham Supplies

367 Kensington Street, Bradford 8, West Yorkshire

FOR SALE

NEW BACK ISSUES of "TELEVISION" available 70p each post free. Open P.O./Cheque returned if not in stock - BEL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

TV TUBE REBUILDING - for everything from a complete plant to sundry materials, training, electron guns etc. WESTERN WHYBROW ENGINEERING, Penzance. (073 676) 2265. DEMONSTRATION PLANT AT LONDON BRANCH.

"TELEVISION" Teletext decoder. Catronics. Professionally aligned. 100%. With manual. £160. Or exchange for N1500VCR. Tel: Wells, Somerset 75306.

FORGESTONE 400 Panels never been used C.R.T. Base Power Unit, also Watford T.V. Game B & W. Offers. Send S.A.E. Box No. 146.

AVO Resistance extension unit. Unused. Cost £40, accept £19. Telephone Kettering 4653.

FOR SALE Southeast England Tube Re-Gunning Plant going concern will train. £5,000 O.V.N.O. Thanet 53771.

WANTED

PRE-1953 TV Sets or parts. Amateur collector will purchase any condition. Can Collect Anywhere. Box No. 147.

NEW VALVES and CRT's required, PCL805, PL504, PL509, PY500A etc. Cash waiting. Bearman, 6/8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

PHILIPS GM7628 Signal Tracer. Price and details to A. Dunsmore, 13 Caledonian Road, Edinburgh.

BOOKS & PUBLICATIONS

DX-TV

Identify your DX-TV signals with the unique book entitled, "Guide to World-Wide Television Test Cards". Over 260 photos of Test Cards, Clock and Identification captions etc., plus additional information on transmission standards and Services.

Available, price £1.30 including postage world-wide, from:-

HS PUBLICATIONS
Dept. T(C), 7 Epping Close, Derby DE3 4HR.

LADDERS

ALUMINIUM Roof Crawlers. Sizes 12ft.-24ft. Also aluminium ext. up to 62 1/2ft. Leaflet. Ladder Centre (TEL2), Halesfield (1), Telford. Tel: 586644. Callers welcome.

EDUCATIONAL

BETTER JOB! BETTER PAY!

GET QUALIFIED WITH ICS IN:

COLOUR & MONO TV SERVICING
COLOUR & MONO TV ENGINEERING
COLOUR & MONO TV MAINTENANCE
PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,

NEW: Self-build radio courses with free kits

Train in your own home, in your own time with ICS, the world's most experienced home study college.

RETURN THIS COUPON TODAY
FOR FREE BROCHURE!

ICS

Int Correspondence Schools
J284 Intertext House, Stewarts Rd.
London SW8 4UJ. Tel: 01-622 9911

Name

Address

TELEVISION & VIDEO SYSTEMS ENGINEERING

15 MONTHS full-time Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO & COLOUR TELEVISION
- CLOSED CIRCUIT TELEVISION
- VIDEO CASSETTE RECORDING
- DIGITAL TECHNIQUES
- TELETEXT & TV GAMES

Shortened courses for applicants with suitable electronics background.

Next session starts September 17th.

(Also available 2 1/2 year course in Marine Electronics & Radar for employment as ships Radio Officer.)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. TT7, 20 Penywern Road,
London SW5 9SU. Tel. 01-373 8721.

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc., 10,000 models. Catalogue 24p plus SAE with orders/enquiries. TELRAY, 154 Brook Street, Preston, PR1 7HP.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc., with Free fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS,
RECORD PLAYERS, TAPE RECORDERS, ETC.

SERVICE SHEETS £1.00 PLUS S.A.E. SERVICE MANUALS ON REQUEST.

BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

TVT '78 TRANSISTOR EQUIVALENT & DATA BOOK. (A TO Z). 272 Pages	£2.75
TVT '78 TRANSISTOR EQUIVALENT & DATA BOOK. (2N. 2S. ETC.). 392 Pages	£3.80
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 1	£7.20
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 2	£7.20
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 3	£8.60
COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition	£7.30
COLOUR TELEVISION THEORY by G. H. Hutson	£6.80
LONG DISTANCE TV RECEPTION FOR THE ENTHUSIAST by R. Bunney	£1.70
COLOUR TV WITH REFERENCE TO THE PAL SYSTEM by G. N. Patchett	£6.20
VIDEOTAPE RECORDING: THEORY AND PRACTICE by J. F. Robinson 2nd Edition	£7.80
TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition	£6.10
BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition	£2.65
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition	£2.65
CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett	£4.00
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition	£5.35
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. Revised Edition	£5.95

(SEND LARGE S.A.E. FOR FREE BOOK LISTS)

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.
FROM 1965-66 EDITION UP TO DATE. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 20p POSTAGE PER COPY.
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, R. CONSTRUCTOR, ELECTRONICS TODAY, ELEKTOR.

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. (HALF DAY WEDNESDAY) PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

COLOUR TV MANUALS

COVERING FOLLOWING MAKES
PLEASE SEND S.A.E. FOR QUOTATION

ALBA, BRC, BUSH, DECCA, GEC,
DEFIANT, MARCONI, EKCO, PYE,
FERGUSON, DYNATRON,
NATIONAL, HITACHI, INVICTA,
ITT/KB, RGD, GRUNDIG, SOBELL,
STELLA, SONY, MURPHY,
PHILIPS, HMV, ULTRA & OTHERS.

CIRCUIT DIAGRAM MANUALS

We supply circuit diagrams for televisions in Giant Binders,
covering most British 'Single' and 'Dual Standard' models, con-
sisting of 2 volumes on colour and 1 on black & white. Price
£12.50 each plus £2 post or all 3 for £37.50 post free.

HUGE G.T. TV/RADIO/ETC. CATALOGUE (with £4 worth of useful vouchers)

Lists thousands of service sheets, manuals, etc. Many unobtainable elsewhere. Plus up dated Chassis Guide, newsletter, etc. Essential for every
firm/engineer - Save ££s - only £1 plus large S.A.E.

S.A.E. for details of our Giant Service Sheet Collections - not available elsewhere.

G.T. TECHNICAL INFORMATION SERVICES

76 Church Street, Larkhall, Lanarkshire ML9 1HE

Largest stocks of manuals, etc. anywhere. £1 + large S.A.E. brings any requested full size service sheet. Service sheets from 50p: S.A.E. for
full details of this and unique T.V. Publications. The new 1979 British Colour T.V. Repair Manual and the First Foreign Colour T.V. Repair Manual for
£4.90 each - both for £9.50.

S.A.E. brings full details of these and other unique publications.

Specialists in Colour & Mono T.V. Information - most manuals can be supplied by return of post at highly competitive prices.

LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS

TV Mono, Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E.,
except Colour TV and Car Radios.

State if Circuit will do, if sheets are not in stock. All TV Sheets are full length 24 x 12, not in Bits & Pieces. All other Data full lengths.
Free Fault Finding Chart or TV Catalogue with order. (MAIL ORDER). Crossed PO's Returned if Sheets Not in Stock.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882.

MISCELLANEOUS

RIGONDA AGENTS. For all spares and repairs.
Fast dispatch Trade Services available. 01-476 1928.
Star Radio, 272 Barking Road, London E13.

THE CED TESTER REACTIVATOR suitable for
most types of colour and mono including P.I.L. and
20AX types checks emission, detects and measures
inter electrode leakage, incorporates a very effective
boost facility. Not a kit but a professional instrument
£69.12 inc. VAT. 10 day money back assurance or
S.A.E. for details. C. E. Developments, 54
Baronsmead Road, High Wycombe, Bucks HP12
3PG.

VIDEO, VCR, and STUDIO SOUND equipment
repair and installation. The VIDEO-WORKSHOP,
Chelsea. 01-603 9649.

MISCELLANEOUS

TIRRO's new mail order price list of Electronic
Components now available on receipt of SAE. TIRRO
ELECTRONICS, Grenfell Place, Maidenhead, Berks.

VIDEORECORDER SERVICE and Technical
consultancy - B & B Electronics, Newark 76895. Call
Steve Beeching.

C.T.V. Panels etc Lists S.A.E. Sole, 37 Stanley St.,
Ormskirk, Lancs L39 2DH.



BELLS AND SIRENS
CARTERS SIREN £5.95
INDUSTRIAL SIX INCH
BELL £8.95
PRICES INCLUSIVE.
SEND CHEQUE. P.O. to:
CWAS ALARM
11 Denbrook Walk,
Bradford BD4 9QS



6 to 12v D.C. 12v D.C.
SAE for full price list of Professional Burglar Alarm
Equipment.

TELEVISION TUBE SHOP

NEW TUBES AT CUT PRICES

EUROPEAN TYPE Nos.

	Price £	VAT %
A28-14W	18.95	2.37
A31-19W/20W	19.95	2.49
A31-120W/300W	17.95	2.24
A31-410W/510W	17.95	2.24
A34-100W	18.50	2.31
A38-160W	17.50	2.19
A44-120W	18.75	2.34
A50-120W	17.95	2.24
A59-23W	18.95	2.37
A61-120W	18.95	2.37

U.S.A./JAP. TYPE Nos.

9AGP4	19.50	2.44
19QAB4/C4	17.50	2.19
230ADB4	28.50	3.56
230DB4/CT468	24.00	3.00
240AB4A	17.95	2.24
CT507	17.95	2.24
CT512	27.50	3.44
310DGB4/DMB4	23.00	2.88
310EUB4	19.95	2.49
310EYB4	18.75	2.34
310FDB4	19.95	2.49
310FXB4	17.50	2.19
310GNB4A	23.50	2.94
310HCB4	23.50	2.94
340AB4	19.50	2.44
340AYB4	25.25	3.15
340RB4/CB4	24.50	3.06
340AHB4	24.50	3.06

Some Rebuilt Japanese & European Types Available at £14.00 + VAT £1.75

COLOUR TUBES (New & Colourex)

12VARP22	62.50	7.81
330AB22	65.00	8.12
470FUB22B	85.00	10.62
A44-271X	65.00	8.12
A47-342X	69.50	8.89
A47-343X	69.50	8.89
A49-191X	59.50	7.44
A51-220X	64.00	8.00
A56-120X	69.50	8.89
A63-120X	69.50	8.89
A66-120X	75.00	9.37
A66-140X/410X	70.50	8.81
A67-120X	82.00	10.25
A67-140X/200X	69.50	8.89
A67-150X	75.00	9.37

ALL TUBES TESTED BEFORE DESPATCH & GUARANTEED FOR 12 MONTHS! 4 YEAR GUARANTEES AVAILABLE ON MOST TYPES

CARRIAGE

Mono £3.00 Colour £4.00 Mainland only. Overseas Rates on Application.

TELEVISION TUBE SHOP LTD. 52 BATTERSEA BRIDGE RD., LONDON, SW11. Tel. 228 6859/223 5088

PHILIP H. BEARMAN

(VALVE SPECIALISTS)

SUPPLIERS TO H.M. GOVT. Etc.

Closed 12.30-2 pm.

NEW valves by Mullard, Mazda, etc. we cannot supply these makes with warranty. (See our lists for explanation)

"QUALITY" BRANDED VALVES ONLY CARRY THE 90 DAY GUARANTEE, SEE OUR LISTS.

IMMEDIATE POSTAL DESPATCH	LISTS S.A.E.	QUOTED PRICES INCLUDING 6% ALLOWANCE IN LIEU OF GUARANTEE	ON BVA VALVES		
DY51 70p	EZ40 & 41 62p	PCF802 £1.00	PL36 £1.20	U25 60p	30P12 70p
DY86/7 75p	GY501 £1.60	PCF805 £1.75	PL84 60p	U26 60p	30PL1 P.O.A.
DY802 80p	PC86 95p	PCF808 £1.75	PL504 £1.50	6F23 60p	30PL14 £1.20
ECC81 75p	PC88 95p	PCF809 £1.75	PL508 £1.55	6F28 60p	30PL15 £1.10
ECC82/3 75p	PC97 80p	PCH200 £1.25	PL508 £1.55	6F28 60p	Also 3AT2, 17DW4A & 40KD6
ECL80 70p	PCC84 35p	PCL82 £1.00	PL509 £3.00	20P4 70p	
EF80 65p	PCC89 75p	PCL83 £1.00	PL402 £2.90	30C1 90p	
EF183 80p	PCC189 75p	PCL84 £1.00	PY81/83 90p	30C17 80p	
EF184 80p	PCF80 95p	PCL85 £1.15	PY800 90p	30FL1 } £1.20	BY 100/127 etc.
EH90 70p	PCF86 95p	PCL80S } £1.15	PY801 90p	30FL2 } £1.20	all 21p each
EY51 85p	PCF200 £1.65	PD500 £3.60	PY500 90p	30L15 } with 10W resistor.	
EY86/7 50p	PCF801 90p	PFL200 £1.50	PY500A } £1.75	30L17 75p	

SENDER SAE FOR COLOUR

TRIPLET LIST (BRC)

ALSO LATEST COMPONENTS LIST.

(Near Sub Post Office)

STOP PRESS PC92/96, PCL200, PL95, PL519. Also some Teleton types. EY500A, EL509, EL519

6 POTTERS RD., NEW BARNET Herts. Tel: 01/449-1934/5 (Tel. recording service 449/1934 only)

Production 30PL1 discontinued

Note: Actual makers of NEW MICRO ALL GROUPS UHF AERIAL (625)- 3" x 1 1/2", amazing results. £3.70 all incl. SAE DETAILED LEAFLET (Tech reports 50p extra)

SOUTHERN VALVE COMPANY

Second Floor, 8 Potters Road, New Barnet, Herts.

Telephone 01-440/8641

Noon to 2 pm excepted

MAIL ORDER ONLY

MINIMUM ORDER 80p

ALL NEW & BOXED, "QUALITY" BRANDED VALVES GUARANTEED 3 MONTHS. BVA ETC. ARE OFTEN AVAILABLE WITHOUT ANY GUARANTEE. (SEE OUR LISTS). QUOTES ON REQUEST.

PROBABLY THE BEST VALUE ANYWHERE

NOTE: Correct only. We regret some increases, at time of going to press. please verify prices.

Some leading makes available. 1.41 invoices issued on request.

DY86.7 55p	EF86 55p	PC86 80p	PCF802 82p	PL36 £1.10	PY500A £1.80
DY802 55p	EF89 75p	PC88 80p	PCF805 £1.75	PL81A 70p	UBF89 50p
ECC81 60p	EF183 55p	PC97 75p	PCF806 75p	PL82 30p	UCC85 55p
ECC82 63p	FF184 55p	PC900 65p	PCF808 £1.75	PL83 40p	UC181 60p
ECC83 63p	EH90 60p	PCC84 35p	PCL82 65p	PL84 50p	UCL82 75p
ECC85 52p	HL41 £1.00	PCC85 53p	PCL83 £1.10	PL500 } £1.20	UCL83 99p
ECH81 55p	EL509 £3.00	PCC89 50p	PCL84 70p	PL504 } £1.20	UCF89 55p
ECH84 85p	EM84/87 90p	PCC189 55p	PCL85 } 85p	PL508 £1.70	UL41 95p
ECL80 52p	EY86/7 48p	PCF80 80p	PCL80S } 85p	PL509 £3.05	UL84 90p
ECL82 65p	EY500A £1.60	PCF80 80p	PCL86 85p	PL802 £2.90	UY41 60p
ECL86 72p	EZ80 43p	PCF86 60p	PCL200 £1.45	PY88 90p	UY85 60p
EF80 41p	EZ81 45p	PCF200 £1.60	PD500 £3.60	PY800 70p	U25/26 60p
EF85 45p	GY501 £1.40	PCF801 60p	PFL200 £1.40	PY801 70p	Also 3AT2, 40KD6

Large valves 2p extra. EZ40 & 41 62p each!

VAT INCLUDED IN PRICES

NO CALLERS

AGENTS NEW UHF "MICRO" AERIAL! Only 3" x 1 1/2". WIDE BAND. PRICE £3.70 INCL. POST & VAT. (625 UHF).

EMO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES ETC., ETC. ● ALL SPARES READILY AVAILABLE ● REBUILT TUBES CREDIT AVAILABLE - TRADE ONLY

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc. NEW - COMBI LOPTX NOW AVAILABLE.

YOU CAN BE 95% SURE WE CAN SUPPLY ANY TV COMPONENT BY RETURN IF YOU NEED SPARES FAST - RING NOW!

ACCESS AND BARCLAYCARD ACCEPTED.

S.A.E. FOR FREE SERVICE CATALOGUE.

TELE-PORT (WTON) THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 773121

PHILIP H. BEARMAN

NEW MONO TUBES. Usually 2 Year Guarantee. Tested prior sale.

BUY NOW - PRICES MUST INCREASE SHORTLY.

A31/410W Mullard £18.00.

A31/120 - CME1220 } (A31/300)* £19.50*

A34/100 - CME1420 } £19.50*

A38/160 - CME1520 } £19.00*

A44/120WR - CME1713 } £19.50*

A50/120WR - CME2013 } £18.00*

A61/120WR - CME2413 } £21.00*

Note* less £1 for 1 year guarantee.

COLOUR TUBES. Prices on application. SAE all enquiries please!

Prices correct at time of going to press but subject to alteration without notice.

Telephone enquiries welcomed. 19", 20" £60; 22" £69.50 £5 allowance old CRT.

6 POTTERS ROAD, NEW BARNET, HERTS.

Tel: 01-449 1934/5. (Answering machine 1934 only)

PRICES INCLUDE 12 1/2% VAT. (Callers welcome)

MAKES INCLUDE TOSHIBA, HITACHI, VEGA, MAZDA, BRIMAR & MULLARD.

CARRIAGE £2.00 (Mainland); £3.50 colour; £1.50.

for Extra Short Sea Journey. Eire Extra.

MULLARD A47-14W (AW47-91) £10, BRAND NEW! Also A59, 15W, £11.00.

MULLARD A47-26WR £15! MULLARD

A59-23WR £16 All Mullard 2 year (NOT 1 year) guarantee. (UNREPEATABLE AT THESE PRICES!)

NOTE - JUST ARRIVED - NEW MAZDA A47.13W £15! (limited stocks)

ELECTRONIC MAILORDER LTD.

VALVE BARGAINS

Any 5-80p, 10-£1.50, 50-£6.00 Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PL504, PY81/800, PY88, 30PL14, 6F28, PFL200.

Colour Valves - PL508, PL509, PL519, PY500/A. All tested. 55p each.

Aerial Splitters: - 2 way, 75 OHMS, Inside Type, £2.50

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11 - For the stereo and standard VHF/FM radio.

B12 - For the older VHF television - Please state channel numbers.

B45 - For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. Price £4.70 each.

STEREO HEADPHONES

Black - Freq. 30-18000HZ.

SAVE ££'s - PRICE £3.50

ALL PRICES INCLUDE VAT P & P 30p PER ORDER EXPORTS WELCOME AT COST

62 BRIDGE STREET, RAMSBOTTOM,
BURY, LANCS.
TEL: RAMS (070 682) 3036.

CALEY TUBES

17-35 Bangor Road,
Edinburgh EH6 5JY.
031-554 4200.

Callers Welcome.

Rebuilt T.V. tubes from Scotland's oldest established rebuilder, all fitted with top quality gun mounts and hot pumped for maximum life.

COLOUR 2 YEAR GUARANTEE.

12" + 14" + 16" Teleton & Hitachi etc. portable types	£29.50 (£3.68)
18" A47 - 342x, A47 - 343x, 470 DUB 22, 470 DKB 22, 470 EMB 22 etc.	£29.50 (£3.68)
18" Toshiba 470 ERB 22 etc. P.I.L.	£37.50 (£4.68)
19" A49 - 11x, A49 - 120x, A49 - 191x, A49 - 192x, CTA 1950, CTA 1951, 490 AXB 22, 490 BKB 22 (A+B) 490 BTB 22 (A), 490 BUB 22, 490 CJB 22, 490 CUB 22	£29.50 (£3.68)
20" A51 - 110x, A51 - 220x, 510 AEB 22A, 510 ARB 22, 510 AUB 22 (A), 510 BMB 22	£29.50 (£3.68)
22" A55 - 14x	£33.00 (£4.12)
22" A56 - 120x, A56 - 140x, A56 - 410x	£33.00 (£4.12)
22" A56 - 500x etc.	£41.00 (£5.12)
25" A63 - 11x, A63 - 120x, A63 - 200x etc.	£37.50 (£4.68)
26" A66 - 120x, A66 - 140x, A66 - 410x, A67 - 120x, A67 - 150x, A67 - 200x	£37.50 (£4.68)
26" A66 - 500x	£45.50 (£5.68)

MONO 2 YEAR GUARANTEE.

All portable thin neck types incl. Japanese.	£14.00
Up to and including 20"	£10.00
23" and 24"	£12.00

Usually same day despatch or your old tube rebuilt and despatched within 48 hours of receipt.

Please enquire for any type not listed as we can rebuild almost anything including V.D.U. and industrial types.

All prices quoted assume the return of your old envelope in rebuildable condition with your order.

Old CRT and cash or cheque with order. Carriage + packing £2.75 inc VAT anywhere on mainland, or advance replacement by special arrangement. Carriage £3.95 both ways.

VALVES ALL NEW AND BOXED

10C2	50p	10F1	50p	10P14	£1.00
20D1	25p	20F2	25p	20L1	25p
20P4	50p	20P5	50p	30P12	25p
30C15	50p	30L1	25p	PCC84	25p
PCL83	£1.00	PL83	25p	PY33	25p
U25	50p	U191	25p	U301	50p
U141	50p				

V.A.T. inclusive.

P & P 15p one valve plus 5p per valve.

Price includes 10% discount in lieu of guarantee.

All valves tested before despatch.

DISPLAY ELECTRONICS

COLOUR TUBES MONOCHROME TUBES VDU/RADAR TUBES

REBUILT IN OUR
OWN FACTORY
IN N.W. LONDON

Customers are asked to note that as a result of the continuing high demand for our products we have moved to a new purpose built factory in UXBRIDGE and the old factory at West Drayton is now closed.

The new address is:—

96/100 WATERLOO ROAD,
UXBRIDGE, MIDDX.
TELEPHONE:
UXBRIDGE 55800

COLOUR T.V. SPARES

Large stock of parts for Decca and Thorn

LOPT		
DECCA	10 or 30	£10.50
	17/1830	£10.50
	80 or 100	£9.90
	1700/2020	£11.75
	12" portable	£10.00
PHILIPS	G8	£12.50
ITT	CVC 25/30	£9.90
	CVC 20	£10.75

TUNER CONTROL UNITS

for DECCA 30, 80, 100

4 Button	£6.50
6 Button	£8.65
7 Key	£13.65

Cut-outs £1.55. Focus £3.50.

Line osc. coil 95p. 3R9 15w

52p. 2020 Dropper £2.05.

1590 Spkr. £4.50. 3000 Mains

Tx £10.44. 1043-05 Tuners £9.

Brand New Decca Receivers Supplied.

Prices include VAT (12½%)

Post & Packing charge per order.

Transformers 70p, others 25p. First class past mainly used. Catalogue 14p (free with an order if requested).

BOTTOMLEY'S TELEVISION

11 Leeds Road, Hipperholme,
HALIFAX (0422) 202979

Callers - Phone first. Exit 26 M62
3000 Panels Ex-equip. now available.

BIRMINGHAM AND DISTRICT DEALERS/ENGINEERS

NEWS FLASH

HIGH VACUUM
QUALITY
REBUILT TELEVISION
PICTURE TUBES

COMPETITIVE PRICES

CONTRACT TERMS
AVAILABLE

2 YEAR GUARANTEE

E.G.		
17" 18" 19"	£29.50 + VAT	£3.69
20"	£32.50 + VAT	£4.06
22"	£34.00 + VAT	£4.25
25"	£37.00 + VAT	£4.63
26"	£40.00 + VAT	£5.00

PIL Tubes our speciality.

All Prices For Tubes available on a Sound "Glass for Glass" basis otherwise £20 surcharge

C.W.O. Carr./Ins. £5.80

"Old Glass Purchased"

TUBESURE LTD.

Unit 111, Middlemore Industrial Estate,
Middlemore Road, Smethwick,
West Midlands. Telephone: 021-558 7777.

G11 Speakers 70R	£1.00	TDA 2680	£1.50
3 × 5 1.W. 50R	50p	TBA 120 AS	30p
ELC 1043/06	£4.00	BSS 68	20p
TBA 750 Q	£1.50	200 + 200	
BZV 15/12R	35p	350V	70p
2N 60 99 } 5 AMP } NPN }	35p	.22/250 AC	10p
BTY 80	25p	BT 138	40p
PYE 731 Mains Dropper		AC 187K	50p
3R/56R/27R	50p	AC 188K	Pair
BD 226	20p	BC 195	7p
BD 238	30p	BC 327	7p
		BF 594	7p
		8 MFD 300V	5p

40V, 2A O.P. Trans NPN PNP BD375-6	Pair 20p
AD 161 - 162	Pair 60p
For Varicap 7 Push Button Units with Variable Resistance, Fascia Plate & Lamps	£2.00
For Varicap 4 Push Button without Fascia Plate 20K	75p
Transistor BF180-1 UHF Tuner Unit with AE Socket & Leads. G.E.C. Rotary Type	£1.35 New
New VHF/UHF Varicap Units AEG	£3.00
£2.50 Each	
10 Watts Mullard Modules LP1173	£2.50 New
BF258	20p
BC303	20p
BD207	30p
BF157	15p
BC238A	10p
BC148B	10p
TIP31A	20p
TIP2955	50p
BF195	10p
8A 800V Thyristors	35p
2N6399A	

7A/Thyristors 400V S2600D	35p
16172 RCA BT119 Type	£1.00
AT1025/08 Blue Lateral Ass.	25p
E1222	15p
BSY95A	7½p
2N930	7½p
4.7NF 5kV	10p
Convergence Panel for GEC 2040	£2.00
11 Pots 5 Coils & Resistors etc	
220 MFD 450V	50p
IN2069A	5p
MODULES	
Reject Units VHF ELC 1042	50p
10 Watt LP1173	£1.00
I.F. LP1170	50p
AM/FM LP1179	50p
Triples LP1174 Mullard	£3.00
TIP 29A	25p
TIP 32	25p
BT106 Special Type	60p
Y827 Diodes	30p
SN76227	50p
TBA 510	£1.00
TBA 540	£1.00
TBA 396	50p

Bridge Rectifiers B30C600A6	15p
B30C500P	15p
RCA Line Output Transistor for use in Low Impedance Line Output Circuits	75p
BT119	£3.00
BT109	60p
BT146 750V S. C. R.	60p
TBA 641 BX1	£1.50
BFT 43	15p
UHF Varicap Units ELC 1043/05	£4.00
UHF Replacement Varicap Units G8	£3.50
3A/100V Rectifiers	7½p
1A/400V Bridge/Recs	25p
TBA 120 S.B.	30p
TBA 120 B	30p
Decca Bradford Tuner Unit	£2.50

TBA 120 A	30p
TBA 920	£1.00
TBA 550 Q	£1.25
SBA 550 B	
SN 76003	£1.00
No Heat Sink	
TBA 800	75p
TDA 1170	75p
2N3583 250V, 1 amp output transistor	40p
Red & Green L.E.D. Mixed	14 for £1.00
Large & Small	
Varicap FM Tuner Tuning range 78.5 to 108MHz	£2.00
(I.F. Panel £2.00)	
PEHT, Triplers Mono 5 stick 18kV-20kV	£1.50
5 stick 25kV colour types Triplers G8 - GEC - AEG	£3.00
400 + 400 350V	80p
Tripler 1174/33 Decca	£3.50

SENDZ COMPONENTS
2 WOOD GRANGE CLOSE,
THORPE BAY, ESSEX.
 Reg. Office only -
 Callers by appointment only. Thank you.
 Free Postage applies in U.K. only.
PLEASE ADD 12½% VAT

AD 161-162	PAIR 60p	15,000 PF 10kV	10p	SN76533N	£1.00	160PF 8Kv	100M 50v
40M/A	20MM Fuses Mixed Values Anti Surge and Quick Blow 30 for £1.00	22,000 PF 10kV	10p	TBA990	£1.00	270PF 8Kv	330M 10v
160M/A		25,000 PF 10kV	10p	SN76660N	50p	1000PF 10Kv	330M 25v
250M/A		F7068 PC 5 Watt O/P.I.C.	£1.00	SN76650N	£1.00	1200PF 10Kv	330M 35v
800M/A		100 Mixed Electrolytics		TBA560Q	£2.00	1000PF 12Kv	330M 50v
1 Amp		1000 MFD to 4 MFD	£2.50	TBA540Q	£1.00	160M 25v	330M 63v
1-15 Amp		SN76530P	35p	TBA54Q	£1.00	220M 25v	470M 25v
1-6 Amp		BYX 38/600R	50p	TIS91	25p	1000M 16v	470M 35v
2 Amp		.1 MFD 400	5p	TAD100	£1.00	220M 35v	470M 40v
2-5 Amp		.1 MFD 2000v	15p	SAB550	£1.50	220M 40v	47/63
3 Amp		.1 MFD 800v	8p EACH	TBA530	£1.00	220M 50v	300PF 6Kv
4 Amp	.01 MFD 1000v	35p.		RCA40506 Thyristors	50p	470M 25v	8M/350v
3500 Thorn Triplers	.047 MFD 1000v			BC108	7p	22M 315v	10p EACH
F7068PC 5 Watt O/P.I.C.	.47 MFD 630v			BD610 }	50p	BC365	10p
TK 25KC 15BL	.0047 MFD 1500v			BD619 }	50p	BD561-2	PAIR 30p
Ex Panel Pye	.0022 MFD 1500v			MJE2955	50p	BD183	50p
ITT 11TDL CVC 20/25/30	.47 1000v		TIP2955	50p	TDA2680	£1.00	
TS2511TDT Thorn	200+200+100M 325v	40p	AC188	10p	TDA2690	£1.00	
TS2511TBQ Pye	470+470 250v	40p	BC149C	7p	SN16862	£1.00	
TS2511TCE	100+200M 325v	30p	Aerial Amp Power		MC1352PQ	£1.00	
1730 Decca	200+200+100+32M 350v	70p	Supplies 15 volts	£1.00	SN76131N	£1.00	
Mains Droppers	150+200+200M 300v	50p	BC158	8p	TBA651	£1.00	
69R + 161R Pye	800M 250v	20p	BC213LA	6p	TBA750Q	£1.50	
Rank/Bush Mains Dropper	600M 300v	£1.00	BF594	6p	TBA920Q	£2.00	
302R/70R/6R2	400M 400v	£1.00	BC147C	7p	SN76003N	£1.50	
147R + 260R Pye	800+800M 250v	60p	BC212LT	7p	SN7660N	£1.00	
Thorn Mains Dropper	300+300+100+32+32 300v	£1	BC182L	7p	SAS570S	£1.50	
80R/6R/054R/720R/317R	100M 450v	25p	BC148B	7p	IN4148	3p	
Thorn Mains Droppers	33/450v	25p	BD131	25p	BF198	7p	
6R + 1R + 100R	47M 450v	25p	Thorn 1590 Mains Lead & On/Off Switch & Control Panel with 3 Slider Pots	£1.00	BF274	5p	
Thorn Mains On/Off Switches, Push Button or Rotary	680M 100v	35p	Reject VHF Varicap Units		BA159	10p	
100 Mixed Diodes	100M 350v	20p	UHF	50p	BY184	25p	
IN5349 Diode }	22M 100v	15p EACH	AE Isolating Socket & UHF Lead	30p	BY187	50p	
12V Z/Diodes }	4-7M 63v	15p EACH	6 Position 12-5k V/Resistors Units for Varicap	50p	TAA550	20p	
400 MFD/350V	MJE2021 90v 80v }	15p	EHT Rectifier Sticks		TBA396	£1.00	
GEC Tripler C2100	SJE5451 5A }	EACH	Used in Triplers		TBA510Q	£1.00	
300 Mixed Condensers	90V 661 NPN }	28p	x80/150	10p	TBA480Q	£1.00	
300 Mixed Resistors	80W 5A 660 PNP }	PAIR	CSD118xMH }	EACH	TBA550Q	£1.50	
30 Pre-sets	EHT lead & anode cap	25p	CSD118xPA	12p	TBA720A	£1.50	
100 W/W Resistors	Thorn 1500 EHT Rec Sticks	10p EACH	3 Off G770/HU37 EHT Rec. Silicone, used in Tripler	15p	TBA790B131	£1.00	
40 Mixed Pots	BRC2108	10p	Bridge Rectifiers 3 Amp	40p	TBA800	95p	
20 Slider Pots	100 Mixed Transistors	£1.50	1A 100v	20p	SN76115N	£1.00	
470M/100v	3 amp Diodes	10p	2A 100v	25p	TAA700	£1.50	
Focus Unit 3500 Thorn	BU500	£2.00	W005M	20p	TBA530Q	£1.00	
Thorn 8500 Focus Unit	BC107	7p	BY127	10p	TBA550	£2.00	
4 Push Button UHF Unit	BF200	10p	IN4005	20 for £1.00	SN76227N	£1.00	
1400 - 1500 Series and 8500	BSY79	19p	IN4006	20 for £1.00	SN76544N	50p	
D.P. Audio Switch	BXY50	15p	IN4007	20 for £1.00	SN76640N	£1.00	
BF127 BC350 BF194	700M/250V	35p	BYX94 1200v 1 Amp.	15 for £1.00	SN76033N	£1.00	
BF264 BF178 BF184	LONG WIRES		BY 210/800	10 for £1.00	TBA120A	50p	
BF180 BF257 BC460	300 Mixed Carbon Film		BB105 UHF		TCA270Q	£2.00	
BF181 BF137 BF395	5 of each type ½ Watt		BA 182 Varicap Diodes		TCA270SQ	£1.00	
BF182 BC161 BC263B	1R to 2 meg. £1.50. ITT		BB103 VHF	12 for 60p	Star Aerial Amps	£4.00	
BC300 BF185 BF273			BY176	50p	CHANNEL B+C	EACH	
AC128 15p EACH			BA248	7p	TV18	40p	
3300/40v 680/40v			BY133	10p	TV20 BYF3214	50p	
680/50v 220/63v			BYX55/350	10p	Rectifier Sticks & Lead		
2200/10v 12½p EACH			BY210/400	5p	R2010B	£1.25	
2N930 BC183			BY206	15p	R2008B	£2.00	
2N2222			BT106	95p	BU105	£1.00	
2N3566 7½p EACH			BT116	85p	BU105/04	£1.00	
BF336 30p			UHF Mullard Tuner Units	£2.00	BU205	£1.00	
TIP41A - 42A PAIR 40p			BY212	15p	BU208	£1.75	
G11 Philips Thyristors			12 Kv Diodes 2 M/A	30p	BU108	75p	
GEC112M 60p			18 Kv BYF3123 Silicone	30p	BU126	£1.00	
Pye Thyristors					BD130Y	20p	
2N4444-OT112					2N3055	40p	
BT116 85p					BRC1693 Thorn	60p	
BU126 £1.00					BD138	20p	
6200PF/2000V 8p					BD252	20p	
.3/600V 8p					Audio O/P Trans.		
Mixed Components 1lb for £1.50					RCA16572 }	40p	
Mains On/Off Switch GEC					RCA16573 }	PAIR	
Push Button or Rotary 30p					SCR957	65p	
					BRC4443	65p	
					5A 300	25p	
					TIC106 Thyristors }	EACH	

SENDZ COMPONENTS

2 WOOD GRANGE CLOSE,
THORPE BAY, ESSEX.

Reg. Office only -

Callers by appointment only. Thank you.

Free Postage applies in U.K. only.

PLEASE ADD 12½% VAT