

MAKING AN ALL

SUPERHET—

See page 52

A
NEWNES
PUBLICATION

Edited by
F.J. CAMM

Vol. 17. No. 413.

Practical Wireless

and

6^d

EVERY
MONTH

November, 1940.

★ PRACTICAL TELEVISION ★

Contents

Amateur Receiver
Design

Service Engineer's Log

Thermion's
Commentary

A.C. Four-wave Three

Practical Hints


Testing L.F. Amplifiers

All-dry Four-valve
Superhet

War-time Experiments

Harmonics in Wireless

Readers' Letters

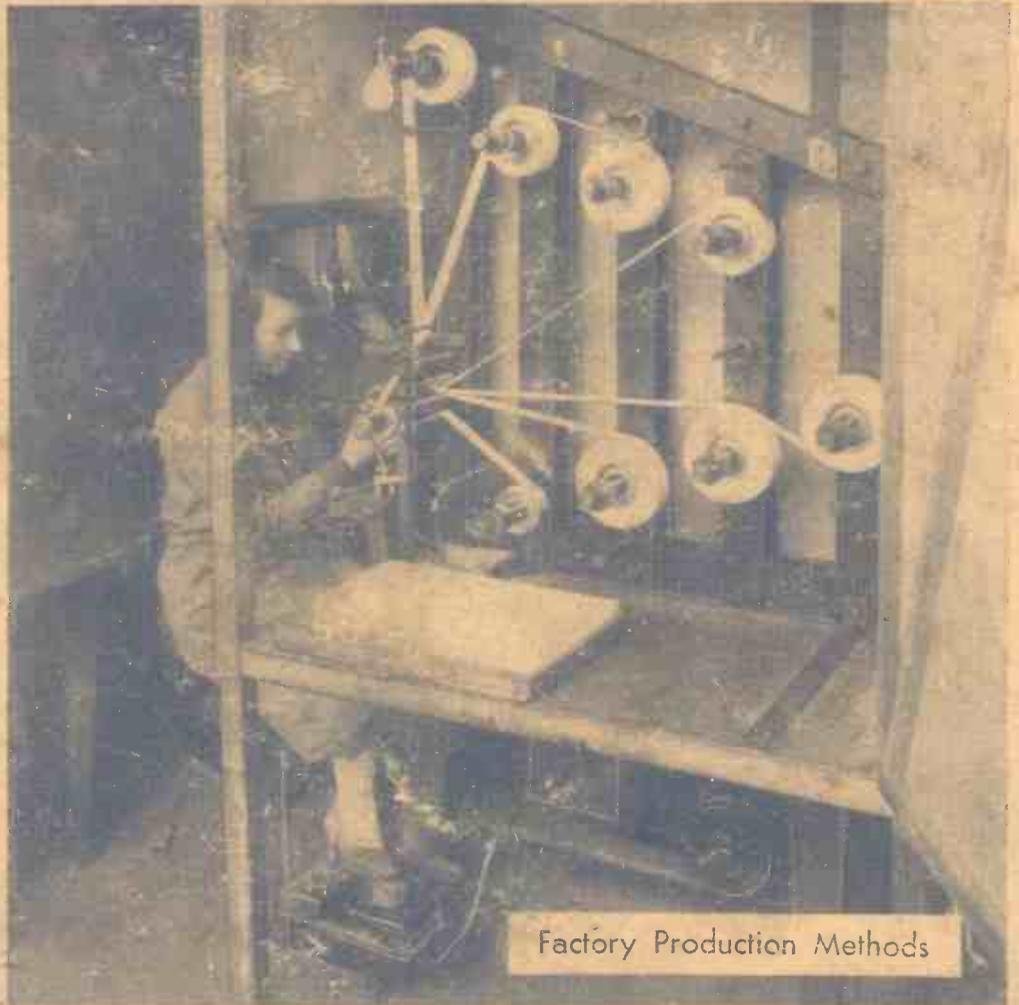

Factory Production Methods


IF YOU WANT THE BEST SHORT WAVE RADIO
PIN YOUR FAITH TO—

LONDON SERVICE:
WEBB'S RADIO, 14, SOHO ST., W.1
BIRMINGHAM SERVICE:
WEBB'S, 41 CARRS LANE

EDDYSTONE

"Eddystone" products are made for outstanding performance. They are used by the Fighting Services—have been employed in Arctic and Tropical Expeditions—in fact whenever utter reliability and the highest efficiency is essential "Eddystone" is used. YOU, too, will obtain the best results if you insist on "Eddystone." Do so to-day.

MANUFACTURERS:
STRATTON & CO.,
B'HAM

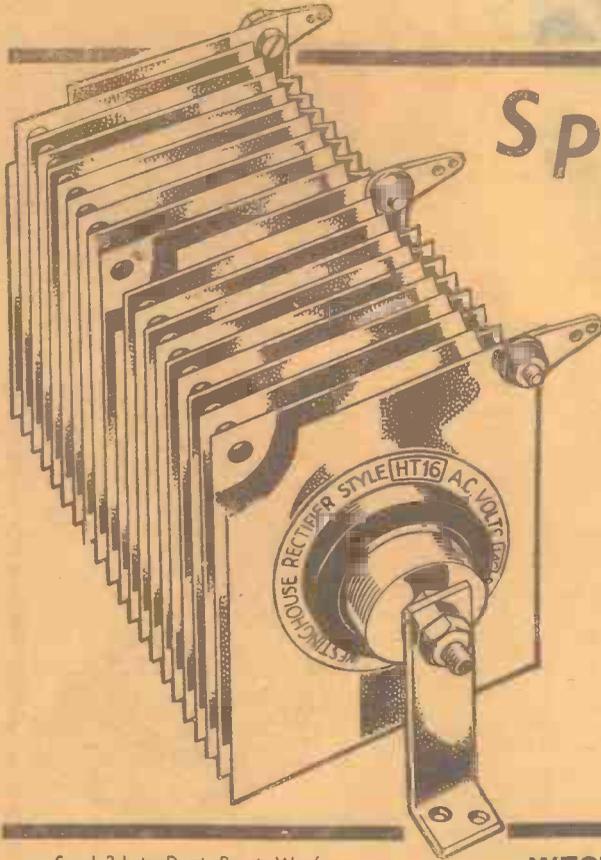

Specified

FOR THE A.C. ALL-WAVE THREE-VALVER

The all-metal construction of the Westinghouse Rectifier makes it impervious to shocks and vibrations; and, as there is nothing to wear out, nor any electronic action, its reliable life is unlimited. That is why Mr. Camm specifies a

Westinghouse
H.T.16

METAL RECTIFIER

for his latest receiver.

Send 3d to Dept. Pract. W. for a copy of "THE ALL METAL WAY"

WESTINGHOUSE BRAKE & SIGNAL CO., LTD.,
PEW HILL HOUSE - CHIPPENHAM - WILTS.

Invaluable to all whose work concerns the tracing of faults and the effecting of repairs.

PRACTICAL WIRELESS SERVICE MANUAL

By F. J. CAMM.

A complete, practical and up-to-date work on the testing and servicing of all types of wireless receivers. With over 200 illustrations. Contents: Theoretical Symbols, Choice and Types of Instruments. Fault-tracing without Instruments. D.C. Multi-range Milliammeter. Measuring Resistance. Measuring A.C. Voltages. Measuring Capacity. Using the Universal Meter. Calibrating and Using the Valve Voltmeter and the L.F. Oscillator. Tracing Faults in a Superhet. A Signal Generator. Trimming and Aligning Receivers. Testing Valves. Valve Replacement. Reaction Faults. Improving Old Sets. Universal (A.C.-D.C.) Receiver Faults. Checking Receiver Performance. Distortion—Causes and Cure. Tracing Sources of Interference. Temporary Repairs. Renovating Cabinets. Servicing with the Cathode-Ray Tube. Tracing and Eliminating Hum. Simple Tests for Components. Adjusting and Testing Coils. Servicing Commercial Receivers. Second-Channel Interference. Background Noises. Speaker Faults and Remedies. Equipping a Workshop. Wireless Calculations, etc.

6/- NET. (By post 6/6).

Of all Booksellers, or by post from:

GEORGE NEWNES, LTD. (Book Dept.), TOWER HOUSE, SOUTHAMPTON STREET, STRAND, LONDON, W.C.2.

George Newnes, Ltd.

WORLD CONTACT WITH A TROPHY

IN THESE HISTORIC TIMES WORLD LISTENING PROVIDES A NEVER ENDING SOURCE OF INTEREST AND ENTERTAINMENT.

THE
TROPHY IS
SPECIALLY DESIGNED
FOR ALL-WORLD
RECEPTION



TROPHY 6 Valve incorporating all latest improvements. 6.5 to 545 metres. Built-in Speaker, A.C.
£11.11.0 or 45/- deposit and 34/6 monthly



TROPHY 8 Valve A.C. A super communication receiver with amazing range. 7 to 550 metres.
£14.19.6 or £3 deposit and 44/- monthly

PETO SCOTT CO. LTD.

Showrooms at 77, CITY ROAD, E.C.1

SEND FOR FULL SPECIFICATION.

TROUBLE-TRACKING SIMPLIFIED

AVO
Regd. Trade Mark
ELECTRICAL MEASURING INSTRUMENTS

● The Universal AvoMinor and the D.C. AvoMinor put within the reach of the serious amateur a means of rapid precision testing of an accuracy unobtainable with other instruments in their class. Their simplicity and versatility make short work of all the normal trouble-tracking problems. They are worthy members of a range of "AVO" Instruments renowned for their high standard of workmanship and efficiency.

THE UNIVERSAL AVOMINOR ELECTRICAL MEASURING INSTRUMENT

22 Ranges of Direct Readings

D.C. Volts	A.C. Volts	D.C. Milliamps
0-75 millivolts	0-5 volts	0-2.5 milliamps
0-5 volts	0-25 "	0-5 "
0-25 "	0-100 "	0-25 "
0-100 "	0-250 "	0-100 "
0-250 "	0-500 "	0-500 "

RESISTANCE
 0-20,000 ohms 0-2 megohms
 0-100,000 " 0-5 "
 0-500,000 " 0-10 "

Complete with instruction booklet, leads, interchangeable crocodile clips and testing prods.

THE D.C. AVOMINOR ELECTRICAL MEASURING INSTRUMENT

13 Meters in ONE

Current milliamps	Voltage volts	Resistance ohms
0-6	0-6	0-10,000
0-30	0-12	0-60,000
0-120	0-120	0-1,200,000
	0-240	megohms
	0-300	0-3
	0-600	

In case, complete with instruction booklet, leads, interchangeable crocodile clips and testing prods.

● Write for fully descriptive pamphlets and current prices.



THE UNIVERSAL AVOMINOR



THE D.C. AVOMINOR

Sole Proprietors and Manufacturers:

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT Co. Ltd., Winder House, Douglas Street, London, S.W.1.

Phone: Victoria 34047



Reg. U.S. Pat. Off

The World's strongest Valveholder

Manufacturers and Servicemen and all other users of valveholders will be interested in the two following important features of the British-made **CELESTION - AMPHENOL - VALVEHOLDERS**



MOULDED-IN-PLATE

The exclusive Celestion-Amphenol method of moulded-in-plate construction gives greater strength and higher efficiency. The plates are of sturdy cadmium-plated steel.

UNIFORM CONTACT

Celestion-Amphenol contacts are specially engineered for this function and their resilience is critically controlled to give adequate and uniform contact on all prangs.

The above and other good features are responsible for Celestion-Amphenol Valveholders being used by numerous well-known radio manufacturers and for their popularity with radio amateurs and experimenters.

All standard British and American types available.

BRITISH MADE by—

CELESTION LIMITED
KINGSTON-UPON-THAMES, SURREY

Works: Kingston-upon-Thames, and Ashted, Surrey
Telephone: KINGSTON 5656-7-8.



asks indulgence from customers until Peace returns.



(Props.: Oliver Pell Control Ltd.)

Cambridge Row, Burrage Road,
WOOLWICH, LONDON, S.E.18

Phone: Woolwich 1422

PREMIER RADIO

NEW PREMIER S.W. A.C. RECEIVER KIT

In response to many requests we have now produced an A.C. version of the popular Premier Short Wave SG3 Kit. Circuit: Pentode H.F. Stage, Pentode Detector, Beam Power Output, and F.W. Rectifier. 200-250 v. A.C. Operation. Built in Power Pack. Hum-free operation. For use in Phones or P.M. Speaker. Complete Kit of Parts with drilled chassis, all components. Plug-in Coils covering 13-170 metres, 4 valves and full instructions and circuits £4-10-0. Completely wired and tested £5-10-0 Send for full details.

SHORT-WAVE GEAR

Short-Wave Coils, 4- and 6-pin types, 13-26, 22-47, 41-94, 78-170 metres, 2/- each, with circuit. Premier 3-Band S.W. Coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/11.
4-pin or 6-pin Coil Formers, Plain or Threaded, 1/2 each.
Utility Micro Cursor Dials, Direct and 100 : 1 Ratios, 4/3.
New Premier 2-Gang S.W. Condenser, 2 x .00015 mf. with integral slow motion, 5/9.
Bakelite Dielectric Variable Condensers. .0003 and .0005 mf. Suitable Tuning or Reaction, 1/6 each.
Short-Wave H.F. Chokes. 10-100 m., 10½d. each. High grade Pie Wound U.S.A. type, 1/9 each.
Lissen Dual Range Screened Coils. Medium and Long Waves, 2/9 each.

"LEARNING MORSE"

Premier Morse Practice Key on Bakelite Base and Brass Movement **3/3**
General Purpose Morse Key ... **5/10**
Heavy Duty TX Key on Cast Base ... **10/-**
Bakelite Buzzers ... **1/9**
3 Henry Chokes ... **7/6**
Complete Kit of Parts for Valve Oscillator as described in W.W. "Learning Morse" ... **25/-**

SHORT-WAVE CONDENSERS

Trolital insulation. Certified superior to ceramic. All-brass construction. Easily ganged.
15 m.mfd. ... 1/9 100 m.mfd. ... 2/3
25 m.mfd. ... 2/- 160 m.mfd. ... 2/6
40 m.mfd. ... 2/- 250 m.mfd. ... 2/11

MAINS TRANSFORMERS

Wire-ends. All L.T. Windings Centre-Tapped

S.P. 301 300-300 v. 150 m.a. 4 v. 2-3a, 4 v. 2-3a, 4 v. 1a, 4 v. 1a ... 15/-
SP. 350A 350-350 v. 100 m.a. 5 v. 2a (not C.T.), 6.3 v. 2-3a ... 14/-
SP. 350B 350-350 v. 100 m.a. 4 v. 2-3a, 4 v. 2-3a, 4 v. 2-3a ... 14/-
SP. 351 350-350 v. 150 m.a. 4 v. 1-2a, 4 v. 2-3a, 4 v. 3-4a ... 15/-
SP. 352 350-350 v. 150 m.a. 5 v. 2a, 6.3 v. 2a, 6.3 v. 2a ... 15/9

MATCHMAKER UNIVERSAL OUTPUT TRANSFORMERS

Will match any output valves to any speaker impedance.
11 ratios from 13 : 1 to 80 : 1, 5-7 watts, 15/9. 10-15 watts, 20/6. 20-30 watts, 35/-.

PREMIER MICROPHONES

Transverse Current Mike. High grade large output unit. Response 45-7,500 cycles. Low hiss level, 23/-.

PREMIER SHORT-WAVE KITS for OVERSEAS NEWS

Incorporating the Premier 3-Band S.W. Coil, 11-86 Metres without coil changing. Each Kit is complete with all components, diagrams and 2-volt valves. 3-Band S.W. 1 Valve Kit, 14/9. 3-Band S.W. 2-Valve Kit, 22/6.

DE LUXE S.W. KITS

Complete to the last detail, including all Valves and coils, wiring diagrams and lucid instructions for building and working. Each Kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.

1 Valve Short-Wave Receiver or Adaptor Kit ... 20/-
1 Valve Short-Wave Superhet Converter Kit ... 23/-
1 Valve Short-Wave A.C. Superhet Converter Kit ... 26/3
2 Valve Short-Wave Receiver Kit ... 29/-
3 Valve Short-Wave Screen Grid and Pentode Kit ... 68/-

PREMIER 1940

"5v.5" COMMUNICATIONS RECEIVER

A 5-valve Superhet, covering 12-2,000 metres in 5 wave bands.

Beat Frequency Oscillator.
2-Spread Band-Spread Control.
A.V.C. Switch.
Illuminated Band-Spread Dial.
Send-Receive Switch.
Iron-Cored I.F.s.
Phone Jack.
Over 4-Watts Output.

Built into Black Crackle Steel case providing complete screening. 10½ in. Moving Coil Speaker in separate steel cabinet to match.

Receiver, complete with all tubes and Speaker ... **£9.9.0**

Auto Transformers. Step up or down. 100-125 v. to 200, 230 or 250 v. A.C., 60 watts, 9/11 ; 125 watts, 13/6 ; 250 watts, 18/6.

L.T. Transformers, all C.T.
4 v. 2-3 a. ... 9/11 6.3 v. 2-3 a. ... 9/11
2.5 v. 5 a. ... 9/11 7.5 v. 3 a. ... 9/11
5 v. 2-3 a. ... 9/11 12 v. 3-4 a. ... 15/-

Lissen Hypnik GPP Driver Transformers. Ratio 8 : 1. 4/3.

Push-Pull Driver Transformers ... 6/6
Universal Output Transformers. 11 Ratios. Single or Push-pull ... 6/6

Moving Coil Mike. Permanent magnet model requiring no energising. Response 90-5,200 cycles. Output .25 volt average. Excellent reproduction of speech and music. 49/-.
Microphone Transformers, Suitable for all

PREMIER BATTERY CHARGERS for A.C. Mains

Westinghouse Rectification complete and ready for use

To Charge : 6 volts at 1 amp. 22/6
2 volts at ½ amp. 11/9 12 volts at 1 amp. 24/6
6 volts at ½ amp. 19/- 6 volts at 2 amps. 37/6

MOVING COIL SPEAKERS

All complete with transformer. Rola 8 in. P.M.s, 16/6 ; 10 in. B.T.H. 1,600 ohm. field, less transformer, 11/6.

ENERGISED MODELS

Plessy 8 in. 175 ohm field, 7/6 ; G.12 energised, 59/6 ; 10 in. B.T.H. 1,600 ohm. field, less transformer, 11/6.

PREMIER 1940 HIGH FIDELITY AMPLIFIER KITS

Each Kit is complete with ready drilled chassis, selected components, specially matched valves and full diagrams and instructions.

	Completely Kit of Parts Wired and with Valves Tested
3-watt A.C. Amplifier...	2 6 6 3 4 0
3-watt A.C./D.C. ...	2 6 6 3 4 0
6-watt A.C. ...	6 2 6 7 0 0
8-10-watt A.C./D.C. ...	5 5 0 6 2 6
15-watt A.C. ...	6 14 0 8 2 6

Black Crackle Steel Cabinet 15/- extra.

REPLACEMENT VALVES FOR ALL SETS

Europa Mains Valves. 4 v. A.C. Types A.C./H.L., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C.P., all 5/6 each. A.C./H.P., A.C./V.H.P., 7-pin, 7/6. A.C./Pens, 1.H., 7/6 ; A.C./P.X.4, 7/3 ; Oct. Freq. Changers, 8/6 ; Double Diode Triodes, 7/6 ; 3½-watt D.H. Triode, 9/9. 350 v. F.W. Rect., 5/6 ; 500 v., 6/6. 13 v. 2 amp. Gen. Purpose Triodes, 5/6 ; H.F. Pens. and Var.-Mu. H.F. Pens., Double Diode Triodes, Oct. Freq. Changers, 8/6 each. Full and Half-wave Rectifiers, 6/6 each.

Triad U.S.A. Valves

We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for TRIAD High-grade American Valves. All types in stock. Standard types, 6/6 each. All the new Octal Base tubes, at 7/6 each. 80-5/6.

Premier Pick-up Heads.

Will fit any tone-arm ... 5/3
ANOTHER SPECIAL OFFER.
Rothermel Brush Piezo Crystal Pick-ups. New Junior P.U. with arm, 19/6. Standard, S.8. Model with arm, 29/6. P.U. head only, De Luxe Model, 19/6.

mikes. Tapped secondaries. A. 20 and 40 : 1 ; B. 30 and 60 : 1. 6/6 each.
Microphone Stands. Bakelite floor stand, 9 in. ring, 7/6 each. Adjustable Table Stand, 8 in. ring. Chrome finish. 26/6.

ALL ENQUIRIES MUST BE ACCOMPANIED BY 2½d. STAMP.

PREMIER RADIO CO.

ALL POST ORDERS to: JUBILEE WORKS, 167, LOWER CLAPTON ROAD, LONDON, E.5 (Amherst 4723).

CALLERS to: Jubilee Works, or 169, Fleet Street, E.C.4 (Central 2833), or 50, High Street, Clapham, S.W.4 (Macaulay 2381).

Practical and Wireless

★ PRACTICAL TELEVISION ★

EVERY MONTH

EDITED BY
F. J. C. AMM

Staff:
W. J. DELANEY, FRANK PRESTON.
H. J. BARTON CHAPPLE, B.Sc.

Vol. XVII. No. 413. November 1940

COMMENTS OF THE MONTH

Broadcast Propaganda

SINCE Capt. Plugge raised the matter in Parliament, as reported in last month's issue, Government spokesmen have announced the intention to improve not only upon the quantity, but the quality of our broadcasts in foreign languages. Germany has taken over many dozens of stations in the lands of the vanquished, and by cunning adroitness, prevarication and carelessness with the truth, she is endeavouring to convince the few neutral countries remaining that her cause is just. Our case, supported by truth and far stronger arguments than anything Germany can invent, may not have been well presented in the past.

We must now, however, overlook the fact that the final result is not always affected by the propaganda which takes place before it. There is a somewhat parallel case in the newspaper articles which precede any national sporting event such as a football match or a boxing contest. Each side breathes optimism, and endeavours to instil fear in the opponent. Newspaper critics add their opinions as to why one side or the other must win or lose. Read after the event this propaganda appears ridiculous. No doubt when this war is over the German propaganda will read equally quaint, for as a large lie it will lie exposed. You cannot win battles by words alone, but as the Germans continue to lie with diabolical consistency it is necessary for us forcefully to tell the truth and with greater assiduity. A lie told sufficiently often and left unchallenged may be believed on the basis that silence conveys consent.

We agree with the speaker in the House of Lords who said that we must appoint to the task an expert newspaper man who knows how to assimilate facts, and also how to present them in a telling way. It is not sufficient to appoint someone who has merely written occasional articles

for the press. Such are not journalists. We must appoint someone who has been trained in the inside routine of newspaper production.

Music at Work

NEARLY three months ago the Music While You Work feature was inaugurated by the B.B.C., and a daily programme of this type has been radiated. Since that time the Minister of Supply and the Minister of Aircraft Production have each announced satisfactory increases in production. It would be impossible, of course, to ascribe this increase entirely to the radio programmes, but we believe that it has had a good deal to do with it.

If such a system is found successful in war it should be found equally so in peace, and the lesson needs to be borne in mind when normality returns.

Illegal

ACCORDING to a recent decision it is illegal to remove a radio set in a car from house to house, or to take it in a car to be repaired. The case in which this was announced was tried at the Norwich bench when a man was fined 2s. 6d. for "Installing

a wireless receiving apparatus in his car." He had carried the set to the dealer to be repaired, but collected it in his car. The Superintendent of Police said that the repairers would have to apply for a permit to return it by car. The bench apparently took a dim view of the attitude of the police by imposing such a small fine. They were evidently anxious to stretch the law in order to make a case. It is monstrous that the time of courts should be wasted in this way. The law concerned was designed against the Germans and Fifth Columnists, not against honest British citizens.

The Sponsored Programmes

NOW that the sponsored radio programmes have ceased owing to Hitler's invasion of the countries which permitted commercial broadcasting, listeners have perforce to listen mostly to our own programmes. These have been so improved that it is unlikely that when the war is over sponsored programmes will regain their audiences. This is all to the good. If this country does want sponsored programmes let us erect a special station in this country to radiate them. This will keep the money in the country instead of allowing it to percolate to foreign powers who use it directly and indirectly to make munitions to use against us.

Sponsored programmes were tried by the B.B.C. some years ago, but they were so hampered by restrictions that they ceased to have any value to the sponsor from an advertising point of view. The programmes were merely prefaced by an announcement that they were sponsored by particular firms. If listeners want sponsored programmes let them have them, but do not make the conditions so onerous that the advertiser is merely paying for the programme, and thereby reducing B.B.C. expenses without gaining publicity in return.

Editorial and Advertisement Offices:
"Practical Wireless," George Newnes, Ltd.,
Tower House, Southampton Street, Strand,
W.C.2. Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by
Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in PRACTICAL WIRELESS. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Problems of Amateur Receiver Design—3

Switching Arrangements : Ganging Wave-change Switches : Combined Wave-change and On-off Switching : The use of Potentiometer Volume Controls with Built-in Switches

By FRANK PRESTON

WITH other than the simplest types of receiver, the question of wave-change and on-off switching is often an important one, particularly in a set designed for reception on three or more wave-bands. It is, of course, an easy enough matter to fit a wave-change switch for each coil, and then to have a separate switch for switching the batteries or mains on and off. But that would be very cumbersome in a receiver of the two-H.F. type, in which there are three tuning units; the same would apply to a single-stage-H.F. receiver if there were a band-pass filter.

In the first place it will be best to take the case of a fairly straightforward set of the type represented by the skeleton circuit shown in Fig. 1. Here there is a band-pass filter in the input circuit, a tuned-grid coupling between the H.F. and detector valves and a battery on-off switch. For simplicity it is assumed that the receiver covers only two wave-bands. That means that a single-pole switch can be used for wave-changing on each of the

are in the same position—that is, that the contacts of each are either open or closed. If this were not done, it would be found after fitting the ganging spindle, that it could not be turned.

Earthing

Another important practical point concerning this arrangement is that the spindle should be well earthed to the chassis or to nearby terminals which are themselves connected to earth. This can be done by making a couple of L-shaped arms from springy brass and mounting them on the baseboard so that the upright "leaves" press against the spindle; Fig. 2 shows the idea. If the chassis or baseboard is metallised nothing further need be done, but if it is insulated (wooden, for example) earth leads must be taken from the screws used to mount the contact plates. Failure to take this precaution may in some instances result in instability or serious hand-capacity effects.

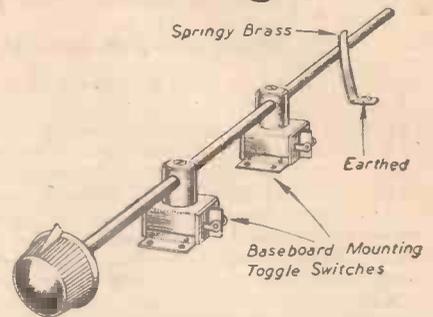


Fig. 2.—How baseboard-mounting toggle switches can be used for a circuit of the type shown in Fig. 1. Only two of the three switches are shown, but any number could be ganged together.

Double-purpose Switch

When adopting this method of wave-change switching it is still necessary to have a separate on-off switch, since it cannot well be ganged with the other three. When only two coils are used in the receiver wave-changing and on-off switching can often be combined by using a three-pole change-over switch of the so-called anti-capacity type, as shown in Fig. 3. Other forms of switch of this type could be used, but it is desirable that the capacity should be low and therefore many forms of multi-point switch are ruled out. Even when using the anti-capacity switch it should be close to both coils if trouble due to instability and loss of efficiency is to be avoided. That is why a four-pole change-over switch is not recommended when there are three coils in the receiver; it would be a practical impossibility to have the switch close to all three coils and at the same time to place the coils so that the grid and anode leads are all short.

It will be noticed that the type of switch mentioned has a central "off" position. Thus when the knob is in its central position the L.T. circuit is broken. When it is turned in one direction the set is switched on and the W/C switch sections are adjusted for M.W. reception; when it is turned in the opposite direction the L.T. circuit is again completed but the W/C switch sections are set for long waves. It should be noted that this type of switch is unsuitable for mains-circuit connection where a quick-make-break action is essential.

Inset in Fig. 3 is shown a flat rotary-type switch of the three-pole, three-way type which could be used in some cases to replace the more bulky anti-capacity switch. The alternative connections to it are shown in broken lines.

(Continued on next page)

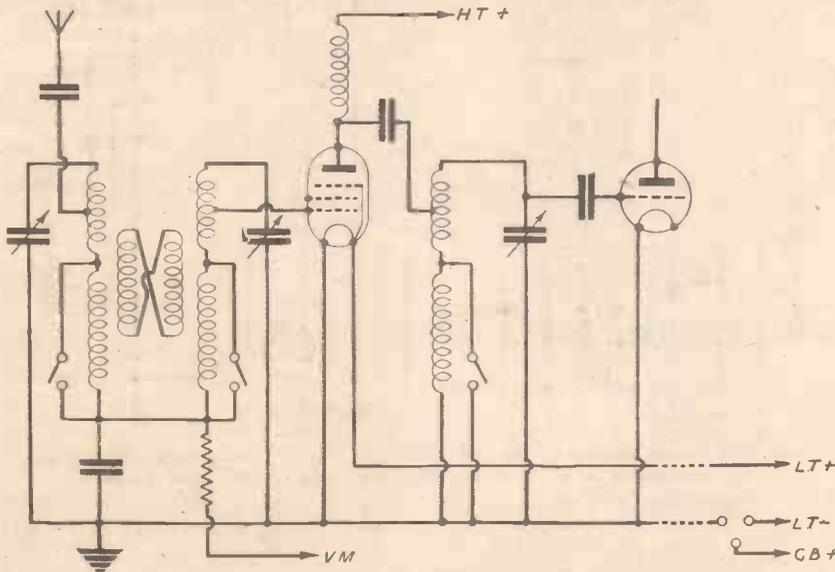



Fig. 1.—A simple H.F. arrangement with band-pass where three wave-change switches are used.

coils. If the coils were bought as a ganged set they would probably have W/C switches built into them, but we will assume that separate coils (probably home-made) are to be used.

Ganged Toggle Switches

As far as wave-change switching is concerned it would be simple enough to use three on-off switches ganged together. Thus, baseboard-mounting toggle switches of the type shown in Fig. 2 could be employed. Each switch would be placed as near as possible to its own coil, the three would be arranged accurately in line and a single rod, carrying a knob, would be passed through them before tightening the locking grub screws. In following this arrangement it is important in the first place to make sure that all three switches

Fig. 3.—How a three-pole two-way "anti-capacity" switch of the old type can be used for on-off and wave-change switching. Connections are also shown in broken lines for three-pole, three-way rotary switch.

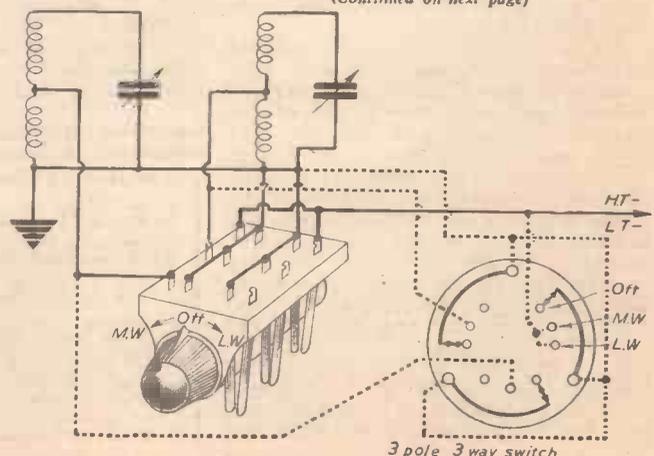

PROBLEMS OF AMATEUR RECEIVER DESIGN

(Continued from previous page.)

Ganged Q.M.B. Switch

When using coils with built-in wave-change switches it is often possible to gang a Q.M.B. or toggle on-off switch by fitting a metal "finger" on the end of the switch spindle, as shown in Fig. 4. The switch arm is slotted, and switches with an arm of this type are available; in fact, the arrangement illustrated has been used on many ready-made tuning-coil assemblies. The metal "finger" is situated so that the first short clockwise movement of the wave-change switch knocks the switch on. After that, the "finger" leaves the toggle arm and serves only for wave-changing until the spindle is moved back to its original position, when it knocks the switch off. If it is necessary to convert an existing coil assembly to this arrangement a certain amount of practical ability is necessary to make the "finger" and also to mount the toggle switch so that it is properly operated. A small metal bracket can be used for the switch mounting and the "finger" can be made from a piece of brass measuring about $\frac{1}{4}$ in. by $\frac{1}{4}$ in., by $\frac{1}{2}$ in. long. It should be filed to the approximate shape illustrated and then drilled to fit over the end of the spindle; after that a small hole should be drilled at right-angles to the latter and tapped to take a small grub screw.

Rotary Switch Units

A form of switching which is probably more widely used than any other at the present time is that in which a number of rotary units are ganged together by means of a square-section spindle. By using a little ingenuity, a set of switches of this type can be used, with one-knob control, to provide wave-changing and on-off switching with almost any combination of coils. The method is especially useful when multi-range coils are used, or when a series of coils is used in each tuning circuit—one for each of the wave-bands covered.

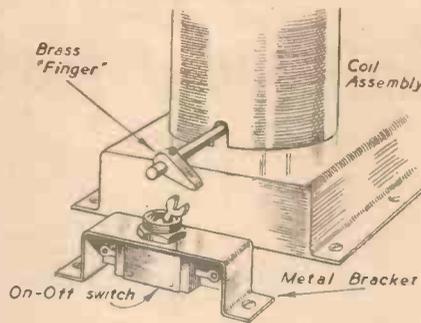


Fig. 4.—A method of operating a toggle on-off (battery or mains) switch from the spindle of built-in wave-change switches.

As an example we might consider the circuit shown in Fig. 5, where there are three different tuning units of similar type. They provide four-range tuning in conjunction with a three-gang condenser. Four switches are shown, of which one is for on-off battery switching. The first three switches are wired as shown inset, the fourth being wired for on-off switching only. It is often possible to employ a system

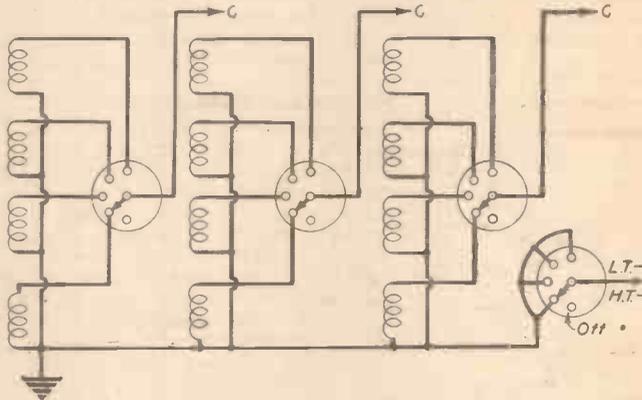


Fig. 5.—Four five-way rotary switches for on-off and wave-change switching in a four-range receiver with three tuning circuits. Various slightly-modified types of switch may be used, but separate units are to be preferred if the coils are not close together.

simpler even than this by having rotary switching with a double-ended contact arm, so that one switch can be used on two coils. Additionally, there are various double-sided rotary switches, each side of which acts as a separate switch unit. These have many applications, but before choosing them the question of capacity between connecting leads of necessity placed close together must be considered.

Potentiometer-switch Units

Reference has been made above to combining the on-off switch with the wave-change switch. This is not always the best arrangement, however, and it is often preferable to combine the on-off switch with a volume-control potentiometer. The latter may be used as a variable-mu control or may (if connected in series with a .0003 to .0005 mfd. fixed condenser) be used to replace the customary variable condenser in the reaction circuit. Provided that the potentiometer is a good one, with electrically-quiet action, this form of reaction control is an excellent one. All switches built in unit with volume controls are of the Q.M.B. type, and can therefore be used equally well on either mains or battery receivers.

New Director of Telecommunications

THE Postmaster-General has appointed Mr. J. Innes, B.Sc., M.I.E.E., Principal Assistant Secretary, to be Director of Telecommunications on the retirement of Mr. F. W. Phillips, C.M.G., last September. Mr. Innes has also been appointed a member of the Post Office Board.

Biographical Notes

Mr. J. Innes, who is 51 years of age, was educated at the Royal High School and Heriot Watt College, Edinburgh, and after training as a Civil Engineer entered the Post Office Engineering Department by examination in 1913. For most of his earlier years of service he was engaged on telegraph and telephone engineering in the field, including a period of service on communications required by the Admiralty in the North of Scotland, Orkney and Shetland, during the last war. Subsequently he returned to Edinburgh where he took charge of the work of converting the Edinburgh telephone system to automatic working.

In 1929, Mr. Innes was lent to the South African Government as an adviser on automatic telephone systems, and was responsible for the schemes installed in Johannesburg and the Cape Peninsula. He visited the United States in 1933 as a member of a special mission on communications, and

has visited Germany and Poland in a similar capacity.

As Staff Engineer and Assistant Engineer-in-Chief, he was employed in Engineering Headquarters on problems affecting the development of the British Telephone System, and in 1936 he was transferred to administrative duties as Assistant Secretary. Since that time, Mr. Innes has been responsible for the administration of the telephone service in this country, and in 1939 became a Principal Assistant Secretary when the war activities of the Post Office on communications were greatly increased and were placed under his charge. He will continue in charge of these functions in his new capacity.

BOOK RECEIVED

RADIO-FREQUENCY MEASUREMENTS BY BRIDGE AND RESONANCE METHODS. By L. Hartshorn, D.Sc., A.R.C.S., D.I.C. 265 pp. 99 illus. Published by Chapman and Hall, price 21s.

THIS is Volume X of a series of Monographs on Electrical Engineering and deals with the main principles of R.F. measurements. There are, of course, many schemes available, but the majority are merely modifications of certain basic schemes which are detailed in this book. The chapters are Impedance and Related Quantities; General Principles of Impedance Measurement; Resonance Methods; The General Principles of Screening and the Radio-Frequency Bridge; Generators; Detectors; Standards of Capacitance; Resistors; Standard Inductors; Measurement of Capacitance and Inductance by Resonance Methods; Resistance, Power Factor, Decrement, etc., by Resonance Methods; Bridge Methods; and Methods for Very Short Waves. These titles will give some idea of the scope of the book which is well written and although, naturally, mathematics have to be entered into, the work is not complicated. There is a list of symbols and a useful bibliography. All students of modern radio should get a copy for reference.

The PRACTICAL WIRELESS ENCYCLOPÆDIA
 By F. J. CAMM
 (Editor of "Practical Wireless") **7/6** Net

Wireless Construction, Terms, and Definitions explained and illustrated in concise, clear language
 From all Booksellers, or by post 8/- from George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2.

A Service Engineer's Log

A Further Selection of Simple Faults and Their Remedies

A RECEIVER which I had to attend to last week was of the "straight" H.F.-Det.-Pen. type, and the fault was lack of signal strength and marked reduction in selectivity. It was a fairly old set, but was of good make, and had been running well for a number of years. In making a preliminary test the first thing I noticed was that the reaction condenser had no appreciable effect. That at once gave me an idea, but before following up my train of thought I checked the H.T. battery connections and took a voltage reading of both this and the L.T. accumulator; both were reasonable.

H.F. Choke Shorted

I was therefore convinced that my first idea was correct. With a short piece of wire I short-circuited the H.F. choke in the detector anode circuit—that gave an immediate improvement and the set could be made to oscillate, but only just. When

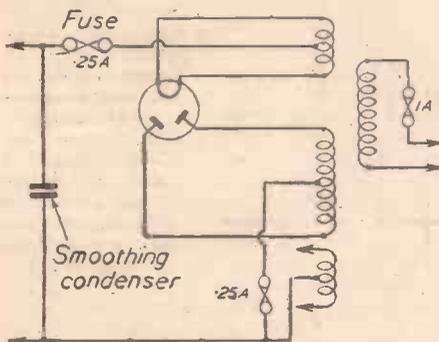


Fig. 1.—Alternative positions for a safety fuse in the rectifier circuit. The fuse in the mains lead should be used in addition. Indicated values are approximate only, and depend largely on the rectifier output.

the choke was replaced by a new one everything was as it should be. The choke had, apparently, developed an open circuit—or, at least, a very high internal resistance—with the result that scarcely any H.T. was able to reach the detector anode. That made the detector extremely inefficient and entirely incapable of oscillating. Where R.C.C. coupling is used it is often found that the same form of trouble as that described above is due to the detector anode resistor being defective. If shorting the choke does not make any alteration, therefore, the next step should be to try a replacement resistor. If that is not available a fair test can be made by placing a short length of moistened string between the resistor terminals; this provides the necessary resistance, although the value may be entirely unsuitable. But having discovered that the resistor is faulty it is an easy matter to obtain a new one of correct rating.

Poor Quality with Bias

Another fault recently traced in a battery set was shown by the fact that signal strength was extremely poor and quality was lacking unless the G.B. negative connection was removed from the battery. This suggested to the owner of the set (which was home-made) that the H.T. battery was at fault, although it had not

been in use for very long. He tested with an H.R. voltmeter, and found that the nominally 108-volt battery showed 85 volts, which was not considered to be too bad. Unfortunately, however, he had made the test when the set was switched off; had he made it while it was in use he would have found that the voltage shown was lower.

The battery had a number of tapping points, and by testing between each of these in turn it was soon found that the cells between one particular pair were practically exhausted. This was probably because an exposed piece of metal had carelessly been left touching them at some time. To effect a simple cure the defective cells were cut out by short-circuiting the two sockets. It should be mentioned, however, that this is not a procedure to be strongly recommended, since the shorted cells soon burst open, make a nasty mess of the battery and eventually damage other adjacent cells.

Hot Mains Transformer

Another owner, this time of a mains superhet of doubtful origin, brought in his set for test, pointing out that the mains transformer was probably in need of replacement. This was because it had obviously been running very hot and the pitch filling had run on to the chassis. The "hot smell" had been noticed for some time before the set finally ceased to operate, but had been ignored. It was not considered wise to connect the set to the mains until a few tests had been made, because this might have resulted in further damage. In making a scrutiny of the set after removal from the cabinet it was noticed that a cardboard-cased electrolytic smoothing condenser looked as if it had been rather "under the weather," for the wax had run from it and the case appeared to be slightly charred.

Continuity and Resistance Tests

A simple insulation test was made by means of a multi-purpose meter set for resistance readings. This showed that there was practically a dead short through the condenser, which was at once replaced. Similar tests made across the transformer windings and between the windings and the core showed that this component had not suffered to any marked extent. The mains supply was therefore connected so that a further test could be made. But the set would not work, although there was no further sign of excessive heating.

It was not until the rectifying valve had been replaced that the receiver be-

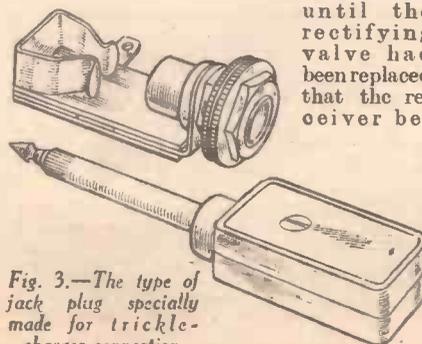


Fig. 3.—The type of jack plug specially made for trickle-charger connection.

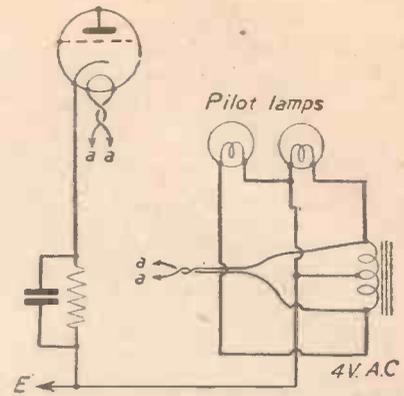


Fig. 2.—Small 3.5-volt flashlamp bulbs, used as pilot lights, may be wired as shown above. If they were merely in series, failure of either bulb would cause both lights to go out.

haved normally. The valve had no doubt been damaged due to the output from it having been short-circuited.

Correct Fusing

There are at least two morals to this experience: if a good, branded condenser of 350 volts working (the H.T. was 250 volts) had been used it would have been very unlikely to break down; if a fuse had been inserted between the rectifier and the condenser, failure of the condenser would not have resulted in damage to the rectifier. Alternative positions for the fuse are shown in Fig. 1.

Pilot-lamp Bulbs

What to many will seem a foolish point was raised recently by a complaint from the owner of an efficient home-made mains receiver that the dial-light bulbs burnt out very quickly—generally after being in use for only an hour or so. They were, as is fairly general, fed from the 4-volt winding of the mains transformer and were of the type intended for use with a 3.5-volt flashlamp battery. The owner was surprised when told that these were entirely unsuitable, since they were being seriously over-run. He overlooked the fact that there is an appreciable voltage drop across a small dry battery when it is supplying .3 amp. (the usual rating of these bulbs) whereas the voltage from the transformer winding is A.C. and remains at the full rating when the set is switched on.

Not only is it desirable to use specially robust bulbs for mains-set pilot lights, but it is also generally desirable to use 6-volt bulbs for connection to the 4-volt heater winding. An alternative method which is sometimes satisfactory is to feed one 3.5-volt flashlamp bulb from each half of the 4-volt winding; that is, to connect one side of each to the centre tap (or earth line in nearly every case) and to connect the other sides to the ends of the winding, or to each of the heater terminals on a nearby valveholder. See Fig. 2.

Trickle-charger Connection

A constructor had decided to fit a neat jack on the cabinet of his set for the connection of a plug connected to the trickle charger. The jack was, of course, permanently connected to the accumulator inside the set, so that to charge the battery it was necessary only to insert the plug after switching on the mains supply to the charger. He was very concerned, however, because he noticed that every time the plug was inserted there were various sparks

(Continued overleaf)

A SERVICE ENGINEER'S LOG

(Continued from previous page)

between the plug tips and the jack. The reason for this was that he had used an ordinary ball-ended plug; when this was inserted into the bush of the jack the ball tip and shank were short-circuited.

The trouble could be overcome by inserting the plug before switching on the charger, but the proper method is to use a special type of plug, as shown in Fig. 3. This has a small-diameter tip which is pointed; thus it cannot make contact with the bush of the jack when the shank has been inserted.

Faulty Volume Control

Volume controls are often a source of trouble after they have been in use for some time. In most cases the fault is shown by the fact that the control operates smoothly for part of the movement of the knob, after which it becomes erratic. Thus, when the knob is turned to about its midway position, there is a sudden "cut-off," but if the control is advanced through another few degrees full volume is given. It is generally best to replace the component when faults of this kind are experienced, but before doing so make sure that the knob is tightly clamped on its spindle and that the potentiometer is secure on the panel or mounting bracket. This is mentioned because in a recent case which came up for investigation it was soon found that the trouble was due only to one connection being loose and to the component not being tightly fitted to the panel. In consequence, the body of the control turned and occasionally caused the terminal contact to break.

Cleaning Method

In other instances it had been found that either the slider arm or the potentiometer element is dirty, so that a bad contact is made at certain settings. A good and generally "safe" method of cleaning is to apply a spot of carbon tetrachloride to the element and then to move the arm backward and forward a few times. After that, wipe the whole with a piece of silk waste to remove any dirt which may have been loosened.



B.L.D.L.C.

IN view of the correspondence we have received concerning super one-valvers, we do not feel that it is necessary to offer any apologies for returning to the subject once again in these columns. As a matter of fact, one member has been good enough to send in sufficient working details about the little set he has been using with such success to enable others to have a shot at getting similar results. We are indebted to Member No. 6,032 (P. Yeates, of Bedford), for the following particulars, and we sincerely hope that other members will take this as a cue to send in practical details of their own particular pet set or circuit. P. Y.'s letter reads: "I have been


Wise Remarks

"I have kept a detailed log-book (a very wise procedure, and one which we are always advocating—Hon. Sec.), giving the date, call-sign, R., Q.S.A., Q.R.M., Q.R.N., Q.S.B., country, time during which the transmission was heard and whether it was calling C.Q. or Test, etc." (Then follows a fine list of the stations logged during a recent month, but space prevents us, or should I say the lack of space, from giving it in detail—H. S.) "The secret lies," continues P. Y., "not so very much with what you listen to, but how you listen. First, the ability to tune in an elusive signal and second, *great patience is essential*. I often used to spend half an hour glued to one spot on the 20-metre band trying to identify an amateur, and I am confident that if I hadn't adopted such methods I shouldn't have logged all the countries mentioned above, i.e., 101. I think that in my RX I happened to strike on a lucky combination of parts and layout, but I would mention in passing that I was experimenting for about 12 or so months before being satisfied with the results.

"The accompanying theoretical circuit tells its own story. It is a perfectly straightforward arrangement, the usual series reaction control, and a 6-pin coil for the three windings. The reaction condenser is an Eddystone incorporating a 10 : 1 slow-motion drive, whilst the tuning is carried out by an ordinary .0005 mfd. variable which has connected in series with it a fixed condenser having a capacity of .0003 mfd., the idea being taken from an article in PRACTICAL WIRELESS.

"The coil constructional data was also given in the journal, and, in spite of its simplicity, it seems very efficient. The coil-former consists of a short length of 1½ in. diameter cardboard tube which had previously been well dried. All winding was carried out with 22 S.W.G. enamelled wire, the aerial coupling section having 1½ turns, the grid coil 6½ turns, and the reaction winding 8½ turns. For tuning control an Eddystone dial giving ratios of 120 : 1 and 20 : 1 is used; the valve-holder (of the low-loss type) and the H.F. choke are both products of the same maker. (Eddystone.)

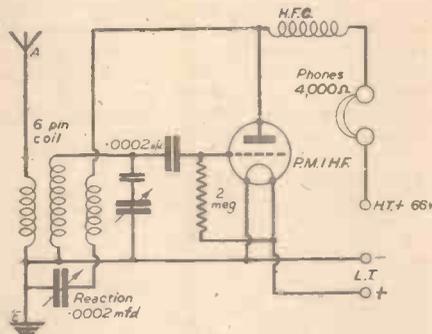"The plan of the set is not strictly to scale, but I think it explains itself. The battery leads are connected directly to their respective points without any intermediate terminals. It will be seen that room has been left on the baseboard for the addition of an L.F. stage if and when required."




The circuit appears to be quite ordinary, but the careful selection of components and the lay-out make it a real Dx'er.

reading lately in the B.L.D.L.C. page about your inquiries for details of super one-valve receivers, particularly as regards construction and circuit. I note that you say many letters have been received on the subject, but the details that matter are conspicuous by their absence; in view of this, I am sending full details of my own.

Results Obtained

"I have received with it transmissions from 101 countries on 'phone (mostly amateurs) and have verifications, which I am willing to send as proof, from the following:—VR6AY, Pitcairn Island, K6NZQ, K6OQE, K6BNR, Hawaii, VLQ, Australia, HS8PT, Siam, VS2AK, Malaya, KA1BH, Philippines, ZS6AT, S. Africa, W9XF, Chicago, HJ1ABE, Colombia, PY5Q, PY2BA, Brazil, LU1HI, Argentina, TF3C, Iceland, and one from Barcelona, Spain.

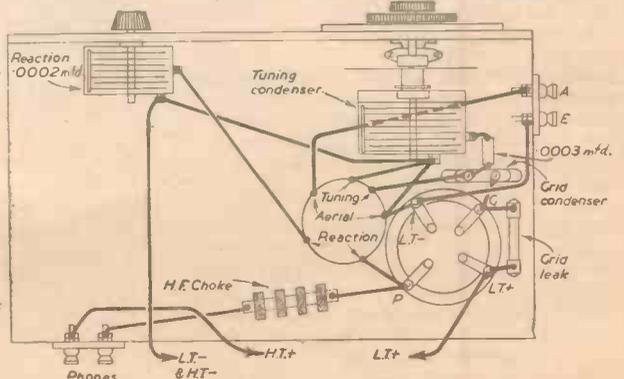

This plan shows how the constructor has endeavoured to keep H.F. leads as short as possible. Ample space is left for an L.F. stage.

VALUABLE TECHNICAL LIBRARY!

- NEWNES SHORT-WAVE MANUAL
5/-, or 5/6 by post.
- PRACTICAL WIRELESS ENCYCLO-
PEDIA
7/6, or 8/- by post.
- EVERYMAN'S WIRELESS BOOK
5/-, or 5/6 by post.
- SIXTY TESTED WIRELESS CIRCUITS
3/6, or 4/- by post.
- COILS, CHOKES AND TRANSFORMERS
3/6, or 4/- by post.
- PRACTICAL WIRELESS SERVICE MANUAL
6/-, or 6/6 by post.
- PRACTICAL MECHANICS HANDBOOK
6/-, or 6/6 by post.
- WORKSHOP CALCULATIONS, TABLES AND
FORMULÆ
3/6, or 4/- by post.
- WIRELESS TRANSMISSION FOR AMATEURS
3/6, or 4/- by post.
- DICTIONARY OF METALS AND THEIR
ALLOYS
5/-, or 5/6 by post.
- RADIO TRAINING MANUAL
3/6, or 4/- by post.
- RADIO ENGINEER'S VEST POCKET BOOK
3/6, or 3/9 by post.
- THE SUPERHET MANUAL
5/-, or 5/6 by post.

All obtainable from GEORGE NEWNES, LTD.,
Tower House, Southampton Street, Strand, W.C.2

ON YOUR WAVELENGTH



The New Interval Signal

AFTER a lot of discussion about the comparatively trifling matter of the interval signal the B.B.C. has decided on the musical notes B.B.C. This is an improvement upon those monotonous bells introduced during Reith's time. I suppose in view of the B.B.C.'s well-known predilection for religious music and programmes it was inevitable that sometime during their career they would choose church bells. They were not joybells and their effect upon me was one of depression and gloom. No doubt this is a reflex action from my youth, when all church programmes were made as miserable as possible. Church bells to me meant miserable church services. As long as an interval is distinctive, however, it does not much matter what it is. There is a certain sadness however about the new signal which is pitched one octave higher than middle C. My waggish mind immediately thought how appropriate the new signal was since most people turn a D.E.F. ear to many of the programmes. B.B.C.—D.E.F. Got it?

The Late Sir Oliver Lodge

THAT picturesque character Sir Oliver Lodge has passed away. Throughout his life he enjoyed a reputation as a scientist, but, and he would have been the first to admit it, he was not a scientist in the accepted sense of the term. He was a student of science, and having studied a particular branch of it, he had the happy knack of being able to re-present what he had assimilated in popular language. His contribution to wireless telegraphy was the production of the tuning circuit. I will not say that he invented it, because so many others had much to do with it. There is very little that can be associated with Lodge's name from the point of view of invention. Nothing readily jumps to the mind as it does with Fleming, Hertz, Newton, Edison, Graham Bell and others. You may gauge from his writings that he was not an inventor. Few inventors are, for example, interested as he was in spiritualism, for inventors, engineers, and scientists are practical people who do not believe in nebulous improbabilities. Here are the titles of a few of his books: "Evolution and Creation"; "Why I believe in Personal Immortality"; "The Reality of a Spiritual World"; "Life and Matter"; "The Substance of Faith"; "The Survival of Man"; "Parent and Child"; "Reason and Belief"; and so on. They are all subjects on which anyone could write anything, and they are subjects on which we can each have our own viewpoints; as the subject is intangible no one can prove or disprove the views of the author. His scientific works were of a somewhat similar character in that they dealt with opinions, and were of somewhat simple and non-scientific character. I give you the titles of a few of them: "Elementary Mechanics"; "Modern Views of Electricity" (note that the book was only an expression of views, not necessarily his own); "Pioneers of Science" (this was something of a pot boiler); "Modern

By *Thermion*

Problems"; "Signalling without Wires"; "Lightning Conductors and Lightning Guards"; "School Teaching and School Reform"; and "Atoms and Rays." None of these books could really be called a scientific work. They were popular presentations of known ideas, to which Sir Oliver contributed very little.

Therefore, it is as a teacher and a student that I prefer to regard the late Sir Oliver Lodge. It is wrong for the world to regard him as a scientist. He was a popular presenter of the discoveries and inventions and theses of others. When asked to lecture or speak he nearly always chose a subject on which it would be fairly safe to express an opinion without fear of contradiction. He was born on June 12th, 1851, at Penk-hull, near Stoke-on-Trent. He was educated at Newport Grammar School, matriculated and entered University College, London, to study mathematics and physics. He was an Hon. D.Sc. of Oxford, and lectured on Physics at the Bedford College for Women and was appointed a Professor at the University College. In 1881 he was elected Professor of Physics at Liverpool, and in 1887 became a Fellow of the Royal Society. In 1900 he was appointed Principal of the University of Birmingham. His book "Raymond" caused great controversy for it dealt with spiritualism and life after death. In it he suggested that they smoked cigars in heaven! As one biographer has said: "Nobody ever solved the problem of how a scientist accustomed to the most rigorous methods of evidence and proof should have accepted evidence of such a different nature for the existence of Life after Death."

He himself deposited in a sealed envelope

Our Roll of Merit

Our Readers on Active Service—Eighth List.

- H. C. P. Stacey
(L/Cpl., R.A.),
Edinburgh.
- A. E. Coleman
(L.A.C., R.A.F.),
Halton, Bucks.
- D. Dudding
(Pte., I.T.C.),
York.
- H. Summons
(Leading Stoker, R.N.),
C/o G.P.O.

certain statements so that when he died mediums could endeavour to find some means of contacting him. Reports say that in the envelope is a formula with a mistake in it, the names of two towns, quotations from three of his favourite songs, the name of a cliff, and some childish idiosyncrasy. There are many who thought that his somewhat childish beliefs in such matters ill befitted one who claimed to be a scientist. The mediums have the answer. Other scientists have died before Sir Oliver, and it is unthinkable that if they are still able to exercise their scientific attainments they would not be able to communicate with us. Hertz and Newton, Galileo and Archimedes—these are a few names that have gone before.

It is, however, beyond all doubt that Sir Oliver spent his life in an endeavour to present scientific facts so that they could be understood by the millions.

The Radio War

NO doubt following the remarks of Capt. Plugge in the House of Commons, I learn that the Government now intend to take steps to combat Germany's radio superiority. Lord Caldecote, the Dominions Secretary, assured the House of Lords on this point recently. Germany has the advantage at present because she has appropriated practically all the broadcasting stations in the vanquished countries, whilst we are confined to stations operating mainly from Britain. Already Great Britain is issuing 72 news bulletins in 29 languages. Good, but it is not regarding the number but the quality that I am concerned. There should be bite, enthusiasm, adroitness, and topicality about news in foreign languages. We do not merely require a recitative of news; such must be presented in a propaganda manner. We have a better case than the Nazis, but we do not present it so well. We want a Ministry of Inspiration as well as a Ministry of Information. We have plenty of material available, and I suggest that the Ministry engages some of the vast army of expert copy writers who are at present disengaged to promote our case over the air. As Lord Addison said during the debate: "I am always afraid of newspaper people. They give me a sort of creepy feeling that they have been brought up in a world of which I know next to nothing. But if you want a case presented you have got to employ someone who is an expert at the job, give him plenty of money, and a free hand." According to Lord Caldecote the Treasury were parsimonious about the use of cables and wireless for propaganda.

A Reader's Offer

L. F. H., of Stourbridge, has a number of copies of this journal—all those issued from January, 1938, to July, 1939—for which he has no further use. The first applicant gets them. If the first applicant is serving with His Majesty's Forces L. F. H. will pay the carriage. Applications should be made on a postcard addressed to me and marked in the left-hand corner L. F. H.

Comment, Chat and Criticism

Outline of Musical History—13

THE name of Richard Wagner—born in Leipzig in 1813, and died in Venice 1883—towers over the century as its greatest figure. His is, in fact, the only other name which might challenge Beethoven's for supremacy; but we won't bring that discussion in now! His contribution to music was so personal, so revolutionary, and so exclusive to one particular form that he can scarcely be classed with anyone else, or with any particular movement or current of opinion; he was, in short, just Wagner.

With the exception of two overtures and one immortal concert-piece—the "Siegfried Idyll"—his work lay entirely in the one sphere of opera, or what he himself designated, music drama. He never wrote a symphony, a sonata or a quartet, but his collection of operas form a fabulous page in musical history, and his peer in that particular domain—as Beethoven's in his—has yet to be born. He was the last great figure in German musical history, only the early to middle period Strauss who, in those days closely resembled him, counts for anything.

Wilhelm Richard was the ninth child of his parents. Shortly after his birth, however, his father caught typhoid—it was during the siege of Vienna—from the many unburied corpses lying about, and died. His much harassed mother, in dire want, then married one Ludwig Geyer, an actor, and gave birth to yet another child, Cäcile.

Early Love of Stage

The master himself tells us that he had a love of the stage from his earliest recollections. Even the orchestra tuning-up at Geyer's theatre used to speak to him of another world of ghosts and shadows.

After a year with his elder brother, who was apprenticed to a goldsmith brother of Geyer's, Richard returned to the theatrical atmosphere of Dresden. Almost all the huge family were either on the stage or training for it. But Richard's passion was to write, not to act. Greek tragedy was his favourite subject at school, and he would invent dramatic scenes by dressing up his sisters' dolls.

Many interesting details of his youth and education must of necessity be passed over. But he tells us himself that it was not long ere he realised that, if the dramatic plots and schemes which were then seething through his mind were to arrive at complete fruition, they could only do so through music. So, at fifteen, his musical studies began in earnest with one Meuller, a violinist in the Dresden orchestra.

As with Greek, he found harmony and counterpoint "bothersome obstacles," and he tells us in his autobiography that he preferred to pore over the scores of "Don Giovanni" or of a Haydn or a Beethoven quartet. But it was performances of Beethoven's Seventh Symphony, "Egmont," and Mozart's Requiem, which made him realise that "music was far more than an adjunct to drama."

In 1829 Meuller advised him to take up the violin, but he soon dropped it—and Meuller. He spent all his time poring over Beethoven's Fifth and Ninth Symphonies. At that time the Ninth was deemed incomprehensible and unplayable, and a product of the master's deaf dotage. But to Wagner it was the most wondrous music

he had ever heard. He made piano arrangements of both works and sent them to Schott, who gave the young master a copy of the "Missa Solemnis" by way of payment. He did not publish them.

Student Days

Some riotous adventures as a student (1830) was a year of revolution, and

A Brief Sketch of the Life and Works of Wagner. By Our Music Critic, MAURICE REEVE

Wagner's enthusiasms could only be restrained with great difficulty), and a spate of compositions culminated in his first opera, "Die Hochzeit"—the Wedding—begun in 1832. It was the result of a thwarted passion for one Jenny Pachber, and the crude libretto told of a girl who pushed her unwanted lover out of her bedroom window to meet his death below. It symbolised a theme that was to haunt Wagner all his life, and which was to occasion some of his most marvellous music—the conflict of love and duty.

In 1833 he wrote his second opera, "Die Feen"—The Fairies. Excerpts were successfully performed, and his actress sister Rosalie managed to get the whole work produced at Leipzig. Though closely modelled on various prototypes, Wagner could at last claim to have learned to write music for the stage, and to win the esteem and forgiveness of his mother and Rosalie from the dissipations of his youth.

Followed a few years during which he travelled about, expressed various opinions on opera, violently changing sides as between Weber and Marschner on the one hand, and Rossini and the Italians on the other; having various amorous adventures, hearing the famous Wilhelmine Schroder-Devrient in "Fidelio" and Italian operas and being greatly moved thereby, commencing his third opera on the Italian model, "Das Liebesverbot"—the Love Ban, the offer of the directorship of the Magdeburg Theatrical Company, and, finally, his marriage to Minna Planer.

"Don Giovanni"

His season at the theatre began with "Don Giovanni," but his extravagance and love of the good things of life soon landed him in trouble as they were to do all his life. Schroder-Devrient appeared as guest artist at two performances, but the public, not thinking that the young Herr Direktor could possibly be serious in making such an announcement, failed to respond. The hall was half empty and Wagner saddled with a considerable debt.

He married Minna in 1836. She, too, had had her adventures, but, unlike Wagner, she was totally without culture or interest in it, and her outlook on life was the most materialistic imaginable. No more ill-assorted match was ever made. Imagine her rage when, on the first morning of her marriage, she discovered her husband's creditors' notes nailed to the door! The theatre had gone bankrupt, and he only married her largely out of jealousy over her outrageous conduct with various members of the company. Possession was evidently ten parts of the law.

It was a wretched failure, and at the second attempt Minna succeeded in running away with one Dietrich. Wagner took refuge in Dresden with his sister Ottalie and her husband. Here he read Bulwer Lytton's "Rienzi," and deemed it an ideal subject for a libretto.

At Riga

Taking up a post in Riga, Wagner was for a time at peace with himself financially. Shortly after, Minna rejoined him. Deserted by Dietrich, she asked his forgiveness, which he readily gave, promising not to mention the man's name. There was apparently a strong attraction between them in spite of incompatibilities of temperament, and they settled down to a much more stable existence.

Debts began to pile up again when he was suddenly dismissed—the result of an intrigue. This didn't worry him unduly, however, as he was pinning all his faith on "Rienzi," with which he was going to conquer the world, via Paris. And to Paris he went, determined not to waste time whilst the thing was being published and getting known, but to conquer even as Rienzi himself conquered.

They left Russia in June, 1839. Few more adventurous journeys can ever have been undertaken. Their passport had been impounded and they had to smuggle themselves over the frontier, past sentries a thousand yards apart. They sheltered in the hut of a bribed sentry out on duty, and finally boarded a tiny merchant ship bound for England. Instead of a four-day journey they took four weeks and, amongst other things, got driven up a Norwegian fjord in a storm. After striking a sandbank and other minor reefs and shoals, they finally sailed up the Thames. They spent a week at the King's Arms in Old Compton Street.

Wagner's wiles and ingenuity in earning some money for himself and Minna whilst waiting for the production of "Rienzi," whilst contracting new debts and holding the creditors at bay, bordered on the fabulous. They cannot be detailed here. A performance of Beethoven's Ninth re-awakened his love for that great master. He also wrote "Eine Faust" Overture. But "Rienzi" brought him bitter disappointment; they would not produce it.

"The Flying Dutchman"

Some readers may have guessed that it was the tempestuous journey to England which gave birth to the plot of "The Flying Dutchman." The score was finished in December, 1840. He offered it to Dresden—not Paris—as a one-act opera, for which he received 500 francs. With this he worked on the full-length score we now know. Dresden produced it. Ferlin staged "Rienzi." Triumph at last!

There was a wonderful part for Schroder-Devrient and for Tichatschek, the famous Dresden tenor. The "Dutchman" was the turning point in Wagner's artistic career as the production of "Rienzi" was materially. It marked the end of their stay in Paris, but not without one more disappointment. Schroder-Devrient, at the last moment, decided to do Gluck's "Armide" first, and the "Dutchman" had to be put back a season.

Modern Factory Production Methods—2

Notes on the Various Tests which a New Receiver Undergoes Before Being Issued to the Public. By "SERVICE"

MANY designers evolve their ideas and put these on to paper in the form of the completed chassis before they even start wiring up an experimental model. From their sketches proper drawings are made, and the major parts constructed in a small workshop. The men operating in these workshops are capable of putting their hand to any type of work and can bend a chassis, turn up an ebonite knob, wind a coil or do any other of the hundred and one jobs demanded by the designer's plans.

The receiver designer even lays out the wiring theoretically, but of course when the first model is made up he will find many problems of instability, hum, etc., to be attended to by rearranging wires here and there. This aspect of the job will be discussed more fully in a later article, as the process layout engineers will also have to modify the wiring and, perhaps, the component positions slightly to make the receiver suitable for mass production.

Components

In the meantime, however, the question of components must be considered. Just as a chain is only as strong as its weakest link, so is a radio receiver no better than its worst component. The most elaborate set will be a costly failure if a particular component consistently gives trouble. No matter how well the set performs between the breakdowns and irrespective of its fine appearance, reasonable price and other attractive sales features, the model and its manufacturers will suffer severely in reputation simply because one small part has been allowed to creep into the assembly without thorough tests or conscientious inspection.

It will be appreciated, therefore, that the component designers have a great responsibility to maintain, and they guard this by a constant vigil over the parts and the materials from which they are made. In addition, they must have available for immediate reference past histories of components similar to those they are at the moment considering. It is here that the service department can, and should, render invaluable assistance.

Designers seldom leave their laboratories, and are rather inclined to lose touch with the practical side of things. The service engineer, on the other hand, is for ever running into troubles and solving them in a practical way, and his experiences must be collected by a responsible person whose job it is to edit the serviceman's reports and bring the troubles that are due to design or manufacturing weaknesses to the notice of those concerned. This function will be fully dealt with under the heading of Service later on in this series.

Life Tests for Components

An, example, however, will demonstrate the necessity for a close liaison between the designs and service departments. A combined volume and tone control passed all life tests satisfactorily, but had a comparatively short life in the field, as many were returned for replacement. On investigation it was found that the tone control section was faulty, due to the fact that the carbon track was burnt out at one spot. This position was where the moving contact of the control remained when full

top cut was used. In other words, the receiver's high note response was such that most users found it too brilliant, and operated the set constantly with a "mellow" reproduction. All the unwanted power of the high notes passed through the one portion of the tone control track and burnt it out, and this fault decided the designers to modify the audio-frequency characteristics of the receiver which resulted in public approval and no more tone control complaints.


Reverting to the progress of the receiver design, the next step is to submit a list of the components to people who have specialised in small parts designs, and to obtain a report on each one that the designer proposes to use. The component designer can tell him whether the particular part the designer wishes to employ will

accelerating the wear and tear on the volume control by causing it to be rotated several times a minute for a predetermined number of operations.

For example, let us assume that the estimated life of a receiver is five years, and it is thought that the volume control will be used on the average four times a day, then a total of some 7,300 operations of the volume control must be allowed for if it is to have a five years' life. Therefore, the life test equipment will be designed to rotate the volume control backwards and forwards 7,300 times; so that if the control is rotated by the test mechanism 10 times per minute it will only require 730 minutes to carry out the test.

Tuning Drives

Other components which require manipu-

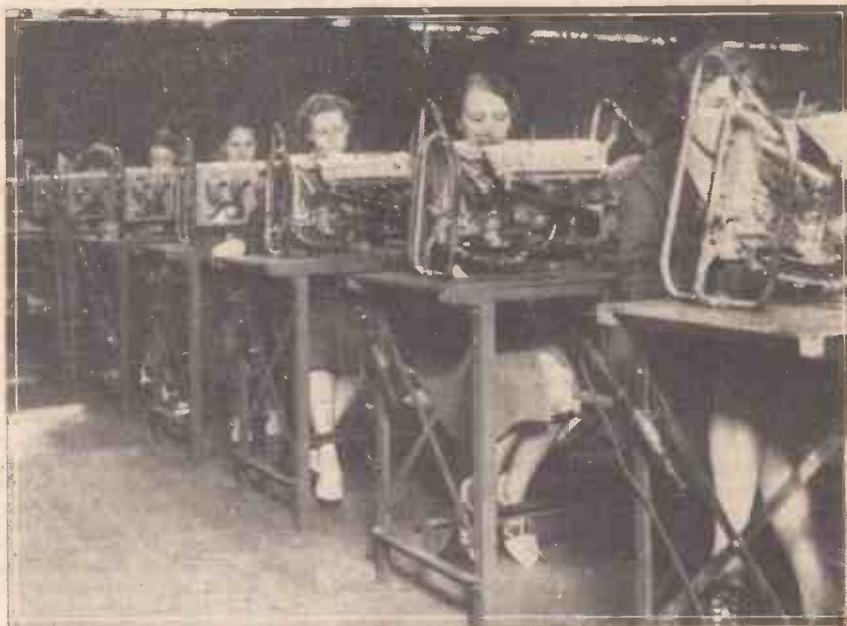

A view of the production desks in a modern radio factory, showing motor-controlled receivers nearly ready to leave their "cradles" for assembly in their cabinets.

stand up to the conditions under which they will work in the receiver.

Sometimes a new design of circuit or a new mechanical drive for the tuning condenser will have to be made up by the component designer because no standard part meets the receiver designer's needs. The new component must then be thoroughly tested after several have been made up for reasonable life, foolproof handling, ability to withstand transit conditions between factory and dealers.

To ensure reliability every component must pass a life test which subjects it to strains and stresses similar to those it will have to endure during the estimated life of the receiver. For example, volume controls must be capable of being rotated hundreds of times before they show signs of wear. A normal volume control may only be adjusted three or four times a day by the owner of the wireless receiver, and to test it under normal working conditions would take a very long time. The component designer must obtain his answer by

lation by the user of the receiver may be life tested in a similar way. It is very important in the case of tuning drives, which may incorporate cord, to see that in addition to there being no undue wear on the moving mechanical parts, that the cord or wire does not stretch, causing misplacement of the pointer in relation to the wavelength scale.

Items such as pilot lamps, valves and ballast lamps are run at a voltage higher than that normally applied to them, and from these tests their life under normal running conditions can be estimated.

If the instrument under consideration is a radio-gramophone other components will have to be reported on. The chief item will be turntable motors, and these will be life tested by running several motors in a temperature approximating that at which they will operate in the radio-gramophone cabinet. The motor is always in a warm position, as it not only develops heat itself, but will have to tolerate the heat from the

(Continued on next page.)

MODERN FACTORY PRODUCTION METHODS

(Continued from previous page.)

radio chassis (valves, transformers, etc.) which concentrates around the motor.

Considerations of Temperature

Another consideration which component designers must always keep in mind is heat. The temperature inside a receiver rises from the moment of switching on until it reaches its maximum, and it is at this temperature that all components must operate satisfactorily.

In the case of tuning drives incorporating cord, or thin wire, the latter must be so constituted that either it does not expand or increase in length with the rise in temperature, or that the effect is counteracted by features in the design of the drive.

Components such as chokes, transformers, loudspeaker field coils, etc., must be tested not only for length of life, and the effect of temperature rise, but also for the effect of atmospherical conditions. For this test the components under consideration are connected so that they are electrically operating under accelerated life test conditions with the additional factor that they are located in a humidity chamber. This is a large cupboard often with a glass front for observation which enables the designer to surround the

component being examined with any condition of air. Generally, of course, a wet- or moisture-laden atmosphere is employed which is the worst possible condition under which transformers and similar components can be operated. Upon this test will depend whether impregnation of the coil windings is sufficient to protect them from adverse atmospherical conditions.

The point which must be considered in all factory tests is that the test must not be stringent. This may sound rather contradictory, but what is meant is that designers must keep the price or cost of the components down to an economical figure. For example, if the windings of a transformer will have only 200 v. between them under working conditions it is a waste of money and material (which is often more important than money these days) to incorporate layers of insulating material between windings capable of constantly withstanding a much higher voltage. Component designers must see to it that quality and quantity is reduced to the very minimum, but he must then ensure that his test equipment is capable of rejecting every component that fails to pass the test applied to them.

Components Approval Meeting

A meeting of all designers will be held when the various component designers have

had an opportunity of reviewing the components required by the designer and have supplied him with samples in the case of new items. At this meeting there will be representatives of the factory, production staff and process layout engineers, the component designers and the service department. Then it is that the experience of the various experts will be aired concerning any possibility of faults that may develop in any of the components.

The service department plays a very valuable part at this stage. Their analysis of faults which they should have passed to all factory authorities during the life of earlier receivers should ensure that no unsuitable component or weakness in design is repeated in the new instrument. It sometimes happens, however, that due to staff changes among the designers a particular design engineer has not studied a certain problem with the regard to its past behaviour as shown by service figures, and has perpetuated a trouble which had previously been reported and corrected.

It is at these meetings, which frequently take place during the evolution of the new chassis, that these points are investigated and modifications put in hand where necessary. Further points which are brought up for discussion at the last of these preliminary meetings, together with the first stages of laying out the job for mass production, will be dealt with in the next article.

Increased Power for American S.W. Stations

It is reported that two more American short-wave stations have applied for permission from the U.S. Federal Authorities to have their power increased to 50 kW. They are the National Broadcasting Company's 25 kW. stations WRCA and WNBI at Bound Brook, New Jersey. Application has also been made to reconstruct the aerial of WRCA, which is beamed continuously on Latin America. The two stations are at present simultaneously operating a continuous sixteen-hour service. Station WNBI's transmission on 17.78 mc/s is beamed on Europe from 1 p.m.-6 p.m. G.M.T.

New Use for Loudspeakers

At a Fighter Command Station in Scotland, the public address loudspeaker system is being put to a novel purpose. Usually this system, with loudspeakers all over the camp and a microphone at some central vantage point, is used for transmitting orders—anything from sending a section of fighters into action to summoning an aircraftman to report to the medical officer.

At this Scottish station, however, it occurred to some smart brain that for much of its time the loudspeaker is unnecessarily idle. So why not, in the B.B.C. manner, bring entertainment and personalities to the microphone? Thus it is announced that at a certain hour, a brief talk will be given, and all who can are requested to be within earshot of one or other of the loudspeakers. A five-minute talk is then delivered by anyone who has something worth while to say.

Short concerts are also held—a selection of gramophone records for a quarter of an hour if somebody can produce some good new ones. Or, again in the B.B.C. style, a couple of experts provide a duologue discussion on some matter affecting the R.A.F.

When there is big news in the papers, or in the B.B.C. bulletins, this also is broad-

NEWS AND NOTES

cast. The latest score of German raiders is regularly announced—with unexpurgated comments.

B.I.R.E. Examinations

We are informed by the British Institution of Radio Engineers that sufficient applications have been received to justify the holding of examinations for associate membership, and the radio servicing certificates at London, Birmingham, Manchester, and Bristol, during the present month.

First F.M. Studio

The new station W2XOR, which commenced operating from Madison Avenue, New York, at the beginning of

August, is claimed to be the first studio built expressly for frequency-modulation transmissions. The studio, which was originally used by the 50-kW parent station WOR, has been equipped with Western Electric audio apparatus to give a flat frequency response from 30 to 15,000 cycles with a total harmonic distortion of less than 0.5 per cent. The 1-kW transmitter radiates on a frequency of 43.4 mc/s.

Licence Figures

The figures recently given by the Assistant P.M.G. show that there was an increase of 21,000 receiving licences during the period from September 1st, 1939, to May 31st, 1940, and it is interesting to compare this figure with that of 135,000 recorded during the eight months preceding the war. The approximate number of licences in force on May 31st was 9,065,000.




A corner of the B.B.C. Monitoring Room as a listening post.

Practical Hints

Two Useful Hints

NO doubt many readers, when in the middle of wiring or rewiring a set, have wished to insulate wires at one or more points when using the popular bare tinned-copper leads. The necessary length of systoflex is not at hand, but an excellent substitute can be used in the form of the rubber covering on rubber-covered flex. It has been my practice for a long time to save all the ends when baring this flex, and using them as sleeving. They are both neat and extremely safe, being a tight fit on 18-gauge tinned-copper wire, as shown

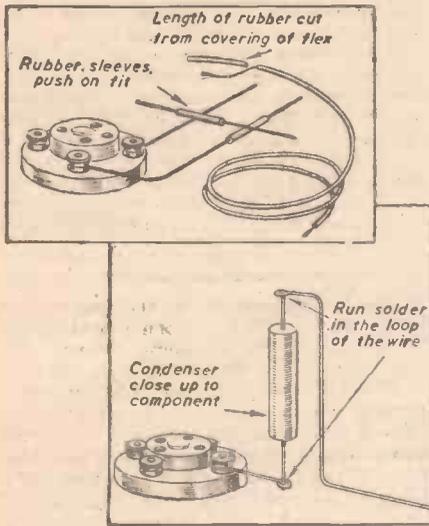


Improvised sleeving; and mounting condensers vertically.

in the illustration. A second useful tip, when space is a prime consideration, is to connect tubular condensers and resistances vertically. The illustration shows clearly how this is done.—W. H. MASON (Dukinfield, Cheshire).

Automatic Pick-up Switch

THE accompanying diagram shows a device which automatically switches in a pick-up as soon as the arm is lifted off its rest. The principle of working is as follows:

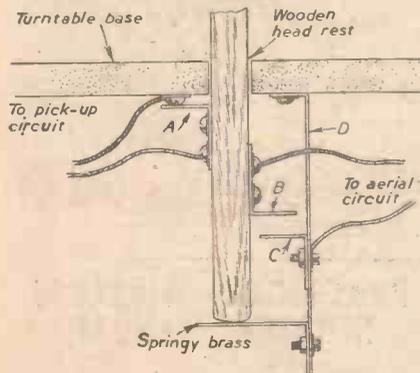When the arm is on the head rest, the weight of the arm will push the rest downwards as far as possible, i.e., until the bracket "B" is in contact with "C," and



A device for automatically switching in a pick-up as soon as the arm is lifted off the rest.

THAT DODGE OF YOURS!


Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay £1-10-0 for the best hint submitted, and for every other item published on this page we will pay half-a-guinea. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints." DO NOT enclose Queries with your hints.

SPECIAL NOTICE

All hints must be accompanied by the coupon cut from page iii of cover.

therefore the grid circuit is joined to that of the aerial circuit.

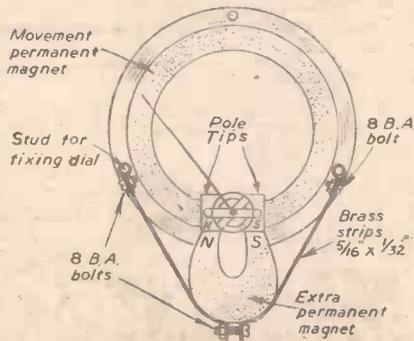On the other hand, if the arm is in use, the force of the springy brass strip will push the head rest up until the bracket "A" comes into contact with the bolt, screwed into the underneath part of the base, and then the pick-up is included in the grid circuit.—A. BURGESS (Trealaw).



Improving a moving-coil speaker.

Increasing the Sensitiveness of a Moving-coil Movement


TO complete a new piece of apparatus I required a moving-coil instrument having a low milliampere deflection (in the order of 0.6). I purchased a second-hand moving-coil movement through an advt. in your paper, but as the current taken for full scale deflection was about 0.14 milliamperes, this was too high for the apparatus under construction; the problem then was how to make the instrument read in the order of 0.6 milliamperes. One way of doing this is to increase the flux density in the coil gap, i.e., to increase the magnetic field strength. I therefore fixed a small but powerful horse-shoe magnet (made of the latest magnet alloy steel) to the magnet

system of the moving-coil instrument. I was then able to decrease the current for full scale deflection to 0.6 milliamperes.

The magnet, which I purchased locally for one shilling, was fixed as shown in the sketch. It will be noticed that the increase in the size of the instrument is small. The instrument was then fixed in a case, and finally connected to the apparatus.—H. WRIGHT (Rawmarsh).

Automatic Switch for an Electric Soldering Iron

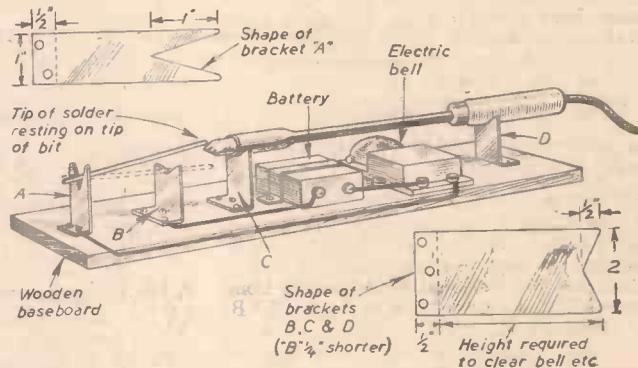AS I often switch on my electric soldering iron and then forget all about it, I hit on the following idea, which, incidentally, saves testing the iron every now and then to see if it is hot enough. A small stick of solder rests on the tip of the iron so that, when the iron is hot enough, the solder in



Details of the automatic switch for an electric soldering iron.

contact with it melts and allows the end of the stick to drop on to a bracket, B, and thus the circuit from A to B is completed by the stick of solder and the bell rings. Other details will be clear from the diagrams. I have purposely not given all the measurements as these vary for individual requirements.—J. F. H. ASPINWALL (Wirtall).

NEWNES' PRACTICAL JOURNALS

Practical Engineering

The weekly journal for those engaged in all branches of the Engineering and kindred industries.

4d. Every Thursday

Practical Mechanics

The only English Journal of its type. It deals with every branch of Science, Mechanics, Invention, Model-making, Chemistry, Astronomy, Photography.

8d. Every month

Testing L.F. Amplifiers

THE L.F. stages of a receiver are those in which most forms of distortion originate, and it is particularly important when designing apparatus solely for amplification (such as public address units) to see that the output is free from any form of distortion if the results are to be worth while. Unfortunately the ear is a very "elastic" unit, and it is safe to say that no two people hear alike. Furthermore, individual preferences differ, and thus what might sound high-pitched to one listener would be quite satisfactory to another. There are forms of distortion, however, which no listener can tolerate, and generally these give rise to reproduction which is commonly described as "scratchy," "woofy" or "harsh." These may all be


Forms of Distortion: Measuring Stage Gain and Other Important Amplifier Hints

By W. J. DELANEY

slight dips being obtained at different points and a falling off at the ends. The general effect should, however, be a more or less even response throughout, the better the amplifier the nearer the approach to a straight line. If there are any large variations from the straight, then the amplifier should be carefully examined for the cause. Generally it will be found that an increase above the normal is due to

condensers, as well as badly-made connections, will also give rise to this trouble, and therefore a test is desirable to ascertain exactly what noise level is introduced in the amplifier. For this purpose a non-inductive and reliable resistance must be joined across the input terminals, the value being equivalent to that which is normally used on the input side, i.e., microphone or pick-up resistance. The output meter should be of a type capable of measuring very low values, and should thus preferably be a valve-voltmeter. Obviously, as there is no input voltage, merely a load across the input, the output should also be a zero value, but, as already mentioned, slight valve noises are unavoidable, but the voltage indication on the output meter should be very low. It may then be expressed as a percentage of the rated output of the amplifier, or converted to a decibel value as already mentioned in previous articles in these pages.

Fig. 1.—Measuring amplifier gain, and set-up of equipment for taking response curve of amplifier.

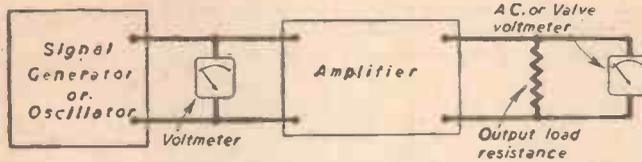

traced to definite faults and may be cured quite easily. Unfortunately, it is not possible to generalise and say, for instance, that harsh reproduction may be overcome by fitting a certain type of valve, or that scratchy results may be improved by the use of a certain type of component. There are, however, certain faults which may be introduced in a receiver, and which may be overcome by proper design or proper use, and it is these which the real experimenter is interested in, as he will be assumed to be using an amplifier which is properly designed.

Measuring Output

The most important point from a test angle, so far as the keen experimenter is concerned, is the question of performance. If an amplifier is giving its correct amplification, and is properly operated, it may generally be assumed that it is working correctly. Certain forms of distortion may, however, still be present. By feeding a given voltage into an amplifier, and measuring the output, the overall gain may be ascertained, and knowing the valves in use, and the approximate amplification which should be given, this will give a clue as to general performance. The same arrangement will also permit certain forms of distortion to be traced, and therefore an A.C. voltmeter and some form of signal generator are needed for such tests. The signal generator should be of a type which may be adjusted throughout the normal frequency range, and then, if a voltmeter is connected across its output and the signal level is then set so that the output of the amplifier is slightly below its maximum rated value, it will be possible to adjust the generator from one end of the frequency scale to the other, and plot the output at all frequencies, from which a curve may finally be drawn to show the frequency response of the amplifier. It is to be noted that for this test it is desirable to keep the output from the amplifier below its normal maximum in order to avoid distortion which might be introduced by overloading.

The final curve of a good amplifier should be somewhat as shown in Fig. 2. It will be impossible to obtain a perfectly straight line from one end to the other, various

some resonance in an anode circuit (wrong values of by-pass condenser or absence of condensers) and a dip in the grid circuit. These must not, however, be regarded as definite causes. There are so many incidental items which can introduce distortion of various forms that a carefully carried out

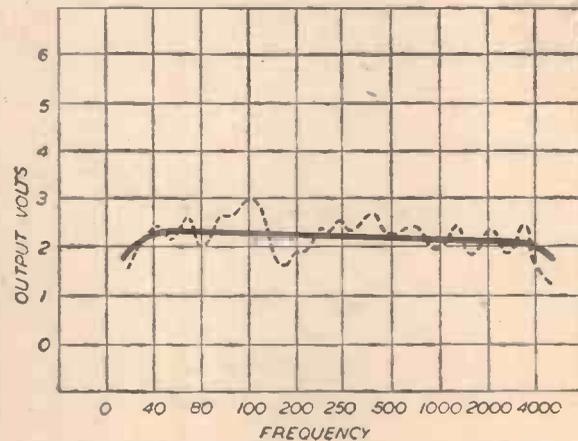


Fig. 2.—Response curve. The real curve will be as shown by the broken line, but this is generally levelled off and represented as shown by the heavy line.

stage-by-stage test is really the only satisfactory way of locating such troubles. When a stage is found in which the effect is introduced, modifications of all components should be made until the curve is straightened out.

Noise

Many modern amplifiers suffer from noise backgrounds, and it is essential to remember that all valves give rise to some noise, but with modern valves this should not be excessive. Faulty resistances and con-

push-pull amplifier is generally regarded as being most free from this trouble, and thus certain constructors adopt this form of amplification in order to ensure that they will have a minimum of distortion introduced in this way. Then, with proper attention to the above points, and with the amplifier set up by means of the instruments mentioned, the only remaining factor is the loudspeaker, and obviously if all previous tests indicate that the amplifier is working properly, and results are unsatisfactory, only the loudspeaker or the method of mounting or using it can be at fault. This should not be a difficult matter to overcome.

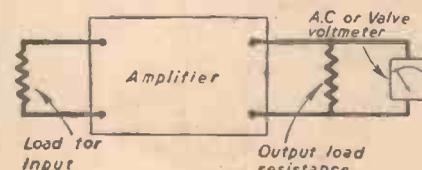


Fig. 3.—Set-up of equipment for measuring the noise level of an amplifier.

PRACTICAL WIRELESS SERVICE MANUAL

By F. J. CAMM.

From all Booksellers 6/- net, or by post 6/6 direct from the Publishers, George Newnes, Ltd. (Book Dept.), Tower House, Southampton St., Strand, London, W.C.2.

Meter Types and Tests

A Description of Modern Service Test Instruments and Their Application

THE average beginner often makes the mistake of assuming that ordinary radio receivers do not need test equipment, and accordingly obtains a simple type of meter with which he expects to carry out experiments at a later date. He finds, however, that many of his tests prove abortive, merely because the meter he is using is unsuitable. In most cases a simple dual-reading meter, that is, one which gives a reading up to 6 or 12 volts on one range and up to 120 volts on the other, is satisfactory for testing the condition of normal batteries. It may not always be suitable for testing mains units—this depending upon the resistance of the meter. It is also possible that such an instrument could be used to measure current by connecting it in series, but again the accuracy will depend upon the type of meter. There are to-day various meters of this type which are more elaborate than the old form of "watch" meter, and are designed to cover several ranges.



The Universal AvoMinor has 22 ranges and allows A.C. and D.C. to be measured.

Current Consumption

The full-scale deflection of a meter is the maximum reading, or the position taken up when the pointer travels to that part of the scale remote from its position at rest. For accurate tests of mains units, and certain other purposes, the current required for full-scale deflection should not be greater than 1 mA. This is equivalent to a resistance, when used for measuring voltage, of 1,000 ohms per volt, and will suffice for all normal requirements. For more elaborate tests, and for certain types of combined instruments, it may be desirable to have a maximum current of only .1 mA, and accordingly the reading will be more accurate. It will be appreciated that when measuring some circuits the current flowing may be only a fraction of a milliamp, and if the meter requires more than that, or put in another way, if the resistance of the meter is lower than that of the circuit being measured, a false reading will be obtained, due to the increased current flow. A good meter is, therefore, essential for all-round reliable tests, and it is possible to make up a combined test meter with only a single milliammeter of the lower-reading type as a basis. The fact that many firms now supply a ready-assembled test unit, consisting of such a meter, and the associated parts, has resulted in an increased use of test meters, and a consequent improvement in the performance of many receivers. Good instances of this type of combined meter are the Avometer and the


AvoMinor; two models of the latter are illustrated on this page. The AvoMinor is a Junior type of multi-meter, giving current, voltage, and resistance ranges. This particular instrument has a resistance of 330 ohms per volt, and the various ranges are selected by means of plug-in test leads. As an example of an instrument at the other end of the scale we may mention the Taylor meter, a 32-range universal instrument (that is, for measuring A.C. and D.C. supplies) and in which the various ranges are selected by means of a rotary switch.

A.C. or D.C.

The standard current meter is, of course, only suitable for measuring D.C. supplies, and when A.C. supplies have to be dealt with a small rectifier of the metal type is joined in series with it. These rectifiers are included in the universal type of instruments, the operation of the range-selecting switch generally bringing the rectifier automatically into circuit. For testing a normal receiver the meter is set to the D.C. range (if of the universal type), and where various current ranges are provided it is set to cover approximately the current taken by one of the valves, and the meter is then connected in series with the anode load component. It will then indicate the anode current of the valve, and from the valvemakers' curves it will be possible then to ascertain whether or not the valve is working properly. If the current is far from what it should be the H.T., L.T. and G.B. (if used in that stage) should be checked. If these are all in order then the valve will be known to be in need of replacement. If the meter is of the A.C. type it may be used to measure the output of a receiver or amplifier, and for this purpose some of the modern all-purpose instruments have the scale calibrated in watts, and also sometimes in decibels. The 46-range universal Avometer, for instance, provides on its scale decibel readings from -10db. to +15 db., with a reference level of 50 mW. The wattage scale ranges from 0 to 4 watts (the lowest indication being 1 milliwatt), taken with a load of 4,000 ohms. This instrument also provides direct-current readings in 10 ranges from 1 mA to 10 amps., D.C. voltage readings in 12 ranges from 50 mV to 1,000 volts, alternating current in 8



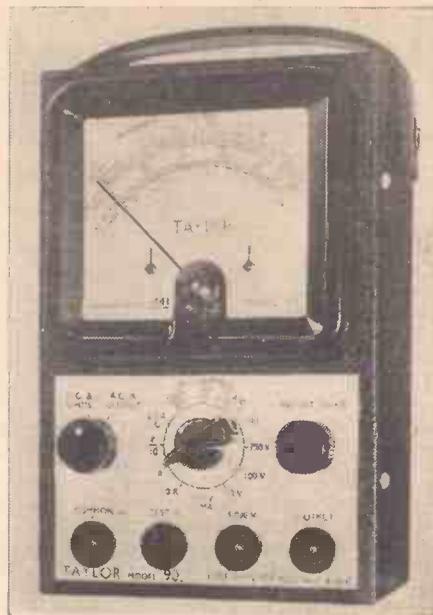The AvoMinor, a younger brother of the famous Avometer. It provides 13 ranges and embodies a 2½ inch moving coil combination.



Taylor model 90 32-range testmeter. A very fine instrument, ideal for service engineers.

ranges from 5 mA to 10 amps., and A.C. voltages in 8 ranges from 5 to 1,000 volts. These are the scale readings for the various ranges, all of which naturally commence at zero. That is to say, the first range in direct-current readings is from 0 to 1 mA and so on. There are two further ranges on this particular instrument. Resistance values are calculated, also from Ohm's Law, when it is known what current and voltage are in circuit, and accordingly it is possible to fit a battery inside the instrument, and then calibrate the scale to give direct resistance readings with the internal battery. In the Avometer just mentioned the resistance values are obtained with two internal batteries, one of 1.5 volts, and one of 9 volts. With these, direct readings are obtainable from 0 to 100,000 ohms. Then, by means of an external voltage supply, it is possible to obtain readings on three further ranges up to 40 megohms. The remaining scale calibration is for capacity-testing purposes, and gives a direct indication from 0 to 20 mfd. For this purpose an external A.C. supply between 65 and 250 volts at 50 cycles has to be connected in series with the condenser and meter, and then direct-capacity readings (within commercial limits) may be taken.

Useful Text Books

The full use of test instruments would take considerable space to detail, but there are many useful books available for the experimenter. In our own range there is the PRACTICAL WIRELESS Service Manual, which not only describes the use of test instruments, but also describes their construction. The makers of the Avo range of instruments also publish a book on Servicing—"Radio Servicing Simplified"—which deals with the matter, and makes specific reference to the Avo instruments. This particular book has now reached its seventh edition, a fact which speaks well for its contents and value to those interested in servicing and general application of associated meters. Many new pages have been added and, in its present form, it represents a work which should be in the possession of all of those connected, in a private or trade capacity, with the investigation and elimination of the varied forms of trouble encountered with radio equipment in general.

in position until the major portion of the wiring has been completed.

It will be found easier if the filaments are wired first, and then the connections from the coils to the wavechange switch. At this stage a word might be beneficial about the small rotary switch employed for wavechanging. In diagram form a switch of this type often appears to be very confusing or complicated to many constructors, but if it is examined it will be found that it is nothing more than a 4-point switch, each point or moving arm having three individual contacts with which it can make electrical connection. In the actual circuit only three points of the switch are used, and only two contacts of each section, therefore no difficulty should be experienced in following the wiring plan.

I.F. Transformers

The transformers used are fitted with four coloured leads each of sufficient length to make contact with their respective connections, thus eliminating the necessity of insulating sleeving. The colours are clearly indicated on the wiring plan, but it will, of course, be necessary to take the usual care to see that the leads are not confused or changed over as regards connections. A word of warning is necessary concerning the two trimming adjustments fitted to the top of each I.F. transformer. When testing a set of this type many constructors adopt the rather unsatisfactory method of varying these adjustments if results are not immediately obtained.

This procedure is not to be encouraged as the components are sent out by the manufacturer adjusted to their specified frequency, and if such adjustment is upset, it can be quite difficult to obtain an accurate



setting again without the use of an external oscillator. When the set is working, it is permissible to make very delicate adjustments to the I.F. transformers to get the maximum response, but it is an item which should be treated with great respect and reserve.

Resistances and Condensers

Whether it is due to the fact that these components are small and insignificant that so many constructors appear to treat them with scant consideration, or whether it is due to the idea that their location and

associated wiring is of no importance, we cannot say, but from actual experience we do know that many good sets can be ruined by slovenly placing and wiring of such parts. Therefore, with the set in question, we would advise all constructors to endeavour to locate each condenser and resistance in the positions shown on the plan, and adjust the wiring accordingly. Short wiring means rigid support for these parts, while on the other hand, instability and inconsistent results can often be traced to resistances and condensers which are free to vibrate, and almost sway in a receiver.

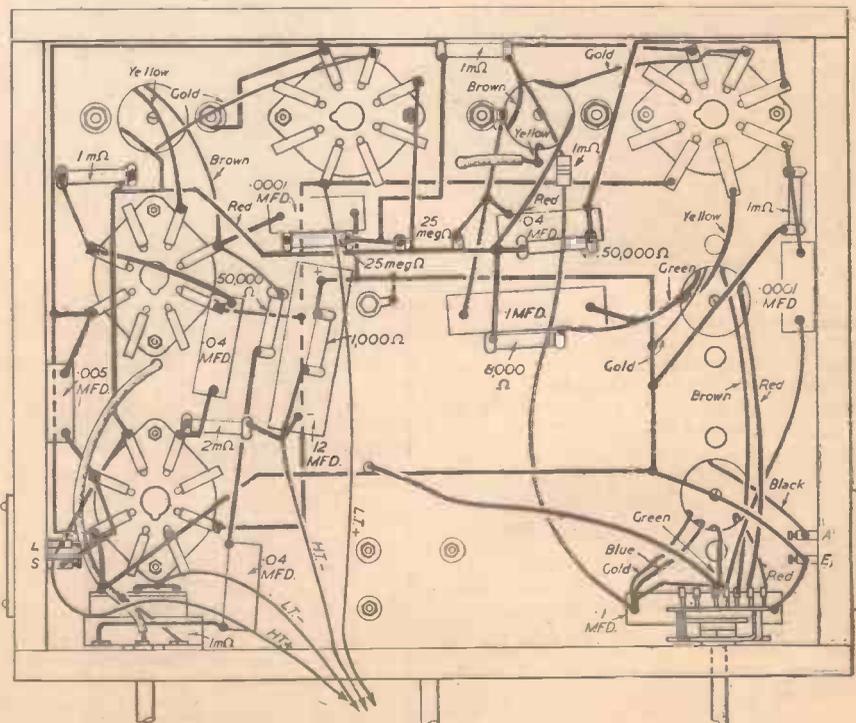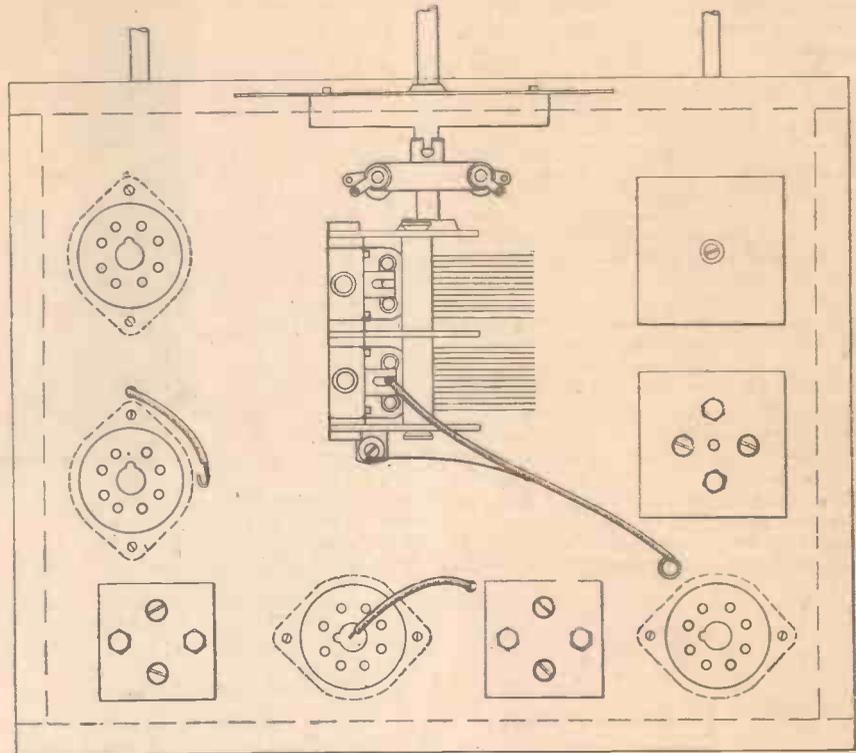WIRING DIAGRAM OF ALL-DRY 4-VALVE SUPERHET



Prize Problems

PROBLEM No. 413

LANE decided to build a four-valve superhet receiver of the battery-operated type. He made a fine job of the assembly work, and as the I.F. transformers he used were purchased secondhand, he lined them up to their correct frequency by means of an external oscillator, which also proved that the L.F. side of the circuit was O.K. On connecting the receiver for an aerial test, he was very disappointed to find that results were most unsatisfactory, that selectivity was non-existent and that all his labours appeared to have been wasted. On making further tests, currents and voltages were within reasonable limits, and all valves were beyond suspicion. Where had Lane slipped up? Three books will be awarded for the first three correct solutions opened. Entries must be addressed to The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. Envelopes must be marked Problem No. 413 in the top left-hand corner and must be posted to reach this office not later than the first post on Monday, October 14th, 1940.

Solution to Problem No. 412

Major made three main mistakes. He should not have arranged the switching to bring the P.U. directly in the anode circuit, as it would thus have to carry the anode current of the output valve, and, bearing in mind the P.U. winding, this procedure might cause a burn out or damage to the movement. He should have used a choke filter coupling or, better still (the second mistake) a proper matching transformer to allow the P.U. to match up with the specified load of the output valve. Thirdly, it was not wise to use a new steel needle.

The following three readers successfully solved Problem No. 411 and books have accordingly been forwarded to them:

- H. Tilbury, "High View," 26, Coningsby Road, High Wycombe.
- A. E. Yorston, 35, Cecil Road, Chadwell Heath, Romford, Essex.
- Hy. Hayes, 5, Springfield Avenue, Golbourne, Nr. Warrington.

ROUND THE WORLD OF WIRELESS

Bombing to Radio

THE crew of one of our bombers over Ludwigshaven dropped their bombs to the accompaniment of the National Anthem. The pilot said: "Just as we were making our run I switched on the radio set and evidently got the Empire programme. 'God Save the King' rang through the machine. It was about halfway through when we picked it up, and it ended exactly as we released our bombs. They made an excellent effect."

South African Broadcasting

ONE of the outstanding features of the recently issued report of the South African Broadcasting Corporation is the successful inauguration of the diversity receiving station which is now being used continuously for the relay of outstanding transmissions from overseas. The cost of the equipment for this station is given in the report as £3,328. An increase in the Union of more than 36,000 licence holders during 1939 is reported.

U.S.A. and International Radio

BBROADCASTING authorities in the United States have decided to spend 2,000,000 dollars for new and more powerful equipment to increase their scope in international radio. The step will be taken because U.S.-originated programmes have proved so popular in South America. International short-wave programmes may be sponsored, but with limitations on commercial announcements. The types of programmes most popular in South America are news, educational talks, fashion notes and Hollywood gossip.

Broadcast Expansion in India

OWING to the increased demand for wireless in that country, the Government of India intend to take early steps to institute the manufacture of cheap radio sets. With this object in view the question of the manufacture of sets has been referred to the Industrial Research Board.

It is felt that medium-wave sets could be produced in India. They would considerably meet the ever-growing demand.

Indian Listeners

AN important milestone in the history of Indian broadcasting has been reached. The number of licensed listeners recently passed the six-figure mark, the actual total being 1,000,388. The 26,690 licences issued during the preceding year is a record.

Radio's Part in War

THE radio industry in Australia are very concerned with the use of radio in all the Australian forces and the need for their being equipped with the most modern radio apparatus—and plenty of it, says the *Radio and Electrical Retailer (Australia)*. Not just a sufficiency, but an over-abundance is required, because it is just as vital in war as petrol, 'planes, tanks and munitions.

Without adequate communication, no army or air force or navy can function successfully.

Don't Dump Used Batteries

THE problem of disposing of all H.T. and G.B. batteries is now solved. No longer is it necessary to litter up the shelves and odd corners of the den with dead cells; the Salvage Dept. of the Ministry of Supply want them, and want them urgently. This also applies to old torch and pocket lamp batteries, so it is now up to every reader of PRACTICAL WIRELESS to get busy, and turn out all the old and useless batteries which, for some unknown reason, we all seem to store rather than dump.

A moment's thought will reveal that these batteries contain very useful products; in point of fact, weight for weight 10 per cent. is zinc, 3½ per cent. carbon rods, 10 per cent. pitch, 50 per cent. a mixture of graphite, manganese ore, beconite, etc., 10 per cent. cardboard, 3¼ per cent. pulverised carbon, and approximately 1 per cent. of brass and copper.

KDKA Pioneer Honoured

IT is reported that Dr. Frank Conrad, assistant chief engineer of the Westinghouse Electric and Manufacturing Co., of America, received the medal of merit of the American Institute of the City of New York, for his pioneering work in short-wave radio communication and for developing the first broadcasting system. Dr. Conrad was responsible for the inauguration of America's first broadcasting station, KDKA.

Nuisance Value!

WE understand that Lancashire County Council have adopted a new by-law imposing a penalty of £5 on persons creating a nuisance by wireless or gramophone in private houses. The areas covered include parts of the Fylde.

Ever-Ready Spitfire

IT is interesting to note that the directors and staff of the Ever-Ready Co. (Great Britain), Ltd., have subscribed to purchase a Spitfire, and a cheque has been forwarded to the proper authorities.

News But Not Music

AN Indian frontier mullah has given an interpretation of the Islamic law to the effect that a radio receiver can be used for the reception of news but not for music. It would appear that this ruling was brought about by a rival fakir who did not own a receiver, and who condemned the use of radio as being opposed to Islamic law.



Radio students receiving training on transmitting apparatus at the College of Wireless and Telegraphy, Manchester.

S.A. Radio Demands Up

THE desire to keep in touch with all the latest war developments and news has given a great boost to the sale of radio receivers in S. Africa. It is estimated that at least one-half of the white population now listens-in and it is fairly certain that this figure will continue to show a steady rise.

Remote Control

THE Westinghouse Electric and Firestone Tyres of U.S.A. have developed a system whereby landing lights for seaplane bases can be switched on by radio from a control point approximately six miles away. The lights, fitted to rubber buoys, are provided with a small battery-operated receiver and a "whip" aerial.

LATE DELIVERY OF "PRACTICAL WIRELESS"

A Message from the Editor

We are doing all we possibly can to ensure that "Practical Wireless" reaches you regularly every month, but occasionally there may be a delay owing to the dislocation of transport caused by air raids.

If, therefore, "Practical Wireless" should arrive after the normal day of sale, please help your newsagent by accepting your copy as usual. Under the Government's Paper Control Order he is unable to return unsold copies, and if you refuse to accept he will have to pay for it himself.

Your newsagent is working under difficult conditions these days, and your kind co-operation in this matter will be greatly appreciated by him—and by ourselves.

Cutting Out Resonance

How Loudspeaker Cabinets can be Improved in Order to Obtain More Faithful Reproduction of the Low Notes

IN an endeavour to obtain good reproduction of the lower notes, many listeners have either purchased a loudspeaker which has a bass resonance, or have fitted a good loudspeaker into a cabinet which resonates to some low frequency, and thus gives that boomy effect which is so distasteful to a music lover. What is resonance? In the case of a

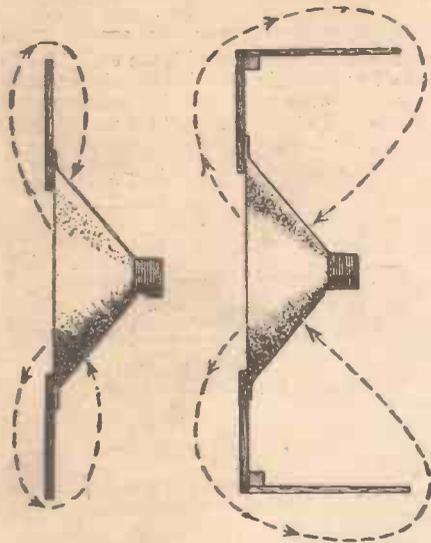


Fig. 1.—Showing the path taken by the surrounding air when movement of the cone takes place.

badly-designed loudspeaker it is a tendency to over-accentuate certain low notes. This may arise from a cone which is too loosely suspended; from a cone which is made from unsuitable material; or from a speaker in which the design of the transformer and speech coil has been so arranged that emphasis is given to a particular frequency. In certain speakers, designed about two years ago, this artifice was often incorporated in order to give the impression that the speaker was good in the bass. When heard standing on a counter, or without a good baffle, it certainly gave that impression, but when mounted in a cabinet, the undue prominence immediately spoils not only musical items but also speech. The wrong design of the amplifier can also give rise to resonance, and especially in the choice of the coupling condenser in a parallel-fed L. F. transformer circuit is the resonance effect noticed. A good moving-coil speaker should have a straight-line response, that is, it should not reproduce any frequency at a different strength from any other. A good speaker fulfils this condition, but in order to hear the low notes in the musical scale it is necessary to exercise certain precautions.

How the Low Note is Produced

When the signals are fed to the speaker, they cause the cone to move backwards and forwards, and this produces movements of the air and so

gives rise to the sounds which we hear. The movement at the extremely low pedal notes of an organ, for instance, is so steady that it may actually be seen if the cone is closely examined. Owing to this slow movement, if we stand an M.C. speaker on the table we should find that the note would be practically lost, owing to the fact that the displacement of the air in one direction is cancelled out by the movement of the air from the opposite side of the cone. This is illustrated in Fig. 1, where the cone has moved forward and should, by so doing, have compressed the air and so caused a forward motion to the air in the direction indicated by the arrows. This movement causes a rarefaction of the air at the rear of the cone, and, therefore, it is easier for the air to rush round to the "space" so formed than it is to compress itself in a forward motion. Consequently, the sound is almost cancelled out. To avoid this we use a baffle, or in other words we interpose something in a line with the edge of the cone to prevent this movement of the air from one side to the other. In order to obtain good response of the various notes it is necessary to make the path of the air from one side to the other a function of the actual wavelength of the sound, and then the cancelling-out will not take place. The actual length of the air path which we must provide for certain frequencies in the lower musical scale is shown by the following table.

Frequency.	Length of air path.
30 cycles per sec. ..	9ft.
45 " " " ..	6ft. 9in.
60 " " " ..	4ft. 6in.
75 " " " ..	3ft. 6ins.
100 " " " ..	2ft. 9ins.

These distances are from the front surface to the back surface of the cone, and, there-

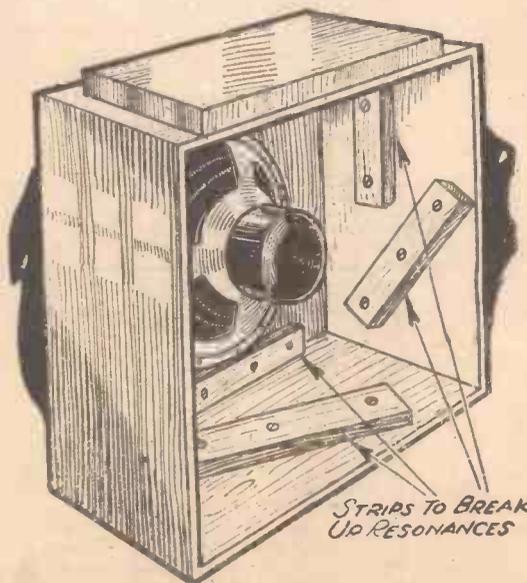


Fig. 2.—A simple method of overcoming box and cabinet resonances. The number and length of strips will depend on cabinet construction.

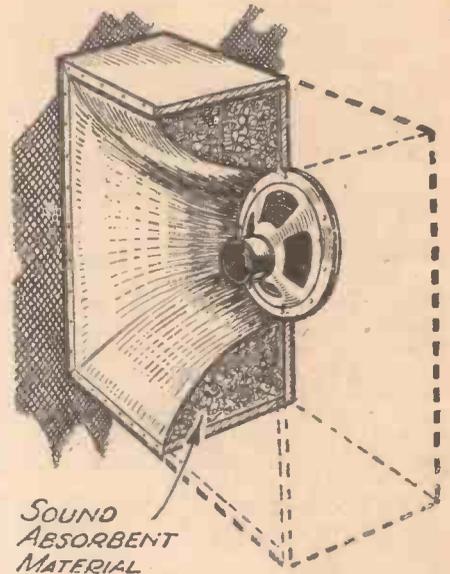


Fig. 3.—One of the best arrangements, provided care is taken with the actual packing and shaping of the absorbent material.

fore, the distance along the surface of the baffle is approximately half of the above distances.

The Ideal Baffle

The ideal baffle consists of a perfectly flat board, and this type may be seen at the Science Museum at South Kensington, where the ideal broadcast receiver is demonstrated. In the home, unfortunately, such a baffle would be out of place, and we are forced to cut it up and bend it to form a cabinet. The first thing to bear in mind, therefore, is the actual length. The above dimensions should not be reduced, but the sides of the cabinet must always be smaller than the front. That is the first point in avoiding resonances. Keep the sides as narrow as possible, and thus approach the flat baffle. If a small table cabinet is to be used, do not close the back. If dust must be excluded, use thin gauze or drill or cut some kind of very large holes in the back and cover these with gauze. It is also important that the cabinet should be stood well away from the walls, so that no box effect is created. The actual thickness of the material should be of sufficient thickness to prevent vibration at very low frequencies, but if thick wood cannot be worked, or an old cabinet is in use where this resonance occurs, strips of very thick wood may be screwed across the sides and front at odd points, and at varying angles, to break up the resonance (Fig. 2). Alternatively, the box may be lined with some sound-absorbent material packed in a canvas lining, or thick felt (carpet underlay) may be glued on the inner surfaces of the box (Fig. 3).

Gramophone Cabinets

All of the above schemes may be adopted in the case of radio-gramophone cabinets, although in this case we have a much larger area at our disposal, but this is often offset by the

(Continued on next page.)

CUTTING OUT RESONANCE

(Continued from previous page.)

fact that the apparatus is generally much more powerful. The usual method of dividing the cabinet into two parts, and packing the receiver equipment into one and the speaker in another is not ideal. One well-known commercial receiver manufacturer has already departed from this method of design and has considerably improved reproduction as a result. A scheme which I have incorporated in my own radio-gramophone for some time now has, however, been found ideal from the point of view of improving the lower ranges, and is shown in Fig. 4. The receiver is supported on a small shelf, only as wide as the receiver chassis, and this is screwed to the front of the cabinet. Thus it performs two functions, it breaks up the tendency of the front to resonate, and it avoids the division of the cabinet into two parts. The speaker is similarly disposed at the bottom of the

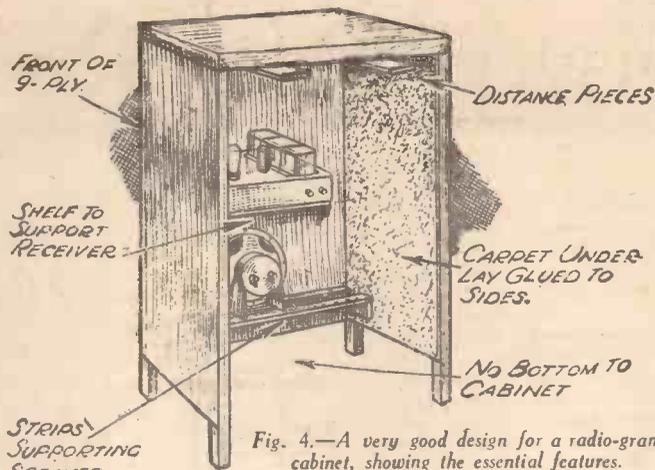


Fig. 4.—A very good design for a radio-gram cabinet, showing the essential features.

cabinet, but to take the weight, strips of quartering are fitted across the inside of the cabinet and it rests on these. Finally, there is no bottom to the cabinet, and it is fitted with distance pieces to prevent it from being pushed up close to the wall. A cabinet improved on these lines will be found to offer better reproduction than the average type of cabinet, and the schemes given above are well worth trying. W. J. D.

A NOVEL SENSITIVITY DEVICE

A System of Reaction Particularly Suited to "Stand-by" Receivers

WE are all familiar with the simple one-valve circuit shown in Fig. 1. It is not, however, suited to modern conditions, even as a "stand-by" set. Generally it is modified to appear as in Fig. 2. The purpose of the modification shown in the dotted area A is to allow reaction, and thus raise the sensitivity of

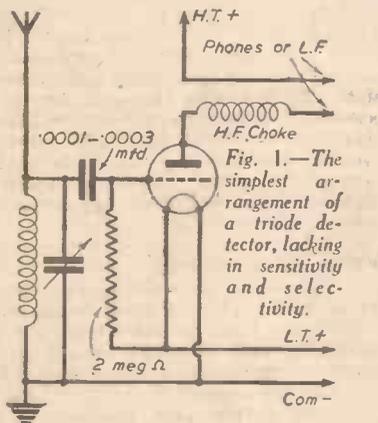


Fig. 1.—The simplest arrangement of a triode detector, lacking in sensitivity and selectivity.

the set. The condenser C is included to make reaction smoother, which is essential, and it may be either entirely separate, or one "side" of a differential condenser.

The modification shown in the dotted

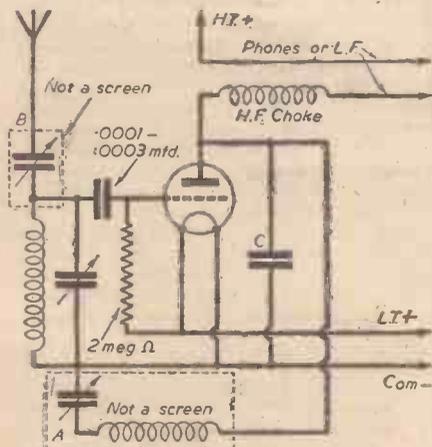


Fig. 2.—A more familiar and likewise more efficient one-valve circuit.

area B of Fig. 2 is an aerial series condenser. Its purpose is, briefly, to reduce aerial damping, and allow the valve to oscillate more readily.

Having briefly run over the simple sets likely to be used as "stand-by" sets, or in the case where a receiver is being installed for a new listener, when a very simple set is usually required, we will now go on to Fig. 3. As shown it is a modification of the original Reinartz. Now to consider its action.

Operation

When the moving vanes, Z, of C₁ mesh with the fixed vanes, Y, the same reaction effect is got as in Fig. 2, but as Z intermesh with Y they separate from the fixed vanes, X, thus reducing the aerial coupling capacity. When Z intermesh with X the reverse takes place.

It may seem that in practice this would give an almost constant level of volume, but it does not really. In any case the purpose of C₁ is not to control volume but to increase (or decrease) the "reaching out" power of the set. The bypass condenser, C₂, should preferably be of the pre-set type, as this allows the smoothness of reaction to be adjusted. A value of .0003 mfd. max. will generally be suitable. The value of C₁ will depend on the coil used, but should be slightly larger than

recommended for use with the coil. This is to allow a certain capacity to exist between Z and X even when reaction is being used to the full at the "high" (in wavelength) end of the band.

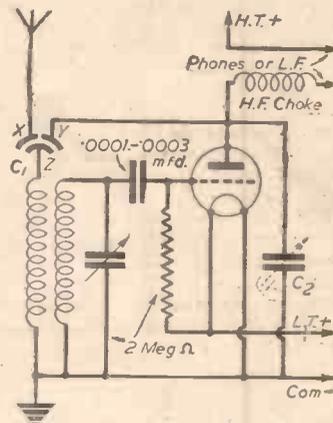


Fig. 3.—Showing the final development of the circuit to embody the features discussed by the writer.

The system has not been tried on short waves but, theoretically, there is no reason why it should not give the same good performance as it does on medium waves. The various "stand-by" sets described in this journal on September 23rd, 30th, October 7th, 14th, December 2nd, and 23rd, 1939, can easily be converted to this system, the only extra components, in most cases, being the pre-set condenser, which may occasionally be omitted.

LATEST PATENT NEWS

Group Abridgments can be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, either sheet by sheet as issued on payment of a subscription of 5s. per Group Volume or in bound volumes price 2s. each.

NEW PATENTS

These particulars of New Patents of interest to readers have been selected from the Official Journal of Patents and are published by permission of the Controller of H.M. Stationery Office. The Official Journal of Patents can be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1s. weekly (annual subscription £2 10s.)

Latest Patent Application.

13251.—Fletcher, H. L.—Wireless receiving apparatus. August 20th.

Specifications Published.

524752.—Naamlooze Vennootschap Philips' Gloeilampenfabrieken.—Tuning mechanisms of radio-receivers.

524776.—Kolster-Brandes, Ltd., and Smyth, C. N.—Television receivers of the superheterodyne type.

524733.—Naamlooze Vennootschap Philips' Gloeilampenfabrieken.—Radio-receivers.

525135.—Crowley, D. J.—Combined articles of furniture and radio-receiving set.

525084.—Nehrke, C.—Apparatus for tuning radio-receivers or like apparatus.

Printed copies of the full Published Specifications may be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, at the uniform price of 1s. each.

War-time Experiments

"The Experimenters" Make a Number of Suggestions for Interesting Experimental and Constructional Work Suitable for Present Conditions

THE whole field of radio experimental work has undergone a change during the past year, and many have even come to the conclusion that there is nothing further that can be done until the war is over. Of course, that is a mistake, although it must be admitted that amateur short-wave work is dormant. There is also the difficulty of obtaining components in some cases, and so the best use must be made of the parts which are already on hand.

Medium and Short Waves Only

One direction in which experiments may be aimed is in designing a simple type of receiver, compact in form, which will give reliable reception of the B.B.C. programmes on medium and short waves. Long waves are not required at present, and this fact helps to simplify home-made coil design, and also tends towards increased efficiency. A very satisfactory tuner for the 19-50 and 200-600-metre bands (approximately) can be made as shown in Fig. 1. Use is made of a 2in. diameter paxolin or shellacked cardboard tube, the upper end of which carries the tuning and reaction windings for short waves, and the lower end the medium-wave windings. This coil is suitable for use with either a Det.-L.F. or an H.F.-Det. type of receiver and the connections are shown in Fig. 2.

It should be noted, in making the tuner, that all windings are in the same direction and that, for convenience in buying the wire, the same gauge is employed throughout. This is shown as 26-gauge enamelled, but

'Phone Reception

In many cases it will be considered preferable to use headphones only for reception, especially if the set is to be used in a shelter, where children may be asleep.

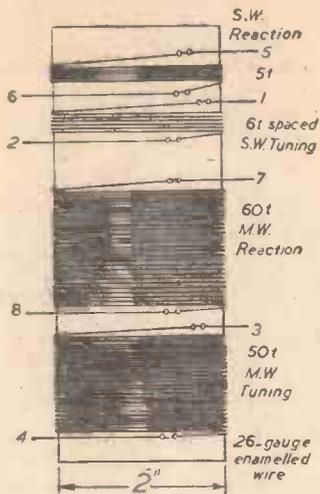


Fig. 1.—Details of a suitable short and medium-wave coil shown approximately to scale, assuming the use of 26-gauge enamelled wire. The length of the former should be about 5in., or 6in. if 24-gauge wire is used.

The two-valve H.F. circuit is then most suitable, because the detector will give an

As an alternative to the tuning condenser it will often be considered better to use three pre-set condensers for the three M.W. transmissions, and a .00016-mfd. variable condenser for tuning the short-wave coil. This method is especially convenient in the case of a Det.-L.F. receiver, since a three-point rotary switch is sufficient to select the required M.W. programme. When there is an H.F. stage, two such switches—ganged together—will be required.

"All-Dry" Valves

Many battery-set users will find it worth while to replace the 2-volt valves at present fitted by the newer valves of the "all-dry" type, which have a filament rated at 1.4 volts. Most of these valves are of the octal-base type, the connections for which are indicated in Fig. 3; it should be noted that the pin positions are those seen from the underside of the valve holders. It should also be remembered that different connections are used in some cases and that Mullard 1.4-volt valves have side-contact bases.

When using this type of valve it is possible to use a single battery of the combined H.T.-L.T. type, but where sufficient space is available it is our opinion that it is worth while to use a larger 1.5-volt cell of the kind generally described as bell cells. These are cylindrical and about 8in. high. By following this arrangement the possible difficulty in certain localities of obtaining a special H.T.-L.T. battery is avoided, and the single cell will have an extremely long life. The price is about two shillings, and therefore running costs are reduced to a minimum.

Valve Replacement

In general, two-volt valves can be replaced by their 1.4-volt counterparts as far as circuit considerations are concerned, the only important change required being in regard to the valve holders and the valve-holder connections. As triodes are not made in this range, however, an H.F. pentode should be fitted in place of the triode probably in use as a detector. By this means the general efficiency of the set will often be improved.

Reception in the Shelter

The question of obtaining radio reception in the air-raid shelter is receiving a good deal of attention nowadays, and the matter has previously been referred to in these pages. If the shelter is quite dry it may be satisfactory to instal a permanent receiver in it, especially if a car-radio is available—and also the battery power to

(Continued on next page)

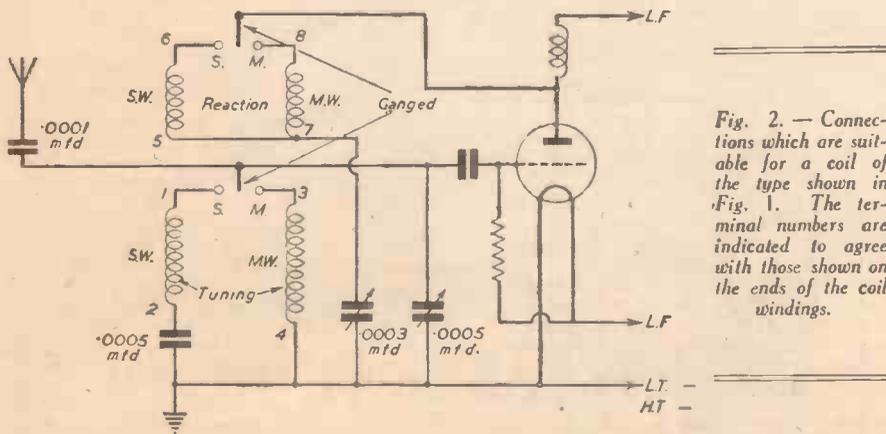



Fig. 2.—Connections which are suitable for a coil of the type shown in Fig. 1. The terminal numbers are indicated to agree with those shown on the ends of the coil windings.

24- or 28-gauge could be used if this were more convenient. It could be argued that wire as fine as this is not ideal for a S.W. coil, but in practice the loss of efficiency is negligible in the type of "emergency" receiver that we have in mind.

If an H.F.-Det. type of set were to be built a coil of the type shown could be used between the H.F. and Det. valves, whilst an even simpler arrangement could be used in the aerial circuit. Thus, the short-wave windings could be omitted and the M.W. reaction winding used for aerial coupling. On short waves, a good S.W. choke could be switched into the aerial circuit in place of the tuner. The chief advantage of this is that the only tuning condenser required would be a single one of .0005-mfd. capacity.

ample output for 'phone operation, and the H.F. stage will give the necessary amplification to ensure that any of the B.B.C. transmissions can be received in all conditions.

Fig. 3.—Valve-holder connections for 1.4-volt valves with International Octal base—Cossor, Osram, Tungram.

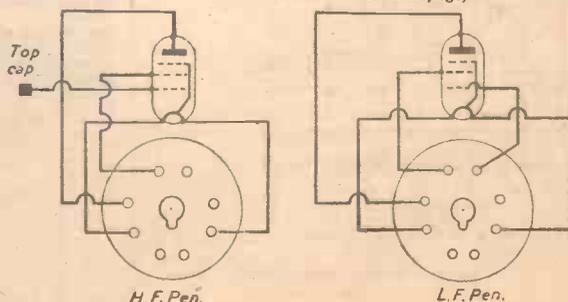

WAR-TIME EXPERIMENTING

(Continued from previous page)

operate it! The battery may be left in the car if the leads from it are not more than about 30ft., and consist of cab-tyre cable.

Limitation of space is an important factor, but a small set can often be fitted to a bracket attached to the wall in a corner. With a steel shelter this can be done by drilling and bolting metal angle brackets and screwing these to the set. Care should be taken, however, that pitch, tar or a bituminous preparation is spread liberally around the holes to ensure that water leakage cannot occur.

With brick-built shelters the mortar can be drilled and plugged. The same

method can be adopted with a concrete shelter, although in that case drilling will be more difficult, due to the hard nature of the concrete.

Mains Connections

Should it be decided to instal a mains operated receiver—and this is not recommended, and is strongly deprecated if there is any possibility of dampness—the mains lead used should be lead-sheathed cable, the sheath of which should be thoroughly earthed to a nearby water pipe or to an earth spike driven into the ground. A three-point connecting socket should also be used, the third socket being earthed to the metal sheathing. Additionally, a lead

should be taken to the earth terminal or chassis of the set from the third pin on the plug. It is strongly urged that a mains switch should not be fitted in the shelter; instead, the set should be controlled by its built-in switch, and by a mains switch fitted inside the house.

In many respects it is better to leave the receiver inside the house and to run extension 'phone leads to a 'phone jack or two-pin socket in the shelter. Additionally, a simple type of volume control, in the form of a 100,000-ohm variable resistor, may be connected across the two points of the socket. It is often convenient to place two or more 'phone sockets in parallel, a single volume control being used for all, or a separate one for each.

ITEMS OF INTEREST

Permanent Detector Efficiency

IN those permanent or semi-permanent detectors in which two dissimilar crystals are held together by a light spring, there is a particular disposition of the crystals which makes for increased efficiency. One of the crystals is attached to a plunger, which is pulled back when adjusting the detector, and then the two crystals are allowed to come into contact.

If the point of the crystal which is attached to the plunger is central, it is obvious that the arc in which it travels when the plunger is turned is very small; in fact, it may touch the other crystal always at about the same place, leaving the main portion of the crystal "unexplored." Whereas if it were at one side it would sweep all over the stationary crystal as it was turned round, owing to the increased arc of its travel.

The remedy is obvious if on inspection the highest point of the moving crystal proves to be nearly central. The crystal is usually held in its cup by a kind of solder. By melting this solder and rearranging the crystal so that a point projects at one side of the centre this state of affairs will be rectified. It is sometimes possible to split the crystal with a razor blade so that a sharp point is obtained.

War Talks

DO they think that the British are morons
When they vapour in front of the mike,
And put on that "Know-it-all" manner,
Which the rest of us greatly dislike?
Do they think that their hokey and slogans
Are the very best ways to win?
Will their ossified brains never tumble
That the British can "take it" and grin?
Will they never forget their Old School tie
And "We can't hit a plane when it's down"?
Will they still argue ethics of warfare
Whilst the Nazis are razing the town?
Do they hope to tame tigers with tea-cakes,
Or cobras by stroking their tail?
Don't they know that mad dogs are a danger
And "cure them by kindness" must fail?
The Nazis are sub-human perverts,
And to win we must treat them as such;
They started their Blitzkrieg of horrors,
To stop 'em—give them twice as much.
A dose of their own foul prescription
They would probably never survive,
Let's start and keep on with this dosing
Till there isn't a Nazi alive.
Soothing syrup's not wanted by Britons;
What they ask for is action, not dope.
We're in total war—make it total.
We want deeds and not talks or soft soap.
"TORCH."

PATENTS AND TRADE MARKS.

Any of our readers requiring information and advice respecting Patents, Trade Marks or Designs, should apply to Messrs. Rayner and Co., Patent Agents, of Bank Chambers, 29, Southampton Buildings, London, W.C.2, who will give free advice to readers mentioning this paper.

German Radio in the Field

ACCORDING to an American contemporary, information has leaked out that not the least part in the success of the German offensive, and the concurrent failure of Norway, Holland, Belgium and, finally, France, lies in the superb communications system which was able to establish and maintain communications with moving tanks and troops at as great distances as 250 miles from home stations. Nothing available in the U.S.A. can touch that at present. Development work along lines towards obtaining long-range mobile type of equipment will probably be done jointly by the Government and the great body of American amateurs.

Still Room in the R.A.F.

EVERY week that passes enables the Royal Air Force to absorb and employ more of the available talent and energy of the younger generation—both men and women.

Wireless mechanics are still wanted. Applicants should have a sound knowledge of the theory and practice of wireless sets and practical experience of the radio trade. Tradesmen rather than instrument makers are required. New opportunities for men anxious to undertake air crew duties have

resulted in a speeding up of enrolment. There is still room for pilots, wireless operator-air gunners and observers. Accepted candidates are now usually called up for training without undue delay.

Intelligent women between the ages of 18 and 43 will find an opening as radio operators in the W.A.A.F. Free training is provided for this interesting work.

Men applicants should apply to the nearest Combined Recruiting Centre and women to the nearest W.A.A.F. Area Headquarters or to Victory House, Kingsway, London.

Australian (Melbourne) Transmission

Call signs	Wavelengths
Before 5.15 p.m. VLR3	Before 5.15 p.m. 25.25 metres.
After 5.30 p.m. VLR	After 5.30 p.m. 31.32 metres.

Power: 2 kilowatts

Frequencies:

Before 5.15 p.m. 11,850 kilocycles.

After 5.30 p.m. 9,580 kilocycles.

Location: Lyndhurst, near Melbourne.

The times given are Australian Eastern Standard, which is 10 hours ahead of Greenwich Mean Time. All mail matter should be addressed to: Australian Broadcasting Commission, Short Wave Section, Box 1686, G.P.O., Melbourne, Australia. Cables and Telegrams, "Abcom," Melbourne.



New Zealanders in this country receiving wireless instruction under the direction of a Canadian Corps Instructor.

For the Beginner

Harmonics in Wireless

An Interesting and Vital Subject Approached from a Fresh Angle so that the Beginner can Secure a Thorough Understanding of Harmonics

WHEN we strike a note on the piano, the sound produced is not a single tone, but consists of a fundamental or primary tone and several secondary tones. The fundamental note is naturally the most predominant, while the secondary ones or harmonics are of less intensity. These harmonics, as their name suggests, are notes which harmonise with the fundamental. This is because the speed of frequency of the vibrations which constitute them is always an exact multiple of the frequency of the fundamental. Thus, the second harmonic is a note which vibrates at twice the speed of the fundamental; the third harmonic, one with a frequency three times that of the fundamental; while the fifth has a frequency five times as great, and so on. We do not ordinarily refer to the first harmonic, as that is the fundamental note itself.

Harmonics and Tone

It is largely the presence to a greater or less extent of various harmonics which gives individual character to the notes of a musical instrument and enables it to be distinguished from any other instrument. Thus it is possible to differentiate between a note on the piano and the same note produced on a harp. You will readily understand, therefore, that for perfect reproduction of speech or music by radio and gramophone it is essential to preserve the

part, but here we are not only referring to the harmonics of the sounds from the studio, but also to the harmonics of the radio and audio-frequency currents associated with the transmitting and receiving circuits. In order to get a clear conception of these it is, perhaps, just as well to examine the nature of the oscillatory motion of which alternating electric currents are constituted, and which is known as harmonic motion.

the same time to describe the same number of degrees, thus if P takes, say, 12 seconds to travel right round the circle, then it will take 1 second to travel each of the divisions round the circle. In the example given here, therefore, each interval marked along XY represents one second of time. At the points 1, 2, 3, 4, etc., along XY, we draw perpendicular lines each the same height above XY as the corresponding points 1, 2, 3, 4, etc., round the circumference of the circle as above DOB. We now join up the tops of these lines in the manner shown and thus produce an S-shaped curve which first rises and then dips below the centre line.

This curve is, of course, the well-known sine curve which represents, among other things, the oscillations to and fro of an alternating electric current. Similar curves must have been reproduced hundreds of times in these pages. Incidentally, the term sine is merely a trigonometrical expression indicating the relationship between MP and OP which is determined by the angle MOP.

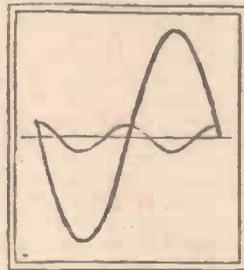


Fig. 3.—Sine curve representing simple harmonic motion together with another curve representing the second harmonic.

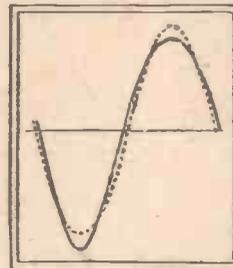


Fig. 4.—The result of combining the two curves, showing how the introduction of second harmonic alters the shape of the pure sine curve.

The Sine Curve

Look at Fig. 1. Imagine the line OP to be rotating at constant speed. From P a horizontal line is drawn to meet the diameter of

How Harmonics Alter the Curve

No doubt by this time you are beginning to wonder what all this has to do with harmonics. The answer is that harmonic motion in many different forms is represented by a sine curve such as this. Such motions include the vibrations of the strings of a musical instrument, the swinging of a pendulum, wireless wave motions in the ether, and high-frequency and low-frequency electric currents, etc. Now, whereas simple harmonic motion is represented by a pure sine curve, the presence of attendant harmonics modifies the shape of the curve in a very definite manner. For example, in Fig. 3 is shown the sine curve representing the fundamental of one of the above forms of motion which is accompanied by second harmonic of about 10 per cent. of the strength of the fundamental. The big S curve is the one corresponding to the fundamental, while the smaller one represents the second harmonic. As we should expect, the curve due to the harmonic has twice as many ups and downs



Fig. 1.—Diagram illustrating simple harmonic motion.

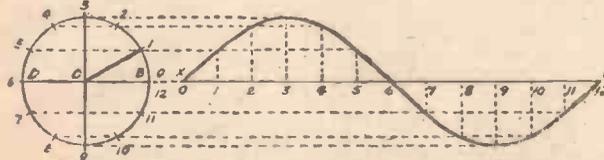


Fig. 2.—How to draw a curve representing harmonic motion. This is called a sine curve and is one of the two most important in wireless.

original notes complete with their attendant harmonics. It is the mutilation of the harmonics which so often mars reproduction and produces characterless sounds from the speaker.

To give a simple instance of how some of the harmonics may be lacking from a receiver which through ultra-selective circuits or some other cause, produces a cut-off of audio-frequencies above, say, 5,000 cycles. Assuming the set to be an excellent reproducer in every other respect, it might be thought that all notes below 5,000 cycles would be faithfully reproduced, and that it would only be the high notes above this frequency which would be distorted. This is not so, however, for many of the lower notes may be rich in harmonics, extending above 5,000 cycles. Thus, for example, a note such as C (1,024 cycles) may be attended by the third, fifth and seventh harmonics, which correspond respectively to 3,072, 5,120 and 7,168 cycles, in this case, owing to the set's lack of response above 5,000 cycles, the fifth and seventh harmonics would be lacking in reproduction with consequent loss of quality.

In wireless, harmonics play an important

the circle, AOC at M. As P rotates, M will move up and down AOC. Now, though the point P is moving at a uniform rate round the circle yet the movement of M is not uniform. It moves slowly as it approaches C and A, but quickly as it passes O. Its movement constitutes simple harmonic motion. If it is desired to show this motion diagrammatically, it can be done by plotting a graph. What we do is to first divide the circumference of the circle into, say, 12 equal parts, as in Fig. 2. The points 1, 2, 3, 4, etc. represent various positions of the point P in its rotation round the circumference of the circle. To the right of the circle we draw the graph. We draw a horizontal straight line, XY, to represent the circumference of the circle, and mark it off in divisions in the same way as the circle. These divisions each represent so many degrees, but they can also be used to represent equal intervals of time, since as P is moving at uniform speed round the circle, it always takes

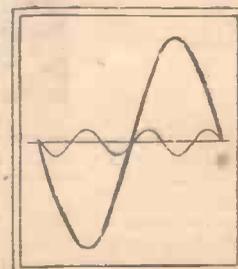


Fig. 5.—Sine curves representing the fundamental and a third harmonic.

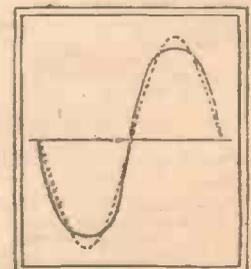


Fig. 6.—The effect of the third harmonic is to flatten the peaks of the fundamental curve.

persecond as the other, indicating, of course, that its frequency is twice that of the fundamental. The effect of combining these two curves, in the relative phases shown, is illustrated in Fig. 4.

The resultant curve is, therefore, a graphical representation of this particular motion comprising fundamental, and 10 per cent. of second harmonic. In order to show clearly how the curve differs from that of the fundamental alone, the latter has been superimposed on the diagram in dotted lines. Perhaps the most striking difference between the two curves is the fact that the compound curve is asymmetrical above the centre line. However, the significance of this will be more apparent when we come to deal with harmonic distortion in valves.

Another very interesting modification of the pure sine curve is that produced by the introduction of the third harmonic. This is shown in Figs. 5 and 6. In Fig. 5 is depicted the two component curves—that of the fundamental and that of the harmonic, while in Fig. 6 is shown the resultant. It will be noticed that in this case the introduction of the harmonic has not produced an asymmetrical curve, but that the curve is very similar to the primary curve, the most obvious difference being that the "humps" have been lowered.

At the beginning of this article it was stated that in order to obtain a faithful and lifelike reproduction of the music in the studio it is essential to preserve the accompanying harmonics as well as the fundamental notes. It was also shown how through the various processes of transmission and reception it was quite possible to lose some of the harmonics with a resultant decrease in quality. Now, these harmonics are, of course, sound harmonics, and are represented in the transmitting apparatus by electrical impulses alternating at sound or audio-frequencies as we call them. They must not be confused with the harmonics produced in radio-frequency circuits with which we shall deal next.

Wavemeter Harmonics

Everyone who has handled a heterodyne wavemeter will be familiar with the pro-

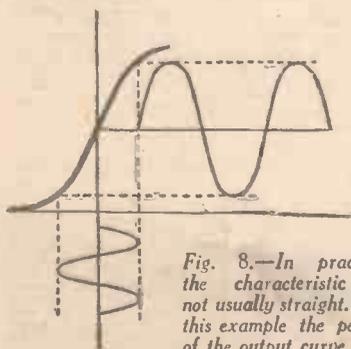


Fig. 8.—In practice the characteristic is not usually straight. In this example the peaks of the output curve are flattened. This means the production of a strong third harmonic.

duction of harmonics by a valve oscillator. A heterodyne wavemeter consists essentially of a valve complete with a grid coil and an anode coil somewhat similar to an ordinary one-valve set employing reaction. The reaction, however, is turned "full on," by closely coupling the two coils, and thus continuous oscillations are set up in the circuit. The grid circuit is, tuned with a condenser, calibrated in wavelengths or frequencies. To use the meter the condenser is set to the desired wavelength, and the valve switched on. The meter then works like a miniature transmitting station

which radiates continuous waves at the wavelength to which the condenser is set. If an uncalibrated receiver is placed near the meter and the tuning dial of the receiver slowly rotated, at the same time keeping the set in a state of oscillation by use of the reaction control, a whistle or chirp will be heard in the speaker when the receiver is tuned to the same wavelength as the meter. This is due to the oscillations produced by the meter clashing with or heterodyning those given out by the receiver. In this way the receiver can be calibrated, since the point on the dial at which the squeal occurs corresponds to the wavelength to which the meter is set.

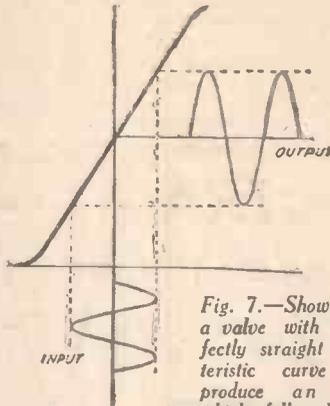


Fig. 7.—Showing how a valve with a perfectly straight characteristic curve would produce an output which followed faithfully the wave-form of the input and would, therefore, contain no harmonics.

This is all quite straightforward, but the trouble starts when it is found that the wavemeter not only radiates waves of the one frequency but also several harmonics. This is usually the case, and it will often be found that an instrument tuned to 1,000 kilocycles (300 metres) will also emit waves at 2,000, 3,000, and 4,000 cycles, and so on. That is to say, it will radiate waves which are the second, third, and fourth harmonics, etc., of the fundamental wave. The harmonics are nothing like so intense as the fundamental wave, but nevertheless confusion is likely to arise if the wavelength range of the receiver under calibration is entirely unknown. In this case it might happen that the fundamental wave emitted by the meter came right outside the wave-range of the receiver, so that one might quite easily mistake the loudest harmonic received for the fundamental, and to calibrate the receiver accordingly.

On the other hand, it may sometimes be very useful to have a wavemeter which emits harmonics, since the harmonics can be used to extend the range of the instrument. For instance, a meter which would not tune below 300 metres could be used for calibrations below this figure by utilising the harmonics. When set to 300 metres the second and third harmonics, if present, would occur at 150 metres and 100 metres respectively.

The production of harmonics by a valve wavemeter or transmitter occurs when the characteristic of the valve is non-linear. If you examine Fig. 7 you will see how a straight characteristic would produce an output which is a pure sine curve representing a simple oscillating current without harmonics. However, with a curved characteristic such as that of Fig. 8, in which the extreme limits of the grid swing run on to the upper and lower bends of the curve, the output is not a pure sine curve, but has the peaks flattened. This you will notice is similar to the curve shown in Fig. 6 and indicates that the valve would produce,

amongst others, a strong third harmonic. Incidentally, if a valve curve is symmetrical about the mid-point of the grid swing, the positive and negative half-waves of the output will be similar, and therefore, any harmonics produced will be only the odd ones—the third, fifth, or seventh, etc. This is what we should expect from what we have already learned regarding symmetrical and asymmetrical curves.

Now if the grid of the valve be biased, or the anode voltage altered, so that the operating potential of the grid comes nearer to, say, the upper bend of the curve than the lower, as in Fig. 9, then the positive and negative half-waves of the output will be unequal, indicating that even harmonics also will be present in the output.

Distortion in Terms of Harmonics

It is not uncommon when reading about the output stage of a receiver or the output valve in radio journals to find references to the presence of a "5 per cent. of second harmonic distortion," or to learn that "with a pentode valve third harmonic distortion is most in evidence." Such phrases can usually be relied upon to impress the layman, and assure the writer of the respect and admiration which such clear evidence of his technical brilliance merits. However, such high-sounding phrases are not really so formidable as they appear. The presence of distortion in an output valve is conveniently spoken of as harmonic distortion, because it is caused by the characteristic curve not being straight over its whole working length, therefore, the output is not a strict replica of the input. In the case of the input being a pure sine curve the output might be a flat-topped curve as in Fig. 6, or unsymmetrical as in Fig. 4. In other words, it might be said to show the presence of third or second harmonics respectively. Figs. 8 and 9, although primarily intended to show the production of high-frequency harmonics, are equally applicable in this case. Fig. 8 shows how, with a large swing in the input voltages applied to the grid the operation extends beyond the straight

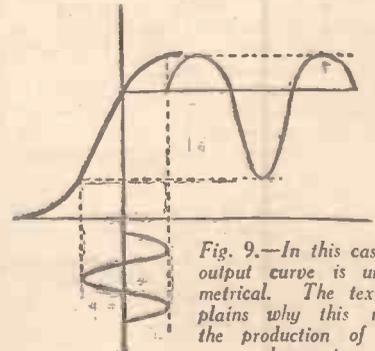


Fig. 9.—In this case the output curve is unsymmetrical. The text explains why this means the production of even harmonics.

part of the curve on to the upper and lower bends, and thus produces a flattening of the peaks of the output current, while Fig. 9 shows how the positive half of the grid swing makes a smaller variation in the output than does the negative half swing, thus giving an unsymmetrical output wave.

When reference is made to "5 per cent. of second harmonic distortion" in the output of a power valve it means that for an input consisting of a pure sine wave the output wave would be distorted similarly to that shown in Fig. 4, and that the amount of distortion would be such that

(Continued on next page)

HARMONICS IN WIRELESS

(Continued from previous page)

the difference between the heights of the two half-waves would be 5 per cent. of the total height of the wave. It is generally taken that 5 per cent. of second harmonic distortion is the maximum amount permissible when this valve is handling its full input. This percentage does not cause a noticeable deterioration in quality, and is the amount allowed when calculating the "undistorted output" of a valve.

A very useful guide to the amount of second harmonic distortion in a valve is the length of what is called the *load-line*. This is a straight line drawn across the usual anode current-anode volts diagram issued by the valve makers. In the middle or thereabouts of the load-line is the operating point, usually marked "O." A comparison of the distances of the two ends of this line from the operating point gives an indication of the distortion present. If they are equal, then there is no second harmonic, but if the difference in their length is, say, 5 per cent. of the total length of the line, then there is 5 per cent. of second harmonic at the maximum input. Third harmonic distortion results in a curtailing of both ends of the load-line, and is, therefore, not immediately apparent from an examination of the load-line.

It is perhaps hardly necessary to point out, in conclusion, that there must be no confounding the harmonics of the received signal, which form the "character" of the music and which it is desired to preserve, with the harmonics produced by receiving valves due to their non-linear characteristics. These latter, as we have just seen, distort the incoming signals by producing an output which is not a faithful reproduction of the wave-form of the input.

TELEVISION PROGRESS IN JAPAN

ONE is often inclined to overlook the fact that intensive television research work is now being carried out in various parts of the world, therefore, to many it may be a surprise to hear that Japan is paying particular attention to this latest radio development. Many institutes and laboratories, including the technical research laboratory of the Broadcasting Corporation of Japan; the Higher Technical School of Hamamatsu; the Tokyo Radio and Electrical Co., Ltd., and the Electric Laboratory of the Communications Ministry, etc., are all actively engaged in television development and investigation work. As a matter of fact, experimental television broadcasts were made quite recently for the benefit of the general public in Japan, and it would appear that the authorities concerned hope to be able to radiate regular sound and sight programmes in the near future.

One research laboratory, namely, The Technical Research Laboratory of the Broadcasting Corporation of Japan, which is primarily devoted to the study of the theory and application of radio-telephone, actually established an experimental television station in 1937 (J2PG), and in May of last year they succeeded in transmitting photographs of the Tokyo Broadcasting House, some 14 kilometres away from the transmitter. Since that event, intensive study and improvements have been sought, and several television transmissions have been made public to try to popularise the new form of entertainment.

RADIO CLUBS & SOCIETIES

Club Reports should not exceed 200 words in length and should be received First Post on the third Monday in each month for publication in the next issue.

ROMFORD AND DISTRICT AMATEUR RADIO SOCIETY


Headquarters: Red Triangle Club, North Street, Romford.

Assist. Sec.: H. G. Holt, 5, Butts Green Road, Hornchurch, Essex.

As from September 3rd, evening meetings are suspended for the time being. All members, old and new, are welcomed at 5, Butts Green Road, Hornchurch, Essex, where a room is at their disposal on Sunday mornings.

Also, members can have the use of workbench and tools for small jobs. The assist. secretary will answer any inquiries at the above address.

RADIO ENGINEER'S
POCKET BOOK

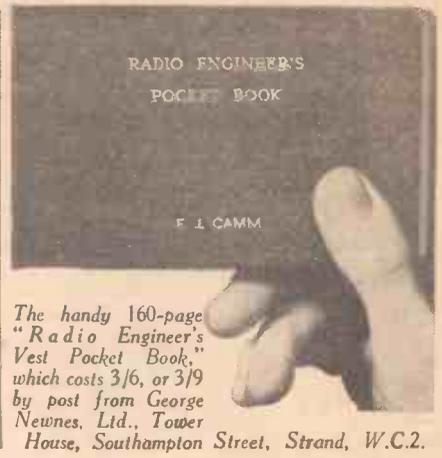

F. I. CAMM

The handy 160-page "Radio Engineer's Vest Pocket Book," which costs 3/6, or 3/9 by post from George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

ELECTRADIX — ELECTRADIX

Radio and Electrical Bargains

Bells. Desk type with movement in rong. 2/8. Wall bells, 3/-. Large size, 7/6. Large ironclad, single stroke, 15/-. Mains outdoor fire alarm bells, 10in. gong, 17/6. Bell Pushes, 6d. Heavy brass, 1/-. Bell Wire, 3/- 100 yds.

SWITCH DIALS. 10-point Finger Switch Dials, as used on G.P.O. Automatic Telephones. Price 2/6. TRUE-TWIN CAMERASCOPES, 2-lens view, 1/-.

RELAYS. For microamps, milliamps or amps. For remote controls, etc. Low, medium and high res. 5 m.a. Moving Iron, 8/6, 10/6 and 12/6. High-grade Moving Coil, 50 microamps, Weston, 60/-; in bronze watertight case, 70/-. New model W.L., 50 microamps. 1in. panel type, 55/-.

SINGLE BLADE RELAYS. No. 1 type 80D, 1,000 ohms "on-off" s.p. 6 volts, 8 m.a., 7/-. No. 2 type 832 s.p. 2,000 ohms "off" only, 10 volts 5 m.a., 8/-.

G.P.O. TYPE B TELEGRAPH RELAYS, with platinum points, 15/-. Silvertown Horizontal Galvos, two jewels, 5/-, post 6d. Vert. needle G.P.O. Galvos, 5/-.

REMOTE CONTROL "OFF" Relays or MAGNETIC SWITCHES, 4 amps., 7/6; 8 amps., 10/-; 10 amps., 12/-; 15 amps., 14/-; 20 amps., 16/-.

THERMOMETERS. Panel 2 1/2 in. dial, 5ft. ether tube for distant indicating, 0 to 100 deg. Cent., 7/6. Cambridge ditto, 10/6. FOURNIER THERMOMETERS by Cambridge Instrument Co., 4in. dial, 10-110 deg. Cent. Fitted adjustable electric contacts, 45/-, 12in. right angle immersion Thermom. to 150 Cent., 3/6.

A.C. MAINS LESDIX TUNGAR CHARGERS. Model No. 1 for 70 volts 6 amps. with meters and controls, etc., 100 cells a day, 27/17/6. No. 2 Tungar for two 5 amps. circuits with meters and variable volt controls, 70 volts, 10 amps., for 200 cells, bargain, 42/12/5.

METAL RECTIFIERS for charging on A.C. mains. The NITDAY will keep your battery fit. Model N/A2, charge 2 volts, 1 amp., 12/6. Model N/A6, Trickle, charge 6 volts, 1 amp., 17/6. Model N/B6/1, Car Charger, charge 6 volts, 1 amp., 24/-. Model N/B6/14, Car Charger, 8 volts, 1 amp., 27/6. Model N/C6/2, Car Charger, charge 6 volts, 2 amps., 37/-. Model N/D12/1 H.M. Car Charger, 12 volts, 1 amp., 38/-.

D.C. ROTARY CHARGERS. 3 h.p. 220 volt D.C. motor, 6 volt 250 amp. dynamo, 21/6. 200 volt motor, 25 volt 8 amp. dynamo, 24. Motor 220 volt, 8 volt, 50 amp. dynamo, 26/10, and others up to 6 kW.

A.C. ROTARY CHARGERS. 3-phase motor, 200 volt to D.C. dynamo, 8 volts 15 amps., 24/17/6. R.C.A. 3-phase motor, 220 volts, coupled to D.C. dynamo, 500 volts, 200 mA., 45/10. Single-phase to D.C. Higgs 230 volt A.C. motor, coupled to D.C. dynamo, 8 volts 16 amps., 25/10. B.T.H. ditto, 1 h.p. motor with starter on bed with 15 volt 30 amp. dynamo, 27/10.

300-CELL A.C. Crypto Motor-Gen. Set, for 220 volt A.C. mains, for Radio Cell Circuits and ten 12 volt, 10 amp. Car Batteries D.C. output, 100/360v., 20 amps. with Starter and Regulator, 232.

STORAGE. You may have charging facilities and want to install high capacity steel accumulators which will hold their charge almost indefinitely.

EDISON HIGH CAPACITY STEEL CELLS at half price for stand-by lightings, 120 A.H. to 300 A.H. at 25/- to 20/-. Makers' Price is 45. Ask for leaflet. FULL PARTICULARS gladly given as far as we are able to A.R.P. ENQUIRIES.

ACCUMULATORS, for stand-by H.T. at 6d. per volt, 3 amp. hours, in 24 volt unit crates, glass cells, 12/- each. Can be parallel charged off 12 volts.

NEW LESDIX 2-AMP SAFETY SWITCH FOR RADIO SETS, THERMO AUTO-TRIP FRONT KNOB CONTROL BACK OFF PANEL FIXING. WORTH A GUINEA, 5/6 ONLY.

Gear for Service Training, etc.

Lamp Signal training is very important. FIELD SIGNAL LAMPS, ALDIS HAND or TRIPOD, Trigger Type 23 10s.

OZONIZERS for sweet air. A.C. mains types. One tube unit 10/6 or in white enamelled wall case with flex and plug, 12/6. Two tube model 15/- or, supplied in Walnut cabinet for 20/-.

COMPASSES. W.D. Marching Compass, jewelled, course setter. Mahogany case 3in. x 3in. x 1in., 10/-.

CRYSTAL SETS. Need no battery, 7/6. Mariners 6in. Binnacle Boat Compass, portable, gimbal bases, etc., 45/-. Kelvin Ship Compass, pattern 14, liquid type, mahogany case, 10in. x 10 1/2 in. x 7 1/2 in., 60/- Plain 1in. pocket compass, 1/-.

TELESCOPES, Navy Gun, spotting, 25/-; Stick Periscopes, 3in. mirror, 6d.

TESTERS. Vest Pocket Tester "Dix-Mipanta" Bakelite case, 2 1/2 in. by 3in. Service on A.C. or D.C. battery or mains. Three ranges of volts: 0-7.5 volts; 0-150 volts; 0-300 volts. 19/6 only.

MORSE RECORDERS. Ex W.D. Standard G.P.O. Paper Tape Inkers record morse signals automatically. Work direct on line or through relay on radio mahogany base drawer contains reel. All are in good order, 27/0/0. Super Type, 28/0/0.

SOUNDERS. G.P.O. Standard Type Sounders, massive brass construction on mahogany base 15/-. Repeater Sounder with platinum output contacts, 25/-.

ARMY PORTABLE FIELD PHONES FOR LISTENING POSTS AND A.R.P. Wood or leather cased W.D. Type. Service Field Phones are useful at the present time. We have battery call fitted morse keys, mike and phone. Also magneto call speech only.

PHONE EXCHANGES. Plug type, 5 line and 20 line. Wire and cables cheap.

TAPPER KEYS for Morse Signal Transmission. Service Silent Practice Keys, 3/-. T.X. Practice Key, front contact, on black moulded base, a good small key, 3/6. Long bar Type Practice Key, T.X.2, with cranked bar, 5/6. Superior model B2, with back contact, a well finished key on polished wood base, 7/6. Operators' P.F. plated pivot bar and terminals, mahogany base, 9/6. Type IV, Superior ditto, nickel-plated pivot bar and fittings, on polished base, 10/6. Panel Keys to fold up flat, 6/6. Fullerphone double acting, Morse Key, solid brass on heavy base, 7/6. Three-colour light Switch Box with morse key for code signals, 4/6. S.G. Brown totally enclosed type, 42/-.

LEARNERS' MORSE PRACTICE SET. Special Duplex with Key Buzzer and Lamp for sound and visual 10/-. Heliographs and tripods.

BUZZERS, small type, with cover, 1/6. Power Buzzers, with screw contact and adjustable armature, 2/6. Heavy Buzzers, in Bakelite case, 3/6. Siemens Morse Line Transmitters, with key and brass-cased Power Buzzer, 17/6. Magneto Exploders, 25/-.

6/- EMERGENCY PARCELS of useful experimental electrical and radio repair material and apparatus, 10 lbs. for 6/- Post Paid.

Stamped envelope must be enclosed for Free Bargain List "N", or for replies to enquiries.

ELECTRADIX RADIOS

218, Upper Thames Street, London, E.C.4

Telephone: Central 4611.

Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

A Reader's Den and Equipment

SIR—As an old reader of PRACTICAL WIRELESS I am sorry that the paper is now published only once a month. I have always been interested in the illustrations of other readers' dens, and I regret I haven't a photograph of mine. I enclose a sketch, however, showing a corner of my den, and the equipment. Incidentally, the R.X. is a Trophy 6 with preselector, and a home-built P.P. amplifier to match. The last named draws its current from the preselector, which has a large mains transformer (identical to the one in the receiver), and feeds the P.A. quite well. However, I did fit a separate smoothing choke and condenser for the P.A. H.T. supply. The arrangement works very satisfactorily. It would be a good idea to publish a set on similar lines—preselector, R.X., P.A., and mains unit. It would make a fine super-set for keen radio amateurs.—HECTOR COLE (Workington).

Spares-box Superhet or Straight 4

SIR—A "Straight 4" in full howl is not a likeable proposition. When screened and doubly de-coupled it is quieter, but then is no better than a well-designed reacting detector "three."

Make it a "Spares-box Superhet," 465 kc/s, Osc. It will be interesting to see how you arrange for constructors to use their present gear with a minimum of purchasing to be done. In my opinion, when a fellow builds a first-class set fitted with costly ganged items, he finishes as a constructor.—W. H. LAZENBY (Penzance).

French Radio Periodicals Wanted


SIR—As a reader of your excellent paper for many years past, I am now writing to ask you a favour which I trust you will be able to accord me.

I am one of those unfortunate individuals who, after nearly 22 years' residence in France, was compelled to clear out in a great hurry, leaving my home wireless laboratory, and perhaps more important than this latter—a considerable library of radio papers, French, English and American. Wireless has only been a hobby of mine up till now (since 1924) but I have been successful in obtaining war work over here in the industry, and often wish I had some of my books to refer to. I have succeeded in obtaining some recent back numbers of PRACTICAL WIRELESS and certain other English periodicals second-hand, but have been unable to get any French or American books. It occurs to me that amongst your vast circle of readers there must be some who have in the past subscribed to these papers, and might be willing either to sell, or loan them to me. The papers I should particularly like to get hold of are:

- L'Amateur Radio
- Toute la Radio
- Radio Constructeur } French
- Radio Plans
- Radio News American

Needless to add, I should take great care of anything loaned me and should be truly grateful.

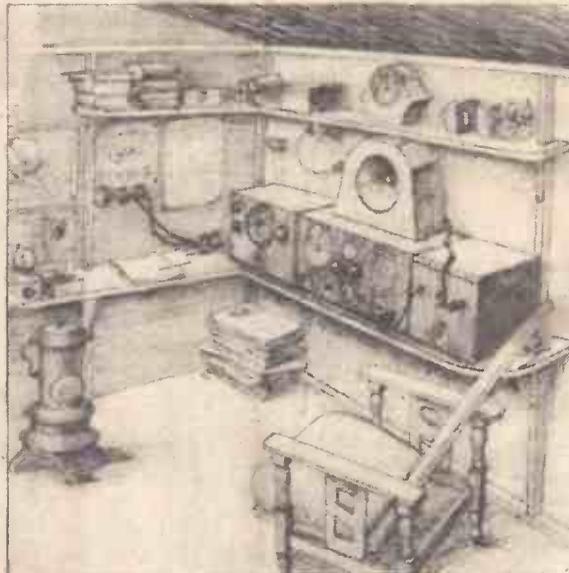In conclusion, may I add that as one who can claim some knowledge of France and her people the latter have not betrayed us, but were themselves betrayed by their leaders. I know this has been said and printed before, but thought perhaps my



A corner of Mr. Hector Cole's den at Workington, showing the neat lay-out of equipment.

brother radio-fans would like an unbiased opinion of one who has no axe to grind.—E. W. J. BRYDEN (8, Elgin Road, Seven Kings, Essex).

A "Super" One-valver

SIR—I have been a reader of your fine paper for over two years, and a short-wave listener for about the same period. I noticed in a recent issue an appeal for readers to send in diagrams and details of their "super" one-valvers for the benefit of fellow-readers. In my set the grid-leak (2 meg Ω) is taken to earth as is the L.T. +, not the L.T. —, as this gives greater sensitivity and signal strength. I also use throttle control reaction, which is much more efficient.

I use 4-pin coils (Premier) and a 160 mmf. (Trolitule) tuning condenser. The valves used have been a PM1HL Mullard (till it met with an accident), then a Tung-ram P215, and a Mazda P.220 at 60v. H.T. With this set I have received America and most of the Europeans, including Finland, Estonia, Hungary, and Turkey. I have also logged Portugal, Spain, Italy, Russia, South America, Manchukuo and Japan.

I find extension rods are necessary because of hand-capacity, and also high-ratio tuning and reaction controls.

I should like to correspond with any young reader interested in home-constructed short-wave receivers and DX listening.—P. DICKERSON (Church Farm, Fritton, Long Stratton, Norfolk).


"Spares-box" Superhet Circuits

SIR—I have often been interested in readers' suggestions for receiver designs, and as greater use of "spares-box" components is likely this winter, I think it would be appropriate if a few circuits were published which would appeal to many readers. Straight circuits are fairly easy to adapt, and modify, and I have successfully constructed many PRACTICAL WIRELESS circuits—including the Kestrel 4—almost entirely from adapted "broadcast" parts.

The superhet is a different proposition, and, taking into account the fact that few constructors would have special frequency-changing valves on hand, and that battery operation is preferable, I suggest the circuits could be on the following lines, the number of valves being limited to four if possible. The frequency changer could be: H.F. Pen. or S.G. in an electron-coupled autodyne arrangement; H.F. Pen. as combined det.-osc. with cathode feed-back for the osc. section; 7-pin H.F. Pen. as det.-osc., utilising the suppressor grid; or S.G. with separate triode osc., with, however, an increase of consumption.

Separate tuning of osc. sections would avoid ganging troubles. The I.F. stage could be H.F. Pen. or S.G., with I.F.T.s home-made or "spares," and anything between 50 kc/s and 465 kc/s—or even modified dual-range coils—with vari-mu volume control. The second detector could be a triode or S.G. with reaction for sensitivity control and C.W. reception, and the output stage a parallel-fed triode or pentode.

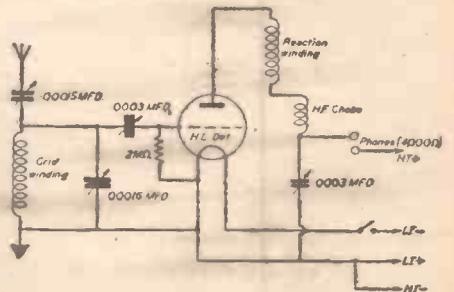The performance of such a receiver would fall short of present-day standards, but it would convert many "straight" enthusiasts.—CECIL MARTIN (Southampton).



Circuit diagram of a "super" one-valver, described by P. Dickerson, of Fritton.

[It is impossible to obtain thoroughly reliable reception from a set of the type mentioned by our correspondent without carrying out a good deal of experimental work.—ED.]

Correspondents Wanted

K. GREENWOOD, 5, South View, K. Cornholme, Todmorden, Lanes., would like to correspond with another young reader residing in Canada or the U.S.A.

G. Knox, 20, Seymour Road, Broad Green, Liverpool, 4, is at home on most evenings and would welcome any S.W.L.s who care to call.

PUSH-BUTTON TUNING MECHANISM

Details of a Suggested Motor-operated Device

WE are all familiar with the kind of motor-operated automatic tuning mechanism which has been a feature of radio receiver design during the last two years. The motor is adapted to be energised through one or other of a number of parallel paths, each of which includes a press-button-operated switch and contacts of a commutator type selector switch which is mechanically coupled to the motor, and to an adjustable component of the receiver, such as the tuning element or the wave-change switch. The arrangement is such that when a selected press button is operated the motor will move the adjustable component to a desired predetermined position.

In the kind of commutator switch commonly used the rotor comprises two commutator strips separated by insulating segments arranged at diametrically opposite points, and the stator contacts are usually radially spaced round half the circumference of the rotor.

It may sometimes be convenient to space the stator contacts round the whole circumference of the rotor, but a difficulty arises in that if two stator contacts are arranged at diametrically opposite points, it is then not possible to obtain the positions selected by those contacts in succession, since the circuits of both selector contacts are opened simultaneously by the commutator switch.

Stator Contacts

The stator contacts of a commutator switch for use with a wave-changing switch need not be adjustable and their positions are determined by the positions of the stator contacts of the wave-changing switch. Consequently, the difficulty referred to may be overcome by careful attention to design during manufacture.

One method of proceeding is to arrange the stator contacts of the wave-change, and commutator switches in pairs of diametrically opposed contacts which are equally spaced round the rotors, and to offset the insulating segments of the commutators.


An automatic wave-changing system of this kind is shown diagrammatically in the accompanying diagram in which 1 is a reversible electric motor. In the illustration 2 is the commutator of the commutator switch, a, b, c and d being the stator contacts, 3 is a bank of press button switches, and 4 a suitable source of electric supply. The pairs of diametrically opposed stator contacts aa, bb, cc, dd are equally spaced round the commutator, and the insulating segments "Z" of the commutator are offset from the diametrically opposite position by an angular distance θ equal to half the angular spacing α of the contacts.

The selector switch shown can select 8 different positions, and is direct-coupled to a wave-change switch (not shown). The wave-change switch must, of course, be provided with stator contacts separated by the angle α . It will be apparent with this arrangement that only one stator contact can bear against an insulating segment at any instant.

The same result may be achieved by arranging the insulating zones of the commutator at diametrically opposite points, and so arranging the stator contacts that no two contacts are diametrically opposed.

An automatic tuning mechanism of the

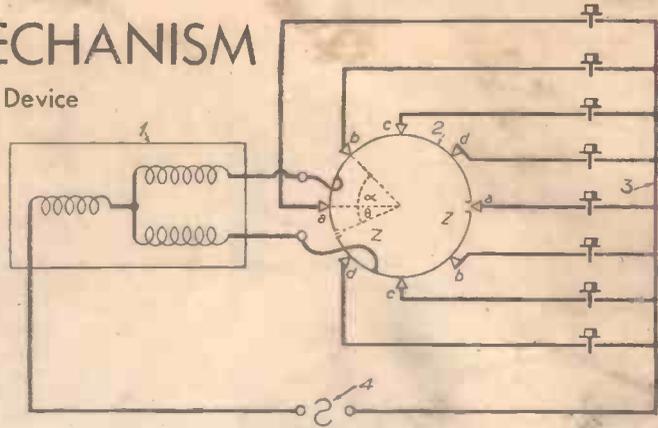kind described is particularly adapted for controlling so-called turret tuning systems in which the reactance elements of the receiver are mounted on, and radially spaced round, the periphery of a turret or drum which can be rotated to bring a desired set of reactance elements into the circuit of the receiver.



The general arrangement of an automatic wave-changing system employing commutator switching devices.

A XMAS BOX that brings in a GOOD INCOME is not a luxury, it is a SOUND INVESTMENT and results in

A PAYING CAREER

A Nett profit of hundreds of pounds per annum

I HAVE HELPED THOUSANDS OF OTHERS

... and when I say thousands, I do not exaggerate, as I can produce well over 10,000 unsolicited testimonials from grateful students who, through our Postal Training, have achieved their life's ambition.

During the last war many people learned how to write short stories, etc.; to-day a number of them are world-famed authors.

By becoming efficient in your vocation you can give the best service to your country and to yourself. The more you increase your earning power the better it is for the country and for yourself personally.

War or no war, earning power always brings its possessor to the front. It is no use waiting for better times. The ideal opportunity never arrives. We have to make the best of existing conditions.



LET ME BE YOUR FATHER XMAS

Therefore, delay is useless; it is worse, it is harmful.

If it is your desire to make progress and establish yourself in a good career, write to us for free particulars on any subject which interests you, or if your career is undecided, write and tell us of your likes and dislikes, and we will give you practical advice as to the possibilities of a vocation and how to succeed in it. You will be under no obligation whatever. It is our pleasure to help. We never take students for courses unless we feel satisfied they are suitable. Do not forget that success is not the prerogative of the brilliant. Our experience of over thirty years proves that the will to succeed achieves more than outstanding brilliancy.

DO ANY OF THESE SUBJECTS INTEREST YOU ?

- | | | |
|---|--|-----------------------------------|
| Accountancy Examinations | Engineering, All branches, subjects and examinations | Pumps and Pumping Machinery |
| Advertising and Sales Management | General Education | Radio Communications |
| Agriculture | G.P.O. Eng. Dept. | Radio Service Engineering |
| A.M.I. Fire Exams. | Heating and Ventilating | Road Making and Maintenance |
| Army Certificates | Industrial Chemistry | Salesmanship |
| Auctioneers and Estate Agents | Institute of Housing | Salesmanship, I.S.M.A. |
| Aviation Engineering | Insurance | Sanitation |
| Banking | Jouralism | School Attendance Officer |
| Blue Prints | Mathematics | Secretarial Exams. |
| Boilers | Naturalisation | Sheet Metal Work |
| Book-keeping, Accountancy and Modern Business Methods | Metalurgy | Shipbuilding |
| B.Sc. (Eng.) | Mining, all subjects | Shorthand (Pitman's) |
| Builders' Quantities | Mining, Electrical Engineering | Short Story Writing |
| Building, Architectural and Clerk of Works | Motor Engineering | Speaking in Public |
| Cambridge Senior School Certificate | Motor Trade | Structural Engineering |
| Civil Engineering | Municipal and County Engineers | Surveying |
| Civil Service | Naval Architecture | Teachers of Handicrafts |
| All Commercial Subjects | Novel Writing | Telephony and Telegraphy |
| Commercial Art | Pattern Making | Television |
| Concrete and Structural Engineering | Play Writing | Transport Inst. Exams. |
| Dranghsmanship. All branches | Police, Special Course | Viewers, Gaugers, Inspectors |
| | Preceptors, College of | Weights and Measures Inspector |
| | Press Tool Work | Welding |
| | Production Engineering | Wireless Telegraphy and Telephony |
| | | Wireless Managers |

If you do not see your requirements above, write to us on any subject. Full particulars free.

STUDY AT HOME IN YOUR SPARE TIME

JOURNALISM

Short Story, Novel and Play Writing

There is money and pleasure in Journalism and in Story Writing. No apprenticeship, no pupillage, no examinations, no outfit necessary. Writing for newspapers, novels or pictures, is not a gift; it is a science that can be acquired by diligent application and proper guidance. It is the most fascinating way of making pastime profitable. Trained ability only is required, we do the training by post. Let us tell you about it.

Department of Literature No. 104

IF YOU ATTEND TO THIS NOW IT MAY MAKE A WONDERFUL DIFFERENCE TO YOUR FUTURE

COUPON—CUT THIS OUT

TO DEPT. 104, THE BENNETT COLLEGE LTD., SHEFFIELD.


Please send me (free of charge) Particulars of (Cross out line which Your private advice about } does not apply.)

PLEASE WRITE IN BLOCK LETTERS

Name

Address

The "Fluxite Quins" at Work.

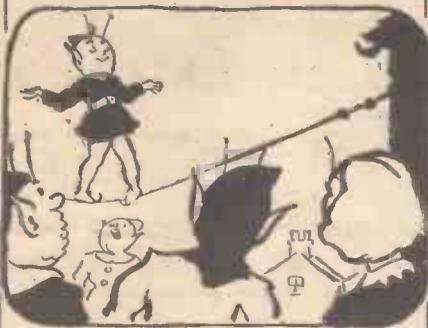

"What's this, a tight-rope display?"
 "No, a trick to impress us," grinned EH.
 "He knows that Fluxite
 Makes a job good and tight,
 It'll 'stay put' for many a day."

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for 30 years in government works and by leading engineers and manufacturers. Of Ironmongers—in tins, 4d., 8d., 1/4 and 2/8.

Ask to see the FLUXITE SMALL-SPACE SOLDERING SET—compact but substantial—complete with full instructions, 7/6.

TO CYCLISTS! Your wheels will NOT keep round and true, unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT

The FLUXITE GUN is always ready to put Fluxite on the soldering job instantly. A little pressure places the right quantity on the right spot and one charging lasts for ages. Price 1/6, or filled 2/6.

Write for Free Book on the art of "soft" soldering and ask for leaflet on CASE-HARDENING STEEL, and TEMPERING TOOLS with FLUXITE.

FLUXITE LTD. (Dept. W.P.),
 DRAGON WORKS, BERMONDSEY ST., S.E.1.

FLUXITE
 SIMPLIFIES ALL SOLDERING

Replies to Queries

Instability

"I recently made up a 5-valve superhet, and am troubled with some H.F. instability which I find it impossible to overcome. I have decoupled all anodes and screens on H.F. and I.F. stages, paid particular attention to screening and trimming and all the other dodges, but without avail. I wonder if you can suggest anything which I may not have done in this connection."—K. F. (Newcastle-on-Tyne).

THE trouble is one of fairly frequent occurrence, and if you examine modern commercial receivers you will see that various schemes have been introduced in an endeavour to overcome the trouble. It is important to remember that, generally speaking, any form of instability will result in a loss of efficiency and therefore to obtain maximum results the instability should be removed. Although this may be done by reducing working voltages and some other schemes, these only operate by reducing efficiency and, therefore, the instability should be removed by some alternative arrangement. Apart from correct trimming and screening, one of the important items which is often found responsible for instability is H.F. resistance in the tuning circuit, introduced by poor connection between the moving vanes of the condenser and the earth line. The condensers are generally provided with an earthing connection, but this is disregarded and the contact between the condenser body and chassis is relied upon. This may cause the trouble, and in your case we think you should try the effect of earthing the moving vanes direct. For this purpose use heavy-gauge flex, or alternatively the screening covering used for screened leads. Strip this off the internal insulated sleeving, press flat and solder thoroughly to the earthing contact on the condenser at one end, and at the other end to the earth line—not the chassis or a holding-down bolt.

Volume Control

"I am experiencing trouble with the volume control on my set, which is a commercial model about five years old. When in the maximum volume position everything is all right, but if the control is set back slightly to reduce volume I find at times there is a crackling noise as a background. This does not appear at all positions of the control, and I wonder if it indicates that I need a replacement. As the firm who made the set is out of business, I am uncertain about such a replacement."—D. R. (Hackney).

THERE are two possible causes for the trouble. In the first case the control may be worn out, dirty, or the moving arm may have weakened, resulting in poor contact at certain positions. In the second case, some other component, such as a valve or resistance, may have changed its characteristics, and at the point where you experience the noises there may be excess current flowing through the control, overloading the element and thus giving rise to the noise. This depends, of course, upon the position occupied by the control, i.e. H.F. gain control. If you can dismantle the control satisfactorily you could test for contact by connecting a good meter in series with a small voltage source and placing this across the control when

adjustment of the arm should give smooth indications on the meter. Any jumpiness will indicate poor contact, and the control should then be taken to pieces to see if this is due to dirt or grease on the arm, or a worn-out element. If the control is in order, then attend to the voltage or associated valve and resistances.

Negative Feedback

"Would you please let me know what negative feedback amplifiers are, and if it is possible to add to my present set, circuit attached? I have been out of touch with radio books for some time owing to Army

RULES

We wish to draw the reader's attention to the fact that the Queries Service is intended only for the solution of problems or difficulties arising from the construction of receivers described in our pages, from articles appearing in our pages, or on general wireless matters. We regret that we cannot, for obvious reasons—

- (1) Supply circuit diagrams of complete multi-valve receivers.
- (2) Suggest alterations or modifications of receivers described in our contemporaries.
- (3) Suggest alterations or modifications to commercial receivers.
- (4) Answer queries over the telephone.
- (5) Grant interviews to querists.

A stamped addressed envelope must be enclosed for the reply. All sketches and drawings which are sent to us should bear the name and address of the sender.

Requests for Blueprints must not be enclosed with queries as they are dealt with by a separate department.

Send your queries to the Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. The Coupon must be enclosed with every query.

service, but now want to come up to date and modify the set I have left at home for my people's use."—G. R. E. (Cambridge).

BRIEFLY, negative feedback or degenerative amplifiers are those in which a portion of the output voltage is fed back to the input voltage in order to cancel out harmonic distortion. This may be done by including a load resistance in series with the output load or in parallel with it, and tapping off from this additional resistance so that it is fed in series with the input voltage. Owing to the loss incurred by this, the input must be proportionately increased to maintain the same output level. You could add it to your old set, but modern valves are, in general, capable of supplying adequate power without the need for introducing such devices.

Amplifier Design

"I want to build up a small mains-operated amplifier suitable for microphone and pick-up, but have been told that one amplifier is not suitable for both purposes, because of the different characteristics of mike and pick-up. I should be glad of your advice as to a suitable design, for use in a very small hall for general entertainment work."—L. R. E. (Kettering).

IT is true that very often a microphone will need more amplification than a pick-up, or that special tone-control methods may be needed with certain types of pick-up. The usual arrangement is to add a fader input circuit—that is, two volume controls in series, with pick-up across one and mike across the other. This enables fading and mixing to be carried out. For

DON'T MISS YOUR RADIO

Install an Extension Speaker IN YOUR SHELTER



A Stentorian gives a quality of reproduction that will surprise you. It does full justice to the finest receivers and yet is modestly priced to suit all pockets. Install an extension speaker in your A.R.P. Room or Shelter and enjoy cheery radio entertainment when you most need it.

Cabinet models from 21/6
Chassis models from 19/3

Literature on application.

Stentorian

THE PERFECT EXTRA SPEAKER FOR ANY SET

WHITELEY ELECTRICAL RADIO CO., LTD., MANSFIELD, NOTTS.

ambitious amplifiers, however, an extra stage of amplifications may be included for the mike, connecting the pick-up via a separate valve in parallel with the second stage of the amplifier. This will also permit mixing to be carried out, and at the same time will enable any tone-control schemes to be fitted. We suggest a three-stage amplifier, with the separate valve mentioned, and the output stage to be of the push-pull type. This, if mains operated, should deliver sufficient output for your requirements.

Temporary Aerial

"I have a very small set of the mains-portable type, but the only difficulty is that the volume is not quite enough. I attached an aerial to the input side, and this worked quite well, but I do not want to fit a permanent aerial, and wonder if you can make any suggestions to improve the volume."—N. H. U. (N.3).

YOU do not state what type of aerial you have fitted to the set, and we are not sure, therefore, whether you have tried to make a receiver without any form of signal pick-up. Some aerial must be used, and generally a length of wire is coiled round the back of the case, or, in order to make the set useful in any district a temporary or throw-out aerial is provided. This consists of about 15 or 20ft. of good flex wrapped round a cardboard strip and stowed away in the back of the set. When the receiver is in use this is laid alongside the receiver, and if this does not provide sufficient pick-up it is uncoiled and laid along the floor, along a picture rail, etc. A good idea is to fit a suction cup at the end of the lead, and this may then be attached to a wall without disfigurement and will give the necessary length and height for the particular local conditions.

REPLIES IN BRIEF

The following replies to queries are given in abbreviated form either because of non-compliance with our rules, or because the point raised is not of general interest.

R. G. B. (Liverpool, 21). The pick-up must not be joined direct. An L.F. choke should be connected across the sockets and the pick-up then connected between the anode socket and earth, via a 2 or 4 mfd. fixed condenser. The arrangement will then work as you require.

G. S. (Sheffield, 6). The indication is not necessarily correct. There may be a faulty component in some other part of the set and a stage-by-stage test is desirable.

R. B. D. (W.2). You cannot adjust correctly by guess-work. A good signal generator should be used and you will be unable to trim if the set is right out of adjustment, unless you use such an instrument.

J. R. S. (Truro). We recommend your first-mentioned nomination, in view of your other qualifications.

S. G. S. (Worcester). At the present time, if the firm in question is unable to supply the Manual we regret that we do not know of any other source.

O. I. D. (Manchester). Silk-covered wire is not essential and the only critical point is the turns per inch. The silk covering will permit more turns as it is thinner, and this must be taken into consideration.

N. B. (Neasden). The screen may be found essential and may be obtained from Messrs. Bulgin. Remember the valve maker's note regarding the grid-leak and condenser position.

H. P. O. (Bristol). The first arrangement is desirable, but we cannot give details under present conditions.

D. O. (Birkenhead). Try the ordinary H.F. stage, using an H.F. pentode of the straight type. This should give the desired increase in range, without altering the rest of the receiver.

The coupon on page iii of cover must be attached to every query

you'll get it QUICKER and on BETTER TERMS from L.R.S.

ARMSTRONG

A FINE NEW CHASSIS & SPEAKER AT LOW COST!

★ NEW MODEL EXP.48. 8-valve, 4-band, All-wave Super-het chassis, 13-160 metres, continuous on normal broadcast band, developed on the lines of the popular AW28, with additional short-wave band and numerous other refinements. CASH PRICE £9 8s., with 8in. speaker, or with order and 6 monthly payments of 25/6; 50/- carriage and packing, 4/6. We confidently recommend this Chassis—write for full particulars of this and other Armstrong models on similar terms.

★ W. B. LOUDSPEAKER CHASSIS

Still the finest permanent magnet unit, ideal as principal or extension speaker. Write for particulars and lowest terms—also all well-known sets, Speakers, Avometers, Valves, Components, etc.

★ We shall be glad to quote for other high-grade equipment such as Ambassador Chassis and Receivers, Sound Sales Amplifiers, Volt Speakers and Pick-ups, Avometers, and Portable A.R.P. Receivers, Vortexion Amplifiers, etc.

★ VICEROY Non-electric DRY SHAVER

(Made by Rolls Razors, Ltd.). Ideal for men in the Services or at home where electricity is not available. No brush, soap or water is needed. Complete in case £2 10s. or 10/- with order and 6 monthly payments of 7/3.

★ DOMESTIC ELECTRIC EQUIPMENT for Cash or EASY TERMS



Despite the war we are still able to supply a number of domestic electrical appliances, e.g., Vacuum Cleaners, Fires, Irons, Fans, etc. Send 2jd. postage for full details and terms of any of the above.

Late of 11, Ost Lane, London, E.C.2. Orders sent by return. All communications to evacuation address— "WINDEN," ARDINGLY RD., BALGOMBE, SUSSEX.

An Expert Says—

"I REGARD THE CANDLER SYSTEM as being the MOST IMPORTANT system of its kind and already large numbers of Members of the Radio Society of Great Britain have intimated to me that they are studying the course of instruction with a view to preparing themselves for service in one branch or another of H.M. Forces."

J. CLARRICOTS, Sec.,
Radio Society of Great Britain.

Candler Code Courses

In the "Book of Facts," which will be sent free on request, you will see that full information is given concerning the subjects covered by Courses for beginners and also for operators.

If you are a beginner, the Candler Junior Course will thoroughly train you so that your services will be valuable to one or other of the branches of government service or to commercial or marine companies.

If you are an operator with a consistent sending and receiving speed of 12 or more w.p.m. the Candler Advanced and High Speed Telegraphing Course will greatly increase your speeds and accuracy.

Courses supplied on Cash or Monthly Payment terms.

COUPON

Please send me a Free Copy of the "Candler" Book of Facts."

NAME

ADDRESS

Post Coupon in ld. unsealed envelope to:

CANDLER SYSTEM CO.

(S.L.O.), 121, Kingsway, London, W.C.2
Candler System Co., Ashville, North Carolina, U.S.A.

TRAINED MEN URGENTLY NEEDED

The R.A.F. wants trained radio men for service as Radio Mechanics. We give the training that enables applicants to pass the Trade Test.

A clerk writes: "I would again express my thanks for the tuition that has enabled me to pass my R.A.F. Examination, and particularly for the personal way in which the Course has been conducted."

A grocer writes: "I passed the Test easily, thanks to your Course."

A shop assistant writes: "I sailed through the questions at the R.A.F. Test and thank you for the utmost satisfaction I received from your training."

Even if you know nothing about radio, we can train you. If you have some knowledge of the subject, we can arrange a special Course to meet your requirements.

Our Home-Study Courses are praised and recommended by leading Radio Authorities. Hundreds of students of all ages who are now in well-paid positions owe their success to our training.

If you are not liable for military service, there are excellent opportunities for spare-time or full-time employment.

POST COUPON NOW and learn how you can study at home and become a qualified Radio Engineer.

T. & C. RADIO COLLEGE

Please note new address.

29, The Broadway, EALING, W.5.

(post in unsealed envelope, 1d. stamp)

Please send me free details of your Home-Study Radio Courses.


NAME

ADDRESS

P.O.

TAYLOR VALVE TESTER

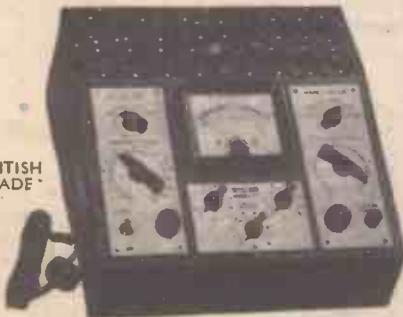With this precision-built Taylor Valve Tester, approximately 1,000 different types of British, American and Continental valves can be put through accurate tests for mutual conductance, cathode leakage emission, etc.



BRITISH
MADE

TAYLOR VALVE TESTER, MODEL 45

£13 - 2 - 6

(Standard Bench Model)

Complete with instruction book & valve chart.

There is also a Portable Model at £13 - 18 - 0

Delivery ex stock. Fully tested. Guaranteed 6 months.

The Taylor range includes:—

UNIVERSAL METERS (4 models).

VALVE TESTERS (3 models).

SIGNAL GENERATORS (4 models),

and an OSCILLOSCOPE.

TAYLOR Electrical Instruments Ltd.,
419-422 Montrose Avenue,
SLOUGH, Bucks. Slough 20061

Practical Wireless

BLUEPRINT SERVICE

PRACTICAL WIRELESS		No. of	SUPERNETS.		
CRYSTAL SETS		Date of Issue.	Blueprint.		
Blueprints, 6d. each.					
1937 Crystal Receiver	—		PW71	Battery Sets : Blueprints, 1s. each.	
The "Junior" Crystal Set	27.8.38		PW94	£5 Superhet (Three-valve)	5.6.37 PW40
				F. J. Camm's 2-valve Superhet	PW52
STRAIGHT SETS. Battery Operated.				Mains Sets : Blueprints, 1s. each.	
One-valve : Blueprints, 1s. each.				A.C. £5 Superhet (Three-valve)	— PW43
All-Wave Unipen (Pentode)	—		PW31A	D.C. £5 Superhet (Three-valve)	— PW42
Beginners' One-valver	19.2.38		PW85	Universal £5 Superhet (Three-valve)	— PW44
The "Pyramid" One-valver (HF Pen)	27.8.38		PW93	F. J. Camm's A.C. Superhet 4	— PW59
				F. J. Camm's Universal £4 Superhet 4	— PW60
				"Qualitone" Universal Four	16.1.37 PW73
Two-valve : Blueprint, 1s.				Four-valve : Double-sided Blueprint, 1s. 6d.	
The Signet Two (D & LF)	24.9.38		PW76	Push Button 4, Battery Model	22.10.38 PW05
				Push Button 4, A.C. Mains Model	
Three-valve : Blueprints, 1s. each.				SHORT-WAVE SETS. Battery Operated.	
Selectone Battery Three (D, 2 LF (Trans))	—		PW10	One-valve : Blueprint, 1s.	
Sixty Shilling Three (D, 2 LF (RC & Trans))	—		PW34A	Simple S.W. One-valver	23.12.39 PW38
Leader Three (SG, D, Pow)	—		PW36	Two-valve : Blueprints, 1s. each.	
Summit Three (HF Pen, D, Pen)	—		PW37	Midget Short-wave Two (D, Pen)	— PW38A
All Pentode Three (HF Pen, D (Pen), Pen)	29.5.37		PW39	The "Fleet" Short-wave Two (D (HF Pen), Pen)	27.8.38 PW91
Hall-Mark Three (SG, D, Pow)	—		PW41	Three-valve : Blueprints, 1s. each.	
Hall-Mark Cadet (D, LF, Pen (RC))	16.3.35		PW48	Experimenter's Short-wave Three (SG, D, Pow)	— PW30A
F. J. Camm's Silver Souvenir (HF Pen, D (Pen), Pen) (All-Wave Three)	13.4.35		PW49	The Prefect 3 (D, 2 LF (RC and Trans))	— PW63
Cameo Midget Three (D, 2 LF (Trans))	—		PW51	The Band-Spread S.W. Three (HF Pen, D (Pen), Pen)	1.10.38 PW63
1936 Sonotone Three-Four (HF Pen, HF Pen, Westector, Pen), Battery All-Wave Three (D, 2 LF (RC))	—		PW55	PORTABLES.	
The Monitor (HF Pen, D, Pen)	—		PW61	Three-valve : Blueprints, 1s. each.	
The Tutor Three (HF Pen, D, Pen)	21.3.36		PW62	F. J. Camm's ELK Three-valve Portable (HF Pen, D, Pen)	— PW65
The Centaur Three (SG, D, P)	—		PW64	Parvo Flyweight Midget Portable (SG, D, Pen)	3.6.39 PW77
F. J. Camm's Record All-Wave Three (HF Pen, D, Pen)	31.10.36		PW60	Four-valve : Blueprint, 1s.	
The "Colt" All-Wave Three (D, 2 LF (RC & Trans))	18.2.30		PW72	"Imp" Portable 4 (D, LF, LF (Pen))	— PW86
The "Rapid" Straight 3 (D, 2 LF (RC & Trans))	4.12.37		PW82	AMATEUR WIRELESS AND WIRELESS MAGAZINE	
F. J. Camm's Oracle All-Wave Three (HF, Det., Pen)	28.8.37		PW78	CRYSTAL SETS.	
1938 "Tri-band" All-Wave Three (HF Pen, D, Pen)	22.1.38		PW84	Blueprints, 6d. each.	
F. J. Camm's "Sprite" Three (HF Pen, D, Det)	26.3.38		PW87	Four-station Crystal Set	23.7.38 AW427
The "Hurricane" All-Wave Three (SG, D (Pen), Pen)	30.4.38		PW89	1934 Crystal Set	— AW444
F. J. Camm's "Push-Button" Three (HF Pen, D (Pen), Det)	3.0.38		PW92	150-mile Crystal Set	— AW450
Four-valve : Blueprints, 1s. each.				STRAIGHT SETS. Battery Operated.	
Sonotone Four (SG, D, LF, P)	1.5.37		PW4	One-valve : Blueprint, 1s.	
Fury Four (2 SG, D, Pen)	8.5.37		PW11	B.B.C. Special One-valver	— AW387
Beta Universal Four (SG, D, LF, Cl. B)	—		PW17	Two-valve : Blueprints, 1s. each.	
Nucleon Class B Four SG, D (SG, LF, Cl. B)	—		PW34B	Melody Ranger Two (D, Trans)	— AW388
Fury Four Super (SG, SG, D, Pen)	—		PW34C	Full-volume Two (SG det, Pen)	— AW392
Battery Hall-Mark 4 (HF Pen, D, Push-Pull)	—		PW48	Lucerne Minor (D, Pen)	— AW426
F. J. Camm's "Limit" All-Wave Four (HF Pen, D, LF, P)	26.9.36		PW67	A Modern Two-valver	— WM409
"Acme" All-Wave 4 (HF, Pen, D (Pen), LF, Cl. B)	2.2.38		PW83	Three-valve : Blueprints, 1s. each.	
The "Admiral" Four (HF Pen, HF Pen, D, Pen (RC))	3.0.38		PW90	£5 5s. S.G. 3 (SG, D, Trans)	— AW412
				Lucerne Ranger (SG, D, Trans)	— AW422
Mains Operated.				£5 5s. Three : De Luxe Version (SG, D, Trans)	19.5.34 AW435
Two-valve : Blueprints, 1s. each.				Lucerne Straight Three (D, RC, Trans)	— AW437
A.C. Twin (D (Pen), Pen)	—		PW18	Transportable Three (SG, D, Pen)	— WM271
A.C.-D.C. Two (SG, Pow)	—		PW31	Simple-Tune Three (SG, D, Pen)	June '33 WM327
Selectone A.C. Radiogram Two (D, Pow)	—		PW19	Economy-Pentode Three (SG, D, Pen)	Oct. '33 WM337
				"W.M." 1934 Standard Three (SG, D, Pen)	— WM351
Three-valve : Blueprints, 1s. each.				£3 3s. Three (SG, D, Trans)	Mar. '34 WM354
Double-Diode-Triode Three (HF Pen, DDT, Pen)	—		PW23	1935 £6 6s. Battery Three (SG, D, Pen)	— WM371
D.C. Ace (SG, D, Pen)	—		PW25	PTP Three (Pen, D, Pen)	— WM399
A.C. Three (SG, D, Pen)	—		PW29	Certainty Three (SG, D, Pen)	— WM393
A.C. Leader (HF Pen, D, Pow)	7.1.39		PW35C	Minitube Three (SG, D, Trans)	Oct. '35 WM396
D.C. Premier (HF Pen, D, Pen)	—		PW35B	All-Wave Winning Three (SG, D, Pen)	— WM400
Unique (HF Pen, D (Pen), Pen)	—		PW36A		
Arguath Mains Three (HF Pen, D, Pen)	—		PW38	These Blueprints are drawn full size.	
F. J. Camm's A.C. All-Wave Silver Souvenir Three (HF Pen, D, Pen)	—		PW50	Copies of appropriate issues containing descriptions of these sets can in some cases be supplied at the following prices which are additional to the cost of the Blueprint. A dash before the Blueprint Number indicates that the issue is out of print.	
"All-Wave" A.C. Three (D, 2 LF (RC))	—		PW54	Practical Wireless (issues dated prior to June 1st, 1940) 4d. Post Paid	
A.C. 1936 Sonotone (HF Pen, HF Pen, Westector, Pen)	—		PW56 (Issues dated June 1st to July 27th, 1940) 5d. Post Paid	
Mains Record All-Wave 3 (HF Pen, D, Pen)	—		PW70 (Issues dated September, 1940 and after) 7d. Post Paid	
Four-valve : Blueprints, 1s. each.			 4d. " "	
A.C. Fury Four (SG, SG, D, Pen)	—		PW20 1/4 " "	
A.C. Fury Four Super (SG, SG, D, Pen)	—		PW34D	Amateur Wireless " "	
A.C. Hall-Mark (HF Pen, D, Push-Pull)	—		PW45	Wireless Magazine " "	
Universal Hall-Mark (HF Pen, D, Push-Pull)	—		PW47	The index letters which precede the Blueprint Number indicate the periodical in which the description appears : Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.	

These Blueprints are drawn full size. Copies of appropriate issues containing descriptions of these sets can in some cases be supplied at the following prices which are additional to the cost of the Blueprint. A dash before the Blueprint Number indicates that the issue is out of print. Practical Wireless (issues dated prior to June 1st, 1940) 4d. Post Paid (Issues dated June 1st to July 27th, 1940) 5d. Post Paid (Issues dated September, 1940 and after) 7d. Post Paid 4d. " " 1/4 " " Amateur Wireless " " Wireless Magazine " " The index letters which precede the Blueprint Number indicate the periodical in which the description appears : Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine. Send (preferably) a postal order to cover the cost of the blueprint, and the issue (stamps over 6d. unacceptable) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

NOTES FROM THE TRADE

Ekco D.C./A.C. Converter

ONE of the latest products which Messrs. E. K. Cole, Ltd., are introducing to the radio market is a particularly useful type of D.C./A.C. converter which we feel sure, in view of the number of inquiries we receive from readers about such units, will be welcomed by a vast number of listeners.

The new converter is designed to enable an A.C. operated receiver or amplifier to be operated on D.C. mains, thus eliminating to a very great extent the limitations previously imposed on those listeners having



A good idea of the neat and robust construction of the new D.C./A.C. converter, by E. K. Cole, Ltd., can be obtained from this illustration of the unit.

D.C. supplies in the choice of suitable apparatus. Similarly, when owners of A.C. receivers are faced with a move from an A.C. to D.C. district, the unit will provide an admirable method of operating their existing set under the new conditions.

The converter is sturdily constructed, yet the measurements have been kept to modest figures (9in. x 7½in. x 6½in.). It delivers an output of 80-100 watts, at 200-250 volts, 50 cycles, and is, therefore, capable of operating most types of receiver, including those incorporating press-button motor-tuning, and other auxiliary mains-operated mechanisms. Extensive tests have proved that the unit is entirely satisfactory, even on extremely noisy mains. The retail price is £5 12s. 6d.

Mr. H. A. Woodyer

WELL known from his previous connections with Dubilier and T.M.C., Mr. H. A. Woodyer has been appointed sales manager of the radio department of Simmonds Accessories, Ltd.

Glasgow Carries On

THE radio trade in Glasgow does not intend that the war should interfere with trade development. Therefore, as in former years, classes for the study of radio technology are being held in the Allen Glens School. The classes have the support of the Scottish Radio Retailers' Association, and the subjects covered prepare radio staff men for the City and Guilds and standard radio examinations.

Philco Car Radio Conversion Unit

PHILCO have now produced a very compact conversion unit for the operation of their car-radio receivers, using a P.M. speaker from A.C. mains. It is most simple to fit, merely a matter of minutes, and is suitable for 6- or 12-volt receivers. The list price is 29s. 6d.

H.T. Battery Prices

THE Association of Radio Battery Manufacturers has announced that they do not anticipate, subject to the operations of war, any increase in consumer prices of batteries. The Association includes the-

makers of Pertrix, Drydex, Ever-Ready, Oldham and Full-O'-Power batteries, and present prices of popular sizes are as follow :

	s.	d.		s.	d.
Winner 120 volt	7	6	Portable 40	10	6
Itadio 120 volt	6	0	Portable 40	18	0
Super 120 volt	10	6	Portable 50	13	9
Portable 24	15	6	Portable 61	6	0
Portable 30	8	9	Portable 63	7	6
Portable 32	12	9	All-dry 3	10	0

Service Engineers

THE vast number of highly experienced service engineers which have already taken up positions in H.M. Forces has raised a very serious problem for the radio trade in general to solve. It would appear that the matter is of such magnitude that it cannot be solved or dismissed by some half-hearted temporary emergency arrangement as, like many other skilled trades, qualified men cannot be found at a moment's notice or produced from raw material in a week or so. In many districts, the traders are getting together and making a genuine attempt to determine what trained labour is available, and then adopting a system of pooling their requirements or, on the other hand, sharing according to the available work on the benches, the total help at their disposal. There must be a great number of keen and experienced radio amateurs who are above military age, and who are quite capable of stepping into the breach and, if not allowing the trade to cater for their clients requirements as before, at least reducing the load to such an extent as to bring conditions nearer normal. It will, no doubt, be argued that an amateur has not had the opportunity of becoming familiar with all types of commercial products but, provided a man has had sound amateur experience, and is of average intelligence, the facilities now provided by the set manufacturers, in the form of data and test sheets and information, should allow the new recruits to the trade to prove their worth in a very short time.

Radio Trade Reserved Ages

IT is important now to remember that the reserved age for wireless engineers and servicemen has been raised to 35. The following are the main trades and ages :

Occupation	Age of Reservation from	
	General Service	Service in Trade Capacity
Wireless Engineer ..	18	35
Fault-finder, tester ..	18	30
Wireless Repairer ..	18	35
Wireless Mechanic ..	18	35
Serviceman ..	18	35
Loudspeaker cone maker ..	30	—

THE PRACTICAL WIRELESS ENCYCLOPEDIA

By F. J. Gamm

A complete guide, in alphabetical order, to the construction, operation, repair and principles of every type of wireless receiver. Includes definitions, explanations, formulae and complete instructions on the making and testing of various wireless components.

Illustrations include a complete series of circuits for every type of modern receiver.

392 pages. Over 500 illustrations.

Of all Booksellers, 7/6 net, or by post 8/- from George Neumes, Ltd. (Book Dept.), Tower House, Southampton Street, London, W.C.2.

TYPE.

NATIONAL EFFORT

IN these times, in many directions, needless to say, we are directing our main efforts and supplies towards the requirements of the Government Services.

However, some supplies of components are still available for Constructors and Radio Servicing, but should delays occur we know our friends will appreciate the difficulties which at present arise from day to day.

We would point out that delays can be minimised and often avoided if alternatives are, wherever possible, specified when ordering.

Prices are being kept as low as possible despite increased costs in every direction. Meanwhile you still have the best and largest range of radio products in the United Kingdom to choose from.

THANK YOU!

A SELECTION OF M.E.S. HOLDERS

- M.E.S. Dual Live 28 Bracket. **6^d**
- M.E.S. Springplunger Contact. **3^d**
- M.E.S. Double Clip Bracket. **3^d**
- M.E.S. Recessed Fixing Bracket Live. **3^d**
- M.E.S. As No. 60, side 62 ears pinched over. **3^d**
- M.E.S. Live Fixing 61 Bracket. **3^d**
- M.E.S. As 27, side 42 ears pinched over. **3^d**
- M.E.S. As 27 less side 45 ears. **3^d**
- M.B.C. As No. 12, ear 14 pinched over. **4^d**
- M.B.C. Baseboard or 6 chassis fixing. **4^d**
- S.E.S. Baseboard or 81 chassis fixing. **4^d**
- S.E.S. Baseboard or 6 chassis fixing. **4^d**

PLUS 16½% WAR INCREASE

ALWAYS DEPEND ON

BULGIN

Advert of A. F. BULGIN & Co. Ltd., BYE PASS ROAD BARKING. Tel RIPolewaz 3474 (4 lines)

Classified Advertisements

ADVERTISEMENTS are accepted for these columns at the rate of 2d. per word (minimum charge 2/- each paragraph). All advertisements must be prepaid. EACH paragraph will commence with the first word printed in bold face capitals. Additional words in bold face capitals are charged at 4d. per word. ALL communications should be addressed to the Advertisement Manager, "Practical Wireless," Tower House, Southampton Street, London, W.C.2.

PUBLIC APPOINTMENTS

VACANCIES IN THE AERONAUTICAL INSPECTION DIRECTORATE. MINISTRY OF AIRCRAFT PRODUCTION.

Vacancies exist for unestablished appointments as Examiners in the General Engineering, W/T Instrument Branches.

QUALIFICATIONS.

All candidates must have good general education, be able to read drawings, understand specifications, use micrometers and other measuring instruments.

(a) Applicants for the General Engineering Branch must have had practical experience in an engineering works. An elementary knowledge of materials testing is desirable.

(b) Applicants for the Instrument Branch must have knowledge of physics and training in light engineering or instrument making. Candidates with knowledge of optical instruments are also required.

(c) Applicants for the W/T Branch must have practical knowledge of W/T and electrical equipment with technical training in radio communication equal to City and Guilds final examination standard.

Accepted candidates will undergo a period of training in inspection as applied to the above subjects, not exceeding three calendar months, and will be paid £3/15/0 weekly during training. Subsistence allowance of £1/5/0 weekly during training is payable to married men normally residing outside the training area. On successful completion of training, candidates will be appointed as Examiners at a salary of £270 per annum (payable monthly in arrear) subject to a deduction of £12 per annum for each year of age below that of 24. Payment for overtime. Examiners must be prepared to serve in any part of the United Kingdom. Normal age limits, 23 to 60.

Candidates should indicate on their applications for which type of vacancy (i.e., (a), (b), or (c)) they wish to be considered.

Applications must be made on Form 786, copies of which can be obtained on application, by postcard only, to: Ministry of Labour and National Service, Box No. 171, Head Post Office, Small Street, Bristol.

CABINETS

A CABINET for every radio purpose. Surplus cabinets (undrilled) from noted makers. We have hundreds in stock (no catalogues). Send measurements of chassis, etc., and say what kind of cabinet required. Stamp for reply. Inspection invited.

H. L. SMITH AND CO., LTD., 289, Edgware Road, W.2. Tel.: Pad. 6891.

LITERATURE

BRAND New Edition "Amateur Radio Handbook." 330 pages, 4s. 2d., post free.—R. S. G. B. 16, Ashridge Gardens, London, N.13.

LOUDSPEAKER REPAIRS

LOUDSPEAKER repairs, British, American, any make. 24-hour service, moderate prices.—Sinclair Speakers, Pulteney Terrace, Copenhagen Street, London, N.1.

REPAIRS to moving coil speakers. Cones/coils fitted or rewound. Fields altered or wound. Prices quoted, including eliminators. Pick-ups and speaker transformers rewound, 4/6. Trade invited. Guaranteed satisfaction. Prompt service.

L.S. Repair Service, 5, Balham Grove, London, S.W.12. Battersea 1321.

MORSE EQUIPMENT

FULL range of Transmitting Keys, Practice Sets, Oscillators, Recorders and other Radio Telegraph Apparatus, designed and manufactured by T. R. McElroy, World's Champion Telegraphist. Sole distributors: Webb's Radio, 14, Soho Street, London, W.1. Phone: Gerrard 2080.


MORSE TRAINING

WIRELESS Code Courses. "Book of Facts" Free.—Candler System Co. (L.O.), 121, Kingsway, London, W.C.2.

ARMSTRONG

SPECIAL OVERSEAS MODEL EXP48

8-v. 4-BAND ALL-WAVE SUPERHET CHASSIS

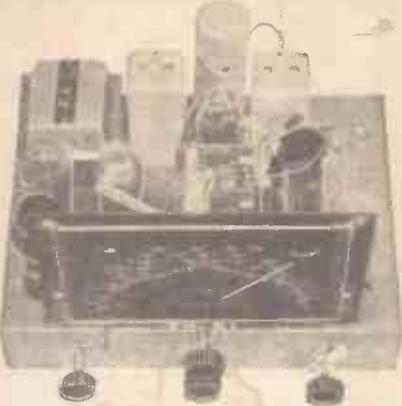

This chassis has been developed on the lines of our Model AW38 which has proved an outstanding success since its introduction at 1939 Radiolympia. Overseas requirements, however, have been given primary consideration. Firstly, an additional short-wave band has been incorporated and the chassis now gives an efficient continuous short-wave coverage from 13 to 160 metres. All coils and I.F. transformers have been specially treated to render them impervious to humidity. Switching is of extra robust construction and contacts heavily plated. The mains transformer is interleaved and has a generous iron content to avoid excessive temperature rise and the steel chassis itself is heavily cadmium plated for tropical use. **3 gns.** EXP48 is equally suitable for Home Market.

Packing and Carriage 4/6 on all models.

With 8" P.P. Speaker £9. 9. 0

With 10" P.P. Speaker £10 3. 0

Please write for Specification.

ARMSTRONG MANFG. Co.

WARTLERS ROAD, HOLLOWAY, LONDON, N.7.

(Adjoining Holloway Arcade)

Phone: NORth 3213



F

RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I. C. S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 94A, International Buildings, Kingsway, London, W.C.2.

Please explain fully about your instruction in the subject marked X.

Complete Radio Engineering
Radio Service Engineers
Elementary Radio
Television

If you wish to pass a Radio examination, indicate it below.

Inst. of Wireless Technology
P.M.G. Certificate for Wireless Operators
Provisional Certificate in Radio Telephony and Telegraphy for Aircraft
City and Guilds Telecommunications

Name Age

Address

(Use penny stamp on unsealed envelope.)

NEW LOUDSPEAKERS

3,000 Speakers, P.M. and energised 4in. to 14in. Including several Epoch 18in.—Sinclair Speakers, Pulteney Terrace, Copenhagen Street, London, N.1.

NEW RECEIVERS AND AMPLIFIERS

CHALLENGER RADIO CORPORATION.—We still lead with best value money can buy; send 2/6. stamp for illustrated catalogues of finest all-wave receivers, handsome cabinets, speakers and valves, firsts only 6/- each; every article fully guaranteed; buy now before prices again rise.

CHALLENGER RADIO CORPORATION, 31, Craven Terrace, Lancaster Gate, London, W.2.

NEW VALVES

BRITISH VALVES AT LESS THAN ONE-THIRD COST (All Guaranteed). Battery types. 2v. Double Diode Triode, 2/- Power, 1/6. Super Power, 1/9. Pentodes 4- and 5-pin, 2/6. Class B, 3/6. Mains types, 4v., A.C./H.L. indirectly heated, 2/6. A.C. Screen-grid, 3/6. S.G. High-Gain, 3/6. S.G. Variable-mu, 3/6. A.C.-D.C. types: K.T.30, 3/6; L.13 Detectors, 1/6; U.30 Rectifiers, Octal, 1/6. All made by well-known British manufacturer. Terms: Cash with order to S.S. (P.), Radio Service, 20, Upper Duke Street, Liverpool.

RADIO CHASSIS

ARMSTRONG COMPANY have a limited number of chassis not included in the current catalogue, but carrying the makers' guarantee. Chassis are offered at especially economical prices. Several examples are given below.

ARMSTRONG RF96 All-wave Radiogram chassis with R.F. pre-amplifier, supplied complete with matched moving-coil speaker. £6 10s. 0d.

ARMSTRONG RFPPT All-wave Radiogram chassis with R.F. pre-amplifier and Push-pull output using PX4 valves capable of handling 6 watts. £7 7s. 0d.

ARMSTRONG 7 stage Radiogram chassis complete with matched speaker, £4 10s. 0d.

ARMSTRONG have several other models. Please write for particulars.

ARMSTRONG COMPANY, WARTLERS ROAD, HOLLOWAY, LONDON, N.7.

RADIO MAP AND GLOBE

WEBB'S Radio Map of the World enables you to locate any station heard. Size 40" by 30" 2 colour heavy Art Paper, 4/6, post 6d. Limited supply on Luen, 10/6, post 6d. WEBB'S Radio Globe—superb 12" full-colour model. Radio prefixes, zones, etc. Heavy oxidised mount. Post Paid. 27/6.—Webb's Radio, 13, Soho Street, London, W.1. Phone: Gerrard 2080.

RECEIVERS AND COMPONENTS

VAUXHALL. Rola 8in. P.M. speakers, 14s. 9d.; Rola 10in. P.M. speakers, 18s. 6d.; Rola 1,500 ohm energised speakers, 12s. 6d.; all with transformers. Electrolytic condensers, cardboard case, 8 mfd., 500 v., 2s.; 8+8 mfd., 500 v., 3s. 6d.; 50 mfd., 50 v., 1s. 9d. Volume controls; 2s.; with switch, 3s. Iron-cored tuning coils on base with terminals, switch, 2-gang, 12s. 6d.; 3-gang, 19s. 6d. Bar-type 2-gang condensers, 0.0005 mfd., 6s. 6d. with trimmers. Resistors, 1 watt, 4d. each. Niclet 33-1 L.F. transformers, 5s. 9d. Skeleton H.T. 10 rectifiers, 11s. Gramophone pick-ups, 11s. and 18s. 9d.

VAUXHALL UTILITIES, 103a, Strand, London, W.C.2. Postage extra orders under 3s. Stamp for list.

SOUTHERN Radio's Bargains.

ALL Guaranteed. Postage Extra.
5/- Parcel of useful components, comprising Condensers, Resistances, Volume Controls, Wire, Circuits, etc. Value 25/- 5/- per parcel.

15/- Service Man's Component Kit. Electrolytic Condensers, Volume Controls, Resistances, Tubular, Mica, Paper Condensers, Valve Holders, etc. 120 articles contained in strong carrying case, 9" x 7" x 7", 15/- the Kit.

5/- 100 Wire-ended Resistances, assorted capacities. 1 and 1 watt, 5/- per 100.

ORMOND Loud-speaker Units, 2/6. Crystal Sets, 5/6; Westcocks Type W2, 2/6; Crystal Detectors, 2/-; Crystals, 6d.; "P.O." Microphones on Stand, for use with any receiver, 5/-; Telsen W349 Iron-core Midget D.L. Coils, 5/6; Morse Tapping Keys, 3/- Buzzers, 1/6.

2/- Tool or Instrument Carrying Cases, ex Government Stock. Wood 9" x 7" x 7", 2/-.

SOUTHERN Radio, 46, Lisle Street, London. W.C. Gerrard 6053.

RECEIVERS AND COMPONENTS

PHILIPS HIGH VOLTAGE CONDENSERS. Infd. at 4,000-volt working, 5/8 each, carriage paid. T.C.C. Electrolytic Condensers, 2,000 Mfd., 12-volt working, 2/6 each, post 4d.

VOLTAGE CHANGER TRANSFORMER, 2,000 watts, 110 to 200/240 volts or vice versa. Price 75/-. Guaranteed 12 months.

D.C. MOTOR BLOWERS, 2in. inlet and outlet. Aluminium body, laminated field, ideal for dust-out ventilation. 100-volt, 25/-; 220-volt, 30/-. Carriage Paid.

A SPECIAL LINE—MAIN: TRANSFORMER for Dugout lighting off 12-volt car bulbs, input of Transformer is 200/230 volts, output is 12 volts at 3 amps. Price 7/6 each, 6d. post.

NEWTON MOTOR GENERATOR, 220-volt, D.C. input, 16 volts 11 amps output, in perfect condition. 45/-. Carriage forward.

MOVING-COIL METER MOVEMENTS, for recalibrating into multi-range meters. Low milliamper collection. 2 1/2 in. dial. Makers: Everett Edgwa and other good makers. Price, 6/- each.

EX-G.P.O. UNI-SELECTOR SWITCHES, with relay, 3 rows of 25 contacts in new condition, 15/- each.

HIGH-VOLTAGE TRANSFORMERS, useful for all test work, or television. Input 200/240 volts, output 5,000 and 7,000 volts, 6/6 each, post 1/-.

MAINS TRANSFORMERS, 200/230 volts input, 12 and 24 volts at 4/8 amps. output, suitable for model trains, etc., 15/- each, post 1/-.

MAINS TRANSFORMERS, 200/240 volts input, 50 volts 8 amp. output, useful for small arcs, etc., 15/- each, post 1/0.

ELECTRO DYNAMIC ROTARY CONVERTOR, 110 volts D.C. input, 600 volts 150 m/a 6 volts 5 amps. D.C. output, 45/-. Carriage forward.

B.T.M. LIGHTWEIGHT HEADPHONES, 4,000 ohms., condition as new, but headgear needs repair. Price 3/- per pair. Post free.

VOLTAGE CHANGING TRANSFORMERS (Auto Wound) 100/110 to 200/240 volts or vice versa. Guaranteed 12 months. 250 watts, 25/-; 500 watts, 32/6; 1,000 watts, 50/-; 1,500 watts, 62/6. Delivery 7 days from date of order.

SMALL ELECTRIC ROTARY CONVERTOR, 110 volts D.C. input. 16 volts at 30 amps. output. Useful for garage charging. 55/-. Carriage forward.

50-VOLT D.C. MOTORS, 1/2 h.p., 1,500 r.p.m., 6/6 each. Ditto, 100 volts D.C., 7/6 each.

EPOCH P.M. MOVING-COIL SPEAKERS, 10-in. cone, 10 ohm speech coil, handle 10/12 watts, 32/6 each. Carriage 2/6.

MAGNAVOX PM PUBLIC ADDRESS MOVING COIL HORN SPEAKERS, handle 15/20 watts, size of horn 40 in., 20-in. flare. Price 47/6, carriage paid.

EX-G.P.O. SMALL RELAYS, 1,000 x 1,000 ohms with multi contacts, new, 5/-. Ditto, 7,000 ohms two-leave type, 3/6 each. Useful for remote control, etc.

DYNAMOS, for charging or lighting, etc., all shunt wound and fully guaranteed. 100-volt 10 amp., 4-pole, 1,500 r.p.m., 90/-; 50/75-volt 15 amp., 1,750 r.p.m., 4-pole, 90/-; 30-volt 30 amp., ball bearings, 1,500 r.p.m., 4-pole, 70/-; 25-volt 8 amp., 1,750 r.p.m., 2-pole, ball-bearing, 37/6; 50/75-volt 25 amp., 4-pole, 1,500 r.p.m., 110/-.

CROMPTON, self-exciting 50/100 cycle Alternator, 70 volts 500 watts. 23/10/6, carriage forward.

X-RAY TUBES by well-known makers, 7-in. bulb Tungsten Targets, 15/- each, carriage forward.

CRYPTO SHUNT WOUND DYNAMO, 12/18 volts, 8/10 amps., 2,200 r.p.m., in new condition, 37/6, carriage forward.

Terms: Cash with Order or C.O.D. charges extra. ALL GOODS SENT ON THREE DAYS' APPROVAL AGAINST CASH.

GALPIN'S ELECTRICAL STORES, 75, Lee High Rd., Lewisham, London, S.E.13. Telephone: Lee Green 5240.

BANKRUPT bargains, genuine offer, brand new 1039-40 models maker's sealed cartons, with guarantees at 25 per cent. to 40 per cent. below listed prices; also portables, midgets; send 1/6 stamp for lists.—Radio Bargains, Dept. P.W., 261-3, Lichfield Street, Aston, Birmingham.

COULPHONE Radio, New Longton, Preston. Prompt personal service. Brand new goods only. Tungstram valves, Cosmocord Crystal Pickups, Rola speakers, American valves (4s. 6d. to 6s.), guaranteed. Armstrong chassis, B.I. electrolytic condensers, Dubilier resistors. All the new 1941 receivers of Decca, K.B., Ferguson, R.G.D., Pilot, G.E.C. Before you purchase any radio goods send stamp for new list and save money. Special offer of Airmaster (British) 8-valve 4-waveband chassis complete with speaker at £8 8s.

RADIO Clearance, Ltd., Temporary Address: 38, Lamb's Conduit Street, W.C.1. We advise all our customers that we are now at the above address. All lines previously advertised in this journal in stock.

TRICKLE Chargers for 2 v. accumulator, 8/6. Metal rectifiers for trickle chargers, 3/6. Guaranteed.—Champion, 42, Howitt Road, London, N.W.3.

The Superheterodyne Receiver

By Albert T. Witts, A.M.I.E.E. A reliable comprehensive and up-to-date guide to the superheterodyne receiver, incorporating all recent developments. It is particularly useful for those intending to become radio mechanics in the Services. Fourth Edition. 182 pages. 4/6 net (by post 5/-).

Order from a bookseller or direct from
PITMAN, Parker St., Kingsway, London, W.C.2.



British Mechanical Productions Ltd.
1. Church Road, Leatherhead, Surrey

Booksellers to the World
FOYLES
New and secondhand books on Wireless and every other subject.
113-125, CHARING CROSS RD., LONDON, W.C.2
Telephone Gerrard 5660 (16 lines)

RECEIVERS AND COMPONENTS

SPARTAN 5-valve Press Button Radio. No manual tuning. 7 stations on press button. Walnut cabinet, provision for pick-up and extension speaker, 4 watts output with negative feed back. Multi-stage Superhet with A.V.C. for A.C. mains only, guaranteed reception. Price £4/5/0, carriage paid.

CRYSTAL SETS, Permanent Detector, suitable for A.R.P. shelters, new only, 7/6, post free. Oldham ex-police used unspillable 2-volt 7 amp. Accumulators, suitable for lamps, portables, etc., 2/-.

B.I. CONDENSERS, 4 mfd., 450 v. working, resin oil filled, 3/-, post free. 25 mfd. 1,000v. working, 2/3 each; 1 mfd. ditto, 2/3.

MORSE keys, 2/11 each. Microphone 80/1 Transformers, 1/9 each.

BALL-BEARING Bakelite Turntables, 6in. diameter, suitable for all purposes, 2/3 each. Universal Output Transformers for Push-Pull Class B. Pentode, etc., 4/0 each. High-note Morse Buzzers, 4 1/2-volts, 2/6 each.

PERMANENT Crystal Detectors, complete with Bracket and Screws, 2/- each. New Malus Energised Speakers, best makes, 8in. 8/9 each. Hand-Telephone Sets, 6/6, with cord 7/-. Dial Communication Telephones with hand set, 18/6 each. Step-up Transformers, 230-100 volts, or vice versa, 30-40 watts 5/-.

ZETOZONE Air Conditioners, 1 valve, 220/250 volts A.C., suitable for shelters, rooms, etc., £1 each. Super Model, 2 valves, with Electric Induction Circulating Fan in handsome Polished Walnut Cabinet, 50/-. 4-valve model in Metal Cabinet, £4/10/6. Geared relays, 12/6 each. Continental Lever 8-day clock movements, 5 1/2 in. enamel dial, 10/6 post free. Positron Dry Electrolytic Condensers, 8+8 mfd. 500 volt working 4-lead, 2/9 each. All goods post free.

LONDON CENTRAL RADIO, 23, Lisle Street, London, W.C.2. Gerrard 2960.

READERS' BARGAINS

JOHN Scott-Taggart 900.—Specified kit built up with specified valves with full range of coils, 10 B.T.S. This set is new, and tried out, it is the goods, price £4/10/0 carriage forward.—William Lawley, Highlands Road, Runcorn.

READERS' BARGAINS

EDISWAL Multi-Circuit Charger, 200-250 A.C. Charge up to 50 cells; almost new, 45 carriage forward.—William Lawley, Highlands Road, Runcorn.

WHAT offers? Secondhand parts, valves, 50 P.W.'s, parts for crystal set, 3 accumulators, headphones, eliminator, 2 v. 1 amp. trickle charger, Fury Four blueprint.—Jordan, Ecclesall Vicarage, Sheffield.

DYNAMO, 12 v. 10 a., switchboard for same; short-wave converter; moving coil speaker with transformer; all as new.—For prices write to Dunnington, Heck, South, Goole.

FOR Sale, pair Unigen Coils, 5/6; pair Lissen Coils, 2/6; Niclet Trans., 3.5/1; 3-; Hypernick Trans., 1/6; "Atlas" Eliminator (D.C.), 4/-; Premier S.W. Condensers, 15mmf., 9d., 100mmf., 1/-, 250mmf., 1/6. Mains and Battery Valves cheap. Send stamp for full list.—Burrell, 91, Burnside Rd., Chadwell Heath, Essex.

SEVEN-WATT Peto-Scott amplifier, as new, £2 6s. carriage paid.—A. Doniger, 2, Snowdon Road, Bournemouth, W.

EVERY issue (31) of Short-Wave Magazine. Sell or exchange for any Short-Wave R.X. gear. Offers: Smith, Police Station, New Stevenston, Lanarkshire.

REPAIRS AND SERVICE

SERVICE With a Guarantee.—Let Challenger overhaul your radio and bring it up to date for the winter; low prices, best workmanship; 3 months' guarantee card given with every job; all replacements; valves 6/- each.—Challenger Radio Corporation, 31, Craven Terrace, London, W.2.

SHORT-WAVE EQUIPMENT

"H.A.C." Short-wave Receivers.—Famous for over eight years. Improved one-valve model now available. Complete kit of precision components, accessories, full instructions, soldering absolutely unnecessary, only 16s., postage 6d. Immediate despatch. Illustrated catalogue free.—A. L. Bacchus, 100, Harrington Road, S.W.5.

TUITION

YOUNG MEN required to train as Radio Officers in the Merchant Navy and R.A.F. Short training period. Low fees. Boarders accepted. Students also prepared for peace-time Radio appointments. Full particulars post free.—Wireless College, Colwyn Bay, or, Calmore, Southampton.

PRACTICAL Postal Courses, radio television, test equipment design, trade-test coaching for I.R.A.F. posts, I.P.R.E. and I.W.T. exams; booklet free.—Secretary, I.P.R.E., 3, Shirley Road, London, W.4.

WANTED

WANTED—Radio amateur call book; state price.—Peacock, 1, Grange Grove, York.

WANTED: Farrex Ultra-Short-wave Attachment for Model F.1 mains converter, or diagram.—Box No. 206, c/o "Practical Wireless."

BOOKS

YOU need a good war atlas when you read the newspapers or listen to the wireless bulletins. "Newnes Comprehensive War Atlas" will make the progress of the conflict understandable in all its aspects.—Of all Newsgagents and Booksellers, 1/6 net, or by post 1/9 from George Newnes, Ltd. (Book Dept.), Tower House, Southampton Street, Strand, London, W.C.2.

KNOW what to do before the doctor comes.—Learn from the new book, "First Aid For The Householder," and your knowledge may be the means of saving a life. Deals in simple language with all kinds of injuries and their treatment, war-gases, shock, and the minor ailments of everyday life. Clearly illustrated.—Of all Booksellers, 1/6 net, or by post 1/9 from George Newnes, Ltd. (Book Dept.), Tower House, Southampton Street, Strand, London, W.C.2.

THE whole amazing science of wireless is contained in "The Outline of Wireless" by Ralph Stranger. The entire theory of reception is clearly explained. Over 800 pages. Illustrated.—Of all Booksellers, 10/6, or by post 11/3 from George Newnes, Ltd. (Book Dept.), Tower House, Southampton Street, Strand, London, W.C.2.

FREE ADVICE BUREAU

COUPON

This coupon is a valuable until November 2nd 1940, and must accompany all Queries and Hints.
PRACTICAL WIRELESS, November, 1940.


FREE!

This IMPORTANT GUIDE to SUCCESSFUL ENGINEERING CAREERS

After months of intensive effort and research we are pleased to announce that the new edition of our handbook, "ENGINEERING OPPORTUNITIES" is now out of the publishers' hands and ready for free distribution. Containing 208 pages of practical guidance, this book is, beyond argument, the most and most complete handbook on Successful Engineering Careers ever compiled. It is a book that should be on the bookshelf of every person interested in engineering, whatever his age, position or experience.

The Handbook contains, among other interesting matter, details of B.Sc., A.M.I.C.E., A.M.I.Mech.E., A.M.I.E.E., A.M.I.A.E., A.M.I.W.T., A.M.I.R.E., A.M.I.P.E., CIVIL SERVICE, and other important Engineering Examinations; outlines, courses in all branches of CIVIL, MECHANICAL, ELECTRICAL, AUTOMOBILE, RADIO, TELEVISION, AERONAUTICAL and PRODUCTION ENGINEERING, DRAUGHTSMANSHIP, TRACING, BUILDING, GOVERNMENT EMPLOYMENT, etc., and explains the unique advantages of our Employment Department.

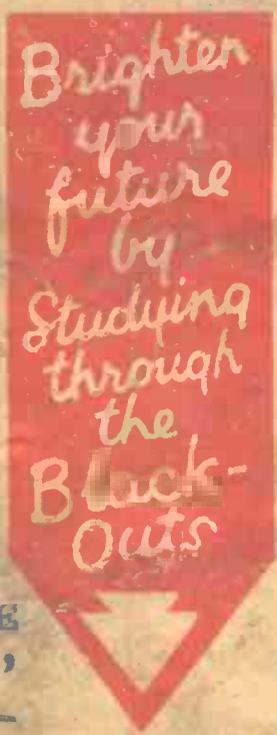**WE DEFINITELY GUARANTEE
"NO PASS—NO FEE"**



If you are earning less than £10 per week you cannot afford to miss reading "ENGINEERING OPPORTUNITIES."

In your own interests, we advise you to write (or forward the coupon) for your copy of this enlightening guide to well-paid posts—NOW. There is no cost or obligation of any kind.

**BRITISH INSTITUTE OF
ENGINEERING TECHNOLOGY**

**409a, SHAKESPEARE HOUSE,
17, 18 & 19, STRATFORD PLACE, LONDON, W.1.**

CLIP HERE
FREE COUPON

To E.I.E.T.,
409a, SHAKESPEARE HOUSE,
17-18 & 19, STRATFORD PLACE,
LONDON, W.1.

Please forward, Free of cost or obligation of any kind, your 208-page Handbook, "ENGINEERING OPPORTUNITIES."

Name

Address

.....

.....

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by THE NEWNES & PEARSON PRINTING CO., LTD., Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH, LTD., South Africa: FRANKLINS & ARNOLD, LTD. Subscription rates including postage: Inland 7s. 6d. per annum, 3s. 9d. for six months; Abroad 7s. 6d. per annum, 3s. 6d. for six months. Registered at the General Post Office for the Canadian Magazine Post.

CONDITIONS OF SALE AND SUPPLY.—This periodical is sold subject to the following conditions, namely, that it shall not, without the written consent of the publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade except at the full retail price of 6d.; and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade; or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.