


epth

9^D

Vol. 26, No. 529
AUGUST, 1950

EDITOR:
F. J. CAMM

PRACTICAL WIRELESS

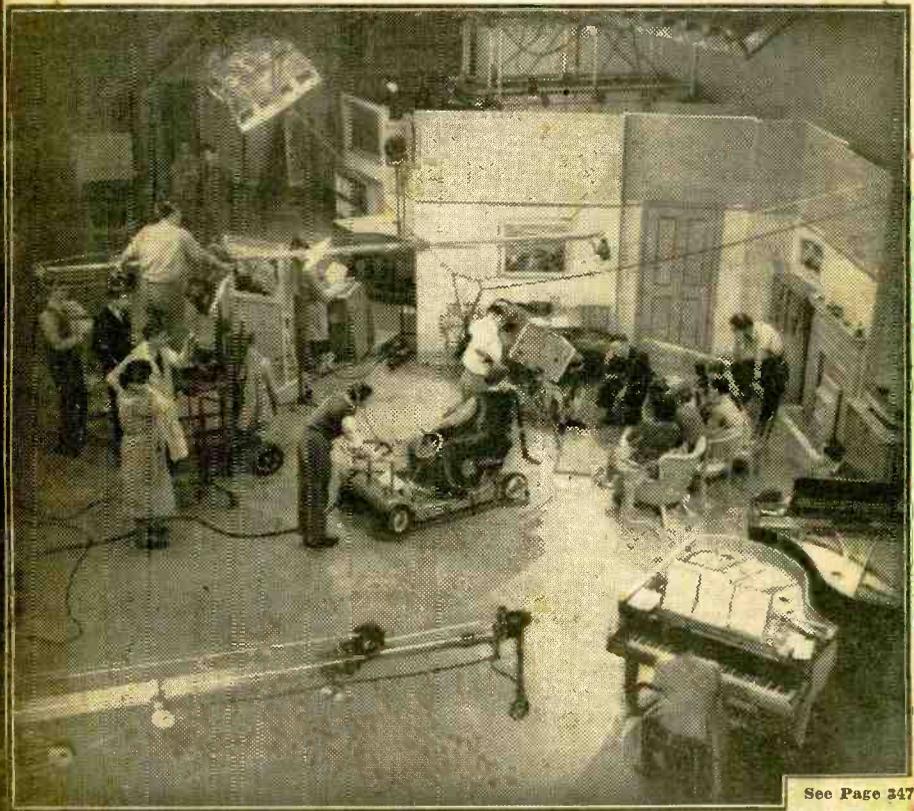

See Page 347

CHIEF CONTENTS

A Simple Transmitter
Two-tube S.W. Receiver
Radio Valve Review
Plastic Recording


Designing Your Own Receiver
Phase-shift Audio Oscillator
Negative Feedback
Equivalent Circuits

LISTEN—IT'S A GOOD SOUND JOB

THE R.A. TUNING UNIT

A really fine design with lasting high performance. P.F. stage on all wavebands. High fidelity superhet or T.R.F. performance, at the turn of the switch. Suitable for any amplifier.

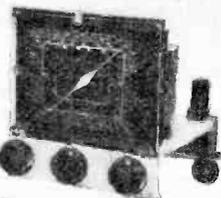10 Gns. plus £2 : 6 : 8 tax
(2 years' guarantee)



Write for our illustrated catalogue



THE K.I. AMPLIFIER

This seven-valve amplifier, designed for the lightweight high fidelity type pick-up. Independent bass and treble controls. Tetrolodes with negative feed-back ensure negligible distortion. Price Complete **17 Gns.** Blueprint separately 2/6 (2 years' guarantee)

DEFERRED TERMS AVAILABLE

Our equipment can also be seen and heard at Webb's Radio, Soho Street London. W. 1. Signal Shop, 51, St. Mary Street, Bridgwater, Som. Ernest Buchan, 20, Belmont St., Aberdeen; Farmer and Co., 83, George Street, Luton.

Charles AMPLIFIERS

(Sales) LTD.

181 Kensington High Street, London, W.8. Phone WESTern 3350.

FOR THE UTMOST REALISM FROM RECORDS & RADIO



CONDENSERS
Pre-eminent since
1906

Specified by the leading designers for Radio, Television and Electronic Applications

USED THROUGHOUT THE FAMOUS "VIEW MASTER" HOME CONSTRUCTOR TELEVISION RECEIVER

THE TELEGRAPH CONDENSER CO. LTD
RADIO DIVISION: NORTH ACTON, W.3. Tel: ACORN 0061

NO WHISTLES!

WITH THE OSMOR 'Q' COILPACKS

As specified for conversion of the Type 25 unit of the TR.1196, and for modernisation of war time utility receivers and others.


SUPERHET and T.R.F.

The OSMOR "Q" Coilpack does not "whistle while it works" but gives you perfect performance in every way. And it saves time, money and hours of wasted effort puzzling over complicated wiring circuits. Just 5 connections, 5 minutes' work and the job is done—and well done!

Send stamp for FREE new circuits, lists of Coils, Coilpacks, Dials and all Radio Components, etc.

* New wavelength scales for Type A dials, 81- each.
OSMOR RADIO PRODUCTS, LTD. (Dept. P7), BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY
Telephone: CROYDON 1220.

A new Super lightweight pickup

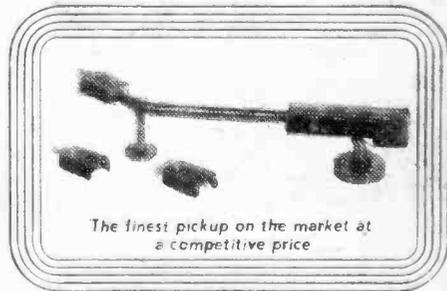


with interchangeable heads
Green Spot for microgroove recordings
Red Spot for modern standard recordings
Yellow Spot for older standard recordings

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Downward pressure 10-12 grams for standard recordings, and 5-7 grams for microgroove recordings.

Prices: With one Head £4 0 0 plus £1 14 8 Purchase Tax
Extra Heads each £2 10 0 plus £1 1 8 Purchase Tax
Spare Armature System with sapphire 14/8 including Tax

Telephone: Hipperholme 6 9 1 6 9
Manufactured by **A Connoisseur PRODUCT**
A. R. SUGDEN & CO (ENGINEERS) LTD.
WELL GREEN LANE BRIGHOUSE YORKS.

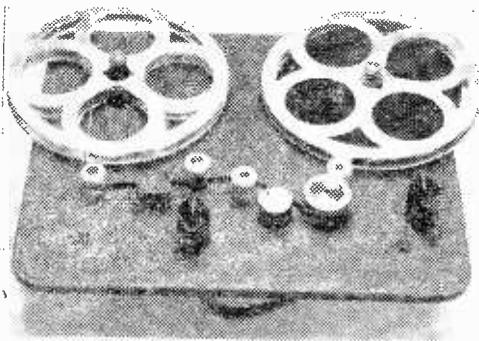**BUILD YOUR OWN
MAGNETIC TAPE RECORDER**



Ideal for Home Amateur Radio Societies, in fact, its uses are unlimited. We can supply Drawings, Motors, Capstan, Drive Mechanism, Record Playback Head, Erase Head, Top and Bottom Plates, Tapes, Amplifier Components, or we can supply the Famous Qualtape Recorder. Complete Kit at £12 10s. 0d.

Write for detailed Price List.

ELECTRONIC SERVICE "HALLAMSHIRE" LTD.
93-95 BUTTON LANE, SHEFFIELD

PRATTS RADIO


1070 Harrow Road, London, N.W.10

Tel.: LADbroke 1731

(Nr. Scrubs Lane).

AMPLIFIERS, READY TO USE.

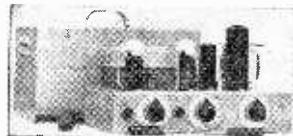MODEL AC10E (As illustrated), 10 watt, 4 valve unit, neg. feedback, separate mike stage and separate mike and gram inputs, 2 faders and tone control. Input volts, mike .002 v., gram .21 v., £8-18-6 (carr. 3-). **MODEL AC18E**, 6-valve unit with P. Full.



Output of 181 watts. Separate mike stage and separate mike and gram inputs, 2 faders and tone control. Feedback over 3 stages, input volts, .003 v. mike, .3 v. gram, £13-19-6 (carr. paid). **MODEL AC10E**, 6 valve, 10 watt unit, spec. as AC10E, for D.C. A.C. mains, £11-11-0 (carr. 5-). All above are complete with Case and Chromo-Handles. Outputs match 3, 8 and 15 ohm speakers. **MODEL AC4C**, A.C. or U4C, A.C. D.C. 3 valve 4-watt amplifier chassis. Output to 3 ohms, £4-19-6 (carr. 2/6). **AC10E, AC10E, AC18E** with tuning unit attachment, 12 G extra. **MODEL TC11**, 3 valve, 3 wave tuning unit. Superhet, flywheel tuning, £9-5-2. Tax Paid. Stamp on list.

SPEAKERS, P.M. L.T.F. W.B. 2 1/2 in. 15/6; 5 in. 17/6. Rola 3 in., 19/6. Truvox 12 in. (3 ohm), 37/6. Plessey 5 in., 9/6; 6 in., 11/9. 10 in., 17/6. Rola 6 1/2 in. M.E. (700 ohm), 10-. Goodmans, 6 in., 18/6.

VALVES, BRAND NEW. GJ5, 6K7, 5Z4, 6J7, 5Y, 6X5, 6Y6, 6Q7, 5U4, 6F6, 6C5, 3Q5, 6/- each. 6K8, 154, 155, 174, 1R3, 351, 6/9.

VARIABLE CONDENSERS, Long Shaft, .0005, 2 gang, 4 3/4; 3 gang, 6/9; Solid Dielectric .0003, 3 3/4; .0001, 3/6. Presets 50pt., 4d.


COILS, ETC. Wearite "P" Coils, 3/- each. Wearite M400B I.F.s 10/6 each. Osmor "Q" coil packs, 33/-.

TRANSFORMERS, Speaker, Pentode (5V6), 2 1/1; Midget 154 354, 3/11. E.H.T. (for VCI97), 2.5 kv., 4 v., 4 v., 27/6.

CONDENSERS, Plessey 16+32+8 450 v., 4/9. T.C.C. 4 mfd, 500 v., 16/-; 25 mfd, 25 v., 1/- each. 25 mfd, 12 v., 8d, each. B.I. cardboard 8+900530, 3 3/4; 8+8, 4/9; 8+10, 6/-; Hunts, 8+8 450 v. or 16+8 450 v., 3/9.

MISCELLANEOUS, Octal bases, Payolin, 4d. amphenol, 6d. BTG, 89C, 9d. Voltage droppers, 2 a., 920 ohm or 3 a., 750 ohm., 4/6. Linecord 3 a. 3-way 60 ohms Pt., 4d. Ft. Volume controls. All values, less Sw., 2/9. With Sw. 4/6. Chokes 60 m.a. 20 hy., 6/6. 90 m.a. 10 hy., 10/6; 150 m.a., 14/3. All Goods New and Unused. Post Free Over £1. C.W.O. or C.O.D.

Wolf ELECTRIC SOLDERGUNS

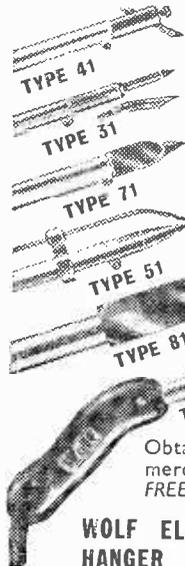

OFF-STRAIGHT EASY-GRIP HANDLE
PERFECT CONTROL
QUICKER HEAT UP
LOCALISED HEAT
LOW CURRENT CONSUMPTION
MAINTAINS CORRECT HEAT
A MODEL FOR EVERY PURPOSE

Obtainable from all leading tool merchants and factors. Write for FREE illustrated technical literature

WOLF ELECTRIC TOOLS LTD.,
HANGER LANE, LONDON, W.5.

The Solder which is recommended for the View Master and other Television Kits



As recommended by the designer, use only ERSIN MULTICORE SOLDER—the Solder wire containing 3 cores of non-corrosive Ersin Flux. 60 ft. of 18 S.W.G. High Tin Television and Radio Solder, 60/40 alloy, is contained in Size 1 Cartons, Cat. Ref. C.16018. Price 5/- retail.


Obtainable from all leading radio shops.

In case of difficulty write to:

MULTICORE SOLDERS LTD.

Mellier House, Albemarle Street, London, W.1. REGENT 1411

RECORD NEWS for MUSIC LOVERS!

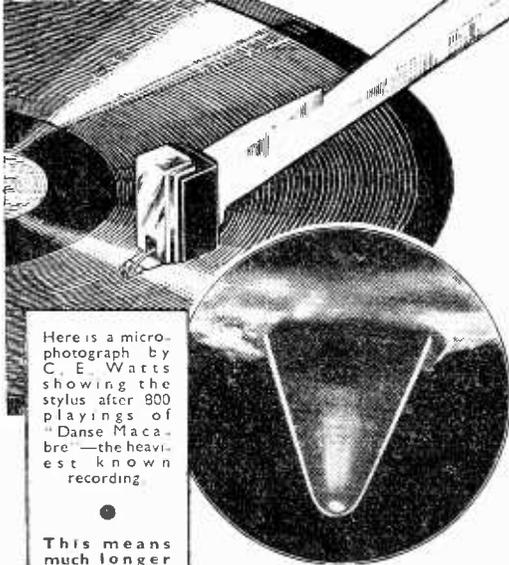

Here is a micro-photograph by C. E. Watts showing the stylus after 800 playings of "Danse Macabre"—the heaviest known recording.

This means much longer life for your records.

A REVELATION awaits every connoisseur of true fidelity who has not heard his records produced via the **acos** G.P.20 NEW-TRUE Fidelity Pick-up. It assures tonal quality and brilliance hitherto associated only with laboratory instruments. Moreover, this outstanding performance is attained WITHOUT RECOURSE TO EQUALISERS—just connect to your radiogram or amplifier. The low needle pressure (14 grms.) of the permanent sapphire stylus virtually eliminates record wear. Output $\frac{1}{2}$ v. at 1,000 c/s—5 to 20 times greater than comparable magnetic types; automatic bass boost; negligible needle talk and motor rumble; unbreakable, non-hygroscopic crystal element.

NOW OBTAINABLE WITH INTERCHANGEABLE HEADS FOR STANDARD OR LONG PLAYING RECORDS. Long Playing Head gives an output of $\frac{1}{2}$ v. at 1,000 cps. and has a needle pressure of 7 grams.

Ask your dealer for a demonstration.

acos

G.P.20 NEW TRUE FIDELITY PICK-UP

COSMOCORD LIMITED • ENFIELD • MIDDX.



'AVO'

Registered Trade Mark

Precision
ELECTRICAL
TESTING
INSTRUMENTS

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set. Stocks are now available of these two famous "Avo" Instruments. If you have any difficulty in obtaining one locally, please send us the name and address of your nearest Radio Dealer.

The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance: 22 ranges of readings on a 3-inch scale. Total resistance 200,000 ohms.

Size: 4 $\frac{1}{2}$ ins. x 3 $\frac{1}{2}$ ins. x 1 $\frac{1}{2}$ ins.
Nett weight: 18 ozs.

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

Price: £8 : 10 : 0

The D.C. AVOMINOR

is a 2 $\frac{1}{2}$ -inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4 $\frac{1}{2}$ ins. x 3 $\frac{1}{2}$ ins. x 1 $\frac{1}{2}$ ins.
Nett weight: 12 $\frac{1}{2}$ ozs.

Complete as above
Price: £5 : 5 : 0

Sole Proprietors and Manufacturers:—
AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder Ho use, Douglas Street, London, S.W.1. Phone: VICTORIA 3404-9

D.C. Voltage

0—75 millivolts
0—5 volts
0—25 "
0—100 "
0—250 "
0—500 "

A.C. Voltage

0—5 volts
0—25 "
0—100 "
0—250 "
0—500 "

Resistance

0—20,000 ohms
0—100,000 "
0—500,000 "
0—2 megohms
0—5 "
0—10 "

D.C. Current

0—2.5 milliamps
0—5 "
0—25 "
0—100 "
0—500 "

GUARANTEE: The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new Avominor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

Practical Wireless

18th YEAR
OF ISSUE

EVERY MONTH.
VOL. XXVI. No. 529 AUGUST, 1950

Editor F. J. CADAM

COMMENTS OF THE MONTH

BY THE EDITOR

Suppressors—No Compulsion

THE Postmaster-General, in a written reply to a parliamentary question, states that he does not propose to take legislative action to make suppressors compulsory in motor vehicles. This problem has become more acute as television has developed, and it will not be disposed of by a parliamentary reply. Sooner or later the weight of public opinion will force the Government to take action, now that there is a visual reproduction of the interference as well as an audible one.

The suppression of the ignition system of motor cars can be carried out for a few shillings. It is argued on behalf of motorists that it is unfair to expect them to go to the small expense of fitting suppressors, and that the problem should be tackled at the manufacturing end. This presumably could be done, but it would be far more costly.

In any case, it is not only motor cars which offend, but many other forms of high-frequency electrical apparatus. The industry has been pressing for legislation to make suppression compulsory for a number of years, and it is a pity that the Postmaster-General in his reply did not give reasons why he proposes to continue to allow it to be voluntary. It is of little use expressing pious hopes that motorists and others will fit suppressors. They will only do so when they find that the interference affects their own receivers.

The problem is by no means shelved, and complaints which at present are confined to two areas will gradually become nation wide. The time to make suppression compulsory is now.

As part of a campaign to overcome the trouble an unusual film has been prepared by the B.B.C., by arrangement with the radio industry, showing how easy it is to fit any car with an interference suppressor.

The film, which is now being televised at intervals, incorporates the sort of interference familiar to most viewers—the "snowstorm" effect on the picture and the "machine-gun rattle" on the sound—when an un-suppressed motor car travels near a television receiving aerial. After the film's opening announcement has been submitted to this form of interference,

the picture steadies for a straightforward demonstration of two kinds of suppressor and how to fit them. One is a simple type, costing between 1s. 6d. and 2s., which is fitted on the car distributor head and will stop most forms of interference. With the other type, also shown in the film, the ignition cable is cut and the ends screwed into the suppressor, which cannot be shaken adrift by the vibration of the engine. The fitting of a suppressor in no way impairs the efficiency of the engine.

The film ends, as it began, with a burst of interference and a reminder from the announcer that sparks from your car spoil people's pleasure.

TV AERIAL BAN

LOCAL authorities in some areas are banning the erection of TV aeriels, and the industry through the R.E.C.M.F. and B.R.E.M.A. have issued a booklet which gives expert advice on the subject of television aeriels. It has been circulated to the surveyors of local authorities throughout Great Britain and Northern Ireland. Although the booklet is intended for private property owners, it is also on sale to the public. The letter to the surveyors expresses the hope that the booklet may be useful not only in advising the council but in dealing with enquiries from tenants who may have their own opinions as to the type of installation most suitable.

The booklet shows the factors which must be considered before an aerial suitable for a particular building or district can be selected. It emphasizes that tests must be carried out on the site before such decision can be made. A list is given of firms who are providing testing facilities and who will advise local authorities and property owners on aerial installation. Eight types of aerial are classified and illustrated. It is only fair to state, however, that owners of radio receiving sets are complaining of the interference caused by adjacent television receivers. Owners of the latter, therefore, should make quite certain that they are not themselves offending in this respect before complaining about interference with their own reception.

F. J. C.

ROUND the WORLD of WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ended April 30th, 1950:

Region	Number
London Postal	2,309,000
Home Counties	1,627,000
Midland	1,715,000
North Eastern	1,878,000
North Western	1,587,000
South Western	1,048,000
Welsh and Border Counties	722,000
<hr/>	
Total England and Wales	10,886,000
Scotland	1,115,000
Northern Ireland	203,000
<hr/>	
Grand Total	12,204,000

The above total includes 363,950 television licences, of which 221,115 were in the London Region.

New Third Programme Transmitting Station for Sheffield

ON June 6th the B.B.C.'s Third Programme transmitter at Manor Lane School closed down, and the service was taken over by a more powerful transmitter which has been installed in a building adjoining the Heeley Baths. The new transmitter has a power of 1 kilowatt and is connected to a "T" aerial, one end of which is suspended from a chimney on the Heeley Baths. The increased power and more efficient aerial will give listeners in the Sheffield district better reception of the Third Programme. The wavelength will remain unchanged at 194 metres.

Amateur Saves 37 Men

AN amateur, listening to the trawler band at 4 a.m. recently heard a call for help.

The message said that two unknown ships had been in collision and one was sinking.

The listener gave the alarm among the Dungeness fishing colony and men and women rushed to the lifeboat house. Within 15 minutes, the James Cooper Henderson was at sea.

By six o'clock the crew of 37 of the 3,712-ton Spanish steamer *Cabo Espartel*, who had taken to their boats, were rescued by the Dungeness lifeboat.

Appointment of Head of Engineering Secretariat

FOLLOWING Mr. F. Williams's appointment as B.B.C. Superintendent Engineer, Studios, Mr. J. H. D. Ridley has become Head of the Engineering Secretariat, a department that deals mainly with the control of expenditure within the Engineering Division.

Mr. Ridley has been engaged on radio work since the earliest days of broadcasting. From 1920 to 1922 he was with the Marconi Company, and from 1922 to 1932 with Burndept Wireless, Ltd. After that he joined the Edison Swan Electric Company, remaining there until 1938 when he came to the B.B.C. In 1945 he became Assistant Head of the Engineering Secretariat.

Mr. Ridley is well known for his cinematograph films of nature subjects. Last year he accompanied Dr. Julian Huxley, F.R.S., and Mr. James Fisher on an expedition to Iceland to make films of bird life for the Television Service.

Customs Use V.H.F.

CUSTOMS and Excise, in stepping up their war against smuggling have ordered new V.H.F. R./T. equipment which will enable them to operate in much the same way as police patrol cars.

This equipment was fitted as an experiment on the *Vigilant*. It proved a great success.

Now it will be installed in the *Valiant* and the *Vincent*.

The *Vigilant* carries two fast launches—one for fine weather, and another for rough seas.



A section of the new Ekco showrooms recently opened in Glasgow.

Danish Radio Exhibition

THE Danish State Radio and Denmark's Radio Industry are arranging an exhibition in Copenhagen, from August 11th to 20th, to mark the twenty-fifth anniversary of the State Radio.

The exhibition, which will be under the patronage of H.M. King Frederik, will include radio and electrical measuring equipment, radio components, radio and television apparatus and will demonstrate working television and music studios. Most of the products on show will be of Danish manufacture.

The Danish Radio plans to illustrate its progress over the past quarter-century and, at the same time, to give visitors an idea of what its future services will be like. The television studio and the music studio will be built round an auditorium capable of holding 1,000; during the afternoons and evenings, performances will be broadcast from these studios.

On the Skyline

THE B.B.C. Outside Broadcasting Department arranged an ambitious coverage of the first post-war R.A.F. Pageant at Farnborough.

There were two major operations in the pageant. The first, which was broadcast in the Light Programme on July 7th, reconstructed an attack, based on the Amiens Prison raid, in which a squadron of low-level Mosquitoes breach the prison wall. Arms are dropped to the escaping prisoners who are then evacuated by helicopter and glider. Raymond Baxter was in the glider to give listeners his impression of the scene as his aircraft was towed in and, later, snatched off the ground by a Dakota. John Ellison was reporting from one of the Mosquitoes and Wynford Vaughan Thomas was on the ground to describe, amongst other things, the aerial combat when the fighter cover to this operation was engaged by "enemy" fighters.

The pageant's second feature, broadcast in the Light Programme on July 8th, consisted of a mock attack on the airfield by Mosquito aircraft bombing from 5,000ft. Charles Gardner was in one of the Mosquitoes, which was later intercepted by a squadron of Meteors taking off at high speed from the airfield. Raymond Baxter was in a Meteor and Wynford Vaughan Thomas again reported from the ground.

All three airborne commentators have served in the R.A.F. John Ellison was a pilot before the war; Charles Gardner flew with Coastal Command and Raymond Baxter was a fighter pilot. Wynford Vaughan Thomas of Anzio fame has been co-opted into this ex-service team.


New Radio Control

A NEW form of radio control was recently demonstrated at Portsmouth. A high-speed sea-going launch, designed as a bombing target for the R.A.F., was put through complicated evolutions up to a distance of eight miles by means of a control which operates by musical tones. It is claimed by the inventor, Mr. F. Parfitt, that this type of equipment which has only five buttons can give complete control and cannot be jammed. The launch, incidentally, is armour plated and unsinkable.

Suppression of E.H.T. Radiation Interference

WITH the extension of television transmission to the Midlands area last December, the problem of interference to normal radio reception by television receivers reached major proportions.

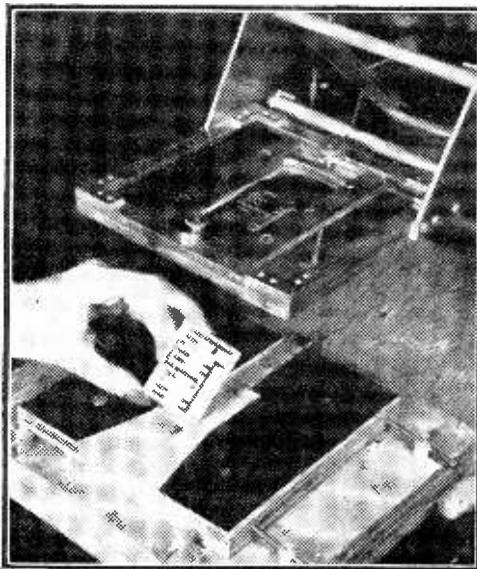Although the trouble originates in the line time base circuit, the associated circuits also radiate, including in a number of cases the wall coating of the C.R.T. itself. It soon became apparent that



A "wired" chassis. The main part of the American miniature receiver in which wiring, resistors, etc., are all chemically printed with oxide silver paint on ceramic.

screens around individual components were not effective, and the only satisfactory method found was a screen around the whole receiver.

In the course of the investigation into this problem Messrs. Acheson Colloids Limited were approached and a special product was developed for the purpose.

The product in question, "dag" Dispersion 479, is a quick-drying water-based paint designed to be brushed on the inside of the cabinet. Tests show that a radio receiver will operate satisfactorily, even on the long-wave band, only a few feet away from a treated television set.

Those interested are asked to write for further technical information regarding the use of Dispersion 479 to Messrs. Acheson Colloids Limited, 18, Pall Mall, London, S.W.1.

Grounds for Divorce

LISTENING on his own frequency on his car radio receiver whilst travelling home recently, an American heard his wife talking over his transmitter to another amateur. As a result of what he overheard he has filed a petition for divorce, citing the other amateur.

Phase-shift Audio Oscillator

A Useful 'Wide-range Instrument Built from "Junk-box" Spares

By J. C. FLIND

THIS simple oscillator covers, in three steps, frequencies from about 40 cycles per second right up to and beyond the limits of audibility. It gives a generous output, in the region of three volts peak, and this remains remarkably high over the full range of frequencies.

The stability of frequency is excellent, and over the range quoted the wave-form produced is good enough for most purposes, but if some measure of distortion can be tolerated a little adjustment of the preset controls (VR3 and VR4) will further extend the lower limit down to about 20 c/s.

The instrument works entirely from batteries, so that the bugbear of mains hum is avoided, and as radio-frequencies are not employed and the circuit includes no inductors, there is no need for screening. Nearly all the components comprised in the brief list of parts are standard items, and, together with the two valves, which are general-purpose two-volt triodes, they will be found in almost every amateur's collection of discarded spare parts.

From the circuit diagram, Fig. 1, it will be seen that V2 is driven by V1 through a conventional R/C coupling, and that negative feedback is applied from the anode of V2, via the blocking capacitor C3 and the potentiometer formed by VR3 and VR4 (VR4 is the cathode bias resistor, common to both valves) to the point marked (B), the cathode of V1. Simultaneously, positive feedback is applied to the point marked (C), the grid of V1, this time through the potential dividing network VR1-C1 and VR2-C2.

The conditions required for the maintenance of oscillation are (a) that the positive feedback at (C) should exceed the negative feedback at (B), and (b)

that the voltages which appear at these two points should be in phase with one another. As regards the first requirement (a), it will have been noted that VR3 and VR4 are variable, and once the optimum setting for VR4, which sets the grid bias voltage, has been determined, VR3 can be adjusted in its turn to decrease the negative feedback to the point where oscillation commences. When we consider (b), however, the position becomes more complicated. Both the points (B) and (C) are fed from the point marked (A), which is common to both positive and negative feedback circuits: (B) is in a purely resistive arm, so that at all frequencies of oscillation it will be exactly in step with the point (A). The positive feedback point (C), however, lies on an arm containing both resistance and capacity, which in the "upper" part are in series, while in the "lower" section they are arranged in parallel. It can be shown mathematically that for any given set of values for VR1, VR2, C1 and C2 the points (A) and (C) will be in phase at only one frequency. Accordingly, by making these values variable, the frequency at which the circuit as a whole will oscillate can be fixed.

Obviously, if the degree of positive feedback obtaining at the point (C) is not to be unduly disturbed, the upper and lower sections of the potentiometer VR1-C1—VR2-C2 must be varied simultaneously: the most economical and convenient way of arranging this, while giving adequate range coverage, is to provide for C1 and C2 each to consist of three capacitors, selected by means of a two-pole

LIST OF COMPONENTS

Resistors :

- 2 x 5,000 ohms.
- 2 x 50,000 ohms.
- 1 x 25,000 ohms.
- 1 x 500,000 ohms.

Capacitors :

- 2 x .0001 μ F.
- 2 x .001 μ F.
- 2 x .01 μ F.
- 2 x .1 μ F.
- 1 x .5 μ F.

Variables :

- 1 x double—1 megohm.
- 1 x 2,000 ohms.
- 1 x 100,000 ohms.

Switches :

- One 3-way 2-pole Yaxley.
- One single-pole on-off.

Valves :

- Two general-purpose two-volt triodes.
- Terminals, control knobs, resistance wire, systofex, etc.

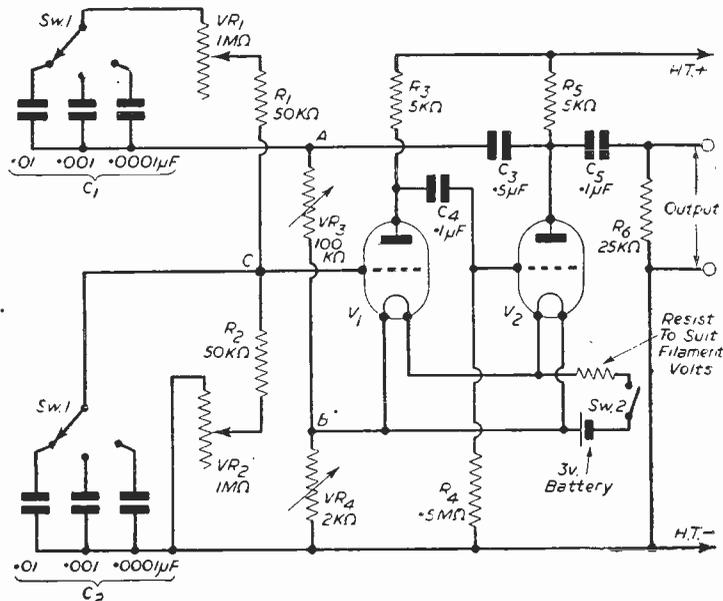


Fig. 1.—Circuit Diagram.

three-way Yaxley switch, while VR1 and VR2 are continuously variable resistors, ganged or geared together. (It so happens that at the time of writing a very suitable component, consisting of a pair of 1-megohm carbon potentiometers, mounted on a common spindle, is offered at 2s. 6d. by Radio Clearance, Ltd., of Tottenham Court Road, London, W.1.)

Ranges

The values chosen for C1 and C2 will depend to some extent on the characteristics and condition of the valves employed: in the author's instrument values of .01, .001 and .0001 μ F provided ranges running respectively from 40-300, 200-2,000 and 1,500-25,000 cycles per second.

The oscillator is intended to feed into a relatively high impedance, such as the grid circuit of an amplifier, and the purpose of the 25,000 ohms resistor placed across the output terminals is to minimise the effect which the varying input impedances of different amplifiers might have on the calibration. If required, however, the instrument will give a good account of itself in conjunction with an ordinary pair of headphones, preferably in series with a resistor of, say, 50,000 ohms. The oscillator described could, of course, easily be combined with an amplifier and built-in speaker to provide a complete unit, but to ensure freedom from back-coupling the amplifier should have two stages, the first giving low gain but acting as a "buffer."

In the prototype instrument as described space has been found for a No. 800 cycle lamp battery which supplies current for the valve filaments—of course, through a short length of resistance wire which takes care of the surplus 0.8 volts given by the battery. This self-contained L.T. battery is doubly convenient, as besides saving one pair of

external leads it makes it a simple matter to keep the L.T. and H.T. supplies separate—it will have been noted from the circuit diagram that H.T. and L.T. negative poles are not directly connected to one another.

If a pair of 1.4 volt miniature valves should be to hand, a very neat "self-contained instrument could be made up with both batteries inside the case: the modern small layer-type H.T. batteries would be suitable, as even with the older 2-volt

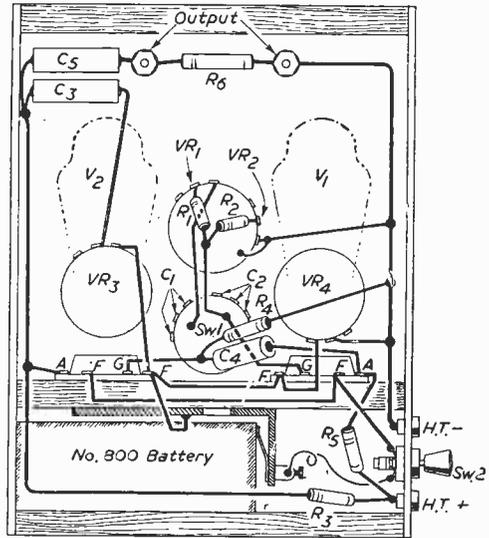


Fig. 3.—Wiring Diagram.

valves the anode current consumption does not exceed 3 milliamperes.

Constructional Notes

Layout is not at all critical, but as high values of resistance are employed in the control circuits some care should be taken to maintain a high standard, of insulation and to avoid leakages. It will be found advantageous to bond the metal cases of VR1 and VR2 to the "earth" line.

The original model was built up in a wooden box, 7½ in. x 5½ in. x 2½ in. deep, whose plywood bottom provided the panel. A partition of ¾ in. thick wood makes one wall of the battery compartment and serves, at the same time, to carry the valves mounted in old-fashioned baseboard-type holders: it will be found that if the valves are positioned well away from the panel, there will be room underneath them for the two variable resistors VR3 and VR4. The scale fixed to the panel can consist of a piece of thin, white card or ivory, and should be marked to show the three positions of the selector switch SW1. The scale traversed by the cursor fitted to the fine-frequency control knob operating VR1 and VR2 can conveniently take the form of three concentric circles, and the cursor itself can be a piece of thick celluloid fastened with cement to the underside of a skirted-type knob and scribed with a hairline. This ensures that the whole

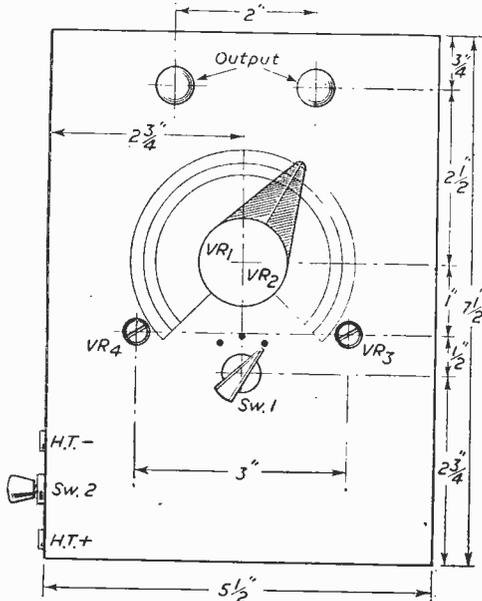


Fig. 2.—Panel Layout.

of each of the three scales is always visible. There are no scale markings for the controls VR3 and VR4, as these will not often need to be touched: the spindles, which protrude through the panel, are cut off short and slotted for adjustment with a screwdriver.

Brass contact pieces for the battery are bent to shape and screwed to the partition. It will be found that with the battery in position there is a spare space of about 2 in. \times 1½ in., and this is used to house the on-off switch and the resistance wire in circuit with the valve filaments, which is threaded through a short length of "systoflex." The sockets for the two leads to the H.T. battery are also brought in here, and in the original model, in order to leave more room for the "control" components, the anode resistors and the components forming the coupling between the valves have all been kept on the battery side of the partition. The anode resistors, by the way, have been kept to the low figure of 5,000 ohms in order to minimise the risk of distortion; even so, the output is quite high enough for most requirements.

Now with regard to the two sets of capacitors forming C1 and C2. These should, of course, be good quality components, preferably mica types, and it is suggested that for convenience the switch-and-capacitor assembly should be "prefabricated." That is to say, the six capacitors should be soldered to the appropriate tags of the switch and finished off with four flying leads, for connection to VR1, R1/R2, VR3 and H.T. negative respectively, and that only then should the switch be fixed in position on the panel. The six capacitors have been omitted from the wiring diagram (Fig. 3) in order to avoid confusion.

V.H.F. Constant Impedance Attenuators

THE problems of variable attenuator design for accurate V.H.F. measurements have been a subject of scientific research since the beginning of the high-frequency era in communications. The familiar techniques employed in designing constant impedance attenuators for use in voice-frequency and carrier-frequency ranges have so far failed to afford the same degree of precision when applied to the V.H.F. range. In this range, unavoidable wiring and resistor reactances coupled with mutual impedances within the attenuator become significant and cause a marked deterioration in performance.

First in the field to meet what has in some quarters become an urgent need for a medium-priced, constant impedance, variable, V.H.F. attenuator in the range up to 50 Mc/s. is Standard Telephones and Cables, Limited. These attenuators set a new standard of performance in the V.H.F. range. Two models for use in 75-ohm circuits are available. One model, variable in 1 db. steps, gives a maximum insertion loss of 9 db. The other, variable in 10 db. steps, provides a maximum insertion loss of 90 db. Both models can be used in tandem and will handle up to ¼ watt input. They are ready for building into customers' own equipment.

Of practical importance and interest to laboratory

Operation

When the instrument has been completed, connect the output terminals to an oscilloscope or a suitable amplifier, plug in to an H.T. battery giving about 100 volts, and switch on. Set SW1 to the middle range and the control of VR1 and VR2 to about the centre of the scale. A little manipulation of VR3 and VR4 should very soon produce a strong "signal" at about 400 c/s.; the fine-frequency control should then be operated to make sure that connections have been made the right way round; it may be necessary to reverse some of the leads.

VR4 should next be adjusted for maximum output and, following this, VR3 should be turned back until oscillation ceases, after which it should again be advanced until the note is heard again. It will be found that if this setting is kept to the minimum, the wave-form is improved. Before deciding on the final setting for V3, make sure that oscillation is maintained on all ranges, as inadequate feedback will cause the oscillations to collapse at the lowest frequencies.

Accurate calibration really demands the use of an oscilloscope but, with care, a good deal can be done by aural comparison with another calibrated source (or even a piano), relying on the ear to detect the unwanted harmonics which indicate a marked departure from the basic sinusoidal wave-form.

This little oscillator will be found invaluable in checking the performance of amplifiers and speakers, and the effect of insertion of various forms of filters and tone-controls. It will also provide a means of tracking down those mysterious buzzes and reverberations which so often spoil the performance of powerful high-fidelity equipment when used in ordinary living-rooms.

engineers and others engaged in making accurate measurements, is the information that the maximum deviation from nominal loss at D.C. does not exceed ± 0.05 db. for any setting on the 0.9 db. model. On the 0.90 db. model, the insertion loss error does not exceed ± 0.06 db. for the 10 db. setting, rising linearly to a value not exceeding ± 0.3 db. for the 90 db. setting.

In keeping with this accuracy of adjustment, the high-frequency performance is quite remarkable. The total insertion loss error at 50 Mc/s. (inclusive of D.C. errors as above) will not exceed ± 0.05 db. for the 1 db. setting, rising linearly to a value not exceeding 0.15 db. for the 9 db. setting. On the 0.90 db. model, the total insertion loss error at 50 Mc/s. (inclusive of D.C. errors) does not exceed ± 0.1 db. per step. The above insertion loss errors are, in all instances, relative to zero db. setting.

Individual calibration charts for the frequencies up to 100 Mc/s. for the 0.9 db. model and 60 Mc/s. for the 0.9 db. model can be supplied.

TWO NEW EDITIONS

"PRACTICAL WIRELESS" CIRCUITS

15th Edition

WIRELESS COILS, CHOKES & TRANSFORMERS

8th Edition

6/- or 6/6 by Post from

GEORGE NEWNES, LTD., Tower House,
Southampton Street, Strand, London, W.C.2.

Negative Feed-back

Some More Details of a Modern Circuit Arrangement

By ERIC LOWDON

TO many amateurs there is something slightly sinister about negative feed-back—an air of mystery that savours more of the black arts than the down-to-earth business of radio circuitry. For instance, the valve manual may give the A.C. resistance of a valve as being X ohms, but put it in a circuit with negative feed-back and, as the amateur has read, the Ra may appear to be much higher, say Y ohms; or to add to his bewilderment he may have read somewhere that negative feed-back makes the Ra much lower, say Z ohms.

appearing between grid and cathode, and Vo the volts output.

In this article the D.C. components in the circuit are ignored, and we are dealing only with A.C. signal currents and voltages. Since C1 and C2 will form short circuits to A.C. (assuming negligible reactance) the circuit can be redrawn as shown in Fig. 1b. It will now be seen that so far as the output is concerned, RL is effectively in parallel with the valve, and the effective grid-cathode signal input is the same as Vi.

But there is still one component that is quite invisible, and that is Ra, the A.C. resistance of the valve. In order to complete the picture, then, we can replace the valve with a generator and series resistance Ra; this is shown in Fig. 1c. Thus we have evolved a circuit that is equivalent in every way to that in Fig. 1a, so far as signal voltages and currents are concerned. Note: it is usual when employing this artifice to label the generator output-voltage as μV_g , that is, the amplification factor of the valve multiplied by the grid-cathode input volts; for the purpose of this article it will be more convenient to call it E as has been done in the diagram.

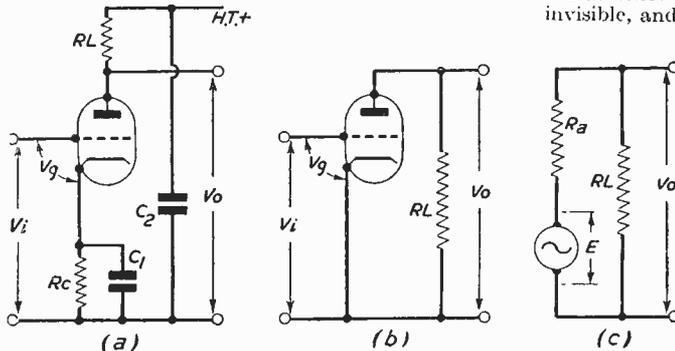


Fig. 1.—Diagrams illustrating the evolution of the equivalent circuit.

It seems that the valve manuals can't be believed any more; the Ra of a valve with negative feed-back may be X ohms, Y ohms, Z ohms or anything you like; in fact, it can be X, Y, and Z ohms at the same time.

Does the Ra really jump about in this mysterious fashion? If so how does negative feed-back operate on the valve? Before we go further, here is a clue; there are two kinds of feed-back (negative is understood from now on), current feed-back and voltage feed-back. One causes the Ra to increase—or so it seems—and the other causes an apparent decrease; perhaps this makes things seem a little more reasonable. Incidentally, neither of these two types feed back current, they both feed back voltage—here we go again!

In actual fact, this question of variable Ra and its effect on the circuit is not difficult provided you look at it in the right way. To answer it we have to consider the relationship between the load resistance RL and Ra.

Amplifier without Feed-back

To begin, then, let us consider a simple amplifier circuit without feed-back as shown in Fig. 1a, where RL is the anode load resistance, Rc the cathode bias resistance, C1 the cathode bypass capacitance, and C2 all the capacitance that usually appears between the HT end of RL and earth—decoupling, smoothing, and stray capacitance, etc.; Vi is the input signal volts, Vg the signal volts

of $E/Ra + R$ amps (ohms law) round the circuit. It will be immediately obvious that if Ra and E are constant, then a given variation of RL will cause the current in the circuit to vary by an amount dependent on the relative values of Ra and RL. If Ra is very large compared with RL then even a large variation of RL will have only a small effect on the current; on the other hand, if Ra is small relative to RL then a large variation in RL will cause a big variation in current.

The effect on the voltage developed across RL is

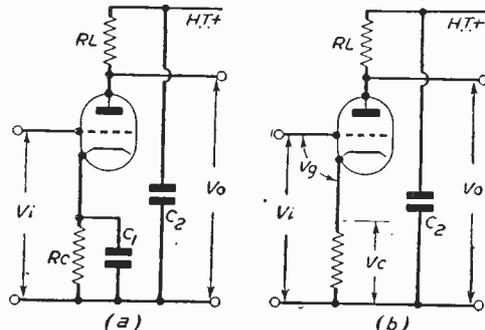


Fig. 2.—Simple amplifier and modification to introduce N.F.B.

no less obvious. In the first case, that of the high R_a , the current variation is small and therefore the change in voltage across R_L will be nearly proportional to the change in its resistance; if, for instance, the resistance of R_L is halved so also will the voltage across it be nearly halved. In the second case, where R_a is very low compared with R_L , change in the resistance of R_L will result in a current variation very nearly proportional to the change in resistance; that is to say, if R_L is halved the current will be nearly doubled and the voltage across the resistance will be maintained more closely to its original value.

A few figures will illustrate this: Suppose that E is 100, 20,000 ohms for R_a , and 5,000 ohms for R_L then,

$$I = E/R_a + R_L \\ = 100/20,000 + 5,000 = 100/25,000 = .004 \text{ amp.}$$

and the volts developed across R_L , call it V_o , will be,

$$V_o = I \times R_L = .004 \times 5,000 = 20 \text{ volts.}$$

If R_L is now halved the circuit current becomes .0044 amp. and the volts drop across the new value of R_L is 11 volts.

Now suppose R_a to be small compared with R_L , thus: E equals 100 volts, R_a equals 1,000 ohms, and R_L equals 5,000 ohms. Calculating in the same way as above we have .0167 for the current and 83 volts across R_L . When R_L is halved, the current becomes .0285 amp. and the volts drop across R_L is 71 volts.

It is seen, then, that the effect of a comparatively high R_a is to cause a large variation in output volts with change in R_L , and a comparatively low R_a tends to maintain the output volts with change in R_L . Armed with this knowledge we can now give our attention to negative feed-back.

Current Feed-back

In Fig. 2a, we again have our simple amplifier circuit in which the input volts are applied between grid and earth, but since C_1 presents a short circuit to A.C. the input is effectively between grid and cathode. Now look at Fig. 2b.

Here the bypass condenser has been removed, and this simple alteration makes a remarkable difference to the working of the circuit. The input signal V_i is no longer applied directly between grid and cathode, but is in series with the cathode voltage V_c and in opposition to it. The effective grid-cathode voltage is therefore $V_i - V_c$. (Don't forget that we are concerned only with signal voltages; D.C. voltage conditions are being ignored.)

A little thought will show that this is so, for if the grid is moving in a positive direction with respect to earth, then the current through the valve must be increasing and the cathode must also be moving positively. If we assume that the grid has moved 5 volts positive and the cathode 2 volts positive, then the grid has moved 3 volts more positive than has the cathode.

Since the valve is only interested in the volts which appear directly between its grid and cathode, it will be obvious that only three volts of the five volts input are effective in producing an output. The other two volts are employed in neutralising the two volts increase across R_c .

This is negative feed-back and since V_c depends on the current through R_L it is called current feed-back.

The first most noticeable effect of current feed-back, then, is to reduce the output for a given input, but as this can hardly be classed as an advantage there must be some other reason for its adoption in amplifiers. In actual fact, it not only reduces the gain of the circuit but also reduces the harmonic distortion generated within the valve in the same ratio, and this is, of course, a decided asset.

However, don't let this fact encourage you to nip the bypass capacitor out of your amplifier output stage, for as we shall see in a moment, current feed-back is particularly unsuitable for this part of the circuit.

Current Feed-back and R_a

Turning again to Fig. 2b, let us suppose that the valve has a fairly low R_a compared with R_L . If R_L is now reduced to, say, half its original value, then the signal current in the valve and therefore through R_L and R_c will increase, and the feed-back voltage V_c must also increase because the voltage drop across R_c will be greater. The effective grid-cathode volts $V_i - V_c$ will thus decrease giving rise to a decrease in output current which tends to balance out the original current rise due to the smaller value of R_L . The current is therefore maintained at somewhere near its original value, but since R_L has been reduced by half so then will the output volts be reduced proportionately. This as we saw earlier in the article (Fig. 1c), is exactly what happens in a non-feed-back circuit where the valve has a very high R_a compared to R_L .

In this case then current feed-back has effectively converted our low R_a into a high R_a so far as change in anode load is concerned. As any high-quality enthusiast will tell you, this is far from the ideal state of affairs required in an output stage where the load is a loudspeaker whose impedance varies with frequency. If the R_a of the output valve is high then the output will vary with frequency and result in distortion. Another important reason why the R_a should be low is that since the reproducer is effectively in parallel with the valve, a low R_a will assist in damping out unwanted natural resonances in the speaker.

For these reasons current feed-back is never used in the output stage of an amplifier, though it may find important uses in other parts of the circuit.

Voltage Feed-back and R_a

Turn now to Fig. 3. This will be recognised as the simple amplifier of Fig. 2a with the addition of a potential divider consisting of R_1 and R_2 connected between anode and earth—for the moment assume that the reactance of C_1 is negligible—and the portion of the output voltage V_a developed across R_2 , is connected in series with the input voltage V_i .

This is an example of voltage feed-back, so called because V_a is proportional to the output voltage across R_L and not, as in the case of current feed-back, to the output current flowing in R_L .

As before, the effective grid-cathode input voltage is the difference between the input volts and the feed-back volts—that is $V_i - V_a$. In this case, however, change in R_L has an entirely different effect on the apparent R_a of the valve.

(To be continued)

On your Wavelength

by THERMION

The Saucepan Special

I CERTAINLY rabbed my eyes the other day when there dropped on to my desk a booklet issued by the Director of Information of Lusaka, Northern Rhodesia entitled "Report on the Saucepan Special," which is described as the Poor Man's Radio for Rural Populations. The report has been written at the request of the Director of Information Services of the Colonial Office because the success of the cheap wireless set for Africans in Central Africa will be an important factor in decisions which have yet to be made in other colonies on the establishment of broadcasting organisations.

The Saucepan Special, a receiver of British manufacture, has been enormously successful in Africa. It has been bought in considerable numbers and it is already having the effect upon Africans that it was meant to have, as an instrument of mass education. The Saucepan Radio is a simple, but efficient, short-wave receiver operated by an



The "Saucepan" Special.

external dry battery of 90 volts H.T. and 1½ volt L.T., giving 300 hours' service.

The cabinet of the receiver is in effect a large aluminium saucepan (without handle) of 9in. diameter with a back plate attached by screws and sealed, and a gauze-covered opening at the front of 4in. diameter. At this opening is the combined

on-off switch and volume control and below it the two-speed tuning control and tuning dial. There is no tone control or other refinement. The set stands on black bakelite knobs, the tuning dial is white; the appearance of the receiver is more attractive than one would imagine. It is painted blue since research in the various colonies in Africa revealed the fact that one tribe or another had some kind of superstition about almost every other colour. The back plate is tight fitting and the three holes in it are gauze-covered, so that the set is entirely insect proof. It is also tropically finished throughout. The receiver is a formal (though simplified) four-valve superhet type. Its range is from 25 to 90 metres. The aerial and earth wires are attached to the set, and it is important that the earth system should be used with this receiver. Before the sets are distributed a small copper plate is soldered on to the earth wire which should be buried about 9in. in the ground.

The receiver and the battery, which is about 8in. by 3in. by 5½in., each weigh just over 7lb.

The aerial wire supplied could with advantage be lengthened.

I understand that the manufacturer is working on a very low margin of profit, relying upon large sales. The government had agreed to suspend customs on all radios of not more than £4 f.o.b. U.K. value. At present there is no system of wireless licences in Africa! I must examine one of these receivers.

Radio Book Reviews

WHY is it that the B.B.C. seldom, if ever, review technical books? There are as many, if not more, readers of technical books to-day than there are of fiction and biography. Five years of war compelled most people to acquire technical knowledge in a wide range of subjects, and the technical book industry in this country has expanded enormously in consequence. One would imagine from the radio book review feature that no one in this country read anything of a technical nature. The newspapers are also remiss in this respect. The B.B.C. and the newspapers are ignoring a feature which would have a very popular appeal. Technical books are expensive to produce, and at a time when the spread of technical education is a matter of national concern, I should have thought the B.B.C. would have been the first to draw attention to important technical works. I know that the B.B.C. boys read this feature, so perhaps I am making a suggestion which they will adopt. Obviously the books would have to be reviewed by a person with technical and scientific, as distinct from literary qualifications. The view seems to be at present that unless the book is a simple one, telling you how to ride a bicycle or paper a wall without dabbing it here and dabbing it there it is of no interest to the public.

For the Experimenter-2

More Experiments in Electromagnetic Induction

By "MICRON"

AT first, when the signal-amplitude is small, rectification will take place around the bend of the characteristic—where the curvature is large, and *varying*. In this region, it will be far from true to say, " I_o is directly proportional to E_g ." The rectification will be "out of proportion," or *non-linear*, causing much distortion in the shape of each half-wave of anode current.

If the experiment is carefully carried out, the effect at the bend will be shown by slow, and *unequal* increments in the meter readings for given changes in volume control settings. When the amplitude of E_g is sufficient to take the peak considerably into the straight part of the characteristic, i.e., much above the bend, I_o will become nearly directly proportional to the signal input: an important requirement of distortionless detection.

Valve Voltmeters ; "Radio Controls"

The fact that we do get a D.C. component from a rectifier suggests construction of numerous useful pieces of apparatus.

The milliammeter will be an accurate tuning-indicator if the received signal is strong enough to give a readable indication—or previous H.F. stages make it strong enough. Thus a tuning condenser may be calibrated in wavelengths or frequencies, making a "wavemeter."

Plotting calibration curves for condensers (when used with various coils) will be a useful series of experiments in themselves. Broadcast frequencies are exact within very close limits for this purpose. The actual shape of graph connecting wavelengths

(or frequencies) with dial settings will depend on the "law" of a given condenser—which provides another line for investigation.

One important advantage of the "lower anode bend" type of detector over all others is the extremely high impedance of the valve grid cathode circuit—equivalent to an open-circuit or "infinite impedance" at low frequencies. This is especially advantageous in valve voltmeters which may be used to show high-frequency voltages existing across other high-impedance R.F. circuits where any appreciable shunting effects would be serious.

Our anode-bend rectifier is in effect a "valve voltmeter." An " E_g " of 50 c/s or even 5 Me/s. frequency is made to give a readable indication on a D.C. moving coil instrument. If we have accurate means of measuring the R.M.S. voltages applied at 50 c/s., a calibration curve may be drawn connecting milliamp readings with R.M.S. volts, and this will remain reasonably correct up to fairly high radio-frequencies.

The "law" of a valve voltmeter (as shown in the calibration curve) will depend whether it is worked over a linear or non-linear part of the characteristic. Once calibrated, of course, the same valve, the same bias, H.T., and filament voltages must be employed as in calibrating.

If a fairly sensitive relay is substituted for the milliammeter, we have possibilities for fascinating experiments in "radio control." Extremely weak signals from a transmitter thousands of miles away (or stronger ones from a local oscillator) could first be amplified by the H.F. stages of a receiver, and applied to grid-cathode of the detector stage. The relay would close under the action of the resulting " I_o ," and could be arranged to initiate all sorts of things—switch-on lights, ring bells or buzzers, control models, etc. etc.

Signal Detection

A next step should be to study what is taking place in the detector when receiving a modulated H.F. carrier.

The emphasis we have put on the "D.C. component" (I_o) should make the matter perfectly clear. Instead of remaining at a fixed value, I_o will start "swinging" up and down at audio-frequency as illustrated in Fig. 6. This is because the amplitude of each rectified "pulse" of anode current is different, Fig. 6b, hence so will the successive average values.

Yet, if the rectification is "linear," a milliammeter will continue to register the *steady* I_o .

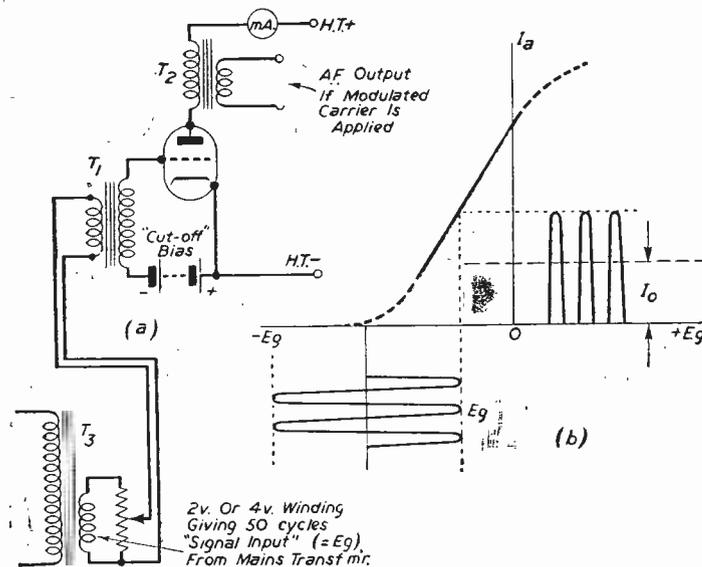


Fig. 5.—Demonstrating "Anode Bend" Detection with a Milliammeter.

A moving coil D.C. instrument cannot follow A.C. changes: it always stops at the "mean value," and if the current swings equally on both sides of I₀, the latter remains a constant "mean."

But if there is any non-linearity, it is possible—to mention one case—that I₀ will increase more at the crest of the modulation than it decreases at the trough, in which case there will be an *average increase* in I₀—the D.C. component rises from I₀ to I₀', say, the effect being to give a sharp upward "kick" in the milliammeter at modulation peaks.

With linear detection another fact may be gleaned from this. If we make sure of the D.C. component for any purpose—A.V.C. let us say—we shall have a current (or the resulting voltage

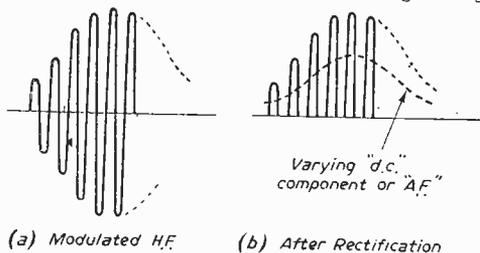


Fig. 6.—Rectification of a modulated signal. The D.C. component will now be varying at the frequency of the amplitude modulation.

developed across resistances) which depends only on the carrier amplitude, i.e., is independent of the modulation—a fact, of course, which can be observed in ordinary tuning indicators, or in A.V.C. (it would be a poor thing if A.V.C. bias varied with modulation).

Studying Mathematical "Laws"

We have already touched upon experimental studies of "quantities," with reference to valves, detection, valve voltmeters, and simple calibrations.

One difficulty here will be measuring equipment, though much can be done in improvising or making up permanently items such as valve voltmeters, rectifier instruments, frequency-measuring devices, low-frequency bridges, etc. The hobby will tend to become costly when developed along these lines, but many may think it well worth while.

Let us start with a job which calls for nothing more than a few coils, a condenser, and an ordinary or improvised receiver, a study of some of the "laws" connecting frequencies or wavelengths with inductance and capacitance values.

The "tuning-point" or resonant wavelength of an LC-circuit is given by:

$$\text{Wavelength (Metres)} = 1885\sqrt{LC}$$

where, $L = \mu H$,
 $C = \mu F$,

or,

$$\text{Frequency, } f(\text{kc/s}) = \frac{160}{\sqrt{LC}}, \text{ approx.}$$

If we omit the constants we may write:

$$\text{Wavelength } \lambda \propto \sqrt{LC}$$

$$\text{Frequency } f \propto 1/\sqrt{LC}$$

the sign "∝" signifying "is proportional to," or "varies as."

The important thing to note is that Wavelength (or Wavelength range) varies as the square root of the tuning capacitance; the Frequency varies *inversely*, as the square root. The same is true of L if C is kept constant.

Note: It is *not* correct to say, varies as the "square" of the tuning capacitance. Transposing the expression gives

$$C \propto \lambda^2,$$

$$\text{or } \propto 1/f^2, \text{ or } (1/f)^2.$$

Take a practical question. What range of wavelengths can be tuned by a variable condenser of 500 μμF. minimum capacitance?

You will know, of course, from the tuning dial of a M.W. receiver that the range is, roughly, 200m.-600m.—a ratio of about 3/1.

But the ratio, 500 μμF./50 μμF. is 10/1, or, as a more convenient figure, let us say 9/1. When the condenser vanes are "all in," the capacitance is *nine times* the minimum with the vanes "all out." Yet the wavelength range is only 3/1. In other words,

$$\text{Tuning range in metres} = \sqrt{\text{Capacitance Range.}}$$

$$= \sqrt{9/1} = 3/1.$$

Consider another question. If with a given coil, 200 μμF is required to tune to 1,000 kc/s, what value condenser will be necessary to tune to 1,200 kc/s?

The frequency ratio = 1,200/1,000 = 1.2/1.

Capacitance ∝ (1/f)², or inversely as (1.2/1)² = 1.44/1. Therefore, since a *smaller* C is required for tuning to 1,200 kc/s.,

$$C = 200 \mu\mu F / 1.44, \text{ or } 200 \mu\mu F \div 1.44 = 139 \mu\mu F.$$

As a preliminary experiment to check these fundamental proportions, suppose you have chosen a coil which should tune from 200m. to 600m. with a variable condenser of about 9/1 capacitance ratio. You make up some sort of receiver or insert this LC-circuit across aerial and earth of an existing receiver.

You find the tuning range is not 3/1, but something like 2/1. Perhaps you can tune-down to 200m. (depending on the coil used), but you cannot go higher than 400m. What accounts for this? Knowing the condenser values, how could you calculate the approximate value of the quantity involved? What is the remedy?

Book Received

"WILLIAMSON AMPLIFIER." Collection of articles on "Design for a High-quality Amplifier," by D. T. N. Williamson, formerly of the M. O. Valve Company, now with Ferranti Research Laboratories. Published April 20th, 1950, at 3s. 6d. (postage 2d.), for "Wireless World," by Iliffe and Sons, Ltd. Size 9 3/4 in. x 7 1/4 in. Thirty-six pages and 31 illustrations.

This 15-watt amplifier has gained world-wide recognition among quality-reproduction enthusiasts for its remarkably low harmonic and intermodulation distortion. The response curve is flat within 1 db. up to 10 kc/s. Direct coupling in the first stage helps to reduce phase shift, which is negligible over the range 10 c/s-20 kc/s.

Input for the main amplifier is 1.9 v. peak. With a simple record-compensated pre-amplifier it is 18 mV.; 1.3 mV. for use with microphones and under 1 mV. with a high-gain pre-amplifier.

The booklet gives full details not only of the basic circuit, but also of ancillary equipment recommended by the designer for high-quality reproduction of records and radio programmes. Circuits for correcting recording characteristics are included and also high- and low-pass filters, the latter variable. There is a fading control for reducing gain to zero when changing records; the rate of fading is automatically controlled.

Contents include: Introduction. Basic Requirements: alternative specification. Details of chosen circuit and its performance. Design data of new version. Design of tone controls and auxiliary gramophone circuits. Design for a radio feeder unit. Replies to queries raised by constructors.

Equivalent Circuits

An Important Aspect of the Set Designer's Work is Described Here

By E. N. C.

THIS article is intended to give the reader an insight into the methods used by designers in nearly all aspects of design work. With the aid of an equivalent circuit the designer's job is somewhat eased, partly because it removes a lot of circuitry which is not necessary in the process of designing, and also because an equivalent circuit often presents to him a clearer picture of what is happening. Let us take as a first example the

here is an equivalent circuit of the potential divider. Now consider the circuit of the potential divider. On the assumption that the 50 v. supply is being delivered by a generator having no internal resistance, if we switch off the generator without disconnecting it the terminal voltage would fall to zero and the generator or 50 v. supply has effectively been replaced by a short circuit. If we were now to look into the V_0 terminals we would see 5Ω in parallel with 10Ω that is $3\frac{1}{3}\Omega$, and if we switched the generator on we would look into $16\frac{2}{3}$ volts as previously calculated. Therefore as far as we are concerned we are looking into a generator of $16\frac{2}{3}$ volts output and having an internal resistance of $3\frac{1}{3}\Omega$, and we can therefore draw an equivalent circuit of the potential divider, as shown in Fig. 2.

If we now want to connect up the 4Ω load and calculate the current that will flow, all we do is divide the generator volts by the load + series resistance as follows:

$$I_2 = \frac{16\frac{2}{3}}{3\frac{1}{3} + 4} = \frac{\frac{50}{3}}{\frac{22}{3}} = \frac{25}{11} \text{ or } 2\frac{3}{11} \text{ amps.}$$

which is exactly the same answer as we arrived at before when we calculated it by the round-about method. We can see now that for any value of load resistance, which we will call R, the current that it will draw is given straight away

by the formula $I = \frac{16\frac{2}{3}}{3\frac{1}{3} + R}$ for that particular potential divider. You can prove this for yourself by trying several examples and working out the results by each method.

Simple Formula

The output voltage delivered by any potential divider can instantly be obtained by the use of a simple formula. We will derive the formula first, then we can see how easily it is applied. Consider the simple potential divider shown in Fig. 3, where actual values have been replaced by symbols.

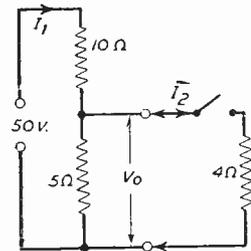


Fig. 1.—Simple potential divider circuit.

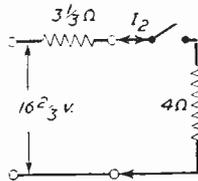


Fig. 2.—Equivalent circuit of Fig. 1.

simple potential divider, the circuit of which is shown in Fig. 1.

If we wish to know the output voltage a few simple calculations will show us as follows:

$$I_1 = \frac{50}{15} = \frac{10}{3} \text{ amps. } \therefore V_0 = 5 \times \frac{10}{3} = \frac{50}{3} = 16\frac{2}{3} \text{ volts.}$$

Now if we connect the 4Ω load to the output V_0 and we wish to know the circuit that will flow, how are we going to do it? It is no good saying that the current flowing is equal to $\frac{V_0}{4}$, because as

soon as we connect up the 4Ω load the output V_0 will fall to a new level because of the extra volts drop on the 10Ω top arm. The only way we can see so far is to go right back to the beginning and start all over again as follows:

$$I_1 = \frac{50}{10 + \frac{5 \times 4}{5 + 4}} = \frac{50}{10 + \frac{20}{9}} = \frac{50 \times 9}{110} = 4\frac{1}{11} \text{ amps.}$$

The output voltage V_0 is equal to the current I_1 multiplied by the 5 and 4Ω in parallel, and is,

$$\text{therefore, } V_0 = \frac{45}{11} \times \frac{20}{9} = 9\frac{1}{11} \text{ volts,}$$

instead of the previous $16\frac{2}{3}$ volts. We can now calculate the current flowing through the load, which is

$$\frac{9\frac{1}{11}}{4} = \frac{100}{44} = 2\frac{3}{11} \text{ amps.}$$

Varying Loads

Now if we want to connect up different loads and calculate the load current in each case we would be letting ourselves in for a lot of unnecessary work. What we want

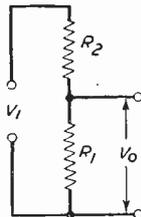


Fig. 3.—Potential divider circuit without values.

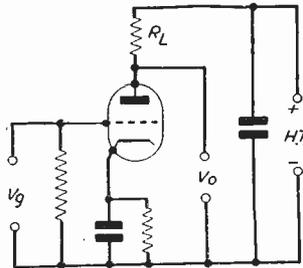


Fig. 4.—Single-stage voltage amplifier.

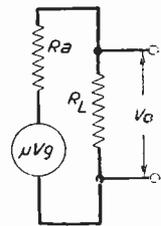


Fig. 5.—Equivalent circuit of Fig. 4.

The current flowing into the divider as a result of the applied voltage V_1 is $I = \frac{V_1}{R_1 + R_2}$ and the output voltage V_0 is equal to the current multiplied by the resistance R_1 , so

$$V_0 = I R_1 = \frac{V_1}{R_1 + R_2} \times R_1 \therefore V_0 = V_1 \frac{R_1}{R_1 + R_2}$$

We can see how this applies to our first potential divider merely by replacing the symbols by their true values as follows:

$$V_0 = 50 \times \frac{5}{10 + 5} = \frac{250}{15} = 16\frac{2}{3} \text{ volts.}$$

The effective output resistance, or internal resistance as it is often called, is straightway got by the formula $R_0 = \frac{R_1 \times R_2}{R_1 + R_2}$ and substituting real values $R_0 = \frac{5 \times 10}{5 + 10} = 3\frac{1}{3} \Omega$.

These formulae and the equivalent circuit then show us, in the shortest time, the capabilities of any potential divider whose arms are composed of components where voltage and current bear a linear relationship.

Valve Equivalent Circuits

Let us now consider another type of equivalent circuit which is much used, that of the thermionic valve. Fig. 4 shows the circuit of a triode valve connected up as a voltage amplifier. Now before we look at the equivalent circuit of Fig. 4, let us consider one of the fundamental properties of the valve, its amplification factor, or μ . μ is defined as the change in anode volts divided by the change in grid volts, the anode current being maintained constant. This, therefore, means that if an alternating potential is applied to the grid such that it does not overload the valve, an alternating potential would be developed between anode and cathode which would be μ times as great; and as the valve has an A.C. anode cathode impedance designated R_a , this impedance can be reckoned as being in series with the alternating potential μV_g .

It is quite logical then to draw the equivalent circuit as shown in Fig. 5. Here all the irrelevant things such as H.T. supply, cathode biasing, valve symbol, have been removed.

When I say irrelevant, I mean irrelevant as far as design procedure is concerned, because we already assume that the valve is operating under correct conditions.

The equivalent circuit (Fig. 5) shows the valve

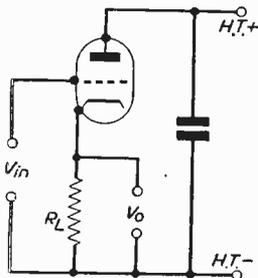


Fig. 6.—Basic cathode follower stage.

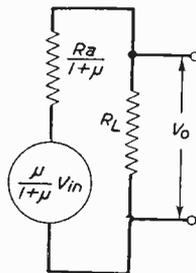


Fig. 7.—Equivalent circuit of Fig. 6.

and its circuitry as being equivalent to a generator delivering an A.C. output voltage μV_g and having an internal impedance equal to R_a of the valve. This generator is feeding the anode load R_L across which the output voltage V_0 is developed. The usefulness of the equivalent circuit can readily be appreciated when we calculate one of the most important things, the stage gain. Now considering it as a potential divider we saw from a previous formula that the output voltage from a potential divider composed of two arms and being fed with a voltage V was $V_0 = V \frac{R_1}{R_1 + R_2}$ and substituting μV_g for V and R_a and R_L for R_2 and R_1 we have $V_0 = \mu V_g \frac{R_L}{R_a + R_L}$. Now the stage gain is equal to the output voltage divided by the input voltage, therefore the stage gain which we will represent by the letter $A = \frac{V_0}{V_g} = \frac{\mu R_L}{R_a + R_L}$, a very well-known formula.

Cathode Follower

The cathode follower has an equivalent circuit which is often used in analysing its performance. Fig. 6 shows the basic circuit of a cathode follower stage.

The only fundamental difference between the

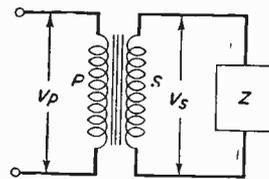


Fig. 8.—Standard transformer circuit.

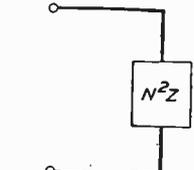


Fig. 9.—Equivalent circuit of Fig. 8.

cathode follower and the normal amplifier as far as circuitry is concerned is that the load R_L has been moved from the anode circuit and placed in the cathode circuit; but this simple change considerably modifies the performance of the stage so far as concerns gain, output impedance and input impedance. Fig. 7 shows the equivalent circuit of the cathode follower stage, and one can readily see the difference between it and the normal triode amplifier by merely comparing their equivalent circuits.

Here the valve and its circuitry have been replaced by a generator delivering a voltage $\frac{\mu}{1 + \mu} V_{in}$ and having an internal impedance of value $\frac{R_a}{1 + \mu}$.

One can see that the effective generator voltage for the same value of input volts is considerably less than that of the normal amplifier (Fig. 5), but we also see that it has a much lower internal impedance, and this is an advantage because it means that the cathode follower will feed into circuits of low input impedance. The cathode follower also has a very high input impedance, and these two factors make it very suitable for such applications as a buffer stage in oscillators or an output stage in pulse generators, etc. Now with the aid of the equivalent circuit and our previous potential divider formula

we will calculate the stage gain of the cathode follower as follows:

$$V_o = \frac{\mu}{1+\mu} V_{in} \cdot \frac{R_L}{R_a + \frac{R_L}{1+\mu}}$$

Multiplying top and bottom by $(1+\mu)$ we get

$$V_o = \frac{\mu V_{in} R_L}{R_a + R_L (1+\mu)}$$

and the stage gain which equals $\frac{V_o}{V_{in}} = \frac{\mu R_L}{R_a + R_L (1+\mu)}$.

Another well-known formula.

Transform

Let us take as a last example the transformer. In order to ease the calculation and make the subject more easy to grasp we will consider the transformer to be perfect, which means that unlike practical transformers this transformer will have no magnetising current, no leakage inductance, no D.C. resistance, etc., and will therefore be 100 per cent efficient. These assumptions are often made when dealing with the transformer simply. Fig. 8 shows our transformer, which in this case is a step-down transformer, such as a speaker transformer.

The secondary has connected across it an impedance Z which could well be the speech coil of a loudspeaker.

We will calculate the effective impedance one would see looking into the primary terminals as a result of the load Z being placed on the secondary. Now calling this imaginary reflected impedance Z_p and remembering that in a 100 per cent. efficient transformer the primary watts will equal the secondary watts the following formula is obtained

$$V_p^2 = \frac{V_s^2}{N^2} \text{ where } V_p = \text{primary volts and } V_s = \text{secondary volts. Rearranging we get}$$

$$\frac{Z_p}{Z} = \frac{V_p^2}{V_s^2} \therefore Z_p = \frac{V_p^2}{V_s^2} Z \text{ and as } \frac{V_p^2}{V_s^2} = N^2$$

where N is the transformer ratio we have $Z_p = N^2 Z$. We could therefore represent the transformer by the equivalent circuit of Fig. 9, which shows an impedance of value $N^2 Z$, and that is the effective impedance the output valve in a radio set would see if the transformer were placed in the anode circuit. Incidentally, the transformer ratio necessary to match an output stage to a speech coil can be calculated from the last formula because as one can see, if $Z_p = N^2 Z$ then $N^2 = \frac{Z_p}{Z} \therefore N = \sqrt{\frac{Z_p}{Z}}$

where Z_p equals the anode impedance of the valve and Z equals the speech coil impedance.

Marine Radar

THE Kelvin Hughes Marine Radar Type 2 is a further development of P.P.I. type radar equipment as used for navigational purposes. While this design includes many of the successful features of earlier types, recent advances in the technique of design and construction enable a simplified, more compact and more efficient equipment to be produced.


The principal features of the Type 2 design are the reduced dimensions and weights of the various units and the larger and improved display; the power consumption has also been reduced. Simplification of the equipment and a substantial reduction in the number of expendable items (particularly valves) contribute to increased reliability, while servicing is greatly simplified by new methods of construction.

Dimensions and power consumption. The reduction in dimensions will be particularly noticeable in the case of the two main units (transmitter and display units), which are usually installed in the wheelhouse. This reduction, together with the low power consumption (1 kW.), extends the possibility of fitting radar to the smallest class of vessel.

The P.P.I. Display. A 12-in. diameter cathode-ray tube is used, and a very high standard of definition has been achieved. The larger diameter of C.R.T. increases the scale of the display—expanding, in effect, the display as seen on smaller tubes, and it will be appreci-

ated that the presentation of a one-mile picture on a tube of this size greatly facilitates pilotage in estuaries or other similar narrow and congested areas.

Four range scales, 25 m., 15 m., 10 m. and 1-5 m., are provided, the 1-5 m. range being continuously adjustable between these limits. Accurate range is measured by an adjustable range marker ring superimposed on the display, and immediate approximate range by superimposed calibration patterns. The values of range interval between the rings of the calibration pattern are 4 m., 4 m., 2 m., and $\frac{1}{2}$ m., respectively, for the four ranges.

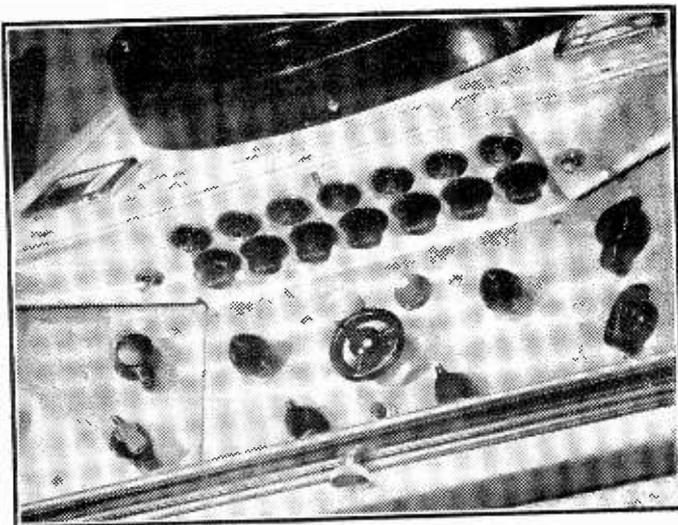

A close-up of the display unit showing fuses and tell-tale neon indicators.

Radio Valve Review-5

Voltage Amplifying Triodes are Dealt with This Month

IT was Lee de Forrest's epoch-making invention—the insertion of a “grid” between the cathode and anode of a simple thermionic diode, thus converting the valve into a triode—which made possible radio telephony and broadcasting as they are known to-day. In theory—and also in practice—the triode can perform each of the three essential processes for tele-communications: it can be used as an *oscillator* for generating alternating voltages; it can be used as an *amplifier* to magnify radio or audio-frequency signals; and it can be used as a *rectifier* for detecting or demodulating signals intercepted by the receiving aerial.

This is clearly indicated by the fact that early broadcasting receivers were equipped with anything up to six identical triodes.

In practice, however, many of the functions formerly fulfilled by triodes can be performed more efficiently by more complex or special purpose valves, and triodes are not to-day used to the same extent as in the past. There are, however, a number of purposes for which this type of valve is quite adequate.

The Triode as an Oscillator

The local oscillator in a superheterodyne receiver is usually a triode. In most cases this triode comprises a small electrode system mounted in the same envelope as a pentode, hexode or heptode which serves as the mixer. This application has already been covered earlier in this series of articles. Triodes for use as power oscillators in transmitting equipment are rather outside the scope of the present article and will be dealt with in a later instalment.

The Triode as R.F. Amplifier

The conventional R.F. amplifier is, of course, the pentode, but there are a few highly-specialised types of triode designed for use as R.F. amplifiers in very-high-frequency communications equipment. Even so, the stage gains obtained are comparatively small, and the valve serves mainly as a buffer to prevent oscillations from the frequency-changer reaching the aerial.

The Triode as Detector

In present day receiver practice the detector is almost invariably a diode, and a diode is merely a rectifier and has no amplifying power. Early receivers commonly employed a triode as detector, and this form of detector was held in esteem because of its great “sensitivity.” A little consideration of the basic circuit of the “leaky grid” triode detector shows, however, that this arrangement is really a combination of a diode detector and an A.F. amplifier. The grid and cathode form, in effect, a diode detector, producing an audio-frequency voltage across the diode load (i.e., the grid leak), and the audio-frequency variations of grid potential produce corresponding variations in the anode current whereby an amplified audio-frequency voltage can be obtained.

The vaunted “sensitivity” of the triode detector, therefore, is merely the normal amplification obtained from the valve in its role of A.F. amplifier. This amplification was, in the past, enhanced by the barbaric practice of applying regenerative feed-back whereby part of the A.F. output was returned to the grid circuit and re-amplified. Blessed were they of the listening fraternity who so handled this “reaction” that the valve did not revert to its third possible function and burst into uncontrolled oscillation!

The Triode as an A.F. Voltage Amplifier

If a diode detector is fed with a really strong signal, a matter of several volts, and is followed by a very sensitive output pentode, voltage amplification between the detector and output stage may not be necessary. Generally speaking, however, the signal available at the detector stage of a broadcast receiver will range from several volts for the local stations down to a small fraction of a volt for the weaker or more distant stations—quite insufficient to load a normal output valve.

A stage of audio-frequency voltage amplification is therefore provided, and this is very commonly a triode. As most modern receivers incorporate A.G.C., the double diode required for this purpose is frequently built into the same envelope as the

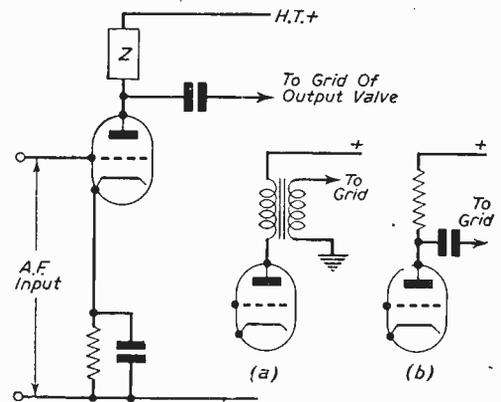


Fig. 1.—Basic circuit of triode amplifier, together with (a)—Transformer coupling, and (b)—Resistance-capacity coupling.

triode amplifier, and the valve is termed a double-diode-triode.

The basic circuit of a triode A.F. voltage amplifier is given in Fig. 1. The amplified A.F. voltage appearing across the load “Z” is transferred to the grid of the following valve, which is usually the output valve. Early triodes for this purpose were of medium impedance, and the “load” in the anode circuit was usually the primary of an iron-cored transformer, the secondary circuit of which

was included in the grid circuit of the following valve. The turns ratio of this transformer gave a voltage step-up of from $2\frac{1}{2}$ to 6 times, and thus

augmented the somewhat modest gain of the valve itself.

An audio-frequency transformer, however, is

VOLTAGE AMPLIFYING TRIODES

Type	Description or Application	Construction and Base	V_g (V)	I_b (A)	V_a (V)	$-V_{g1}$ (V)	I_a (mA)	μ_m (mA/V)	r_a (K Ω)	μ
Mullard										
(1) BATTERY TYPES										
Equipment Types										
DAC32 ..	Diode triode ..	Octal ..	1.4	0.05	90	0	0.15	1.275	240	65
KBC32 ..	Double diode triode ..	Octal ..	2.0	0.05	100	0	2.4	1.2	21	25
Replacement Types										
PM2HL ..	Medium impedance triode	4-pin ..	2.0	0.1	135	1.5	2.2	1.4	21.5	30
TDD2A ..	Double diode triode ..	5-pin ..	2.0	0.12	135	1.5	1.95	1.2	25	30
Type	Description or Application	Construction and Base	V_h (V)	I_h (A)	V_a (V)	$-V_{g1}$ (V)	I_a (mA)	μ_m (mA/V)	r_a (K Ω)	μ
(2) A.C. MAINS TYPES										
Equipment Types										
EBC33 ..	Double diode triode ..	Octal ..	6.3	0.2	250	5.5	5.0	2.0	15	30
EBC41 ..	Double diode triode ..	B8A ..	6.3	0.225	250	3.0	1.0	1.3	54	70
EC31 ..	Low impedance triode	Octal ..	6.3	0.65	250	16	20.0	3.2	3.3	10.5
ECC33 ..	Double triode ..	Octal ..	6.3	0.4	250	4.0	9.0	3.6	9.7	35
ECC34 ..	Double triode ..	Octal ..	6.3	0.95	250	16.0	10.0	2.2	5.2	11.5
ECC35 ..	Double triode ..	Octal ..	6.3	0.4	250	2.5	2.3	2.0	34	68
ECC40 ..	Double triode ..	B8A ..	6.3	0.6	250	5.2	6.0	2.7	11	30
ECC91 ..	Double triode ..	B7G ..	6.3	0.43	100	0.85	8.5	5.3	7.1	38
Maintenance Types										
ECC31 ..	Double triode ..	Octal ..	6.3	0.95	250	4.6	6.0	2.3	14	32
TDD4 ..	Double diode triode ..	7-pin ..	4.0	0.65	250	7.0	4.0	2.0	13.5	27
354V ..	Medium impedance triode	5-pin ..	4.0	0.65	250	4.5	6.5	3.5	11.5	40
EBC3 ..	Double diode triode ..	P base ..	6.3	0.2	250	5.5	5.0	2.0	15	30
Type	Description or Application	Construction and Base	V_h (V)	I_b (A)	V_a (V)	$-V_{g1}$ (V)	I_a (mA)	μ_m (mA/V)	r_a (K Ω)	μ
(3) D.C./A.C. TYPES										
Equipment Types										
UBC41 ..	Double diode triode ..	B8A ..	11	0.1	170	1.6	1.5	1.65	42	70
Replacement Types										
HL13 ..	Medium impedance triode	P base ..	13	0.2	200	3.7	5.0	3.3	12	40
HL13C ..	Medium impedance triode	7-pin ..	13	0.2	200	3.7	5.0	3.3	12	40
TDD13C ..	Double diode triode ..	7-pin ..	13	0.2	200	5.0	4.0	2.0	13.5	27

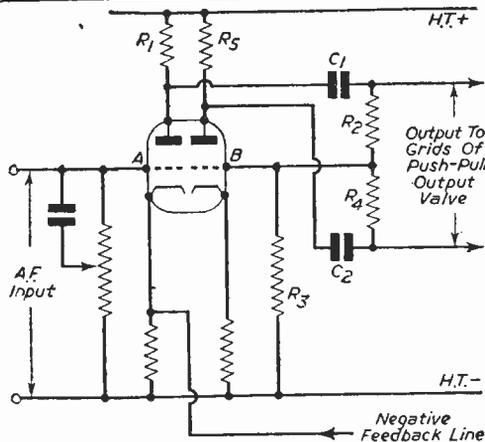


Fig. 2.—Basic circuit for phase inverter using a double triode.

a fairly expensive piece of apparatus, and this arrangement is now seldom used, being replaced by a triode of greater internal resistance operated with a resistive load, a coupling capacitor being employed to transfer the amplified A.F. signal to the grid of the next valve.

The Triode as Phase Splitter or Inverter

In amplifiers employing two output valves in push-pull it is necessary to supply two signals of equal magnitude, but of opposite phase to the grids of the two output valves. This was at one time achieved by using an A.F. intervalve transformer with centre-tapped secondary winding, but with transformer coupling becoming somewhat out-moded, a form of resistance capacity coupling employing a double triode is the more usual arrangement.

Of the many suitable circuits, a typical example is shown in basic form in Fig. 2. The A.F. input is applied to the grid circuit of Section A of the double triode and is amplified in the usual way.

(To be continued.)

E.M.I. EQUIPMENT

of special interest to

AMATEURS AND EXPERIMENTERS

at attractive prices including :—

- AD40** Miniature Mains Transformer, 310-0-310, 4v., 6.3v. 230-250v. input, 65-80 m.a. current rating : 13/6 plus 1/6 postage.
- AD41** Mains Transformer. 325-0-325, 4v., 6.3v. 100-250v. input. App. 100 m.a. current rating. 19/6 plus 1/6 postage.
- AD16** Smoothing Choke. Approx. 8 hys 200 m.a. 250 ohms D.C. Res. 6/6 plus 1/6 postage.

● Also available in limited quantities :—
AMPLIFIERS, MICROPHONES and LOUDSPEAKERS.

Full details and prices from :

E.M.I. SALES & SERVICE LTD.

AMATEUR DIVISION

HEAD OFFICE, HAYES, MIDDLESEX



SEE THE WORLD in well-paid and interesting jobs! Our 1-year Marine or Air Radio Officers Courses will train you to 1st Class P.M.G. Standard—the stepping stone to well paid posts. Training for Radio Officers' Certificate is recognised as providing grounds for deferment of call-up. Personal supervision by expert instructors.

Write for full details and FREE BOOKLET.

Write to Dept. 32.

E.M.I. INSTITUTES

10, PENBRIDGE SQUARE, NOTTING HILL GATE,
LONDON, W.2. TELEPHONE: BAYSWATER 5151/2


Associated with
"H.M.V."
MARCONIPHONE
COLUMBIA
ETC.

14

Unfortunately we have to increase the price. The rising cost of materials is partly to blame—the rest is due to our striving after perfection. Hundreds of *HOMELAB'S* have now been supplied, and in the course of production all improvements resulting from continued development have been incorporated. The result is an instrument of really outstanding performance which is being used in Universities, Industrial Organisations, Medical Research and other fields where the requirements are exacting and the price a secondary consideration. For those experimenting with television and radio receivers the *HOMELAB* with its wide frequency coverage is an ideal instrument, and many are being used very successfully for these purposes. Why not call and see it yourself, not just the finished article in its attractive cabinet, but the works as well—we have nothing to hide. If you cannot call send s.a.e., for full particulars enclosing P.O. for 2/6d. if the circuit diagram is required.

IMPORTANT.—Orders at present on our books will be executed at the old price.

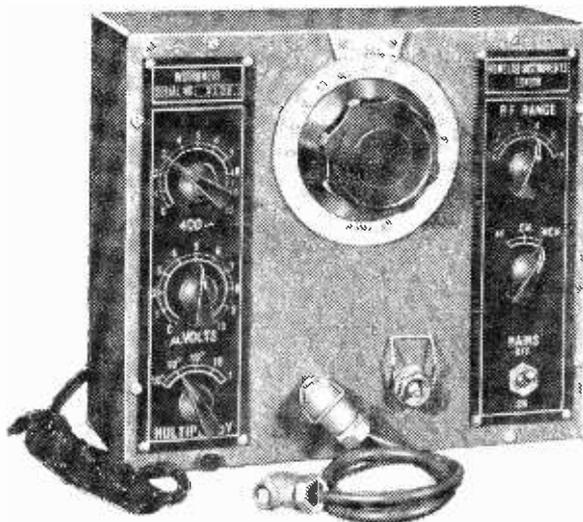DELIVERY.—The *HOMELAB* is not yet available ex-stock. The supply position of difficult items has improved and a steadily increasing rate of production is being achieved. All enquiries will receive our prompt and courteous attention.



HOMELAB SIGNAL GENERATOR (100 kcs.-130 mcs.)
PRICE : £9 9s. 0d. •

Orders and enquiries to :—

HOMELAB INSTRUMENTS,
116, GROVE ROAD, LONDON, E.17

Showrooms : 374, High Road, London. E.11

PREMIER Long Range TELEVISOR KITS

FOR LONDON AND BIRMINGHAM

USING 9" OR 12" MAGNETIC C.R. TUBES.

£19.19.0 including all parts, valves and loud-speaker, but excluding C.R. TUBE (Carriage, etc., 15/-)

The Vision Receiver, 4 R.F. stages (EF54s), Diode Detector and Noise Limiter (6H6) Video valve (6F54). Complete Kit with valves, **£3/16/0**. Carriage 2/6.

The Sound Receiver, 3 R.F. stages (6SH7s), Double Diode Triode (6Q7), which acts as Detector and L.F. Amplifier, Noise Limiter (EA50), output valve (6V6). Complete Kit with valves, **£3/1/0**. Carriage 2/6.

The Time Bases, blocking oscillators on Line (6SH7 and 807), and Frame (VR137 and 6V6). E.H.T. from Line Output Transformer, 10in. P.M. Speaker, Sync. separators 6H6 and 6V6. Complete Kit with valves, **£8/5/6**. Carriage 5/-.

The Power Supply, double wound transformer isolating the receiver from the mains. Rectifier 5U4G. Complete Kit with valves, **£4/16/6**. Carriage 5/-.

CONSTRUCTION BOOK 3/-

USING VCR97 C.R. TUBE. **£17.17.0**. (Carriage) etc., 15/-)

Five Easy to Assemble Kits are supplied:
 Vision Receiver with valves, carriage 2/6 .. **£3/13/6**
 Sound Receiver with valves, carriage 2/6 .. **£2/14/6**
 Time Base, with valves, carriage 2/6 .. **£2/7/6**
 Power Supply Unit with valves, carriage 5/- .. **£6/3/0**
 Tube Assembly, carriage and packing 2/6 .. **£2/18/6**
 This unit includes the VCR97 Tube, Tube Fittings and socket and a 6in. PM Moving Coil Speaker with closed field for Television.

The Instruction Book costs 2/6, but is credited if a kit for the complete Television is purchased.

Any of these Kits may be purchased separately; in fact, any single part can be supplied. A complete priced list of all parts will be found in the Instruction Book.

20 Valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver are a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

WORKING MODELS CAN BE SEEN DURING TRANSMITTING HOURS AT OUR FLEET STREET AND EDGWARE ROAD BRANCHES.

The following Sensitivity figures prove that the Premier Telesvisor Kits are capable of reception at greater distances than any other Standard Commercial Kit or Receiver whether T.R.F. or Superhet.

VISION RECEIVER. Sensitivity: 25 μ v for 15v. peak to peak measured at the Anode of the Video Valve. Sound Rejection: Better than 40 db. Adjacent Sound Rejection: Midland Model. Better than 50 db

SOUND RECEIVER. Sensitivity: 20 μ v. Vision Rejection: Better than 50 db.

Now Summer List now ready, 6d

PREMIER RADIO CO.

MORRIS & CO. (RADIO) LTD.

POST ORDERS TO 167, LOWER CLAPTON RD., E.S.
 Phone: Amherst 4723.

CALLERS TO 152/3, FLEET ST., E.C.4. Central 2833.
 207, EDGWARE RD., W.2. Ambassador 4033.
 This branch is open until 6 p.m. on Saturdays.

HENRY'S

SPECIAL OFFER.—Brand new S.T.C. H4/200 rectifiers. Output 2,400v. 3 m.a. our price, 15/- ea. only (plus 4d. post).
SLIDER POTS. As used in latest commercial T.V. Bank of 4, comprising 2 of 10,000 ohm, 500 ohm and 100 ohm. Only 6/- ea. the complete set.

TYPE 6A INDICATOR UNITS. As recommended for ex-Govt. T.V. construction. Absolutely complete (included VCR97 with mu-metal shield, 4 EF50 and 3 EB34). Limited quantity only. at 67/6 each, plus 7/6 carriage and packing.

R.3515 I.F. STRIP. A complete I.F. Unit, comprising 6 SP16 I.F. Stages tuned to 13.5 mc/s. 1 EA50 diode detector, and 1 EF36 or EF33 output or video stage. A few modifications only are required to adapt this unit, which will give pictures of extremely good quality. Price, complete with valves, and foolproof modification instructions, is 45s. plus 5s. packing and carriage. Limited quantity only.

DUAL PURPOSE MAINS TRANSFORMERS. Special 350-0-350v. 90 m.a. 6.4v. tapped 4v. at 3a., 5v. tapped 4v. at 2a. Top chassis mounting, and fully guaranteed. 18/6 only (plus 9d. post).

IGRANIC MAINS TRANSFORMER. A special purchase enables us to offer the following (—250-0-250, 70 m.a., 6.3v. 2a., 5v. 2a., half-shrouded, drop-through type, with voltage adjuster panel. Absolutely brand new and guaranteed. 15/- only, plus 9d. post.

R.1355 MAINS TRANSFORMER. 200/250v. input. Outputs 250-0-250, at 120 m.a., 6.3v. at 6a., 5v. at 3a. Fully shrouded top chassis mounting and guaranteed 100 per cent. Only 28/6.

MINIATURE MAINS TRANSFORMER. 250-0-250, 60 m.a., 6v. 3a., 5v. 2a., fully shrouded, well finished, size 3 1/2in. x 3 1/2in. Price 21/-.

EX-GOVT. VALVES. The following valves, ex-Government, brand new and guaranteed, can be supplied:—6J6 at 12/6. 6AK5. PEN46. 6L6 metal at 10/- each. EF50. EF54. EF55. RL37. VU120A. VU111. VU133. U18. 5T4. 5R4G. RL18. 6F7. 6AG5. 6K6. PM22A, all at 7/6 each. 5U4. 6SN7GT. 5Z4. MU14. 6K7GT. 6J7GT. 6K8GT. M4. 12SR7. 12SA7. 12SK7. 6SL7GT. 6SC7GT. 6CB. 6V6G or GT. 7CT. 7T4. 7S7. 7B6. 7C5. 1299A. 9D2. VP23. P2. 12AB. 8D2. 15D2. EF36. EF39. EBC33. EK32. EL32. 6X5GT. 2X2. 6AC7. 6N7. 78. 9003. IN5GT. 6J5GT. 6C5. KTW61. DH63. TDD2A. KT. 210 DET. 220 SC. VP2B. AC6Pen. EF8. all at 6/6 each. Also 9002 and ILN5GT. 8/6. 807. 7/- 4D1. 5/- EA50. ST61. 95A. EB94 at 3/6 each. Di Diode at 2/6 only. And the midrange of 1.4v. battery valves 1T4 and 1S5 at 6/6 each. 1R5 and 1S4 at 7/6. 3S1 at 9/- each. Most of these valves are boxed. In addition to the above few types we have tremendous stocks of both ex-Govt. new valves at equally competitive prices and B.V.A. valves at current B.O.T. prices.


Send stamp for Current Component List.

5, HARROW ROAD, LONDON, W.2
 PADdington 1008/9, 0401

The STEPPING STONES TO SUCCESS!



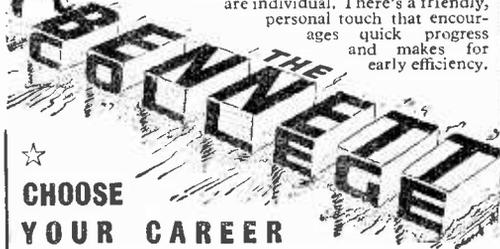Don't hesitate about your future! Go forward, confident that The Bennett College will see you through to a sound position in any career you choose. The Bennett College methods are individual. There's a friendly, personal touch that encourages quick progress and makes for early efficiency.



CHOOSE YOUR CAREER

- Blue Prints.
- Book-keeping.
- Building.
- Carpentry and Joinery.
- Civil Engineering.
- All Commercial subjects.
- Shorthand (Pitman's).
- Telecommunications (City and Guilds).
- Draughtsmanship.
- Radio (Short Wave).
- Quantity Surveying.
- Radio Service Engineering.
- Mathematics.
- Matriculation.
- Plastics.
- Wireless Telegraphy and Telephony.
- Surveying.
- Teachers of Handicrafts.
- Television.

If you do not see your own requirements above, write to us on any subject. Full particulars free.

—Direct Mail to DEPT. 104—

THE BENNETT COLLEGE LTD.
 SHEFFIELD

Two-valve S.W. Receiver

A Long Range Simple Receiver for the Beginner

By A. W. MANN

THE receiver to be described, is of simple design, but is nevertheless one of proved efficiency. It should be of interest to those who like to build experimental receivers in which they can incorporate suitable spare components which are to hand. The use of doubtful and junk components should however be avoided.

The Circuit

Fig. 1 shows the theoretical circuit, in which will be seen a regenerative triode detector, six-pin plug-in type coils, and a simple yet efficient form of band spreading. The extra expense of a band-spread condenser and slow-motion dial will prove in terms of results to be fully justified.

Components Values

The grid leak and grid condenser values specified are, in the writer's opinion, the most suitable for use with triode detectors, and enable the operator to obtain smooth regeneration throughout the full tuning range, providing of course that too high a voltage is not applied to the plate of the detector valve. That, however, is a matter for experiment.

The H.F. Choke and Coils

If you have a set of plug-in coils which cover all ranges between ten and one hundred metres, the H.F. choke should be of the type which will function efficiently throughout the full range with entire freedom from resonance peaks. The Eddystone type No. 1010 or one of the old Graham Farrish screened all-wave type meet these requirements.

Should you have suitable tuning condensers and slow-motion dials to hand, by all means use them. There are various makes of coils available and the theoretical diagram shows how the aperiodic or primary winding may be cut out of circuit.

Thus you can use only the grid and reaction winding of the six-pin coil, or four-pin coils if these are to hand. The .00005 μF pre-set, aerial series condenser should be used on all bands apart from the trawler and 160 metres amateur band, and in these circumstances true aperiodic coupling should be used.

If however you are using four-pin plug-in coils, the above trawler and amateur bands are best received using a .0001 μF pre-set condenser in series with the aerial

L.F. Coupling

Transformer coupling is used between the detector and output stage, and decoupling is also included. A suitable pentode L.F. transformer can be used if loud-speaker reception of the more powerful Europeans is desired, and is to hand.

As the original model was required for headphone reception only, a Lissen Hypermu Nickel-iron core type was used. The Ferranti AF4 is also suitable. A pentode output choke, however, should be used.

Depending on the form of H.T. supply used, some modification of the decoupling resistance might be found necessary. If an H.T. battery eliminator is used and the detector plate voltage on the lowest tapping is found to be excessive, the value of this resistance should be increased to 50,000 ohms or higher.

If when tuning on the higher range coils, the regeneration starts with what may be aptly termed a bump, the detector voltage is definitely too high. Some experiment is necessary on each aerial coupling. Note the following. A cuts out aperiodic winding, B is for use on 160 metre bands. C for use on all other bands.

Layout

Fig. 2 shows the component layout. The valve holders and coil holder as shown, are of the base-board type, as used in the original model. If however you have none of these on hand, I would strongly advise the purchase and use of the more modern chassis mounting type.

The layout diagram conveys the relative positions of the components at a glance. The coil holder and the detector valve holder should be as

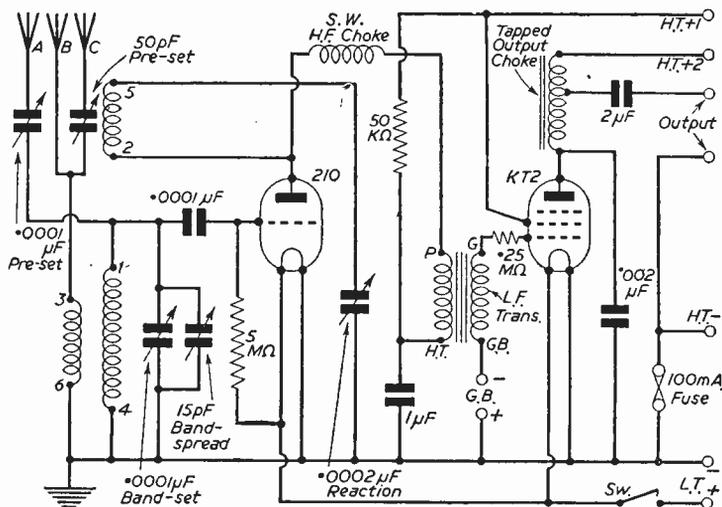


Fig. 1.—Circuit of the Regenerative Detector and Pentode Output receiver.

close together as the grid condenser coupled between them will allow. The leads from the band-setting condenser should go to the coil holder connections. The band-spread condenser being wired in parallel with the band-setting condenser.

The Wiring

All leads should be short and as direct as possible, but the tuning condensers should not come within the magnetic field of the coil winding. Do not use old wire. Push-back insulated wire is now available and is very handy to use. My own method when using this is to remove the insulation from one end, and push back the other end. This avoids the piling up of the insulation, and certainly looks neater.

Chassis and Panel

Chassis and panel dimensions will depend upon the relative size of the larger components. An aluminium chassis and panel should be used. Alternatively a plywood chassis with two side runners, and a plywood top face with aluminium sheet could be made at low cost.

It should be understood, therefore, that the chassis and panel dimensions are given only as a guide, and some slight modification may be found necessary.

When building this receiver, do not make the chassis and panel first and then lay out the components. Take a sheet of drawing paper, mark out a plan of the 12in. by 10in. chassis to full size.

Follow this by arranging the components in their relative positions as shown at Fig. 2.

This method will enable you to avoid cramped layout, and on the other hand excessive spacing between components, which would result in long leads.

Apply this method to the panel layout but in this instance use cardboard. The relative position of the tuning condenser and dials can be determined at a glance and mistakes avoided.

One point which should be understood is that unless the chassis and panel assembly of this, or for that matter, any short-wave receiver built as a rigid assembly, tuning operations will be accompanied by a series of crackles.

The panel should therefore be of stout gauge material, and the brackets used should have at least a 2 1/2 in. base. (See Fig. 3.)

It is also a sound idea to bend over about half an inch at the top of the panel at right angles. This, together with the support provided by the chassis, will guard against panel whip when tuning.

Another point is that the panel should not be depended upon to provide effective earthing of the tuning and reaction condenser moving vanes, or rotors. Wire up to both sides of these condensers: it may save trouble later.

Tuning Dials

The writer is strongly in favour of panel-mounted slow-motion dials (where direct calibration is not desired): the Utility and Muirhead are good examples.

These could be used in conjunction with Raymart tuning condensers. A reaction condenser with integral s.m. drive was used in the original model.

Safety First

Beginners and others are sometimes worried when about to try out a new home-constructed receiver in case a wiring mistake has passed undetected, with the possibility of burnt-out filaments. Two components should be common to all battery receivers—a fuse and fuseholder. Fuses are cheaper than valves.

Two versions of this receiver were built, the second one now being under test. So far as performance is concerned, there is little to choose between them. This version, however, is far simpler to build and wire.

Experimental Designs

This is an experimental design, as distinct from a sponsored, complete kit receiver. It is intended solely for the experimenter who wishes to use spare components and build his receivers with the minimum of extra outlay.

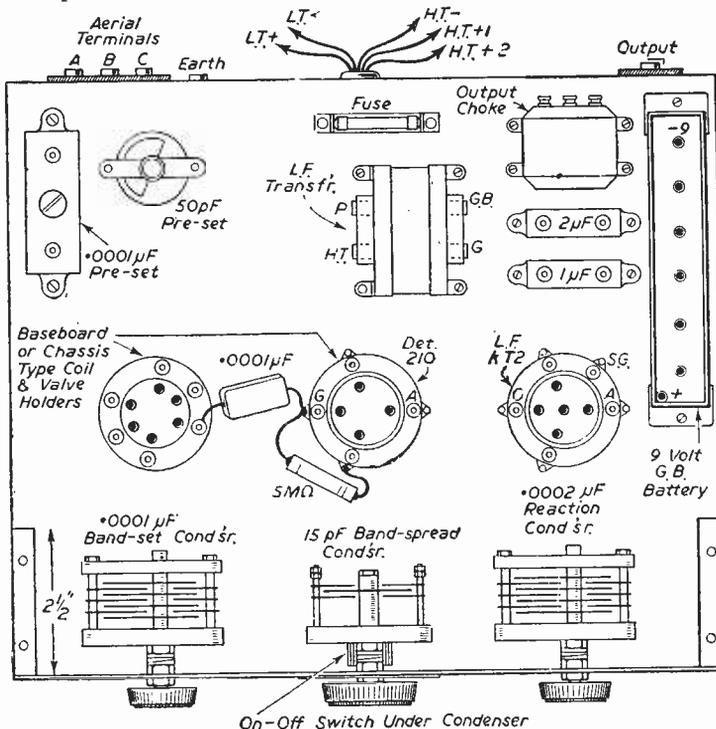


Fig. 2.—Chassis and Component layout.

It is therefore only suitable for those who have previous constructional and trouble-tracking experience. I stress these points because every single model built will include in it different components from those used by the author. In fact, no two

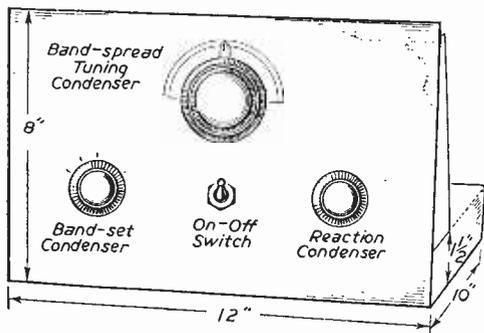


Fig. 3.—Panel and chassis panel mounting.

versions will be alike. Such differences may result in instability or other trouble being experienced, or, on the other hand, a receiver better than the original model.

Point-to-Point Wiring

The true experimenter, given a suitable circuit and layout, should be able to go ahead with the construction, trace the cause of any trouble and effect a cure.

If not, with practice, and by following the methods outlined, he should eventually find it possible to do so. Those are the reasons why point-to-point wiring diagrams are not given.

The original model used by the writer has proved to be a good DX receiver. Those who are interested in all continents, all zones, and set listening period reception should find that it will meet their requirements if carefully built.

It is a good performer on the world broadcast bands, and equally good on the amateur bands. The New Zealand 20 metre amateur phone station ZL4HP has been heard with this receiver, and later verified by QSL card. (Incidentally, this report was sent because no other station came back to his repeated CQ and QRM was bad.)

There is much activity on 160 metres at the time of writing. The low noise level of this receiver makes it ideal for reception on this band.

In conclusion, the writer will be interested to hear of the results obtained with a receiver built on these lines, especially in the case where the aerial is the indoor one described in the April issue of this journal.

Television on Tap

SIX months from the date of the Postmaster-General's licence, the first resident of the City of Gloucester will be able to have trouble-free TV laid on to his home by wire for 7s. 6d. a week. This charge will include four ordinary radio programmes (3 B.B.C. and 1 special) as well as the TV programme whenever there is one on the air. Seventy miles from Sutton Coldfield, he will get reception, free from all interference, as brilliant as though he were only a mile or so from Alexandra Palace. And there will be no aerial to bother with, and only one selector knob to adjust.

Before deciding to go ahead with this progressive scheme, the first of its kind to exist, the Gloucester County Borough Council made a close study of various systems, especially the experimental installation that has been operating on test for a year at Northampton in conjunction with the Northampton Wireless Relay Company, Ltd.

Equipment

This equipment, designed and installed by Link Sound & Vision, Ltd., a firm owned jointly by Pye, Ltd., of Cambridge, and Murphy Radio, Ltd., was finally approved, and work is now going ahead on the Gloucester installation.

Basically, the system comprises a master receiving station picking up programmes from Sutton Coldfield and redistributing them by wire throughout the Gloucester area. Sets similar to ordinary TV sets in appearance are installed in subscribers' homes, and ease of installation is a great advantage of the system. This is the first time that an entire town or area (as distinct from blocks of flats) has been equipped in this way, and town-planning authorities throughout the country are taking a keen interest in Gloucester's pioneer lead.

Our Cover Subject

MRS. CLEMENT ATTLEE, the wife of the Prime Minister, opened the first of the new B.B.C. television studios at Lime Grove, Shepherd's Bush, London, recently. Titled "Studio D," the premises form the B.B.C.'s biggest studio now in operation—5,400 square feet, or more than twice the area of the two studios of Alexandra Palace. Studio D is to be the first "Television Nursery" in the world. Devoted mainly to children's programmes, it will eventually extend the range of children's broadcasts. The first hour additional to the normal Sunday "Hour" was broadcast on Wednesday, May 31st. To cope with the increase in programmes, the B.B.C. has appointed three men and four women as "Children's Hour" producers. Programmes produced in Studio D are fed by special cable to Alexandra Palace for broadcasting.

Our cover this month shows a general view of the new studio as the first programme was being broadcast from the premises.

Our companion paper, *Practical Television*, gives up-to-the-minute news on all topics relative to both the programme and the technical side of this new art.

THE NEW NEWNES MONTHLY

Practical Television

Edited by F. J. Camm

No. 4. Now on Sale Price 9d.

Get Your Copy Now!

"WHAT is QRP?" is fast becoming perennial and vexed a question as "What is DX?" To the American ham, able as he is to use as much as one kilowatt input legally, QRP is undoubtedly something in the region of 100 watts or under. Transmitters of 250 watts are termed "medium power." And in this country it is not uncommon to hear hams talk of their 25-watters as QRP. Of course, it is all a matter of opinion, but for real QRP the basis should probably be 5 watts or under, possibly even lower. The dyed-in-the-wool low-power fan also considers that for QRP work the valves should be directly heated types—any form of mains supply (even for heaters) being definitely *de trop*.

On this basis, and using a normal H.T. block, it would be difficult indeed to produce an input in excess of a couple of watts. But experience has shown that the increase from 1 to 5 watts makes very little difference at the receiving end. So the QRP fan normally contents himself with anything up to 2 watts, and even this is considered to be QRO by some diehards who go on the air with commendable faith using a fraction of a watt! The line must, however, be drawn at some point and so we will consider that one single solitary watt will meet our requirements. And if anyone doubts what can be done on this power (if it can be called such!) the exploits of such QRP giants (excuse the metaphor) as G3XT, G6ZN, *et al*, should prove to be an eye-opener.

It is no great achievement to work DX using 150 watts input, 100 watts or even 50. Given an average aerial and location WAC is child's play on even 25 watts; before the war we used to do it with 10. But when one gets down to real QRP then contacts of what normally are considered to be "local" become feats. By this, it is not

A SIMPLE TI

An Effective One-watter for the QRP Enthusiast and

implied that QSO's will become few and far between, but that contacts assume some sense of achievement in proportion to the power used.

So for the ham who wishes to tread new pastures, probably due to finding the chasing of super-DX a little tedious, and to the newcomer to transmitting, maybe a little QRP work would prove to be not only diverting but fascinating and instructive. At any rate, in both instances, it is certainly worth a trial.

The simple transmitter to be described was originally constructed to meet the requirements of a "hunt-the-transmitter" outing, but it operates very successfully in the shack. The original requirements were that it should put out a strong enough signal to be picked up easily by the marauding bands of receiver teams using simple one- and two-valvers. This on a hastily slung-out aerial.

It was used for its field day activities on top band and this is probably the best frequency to operate it on when used in the shack. But by suitably changing the coils, other bands can be covered. Eighty metres is the next best bet, with 7 Mc/s following as a further choice. It has not been tried on 14 and 28 Mc/s, simply because the writer has no 14 Mc/s crystals; in any case, unless one has 28 Mc/s crystals it means using the PA as a power doubler which would hardly be a practical proposition in this case! So the prospective QRP operator is advised to tackle the low frequency bands, with a special emphasis on 1.7 Mc/s, where surprising results can often be obtained using this type of very low-powered gear.

The Circuit

The one-watter is more or less the same on paper as its larger cousins, though, of course, in a rather diminutive fashion. It is a two-stage transmitter—CO/PA—using the 2-volt KT2 tetrodes in both stages. With 120 volts H.T. the PA should draw around 10 mA., perhaps a little under, which with a little mental calculation works out at

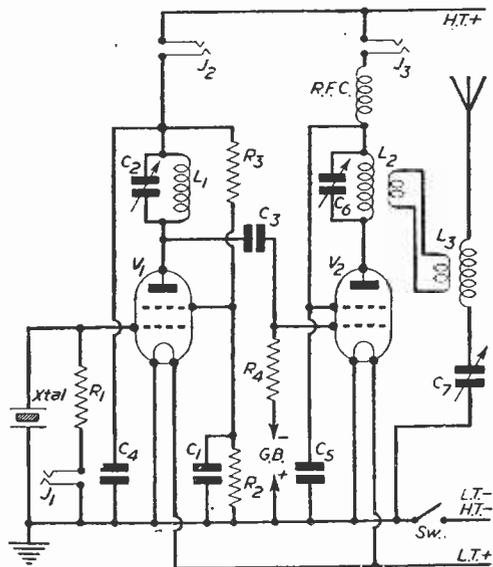


Fig. 1.—Theoretical circuit of the complete unit.

LIST OF C

Resistors

- R1—47,000 ohms.
- R2—100,000 ohms.
- R3—10,000 ohms.
- R4—10,000 ohms.

Capacitors

- C1—0.002 μ F.
- C2—160 μ F, variable.
- C3—100 μ F.
- C4—0.002 μ F.
- C5—0.002 μ F.

- C6—160 μ F, variable
- C7—250 μ F, variable

Valves

- V1—KT2.
- V2—KT2.

Jack sockets

- J1—Keying jack.
- J2—CO anode current jack.
- J3—PA anode current jack.

TRANSMITTER

Transmitting Beginner

By "ELECTRON"

1.2 watts input. If the H.T. is increased to, say, 150 volts then it is possible to squeeze about 2 watts from this little transmitter. But believe me, the difference in results between the two inputs will be negligible, so it is advisable in the interests of economy to use but 120 volts, or even 100.

The crystal oscillator stage follows convention. The key is inserted in the earthy end of

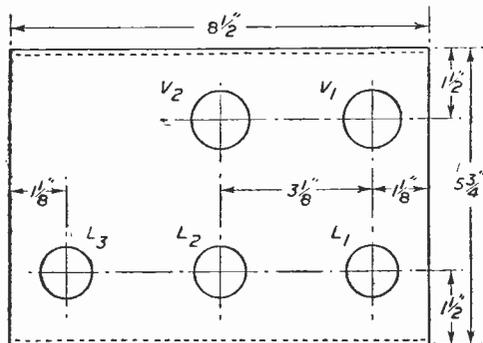


Fig. 2.—Chassis drilling data.

the grid resistor return and this was found to be the most favourable position. Some may prefer keying the screened-grid line, or even the H.T. On no account key the filament circuit—if you do the results will be no oscillation, for the valves must "warm up"!

The anode circuit consists of the usual tuned circuit made to resonate with the grid circuit frequency (that of the crystal). The screened-grid feed is of the potential divider type, as this tends to give better stability, a factor that is of utmost importance when QRP is used.

The CO is coupled to the PA stage through the capacitor C3. Battery bias is applied to the PA valve. The output of the PA valve comprises a tuned circuit of the same frequency coverage

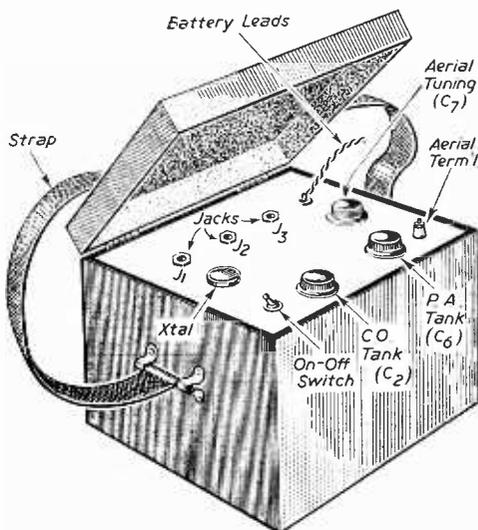


Fig. 3.—Appearance of finished unit.

as that in the anode circuit of the CO stage. Since the transmitter was designed for a throw-out Marconi-type aerial, a tuning circuit for this aerial is an integral part of the transmitter. This aerial tuner is link-coupled to the PA tuned tank circuit and is built into the unit.

The two jacks shown in the circuit, J2 and J3, are respectively for checking the anode currents of the CO and PA stages and are used when the transmitter is tuned up. Details will be given in a later paragraph.

Choice of Components

When dealing with medium- and high-power transmitters it is most important to take the utmost precautions against RF leakages and losses. But on QRP work it is vital—for there is so little power to spare that losses must be reduced to the barest minimum. First of all, use ceramic or other low-loss holders for the valves and the coils. Use air dielectric variables and preferably those with ceramic insulation. The crystal holder, which is actually an 807 base, must be of low-loss construction, also.

Regarding resistors, there are but four in the complete unit. These can be of very low ratings—say, $\frac{1}{4}$ watt. Capacitors required number three, apart from the variables in the tuned circuits. Make sure the capacitors are efficient.

As to coils, the prospective builder of the one-watt has several choices. In the original model standard five-pin coil formers were used and the actual coils home-wound. Details of these coils will be given in the next instalment. If the transmitter is to be used on the higher-frequency bands it would be an advantage to use self-supporting horizontally mounted inductors; this contingency was not visualised in the original transmitter, but each constructor will have his own

COMPONENTS

Other components

- One crystal holder.
 - Two British 5-pin ceramic valveholders.
 - Three sets of coils and holders (see table for coil data).
 - On/Off switch.
 - Aerial feed-through terminal.
 - Two extension rods and couplers.
 - Three control knobs.
 - One RF choke.
 - Two condenser brackets (insulated).
- N.B.—For measuring anode currents a milliammeter of 15-50 mA. FSD is required.

ideas on matters like this as it is purely one of personal choice.

The remainder of the components leave little to be commented upon and so we can now proceed to discuss the details of construction.

Housing the Transmitter

A somewhat unusual form of housing is used, due to the requisites of the original model. The chassis is mounted in a hinged carrying case in a vertical position—the opposite to normal chassis position. The case was purchased at one of the local surplus radio stores and it may be easily possible to find a similar one fairly rapidly. For those desirous of using an identical case it will be of

batteries! But, if the prospective builder has midget batteries or is prepared to purchase them, it is by far the better policy to adopt. For instance, the Ever Ready number 67 battery is very suitable. It will supply 103½ volts and has a grid bias tapping of—4.5 volts. The dimensions of the battery are

Dimensions of Metalwork

- Chassis: 8½ in. wide × 5½ in. long × 2½ in. deep.
- Panel: 9 in. wide × 9 in. deep.
- Cabinet (inside measurements): 9½ in. × 9½ in. × 6½ in. (with ½ in. flange around the top for bolting chassis and panel). Cabinet hinged lid measures 2 in. deep.

2½ in. × 6½ in. × 5½ in. and this can easily be accommodated in the main case. Other small batteries could, of course, be used, and the grid bias block could be fitted to the inside of the hinged lid with a simple metal clip.

Construction

The layout drawings will show how the whole unit is constructed and it is hoped that the following notes will clear up any odd points that may occur. As it is assumed that many of the readers of this article are beginners in the field of transmitters the notes are designed primarily for their benefit.

The first task, of course, is to drill the necessary holes. The panel and chassis fixing holes are the preliminary drillings and then the holes common to both, such as for the spindles of the variables, the switch and the aerial terminal. As the variables are mounted on brackets set back from the face of the chassis (about which more later) the holes should be a good clearance for the extension spindles (say about ¼ in. diameter). The switch and aerial feed-through holes will naturally depend upon the type of components used. The remainder

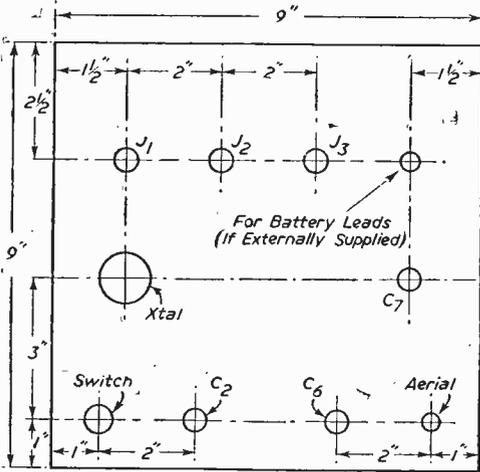


Fig. 4.—Details for panel drilling.

interest to note that it was originally used for an aerial coupling unit and it has these words stencilled on the outside of the lid—"Aerial Coupling Equipment. Aerial Unit F. ZA0841." If one of these cases cannot be unearthed and the constructor wishes to build his one-watter the same as the original one, the sizes of the case, chassis and panel will be found in the panel above.

With the chassis mounted in the way described all one has to do to tune up the transmitter is to lift up the lid of the case and the controls will be exposed for simple adjustment. The sketch will show this quite clearly. And the final touch was the webbing strap. This was taken from a glass D wavemeter and forms an ideal carrying strap when using the transmitter on field days.

Regarding batteries, it is possible to fit these into the carrying case itself providing that midget accumulator and H.T. blocks are used. A couple of simple metal clips could be made up for securing the batteries in position to avoid their moving around inside the case. Arrangements were made, however, in the model described to use external batteries. It was agreed at the time that a self-contained unit would have been better, but the club committee decided that as we already had standard 2-volt accumulators and 120-volt H.T. blocks, it would not be in keeping with the club's current financial status to invest in entirely new

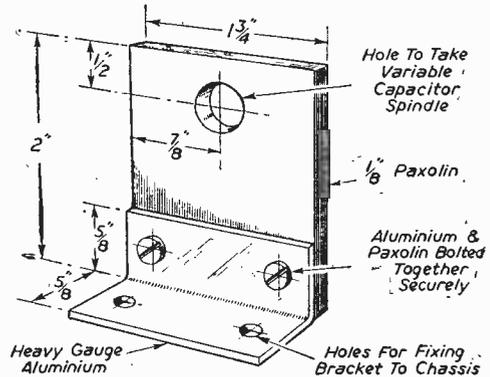


Fig. 5.—Bracket for condenser.

of the panel holes are perfectly straightforward; a valveholder must be fixed for the crystal, three jacks inserted and the aerial tuning variable mounted. Since this component's rotor is earthed the capacitor can be mounted direct on to the panel without any extension rod. The only other panel holes are minor ones—the two small holes to accommodate the anchor tags.

(To be continued.)

Radio Valve Faults-2

Types of Fault and the Process of Fault Finding in the Modern Radio Valve

By H. GARDNER

FUNDAMENTALLY any valve consists of a cathode which when heated will emit electrons, an anode to which these electrons finally flow, and one or more grids to control the flow or act as screens.

The cathode must be of such design that it is capable of emitting the required number of electrons to constitute the maximum anode current when it has reached some chosen temperature.

The earliest valves had cathodes made from plain tungsten wire which had to be heated to bright incandescence in order to obtain the necessary emission, but these were soon replaced by

Cathode Insulation

It thus became necessary to insulate the cathode from the heater and as insulators of electricity are also good insulators of heat, it became desirable to construct the cathode with no more insulation than was necessary to be effective.

A glance at the circuit diagram of various forms of mains receivers will show that the requirements of the insulation between the heater and the cathode will vary according to the type of circuit in use.


In a straightforward A.C. mains set there will rarely be a potential of more than a few volts between heater and cathode, but in the case of series operated valves and valves used in some types of special applications, the potential may amount to a considerable figure.

Consequently, the manufacturer will vary the insulation between heater and cathode in accordance with the normal requirements of the circuits for which the valves were designed.

Breakdown of the heater-cathode insulation is not a usual fault in modern valves operated in accordance with the makers' specified conditions, but if hum in a receiver is believed to be caused by such a condition a straightforward test can be applied to the insulation between the cathode and heater of the valve.

There are, however, several important precautions to take in making this test. The use of a test voltage higher in value than that specified as the maximum to be applied between the heater and the cathode of the type of valve under test, may easily result in breakdown of the insulation of a good valve, so reference should be made to published characteristics before undertaking the test.

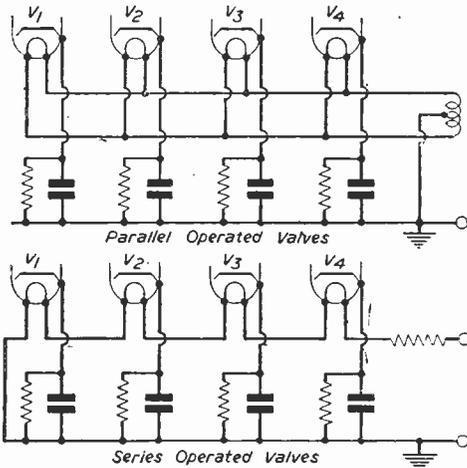It is also worthy of note that expansion and



Figs. 1 and 2.—Note the possible difference of potential between heater and cathode of V4 in each case.

valves in which the cathode contained a percentage of thorium oxide which enabled them to be run at a lower temperature. In these cases the cathode was directly heated by means of an electric current being passed through it, but the necessity for heating the cathode from an A.C. mains supply required a construction which would allow of the retention of heat so the temperature fluctuations caused by the rising and falling values of the A.C. mains should not be reflected in the operation of the valve.

Consequently, it was necessary to provide a cathode of such physical dimensions that temperature fluctuations of this nature could not occur. In the case of output valves, the filament itself was of sufficient thickness to cause no appreciable trouble, but in valves used in early stages further precautions were necessary.

The emission material or cathode proper, was therefore separated from the heating filament, the cathode being made of suitable dimensions to allow of it retaining a constant temperature.

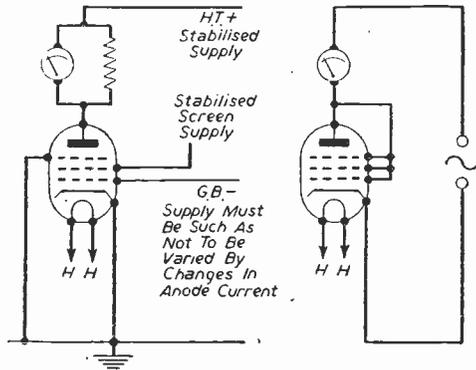


Fig. 3.—Heater supply must apply accurate potential across heater. This supply must give correct voltage for any current drawn. Care must be taken to prevent oscillation through arrangement of leads to electrodes.

Fig. 4.—A not uncommon method of checking emission. Pitfalls concerning this test are discussed in the text. One of the most serious is the possibility of breakdown due to excessive current.

contraction of the parts comprising the heater and cathode may cause the fault to appear only under certain temperature conditions and it is therefore important to test the valve not only with a cold cathode, but also with the cathode at normal operating temperature.

Cathode Tests

The purpose of the cathode being to provide electrons for the current flow of the valve, it follows that a drop in its emissive properties will throw the valve off characteristic.

The emissive properties of the cathode are reduced with use. If the valve has been severely over-run, or the heater under-run, such properties may be damaged in a short space of time. Testing the condition of the cathode in this respect is not the simple matter that it appears at first sight. In the first place it is necessary to have some sort of a "yardstick" against which to make the measurement, and the only one usually available is the data given by the manufacturer for new valves in good condition operated under certain stated conditions. Testing a valve under these conditions it is possible to see how far it may fall short of the performance to be expected from it when new. This still leaves the tester in the position of having to use his judgment as to whether the trouble is serious enough to affect the working of the particular apparatus in which it is used.

There are numerous pitfalls to be avoided in making this test. Unless the cathode is put fully to work, in other words unless the valve is operated under the conditions specified by the maker, the true drop in emission will not be shown although some drop will be indicated. The ideal test, therefore, is to put the valve under its normal operating conditions as stated by the manufacturers and check the anode current against that given as correct under those particular conditions.

Unfortunately, it is possible for a valve to show up well under such a test when in fact this is far from being the true state of affairs, for unless all the other electrodes and vacuum are in order the anode current may actually be in excess of that given for the conditions of test.

Care must also be taken to ensure that self-oscillation is not present. Capacity between the wiring leading to the electrodes may easily provide a circuit which in the case of high slope valves will cause this trouble. Such self-oscillation will, of course, give an entirely fictitious reading of the anode current.

A not uncommon method of testing the condition of the cathode is to strap together all other electrodes in the valve, apply an alternating current, use the valve as a rectifier and measure the rectified current. Manufacturers' published data does not usually provide useful information for this test. There is also a word of warning to be given concerning it inasmuch as an unsuitable value of A.C. supply to the valve may seriously damage it either by causing too much current to be drawn from the cathode or overheating of the control grid or other electrodes to a temperature which may cause gas to be driven from them.

No mention has so far been made of the first and most obvious test which should be carried out on a valve. That is, to ensure that the filament or heater circuit is intact. This may sound exceedingly

simple, but there are two points worth watching. In the older types of valves it is not uncommon for the heater or filament wire to become intermittent or disconnected by reason of faulty soldering to the pins in the base. In the case of the old split types of pin, this sometimes was the result of an endeavour to open out the splits in order to obtain better contact between the pin and the socket. Examination of valves of this type with a view to checking this fault may result in a few minutes' job with a soldering iron saving an otherwise good valve from the scrap heap. As nearly all types of valves fitted with these pins are now obsolete, an irreplaceable valve may be saved from destruction by watching this point.

Even a straightforward filament or a simple heater can occasionally develop a fault worth checking, and it can be of interest to make a test as to whether the filament or heater still retains the resistance value that it was designed to have. This test must, of course, be made by measuring the necessary voltage required to pass the stipulated current through the filament or heater under test, as otherwise variation of the resistance of the filament or heater due to temperature change will provide a fictitious result.

Technical Literature Received

A USEFUL range of photo-electric and electronic equipment is described in the new series of leaflets received from Radiovisor Parent, Ltd., of 1, Stanhope St., London, N.W.1, founded 21 years ago. These include the firm's new photo-electric press guard and the recently developed type FR49 Flamestat flame control device for the protection of industrial gas-fired ovens, etc.

Other leaflets deal with units for indicating the density of smoke emission from chimney stacks, counting moving articles on conveyors, automatically controlling the switching of street lights, and the protection of premises by infra-red beams. Other applications of the firm's products include automatic fire detection, the control of hopper filling, the detection of turbidity in liquids, as well as countless specialised applications for almost every trade.

"Mermaid" R/T Equipment

A leaflet has recently been issued by the communications department of Philips Electrical, Ltd., and is now ready for mailing to the trade.

The leaflet concerns a compact "Mermaid" radio-telephone equipment specially designed for small vessels. It conforms with G.P.O. requirements.

New Aid to Valve Dealers

A comprehensive price list of all current radio and television valves at present manufactured in this country, together with their Mullard equivalents where applicable, is now being distributed to the trade by the valve sales department of Mullard Electronic Products, Ltd.

This list, which is in the form of a chart measuring 26in. wide by 22in. high, is intended for wall-mounting. It has been designed for quick and easy reference, and should prove of great value to all radio and television dealers.

MAGNETIC RECORDING

Hints and Tips for Experimenters

By F. C. BLAKE

FROM the number of letters received in the past six months, the construction of magnetic recorders, both wire and tape varieties, has become very popular. Recording by magnetic means is not a new invention, Poulsen having used it at the beginning of the century for recording telegraphic messages, before the advent of the thermionic valve.

The discovery in recent years of the use of high-

should not be cut or bent more than absolutely necessary, as this will tend to harden it and destroy its particular properties. Mumetal is recognisable by its silvery appearance—but unless you are certain of the core material you will be using, it is best to get several samples from different sources. Radio metal is also silver in colour and, although this is not suitable for record-playback heads, it will be useful for making erase heads. If you have some silicon iron stampings these will be ideal for erase heads, which can be made in the same way as the record-playback heads but with a 2 thou. brass shim inserted in the gap instead of the aluminium foil.

A brass bracket is made to secure the lamination which is drilled in the centre to clear a 6 B.A. screw, the tips of the "lam" if previously cut out must be perfectly square and clean edged, the inside butting edges should be tinned.

After covering each side with a layer of medical plaster, two windings of fifty turns are carefully put on. Next, the ends of the "lam" are carefully bent with a small pair of pliers so that the tips touch each other squarely. This is most important, and demands just a little patience.

When satisfied that all is correct, carefully insert a small shim of aluminium foil such as is used for wrapping chocolates. The foil is usually in the neighbourhood of 1 thou. thick.

A little solder is now run on to the ready tinned undersides of the tips to lock the gap at its set width. Finally, the face of the gap is carefully filed dead level with a magneto or other very fine file, and then polished with a well-worn strip of emery cloth. If care has been taken in correctly aligning the gap and pole pieces very little filing

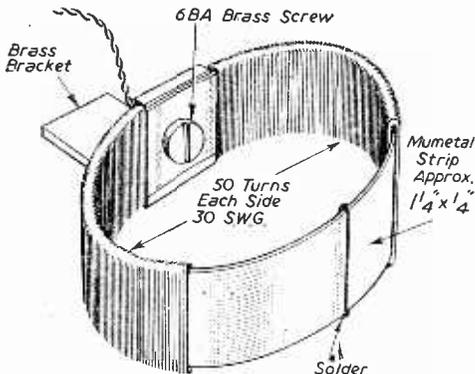


Fig. 1.—A simple record-playback head.

frequency current, as distinct from the earlier D.C. biasing, has helped considerably in improving the reproduction, giving a greater dynamic range, and great reduction, if not elimination, of background noise.

To obtain the best results, the wave-form of the H.F. bias frequency must be sinusoidal, or at least symmetrical, otherwise a noisy background will be produced on playback, equivalent to a small direct current bias, the amount depending on the proportion of "unbalance" of the wave-form. The use of a buffer stage will help to keep the wave-form correct, especially if there is a considerable load to supply, as when erasure current is also being taken from the same source.

Difficulty is often experienced in getting sufficient current to erase, and I find the best scheme is to feed the erase head through a series condenser of suitable capacity to act as a resonant circuit. The precise capacity can easily be found by placing a small lamp, such as a 6.3v. .3 amp. pilot light in series with head and condenser, and changing the capacity until optimum brilliance of bulb is found. The actual frequency of the oscillator is not critical, and is usually in the neighbourhood of 30-50 kc/s.

Although heads may now be obtained ready-made, a simple yet quite efficient head may be made from a strip of mumetal as shown in Fig. 1, which is suitable for both tape and wire.

The strip is best obtained from a discarded para-feed or similar inter-stage transformer, and it

Mumetal Strip Mounted On Bracket & Insulated With Medical Tape

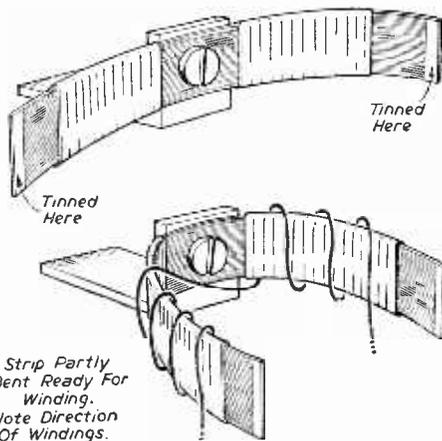


Fig. 2.—Details of construction of the head.

should be necessary. Too much filing is detrimental.

The lead ends should be covered with silk sleeving

heads are used, the through a resistor. described is shown

recording head should be fed A suitable circuit for the head in Fig. 3. The resistor R2 keeps the audio recording current reasonably constant at all frequencies, and without it there would be a preponderance of bass, and serious overloading. This is due to the fact that the head acts almost as a pure inductance. At high frequencies, the head impedance would be high, with consequently a low current flow through its windings; as the recording frequency is decreased more and more current would flow, until saturation with attendant distortion commenced.

The most satisfactory way of finding correct level of audio current is to use a "loop tester," Fig. 4. An endless wire or band of tape is made up, and either fitted to the recorder mechanism with a spring-loaded pulley to hold it taut, or to a gramophone motor, on the spindle of which is mounted a suitable pulley. By fitting two heads, one for recording,

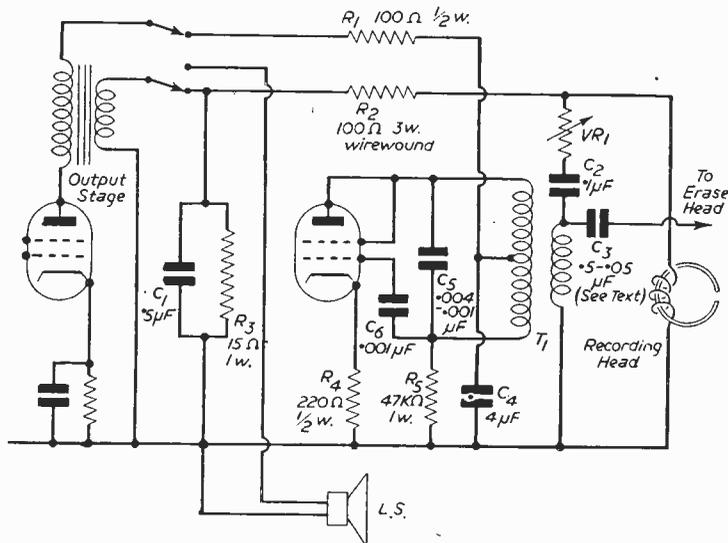


Fig. 3.—Oscillator and head circuit. The oscillator coil may be obtained from Wright and Weare, Judge Industries, etc.

taken from an odd piece of flex and twisted together to reduce hum pickup.

It is a good plan to make several heads at the same time, selecting the best after testing each one individually. The D.C. resistance of the head is about .5 ohms.

Impedance Counts

Several readers thought that the head should have a D.C. resistance of 15 ohms when connecting it to a "15 ohm" transformer. This, of course, is not necessarily so, as it is the impedance of the head that matters, which is governed by the number of turns, the core, and the gap width, whilst the D.C. resistance is due to the size of wire used. In the head described 30 s.w.g. silk and enamelled wire was used; any gauge, however, around this figure will be quite satisfactory.

High-impedance heads are rather difficult to make as the large number of turns necessitates the use of thin gauge wire, but as already stated, they may be purchased ready-made, should the constructor wish to record at high impedance direct from the anode circuit of the output valve, and to dispense with the input transformer.

In either case, whether high- or low-impedance

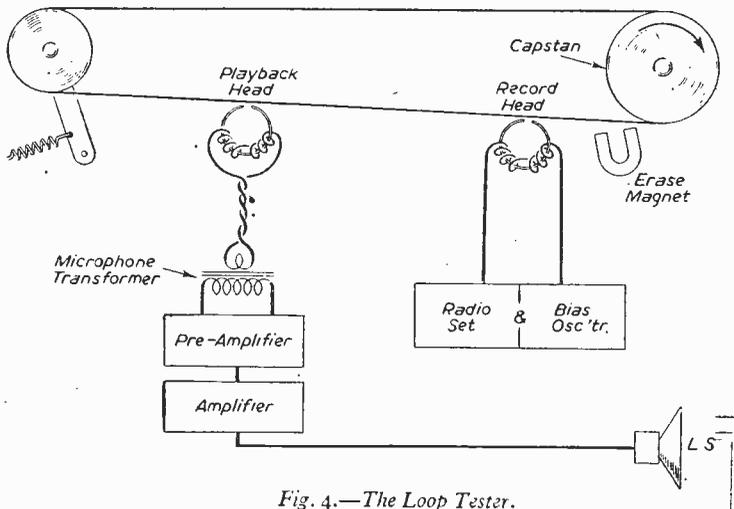


Fig. 4.—The Loop Tester.

the other for playback, instantaneous checks can be made with different bias and recording current levels. It is most important to see that the heads are aligned correctly with one another, otherwise there will be a serious loss of top response.

ADDRESS CORRECTION

WITH reference to the article on Tape Recording in our July issue, will readers please note the new address of Audigraph, Ltd.: 74, Gt. Hampton Street, Hockley, Birmingham, 18.

CLYDESDALE

Bargains in Ex-Services Radio and Electronic Equipment

A.C. Mains Power Unit with Built-in Modulator.

A complete 110 to 250 volt 50 cycle A.C. Mains Power Unit, consisting of one L.T. supply transformer—4 v. 4 a. (3 windings) for the rectifier, etc., at 3.25-0.325 v. 8 a. winding supplying the 6.3 v. circuit of a built-in modulator, suitable for swinging a transmitted carrier of 100 w. input, plus an outlet for the supply of an external transmitter. A 200-0-200 v. 50 mA fully smoothed supply for bias needs. A second transformer (H.T.)—500-0-500 v. 200 mA (twice), rectified and smoothed, one supply for the internal modulator, the second supply is carried to an outlet for external use.

Valves include 36C5, 2/807 and 2/AV1 (FW4/5/800). Controls are located on the steel front panel. Unit complete in varnished wooden cabinet with carrying handles. 22 1/2 in. x 16 in. x 13 1/2 in. CLYDESDALE'S **£12.10.0** CARRIAGE PRICE ONLY. PAID.

Infra-red Image Converter Cell. Sniper-scope. Snooper-scope. This cell converts images bathed in infra-red light into normal visible objects. CLYDESDALE'S **12/6** POST PRICE ONLY. PAID. each.

Now Ready, List No. 7

of ex-Services Bargains fully illustrated. Send 6d. to cover distribution cost. Please print name and address.

Order direct from:

CLYDESDALE SUPPLY CO. LTD.

2, Bridge St., Glasgow, C.5. Phone: SOUTH 270619
Visit our Branches in Scotland, England and N. Ireland.

Ex British Army. Tele-sonic Xmtr/ Rcvr.

Designed for 2-way communication on audio voice frequencies (Ultra long wave). No R.F. is employed. The range is limited. Ideally suitable for working locally. space for batteries within the Tx. and Rx. (separate units). Dim.: 14 1/2 in. x 11 in. x 8 in. and 7 in. x 6 in. x 2 in. respectively; valves include 2/VP23, 2/ATP4 Xmtr. 3XH 1.5 v., 1XP 1.5 v. Rcvr. with pick-up coil, but Xmtr. less coil.

CLYDESDALE'S PRICE ONLY. **£3.0.0** CARRIAGE (as detailed)

HEADPHONES.

Balanced. Ideal for crystal sets. 500. Brown type "P." High impedance, 30 P per pair. MORSE KEYS. Practice type. All parts in brass on polished wood base. 3/3.

CRYSTAL SET COILS. Medium wave. Boxed with circuit. 2/3. **CRYSTAL DETECTORS.** Semi-permanent type. 3/6. Cat-shaker type. 3/6. crystal 3/-. Packet containing crystal and spare whisker. 1/-. **CRYSTAL DIODES.** 4/3.

CRYSTAL SETS. Standard with "Caterpillar" detector. M.W. only. 11/-. De-Luxe type in cream plastic with semi-permanent detector. M.W. only. 6/-. **EMERALD COPPER WIRE.** 4lb. reels, 16, 17, 18, 19 and 20 S.W.G., 2/3. 21 and 22 S.W.G., 2/6. 23 and 24 S.W.G., 2/8. 25, 26 and 27 S.W.G., 3/-. 28, 29 and 30 S.W.G. 3/2. 32 S.W.G., 3/3. 33, 34 and 35 S.W.G., 3/7. 36 and 37 S.W.G., 4/-. 38 and 39 S.W.G., 4/3. 40 S.W.G., 4/6. **DOUBLE SILK COVERED COPPER WIRE.** 25 S.W.G., 2/3. 26 S.W.G., 2/5. 28 S.W.G., 2/7. 30 S.W.G., 2/9. 32 S.W.G., 3/1. 34 S.W.G., 3/5. 36 S.W.G., 3/7 2 oz. reels. **DENCO POLYSTYRENE SOLUTION.** Ideal for winding coils. Low loss and damp resisting. 1oz. 5/3 per sq. ft. plus post

bottle. 13, 2 oz., 2/7. **BAKELITE SHEET.** Ideal for panels, etc. 1/4 thick, Brown available in the following sizes—6 in. x 4 in., 2/5. 6 in. x 6 in., 3/-. 6 in. x 8 in., 3/7. 6 in. x 10 in., 4/2. 8 in. x 10 in., 5/-. 8 in. x 12 in., 5/10. Black, 6 in. x 6 in., 3/-. 6 in. x 8 in., 3/9. **AERIAL WIRE.** "Perlite". Plastic covered 50ft. coils. 4/-. **TUNING CONDENSERS.** .0005 outd. Air spaced, 4/6. Midget bakelite, 5/3. **TERMINALS.** Screw down type, 1/- each. Red and Black. **MINIATURE OUTPUT TRANSFORMERS.** Ideal for personal receivers, matches 354, 3V4 valve

to 10 ohm speaker. 4/6. **MIDGET P.M. LOUD-SPEAKER.** (Celestion 21n. 3 ohm voice coil, 2/3. Plessey 5in. 3 ohm voice coil, 1/6. 6. Truvox elliptical 6in. x 4in. x 2 1/2 in. deep. 3 ohm voice coil, 19/6. Midget Valves, 1K5, 16/6. IT4, 14/8. 1A5, 16/6. 354, 3V4, 14/8 post free. **SCREENING CANS.** 3 Piece type for octal valves, 2/3. **TUNING CONDENSERS.** Twin gang, 500 pf. less trimmers, 3/6. **ALUMINUM SPEAKER PRET.** OP756. Used by leading manufacturers. Gold or Bronze, 12in. x 12in., 12in. x 9 in., 3/9. Any other size available on order at 2/3 5/7/5/15 ohms, 5/3 9d. and 10d. **GOODS CAN BE SENT C.W.O. or C.O.D.**

and packing. When ordering, please state whether you require the longer dimension to be horizontal or vertical.

TELEVISION COILS.

Complete set of coils and one video choke (Station Coldfield and Alexandra Palace) for "Practical Wireless" T.R.F. Television, 17/3. **ALUMINIUM CHASSIS,** with reinforced corners. 14 S.W.G., 2 1/2 in. deep, 6 in. x 4 in., 5/2. 8 in. x 5 in., 7/-. 10 in. x 6 in., 9/5. 12 in. x 8 in., 10/5. 12 in. x 9 in., 11/-. 10 in. x 9 in., 12/-. 10 in. x 10 in., 13/3. 3 in. deep, 8 in. x 6 in., 5/6. 10 in. x 8 in., 9/8. 12 in. x 8 in., 10/8. 14 in. x 9 in., 13/6. 16 in. x 10 in., 14/3. 18 in. x 12 in., 17/3.

P.P.T. TRANSFORMERS FOR "QUALITY" REPRODUCTION. GARDNER'S 750.

Special high fidelity transformer for single OP756. Special high fidelity transformer for two PX4 class valves in push pull. Primary, 3,800 ohms. Secondary 0.2-5.5/7.5/15 ohms. 42/- post free.

Special high fidelity transformer for two PX25 class valves in push pull. Primary, 6,000 ohms, centre tapped. Secondary 0.2-5.5/7.5/15 ohms. 48/9 post free. Special high fidelity transformer for two PX25 class valves in push pull. Primary, 6,000 ohms, centre tapped. Secondary 0.2-5.5/7.5/15 ohms. 51/9 post free.

VALLANCE'S. Vallance & Davison, Ltd., Dept. P.W., 144, Briggate, Leeds, 1 phone 29428/9

HR TELEVISION

TELEVISION RECEIVERS
SCANNING AND FOCUS COILS
P.M. FOCUS UNITS

5/8 kv. R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS

Technical Publications post free.

"TELEVISION CIRCUITS" a booklet compiled for the Constructor, post free 1/6

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

TRANSFORMERS

230v. A.C. INPUT

150.0.150 volts at 100 ma. Size 3 1/2" x 3 3/4" x 4 1/2" PLUS 1/- POST.

SIMILAR.

150.0.150 and 0, 10, 20, 30 and 40 volts. All at 70 ma. Size 2 1/2" x 3 1/4" x 3 3/4".

CHOKES 20 Hy. 80 Ma. Standard 6/-, 10 Hy. 60 Ma. Shrouded 4/6. 10 Hy. 30 Ma. Midget 2/-, Post 6d. each extra.

MONEY BACK GUARANTEE.

FIELD'S, 435-437, STRATFORD RD., B'HAM., 11.

STERN'S BATTERY PORTABLE "PERSONAL" KIT

A complete kit of parts to build a Midget 4-valve All Dry "Personal" Set.

Consists of regenerative T.R.F. Circuit, employing Flat Tuned Frame Aerial with Denco Iron Dust Cored Coil, thereby ensuring maximum gain for Single Tuned Stage, covering Medium Waveband. Valve Line-up: IT4 (R.F. amp.), IT4 (Detector), IS5 (1st A.F.), and 354 (Output). Includes 6 1/2 in. P.M. Speaker and with chassis already drilled and shaped.

Consumption of only 7m A. ensures long battery life. The kit is designed for a cabinet, minimum dimensions 4 1/2 in. x 3 1/2 in. Detailed Building Instr. and circuit. Including Practical Layout included with each Kit, make assembly very easy (supplied separately for 1/-).

PRICE FOR COMPLETE KIT, £3/8/9 (plus 16/7 P.T.). Suitable Unpolished Cabinet, 12 9; E. Ready B114 Battery, 9/7.

The MIDGET A.C. MAINS 2 VALVE RECEIVER. All the Components to build this Popular Set, as specified in the March 1949 issue of Wireless World, can be supplied complete for £3. Reprint of detailed building instructions, giving practical layout and circuit supplied separately for 9d.

The WIRELESS WORLD 3 VALVE A.C. MAINS SET. Covering long and medium waves. We can supply the complete components to build this set, including drilled chassis, valves, M coil speaker, etc., for £4 5/0. Complete wiring diagram and instructions included (supplied separately for 9d.).

We can now supply an attractive Walnut cabinet for the Wireless World 3-valve set, with a complete slow-motion dial and drive assembly. (Station named dial to latest wavelength.) Inclusive price, £11 5/0.

A Complete Kit of Parts to build a MINIATURE "ALL-DRY" KIT. E.H.T. 60 Volts (approx.) and 1.4 Volts. Suitable for use with any Personal Receiver requiring above voltages. It is housed in a light metal case, size 4 1/2 in. x 3 1/2 in., and can be accommodated in most Personal Sets. Price of Complete Kit, including detailed Assembly Instructions and Layout, £11/7/6.

Send 3d. stamp for our Comprehensive Component Stock List, which also shows our various Kits of Parts. When ordering please cover post and packing.

STERN RADIO LTD.,

109 & 115, FLEET STREET, E.C.4.

Telephone: CENtral 5814 & 2280

Designing your own Receiver

Advice and Guidance for the Beginner

By STANLEY BRASIER

THERE are always beginners in radio and there always will be, but the subject cannot be learned quickly, and a start is usually made by building one or two simple receivers to strict design—such as those found in this journal. This is all very well, but before long the time comes when the student wants to try his hand at building a receiver to his own design, but the desire is thwarted by the fact that he does not know how to start. To this one may answer that if the student has not that knowledge he is not in a position to start designing. The argument to offset this, however, is that by such designing he will absorb far more in the matter of knowledge and in a quicker period. For it is an undisputed fact that a little practical experience is worth a whole lot of theory. For instance, if one wants to know something of the workings of a certain test instrument, one may wade through pages of literature on the subject and still not find the exact information desired, but make the thing up—be it only on the breadboard principle—and after a little experiment, this knowledge, plus a lot more, will soon be acquired.

Similarly, in receiver design, the same benefits are conferred. With a published design, one takes it for granted, knowing that it *will* work and that is the end of it. With a receiver of one's own design,

however, there is always the stimulus of pride in one's own efforts, and the added interest spurs one on to get the utmost out of the set. Quite probably the finished result will be little or no better than a published design, but what a lot of knowledge has been gained.

Having started the ball rolling, so to speak, the thirst for knowledge increases and is supplemented by theoretical and technical learning from the many books on the subject. By this means, practise helps theory and vice versa.

It is the experience of the writer that these would-be designers have a reasonably good idea of the requirements of the radio section of the receiver and in this respect need only a little guidance in the method of procedure. It is usually the calculation of values of the various components in the power section which cause the most worry.

Symbols

The beginner will naturally have studied the design of various receivers, and should be familiar with the numerous diagrammatical symbols used to denote components, types of valves, etc. The ability to draw theoretical circuit diagrams is essential before anything is attempted and in this connection most textbooks include a page or two

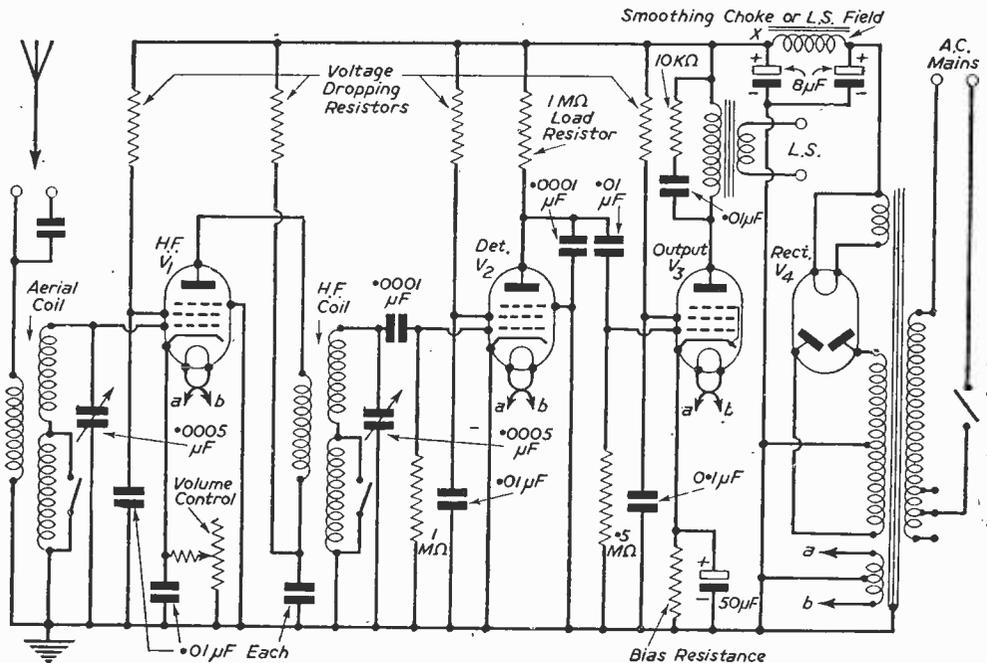


Fig. 1.—A suggested circuit for a simple 3-valve plus rectifier A.C. Mains Receiver. Details of design and the principles involved will be described in this series.

devoted to symbolic diagrams. Similarly, valve data books provide lots of information on the various types of valves. All this should be studied earnestly.

With a beginner having a natural and keen interest in radio, certain factors are easily or automatically absorbed and are implanted upon his memory for good and all. It is the theory, after a certain point, that is so difficult to master. The enthusiast knows, from constant reference to these pages, that one must observe various rules of thumb. He knows, for instance, that a condenser will pass A.C. and will block D.C. but does not know why; and that A.C. has to be rectified before it can be used for H.T. at the valve electrodes, but has no notion of A.C. theory.

Given a certain standard of intelligence, such things, and many others, are readily absorbed, and usually provide all the bare information to start on the venture of receiver design.

Naturally, a certain amount of elementary knowledge on the subject of radio is necessary. We have already discussed the question of circuit diagrams but to emphasise the ease with which such a diagram may be read—as compared with a wiring or block diagram—refer to any typical receiver design. Most novices tend to avoid the theoretical counterpart, until it is realised that a block diagram is quite tedious to unravel, and that once mastered, the essential details of a theoretical diagram can be appreciated in a few moments. In this respect it is interesting to see how long it takes to decipher a block diagram into its theoretical equivalent.

Ohms Law

A thorough knowledge of Ohms Law is also essential because it is the key to many calculations necessary even to simple design. This is also available in most text books, but for ease of reference it is given here. It denotes the relationship between voltage, current and resistance, and is the law by which, if two quantities are known, the third may be assessed. Where E=voltage (electro-motive force) I=current in amps., and R=resistance in ohms, the various formulæ are:

$$I = \frac{E}{R} \quad R = \frac{E}{I} \quad E = I \times R$$

Note that in all cases I is in amps., not milliamps., so that the result must be multiplied or divided by 1,000 if milliamps. are used.

And since wattage (or power) is dependent upon the quantities used in Ohms Law it can be assessed as follows:

$$\text{WATTS (or } W) = \frac{E^2}{R} \quad \text{or } W = E \times I \quad \text{or } W = I^2 \times R.$$

Resistances

Whilst on the subject of simple mathematics it would be as well to consider resistances and condensers in series and parallel, for such calculations are always useful during receiver adjustments. Resistances in series are merely added together thus, $R = R^1 + R^2 + R^3$, etc. Resistances in parallel are more difficult since the resultant R is the reciprocal (the quantity divided into 1) of the sum of the reciprocals, thus:

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{1}{\text{TOTAL}} = R$$

In this connection it is useful to remember that two

resistances of the same value, joined in parallel will have a total resistance of half the value of one.

Capacity

Turning now to capacity, the formulæ are similar, but reversed. Therefore, condensers in parallel are calculated thus: $C = C^1 + C^2 + C^3$, etc., while condensers in series are:

$$\left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) = \frac{1}{\text{TOTAL}} = C.$$

Here, again, two condensers of the same value joined in series have a resultant value half that of one, so that two 0.0005 μF . condensers in series result in a total capacity of 0.00025 μF .

Inductance

Regarding inductance, it is not necessary at this stage to wade through pages of elucidation on coil design. This is a case where one can study the matter at any time and at any length. For the purposes of initial receiver design it is sufficient to think of inductance in terms of, say, a long- and medium-wave coil, or a 20 henry low frequency choke. It is far safer and more reliable in the first stages of construction to make use of commercial coils—home construction to one's own design can come later, when the theory has been grasped. But there is no point at the moment in worrying and making lengthy coil calculations when the ready-made component, tried and tested, is available at a modest price, and provides an acknowledged standard of efficiency.

The novice should be able to discriminate between high frequency and low frequency, alternating and direct current, and appreciate the basic principles of voltage dropping, smoothing, decoupling, etc.

Knowing these, he will, in turn, be able to analyse a circuit diagram into its H.F., DET., and L.F. sections. The same applies to the A.C. and D.C. power supplies.

Regarding such items as coupling and decoupling condensers, grid leaks, paths, etc., here again we may rely on the rule of thumb, or accepted practice. From reference to various designs we know that the value of a grid condenser of a detector valve comes within a certain range, therefore we would not be likely to make this value 2 μF .

For the remainder of the circuit, Ohms Law can be relied upon to see us through and an explanation of calculations, together with a certain necessary standard of ability in simple mechanics, will be given later.

Assuming we are now in a position to estimate our requirements with regard to a suitable receiver, this will naturally vary according to individual ideas and localities, but for the purposes of this article we cannot do better than to decide on a three-valve H.F. detector and L.F. receiver which always has good average sensitivity and acceptable quality. And for the purposes of greater explanation, the power can be provided from A.C. mains.

Design

If we attacked the problem of design scientifically we should say that for a given tiny input, a certain power output is required, and then proceed to find out how many valves would be wanted and the stage gain required to produce the results needed. However, previous designers have shown us that our

three valves will give a good performance and it is now only necessary to decide on the types of valves to be used. This is where one's preferences may come into play and provides an opportunity to design the set around valves of one's own choice.

Output

The first thing to decide is how much power output (in terms of watts) is expected and as we are not concerned with batteries we can afford to be somewhat extravagant with current, upon which output is always dependable. On the other hand, the receiver is to be limited to three valves, only one of which will provide L.F. amplification. However, by using a pentode output valve which gives more watts output for a given anode current than does a triode, we can rely on about 2 watts, which (we will assume) is ample for our requirements. It should be appreciated that to realize this output a reasonably large input signal, such as that from a local station is necessary.

In order to provide as much sensitivity as possible to the receiver it would be wise to use H.F. pentodes for the detector and H.F. stages, so that we are now in a position to choose the valve types. In practice, of course, valves may be on hand which could be used, but as a start must be made somewhere, it is suggested that the receiver is built around type 6K7 for the H.F. stage, 6J7 for the detector and 6V6 for the output stage.

Coupling

The next question is that of intervalve coupling between detector and output valve. If a triode were being used as detector we could be sure of plenty of amplification by using an L.F. transformer. The use of this component, however, encourages hum pick-up and, in any case, is not suited to the H.F. pentode which it is proposed to use. On the other hand the gain of the H.F. pentode is greater than the triode so that with resistance capacity coupling, good amplification will still be obtained.

There is quite a choice of the type of coupling between the H.F. and detector stages; that most common being by means of an H.F. transformer. Choke coupling is also very efficient and may be considered as an alternative.

Selectivity

The question of selectivity has also to be dealt with; but in order to avoid complications at this stage we will content ourselves with two tuned circuits, one of which will provide coupling between the aerial and the first valve.

Reaction should be provided in order to increase the overall sensitivity of the receiver, but since this method of control is passing out of favour it can be omitted, thus obviating an extra control. We shall see later, however, when testing the completed set, how an alternative system may be applied.

Power Supply

The circuit is now pretty well lined up and it remains to provide a power supply to the valves. This is to be drawn from A.C. mains via a transformer. (It is proposed to explain later the requirements for an A.C./D.C. receiver.) The mains transformer primary winding should be rated at the

voltage of the mains and in practice it is tapped for voltages between 200 and 250. On the secondary side, three windings will be required, i.e., the H.T. winding, the rectifier heater winding, and that which supplies the ordinary valve heater in the receiver. These latter are always run in parallel, therefore the current required is additive, the voltage being that of one valve. Reference to the valve data will show that this voltage is 6.3, whilst the combined current consumption of the three heaters is 1.05 amps. This then, is the rating for the transformer heater winding. Although the voltage rating should be correct, it is usual to allow a safe margin of current working and in this case up to 2 amps would be permissible.

Regarding the rectifier, we could have used the metal type, thus saving a secondary winding, but since this is intended to be shown in the A.C./D.C. version, the valve counterpart is suggested here for purposes of explanation. It is usual for a transformer incorporating a 6.3 v. winding to be provided with another at 5 volts for the valve rectifier. This is quite convenient as there are various types from which to choose, but we cannot decide on this until the H.T. requirements have been calculated.

Transformer Requirements

Full wave rectification is standard in A.C. (only) receivers and for this reason a centre tapped H.T. winding is required and it is now necessary to find out what voltage and current is to be drawn from it. Further reference to the valve data shows that at 250 (max. voltage) the 6V6 consumes 50 milliamps including the screen grid, which must not be forgotten. The 6K7 anode and screen will take 13 milliamps and the 6J7 a further 2.5. Actually this latter current will be lower because of the anode load resistance connected in the 6J7's anode, causing a severe voltage drop, with consequent low current; but the difference will not be sufficient to upset our calculations. The total current is therefore 65½ milliamps and it now remains to find the voltage required. The maximum voltage permissible for the anode of the 6V6 is 250. Note that this is *at the anode* and in the interests of quality and watts output it is advisable to maintain it. It is now necessary to calculate how much resistance (therefore voltage drop) will be in circuit between this point and the output point of the rectifier.

Loudspeaker

If we are to consider using a mains energised loudspeaker, now is the time to decide, because it will affect the voltage needed at the H.T. secondary quite considerably. The field coil of this type of speaker may well have a resistance of 2,000 ohms, to which may be added about 400 ohms for the primary of the output transformer. Note that the total current will pass through the loudspeaker field coil whereas only that of the output valve anode will flow through the transformer primary. By applying ohms law ($I=C \times R$) the voltage drop across the field coil will be $\frac{65 \times 2,000}{1,000} = 130 \text{ v}$

and that across the transformer primary $\frac{45 \times 400}{1,000} =$

18 v. In addition to this the grid bias voltage of 12 must also be considered.

(To be continued)

RADIO BULLS
 246, HIGH STREET, HARLESDEN, N.W.10
RCA 6AB7
 /1853 Metal
3/11

BRITISH AMERICAN BATTERY, A.C. and UNIVERSAL TYPES.
 All fully guaranteed

If yours is a Valve Problem—BULLS are the People who will most likely solve it. Mullard, Brimar, Cossor, Mazda, Marconi, Osram, Tungarum, Hivac—any type. British and American. All prices include Purchase Tax, most valves are Ex-Ministry of Supply, new and unused. There is only one "BUT."

- You must HURRY!
AMERICAN TYPES
 (Unused and Boxed)
- OZ4. 6/-; 6B8. 7/-; 6SL7. 6/-; 19. 9/-; 1C5. 7/-; 6C5. 7/-; 6S7. 9/3; 25L6GT. 7/-; 1LA4. 6/-; 6C6. 9/-; 6SN7. 7/-; 25Y5. 9/-; 6R5. 8/-; 6D6. 9/3; 6R9. 8/3; 25Z4. 8/-; 1S5. 8/6; 6F5. 6/-; 6U7. 8/3; 25Z5. 9/-; 1T4. 8/-; 6P6. 7/-; 6SA7. 7/-; 25Z6CT. 8/-; 1S4. 8/-; 6P7. 8/-; 6V6. 6/-; 35Z4GT. 9/-; 1V. 9/-; 6P8. 9/-; 6X5. 7/-; 32. 4/3; 6/-; 6C6G. 7/-; 1A7. 7/-; 39. 4/3; 2X2. 6/6; 6H6. 3/9; 7A8. 7/-; 42. 10/-; 3S4. 8/-; 6J5. 5/-; 7B6. 7/-; 41. 8/3; 3Q5. 8/-; 6J6. 11/-; 7C7. 8/-; 43. 10/9; 5U4. 6/-; 6J7. 7/-; 12A6. 5/3; 7S. 8/9; 5Z3. 11/-; 6K7. 7/-; 12H6. 9/-; 7S. 8/-; 2A4. 6/-; 6KTGT. 5/3; 12K7. 8/3; 80. 9/3; 6A3. 10/-; 6K8. 7/-; 12K8. 7/3; 807. 6/3; 6A7. 12/6; 6L6G. 9/-; 1247. 9/-; 84/6Z4. 7/-; 6ACT. 6/-; 6L7. 7/2; 12SH7. 7/3; 9001. 7/-; 6AC5. 7/2; 6N7. 9/-; 12SK7. 7/3; 9002. 7/-; 6AG7. 7/-; 607. 7/3; 12SQ7. 7/3; 9003. 7/-; 6B4. 7/-; 6SG7. 7/-; 12SR7. 7/3; 954
 Acorn. 4/-; 6BT. 11/-; 6SH7. 6/-; 14F6. 10/-; 955. 4/-; 6V. 7/-; 6SK7. 6/-; 18. 10/-; 86A. 11/-; 613. 35/-

- BRITISH REPLACEMENT TYPES** (Unused and Boxed)
- BATTERY TYPES** (or equivalent)
- 210VPT. 8/-; SP2. 8/-; 10LE. 4/-; TDD2. 8/-; PMHF. 3/6; PM22A. 5/9; LP2. 4/3; QP21. 7/-; PD220. 10/-
- MAINS TYPES** (or equivalent)
- ACTH. 16/-; SP4. (7). 9/-; FW4500. 7/6; SP4 (5). 8/-; FC13C. 8/-; VP44. 12/-; FC13. 8/-; MS4. 10/-; VP13C. 9/9; ACHL. 7/3; VP13. 8/-; D41. 9/3; TDD13. 8/-; AC.Pen (5). 12/-; HL13. 7/-; AC.Pen (7). 12/3; SP13C. 9/9; U10. 7/-; PEN3520. 12/-; MU12. 7/3; PEN40DD. 18/-; AC2PENDD. 18/-; U4020. 18/-; AC5PEN. 12/-

- SPECIAL TYPES**
- ACTP. 16/-; U74. 8/6; X65. 8/-; TP2620 16/-; KTW74. 9/9; U31. 8/6; VP133. 10/-; DL74. 9/6; EF80. 8/-; TP23. 13/-; U11. UT1. 8/6; EL33. 8/-; TP22. 13/-; HL473. 9/6; ECC31. 8/-; PEN453DD. 13/-; X73. 10/9; EF39. 7/-; ME41. 10/-; KTW73. 9/9; EL32. 7/-; PEN363. 10/-; KTW72. 9/9; EF36. 7/-; U22. 10/-; KT74. 9/9; EK32. 8/-; HL133DD. 9/-; DH76. 9/-; EH34. 7/-; HL42DD. 12/-; KT76. 9/9; EL50. 7/-; PEN45. 9/-; U76. 8/6; CCH35. 9/-; PEN45DD. 9/-; W76. 9/9; DL2. 7/-; KT33C. 8/-; DL35. 8/-; VT32. 12/-; KT32. 7/-; 61MPT. 7/-; ACVF1. 12/-; KT35. 9/9; C1. 9/10; TP23. 12/-; U52. 9/-; C1C. 9/10; HL41. 7/-; DH63. 7/-; XP. 6/-; PEN25. 7/-; KTW61. 7/-; XH. 6/-; TP25. 8/-; U50. 7/-; ECH35. 9/-; VP23. 6/-; U17. 9/-; HVU1. 9/-; HL25DD. 5/-; H63. 7/-; PENDD2530. 9/3.

EX-EQUIPMENT TYPES

VR91. 6/-; EF54. 5/-; VR65. 4/3; VR54. 3/3; 9D2. 6/3; VR65A. 4/-; VR56. 4/3; V478. 3/-; 8D2. 6/3; VR53. 4/3; VR92. 3/-; VT52. 5/-; S130. 6/-; Postage 9d.

STOP PRESS:
EX-W.R.D. CHASSIS with valves in brand-new condition. 1R5, 1T4, 1S5, 1S4, complete with Circuit Diagrams, showing how this can be converted to excellent set for Beach, Lawn, etc. Only 27/6, post 1/-. Mark envelope P.W.



HIGH FIDELITY
 and
INCREASED REALISM
AT LOW COST

The system of using a "separator" for dividing bass and treble between two loudspeakers is widely used in the most expensive reproducing systems. You can now achieve similar results by using your existing 12in. L.S. Unit for bass reproduction, with a second speaker for treble, both fed from a Webb's "Cross-over Unit." You will find the bass is cleaner and the treble improved in brilliance and attack; in fact the entire reproduction becomes nearer the real thing.

- WEBB'S CROSS-OVER UNITS**
- Type "A." Cross-over 2,000 cycles ... £2 2 0
 Type "B." Cross-over 1,000 cycles ... £2 12 6
 Type "C." Cross-over 1,500 cycles ... £3 7 6
- Full details of these Units are given in Webb's Catalogue, price 10d., post free. This also includes circuits and values to enable you to BUILD THE UNITS UP YOURSELF

A SELECTION OF ITEMS FROM WEBB'S UNRIVALLED STOCK OF APPARATUS FOR "QUALITY" REPRODUCTION

- "STENTORIAN" S812**
 An Bin. L.S. Unit at reasonable price recommended by Webb's for use as treble reproducer in a dual speaker system. (Available 15 or 30 ohms) £1 8 0
- "W.B." CONCENTRIC DUPLEX SPEAKER**
 Modern design gives outstanding quality of reproduction ... £6 6 0
- "DECCA" PICK-UP**
 Does justice to a good amplifier ... £3 15 4
- "COSMOCORD" GP20 PICK-UP**
 The new crystal approach to "hi fi" ... £3 11 5

WEBB'S RADIO
 14, SOHO ST., OXFORD ST., LONDON, W.1.

Note our SHOP HOURS: 9 a.m. to 5.30 p.m. Sats., 9 a.m. to 1 p.m. Telephone: GERrard 2089.

SALE! SALE!! SALE!!!

To make space in our warehouses in preparation for re-organisation we are "slaughtering" prices of goods offered below. Help us and help yourselves while supplies last. First come, first served, so avoid disappointment and order early.

R1155 COMMISSION RECEIVERS.
 This world renowned 5 waveband R.A.F. receiver is too well known for the specification to be repeated. Every set is guaranteed in working order, and is aerial tested before despatch. Full conversion details for mains use supplied. ONLY £7/19/6 (carriage 12/6).

RECEIVERS TYPE 25.73. Part of the TR 1196. Covers 4.3-6.7 mcs, and makes an ideal basis for an all-wave superhet, modification details supplied. Complete with six valves; 2 ea. of EF 36 and EF 39, and 1 ea. EK 32 and EBC 33. New condition. ONLY 19/6 (postage, etc., 2/6).

RECEIVERS 18. Covers 6-9 mcs, and only requires normal battery supply to operate. Complete with 4 valves; 3 of VP 23 and 1 of HL23DD. New condition. ONLY 15/- (postage, etc., 2/6).

BATTERY AMPLIFIERS. EX-R.A.F. Originally used for inter-comms. on aircraft, but ideal for use as a pre amp or with a grammo pick-up. Complete with valves, QP 21 and HL 210 in original transit cases. ONLY 19/6 (postage, etc., 2/6).

RECEIVERS R1132A. Covers 100-124 mcs, but lends itself to conversion for other frequencies. Has super slow-motion drive and tuning scale, and 0-5 ma tuning meter. Complete with 11 valves, and only requires normal power pack for 6.3v. valves to operate. ONLY 59/6 (carriage, etc., 12/6).

T1154 TRANSMITTING ASSEMBLY. A vital part of the famous T1154 Transmitter, this assembly contains some beautiful transmitting condensers, pre-set tuning devices, variable inductances, large bar and circular knobs, etc., etc. Designed as a complete replacement unit these are BRAND NEW IN MAKER'S CARTONS. ONLY 7/6 (carriage, 3/6).

POWER UNITS TYPE 10. EX-R.A.F. Input 24v. Output 6v, 5 a., 150v, 10 a., 300v, at 70-240 m a. ONLY 12/6 (carriage, 5/-).

AMERICAN INDICATOR UNIT APN4. Less valves but complete with CR Tube 6CP1. Ideal for conversion into a scope, or with pounds in breakdown value. In perfect condition. ONLY 37/6 (carriage, etc., 12/6).

AMERICAN RADAR RECEIVER APN4. Less Valves. In addition to the receiver components this aircraft receiver contains the power supply for the indicator. Contains shoals of components, including 15 valve holders, high voltage condensers, switches, I.F. transformers, etc., etc. Perfect condition. ONLY 17/6 (carriage, etc., 5/-).

INDICATOR TYPE 62. Less valves and CR Tube. This fine two-deck unit is another first-class proposition for component value. Contains 20 valve holders, condensers, resistors, potentiometers, etc., etc. ONLY 17/6 (carriage, etc., 7/6).
 Cash with order and please write name clearly.

U.E.I. CORPORATION

The Radio Corner
 138, Gray's Inn Road, London, W.C.1
 (PHONE: Terminus 7937)

Open until 1 p.m. Saturdays. We are two minutes from High Holborn (Chancery Lane Station) and 5 minutes from King's Cross.

PLEASE NOTE THAT WE SHALL BE CLOSED from AUGUST 8th-14th.

LASKY'S RADIO

Receiver Units Type 25. New and unused. The receiver section of the TR1186 equipment. Easily converted to an all-wave receiver. 6-valve Superhet. Supplied with 6 brand new valves: 2 EF36, 2 EF39, 1 EK32, 1 EBC33. Full details and Circuits supplied free with every unit.

Lasky's Price 25/-. Carriage 2/6 extra. Antenna Rods, Sectional type aerials. Each rod is steel heavily copper plated, 12in. long. Any number can be fitted to set-up ash. diameter.

Lasky's Price 2/6 Post Doctor. Post Free. Radar Indicator Units. Brand new in Original Wood Transit Case

Contains 1 6in. Cathode Ray Tube Type VCR517 and mu metal screen for same. Also the following valves: 3 SP1, 1 6J5, 3 EA50, 1 D1. Dozens of components, including 7 pot/meters, resistances, etc. Enclosed in metal cabinet, size 12in. x 9in. x 19in. Weight 40 lb.

Lasky's Price 49/6. Carriage 7/6 extra. 30ft. Aerial Masts, Brand New in Wood Cases. Ideal for Field Days, or on a permanent site. Supplied complete with all guy ropes, base plate, clamps, hooks, etc. Built in 10 strong ash wood sections, each 3ft. 3in. long, with metal sockets and spigots. Supplied with diagrams and assembly instructions. Weight only 17lb.

Lasky's Price 45/-. plus 5/- carriage. 20ft. Telescopic Aerial Masts, 4 sections, each of heavy gauge metal. Fully extendible.

Lasky's Price 27/6. plus 6/- carriage. Valve Specialists. All Fully Guaranteed.

each	each	each	each
VR91 5/-	KT61 7/6	5Z4 6/-	
VR91 Sylvania 6/6	6J6 5/4	6/-	
3B21 7/6	DH63 6/6	6X5 6/-	
6J6 12/6	KTW61 6/6	P2 3/6	
	HL2 3/6	SP11 3/-	
	32 3/6	SP61 3/-	

These are only a few of the many available from Stock.

Send a 3d. stamp with your name and address for a copy of our current stock list.

LASKY'S RADIO

370, Harrow Road, Paddington, London, W.9 (opposite Paddington Hospital).

Telephone: CUNningham 1974.

Hours: Mon. to Sat., 9.30 a.m. to 6 p.m. Thurs. half day.

Component Mart

VALVES. Brand new and boxed. Two special offers this month: 6J5GT, 3i each, or 6 for 15/-; 6K7GT, 4/9 each, or 6 for 25/-. For single valves add 6d. postage.

HOOVER ROTARY TRANSFORMERS. Brand new and boxed. Type 32. Input 12v. D.C., output 490v. at 65 mA., 3/11 each, plus 1/6 postage.

METAL RECTIFIERS. Westinghouse type. H.T. 300v., 80 mA., 3/6 each. Selenium full-wave bridge, 12v., 5 amp., 15/- each.

ACCUMULATORS. Brand new and boxed. 2v. 15 amp. hours. 4/6 plus 6d. postage.

MAINS TRANSFORMER. Primary 200-250v. 50 cycles; 300-0-300v. 80 mA., 4v. at 2 amp., 6/3 v. at 3 amp. Small size and upright mounting. Ideal for replacement in Philips sets, etc. ONLY 10/6, plus 1/- postage. A very limited number available. Order early.

ELECTROLYTIC CONDENSERS. 3 x 16 mfd., 450v. working. Metal can type, 3/6 each with clip; 1 x 16 mfd., 500v. working. Especially suitable for high ripple currents, 6/6 each with clip.

CHOKES. 6 H., 70 MA., 2/9 each; 20 H., 250 mA., compact size, half shrouded drop through type, 10/6 each.

TUNING CONDENSER. 4-gang, .0005 mfd. tuning condenser, ceramic insulation. Small size, 2/6 each. Please add extra for postage on orders under 1/.




Best Buy at Britain's
**CHARLES BRITAIN
(RADIO) LTD.**

11, Upper Saint Martin's Lane, London, W.C.2. TEL. 0545

Shop hours, 9-6 p.m. (9-1 p.m. Thursday)

OPEN ALL DAY SATURDAY

LONDON CENTRAL RADIO STORES

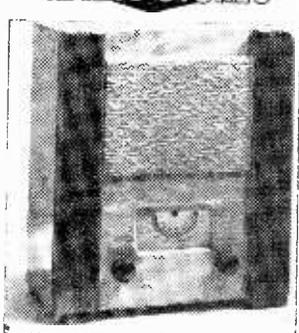

UNREPEATABLE OFFER

4-VALVE SUPERHET UTILITY RECEIVER. Guaranteed in working order. Medium Waveband only. 4 valves, P.M. speaker, pinewood cabinet, size 11" x 12" x 6 1/2". A.C. mains 200/250 volts in good condition, £319 6. plus 5/- carriage and packing.

6 VALVE SUPERHET RECEIVING UNIT No. 25. Easily adapted for S.W. reception for home use. Contains two EF36, two EF39, one EK32, one EBC33 valves, condensers, resistances, etc. Circuit diagram free with every set, 22/6.

BLOWER NEW 2-VOLT VIBRATORS. 7-pin. Self rectifying. 200 volts 60 mA. 7/6.

UNISELECTOR SWITCHES. 6-Bank, a new 37/6.

BLOWER MOTORS. 12-24 and 80 volt, 12/6.

ELECTRIC MAGNETIC COUNTERS. EX-G.P.O. Every one perfect, as new. 500 ohm coils counting to 9,000. Operates from 25-50 v. D.C. 7/6.

NEW U.S.A. HEADPHONES, 120 ohms, 4-pair.

EX-GOV. COPPER AERIAL with Insulators, 4/3 100ft.

NEW OSRAM PROJECTOR LAMPS. 12 volt 100 watt, 9/6.

12 inch A.C. 140 TUBES. Blue Screen Magnetic Deflection, magnetic focus, 6kv. Heater, 4-volt International Octal Standard Connections, £4/10. VALVES EF50, 5/6, SP11, 4v. 6/3, 3/6; 6J5, 3/6; EBC33 and D1, 2/6 each.

5-WAY COVERED COPPER WIRE. 12 yards 5/6.

TELEPHONE HAND SETS. 8/6.

NEW 130 H.P. MOTORS. 200 volt A.C. D.C. double ended, 37/6.

MOVING COIL HAND MICROPHONES. 30 ohm Voice Coil, 5/6.

We have a large stock of A.C. Mains Sets at greatly reduced prices, from 45/- to £15, for callers to suit themselves. R1155, equal to new, with power pack, £16. Set only, £9/15/-, all guaranteed, 7/6 carriage and packing. Diagram with all Receivers.

W.A.K.H. TALKIE No. 38, MR. H. Complete with valves, ONE PAIR Throat Microphones, ONE PAIR Headphones, Ready for use. Except for Aerial and Batteries. Wiring Diagram and Instructions with each set. £3 8/6. Postage and Packing, 2/6 extra.

EX-R.A.F. 1155 RECEIVER. complete with Power Pack and Eight-inch P.M. Speaker, 200 250 volts A.C. £14 10/- carr. paid.

EX-R.A.F. 1155 POWER PACK. 200 250 volts A.C. £4 10/- Carriage and Packing 5/- extra.

12 VOLTS POWER PACK. Suitable for Philips 12 volts Communication Receiver P.C.R.11, £5. Carr. paid.

ACCUMULATORS. New 6 volts 85 amps. Size 12in. x 9in. x 7in. Weight approx. 47lbs. £3/10/- Carr. and packing 5/- extra.

ACCUMULATORS. New 6 volts 125 amps. Size 13in. x 8in. x 10 1/2in. Weight approx. 52lbs. £4 7/6. Carr. and packing 5/- extra.

23, LISLE STREET, W.C.2.
Telephone: CBRard12699

SAMSONS SURPLUS STORES

Crystal Lapel Mikes, 1 1/2in. diameter, extremely sensitive, 12.6, post 9d.

Co-AXIAL Cable, 30ft. lengths, complete with Fye female plug each end, 80 ohms. Brand new, 7/6, post 1/3.

Heavy Duty Auto Transformer, tapped at 110, 150, 190, 230 v. 1.6 Kva. £4 10s. Od. Carriage, 5/-.

L.T. Transformers, 6.3 volts 15 amps. 15/- brand new. Post 1/6.

Aerial Masts, 36ft. R.A.F. Type 50. Complete kit consists of 9 tubular sections, 2in. diameter, set of pickets, Box plate, guy and all fittings. Brand new in canvas carrying bag, £3 15/-, Od., carriage 7/6.

Type "38" Trans-Receiver, brand new and complete with 4 ARP2s, but less ATPJ and control switch. Freq. range 6-9 mc/s., 15/-, post 1/6.

Throat Mikes, and Earphones for the "38" are in stock at 3/6 each.

Brand New 12 v. Vibrator Packs, completely smoothed and rectified, output 210 v. D.C. 70 ma. 19/6, post 16/-.

A.H. Alkali Batteries, 2.5/2.0 volts 10 A.H. A.C. new. Made by Britannia Batteries Ltd. 12.6, post 1/-.

12 Volt 14 A.H. Batteries by Pritchett & Gold. Brand new, in teak cases. 25/-, post 2/6.

Heavy Duty Slide Resistor, 152 ohms 2 amps. Twin coils with wheel control. Brand new. 32/6, post 1/6.

169/171 Edgware Road, London, W.2.
Tel.: Pad. 7851.

125 Tottenham Court Road, W.1.
Tel.: Eus. 4982.

All orders and enquiries to our Edgware Road branch, please.

MIDLAND INSTRUMENT CO.

For New Govt. Surplus Stock.

TRANSFORMERS (AUTO), 1.6 KVA., 230v., 1-phase 50 cycles, tappings for 40-80-110-120-150-190v. at 7 amps., 45/-, carriage 5/-.

TRANSFORMERS, 0.4 KVA., tapped primary 100-200-250v., 1-phase 50 cycles, output 17.5v. tapped at 14v. at 20 amps. 35/-, carriage 5/-.

L.T. RECTIFIERS, metal, full wave, 12v. 1 1/2 amp., with all data, 7/6, post 9d.

TRANSFORMERS, input 210-230-250v., output tappings for 3-4-5-6-8-9-10-12-15-18-20-24-30v., 20 amp. 20/-, post 1/-.

PARMEKO RADIO TRANSFORMERS, drop through shrouded type, input 110-225-245v., output 250-6-250v. at 90 mA., 5v. 2amp., 6.3v. at 3amps., screen, 17/6, post 1/-.

PARMEKO POTTED CHOKES, 3.6 to 4.2 H., at 150 mA., 20 H. at no D.C., weight 4 lbs. 7/6, post 1/-; ditto 100 H. at 10 mA., 5,000 r.m.s., weight 1 1/2 lbs., 5/-, post 9d.

BELL TRANSFORMERS, output 230/250v., output 4 and 8v. at 1 amp., 2/8, post 7d.

IMPERIAL 1155 TRANSFORMER, 230v. A.C. D.C. 500 volts, fitted high grade thermostat which cuts out at 80 deg. C. and in at approx. 3 degrees less, 12/6, post 1/-.

HIGH VACUUM PUMPS, also suitable as air compressors, rotary type gives even pressure, fitted 2in. lumps, 1in. dia. shaft, 15/-, post 1/3.

GENERATORS, MK-11 "A", for electrical engine speed indicators, 10/-, post 1/-.

BON KITES, dinghy antenna type, 36in. x 17in. 47in. flying cord and screw cap metal box container, 12/6, post 9d.

OIL TEMPERATURE GAUGES, 0-100 deg. C., 40ft. flexible tube and mercury capsule, 7/6, post 9d.

TELESCOPIIC DITCHING MASTS, extend to 7ft., 1in. dia. 1/2in. electric line motor for electric line, tapers to 7 1/2in., ideal for T.V. Aerials, microphone stands, fishing rods, etc., weight 6 oz., 7/6, post 6d., 3 for 20/-, post 9d.

SERIES MOTORS, 12v. 20 amp. D.C., 1 h.p., fitted 1in. dia. shafts, 7in. long, 4in. dia. an ideal motor for electric lawnmowers, etc., 15/-, post 1/4.

TELEPHONE SETS, consists of 2 combined microphones and telephones, coupled with twin flex they provide Perfect 2-way communication, sound power, no battery required, with 25ft. twin connecting flex, 7/6, post 9d.

MOORPOOL CIRCLE, BIRMINGHAM 17

Tel. HARBORNE 1308 or 2864.

Programme Pointers

This Month MAURICE REEVE Deals with Some More Recent Programmes

FREQUENTLY a certain thing happens with persistent regularity—under our very noses, as the saying has it—of which we are going to take notice some day, but never do. Usually it is something of no very great consequence to us, otherwise we would not let it go by week after week without giving it our attention. Nobody could imagine the original "Twenty Questions" or "Itma" living very long without receiving our very prompt and favourable patronage: might as well think of a leaking burst pipe or a barking dog going unnoticed. And so it was with "The Soviet View" until I read that questions about it had actually been asked of Ministers in the Mother of Parliaments as to the unwisdom of letting the thing be put over. I at once looked it up in the *Radio Times* and learned that no less than the twentieth instalment was to be heard on May 3rd.

What was all the fuss and blather about? We know funny questions get asked at Westminster about all sorts of peculiar things, but if number 20 of this excessively lengthy series struck the average for the whole, some of our representatives certainly seem to get the wind-up over very little. The usual quotations from the Soviet press—the whole thing is a collection of Russian press and broadcast points of view as directed to listeners in the U.S.S.R.—about the "capitalist beasts" and "the Western warmongers" left me stone cold and more than a little sceptical of the translator's abilities. Of the rest, I faintly remember something about barber's shops, the difficulties of the Russian housewife, and such-like innocua. All very silly, futile and boring.

A very good programme of its type was "The Story of Madame Tussaud," April 18th. The first half, or more, might have been mistaken for "Scenes and Incidents in the French Revolution," so many heads fell into the basket, and so long and lusty were the shouts and huzzas of the mob—too lusty and too plentiful. But the story of how the original and young Madame Tussaud modelled them and afterwards brought them to England and toured with them, thus founding the famous exhibition, made a capital story which few of us, probably, knew anything about.

Scrapbook

"COUNTRY MIXTURE." The sixth of this scrapbook programme series, presenting facts, fancies, legends, songs and stories of the western counties, presented Dorset, and gave a delightful hour's entertainment. I hope the whole of Great Britain can be similarly covered. Dorset has ever been one of our most beautiful counties, perhaps a little undeservedly overshadowed by its illustrious western neighbour, but given a new lustre and added fame in recent years by the immortal Hardy. The series, free from the blight of the cheap, vulgar record which so mars "Down Your Way"—an otherwise rather similar feature on a parochial scale—brings home to us the beauties

of our country in all its manifold variety and tradition; a salutary lesson for all.

Scott has long been a favourite author of mine, and though sales of his works are not what they once were, it does not necessarily prove us right and our fathers and grandfathers wrong. In any case, their bulk is sufficient to make any budding writer of to-day employ a whole-time secretary working out the income-tax they would render him liable to pay. The three-part adaptation of "Ivanhoe," by J. R. Gregson, made capital radio material, full of colour and alive with action. The effects department had a glorious time and did not labour in vain. "The Talisman" should be equally effective. And how about "The Bride of Lammermoor" for a Sunday evening serial? Galsworthy and Trollope are, I learn on the best authority, badly in need of a long rest.

Steel

"WE WORK IN STEEL" (April 11th) I also liked very much. The story, briefly, only dealt with the industry during the last 20 years, and was based on a steelworker and his family who, after passing through the great depression and drawing the dole in the '30s, recover their prosperity and a bit more in the boom of the war years, the whole winding up with a diplomatically balanced peep into the industry's future under nationalisation. Whether the programme might have been even more effective had a more historical approach been made to the subject; whether a little more of the origins and developments of steel-making processes and a little less of the joys and sorrows of Mr. and Mrs. Wilson and family would have been more acceptable, I wouldn't know. It would certainly have made a different feature. So we'll leave it at that and repeat that it was a very moving and human documentary.

"Itma's" Successor

"TAKE IT FROM HERE" may be "the successor to Itma," just as anything else may be styled the successor to Gilbert and Sullivan or "The Merry Widow." Whether the succession is justified is quite another matter. Everything has to be succeeded, we know, and if the heir is not as worthy as its sire it's just too bad, and the best available must come into the inheritance. But anyone who tells me that the present No. 1 radio variety show—which is how I believe it is ranked—is as good as Itma was, then I say, with all the deference that emphatic disagreement permits, "Sir, or Madam, you simply do not know what you are talking about." A very easy way of proving this would be to listen to an old Itma programme and compare the almost continuous hail of laughter which accompanied those programmes throughout their lengths with the comparative quietude and sobriety in which the present shows are played. There is not one character of "Take It From Here"

that will be talked of five minutes after it gives its last show. But Col. Chinstrap, to name only one from Itma, is still talked of and quoted as we quote Dickens.

Theatre Productions

"FLARE PATH" and "Mary Read"—the latter notable for the presence of Flora Robson in the title role—were good theatre productions. "Flare Path" set Terrence Rattigan on his very successful career as a playwright. But, good as "Flare Path" is—and what a success it achieved during the war!—it seemed strangely unreal five years after; unlike "Journey's End," which moves us to our depths every time it is put on.

"Silence in Heaven" was also very interesting but I was very amused to notice that, though the story occurred in the house of a family which must have been able to easily afford excellent quality stair carpets, there was an excessive amount of running up and down obviously uncarpeted staircases.

The opera orchestra has settled down to a very capable instrument under the leadership of John Sharpe and conducted by Stanford Robinson. They give many well varied and interesting programmes. In a "Music in Miniature," one Friday, Cyril Smith played Albeniz's glittering "Triana" as though it were "Tunbridge Wells," by Archibald Snooks, from his "Famous Spas" cycle.

News from the Clubs

SOUTH MANCHESTER RADIO CLUB

Hon. Sec. : M. I. Wilks, 57, Longley Lane, Northenden, Manchester.

AFTER a very successful run with membership increasing at each meeting, activities were concluded with D/F Contest. The club station operated portable at Castle Mills and the first team under G2AUC located the site in one hour ten minutes, followed by G3ESK and his followers nineteen minutes later. Three other entries had difficulties with their receivers and in order to join the rest of the club for tea had to open the sealed envelopes containing details of the location of G3FVA/P. In spite of bad weather, all agreed it had been a most successful afternoon and plans are already under way for a repeat performance, with the winners this time operating the transmitter and the committee forming a team. An 8 mm. cine film was taken of the event by G3BYP, and it is hoped to show this at the Hamfest.

A later meeting was devoted to a general discussion, and a special general meeting was held to amend certain parts of the club's constitution the evening being concluded with last-minute arrangements for the D/F contest.

At the meeting on the 9th June, G2AUC and G3ESK spoke on their experiences during the D/F contest, explaining the gear used.

Several talks by outside lecturers have been arranged, but dates for these are not yet available.

Prospective members are invited to our fortnightly meetings at the Church Schools, Northenden, meetings for July are 7th and 21st at 7.30 p.m.

WORTHING AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec. : A. B. Forge, G3FRG, 2, The Plantation, Worthing, Sussex.

MEETINGS of the above club are held the second Monday of the month at the Adult Education Centre, Worthing, at 7.30 p.m.

THE MIDLAND AMATEUR RADIO SOCIETY

Hon. Sec. : W. J. Butler, 32, Pilkington Avenue, Sutton Coldfield.

DR. SUMNER recently lectured on The Human Vision in relation to Television. The membership greatly appreciated the lecture and looked forward to further evenings with Dr. Sumner.

The Society holds monthly meetings on the third Tuesday at the Imperial Hotel.

THE WEYMOUTH RADIO AND TELEVISION CLUB

H.Q., 74, Franchise Street, Weymouth, Dorset.

THE Club has now settled into new H.Q. A transmitter has been installed with the call-sign G3GNU. Membership is good; a few members holding their own licences. A receiver has been installed and various equipment for the use of members. Monthly meetings are held on the last Thursday of each month at 7.30 p.m. The club is open every evening and members have their own keys for the H.Q. Lectures are being given each week on the construction of television and of local details for the club's own television in the future. Prospective members are always welcomed. The section is anxious to increase its membership. A club news sheet is published each month. Morse classes are available for those wishing to commence or improve their C.W. The club is now eight months old, and it is hoped to increase the membership. A visit to a B.E.C. transmitter is soon to be arranged for members.

READING RADIO SOCIETY

Hon. Sec. : I. Hensford, G2BHS, 30, Boston Avenue, Reading.

RECENTLY Dr. Lemon (G2GL) gave a talk and demonstration on Lightning. The generation of high voltage electric charges, and some of the properties of these charges were shown. The effect of installing lightning conductors was demonstrated by subjecting models to very high voltage D.C. discharges (100KV approx.). Many questions followed.

Mr. Stride, of Ekco, Ltd., talked on Frequency Standards and Frequency Measurement, demonstrating a "Ham"-built frequency meter, with an accuracy of two parts in 100,000.

A postal ballot has shown the majority of members to be in favour of the present system of two main society and one instructional section meetings per month; but with a higher proportion of talks and demonstrations by local Hamns at the main society meetings, in place of the commercial firms as at present.

BRIGHTON AND DISTRICT RADIO CLUB

Hon. Sec. : L. Hobden, 17, Hartington Road, Brighton.

CLUB evenings, during the summer months, will have talks and ragchews on alternate Tuesdays. More ragchew time seems essential, as members find time short after any talk or demonstration held. The club TX (G3EVE) will also get more frequent "airings." June programme includes a further talk on aerials and a lecture by a local society connected with T.V.I. locating. The club is also participating in NFD.

EDINBURGH AMATEUR RADIO CLUB

Hon. Sec. : David A. E. Sanson, 56, Elm Row, Edinburgh, 7.

THIS club is going along very well and now has its own transmitter operating under the call sign GM3HAM.

During the summer months meetings will be curtailed, but weekly meetings will continue until the first Wednesday after NFD, and thereafter at fortnightly intervals until the annual general meeting on September 13th.

POOLE AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec. : J. Loader, 5, Highwood Road, Parkstone, Dorset.

THE club, now five months old, is going ahead, three more members being enrolled at the last meeting, when G5GG gave a talk on Audio Filters. Meetings are held on the first and third Mondays in the month, a junk sale being held shortly in order to raise funds for the club's ticket, due any day now, when the club's TX will be active on 160, 20, 10 and 2. New members are always welcome and will be sure of a seat as the club can seat 50 comfortably (on chairs, too!). Refreshments will shortly be provided.

THE WEST MIDDLESEX AMATEUR RADIO CLUB

Hon. Sec. : P. F. Blomfield, 213, Harrow View, Harrow, Middlesex.

MEETINGS of the club are held on the second and fourth Wednesdays of the month at 7.30 at the Labour Hall, Uxbridge Road, Southall, Middlesex.


At the annual general meeting the following were elected as club officers and committee.

Hon. Chairman: H. C. Bostock.
 Hon. Sec.: P. F. Blomfield.
 Hon. Treasurer: C. Gott.
 Hon. Asst. Sec.: G. E. Bunt.
 Hon. Librarian: H. K. Winwood.
 Committee: L. E. Hickingbotham, P.T. Smith.

News from the Trade

A New "Melody Maker"

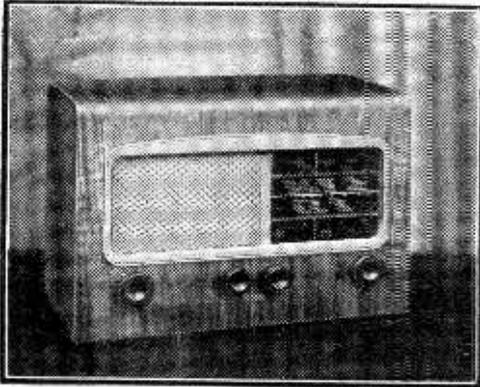LAST year's Radiolympia revival of the Cossor "Melody Maker" has proved immensely popular with both trade and public, but there are many who have asked for a wood cabinet version. This has now made its appearance as Model 500 at 17½ gns., tax paid. While following the general specification of the current set, the opportunity has been taken to introduce one or two circuit



The new "Melody Maker," Model 500.

modifications which result in improved signal-to-noise ratio and more efficient tone control.

The appearance is very nice, with polished walnut cabinet, larger dial with three-colour calibrations, and "gold" metal grille.

A. C. Cossor, Ltd., Highbury Grove, N.5.

High-voltage Adaptor

IN the next column is an illustration of the Model 341 High Voltage Adaptor being produced by Taylor Electrical Instruments, Ltd., the nett price being 37/6.

By use of this adaptor the D.C. voltage range of the Model 170A Electronic Testmeter can be extended up to 10 kV.

With the present demand for reliable indication for voltages up to that figure this adaptor increases the scope of usefulness of Model 170A to a considerable extent, particularly where television service work is concerned.

Taylor Electrical Instruments, Ltd., 419-424, Montrose Avenue, Slough, Bucks.

New Miniature Hearing Aid

FOR the past 27 years Mr. Victor Foot, F.I.P.I., A.M.Inst.B.E., the well-known radio engineer and inventor, has devoted his life to the

improvement of hearing aids. In 1938 he was the first man to instal Hearing Aids in London Theatres, Cinemas and Concert Halls.

Now Mr. Foot has produced a new Ossi-Caide hearing aid which weighs only 4 ozs. This compares most favourably with the government "issue" hearing aid which weighs 1 lb. 10 ozs. It incorporates the three miniature valves recently developed by Mullards. Made of aluminium its case contains two minute dry batteries and its size is only about 3 x 4 in. But these new Ossi-Caides can also be bought with an electro-magnetic pick-up and would thus enable a deaf person to listen in to the radio while working out in the garden, hearing a baby cry indoors while outside their house, etc. The retail price is £31 10s. 0d. (thirty guineas).

Ossicaide, 24, Kensington Church Street, W.8.

Service Aids

THREE interesting new lines are announced by the British Distributing Co. They are:

Nylon Drive Cord.—50ft. cord, retail price, 4s. 6d. A guaranteed perfect grip, non-stretch, glass-cored drive cord. This material is available to manufacturers and large users, on reels of a few gross yards at a lower price.

Radio Cement.—Retail price, 1s. 6d. Perfect adhesive for all radio and workshop uses. (Cellulose cement based).

Switch and Contact Cleaner.—Retail price, 3s. A very efficient dirt and verdigris remover, for use on all electrical and radio contacts.

The British Distributing Co., 66, High Street, London, N.8.



Mr. Victor Foot demonstrating his latest miniature hearing aid to trade buyer Joan Masters, of New Malden, Surrey, at the B.I.F.

OPEN TO DISCUSSION



The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

R.F. Capacity Meter

SIR,—I have studied with interest the article describing the "R.F. Capacity Meter," in the June issue of PRACTICAL WIRELESS, and wish to point out that the appendix to the article contains a number of errors, some of which may have been introduced in printing and of them you may well be aware.

The whole of the proof, however, is very misleading since it sets out to prove that the capacity of a condenser can change with frequency, which is not true. The writer of the article has, in fact, shown that a given parallel circuit of resistance and capacity can be replaced by an equivalent series circuit (with properly chosen values of R_s and C_s) giving the same impedance and phase relationships for a given frequency as the original. At low frequencies the values of R_s and C_s will approximate closely to the values of R and C used in the parallel circuit but at high frequencies the formulae derived in the appendix to the article will have to be applied to given values of R_s and C_s applicable to each frequency used. Under no circumstances, however, can the capacity of a perfect condenser be regarded as anything but a fixed quantity.

The true reason why a low frequency investigation of capacities below about $0.1 \mu\text{F}$ cannot be made with accuracy is that the impedance offered by such condensers to low frequencies is very high and small differences between these high impedances are difficult to measure. Using the apparatus described with a frequency of 1 Mc/s or so and producing audible beat notes with a fixed radio frequency carrier, a high degree of accuracy may be expected. The use of too high a frequency would, of course, make the reactance of the condensers used very small and the ordinary circuit wiring losses would become important, and 1 Mc/s would seem to be a good compromise frequency for the range of capacities to be tested.—A. W. DALE (Leeds).

[The Author states: I have given Mr. A. W. Dale's letter a very careful reading and have come to the conclusion that he has failed to grasp the purpose of the appendix to my article. That purpose was, as the first sentence states, "To prove that a condenser behaves as a lower value of capacitance at increased frequencies due to series resistance." We are not considering perfect condensers, such do not exist except as concepts to simplify and clarify calculations. What we do consider is the sort of condenser an amateur or a radio service engineer handles every day—a practical condenser possessed of a variety of imperfections due to dielectric polarisation, lead resistance, plate resistance (especially in silver mica), etc., insulation resistance and effects due to corona in high-power, high voltage condensers.

It is standard practice, as you will very well know, to consider a normal, every-day condenser as being equal to a perfect con-

denser with a resistance added either in series or in parallel to simulate the effect of lumping all the causes of power-loss into one easily handled quantity. The magnitude of the resistance is chosen so that an equal amount of energy is lost in it as would be lost in all the imperfections of the normal condenser.

I would refer Mr. Dale to the following text-books, where he will find that the capacity of a condenser can and does change with frequency.

1. "Experimental Radio Engineering"—Rapson. Exp. 43 and 44. Pp. 69-71.

2. "Fundamentals of Radio"—Terman. Pp. 10-12.

3. "Radio Engineers' Handbook"—Terman. Pp. 109 and 110.

As to the errors in the equations these are so slight that nobody is likely to be led astray by them. They are, 1. three " μF s" have slipped down out of line with the division bar, they also should be pF s, i.e., Farads. 2. A slide-rule slip gave the final answer as 42.3 pF , this should be about 46 pF .—R. H. Q.]

One-valve Signal Generator

SIR,—In the June, 1950, issue of PRACTICAL WIRELESS you have printed a circuit of a one-valve signal generator (Page 249) from 5-206 metres.

Looking at the circuit at A.2, R.F. is connected to a $25 \text{ k}\Omega$ pot via $.005 \mu\text{F}$ condenser to H.T. +.

Surely no signal will pass due to the $16 \mu\text{F}$ electrolytic condenser from H.T. + to earth? This will stop any signal passing. Can you please check this, as I am very interested in the circuit? Also, can you explain the need for a 150 pF trimmer across the 500 pF tuning condenser for extending range?—P. POYNTER (Sutton).

[In reply to Mr. Poynter's letter, may I say he is quite correct in his opinion that the $16 \mu\text{F}$ electrolytic will bypass the R.F. to earth. The original signal generator was built as a separate unit and used with a commercial power pack which, no doubt, had a dropper resistor between the $16 \mu\text{F}$ capacitor and the output terminals which in this case would, of course, be the R.F. output connection. The power pack diagrammed was, in fact, an afterthought added simply for the benefit of younger readers who may not be familiar with power supply connections.

An H.F. choke or a resistor of about $10,000\Omega$ will serve effectively to prevent this bypass action if placed between the electrolytic and the R.F. terminals.

The purpose of the 150 pF trimmer is to extend the range of the medium-wave coil to cover the 465 to 473 Kc/s frequencies used in so many I.F. stages. The coil used is a standard medium-wave coil which, with a $.0005 \mu\text{F}$ tuning condenser, covers up to about 550 metres. The addition of the trimmer extends the range to 645 metres, in other words 465 Kc/s .—T. W. D.]

"Simpliscope"

SIR,—With reference to my article in the June issue, the "Simpliscope" was designed for use in the audio frequency band. Only one range of sweep control was incorporated in the oscillator circuit as it was felt that there was little to be gained by including sweep frequencies much below 50 c.p.s., and the range chosen has an upper limit at about 500 c.p.s. For normal use this is quite

sufficient if the user does not mind seeing a number of waves in the trace; for instance, a 5,500 c.p.s. input will give about 10 waves on the screen and normal sine wave distortion may readily be observed. If a higher range is desired, the 500 pF condenser from V_1 anode to grid should be reduced to, say, 100 pF. It should not be necessary to alter the value of the screen to suppressor condenser, thus a simple switch may be used, but the leads must be kept short.

The signal amplifier will give reliable results up to the highest audio frequencies, but there is no compensation for the phase shift which occurs at high frequencies and may lead to some distortion on, say, a square wave trace at frequencies above 5 Kc/s.

I have taken care to point out and even exaggerate the shortcomings of the instrument when compared with a normal commercial machine, but over ten years of experience with oscilloscopes has convinced me that simplicity is the goal to aim at in the design of a general workshop scope and, if any extra facilities are required, the circuits can be "added on" and designed to suit the type of work in hand.—F. R. PERRY (Herne Bay).

Delivery Dates

SIR,—I read with interest in your discussion columns Mr. Baker's letter from Bristol re "delivery dates" in the June issue. I have had a similar experience.

I purchased a double-diode-triode battery valve of a well-known make at the full standard price (14s.) through one of your advertisers. Unfortunately for me, I had it some time before using it, as my time was very limited towards building the set I intended it for, which was a P.W. experimental set for battery fidelity in which the valve was used as a detector amplifier.

The results were excellent, excepting that the valve was intermittently microphonic. Clarity and volume were good, but the slightest touch on the valve caused the speaker to ring like a bell, and the slight ringing rose and died away intermittently whilst the set was in operation.

The retailer to whom I returned the valve for his opinion suggested sending it to the manufacturer for "test" with a view of replacement, and gave me the necessary form to fill out. And that was the last I saw of my valve. The result of the "test" was contained in a statement from the manufacturer a fortnight later, which told me that the guarantee period had expired—just that and no more.

I waited a fortnight or so for the return of the valve and then wrote asking for it back. The reply came back stating that as it had been through a third person's hands they hinted the retailer might have it. I wrote him and he, of course, had not received it.

I wrote a second letter to the manufacturers and informed them of this, and asked for my property back as they should have no interest, as the guarantee had expired, and offered to send the cost of packing and postage.

Their reply to this was that *all valves* sent to them were "tested" irrespective of the guarantee having expired. Those valves which did not come up to their standard were disposed of. This I was told was the usual method of the trade.

I wrote a third letter pointing out that legally I considered they had no right to destroy my property, especially as the valve was perfectly usable and I might have been able to minimise the defect by cushioning the valveholder.

To this I had a reply that since I sent the valve at my own invitation they could not be expected to accept any responsibility for its safety—but had I stated on the form or with it, which accompanied the valve to the manufacturers, that I wanted it to be returned they would have returned it.

Unfortunately for me, this question did not appear on the form as to the valve being returned to me, so I unknowingly sent the valve 200 miles or so to be scrapped after a try-out with the set and at a cost to me of 14s.

These faults should be found out at the test bench before the valves are marketed, and not at the user's expense.—W. GOSLING (Liverpool).

The Beginner

SIR,—I have recently spent a few evenings in reading through back numbers of PRACTICAL WIRELESS, and a paragraph on the Editorial page of one of them has prompted me to write to you.

On February 1st, 1936, you wrote: "... Future issues will devote a considerable amount of space to the newcomer, and articles will be given ... to bring the beginner into line with the experimenter who has been following broadcasting since its inception."

This was practical and sensible and I, for one, would be glad to see this policy adopted afresh to meet the needs of a new generation of newcomers to this most fascinating of hobbies.

The basic principles of radio, I suggest, are best learned by a combination of theory and practical work. Would it be possible to embark on a course, starting with the simplest receivers as a basis to illustrate elementary theory and adding to these as the reader's knowledge increased?

With proper guidance, such as your journal could give, it is possible to obtain a good deal of knowledge and experience without heavy expense, and I suggest that to help your less experienced readers along such lines would be to render a real service to amateur radio.—F. PICKBOURNE (Liverpool).

[We commence a useful series for the Beginner on page 356 of this issue.—ED.]

Editorial and Advertisement Offices: "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. 'Phone: Temple Bar 4363. Telegrams: Newnes, Band, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

RODING LABS.

2 volt Battery Superhets, 6.9 Mcs. Chassis taken from No. 18 Tx/Rx. Tested ready for use, 18/6, post 1/6.

New IN34 Crystal Diodes, 5/3.

Meters, 4 1/2in. 0-200 microammeters. First grade, 42/9. 2in. 0-500 microammeters, 8/- . 2in. Mic 0-300 v., 10/- . 0-40 v., 7/6.

Multimeters, 2 1/2in. Supplied with black bakelite case, 6in. x 4 1/2in. x 1 1/2in., and resistors for D.C. ranges 0-30 v., 150 v., 300 v., 600 v. and 60 mA. Also scale reads ohms 0-5,000 with 1.5 v. battery, 16/6 each.

Headphones, with breast plate microphone. Packed in wooden boxes. Operate with 4 1/2 v. battery, 10/- a set.

Miniature Slow Motion Dials, 100-1, worm geared, 2 1/2in. x 2in. Scale 0-100, precision made, 4/- each.

New Brown's Moving Reed Headphones. Best in the world, 6/6.

200-250 v. A.C. or D.C. Motors, about 1/2 h.p., fitted with 2 1/2in. x 1/2in. high grade grindstones, medium or fine, made by Nortons, 20/-.

New Carbon Microphones, U.S. made for Type 58 Walkie Talkie, 3/-.

Powerful Small Motors, 3 1/2in. x 2 1/2in. x 2 1/2in., 24 v. A.C./D.C., with geared spindle, 8/6. Transformer 230/24v., 16/-.

24 v. A.C./D.C. Motors, 5in. x 3in., fitted with powerful blower fan. Can be used for paint sprayers, vacuum cleaners, etc., 14/- . Transformer 230/24v., 16/-.

Filament Transformers, 4 or 6v. 4A. 6/6.

All post paid. Money back guarantee from:

THE RADIO & ELECTRICAL MART
253b, Portobello Rd., London, W.11
Phone: Park 6026.

have the following out-of-Season brand new stock for disposal. BUY NOW AT UN-REPEATABLE PRICES! Mail only.

LOUDSPEAKERS: P.M. 5in., 10/- 6in. w/t, 15/- 8in., 16/6 10in., 22/- Mains energised 8in., 1.250 ohms or 400 ohms field, 15/- 10in. w/t 1.250 ohm field, 22/- . Please add 1/- post per speaker.

CONDENSERS: .005 1,000 v., .002 1,000 v., 2/9 doz. .002 miniature, 3/6 doz. (Special bulk prices for manufacturers), 100 pl. S.M. 4/6 doz. (post extra).

RESISTORS: 1 w., 2/- doz.; 10- 100 (2.7 k., 270 k., 1.2 meg.) (post extra).

CATHODE RAY TUBES: New VCR97 (in crates) especially selected for Television receivers 40/- plus 3/- carriage.

CHASSIS: Polished Aluminium 12 x 9 x 2 1/2in., 16 s.w.g. folded 4 sides, 8/6 (post 9d.).

CABINETS: Walnut veneer (polished) sloping front, with baffle and back, size 2 1/2in. x 1 1/2in. x 10 1/2in., 35/- (post, etc., 4/-).

VALVES, etc.: VR91's, 4/-, 71A, 2/- ea. or 15/- doz.!!! VR91 holders, 6d. ea. Selenium rectifiers 230 v. 30 mA, 4/3 ea. Neons (no resistance), 2/- ea. (Post extra).

CAR RADIO: 1 only. EKO 12 v. (latest model—slightly soiled), 15 gns. (2/- post).

Be quick! First cheque secures. Our standard lines are, of course, available as usual from stock.

MODEL 30. Famous 5 waveband superhet Coil Packs, aligned and sealed, 29/9 inc. **MODEL 40** Coil Packs—similar, with R.F. stage, aligned and sealed, 57/6 inc.

I.F. TRANSFORMERS, i.e. high stability, aligned and sealed to 465 kc/s, 13/6 pr. **MODEL 30 TUNING UNIT:** Consisting of 30 Coil Pack, pair of "M.M." I.F. Transformers, matched 2-gang and attractive Dial. Components aligned together as a unit and sealed, 54/9 inc.

MODEL 40 TUNING UNIT, similar, with R.F. stage, 66/9 inc.

BITTER unit available with JB Spin-wheel tuner for 20/9 extra.

For further information, host of circuits, etc., let the "Home Constructor's Handbook" be your guide to radio realism at low-cost! Price 1/6 or FREE copy given with all orders over 1/.

RODING LABORATORIES (Dept. W.A.),
70, Lord Avenue, Ilford, Essex.

YOU can become a first-class RADIO ENGINEER

We are specialists in Home-study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

T. & C. RADIO COLLEGE

Post in unsealed envelope, 1d. postage

To: R. Heath Bradley, T.C.R.C.,
50, Harland Road,
Southbourne, Bournemouth.

NAME

ADDRESS

P.1c8

THE MODERN BOOK CO.

The Radio Amateur's Handbook.

By A. R. R. L. 20s. Postage 9d.

A Home-built F M Receiver. By

K. R. Sturley. 4s. 6d. Postage 3d.

Practical Wireless Circuits. By F. J.

Camm. 6s. Postage 4d.

Wireless Coils, Chokes and Trans-

formers. By F. J. Camm. 6s.

Postage 5d.

Television Servicing Manual. By

E. N. Bradley. 4s. 6d. Postage 3d.

Cathode-Ray Oscillographs. By J. H.

Reyner. 8s. 6d. Postage 5d.

The Antenna Book. By A. R. R. L.

10s. 6d. Postage 9d.

Radio Valve Data—Compiled by

"Wireless World." 3s. 6d. Postage

3d.

Radio Servicing—Theory and

Practice. By A. Marcus. 35s. Postage

9d.

Reproduction of Records. By J. H.

Brierley. 3s. 6d. Postage 2d.

Loudspeakers. By G. A. Briggs. 5s.

Postage 3d.

The Magnetic Amplifier. By J. H.

Reyner. 15s. Postage 9d.

Radio Amateur Call Book Magazine

—Spring number, 16s. Postage 9d.

Radio Handbook, 12th Edition.

By Editors and Engineers. 25s.

Postage 9d.

Vacuum-Valve 1950. By P. H. Brans.

21s. Postage 9d.

We have the finest selection of British

and American television and radio

books in the Country. Complete list

on application.

19-23, PRAED ST.

(Dept. P 8)

LONDON, W.2.

PADddington 4185

TELEVISION COILS

(Suitable for Viewmaster)

MIDLAND 25/6

WAVELENGTH

LONDON 18/6

WAVELENGTH

per complete set.

From your local retailer, usual

factor, or:—

British Distributing Co.

66, High Street, London, N.8

AUCTION SALE

A Nationally Advertised AUCTION

SALE of Manufacturers, Wholesalers

and Dealers Surplus Stocks will be held

at the

BINGLEY HALL, BIRMINGHAM

Largest Hall in the Midlands

Sale days: Wednesday, Thursday, Friday,
July 19th, 20th, 21st, 1950. Viewing days:
July 17th, 18th.
1,500 Lots include a large quantity of Radio,
Electrical and ex-Government stock.
Prospective Buyers should write for a
Catalogue (to be forwarded when ready)
enclosing 6d. stamps.
Write or phone the ORGANISER (to the sponsors)
J. E. FARMER,
Farmer & France, Ltd.,
St. John St., Bromsgrove, Wores.
Tel.: Bromsgrove 2442 or
HARBORNE (B'ham) 1308
Auctioneers to the Sale:
Walters & Son, Bingley Hall, Birmingham



Simple self-feed speeds up soldering. Better work. Saves solder. Write for interesting leaflet 29 J

RUNBAKEN - MANCHESTER

LOUDSPEAKER SEPARATOR

A unit to divide the output between two loudspeakers feeding one with bass and the other with treble. This increases frequency response, improves clarity and reduces inter-modulation.

The unit may be used with any speakers of 15 ohms or less, and will be pleased to recommend suitable units for customers' equipment.

Kit of parts for above ... 30/-
Unit built and tested ... 40/-

From:—
RADIO COMPONENTS,
EAST STREET, DARLINGTON.

TELEPHONE SETS. Consists of two balanced armature telephones connected 25ft. P.V.C. flex, no batteries, self energised, cheapest form intercom, remote listener, etc., 9/- set. Reduction for quantity.
Many other Radio & Electrical bargains, etc.
INSTRUMENT WIRE.
Send S.A.E. for list.
L. C. Northall, 16, Holly Rd., Quinton, B'ham, 32. Retail Stores, 416, High St., Smethwick.

LYONS RADIO

Dept. M.P.,
3, Goldhawk Road,
Shepherds Bush, W.12
Telephone: SHEpherds Bush 1729

RESPONDER UNITS. 10 valve 11 metre superhet units, ideal for conversion into a Midlands or London Television receiver. Contains 6 12Mc. I.F. Transformers. 4 Mc. band width. 6 valves type VR65 (SP6), 2 VR92's (EA50), and 1 each YR136 and 137. 3 tunable slugged coils and dozens of other useful components. PRICE 22/6, carriage 4/6.

INDICATOR UNITS TYPE 6A.—As specified in several T.V. designs, these units contain C.R. tube, VCR97, 4 VR91's, 3 VR84's, etc. In brand new condition, supplied in maker's transit case. PRICE 85/-, carriage 7/6.

AERIAL RODS.—Coppered steel rods, 12in. long, can be plugged into each other to form an aerial any desired length. PRICE 3/- per dozen, post paid.

TRANSMITTERS TYPE BC778. Powered by built-in hand generator, sends automatic S.O.S. on 500 Kc., or can be manually operated. Complete with Morse Tapper, valves (1 each 12SC7 and 12A6), neon indicator lamps, aerial wire, etc. Housed in waterproof cases which are slightly dented and marked externally, but in good condition internally. PRICE 30/-, carriage 4/-.

0'300 v. A.C. VOLTMETERS.—Switch-board mounting type, first grade m. iron, scale length approx. 6in., diam. over fixing flange 8in. PRICE 35/-, post 1/6. Round, plug-in type, 2in. diam. m. iron with dropping resistance. PRICE 10/6, post paid.

INEXPENSIVE TELEVISION.—How to convert Gov. surplus equipment for T.V. reception. New enlarged edition. Price 2/8, post paid.

GLOBE KING SHORT-WAVE **REGD.**
"The World at your fingertips" ★ Real LONG DISTANCE ★
★ Best for Radio Reception ★
SEND FOR **FREE** PROBABLY THE SMALLEST ONE
WORLD WIDE RADIO VALVE SHORT-WAVE RADIO THE WORLD USING
GLOBE KING VALVES SEND FOR **FREE** 49/6d
COPY OF CATALOGUE (1d stamp postage) (1d stamp postage)
TRADE & OVERSEAS ENQUIRIES INVITED WRITE TO
JOHNSONS (Radio) MACCLESFIELD
(Specialists) CHESHIRE (ENGLAND)

ENAMELLED COPPER WIRE ON REELS

for immediate delivery, quantities in all gauges from 10—50 s.w.g., very attractively priced, well below manufacturers' prices.

Products & Commerce, Ltd.,
14, Dominion Street, London, E.C.2.
MET 9542/3 & 0530.


THE WORLD'S GREATEST BOOKSHOP

FOYLES

★ FOR BOOKS ★

New and secondhand Books on every subject. Stock of 3 million volumes.
Large dept. for Technical Books
119-125 CHARING CROSS RD.
LONDON W.C.2
GERrard 5660 (16 lines)
Open 9-6 (inc. Sat.)

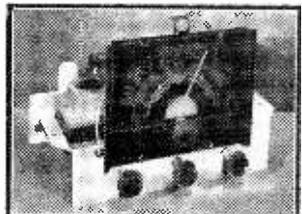YOU CAN MAKE A FINE AUTO-RODIAGRAM WITH THIS CHASSIS
1950 5 VALVE FOUR WAVEBAND A.C. SUPERHET. Product of a Leading Manufacturer.



Dimensions, 14in. x 8in. x 3in. Finished in cream cellulose. For A.C. operation only. 200-250 volts, 40-60 cycles. Consumption 60 watts.
FOUR WAVEBANDS. 12-30 m., 30-60 m., 200-550 m., 900-2,000 m. Valve combination, Mazda TH1, VP41, HLADD, FEN45, UUG. Large illuminated glass dial, size 8in. x 5in., with coloured waveband scales and station names. **IRON-CORED COILS** and I.F. Transformers.
HIGH SELECTIVITY and **SENSITIVITY.** PICK-UP Sockets fitted and switched in Wavechange assembly. Power output 4 1/2 watts. Variable tone control. Extra L.S. sockets. Price includes 8in. P.M. speaker.
A MAGNIFICENT INSTRUMENT IN EVERY RESPECT. £11-19/6 (incl. post).
MARCONI AUTOMATIC RECORD CHANGER with pick-up matching trans. £10-10/8 Carriage paid.

With these two units and a cabinet which you can make yourself you will have a fine instrument equal to any costing three times as much.
PROMPT DELIVERY PER PASSENGER TRAIN. SATISFACTION AND SAFE DELIVERY GUARANTEED.

H.P. RADIO SERVICES LTD.
515's Leading Radio Mail Order House
55 County Rd., Walton, Liverpool 4.
Tel.: Aintree 1445 Estab. 1935

"YOU CAN RELY ON US" FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

IMMEDIATE DISPATCH

- MIDGET COIL PACKS**
MW/LW, MW/SW ... 25/-
LW/MW/SW of very small dimensions 28/6
465 K/cs. ...
- COILS**
Medium wave iron-cored with reaction (small) ... 3/6
TRF MW/LW matched pair with circuit 7/8
- FORMERS**
Aladdin 4in. with cores ... each 10/4
Aladdin 4in. with cores ... each 7/4
4in. Bakelite with adjustable iron core ... each 9/4.
- FILAMENT TRANSFORMERS**
210/240 v. to 6.3 v. 1.5 a. Small, with green crackle finish ... 8/6
210/240 v. to 4 v., 3 a. ... 12/6
- SPEAKER TRANSFORMERS**
Super midget, to match 3S4, DL92, to 2-3 ohms ... each 4/8
- LOUDSPEAKERS**
2 1/2in. Cestation Midget, 25/6; 3 1/2in. 12/6; 5in. with dust cover, 9/9; 5in. Television 4 Type small magnet, 10/6; 6 1/2in. Goodmans, 12/6; 6 1/2in. Truvox with trans., 16/-; 8in. Lightweight Television type, 15/-; 8in. R. & A. with pentode trans., 19/6; 10in. Television type, 21/6; 12in. Truvox, 39/6.

Write 'Phone, or Call for CATALOGUE No. 7, 21d. Stamp.

RADIO SERVICING CO.

444, WANDSWORTH ROAD, CLAPHAM, LONDON, S.W.8

Telephone: MACaulay 4155
77, 77A Bus; 26, 28 Tram. S.R. Station, Wandsworth Road.

WE DON'T supply anything Ex-Government. All Brand New Goods — fully guaranteed —

AUTO CHANGERS IN STOCK

GARRARD RC85A A.C. D.C. MIXED RECORDS. Standard lightweight magnetic head. £20 15/-
GARRARD RC85A A.C. MIXED RECORDS. Standard lightweight head. £15 13/6.

INTERCHANGEABLE plug-in heads for the above. Lightweight, £2 6/8; High-fidelity, £3 5/-; Adaptor for RC65 and 70. 6/6.

F.M.I. MARCONI A.C. Auto-changer. NON-MIXED, Hi-Fi. head. Complete with transformer. £10 10/8.

COLLARO RC500. A.C. Auto-changer. NON MIXED. Crystal or Hi-Fi. head. £10 15/-.

CABINETS. Unpolished for all the above changers. Motor boards ready cut to fit. £3 10.
SPECIAL OFFER. Goodman speakers. 8in., P.M. 3 ohms. 17/6.

TAYLOR TEST GEAR
The entire range by this famous maker is now available on hire purchase. S.A.E. for catalogue and terms.

ALL AVO TEST GEAR NOW IN STOCK.
AVO 7. Leather cases, £22/6, post free. We are the largest actual stockists of AVO METERS in England. S.A.E. for catalogue and price list.

WE ARE NOW ACCEPTING ORDERS for 2-speed Gram. units. 33 1/3 and 78 r.p.m. for early delivery.
All items can be supplied C.O.D. up to 15lb. in weight. Otherwise cash with order, please. Special attention to overseas orders, which are free of purchase tax.

MODERN ELECTRICS, LTD.,
164, Charing Cross Road, London, W.C.2
Telephone: TEMple Bar 7587

J. E. ANNAKIN

.01, 5kv, Morse Keys, 1/6.
12.v. 1/2A Rects 1/-. Valves from 1/-.

Many other Bargains. S.A.E. LISTS. No C.O.D.

25, Ashfield Place, Otley, Yorks.

SUPACOILS OFFER

★ A complete range of High Q variable iron dust cored coils in wavelengths 10-30, 15-50, 30-75, 75-200, 190-550 and 300-2,000 metres: Aerial, H.F. or Oscillator, at the remarkable price of 3/- each.

★ I.F. TRANSFORMERS improved, iron-cored, high stability, aligned to 465 Kc/s., 13/6 pair.

★ MODEL 30 famous 3 waveband superhet Coil Packs, aligned, 29/9 each.

★ MODEL 40 Coil Packs—similar, with R.F. stage, aligned, 57/6 each.

★ 6 BAND COMMUNICATION Coil Packs—aligned especially for the "Ham" and covering 5 to 2,000 metres, decoupling resistances and condensers being built into the pack. £8.11.10.

★ TUNING UNITS and COIL GROUPS of all types in stock.

★ GRAMOPHONE MOTORS. Comprehensive stock from £5.18.2.

★ RECORD CHANGERS. Collaro £9.15.0, Plessey £16.6.9, Richard Allan (in de luxe cabinet) £27.19.0.

★ MICROGRAMS, pickups, headphones, loudspeakers, mains transformers and valves of all types available.

★ FREE. A copy of the enormously successful Home Constructor's Handbook will be forwarded FREE with orders of 20/- or more, or a copy can be obtained for 1/6 only from

SUPACOILS, MAIL ORDER OFFICE,
85, Greenway Avenue, London, E.17.

Impressions on the Wax

Review of the Latest Gramophone Records

FRANZ SCHMIDT'S opera "Notre Dame" was a big success when first performed at the Vienna Opera in 1914, and the "Czar-das" which has been recorded on *H.M.V. C3975* gives ample indication of its tuneful attraction. An Austrian born in Bratislava, Schmidt was at first a 'cellist in the orchestra of the Vienna Court Opera, before concerning himself quite extensively with composition until his death in 1939. Four symphonies of his show his qualifications to use an orchestra. Johann Strauss's "Furstin Ninette," which is on the reverse side, appeared in 1893, product of a period in which Strauss was producing operas at a rate of nearly one a year. This "Ninette Polka" is typical of his engaging style. For both dances the Vienna Philharmonic Orchestra under Karl Bohm give sparkling performances of this Austrian music.

A set of records that should appeal to most is a recording of Sibelius's "Symphony No. 6 in D Minor, Op. 104," on *H.M.V. DB6640-2*. It is played by the Royal Philharmonic Orchestra under the able baton of Sir Thomas Beecham, Bart.

Bach's "Prelude and Fugue in E Minor" for the organ, recorded by Fernando Germani, is notable for the fact that it was made in Westminster Cathedral, London. The Prelude is in four parts on two 12in. records—*H.M.V. C3984-5*.

Other orchestral recordings from which you may take your choice are "Siegfried Idyll," by Wagner, played by the Philharmonia Orchestra conducted by Paul Kletzki on *Columbia LX1296-7*. "London-derry Air" and "Handel in the Strand," played by the Philharmonia Orchestra conducted by Warwick Braithwaite on *Columbia DX1660*, and Borodin's "Overture Prince Igor" orchestrated by Glazounov and played by the Philharmonia Orchestra conducted by Issay Dobrowen on *H.M.V. C3979-80*.

Recordings from Italy

The Parlophone Company continue with their Cotra Series of recordings from Italy by Italian artists with "Don Carlos," song by Cesare Siepi, bass, accompanied by the Orchestra Sinfonica Della Radio Italiana conducted by Arturo Basile on *Parlophone R30016*. "Don Carlos," first produced in Paris during the Universal Exposition in the spring of 1867, was the last work written by Verdi before he achieved acclaim with "Aida." The libretto of "Don Carlos" was adapted from Schiller's tragedy, and although the opera has not succeeded in remaining in the regular repertoire as a complete work, there are several excerpts of wide popularity. This recitative and aria from Act 4 is one of the most famous fragments. This fine Italian bass gives full dramatic intensity to the situation. Also in this series is a recording by Gabriella Gatti, soprano, of the Mozart aria from the second act of "The Marriage of Figaro" and Act 3 of Weber's "Oberon." The number of this record is *Parlophone R30017*.

Light Music

Two very old favourites are introduced by Andre Kostelanetz for his latest recording of "St. Louis Blues" and "Stormy Weather," on *Columbia DX1662*.

"Waltz of my Heart," from Ivor Novello's "The Dancing Years," is featured by Roberto Inglez and his Orchestra on *Parlophone R3287*, coupled with "Los Celos Y El Viento" and Josef Loeke, the popular tenor, gives us that firm favourite of Milho's, "Christopher Robin is Saying His Prayers" on *Columbia DB2696*, on the reverse being "The Story of the Sparrows."

Records by two well-known choirs will be welcomed by those who like this type of singing. The Luton Girls' Choir whose records are becoming increasingly popular, have chosen "Some Day, My Heart will Awake," from Ivor Novello's "King's Rhapsody," and "Take the Sun," from the film "The Glass Mountain"—*Parlophone R3293*. The choir is conducted by Arthur E. Davies, with orchestra conducted by Philip Green.

The Kirkintilloch Junior Choir, conducted by the Rev. J. R. Macpherson, sing "Morag's Cradle Song" and "The Isle of Mull" on *Parlophone R3294*.

Debussy's "Ballade" forms a fitting subject for a pianoforte solo by Walter Gieseck on both sides of *Columbia LB97*.

Variety and Dance Music

The popular Saturday night broad casting singer, Terry, the Irish Minstrel, has recorded "Peggy O'Donovan" and "My Way" on *H.M.V. B9917* and the Tanner Sisters, with the Hedley Ward Trio, have selected the hit tune of the moment "Choo'n Gum," coupled with "A Load of Hay," on *H.M.V. B9923*.

When Donald Peers resumed broadcasting earlier this year, after a break of several months, it was suggested by some listeners that his voice had gained fresh quality. Certainly the reception he has been given since his return proves that he is indeed one of the biggest attractions in show business. His latest *H.M.V.* contributions include the British ballads, "Down in the Glen" and "When There's Love at Home" on *H.M.V. B9907*.

Ivor Morton and Dave Kaye continue their series of Tin Pan Alley Medleys with a number of popular tunes on *Parlophone P2408*; Jack Simpson and his Sextet play "I'd've Baked a Cake" and "Six Times a Week and Twice on Sunday," on *Parlophone F2411*; and finally, Joe Loss and his Orchestra play "A Media Luz" (Tango) and "Chiquita Bacaua" (Samba), on *H.M.V. DB6069*.

REFRESHER COURSE IN MATHEMATICS

8/6, by post 9/- 4th Edition By F. J. CAMM

From: GEORGE NEWNES LTD.
Tower House, Southampton Street, Strand, W.C.2

PERSONAL PORTABLES. This new book by E. N. Bradley contains full constructional details of five different circuits. Book 2/6 post free. We can supply all the necessary components from stock. **M. WATTS & CO.,** 8, Baker Street, Weybridge, Surrey.

"A PORTABLE TELEVISOR" - Bradbrooks proudly announce their second "first-ever" publication by Edwin N. Bradley. The result of months of experiment, "A Portable Televisor" gives complete information for building a 3in. or 6in. TV receiver, the 3in. prototype measuring only 15in. x 11in. x 7in., with powerpack, tube, speaker, etc., all self-contained. Not a hashed-up conversion job, but a tested new design with frame line arising and other new features. Order your copy 5/6pp. price 3/- (3d post free) from **BRADBROOKS,** Sennen, Penzance, Cornwall. Don't forget to order "Personal Portables" too, a mine of information at 2/8, post free.

EVERYTHING for Radio constructors, Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH,** 98, West End Road, Morecambe. Quick service.

25 Resistors, 2/-; 230v. Soldering Irons, 5/6; 1-Valve Units, 2/6. Midget Components. List 2d. **CARTER'S,** 67, Bell Lane, Marston Green, B'ham.

SALE, T1154 £5, R1116A £6/10/-; working order, no power packs; buyers collect, 5, Henty Walk, Dover House Road, Roehampton, S.W.15.

CONDENSERS, 2 mfd., 500v., 1/6; 4 mfd., 350v., 1/6; 001, 002, 005, 500v., lin. x lin., 7d.; 0005 midget, twin gang with trimmers, 8/6. 50pf Trimmers, 5d.; 100pf, 7d.; 8 mfd., 450v., small Conds., 2/- Speakers, Alni mag. dust covers, 10in. 2/-, 8in. 1/7, 6in. 14/6. Denco TV Coils, Sup. or TRF, from 2/- ea. **S.A.E. Enquiries to RADIO MART,** 22, Tubwell Row, Darlington.

PERSPEX, Catalin, Aluminium Sheet cut, drilled and made up to your requirements. Metal small parts made to sample or drawing. Any quantity from one upwards. Enquiries welcome. **THE H.B.H., CO.,** 21, Portland Crescent, Leeds, 1.

ELECTROLYTICS, 8 mfd. 600 Ali., 1/3; 16 mfd. 2/-; 2.4 mfd. 350 round cardboard, 4/6 doz.; 0.1 350v 150 doz.; Resistors, popular kits £4/10/-; new, 50 used, 5/6. **AUTOREX MOTORS,** New Whittington, Chesterfield.

SENSATIONAL NEW AMPLIFIER by N.R.S.: The Symphony No. 1 is the most flexible in the market to-day. Three separate channels giving entirely independent control of bass, middle and top, also scratch cut for records. Gram, and tuner inputs. 5 watts undistorted output matched to 3 or 15 ohms. Price £8/19/6. No. 1 High Fidelity Tuner, L and M wave, T.R.F., infinite impedance detector. Complete kit £4/10/-; ready built, £5/10/- No. 2 Superhet Tuner, L.M. and S. wave, special quality bandwidth, elaborate full-vision dial assembly. Kit, £7/10/-; ready built, £8/10/-, Collaro RC49 mixed 8-record Autochanger, with crystal pickup, £14/6/8. Marconi AC100 10-record Autochanger, with hi-fidelity pickup and trans, £10/10/8. Collaro AC504 Motor/Pickup/Autostop Unit, £5/3/2. Collaro list grade centre-drive Motor, with 12in. iron-magnetic turntable, var. speed, £5/18/4. Collaro standard model Microgram, 2½ watts output, centre-drive motor, special offer, £13/10/-. Portable case only, uncut motorboard, 4/6. Full bargain list 2d. Immediate delivery of all above. Terms: C.W.O. or C.O.D. N.R.S., 16, Kings College Rd., London, N.W.3. (Primrose 8314).

RATES: 3/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

NEW BOXED VALVES: ECH21, EL33, KT61, TP22, 4THA, 1622 (6L6M). 10/-; 1C5, 5V4, 7D5, TH233, 8M1, EM34, VP4, SP4, CL4, AC/VP1, 8/6; IR5, IS5, IT4, 3S4, 6B4, 6Y5, 6V6, 12Q7, 3Z4, 42, VP133, HL133DD, PEN 383, EL33, KT33C, 11D3, U18, U52, AC5/PEN/DD, 7/6; IS4, 5U4, 5Y3, 5Z4M, 6A6, 6ACTM, 6B8, 6F6, 6J7M, 6K7, 6K7GT, 6K8M, 6L7, 6Q7GT, 6S7GT, 6SL7GT, 6SN7GT, 6U7, 6V6, 6V6GT, 6X5GT, 12Z3, 80, KTW61, DL63, 5U0, MU12/14, EF39, EBC33, 15D2, S130, 6/6; 6J5GT, 6SG7M, 5/-, Valves unboxed, but guaranteed, EF36, EL32, TT11, ML6, 8D2, VP23, KTZ63, 6ACTM, 6C5, 6J5, 6SH7M, 12A6M, 12SC7M, 4/-; ECH35, L63, HL23DD, 5R4G7, 5U4, 9003, 5/-; Electron Multiplier Photo Cell Tubes, type 931A, 27/6; Electrolytic Condensers, 8-8 MFD, 450V.W., 2/9; 32MFD, 350V.W., 2/9; 50MFD, 50V.W., 1/6; Volume Controls, less switch, lin. diam., 50k, 100k, 200k, 250k, only 1/6 each; Meg., 2/-; Colvern Wirewound 25k and 30k, 2/6; Mains Droppers 2 amp, 750 ohms, 6 fixed tapings and 1 adjustable slider, 3/-; "Test Gear," 3 amp, 750 ohms, with 2 sliders, 4/-; Condenser Clips, assorted, 2/6 doz.; Paxolin Valve Holders, most types, including UX4, 5 and 6 Pin 4D; personal Portable Cases; Hermes "tourist" complete with back, chassis, oscillator coil, battery support and frame aerial former, 10/-, All goods post free. Send for free lists of other bargains. S.A.E. with inquiries, please. **ELECTRAD RADIO,** 64, Gt. Victoria St., Belfast.

NEW VALVE BARGAINS! IS4's 3 for 15/6; 6J5M's 3 for 13/-; AC6Pen, 6N7GT, 6J5M, 6/-; IT4, IR5, IS4, 5Z4M, 5Y3G, 6/6; 6V6M, 6J7M, 6N7M, 6P6G, 6SG7M, 5U4G, 7/-; 10K, 10W, W/W Pots, 3/-; 100 ass. waxed Tub. Conds., 9/6 100 ass. Resistors, 9/6. All C.P. S.A.E. list. **J. T. ANGLIN,** 106, Cleithorpe Rd., Grimsby.

VALVES, 6S7GT 4/6, CV72 and 73 4/-, VU12 5/-, VU133 3/-, CV63 2/-, Condensers, 1 at 350v. 100 for 10/-, 1 at 500v. 100 for £1. Trade supplied. BARDWELL & CO., 473, Abbeydale Road, Sheffield, 7.

VALVES, EX. GOVT. - EF50 4/9, 807 5/-, 8D2 4/-, EF55 7/6; IFT's 465, 6/- PR; 3 WB Midget iron-cored Coil Pack Kit, L.M.S., 9/6; 8mfd 450v., 2/-; 16-16mfd 350 v., 2/6; .01 450v., 2/9 doz.; .1 350v., 2/9 doz.; .1 500v., 3/3 doz.; .1+1+1, 1/6 doz.; 100 assrt. Mica, 10/-; 50 assrt. Res., 4/6; Trans., 4/-; Slugs, 6d. doz. yds.; Console TV Cabinets, really super job, £10. Many more bargains. Send for latest "cheapest list in England." **SUSSEX ELECTRONICS, LTD. (P.),** Riley Rd., Brighton, 7.

POTS, 2K, 5K, 30K, W.W., 12/- doz., 100K, 1M, 2M, 10/- doz., no presets; 100K c/s. Xtals. 20/-; Xtal diodes, 2/9; Valves, EF50, 6G6G, EL50, 5U4G, 5Z4, 6K7G, U10, 6SN7, 6SL7, 6SA7, IT4, IS5, 9003, 6P6G, 6SGT, 6J5GT, 6N7GT, 7V7, 7Q7, 2X2, VR105, VR150, EAC91, 6AG7, 6AC7, ML4, all at 5/6 each. Post 6d. under 20/-. Stamp for list. R. T. & I. SERVICE, 254, Grove Green Rd., London, E.11.

PHOTO-ELECTRIC Meter Components. - Selenium Light Cell, 6/8; Micro-amp. Meter Movement, 10/6; Perspex Instrument Case, 9/-; Assembly Instructions, 2/6. S.A.E. full details. **G.R. PRODUCTS,** 22, Runnymede Avenue, Bristol, 4.

QUARANTEED ELECTROLYTICS by manufacturers of repute, metal cans. 8-mfd. 450v. or 16-16mfd. 350v., 2/6; 8-mfd. 450v. or 16mfd. 350v., 2/3. Also 2pf., 5pf., 20pf., .0001, .001, 2/6 doz.; .005, .01, 1, 3/- doz.; .25 or .5mfd., 5/6 doz. B.V.A. Valves, ex-stock. Over 10/- post free. **ELECTRONIX,** 220B, Canterbury Street, Gillingham, Kent.

SERVICE SHEETS wanted, any quantity, high prices paid immediately. **J. BULL,** 246, High St., Harlesden, N.W.10.

VALVES, IS5, IR5, IT4, at 7/6 ea.; 6J5, 9D2, VU11, 5/- ea.; 6K8, 6K7, 6Q7, 6V6, 6F6, 5Z4, 5U4, 6J7, 6AC7, KTW61, EK32, 807, AC/XL 1½, IS4, bnd. new, bxd., 6/3 each, post paid; 25Z6, 5Y3, 80, 7/6 ea.; 3R, APV4, 6L6M 9/- ea. Speakers, 3in. 11/6, 3½in. 14/6, 5in. 10/6, 6½in. 11/6, 8in. 13/6, 10in. 16/6, 12in. 35/-, Vol. Contrls., 2½in. spindle, 10K to 2M, less sw., 2/6 ea.; ditto, with sw. 3/9 ea. Condensers, 1, 350v., 6/- doz.; 80, 450v., 2/6; 8, 500v., 2/9; 16, 500v., 3/6; 16/16, 450v., 4/3. Mains Trans., 270/270, 6, 5, 4v., 80ma, 15/6; ditto, 350/350, 16/6 each. Special offer, 4v., 350/350, 80ma, M/Ts, by Bryce, Porthminster, etc., at half list price. BA5 Hphones with throat m.c., 4/-; twin meter Test Panel with 0/5ma, 0/40v., pots, switches, shunts, etc., 12/6, post free. Id. stamp list to: **LORNE RADIO SUPPLIES, 7, Lorne Rd., Walthamstow, E.17.**

R.F. UNITS type 24, mod. 27, 12/6 ea.; 60-80mc approx by 5 pos. switch, ideal for Midland T.V., type 25 for A.P., 12/6; T.V. Pre-Amps., adaptable for either station, uses two EF50's, less valves 9/6 ea.; Indicator units, type L, similar to 6a, new and boxed £4/5/- ea., others from 50/-; Valves, new, 6AK5 8/6, 9001 5/-, 6AC7 7/6, EA50 2/6, soiled VR65s at 18/- doz.; Sprague Id. stamp 0.1 350v. 4/- doz., 36/- gross. We have hundreds of bargains in ex-Gov. Radio and Elec. items; also a wide range of Optical Gear. Booklet on ex-Gov. Lenses, etc., 2/6 ea. New 16-page lists free on receipt of your stamped and addressed envelope. **H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.**

VALVES, guar., boxed: EF50, EF54, EF85, 5Z4, 5U4, ECH35, 6K8, 6Q7, M/12/14, 5/6, 4 for £1; EBC33, 6V6, 6K7, 5/-; EF40, 500v., 8/6, 6 for £1; SP61, SP41, 3/-; EA50, 1M, 11/9; 10/-; 807, 6/-; IR5, IS5, IT4, 3S4, HVR2A, 7/6. Spkrs., 8in. P.M., 11/9; 10in. ELIP M/E 720 ohms, 14/9. H.R. Phones, 6/-; Browns, 8/6, 0-500 Microamp Meters, 5/6. New Mine Detectors, with valves, less probes and phones, 12/6. £1 orders post free. **T.R.S.,** 71, Meadvale Rd., E. Croydon.

SOUTHERN RADIO SUPPLY LTD., late 46, Lisle Street, W.C., have now removed to new premises at 11, Little Newport Street, London, W.C.2. Five doors from Charing Cross Road and Leicester Square Tube Station; Telephone Number Unchanged. Gerrard 6653. All goods previously advertised still available. Please note new address. **SOUTHERN RADIO SUPPLY LTD.,** 11, Little Newport Street, off Charing Cross Road, London, W.C.2. (Gerrard 6653).

ALL WAVE Crystal Diode Kits, 17/6; Crystal Set Kits (M.W.), 3/3 and 3/9; each with instructions. List id. **ALEXSTONE,** Hillworth, Longdon, Glos.

VACUUM CLEANERS and Gram. Motors, repairs our speciality. Armature rewinds, new bearings and commutators fitted, also transformers rewound, speakers repaired. Competitive prices. Trade enquiries invited, 2 to 5 days c.o.d. service. Send s.a.c. for price lists to: **A.D.S.,** Dept. 1, 261-3, Lichfield Road, Aston, Birmingham, 6, Est. 1935.

BRAND NEW Guaranteed Goods.—
Electrolytics, tubular, 8mfid 450v.
1/11, Can 8-mfid 450v. 2/9, 8-16mfid
450v 3/3, 16-16mfid 450v. 3/11, 32-16-
mfid 450v. 4/9; Vol. Controls, Erie,
Morganite and Centralab, long
spindles, less switch, 5meg. 1meg.
1/11; with switch 10K, 25K, 2/9;
50K, 100K, 250 K, 5meg. 1meg. 2meg.
3/11; ex-Gov. Valves, DL, EB34, 114,
954, SP41, VU133, 2/11; 6J5GT, 9003,
VU11, VU133, 3/11; 6C5GT, 9003,
4/11; 6K7G, 5ZMet, EB33, 5U4G,
5/9; 6J7 Met, 6V6G, 6P6G, 5/11;
6L6Met, 7/9; Mains Energised
Speakers, 8in. Ultra with 5,000 ohm,
trans. (Field 1,000 ohms), 18/9;
Mains Transformers, drop-through
types with top shroud, primaries
standard, 200-250v. 50 c/s., 260-0-
260v. 70ma. 6.3v. 3a. 5v. 2a. 12/11;
Midget 21-3-21jms., 20-0-250v. 60ma.
6.3v. 2a. 5v. 2a. 15/6; 350-0-350v.
60ma. 6.3v. 3a. 5v. 2a. 17/9; 250-0-
250v. 100ma. 6.3v. 6a. 5v. 3a for 1355
Conversion, 22/9; 350-0-350v. 150ma.
6.3v. 4a. 5v. 3a. 25/9. Full range of
Mains Trans. in stock, Midget
fully shrouded, 250-0-250v. 60ma. 6.3v.
2a. 5v. 2a. size 21-3in., 15/6. A dis-
count of 20% may be deducted from
orders of 1 doz. of any preceding
items. T.V. Focus Coils, 9/6; T.V. 6in.
and 9in. Cream Masks, 7/6 Magnify-
ing Lenses, 6in. for CR97, 25; P.M.
Speakers, Truxov, 23 ohms, 10in.,
15/9, 8in., 12/11, 5in. 9/11; Plessey 5in.
with trans., 12/6. Full list of bar-
gains 3d. Special list for trade,
C.W.O. or C.O.D. over £1. Over £2
post free. **RADIO SUPPLY CO.**, 15,
Queen Square, Leeds, 2.

MAGNETIC RECORDING, stainless
steel wire, .0036in. dia; special offer,
8oz., spools 15/-, 12oz., spools 20/-,
Experimental data and sample of
wire, 2/6. H. WILSON, 17, Berwood
Farm Rd., Sutton Coldfield.

MAGNETIC SOUND Recording Wire,
stainless steel, temporary wooden
spools, approx. 1 1/2 hours running
time at 2ft. per sec.; 14/- per spool.
A. SMART, 40, Grange Rd., Hales-
owen, Worcs.

BARGAINS.—Hand Generators, out-
put 300v./28v., 6/6; Blower Motors,
small, 6/-; Dynamotors, small, 6v.
to 250v., 65ma., 10/-; Microswitches,
OC/CC, 2/6; No. 18 set 4v. Bat.
Shet., 6.9 mcs. 465kcs. IFTs. with
circ. and mod. instructions for other
w/bands, 17/6; Xcals, 455kcs, 10/-;
other Ircqs. 1/6; (no Hambands), 100
kcs. 3-pin 15/-; Diodes IN22, 3/-;
Tuneons 1/6; Condensers, block
8kv. 25 or 5mfid. 4/-; Potenti-
meters, new, asstd., 7/6 doz.; Con-
densers, bathub, new, asstd., 6/-
doz.; Yaxleys, new, asstd., 7/6 doz.;
Coils, IFTs, etc., U.S.9., 6/- doz.; Pvc
Plugs/Skts, 6d., double-ended, Skts,
1/-, "T" Skts, 1/3, "T" Skts, Plugs
1/3, Plugs 2in. in lyd co-ax, 1/6, Plugs
(2) on 20ft. 4in. co-ax, 1800), 3/6;
Cone ceramic Standoffs, ribbed 3in.,
1/-; Min. var. Conds.: ceramic 7in.
75pf, 2/6; D.E. 75pf 1/6, preset 30pf
1/-, 3-gang 25pf 4/6, 50pf d/space
with SM drive, 3/6; Epicylic SM
drives, 1/3; Resistors, new, 50 asstd.,
5/6; Ins. knobs, new, 5/6 doz.; metal
Recs., HW, 240v. 80ma, 5/-, 120v.
30ma, FW, 3/6, 15v., 6a, FW 22/6,
40ma, 3a 15/-; Togglees SP 1/1-
DP 1/-, DPDT 2/-; Transformers,
std. inputs, 50c-13v. CT 2a. 8/-, 300-0-
300v. 200ma. 6v./5a. 5v./3a. 70v./1a.
20v./75a. 30/-; Parmeko. 620-0-620
tapped, 550, 375v. 250ma. 2x5v./3a.
42/-; RCA shrouded, 190/250v. input,
400-0-400v. tapped 350v. 200 ma. 6v./
6a. 5v./3a. 37/6. Valves, as June
adv't. Hundreds available (surplus).
Immediate quotations on request.
Specials: New PT15 8/6, VR21, EA50
2/6, ML6, 6AC7, 6C4, 6SN7, 5/-,
VS110a, QP21, 6V6GT 6/-. C.W.O.
S.A.E. enquiries please. W. A.
BENSON, 308, Rathbone Qd., Liver-
pool, 13.

SURPLUS UNUSED: 1 350v. 2/6
doz., .01 100Gv. 3/- doz., .05 500v.
3/- doz.; 1 300v 6/- doz.; .01 Mica
3/- doz.; 4pf, 20pf, 2/- doz.; 2 mfd
500v. 9/6, each; TRF Coils, 4/9 pair,
etc. Bargain list from T. G. HOWELL
& CO., 29, McWilliam Rd., Bright-
on, 7.

FRITH RADIOCRAFT, LTD., Leices-
ter, offer:—A.C. Generators, output
230v. 100w 54c/s. input 24v DC, ideal
for mobile PA, etc., £3/15/-, carr. pd.
Unused R.A.F. surplus, tested and
guaranteed perfect; in stout case, 15
x 10 x 8in., weight 40lbs. Telephone
Handsets, carbon mike, with 4-way
lead and plug, latest streamline type,
10/6 + 9d. post. or two for £1, post
free; brand new and fully guaran-
teed. Sleeving 1.5mm black Peri-
braided, reels of 1 gross yds. 7/6, 2
gross 12/6, 3 gross 12/6, post 6d. per
gross, extra discount quantities.
Single PVC Hook-up Wire, 72 yds. for
5/- + 6d. post. Seven lb. Parcels
of 40 to 50 assorted New Components,
Resistors, Condensers, Switches, etc.;
every parcel different; 5/- + 9d. post.
Workshop Parcel of Wire, sleeving,
Grommets, Screwed Rod, Nuts and
Bolts, bumper size, 10/- + 9d. post.
Tallon packed-flat TV Cabinets, 9in.
table Viewmaster, £5/45/-, 19in. Con-
sole Viewmaster, £12/10/-, 13in. Con-
sole Elect. Eng., £13/10/-. Full range
of TCC Condensers, Morganite Resis-
tors, Egen & Reliance Pots, Woden
Transformers and Chokes, and all
TV parts from stock. Descriptive
lists free on request. **FRITH RADIO-
CRAFT, LTD.**, 69-71, Churchgate,
Leicester.

MINISTRY OF CIVIL AVIATION.—
Vacancies for Radio Mechanics. Men
between ages of 21 and 40 are in-
vited to apply for appointment as
Radio Mechanics in the Ministry of
Civil Aviation for service at civil
aviation radio stations. Candidates
should possess knowledge of the
fundamental principles of electricity
and radio and have had practical
experience in the maintenance of
radio or radar equipment. Full par-
ticulars and application forms can be
obtained from the **MINISTRY OF
CIVIL AVIATION**, Estla/E5/24.1.1,
19/29, Woburn Place, London, W.C.1.

SUPREME RADIO, 746s, Romford
Road, Manor Park, London, E.12.
(Tel.: ILF. 1260). Midget Valves:
1T4, 1S5, 1R5, 1S4, 7/- ea., boxed,
0.0005 mfd. Mica Dielectric Variable
Condensers, 2/9 ea. 2 1/2in. and 3in.
Moving Coil Speakers, 2-3 ohm, voice
coil, 14/11 ea. Midget Personal Out-
put Trans for DL82, valves, etc.:
Really tiny, 4/- ea. B.7G Amphinol
type Valve Holders, 9d. ea. 1 watt
Resistances; 10 ohm, 22, 47, 27, 82,
120, 180, 250, 330, 390, 820 ohms.
IK, 3.9K, 11K, 470K and 10 megohm,
1/9 doz. or assorted doz., 18/6 gross
only. 1 watt Resistances, 2.2K ohm,
6.8K, 16K, 18K, 33K, 100K, 150K,
250K ohms, 2/- doz. or assorted doz.
21 gross only. 130 ohms 0.2 amp
Flat Type Mains Dropper, tapped for
200-250v., 1/6 each. Mica Cond.:
40PF, 50PF, 60PF, 65PF, 70PF,
305PF, 307, 500, 530, 570, 1.800
and 4.550PF, all at 2/6 doz. or
assorted doz. only. Balanced arma-
ture type Headphones with headband
and lead, 2/6 per pair, CV192 Crystal
Diodes, 2/6 ea. 3in. bore brass
bushed brown Knobs, 2/- doz. 200v.
120 M/A Selenium Metal Rectifiers
or 250v 75 Ma. 4/- ea. 1 meg. Carbon
Vol. Controls, 1/- ea. 5 k-ohms Vol.
Controls, 6d. 3 meg. Var. Carbon
Controls, 7d. ea. Noise Suppressor
Units, consisting of 2, 0.1 mfd Cond.
and Iron-Covered Choke, 6d. ea., 5/-
each, 100 k-ohm Long Spindle Vol.
Controls with S/P switch, 2/6 ea.
0.25 meg. Vol. Cont., less switch long
spindle, 2/- ea. Terms C.W.O. No
C.O.D. Send 6d. extra for postage
orders under £5. 21d. S.A.E. all
enquiries and lists.

97/6 CHARGING SWITCHBOARDS.
12/32v., 500 and 1,260 volts, amps.
cut-outs, fuses, resistances, etc., 4
take-off super unit, in case, 75/-;
Dynamos, 24v., 1,000 w., 9in. x 7in.;
3in. spindle, 75/-; Motor Alternators;
from 1-12 kw. 110 and 220v. D.C. to
230v./150 A.C. from £15. Motor
generators 1-6 kw., 110 and 220v.;
D.C. to 24/35v. D.C. £5-£59; Mains
Transformers, 1-200 kva., all types.
POWERCO. Wandsworth Town Stn.,
York Rd., London, S.W.18. BAT
5234. (10 mins. Waterloo).

ENGRAVING.—Amateurs and trade
requirements, panels, plates, metal
and plastic. Attention to urgent
deliveries. One knob or repetition
equally entertained. Call or write
A.G. ENGRAVING, 19a, Windmill
Road, Wandsworth, London, S.W.18.

DUKE & CO. Extracts from Sum-
mer price lists: New resistors,
assorted, 2/- watt to 1 watt, 10/-, 100-
5/6 50, 3/-, 25 Philco Table Cabinets,
new, in brown bakelite, a few left
only, 15/-, post and packing 2/6
extra. Ex-speaker Cabinet, walnut,
metal grid, position for v/control,
with baffle for 10in. speaker, our
price 25/-; original price 5 gns. H.T.
Batteries, 180v. tapped 90v. 21v bias,
11 L.T.; all those tested so far are
fault free; they are despatched in
sealed case but are not guaranteed;
5/6 plus 1/- post. Speaker, in ex-
tension cabinet, 14/6. Walky Talky's
No. 38, all new valves, in first-class
condition, one valve (ATP4) and
switch (send-recv) only removed,
17/6, bargain; 500 only available.
Circuit and switch connections sup-
plied. Short Wave Superhet Receiver,
complete and tested, New pair of
headphones included for 17/6. Note,
set with little alteration makes first-
class portable or car radio. I.F.s 465
ex. to P. coils for medium wave.
Dunlopillo, 34 x 18 x 2ins., 8/6 plus
1/6 post. Dunlopillo Seats, plywood
backed moquette covered, 12/6 plus
2/-, Plywood, 2ft. x 3ft. 3/-, 2ft. x
17in. 2/-. Cash with order, please,
and allow sufficient for post. Stamps
only for lists. 219, Ilford Lane,
Ilford, Essex. Valve price reduc-
tions: 6V6, 6P6, 6K8, 6K7, 6Q7,
KT33C, etc., 5/9 each; other types
from 2/6 each.

EDUCATIONAL

NO B.N.R.S. Student has ever failed
to pass his examinations after com-
pleting our appropriate study course.
Now in our eleventh year and this
claim is still true. All our courses
are conducted by correspondence and
our syllabus includes Brit.I.R.E., City
and Guilds exams. Also maths,
physics and radar. Nothing succeeds
like success and what we have done
a thousand times already for your
colleagues, we can do again, for you
and all for £14/1/- per month.
Free booklet from **BRITISH
NATIONAL RADIO SCHOOL**, 66,
Addiscombe Road, Croydon, Surrey.
(Telephone: ADDiscombe 3341.)

WIRELESS. Postal Course of In-
struction for Amateur Radio Trans-
mitting Licence complete with text
book at a moderate fee. Apply
**BRITISH SCHOOL OF TELEGRAPHY,
LTD**, 179, Clapham Road, London,
S.W.9. (Estd. 1906.)

THE INSTITUTE of Practical Radio
Engineers have available Home Study
Courses covering elementary, theo-
retical, mathematical, practical and
laboratory tuition in radio and tele-
vision engineering; the text is suit-
able coaching matter for I.P.R.E. Service,
entry and progressive exams. Tuition
fees at pre-war rates are moderate.
The Syllabus of Instructional
Text may be obtained, post free,
from the **SECRETARY**, Fairfield
Road, Crouch End, N.8.

INSTRUMENT CO. offers . . .

COIL PACKS

Osmor Q Coil Pack, type H.O. Long-, medium-, short-waves (short-wave band 15.5 metres to 52 metres). Small, compact and remarkably efficient. Size 3 1/2" x 2". Coils wound on low-loss formers, price 33/-. As above, with H.F. stage, price 48/-. Battery Model (long-, medium- and short-waves), price 37/6.

All the above coil packs are designed for 465 kc/s I.F.

TUNING CONDENSERS

Two-gang, .0005 mfd., 4/6
Four-gang, .0005 mfd., 3/9

I.F. TRANSFORMERS, STANDARD SIZE

465 kc/s ... 6/9 per pair

MIDGET SIZE

465 kc/s ... 12/6 per pair

VALVES

Owing to limited space only a very few can be listed.

IS4	...	7/6	6K8	...	7/6
IS5	...	7/6	6L6	...	10/6
IT4	...	7/6	6Q7	...	6/6
IR5	...	7/6	6V6	...	7/6
5U4	...	7/6	41	...	7/6
5Z4	...	7/6	42	...	10/6
6I5	...	6/6	78/6D6	...	7/6
6I6	...	15/-	80	...	11/-
6I7	...	7/6	807	...	7/6
6K7	...	7/6	866A	...	12/6

Large numbers of other types in stock.

ELECTROLYTIC CONDENSERS

8 mfd., 450 volt	...	11/1	8-16 mfd., 450 volt	...	3/6
8 mfd., 350 volt	...	1/6	16+16 mfd., 450 volt	...	3/9
8-8, 450 volt	...	3/6	25 mfd., 25 volt	...	1/-
16 mfd., 500 volt	...	3/6			

Mail Order only

INSTRUMENT COMPANY,
11, GUNNERSBURY LANE, ACTON, W.3.

RECEIVER TYPE 18. A four valve superhet, covering 6-9 mcls., and with a first class performance. Complete with circuit, connecting data and batteries, 27/6.

BALANCED ARMATURE PHONES matched for the above set, complete with jack-plug, 2/9.

STATIC INTERFERENCE LIMITERS, just plug these into the output circuit (low impedance), 3/6.

FIELD TELEPHONES of American manufacture, with hand ringing generator, bell and standard type handset; in webbing cases, 37/6 or in solid leather cases, 45/-.

VALVES ARPI2 (VP23), 2/6. AR8 (HL23DD), 2/11. ATP7 (V226 output pentode), 2/6.

METERS. 0-1 mA. (new and boxed), 7/6. 0-3A thermocouple, 3/6. 0-2.5 A. thermocouple, 3/6. 0-8 A. thermocouple, 3/6.

RECEIVER TYPE 21 with 9 battery operated valves, BFO, precision dial, crash limiter, etc. and covering 4.2-7.5 and 18-31 mcls.; this is supplied with circuit, connecting data and a super capacity all-dry battery, 42/6.

BRAND NEW 1355's. Specified for "inexpensive television" and complete with 11 valves; in original maker's cases, but with slight metal discoloration due to long storage. ONLY 55/-, plus 7/6 carr.

MIDGET MOTORS. 1 1/2 in. dia. x 2 1/2 in. long, fitted with removable fan and housing; input is 27 v. A.C. or D.C. (a lamp is a suitable dropper), price 9/6.

TYPE 21 VIBRATOR PACKS. With electrolytics, condensers, resistors, five chokes, transformer, metal rectifiers, etc., these store soiled units are a "snip." ONLY 7/6.

BRAND NEW CONDENSERS. Assorted packets at 2/6 doz.

MERCURY BATTERIES 24v HT, and 1.3v LT. ONLY 5/6.

RADIO EXCHANGE

9, Cauldwell Street, BEDFORD.

Phone 5568

D. COHEN, Radio and Television Components

67, Raleigh Avenue, Hayes, Middx.
POST ORDERS ONLY
6-STATION SWITCHED SUPERHET COIL UNIT, by famous manufacturer, ideal for car radio or radio set. Range coverage Pos. 1, 200-300 m.; 2, 250-360 m.; 3, 250-360 m.; 4, 320-460 m.; 5, 400-550 m.; 6, 1,100-1,850 m.; no oscillator required for lining up, complete with Circuit. 15/6, post and packing 1/-.
Pre-aligned fitted 465 IFS, Q.120, p. & p. 6d., 8/6 per pair. Chassis to fit Coil Unit and IFS, 1 1/2" x 5 1/2" x 1 1/2", 2 6 each.

Mains Transformer, to fit above chassis, Pri. 200-250, sec. 250-0-250 60 mA, 6 v. 4 amp., p. & p. 1/-, 13/6.

Mains Transformer (I) 350-0-350 120 mA., 6 v. 4 amp., 5 v. 2 amp. Pri. 200/250, p. & p. 1/-, 18/6. (II) 350-0-350 250 mA., 6 v. 4 amp., 4 v. 3 amp., 1 in. gap between laminations and bobbin. Extra heaters could be easily wound.

Pri. 110/250, p. & p. 2/-, 29/6. (III) 350-0-350 70 mA., 6 v. 2.5 amp., 5 v. 2 amp. Pri. 200 250, p. & p. 1/-, 13/6.

Heater Transformer.—(I) Pri. 230 250, 6 v. 1 1/2 amps., p. & p. 9d., 6/-.

(II) 2, 4 or 6 v. 2 amp., p. & p. 9d., 7/6.

Mains Droppers.—(I) 2 amp., 1,000 ohms tapped 90c, 1/9.

(II) 2 amp., 717 ohms tapped 100, 1/6. (III) 3 amp., 520 ohms tapped, 2/6. (IV) 3 amp., 460 ohms tapped, 1/9.

p. & p. on each of above, 3d.

Wave Change Switches, 6 pole 3-way, 3 pole 2-way, 6 pole 2-way, 5 pole 3-way, 1 2 each, post 3d. each. 12-way single pole, 2/6; 12-way double post, 3/6; p. & p. 3d. each extra.

Standard 465 Kc. IFS air cored, Q. 110, per pair, 6/-.

Standard 465 Kc. IFS, iron cored, Q. 120, per pair, 7/-.

Miniature 465 Kc. IFS. Wearite type, M.400B, per pair, 12/6, plus 6d. post and packing.

Similar to above, slightly larger. By good Manufacturer. 10/6 per pair.

Ceramic Pfs., 3 each of the following:—330, 220, 180, 82, 2/6.

50 or 100 pf. Postage Stamp Trimmers, 4d. each.

Set of 6 iron-cored coils. L., M. & S. on moulded formers with 4-pole 4-way switch and circuit. 7/6 per set.

Line Cord 3 way .3 amp; 60 ohms per foot. 10d. per yard.

Volume Controls with switch by famous manufacturer, long spindle, 4, 1/2, 1 and 2 meg., 3/3 each. p. & p., 3d. each.

Stamp for list.

FREE TO AMBITIOUS ENGINEERS!

This 176-page Book

Have you sent for your copy?



'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £10 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.
Electrical Eng.
Civil Engineering
Radio Engineering
Automobile Eng.
Aeronautical Eng.
Production Eng.
Building, Plastics,
Draughtsmanship
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!
A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
CITY & GUILDS
MATRICULATION, etc.

*** FREE COUPON ***
Please send me your FREE 176-page "ENGINEERING OPPORTUNITIES"
NAME
ADDRESS
Subject or Exam.
that interests me
British Institute of Engineering Technology,
409B, Shakespeare House,
17/19, Stratford Place, London, W.1

BIET

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

- Blueprints, 1s. each.**
 1937 Crystal Receiver ... PW71*
 The "Junior" Crystal
 Set ... PW94*

STRAIGHT SETS

Battery Operated

- One-Valve : Blueprints, 2s. each.**
 The "Pyramid" One-
 valver (HF Pen) ... PW93*
Two-valve : Blueprints, 2s.
 The Signet Two (D &
 L F) ... PW76*
Three-valve : Blueprints, 2s. each.
 Summit Three (HF Pen,
 D; Pen) ... PW37*
 The "Rapide" Straight
 3 (D, 2 LF (RC &
 Trans)) ... PW82*
 F. J. Camm's "Sprite"
 Three (HF, Pen, D,
 Tet) ... PW87*
Four-valve : Blueprints, 2s. each.
 Fury Four Super (SG,
 SG, D, Pen) ... PW34C*

Mains Operated

- Two-valve : Blueprints, 2s. each.**
 Selectone A.C. Radio-
 gram Two (D, Pow) PW19*
Three-valve : Blueprints, 2s. each.
 Double - Diode - Triode
 Three (HF Pen, DDT,
 Pen) ... PW23*
Four-valve : Blueprints, 2s. each.
 A.C. Fury Four (SG, SG,
 D, Pen) ... PW20*
 A.C. Hall-Mark (HF
 Pen, D, Push-Pull) ... PW45*

SUPERHETS

- Battery Sets : Blueprints, 2s. each.**
 F. J. Camm's 2-valve
 Superhet ... PW52*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprint, 2s.**
 Simple S.W. One-valver ... PW88*
Two-valve : Blueprints, 2s. each.
 Midget Short-wave Two
 (D. Pen) ... PW38A*
Three-valve : Blueprints, 2s. each.
 Experimenter's Short-
 wave Three (SG, D,
 Pow) ... PW30A*
 The Prefect 3 (D, 2 LF
 (RC and Trans)) ... PW63*
 The Band-spread S.W.
 Three (HF Pen, D
 (Pen), Pen) ... PW68*

PORTABLES

- Four-valve : Blueprint, 2s.**
 "Imp" Portable 4 (D,
 LF, LF, Pen) ... PW86*

MISCELLANEOUS

- Blueprint, 2s.**
 S.W. Converter-Adapter
 (1 valve) ... PW48A*

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

- One-valve : Blueprint, 2s.**
 B.B.C. Special One-
 valver ... AW387*
Two-valve : Blueprints, 2s. each.
 A modern Two-valver ... WM409*

Mains Operated

- Two-valve : Blueprints, 2s. each.**
 Consoelectric Two (D,
 Pen). A.C. ... AW403

SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.
 The index letters which precede the Blueprint Number indicate the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.
 Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprints, 2s. each.**
 S.W. One-valver for
 America ... AW429*
Two-valve : Blueprints, 2s. each.
 Ultra-short Battery Two
 (SG. det Pen) ... WM402*

- Four-valve : Blueprints, 3s. each.**
 A.W. Short-Wave World-
 beater (HF Pen, D, RC,
 Trans) ... AW436*
 Standard Four-valver
 Short-waver (SG, D,
 I.F. P) ... WM383*

Mains Operated

- Four-valve : Blueprints, 3s.**
 Standard Four-valve A.C.
 Short-waver (SG, D,
 RC. Trans) ... WM391*

MISCELLANEOUS

- Enthusiast's Power Am-
 plifier (10 Watts) (3/-) WM387*
 Listener's 5-watt A.C.
 Amplifier (3/-) WM392*
 Harris Electrogram
 battery amplifier (2/-) WM399*
 De Luxe Concert A.C.
 Electrogram (2/-) WM403*

HINTS COUPON

This coupon is available until August 7th, 1950, and must accompany all Practical Hints.
 PRACTICAL WIRELESS, AUG. 1950.

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEAIGHT & SONS, LTD., Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (Asia), LTD., South Africa: CENTRAL NEWS AGENCY, LTD. Subscription rate including postage, for one year: Inland and Abroad 10s. 6d. (Canada 10s.). Registered at the General Post Office for the Canadian Magazine Post. CONDITIONS OF SALE AND SUPPLY: This periodical is sold subject to the following conditions, namely, that it shall not, without the written consent of the publishers first given, be lent, re-sold, hired out or otherwise disposed of by way of Trade except at the full retail price of 9d.; and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade; or affixed to or as part of any publication or advertising, literary or pictorial matter, whatsoever.

M-O-S INTRODUCTION A NEW FULL VISION DRIVE ASSEMBLY


Vertical dial with new station markings on short, medium and long wavebands (3 colours). Size of dial approx. 5ins. x 7ins., made from unbreakable Perspex with back illumination plate. Drive mechanism absolutely positive and non-slip, with nylon cord.

Complete with assembly instructions. ONLY 17/6 post free.

Illustration shows Drive, mounted on a 5-valve heavily cadmium plated chassis (size 13in. x 5in. x 2in.), fitted with international octal valve holders and terminal strips, together with cabinet fixing feet. A Plessey two-gang .0085 mfd. tuning condenser, with ball race bearing and rotor brushes giving noiseless tuning on short wavebands, is also fitted.

We can supply chassis assembly less condenser for 11/- or with tuning condenser 16/- (postage 1/-)

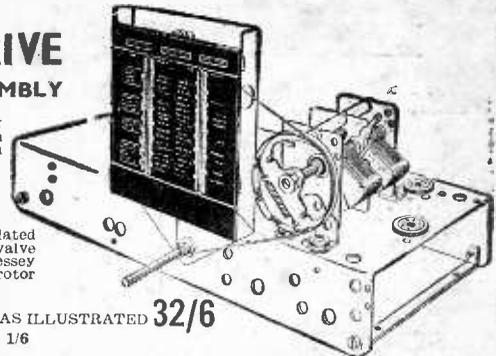COMPLETE ASSEMBLY AS ILLUSTRATED 32/6 Postage 1/6



PARMEKO DUAL SPEAKERS

Type G. A very high grade twin speaker with matching transformer. The frame of speakers is of a handsome black moulded plastic. Weight 18 lbs. Speaker grilles, 8in. diameter. Mounted back to back with baseplate for fixing. Ideal for out of door van, P.A., etc. Admiralty type W6882. 10 watts.

ONLY 50/- carriage paid.

CV226 CRYSTAL DIODES

A very efficient permanent crystal detector sealed in lead case. 3/6 each, postage 3d.

REMOTE CONTROL GROUND STATION

A device for remote control with sensitive relay incorporated. Includes fine precision heavy duty totally enclosed morse key. All components housed in solid wooden case.

ONLY 5/- carr., pku. 1/6.

HEADSET ADAPTORS

For matching low resistance 'phones to high resistance output. With jack plug and socket. 2/- each, postage 6d.

UNIVERSAL MAINS TRANSFORMER

A mains transformer for use with either 4v. or 6v. valves. Secondary 350-0-350 at 80 mA. Fully interleaved and guaranteed.

BRAND NEW. 21/- postage 1/6

SPEAKERS

A high-class 8-in. mains energized speaker, complete with matching transformer. New and boxed, 18/- each, postage 1/6.

SOLE STOCKISTS of the famous BURGEOYNE "INSTANT HEAT" SOLDER GUN, 52/6 Post Free

M-O-S MAIL ORDER SUPPLY CO., The Radio Centre, 33 Tottenham Court Road, London; W.1. Tel: MUSeum 6667



HOME STUDY

backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an I.C.S. Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of Instruction covering radio and, if necessary, television including the following:

Complete Radio Engineering, Radio Service Engineers Radio Service and Sales, Advanced Short-Wave Radio Elementary Electronics, Radar, Radio, and Television Technology.

And the following Radio Examinations:

British Institution of Radio Engineers P.M.G. Certificates for Wireless Operators City and Guilds Telecommunications

Write today for our FREE "Radio" booklet, which fully describes the above ICS Courses.

International
CORRESPONDENCE SCHOOLS

Dept. PW9, International Bldgs., Kingsway, London, W.C.2

GARDNERS RADIO Ltd

will be pleased to send you a complimentary copy of their NEW 28 PAGE BROCHURE describing the

"SOMERFORD" MAINS TRANSFORMERS

including the new types

"BURLEY" and "HENGIST"

—POST THIS COUPON TO-DAY—

To: GARDNERS RADIO LTD., SOMERFORD, CHRISTCHURCH, HANTS.

Please send me your New 28 page Brochure.

Name

Address