


1/-

Vol. 27 No. 537

JULY, 1951

EDITOR:  
F.J. CAMM

# PRACTICAL WIRELESS

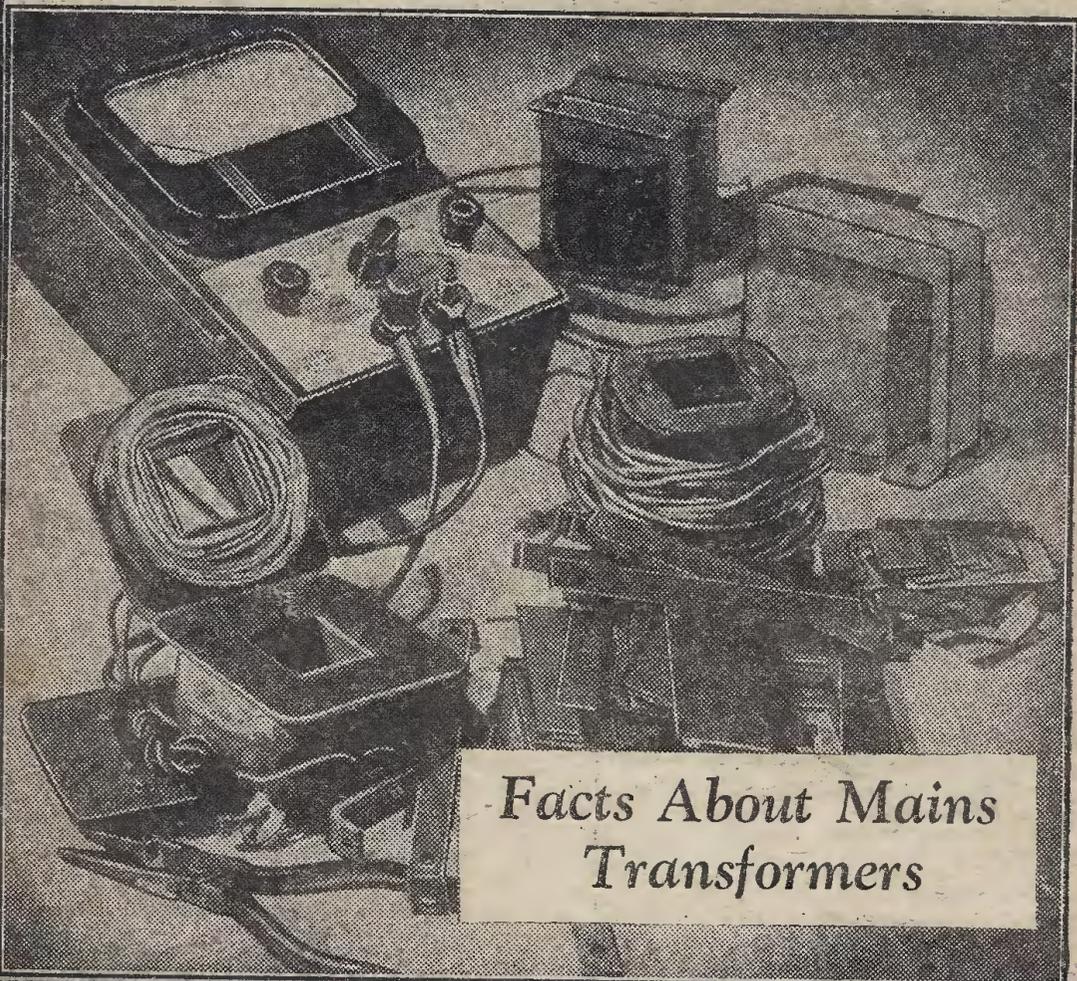

*Facts About Mains  
Transformers*

## IN THIS ISSUE

Electrify Your Gramophone  
 Radio Control of Models  
 Lining Loudspeaker Cabinets




Quality Straight Three  
 Building the "Alignoscope"  
 Using Multiple Valves

**THANK "Q"  
FOR BETTER  
LISTENING**

**- and for  
easier assembly!**



**...at LESS cost, too!**

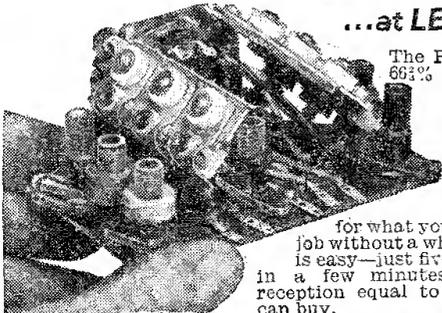

The P. Tax increase to 66½% on new receivers makes listening very expensive. Build your own simply, efficiently and cheaply by means of the Osmor "Q" Coilpack and pay only for what you get! It does a fine job without a whistle, and assembly is easy—just five connections made in a few minutes and you'll have reception equal to the finest money can buy.


As specified for conversion of the Type 25 unit of the TR1193, Type 18 and Wartime Utility receivers and others.

**OSMOR  
"Q" COILPACKS**

Send 5d. (stamps) for free circuits and new illustrated lists of Coils, Coilpacks and all Radio Components.

**OSMOR RADIO PRODUCTS LTD**  
(Dept. P.14.), BRIDGE VIEW WORKS, BOROUGH HILL  
CROYDON, SURREY Telephone: Croydon 1220

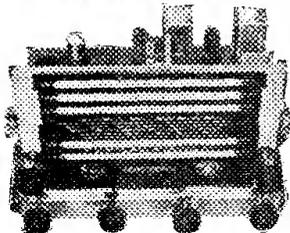**UP to the ARMSTRONG standard  
DOWN to 10.9 Metres!**



ARMSTRONG Model  
EXP 125/3 "All-Wave"  
14 Valve (inc. Cathode  
Ray) RADIOGRAM  
CHASSIS.

Produced primarily for the export market but available also to the home listener, provision of a continuous Wave-Band from 10.9-500 m. (plus 1,000-2,000 m. on the home model), is an outstanding feature of this chassis which combines exceptional performance with superb quality of reproduction.


- ★ Continuous Wave-Band Coverage from 10.9—550 m.
- ★ Radio Frequency Pre-Amplifier.
- ★ 2 Intermediate Frequency Stages.
- ★ Variable Selectivity.
- ★ Bass and Treble Lift Controls.
- ★ 15 watt Push-Pull Output.

The Armstrong range of chassis includes models from 7 to 14 valves.  
Kindly write for illustrated catalogue.

**Armstrong**  
**THE CHASSIS PEOPLE**

Armstrong Wireless & Television Co., Ltd., Warblers Road,  
Holloway, London, N.7. Tel: NORTH 3213  
**SOLE BIRMINGHAM AGENT:**  
Hayes Company, 1, Alcester Road, Moseley, Birmingham, 13.

**Three heads are  
better than one!**

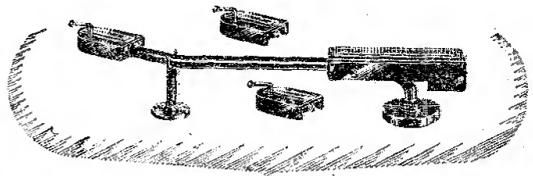

**For Standard and Microgroove recordings**

Microgroove recordings Green Spot.  
Modern standard recordings Red Spot.  
Older standard recordings Yellow Spot.

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Downward pressure 10-12 grams for standard recordings, and 5-7 grams for microgroove recordings.

Prices: With one Head £4.0.0, plus £1.14.8 Purchase Tax. Extra Heads each £2.10.0, plus £1.1.8 Purchase Tax. Spare Armature System with sapphire 14s. 8d. including Tax.

**a Connoisseur product**

Telephone: HALIFAX 69169

**A. R. SUGDEN & CO. (ENGINEERS) LTD.**  
Well Green Lane, Brighouse, Yorkshire.

**ICS**

**HOME STUDY**

**backs radio experience with  
sound technical knowledge**

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an I.C.S. Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television include the following:

Complete Radio Engineering, Radio Service Engineers  
Radio Service and Sales, Advanced Short-Wave Radio  
Elementary Electronics, Radar, Radio and  
Television Technology.

And the following Radio Examinations:

British Institution of Radio Engineers  
P.M.G. Certificates for Wireless Operators  
City and Guilds Telecommunications

Write today for our FREE "Radio" booklet,  
which fully describes the above ICS Courses.

**International  
CORRESPONDENCE SCHOOLS**

Dept. PW18, International Bldgs., Kingsway, London, W.C.2

# The New 1355 Conversion

Data for ALL FIVE TV Channels, 3/-.  
**AMPLIFIER 1135A** with EF39, EK32 and EL32, twin inputs, circuit, and our "1135A conversion data," these may be modified into a really fine little public address amplifier. ONLY 16/6.

**MAINS POWER PACK KIT**, providing 200 v. at 30 mA, approx., and 18 v. at .2 A. These are suitable for use with the above unit, to make a small self-contained amplifier. 19/6, complete with full instructions.

**TRANSMITTER 21**. Sending speech, CW or MCW, these are complete with valves, control panel, and key. The PA coils (not formers) and relays have been stripped by the M.O.S., but may easily be replaced with our circuit and instruction sheet. Tuning 4.2-7.5 and 18-31 mc/s. In First Class condition. OUR PRICE, 25/-.

**VIBRATOR PACK 21**. Delivering approx. 140 v. at 40 mA. from 6 v. input. These include a LT filter, and contain 2 metal rectifiers, six .1, two 4 µF., two 75 µF. condensers, etc., five chokes, vib. transformer, etc. 15/6. Soiled, for stripping, 9/-.

**ACCUMULATORS**, Brand New, multiplate, in spillable celluloid cases (3 1/2 in. x 1 1/2 in. x 4 in.), 7 AH., 5/11.

**RECEIVER 1225**. Complete with five EF50's, two EF39's, one EB34, these are ideal for 2 metres. ONLY 39/6.

**POWER PACK 532** with one 5Z4, one VU120 (5 KV), high voltage rectifier, two high cycle transformers, choke, etc. 17/6.

## RADIO EXCHANGE CO.

9, CAULDWELL STREET, BEDFORD. Phone 5568

## SOUTHERN RADIO'S WIRELESS BARGAINS

**WALKIE-TALKIE (TRANSMITTER-RECEIVER)**. Type 38 Mark II. Complete with 5 valves. Throat Microphone, Headphones and Aerial. 7 mc/s Amateur Band suitable for field use. Powerful Superhet Receiver. Modulated Transmitter. Guaranteed ready for the Air, less batteries, £3/10/-.

**R.3515 TELEVISION UNITS**. Complete with 21 valves, 6 Stage 14 mc/s I.F. Strip. Ideal for T.V. Conversion. Brand new in original wooden cases, £3/10/-.

**R.1355 RECEIVERS**. Brand new, as specified in Inexpensive Television, £3/5/-.

**RECEIVERS B.C.454 (49-100 Metres), B.C.455 (39-49 Metres)**. BRAND NEW, COMPLETE WITH 6 VALVES. BLACK CRACKLE FINISH, £3/10/-.

**COMMAND RECEIVERS**. Type CCT-461-04 (1.5 mc/s to 3 mc/s). Complete with 6 valves. 28 volts Dynamotor. Brand new, black crackle finish, £4.

**LUFBRA HOLE CUTTERS**. Adjustable from 1/8 ins. to 3/16 ins. for use on Wood, Metal, Plastic, etc., 5/9. **LUFBRA FLY CUTTERS**, 14/6.

**LIONEL "BUG" KEYS**. Genuine U.S.A. Automatic Morse Key. Type J-36. Few only, £3/7/6.

**THROAT MICROPHONES**. Magnetic type complete with long lead and plug, 4/6.

**CONTROL CABLES for COMMAND RECEIVERS**. B.C. 453/4/5, 14 feet, with adaptors, 9/6.

**RADIO COMPASS INDICATORS** with internal Selsyn Motor. Type T-82a, 3 inch Dial, 13/6. 5 inch Dial, 15/6.

**HAND GENERATORS**. 6 volts at 5 amps. With Crank, 21/-.

**SPEAKERS**. Celestion 2 1/2 inch. P.M. Moving Coil 3 to 5 ohms, 17/6.

**PLASTIC TRANSPARENT MAP CASES**. 14 inches by 10 1/2 inches. Ideal for Maps, Charts, Display, Photographs, etc., 5/6.

**STAR IDENTIFIERS**. With Hydrographic Office Modifications A-N Type I. Complete in case, 5/6.

**CONDENSERS**. 100 Assorted Tubular and Mica, all useful sizes up to 2 Mfd., 15/- per 100.

**WESTECTORS**. Type WX6 and W112, 1/- each, 11/- doz.

Full List of Radio Publications, 2 1/2d.

### SOUTHERN RADIO SUPPLY, LTD.


11, Little Newport Street, London, W.C.2. (Gerrard 6653)

## PRATTS RADIO

1070 Harrow Road,

London, N.W.10

Tel.: LADbroke 1734.

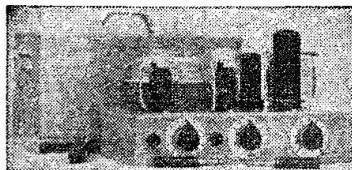

(Nr. Scrubbs Lane)  
**AMPLIFIERS READY TO USE.**

**MODEL AC10E** (as illustrated), 10 watt, 4 valve unit, neg. feedback, separate mike stage and separate mike and gram inputs, 2 faders and tone control. Input volts, mike .002, gram .21 v., £9-15-0.

**MODEL AC18E**, 6 valve unit with p/pull output of 18 1/2 watts, separate mike stage and separate mike and gram inputs, 2 faders and tone control, feedback over 3 stages. Input volts, mike .003, gram .3 v., £14-14-0.

**MODEL AC32E**, 6 valve unit with p/p output of 32 watts. Spec. as AC18E, £17-17-0.

**MODEL U.10E**, D.C./A.C. mains. P/p output of 10 watts. Spec. as AC18E, £12-12-0. All above are COMPLETE WITH CASES and chrome handles. Outputs match 3, 8 or 15 ohm Speakers.

**MODEL AC4C**, A.C., or **U4C**, D.C./A.C., 3 valve, 4 watt amplifier chassis, output to 3 ohms, £5-5-0. All above carriage paid. As supplied to domestic and industrial users since 1945.

**SPEAKERS**. Plessey, 5in., 12/6. W.B., 2in., 17/6; 5in., 19/-; Goodmans, 12in., 130/-; Rola, 8in., 30/-; 10in., 35/-; 3in., 21/-.

**RECORD PLAYERS**. Collaro, A.C. only. Rim drive, complete with pick-up, auto-stop, Magnetic, £6-9-0. Crystal, £6-15-6.

**VALVES**. 1S4, 1T4, 1R5, 1S5, 3S4, all at 9/6. 6V6, 5Z4, 6F6, 6X5, all 10/-; 6J7, 6J5, 6K7, all 5/9. Brand new.

**COILS**, ETC. Wearite "P" coils, all types, 3/- ea. Weymouth "H" coils, 3/3. Osmer "Q" coil packs, 40/4, tax paid. Wearite M400 I.F.'s, 10/6 ea. Weymouth P4's, 15/- pair. Denco T.R.F. with reaction L. & M.W., 6/6 pair. Dual range coil with reaction, 4/6.

**TRANSFORMERS, CHOKES, ETC.** Mains, 2 x 350 v., 80 m.a., 0-4-5 v., 2 a.; 0-4-6-3 v., 4 amp., 18/6. Ditto, 2 x 250 v., 17/6. Filament 6 v., 1 1/2 a., 5/9. Speaker Transformers, 6V6 P/P to 3, 8, 15 ohms, 19/6; 6V6 to 3 ohms, 3/11; miniature 1S4/3S4 O/Transfrs., 4/2.

**Chokes**, 60 m.a., 20 hv., 380 ohms, 6/9; 20 hv., 100 m.a., 400 ohms, 14/6; 10 hv., 150 m.a., 200 ohms, 14/6; 90 m.a., 10 hv., 180 ohms, 11/6; 40 hv., 20 m.a., 1,250 ohms, 5/9.

**CONDENSERS** (only 1951 stock offered), .0001/2/3/5, all 7d. ea. .01, .005, .001, all 9d. .05, .1 x 500 v., 10/4d. B.I. (all 500/550 v.) 8 mfd., 3/3; 8+8, 4/9; 16 mfd., 4/-; 8+16, 6/-.

**MISCELLANEOUS**. Octal bases, Pax., 4d. Amphenol, 6d. Voltage droppers with feet and two sliders, .2 a. 920 ohms or .3 a. 750 ohms, 5/- ea. Linecord (thick good quality type), .3 amp. 3 way, 60 ohms ft., 7d. ft. Presets, 50 pf., 4d.; 100 pf., 1 1/2; 250 pf., 1/9; 500 pf., 2/-; B7G valve bases, Pax., 9d.

All goods new and unused. No W.D. or manufacturers' surplus components offered. Post paid over £1. C.W.O. or C.O.D.

## The solder for all HOME TELEVISION CONSTRUCTOR SETS

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60/40 High Tin Television and Radio Alloy. The size 1 Carton contains 37 feet of solder, costs 5/-.



## Ersin Multicore Solder

In case of difficulty in obtaining supplies, please write to:  
**MULTICORE SOLDERS LTD., MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1 • REgent 1411**

# By request

At the request of many of our constructor friends, we give here full details of the famous range of Stentorian chassis.

Type	Cone dia.	Flux Density (Gauss)	Pole dia.	Gap length	Flux face	Total Flux	Speech coil Impedance (ohms)	Handling Capacity (Watts)	PRICES		
									With Trans.	Without Trans.	
									£	s.	d.
*S.2.57	2½"	7,000	.375"	.033"	.093"	5,285	3	.3	—	17	3
*S.3.57	3½"	7,000	.625"	.035"	.125"	11,500	3	2	—	18	6
S.507	5"	7,000	.75"	.040"	.125"	14,000	3	2.5	1	8	0
*S.610	6"	10,000	.75"	.040"	.125"	20,000	3	3	1	11	9
S.707	7"	7,000	1"	.043"	.187"	27,650	3	3.5	1	14	0
S.810	8"	10,000	1"	.043"	.187"	39,500	3	5	1	17	3
S.912	9"	12,000	1"	.043"	.187"	47,400	3	7	2	3	6
S.1012	10"	12,000	1"	.043"	.187"	47,400	3	10	2	16	9
S.12135	12"	13,500	1.5"	.050"	.25"	106,000	15	15	9	6	9
S.1814	18"	14,000	2.5"	.0625"	.312"	227,000	12	30	—	24	0

Further details of these speakers and of the famous Concentric-Duplex models gladly sent on request.


\* All chassis material is of Mazak 3 except S.2.57, S.3.57 and S.610 which are of Drawn Steel



# Stentorian
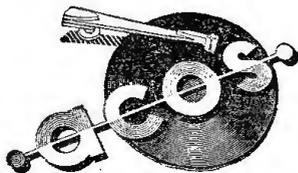
## LOUDSPEAKER CHASSIS

WHITELEY ELECTRICAL RADIO CO. LTD. MANSFIELD · NOTTS



## high fidelity MICROPHONES

FOR PUBLIC ADDRESS, RECORDING, AMATEUR RADIO

TYPE MIC 22 incorporates the famous Acos "Filtercel" insert, giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 cps. The microphone is vibration- and shock-proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head:—



**MIC 22-1** is for fitting to any British or American type standard floor stand and can also be used as a hand microphone.



**MIC 22-2** is supplied as a complete unit incorporating an attractive desk stand with side cable entry.

**PRICE £6.6.0** (Either Model)

TYPE MIC 16 incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 cps. Performance is unaffected by vibration or shock and low frequency wind noise. As in the case of the MIC 22 described on the left two alternative mountings are available for the MIC 16 head:—



**MIC 16-1** is ready for fixing to either British or American type floor stands by means of a knurled ring.



**MIC 16-2** is a complete desk stand unit with side cable entry.

**PRICE £12.12.0** (Either Model)

# Practical Wireless

19th YEAR  
OF ISSUE

EVERY MONTH.  
VOL. XXVII. No. 537. JULY, 1951

Editor F. J. CAMM

COMMENTS OF THE MONTH

BY THE EDITOR

## The TV Accident

**I**N the early days of radio one or two accidents were caused due to electric shocks.

One person was killed because there was a flash of lightning at the particular second that he went to connect his aerial lead. Another suffered a fatal shock by touching the earth terminal.

In the early days of television an engineer was electrocuted at Alexandra Palace when he happened accidentally to touch the positive and negative terminals of a 2 Kv. supply. Milder accidents have been caused by inexperienced people placing their hands inside a wireless set for the purpose of making some adjustment whilst the set is switched on. In all of these cases the newspapers endeavoured to make the public's blood curdle by representing a wireless set as a lethal machine, the operation of which imposes great risks.

The number of accidents during the past 30 years could be counted on the fingers of one hand, and the very rarity of these occurrences is an indication of the minuteness of the risk.

In a recent case, a small child had its feet on a metal curb in front of an electric fire which was plugged into the same point as the set. By a million-to-one chance he happened to touch the curb and the metal grille of the set at the same time, and was killed. This was, undoubtedly, a freakish circumstance which might not happen again in a lifetime, and it is one against which no manufacturer could safeguard.

The circuit used in this particular receiver is one which is common to a number of manufacturers, and, doubtless, now that the accident has happened steps will be taken to see that it does not occur again. The public should not presume from some of the lurid statements made in the newspapers that television sets are dangerous. The design of the receiver in question is in accord with standard radio and TV practice, and at least 300 sets at present in use employ the same circuit. Undoubtedly some defect had occurred since the receiver was sold because the accident could not have happened on a factory-tested receiver.

All manufacturers submit their sets to a

soak test, under load, and are then rechecked to see whether any of the vital components, such as resistances, condensers and transformers, have broken down or altered in value.

In the case in question it was disclosed that the baffle holding the speaker was in contact with the metal chassis, and this could not have been so when the receiver passed its final factory test. The contact was caused by a protruding metal screw in the speaker, which was touching the metal grille, which had probably been dented by a blow.

All forms of electrical apparatus have at times caused accidents, sometimes fatal, and it would be wrong to assume that television receivers are more dangerous than, say, an electric hair-drier. However, we learn that manufacturers are making the necessary adjustments to design to prevent a recurrence of this infinitesimally remote risk.

### V.H.F.

V.H.F. was demonstrated to the Parliamentary and Scientific Committee, and following this the Postmaster-General was asked in Parliament when plans are to be announced for nation-wide V.H.F. broadcasting coverage. He replied that the B.B.C.'s proposals for a V.H.F. system using F.M. were being examined. The proposals are far-reaching and it was, therefore, too early for him to make a statement.

The impression we have gained from our own enquiries is that the rearmament programme, and the general worsening of the international situation, will cause these plans to be postponed for a considerable time.

### Up and Up

Nearly 12½ million broadcast receiving licences, including nearly 764,000 for television, were current in Great Britain and Northern Ireland at the end of March, 1951. Absorption point has by no means yet been reached, but we must expect to see the television licences go up and the ordinary broadcast receiving licences slow up within the next five years.

The number of television licences has more than doubled within the past year.—F. J. C.

# ROUND the WORLD of WIRELESS

## Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ended March 31st, 1951.

Region	Number
London Postal .. ..	2,364,000
Home Counties .. ..	1,650,000
Midland .. ..	1,754,000
North Eastern .. ..	1,906,000
North Western .. ..	1,609,000
South Western .. ..	1,065,000
Welsh & Border Counties ..	729,000
<b>Total England &amp; Wales ..</b>	<b>11,077,000</b>
Scotland .. ..	1,120,000
Northern Ireland.. ..	207,000
<b>Grand Total .. ..</b>	<b>12,404,000</b>

The above total includes 763,767 television licences.

Complaints are sometimes made that it is inconvenient to put down the whole licence fee (£1 for sound; £2 in the case of television and sound) when a licence has to be renewed. The Stamps Saving Scheme allows money to be accumulated in small amounts for encashment later; one six-penny stamp a week would more than provide for the renewal of a sound licence. Savings stamps may be purchased at any post office; books to take the stamps may be had free of charge.

## The Morale Raiser

A RADIO device which is causing a lot of comment and amusement in the Lion and Unicorn Pavilion of the Festival of Britain is the "Morale Raiser," a machine which steadily pats its wearer on the back and vociferates words of encouragement. It was described by Brian Johnson in "In Town To-night," and we understand is shortly to be shown upon the television newsreel.

The Morale Raiser incorporates a Scophony-Baird Home Recorder, made by the manufacturers of Baird television. This was chosen after a number of comparative tests and will now be in use continuously throughout the Festival.

## P. G. A. H. Voigt

NEWS of this well-known personality in the field of high-quality sound reproduction has reached us from Canada, where Mr. Voigt, B.Sc., A.M.I.E.E., F.B.K.S., is part-time instructor in electronics at the Ryerson Institute of Technology in Toronto.

On March 15th last at the University of Toronto he gave a lecture on high-fidelity reproduction to the Wireless Association of Ontario, including a demonstration of his re-matched diaphragm loudspeaker with 22,000 gauss field magnet. The equipment used was an American version of the William-

son amplifier, the Voigt moving-coil pick-up with diamond stylus and his latest P.M. loudspeaker. Decca 78 r.p.m. "London" "ffrr" records were used for the demonstration which was attended by a large audience, including Frank Murphy, now resident in Toronto.

Mr. Voigt has expressed the opinion that this was the best demonstration he has ever given, largely due to the application of technical developments of recent years. He adds the comment that the 33½ slow-speed is definitely regarded as the best speed for handling all serious music recordings, but the 45 r.p.m. speed is considered an unfortunate innovation. Even with long-playing records automatic changers are popular, so as to permit one to load up a batch of records and obtain a long period of music uninterrupted by commercial announcements in the radio programmes.

Mr. Voigt is making a slow recovery in his health, which was the main reason for his emigration to Canada.

## Marconi Veterans' Reunion

THE Fifteenth Reunion and Annual General Meeting of the Marconi Veterans' Society was held on Saturday, May 5th, 1951, at Caxton Hall, Westminster. The qualification for membership is 25 years' service with the Marconi Companies, and of the total membership of 2,200 no less than 1,900 are still serving. At noon 160 veterans gathered to talk over old times, and at lunch H. E. Watterson (1902) presided, with W. I. McGhee (1904) as deputy. In support were C. E. Rickard (1898), H. M. Dowsett, C. S. Franklin, and Andrew Gray (1899), W. Davies, A. A. Kift, H. T. Round, G. E. Turnbull, and W. M. Sampson (1902), W. Platt (1904), F. Beatson, A. J. Chesterton, Sir Ernest Fisk and C. C. Howe (1906). R. C. A. Kroes and L. F. Meyer were present representing the Dutch members and received a very cordial welcome.

The chairman proposed the health of New Veterans, to which R. H. G. Cox replied, and F. H. Lansbury proposed the toast to Absent Friends.

## Radio-sonde

ONE of the many interesting exhibits shown by the General Electric Company at the Festival of Britain is the Radio-sonde Mark II. It is on view in the Dome of Discovery, and was manufactured by Salford Electrical Instruments, Ltd., a subsidiary company of the G.E.C. The Radio-sonde was developed in conjunction with the British Meteorological office. Elevated by a hydrogen-filled balloon it measures pressure, temperature and humidity up to a height of about 65,000ft. The instrument comprises, in the main, a radio transmitter, amplitude modulated by three units which convert pressure temperature and humidity into audio frequency. Each meteorological unit is successively switched in the modulation circuit of the Radio-sonde, and is picked up by

means of a radio receiver and the frequency determined by an interpolation oscillator on the ground.

#### Mr. H. J. Leak

**H. J. LEAK**, M.Brit., I.R.E., managing director of H. J. Leak & Co., Ltd., is visiting his European agents. While in France he has been asked to call upon the President of the Association des Amateurs de l'Enregistrement Sonore, and in Switzerland on the President of the Association Suisse des Amateurs de l'Enregistrement Sonore to convey fraternal greetings from the members of the British Sound Recording Association, and to discuss the proposals from these Associations to affiliate with the B.S.R.A.

#### Engineering Services Group

**THE** B.B.C. announce that Mr. L. W. Turner, A.M.I.E.E., has been appointed assistant head of the Engineering Services Group in succession to Mr. E. L. E. Pawley, who is now head of that Group. Mr. Turner joined the B.B.C. in 1936 from the International Marine Radio Company. After four years at the Daventry short-wave station he was made responsible for the aerial system there, and in 1943 became assistant engineer-in-charge. In 1948 he was transferred to Head Office and appointed an assistant to the Superintendent Engineer Transmitters.

#### British Transmitter for Sweden

**A** FURTHER contribution to Britain's export drive in hard currency areas is the recent addition to the broadcasting services in Sweden of a "Standard" medium-wave broadcast transmitter at Gothenburg. This transmitter has a power output of 150 kW. with two radiators giving a directional field pattern with maximum field strength on the landward side and minimum towards the sea.

To minimise interference, the signal is reduced in the direction of N. W. Africa, where a broadcast transmitter is working on the same frequency.

It is interesting to note the growth of Gothenburg station. Built in 1925, it was one of the first radio broadcasting stations in Sweden, and was equipped with a transmitter of 500 watts power; in 1928 it became a 10 kW. station serving a public of about 400,000 and now in 1951 the new 150 kW. transmitter is serving about 750,000 of the Swedish population. In each case the equipment was manufactured by Standard Telephones and Cables, Ltd., a tribute to British workmanship.

#### N.F.G.S.

**THE** second conference on the gramophone and its repertoire, organised by the National Federation of Gramophone Societies, was held at High Leigh, Hoddesdon, Herts, in March, 1951. The first conference of this kind was held at High Leigh in 1938.

About 70 representatives of gramophone and recorded-music societies from all over Great Britain attended the week-end activities. Speakers included Mr. Julian Herbage (of B.B.C. Music Magazine), who opened the conference, Lionel Salter on record criticism, Ian McPhail and A. C. Cameron on the gramophone in education, and a technical session by K. R. McLachlan and R. Yorke,

of the University College, Southampton. Demonstrations of high-quality record reproduction were given by Mr. H. J. Leak, Mr. P. J. Walker (Accoustical Manufacturing Co., Ltd.), and Col. F. G. G. Davey (E. M. G. Handmade Gramophones, Ltd.).


#### Mr. W. J. Chalk

**MR.** W. J. CHALK, B.A., has joined the staff of the Overseas and Engineering Information Department of the B.B.C. to deal mainly with work connected with the allocation of wavelengths for broadcasting, and to take part in international and other conferences on this and related subjects.
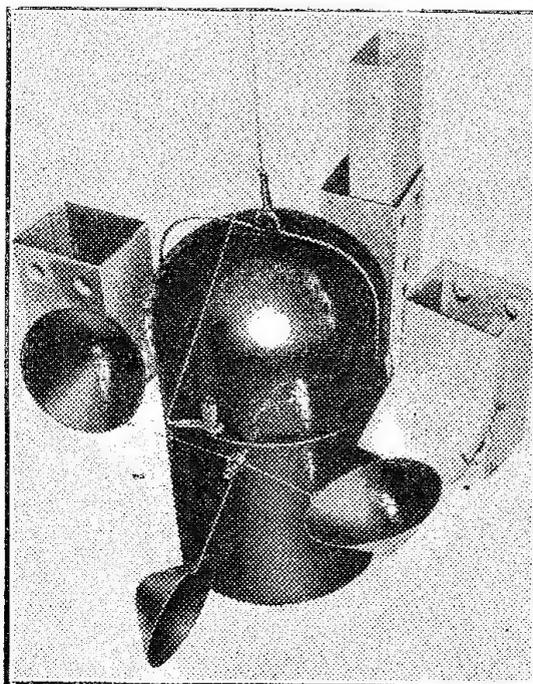
#### Faraday Medal Award

**THE** President of the Institution of Electrical Engineers, Sir Archibald Gill, M.I.E.E., together with a large number of members, attended at the Marconi Works, Chelmsford, recently to present the Faraday Medal to Mr. T. L. Eckersley, B.A., B.Sc., M.I.E.E., F.I.R.E., F.R.S.

Owing to illness Mr. Eckersley was unable to attend a London function and, such is the esteem in which he is held by brother members, the un-



*The Radio-sonde equipment which is exhibited at the South Bank Exhibition.*

precedented step was taken to hold the ceremony near his home.

#### B.B.C. Networks

**SPECIAL** telegraph equipment has been designed, including test gear and a switchboard, all of which incorporate many novel features and enable a very rapid and accurate transmission of scripts, news, etc., to be achieved. One telegraph channel has been allocated as an engineering teleprinter network, connecting the control rooms in London, Tatsfield, Birmingham and Manchester together, on an "omnibus" circuit (later on Glasgow, Bristol and Bush-House will be added) primarily for the transmission of service messages.

# Electrify Your Portable Gramophone

A Miniature Amplifier for Record Reproduction

By L. FURTH

**T**HE recent release of a new Mullard valve, type ECL80, a triode/output pentode combination, opens up new fields for the miniature equipment enthusiast. One of its many possibilities is described in this article, which deals with the construction of a small, entirely self-contained amplifier for use with a pick-up. It can easily be accommodated in the cabinet of a portable hand-wound gramophone.

The amplifier has a two-stage circuit of conventional design, using the triode-section of the valve as voltage amplifier, with resistance/capacity coupling to the output pentode.

In considering the details, let us begin with the heater supply for the valve. As A.C. mains are now almost standard everywhere, a heater transformer delivering 6.3 volts is best suited, mainly on account of its small size, cool operation (as against mains dropping resistors or line cords, which will still have to be used with D.C. mains), and—not a point of small importance these days—cheapness. An indicator lamp may be added as a refinement and should, of course, be paralleled with the valve-heater.

The A.C. input to the metal rectifier—also cheaper as well as cooler than a valve—is taken from the mains via a ¼-watt 150 ohms surge limiter (R9). The wattage, being quite sufficient for normal operating conditions, ought not to be exceeded. Should the smoothing condenser develop a short-circuit, replacement of the 150 ohms resistor (which will burn out) will be found more economical than replacing the rectifier.

C.R. smoothing is employed in this model, but a smoothing choke could be used with correspondingly smaller associated condensers. As the maximum D.C. voltage on the triode-anode should be limited at 200 volts, the value of R9 might, in that case, have to be increased, and the values of the two bias resistors modified.

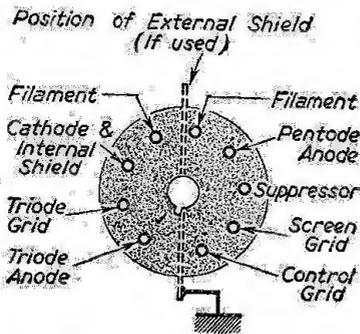


Fig. 2.—Details of valve base for the ECL80 valve.

### Precautions

Taking the rectifier A.C. input direct from the mains necessitates the use of the mains as return circuit, since no separate H.T. transformer winding is provided. Following the usual practice of using the chassis as the common "earth," certain safety precautions will have to be taken.

The pick-up, the control spindles and other metal parts which may be exposed might carry the full mains voltage with respect to true earth. It is therefore imperative to use isolating condensers in the pick-up leads, a type of indicator lamp whose exposed metal portion is not connected electrically to any part of the circuit (no, not even chassis!), and a screened, insulated speaker cable. The grub-screws securing the plastic knobs must be sunk so that they cannot be touched. And remember that all these precautions are wasted efforts if you use chassis bolts which raise their ugly heads on the outside of the cabinet. Use plastic or wooden mounting blocks secured—inside the cabinet—by wood screws. It's safer and neater.

Almost any type of high-impedance pick-up can be used as shown in the diagram, but other types will probably require an input matching transformer. In such cases the maker's instructions regarding the input circuit should be followed. In the case of crystal pick-ups the tone-control will, as a rule, take the form of a scratch filter (with its property of high-frequency attenuation), and that type of tone-control will then be part of the input circuit. There again, the pick-up manufacturer's recommendations should be observed regarding the choice of component values.

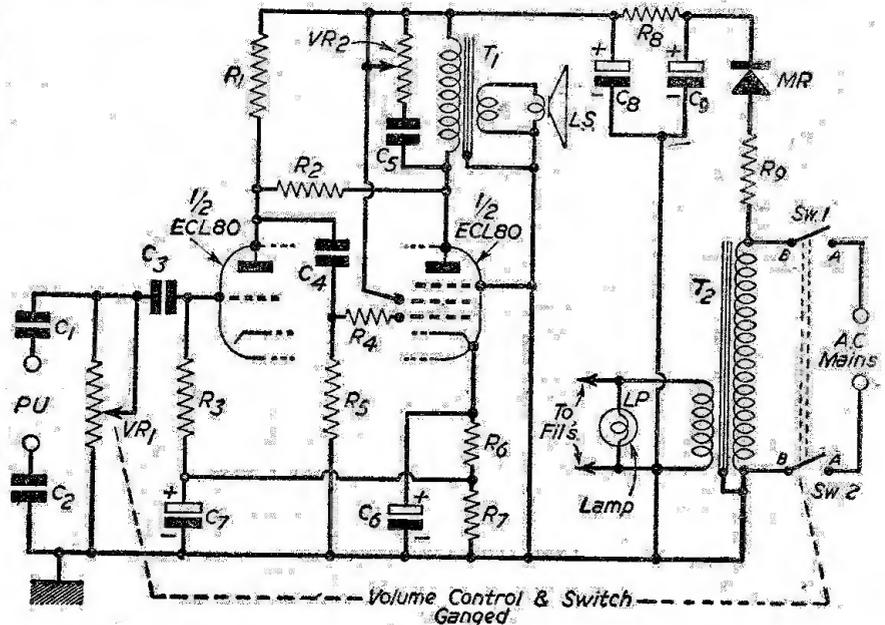


Fig. 1.—Theoretical circuit of the amplifier.

At the same time, however, a fixed C.R. shunt should be left across the output transformer primary so as to prevent a rise in the load impedance (and consequent distortion) at the high audio-frequencies. The choice of values for this shunt is best determined experimentally and will depend largely upon how much you value fidelity in the matter of high-frequency reproduction.

A simple form of negative feedback is employed by putting a resistor (R2) between the two anodes. Its omission, though increasing the gain, will have detrimental effects on the quality, especially at low frequencies.

**Speaker**

Correct matching to the speaker is important. Here a word of advice to all who, as I, like to play about with midget parts : be midget-minded in all respects if you must. But do not sacrifice quality of reproduction to a couple of cubic inches. It will bring you no joy, nor pats on the back from others. That means use a decent-sized speaker (not less than a minimum of 5in.) and an output transformer which is not only correctly matching output valve to speaker but also constructed on more generous lines than the smallest one you can buy. The speaker can easily be accommodated in the cabinet lid (suitably protected, and facing outwards so that you can play the gramophone with the lid closed), so why not use 6½in. at least ? Flat (" wafer type ") speakers of that diameter are available.

Now a word about the bias network. The ECL80 has a common cathode, but the two grids require different standing bias voltages. Although there are

a number of ways in which they can be obtained, the simplest is by tapping the cathode resistor as shown. The value of C6 will seem unusually high. Its purpose is the prevention of feedback through the common cathode resistor, which may give rise to low-frequency distortion or even continuous oscillation.

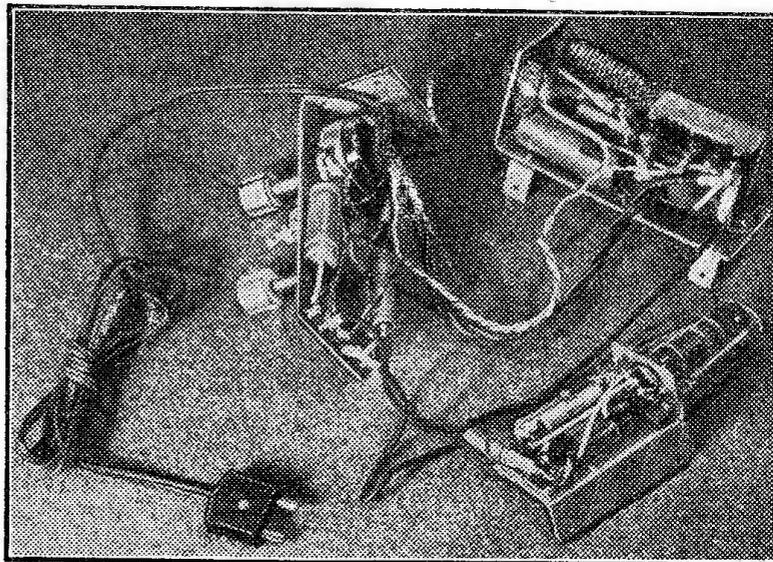


Fig. 3.—The separate units as depicted in Fig. 4.

To prevent feedback at the valve socket, a shield may be placed across the socket between triode and pentode pins. This shield, which is easily made from tinned iron sheet, is soldered to the centre spigot (which, incidentally, should be earthed, anyway) and pin 5, and bonded to chassis. It may not be required at all, but should be tried if no other method of combating feedback succeeds.

**PARTS LIST FOR MIDGET GRAMOPHONE AMPLIFIER**

No.	Function	Value	Rating or Specification	Remarks
C 1	Isolating	0.1 $\mu$ F	500 v. wkg.	Pref. Metallised
2	DC-Blocking	0.005 $\mu$ F	350 v. or more	" "
3	Coupling	500 pF	500 v. wkg.	Pref. Mica
4	Tone Control	0.02 $\mu$ F	350 v. wkg.	
5	Decoupling	100 $\mu$ F	12 v. wkg.	Electrolytic
6	Bias Reservoir			
7	"	20 $\mu$ F	12 v. wkg.	"
8	Smoothing	32 $\mu$ F	350 v. wkg.	"
9	Reservoir	8 $\mu$ F (max.)	350 v. wkg.	"
R 1	Triode Load	0.22 M $\Omega$	½ W or more	"
2	Feedback	0.68 M $\Omega$	"	"
3	Triode Bias	0.22 M $\Omega$	"	"
4	Grid Stopper	10 k $\Omega$	"	"
5	Gridleak	0.68 M $\Omega$	"	"
6	Common Bias	230 $\Omega$	"	"
7	"	275 $\Omega$	"	"
8	Smoothing	3.3 k $\Omega$	1 W or more	Pref. Wirewound
9	Surge Limiter	100 $\Omega$	½ W	"
VR 1	Vol. Control	0.25 M $\Omega$	Log	With DP switch
2	Tone Control	10 k $\Omega$	"	"
LP	Indicator	6.3 v.	0.15 or 0.3 A.	
TI	Output	Z prim=11 k $\Omega$		Ratio 66 : 1 for 2.5 $\Omega$ Speech coil impedance
T2	Filament	6.3 v.	3 W or more	
MR	Rectifier	250 v.	30 mA.	

**Layout**

The general physical layout is not too critical and will, in most cases, have to be guided by the available space. Along with the speaker its transformer might best be mounted in the lid, and the whole apparatus could, if necessary, be split up into a power pack and the amplifier proper. A separate control panel carrying tone- and volume-control as well as indicator lamp might be found suitable where space is really restricted.

Constructing and installing the particular amplifier on which I carried out experiments necessitated this splitting up into separate units. Screened leads, soldered to tag panels on each individual unit, form the connections. Details of

Two and single insulated screened lead, connecting wire, nuts, bolts, woodscrews, B9A valveholder and valve retainer, 1 ECL80 valve, 2 control knobs, P.M. speaker, mains lead and plug, pick-up, indicator lamp holder, tag strips.

them are given in the unit block diagram. All the screening braids are themselves insulated.

Concerning the question of screening, I would say, as a general rule, when in doubt—screen it. Leads which carry A.C., whether they be heater wires or the connection between output-anode and output transformer, are liable to radiate, and induce hum or feedback voltages in adjacent parts. It is therefore clearly necessary to prevent them from doing so.

Equally, connections and components in the early stage of the amplifier are vulnerable, and should be protected from unwanted radiation. It may be advisable to screen C1 and C2; and certainly the metal casings of the tone and volume controls should be bonded to chassis. In the amplifier illustrated in the photograph, the input (isolating) condensers have a metal casing which facilitated connecting them to chassis. Such practice may be of doubtful merit in some R.F. circuits, but can usually be followed with impunity and advantage in audio work. Excessive heating up during soldering must be avoided. If a metal pick-up is used, the pick-up casing must not be connected to chassis directly, but via another isolating condenser. 0.1  $\mu$ F./500 v. is a suitable value.

**Final Details**

The ECL80 operates at a pretty high bulb temperature, so provide some airflow by drilling a few holes below and above its mounting place in the cabinet. The holes on top may be hidden by the turntable, and should be covered with metal gauze or some textile material. Gramophone needles have a nasty habit of disappearing through such holes and causing trouble in the "works."

The amplifier is meant to be portable, and a valve retainer will, therefore, be found useful. The power output is definitely more than adequate for normal home requirements; but this is not a public

address amplifier. With care in the construction, especially with adequate screening and discriminating choice of output transformer, very good quality can be obtained. And there is absolutely no microphony present.

All important voltages and currents have been

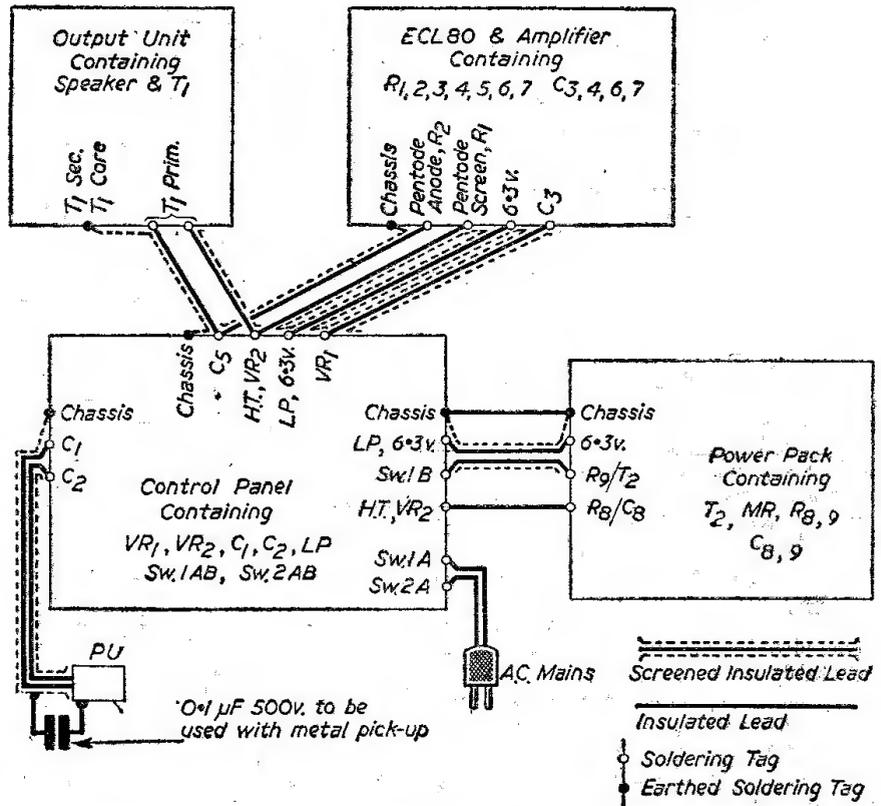


Fig. 4.—Unit block diagram of the amplifier. The parts are shown in Fig. 3.

tabulated, and should be regarded as guiding values. No serious view need be taken of slight departures from them. The same applies to the component values. In the design of this amplifier, the valve makers' application data and published valve characteristics have been studied, and it is recommended that this should be done by anyone using a type of valve which is new to him.

Basically, the circuit described here lends itself to various adaptations, especially for intercom. installations, midget radio sets, or small recording apparatus.

**TEST VOLTAGES AND CURRENTS**

Avo 7 Range	Volts	Milliamps	Measured at—
400 v. D.C.	120	—	Triode Anode
400 v. D.C.	198	—	Pentode Anode
400 v. D.C.	207	—	Pentode Screen
10 v. D.C.	4.2	—	Junction R7/C7
10 v. D.C.	7.8	—	Cathode
0.01 A. D.C.	—	4	Triode Anode Pin
0.1 A. D.C.	—	11	Pentode Anode Pin
0.01 A. D.C.	—	1	Pentode Screen Pin
0.1 A. D.C.	—	16	Junction R8/MR-C9

Readings were taken with supply volts=210 A.C., vol. contr. max., no signal input,  $E_F=6.3$  v.

**JOIN THE PRACTICAL GROUP**  
 Edited by F. J. Camm

---

**PRACTICAL ENGINEERING, 6d.**  
 Every Friday.  
 For Engineers, Mechanics, Designers and Works Managers.

**PRACTICAL MECHANICS, 1/-**  
 Every Month.  
 Devoted to Mechanics, Science and Invention

**PRACTICAL TELEVISION, 1/-**  
 Every Month.

# Radio-controlled Models

Constructional Details of a 3-stage Lightweight Receiver

By R. SANVOISIN, B.Sc.

**N**OW that the Hivac sub-miniature valves are available at reasonable prices from many dealers the field of radio control for model boats and 'planes is opened to many people who otherwise would never bother, due to the outlay on equipment which is exposed to the danger of complete destruction in a runaway model.

The writer had for some time been experimenting with the usual single-valve super-regenerative receiver operating in the band 26.96-27.28 Mc/s, but without much success in the case of these sub-miniature valves. With their low value of mutual conductance and low maximum anode voltage (30 volts) complete super-regeneration was found almost impossible to attain, whatever the other circuit values were. Although the receiver was quite sensitive, the change in anode current on switching on a carrier was not of sufficient magnitude to operate a relay, nor was the operation very stable.

Slight changes in filament voltage would throw the circuit into or out of oscillation quite unpredictably.

Hence, experiments were carried out to see if it were possible to employ a modulated carrier at the transmitter and amplify the modulation tone in the receiver to a sufficient level to operate a trigger circuit and then a relay. This was found to be highly successful, giving greatly improved results with only slight increase in the overall weight of the receiver.

## The Circuit

In order to operate a relay from the tone an A.F. pentode biased to cut-off, and positive feedback to the grid, was employed. Fig. 2 gives the final circuit. The tone is impressed on the grid of the valve from the anode of the preceding stage at A, while a negative bias is also applied via the resistance R and is of sufficient magnitude to prevent the valve from drawing anode current.

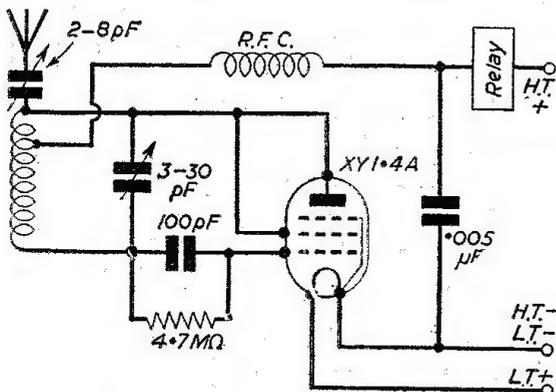


Fig. 1.—Detector stage of the receiver.

If the amplitude of the tone exceeds that of the bias the tips of the A.C. wave will bring the grid sufficiently positive to allow anode current to flow. A.C. will then flow in the anode circuit and be communicated to the rectifiers X1 and X2. These rectifiers rectify the A.C. to produce a D.C. voltage drop across R, which opposes the bias and so drives the grid positive. This causes more anode current to flow and so by a cumulative action causes the valve to conduct and pass its maximum anode current, limited only by the emission of

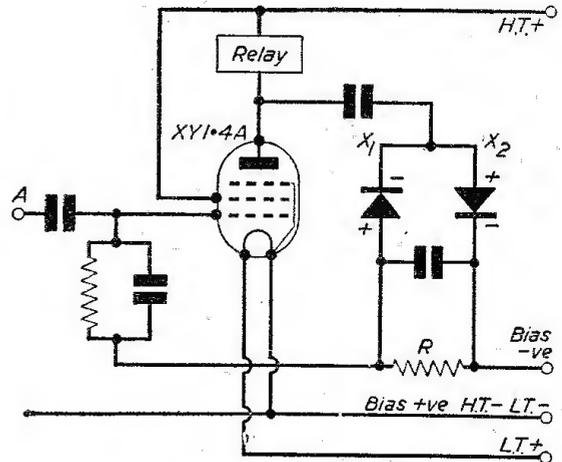


Fig. 2.—Final circuit of the A.F. stage.

the filament. In the case of the sub-miniature valve type XY1.4A, this was about 2 mA., and was quite sufficient to hold in the relay a sensitive, high-impedance type as used in the American SCR522 receiver as squelch relay. When the tone ceases the circuit returns to its original condition, no current flows in the valve, and the relay drops out.

This circuit was employed with the original super-regenerative detector, plus an intermediate audio-frequency amplifying stage to form the final receiver, which was mounted on a piece of bakelite, 3in. by 4in. by 1/16in., the whole receiver weighing 4.7 oz. Fig. 3 shows the circuit.

## Constructional Details

The coil is wound with 15 turns of 18 S.W.G. enamelled wire, and is 3/4 in. diameter and 1in. long, tapped 6 1/2 turns from the anode end. To keep down the weight no former is used, but the finished air-spaced coil is thoroughly soaked in polystyrene cement to make a really firm, rigid assembly that will not vibrate and change frequency with the movement of a model. With the tuning condenser specified—a Phillips concentric trimmer—the complete 27 Mc/s band allowed for radio control of models plus part of the 28 Mc/s amateur band is

covered, and once the centre of the band (27-12 Mc/s) is found the trimmer may be locked in position with a spot of Durofix to prevent frequency shift with the movement of the model. The R.F. choke employed is not very critical—about 50 turns of 38 S.W.G. enamelled wire wrapped round a  $\frac{1}{2}$  in. diameter paper tube is quite satisfactory, and this should be mounted at right angles to the axis of the tuning coil to prevent coupling, since all the components are necessarily very closely spaced.

After the detector stage a perfectly normal A.F. amplifier follows, with slight modifications to suit the tiny valve which, in this case, has a 0.75 volt filament. To drop the other 0.75 volts from the 1.5 volt filament battery, a 22 ohm  $\frac{1}{2}$  watt resistor is employed. From the anode of this stage a .005  $\mu$ F condenser couples the output to the positive feedback trigger circuit with the relay in its anode circuit. Two of the new germanium crystal diodes were employed for X1 and X2, but the cheaper Westinghouse midget Westectors will be quite satisfactory and much less expensive.

As far as mechanical considerations go, the only facts that need to be taken into account are to keep the tuned circuit as far away from the relay, etc., consistent with the compactness of the whole receiver, which, of course, has to be mounted inside a model, supported on elastic bands or springs to damp out vibrations.

### Aerial

The aerial is most satisfactorily a length of about 18 in. of fine wire connected at a convenient point on the model, though this may be varied to suit the layout of any particular model. The aerial coupling condenser has to be adjusted for optimum operation when the receiver and transmitter are well separated. Quite loose aerial coupling is usually found to give best results.

Batteries are carried in a separate compartment in the model to give an even distribution of weight. A 30-volt deaf-aid layer-built battery, type B23, for H.T., and half of a pen torch battery for L.T. The filament consumption of these tiny valves works out at about 25 mA. each, so the load on the pen-cell is not unduly great, although it is not advisable to allow the cell to run down too much, and it should be replaced after four to five hours' use

at the outside. Three or four pen-cells are the most convenient bias supply and last indefinitely, as they are not used to supply current. To conserve weight here it is possible to strip one of the B21 15-volt deaf-aid batteries and take out four sections, so giving a 6-volt battery. Contacts to the end faces may be made by wires held in place by rubber bands and then the whole assembly may be dipped in warm (not hot) wax and allowed to set, forming quite a serviceable unit.

### Operation

The receiver requires for its operation an R.F. signal modulated at between 300 and 15,000 c.p.s. from the transmitter. Each time the modulation is switched on the receiver relay closes; each time the modulation is switched off the relay opens, the carrier being left on the whole time. The opening and closing of the relay is then used to operate the intermediate mechanical equipment for moving the model's control surfaces and adjusting its engine, etc. The mechanisms employed in this connection are infinitely varied, and it is not the purpose of this article to discuss them.

This receiver as it stands is suitable only for the radio control band at 27 Mc/s, and not for the other permitted band at 465 Mc/s. These Hivac valves will not work at this high frequency, but there is another battery valve in surplus that can be persuaded to oscillate at 400-500 Mc/s—the American acorn type 958-A. This, however, requires a somewhat higher value of H.T.—60 volts. For model boats this higher value is of less importance as weight is of less consequence than in a plane, and a satisfactory unit can be built without much trouble by the experimenter interested in V.H.F. work. Such a unit will be described in a future article, also the transmitter equipment for both receivers and the mechanical control equipment.

The writer hopes that this short article will inspire those who have not previously considered radio control of models as a worthwhile subject for experiment to take up this fascinating work and construct a really lightweight, stable receiver having a long range. All mechanical equipment can be hand made, and there is endless variety and interest in the different designs that can be made to fit any specific model.

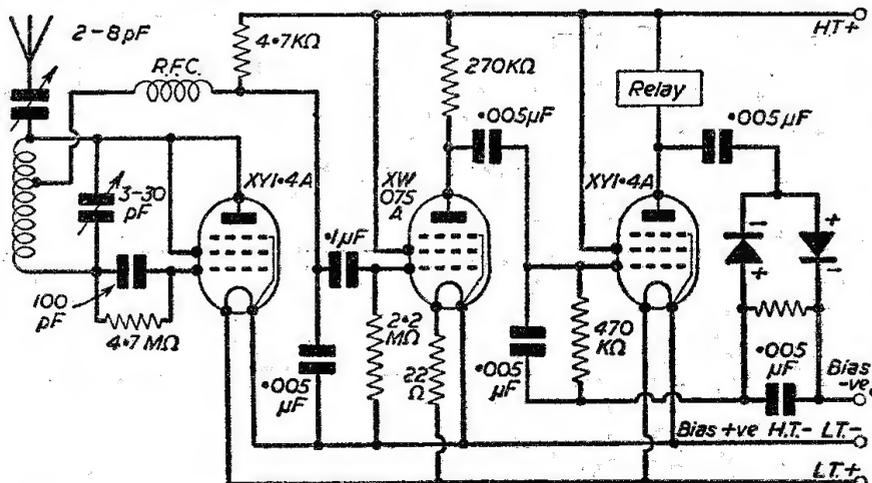


Fig. 3.—Three-valve receiver circuit with the tone-operated A.F. stage.

### NOW READY!

The Entirely New 12th Edition of  
The Famous Standard Work

## THE PRACTICAL WIRELESS ENCYCLOPEDIA

By F. J. CAMM

Considerably enlarged, amplified  
and entirely re-written and re-  
illustrated.

All the facts, figures, and constructional  
data of Radio and Television  
—Definitions, Terms, Units—Principles,  
Circuits, etc.

Over 300,000 copies sold

Price 21/- or 21/10 by post from :

GEORGE NEWNES LTD.,  
Tower House, Southampton  
Street, Strand, W.C.2

# On your Wavelength

by THERMION

## Jewel-tipped Gramophone Needles

A READER asks me whether I think that jewel-tipped gramophone needles cause less wear than steel ones. My own experience of them is that they do not. I have never believed in fancy gramophone needles, and, having conducted tests on most of those which have appeared on the market during the last 30 years, I can say that the normal gramophone needles give as good a service as any.

With motor cars there are those who think that a special lubricating oil, or a special make of sparking plug improves the performance. The results may be real or imaginary. With gramophone needles I am certain that they are imaginary.

Quite apart from the question of the expense of jewel-tipped needles, which is not inconsiderable, I have found that they scurf up the grooves worse than steel ones. If the claim is that sapphire needles last longer than steel ones I would be inclined to agree, but I think it is at the expense of the records on which they play. Everyone who has any knowledge of engineering knows that soft materials lap harder ones. It is the hardened shafts which wear most, not the white metal bushes in which they run. In fact, if you wished to lap a hardened steel bush a lead lap would be used.

I should like, therefore, to know how many manufacturers can claim that the process becomes inverted when a comparatively soft record is rotated against a jewelled needle point. Theoretically a steel needle can be made to a higher degree of accuracy than say a sapphire.

The sharpened steel point, however, can dig into the bottom of the groove whereas with the jewel it is claimed they are accurately ground to the correct theoretical angle and contact only the sides of the groove. I have played a particular record with which I am well acquainted with both types and have noted no audible difference in the quality of reproduction.

I have noted, however, in a destruction test I conducted a few years ago that the record on which the steel needle had been used lasted longer than a record of the same composition on which a sapphire had been used. Therefore, the relative merits of both types is concerned with cost, with the mild advantage in favour of the jewel that one does not have frequently to change the needle as with the steel one.

You may have noted that after two or three playings the steel point of a needle becomes blunt, which proves my statement that the soft material laps the harder. I do not know the relative Brinell Hardness Numbers of sapphire and steel, but the same lapping action must apply. Whether sapphires or other jewels give a more faithful reproduction is a matter for personal opinion, and mine is that it is largely a matter of imagination.

If the gramophone companies thought that sapphire needles gave a better reproduction, surely they would recommend them? There was a myth amongst gramophone fans a few years ago that

fibre needles gave better reproduction, just as in the early days of radio the ignorami thought that the reproduction from a crystal set on a pair of headphones was better than that of a valve set. The correct answer, of course, is that if the signal received on a crystal set were to be amplified to the same output wattage as the valve set, the quality would be indistinguishable. With fibre needles the output in decibels is much less than with a steel needle, because fibre is more flexible.

Therefore, it was thought that the lesser volume was necessarily of higher quality. Precisely the same effect could be obtained by reducing the volume on a radiogram; this is not possible on the ordinary acoustic gramophone.

There are still cranks who make learned dissertations on quality receivers, when they cannot possibly know what quality is, because you cannot listen in to the transmission and the reception at the same time. Fortunes have been made out of fancy needles. For myself I am content to use the needles recommended by the record manufacturers, and leave the high quality, less record wear, improved reproduction boloney to those who like to talk about it.

## Disc-less Recording

YOU will remember my comment on disc-less recording and my reference to the Ozaphone. One of my readers, Mr. D. G. Newman, of Chester, has sent me a catalogue of this machine entitled, "Music from a Beam of Light." The company had showrooms in Albemarle Street, Piccadilly. The catalogue states that the Cell-o-phone, which was the trade mark used by the Ozaphone Company, "Uses a beam of light instead of a needle—a ribbon instead of a disc. This fascinating new instrument enables you, for the first time, to enjoy continuous home entertainment of your own choosing. Six to 60 minutes of uninterrupted programme at the turn of a switch." The recordings available at the time included symphonies, opera, variety and dance, by well-known artists. The catalogue is very complete and interesting. It seems a great pity that the production of this instrument ceased, as with the many improvements in sound-on-film technique by now we should no longer be using steel needles, or jewelled ones.

## No R.S.G.B. List of Members

I WONDER why it is that the Radio Society of Great Britain does not issue to its members a list of its members? Every other society of which I am aware does this, for it enables members to write to one another, and to check up on addresses. Every member of a society is entitled to know who his fellow members are. If a society claims a membership of so many thousands they should be supplied in printed form. I suggest that the Council of the R.S.G.B. should include such a list in its printed rules.

# LINING LOUDSPEAKER CABINETS

A Useful Idea for Avoiding Cabinet Resonance

By B. D. SIMMONS

**R**EADING the article on loudspeaker cabinets in the April edition of PRACTICAL WIRELESS has prompted me to write about a recent discovery of mine which, although not claimed to be novel, does provide a very cheap and effective method of lining loudspeaker cabinets. It is primarily intended for use in acoustic chambers of the reflex or infinite baffle type having cabinet volumes of several cubic feet. The entire interior wooden surface of the cabinet is lined with a layer of papier mâché egg crates, as illustrated in the accompanying sketch.

Egg crates are very easily obtainable from any grocer and it was my experience to find that retailers were only too glad to dispose of them. It is difficult to give quantitative treatment on the effectiveness of this method. Owing to the widely different forms of cabinet shape and volume, which individual readers may possess, and to the varying stiffness of the egg crate material, no simple mathematical generalisation can be made. Thus, brief qualitative reasoning will be taken only.

Unlike the usual materials used, i.e., glass fibre, felt, etc., this lining is of a more solid texture but, due to certain physical properties it possesses, acoustic absorption and damping is obtained.

Here, as in most considerations of power transfer from source to load, a maximum amount of energy will be transferred when source impedance matches load impedance. In this particular case, total absorption by the cabinet lining of all energy radiated from the back of the speaker cone is the ideal condition. This means that the impedance of the lining material should match the impedance of the air delivering the energy to eliminate box resonance caused by the unabsorbed energy reaching the woodwork.

## Unlined Cabinet

Consider first an unlined cabinet. Here there is a

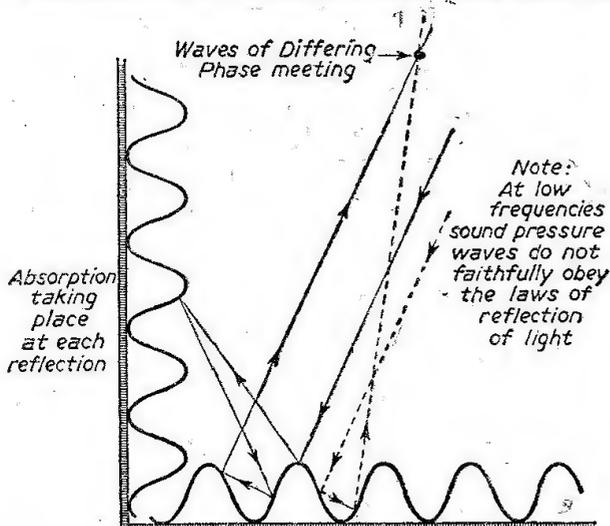


Fig. 2.—Part cross-section of lined cabinet showing possible paths of sound waves from loudspeaker.

large mismatch. Typical figures for the characteristic impedance of air are 41.5 C.G.S. units (acoustical ohms) per sq. cm. as opposed to that of wood which can have from  $1 \times 10^5$  to  $4 \times 10^5$  units, depending on its density. Now the higher the ratio of the two impedances between which energy is being transferred, the smaller will be the energy absorbed and consequently the greater will be the reflection. This will result in standing waves in the cabinet, one of the most likely causes of cabinet resonance.

Energy can also be dissipated by causing frictional losses. A rough, fibrous surface of large area over which the sound waves must travel will result in energy being lost in the form of heat over the surface. The effective area can be increased by making the material in the form of a series of small pockets and this also aids absorption by virtue of the fact that a wave reflected from the back of a pocket

must, on reflection, pass over the same surface which it originally did on entering. An extreme example of this is given by considering the anechoic chamber where numerous pocket-forming wedges of highly-absorbent material line the entire chamber.

An apparent way of removing unwanted energy is by phase cancellation. This can occur if any two or more reflected waves meeting at a point have an algebraic sum of zero (for complete cancellation) or whenever any degree of cancellation takes place there will be a corresponding reduction in energy. This phase difference will be caused by waves reaching a point via paths of different lengths. A highly-irregular surface will reflect waves at numerous angles and thus enable the "split up" in phase to be considerable. It must be appreciated that in a similar way certain build-ups of energy will take place thus the net effect is likely to result in no overall reduction, although at each reflection absorption will take place.

Absorption also varies with frequency. This unfortunately means that whatever material we use to line the cabinet, there will be less attenuation of the lower frequencies (the troublesome ones in this case) than of the higher.

## Advantages

It is now possible to enumerate the advantages to be gained by using papier-mâché egg crates:

- (1) The fibrous, porous material gives good

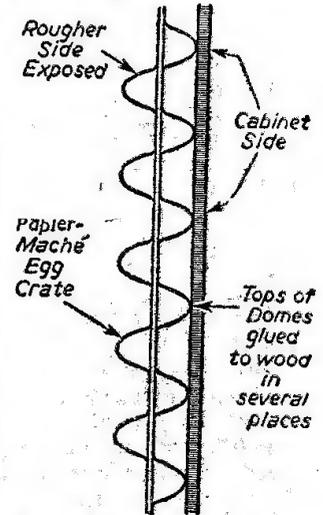


Fig. 1.—Method of fixing lining.

impedance matching and therefore good absorption.

(2) The large, rough surface area with numerous pockets causes frictional losses which dissipate unwanted energy.

(3) The highly irregular surface causes much random reflection.

The overall effect is a considerable improvement

in cabinet performance with negligible expense and trouble.

It must be noted that primarily a speaker with large piston displacement must have the fundamental cone resonance damped by low amplifier output impedance and suitable cabinet design to gain full advantage of this method of reducing unwanted cabinet resonances.

## Surplus Neon Voltage Stabilisers

Details of Cold Cathode Discharge Tubes, or Regulators

By E. G. BULLEY

**V**ALVES of this nature are sometimes known as cold cathode glow discharge tubes, voltage regulators or voltage stabilisers. These should not be confused with valve voltage regulators, as they usually comprise a high vacuum or gas-filled triode incorporated in a suitable circuit, and the valve being capable of passing fairly large anode current.

The cold cathode types, however, consist of two or more electrodes assembled on to a glass stem which in turn is sealed into a glass envelope. The finished product being gas-filled with neon to specified pressure.

It can therefore be stated that when a voltage is applied between the electrodes, ionisation of the gas occurs, that is to say, such valves give a constant voltage drop over a wide range of current. This can be explained by the fact that owing to the applied potential to the electrodes, the electrons present in the gas collide with the gas molecules and cause the release of ions which in turn collect and form a positively charged cloud near to the cathode electrode. Now it is this positively charged cloud and its ability to carry large currents that causes more electrons to be released from the cathode. This phenomena acts very quickly and furthermore, as the conduction property of the gas increases between the electrodes, so the current flow increases. It will therefore be appreciated that the gap between the electrodes of such valves is an important parameter of their design.

However, there are quite a selection of these stabilisers on the surplus market and use can be made of them by the radio amateur where stabilised voltages are required.

### Equivalents

Many of these valves have commercial equivalents and perhaps the most well-known type is the "Stabilovolt" (trade mark of M.O.V.). This type of regulator is composed of several electrodes sealed into the same envelope, thus enabling various values of stabilised voltages to be taken from the one valve.

It is as well to mention, however, that an external resistance must always be connected in series with the stabiliser, and must be capable of carrying the maximum input current continuously. Likewise, the resistor should be able to absorb approximately half the voltage of the valve in question, thus preventing a heavy current density through the valve. It is therefore essential that the filtered

D.C. supply to the valve must be approximately 50 per cent. higher than the actual working voltage of the regulator. Such valves of this nature that are at present available from surplus are shown in Table I, with their commercial equivalents. Before proceeding to deal with other types, there is an important point to remember; that is, when using such regulators as just described, one must ensure that a suitable resistor is incorporated in the supply line of each electrode. The presence of these resistors enables the regulator to be struck at a much lower voltage than if each electrode was struck in turn.

There are, of course, various types of American regulators available as will be seen on page 302; these are of a different design from the multi-electrode type and contain two electrodes. Nevertheless, a resistance must also be used in series with these types to limit the current through the regulator.

### Circuits

Typical circuits using such types are shown in Figs. 1 and 2, the former being a straightforward stabiliser circuit, whereas the latter shows two such valves in cascade. By this method, two values of stabilised voltages can be obtained, which is more or less what the "Stabilovolt" does, the difference being that the latter has all the electrodes in one envelope, whereas the former utilises two or more valves to get the same result.

It is as well to mention at this stage, however, that if these surplus stabilisers have at some time or other been used, the regulating characteristic

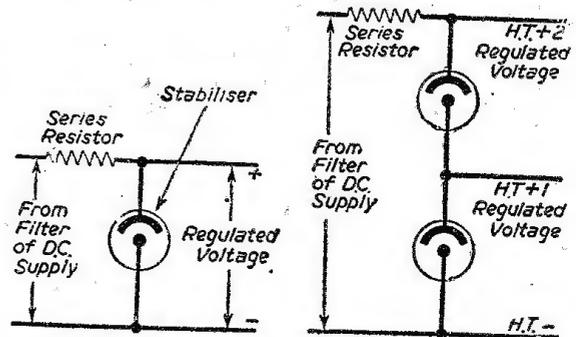


Fig. 1.—Circuit of straightforward stabiliser circuit.

Fig. 2.—Stabilising circuit using two valves in cascade.

may have changed, or on the other hand, a long idle period may also have affected their characteristics. One is therefore advised to give these valves a suitable ageing before incorporating them for good in their particular piece of equipment.

The ageing of such valves is quite simple, and is the operation of the valve in question at the

#### SURPLUS NEON STABILISERS

Surplus No.	Comm. Equiv.	
CV45	S130P	British
CV188	ST11	British
CV216	OD3/VR150	American
CV643	874	American
CV686	OC3/VR105	American
CV3712	STV280/80A	British
CV3798	OA3/VR75	American
CV3799	OB3/VR90	American

ratings one wants and should continue until the regulator develops a steady condition; one must also remember to operate the valve at or within its ratings and not overload it.

#### Safety Device

Many of these stabilisers, and especially the American types, have what is known as a "jumper" incorporated in them. This, in fact, is a connection within the actual base of the valve between two pins and thereby acts as a switch, the connection forms a part of the A.C. supply line, so that should the valve be removed from the equipment whilst operating, the A.C. supplies to the transformer are

broken and the equipment made inoperative and thereby safeguarded. Reference to Fig. 3 will, it is hoped, assist the reader and clarify this point of discussion.

To conclude this article, one must bear in mind

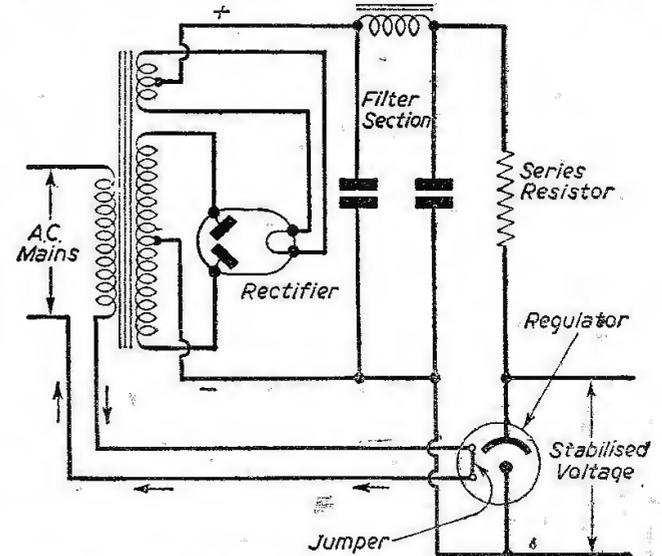


Fig. 3.—Circuit of a mains unit showing "jumper" connection.

that voltage regulators must not on any account be operated without a series resistor, otherwise a direct short will occur through the regulator which will in turn cause damage to the power unit.

## New Transmitter Technique

A NEW type of high-power air-cooled broadcasting transmitter is announced by Marconi's Wireless Telegraph Co., Ltd. It embodies the perfection of a technique, known as "Ampliphase," which is a great advance in transmitter design. "Ampliphase" allows higher power medium-frequency installations to be completely air cooled, greatly reduces size-to-power ratio and effects a considerable saving in capital outlay.

One of the greatest advantages of this technique is that by eliminating the modulation transformer and reactor, the use of iron and other valuable material is reduced by approximately eight tons for a 100 kW. transmitter.

#### Testing Period

For the past 12 months a Marconi 60 kW. experimental "Ampliphase" transmitter has been on trial in the service of the British Broadcasting Corporation, carrying the Third Programme.

"Ampliphase" minimises valve stages and other equipment and is a technique which combines extreme reliability with greater freedom from technical faults. Basically "Ampliphase" gives a normal audio-modulated carrier by internal phase modulation in the transmitter. Since the phase modulation is effected at a low power level, the audio-frequency stages are of low output and contain very few stages of amplification. The radio-

frequency stages deal only with phase modulated energy and they work at a high efficiency at all levels of modulation. The result is a high-power transmitter of great simplicity, electrical efficiency and reliability.

#### Reliability

Performance figures obtained during the B.B.C. trial period vividly illustrate these claims. Out of a total programme time of 2,012 hours, only 12.5 minutes were lost due to breakdown of the transmitter itself, or .01 per cent. on a purely experimental development model.

Operation and maintenance of "Ampliphase" transmitters is simple and parallel working, or unattended working, is entirely practicable.

### BUILDING THE "PRACTICAL WIRELESS" TELEVISION RECEIVER

A large number of readers unable to obtain back numbers of the issues containing the series of articles on the construction of the "Practical Wireless" television receiver, have asked us to reprint these articles in book form. This has now been done, and copies may be obtained from or through any newsagent, or for 3s. 9d. by post from us.

Orders should be addressed to The Publisher, Book Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Printed on good quality paper, this 32-page book gives complete stage-by-stage instructions for the construction of this highly efficient 18-valve television receiver, which received so many favourable comments when it was exhibited on our stand at the recent Radio Show at Birmingham.

In order to secure a copy of this limited edition readers should place their orders without delay.

# Facts About Mains Transformers

Choosing and Testing New and Surplus Components

By BERNARD BARNARD

**I**N the days before the war the purchase of second-hand apparatus was usually a fairly safe business because almost every component bore the maker's label, and it was only necessary to look up that manufacturer's specification to see if the item in question was fit for some particular job.

To-day, however, it is all very different. Most of us are always on the look out for a bargain, and, of course, we do not have to look very far, for the market is still flooded with very excellent ex-Government apparatus. The only snag is that we have to find some way of deciding, often merely by the appearance of a component, whether it is suitable for our requirements.

Apart from obvious external defects, there is only one way in which we can hope to do this and that is by having a fairly complete knowledge of the fundamental principles on which the component in question operates.

Let us suppose, then, that we have been offered a mains transformer at a very tempting price and that we have to make up our minds on the spot whether to buy it or let it go. We therefore consider the problem in the light of basic principles of transformer action and our line of thought will run something like this.

The shape, size, weight—in fact everything about a mains transformer—depends finally upon the basic principle that a wire carrying an alternating current has around it a magnetic field which also alternates in strength and direction and that any other conductor which is close enough to be affected by this magnetic field will have an alternating voltage induced in it.

The frequency of this induced voltage will, of course, be the same as the original one but its magnitude depends on a number of factors, some fixed and some controllable.

The magnetic field is conveniently considered as consisting of "lines of force" in the form of concentric circles around the first wire and we may think of them as expanding and contracting around the wire as the applied voltage rises and falls.

The magnitude of the induced voltage in the second wire depends on the rate at which the lines of force cut the second wire. And from this it follows that this voltage depends on frequency, strength of the field and the length of the second wire that is influenced by the field.


In our mains transformer the frequency is, of course, fixed at 50 cycles per second but the strength of field is determined by the number of primary turns (analogous to the first wire) and the design and size of the iron core. The "length of the second wire" becomes, of course, the number of turns on the secondary winding.

We cannot find out very much about the windings of a transformer by simple inspection beyond the obvious conclusions to be drawn from the bulk of the component. But quite a lot can be deduced from the size and construction of the iron core.
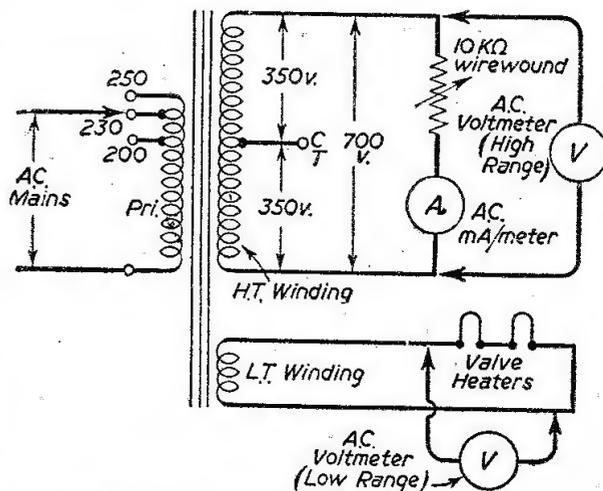
## The Core

The purpose of the core is to confine the magnetic field set up by the primary to the narrow path offered by the soft iron and so to ensure that all the lines of force do useful work in cutting secondary turns. Without this iron path, we should have to have an enormous number of secondary turns to get a given induced voltage because most of the magnetic field would be lost in the space surrounding the transformer. A good transformer will have, then, a very generous iron core which will pass through the centre of the windings and will loop round to form a complete ring around the outside of the transformer.

Another point about the core is that it should be made up of laminations, that is, thin strips of E- or L-section which are insulated one from the other by paper or varnish, and bolted together. This is very necessary to avoid the very heavy power loss which would otherwise occur due to eddy currents. The principle of induced voltages applies to the iron as well as the copper of the secondary winding and voltages are in fact induced in the iron. These would cause strong currents to flow



Circuit of a typical Mains Transformer and method of testing.

were it not for the high resistance path set up by the layers of insulation between the iron laminations.

There are on the market to-day very many ex-Government "high-cycle" transformers which are quite unsuitable for mains use. They were designed for use at a frequency of approximately 500 and therefore produced the required secondary voltages with comparatively few turns and a small iron core, the high frequency being depended upon to give the necessary "rate of cutting lines of force." These are easily recognised by their small bulk and scanty iron core and will be avoided by the discerning purchaser.

## Testing

Now, to get a little further in our study of the behaviour of the transformer, let us assume that we have one on the bench for test. First of all we will connect the primary to 50 cycle A.C. mains of the correct voltage and, with no connections whatever to the secondary, we will note what is going on inside the windings.

When we switch on the supply, a good transformer will pass a very small primary current—and that is all. This current is merely doing the job of maintaining the magnetic field and, if the losses in this transformer are small, practically no power will be drawn from the mains. In point of fact, no power at all is used in establishing a magnetic field and therefore any that is taken from the mains must be due to losses, such as the resistance of the windings and eddy currents in the core. A first-class transformer will have its windings of fairly generous gauge copper wire in order to keep the resistance down, and the core will also be generous in size and carefully laminated.

The "no load" primary current is small because the primary winding has a large inductive reactance; that is to say, it offers a very large opposition to the flow of alternating current; the better the transformer, the smaller this current will be because the good component will have a very large number of primary turns, and, therefore, a very large primary inductance.

Now we will see what happens when we connect a load across the secondary. This can be a resistance, an inductance or a capacitance—or a mixture of all three. In our work it is nearly always a resistance, so we will look at this case in some detail and merely mention the others for the sake of information.

As soon as we connect a resistance across the secondary, a current will flow in the secondary circuit whose magnitude will be found by dividing the total resistance of the circuit into the induced secondary voltage. This current will cause a magnetic field to be set up around the secondary windings which will interact with the primary field; this field is in opposition to the primary field and will, therefore, reduce the total magnetism in the core. As a result, the primary now has less magnetism and its inductive reactance falls—and, of course, the primary current rises.

The effect, then, of loading the secondary is to increase the primary current and the transformer now draws power from the mains. Ignoring losses again, the power consumed in the secondary circuit will be exactly equal to the power drawn from the mains by the primary.

But we cannot ignore losses when testing our transformer. If the secondary winding has been wound with too fine a gauge of wire, or wire of poor quality, then it will have an unnecessarily high resistance and we shall lose a lot of watts in this winding. The transformer will get hot when in use and will be very inefficient. The windings will also probably break down after a time due to this heat causing excessive temperature rise.

As a matter of interest—and a point which throws further light on transformer action—we will see what happens if either an inductance or a condenser are connected to the secondary.

In the first case, a secondary current is established but no power is used. This is because the current

will lag on the voltage by 90 deg., as is always the case when A.C. is applied to a pure inductance. The effect in the primary will be exactly the same, that is a large lagging current will flow but, due to the 90 deg. lag, the power consumed ( $V \times I \times \cosine 90^\circ$ ) will be zero.

The effect with a pure capacitance would be similar except that, in this case, the phase angle would be 90 deg. lead.

We can now complete our investigations by assuming that the seller of the transformer has been kind-hearted and allowed us to take the component home to test before we make our final decision. In the light of the foregoing we can very easily carry out exhaustive tests which will decide whether the instrument is suitable for any particular purpose.

The only test gear necessary is a voltmeter and ammeter which will read A.C. These can be combined in the one instrument for we shall not require both readings at the same time.

## Practical Work

Connect the transformer up as shown on page 303. We will assume that the rated secondary voltage is 350-0-350 and that we require this voltage to be maintained at 100 milliamps. Start by connecting the A.C. milliammeter in series with the variable wire-wound resistance and adjust the resistance until the meter reads 100 mA. Now take the meter out of circuit, switch it to the appropriate volts range and connect it across the secondary terminals. It should read approximately 700 volts. Leave the transformer connected in this way, with the supply on, for at least an hour. At the end of this time if the transformer is up to the job, the voltmeter reading will not have altered and the transformer itself should not have become appreciably warm. If it is hot to the touch or if the voltmeter reading has fallen then the component should be rejected.

It is also worth while to connect the A.C. milliamps range into the primary circuit and to note the primary current. It should be greater than the secondary—somewhere about  $1\frac{1}{2}$  times—and the primary watts (mains volts  $\times$  primary current), will be similarly greater than the secondary watts (secondary watts  $\times$  secondary current). The lost watts are, of course, accounted for by the fact that the best of transformers are considerably less than 100 per cent. efficient and the resistance of the windings and other sources of loss that we have noted have added their quota to the total power drawn from the supply.

Although the L.T. windings seldom cause trouble, the test can be extended to include these if desired. The heaters of some spare valves of suitable voltage rating form the most convenient load and the number chosen should be that which it is proposed to use when the transformer is put into service. A voltage test is made under load.

One further useful and informative test can be made after the above has been completed. This is to use the voltmeter to check that the voltage either side of the centre tap is really 350. In some cases you may find that you will get as much as 370 volts one side and only 330 on the other. Such a transformer should be rejected as the unbalanced voltage will play havoc with reservoir condensers in a full-wave rectifying circuit.

# A CHASSIS PUNCH

A Useful Tool for Metal Chassis Constructional Work

By V. MANNOOCH

WHEN drilling radio chassis for the insertion of screens, as in the P.W. vision receiver, one often finds that the drill wanders or tears the metal, producing a ragged hole which is difficult to clean up. The gadget described here is simple to make and proves very effective in making holes which are clean, in perfect alignment and quickly produced. Holes up to  $\frac{1}{2}$ in. diameter in 16-gauge aluminium have been successfully produced using this method.

The gadget consists of two plates which are drilled in conjunction with one another, bolted together, and spaced apart by washers on the bolts. Short lengths of silver steel rod, which may be obtained from most ironmongers, are used for the punches. These are sawn off to a convenient length and faced off square with a file. It is not necessary to harden the punches or punchplate unless a large number of holes are to be produced.


The distance from the punch to the nearest assembly bolt should be sufficient to allow holes to be punched in the centre of the chassis, and the distance between assembly bolts should not be less than about 3in. to 4in.

Holes in the punchplate should be opened out on the underside to allow clearance for the blanked-out piece to fall away, by drilling half way through its thickness with a drill  $\frac{1}{32}$ in. larger than the punch hole. Drilled holes are quite suitable and it is not essential to ream.

Holes can be arranged in any combination, such as  $\frac{1}{8}$ in.— $\frac{5}{16}$ in.— $\frac{1}{2}$ in. for TV coil formers, and

the holes then punched in the correct relation to one another.

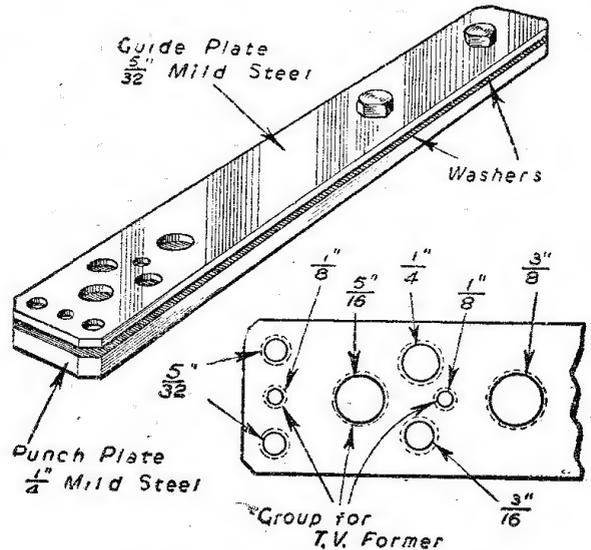When using this device the punchplate should be well supported in line with the punch on a good



Details of construction of the punch.

solid piece of metal arranged to project sideways from the vice.

There should be no difficulty in producing good clean holes, and one or two good blows with a hammer on the punch should be sufficient for any size hole.

## R.S.G.B. CALL BOOK


THE Council of the Radio Society of Great Britain has decided to publish, towards the end of this year, an "R.S.G.B. Call Book," containing the call signs, names and addresses of licensed amateurs in Great Britain, Northern Ireland, Isle of Man, and the Channel Islands.

Any licensed amateur who wishes his call to appear in the first edition is asked to write his full call sign, name and address on a postcard and send it to:

Mr. J. P. P. Tyndall, 174, The Drive, Ilford, Essex.

Postcards cannot be acknowledged, but for changes of address to appear in subsequent editions notification of receipt will be sent. Non-members of the R.S.G.B. are asked to send changes of address direct to Mr. Tyndall on a prepaid postcard.

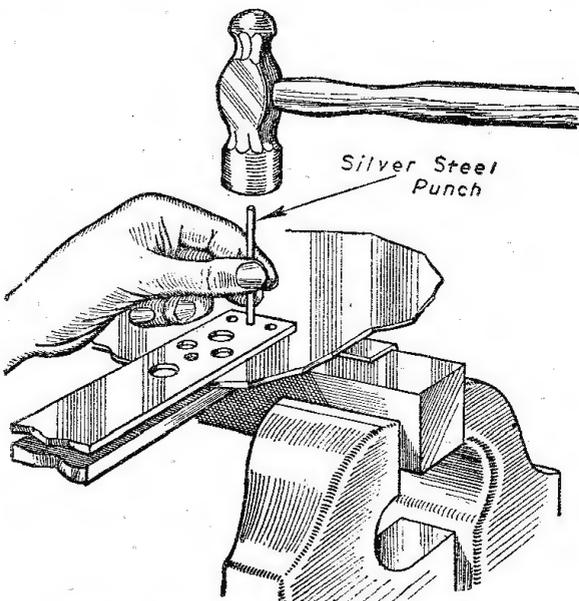An announcement with regard to details of the publication of the first edition will be published in these pages in due course.



How the punch is used on the chassis.

# Using Multiple Valves

Hints on Modernising Old Receivers and Building New Experimental Circuits

By W. J. DELANEY (G2FMY)

**T**HERE is a wide range of multiple valves now available in both surplus and new ranges, and in view of the increased purchase tax any scheme designed to save valves is obviously worth while. Generally, valve economy means cutting down the efficiency of a circuit, but by making use of a valve of the type which contains two or more assemblies in a single glass envelope it is possible to use a single valve unit for two or more stages without loss of efficiency—indeed, in some cases it may even be possible by doing this to improve the performance.

The types of valve referred to are generally those of the frequency-changing type (except those which have both sections internally inter-connected), single and double diode, triodes, and double triodes.

## Double Triodes

Dealing with the latter class first, it will be seen that these may be used in re-designing or "hotting up" an old receiver or in building a new one. In the case of an old set it may be found that, say, the detector or L.F. valve is in need of replacement. If a modern double triode is purchased instead of the necessary single triode, the wiring may be modified so that the replaced valve and the next stage are both incorporated in the single valve and thus a spare triode is provided, should it be needed for replacement. The receiver may consist, for instance, of H.F., detector, L.F. and output stage. The detector or L.F. may have gone, and the two stages are, therefore, incorporated in the single stage so that a double triode may be used to supply both stages. In building a new receiver of this type the same idea would, of course, be used, and it may be found that the shorter inter-stage wiring which results by using one valveholder for the two stages will enable a more stable circuit to be built.

## Amplifiers

In the case of amplifiers, either P.A. or domestic, the double triode may also be found extremely useful. The popular Williamson amplifier, for instance, may be built with one double-triode fulfilling the function of the two separate input stages, whilst another similar valve may be used for the first push-pull stage, thus reducing the actual number of valves in that amplifier to only four instead of six. This also enables a smaller chassis to be employed, cuts down wiring difficulties, and often produces better stability. There is, of course, the drawback that if one section should fail a replacement for two stages has to be obtained, but over the long run there is an obvious economy in using the double valve.

## Frequency Changers

Some valves of this type consist of a triode and a

pentode not internally connected, and it is possible to use one of these valves for an H.F. stage, followed by a rectifier, but care must be taken that the valve is not of a type wherein provision has been made for intermixing the electron stream. Such a valve would, of course, lead to all kinds of trouble if an attempt were made to use it for two separate stages, such as H.F. and detector. An experimental amplifier has been built, using the pentode section as an input stage, with the triode functioning as phase inverter, and an efficient tone control circuit may be included with the pentode valve without losing too much amplification.

## Diode-triodes, etc.


The diode-triode is, of course, a typical example of a multi-valve used for separate functions, as it is usually employed with a diode as rectifier, followed by the triode section as L.F. amplifier, and if two diodes are included in the valve the second diode is generally used for providing A.V.C. voltages. It is not, of course, essential to use this type of valve in a superhet, and the keen experimenter might like to try the effect of using a double-diode-triode with the two diodes operating as a full-wave rectifier in a straight receiver. In the American range of valves there may sometimes be found a type in which a pentode is combined with a diode, the latter being designed to withstand mains voltages and it is sometimes incorporated in A.C./D.C. receivers, providing the necessary half-wave rectification of the mains supply on A.C. As a point of interest, in an A.C./D.C. receiver which has been built round one of these valves used in this manner, and the valve has failed, if a replacement cannot be obtained the circuit should be modified so that a metal rectifier replaces the diode section of the valve.

## Class B and Q.P.P.

Some readers may have an old receiver lying idle in which a Class B or a Q.P.P. valve is employed. These valves were double triodes and double pentodes, and if the valves require replacement separate valves may be used if it is not desired to change the circuit, but if the receiver is being re-designed, and the valves are in good order, then they may be used as separate stages in the manner just described, ignoring the Class B or the Q.P.P. feature. The only difficulty which might arise here is in the use of the two pentode sections of the Q.P.P. valve. It will generally be found that if these are used for two separate L.F. stages the output from the first will be too much to be handled by the second, and therefore there should be a reliable volume control between the two sections to take care of powerful signals. The high gain may be useful for weak signals.
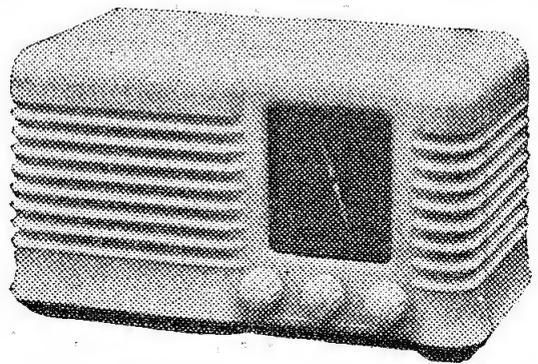
# Build a professional-looking Radio at less than half today's price

The Kits are housed in attractive Bakelite Cases, size 12in. x 5in. x 6in. Each Kit is complete in every detail, nothing has to be made or improvised. Easy to follow, point-to-point diagrams are supplied, making construction very simple. They are for use on 200-250 volt mains, and both A.C. and Universal Models can be supplied. The Dials are illuminated, and the receivers present an attractive appearance. We regret the necessity for the increase of prices due to continually rising costs and increased P.T.



## TRF

Valve line up : EF22 H.F. Pentode ; VR116 Detector ; CV1510 Beam Power Output in the A.C. Model. The A.C./D.C. Output Valve is 12A6. Both use Metal Rectifiers. Waveband coverage is for the Medium and Long bands. Price £5/19/6 (carriage and packing 2/6). With Walnut or Ivory Cabinet.

## SUPERHET

Valve line up : 6K8, 6K7, 6Q7, and CV1510 Beam Power Output in the A.C. Model. The A.C./D.C. Output Valve is 12A6. Both use Metal Rectifiers. Waveband coverage is 16-50, 190-540 and 1,000-2,000 m. Price £7/19/6 (carriage and packing 2/6). With Walnut or Ivory Cabinet.

Circuit diagrams only can be supplied at 1/6 each. Cabinets only available at 17/6.

# PREMIER RADIO CO

MORRIS & CO. (RADIO) LTD.

Callers to : 152/3, Fleet Street, E.C.4. CENTRAL 2833

207, Edgware Road, W.2. AMBASSADOR 4033

(This branch is open until 6 p.m. on Saturdays.)

Due to the large number of orders in hand, coupled with supply difficulties, we are reluctantly compelled to temporarily close our Postal Service.  
 No post orders can be accepted after June 14th until further notice.  
 Our Technical advice and service departments remain in operation. Resumption of Postal Service will be announced in these columns.

## SUCCESS?

Never before has such a vast field of opportunity been open to the technically minded. Because we can call on the unique experience of the great E.M.I. Group ("H.M.V.", Marconiphone, etc.), our courses are based on the needs of modern industry. Let us help you to take advantage of the great demand for technicians in Radio, Television and all branches of Engineering. Take the first step NOW!

START  
HERE

**--- FILL IN FOR FREE BROCHURE ---**

Mark the subject(s) which interest you, and post (without obligation) :—

E.M.I. INSTITUTES, Dept. 32, 10, Pembridge Sq., London, W.2

Radio       Aeronautical Eng.     Production Eng.  
 Television     Draughtsmanship     Matric  
 Electrical Eng.     Mechanical Eng.     Civil Service  
 Other Subjects.....

NAME .....

ADDRESS .....

.....(BLOCK CAPITALS)

E.M.I. INSTITUTES—The only Postal College which is part of a great Industry.

G2AK

### This Month's Bargains

G2AK

**RECEIVERS TYPE 18.**—Cover 6-9 mcls and are for battery operation. Good condition, 17/6. Packing and postage 1/-.

**OSMOR Coil Packs** for conversion of above complete with frame aerial, 54/2. All types of OSMOR packs available. Ex stock.

**MIDGET SPEAKERS.**—Philips 2½in., 12/11. Goodman and W.B. 2½in., 16/6. J. and P. 3½in., 13/11. Elac 6in., 17/6.

**WEYMOUTH MIDGET I.F.'s** 465 kc/s. Type P4J and P4K, 15/- pair. Kit of 4 Midget 1.4 v. valves 1R5, 1T4, 1S5 and 1S4, 30/- New and Boxed.

**MIDGET OUTPUT TRANS.** for Personal Portables, 6/- each. Balanced armature L.R., 'Phones, 6/6 pair.

**XTAL DIODES**, 3/9 each, or 4 for 14/-. Germanium diodes, 5/6 each.

**AR88D SPARE CRYSTALS.** 455 kc/s, 15/- each.

**AR88 MATCHING SPEAKERS.** Black crackle cases. 2.5 ohms. Price 75/-.

**POTENTIOMETERS.**—5 watt wire-wound .20 k., 25 k., 2/-, 500 ohm and 2,000 ohm 50 watt wire-wound, 3/6 each. Carbon Type Potentiometers, .50 k., 100 k., 1 meg., 2 meg., 1/6.

**TWIN FEEDER.** 300 ohm Heavy Twin Ribbon Feeder, 5d. per yd. Standard K25 300 ohm Twin Ribbon Feeder, 9d. per yd. Co-ax Cable, ½in. dia. 70 ohm, 8d. per yd., ¼in. dia., 1/3 per yd. Post on above feeder and cable 1/6 any length.

Postage free on all orders over £1 except where specifically stated.

Please print your name and address.

**CHAS. H. YOUNG, G2AK**

All Callers to 110 Dale End, Birmingham  
CENTRAL 1635

Mail Orders to 102 Holloway Head, Birmingham  
MIDLAND 3254

**Hitch your AERIAL to a STAR!**




**Skyway "Seven" RADIOGRAM CHASSIS**

3-wave Sheet 16-2000m. Push-pull 6V6s. Separate POWER PACK for easy fitting.

Basic Parts cost less than (excluding Valves) **£5**

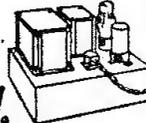Full home constructor design in **FOUR EASY STAGES** 1/6 post free.



**Frith RADIOCRAFT Ltd.** PHONE 58927  
69-71 CHURCH GATE-LEICESTER

**FROM COAST TO COAST : BY RETURN OF POST**

**"RADIO UNLIMITED"**

ELM ROAD, LONDON, E.17. Tel.: KEY 4813

**AMPLION CONTROLS.**—10, 25, 50, 100, K. ohms. 1, 1, 1 and 2 Meg all long in. spindle. Less sw., 4/-; SP/sw., 5/9; DP/sw., 6/6 each.

6V6G, 10/-; 6J5G, 5/-; 12A6, 7/6; 6H6, 3/11; 6K7C, 6/9; 6J7G, 7/6; 6L6G, 10/6; 6N7GT, 7/6; 6F6G, 9/-; SP61, 9/6; SP41, 8/6; 6B8G, 7/6; 6K6GT, 7/6; VR65, 5/-; VR65A, 5/-; 6X5G, 7/6; EF39, 7/6; EF36, 6/6; EK32, 6/6; EBC38, 8/6; EL32, 7/6; 5Z4M, 8/6; 5U4G, 9/6; EF50, 6/9; 1C5GT, 9/-; VR92, 4/6; 9D2, 4/6; KT2, 6/6; 1S4, 7/6; 1R5, 9/-; 1T4, 9/-; 3S4, 10/6; 1S5, 10/6; 6SJ7, 8/-; 25L6, 10/-; QP21, 5/6.

**P.M. Speakers. All Less Transformer.**  
2in., 13/-; 3in., 11/6; 3 1/2in., 14/-; 5in., 14/6; 6in., 14/11; 8in., 16/9; 10in., 25/-; 12in., 66/-; 5in. with T., 17/6.

Standard Size Volume Controls. Leading Manufacturers. Less Switch, 3/- each. S.Pole Switch, 4/9 each.  
Prices are still rising—BUY NOW!!!!!! Valve and components list available—Stamp.

**Experimenters! Build the MATCHBOX RADIO SET**

With the aid of our full instructions you can build a complete radio set in a matchbox, using parts purchased from your radio dealer.

Tuning arrangements include a medium-wave inductor with station selector switch, and a long-wave coil for the B.B.C. Light Programme on 1,500 metres.

Demodulation is achieved by the use of a non-linear impedance unit of a new type, giving loud, clear reception.

This receiver works off a short indoor aerial in many districts, and being powered entirely by the incoming signal requires no batteries.

Full step-by-step instructions, working drawings, and theoretical wiring diagram.

PRICE 3/-. POST FREE.

**JOHN O'BEIRNE (W),**  
137, COTHAM BROW, BRISTOL, 6.  
MAIL ORDER ONLY.

**"ADCOLA" SOLDERING INSTRUMENTS**

Regd. Trade Mark



Regd. Design No. 800302  
(British, U.S. and Foreign Patents)

**For Wireless and Television Assembly**

The advanced design of the Adcola Instruments meets the modern requirements of **Television, Telecommunication and Radar Engineers.**

SUPPLIED FOR ALL VOLT RANGES FROM 617v. to 230/250v.

3/16in. dia. Bit. Standard Model ...	22/6
1/2in. dia. Bit. Standard Model ...	25/-
3/16in. dia. Detachable Bit. Model ...	30/-

Sole Manufacturers:

**ADCOLA PRODUCTS LIMITED**

GENERAL OFFICES & WORKS: CRANMER COURT, CLAPHAM HIGH STREET, LONDON, S.W.4. (MACaulay 4272)

STUDY AT HOME

IN YOUR SPARE TIME

**THE BENNETT COLLEGE**

*will set you on the right course for success*

You make sure of planned progress in the career of your choice when you let the most progressive, most successful Correspondence College in the world coach you through the post. By friendly, individual training we equip you with the specialised knowledge you must have for a well-paid key position. Make the first move TO-DAY—post the coupon below.

**ALL TEXT BOOKS ARE FREE!**

to students of The Bennett College. We send as many volumes as the subject demands, and they become your personal property.



**IS YOUR CAREER HERE ? IF NOT, WRITE FOR FREE ADVICE**

Accountancy Exams.	General Cert. of Educational Exams.
Blue Prints	Languages
Book-keeping	Mining
Chemistry	Secretarial Exams.
Civil Service	Shorthand (Pitman)
Commercial Art	Wireless
Draughtsmanship	Works Managers
Engineering	

To Dept. 104, THE BENNETT COLLEGE LTD., SHEFFIELD.

Please send me (free of charge) Particulars of .....

Your private advice about ..... PLEASE WRITE IN BLOCK LETTERS

Name .....

Address .....

Age if under 21.....

Cross out line which does not apply

**SPARKS' DATA SHEETS**

Recognised as the Safest, the Simplest and the finest Radio Constructional Sheets: All my Designs are Tested and FULLY GUARANTEED.

**THE POCKET PAK.** The finest little self-contained Pocket Portable one-valver obtainable. Med. waves. Good phone sigs. Most widely used and always praised. All-dry Batteries. 3-

**THE CRUISER.** A three-valve T.R.F. High-gain Set. Specially designed for use with a short aerial. Ideal for Caravans, Camping, Yachts, etc. M/L waves. All-dry! Batteries. 3-

**THE "UNIVERSAL FOUR."** A 3-valve plus Rect. M.L wave T.R.F. Circuit giving 4 watts output. A.C./D.C. operation. 3-

**THE "CUB."** A.C./D.C. 2-valve plus Rect. Power and Quality on the "local" stations. A fine little set on M/L waves 3-

**THE CORVETTE.** A compact all-wave Superhet. Good results anywhere with "hook-up" aerial, or a good Portable with self-contained aerial. Chassis 5 1/2 x 4 1/2 x 2in. All-dry Batteries. 3-

The above are only a few of my designs.  
SEND STAMP FOR COMPLETE LIST.  
COMPONENTS SUPPLIED.

**L. ORMOND SPARKS (M)**  
48A, HIGH STREET, SWANAGE, DORSET

**TR TELEVISION**

TELEVISION RECEIVERS  
SCANNING AND FOCUS COILS  
P.M. FOCUS UNITS  
5/10 kv. R.F., E.H.T. UNITS  
E.H.T. and OUTPUT TRANSFORMERS

Technical Publications post free.

**"TELEVISION CIRCUITS"**  
Second Edition, post free 1/6

**HAYNES RADIO Ltd.,** Queensway, Enfield, Middlesex.

# "Modern" Radiogram Control Amplifier

An Extra Unit for This Popular Receiver or any Similar Circuit

By R. HINDLE

**M**ANY who build the "Modern" or similar amplifier will wish to use it with a tuner chassis already available. They will require a subsidiary audio-control chassis giving gain and tone controls operative on either radio or gram input and, if the recommendation to avoid all controls on the main amplifier as was done in the case of the "Modern" amplifier is followed, mains

the output coaxial lead to the point previously connected to the volume control. The controls on the tuner will then be tune, wavechange and on/off switch, and a volume control without switch will be used on the control amplifier in place of the one specified in the list of parts. An additional power socket to supply the heater and H.T. voltage to the control amplifier will have to be provided

either on the main amplifier or the tuner; only a three-way socket and cable is needed if switching is carried out on the tuner.

The circuit used is similar to the audio amplifier circuit of the original tuner and is given in Fig. 1. The same wide-range treble and bass controls are provided. This circuit does not give sufficient gain for the very low output pick-ups that some quality enthusiasts use, but is adequate for the more normal variety of modern pick-ups giving upward of .05 volt and is suitable for crystal as well as the armature type. Any input filter recommended by the particular pick-up manufacturer (as in the case of some crystal pick-ups) should be incorporated in the chassis between the gramophone input socket

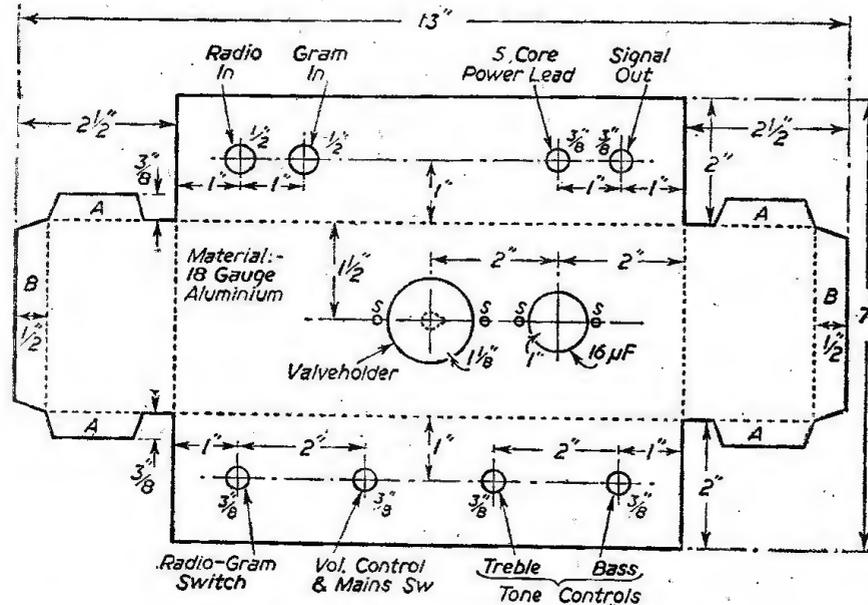


Fig. 2.—Chassis layout and drilling data.

switching. The following is a unit designed expressly for this purpose.

Some constructors of the "Modern" superhet tuner will find it more suitable for their cabinet layout to use the unit now being described in place of the subsidiary tone-control unit included in the tuner design. In this case they will need to omit the audio amplifier stage from the tuner, connecting

and the radiogram switch where it will not affect radio reproduction. The purpose of the audio stage is, of course, mainly to make up for the loss inevitably introduced by a tone control network.

### LIST OF COMPONENTS

- R1 : 1/2 MΩ potentiometer with switch.
- R2 : 10 KΩ, 1/2 watt.
- R3 : 47 KΩ, 1 watt.
- R4 : 1 KΩ, 1/2 watt.
- R5 : 100 KΩ potentiometer.
- R6 : 100 KΩ, 1/2 watt.
- R7 : 1 MΩ potentiometer.
- R8 : 10KΩ, 1/2 watt.
- C1 : .1 µF 350v. wkg.
- C2 : 50 µF 12v. wkg.
- C3 : 16 µF, 350v. wkg.
- C4 : .25 µF, 350v. wkg.
- C5 : .003 µF, 350v. wkg.
- C6 : .02 µF, 350v. wkg.
- C7 : .005 µF, 350v. wkg.
- C8 : .02 µF, 350v. wkg.
- Valve : 6SJ7.
- Sw. 1 : 2-pole, 2-way rotary.

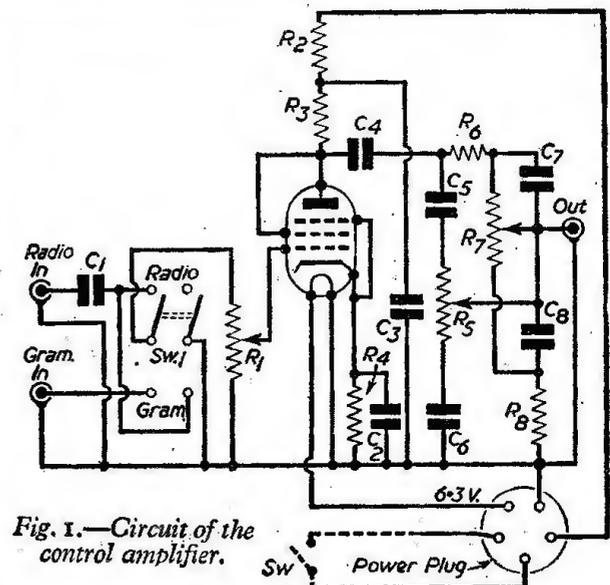


Fig. 1.—Circuit of the control amplifier.

### Construction

The chassis used measures 5in. x 3in. x 2in. deep and is shown in the "flat" in Fig. 2. The position of the holes is indicated. The size of the holes will be determined by the particular components used, but the size for the original components is indicated. The direction in which the octal valve-holder points is also shown. Soldering tags for earth connection are required on the holding-down bolts in the holes indicated by the letter "S," and care should be taken to ensure that a good, clean electrical contact is made. The aluminium is folded so that the markings as given are inside the chassis. Flanges marked "A" are bent upwards and go inside of the front and back pieces to which

they are bolted or riveted, giving neatness and strength to the corners. Flanges marked "B" are bent outwards to form fixing flanges.

Avoid tag-boards by connecting resistors and condensers direct to the major components and valve-holder tags. In this way hum pick-up will be minimised. It will be realised that the part of the receiver built on this chassis is most vulnerable to hum pick-up and, as it is not included in the feedback loop of the main amplifier, automatic cancellation is not available. Screened leads should be used for pick-up and tuner to control amplifier and from control amplifier to main amplifier. Coaxial plugs and sockets are used and the most convenient and satisfactory link is coaxial cable.

# Building and Buying S.W. Receivers

Points of Interest in Receiver Design and Construction

By A. W. MANN

**A**MONGST the readers of this journal there are perhaps some who are contemplating the purchase of a second-hand communications type receiver.

In the second-hand market, there are bargains to be had. There are also reputable firms who specialise in the overhaul and realignment of second-hand communication receivers, which are later advertised for sale. As these firms handle only the best types and do not offer obsolete models, the prospective buyer is assured a fair deal.

The same applies to most of the private advertisers, especially in the case of post-war models.

In pre-war years, however, a considerable number of American makes were sold in this country. Amongst them are quite a lot capable of good service and for which the original types of valves are still available.

There are some makes which have, over a period of years, been redesigned and improved, the valves used being of a more up-to-date type.

The manufacturer, in advertising his products, usually follows the trade name with a type number. Unfortunately, some private advertisers who wish to dispose of a receiver made by one particular firm, do not quote the type number at all.

This may or may not be in good faith, according to the individual. The prospective purchaser who takes too much for granted and who sends cash without making inquiries, may find that he has one of the later pre-war models, and a good one, or on the other hand that he has bought a much earlier model, with the result that at a later date it may be difficult to obtain spare valves of identical type. He may even be dismayed to find that the valves he requires are no longer manufactured.

Rather than clinch a deal for what appears to be a good bargain, the prospective buyer would be well advised to obtain the fullest particulars as to type, year of manufacture, full specification, and the position so far as the spare valves situation is concerned.

The reply to his inquiries may be satisfactory in which case he can go ahead.

### Replacement Alternatives

Suppose, however, that he is informed that the model is sufficiently obsolete to make the replacement of the valves difficult. My advice is take no further action.

It may be that a list of modern valves are quoted along with the suggestion that they can be used to replace the original types around which the receiver was designed. In the writer's opinion such an idea should not be entertained.

Modern valves, being much more efficient, instability is to be expected. As a result, quite a lot of experiment and modification might be necessary, and in the end, the results may well prove that neither the time and money expended has been justified.

Complaints are sometimes heard over the air that while the receiver in use is satisfactory, the user is handicapped through lack of an instruction book, service data and theoretical circuit diagram. If possible the user should at least obtain the latter.

Here again we have recognised firms who cater for our requirements. The receivers are of various types, some for A.C. mains operation and others for use with battery and accumulator.

Lists, catalogues and advertisements give a considerable amount of detail, and the receivers are graded in price according to their condition. Such receivers are sold in their original form. Thus we know exactly what to expect according to the price asked.

Quite a lot of this apparatus has been sold after modification by firms who specialise in such work. Thus a reliable job has been made available for use straight away, at an extra charge.

A considerable number of these receivers have been bought by enthusiasts for modification purposes with a particular purpose in view. In a number of instances the work, as described by various writers, has been carried out successfully.

### Unsuccessful Modification

As is always to be expected, a departure from recommended procedure and the introduction of

original ideas, has at times resulted in failure, due to complications which, owing to lack of knowledge, could not be overcome.

These include conversions from battery to mains operation and the use of A.C. type valves; band spread—followed by attempts at realignment by ear; and the incorporation of built-in power supplies, etc., on original lines. Had the individuals realised their limitations and followed published modifications, as carried out successfully by others, satisfaction would in all probability have been obtained.

The apparatus which has been modified under the above circumstances is of little value to anyone. It is obvious, therefore, when contemplating the purchase of modified ex-Service receivers, that full details as to the success of the modifications should be obtained, together with a copy of the theoretical differences as compared with the original. Not only will the genuine advertiser benefit by the opportunity offered him to provide full details, but the buyer will avoid the risk of paying for the dabbler's mistakes.

### Home Construction with a Difference

In the days of KDKA, the writer, like many others, built short-wave receivers in which were incorporated modified and unmodified broadcast receiver components.

The reasons why this procedure was followed was because specialised components as we know them to-day were few, and very expensive. Under present-day circumstances, when highly efficient components (especially tuning condensers which are silent in operation on the highest frequencies) are obtainable for a few shillings, it is surprising to find that a considerable number of beginners follow the same procedure.

The idea is, of course, to explore the short-wave field at the minimum of expense, with a view to finding out if further expense is justified. Such methods of procedure are a waste of time, and the results obtained will prove far from satisfactory.

If a manufacturer produced a short-wave receiver without any other consideration but that it should be sold at a ridiculously low figure, the people who bought it would soon complain because they could not get the results expected.

The manufacturer realises that in order to achieve the necessary standard of all-round efficiency his production costs must not be set below a certain figure. By adhering to this policy his clients get what they pay for, and in most instances expect.

Exactly the same thing applies to the home constructor of short-wave receivers. Unless he is prepared to invest a sufficient sum of money, in order to obtain components specially designed for the purpose he has in mind, he cannot expect to build an efficient receiver. There is no room for make-do and bodging in short-wave radio, and the sooner this is realised the better for the pastime as a whole.

The writer follows with interest the monthly DX logs as published in various short-wave publications, and is especially interested in those sent in by users of home-constructed receivers. I would not believe for one moment that these DX operators use junk receivers and haywire assemblies. Undoubtedly they have in the first place used suitable

components, taken care with the layout and wiring, and by their reports give convincing proof that the results achieved fully justify the outlay.

### Proof

Money invested in first-class components is well spent. Proof of this is found in the fact that the writer has in use Eddystone and Raymart components dating back to some years before the war. Post-war products of the same types are also to hand, and were chosen because of the long and satisfactory service given by those of pre-war days which are still in use.

### Ways and Means

There are ways and means whereby the costs of the first short-wave receiver can be kept comparatively low. Chassis consisting of two side runners, with a plywood top can be used, and either the top or underside covered with aluminium sheet. Such chassis are easy and cheap to make. Chassis type valve-holders can be used, and are at present cheaper than the pre-war baseboard type.

While low-loss principles of construction should be the rule, there is no need to carry it to extremes. This, in my opinion, applies especially in the case of valve and coil holders respectively.

While it is admitted that the ceramic types are the most efficient from the low-loss point of view, it does not follow that if the paxolin type is used, an inefficient receiver will be the result. The Services incorporated a considerable number of the latter type in their equipment.

I have referred in previous articles to the inadvisability of using old valves. Taking into account the comparative cheapness of ex-Service valves of all types, and which, by the way, had to conform to definite standards of efficiency or be rejected, it is surprising that some experimenters and beginners adhere to this practice.

### Poor Results

Much has been written about dead spots in tuning, lack of regeneration, low-level amplification and the like. In many instances there is no doubt but that the root cause of such troubles could be traced to the use of valves whose bases should long ago have been used as coil formers.

It is quite possible to wind efficient coils on old discarded valve bases. The windings of these may be close wound. Such coils will give good service until the highly efficient commercial types can be obtained.

### Always Remember

You may be a beginner with very little practical experience, but at the same time an avid reader of magazines of short-wave interest. In time you will accumulate a considerable amount of reference material in the way of circuits, layouts and technical information.

Thus you will have on hand the work and advice of many authors upon which to draw, and apply in practice. Not only what they think, but what they have proved by practical test and experiment to be the correct procedure to follow. Whatever personal preferences and ideas they may have individually, they have one thing in common. They do not use junk components or expect those who attempt to duplicate their work to do so.



# NOSCOPPE "

the 198 or 73 Unit

PETER LEWIS

**Remove :**

All wiring, the transformers, the various coils (which must be rewound), the 18-point connector, the controls marked "SM," Gain, "B-amp." All the controls at rear left-hand side. Also the 0.1 $\mu$ F. 2.5kV. condenser (front left) and trimmer from rear of unit.

**Modify :**

The switch "HT" by cutting off the lugs actuating the spring which returns lever to mid-position. Remove and strip down the coils, rewind the I.F. coil with 140 turns 34 S.W.G. in short multi-layer fashion to give an inductance of 350 $\mu$ H. (Fig. 5a). The other coils are rewound as follows : 75 turns of 34 S.W.G. single layer, close wound, tapped at 50 turns (Fig. 5b).

On the other former 100 turns 34 S.W.G. and on top of this layer interleaved with waxed paper another 100 turns of the same wire wound in the same direction. Dope the coils with wax or polystyrene solution to keep the wire in place (Fig. 5c). S.W. Coil : 20 turns  $\frac{1}{4}$ in. dia. Fig. 5d.

**Assembly**

Fix the mains transformer in position at the rear of unit (Fig. 3b). It might be necessary to provide a metal screen around it if the external field causes any deflection of the cathode-ray.

If used, the separate heater transformer should be mounted immediately behind the C.R.T. base. The two J50's are mounted on the panel with the two 0.1 $\mu$ F., 2.5 kV. condensers. The third 0.1  $\mu$ F. is placed just behind the focus control.

A metal plate 3 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. (Fig. 3c) is made to cover the hole left by removal of the 18-pin connector, and an 80 pF. variable condenser is mounted on a bracket so that its spindle protrudes through the  $\frac{1}{4}$ in. hole in the plate. The 100 pF. trimmer is mounted nearby. (Trimmer is already in place on the 73 unit.) Fix a potentiometer 1 k $\Omega$  in place of control "SM" and one of the black volume

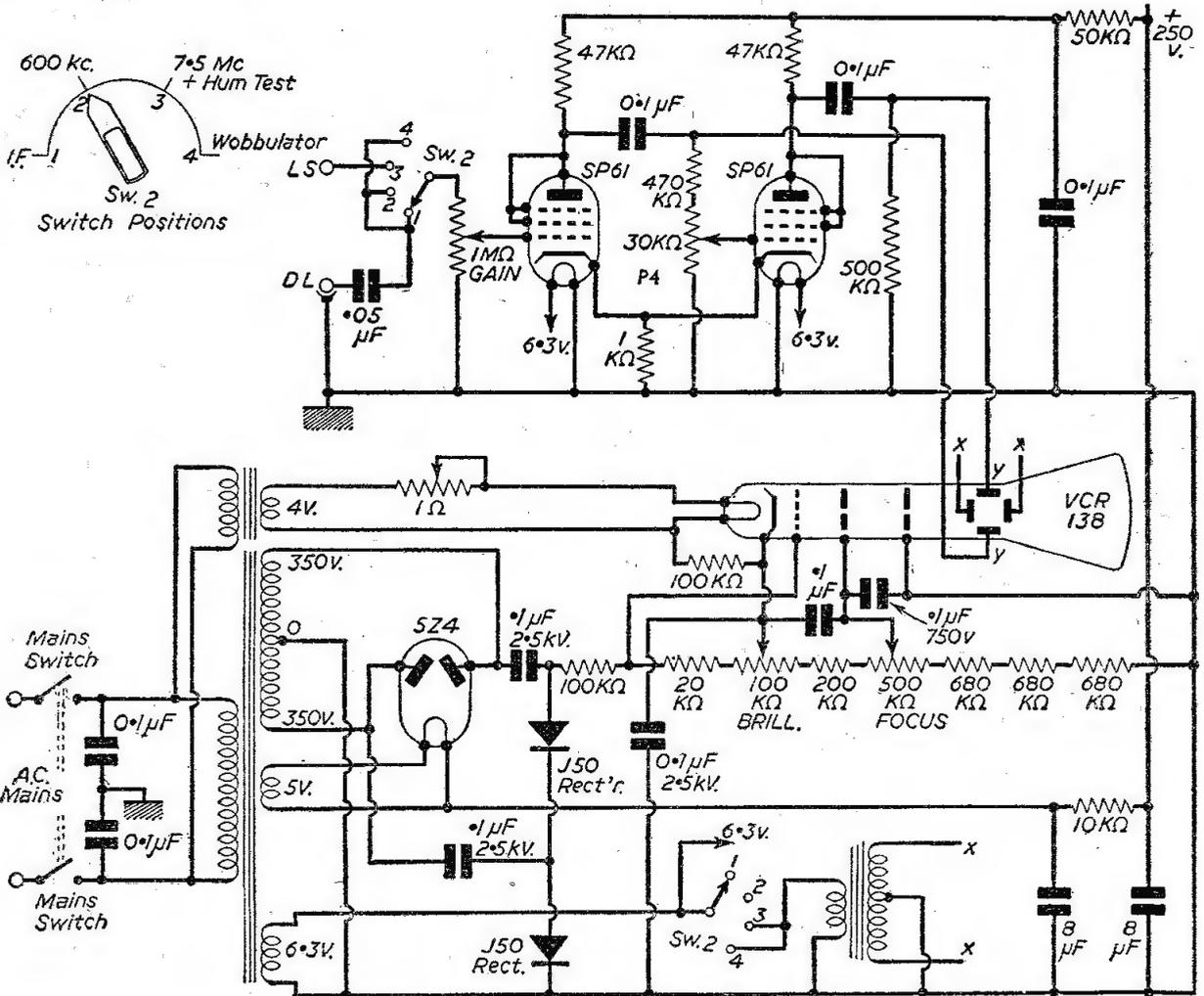


Fig. 2.—Tube and power supply circuits.

controls (marked "Shift") instead of the wire-wound potentiometer marked "Gain."

Replace control "B-amp" by a 5 kΩ potentiometer. In case the rectifier valve does not fit in the space formerly occupied by the 6H6, the socket for the 5Z4 must be mounted on a bracket beside the ganged switch, as shown in Fig. 3b. The A.F. transformer is mounted at the rear of unit wherever its field will cause no deflection of the C.R. beam.

One of the existing transformers in the unit can be used with about half of the primary turns removed to give higher ratio (Fig. 5). The mounting for the coils is also beside the switch, as seen in Fig. 3b and 5d. The two wobulator coils should be at right-angles to each other, and the

other coils screened. Coil b is fixed to a paxolin strip attached to side of mount.

Pieces of white card or ivorine should be fitted to the controls to be calibrated when the instrument is working. For the I.F. control a size of 2½ in. x 3½ in. is needed; for the ganged switch, 1½ in. x 2½ in., and for the gain control, 1½ in. x 1½ in.

After these mechanical preparations the wiring and calibration of the instrument can be carried out.

**Wiring**

The wiring should be carried out according to the diagram, giving especial attention to keeping H.F. connections as short as possible and very rigid, and using very good insulation on all E.H.T. leads. H.T. and E.H.T. potential dividers or smoothing resistors are mounted on the paxolin strip beneath the C.R.T. All earthing points of one stage are taken to one point, pin 6 on the valveholders, and thence to chassis. One side of the heater winding is earthed. The "live" side is used to modulate the I.F. oscillator and supply horizontal deflection for the C.R. beam. The A.F. transformer steps up the voltage and provides a symmetrical supply to the X-plates. On position 1 and 2 of the ganged switch the A.F. transformer is cut off from the supply. In position 1 the I.F. oscillator is operating. On position 2 the same valve is used to generate 600 kc/s; and on position 3 7,500 kc/s are supplied. In this position the input to the Y-amplifier is taken from the loudspeaker leads of the set under test, and the X-plates receive a 50 c/s supply, so

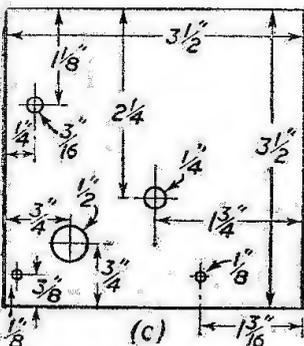
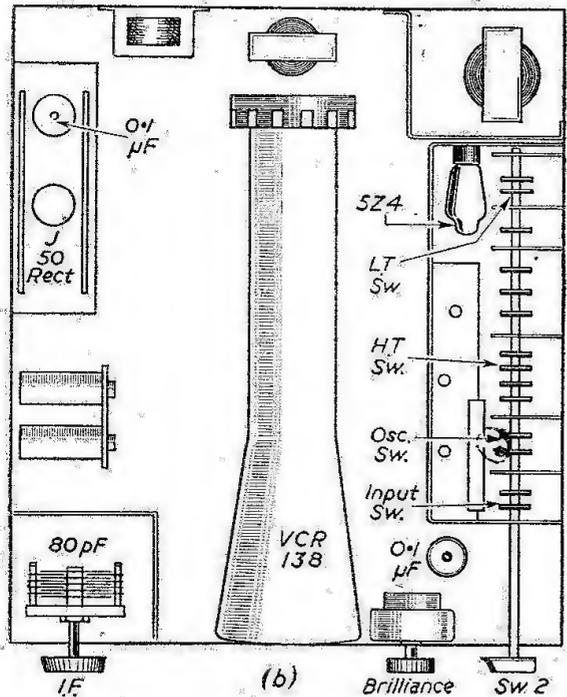
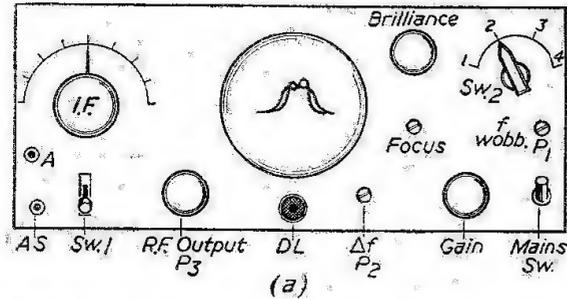


Fig. 3.—Details of the layout, etc., showing components which are left in place.

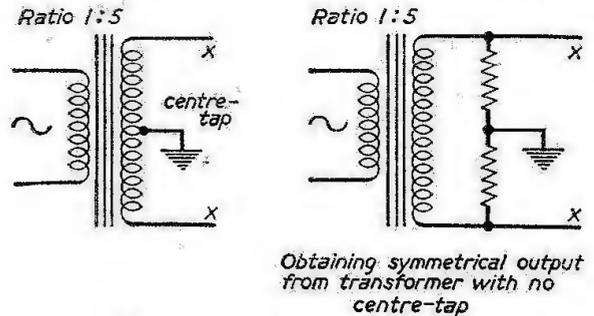


Fig. 4.—L.F. transformer data.

that any hum from the set will show up as a horizontal figure of eight if the hum frequency is 100 c/s; 50 c/s will show up as a loop. On the fourth position of the switch the wobulator is brought into operation and the input of the deflection amplifier is as in position 1 and 2 again taken via Pye-plug and cable to the diode load resistor of the set under test. The switch beside the socket (S.W.) for the lead of the "Aerial" and "Earth" terminals of the receiver allows this lead to be connected to the oscillators in the unit or to an outside aerial.

E.H.T. for the tube is generated by a circuit similar to the Westekt system. H.T. is smoothed by the four 4μF condensers and a 10,000 ohm resistor. Additional decoupling is provided for the oscillators. The horizontal deflection amplifier uses two S.P.61s wired as triodes in push-pull, phase-shift being obtained by feeding a small portion of the signal from the anode of the first valve to the grid of the second. Amplitude is adjusted by means of the 20 kΩ potentiometer mounted on the valve panel.

The I.F. generator utilises another S.P.61 in which the tuned circuits are switched between suppressor grid and chassis in a Transitron circuit. Thus no tickler-coil is needed. For I.F. and 600 kc/s the same coil is used and the capacitors are switched; for 7,500 kc/s a trimmer tuned S.W. coil is used, Fig. 5d. R.F. is taken from the anode via 50 pF, and changes of load have negligible effect on frequency. The wobulator also makes use of a VR65 (S.P.61), and has proved to be very effective and stable in operation. The operating frequency can be varied slightly by adjusting D.C. bias by means of a potentiometer. Frequency deviation is controlled by the A.C. voltage fed to grid 1 through potentiometer 2. These controls can be preset and need not be touched after initial adjustment. Trimmer t2 across coil b should be set for minimum current through the valve. The centre frequency obtained with the coils described was approximately 1,350 kc/s, but any other similar frequency can be used as long as there is no strong station on it. Strong harmonics are produced and the unit has been used for aligning S.W. receivers, the tenth harmonic (22 m.) being strong enough to give a clear indication.

The capacitive attenuator in the anode of the wobulator prevents changes in the load from affecting the oscillator. A fine control of the R.F. output is possible by means of potentiometer P3. Normally this output should be as low as possible in order to render the A.V.C. in the set inoperative.

**Check-up**

On completing the wiring according to the diagram a careful check of all connections is advisable. The voltages at the socket of the C.R.T. should be measured before the C.R.T. is inserted. A high-resistance voltmeter must be used. Note that in this circuit the anode of the C.R.T. is earthed. The grid of the C.R.T. should show the highest negative potential, the cathode is about 10-50 volts more positive according to the setting of the "Brilliance" control. The first anode will be about 250 volts positive in relation to the cathode, depending on the setting of "Focus" control. After switching off and discharging the condensers the C.R.T. can be inserted and the unit tested. Make sure that the filament voltage of the C.R.T. when warmed up is exactly 4.0 volts. Switch to position 3 and slowly advance "Brilliance" control clockwise. A horizontal line should appear across the screen and the "Focus" control can then be adjusted. Advance "Gain" about half-way and touch the input terminal; a loop will appear owing to hum pick-up.

To set push-pull amplifier for symmetrical output switch to position 1, apply 1-4 volts A.C. to input terminal and adjust "Gain" for trace lin. long, making sure that potentiometer 4 is set to zero. Then slowly advance potentiometer 4 until the length of the trace is exactly doubled.

**Test and Calibration of Oscillators**

Turn switch to position 1 and aerial switch upwards, connect a receiver to the aerial cable from the unit and tune set to 900 kc/s. (333.3 m.) (Milan 1), connect the amplifier input to the diode load in the set and try to receive signal by adjusting the I.F.


tuning on the unit by the 80 pF condenser or the 100 pF trimmer. The pointer on the 80 pF tuner should stand slightly to the left of centre position. Providing the calibration of the receiver is accurate, this position can be marked 450 kc/s. In the same manner adjust 880 kc/s (check with Welsh Reg.), 940 and 960 kc/s.

The 600 kc/s oscillator can be checked against Lyons (602 kc/s) and on the S.W. band the second harmonic of the 7.5 Mc/s frequency should fall on WWV (15 Mc/s).

Of course, if an accurate signal generator is at hand or can be borrowed, calibration becomes very easy indeed.

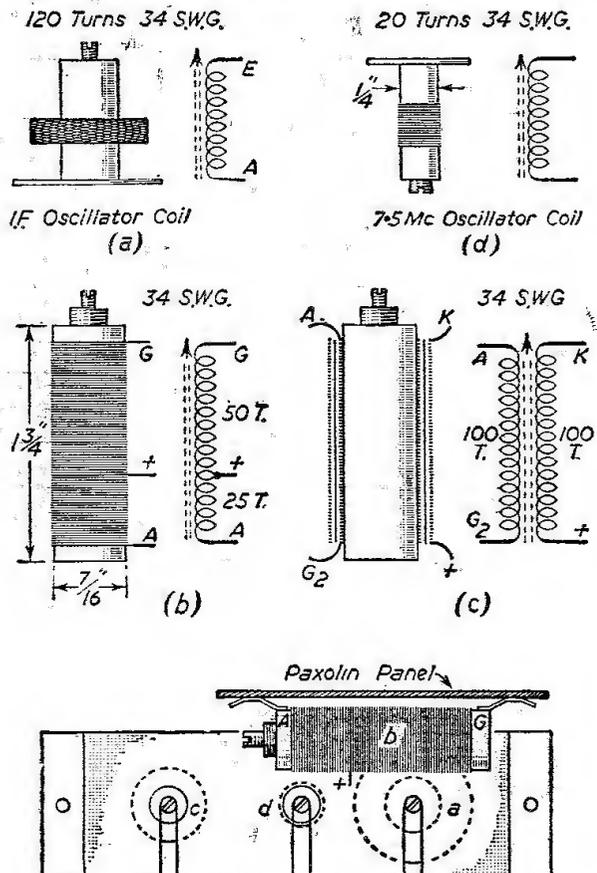**Test and Calibration of Wobulator**

On switching to point 4 the wobulator should start working and a strong signal should be obtained with the attenuator set half-way. Tune the receiver connected to the unit between 900 and 1,500 kc/s and listen for the signal or watch for it on the 'scope. Should no signal be found, check whether unit is oscillating by connecting a high-resistance voltmeter to point "T," that is the tapping on the phase-shift coil of the wobulator.



(e) Assembly of Wobulator Coils  
Fig. 5.—Details of the coils.

About 180 volts should be at this point. Adjust potentiometer 1 until a sudden increase in voltage occurs and then adjust trimmer T2 for maximum voltage. The bandwidth covered can be set by potentiometer 2, and this might alter the frequency slightly. Make a note of the final working

frequency, and make sure it is not too near that of a strong broadcast station or interference will result.

The figure on the 'scope will generally show two peaks as the flyback is not suppressed. The tuned circuits of the receiver should be adjusted to give a symmetrical pattern. Owing to the slight delay in the voltage build-up in a tuned circuit the leading edge will be slightly lower. Fig. 6a shows the correct trace.

Fig. 6b gives a picture of a set which is unstable and on the verge of oscillation. Fig. 6c was obtained from a set in which a volume-control of too low a value (50 k $\Omega$ ) had been used.

Make sure that all the mica condensers used in the oscillatory circuits are really beyond reproach, as leaky condensers will make operation most temperamental!

**The Alignoscope at Work**

Connect set to unit, Aerial and Earth terminals, and "DL" to diode load resistance (Fig. 6d).

Set switch 1 to position 1 and switch 2 to position 1, adjust I.F. to required value, tune receiver to approximately 550 kc/s and short-circuit oscillator section of tuning condenser. Turn potentiometer 3 and "Gain" up until a vertical line  $\frac{1}{4}$  in. long is obtained, and align I.F. transformers for maximum length of trace. After this set I.F. trap (if fitted) for minimum deflection. Turn switch 2 to position 2, remove short-circuit from oscillator of set, and align set at 600 kc/s. Now switch to position 4 and tune in to centre response curves on 'scope. Adjust I.F. and R.F. trimmers for correct figure. See that frequency indicated on receiver dial corresponds with that of the wobblator. Otherwise adjust by setting oscillator trimmers in the set and re-aligning the R.F. trimmer. Receivers with variable selectivity must be aligned with the selector in the "narrow" position and then checked

accordingly on "wide" to see whether response curve widens accordingly without becoming lop-sided.

For this kind of work the Alignoscope is indispensable!

For alignment on shortwaves the frequency of 7.5 Mc/s (40 m.) and 15 Mc/s. (20 m.) is used. Harmonics from the wobblator are, of course, also available. As all indications are visible on

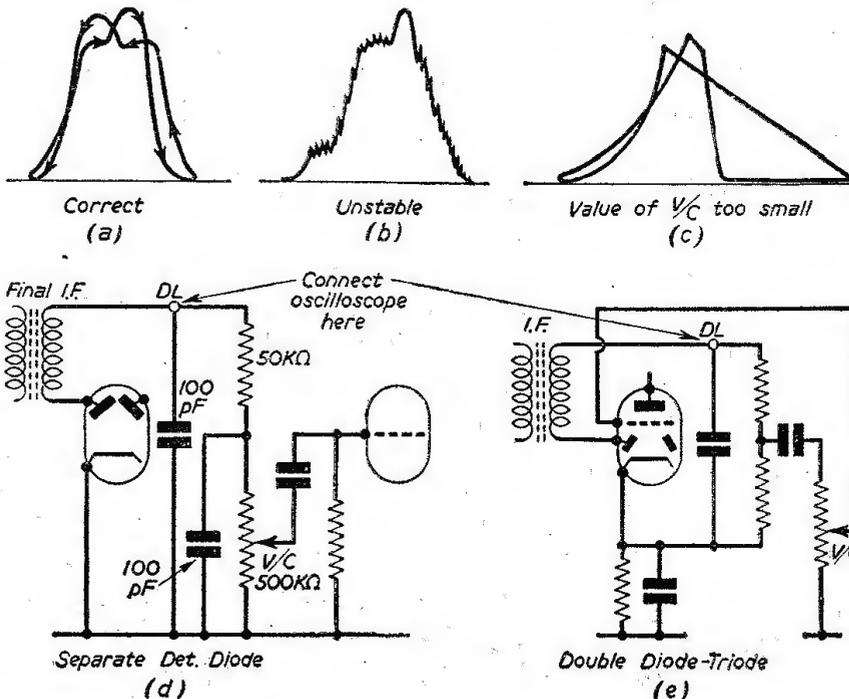


Fig. 6.—A.F. testing, showing typical oscillograms.

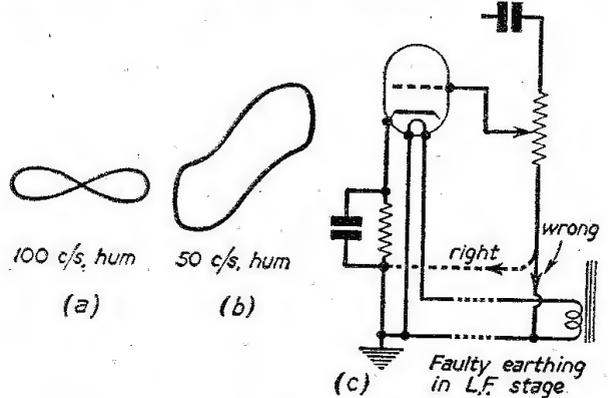


Fig. 7.—Hum tracing.

the 'scope, the volume-control on the set can be turned down, thus causing less irritation to the other occupants of the workshop!

**Test for Hum**

Connect lead "LS" of 'scope to low-impedance output of set (secondary of output transformer). Set switch 2 to position 3, a horizontal line or very flat loop should appear on the 'scope with "Gain" turned full up. Undue 100 c/s hum will show as a horizontal figure of eight, and denotes insufficient reservoir capacity (Fig. 7a). Effect of added smoothing will result in a marked flattening of the figure.

An ellipse denotes 50 c/s hum pick-up due to faulty screening or earthing in the A.F. stages, cathode-heater short in a valve, etc. (Fig. 7b).

This method of hum-detection and its cure is especially valuable in noisy workshops where aural methods fail.

If, when turning up the volume-control, the hum increases, the fault is in the circuit preceding the control. If the loop widens on returning the volume-control to zero, a bad earth connection for the latter is indicated (Fig. 7c).

Hardly any trouble should be experienced in building this instrument, but its constant use in the workshop will save a lot of time while ensuring that every receiver tested on it is properly aligned and shows no sign of instability or hum.

This unit should soon have its place on the bench of every test and service department.

# Hum Problems in Low-level Amplifiers

Overcoming a Difficulty in the Heater Supply of Modern Equipment

By GORDON J. KING

A HIGH-GAIN head amplifier is often necessary for microphone, or tape playback pre-amplification, and also where the output voltage obtainable from the generator source is insufficient to drive fully a standard power amplifier system. Most medium-quality moving-coil and crystal microphones deliver adequate output voltage, thus enabling connection to be made direct to the microphone input terminals of a standard amplifier; maximum output is realised at normal speech levels when the announcer is situated a few inches from the microphone. Owing to the diminutive output from the better quality microphones of the ribbon variety, a stage of high-gain head amplification is required between the microphone and the main amplifier. Again, the output from a good quality tape recording is usually very small and does not often exceed about 1 mV. This minute voltage is of insufficient magnitude to drive a standard amplifier for satisfactory tape playback service; also the attenuation caused by the inclusion of the tape corrector circuits further reduces the effective output voltage. It will be necessary, therefore, to introduce a stage of high-gain voltage amplification.

## The Hum Factor

A head amplifier designed to have an amplification of between 100 and 200 times is usually sufficient to enable the main amplifier to be fully driven. The overall amplification is thus the product of the two amplifier gains, and at these low input levels when using A.C. mains to power the system special precautions are necessary in order to keep the mains hum at a minimum. Indeed, the usable amplification is governed by the ratio of hum to amplification. It has been proved by the writer that a large percentage of the hum is injected into the amplifier from the A.C. used to supply the heater of the first valve, and is a combination of three factors: emission from the heater to the cathode; capacitive coupling from the heater connecting leads and the valve heater to the anode and grid electrodes; and also to the slight leakage between the heater and the cathode. In order to eliminate completely the hum factor due to the above effects, it is essential to feed the heater of the first valve from a D.C. supply.

## A Source of D.C.

A supply of D.C. for this purpose may be obtained from a low-impedance bridge rectifier circuit, and may be energised from a separate L.T. winding on the mains transformer, or a special heater transformer may be utilised. The voltage drop across the rectifier must be taken into consideration when computing the output voltage required from the heater transformer. This circuit arrangement is shown in Fig. 1. The very large capacity condenser shunting the heaters is necessary to rid the L.T. circuit of any ripple voltage, and may be a 6-volt working electrolytic type.

## Alternative

An alternative arrangement for obtaining the D.C., and a system used by the writer to reduce the hum in a tape playback amplifier is shown in Fig. 3. It is clearly seen that the potential for the heater of the head amplifier valve is derived from the rectified H.T. voltage in the main amplifier. It will, of course, be appreciated that the total H.T. current of the amplifier is passing through the heater of the valve, and to ensure that the voltage across the heater is correct a valve must be selected that requires a heater current similar to the total H.T. current of the amplifier. The heater voltage is not so important, although it should be remembered that the voltage dropped across the valve will reduce the main H.T. voltage by the same figure. If it is desired to use a valve that has, say, a 22-volt heater at a current of 0.1 Amp., and the total current consumption of the amplifier is found to be 150 mA., the surplus 50 mA. may be passed through a resistor that is connected in parallel with the valve heater, R1 in Fig. 3. The value of R1 is readily calculated from the Ohms law formula: thus  $R1 = \frac{E}{I}$  where E = the heater voltage, and I = the surplus current, in the case illustrated the value of the resistor  $R1 = \frac{22}{0.05} = 440$  Ohms. If on the other hand it was found that the current was only 90 mA., it would then be necessary to arrange the amplifier to pass an extra 10 mA. by shunting the main H.T. line by a resistor, R2, Fig. 3, of value  $\frac{E}{I}$ , where E = the

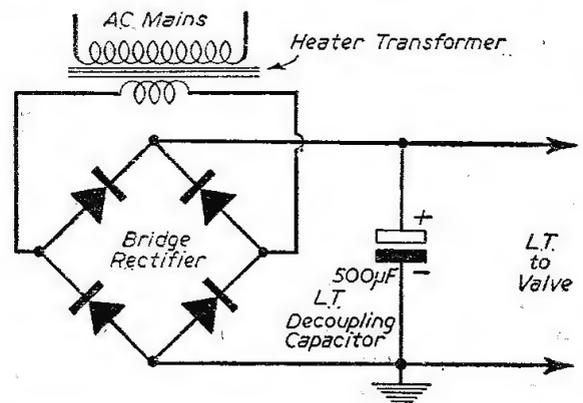


Fig. 1.—Method of obtaining D.C. for the first valve, using a Bridge Rectifier.

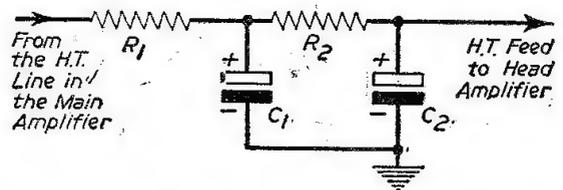


Fig. 2.—Circuit of the H.T. filtering.

main H.T. line voltage, and  $I$ =the additional current required to bring the total consumption to 0.1 Amp. (in this case 100 mA.—90 mA.= 10 mA. or 0.01 Amp). The wattage rating of the resistors may be computed from the formula  $W=I^2 R$ , where  $I$ = the current flowing through the resistor in Amps., and  $R$ =the value of the resistor in Ohms. Two electrolytic capacitors  $C3$

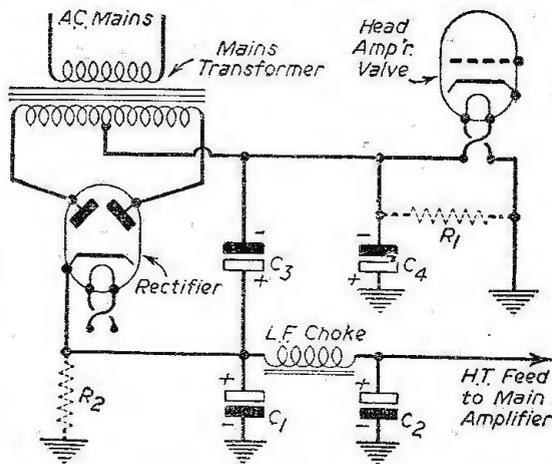


Fig. 3.—Another method of obtaining D.C. for the first valve.

and  $C4$  are employed to decouple any ripple voltage that may be otherwise present in the L.T. line. The value of  $C3$  should be at least  $8 \mu\text{F}$ , and of a working voltage higher than the main H.T. voltage,  $C4$  should be about  $50 \mu\text{F}$ , and the working voltage should not be less than the valve heater voltage. In most instances a 50-volt cathode decoupling capacitor is suitable. Most high-fidelity amplifiers use a push-pull output stage bringing the total H.T. current to between 100 and 150 mA., thus rendering the system suitable for this type of L.T. feed. Breaking the H.T. circuit at the point indicated in Fig. 3 is very convenient, since one side of the valve heater may then be at earth potential. This method of obtaining D.C. for the head amplifier valve should not be used on amplifiers other than those employing an output stage that is biased to class "A" conditions, since the fluctuation of the H.T. current will vary the heater voltage of the valve continually, with dire consequences. Valves of the 12J7 and 12SJ7 class are very suitable for this mode of operation if sufficient H.T. current is available. A very satisfactory high-gain head amplifier employing a high Gm. television pentode, and obtaining the heater voltage by the above method, is in use by the writer, functioning in front of a standard amplifier which can now be used as a tape playback and microphone amplifier. Very high gains are possible from this type of valve with very good frequency characteristics.

### High Tension Filtering

A smaller percentage of the hum may be caused by insufficient H.T. filtering for the first valve, and if the H.T. for the head amplifier is derived from the main amplifier H.T. supply, two stages of resistor-capacitor filtering should be used, keeping the values of  $C1$  and  $C2$  as large as possible, preferably  $16 \mu\text{F}$  electrolytics, see Fig. 2. The combined value of  $R3$  and  $R4$  should be made approx-

imately one-fifth the value of the anode load resistor, or greater if the supply voltage is sufficiently high. The total value of resistance may be calculated thus:

$$R1+R2 = \frac{E_d \times 1,000}{I_c}$$

where  $E_d$ =the required voltage drop in  $R1+R2$  and  $I_c$ =the cathode current of the head amplifier valve in mA.

### Unwanted Coupling

Owing to the extended low-frequency response of a high-fidelity audio amplifier, the effects of hum due to electrostatic and electromagnetic coupling can present a serious problem when dealing with low level equipment. Electrostatic coupling is usually caused by the leads that are carrying A.C. being in close proximity to the signal input leads. Judicious component and circuit arrangement reduces this effect, which may be further minimised by the use of screened leads. These should be earthed at a common point, and care should be taken to ensure that they do not make random connection with the chassis, since the small potentials so produced will be greatly amplified, thereby increasing the residual noise of the amplifier. It should be borne in mind that screened wire has a considerable capacitance and serious attenuation of the upper frequencies is possible if long, high-impedance screened signal leads are used. These should be avoided wherever possible in favour of separate screened compartments.

Electromagnetic coupling is usually caused by the external field from the power transformer and choke embracing the low-level input transformer. A noticeable reduction of hum due to this cause can be achieved by screening completely the input transformer with mu-metal, and before finally securing to the chassis it should be oriented for minimum hum pick-up. It is advisable to construct the head amplifier on a separate non-magnetic fully-screened sub-chassis, and should be mounted well away from the power equipment. It should be wired very rigidly, using short leads; a busbar earth should be avoided and a common "grounding" point made available for the earth returns.

## Books Received

### RADIO CIRCUITS.

By W. E. Muller, M.A. (Cantab.), M.Brit.I.R.E. Third Edition. 120 pp., 64 illustrations. Published by The Trader Publishing Co., Ltd. Price 5s.

### MAGNETIC TAPE RECORDING.

By P. A. Tarry, A.M.Brit.I.R.E. Fourth Edition. 70 pp., 12 illustrations. Published by Audigraph, Ltd., 74, Gt. Hampton Street, Birmingham, 18. Price 6s. 6d.

### WIRELESS AND ELECTRICAL TRADER YEAR BOOK.

22nd Edition. Published May 22nd. 202 pp. Price 10s. 6d. (with a reduction to subscribers of the "Wireless and Electrical Trader").

### RADIO AND TELEVISION RECEIVER CIRCUITRY AND OPERATION.

By A. A. Ghirardi and J. R. Johnson. 669 pp., profusely illustrated. Published by Rinehard Books Inc., 232, Madison Avenue, New York, 16. Price \$6.50.

**EX-R.A.F. INDICATOR UNIT TYPE 62.** Containing VCR-97 CRT with mu-metal screen; Xtal unit and valves 16/VR65 (SP61), 2/VR54 (EB34), 2/VR92 (EA50), etc., etc.; two deck chassis in metal case, 18 x 18 x 1 1/2 ins. New condition, 67/6 each. Plus 7/6 packing and carriage.

**RECEIVER TYPE 21.** The receiver portion of the W/S 21 operating from 4.2-7.5 Mc/s Double superhet from 18-30 Mc/s. Incorporating B.F.O. and crash limiter. Valve line-up 7-AR12 (VP23) and 2-AR8 (HL23DD). Absolutely brand new, complete with circuit. Only 45/- complete. Vibrator power unit for above, brand new, 17/6 only.

**R3515 I.F. STRIP.** A complete I.F. unit, comprising 6 SP61 I.F. stages, tuned to 13.5 Mc/s, 1 EA50 diode detector, and 1 EF36 or EF39 output of video stage. A few modifications only are required to adapt this unit which will give pictures of extremely good quality. Price complete with valves, and fool-proof modification instructions, is 45/-, plus 5/- packing and carriage. Limited quantity only.

**R3547 RECEIVERS.** Absolutely brand new, in sealed manufacturer's packing cases. Incorporating 15 valves type EF50, 2 of SP61, EF36, EBC33, 3 of EB34. Complete 45 Mc/s. I.F. Strip, motor, dial and drive, pots, etc., etc., £6 only, plus 10/- packing and carriage. Whilst they last!

**INDICATOR, Type 6**—Needs no introduction. Absolutely new in manufacturer's packing case. As recommended for ex-Government T/V construction, and "Wireless World" Oscilloscope. Incorporates VCR97 and mu-metal shield, 4 valves EF50, 3 of EB34. Only 75/- (plus 7/6 carriage and packing).

**RECEIVER TYPE 25.** The receiver portion of the T/R 1196. Covers 4.3-6.7 Mc/s and makes an ideal basis for an all-wave receiver, as per "Practical Wireless," August, 1949, issue. Complete with valves types EF36(2), EF39(2), EK32 and EBC33. Supplied complete with necessary conversion data for home use. 35/- new condition. Chassis only, 8/6.

**FREQUENCY CONTROL CRYSTALS.** By American G.E. Co. Octal base fixing. Following frequencies only: 2,500 kc/s., 3,500 kc/s., 4,600 kc/s., 6,200 kc/s., 8,000 kc/s., 7/6 each. Also FT243 1/2 in. pin spacing. 5765 KC/7975, 10/- each, 8000/8425KC, 12/6. New and unused.

**RECTIFIERS.** S.T.C. 300 V., 76 mA., 5/-. 12v. 2 amp. 12/6. 6 V., 1 A., 4/-. W6, WX6, 1/6. CV102 Crystal Rect., 3/6. H4/200 E.H.T., 2,400 V., 3 mA., 15/-. 650v. 1 m/a., 4/7. 1,000v. 1 m/a., 6/-. 5 m/a. Meter Rect., 5/-. Also J50 500v. 2 m/a., 7/6.

**R.3084 RECEIVER.** Incorporating 7 EF50, 2 EF54, 1 EC52, 1 VU39A, 1 HVR2, 1 EA50, plus 30 mc/s. I.F. Strip. Guaranteed absolutely brand new in maker's original packing case, 75/- (plus 10/- carriage and packing). This receiver is ideal for conversion to vision receiver.

**I.F. TRANSFORMERS.** Manufacturer's surplus. Iron cored. 465 kc/s. Size 4 x 1 1/2 x 1 1/2 in. Pair, 8/6. Whilst they last.

**HENRY'S 5 HARROW RD., LONDON, W.2**  
PADDINGTON 1008/9, 0401.

## SHORTAGE OF RADIO & T/V ENGINEERS

The demand of Industry for our trained students is still far greater than we can supply—and is likely to remain so for many years.

We offer :

### FULL TIME DAY COURSE

1 year Course in Principles and Practice of Radio and Television.

Next Course commences 27th August

Write for FREE BROCHURES giving details of the above, of our 3-year course and of others.

E.M.I. INSTITUTES—the only college which is part of a great industry.

# E.M.I. INSTITUTES

Dept. 32, 10, Pembroke Sq., Notting Hill Gate, London, W.2. Bayswater 5131/2


Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.

# CONSTRUCTORS!! HERE'S A BARGAIN FOR YOU!


## POUNDS WORTH OF COMPONENTS
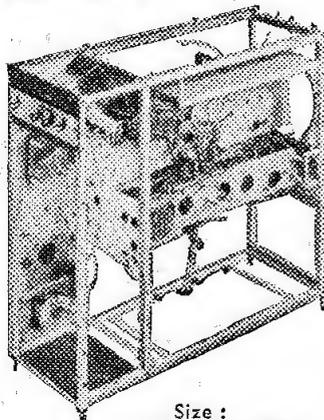
# FOR ONLY 5/-

The home constructor should derive a lot of satisfaction from this chassis—it contains so much of value to him. It might even have the very component he has been looking for. The light but immensely strong steel framework, paxolin and aluminium panels, stand-off insulators and the innumerable lengths of high quality, beautifully insulated leads are all worth far more than is being asked for the whole chassis.



Size : 21 1/2" x 7 3/4" x 19" high.

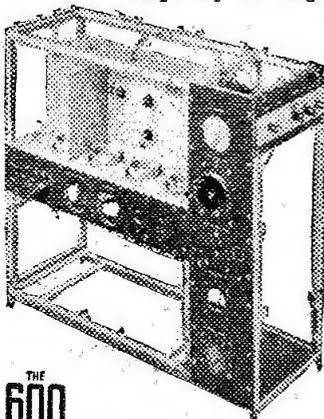

### Average Contents

(all new and unused)

- 10 pin, Plug Strip.
  - 5 250 K. 1-watt Resistors.
  - 4 100 ohm 1-W Resistors
  - 2 600 V 1 mf. Condensers.
  - 9 High-voltage Condensers 0.001 to 0.01.
  - 1 3-way Switch.
  - 2 H.F. Chokes.
  - 1 Relay Switch.
  - 1 Ceramic Valve Holder.
  - Lamp fuse with holder.
  - Spring Terminals.
  - Paxolin Panel 6 1/2 in. x 5 in.
  - Aluminium Panel, black finished.
  - Large number Multi-coloured sleeved leads.
  - Very strong steel framing.
  - Innumerable Nuts and Bolts, Soldering points.
  - Stand-off insulators, etc. etc.
- The whole outfit, weight 18 lb., sent to any address for only 5/-, plus 2/3 part cost of packing and carriage.

### SPECIAL OFFER :

4 for 22/6, carr. paid

Satisfaction guaranteed or money refunded.

**The NEW LONDON ELECTRON WORKS Ltd.**

(6) EAST HAM LONDON, E.6

Telephone : Grangewood 0044-1363

# QUALITY STRAIGHT THREE

An A.C./D.C. Receiver With A.V.C. and Negative Feedback

By W. GORHAM

**T**HE receiver is a conventional straight three stage plus rectifier, with a few refinements to improve the quality, and designed for operation on A.C. mains. The author prefers this type of supply to the A.C./D.C. types. By use of ex-Government valves and components the original model was built for under £4.

## The Circuit

Great liberties can be taken with the layout and wiring, but it is better to use short leads and an "in line" layout for stages.

The first stage, a conventional R.F. amplifier, is tuned by C2, one half of the twin-gang tuning condenser. R1 acts as a combined volume and "throttle reaction" control, first varying the bias on the grid of V1 and altering the damping on the aerial circuit.

After amplification through V1 the signal is fed via the H.F. transformer, a Wearite PHF2 coil, whose "hot end" of the coupling winding is decoupled to earth via C8, to the diode of V2 via coupling condenser C9. The transformer is tuned by the second half of the twin gang C3, the "bottom end" of the secondary winding being returned to the cathode of V2. R4 and R5 act as the filter and diode load respectively, and C11 is the R.F. decoupling condenser.

A.V.C. is taken from the junction of R4 and R5 via R7, decoupled by C12, to the "bottom end" of the grid winding of the PA2 aerial coil. If the reader feels that A.V.C. is not required on his

model, just omit C12 and R7 and return the bottom end of the grid coil to chassis.

The A.F. feed is also taken at the junction of R4 and R5 via C10 to the grid of the triode. R8 is the grid resistor. Bias is obtained by R6 in the cathode circuit. It will be noted that this resistor is not "by-passed" by the usual condenser. The author found that by omitting this condenser a good degree of negative feedback was obtained across the resistor and so improved the quality of the receiver. By the use of a diode for detection the receiver had the crisp, clear tone of a superhet receiver as against the harsher tone from the usual "leaky grid" detector. The other diode is not used, and is connected to chassis.

After amplification of V2 the detected signal is passed into the anode circuit and developed across R9, its load resistor, which is decoupled by R10 and C13. The signal is fed via coupling condenser C14 to the grid of the output valve, amplified through this valve and passed via the output transformer to the speaker. In the diagram it will be noted that a condenser is shown in dotted lines between chassis and grid of V3. Its purpose is to modify the tone of the receiver and in the author's model a value of .001  $\mu$ F was found to give the best results.

## The Power Pack

This is a conventional half-wave rectifier circuit employing a 6X5 with its anodes "strapped." The anodes are fed direct from the mains, one side

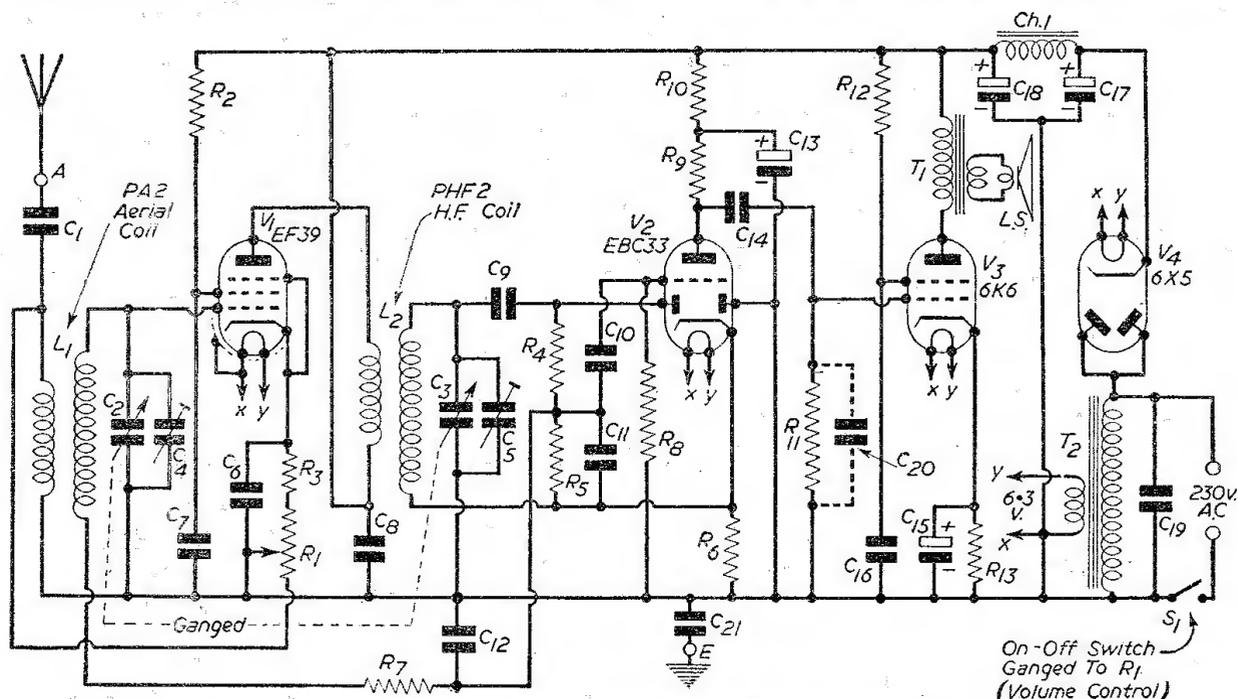


Fig. 1.—Theoretical circuit of the Quality Straight Three.

of which is connected to chassis via the On-Off switch S1. One side of the secondary of the filament transformer T2 is connected to chassis and one side also of all filaments. C19 acts as a filter across the mains and should be a good quality component. Note that as one side of the mains is connected to chassis the set must always be earthed via a condenser (C21).

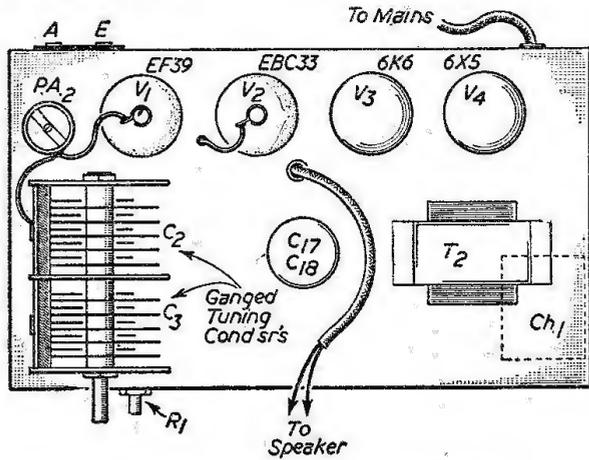


Fig. 2.—Layout of the receiver.

### The Chassis and Cabinet

The chassis was four sided, bent up from 18 s.w.g aluminium sheet, being 9in. x 7in. x 2in. deep. The speaker and transformer together were mounted on the cabinet. The cabinet was made from five-ply and enamelled cream. The dial was drawn in Indian ink on pink paper which was then covered with nail varnish and stuck on the cabinet. The tuning knob used was a 2½in. pointer type.

### LIST OF COMPONENTS

- R1—10,000Ω vol. control.
- R2—4,700Ω ½ watt.
- R3—200Ω ½ watt.
- R4—47,000Ω ½ watt.
- R5—22,000Ω ½ watt.
- R6—2,200Ω ½ watt.
- R7—100,000Ω ½ watt.
- R8—470,000Ω ½ watt.
- R9—220,000Ω ½ watt.
- R10—22,000Ω ½ watt.
- R11—470,000Ω ½ watt.
- R12—4,700Ω ½ watt.
- R13—470Ω 1 watt.
- C1—.001 μF. 350 v.w. Mica.
- C2, C3—.0005 μF. twin gang.
- C4, C5—60 pF. stamp trimmers.
- C6, C7, C12, C16—.1 μF. 350 v.w.
- C8—.5 μF. 350 v.w.
- C9, C11—100 pF. Mica.
- C10—.01 μF. 350 v.w.
- C13—8 μF. 350 v.w. Electrolytic.
- C14—.05 μF. 350 v.w.
- C15—25 μF. 25 v.w. Electrolytic.
- C17, C18—8 x 16 μF. 450 v.w. Electrolytic.
- C19—.01 μF. 1,000 v.w. Sprague.
- C20—Up to .001 μF. Mica (see text).
- C21—.01 μF. 1,000 v.w. Sprague.
- T1—60 : 1 output trans.
- T2—230 v. input. 6.3 v., 2-3 Amp. filament trans.
- CH1—20 H. 60 mA. 400Ω smoothing choke.
- S1—On-off switch ganged to R1.
- V1—VR53 (EF39).
- V2—VR55 (EBC33).
- V3—6K6.
- V4—6X5.
- 1 6in. 2-3 ohm. Rola P.M. speaker.
- 4 International octal valve bases.
- L1 PA2 aerial coil, L2 PHF2 aerial coil.

## News from the Clubs

### GILLINGHAM TELECOMMUNICATIONS SOCIETY

Hon. Sec. : C. E. Pellatt (G2FAQ), 101, Boundary Road, Chatham, Kent.

**D**URING April, a lecture was given on "Electronic Interval Timers," by G2FAQ. Lectures arranged for June and July include, "Home Production of QSL Cards by Photographic Methods (G2CM); "Frequency Modulated Oscilloscope (G3GSP); "Superhet Aligning" (G2HAW); "Oscilloscope Construction, with Particular Reference to Power Supply" (Mr. Walker).

The N.F.D. transmitter has been modified as a result of last year's experience, and is all ready for use. New members are welcome—meetings alternate Tuesdays, 7.30 p.m., Medway Technical College, Gardiner Street, Gillingham, Kent.

### READING RADIO SOCIETY

Hon. Sec. : L. A. Horsford (G2BHS), 30, Boston Avenue, Reading, Berks.

**A**T the A.G.M. in March the new committee were elected, mostly consisting of the 1950 committee.

It was voted that there be two meetings per month instead of the three which were held last year, the first to be held on the second Saturday of the month and run as an Instructional Section by Mr. Woodhouse (G2AHY); the other meeting to be the main meeting and held on the last Saturday on the month and consist of lectures and demonstrations, etc.

At the main meeting in April a film meeting was held; this ending with questions and answers.

Lectures and demonstrations for future meetings are now being planned and will be given in future publications.

### CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec. : W. A. Martin (G3FVG), 21, Brixton Hill, Brixton.

**C**LUB meets every Friday evening at 7.30 p.m. at 225, New Cross Road, New Cross, London.

Meetings during April were : 6th.—Demonstration of the Decca long-playing record system, given by Mr. A. Gilham, of Decca's.

13th.—Demonstration of top band 'phone cabinet TX by G3FNZ.

20th.—Debate. Subjects were QRO v. QRP; Are SWL's

necessary to the working of the amateur movement? Is aerial design neglected in favour of transmitter design? 27th.—Valve theory lecture given with the aid of 35 mm. film strips.

Average weekly attendance is now 30, but all new members, visitors and old friends are sure of a welcome.

### SHEFFORD AND DISTRICT RADIO SOCIETY

Hon. Sec. : 308959 S.A.C. Raby, R. D., Radar Link, T. Division, R.E.U., R.A.F., Henlow, Beds.

**S**EVERAL members under the watchful eye of G2DPQ, who is noted for his QRP work, have suddenly gone QRP mad.

Mr. Stan Edney recently gave a very interesting lecture on the alignment of superhets, and R. D. Raby has concluded his chats on radar and centimetre technique. Future events include a junk sale and it is hoped to give a demonstration of the 13 cm. gear mentioned in last month's report. Recently the club was granted affiliation to the R.S.G.B.

The club's QTH is Wharf Buildings, Shefford, Beds. Meetings are held every Friday evening at 19.30 hrs. and new members and visitors can be sure of a hearty welcome.

### TORBAY AMATEUR RADIO SOCIETY

Hon. Sec. : Mr. W. A. Launder, B.Sc., (Eng.) (G3FHI), 15, Cambridge Road, St. Marychurch, Torquay.

**R**EPORTS of the year's working were presented at the A.G.M. held in April, including a special review of Field Day, 1950. Statements of accounts were received and adopted, the financial position of the Society permitting a reduction in the annual subscription, which is now : full members 5s.; junior members 2s. 6d. per annum, and visitors 6d. per visit.

Principal officers elected were : president, W. B. Sydenham, B.Sc. (G5SY); chairman, F. J. Wadman (G2GK); treasurer, F. D. Cawley (G2GM); experimental manager, K. J. Grimes (G3AVF); auditor, G2BMZ.


On the relinquishing of the post of secretary by G3AVF, Mr. W. A. Launder, B.Sc. (Eng.) (G3FHI) was elected secretary. He will attend to enquiries of membership and normal business of the society.

Meetings at Y.M.C.A., Castle Road, 7.30 p.m., every third Saturday in the month. Visitors welcomed.

## TRADE NOTES
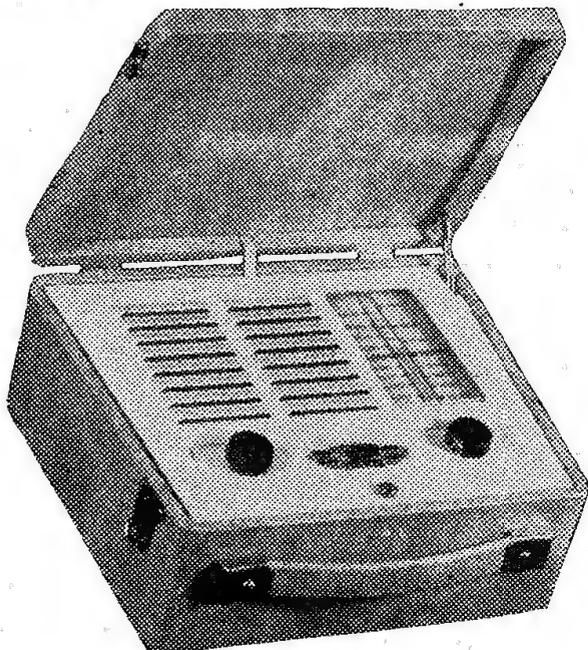
### New Vidor Portable

THE illustration below shows the general appearance of the new Vidor Portable, a battery-operated attaché type receiver incorporating some novel features. The most interesting of these is the automatic switch which is fitted so that the set is automatically switched on when the lid is opened. As a result, the set cannot easily be left on when not required and battery economy is thereby effected. The circuit incorporated is a



*The new Vidor battery portable.*

four-valve superhet, and it will be noted that the usual unsightly battery compartment has been eliminated. The receiver is completely accessible for battery replacement, and servicing is effected by raising the hinged front panel. The price is £15 10s. including P.T. but without batteries. These cost 12s. 5d. for the H.T. (Type L.5512) and 1s. 4d. for the L.T. (L.5040).

### "Elpico" Car Radio Aerials

LEE PRODUCTS (GT. BRITAIN) LTD., 90, Gt. Eastern Street, London, E.C.2, regret that due to increased prices of raw materials the list prices of their range of car radio aerials are amended as follows for all future deliveries 1951: Model CA/2 39s. 9d., CA/2E 63s., CA/5 43s. 9d., CA/7 42/-, CA/7E 65s.

### Cossor Change

A. C. COSSOR LTD. announce that Mr. L. L. Roberts, general manager of this company and director and general manager of Cossor Radar Ltd., resigned from these posts as from March 1st,

1951. Mr. Roberts left to take up an important position with Messrs. Rootes Ltd. in connection with their export business.

### The Philco "Richmond" Radiogram

THIS contemporary design, which has been chosen for the Festival of Britain Exhibition, is the outcome of close collaboration between two of the leading furniture designers and the Philco engineers, resulting in a specialised instrument of great beauty and technical refinement.


The cabinet is carried out in mahogany with bird's eye maple panels; the handles, ferrules on the legs and the bezel to the loudspeaker opening are of hand-made satin-finished brass. The loudspeaker grille is in hand-woven split cane.

The upper centre panel is a drop-front giving access to the tuning dial, radio and gramophone controls. The upper right-hand panel is a smoothly running pull-out drawer on roller bearings housing the automatic record changer. The two lower panels are sliding doors covering the record storage cupboards, giving accommodation for upwards of 300 records.

The technical equipment consists of a nine-valve radiogramophone combining all-wave radio and a record reproducer capable of handling all types of disc recordings.


A superheterodyne radio tuner chassis is coupled to a high quality audio amplifier with push-pull triode output. Provision is made for separate wide range control of bass and treble, so that satisfactory tonal balance can be obtained on both radio and recordings. The main amplifier has a peak output of 15 watts which is fed to a high fidelity 12in. speaker; overall negative feedback, in conjunction with triode-connection of the output valves, ensures a very low distortion level and a wide audio frequency response.

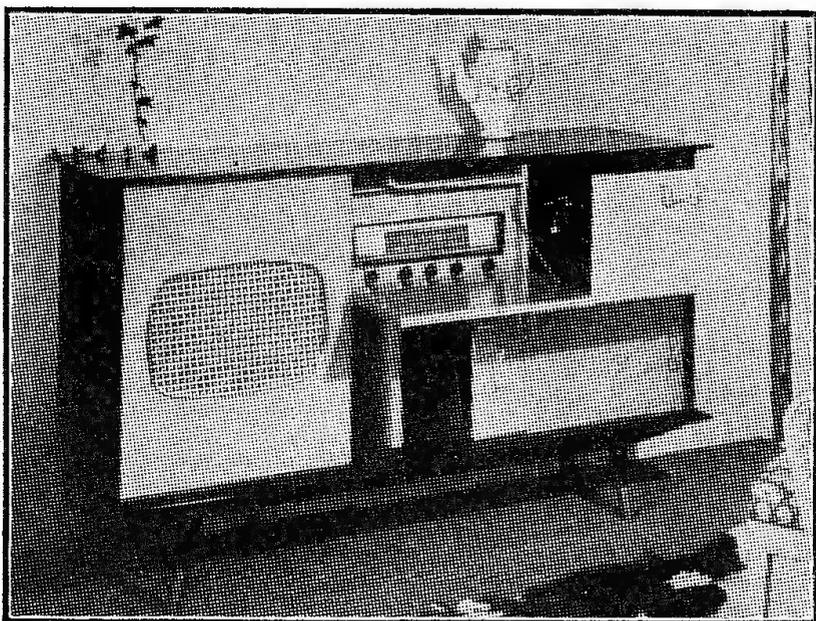The price of the Philco "Richmond" radiogram, which is made to order only, is 275 guineas, including tax.



*Philco "Richmond" radiogram which is on view at the Festival of Britain.*

# BATTERY PERSONNEL CHASSIS

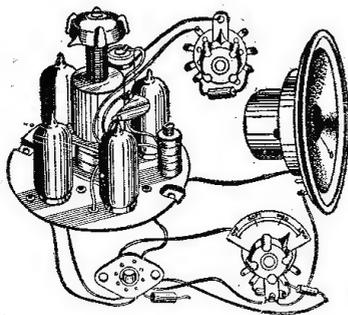


This 4-valve all dry battery operated receiver is of such small dimensions that it will fit into a cabinet only about 6in. x 4in. x 3in. and still leave ample room for batteries. The chassis is all wired and complete with speaker, volume control, wave-change switch, etc., etc., and only first-grade components have been used. Prices are: Chassis complete with valves (three type 1T4 and one type 3V4) —ready to operate on long and medium wave-bands, 99/6. Ditto, Chassis without valves, long and medium

but medium wave only, 89/6. Chassis without valves, long and medium wave-bands, 59/6. Ditto, but medium wave only, 49/6. Add 2/6 to cover postage and insurance.
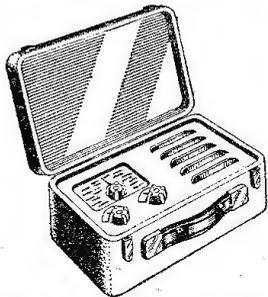
## CABINETS FOR ABOVE


Here is an illustration of the type of cabinet you could make for this set. We have none to supply at the moment, but expect some and will give purchasers of the chassis first-refusal of them if and when they arrive.


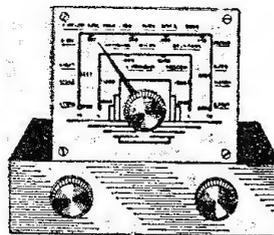
# ALL MAINS CHASSIS

This is the equivalent of a 4-valve receiver for it uses three valves and a metal rectifier. It is all wired up ready to work off A.C. mains, complete with modern valves, ganged tuning, high precision dust-cored coil, first grade condensers and resistors, all on metal chassis. Tunes long and medium wave-bands. Large clear dial. Receives home

services; light programme, Luxemburg, etc. Chassis size approximately 9in. x 4in. x 5in. Complete with valves, but less speaker, 59/6. Suitable speaker with matching transformer, 1/6—nothing else needed.



**ELECTRONIC PRECISION EQUIPMENT, 7 ELECTRON HOUSE, RUISLIP MANOR, MDDX.**

## CLYDESDALE

Bargains in Ex-Services Electronic Equipment

**INDICATOR TYPE 6 AND TYPE 6H.**—These units are mentioned in the INEXPENSIVE TELEVISION design and are complete and brand new, being fitted with a VCR97 Cathode Ray Tube. This Tube is probably the most adaptable of all the radar CRT's for T.V. operation.

The indicator unit is fitted with 4VR91 (EF50), 3VR54 (EB34), plus a host of T.V. components, condensers and potentiometers. The complete unit is enclosed in a metal box, 18in. x 8 1/2in. x 7 1/2in., finished in grey.

**CLYDESDALE'S PRICE ONLY £3. 19. 6 CARRIAGE PAID**

Please enclose 10/- to cover cost of transit case.

**STILL AVAILABLE.**—Brand new R.1355 I.F. VIDEO RECEIVER for T.V. vision or sound, readily available for use on your specific T.V. frequency in that the R.F. is fed in via a removable R.F. unit, i.e., the R.F.24-25-26 or 27. Space for an integral mains power pack is provided by the removal of the existing 80v. 400 cycle pack.

The R.1355 is complete with valves, 5 stages of 7.5 Mc/s. I.F. (SP61's), Detector (EA50), Video amplifier (SP61), and Cathode follower (SP61), also an E.H.T. rectifier (SU2150) and H.T. rectifier (5U4G).

Enclosed in a metal case, 18in. x 18 1/2in. x 7 1/2in. Please enclose extra 10/- to cover cost of transit case. **CLYDESDALE'S PRICE ONLY 67/6 each CARRIAGE PAID**

**H4- RECEIVER R.3601.**—Comprises of two individually-built chassis, hinged at one end to allow the two sections to be closed together. One chassis comprises of an R.F. stage, Mixer, and Oscillator, 3/EF50's, followed by a 45 Mc/s I.F. strip employing 5 VT65 (SP61's) and an EA6.

The remaining section is built up with the "following" stages of the R.F. deck, E.H.T. and H.T. power packs (high frequency primary transformers), a 24v. D.C. motor and antenna sweep switch assembly, together with various condensers, etc.

The two sections hinge together as one unit and is enclosed in a metal retainer, 18in. x 9in. x 8in., finished in R.A.F. blue. **CLYDESDALE'S PRICE ONLY £4. 12. 6 CARRIAGE PAID**

### FOR EXPORT ONLY

Brand new WIRELESS SET No. 38 Mk. 2. Transmitter/Receiver for portable use on 7.4 to 9 Mc/s. Complete with all accessories. PLEASE ENQUIRE FOR DETAILS, PRICE, ETC., QUOTING H.519.

**EX-R.A.F. R.3547.** comprises of a chassis of remarkable breakdown value, and comprises of a 24-volt D.C. reversible motor, 700 : 1 gear box, sweep switching unit, relays, over 100 various resistors, 50 Mica condensers, 11 potentiometers and numerous included components.

Enclosed in the chassis is a 45 Mc/s I.F. strip employing EF30's and a total of 23 valves, i.e., 15 EF50's, 3 EB34's, 2 EF36's, 2 V8T2's, 1 EA50.

Complete unit is housed in a metal box 18in. x 13in. x 7 1/2in., finished in black.

**CLYDESDALE'S PRICE ONLY £5. 19. 6 CARRIAGE PAID**

**U.H.F. TRANSMITTER.**—JEFFERSON-TRAVIS U.F.-2. This unit consists of a 3-valve trans-receiver chassis, which is complete except for the tuning inductance, and one or two connections to the amplifier valve. The original unit operated on approx. 70 Mc/s. The transmit receive side of the unit has been left untouched with all transformers, valve holders and relative components in place but less valves, original valves were 2 8Y7's and a 12J5.

The U.F.-2 consists of two units mounted by means of their front panels—one contains the R.F. tuning control, T/R switch and V control with the antenna insulation feeding through the panel. The second panel mounts a 3in. P.M. speaker, telephone handset jack and change-over switch. Both panels are "silver" finished, measuring 8in. x 7in.

Complete U.F.-2 is housed in a black crackle cabinet approx. 19 1/2in. x 15in. x 7in., fitted with handles.

**CLYDESDALE'S PRICE ONLY 50/- each CARRIAGE PAID**

**V.H.F. TRANSMITTER.**—H517-85-96 Mc/s 'Phone transmitter by STRATTON. This transmitter is extremely suitable for "144" modifications and consists of a 6V6 crystal oscillator stage (9 Mc/s plus) RK34 multiplier stages and RK34 final. Speech and modulation by two 6AV7's.

The unit is practically complete except for valves—there has been one or two of the inductances removed, but these would need to be replaced in any case for 2 metre operation. Complete in die-cast mounting with louvred cover, 14in. x 8in. x 7in., finished in grey.

**CLYDESDALE'S PRICE ONLY 27/6 CARRIAGE PAID**

Circuit details will soon be available, also details of a suitable power pack.

Order direct from:

## CLYDESDALE SUPPLY CO. LTD.

2, Bridge St., Glasgow, C.5. Phone: SOUTH 2706/96  
Visit our Branches in Scotland, England and N. Ireland.

## BUILD YOUR OWN MODERN RECEIVER for HALF the normal cost

You're **SURE** to get it at  
**STERN'S**  
ESTABLISHED 25 YEARS

## SOME POPULAR CIRCUITS for the HOME CONSTRUCTOR

★ **A MIDGET 4 STATION "PRE-SET" SUPERHET. RECEIVER**, for A.C. mains. Designed to receive any three stations on Medium Waveband and one on Long Wave by the turn of a Rotary Switch, no Tuning being necessary. The set can be supplied either as a complete Kit of Parts, or by purchase of the Components separately. The Complete Assembly Instructions, showing the Wiring Diagram and Component Layout and Point to Point connections, together with a Component Price List, available for 1/9.

★ **A 4-VALVE T.R.F. BATTERY PORTABLE "PERSONAL" SET**, available as a Complete Kit of Parts or by purchase of the Components separately. The complete price details, including an individual Component Price List, are included in our set of Assembly Instructions, which is obtainable for 9d. In addition, these detailed Assembly Instructions also show the complete circuit, with a Practical Component Layout, which in themselves make the assembly of the set quite simple.

★ **A MIDGET 4-VALVE SUPERHET. PERSONAL SET**, covering Long and Medium Wavebands and designed for Mains or Battery operation. This receiver is designed to operate on A.C. mains or by an "All-dry" Battery; either method is selected by means of a Rotary Switch. It is so designed that the Mains Section is supplied as a separate section which may be incorporated at any time. The set, therefore, can be made either as an "All-dry" Battery Personal set or as a Midget Receiver for Combined Mains/Battery operation. The set can be supplied either as a complete Kit of Parts or by purchase of the Components separately. The Assembly Instructions, which include Wiring Diagram and Practical Component Layouts, are available for 1/9. This also includes a separate Component Price List.

★ **THE MIDGET A.C. MAINS 3-VALVE RECEIVER**, as designed and published by "Wireless World," covering Long and Medium Wavebands. Cost of all Components to build this set is £4 17/9. A reprint of the complete Assembly Instructions, including Practical Layouts, is available for 9d.

★ **THE "WIRELESS WORLD" MIDGET A.C. MAINS 2-VALVE RECEIVER**. We can supply all the components, including Valves and M/Coil Speaker, to build this set for £3/10/0. Reprint of the original Assembly Instructions and Circuit may be obtained for 9d.

★ Complete Assembly Instructions, showing how to build a **3-VALVE (plus Rectifier) T.R.F. RECEIVER** for operation on A.C. or D.C. Mains. Price 9d.

★ **A COMPLETE KIT OF PARTS** to build a MIDGET "All-dry" BATTERY ELIMINATOR, giving approx. 69 volts and 1.4 volts. This eliminator is suitable for use with any 4-valve Superhet. Personal Set requiring approx. 70 to 85 volts. It is easily and quickly assembled and is housed in a case size 4 1/2 in. x 1 1/2 in. x 3 1/2 in. It can therefore be accommodated in most makes of Personal Sets. Price of Complete Kit, 42/6.

★ For 25/17/9. A Complete Kit of Parts, including Drilled Chassis and Valves, to build a 6 to 8 watt **PUSH-PULL AMPLIFIER** for operation on A.C. Mains. Incorporates Tone Control and is suitable for use with any type of pick-up. The complete set of Assembly Circuits, including Practical Layouts, is available for 9d.

★ An entirely complete **3-VALVE AMPLIFIER KIT OF PARTS** for £4/12/6. Has a max. output of 3 1/2 watts, with valve line up of 25A6, 6J7 and U3L. Includes matched 6 1/2 in. FM Speaker and Drilled Chassis.

★ Send 9d. P.O. for our **NEW STOCK LIST**, showing many **KITS OF PARTS** for Sets and Battery Chargers and "hundreds" of Wireless Components. When ordering please cover cost of postage and packing.

**STERN RADIO LTD., 109 & 115, FLEET STREET, E.C.4.**

Telephone:  
CENTRAL 5814 & 2280

## NOW AVAILABLE GERMANIUM CRYSTAL DIODES

LATEST, SMALLEST  
SUPREME CRYSTAL DETECTOR.

Midget Size, 5 1/16 in. x 3 1/16 in.  
Wire Ends for Easy Fixing.  
4/6 each, postage 2 1/2 d.

Wiring instructions for a cheap, simple but high quality Crystal Set included. Technical Details and Selected Types available.

**SILICON CRYSTAL VALVE**  
3/6 each, postage 2 1/2 d.  
Fixing Brackets 3d. Extra


**COPPER INSTRUMENT WIRE**  
ENAMELLED, TINNED, LITZ,  
COTTON AND SILK COVERED.  
Most gauges available.  
B.A. SCREWS, NUTS, WASHERS,  
soldering tags, eyelets and rivets.  
EBONITE AND BAKELITE PANELS  
TUFNOL ROD, PAXOLIN TYPE COIL  
FORMERS AND TUBES.  
ALL DIAMETERS.

Latest Radio Publications.  
SEND STAMP FOR LISTS.

**CRYSTAL SET**  
INCORPORATING THE SILICON  
CRYSTAL VALVE

Adjustable Iron Cored Coil.

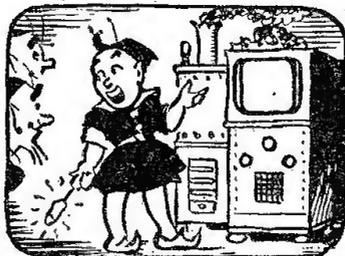**RECEPTION GUARANTEED**  
Polished wood cabinet, 15/-, post 9d.  
A REAL CRYSTAL SET, NOT A TOY.  
**POST RADIO SUPPLIES**  
33 Bourne Gardens, London, E.4



The "Fluxite Quins" at Work

"Here's the last word in sets. It's supreme!  
And made from odd bits. It's a dream!  
Every wire soldered right,  
Of course, with FLUXITE.  
Power cuts? No—it's driven by steam!"

See that **FLUXITE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, from 1/- upwards. The **FLUXITE GUN** puts **FLUXITE** where you want it by a simple pressure. Price 2/6, or filled 3/6.

# FLUXITE

**SIMPLIFIES ALL SOLDERING**

Write for Book on the Art of "SOFT" Soldering and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with **FLUXITE**. Price 1d. each.

**FLUXITE Ltd., Dept. W.P.**  
Bermundsey Street, London, S.E.1.

## MIDLAND INSTRUMENT CO.

A FEW ITEMS FROM OUR  
NEW LISTS:

Mains A.C./D.C. and capacitor motors. Large range of L.T. motors. Rotary converters and alternators. Microphones, carbon and moving-coil throat, etc. Headphones. Cables and flexes, telephone wires. H.T. and L.T. rectifiers. Radio and multiple L.T., etc., transformers. Valveholders. Neon lamps. Switches. Telephones and associated equipments. Relays and selector mechanisms. Burglar and fire-alarms. Micro switches. Thermostats. Flexible drives. Gears and couplers. Counters. Bombsight computers and predictors. Plugs and sockets. Motor generators. Fuseholders and fuses. Press-button and control units. Dinghy masts. Crystal valves. Motor blowers. Accumulators. Amplifiers. Compressor air reservoirs. 45 mc/s I.F. strips. Electric time clocks. Loudspeakers. Terminal blocks, etc., etc.

Send stamped, addressed envelope (not too small) for a copy.

**MIDLAND INSTRUMENT CO.,**  
MOORPOOL CIRCLE,  
BIRMINGHAM, 17.  
Tel.: HAR 1308 or 2664

# Programme Pointers

This Month MAURICE REEVE Deals with Some Recent Programmes

**L**ET us leave plays till later, this month. I will start, as usual, with two grumbles. One an old one—studio audiences. I feel no qualms about this question as almost the entire national press condemns them root and branch. They give the impression that a considerable number of very idle people are in permanent session, somewhere or other, all marshalled up and awaiting the sergeant instructor's orders to beat hands together, with a cheer leader every here and there to whistle, fingers in mouth. Exactly the same volume and type of applause is meted out to every show. Whether it is 10 a.m. or 10 p.m., Home or Light, or a series of shows one after the other; there they are, hour after hour, all present and correct right down to the woman with the hen-rooster's laugh, right under the mike. It's terrible.

The other point is the pronunciation of certain foreign proper names and surnames. If a French announcer has to utter the names of "Elgar," "Sir Thomas Beecham," or "London" or "England," he does so as he would normally pronounce them as an ordinary Frenchman. And good enough it is. But not so for our people. The most frightful splutterings and gurglings go on when, in particular, Debussy, Ravel, and Monsieur Vincent Auriol are mentioned. I invariably make for my handkerchief when I hear Debussy's name—DAY-BUUES-SSSSSE—an incredible number of Ss; I feel spattered all over. Whilst I am certain RAVEL would have beaten G. B. S.'s 40-vowel alphabet as pronounced by most. Some of the announcers must get tied up in knots with their mikes.

## Gieseking

And so to programmes. I heard that most distinguished pianist, Gieseking, play what are perhaps the two greatest of all concertos, Beethoven's "Emperor" and Mozart's in A, K488. The former the most sublime, magnificent, noble, lofty, whilst the Mozart is the most enchantingly, ravishingly and entrancingly beautiful. The Beethoven is the greater because it possesses Mozart's as well as its own qualities. Between the two of them they left nothing for Tchaikowsky, Rachmaninov or even Brahms to say. Gieseking was perfect in the Mozart and the second and third movements of the Beethoven. But the first part of the "Emperor" sounded strangely cold and rushed.

Mozart's Mass in C Minor and the "Jupiter" symphony made a glorious programme at the B.B.C. symphony concert, under Beecham. The over-worked orchestra has played better, but the combination was irresistible.

## Memories

Arthur Askey and Kenneth Horne gave a very funny half hour of Band Wagon memories. It served to prove what a long way behind these old masterpieces the current variety programmes have fallen.


## "We Beg to Differ"

A much-anticipated and looked-forward-to event was "We Beg to Differ" with, excepting the genial chairman, Roy Plumley, an entirely new cast. To wit, Margaret Rawlings, Margaret Lindsay, Helga Moray, Athene Seyler, Griffith Jones and Robert Henriques. I found it entirely satisfactory and delightful. Naturally, we do not like to part with old friends, especially when they have served us as well and faithfully as the old cast did. But there can be no doubt that it is the only way to keep these regular features vital and fresh. Perhaps a change of individuals, as with the critics, with return, at intervals, of everybody, is the best way. We would all enjoy meeting the others again, after they have had a break.

## Clogging Narrators

The narrators in the Sunday evening serials are clogs in the machine, if ever there were clogs. Mr. Chapman and Mr. Hall—the original publishers of the Pickwick Papers—and the two narrators in the current serial of that immortal masterpiece, are, to put it mildly, blithering nuisances; worse, even, than "Mr. Thackeray" was in Vanity Fair. There is enough material for fifty-seven—let alone seven—thirty-minute instalments. Why waste half the precious time over two old sanctimonious

## PROFESSOR BOFFIN

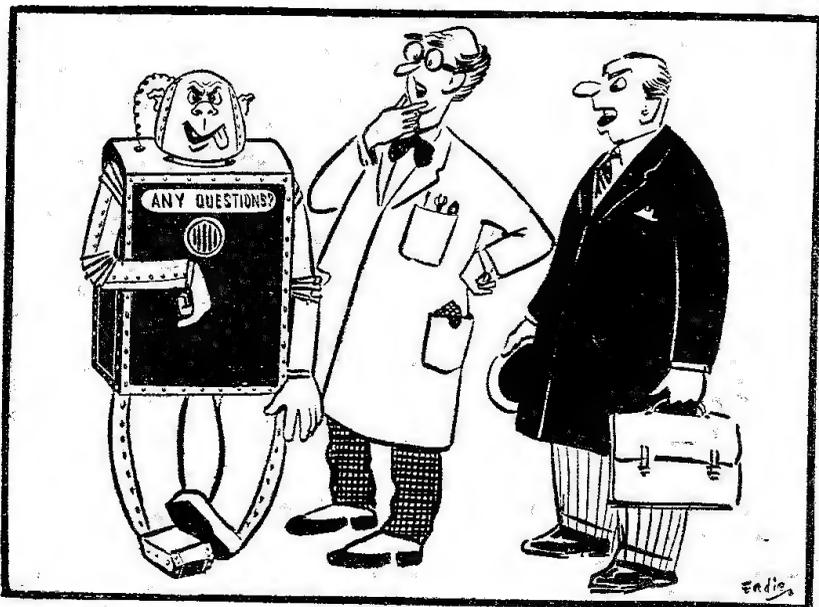

"I'm afraid your information robot for the Festival has slipped up somewhere between drawing-board and production, Boffin!"

so-and-so's trying to claim the credit for what was entirely and completely Dickens's.

### Plays

Of the month's plays, two were unquestioned and proclaimed masterpieces. Shaw's "Heartbreak House" and O'Casey's "Juno and the Paycock." Although so different in many respects, the racial relationship of the two authors is plain for all to see. Captain Jack Boyle, Captain Shotover and, to go back a mere two hundred years, Captain Lismahago are brothers under the skin. And Irish, too, begorrah. It would be fascinating in the extreme to see "Juno" and "John Bull's Other Island" in equally close juxtaposition.

Most of Shaw's prefaces are as good as his plays. That to "Heartbreak House" probably greater, and the greatest of all. I would suggest that, in all future productions of Shaw plays, they be read and made to appear as—what they really are—part and parcel of the whole. Distinguished casts fully realised the greatness of their material.

"Cæsar's Friend" was an interesting dramatisation of the Crucifixion story. "Background" dealt with the evil effects suffered by children when parents divorce. "Love and Mr. Arkwright" proved the wisdom of the old adages that a fool and his money/heart soon part, and there's no fool like an old fool. "Housemaster" was another silly and unreal school story in which the gifts of Jack Hulbert were completely lost. The others were all good.

### Serials

Should Sunday evening serials have a narrator? My own view is, emphatically no, or very, very, sparingly. In "Vanity Fair" and the recent "Pickwick Papers" I thought they stifled and clogged the pace of the story-telling horribly and most unnecessarily. The amount of "Pickwick" material—there were only, I think, eight instalments—might probably have been nearly doubled but for the twaddle of "Messrs. Chapman and Hall," to the benefit of all concerned.

The idea of devoting the whole of the Third Programme to events and items which took place in the year of "the" great exhibition—1851—was, on the whole, a great success. The music performed was that actually being played that year. The speakers, the best thing in the week, I thought, were those people who would undoubtedly have been "brought to the microphone" had microphones then been in use. And there were talks and descriptions of events of that year such as the exhibition itself, the *coup d'état* of Napoleon III, and, best of all, life among the London poor. News bulletins of the period were a feature.

The music was the least satisfactory. The masterpieces, up to and including Beethoven, were, of course, what we hear almost every day of the year. Without the presentation of them, both as to standards of performance and the visual aspect, they afforded little or no interest. The remainder were only fit for where they have lain ever since—and will doubtless lie till 2051—the rubbish basket. But they at least served to, at any rate, partially answer the vexed question why do we get so much Beethoven, etc., in our concert

programmes by proving that there is little else worth listening to.

### Chopin's Piano

It was a mistake to give piano recitals on Chopin's piano, as it only served to create the impression that that great composer-pianist played on an old bone-shaker of a tin-lizzie Ford, which is all it sounds like to-day. It was rather like christening a new baby in great-great-great-grandmother's christening robe—a sop to sentimentality.

It was strange, and sinister, that, no sooner was the ink dry of my praise of Gilbert Harding as the questionmaster in "Twenty Questions" than he was removed from that and other programmes. Poor Gilbert, "live" mikes have been unkind to many others, though that one dealt you a particularly scurvy blow.

The acoustics of the Royal Festival Hall were heard over the air for the first time in the concerts which helped to launch the Festival of Britain. They are not perfect, especially with strings. Percussion sounded very brilliant, whilst I have never heard such dazzling virtuosity in applause. One could almost count three thousand odd individual, separate hand-clappers. Perhaps we are entering on an age of great applauders.

### The Police Force

"... like any other Bobby," a dramatised impression of provincial police forces at work was a pleasant feature, an hour in length, about a body of men who go about their duties in the best possible way—quietly and unostentatiously, and who are, therefore, universally liked and respected. The programme, which was made with the co-operation of the Chief Constables of Devon and Plymouth, was built up round the escape of a convict from Dartmoor and his subsequent capture in a Torquay cinema. It had a refreshing air of reality as being something near to us in our ordinary daily comings and goings. The stories of shipwreck, mine disaster or earthquake cannot, of course, claim this quality, though they may be more stirring and dramatic in consequence. A good cast was headed by Paul Rogers as narrator.

A point in the story caused me the greatest astonishment, and caused me to ponder over such things as the "British Way of Life," etc. The convict, who must, by all standards, have looked a tough customer, sought, and obtained, asylum by hiring a room, early one morning, in a Torquay boarding house. When he is arrested in the cinema the same afternoon, in whose company should he be but that of the small daughter, a school child, of the woman owning the establishment! When the police first called there she gave them a full description of both her daughter and the man, so she was obviously fully aware of the fact that her child had "gone out" in the company of this perfectly strange, and doubtless unkempt, man. Is there any wonder that our children and young people meet with sticky ends?

### Gladys Young's Jubilee

Gladys Young's jubilee of broadcasting was properly honoured by casting her in the title role of St. John Ervine's brilliant "The First Mrs. Fraser." She gave a very accomplished performance.



**"DEMOBBED VALVES"**

**MANUAL**

2/9

Post free

giving Equivalents of British and American service Types and Cross Reference of Commercial Types, with an Appendix of B.V.A. Equivalents and comprehensive Price List. (Some prices are PRE-BUDGET.)

**SPECIAL OFFER :**

- ATP4, 6/-, PM22A, 7/6, 6K7, 8/6, 6SC7, 9/9, 6AB7, 10/-, 1R5, 10/6.
- EX-GOVN. HEADPHONES**, 60 ohms (limited quantity), 7/6, post 1/6.
- CRYSTAL SETS**, luxury model, 16/6, post 1/6.
- CRYSTAL SET KITS**, with diagram, 11/3, Post 1/6.
- AERIALS**, insulated copper, 50ft., 3/3; 75ft., 4/9; 100ft., 6/-.
- JUNEERO Engraving Tool** for Metal, Plastics, etc. A.C. model, 12/6, post 1/6.
- JUNEERO** multi-purpose tool for bending, cutting, punching, slotting, etc., 20/-, post 2/-.
- With "XAKTO" slide gauge, 27/6.
- HANDY-UTILITY** electric drill (4in.), £3 10/0, carr. 3/-.
- Bench Stand, 59/6; Horizontal Stand, 17/6, carr. extra.
- TAYLOR ON EASY TERMS.**
- EASY TERMS** up to 10 months—and very near Cash Price on all **TAYLOR METERS.** Catalogue **FREE.**

- Taylor 240A Pattern Gen.
- 30A Oscilloscope.
- 47AS Valve Tester.
- 260A Wobbulator.
- 70A Multi-range Meter.
- 75A Multi-range Meter.
- 85AP Multi-range Meter.
- 110B Bridge.
- 170A Electronic Test.
- Meter and the complete range.

**AMPLION TEST METER**, 1,800 ohm per volt on all D.C. and A.C. ranges, 10 v., 100 v., and 500 v., D.C. and A.C., 50 mA. and 500 mA. D.C. Resistance up to 200,000 ohm. (3,000 ohm. centre scale), with self-contained battery, 5,000 v. range, with a separate H.T. test prod. (9/6 extra). Supplied with test prods. Multi-colour scale easily readable, £47/6.

**AV-MINOR UNIVERSAL METERS £10.**

**CONDENSER TESTERS** and Rectifier Units. Plugs straight into A.C. mains, 200/240 v. and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete 39/6.

**SERVICE SHEETS**, the one you require on **FREE** loan if you buy one dozen assorted at 10/6.

**3/16in. DIA. BIT SOLDERING INSTRUMENT**, Miniature Type, to meet every requirement for Radio, Television, etc., 22/6, post 1/6.

**SOLON PENCIL BIT SOLDERING IRON**, 65 w., 230-250 v., 21/-, post 1/6.

**MORSE BUZZER OUTFITS**, Consisting of a buzzer, a morse key and a battery compartment, all mounted on a polished base board. All parts high-grade ex-Air Ministry. An excellent gift for a boy. 6/-, post free.

Goods can be sent C.O.D. (over 20/-). Kindly mark envelope (PW7).

**RADIO BULLS VALVES**  
246, HIGH ST., HARLESDEEN, N.W.10

**Cabinets of Distinction...**

Catalogue available on request.

**Chassis**

A.C., 5-valve 3 w/b Superhet Radiogram chassis. Absolutely complete kit of parts, including wiring diagram .. **£10.10.0**  
Or fully wired and tested .. **£12.5.0**

**Amplifiers**

Four to fifteen watts output. Wired, or in kit form, from .. **£3.19.6**  
Full details of above available on request.

**LEWIS RADIO CO.**

(Dept. K.10), 322, HIGH ROAD, WOOD GREEN, LONDON, N.22.  
Telephone-BOWes Park 5997

**DUKE & CO.**

**SPEAKERS**, 2in. and 3in. New, complete with transformer, 13/6. Also new but slightly damaged, 12/6. Same size speaker less transf., 13/6.

**CRYSTAL SETS**. In round bakelite cabinet, complete, reception guaranteed, 9/9. Full instructions. Also Luxury model in attractive oblong bakelite cabinet, 16/6 plus 1/- post. With Germanium Crystal.

**PHONES**. Single head sets, 1/9. Double head sets, 3/9. Tannoy phones, 8/6. Plus post.

**TRANSFORMERS**. O.P. Standard, 4/9. Tropicalised, 3/9 each.

**CHOKES**. Bulgin, 50 m/a, 1,000 ohms, 30 henries, 10/- each.

**CHOKES**. Midget, 50 m/amp., 300 ohms, 10 henries, 4 for 5/-.

**"SOLON" SOLDERING IRONS**. Pencil bit, 15/-.

Half to-day's price. 110 v. fit element for 230 v.

**T.V. LENSES**. Still limited supplies. 12in., 75/- clear; 8in., 9in., or 10in., 55/-.

Post 1/6.

**METAL RECTIFIERS**, 360 v., 150 m/a., half wave, 7in. x 14in. dia., 7/6 each.

**TOGGLE SWITCHES**. Single, double or rotary type single, 1/6 each.

**BEDSIDE RADIO KIT**. In bakelite cabinet, 4 valve T.R.F. Universal or A.C. for only £4.15.6. In ivory cabinet, 6/- extra. Or assembled, 35/- extra. New and improved circuits. An amateur can build this set, with practically no knowledge. The ONLY set now available at this price. Post and packing, 2/6.

**VALVES**. NEW. Old Tax (half rate), EL33, CL33, 6V6 at 13/-; AZ31, 5Z4, at 10/6; 6Q7 at 12/-.

Plus P.T.

**50 yd. SPOOLS OF NI-CHROME**. .014 wire for only 2/-, or 25 yds. .032 same price. These bargains are a fraction of to-day's price (if you can buy it), postage extra.

**EX-MILITARY BOAT**. Inflatable, 13ft. New. In two packing cases, including all accessories. Bargain 6 gns. plus carr. (shoulder pack).  
Money back guarantee. Please send cash with order, or C.O.D. post.

219, ILFORD LANE, ILFORD, ESSEX  
ILFord 0295. Stamps ONLY for lists.

**£7 19s. 6d.**

for a first-class **COMMUNICATIONS RECEIVER**. This is the famous ex-R.A.F. type R 1155, which is justly known as being a really tip-top set. Covers 5 wave ranges, 18.5-7.5 mc/s., 7.5-3.0 mc/s., 1,500-600 kc/s., 500-200 kc/s., 200-75 kc/s., and is easily and simply adapted for normal mains use, full details being supplied. These receivers have had some use, but are in very good condition, and are all aerial tested and guaranteed in working order before despatch. Please remit 10/- extra for packing and carriage on post orders.

**INDICATOR UNIT TYPE 6**. The very popular indicator unit which is recommended for so many uses, and in particular for conversion to the "Wireless World General Purpose Oscilloscope." Contains a 6in. C.R. Tube type VCR97, 4 valves EF50, and 3 of EB34. BRAND NEW IN MAKERS' CRATES. Only 79/6 (carriage 7/6). Constructional data as above supplied free with each unit, or available 9d. The following components required for the conversion are also available: EHT TRANSFORMER FOR VCR97, 32/6 (postage 1/6), 4v. EHT RECTIFIER with ceramic base 8/6 (post 9d.), 20h. 80 m.a. CHOKES, 6/6 (post 9d.).

**BATTERY SUPERSEDER**. A "must have" for everyone dependent on H.T. Batteries. Operates from a 2-volt accumulator, and delivers 67 volts at 4.7 m.a., 130 volts at 13-25 m.a., and 1.4 volts L.T. This is a first-class American made vibrator unit, and is easily modified for use with any set, fully illustrated details being supplied. For the few coppers cost of charging an accumulator constant H.T. is derived, and the initial outlay is soon regained in saving on batteries. Only 60/- (postage 1/6) or with two 2-volt accumulators in metal case 90/- (carriage, etc., 5/-).

**"PYE" 45 M.C.S. I.F. STRIP**. Ready made for the London vision channel, this 5-stage strip contains 6 valves EF50 and 1 EA50. Circuits and simple mod. data supplied. BRAND NEW. Only 60/- (postage etc., 2/6). Less valves, 37/6 (plus postage 2/6).

**10 VALVE 1 1/2 METRE SUPERHET ZC 8931**. The ideal receiver for long distance TV results. The valve line up is 6 of VR65, 2 of VR92 and 1 each VR136 and VR137, and the 12 mc/s. 6 stage I.F. Strip gives tremendous amplification with ample bandwidth of 4 mc/s. Easily modified, full details being supplied. BRAND NEW IN MAKERS' CARTONS. Only 59/6 (carriage 5/-).

**R.1355 RECEIVER**. The unit specified for "Inexpensive Television." Complete with 8 valves VR65, and 1 each 5U4G, VU120, VR92, and a copy of the book, BRAND NEW. Only 55/- (carriage, etc., 7/6).

**194 I.F. STRIP**. Another strip easily modified for TV. Contains 6 valves VR65, and 1 each VR53 and VR92. This 6-stage strip measures only 16in. x 5in. x 5in., and is particularly recommended for constructors who have built televisions but are having trouble in the vision or sound receivers. Full modification data supplied. BRAND NEW. Only 45/- (postage, etc., 2/6).

**INDICATOR UNIT TYPE 184A**. Contains two C.R. Tubes, a 6in. VCR517 and a 3in. VCR139, 5 valves EF50, 3 of EB34, 3 of SP61, and 5 diodes EA50. Only 75/- (carriage, etc., 12/6).

**OSMOR MIDGET COIL PACK TYPE H.O.** Covers S, M, and L waves, and is complete with full circuits for 465 kc/s. superhet. unit. Limited quantity only available at pre-budget P.T. rates. Only 40/4 (postage 8d.).

**3in. VITAVOX P.M. SPEAKER**. A really beautiful job, incorporating an aluminium cone which gives better response and volume. IN SEALED MAKERS' CARTONS. Only 11/9 (postage 9d.).

Cash with order please, and print name and address clearly. Amounts given for carriage refer to inland only.

**U.E.I. CORPORATION**  
The Radio Corner

138 Grays Inn Rd., LONDON, W.C.1  
(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Stn.) and 5 mins. by bus from King's Cross.)

## MODERN ELECTRICS LTD.

Decca 3-speed A.C. gram units, complete . . . £7 3s. 4d.  
 Dual PICK-UPS for above, for L.P. and standard recordings . . . £3 19s. 2d.  
 Cosmocord G.P.20—we still have a small stock of these famous PICK-UPS, price . . . £3 11s. 5d.  
 G.P.19 Spare Heads—L.P. and standard for the above £2 3s. 4d.  
 GARRARD, PLUG-IN type HEADS, for 65A and 70A.  
 GARRARD ADAPTORS to convert older models.

Recording TAPE, by E.M.I. and SOUNDMIRROR, price £1 5s. 0d.

Recording TAPE, by G.E.C. £1 10s. 0d.

Recording TAPE, by DUREX £1 15s. 0d.

(per 1,200ft. reel.)

Just released—"MAGNETIC RECORDING," by Chief Engineer, Brush Development Co. The most comprehensive publication on Tape and Wire recording. 26/- post free.

## MODERN ELECTRICS LTD.

164, Charing Cross Rd., W.C.2  
 TEMPLE BAR 7587.

Export enquiries welcomed.

### Something for you!

**MOTOR PUMPS** for Table Decoration, battery model, bakelite body fitted motor, switch, battery holder, taking two U2 cells covered with Chrom. plated dome, jet and spray attachments. A filter fitted in base. Mounted on rubber feet for submersion in water in table bowl, unused, £2/15/-. A.C. model for use through Transformer from 230 volt A.C. main, 57/6.

**MOTOR D.C.** 110 volt,  $\frac{1}{2}$ H.P., 1,400 r.p.m. A.E.G., 25/-, post 2/-. 80 volt,  $\frac{1}{6}$ H.P., 2,000 r.p.m. G.E.C., 85/-.

**MOTOR BLOWERS.** Small 24 volt for valve cooling, etc. Enclosed D.C. Motor fitted blower, with  $\frac{1}{2}$ in. x  $\frac{3}{4}$ in. outlet, 21/-, post 2/-. 200/225 volt A.C. Motor Blower, 40 cu. ft. per min., 10in. water gauge, £16/10/-. carr. extra.

**HEATER ELEMENTS.** 24 volts, 75 watts, flat copper plate with insulated connector fitted one end. 4in. x 2in. x  $\frac{3}{8}$ in. thick. Useful for soil heating, 1/6 each.

**HAND MIKES.** No. 3 double-button type with Switch in handle, 6/6. Post 1/-. G.P.O. in bakelite case, fitted carbon inset, 3/6, post 9d.

**RESISTANCES.** Variable, wire wound double tube, 152 ohms, 2 amps. New and boxed, 30/-. Single tube, 5 ohms 10 amps., 21/-; 300 ohms  $\frac{1}{2}$  amp., 15/-. Small rotary, 10 ohms 1 amp., 2/6, post 6d.

**CRYSTAL SETS.** The Lesdix Festival Model, wound tuning coil, var. cond., ever-set diode Detector, special 'phone Transformer with plug-socket. All fitted in black bakelite case and supplied with pair headphones sensitive to crystal reception. With headband, cord and plug. All serial tested, 30/-, post 1/6.

## ELECTRADIX RADIOS

214, Queenstown Road, Battersea, London, S.W.8

Telephone: MACaulay 2159

## LONDON CENTRAL RADIO STORES

**PHILCO 5-VALVE RECEIVER.** Superhet, long and medium wavebands, A.C. or A.C./D.C. 200-250 volt mains energised Speaker in Walnut cabinet, slightly soiled. 90/- plus 7/6 carriage and packing.

Owing to purchase of large consignment we can still supply at prices quoted.

**WALKIE TALKIE (Transmitter and Receiver).** Type 38 Mk. II, range 7.4 to 9 Mc/s. Requires 3 v. L.T. 120-150 H.T. in working order. Complete with 4 ARP, one APT4 valves, 1 pair throat mikes, 1 pair headphones and aerial. In metal case, diagram with each set Free. Batteries not supplied, but obtainable from local radio dealers, £3.8.6. carriage and packing 2/6.

**2-VOLT VIBRATORS.** Type R76C, 7-Pin Self-Rectifying, 200 volt at 60 mA., made by Electronic Laboratories Inc., 7/6.

**12-VOLT VIBRATOR,** Mallory, Type G629C. American base, 7/6.

**NEW NIFE ACCUMULATORS,** 2.5v. 2 $\frac{1}{2}$  amp., for 8 hours. Size 3in. x 4 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. Flat, 6/6.

**MAP READING TORCH.** Magnifying lens, 3in. diameter, in bakelite case, with dimmer switch. Takes two U.2. batteries, 22/6, less batteries.

**EVERLASTING NEW INERT CELL ACCUMULATORS.** No acid or charging required; great many uses for them. 1.5 volts. Size 2in. x 2in. x 5 $\frac{1}{2}$ in., 2/9 each; 3 for 7/6.

**EX - ADMIRALTY PHOSPHOR BRONZE AERIAL WIRE.** 100ft. on drums, 5/6.

**NEW 1/30 H.P. A.C./D.C. DOUBLE-ENDED SPINDLE MOTORS.** Size 5 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in., 200-230 volts, 37/6; packing and carriage 2/6.

**5-WAY V.I.R. FLEX CABLE,** 6/6 12 yds.

**VOLT METERS.** Centre zero, 0.3 and 0.30 D.C., 17/6.

**12 v. 3 amp. METAL RECTIFIERS,** 15/-; 1/6 post, etc.

**METAL RECTIFIERS, H.T. 10., 15/-;** 1/6 post, etc.

**SELF ENERGISING TABLE MIKE** and pair headphones, 14/6.

**BUBBLE SEXTANTS Mk.9A.** Equal to new, 45/-. Mk.9, 35/-.

**NEW SIMPSON OHMMETER.** 0-5,000 size 4 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in., 57/6.

**MILLIAMM METERS,** centre zone 0-15 D.C., 17/6.

**MOVING COIL TABLE MICROPHONE** and headset, 12/6, postage 1/2.

**MICROPHONE,** moving coil. 30 ohms, 5/6, postage 1/-.

**PEDESTAL TABLE MICROPHONE,** 7/6, postage 1/-.

WE DO NOT ISSUE LISTS.

Carriage charges relate to British Isles only.

23, LISLE STREET, W.C.2

Telephone: GERrard 2969.

## THE MODERN BOOK CO.

Radio Circuits, by W. E. Miller. 5s. Postage 4d.

The Radio Amateur's Handbook—1951 edition, by A. R. R. L. 22s. 6d. Postage 10d.

Television Receiving Equipment, by W. T. Cocking. 18s. Postage 9d.

Practical Wireless Service Manual, by F. J. Camm. 8s. 6d. Postage 6d.

Sound Reproduction, by G. A. Briggs. 10s. 6d. Postage 6d.

Time Bases, by O. S. Puckle. 30s. Postage 10d.

Magnetic Tape Recording, by P. A. Tarry. 6s. 6d. Postage 4d.

Practical Wireless Encyclopaedia, by F. J. Camm. 21s. Postage 10d.

Radio Servicing—Theory and Practice, by A. Marcus. 35s. Postage 1s.

Outline of Radio, by H. E. Penrose. 21s. Postage 10d.

Inexpensive Television for the Home Constructor. 2s. 6d. Postage 2d.

Electronic Musical Instruments, by S. K. Lewer. 3s. 6d. Postage 3d.

Mullard's Valve and Service Reference Manual. 5s. Postage 4d.

Brimar Radio Valve and Teletube Manual. 4s. Postage 3d.

Ediswan Mazda Valves, 1949-50. 2s. Postage 3d.

Guide to Broadcasting Stations, by "Wireless World." 1s. 6d. Postage 2d.

We have the finest selection of British and American radio books in the Country. Complete lists on application.

19-23, PRAED STREET,  
(Dept. P.7)

LONDON, W.2.

PADDINGTON 4185.

2 VOLT BATTERY SUPER-HET. 6-9 mcs. Chassis taken from the No. 18 Tx/Rx. Tested and ready for use. 32/- Chassis less valves, contains 2 465 kc. Trans., 7/6.

New IN34 CRYSTAL DIODES, 5/6.

METERS. M/c 0-300v. 2in., 10/-. 0-40v. 7/6. 0-500 micro amp., 11/-.

MULTIMETERS. 2 $\frac{1}{2}$ in. Supplied as kit with black bakelite cases, 6 x 4 $\frac{1}{2}$  x 1 $\frac{1}{2}$ in. and resistors for D.C. ranges 0-3, 0-30, 0-150, 0-300, 0-600v., and 60in. A. Scale also reads OHMS 0-5,000 with 1 $\frac{1}{2}$ v. battery, 17/6.

MOVING COIL MICROPHONES with switch, 6/6. Trans to match, 5/-.

New 12in. ULTRA ELLIPTICAL ENERGISED SPEAKER with transformer. 400 ohm field. 10 watt. 26/6.

24v. AC/DC MOTORS 5 x 3in. fitted with powerful blower fan, 14/-.

R.C.A. 100 kc CRYSTALS. First Grade, 25/6.

230/240v. AC/DC MOTORS  $\frac{5}{16}$ in. spindle each end.  $\frac{1}{16}$  HP. 5 $\frac{1}{2}$  x 3 $\frac{1}{2}$ in. 26/6, or fitted with 2 $\frac{1}{2}$ in. grindstone 32/-.

ARMY CARBON MICROPHONE with switch, 4/6. Trans to match, 3/6.

TRANSFORMERS, 200-240 volts. Tapped 3-4-5-6-8-9-10-12-15-18-20-24 volts at 2 amps. 21/- Post Paid.

All Carriage Paid. Money back Guarantee from—

## THE RADIO & ELECTRICAL MART

253b, Portobello Road, London, W.11.  
 Phone: Park 6026.

# OPEN TO DISCUSSION



The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## P.A. for the Amateur

SIR,—With reference to Mr. Denney's article on P.A. Equipment in the May issue of PRACTICAL WIRELESS, and criticisms in the June issue.

May I suggest a remedy which would overcome the problem? The chassis can be made perfectly safe for all conditions by taking all the internal earth connections to a fairly heavy copper or otherwise conductive strip running the length of the chassis; the strip to be insulated from the chassis. This common earth can then be connected to the chassis via a .1 microfarad capacitor of an adequate voltage rating—preferably 1,000 volt working. The chassis is then externally earthed in the usual way. These remarks apply, of course, to both the main amplifier and the pre-amplifier unit.—T. W. BENNETT (Wisbech).

## Service Engineers

SIR,—The correspondence on service engineers has provided much interest for me, and although not wanting to provoke a further intensification of argument prior to the correspondence closing, I feel that the following viewpoint should be ventilated. Radio has been my hobby for about 28 years, and, additionally, I have been employed in the industry, on manufacturing side, with my present firm since 1928. Having spent many years on the bench as service engineer, it has been my lot since 1945 to have charge of a section in what must be regarded as one of the leading manufacturer's service departments.

During the period from above date till now well over 100 engineers have passed through my hands—good, not so good and, frankly, bad. The standard of workmanship demanded in my department is high, and at the moment I am fortunate in having a pretty good selection of engineers; not always the case, however. I feel it must be stated that I have found during these years that the best types of engineer come usually from the keen amateur type, often with little or no previous commercial experience. Some have, however, had radio training in the Services. This seems to tie up with Mr. G. H. Gunter's experience. Ex. dealer's service engineers usually find it hard to work to our high standard, and seem to have the "patch it up" mentality.

My section is chiefly concerned with completely overhauling—sometimes completely rebuilding—

pre-war sets of good type, sometimes very expensive ones. In the course of this duty, I regret to have to say, a large part of the unpleasantness of this work is in putting right the general mess that has occurred over the years due to repeated servicing—most of which I am satisfied can be accredited to various dealers' departments. In fairness to dealers, I should point out that their service, by its very nature, should be regarded as first-aid and, as such, should be judged. There are, of course, exceptions to this. But, and I am expressing my personal opinion based on much commercial servicing experience, I do feel that there are as many "quacks" (to quote Mr. Gordon King) in the trade as outside it, and I say this fully realizing the storm that may break over my head.

Mr. Gunter would have been well advised, as he knew what was wrong with his set, to have blown out the dust and changed the volume control himself. His lack of equipment would hardly have been a handicap for such a small job and, apparently, he would have saved £10.—R. W. BRYANT (Longford).

SIR,—I have been following with mixed feelings the various correspondence in "praise and condemnation" of the dabbler.

Now, I am a dabbler, an "honest dabbler"—I repeat the word "honest"—and I am not in the least ashamed of the fact.

I am a licensed amateur living in a very small village, consequently a fair number of the locals ask if I can help them out when their radio fails, and this I do with pleasure.

I make the usual voltage, current and resistance checks, check valve emission, etc., and inform the set owner of the trouble. I also tell the owner of the spares required which they buy themselves. My charge for all this? About 1s. an hour, partly to cover cost of electricity used during repairs, the remainder to help buy a new supply of solder! I think Mr. A. Harrison will agree with me that it is at least *honest*. I doubt also if he can accuse me of taking the bread from the mouth of the registered service engineer, because the number of radios I repair during a year would not give him much gain—not even at to-day's high prices which some of them see fit to charge.

I would also like to state that the greater part of my test equipment was built from circuits printed in PRACTICAL WIRELESS and they all work perfectly.

Long may you continue.—E. FORD (Kent).

### Alternative I.F. Couplings

SIR,—Allow me to comment on W. Nimmons' article in PRACTICAL WIRELESS (June). His remarks on I.F. transformers and the loss of power in I.F. stages call for some comment.

First, the purpose of an I.F. stage is to increase the I.F. signal voltage, not the power (if that is what he meant).

Secondly, a circuit of high "Q" is selective and develops a voltage gain across it. (The normal I.F.T.s have a "Q" of at least 100.) The L/C ratio of these coils is made suitable for a reasonable voltage step-up and for good selectivity. The coils cannot be over-coupled or the resonance curve becomes peaked at two points, with a trough in the middle, reducing the voltage developed.

The transference of energy is quite sufficient for normal purposes.

In his circuit of the 3-valve superhet W. Nimmons puts the coil in the grid circuit. I suggest that it is put in the anode circuit to reject the unwanted frequencies at the source.—D. SULLY (Wimbledon).

### The RX18

SIR,—Being a RX18 "fan," like your correspondent from Ceylon (S. Pathmanathan), I would like to let you know my own method of treating this superb little receiver.

I find that there is quite enough interesting transmission to listen to between 6 to 9 Mc/s (especially the 40-metre amateur band) so I have not altered the wave-band, but I have added a pentode valve to bring it up to L.S. strength.

This can easily be done as follows: construct a metal chassis to add on to the existing receiver.

It is all quite simple and now that I have painted the extra portion of chassis to match the receiver it is hard to believe the set was not made in one piece.

The results I get are really wonderful—all transmissions come through on the loud-speaker quite nicely—amateurs especially—as, for instance, the other morning a contact between two amateurs, one from Kingston-on-Thames and the other from Stockholm in Sweden; the Swedish station came in very little short of the English one.

Like your correspondent I do *not* use grid bias at all, it is not needed, even for the pentode.—H. R. MILLARD (Brentford).

### Component Market

SIR,—The suggestion contained in your June number article that dealers and manufacturers should give attention to the component market is one that should not be ignored. However, when advertising their wares these people could too frequently give a little more honest attention to their customers. I have found many articles not as advertised and new components obviously packed unexamined and faulty.

Then with regard to ex-Government goods, some firms despatch immediately, others acknowledge receipt of cheque but it is weeks before the goods are despatched, while others send no acknowledgment at all and it may be many weeks after many inquiries that the goods are eventually received, yet these goods are in stock, surely, when advertised.

There is far too much casual indifference about advertisers these days.

The most glaring example was a Midland firm who advertise a 3-5 day repair service. I sent them a small motor by registered post; after 15 days I had to write to know if it had been received and after about four months it was returned "repaired." All but two segments of the commutator were "dis" and it was useless. The charge was £3 7s. 6d., more than twice the original cost of the motor. I was too disgusted to do anything about it, but vowed never to take further notice of advertisers.

Eventually it will be the advertising revenue of such journals as yours that will suffer through the ever increasing casual, if not dishonest, advertiser.—R. T. COWLAN (Rickmansworth).

### Condenser Testing

SIR,—After having experienced several constructional failures due, as was found by an expert, to the use of faulty ex-Service condensers, I should like to pass on a tip which has saved me considerable worry. I could not afford a good condenser bridge, but I have made a small panel with two terminals to which any condenser may be joined and another pair of terminals to which I connect my multi-testmeter. The panel has two flying leads which I connect to the H.T. positive and negative lines of my broadcast mains receiver (250 volts). The flick of the meter needle on a high range gives me a very good indication of the condenser leakage, and a steady reading, of course, means "scrap it." Electrolytics should not be checked by this method.—D. ROYLANCE (N.W.9).

### A Summer All-dry Portable

A NUMBER of queries have been received concerning the supply of components for this receiver which was described in last month's issue. We are informed by the author that the cabinet referred to was obtained from Alextone Advisories (Regd.), of Hillworth, Longdon, Glos, and that the coil unit was supplied by Howells, 29, McWilliam Road, Brighton, 7. For those who wish to make their own cabinet the following details are given.

For the front, back and sides  $\frac{1}{2}$  in. wood should be used. Front and back should both be 7 in. by  $4\frac{1}{2}$  in. The sides will be 6 in. by  $4\frac{1}{2}$  in., and overlapped by both front and back, when the pieces are secured together by small cabinet nails. (Glue can be applied beforehand to strengthen the joints.) The top and bottom, each of three-ply and 7 in. by  $6\frac{1}{2}$  in., should then be fixed on, using glue and short cabinet nails.

When the glue is dry the whole should be glass-papered thoroughly. A line is then drawn round  $1\frac{1}{4}$  in. from the top and the lid of the cabinet sawn off with a fine-toothed tenon saw. The edges are smoothed off and small hinges attached by  $\frac{1}{4}$  in. or  $\frac{3}{8}$  in. screws. A thin coating of quick-drying varnish of a fairly dark colour is then applied. A fastening clip can be added at the front if required.

The frame upon which the aerial is wound should be a push-fit in the lid, and the four strips from which it is made should have an  $\frac{1}{8}$  in. thickness of wood removed for about  $\frac{3}{8}$  in. width, in order to form a recess in which the aerial winding can be placed. This was shown in the end view of the frame in Fig. 4 last month. If  $\frac{1}{4}$  in. thick wood is used, two pieces  $6\frac{1}{2}$  in. by 1 in. and two  $5\frac{1}{2}$  in. by 1 in. will be required for the frame mentioned.

A.C./D.C. Voltmeter, 0-300 volts, 17/6. Bond Tester, 0 to .1 ohm, 4in. scale, can be easily converted into ohmmeter or megger, 12/6. Vacuum Gauges, 0-30in., mercury, 6in. scale, 10/-. Centre Zero Voltmeter, 0-3 and 0-30 volt, 10/-. A.C. Voltmeter, 0-150 volt with 12 k resistor, will read 300 volts, 7/6; 100 m/a meter, 2in., 4/6. Special Offer, 100 to 124 Mc/s Transmitter in four channels (BC950-A400), less valves, 17/6, plus 1/6 post. Metal Rectifiers, 12 volts 1 amp., 4/6. 6-way on/off press button switches, a really beautiful job, 3/6. Moving Coil Mikes (hand type), 6/6. Carbon Hand Mikes, 4/6. Fully shrouded Mike Transformer, 4/6. 2 mfd. condensers, 500 v., screw mounting, 2/6. 8 mfd. 600 volt, 4/-. 4 mfd. 600 volts, paper, 2/6. 10 mfd., paper, 600 volts, 6/-. 32 mfd. 500 volt (larger size with clip), 5/-. 25 mfd. 25 volt, 1/-. 50 mfd. 12 volt, 1/6. 12 mfd. 50 volts, 1/-. 8 x 8 x 8 mfd. 450 v., 5/-. 5 mfd. 500 volt, paper, 9d. 1 mfd. 2.5 Kv., 2/6. Miniature Speaker Cabinets to suit 3in. speaker in very attractive colours, 7/6. 200 to 250 volt motors, A.C./D.C., with three-speed gear-box, 19/6. M.L.A. 5/-. VR137, 7/6. 12C8, 8/-. 12SL7, 8/6. NGT1 Thyatron, 6/-. Battery output pen, 6/-. EL3, 10/-. ECH3, 10/-. HVR2A, 7KV, EHT Rectifier, 6/-. B.K32 6.3 volt, 2 Frequency Changer, 6/-. MS Pen., 6/6. VP4B, 7/6. 12A6 output Pen., 6/-. 4Pin. Barreter 2amp., 5/-. 4Gang Tuning Cond., .0005, 3/6. 100 P.F. Double-spaced Butterfly Condenser, 2/6. Anti-interference radio mains suppressors, 7/6. 3 to 6 meter Transmitter receiver, works from 6 volt Vibrator Pack, price 27/10/0. Metal rectifier, 12 volt at 1 amp., price 4/6. 5in. enameled 12 speaker suitable for car radio, 15/-. 15 amp. Shidecock fuse, 2/-. 230 v. Bridge type resistor less resistance box, 25/-. G.B.C. and Ediswan Germanium crystal diodes, price 5/6. Superhet Chassis suitable for radiogram, 5-valve A.C. Complete with dial and speaker by well-known makers. We have a very comprehensive stock of all Radio, Electrical and TV Spares. Write, call or phone. All enquiries answered.

**SOLIDAS LTD.**

4 PRAED ST., LONDON, W.2.  
AMBASSADOR 4670

**TELEVISION**

The advance of Radio Technique will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook.

Full details are given of A.M.Brit.I.R.E., City & Guilds Exams., and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc. etc. We guarantee "NO PASS—NO FEE". Prepare for to-morrow's opportunities and future competition by sending for this very informative 176-page guide NOW—FREE and without obligation.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**  
(Dept. 242),  
17, Stratford Place, London, W.1.

**STAN WILLETTS**

43, SPON LANE,  
WEST BROMWICH,  
STAFFS.

TEST METERS (M/c.), 7 Ranges, 1.5 v., 3 v., 150 v., 6 M/a., 60 M/a., 5,000 ohms., 25,000 ohms, 2in. dia., in Black Bakelite Case, 6in. x 4in. x 4in. Less Batteries, 24/6. AMPLIFIER, Type A1368, complete with 2 Battery-operated Valves QP21, 210LF. Brand New in Wood Transit Case, 15/-. post 1/6. R1155 COMMUNICATION RECEIVERS, complete with Valves, All tested and guaranteed, 25 10s., carriage 10/-. EA50 (VR92), 1/11 each, 6 for 10/6. Post 4d. ATP4, 3/9. 12A8, 4/6. Post 4d. 3 AMP. MAINS DROPPERS, 717 ohms, tapped at 100 ohms, 1/6 each, 5 for 6/-. post 6d. U.S. ARMY BLASTING GALVANOMETER, size 4in. x 3in. x 1in., complete with chloride of silver cell. Brand New in Leather case, 17/6, post 6d.

**RECEIVER TYPE 25  
(TR1196)**

Makes an ideal basis for an all-wave receiver and is supplied with full conversion data.

Is fitted with 6 valves types EF36 (2), EF39 (2), Ek32 and EBC33. An excellent article on this set appeared in the May issue of "Practical Wireless." 140 only available.

Price 39/6, plus 1/6 postage.

Owing to enormous advances in buying costs we recommend you to buy now and save money. These sets will be absolutely unobtainable in a few months' time.

**H.P. RADIO SERVICES LTD.**

Britain's Leading Radio Mail Order House,

55, COUNTY ROAD, WALTON,  
LIVERPOOL, 4.

Tel. : Aintree 1445. Etab. 1935.

**SECTIONAL  
STEEL MASTS**

Ex-Government Surplus Steel Tubing, made into Sectional Masts. Ideal for Television, Radio, Flag Staffs, etc. Each Section approx. 2in. dia. and 5ft. 6in. long.

11ft. Mast (2 sections), 12/6d.  
(Carr. 2/6d.)

22ft. Mast (4 sections), 22/6d.  
(Carr. 3/6d.)

AT THESE PRICES THEY  
CANNOT LAST LONG.

Send S.A.E. for our latest Clearance List of Radio and other Equipment.

**WALTON'S WIRELESS  
STORES,**

203, STAVELEY ROAD,  
WOLVERHAMPTON

**LYONS RADIO  
LTD.**

3, GOLDHAWK ROAD, Dept. M.P.,  
SHEPHERDS BUSH, LONDON, W.12

Telephone: SHEPherds Bush 1729

**OSCILLATOR UNITS TYPE 76.** This unit is a simple signal generator providing a test signal, C.W. or M.C.W., over a frequency range of 98 Mc. to 152 Mc. Valves employed are 1 each of VR66 and VR67. H.T. required about 60v. D.C. and L.T. 6 or 6.3v. A.C. or D.C. Housed in metal case approx. 9in. cube containing battery compartments and hinged flap covering controls. In good working order and tested before despatch. PRICE 55/-, carriage 3/6.

**MAINS TRANSFORMERS.** Primary 200 to 250v. 50 cps. Secondaries : 350-0-350v. at 80 m.a., 4v. at 5A., or 6.3v. at 4A. and 4v. or 5v. at 2A. For upright, sideways or as drop-thro. chassis mounting. Brand new and fully guaranteed. PRICE 18/6, post 1/6.

**RECEIVERS TYPE R1224.** A five-valve superhet receiver with a frequency coverage of 1 to 9 Mc. (300 to 30 metres). Valves fitted are 2-VP23 and one each of FC2A, 210LF, 220PA. Batteries required : H.T., 120v.; G.B., 9v.; L.T. 2v. Outside of wooden cabinet may be slightly soiled and broken, but receivers are in otherwise new, unused condition. Supplied complete (less batteries) with LR phones and tested before despatch. PRICE 24.19.6, carriage 5/-. post 1/6.

**L.T. MAINS TRANSFORMERS.** Primary 200-250v. 50 cps. Secondaries 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volts at 2 amp. total loading. Brand new and guaranteed. PRICE 17/6, post 1/6

**LOUDSPEAKER SEPARATORS**

The many advantages of the use of separator and two speaker units in high fidelity equipment are fairly well known; for those who may not be so familiar with them, however, we offer our leaflet S.E.3.

Units available ex-stock are :

Model A, kit of parts 18s. 6d.  
Model A, built and tested 22s. 6d.

Model B. This model permits the adjustment of treble relative to bass or the use of speakers of different impedance.

Kit of parts, 32s. 6d.  
Built and tested, 41s. 6d.

Post and packing 1/-.  
S.A.E. for further details or leaflet S.E.3.

**RADIO COMPONENTS  
EAST STREET, DARLINGTON**

**RADIO AND TELEVISION  
COMPONENTS**

All parts in stock for :  
Electronic Viewmaster and Easy Built Televisors

**ITEMS SOLD SEPARATELY**

Test Meter, 0-15 and 250v. with test prod. 10/-.  
12ft. Aerials, 3 screwed sections, 5/-.  
Min. Speakers, Adjustable diaphragm, 2/6.  
J1 500 Con., 4d.  
500+500 Trimmer, 1/-.  
ALL NORMAL RADIO COMPONENTS STOCKED.

ALL GOODS POST FREE OR C.O.D.

**T. N. B. RADIO**

166a, Rookery Road, Handsworth,  
Birmingham, 21.

**Best Buy at Britain's**

**Coil Pack.** 3 waveband, short, medium, long, complete with all trimmers, padders, switch, etc., ready for use. Employs slung tuned iron cored coils throughout. With circuit diagram. 17/6d. each, plus 1/- post & packing.

**Mains Transformers.** Standard primaries. Universal mounting. 350-0-350v. 80 mA., 0-4-6.3v. 4a. and 0-4-5v. 2a. 250-0-250v. 80 mA., 0-4-6.3v. 5a. and 0-4-5v. 2a. 30v. 2a. tapped 3v., 4v., 5v., 6v., 8v., 9v., 10v., 12v., 15v., 18v., 20v. and 24v.

All these transformers are brand new, fully guaranteed and priced at 18/6d. each, plus 9d. post & packing.

**EHT Transformer.** For VCR517 or VCR97 tubes. 2,000v. 4v. for tube heater and 4v. tapped at 2v. for EHT rectifier. Brand new and fully guaranteed. Our price: 35/- each, plus 9d. post & packing.

**Special Mains Transformer.** Manufacturers' surplus. Very few only. 300-0-300 70 mA., 6.3v. 2 1/2 a., 5v. 2a. Only 12/6d. plus 9d. post & packing.

**Output Transformer.** 6 ratios. 7/6d. plus 6d. post.

**Metal Rectifier.** 12v. 2a. full wave bridge, 12/6d. plus 6d. post. Miniature H.T. rectifier type RM2. 125v. 100 mA. 4/3d. each or 2 for 8/-, plus 6d. post one or two.

**Speakers.** 3in. P.M. Brand new. 11/9d. plus 9d. post. 6 1/2 in. P.M. Heavy duty magnet, 9/6d. This item callers only.

**Electrolytic Condensers.** 8 mfd. 600v. wkg. 700v. surge, 3 for 10/- post paid.



**CHARLES BRITAIN (RADIO) LTD.**

Upper Saint Martin's

Lane, London, W.C.2. TEL. 0545  
Shop hours, 9-6 p.m. (9-1 p.m. Thursday)

OPEN ALL DAY SATURDAY

**NEW BOXED VALVES.**—1R5, 1T4, 1S5, 3S4, VP2B, TDD2A, PEN.220A, KTW63, SP4B, VP1B3, 10/-; 1L4, 3A4, 3Q4, 6C4, ATP4, 8/6; 6K7GT, 9002, 6ACTM, 7/6; 6SG7M, 12A6M, EF54, 6/6; 9D2, 5/-; 954, 955, 3/6. Unboxed EF36 (Canadian), 4/- each, or 6 for 4/1. All guaranteed.

**SMOOTHING CONDENSERS.**—20+10mfd. 350v. wkg. soiled but perfect, 2/3 each. Knobs, with brass inserts, 6d. each.

**ALADDIN COIL FORMERS** 2d. each.

**METERS.**—50 micro-amp, 2 1/2 in. scale, round flush mts., 32/6 each. Miniature Moulded Mica Condensers, 100 pf., 4/6 doz. I.F. Transformers, ex-Govt., 485 kc/s, with adjustable cores, 7/6 pair.

**LOUDSPEAKER CABINETS** for 8in. Speakers, 8/6 each.

Send stamp for new list of hundreds of valves and other components. Please add postage on orders under 4/1.

**ELECTRAD RADIO,**

64, Gt. Victoria Street, BELFAST, NORTHERN IRELAND.

**RADIOLECTRON**

22, Frances Street, Scunthorpe, Lincs. NEW GOODS ONLY

**CONDENSERS.**—450 V.W. 4 mfd. 2/6; 8, 2/-; 16, 4/-; 8-8, 5/9; 8-16, 7/6; 16-16, 7/9; 500 V.W. 8 mfd. 4/-; 16, 6/6; 8-8, 6/6; 8-16, 8/6; 16-16, 10/6; 25X25V, 2/-; 25X50V, 2/3; 50X, 12V. 2/-; 50X50V, 2/6. Tubulars, 500 V.W. up to .01, 11d.; to .1, 1/1; .25, 1/9; .5, 3/6; 450 V.W. 1 mfd. 2/9; 2 mfd., 3/3; Moulded Mica, up to .0003, 10d.; to .003, 1/-; to .01, 1/6; Sil. Mica, up to 80 pf., 9d.; to 8K pf., 1/-.

**VOLUME CONTROLS.**—Lg. 1in. dia. Spdls. all Values, 3/-; with SW, 5/-; with D.P. SW, 6/-; Midg. Type, 1 1/2 meg., 4/6; with SW, 6/6; with D.P. SW, 7/6; Wire Wound, 1 K. to 80 K., 6/6; 100 K., 7/9.

**RESISTORS.**—Carbon, all values, 1 watt, 8d.; 1 watt, 10d.; 2 watt, 1/3; Wire Wound, 5 watt, 50 ohms to 2 K., 2/-; 3 K. to 50 K., 2/6; 10 watt, 50 to 2 K., 2/6; 20 watt, 50 to 2 K., 4/-; Mains Droppers with Pt. and 2 adj. taps, .2 A., 5/-; .3 A., 5/4; Linecord, 3-way, .2 A. or .3 A., 2/3 yd. Terms—Orders up to 10/- post 4d.; over, free. List 4d. stamp. Please print your name and address.

**5-VALVE ALL-WAVE CHASSIS**

The HAYES RG/120 is an outstanding 5-valve chassis with high sensitivity and selectivity. Octal valves 6K8, 6K7, 6V6, 6Q7, 5Z4. 16-50, 195-550, 900-2,000 metres. Iron-cored high "Q" coils. Illuminated glass dial, 6in. x 5in., var. tone control, switched P.U. sockets, and high quality 4-watt output. Chassis size 1 1/2 in. wide, 7in. deep. A beautiful bronze escutcheon is supplied. For 200-250 volts A.C. These chassis are new and fully guaranteed. With 10in. l.s., price, £14.10s. Full details gladly sent by return of post. Please mention "P. W."


Push-pull version of RG/120 and feeder unit now ready.

**THE HAYES COMPANY**

1 ALCESTER RD., MOSELEY, BIRMINGHAM, 13  
Phone: SOUTH 0202

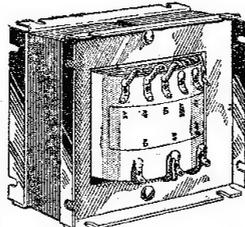**TRANSFORMERS**

M.T.1.—250-0-250 v. 80 mA.; 0-4 v. 5 a.; 6.3 v., 3.5 a.; 0-4-5 v., 2 a.  
M.T.2.—Same as M.T.1. but 350-0-350 v.  
M.T.3.—30 v.; 2 a.; tapped every 3 volts.  
All primaries tapped for 200 to 250 v.



M.T.4. Auto 0-10-120-200-230-250v. 100 watts. Examine what you buy. From component dealers or write to us if unobtainable. The correct price for these transformers is £1 each.

Interleaved and Impregnated

**THE DOUGLAS COIL CO., BRINKLOW, RUGBY.**

**YOU can become a first-class RADIO ENGINEER**

We are specialists in Home-study Tuition in Radio, Television and Mathematics.

Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

**T. & C. RADIO COLLEGE**

Post in unsealed envelope, 1d. postage

To: R. Heath Bradley, T.C.R.C., 50, Harland Road, Southbourne, Bournemouth.

NAME.....

ADDRESS.....

P.115

**MAINS TRANSFORMERS**

(Postage extra under £2)

Screened Primaries 200/250 v. Interleaved and impregnated. Drop through type.

- (a) 250-0-250v. 60 mA., 6.3v. 3A., 5v. 2A. — 18/6
- Following Types have UNIVERSAL L.T. Windings, 0-4-6.3v. 4 A. C.T. 0-4-5v. 2A.
- (c) 250-0-250v. 80 mA. ... .. 22/6
- (d) 300-0-300v. 80 mA. ... .. 22/6
- (e) 350-0-350v. 80 mA. ... .. 25/-
- (f) 250-0-250v. 100 mA. ... .. 25/-
- (g) 300-0-300v. 100 mA. ... .. 25/-
- (h) 350-0-350v. 100 mA. ... .. 25/-

- Upright Types Fully Shrouded.
- (i) 350-0-350v. 150 mA., 0-4-6.3v. 6 A. C.T. 0-4-5v. 3 A. ... .. 42/6
- (j) 425-0-425v. 180 mA., 6.3v. 4 A. C.T. 6.3v. 4 A. C.T. 5v. 3 A. ... .. 52/6

**GOVERNMENT SURPLUS R28/ARC5 RECEIVERS.** 100/150 Mc/s, 10 Valves... 42/6

**MOVING COIL HEADPHONES,** with M.C. Microphone ... 8/6

**ELECTRIC MOTORS,** 1/40 H.P., 50v., 50 c/s., 3 phase. Circuit supplied to convert to 230v. single phase ... 8/6

**AERIAL INSULATORS.** Bakelite ... 3d.  
Per doz. ... 2/6

**SET OF 2, 4, 6BA SPANNERS ...** 1/6  
**ROTARY MAINS SWITCH.** D.P.S.T. ... 1/6

**MALLORY 12-VOLT VIBRATOR PACKS.** Output 150v. 30 mA. ... 12/6

**MINE DETECTOR AMPLIFIERS** with three IT4 valves ... 22/6

**T1154 TUNING PANELS** with three tuning condensers ... 4/6

**PACKARD BELL PRE-AMPS.** Complete with valves and spares in makers cartons ... 16/6

**SMOOTHING CHOKES** 40 mA., 5/-; 60 mA., 6/6; 90 mA., 7/-; 100 mA., 15/6; 200 mA., 25/-

**VIEW MASTER TV RECEIVER.** All parts stocked. Constructional envelopes, 5/-

**COULPHONE RADIO** "The Return of Post Mail Order Service." 53, Burscough Street, Ormskirk, Lancs. Send 5d. stamps for catalogue.

**H.A.C. SHORT-WAVE EQUIPMENT**

Noted for over 15 years for Short-Wave Receivers and Kits of quality.

One Valve Kit, Model "C" Price 20/-  
Two " " " " " " " " 43/-

These kits are complete with all components, accessories, and full instructions.

Before ordering send stamped, addressed envelope for descriptive catalogue.

"H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 11, Old Bond Street, London, W.1.

**VALVES ?** We probably have just the one you want, such as 6A7, 18, 30, 39, 42, 43, 45, 75, 77, 78, 80, etc. We hold one of the largest stocks in the country. Why not drop us a card or phone Luton 2677? We will dispatch by next post.

You can rely on

**COVENTRY RADIO**

189, Dunstable Road, Luton, Beds.

# Impressions on the Wax

## Review of the Latest Gramophone Records

**T**HE London Baroque Ensemble, conducted by Karl Haas make this month what is believed to be a first recording of Haydn's "St. Anthony Divertimento" on three sides of *Parlophone SWS1201*. It is the work that provided Brahms with his main theme for his magnificent "Variations on a Theme by Haydn." The "fill-up" on the fourth side—Mozart's "Adagio K.580A," merits attention, too. It is a piece for cor anglais, two violins and cello, an unusual combination.

For ballet-lovers there is the ballet music of Arnell's "Punch and the Child," played by the Royal Philharmonic Orchestra, conducted by Sir Thomas Beecham on *Columbia LX1391-2* and *LXS1393*. Londoner Richard Arnell, was really "discovered" in America where he has been resident since 1939. He was the B.B.C.'s Music Adviser in New York from 1943-1946. Sir Thomas Beecham was an early champion of Arnell's work. He has conducted this ballet in New York and he will perform it at the Royal Albert Hall on June 17th.

Other interesting orchestral recordings are the Hallé Orchestra, conducted by Sir John Barbiroli, playing "A Song of Summer," on three sides of *H.M.V. DB9609*. Mozart's "Andante" (from Cassation in G Major, K.65), appears on the fourth side. The Overture "Hansel and Gretel," by Humperdinck, played by Leopold Stokowski and his Symphony Orchestra on *H.M.V. DB21256*, the Overture "Pique Dame," by von Suppé, played by the Philharmonia Orchestra, conducted by Constant Lambert, and finally the "Hungarian Rhapsody No. 9 in E Flat Major," by Liszt, played by the Boston Promenade Orchestra, conducted by Arthur Fiedler on *H.M.V. C4083*.

Coming now to instrumentalists we have Chopin's "Scherzo No. 4 in E Major," a pianoforte solo, by Claudio Arrau on *Columbia LX8792-3*. On the fourth side is Chopin's "My Joys," arranged by Liszt.

Yehudi Menuhin needs no introduction and for his violin solo accompanied by Louis Kentner on the piano he has chosen Bach's "Sonata No. 1 in B Minor"—*H.M.V. DB9607-8*.

There is an interesting story behind the recording of intermezzo from the "Jewels of the Madonna" and "Valse Oubliée," by those two masters of the keyboard, Rawicz and Landauer on *Columbia DB2851*. In the B.B.C. programme, "Hullo There," a midday feature for older children, Marcel Stellman ran a short serial account called "In the Groove," a stage-by-stage story of how a record is made. It is this record of the Intermezzo that was involved.

### Vocal

A fine young dramatic soprano, Amy Shuard, joins the ranks of Columbia. Her Santuzza, Marguerite, Musetta and Princess E foli (Don Carlos), are well known and much admired by Sadler's Wells audiences. Here she sings "You Here, Santuzza" and "Cavalleria Rusticana," as duets with James Johnson on *Columbia DX1748*.

The well-known radio tenor Harry Dawson, has chosen the popular "Life's Desire," coupled with "I'll Always Love You," for his latest recording on *H.M.V. B10068*, whilst Dennis Noble sings "The Frost-bound Wood," and "The Fox" on *H.M.V. B10075*.

### Variety

A deeply rooted love throughout the world for the late Sir Harry Lauder, coupled with a marked revival of interest in this great Scottish character (the recent B.B.C. broadcast about him, for instance, and the tribute paid to him by Sir Thomas Beecham in his broadcast programme of "Records I Like"), have brought about the re-issue by *H.M.V.* of records of many of his famous songs.

A dramatised version of "Cinderella" told as a story, with Ilene Woods as Cinderella and the voices of the various characters as heard in the film has been recorded on *H.M.V. DB1270-1*. These records should not in any way be confused with the two records by Ilene Woods issued in October, 1950, which contained the song hits from the film. These latest recordings are just like listening to the sound track with a story-teller knitting the whole thing together.

If you desire just the orchestral selections from the film they have been recorded by the Melachrino Orchestra on *H.M.V. B10064*.

### Dance Music

All the latest hit songs of the moment have been recorded by popular bands. That well-known combination of Billy Thorburn's, "The Organ, the Dance Band and Me," play "Beautiful Brown Eyes" and "Mockin' Bird Hill" on *Parlophone F2460*; Phil Cardew and his Corn Huskers play "Crackin' Corn—Square Dance" and "The Irish Washerwoman" on *Parlophone R3391*, and Joe Loss and his Orchestra play in dance tempo two quicksteps, "Festival Hop" and "Rose, Rose, I Love You" on *H.M.V. BD6094*.

Finally, a Festival of Britain record, displaying British artistic achievement, called "Columbia Cavalcade"—a salute to British artists and composers—appears on *Columbia DX1750*.

Editorial and Advertisement Offices :  
 "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone : Temple Bar 4363.  
 Telegrams : Newnes, Rand, London.  
 Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed : The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

## BOOKS

**R.S.G.B.** "Amateur Radio" publications: Transmitting Licence, 32pp., 1/-; Service Valve Equivalents, 32pp., 1/3; Transmitter Interference, 32pp., 1/6; Simple Transmitting Equipment, 52pp., 2/3; Microwave Technique, 68 pp., 2/3; Receivers, 96pp., 3/9; Valve Technique, 104pp., 3/9; V.H.F. Technique, 96pp., 3/9; R.S.G.B. Bulletin, current issue, 1/6. Five recent issues, 2/6. Prices include postage. **RADIO SOCIETY OF GREAT BRITAIN**, 28, Little Russell St., London, W.C.1.

**BRITISH SHORT WAVE LEAGUE** is devoted to the interests of amateur radio enthusiasts. Publishes 12-page "BSWL Review" monthly (members only). Offers many services and activity departments. World wide membership. Founded 1935. Apply for details to: **BRITISH SHORT WAVE LEAGUE**, 53, Victoria St., London, S.W.1. (Abbey 2384.)

**ALIGNMENT PEAKS.** Second edition. 5,000 superheterodyne alignment peaking frequencies, 4/9 post free. The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free. Membership and examination data 1/- post free. Secretary, I.P.R.E., 20, Fairfield Road, London, N.8.

**THERE IS PLENTY** of time to beat the Budget and have radio on your holiday—get "Personal Portables," 2/8, post paid, for 5 completely described circuits. Going to Town? Then take your Personal Televisor, built from "A Portable Televisor," 3/2, post paid. Both from **BRAD-BOOKS**, Sennen, Penzance, Cornwall.

## RECEIVERS &amp; COMPONENTS

**RADIO COMPONENTS.** Valves, etc., quickly obtained from our regular bargain lists. Send S.A.E. today! Goods C.W.O.; money back guarantee. **ANNAKIN**, 25, Ashfield Place, Otley, Yorks.

**COMPONENTS** and Valves. Wide range stocked. 1951 catalogue free upon request. **M. WATTS & CO.**, 8, Baker St., Weybridge, Surrey.

**MAKE** these Receivers—complete with cabinet and valves: TRF 2WB, £5/10/-. MSS S'het, £6. LMS S'het, £6/5/-. Concise books of instructions, 1/6 ea. Thousands of components available: "P" type coils, 2/6; TRF coils, 5/3 pr.; .01 x 1,000v tub., 3/6 doz.; 1 x 350v tub., 2/9 doz.; Dial Drum, 2½in., 6d.; Microphones, 1/6; Sleeving, 1, 1½, 2 or 3 m/m, 1/- doz. yds.; ex-R.A.F. 40:1 Trans., 6d.; plastic covered Wire, 22 SWG, 1/- doz. yds., etc. etc. 3d. stamp for latest list. **SUSSEX ELECTRONICS LTD.**, Princes St., Brighton.

**MIDDLESBROUGH** . . . phone 3096 or call **PALMERS**, 114, Waterloo Road. Large stocks Radio and TV components.

**EVERYTHING** for Radio constructors, Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH**, 98, West End Road, Morecambe. Quick service.

**TR9 COMPLETE SETS** with 9 valves, not guaranteed 16/-. Yaxley 2-way Switches, 1/9. 50 new, 50 used Resistors, ½ to 5w.; our selection, 6/6. Unselected Nuts and Bolts, 1/9 lb. 50 Wire-end Electrolytic Condensers Assd., including 2 and 4 mfd. 350. 500v.; knock-out price, 10/6. 8 mfd. 600v. Cans, damaged, 1/3. All post paid. Indicators, 6a, complete in maker's crate, 75/-. **AUTOREX MOTORS**, New Whittington, Chesterfield.

**RATES:** 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

**TRANSMITTER - RECEIVERS,** ex-R.A.F. T.R.9 9-valve Sets, not guaranteed owing to storage corrosion effects, but all valves present and checked. Complete with transit case, 25/-, carriage paid. P.O. to "ELECTROMART," 14, Broad Pavement, Chesterfield, Derbyshire.

**RADIO SUPPLY CO.,** 34, Hanover St., Park Lane, Leeds. Ex-Gov. items: Smoothing Chokes, 100 ma 10h 100 ohms, trop, 4/3, 200 ma 5h 100 ohms 5/9; Selenium Rectifiers, 12/24v 1a H.W., 3/6; Microphone Trans., 100:1, 2/6; 12 mfd 50v Met. Tubs., 7/- doz.; Brand new, boxed, Valves, 954, 955, 956, 2/9; SP4 (MS/PEN), 3/9; 12A6 Met., 5/3; 6C4, 6SG7 Met., KT24, 4/11; 6B8 Met., 6D6, 6C6, 6K7G, 6N7 Met., 6/9; KTZ41, KT66, 8/9; 42, 7/11; 9D2, 3/3. New, unboxed, D1, 1/3, 6X5GT, 6/11; EL32, 7/6; 5R4GY, 8/6. Ex. new equipment, HL210, 2/3; KT2, 4/3; EF36, 4/9; EL32, 6/11; EF39, 5/11; EF50, 4/11. All goods guaranteed. C.W.O., or C.O.D. over £1. Post 1/2 all orders. Full list 4d.

## VALVES

**VALVES:** X63, KT66, KT63 at 7/6; KTW61, KTW63, DH63, DL63 at 6/-; L63, U50, U52, MH4 at 5/6; post 6d. extra. Any 5 at 32/- post free. **HOLDSWORTH**, 66, Front St., Bedlington, Northumberland.

**VALVES,** new, bxd., 6AC7, 6C5, 6K7G, 6J5GT, EF50, EF36/VR56, 9003, 12A6, SP61, SP41, VU111, 6B8, 6K6, 6N7, KTW61, 9D2, all at 6/6 each; 6L6G, 5U4G, 6V6G, 6X5G, 3S4, 25L6, EBC33, VR101, EL32, all at 10/- ea. "Universal" Mains Trans., 350/0/350 80ma, 6.3v and 5v, both tap. 4v, unshd., universal mntg., 16/11 each. 75 ma, 10H, LF Chokes, 6/9 each. **LORNE RADIO SUPPLIES** (Mail Order), 7, Lorne Rd., Walthamstow, E.17.

**NEW BOXED VALVES:** EK32, KT2, EF36, at 6/6; 9D2, 4/-; 6K7G, 6/-; SP41, 5/6; SP61, 4/9; 6F6G, 7/6; 6V6G, 10/-; 6K6GT, 7/- Stnd. 80 ohm, ½in. CoAx, 12/- doz. yds. New PM Spkrs., 3½in. 14/6, 5in. 14/6, 6½in. 14/11, 8in. 16/-, 10in. 21/-, 12in. 66/- V/Hdrs. Int. Oct. Amph, 7/- doz.; B7G, 9/6 doz.; EF50, 7/6 doz. Sprague 1/350v. 7/- doz. 8 mfd. 450v. 2/9, 7H 60 ma. Chokes, 6/6 ea. Stamp for list. **RAEMOS**, 52, Pendlestone Rd., Walthamstow, E.17.

## REPAIRS AND REWINDS

**ELECTRICAL TEST METERS,** all makes single or multi-range repaired and standardised. **THE ELECTRICAL INSTRUMENT REPAIR SERVICE**, 329, Kilburn Lane, London, W.9. (Tel.: Lad. 4168.)

**VACUUM CLEANERS** and Gram. Motors, repairs our speciality. Armature rewinds, new bearings and commutators fitted, also transformers rewound, speakers repaired. Competitive prices. Trade enquiries invited, 2 to 5 days c.o.d. service. Send s.a.e. for price lists to: **A.D.S. Co.** (V.E.M. Dept.), 261-3, Lichfield Rd., Aston, Birmingham, 6, Est. 1935.

**LOUDSPEAKERS** repaired promptly. **MODEL LOUDSPEAKER SERVICE**, 34a, Billington Road, Oxford.

**CABINETS.**—Why buy one when you can make a first-class veneered or hardwood cabinet yourself at a fraction of the cost? We supply detailed drawings and instructions of easily constructed, well-designed cabinets. Send for illustrated catalogue to **CHAFFEY-CONSOLE**, 6, Sefton Rd., Potts Wood, Kent.

**T/V "H" TYPE AERIALS,** complete with mast and lashings, any channel, 49/6. T/V Dipoles only, London or Holme Moss 12/-. Birmingham 10/- per set of four, 11/32in. O.D., dural tube. Cross Booms, complete with dipoles, no mast, any channel, reflector type, 32/6. Single Dipole type, complete with mast and lashings, 35/-. Indoor Aerials, 15/-. All above goods carriage paid, with money-back guarantee. **SOUND T/V CO.**, 42, Elms Rd., Aldershot.

**ALL-WAVER** with 1,000-mile range and modern detector circuit, needing no batteries or mains. Full plans and text, 2/6. Descriptive list 1d. **ALEX-TONE**, Hillworth, Longdon, Glos.

**DECCA** Three-speed Elec. Gram. Motors with turntable, £7/3/9, post 2/6. Decca Lightweight Pickups with 2 push-in high-fidelity Acos crystal heads with permanent sapphires for Standard and L.P., 84/6, post 1/6. Send 2½d. now for new list of these and other bargains, including Full Constructional Manuals how to build wireless sets, amplifiers, tuners, bass reflex cabinets, etc., for half normal cost. **NORTHERN RADIO SERVICES**, 16, Kings College Road, London, N.W.3. (Primrose 8314.)

**RF UNITS TYPE 24**, and 24 mod. 27 at 12/6 ea., plus 1/3 carr.; R1124, with 6 universal valves, OK for TV sound, 21/- ea. We have large stocks of ex. Gov. Radio, Electrical and Optical goods. S.A.E. will bring you complete lists. **H. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

**FLEX**, super quality, Aero intercom. leads containing 4 lengths, approx. 24ft. 2 screened, 2/- each, 5 for 10/-, post free. **L.T.S., LTD.**, "Bromyhurst," Barton Rd., Urmston.

**WHILE THEY LAST!!** 2v 3aH LA Accs, new, unfilled, size 4½in. x 1½in. sq., only 4/- ea. .002 mfd 5 Kv wkg mica, 2/- ea. 10 K 10 W w/w Pots, 5/- ea. Twin gang 75 pfd variables, 3/- ea. Ex stock, Amplion Multirange Testmeter, £4/7/6. Goodmans Audiom 60, £8/12/6. ANGLIN, 106, Cleethorpe Rd., Grimsby.

## TAPE RECORDINGS, ETC.

**TAPE RECORDING.** Complete Line-A-Tone Recording Panels, speeds 7½ and 15in. per sec., or 3½ and 7½in. per sec., £20. The Line-A-Tone Recording Unit, in attractive walnut cabinet, complete with tape, microphone, etc., £68. Recording Heads, Oscillator Coils, and all accessories. Send for price list. **MORECAMBE SOUND SERVICE**, Sealand Works, Cross Cop, Morecambe.


**DISC RECORDERS** for the amateur. Tracking and motor units, discs styli, amplifiers. **SIGMAPHON**, 50, Mill Vale, Bromley, Kent.

**MAGNETIC RECORDING.**—Stainless Steel Wire, .0036in. diam.; 8oz. spools; 14,000ft.; playing time, 2 hours; 15/-, post free. **H. WILSON**, 17, Berwood Farm Rd., Sutton Coldfield.

**MAGNETIC SOUND** Recording Wire, stainless steel, temporary wooden spools, approx. 1½ hours' running time at 2ft. per sec.; 14/- per spool. **A. SMART**, 40, Grange Rd., Halesowen, Worcs.

**ELECTRONIC ORGAN** Construction Data. Component values, practical layout, etc. Further details C. & S., 10a, Duke St., Darlington.

**EDES STUDIOS**, Chelsea. We are dismantling Ekco Radios and offer these used but good quality radio spares: Mains Transformers, 200V-250v prim. 300-0-300 100 ma 4v 4 amp 4v, 1 amp with voltage adj. and fuse panel, 10/- ea. Rola mains energised Speakers, 8in., 1,000 ohm field complete with pentode trans. and small baffle, 17/6. 4,000 ohm field, less trans. 12/6 ea., or with damaged cone 7/6. Pentode Speaker Trans., 3/- . Smoothing Chokes, 3/- ea. IF Trans., 110 kcs. in all. cans with trims and diag., 4/6 pr. 110 kcs. Osc. Coil with diag., 3/6 ea. Three-gang Condensers, 0005 with trims. slow motion drive and drum, 6/- ea. Three-gang Cond. screened, with osc. sect. with cut-away vanes for 110 kcs. and trims, complete with slow motion drive, dial and large knob, 7/6 ea. Band Pass Aerial Coil with w/ch. switch and Diag., 7/6 ea. Special offer to callers only: Ekco A.C. D.C. Radio Receivers, m.w. l.w. superhet; complete in round-type bakelite cabinets, less valves, 25/- ea. Terms C.W.O. or C.O.D. Please add enough for post. **EDES STUDIOS**, 255, Fulham Rd., Chelsea, S.W.3. (Phone: FLA 5587). Nos. 96, 45, 14 buses pass the door.

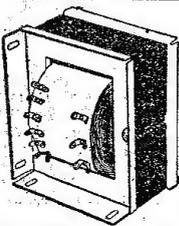

Mains Transformers UPRIGHT - DROP THROUGH - AS ILLUSTRATED. Two Types Only. Guaranteed. No. 1: 250-0-250v., 80 mA., 0-4-6.3v., 5 amp. 0-4-5v., 2 amp. No. 2: Same, but 350v. Both 15/-, post 1/- for 1 to 3

**"YOU CAN RELY ON US"**  
FOR CLEAN COMPONENTS  
AT COMPETITIVE PRICES

IMMEDIATE DISPATCH

**VALVES.**—7C5, 8/6; 6SL7, 8/-; 6C5, metal, 7/6. EF50, NEW, Red, 8/6; Silver, 7/6. 3A4, 7/6.

**I.F. TRANSFORMERS.**—RS/GB. Semi-Midget, 465 kcs., 12/6 pair. Wearite Midget M400B, 465, 21/- pair. Weymouth P4, 15/- pair.

**COILS.**—All Wearite "P" Coils stocked, 3/- each. TRF matched pair, MW/LW with reaction, 7/6. Weymouth CS3W3, 11/6 pair. CT2W2, 9/6 pair.

**SPEAKER TRANSFORMERS.**—Super Midget for personals, 1S4, 3S4, DL92, etc., 4/3. Mains Midget Type, 3/9. Standard type, 48 : 1, 4/6. 55 : 1, 4/6. 60 : 1 and 30 : 1, 4/6. Push-Pull 6V6 to 2-3 ohms, 8/6.

**I.F. FILTERS.**—Aerial, 465 kcs. Filters, complete 6/3, not surplus.

**LINECORD.**—2a. 100 ohms per foot, 8d. ft. 3 a. 60 ohms per foot, 8d. per ft.

**CERAMIC TRIMMERS.**—30 pf., 50 pf., 9d. 100 pf., 1/-, 250 pf., 1/7. 500 pf., 2/-, 750 pf., 2/3.

**TWIN GANGS.**—0005 μF. Complete with rubber-mounted feet and slow motion driver, 10/6.

**SPEAKERS.**—W.B. 2 1/2in., 17/3. R. and A. 6 1/2in. P.M., 12/6. Stockists of Haynes, Weymouth, Wearite, Viewmaster, Easy-built Television and 10,000 Valves, Surplus and List Price. Don't forget postage, chaps, and write for Catalogue No. 9 and Bargain Valve List. Price 6d.

**RADIO SERVICING CO.**  
444, WANDSWORTH ROAD,  
CLAPHAM, LONDON, S.W.8

Telephone: MACaulay 4155.  
77, 77A, 168, 169 Bus: S.R. Station,  
Wandsworth Road.

**WALNUT RADIOGRAM CABINETS**, stamp details. E. WISKER, 501, Hale End Road, Highams Park, E.4.

**A CAR RADIO** for £7/10/-. Inst. 3 d. drgs, 2/6 post. 40, Stamshaw Rd., Portsmouth.

**WANTED.**—American Radio Magazines. **FREDDIE FOX**, 101, Derby St., Bolton.

**RECEIVERS**, Valves, Components. Rock bottom prices. Stamp for details. Box 201.

**SALE**, 4 bound volumes "Practical Wireless," 1941-44; 1945-46. Offers? Box No. 202.

**EDUCATIONAL**

**A.M.I.Mech.E.**, A.M.Brit.I.R.E., City and Guilds, etc., on "No Pass—No Fee" terms. Over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 176-page handbook—Free. B.I.E.T. (Dept. 242B), 17, Stratford Place, London, W.1.

**NO B.N.R.S.** Student has ever failed to pass his examinations after completing our appropriate study course. Now in our eleventh year and this claim is still true. All our courses are conducted by correspondence and our syllabus includes Brit.I.R.E., City and Guilds exams. Also maths, physics and radar. Nothing succeeds like success and what we have done a thousand times already for your colleagues, we can do again, for you—and all for £1/1/- per month. Free booklet from **BRITISH NATIONAL RADIO SCHOOL**, 66, Addiscombe Road, Croydon, Surrey. (Telephone: ADDiscombe 3341.)

**NORWOOD TECHNICAL COLLEGE**, W. Norwood, London, S.E.27. Full-time, part-time day and evening courses in Radio and Television (Technology and Servicing), Radar and Line. Preparation for following examinations: C. & G. Full Technological, R.T.E.B., Amateur Transmitting Licence, P.M.G. Free Telecom. Prospectus (B) from the Secretary, (170.)

**SEE THE WORLD**—600 Radio Officers required. Send 2d. stamp for prospectus to Britain's leading college. We train most in shortest period, at lowest cost. **WIRELESS COLLEGE**, Colwyn Bay.

**WIRELESS.**—Postal Course in theory for Amateur Transmitting Licence, complete with text-book at moderate fee; also instruction at school for P.M.G.'s Certificates to become Radio Officers in Merchant Navy at good salaries. Recognised by Ministry of Education. Apply, B.S.T., LTD., 179, Clapham Road, London, S.W.9. (Estd. 1906.)

**MERCHANT NAVY** and Air Radio. Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses. S.A.E. Prospectus from Director, **THE WIRELESS SCHOOL**, 21, Manor Gardens, Holloway, London, N.7. (Estd. 30 yrs.) (Phone: ARC 3694.)


**THE INSTITUTE** of Practical Radio Engineers have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E. Service, entry and progressive exams. Tuition fees at pre-war rates are moderate. The Syllabus of Instructional Text may be obtained, post free, from the **SECRETARY**, Fairfield Road, Crouch End, N.8.

**NUTS, BOLTS**, etc., ass. 2/- lb., 6d. boxes; Crystal Sets, 5/6; Midget Speakers on baffles, 5/-, in cases, 6/6; Midget Components, List 23d. **CARTER'S**, 67, Bell Lane, Marston Green, Birmingham.

**SYNCHRONOUS MOTORS**, 200-250v. A.C., 50 cycles, clock type, 12/6 each. 1/- postage; suitable for model engineers. **UNIVERSAL ELECTRICAL**, 217a, City Rd., London, E.C.1.

**WALNUT RADIOGRAM CABINETS**; sample designs; few only; stamp details. **SHAW**, 69, Fairlop Rd., E.11.

IR5, 9/-; 6V6, 9/6; EF91, 11/6; MU14, 9/-; 1T4, 9/-; 6K8, 12/6; EF55, 12/6; VR92, 3/6; 1S4, 9/-; 6Z4, 9/-; 6J6, 12/6; 50L6, 10/6; CCH35, 12/6; 6A7, 15/6; 6L6, 12/6; E1148, 4/6, etc., etc. BVA stocks at pre-budget prices. **ELECTROLYTICS**, 8/500v., 2/6; 16/450v., 3/6; 16/24 350v., 5/-; 25/25, 1/6. Speakers, 3in., 11/6; 5in., 13/6, Post 6d. List 21d. **V/CONT.** W SW, L spindle 1 and 1 meg., 3/6. 1lb. reel Multicore solder 16G 4/3. **TRS, 71 Meadvale Rd., E. Croydon**  
Callers: 2 Pawsons Rd., W. Croydon. **THO 1665**

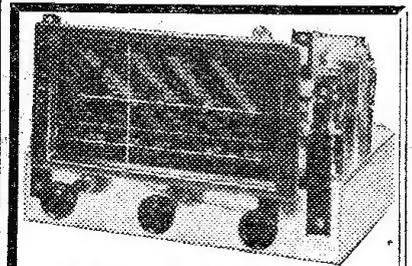

**BUILD**  
**THIS RADIO & SAVE POUNDS!**

Build radios a completely new and easy way! Our range of aluminium chassis are completely prefabricated for ALL components. These—and our unique Construction Sheets and ALIGNED AND SEALED Tuning Units—enable ANYONE, whether novice or expert, to build a variety of domestic receivers, feeder units and quality amplifiers with the sure knowledge that failure is impossible!

Full details of this 5 valve Superhet, and many other sets (including circuits and parts) in the NEW EDITION of our famous "HOME CONSTRUCTOR'S HANDBOOK," which has been acclaimed the world over. From the vast quantities sold, also from letters in our files, there is no doubt this book satisfies EVERYBODY interested in radio. If by chance, you haven't had a copy you really are missing to-day's best value! Send us NOW for the latest issue, price 2/-. (Worth very many times this purely introductory price.)

**RODING LABORATORIES**  
(OF ILFORD)

MAIL ONLY to:—Dept. P.W.J.  
694, LEA BRIDGE ROAD, E.10.

# RADIO SUPPLY CO.

34, Hanover Street,  
Park Lane, Leeds

**BRAND NEW GUARANTEED GOODS**  
TERMS.—C.W.O., or C.O.D. over £1 postage  
1/2 extra on orders under £2.

## R.S.C. MAINS TRANSFORMERS

Fully interleaved and impregnated.  
Primaries 200-230-250 v. 50 c/c's. Screened.  
**HALF SHROUDED DROP THROUGH**  
280-0-280 v. 70 m.a., 6.3 v. 2 a., 5 v. 2 a. 12/11  
350-0-350 v. 70 m.a., 6.3 v. 2 a., 5 v. 2 a. 14/11  
350-0-350 v. 90 m.a., 6.3 v. 3 a., 5 v. 2 a. 19/9  
250-0-250 v. 100 m.a., 6.3 v. 6 a., 5 v. 3 a.  
For R1355 Conversion ... 23/11  
350-0-350 v. 150 m.a., 6.3 v. 4 a., 5 v. 3 a. 27/11  
350-0-350 v. 100 m.a., 6.3 v. 4 v. 3 a.,  
C.T., 0.4-5 v. 3 a. ... 21/11

**FULLY SHROUDED UPRIGHT**  
250-0-250 v. 60 m.a., 6.3 v. 2 a., 5 v. 2 a.,  
Midget type 2 1/2-3 in. ... 16/11  
350-0-350 v. 70 m.a., 6.3 v. 2 a., 5 v. 2 a. 18/9  
250-0-250 v. 100 m.a., 6.3 v. 4 v. 3 a.,  
C.T., 0.4-5 v. 3 a. ... 23/9  
250-0-250 v. 100 m.a., 6.3 v. 6 a., 5 v. 3 a.,  
For R1355 Conversion ... 26/9  
350-0-350 v. 100 m.a., 6.3 v. 4 v. 3 a.,  
C.T., 0.4-5 v. 3 a. ... 23/9  
350-0-350 v. 150 m.a., 6.3 v. 2 a., 6.3 v.  
2 a., 5 v. 3 a. ... 31/-  
425-0-425 v. 200 m.a., 6.3 v. 4 v. 4 a.  
C.T., 6.3 v. 4 v. 4 a. C.T., 0.4-5 v. 3 a.  
Suitable Williamson Amplifier ... 47/9

**OUTPUT TRANSFORMERS, Push Pull**  
10-12 watt to match 6V6, 6L6, 6X4,  
etc. to 3-5-8 or 15 ohm Speaker ... 15/11  
15-18 watt for 6V6, 6L6, etc., to 3 or  
15 ohms ... 21/9

Williamson type exact to author's spec. 72/-  
**SMOOTHING CHOKES**.—80 m.a. 12 h. 350  
ohms, 5/6; 100 m.a. 10 h. 100 ohms, 7/6; 200  
m.a. 5 h. 100 ohms, 7/6; 200 m.a. 10 h. 100  
ohms, 11/9.

**ALUMINIUM RECEIVER CHASSIS**.—  
Undrilled 16 s.w.g., 10-51-2ins., 3/8; 11-6-  
2ins., 3/9; 12-8-2ins., 4/6; 16-8-2ins., 5/6.  
FULL LIST 3d. SPECIAL LIST FOR  
TRADE, 3d. FOR EX-GOVT. ITEMS SEE  
CLASSIFIED ADVT.

# ALPHA OFFERS

## SPEAKERS

5in. Goodman P.M., 2/3 ohms ... 13/6 each  
6in. Truevox P.M., 2/3 ohms ... 13/9 each  
6in. Rola Type 6Z, Field 1,140  
ohms, with output transformer 15/9 each  
8in. R. & A. Mains Energised ... 16/9 each  
10in. Goodman P.M., 15 ohms ... 25/- each

**INVICTA SPEAKER CABINETS**  
With carrying handle, size 17in. x 17in. x 6in.  
to take a 10in. Speaker unit, Sprayed brown,  
13/6 each.

## METAL RECTIFIERS

L.T. 2V. 1/2 amp. ... 5/- each  
L.T. 12v. 1/2 amp. ... 1/- each  
H.T. 300v. 80 m/A. ... 4/9 each  
H.T. 230 v. 60 m/A. ... 4/6 each

## VOLUME CONTROLS

1/2, 1 and 2 meg. Morganite with  
switch ... 4/3 each  
2K ohms, 3K ohms, 5K ohms, 10K,  
15K, 25K, and 35K ohms, less switch 2/3 each

**BUZZERS**.—For Battery working,  
suitable for doors, etc. ... 1/6 each  
**BELL PUSH**, with warning light,  
numerous uses, ideal for offices 1/6 each

**CAR BULBS**, 6-7 volt, 18 watt.  
Headlamp or Spot Lamp, out-  
standing value ... 1/6 each

**HEAVY DUTY ROTARY  
COOKER SWITCH**, 30 amp. 4  
position ... 4/- each

## VALVES

Guaranteed new and boxed.  
12K8, 6V6, 6P6, 5ZAM, 0Z4, 1S5, 1R5, 1S4,  
3S4, 1T4, 5U4G, 6D6, FWO/500, VU39, 6C6,  
78, all at 9/-, EF8, EF36, 7Q7, EK32, EL32,  
12A6, 12H6, 12SG7, 12AH7G, 6AC7, 12SH7,  
12SK7 6N7, 6G6G MS/Pen, 6C5, 6K7, 6J7,  
6B8, all at 7/9.  
VS39, 14F6G, DLS10, at 6/-.  
DDLA, SP61, VU111, 955, VR54, CV73, at 5/-.  
VU120A, 215SG, 2X2, PEN 220A, 37, at 4/-.  
954, 956, SF41, E1148, V161A, 7193, at 3/9.  
C.W.O. or C.O.D. Carriage Paid over £2.  
For Lists send Stamp. Post Orders only.

# ALPHA RADIO SUPPLY CO.

5/6 Vince's Chambers,  
Victoria Square, LEEDS, I.

**OUTPUT TRANSFORMERS**. Parallel  
P/P 6L6's to 200 and 500 ohms.  
Secondaries. 50-75 watts output, size  
4 1/2 in. x 5 in. x 5 in. Brand New, 17/6.  
**BATTERY AMPLIFIER**. A1134 Com-  
plete with 210LF and QP21 valves 2 volt  
and 120 volt. 12/6

**RECTIFIERS**. 12 v. 2 amps. Westing-  
house bridge type. Brand New. Ideal for  
Battery Chargers or Relay Operations. 11/6  
**ROTARY CONVERTOR**. 6 v. D.C. to  
190 v. 80 m/a. Ideal for portable rigs and  
Car Radio. H.T. 8/6

**MODULATION TRANSFORMERS**.  
U.S.A. manf. Potted. P/P 211 to single  
211 Ratio 1 to 1.2, 100 Watt size. Suitable  
P/P 807's to 807 single. 6/-

**DRIVER TRANSFORMERS**. Class B.  
Suitable 6L6 to P/P 807's with monitor  
windings. 6/-

**OUTPUT TRANSFORMERS**. P/P 3  
ratio 45 m.a. twice. 32-1, 55-1, 80-1.  
Brand New and Boxed. 5/-

**OUTPUT TRANSFORMERS**. 60 m/a.  
3 ratio 32-1, 55-1, 80-1. Brand New and  
Boxed. 5/-

**OUTPUT TRANSFORMERS**. 60 m/a.  
6V6 to 3 ohms Speaker. Brand New and  
Boxed. 4/6

465 IF's TRANSFORMERS, Standard  
Size. 5/- pr.

**CONDENSERS**. 6 Mfd. 2,000 v. Test. 3-  
**CONDENSERS**. 1 Mfd. 1,500 v. Wkg.  
Cornell Dubilier Porcelain Insulated  
Terminals. 4 1/2 in. x 1 1/2 in. Ideal for  
Scopes. 2/6

**HAND MIKES**. Moving Coil with switch.  
3/5


Please add something for postage.  
**MONEY BACK GUARANTEE**.  
Send P.C. for Lists.

# RADIO MAIL ORDER COMPANY

64-65, CHURCH LANE,  
WOLVERHAMPTON

**Preciton**

**5 VALVE  
RADIO-  
GRAM  
CHASSIS**

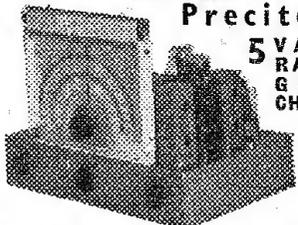

16-2,000 metres.  
Triode output  
stage. Floodlit  
Perspex scale.  
Price £15-15-0.  
Also 7-valve  
model at £21-15-0  
and 9-valve De  
Luxe chassis at  
£25-5-0. Data  
sheets on request.

**ELECTRO  
Acoustic  
DEVELOPMENTS**  
15 Broad Road,  
Willingdon, Sussex

**"GLOBE-KING"**

Amateur Radio. Beginners should send  
for our interesting free literature and  
catalogue (enclose stamp for postage)  
"Globe-King" Amateur Short Wave  
Radio Kits from as low as 25/- to 99/6,  
post paid. Direct from makers:  
**JOHNSONS (Radio)**  
46, Friar St., WORCESTER.

**SUPACOILS**

**OFFER**

★ **COILS**.—A complete range of High Q  
variable iron dust cored coils in  
wavelengths 10-30, 18-50, 30-75, 75-200,  
190-550 and 800-2,000 metres; Aerial  
H.F. or Oscillator. — As recom-  
mended for the Practical Wireless  
9 valve All-wave Superhet. 3/- each.

★ **COIL GROUPS**.—The increasing  
popularity of our recently intro-  
duced Coil Groups proves that more  
and more Constructors are finding  
them an invaluable aid to set building.  
Coil Group "A" consists of 6 of the  
above coils (your own selection), 1  
Miniature 4p 3w rotary switch, 2  
fixed padders (to suit coils selected),  
6 variable trimmers. Complete  
group. £1.9.0.  
Coil Group "B" consists of 9 of the  
above coils (your own selection), 1  
rotary 7p 4w switch (3 w/bands and  
gram.), 2 fixed padders (to suit coils  
selected), 9 variable trimmers.  
Complete group. £2.7.6.

★ **COMPONENTS**.—Complete range of  
good quality components in stock.  
Models 20 and 40 Coil Packs and  
Tuning Units, Chassis, Chokes,  
Condensers, Trimmers, Switches, etc.

★ **LOUDSPEAKERS**.—5in. P.M.  
15/- each.

★ **FREE**. Home Constructor's Hand-  
book, containing 11 tested circuits  
forwarded FREE with orders of 20/-  
or more, or obtainable for 2/- from:

**SUPACOILS MAIL ORDER OFFICE**,  
98, Greenway Avenue, London, E.17.

# MORSE CODE Training

**COURSES for  
BEGINNERS and  
OPERATORS**, also  
a **SPECIAL COURSE**  
for passing the G.P.O.  
Morse Test for  
securing an  
**AMATEUR'S  
TRANSMITTING  
LICENCE**.

Send for the **Candler  
BOOK OF FACTS**  
It gives details of all  
Courses.

**THE CANDLER SYSTEM CO.**  
(Dept. 5LO), 52b, Abingdon Road,  
Kensington, London, W.8.  
Candler System Co., Denver, Colorado, U.S.A.

# WOT! NO BRAND NEW VALVES?!

Don't worry, we still have a good selection at  
keenest prices. (Send for List.). But this month  
here are some other brand new goods we can offer:

**LOUDSPEAKERS** (surplus).—"Rola" 6in. en-  
ergised, 13/- (2/6 post and packing). **HIGH-VOLTAGE  
CONDENSERS** Mica (high R.F. current), .01 (2kv.  
wkg.), .001, .0008, .0006 (5kv. wkg.), 10d. each.  
Other types: mica, .015, 1/-; .002, 10d.; .00025,  
8d.; ceramic, 50 pf., 3in. dia., 3in. long, 8d.  
(all 2500v. wkg.). **SPECIAL MICA TYPE** with  
extended tags (made for R.C.A. transmitter), .01,  
6d. **METAL CASE CONDENSERS**, 1+1 (500v.),  
5+5 (400v., American), 1+; .25, 6d. **RESISTORS**;  
5-watt, 500, 700, 3k, 4k, 5-6k, 12k, 20k, 30k, 200k,  
8d., 7/- doz. **HIGH-VOLTAGE VALVE CAPS**;  
8d. **FLEXIBLE SHAFT COUPLERS**; 1-  
**CERAMIC SPACERS** (for aerial feeders, etc., 6in.  
spacing), 5/- doz. **VALVE HOLDERS**; B9C, 6d.;  
I.O. (Amphenol), 9d. **SYSTOFLEX SLEEVING**  
(1-5 mm.), 12yds. or more, 1d. per yd. (less, 1 1/2  
per yd.). (4 colours available).  
Orders over £1 post free.  
**REED & FORD**  
2A, BURNLEY ROAD, AINSDALE, SOUTHPORT

# RADIO G200 ANNOUNCES

**RADIO VALVES**, all at 7/6, by return  
post. C.W.O. or C.O.D.

- |       |       |          |
|-------|-------|----------|
| 6SA7  | 6N7GT | 6AC7     |
| 6K6   | 12SG7 | AC6Pen   |
| 6K7G  | 1CSGT | VU120A   |
| 6K7GT | 6D6   | VU111    |
| 6J5GT | 6C4   | 12SH7    |
| 6J5   | 9006  | 2X2A     |
| 6J7G  | 6L7   | 6N7G     |
| 6J7   | 1625  | CV66     |
| 6K7GT | TT11  | 6K7G     |
| 3A4   | VT501 | 6SQ7     |
| 8012  | EF22  | 3B7/1291 |
| 6SG7  | EF8   |          |

Trade and Overseas enquiries invited.

# ARTHUR HOILE

55, Union Street, Maidstone, Kent  
Phone: 2812

# Practical Wireless BLUEPRINT SERVICE

## PRACTICAL WIRELESS

*No. of  
Blueprint*

### CRYSTAL SETS

- Blueprints, 1s. each.  
1937 Crystal Receiver .. PW71\*  
The "Junior" Crystal  
Set .. .. PW94\*

### STRAIGHT SETS

Battery Operated

- One-Valve : Blueprints, 2s. each.  
The "Pyramid" One-  
valver (HF Pen) .. PW93\*  
Two-valve : Blueprints, 2s.  
The Signet Two (D &  
L F) .. .. PW76\*  
Three-valve : Blueprints, 2s. each.  
Summit Three (HF Pen,  
D, Pen) .. .. PW37\*  
The "Rapide" Straight  
3 (D, 2 LF (RC &  
Trans)) .. .. PW82\*  
F. J. Camm's "Sprite"  
Three (HF, Pen, D,  
Tet) .. .. PW87\*

- Four-valve : Blueprints, 2s. each.  
Fury Four Super (SG,  
SG, D, Pen) .. .. PW34C\*

Mains Operated

- Two-valve : Blueprints, 2s. each.  
Selectone A.C. Radio-  
gram Two (D, Pow) PW19\*  
Three-valve : Blueprints, 2s. each.  
Double - Diode - Triode  
Three (HF Pen, DDT,  
Pen) .. .. PW23\*  
Four-valve : Blueprints, 2s. each.  
A.C. Fury Four (SG, SG,  
D, Pen) .. .. PW20\*  
A.C. Hall-Mark (HF  
Pen, D, Push-Pull) .. PW45\*

### SUPERHETS

- Battery Sets : Blueprints, 2s. each.  
F. J. Camm's 2-valve  
Superhet .. .. PW52\*

*No. of  
Blueprint*

### SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprint, 2s.  
Simple S.W. One-valver PW88\*  
Two-valve : Blueprints, 2s. each.  
Midget Short-wave Two  
(D, Pen) .. .. PW38A\*  
Three-valve : Blueprints, 2s. each.  
Experimenter's Short-  
wave Three (SG, D,  
Pow) .. .. PW30A\*  
The Perfect 3 (D, 2 LF  
(RC and Trans)) .. PW63\*  
The Band-spread S.W.  
Three (HF Pen, D  
(Pen), Pen) .. .. PW68\*

### PORTABLES

- Four-valve : Blueprint, 2s.  
"Imp" Portable 4 (D,  
LF, LF, Pen) .. PW86\*

### MISCELLANEOUS

- Blueprint, 2s.  
S.W. Converter-Adapter  
(1 valve) .. .. PW48A\*

## AMATEUR WIRELESS AND WIRELESS MAGAZINE

### STRAIGHT SETS

Battery Operated

- One-valve : Blueprint, 2s.  
B.B.C. Special One-  
valver .. .. AW387\*  
Two-valve : Blueprints, 2s. each.  
A modern Two-valver .. WM409\*

Mains Operated

- Two-valve : Blueprints, 2s. each.  
Consoelectric Two (D,  
Pen), A.C. .. .. AW403

### SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of  
Blueprint*

### SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprints, 2s. each.  
S.W. One-valver for  
America .. .. AW429\*  
Two-valve : Blueprints, 2s. each.  
Ultra-short Battery Two  
(SG, det Pen) .. .. WM402\*  
Four-valve : Blueprints, 3s. each.  
A.W. Short-Wave World-  
beater (HF Pen, D, RC,  
Trans) .. .. AW436\*  
Standard Four-valver  
Short-waver (SG, D,  
LF, P) .. .. WM383\*

Mains Operated

- Four-valve : Blueprints, 3s.  
Standard Four-valve A.C.  
Short-waver (SG, D,  
RC, Trans) .. .. WM391\*

### MISCELLANEOUS

- Enthusiast's Power Am-  
plifier (10 Watts) (3/-) WM387\*  
Listener's 5-watt A.C.  
Amplifier (3/-) .. WM392\*  
Harris Electrogram  
battery amplifier (2/-) WM399\*  
De Luxe Concert A.C.  
Electrogram (2/-) .. WM403\*

### HINTS COUPON

This coupon is available until July 2nd, 1951, and must accompany all Practical Hints.  
PRACTICAL WIRELESS, JULY, 1951.



**79/6**  
Post free


## Press-button soldering! The "BURGOYNE" 7-SECOND SOLDER GUN

Here's the tool every home handyman has always wanted. This amazing new tool saves electricity bills. Makes soldering child's play. No current used unless actually making a joint; cold when not in use; no element to burn out; heats up in 7 seconds; no risk from touching the "wrong end." No constant re-tinning. Ideal for handyman or radio enthusiast.

SPARE BITS AVAILABLE, 7/6 for ten.

A.C. only 200-250 v.

## A "SIX-in-ONE" KNIFE

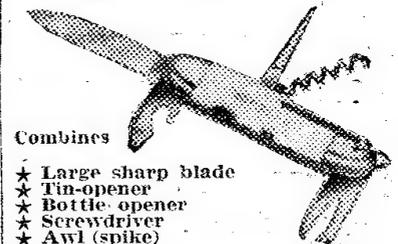

Combines

- ★ Large sharp blade
- ★ Tin-opener
- ★ Bottle-opener
- ★ Screwdriver
- ★ Awl (spike)
- ★ Corkscrew
- ★ Safety ring

A really useful knife of high-grade steel with dozens of uses. "Pearl-teen" handle.

ONLY  
**7/6**  
Plus 6d. Postage

## B.S.R. TAPE & WIRE RECORDER MOTORS

This small induction motor is specially designed for magnetic tape and wire recorders. Absolutely silent in operation and virtually free from vibration. Minimum stray magnetic field for A.C. mains 100-250 v. 50 cycles.

**38/-** Post free.



**£12-1-6**  
carriage paid

## DECCA TWIN-SPEED (78 & 33½ r.p.m.) RECORD PLAYERS Type 37A

Manufactured by the pioneers of long-playing technique on a commercial scale in this country, the Decca 37A Twin-speed Player gives the user facilities for playing both Long-playing and Standard records on the same machine.

The turntable is mounted on a heavy, pressed-steel base and the change-over from 78 to 33-1/3 r.p.m. is accomplished by a simple but positive lever movement.

Instead of the usual interchangeable heads, the crystal element of the pick-up is rotated to change from a 78 r.p.m. stylus to a 33-1/3rd r.p.m. stylus.

A compact and reliable unit, the 37A Player gives not only first-class reproduction, but first class value for money.

Fully Guaranteed

We stock a full range of  
**VIEWMASTER COMPONENTS**  
which are available on cash or  
**HIRE PURCHASE TERMS**  
Your enquiries will be welcomed

TERMS: CASH WITH ORDER

**M.O.S** MAIL ORDER SUPPLY CO., THE RADIO CENTRE,  
33, Tottenham Court Road, London, W.1 MUS. 6667

# LASKY'S RADIO

### RECEIVER UNITS TYPE 25.

The receiver section of the TR1196 equipment. Easily converted to an all-wave receiver. 6 Valve superhet. Valve line-up:— 2 EF36; 2 EF39; 1 EK32; 1 EBC33. Full details and circuits supplied free with each receiver. Slightly soiled, but unused. **LASKY'S PRICE 35/-** Carriage 4/6 extra.

### EX-A.H. RADAR INDICATOR UNIT TYPE 62.

Unused but soiled. Containing 20 valves and a 6in. C.R. tube type VCR97. Valve line-up:—16 SP61; 2 EA50; 2 EB34. Dozens of components, resistances, coils, condensers, 117 Mc/s crystal pot. meters, etc. Totally enclosed in metal case. Size: 18in. x 9in. x 11in. Weight 40lb. Enamelled grey or black with coloured control knobs.

**LASKY'S PRICE 89/6**

Carriage 10/- extra.

### RADAR INDICATOR UNITS TYPE 162C.

BRAND NEW IN MAKER'S ORIGINAL WOOD CASE. Contains 2 cathode ray tubes, 1 6in. VCR517 and 1 3in. VCR139. Also the following valves: 3 SP61; 1 6J5; 3 EA50; 1 D1. Dozens of components, coils, resistances, condensers, 7 pot. meters, etc. Enclosed in metal case, size 12in. x 9in. x 10in. Weight 40lb. **LASKY'S PRICE 79/6.** Carriage 7/6 ex.

**COIL PACKS. BUY NOW AT PRE-BUDGET PRICES.** WEYMOUTH. Long, medium and short. Simple fixing. For use with 465 kc/s I.F.

**LASKY'S PRICE 39/6.** Postage 1/6 extra.

**OSMOR TYPE "Q" COIL PACKS.** Supplied complete with circuit diagrams. Simple single hole fixing. S'het for 465 kc/s I.F. These coil packs are aligned and tested in actual frequencies. All prices include purchase tax. Long, medium, short (LMS) 44/-, with H.F. stage, 62/4. Long, medium and trawler band (LMTB), 45/10. Medium, short, short (MSS) 42/10. Batt. s'het with frame aerial, 45/10.

**VALVES. LARGE STOCKS.** Over 15,000 valves now in stock. D.V.A., ex-Government and Manufacturers' Surplus. **WRITE FOR VALVE LIST. PRICES ARE RISING—BUY NOW.**

**SAFETY FIRST.** Fused test prods. Fully insulated pencil type with retractable point. Contact is only made when desired by pressing top. Each prod contains a cartridge type fuse and spring.

**LASKY'S PRICE 4/11** per pair (one red, one black). Post 6d. extra.

**V.H.F. RECEIVER UNITS.** Contains 8 valves: 4 EF50; 1 EL32; 2 EF39; 1 EBC33. Also many useful components, coils, condensers, resistances, etc. Frequency covers 124 Mc/s. This is a superhet unit with an R.F. stage and three I.F. stages. Dimensions: 10½in. x 7½in. x 6in.

**LASKY'S PRICE, specially selected, 35/-,** carriage 5/- extra; soiled units, 29/6, carriage 5/- extra.

**EX-A.M. RECEIVERS TYPE R1481.** BRAND NEW AND UNUSED, IN ORIGINAL WOOD CASES. Frequency coverage: 60-86 Mc/s. Description: Contains 11 valves: 1 VR65; 1 VR66; 4 VR53; 2 VR54; 1 6J5; 1 VS70; 1 VR87. Large tuning scale with slow motion drive, 0-5 m/a tuning meter, R.F. and L.F. gain controls, jack sockets for line and 'phone. Totally enclosed in metal case, grey enamelled, with plated handles. Size 18in. x 10in. x 11in. Weight packed, 5½lb. Supplied complete with circuit and calibration chart.

**LASKY'S PRICE 99/6 each.** Carriage 10/- extra.

# LASKY'S RADIO, 370, HARROW ROAD, PADDINGTON, LONDON, W.9 (Opposite Paddington Hospital.)

Telephone: CUNningham 1979 and 7214.

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. half day. Send a 2½d. stamp with your name and address (in block letters please) for a copy of our current list of new manufacturers surplus and ex-Government equipment. The Lasky's Radio Bulletin.