


1/-

Vol. 77 No. 542

DECEMBER, 1951

EDITOR:
F.J. CAMM

PRACTICAL WIRELESS

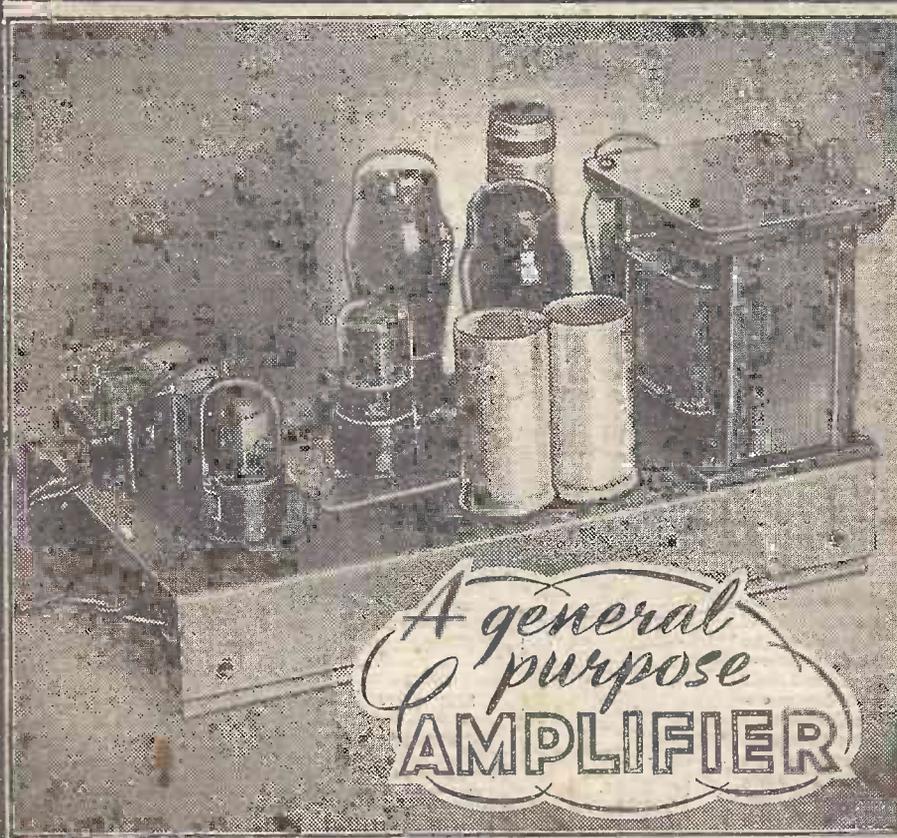

IN THIS ISSUE

SCREEN MODULATION
RADIOGRAM COMBINATIONS
REPAIRING DIAL DRIVES

50 YEARS OF RADIO
SHORT-WAVE SECTION
FREQUENCY MODULATION

If you must have a fit... fit an OSMOR 'O' COILPACK



—for easy assembly and whistle-free reception. No complicated wiring circuits—just five simple connections for the OSMOR, pre-aligned Coilpack to be installed—and you're all set for receiving 'Loud and Clear.' All types available for battery and mains, with full instructions and circuit diagrams.

As specified for conversion of the Type 25 unit of the TR.1193, also Type 18 and Warbirds utility receivers, etc.



Send 5d. (stamps) for complete receiver circuits, also lists of Coils, Coilpacks and all Radio Components.

OSMOR RADIO PRODUCTS LTD.
 (Dept. P.19.), BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY.
 Telephone: Croydon 514819

The solder for all HOME TELEVISION CONSTRUCTOR SETS

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60/40 High Tin Television and Radio Alloy. The size 1 Carton contains 37 feet of solder, costs 5/-.



Ersin Multicore Solder
 In case of difficulty in obtaining supplies, please write to:
MULTICORE SOLDERS LTD.,
 MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1 • REGent 1418

Come to **SMITH'S** of **EDGWARE ROAD**, the friendly shop, for all radio components

We stock everything the constructor needs—our 25 years' experience of handling radio parts and accessories enables us to select the best of the regular lines and the more useful items from the surplus markets in:—

- | | |
|--|--------------------------|
| Loudspeakers and Phones | Valves and CR Tubes |
| Transformers and Chokes | Cabinets and Cases |
| Meters & Test Equipment | Capacitors and Resistors |
| Pickups and Turntables | Coils and Formers |
| Switches and Dials | Plugs and Sockets |
| Metalwork and Bakelite | Aerials and Insulators |
| Books and Tools | Motors and Generators |
| Valveholders and Cans | Wires and Cables |
| Metal Rectifiers | Panel Lights and Fuses |
| Sleeving, Nuts and Bolts, Tags, Clips, Grommets and all other bits and pieces. | |

NOTHING TOO LARGE—NOTHING TOO SMALL
 Everything you need under one roof—including all the parts specified for the "Viewmaster," "E.E." and "Easybuilt" Home-Constructor Televisors, both London and Birmingham models (No catalogue available.)

H. L. SMITH & CO. LTD.
287/9 Edgware Road, London, W.2
 Telephone: Paddington 5891
 Hours 9 till 6 (Thursday 1 o'clock)
 Near Edgware Road Stations, Metropolitan and Eckerlo

- BATTERIES.** 72 v. (Layer), plus 1.5 v., 6/6.
AMPLIFIER 1135A, less valves, 8/6.
P40 UHF RECEIVERS, with 10 valves, covering 55,95 mc/s. Brand New. 69/6 with circuit.
MIDGET AMPLIFIERS, 5in. x 3in. x 3in., with two 12SJ7's and one 12SH7. 13/6 (Carriage 1/6).
TRANSMITTER 21. Sending speech CW or MCW, these are complete with valves, control panel, and Key. The PA coils (not formers) and relays have been stripped by the M.O.S., but may easily be replaced with our circuit and instruction sheet. Tuning 4.2-7.5 and 18-31 mc/s. In first-class condition. **OUR PRICE, 25/-.**
CARRIER LEVEL ("S") METERS (2 mA.). 2in. square, flange mounting. New and Boxed. 7/6 (Post 6d.).
VIBRATOR PACK 21. Delivering approx. 140 v. at 40 mA. from 6 v. input. These include a LT filter, and contain two metal rectifiers, six 1, two 4 μF, two 75 μF condensers, etc., five chokes, vib. transformer, etc. 16/6.
ACCUMULATORS. Multi-plate, in unspillable celluloid cases. 7 AH, 2 v. 3in. x 1in. x 4in., 6/6. 20AH, 2 v., with built-in hydrometers (ex 58 set), 15/-.
RECEIVER 1225. Complete with five EF50's, two EF39's, one EB34, these are ideal for 2 metres. **ONLY 39/6.** 1/6 Post.
POWER PACK 532, with one 5Z4, one VU120 (5KV), high voltage rectifier, two high cycle transformers, choke, etc. 19/6, complete with our 50 cps. EHT or HT conversion.


We have a number of bargains for callers only: P40 UHF Rx's., 45/-, wavemeters from 5/-, control units, test sets, etc., etc. Quantities are too small to advertise.

RADIO EXCHANGE CO.
9, CAULDWELL STREET, BEDFORD
 Phone: 5563

A *New* WINDSOR TEST METER

20,000 o.p.v.

MODEL 77A

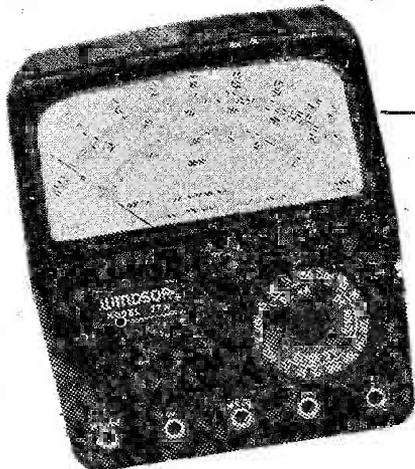

An entirely new instrument incorporating the latest improvements in manufacturing technique. Refinements include shockproof moulded case, clear and easy to read scales and many other features.

SENSITIVITY

20,000 ohms per volt D.C.
5,000 ohms per volt A.C.

METER

Precision engineered moving coil, fitted with 5in. scale and knife edge pointer.

RANGES

VOLTS D.C.: 0-7.5-30-75
—300-750-3,000.

VOLTS A.C.: 0-7.5-30-75
—300-750.

RESISTANCE: 10 ohms-
5 megohms in two ranges,
self contained.

MILLIAMPS D.C.: 0-15
—15-15-150-1,500.

AMPERES D.C.: 0-15.

OUTPUT: As for A.C.
voltage ranges except 3,000 v.,
via a condenser.

Please write for illustrated leaflet featuring our new range of radio and television test gear.

List Price £16.0.0

TAYLOR ELECTRICAL INSTRUMENTS LTD.

419-424, MONTROSE AVENUE, SLOUGH, BUCKS.

Phone: SLOUGH 21381.



ELECTROLYTIC CONDENSERS

The choice of T.C.C. Condensers by so many knowledgeable manufacturers is testimony to their worth.


'LECTROPACK' ETCHED FOIL ELECTROLYTICS

Cap. μ F.	Peak Wkg.	Length	Dia.	Type No.
8-32	275	2 3/4 in.	1 in.	CE34HE
60-100	350	4 1/4 in.	1 1/8 in.	CE37LEA
8-16	450	2 1/2 in.	1 in.	CE34PEA
32-32	450	4 1/4 in.	1 1/8 in.	CE37PE
100-100	350	4 1/4 in.	1 1/8 in.	CE36LEA



'PICOPACKS' MINIATURE ELECTROLYTICS (Plain Foil)


Capacity μ F.	Peak Wkg. Volts	Dimensions		Type No.
		Body Lgth.	Dia.	
8	6	1 1/8 in.	.25in.	CE72A
20	12	1 1/8 in.	.34in.	CE30B
30	15	1 1/8 in.	.43in.	CE71B
10	25	1 1/8 in.	.34in.	CE30C
5	50	1 1/8 in.	.34in.	CE30D
2	150	1 1/8 in.	.34in.	CE30G
1	350	1 1/8 in.	.34in.	CE30N

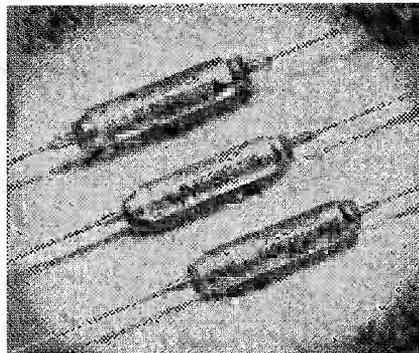

(Regd.)

THE TELEGRAPH CONDENSER CO. LTD.

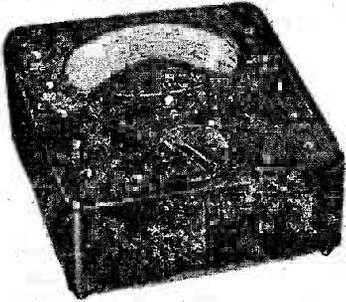Radio Division: North Acton, London, W.3. Tel: Acorn 0061



'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark.

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set.

The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance: 22 ranges of readings on a 3-inch scale: Total resistance 200,000 ohms.

Size: 4½ ins. x 3½ ins. x 1½ ins.
Nett weight: 18 ozs.

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

Price: £10 : 10 : 0

D.C. Voltage
0-75 millivolts
0-5 volts
0-25 "
0-100 "
0-250 "
0-500 "

A.C. Voltage
0-5 volts
0-25 "
0-100 "
0-250 "
0-500 "

D.C. Current
0-2.5 milliamps
0-5 "
0-25 "
0-100 "
0-500 "

Resistance
0-20,000 ohms
0-100,000 "
0-500,000 "
0-2 megohms
0-5 "
0-10 "

GUARANTEE: The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new Avominor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

The D.C. AVOMINOR

is a 2½-inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4½ ins. x 3½ ins. x 1½ ins.
Nett weight: 12 ozs.

Complete as above
Price: £5 : 5 : 0

Sole Proprietors and Manufacturers:—

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder House, Douglas Street, London, S.W.1. Phone: VICtoria 3404-9



high fidelity MICROPHONES

FOR PUBLIC ADDRESS, RECORDING, AMATEUR RADIO

TYPE MIC 22 incorporates the famous Acos "Filtercel" insert, giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 cps. The microphone is vibration and shock-proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head:—



MIC 22-1 is for fitting to any British or American type standard floor stand and can also be used as a hand microphone.



MIC 22-2 is supplied as a complete unit incorporating an attractive desk stand with side cable entry.

PRICE £6.6.0 (Either Model)

TYPE MIC 16 incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 cps. Performance is unaffected by vibration or shock and low frequency wind noise. As in the case of the MIC 22 described on the left two alternative mountings are available for the MIC 16 head:—



MIC 16-1 is ready for fixing together British or American type floor stands by means of a knurled ring.



MIC 16-2 is a complete desk stand unit with side cable entry.

PRICE £12.12.0 (Either Model)

Practical Wireless

EVERY MONTH
VOL. XXVII. No. 542 DECEMBER, 1951

Editor F. J. CAMM

19th YEAR
OF ISSUE

COMMENTS

By THE EDITOR

ON BBC CRITICS

ALMOST every newspaper in this country has a radio and television critic, and for nearly thirty years that criticism has, on the whole, been adverse. The BBC also has its own internal critics and, of course, its listener research department. Yet after thirty years of criticism the number of licences has steadily increased from a few thousand to 12 millions.

This raises the question of whether criticism of BBC programmes is of value. If we can take the theatre as an ordinary example, it would appear that the answer is in the negative.

Bad shows are still put on, and the critics give their opinions when it is too late. Why not invite the critics to see shows before they are put on the air or on the stage? The bald fact is, as far as radio is concerned, that people will buy a radio licence even though the programmes are uniformly bad, just as in the same manner they will have the telephone laid on even though the service after all these years is full of imperfections.

The BBC is thus in the happy position of being able to ignore criticisms in the full knowledge that it will not affect their licence revenue, and they can fortify that attitude by the inexorable and ineluctable fact that the critics must be wrong and the BBC right, in view of the continued growth in the number of listeners.

Everyone likes to have on tap an instrument for listening to important news. No one has yet given up a licence because the programmes are bad.

It has been suggested that competitive programmes radiated by commercial broadcasting stations would keep the BBC on its toes. We do not think so. The BBC cannot make a loss; its turnover has consistently increased and that is sufficient answer to the critics. This argument does not, of course, apply to the live theatre.

RESALE PRICE AGREEMENTS

THE Government (the one in force at the time this goes to press) in its efforts to delude the public into believing that the high cost of living and the high cost of essential items such as radio receivers and batteries is due to profiteering on the part of the manufacturers instead of to the monstrous Purchase Tax of 66½ per cent.,

threaten to introduce legislation setting aside all of the existing Resale Price Agreements at present in force, and thus virtually destroying the main reason for the existence of trade associations. The policy adopted by the Government is not to abolish such agreements, but to give retailers the right to sell below such minimum prices if they so wish, without fear of disciplinary action being taken by trade associations.

There has been no call on the part of retailers to be permitted to break their agreements with suppliers, nor is there any evidence that retailers charge more than the fixed price.

Proposed legislation is an attempt to reduce the cost of living by taking away some of the reasonable retail profits.

As such agreements have been drawn up at the express desire of retailers, the Government evidently intended to present to the public the impression that trade associations were octopus-like organisations whose tentacles reached to the remotest depths of the purchaser's pocket.

Fortunately, there is not a retailer in the country who will undersell price-maintained goods, if indeed it is ever introduced. Resolutions all over the country have been passed calling upon the Government to refrain from introducing it. Equally, we call upon the Government to reduce and in some cases remove its profiteering Purchase Tax.—F. J. C.

A DELIGHTFUL CHRISTMAS GIFT FOR YOUR FRIENDS AND RELATIONS

At the present time when many of the good things of life are either extravagantly expensive or in short supply, the Christmas Gift Season presents many problems.

There is, however, a simple and effective solution—you can send your friends and relations special subscriptions to **PRACTICAL WIRELESS**.

Christmas Gift Subscriptions are not only original, but give pleasure and act as a reminder of your good wishes the whole year through.

AN ATTRACTIVE GREETINGS CARD WILL BE SENT IN YOUR NAME WITH THE FIRST GIFT COPY.

It is simple to arrange, for we can send subscription copies to any address, at home or abroad, at the annual rate of 13s. 6d. (Canada, 13s.).

Just write to the Subscription Manager, **PRACTICAL WIRELESS** (Dept. G.2), Tower House, Southampton Street, Strand, London, W.C.2; enclosing the addresses of your friends, with remittance to cover and we will do the rest.

ROUND the WORLD of WIRELESS

Radio Servicing Examination, 1951

THE Radio Trades Examination Board and the City and Guilds of London Institute recently announced the results of the Radio Servicing Certificate Examination.

One hundred and seventeen of the 290 candidates, who appeared for the examination held in May, were able to satisfy the examiners in both the practical and written tests. Forty-six candidates, passing the written test only, were referred in the practical, while 19 candidates who had been referred in the practical test in last year's examination, completed the test this year.

Chemical Exhibition

AN impressive Chemical Exhibition, entitled "One Hundred Years of Chemistry," was held on September 27th in the Manchester Civic Centre to mark this year's Dalton Lecture of the Royal Institute of Chemistry. The exhibition, which was presented by eight large north-western industrial companies, was based on the same theme as the "Festival" Lecture and was delivered by Lord McGowan, K.B.E.

Among the exhibits depicting the history of the science in various fields was one by Chloride Batteries, Ltd., following the development of the lead-acid storage battery.

Death of Gramophone Pioneer

WITH the death of Frederick W. Gaisberg, in his 79th year, at his Hampstead home on September 2nd, a link with the fascinating history of the gramophone was broken.

Fred Gaisberg was born in Washington, D.C., and began his professional career as a chorister in a local church. At the age of 21 he became assistant to Emile Berliner and helped him to perfect the disc record. In 1895, in Philadelphia, he was largely responsible for persuading a group of shareholders of the Pennsylvania Railroad Co. to

subscribe 25,000 dollars with which the Gramophone Co. (later to become H.M.V.) was founded.

During 1898 he was appointed chief recordist with the newly formed Gramophone Co. in London and, in 1925, with the coming of modern electrical recording, he was appointed International Artists' Manager to the Gramophone Co. All the great personalities of the gramophone world passed through his hands, including Tamagno, Patti, Melba, Chaliapin, Peter Dawson and, of course, Enrico Caruso.

Although Fred Gaisberg made London his home and the centre from which he made many world-wide recording expeditions, he retained his American citizenship to the end.

Radio at the Motor Show

AT this year's Motor Show, E. K. Cole, Ltd., showed a full range of car-radio models.

Models were mounted on the dashboards of famous cars, such as the Austin "Princess" and

"Sheerline," Alvis three-litre, Daimler, Bristol and Jaguar.

The C.R.117, a six-valve super-het with provision for pre-set medium-wave stations and free tuning on long and medium wavebands, was exhibited in variations for Ford, Daimler and Alvis and a version designed to operate up to four speakers.

On view also was the C.R.61 short-wave model, incorporating such radio requirements as band-spread tuning, seven short-wave ranges, push-pull output and three-position tone control.

Sound Recording and Reproducing Equipment Exhibition

AT the Portsmouth City Council Chambers on Thursday, October 11th, was held an Exhibition of Sound Recording and Reproducing Equipment organised by the local centres of the British Sound Recording Association and the Institution of Electronics.

Eleven exhibitors took stands in the Minor Hall and demonstra-



At the Post Office Research Station at Dollis Hill, a piece of quartz is being sliced by a diamond wheel in the process of making H.F. crystals.

tions of the latest magnetic tape and wire recorders, as well as high-quality pick-up, amplifier and loudspeaker combinations were given between 5 and 10 p.m. In the main Council Chamber Mr. J. W. Clark demonstrated a tape recorder, as supplied to the Admiralty, which is capable of twin-track recording at 1 1/2 in. per second.

World's First Wireless College

OCTOBER 12th marked the 50th birthday of the first wireless college in the world. It was opened by Marconi's Wireless Telegraph Co., Ltd.

It was moved to the Chelmsford works in 1904 and was re-established at its present site in Arbour Lane in 1920. It has since become one of the finest technical colleges in the world.

Facility for Amateurs

PROVIDED that no interference is caused to Government services, radio amateurs in the United Kingdom will soon be allowed to use Frequency Modulation on frequencies within the band 144.5 to 15.5 Mc/s.

This follows negotiations between the G.P.O. and the Radio Society of Great Britain, and the progress and situation will be reconsidered after one year.

Broadcast Licences

THE following figures show the approximate numbers of licences issued during the year ended August, 1951:

Region	Number
London Postal ..	2,359,000
Home Counties ..	1,656,000
Midland ..	1,757,000
North-eastern ..	1,921,000
North-western ..	1,621,000
South-western ..	1,074,000
Welsh and Border Counties ..	733,000
<hr/>	
Total England and Wales ..	11,121,000
Scotland ..	1,113,000
Northern Ireland ..	210,000
<hr/>	
Grand Total ..	12,444,000

The above total includes 933,050 television licences.

B.I.R.E.

THE following meetings of the Institution will be held during November, 1951:

London Section.—Wednesday, November 21st, 6.30 p.m., London

School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1: "Developments in High Frequency Transmitter Cables," R. C. Mildner (Telegraph Construction & Maintenance Co.).

North-eastern Section.—Wednesday, November 14th, 6 p.m., Neville Hall, Westgate Street, Newcastle-on-Tyne: "Television Aerial Design," G. L. Stephens (Belling & Lee).

Scottish Section.—Thursday, November 8th, Institute of Engineers and Shipbuilders, Glasgow, 7 p.m.: "The Brain as a Piece of Communication Equipment," H. W. Shipton, A.M., Brit.I.R.E. (Burd Neurological Institute, Bristol).

The above three meetings will be held jointly with the Scottish Sections of the Institute of Physics.

South Midlands Section.—Wednesday, November 14th, To be held in Rugby. Details may be obtained from the Local Honorary Secretary.

West Midlands.—Tuesday, November 27th, 7 p.m., Wolverhampton and South Staffs Technical College. Details may be obtained from the Local Honorary Secretary.


British Dry Batteries Standard

THIS British Standard prescribes the dimensions and performance of a range of dry batteries for domestic radio receivers and allied equipment. Experience has shown that the information in B.S.397:1946, "Leclanché-type Primary Cells and Batteries," in respect of dry batteries for radio receivers, is inadequate in the light of present-day needs and it was, therefore, decided that requirements for such batteries should be the subject of a separate British Standard.

This Standard, therefore, has been prepared and embodies the relevant data from B.S.397 together with details of the sizes of

radio battery plugs and a description of the connectors. The provisions of B.S.397, in so far as they apply to radio receivers, are therefore superseded by the standard.

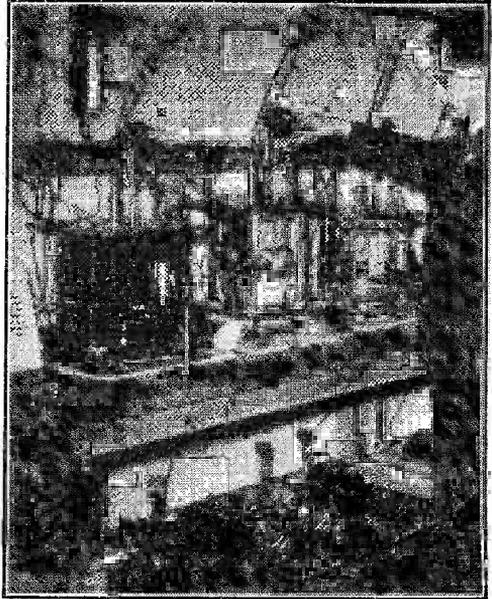Copies of this standard may be obtained from the British Standards Institution, Sales Dept., 24, Victoria Street, London, S.W.1, price 2s., post free.



In this part of the G.P.O. Research Station water-soluble piezo-electric crystals are being "grown" in various solutions.

Royal President

IT is announced that H.R.H. The Duke of Edinburgh, K.G., F.R.S., has graciously accepted the office of President of the City and Guilds of London Institute for the Advancement of Technical Education. He was elected at a Special General Meeting of the Members of the Institute on September 21st, 1951.

B.S.R.A.

ON Friday, November 16th next (7 p.m.) at the Royal Society of Arts, John Adam Street, Adelphi, London, W.C.2, a Lecture on "Electrical and Mechanical Problems of Record Reproduction" will be given by K. R. McLachlan and R. Yorke under the auspices of the British Sound Recording Association.

FREQUENCY MODULATION

A NEW SERIES

3.—FURTHER TECHNICAL NOTES AND AN INTRODUCTION TO F.M. RECEIVERS

By J. F. Golding

(Continued from page 517 November issue.)

A CERTAIN amount of A.M. is superimposed on the F.M. output from the transmitter. This arises from two sources, the modulated oscillator itself and the amplifying stages.

The A.M. from the oscillator is produced because when the gm of a variable-mu valve is altered by

reactor is inversely proportional. With the A.F. signal applied in anti-phase to the grids of the valves the effects of their reactance changes are additive while the changes in anode resistance cancel each other.

The A.M. introduced in the R.F. amplifier stages is due to the fact that, as the signal frequency is being swept through the hump of the amplifier frequency response characteristic, the gain of the amplifier is being effectively varied as shown in Fig. 5. This is a composite graph, in which the signal frequency is plotted against time in Section A, the response curve of the amplifier is shown in Section B, while Section C shows the resultant relative change in output power level. The diagram shows quite clearly that, as the deviation approaches maximum in either direction, the amplifier gain falls so that the peak of the response curve for each half cycle of the modulating frequency. This results in amplitude modulation at twice the frequency of the A.F. modulating signal.

This effect can be reduced to a minimum by using band-pass amplifiers of careful design, having a pass-band of three to four times the maximum deviation. The bandwidth of the BBC F.M. station at Wrotham is approximately 240 kc/s; maximum deviation is 75 kc/s.

This latter type of amplitude modulation is also introduced by the tuned stages of an F.M.



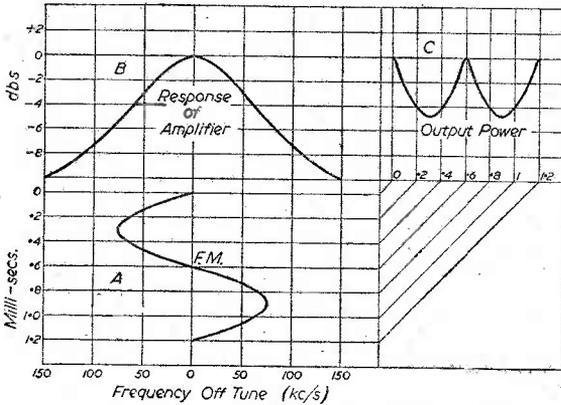


Fig. 5.—Composite graph, illustrating the introduction of A.M. on an F.M. signal when passed through a tuned stage having a response as shown in A. Note that the output power waveform in C is really the shape of the resultant amplitude modulation envelope.

the grid voltages the anode resistance also varies by a small amount. This has the effect of placing a varying resistive load across the oscillator and, by so doing, modulating its output voltage. It can be reduced to a minimum by using a balanced reactor circuit consisting of two reactor valves in push-pull, one acting as a variable inductance and the other as a variable capacitance. It can be seen from Fig. 2 that the capacitance of a capacitive reactor is directly proportional to its gm whereas inductance of an inductive

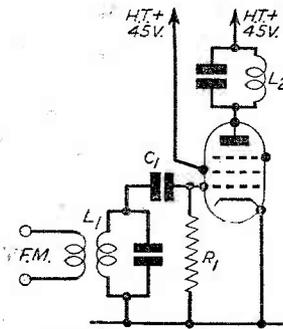

(a) Saturated Amplifier

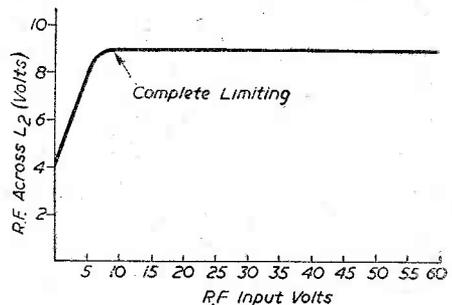

(b) Response of Saturated Amplifier

Fig. 6.—Basic circuit and typical response curve of an amplitude limiter of the saturated amplifier type.

receiver. For this reason and also to eliminate any spurious A.M. caused by noise voltages, a device known as an amplitude limiter is always included as the last stage before the demodulator. The action of this limiter is virtually to flatten the peaks of the R.F. waveform so that the output is of constant amplitude irrespective of the input variations.

Amplitude Limiter

The most common type of amplitude limiter is a saturated amplifier, a circuit of which is shown in Fig. 6 (a). It consists of a tuned amplifier using a short grid-base pentode, which is operated under class C conditions by the self-bias action of a grid-leak and capacitor. Here the grid and cathode

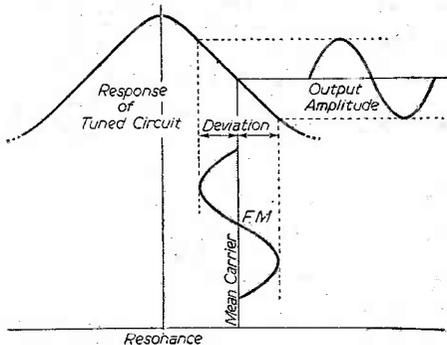


Fig. 7.—Using a mistuned resonant circuit to convert F.M. to A.M.

behave as a diode with the grid-leak resistor as the diode load. During each positive peak of the R.F. voltage, this diode conducts and discharges the grid capacitor. At the negative peaks, however, the diode does not conduct so that the capacitor discharges through the resistor. This discharge current causes a negative voltage drop across the resistor, proportional to the peak R.F. voltage.

The valve is operated with low anode and screen voltages, sufficient R.F. voltage being applied to the grid to bias the valve to cut off at negative peaks and to saturate at the anode bend of the I_a/E_g characteristic at positive peaks.

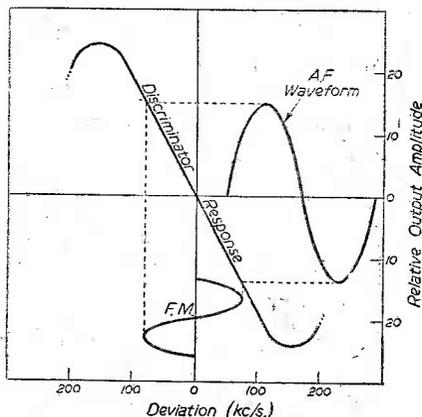


Fig. 9.—Response characteristic of amplitude discrimination.

It is important that the R.F. drive voltage is sufficient completely to saturate the valve or it will behave as a leaky-grid detector causing considerable distortion in the final audio signal. The curve in Fig. 6(b) shows a typical limiter characteristic, from which it can be seen that complete limiting first occurs for an input of 5 volts. The valve would normally be operated with an input of approximately twice this value.

Having passed through the limiter, the signal is now fit for application to the demodulator, which, in its simplest form, may consist of a single-tuned circuit resonating at a frequency above or below the mean carrier by an amount slightly exceeding the maximum deviation frequency, followed by a simple diode detector. The action of such a device is shown graphically in Fig. 7, from which it can be seen that the F.M. is simply converted to A.M..

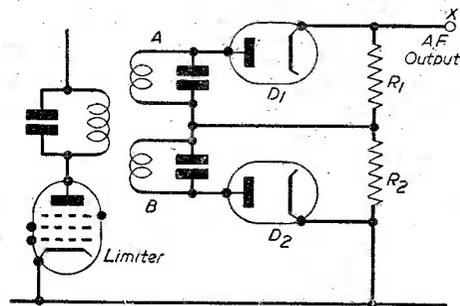


Fig. 8.—Basic circuit of amplitude discriminator.

which may be applied to an orthodox type of detector. This method is not by any means satisfactory because the linear portion of the resonance curve is so short that, for any but the smallest deviations, considerable distortion is bound to occur.

One of the most commonly used types of demodulator circuit is the amplitude discriminator, which consists of two circuits of the type described in the previous paragraph, connected back to back, as shown in Fig. 8. Tuned circuits A and B are adjusted to resonate at frequencies symmetrically spaced above and below the carrier respectively, the spacing from the mean carrier being rather more than the maximum deviation.

Then, while the carrier is unmodulated the voltages across resistors R1 and R2 are equal and opposite so that the voltage between point X and chassis is zero. When modulation is applied, however, as the signal frequency deviates high, it

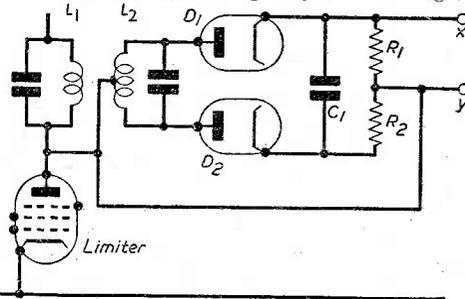


Fig. 10.—Basic circuit of phase discriminator.

approaches the resonance of circuit A, causing the p.d. across R1 to increase while that across R2 decreases to give a positive voltage at point X. Then, as it swings low towards the resonance of circuit B, the reverse action occurs with a resultant negative voltage at point X. The voltage at this point, therefore, varies directly with the signal frequency and may be fed to the audio amplifier stages. The response characteristic of this type of demodulator is shown in Fig. 9.

An alternative type of discriminator circuit is shown in its basic form in Fig. 10. This type is known as a phase discriminator, and operates by virtue of the fact that the voltages across the windings of a tuned transformer are normally 90 deg. out of phase. It has the advantage that only one tuned transformer is used, resonating at the centre carrier frequency.

When the carrier is unmodulated half the secondary plus the full primary voltage appears across each diode.

When the frequency swings off tune in either direction the secondary circuit reactance becomes either more capacitive or more inductive so that the voltage across L2 becomes either more or less than 90 deg. out of phase with that across L1. This throws the voltages across the two diodes out of balance so that an A.F. voltage between points x and y is directly proportional to the frequency swing.

In addition to this phase change, the amplitude is varied by the change in frequency. Up to a point these two effects are additive, but if the frequency deviation is too great, the amplitude change will reverse, having a negative effect, and distort the final A.F. output. Due to this amplitude change, the response characteristic is very similar to that of an amplitude discriminator, as shown in Fig. 9.

In order to improve performance and to provide for convenient connection into the receiver circuit, both of these basic types of demodulator are used in a somewhat modified form in actual practice. However, as it is necessary to consider the receiver as a whole in order fully to understand the reasons for these modifications, these points will now be dealt with.

Reception of F.M. Signals

A frequency modulation receiver differs from its amplitude modulation counterpart in only two major respects. A discriminator circuit takes the place of the usual detector and is always preceded by an amplitude limiter to eliminate any spurious A.M. which may be present in the signal.

Without being too pedantic, the limiter and discriminator may be regarded as a single unit and called the demodulator. This is an efficient but not very sensitive device because, as explained in the previous article in this series, an R.F. input of approximately 10 volts is necessary to ensure complete limiting. If the receiver is to be reasonably sensitive, it is obvious that the demodulator unit must be preceded by a high-gain amplifier. Since it is extremely difficult to amplify V.H.F. signals directly, particularly with variable tuning, a T.R.F.

receiver cannot be used for broadcast F.M. reception, a superheterodyne being the only type suitable.

The block schematic diagram shown in Fig. 11 is identical with that of the equivalent A.M. receiver except that the composite F.M. demodulator replaces the simple A.M. detector. There are, undoubtedly, variations on this plan; for example, receivers situated close to the transmitter may well do without the R.F. stage preceding the frequency changer. Alternatively, some designers may favour a double heterodyne system, which certainly has its advantages and will be discussed later in this series. However, as the straightforward set up of one R.F. amplifier stage, followed by a simple superheterodyne circuit, has proved to be the most satisfactory for F.M. communication receivers and for the 45 Mc/s band broadcast work in the U.S.A., there is no reason to suppose that it will not prove equally satisfactory on the 90 Mc/s band broadcasts in this country.

The Receiving Aerial

Having broadly decided on the general arrangement of the receiver, we are in a position to consider each section in some detail beginning, logically, with the aerial.

It has now been definitely accepted, as a result of extensive tests, that for V.H.F. broadcast work, horizontally polarised waves do provide a more efficient link. It may, therefore, be taken that all F.M. broadcasts in the near future will use horizontal as opposed to vertical polarisation, three transmitting aerials of this type having already been erected.

The most suitable type of receiver aerial is, then, a horizontal half-wave dipole tuned to the centre of the frequency band in which it is intended to operate. Its overall length should be rather less than half the dimensional wavelength of its resonant frequency because, owing to a phenomenon known as the end effect, the effective length of a tuned aerial is about 5 per cent. greater than its physical length.

In order to cover the wave-band required as efficiently as possible, a folded dipole is sometimes


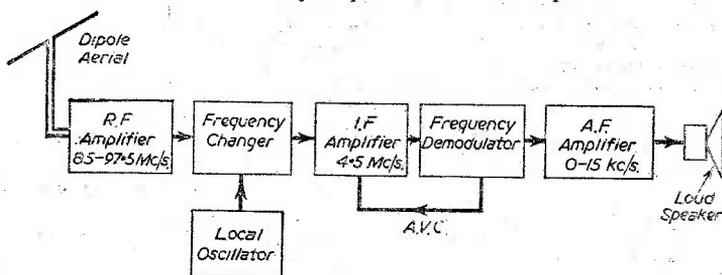


Fig. 11.—Block schematic of an F.M. receiver.

used, in which the elements of the aerial are bent back on themselves to form a flattened loop.

These types of aerial are sensitive only to waves approaching from a direction at right angles to the aerial elements. They can be made uni-directional by the addition of a reflector rod rather more than a half wavelength long and spaced parallel to the aerial itself by about a quarter wavelength. The direction of sensitivity is, of course, away from the reflector.

(To be continued.)

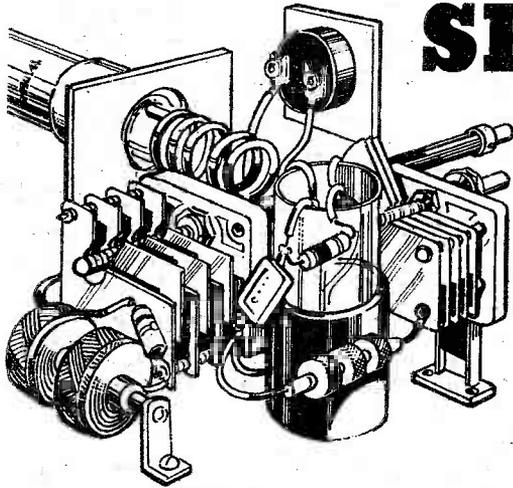

SHORT-WAVE SECTION

BREAKTHROUGH WAVE-TRAPS AND SHORT-WAVE ADAPTORS

By A. W. Mann

phone transmission. While doing this the wave-trap tuning condenser should be set at its minimum capacity. Next, tune out the undesired 40-metre 'phone transmission with the wave-trap.

This simple device will be found to be very effective. Once set, a considerable portion of the band can be covered without further adjustment, and it is not such a tiresome idea as might first appear.

WHILE we never associate wave-traps with the modern selective broadcast type superhet, this old aid to selectivity can be effectively used in conjunction with the simpler types of short-wave receiver, such as the straight detector and untuned H.F. arrangements.

For example, it is well known that some top-band listeners are troubled with breakthrough from the local third programme transmitter. A wave-trap consisting of a suitable coil and tuning condenser capable of being tuned to the frequency of the offending transmitter, placed in series with the receiver aerial, will effectively remove the interfering transmission.

R1116, R1116A

Some of these receivers are prone to the defect of the reception of 40-metre signals, while switched to the 80-metre range. On the other hand, some are not. These repeat points are not, in the writer's opinion, a straightforward case of second channel. While an I.F. trap circuit in series with the aerial or, alternatively, across aerial and earth sockets of the ordinary super would in most instances effect a cure, it is not so simple in this instance.

The R1116 is a double frequency-changing super, the I.F.s being 1,700 kc/s and 100 kc/s, and this rather complicates matters. While I would not claim at the moment that the defect is definitely due to one particular thing, I am of the opinion that the generation of spurious harmonics has something to do with it. At some future date I hope fully to investigate this problem.

The most satisfactory method of removal would undoubtedly be the addition of tuned H.F. stage. Those who experience this trouble, however, might care to try a series aerial wave-trap, consisting of a 100 pF tuning condenser and a 4-pin coil capable of tuning through the 40-metre band. If you have on hand one of the single winding TR9 receiver tuning coils, this is ideal for the purpose.

The procedure is as follows. Fit the tuning coil in series with the aerial lead, and parallel tune it with the 100 pF tuning condenser; if possible use a slow-motion tuning dial. Switch the receiver to the 80-metre range. Tune in the undesired 40-metre

Signal Strength Measurement

The best types of communication receiver are either fitted with a built-in "S" meter, or have provision for plugging in a suitable one which has been specially produced for use with the model.

Even so, the calibrated values as shown on the meter scale are only arbitrary, and S9, plus so many db's as shown on the "S" meter scale of one particular receiver, may differ when compared with another of different make. This, however, is a controversial subject. Nevertheless, most amateurs regard their "S" meters as a useful guide and not as a precision instrument.

The simpler type of receiver cannot be fitted with an "S" meter, but use can be made of a calibrated volume control. The procedure to adopt in calibrating is to tune in the loudest transmission consistently received and calibrate in "R" strengths. Adjust the volume control until this signal just disappears. Call this R9 and follow up by searching for signals of proportionate volume, which will enable you to calibrate the volume control dial from R1 to R9.

Now this idea is easier to write about than to put into practice. The writer, however, did it with a fair measure of success some years ago. Some concentrated listening is called for and one must have a good idea with regard to relative signal strengths.

Admittedly, the use of a variable potentiometer or a variable resistor has disadvantages, but the advantage of the system is that one's idea of R8 does not vary from hour to hour and the entries in the log possess some measure of consistency.

One listener's idea of R8 may differ from that of another and much depends on individual ideas of relative signal strengths when first calibrating the control. Just as the "S" meter is a useful guide, the calibrated volume control is an improvement on sheer guesswork.

Receiver Calibration

The present trend is to calibrate directly on the tuning dial plate, specially designed dials being available for the purpose. Beginners, however,



On Your Wavelength

By Thermion

Interference

IN future those who complain to the Post Office of electrical interference with their reception will be handed a pamphlet which tells them how they can make simple tests to ascertain whether the trouble is due to a faulty receiver or inefficient aerial and earth system.

Interference due to such causes should not be referred to the Post Office Interference Investigation Service, but should be dealt with by the owner of the receiver, or his radio dealer.

None of my readers would complain to the Post Office, of course, without being quite sure that the aerial and earth system was in good order.

When it is known that the interference is due to causes outside the control of the owner of the set he should fill in the form at the end of the pamphlet enlisting the services of Post Office engineers to track down the source of the trouble.

I am informed that this new method of dealing with complaints of radio interference has been adopted because in a large proportion of the cases investigated by the Post Office, it was found that the cause was due to faulty receivers, or to faulty aerial and earth systems.

Heavy calls are made upon the P.O. I.I.S. and it is hoped by this new method to effect an appreciable reduction.

About Nickel

I WAS only able very briefly last month to deal with the criticism I had received from one who informed me that, if we detach a piece off a magnet, it will try to attach itself to any pieces of iron, nickel, etc. I said that nickel was a non-magnetic material. What I really intended to imply was, of course, that by comparison with iron, for example, it is only weakly magnetic.

I have a piece of pure nickel, which is only just attracted by a powerful car-magneto magnet. A piece of nickel supplied by the Mond Nickel Corporation just limply attaches itself to the magnet. According to the textbooks nickel has a saturation value of 6,150 gauss, and a permeability ($H = 10$ oersted/cm.) of 400. I am well aware that nickel is used in special alloys such as permalloy, nickeloxy, and other of the nickel steels. It is, of course, a well-known fact that all materials are magnetic though most so feebly that to all intents and purposes they are practically non-magnetic or the effect is swamped by much larger paramagnetism or ferromagnetism. Many thanks to the three readers who wrote to correct me on this point. I am wiser now.

P.T. on Radio Batteries

I AM glad to note that at the Autumn Conference of the National Chamber of Trade attention was drawn to the anomaly created by the imposition of purchase tax on radio batteries, which are largely used by rural workers and others in areas where electric mains are not available. Requests have been sent to the Government to remove the injustice by abolishing purchase tax on batteries and accumulators used for radio receivers.

Competition from TV?

THE rapid strides at present being made in television might lead one to suppose that experimenters were deserting radio and devoting their attention to TV. Such, however, is not, in fact, the case. More people than ever are interested in building receivers. Each year there is a new influx of youngsters who become interested in radio for the first time. Technical journals are rather apt to overlook the needs of these beginners, and to omit articles of an elementary nature. The fact is that year by year the same old elomen ary story must be told. This may be distasteful to, or considered a waste of space by, the experienced man, but we must remember that we were all inexperienced once.

The proprietors of this journal publish a very elementary book on radio entitled "Everyman's Wireless Book." Its sales have reached enormous proportions and it is now in its tenth edition. It is an excellent primer for the very beginner, and indeed is used for that purpose in many schools.

Memorial to Baird

I AM pleased to note that the London County Council has decided to erect a commemorative plaque to John Logie Baird on the front of 22, Frith Street, Soho. This plaque is the 200th to be erected or re-erected by the Council since 1903. It will be circular in shape and the inscription in white letters on a blue background reads:

"LONDON COUNTY COUNCIL
IN 1926
JOHN LOGIE BAIRD
1888-1946
FIRST DEMONSTRATED
TELEVISION"

Baird was born in Scotland and was educated at the Royal Technical College, Glasgow. He moved to Hastings where a house in Queens Avenue bears a plaque recording the experiments in television which he conducted there in 1924. At the beginning of 1926 he occupied the attic laboratory in Frith Street, where the plaque is erected.

It was on Tuesday, January 26th, 1926, that he carried out the world's first demonstration of television before an audience consisting of about 40 members of a Learned Society. The image was transmitted from one room to another. The apparatus is now in the Science Museum.

Radio Receiver Design at V.H.F.—2

FADING : ATMOSPHERIC INTERFERENCE : OSCILLATOR STABILITY : TUNED CIRCUITS

By G. P. Lowther

(Continued from page 508 November issue.)

Fading

It has sometimes been stated that V.H.F. transmissions are not susceptible to fading, at any rate until communication is attempted over greater than optical range, i.e., when propagation depends upon refraction of the earth's atmosphere. Actually, this statement should be slightly modified; no rapid fading is encountered, but there may be variations of several decibels with changes in atmospheric conditions, particularly when there are unmixed layers of warm and cold air above the surface of the earth. Whilst fading does not prove troublesome, multi-path propagation may do so, however. Fig. 4 shows how such conditions may arise.

Fortunately, such conditions do not usually

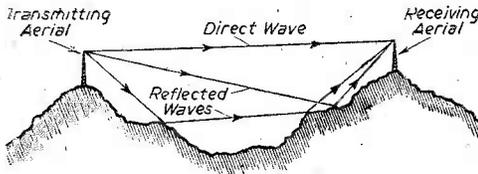


Fig. 4.—This diagram shows how a signal can be split up in radiation.

prove troublesome unless transmissions susceptible to phase distortion are involved, e.g., television, where multi-path propagation may produce ghost images, or multi-channel radio telephony in which cross-talk may be caused. In the case of such transmissions, aerial sites and ground slopes must be carefully selected, and antennae which discriminate vertically as well as horizontally (e.g., rhombics) should be employed. Single channel telegraphy or telephony such as the amateur is likely to use will not be appreciably affected.

Not only is transmission at V.H.F. optical, but it is considerably influenced by objects placed in the path of the radio waves. For instance, it was noticed in one case that reception was much better during the winter than the summer months, and investigation proved this to be due to the fact that the radio path was through a thin screen of trees, the foliage of which in summer caused an appreciable reduction in signal strength. Metal objects, buildings, etc., produce far more troublesome effects, and apart from giving reflections, may completely block reception if located in the optical path. When experimenting at V.H.F. it is therefore advisable to try various positions for the aerial until optimum reception is obtained. (This will not necessarily be the most obvious one.)

Atmospheric Interference

Atmospheric interference is seldom troublesome at V.H.F., but severe interference is often caused by man-made static such as motor-car ignition systems. Fortunately the radiation is chiefly over

the surface of the ground and its effect is much reduced if the aerial is well elevated.

A rather peculiar form of interference is sometimes evident at V.H.F. and is often difficult to cure. It is found that metallic objects making loose or scraping contact, even though connected to no other apparatus, cause noises in the receiver, which can only be prevented by bonding the wires which give rise to the interference to earth or to each other or by separating the offending objects.

Above 30 mc/s

The advantages and disadvantages of working at frequencies above about 30 mc/s thus depend upon the conditions of transmission required and may be summed up as follows: If wide-band transmission is necessary, i.e., the band-width is of the order of 1 mc/s or greater, very high frequencies must be used even though this necessitates relay station working owing to the propagation being limited to optical distances. Where band-widths between about 50 kc/s and 1 mc/s are required, as in commercial frequency-modulated transmissions, it is impossible to make use of the short-wave band owing to selective fading if the sky wave is used, and while propagation on medium or long waves is theoretically possible, considerations of available ether space make this impracticable and once more recourse must be had to V.H.F. working.

Commercial narrow-band transmission for entertainment or cultural purposes is not, however, easily adapted to working above 30 mc/s, i.e., below 10 metres, because not only would such services provide only limited local reception, but tuning would be extremely sharp and calibration of stations would be almost an impossibility. For the amateur, however, these last two considerations are of far less importance and experimental work at these frequencies opens up a wide field of research. The cost of constructing suitable apparatus is not great and much work can be done with the help of a small local oscillator, the construction of which will be described in a later article, though even this is not essential.

Before discussing actual design considerations, one more question must be answered, the hoary problem of "straight versus superhet." While for long, medium and short-wave working no other type of receiver can compare with the superhet for sensitivity and selectivity, the problem is somewhat different at V.H.F. as the efficiency of frequency-changers falls off rapidly above about 50 Mc/s, and therefore apart from the reduction in gain, the performance deteriorates as the receiver is inherently more noisy as will be shown later. Also, since it is normally unnecessary to provide a large percentage change in the frequency to which the receiver is tuned, the advantages of fixed frequency amplification obtained with a superhet are reduced.

Oscillator Stability

Another difficulty is that of maintaining a sufficient degree of oscillator stability for narrow-band transmissions. Nevertheless, the superhet remains the receiver of choice, since it reduces to a minimum the number of circuits operating at signal frequency. The frequency-changer may be incorporated in a complete receiver or used as a converter with an intermediate frequency of 10 Mc/s-40 Mc/s.

It is, of course, possible to employ super-regeneration at V.H.F., and circuits of all three types of receiver will be described later.

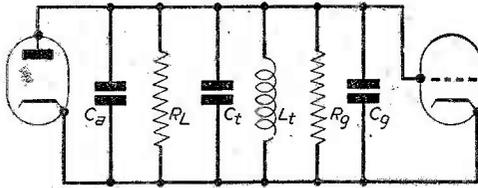


Fig. 5a.—Single parallel circuit.

the narrowest band width that can be expected is of the order of several hundred kilocycles. Any greater degree of selectivity must be achieved in subsequent I.F. stages. For experimental amateur work it is clearly unnecessary to work with bandwidths of the order of megacycles, particularly as a reduction in gain would result, but since many commercial and other transmissions employ broad-band working, suitable tuned circuits will be briefly described.

1. *Narrow band circuits.*

(a) Single parallel (Fig. 5a).

(b) Single parallel with untuned primary (Fig. 5b).

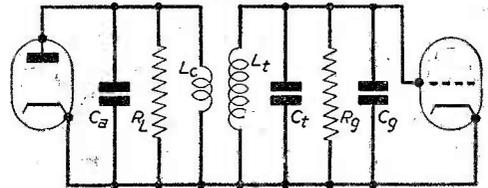


Fig. 5b.—An untuned primary is shown here.

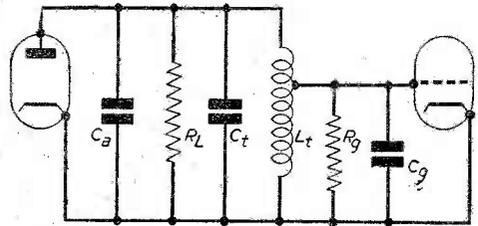


Fig. 6.—A tapped parallel circuit. The step-down voltage ratio = r .

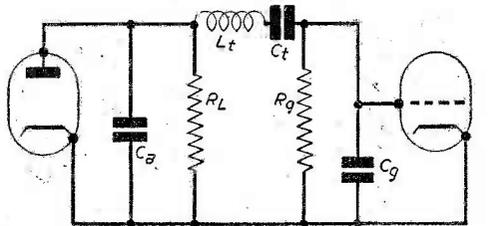


Fig. 7.—A series circuit.

The table below compares propagation at V.H.F. with that at lower frequencies:

Tuned Circuits

Not only is valve technique different, but tuned circuits must be treated rather more carefully at V.H.F. than at lower frequencies. They may be roughly classified as narrow and broad band, though what is called narrow at V.H.F. would be termed broad at lower frequencies. In other words,

(c) Tapped parallel (Fig. 6).

(d) Series (Fig. 7).

2. *Broad-band circuits.*

(a) Double parallel (Fig. 8).

(b) Common inductance coupled-shunt (Fig. 9).

(c) Common inductance coupled-series (Fig. 10).

(d) Parallel staggered.

(e) Series staggered.

Figs. 5 to 10 show diagrammatically the most convenient circuits for use at very high-frequencies, (H.T. blocking condensers, cathode resistors, etc.)

	Long waves 150-300 kc/s (2,000-1,000 m.)	Medium waves 500-1,500 kc/s (600-200 m.)	Short waves 3-30 mc/s (100-10 m.)	Very short waves 30-300 mc/s (10-1 m.)
Ground wave	Strong — absorbed very slowly	Absorbed more rapidly	Not normally used	Used over optical range
Sky wave	Same order as ground wave	Causes interference at night	Provides long-distance reception	Lost in outer space
Fading	Slow and slight	Troublesome at night	Considerable, varied and sometimes selective	Negligible over short distances
Power required	Very large	Large	Medium	Small
Aerials	Very large, usually non-directional	Large and usually non-directional	Medium, are usually beamed	Small, and easily made directional

are omitted as these do not normally affect the operation of the tuned circuit.) Before analysing them a simple example will be given to justify the statement that wide-band coupled circuits are only necessary in special cases.

C_t (tuning capacity) = 20 pF ($\mu\mu\text{F}$). Assume $f = 40$ Mc/s.

R_L (impedance of anode circuit to earth, including losses) = 40,000 Ω .

C_a (output capacity of valve including strays) = 7 pF.

R_g (impedance of following grid circuit to earth, including losses) = 10,000 Ω .

C_g (input capacity of following valve including strays) = 10 pF.

Then, as will be shown later, the bandwidth of the circuit shown in Fig. 6 (which provides good selectivity):

$$= \frac{1}{\pi^2 R_g (C_a + C_g + C_t)} \text{ cycles.}$$

$$= \frac{1}{\pi \times 2^2 \times 10^4 [7 + \left(\frac{10}{2^2}\right) + 20] 10^{-12}} \text{ cycles.}$$

$$= \frac{1}{4\pi \times 29.5 \times 10^{-5}} \text{ kc/s.}$$

$$= 270 \text{ kc/s.}$$

If a higher frequency had been chosen, the bandwidth would have been still greater. It may

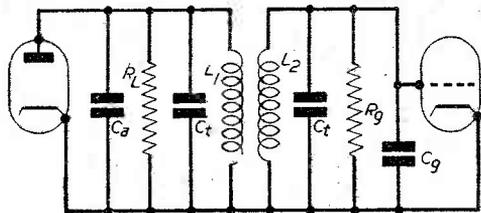


Fig. 8.—A double parallel circuit.

perhaps be remarked here that all numerical examples quoted are typical of conditions at V.H.F. and will give a good indication of the results to be expected.

Analysis of Fig. 5a

It is not thought necessary to prove the well-known formula that the gain of a stage = $\frac{\mu R_L}{R_a + R_L}$ where R_L is the total effective load. When R_a is much greater than R_L (a justifiable assumption at V.H.F.) gain = $\frac{\mu R_L}{R_a}$. But $\frac{\mu}{R_a} = G_m$ (these symbols representing the static characteristics of a valve). Therefore gain = $G_m R_L$ (approximately).

At low and medium frequencies the bandwidth of a circuit is usually taken 6db below the maximum response, but here it will be taken 3db for a reason shortly to be explained.

By definition $Q = \frac{\omega L}{r}$ (where r represents the series resistance of the circuit).

As may be shown fairly simply, but at some length, the effective parallel impedance (R) of a tuned circuit at resonance = $\frac{L}{C_t}$ or $r = \frac{L}{RC}$

Hence $Q = \omega L / \frac{L}{CR} = \omega CR$.

This is a much more convenient form as L and r are seldom known, whereas a fairly accurate estimation of C and R can usually be made. A well-known method of measuring Q experimentally is to note the bandwidth when the response is $\frac{1}{\sqrt{2}}$

(0.707 or 3db) below the maximum.

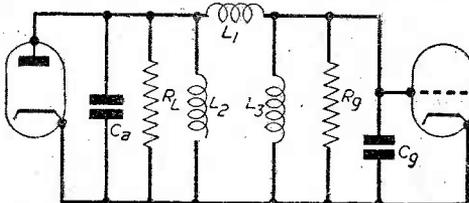


Fig. 10.—Common inductance coupled-series.

Then $Q = \frac{f_o}{2\delta f_o}$ where f_o = mid-band frequency and $2\delta f_o$ = total bandwidth 3db down.

Hence bandwidth = $\frac{f_o}{Q} = \frac{f_o}{\omega CR}$

= $\frac{1}{2\pi CR}$ again a very convenient expression.

In Fig. 5a, bandwidth = $\frac{1}{2\pi R_g (C_a + C_g + C_t)}$ and gain = $G_m R_g$, assuming in both cases that R_L is much greater than R_g , i.e., that R_g is the resistor limiting the gain and broadening the band. This condition is approximately fulfilled, but for accuracy R_g should be replaced in the gain and bandwidth expressions by R , where $R = R_g$ in parallel with R_L .

Gain \times bandwidth = $\frac{G_m}{2\pi (C_a + C_g + C_t)}$

("Goodness" factor of circuit.)

As a typical example, assume $R_L = 20,000\Omega$, $R_g = 2,000\Omega$, $C_a = 7$ pF, $C_g = 10$ pF, $C_t = 20$ pF,

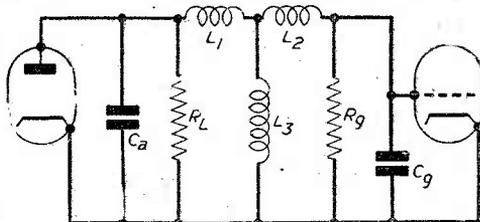


Fig. 9.—A common inductance shunt.

$G_m = 6$ mA/V, $f =$ approx. 50 Mc/s, gain = $6 \times 10^{-3} \times 1820$.

= 11 times, or 21db

Bandwidth = $\frac{1}{2\pi \times 1820 \times 37 \times 10^{-12}} \text{ cycles}$
= 2.4 Mc/s.

These unsatisfactory figures are due to the heavy damping imposed by the grid circuit.

In Fig. 6 this is minimised by tapping the grid down the tuned circuit, which thus acts as an auto-transformer.

(To be continued.)

Radiogram Combinations

VARIOUS METHODS OF USING A PICK-UP WITH HOME-MADE OR COMMERCIAL RECEIVERS

By W. J. Delaney (G2FMY)

MANY amateurs are desirous of possessing a radiogram but already have a radio receiver—either home-made or factory built, and wish to utilise that as part of a complete installation. We are often asked if we can supply a blueprint for a radiogram, but actually, of course, there is no need for a print of that description. Provided that an amplifier is available, together with a motor and suitable pick-up it is a simple matter to combine them to produce a radiogram. It is not proposed to deal with the constructional work which can take any desired form—either a large cabinet housing the complete equipment, or a console radio receiver with a separate unit consisting of a motor and turntable with the pick-up. In an elaborate unit, of course, record storage space is also provided.

To-day it is possible to obtain simple motors running at 78 r.p.m. for standard records, or two or three-speed motors suitable for use with long-playing discs in addition to the standard types. If one of these is selected it will also be necessary to obtain a pick-up of the type fitted with interchangeable heads as these must also be changed when playing the different types of disc. Most modern pick-ups require a matching transformer

Pick-up Output

The output delivered from a pick-up varies according to the type and it is necessary to ascertain from the maker's data sheet whether or not this is so low that what is known as a pre-amplifier is required. Ignoring this type of instrument for the minute let us assume the use of one of the older types of instrument which has an output of just over 1 volt. This must be fed into a low-frequency amplifying stage followed by one or more stages to deliver sufficient output to operate a loudspeaker satisfactorily. Most commercial radio receivers are provided with sockets marked "Pick-up" or "Gram." It is usual for these to be included in or immediately following the detector stage so that the L.F. stages of the receiver may be used for record amplification. In its very simplest form this will consist of a pair of sockets, one of which is connected to earth and the other to the grid circuit, although there may be included a single-pole change-over switch as shown in Fig. 1. The radio components are terminated at the socket or point marked R in this sketch and the pick-up is connected with one side to earth and the other to the point G. Obviously, therefore, when the switch is on R the radio signals will be heard, and when

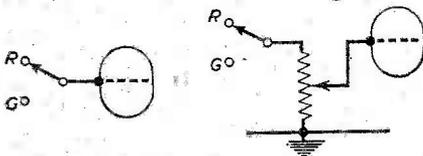


Fig. 1 (left).—Simple radiogram change-over switching. Fig. 2 (right).—Switching arranged to retain a single volume control operating on both radio and gram.

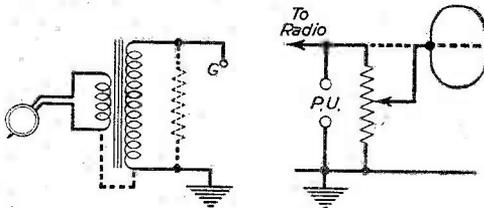


Fig. 3.—A resistor is sometimes necessary across the pick-up transformer secondary, and it is generally desirable to earth the primary winding. Fig. 3 (a) (right).—Pick-up sockets may be connected direct across a radio volume control if this is on the L.F. side.

to be used between them and the amplifier, and usually the makers are prepared to supply these with the pick-up. Suitable cabinets are easy to make to house the turntable and pick-up, and all that remains is to ascertain how to utilise the output from the pick-up. This is the principal stumbling block and it is the association of the pick-up with some amplifying system which introduces the major problems.

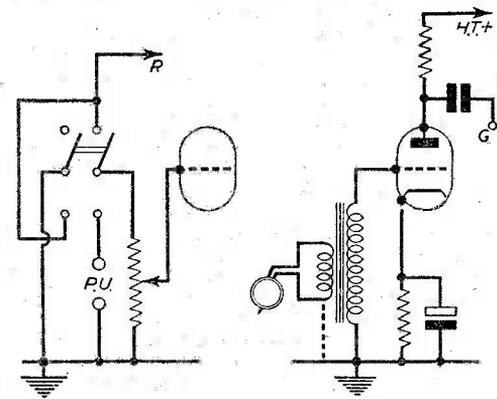


Fig. 4 (left).—A double-pole change-over switch arranged as shown here will enable radio to be silenced when using gramophone. Fig. 5 (right).—A simple pre-amplifier stage which is necessary with low-output pick-ups.

turned to G the radio will be cut out and the output from the pick-up will be heard. In many cases this is all that is required, and if there is no radiogram switch it is usually found that when a record is played the radio signal may be cut out, should it be heard in the background, by detuning the radio. If there are no pick-up sockets, the first thing to do is to ascertain why—there may be a very important reason for their omission. In an A.C./D.C. or D.C. receiver, for instance, special

precautions are necessary to avoid a serious shock as a direct earth is not employed and the chassis may be "live" to one side of the mains. In many cases a simple fixed condenser may be included in each of the pick-up leads, but the makers of a commercial receiver should be consulted if there are no pick-up connections in order to make certain that the receiver is suitable for use with a pick-up.

Fitting Sockets

If the receiver is suitable and sockets or terminals are not provided they may be included by breaking

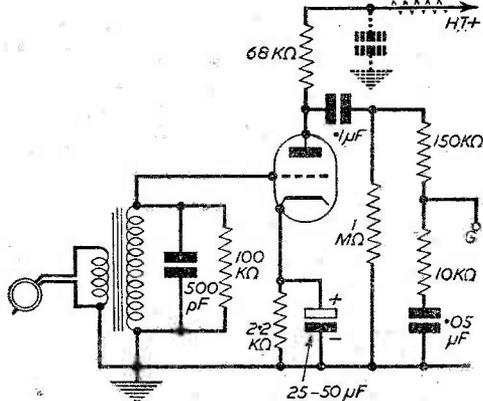


Fig. 6.—To provide bass compensation a tone-control pre-amplifier is desirable using a circuit similar to that shown here.

the connection to the grid of the first L.F. stage and fitting a change-over switch as shown in Fig. 1. If there is an L.F. volume control it is preferable to utilise this as the input arrangement, in which case the connections will be as shown in Fig. 2. The switch is, of course, a single-pole changeover component and may be of the simple toggle type. If the pick-up is of the type requiring an input transformer for matching, this should be included as shown in Fig. 3, where it will be noted that the secondary of the transformer is regarded as the former pick-up. The primary should, as a rule, have one end connected to the earthy end of the secondary, and to remove the risk of hum the connections from the pick-up to the transformer, and from the transformer to the input sockets, should be of screened lead. The transformer should be mounted as close to the pick-up as possible and usually a fixed resistor should be connected across the secondary, using a value recommended by the pick-up makers. To avoid having to detune the radio it is possible to use a double-pole change-over switch, making the connections as shown in Fig. 4. It will be seen here that when switched to gramophone the radio input to the switch is short-circuited.

Pre-amplifiers

The arrangements so far described are the simplest which can be adopted and will allow a reasonable output to be obtained. If the volume is insufficient additional L.F. stages will have to be employed. In many cases it will probably be found desirable to build a special amplifier and to cut out

the L.F. side of the radio receiver, using the actual radio side, plus the gramophone pick-up in conjunction with the amplifier. In its simplest form an additional stage could be added as shown in Fig. 5, where a single L.F. amplifier is indicated and the output from this is taken, instead of the simple pick-up lead, to the input sockets. The valve will, of course, be alight all the time that radio is on unless a switch is inserted in the heater circuit to switch it off when not needed. The slight extra current, however, should not prove troublesome and it may generally be left in circuit without difficulty.

Compensation

As already mentioned, these are the simplest methods of using a pick-up, but as is well-known the recording characteristic of gramophone records is not straight and some compensation of the bass is necessary to obtain balanced reproduction—even if a tone-control is used. There are various arrangements which may be used and one which is very satisfactory with most ordinary types of modern pick-up is that shown in Fig. 6, and which is recommended by the makers of the Connoisseur

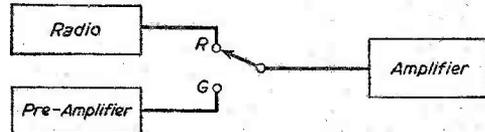


Fig. 7.—A radiogram consists merely of a radio tuner, a pre-amplifier and a main amplifier, with input switching as shown in this block diagram.

pick-up. This gives a rising characteristic to the bass and slight amplification making it suitable for use before most types of amplifier. The output from this or any similar type is treated again, as in the case of the normal pick-up, and is shown diagrammatically in Fig. 7. If desired, additional tone control circuits may be added to the compensating circuit of Fig. 6 and all should be regarded, from the point of view of switching, as the simple pre-amplifier of Fig. 7.

Where one wishes to make up a complete radiogram as a domestic unit this may be done by building or purchasing as separate items an amplifier and a radio tuner. It is also possible to purchase to-day pre-amplifiers of various types as well as tone-controls built as separate units and containing the necessary valves to make up the loss which is incurred by the tone-control networks. In most cases plug-and-socket connections are provided on the separate units and those of different makes may often be combined to give a special combination.

NEW POCKET BOOK

EVERY CYCLIST'S POCKET BOOK

By F. J. CAMM

400 pages. 84 pages Indexed Road Routes. Equipment, Overhauling, Adjustment, Touring, Records.

Price 7/6. By Post 8/- from

GEORGE NEWNES, LTD. (Book Dept.),
Tower House, Southampton Street, Strand, W.C.2.

Repairing Dial Drives

Hints for the Serviceman.

By J. S. KENDALL

THE subject of repairs to dial drives is one very rarely written about but is of great importance to the repair man and to the home radio enthusiast. Quite a number of manufacturers employ what at first sight are very complicated drives. The Philips is an example of this, but on examining them in a cool, collected manner they are found to be just a matter either of cords running over pulleys, or Bowden cables. First I will deal with the cord drives.

In the threading of the cord of cord drives the two tools shown in Fig. 4 are of very great use. These were designed by the writer in order to get the cord into inaccessible places. They are made out of two pieces of silver steel $\frac{1}{16}$ in. dia. and 6 in. long. The end half inch is filed flat to a thickness of about $\frac{1}{16}$ in., and one has a vee and the other a hook. Great care must be taken when filing the two grooves in the ends so as not to leave sharp ends or rough surfaces which will chafe the dial cord.

The choice of cord is very important, and I have found that the best is Allcocks No. 8079 pike line. This is fairly expensive, but it does not chafe easily and has a test strain of 20 lbs. giving a very good life and being free from stretch. There is nothing more annoying than to thread up a new cord, reassemble the receiver, try it out and find that the cord has stretched and that it is slipping and the job has to be stripped and done again.

Starting

In most drives at least one end of the cord terminates on a spring, but if only at one end, make off the cord, starting with the fixed end first. This can be done by taking the cord through a loop and tying it back on itself with two or three

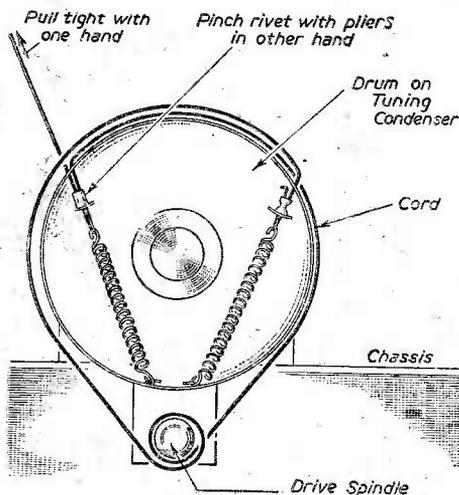


Fig. 1.—The simplest type of cord drive showing method of terminating cord.

half-hitches. Another way of securing the cord, and much easier, is to thread on a tubular aluminium rivet so that the cord passes through it twice, then pinch as shown in Fig. 3. This method is used by several manufacturers and is to be recommended for its simplicity.

Once the cord is made fast at one end the required length is cut off; it is better to do this and waste a little than to get in a mess trying to thread on just the correct amount, as the fact

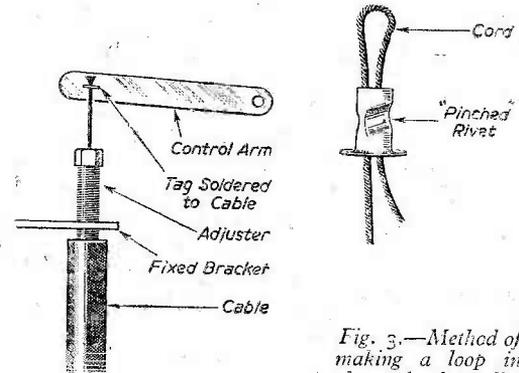


Fig. 2.—Construction of a Bowden cord adjustment.

Fig. 3.—Method of making a loop in the end of a dial cord by using a rivet.

that one end is anchored allows the cord to be held tight against the pulleys. This does not matter so much with the type of drive shown in Fig. 1, but is of great importance in threading the more complex type of drive. The drive pulley, or spindle, should have one-and-a-half to two turns, no more and no less. If too many turns are used they tend to ride up on to each other and bind, making the drive hard and greatly increasing the backlash. Awkward places can be threaded by means of the two tools described earlier.

Finishing

The best way to make off the second end is shown in Fig. 1. This method has the great advantage over the more usual one as it only requires two hands and not three! After the dial is threaded the cord is pulled tight so that the spring is fully extended, and the tubular rivet is then pinched with a pair of pliers to secure it. The pinching has to be tight and a pair of pliers, not cutters, used, or the cord will be cut.

Cable Drives

The other type of drive is the Bowden cable. This is sometimes used for all the controls on the set! The main thing with this is to get some good cable and some suitable solder. In this respect I find that there is nothing to beat Arrax cored solder, as it tins steel cable very easily.

The method of threading is first to tin the end of the cable, this ensures that the loose ends do not

catch when the cable is being threaded into the sheath. The make-off is usually a hollow brass thimble soldered over the wire to stop it slipping, and this thimble fits into a groove on the control, as shown in Fig. 4. The adjuster has the effect of shortening or lengthening the amount of space between the end of the sheath and the control arm. In some cases the cable can be made off with the aid of a tubular rivet in the same way as described earlier for the more common cord drives.

If the foregoing instructions are adhered to the

matter of repairing dial drives becomes one of relative ease.

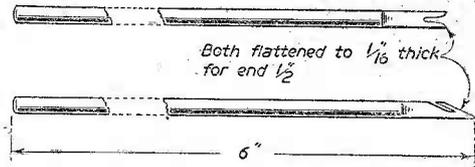


Fig. 4.—Threading tool for dial cord.

Improved Home Service

AT present the BBC Home Service is satisfactorily received by about 92 per cent. of the population of the United Kingdom, though in some areas it is subject to interference from foreign broadcasting stations, especially during the evenings in winter. It is not possible to make any widespread improvement in coverage because of the shortage of wavelengths available for use by the BBC; these were allocated by agreement between the Governments of countries in the European Zone at a conference held in Copenhagen, and the resulting Wavelength Plan was put into effect in March, 1950.

BBC engineers have made a detailed study of reception conditions since the Copenhagen Plan came into force and have worked out a scheme for making local improvements in reception of the Home Service in certain parts of the country. This plan, which has now received the approval of the Postmaster-General, provides for twelve low-power transmitters to be brought into service in areas where they are most needed and will benefit the greatest number of people.

In finding wavelengths for these new stations, either wavelengths must be shared with existing BBC transmitters or use must be made of the International Common Wavelength which most countries have the right to use. There are objections to both these courses. When two transmitters share a wavelength an "interference area" is created in which reception is poor and may be intolerable. Stations which share a wavelength must, therefore, be chosen very carefully or the loss of population coverage may be greater than the gain. Of the two International Common Wavelengths, 188 metres is off the tuning scale of most receivers at present in the hands of the public and will therefore not be used in this scheme. The other, 202 metres, is of limited value because the power is restricted to 2 kilowatts by the Copenhagen Plan and the range is further limited by interference from the many Continental stations also using it. The present scheme for additional Home Service transmitters is tabulated below. It will be seen that in some areas it is not practicable for the transmitter to radiate the Home Service of its own Region for the reason already explained. It is expected that at least some of the transmitters will be in operation before the winter of 1951/52.

Unfortunately, reception conditions in Europe on the medium-wave band are likely to get worse as the number of broadcasting stations and their power increases. It is therefore of the utmost importance

that listeners should realise the need to keep their receivers in good working order, because the slow deterioration in performance that inevitably occurs in the course of time leads to weak reception, fading,

ADDITIONAL TRANSMITTERS AND AREAS SERVED:

Location	Wavelength	Frequency	Programme radiated
Barnstaple ..	285 m.	1,052 kc/s	West of England
Scarborough ..	261 m.	1,151 kc/s	Northern Ireland
Bexhill ..	206 m.	1,457 kc/s	West of England
Folkestone ..	206 m.	1,457 kc/s	" " "
Brighton ..	206 m.	1,457 kc/s	" " "
Whitehaven ..	434 m.	692 kc/s	North of England
Barrow ..	202 m.	1,484 kc/s	" " "
Ramsgate ..	202 m.	1,484 kc/s	London
Pwllheli ..	341 m.	831 kc/s	Welsh
Cromer ..	330 m.	908 kc/s	London
Montrose ..	202 m.	1,484 kc/s	Scottish
Dumfries ..	371 m.	809 kc/s	"

and interference from other stations. A good outdoor aerial should always be used whenever circumstances permit, to allow the receiver to give of its best.

Three of these stations—Brighton, Ramsgate and Hastings—were put into operation on September 16th.

Two more of the twelve proposed stations, making five in all so far, came into operation on October 7th, at Whitehaven and Barrow. Both transmitters radiate the North of England Home Service, Whitehaven on 434 metres (692 kc/s) and Barrow on 202 metres (1,484 kc/s).


Both transmitters will ultimately have a power of 2 kilowatts, but as the completion of the permanent installation will take some time, temporary transmitters of lower power will be used to provide a service before winter sets in. It is expected that these temporary transmitters will improve reception only in the immediate vicinities of the towns in which they are situated.

STANDARD TEXT BOOKS


By F. J. CAMM

Everyman's Wireless Book, by post, 9/-. *Newnes Radio Engineer's Pocket Book*, by post, 5/6. *The Superhet Manual*, by post, 6/6. *Practical Wireless Circuits*, by post, 6/6. *Radio Training Manual*, by post, 6/6. *Wireless Coils, Chokes and Transformers*, by post, 6/6. *Radio Valve Data Book*, by post, 5/6. *Refresher Course in Mathematics*, by post, 9/-. *Mathematical Tables and Formulae*, by post, 5/6. *The Slide Rule Manual*, by post, 5/6.

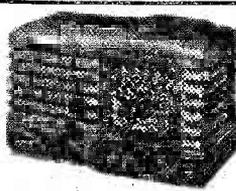Obtainable from
GEORGE NEWNES, LTD.
 Tower House, Southampton Street, Strand, W.C.2.



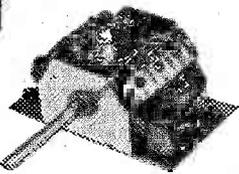Walnut Bakelite Cabinet, 12in. x 7 1/2in. x 6 1/2in. scale aperture 3 1/2in. x 4 1/2in. complete with three wave-band scale, back plate, 5-valve superhet chassis, back, drum and push-on pointer. 25/- post paid.



Three Waveband Coil Pack, iron cored coil 16-50, 180-550, 1,000-2,000 metres, I.F. frequency 465 Kcs. Size 4 1/2in. x 4 1/2in. x 2 1/2in. 24/- Post paid. Double-ended Perspex trimming tool given free with each pack.


Mains or Battery Superhet Portable Coils, comprising medium-wave frame aerial and long-wave loading coil, used as aerial coils. Midget iron-cored screened L.M. osc. coils, complete with circuit. I.F. frequency 465 Kc. 9/6
6 Iron Cored Long, Medium and Short Superhet Coils coupling winding on all bands, 13.5-50, 180-550, 1,000-2,000 metres, complete with circuit. 8/6
Metal Rectifiers, 250 v. 60 mA, latest midget Selenium type. 7/-

Walnut Bakelite Cabinet, Size 12in. long x 7 1/2in. high x 6 1/2in. deep, scale aperture 3 1/2in. x 4 1/2in.; louvred front, complete with 3 wave-band scale, back plate, 5-valve superhet chassis and back. 19/6. Post and packing 2/-

Output Transformers, Stand-Pull 6 v. 6 matching 10 watt 2 ohms speech coil. 4/8; Push-Pull type, 5,000 ohms imp., 2 ohms speech coil, 6/9. Miniature type to suit IS3 5/-
Set of 3 Brown Knobs marked "wave change," "tuning," and "volume." 1/6.

Shooting Chokes.

30 mA 300 ohm	1/6
45 mA 300 ohm	3/-
60 mA 6-8 hen.	4/9
80 mA 10 hen.	6/6
6-pin 6 volt synchronous vibrator	8/6
6 volt standard 4-pin vibrator	8/6
Vibrator transformer 250-0-250 30 mA 6 volt Pri.	8/6

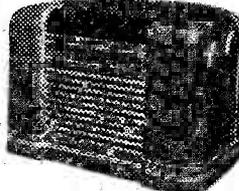

Pensolda 6 volt light weight soldering iron, weight 31 ozs., complete with 1 1/2 yards circular flex. 8/6. P. & P. 1/-

Complete with suitable heater transformer Primary 230, 250 volts, 10/6. P. & P. 1/9. Transformer not sold separately.

Midget Components, Twin gang 5in. diameter, 2in. long. (The dimensions of this gang are slightly deeper than a standard volume control.) Pair Medium and Long iron cored T.R.F. coils 2in. long x 3/4in. wide complete with a 4-valve all dry circuit, tuning scale and pointer knob. All the items 10/- post paid.

Midget Bakelite Cabinet, 7in. x 5 1/2in. x 5in. c.w. 5-valve S.H. chassis med./long wave scale and back (takes std. twin gang condenser and 3/4in. speaker). 15/- P. & P. 1/6.

Wave Change Switches, 6-pole 3-way, 2/-; 9-pole 2-way, 1/2; 4-pole 3-way, 1/9; 5-pole 2-way midget. 1/9. P. & P. 3d. each. Pre-Aligned Midget 465 Kc. Q. 120, 9/- per pair, post 6d.

Miniature 465 Kc. I.F.s. Q. 120, per pair, 10/-
465 Kc. Midget I.F.s. Q. 120, size 1 1/2in. long, 1in. wide, 2in. deep, by very famous manufacturer. Pre-aligned adjustable iron dust cores, per pair, 12/6.

Iron Cored 465 Kc. Whistle Filter, screened, each 2/6
Valve Holders, Paxolin international octal, 4d. each. Moulded international octal, 7d. each. EF50 ceramic, 7d. each. Moulded EF3 slightly soiled, 6d. each.

Line Cord, 3-way 0.3 amp., 190 ohm per yard, 1/3 per yard.
Ceramic P.F.S. 3 each of the following: 330, 220, 180 and 92, 2/6.
Trimmers, 5-40 pf., 5d.; 10-110, 10-250, 10-450 pf., 10d.
Twin Gang .0005 Tuning Condenser, 5/-. With trimmers, 7/6. Post and packing 6d.

Twin Gang Midget .00037 with perspex dust cover and trimmers, 8/6. Post and packing 6d.


Terms of business:—Cash with order. Dispatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 6d. up to 10/-; 1/- up to £1 and 1/6 up to £2. All enquiries and Lists, stamped-addressed envelope.

D. COHEN

RADIO AND TELEVISION COMPONENTS


23, HIGH STREET (Opposite Granada Cinema) ACTON, W.3

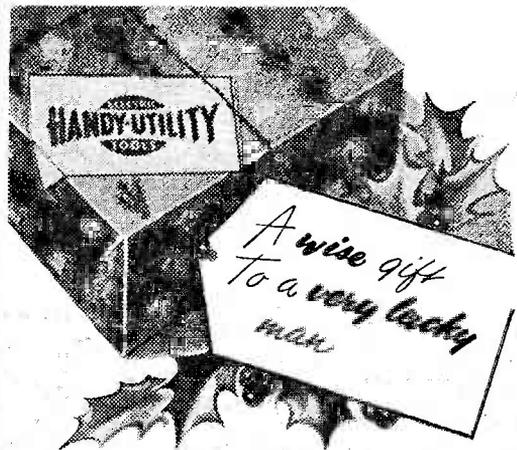Hours of Business: Saturdays 9-6 p.m. Wednesdays 9-1 p.m. Other days 9-4.30 p.m.



Make somebody proud and happy with one of these sturdy, useful electric tools! They work off your household mains. Hosts of accessories that can be added separately. Shop early for 'HANDY-UTILITY' tools—they're in great demand!

- 1 No. HU-1 1/4" DRILL. (Capacity in steel 1/4", Hardwood 1/2"). £6-10
- 2 No. HU-2300 1/4" DRILL-STAND (For 1/4" Drill or Sander-Polisher). 59/6
- 3 No. HU-20 1/2" DRILL. (Capacity in steel 1/2", Hardwood 1"). £11-7-6
- 4 No. HU-2301 1/2" DRILL-STAND (For use with the 1/2" Drill). £5-10
- 5 No. HU-50 5" SANDER-POLISHER. (Takes Drill Bits up to 1/4"). £9-17-6
- 6 No. HU-2302 HORIZONTAL STAND (For 1/4" Drill or Sander-Polisher). 17/6
- 7 No. HU-60 6" HEAVY-DUTY ELECTRO-SAW. £15-15

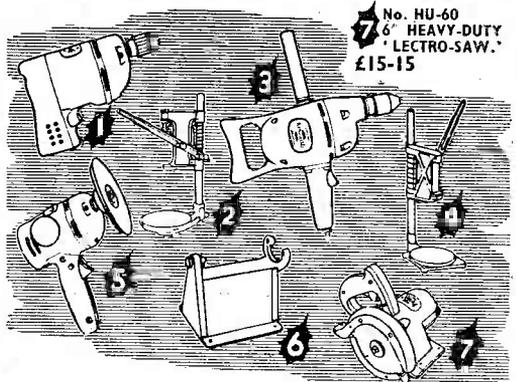

ELECTRIC HANDY-UTILITY TOOLS

and an extensive range of 'HANDY-UTILITY' accessories and attachments, saw blades, etc. PRODUCTS OF THE H.U. DIVISION OF BLACK & DECKER LTD.

OBTAINABLE FROM YOUR LOCAL TOOL SHOP, ELECTRICAL DEALER, IRONMONGER OR STORE.

FREQUENCY CONTROL CRYSTALS by American G.E. Co. Octal base. Following frequencies only: 2,500 kc/s, 3,500 kc/s, 4,000 kc/s, 6,200 kc/s, 8,000 kc/s. 7/6 each.

R.3515 I.F. STRIP. A complete I.F. Unit comprising 8 SP61 I.F. Stages, tuned to 13.5 Mc/s, 1 EA59 diode detector and 1 EF36 or EF39 output or video stage. A few modifications only are required to adapt this unit, which will give pictures of extremely good quality. Price, complete with valves and fool-proof modification instructions is 45/- plus 5/- carriage and packing. Limited quantity only.

5CP1 C.R. TUBES. Brand New and Boxed. 25/- carriage paid.

3547 RECEIVERS. Absolutely brand new, in sealed manufacturers' packing cases. Incorporating 15 valves type EF50, 2 of SP61, EF39, EBC33, 3 of EB34. Complete 45 Mc/s I.F. Strip motor dial and drive, pots, etc., etc. 25 only, plus 10/- packing and carriage. Whist they last!

I.F. TRANSFORMERS. Manufacturers' surplus. Iron-cored. 465 kc/s. Size 4in. x 1 1/2in. x 1 1/2in. Per pair, 8/6, whilst they last.

VIBRATOR POWER UNITS, 2 volt. As for Canadian 18 set. Completely Smoothed, output 1.5v. L.T. and 90v. and 180v. H.T. at 35 m.a. Complete in grey metal box. Size 8 x 3 1/2 x 4 1/2. 50/- only.

METAL RECTIFIERS. S.T.C. 300 volts 75 m.a., 6-. G.E.C., 6 volts 1 amp., 4-. Westinghouse, 12 volts 2 amp., 12/6. Pencil Type E.H.T., 600v., 1 m.a., 4/7; 1,000v., 1 m.a., 6/7.

BATTERY VALVES, 2 VOLT. P2. Super Power. 4/-; HL2. Detector, 2/6; 2155C. 4-Pin Screen Grid, 6/-; PEN 320A. Pentode, 6/-; VP2. Var. Mu. H.F. Pentode, 7-Pin, 8/6; VP23. Var. Mu. H.F. Pentode, Mazda Octal, 8/6; QP25. Q.P.P. Output, Mazda Octal, 12/6; A1P4. Trans. R. Output, Mazda Octal, 7/6; TDD2A. Double Diode Triode, 8/6.



5 HARROW ROAD, LONDON, W.2

**PADddington 1008/9
" 0401**

RECEIVER TYPE 25. The receiver portion of the TR 1196. Covers 4.3-6.7 Mc/s and makes an ideal basis for an all-wave receiver, as per *Practical Wireless*, August, 1949, issue. Complete with valves type EF36 (2), EF39 (2), EK32 and EBC33. Supplied complete with necessary conversion data for home use. 35/-. Now condition.

No. 39 "WALKIE TALKIE" TRANS-RECEIVERS. Complete with Throat Mike, Phones, Aerial Rods and Junc. Box. Freq. Range, 7.4 to 9 Mc/s. As new and guaranteed. 24 19/6. Carr. 2/6.

RECEIVER R.1355 as specified for "Inexpensive Television." Complete with 8 valves VR85, and 1 ea. 5U4G, VU120, VR92, and a copy of "Inexpensive TV." ONLY 55/- (carriage, etc., 7/6).

Send stamp for current Component List. Please include postage under 2/1

A SIGNAL TRACER at minimum cost. An easy-to-build unit that can be used for R.F., I.F., and Audio signal tracing, without any switching or tuning. Highly sensitive, easy-to-build, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain, 3-stage resistance-coupled audio frequency amplifier, with a 6in. speaker in the Output of the Power Amplifier stage. We shall be pleased to supply a complete kit for the construction of the above, right down to the last nut and bolt for the low price of 23 18/6. Concise instructions and circuits are supplied. If preferred, circuit and instructions only can be supplied for 1/6 post free. All items may be purchased separately. This is a highly efficient instrument, and a MUST for every radio man. Completely assembled and tested, ready for use, 25/5/0.

EX-GOVT. VALVES. The following are brand new: EF50 Red Sylvanian, original boxes (U.S.A.); 10/-; EF50, English Types, original boxes, 8/6; EF50, ex-Units, guaranteed, 8/6. The following at 8/6 each: EF50, EF54, EF55, CV66, EF8, EF36, EF39, EK32, EL32, EBC33, 6K7GT, 6J7GT, 6L7GT, 6SK7GT, 6S7GT, 68AGT, 6N7GT, 6S5GT, 6C5GT, 6AC7GT, 6S47GT, 6SH7GT, 6J6, 6C9, 6N7GT, 12SA7GT, 12SK7GT, 12S7GT, 12SQ7GT, 12C8, 12SR7GT, 12S7GT, 12A6GT, 14A7GT, 12Q7GT, 17A7GT, 7C7GT, 7H7GT, 7S7GT, 7BG7, 41MP, 6S, 6002, 9003, 6B7, 2E6G, 2E7G, 9D2, 4D1, 15D2, VU111, VU133, VU120A, OZ4, 6X5, VU120, 5Z4, 5Z4G, U50, U22.

The following at 10/- each: 35L6GT, 50L6GT, KT61, 6F7, ACBPEN, MU14, 6AM6, 6V6GT, 5U4G, 6Q7, 6A8G, U52, 6AG5, PEN46, 6S17GT, EF91. The following at 12/6 each: 12K8GT, 6XK6, 6N7GT, 6J6, 6V7, 2E6G, 2E7G, 4C3, 6L6 (1822 Metal). Also EA50 (VR32), 3/6; D1, 3/6; EB34, 3/6; VR85 (SP61), 7/6; RL18, 5/-; 954, 5/-; 616, 5/-; S190, 7/6.

ALL DRY BATTERY VALVES. 3V4, 1C5, 1N5GT, 1H6, 1T4, 1S5, 1R5, 1LN5GT, 1S4, 384, all at 10/- each. Also H1VAC XH at 7/6.

FREE To AMBITIOUS ENGINEERS!

This 144-page Book



'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £14 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.
- Electrical Eng.
- Civil Engineering
- Radio Engineering
- Automobile Eng.
- Aeronautical Eng.
- Production Eng.
- Building, Plastics, Draughtsmanship
- Television, etc.

GET SOME LETTERS AFTER YOUR NAME!
A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
CITY & GUILDS
GEN. CERT. OF EDUCATION etc.

--- FREE COUPON ---
Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME
ADDRESS
Subject or Exam.
that interests me
British Institute of Engineering Technology,
409B, Shakespeare House,
17/19, Stratford Place, London, W.1

PRESS-BUTTON SOLDERING!
The 'BURGOYNE' 7-Second **SOLDER GUN 79/6**
AC only 200-250v. POST FREE
Here's the tool every home handyman has always wanted. Makes soldering child's play. No current used unless actually making a joint, cold when not in use; no element to burn out; heats up in 7 seconds; no risk from touching the "wrong end." No constant re-tinning.
Spare bits 10 for 7/6

THE NEW PLESSEY MULTI-SPEED AUTOMATIC RECORD CHANGER
For 33 1/3, 45 or 78 r.p.m. and will play 10 MIXED 10in. or 12in. records. **£23.13.0**
Will also play 7in. records. The only changer available from stock that can cover all your requirements. **CASH or £7 down and 12 monthly payments of 31/6.**

All the following popular motors are in stock, and are available on h.p. terms:
BSR MU10 MOTORS for 33 1/3 and 78 r.p.m. ... **£3.15.0**
MU14 ... **£7.3.4**
COLLARO ACS14MB MOTORS for 78 r.p.m., with pickup, ... **£6.10.5**
COLLARO ACS14CB ... **£6.16.11**
CONRAD 33 1/3 r.p.m. MOTORS, Special clearance, **£3**
COLLARO RECORDING MOTORS, clock or anti-clock, 42/-
BSR FP10 RECORDING MOTORS, 38/-; SRI, 32/-; SR2, 25/-.

VIEWMASTER COMPONENTS ON H.P. TERMS
Send for our lists of hire purchase facilities on all radio and T.V. equipment. S.A.E. Please.
BIET MOS MAIL ORDER SUPPLY COMPANY
The Radio Centre (Dept. PW12)
33, Tottenham Court Road, London, W.1

50 YEARS OF RADIO



SOME HISTORICAL NOTES ON THE POLDHU STATION, ERECTED IN 1901

MARCONI'S endeavour to span the Atlantic by wireless was planned in the face of predictions, by distinguished mathematicians, that communication by means of electromagnetic waves would be limited to a distance of about 165 miles.

Erection of Poldhu transmitting station commenced in October, 1900, and the plant was completed ready for preliminary experiments in mid-January, 1901. The original aerial system consisted of a ring of 20 wooden masts, 200ft. high and arranged in a circle 200ft. in diameter, supporting 400 aerial wires forming an inverted cone.

A gale on September, 17th 1901, wrecked the aerial at Poldhu and it was replaced by a fan shaped aerial of 54 wires suspended from a triatic at 1 metre intervals. Height 150ft.

Transmitting apparatus was finally arranged for the attempt: A 32 h.p. Hornsby-Ackroyd oil engine, driving a Mather and Platt 50 cycle alternator, output 25 kW. at 2,000 volts. The 50 cycle A.C. was raised in voltage by two 10/1 ratio transformers in parallel. This output was connected through H.F. chokes to a closed oscillatory circuit in which a condenser discharged across a spark gap through the primary of a H.F. transformer. The secondary of the transformer was connected to a second spark gap and condenser and the primary of a second H.F. transformer. The secondary winding of this transformer was in series with the aerial. Keying of the transmitter was effected by the short-circuiting of chokes connected in the output from the alternator.

The condensers mentioned were each constructed by placing twenty glass plates 16in. square, coated on each side with a square foot of tinfoil, in stone-ware boxes filled with linseed oil.

Wavelength—No Record


The wavelength of the transmission was not recorded. In fact no means then existed of measuring high frequencies. From data available and results achieved it is estimated that the fundamental wavelength emitted was of the order of 1,000-2,000 metres.

A corresponding station had been commenced at South Wellfleet, Cape Cod, Massachusetts, but the circle of masts there suffered the same fate as those

at Poldhu. It was decided thereafter to make a first attempt to receive Poldhu in Newfoundland.

Marconi left England with his assistants Paget and Kemp on November 27th, 1901, arriving at St. Johns, Newfoundland, on December 5th. Every assistance was afforded him by Sir Cavendish Boyle, the Governor and Sir Robert Bond, the Prime Minister, a room in a Government building at Signal Hill being provided for Marconi's use as a receiving station.

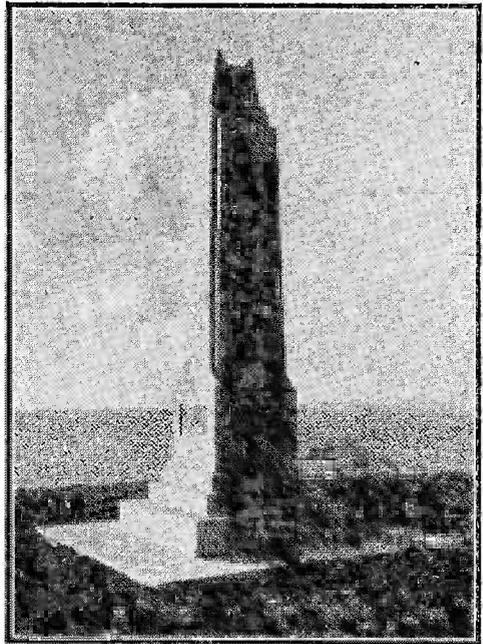The pre-arranged signal which Poldhu had been instructed to transmit was the letter "S" in



The granite column erected by the Marconi Company to commemorate the site of the former Poldhu Wireless Station at Poldhu Cove, Cornwall —November, 1937.

Morse (a succession of three dots) to be sent continuously from 3 p.m. to 6 p.m. Greenwich time, each day and, on Marconi's cabled instructions, this programme commenced on Wednesday, December 11th, 1901.

The receiving aerial at Signal Hill was supported in the first place by a balloon. Weather was rough and on its first ascent it broke away and was lost. On Thursday, December 12th, a large kite carrying an aerial wire was successfully flown to a height of 400ft. The rise and fall of the kite in the wind caused variations in the capacity of the aerial and this precluded the use of any of the syntonic receiving apparatus then available. The apparatus

should each receive a message before anyone else, it was not forwarded until, on December 21st, these telegrams had been acknowledged and communication across the Atlantic was announced to the Press.

The variable reliability of communication was still the subject of much investigation and commercial operation of this channel was not yet practicable. In the course of these researches Marconi sailed on the 22nd August, 1902, in *S.S. Lucania* to New York, having arranged for both Poldhu and Glace Bay to transmit throughout the voyage. The news sent was published on board in a daily sheet called the "Cunard Bulletin" the

success of which later instigated the general publication of similar newspapers on board ocean liners.

To meet this demand for news on board vessels—and as it had become plain that Poldhu and Glace Bay, as they stood, could not sustain a full transatlantic commercial service—it was decided to inaugurate a long-distance news service to ships from these two stations. The long series of experiments were continued elsewhere and Poldhu entered upon its career as the friend of transatlantic shipping in peace and war, in which role it will ever be remembered with affection by those whose need it served.


Progress

Progress in radio development was reflected in the various modifications to the Poldhu apparatus during these years until in 1920 experiments were made from there in telephony transmission to ships. *S.S. Victorian*, carrying delegates from the Empire Press Conference, sailed to Canada on July 26th that year and received music and speech throughout the voyage from Poldhu and Newfoundland, the experiments on board being conducted by Mr. Arthur Burrows (later "Uncle Arthur" of the BBC).

These trials, however, had soon to cease owing to the reports of what, in those days, was considered to be interference with Service communications.

Poldhu finally closed down for public transmissions on June 10th, 1922, and a series of experiments were commenced there under Mr. C. S. Franklin in methods of directional short-wave transmission in continuation of those which Marconi had made in Italy with Franklin in 1916.

At this time an elaborate scheme of high-power medium-wave Government stations to link the countries of the British Commonwealth was in hand. Contracts had been issued and in some cases work had actually commenced on the sites. But the success of these directional short-wave developments was such as to warrant dramatic eleventh-hour intervention by Marconi's Wireless Telegraph Co. Their proposal to provide the specified channels of communication at one twentieth of the cost, using one fiftieth of the power, was too sweeping to be disregarded. A contract bearing the most

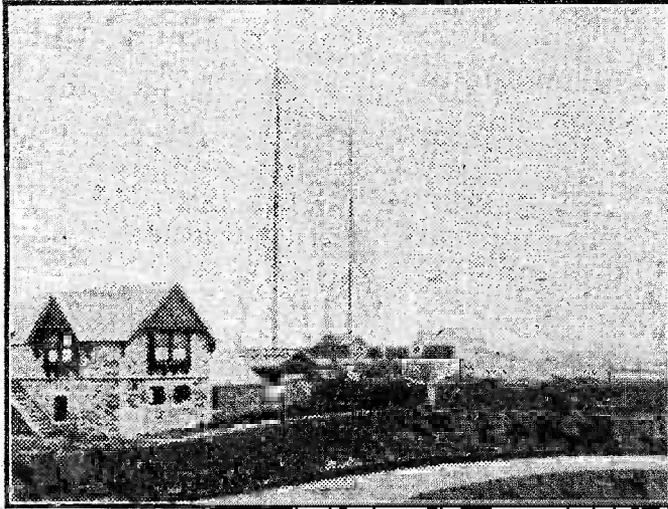

170ft. masts with 60 wire fan-shaped aerial at Poldhu, used for Marconi's first Trans-Atlantic experiment in 1901. A power of 12 kW. was used.

used was simply a self-restoring coherer in series with the aerial and a telephone earpiece.

Success!

Marconi's pocket diary carries the laconic entry for December 12th, "Sigs at 12.30, 1.10 and 2.20." On the following day, Friday, he records "Sigs at 1.38." A recognisable wireless signal had been sent across the Atlantic to the astonishment of a sometimes outspokenly incredulous world. Much, however, had yet to be learned of the laws governing the propagation of wireless waves, which to-day is common knowledge, before communication sufficiently reliable for the transmissions of coherent messages could be attained.

During the progress of the experiments, which continued for the following 12 months, a more powerful transmitting station was established at Glace Bay in Canada and Poldhu Station was used for reception.

On December 14th, 1902, Poldhu was at last able to report reliable reception throughout a two hour programme. The following day the first transatlantic wireless telegram was received at Poldhu. It was addressed to *The Times* in London but as Marconi desired that the Kings of England and Italy

stringent guarantees was signed on July 28th, 1924, and resulted in the network of Marconi-Franklin Beam Stations which now link the Commonwealth.

A Memorial

After further experimental use "Poldhu" was dismantled in 1933 and to-day no trace of this historic station remains. A memorial column of granite marks the cliff-top site. The inscriptions on its four sides read:—

Plaque Number 1.—One hundred yards North East of this column stood from 1900 to 1933 the famous Poldhu wireless station, designed by John Ambrose Fleming and erected by the Marconi Company of London, from which were transmitted the first signals ever conveyed across the Atlantic by wireless telegraphy. The signals consisted of a repetition of the Morse letter "S" and were received at St. Johns, Newfoundland, by Guglielmo Marconi and his British associates on 12th December, 1901.

Plaque Number 2.—The Poldhu wireless station was used by the Marconi Company for the first trans-oceanic service of wireless telegraphy which was opened with a second Marconi station at Glace Bay in Canada in 1902. When the Poldhu station was erected in 1900, wireless was in its infancy; when it was demolished in 1933, wireless was established for communication on land, at sea, and in the air; for direction-finding, broadcasting, and television.

Plaque Number 3.—From the Marconi Company's Poldhu Station in 1923 and 1924, Charles Samuel Franklin, inventor of the Franklin Beam Aerial, directed his short-wave wireless beam transmission

to Guglielmo Marconi on his yacht *Elettra* cruising in the South Atlantic. The epoch making results of these experiments laid the foundation of modern high-speed radio-telegraphic communication to and from all quarters of the globe.

Plaque Number 4.—The site of this column and some six acres of land on the edge of these cliffs together with the cliffs and the foreshore beneath



Some of the early apparatus at the Poldhu Wireless Station. On the extreme left are the transformers. The banks of condensers are carried in metal containers in the wooden rack. On the extreme right is the spark gap consisting of two steel spheres mounted on insulating rods. Used in sending first Trans-Atlantic signals, 12th December, 1901.

them were given to the National Trust in 1937 by the Marconi Company to commemorate the pioneer work done at the Poldhu wireless station between 1900 and 1933 by its research experts and the engineers.

Speed of Light

LAST year it was announced that experiments at the National Physical Laboratory had shown that the figure normally accepted for the speed of light was inaccurate by eleven miles a second. The apparatus used in the experiments is on show at the Institution of Electrical Engineers, Savoy Place, Victoria Embankment, W.C.2, until November 30th, 1951.

The exhibit consists of a cavity resonator in which a radio wave is reflected backwards and forwards between the two ends. When the time of travel between the ends equals the time interval between successive waves, they build up to an electrical resonance which can be detected with very high precision. Visitors are able to do this themselves.

The time of travel is about one ten-thousand-millionth of a second (1/10,000,000,000). This means that the waves follow one another at a frequency of 10 thousand million per second, and it is necessary to measure this frequency with an accuracy better than one part in a million.

Brit.I.R.E. in India

MR. G. D. CLIFFORD, secretary of the British Institution of Radio Engineers, has been invited to spend some time in India for the main purpose of establishing sections of the institution to be operated under an Indian Advisory Committee. The Government of India has given all possible help in arranging the visit which has been sponsored by the Ministry of Natural Resources and Scientific Research.

A convention of Indian members will be held in Bombay in February, 1952, for the presentation of local and other papers intended to show the development and application of radio and electrical engineering in India in both the communications and industrial fields.

Members in India are being advised separately of all arrangements for meetings, but other members who are visiting India and who wish to be advised of meetings should address their enquiries to: G. D. Clifford, British Institution of Radio Engineers, c/o Government House, Bombay, India.

For the Transmitter

SCREEN MODULATION

DETAILS OF ECONOMY CIRCUITS FOR SMALL INSTALLATIONS

By O. J. Russell, B.Sc., A.Inst.P. (G3BHJ)

ONE seldom obtains "something for nothing," and this is particularly true in the case of modulation systems. However, there are many cases where the so-called "efficiency" modulation systems are of value. Without here detailing the various "pros and cons" of high-level anode modulation versus efficiency systems of modulation, it is well known that the very small audio power requirements for efficiency modulation systems are their chief attraction. Thus, the modulation equipment required is quite modest, consumes negligible power, and requires no costly audio transformers of high power-handling capability. The actual carrier output obtainable with a given tube is, of course, reduced, but this is counterbalanced by the simplicity of the modulation amplifier.

One efficiency system of growing popularity is the screen modulation method. Perhaps this is a matter of necessity. Most popular transmitting valves nowadays are tetrodes, and unlike the pentode types no suppressor grid modulation is possible. Apart from normal signal grid modulation, screen-grid modulation is the only alternative to cathode or anode modulation. However, not all tetrodes are suited to screen modulation, and with some valves it is possible to modulate only to a depth of 30 per cent. or so before serious distortion occurs. However, the ever-popular 807 and the 6L6 are particularly suitable for screen modulation, particularly as the power requirements for modulating the screen are small. With these valves modulation can be carried to about 100 per cent. without serious distortion.

Before considering the circuit arrangements commonly employed, the operating conditions for screen modulation should be discussed. As the maximum permissible operating screen voltage sets a limit to the screen voltage swing, it is advised to adjust the screen-operating voltage to one-half of the normal operating voltage for Class C C.W. conditions. Thus, under modulation, the screen volts are swung from zero to full normal screen voltage when the peak modulation voltage equals the standing screen voltage. To be specific, the maximum screen voltage for an 807 is 300 volts. However, in normal C.W. operation 280 volts is a comfortable operating figure. Thus for screen modulation the screen volts would be 140, that is, half the normal C.W. figure. With 140 volts on the screen, full sine-wave modulation would be achieved with a peak sine-wave input of 140 volts to the screen, which for all practical purposes is almost exactly 100 volts R.M.S.

However, that is not quite the whole story. Like other efficiency modulation systems, the performance is dependent upon R.F. drive and aerial loading to a much greater extent than anode modulation systems. Thus it is advisable to have both the R.F. drive to the P.A. and the aerial

loading fully adjustable, so that optimum drive and loading can be obtained. In this respect it is as well not to adjust for maximum output. As a guide it will be found that the R.F. drive is somewhat less than for normal C.W. operation. However, unlike control-grid modulation where the same electrode is used for both the R.F. and audio signals and the best adjustment is a compromise between the two factors, in screen modulation, the modulation is applied to a separate electrode, so that R.F. drive and audio drive can be adjusted independently for optimum results. Screen modulation is thus considerably simpler to set up. It must be remembered, however, that the screen represents an impedance into which the modulator works. For the very good reason that the screen impedance under modulation may instantaneously vary between wide limits, it is advisable to use a modulator having good regulation. This may be achieved either by negative feedback or, as the power requirements are so low, a small triode may be used as the modulator. The average impedance of the screen-grid may be obtained by measuring the screen current at the operating value of screen voltage. With an 807, the screen may draw some

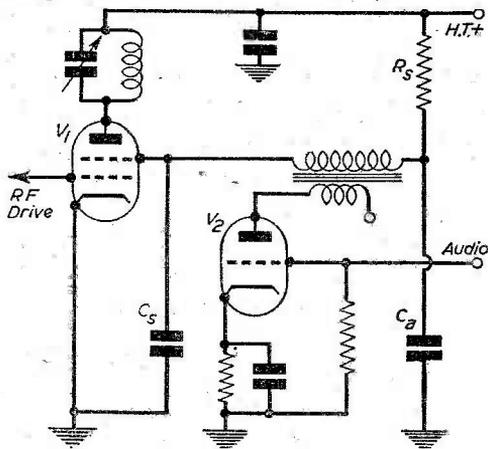


Fig. 1.—Transformer-coupled screen modulator.

C_s —0.01 μ F.
 C_a —1 μ F.

V_1 —807.
 V_2 and R_s —See text.

3 mA. to 4 mA. at 140 volts, and this represents an impedance of from 45,000 ohms to 35,000 ohms. With a triode modulator, however, it would be advisable to take a lower figure than this in view of the impedance variations under modulation. If a figure such as 15,000 or 20,000 ohms is taken, and the transformer ratio adjusted accordingly, it does not matter if the actual impedance is higher than this when using a triode. Distortion with a triode

occurs most seriously when the load impedance is lower than the optimum load, and is not at all serious if it works into an impedance higher than the optimum load. The modulating power requirements are slight. The theoretical power is half the D.C. input to the screen. This, under the reduced screen volts needed for screen modulation, is around half a watt. A small triode such as a 6C5 will usually be found adequate, and the writer has successfully used a 6C5 to screen modulate both 807s and 6L6 power amplifiers.

Alternatives

We can now briefly consider one or two circuit arrangements for screen modulation. The most simple and straightforward one is to use transformer

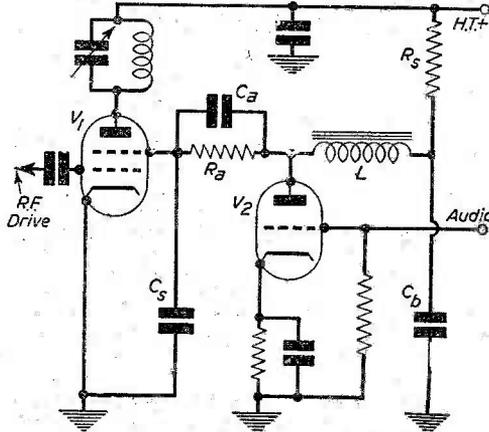


Fig. 2.—Choke-coupled screen modulator.

- V1—807. V2—6C5, etc.
- Ca and Cb—1 μ F. Paper.
- RA—30,000 Ω approx.
- L—L.F. choke at least 10 H.
- RS—20,000 Ω approx.
- CS—.001 μ F.

modulation. In view of the low power requirements, a small intervalve step-up transformer can often be pressed into service for screen modulation. Only the modulating valve itself is shown in these circuits, of course, and depending upon the microphone in use a certain amount of preamplification will be required. With a carbon microphone one R.C.-coupled preamplifier is adequate, while for a crystal microphone, two preamplifier stages will be desirable.

Fig. 1 accordingly shows a transformer-coupled triode used to modulate the screen of an 807. As the screen voltage is derived through a dropping resistance from the main H.T. line, its value will depend upon the actual H.T. line voltage. With a 500 volt supply the screen dropper will be 100,000 ohms approximately. However, with screen modulation, it is advantageous to operate the P.A. valve with a high anode potential, and with an 807 the H.T. can be increased to 750 volts. The value of screen resistor will rise to some 150,000 ohms with an anode voltage of 750. In setting up it is advisable to measure the screen potential with a suitable high-resistance voltmeter to make sure of the optimum conditions. Thus for the 807 the screen voltage should be approximately 140, and should certainly not exceed 150 volts. Lower

voltages than 150 can do no harm, merely resulting in reduced power input. Excessively high screen voltages, on the other hand, may cause bad overloading of the screen on modulation. It is well to err on the side of caution therefore, and to use a screen voltage on the low side, and 140 volts is as good a figure as any.

The component values of Fig. 1 need little comment. The screen R.F. by-pass condenser Cs should not exceed about .001 μ F. as otherwise it will cause excessive top cutting. The audio by-pass condenser Ca prevents modulation energy being wasted in the screen dropping resistance, and can be a 1 μ F. high-voltage working condenser.

In view of the low power requirements, and the possibility of using a small triode as the screen modulator, it is even possible to use the simple choke modulation system shown in Fig. 2. No comment is needed, except that an additional dropping resistance, by-passed to audio, enables the modulator valve to operate with an adequate H.T. so that it can fully swing the screen without itself overloading. With 140 volts on the screen, the modulator anode should have some 280 volts. The value of RA would then be adjusted to drop the screen to 140 volts, and would be approximately 30,000 ohms. The value of the main dropping resistor would be dependent upon the current drawn by the modulator and screen combined, and would have to be calculated or adjusted from the modulator and screen currents. With a 6C5, and a total high-tension supply of 600 volts, the

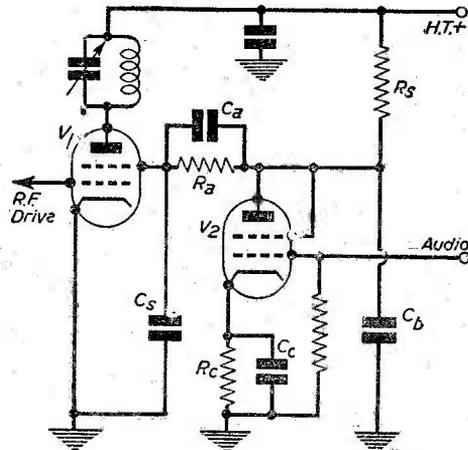


Fig. 3.—Resistance-coupled screen modulation.

- V1—807. V2—6L6 triode connected.
- Ca and Cb—1 μ F.
- CS—.001 μ F.
- RA—60,000 Ω approx.
- Cc—25 μ F. 50 volt working.
- RS—50,000 Ω approx.
- Rc—2,000 Ω . 1 watt.

value would come out at approximately 20,000 ohms and a wattage rating of 10 watts. However, with other modulators a higher wattage rating might be necessary. This system should be set up with the aid of a meter to check the current and voltage figures so that the screen volts are at the recommended figure of 140 volts for the 807.

The circuit of Fig. 2, however, using a modulation choke, is only given here for illustration purposes, although, of course, it is perfectly practicable.

It serves, however, to make the system of Fig. 3 more understandable. This is simply a resistance-coupled version of Fig. 2, in which the choke is replaced by a resistance. The power requirements for screen-modulation are so small that it is possible to tolerate the wasted audio lost in the coupling resistor. It is, of course, impossible to by-pass the resistor, as this would prevent it acting as the coupling impedance allowing the audio to be developed on the screen. The auxiliary screen dropping resistance is by-passed. The value of this arrangement is that it can be improvised from the so-called "clamp tube" circuit used to protect the screen of a tetrode when the drive is removed from the grid. It is usual to find a triode-connected tetrode such as the 6L6 used as the

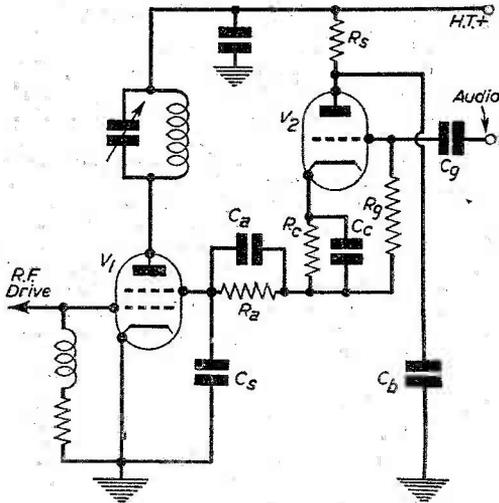


Fig. 4.—Series-screen modulator.

V₁—807. V₂—6C5.
R_a—20,000 Ω . 1 watt.
R_s—Adjust for correct voltage drops as in text, for Fig. 3.
R_c—1,500 Ω . 1 watt.

R_g—100,000 Ω . 1 watt.
C_a and C_b—1 μ F. Paper.
R_c—25 μ F. 50 volt working.
C_g—0.1 μ F.
C_s—0.01 μ F.

Synchrophase Sound Installation

A NOVEL type of sound amplification system is being installed in the Manchester Free Trade Hall by E.M.I. Sales & Service Ltd.

This new equipment is designed to overcome the unpleasant echo effect normally experienced in large halls due to the natural sound of a speaker's voice reaching the audience a fraction of a second later than the sound radiated from the loudspeakers in the body of the hall.

The echo (Haas) effect is eliminated by delaying the sound radiated by the loudspeakers until the natural sound has reached the audience so that sound from both sources is heard simultaneously. The Synchrophase Sound unit which effects the necessary delay incorporates a high-speed turntable, the edge of which is continuously coated with magnetic iron oxide.

Four magnetic heads (for recording, replay (2) and erasure) are situated so that the magnetisable edge of the turntable passes by each in turn.

The first head records the sound on the magnetic

"clamp tube." With a little auxiliary switching, it is readily possible to convert the clamp tube circuit into a screen modulator. The exact circuit constants will depend upon the tubes employed. With a triode-connected 6L6 and an 807 P.A., the values shown will be approximately correct, and can be adjusted to give correct screen operating voltage together with good audio coupling.

In view of the absence of a modulation choke in Fig. 3, at the expense of wasting some audio in the coupling resistance, it is also possible to avoid even that loss. In Fig. 4 we have what is in effect a series modulation circuit. The resistor can now be by-passed to audio, as it is merely a dropping resistor. The modulator tube is, in fact, operating as a variable impedance whose value instantaneously follows the modulating voltage. There are several points to watch about such a system. It requires a separate heater winding for the modulator tube, as the cathode is some 200 volts above ground. Also the conditions need careful juggling to get the screen potential correct, together with sufficient drop across the modulator tube to allow of adequate modulation. Despite these difficulties, at least one amateur has been heard producing good results when using such a system.

Incidentally, while a single 807 has been shown in these circuits, a pair of 807s can be readily screen modulated, giving a really healthy carrier of some 40 watts. It should be noted that the screens are connected in parallel for modulation, irrespective of whether the R.F. anodes are in parallel or push-pull. As the two screens will draw twice the current of a single screen, the dropping resistors must be modified accordingly. In the simplest case, as in Fig. 1, this will merely mean halving the screen resistor, and possibly adjusting the transformer ratio to match the halved load impedance to the modulator valve. For obvious reasons, the simple transformer system of Fig. 1 is the one recommended to beginners. The choke-coupled system is a little more tricky, while the other two systems need considerably more care in setting up and adjusting. The warning about the necessity for R.F. grid drive adjustment should be remembered.

coating, the recorded portion of which then passes by the two replay heads, spaced from the recording head to give the necessary delays.

The spacing between the recording and replay heads is adjustable to give different delay times. After passing the two replay heads the recorded edge of the turntable then passes the erase head to prepare it for subsequent re-recordings.

Two delay channels are provided, each fed by one of the replay heads. The first channel can be adjusted for delays of between 25-100 milli-seconds and feeds the loudspeakers situated in the front part of the Hall. Delays of between 70-200 milli-seconds are provided by the second channel which feeds the loudspeakers at the rear of the Hall.

The Synchrophase Sound unit is used only for speech amplification, music reproduction, etc., being effected by a normal sound amplification system. A speech filter is also incorporated to improve intelligibility.

A total output of 240 watts is given by the installation.

Down from the Olympian Heights

A CONTRIBUTOR LOOKS BACK ON THE RADIO SHOW

SIR.—It was a good show—make no mistake about that—but something was missing!

Several thousand people were missing, of course, as the attendance figures showed, but there was also a more subtle difference which made every second person you met say “I don't know what it is, but . . . !”

Now, there are a large number of obvious reasons which might account for the fact that the glory has departed . . . some of them were even advanced as official excuses.

Change of Place and Date.—First there was the change of venue—Earls Court instead of Olympia. This implied a change of name, for the National Radio Exhibition could no longer be neatly labelled “Radiolympia.” Change of name meant some loss of “good will” built up over the years. As against that Earls Court is a fine exhibition building which has housed many successful shows, and it is just as accessible, if not more easy to get to than Olympia. Indeed, the short link-line from Earls Court to Olympia was always a nuisance. By Underground you came to Earls Court first. Bus services and car parks are about equal.

This year they changed the date, too, making it a summer rather than an autumn event. In 1951 this was probably justified in order to catch the crowds already in London anyway for the Festival. On the other hand, the various Festival shows—South Bank, Battersea, Victoria and Albert and Stepney—were a considerable competition which must have seduced many of the public—especially the non-technical public from the attraction of radio and television.

Nor must we forget the big excuse put forward by the manufacturers and dealers—a crippling purchase tax. Undoubtedly 66½ was a nail in the Radio Show coffin . . . but it wasn't the lethal weapon that produced the corpse! The public, in spite of having less to spend, can still buy cars and cigarettes, can still drink spirits and go to the cinema . . . if they really want to!

The Idea is Out-moded.—If there was something wrong—and ask yourself if you got all the old excitement—it was not any of these things alone. It was all of these things plus the fact that the Radio Show idea is obsolete. It may have died with the war, or with Olympia, or with that symbol and inspiration, Alex Moody. But it's dead . . . a new idea is wanted based on the present place of radio and television in the everyday life of the people.

I suppose that the basic idea of having a show at all is to sell more sets . . . and probably in the BBC's case to preserve good public relations. Now does it want an Olympia, an Earls Court or a Castle Bromwich to do these things? I think not.

Radio, even television, has ceased to be a wonder. People buy it like they buy a hot-water boiler. They just expect it to work and few of them care much else. So I suggest that the manufacturers run one or two trade shows for dealers and servicemen, with, perhaps, a public day to round off,

rather on B.I.F. lines. Simultaneously, I think the BBC should run an “at home” week—if you like, on the lines of the R.A.F. Battle of Britain week. The public, in regions, could be asked to visit studios and transmitting stations, administrative offices and, indeed, anything that they pay for and are entitled to see. These “at homes” could be glamourised by the presence of the programme “stars”—it might even be that a hall in the vicinity should be booked as the focal point . . . and it might even be that the manufacturers could make their trade show coincide with these “at home” weeks, perhaps to the extent of becoming a technical annexe to the main function.

The fact is that few utilities can afford a national show of their own—and, let's face it, broadcasting (sound or vision) is just a utility to this generation. Is there a national gas show, a national railway show, a drainage exhibition and a hot and cold water jamboree? Of course not, and you would not expect to fill Earls Court for 10 days if you organised them. But all these utilities, not without their glamour and interest in the hands of showmen, have their own ways of displaying their wares—let us do likewise and replace this Earls Court apathy with local and realistic enthusiasm.

Does it matter if a few radio dealers, manufacturers' representatives and exhibition club lizards are deprived of a week's holiday in London at the firm's expense? And the publicity boys can soon find another way of showing how clever they are. In short, who would worry if there never was another Earls Court, vainly trying to recapture days that have gone?—“ELECTRON.”

“Practical Television”

THE current edition of our companion paper *Practical Television*, now on sale, contains practical and theoretical articles on this new hobby. Practical constructional details are given for a Pre-Amplifier with coil data for the existing three transmitters, as well as further notes on the conversion of the popular ex-Service unit the R.D.F. 1 which makes an efficient television receiver. Interference suppression is explained in two articles, one dealing with the Post Office Interference tracking service, and the other giving circuits which may be used in various types of receiver for removing the annoyance. A servicing article on Masteradio models T851, T852, T412 and T409 is also given, whilst other articles include Afterthoughts of the Show, The Design of V.F. Output Stages, Underwater Television and Colour Television.

Learn all about this new and fascinating science by placing a regular order with your newsagent for *Practical Television*, the only technical television periodical in this country. It is served by all the leading authorities, and practical articles on servicing commercial receivers, as well as constructional articles, regularly appear.

PRATTS RADIO

1070 Harrow Road, London, N.W.10

Tel.: LADbroke 1734, (Ny, Scrubbs Lane)



AMPLIFIERS READY TO USE

MODEL AC10E (as illustrated), 10 watt, 4 valve unit, neg. feedback, separate mike stage and separate gram inputs, 2 faders and tone-control, input volts, mike .003, gram 3v, £14-14-0. **MODEL AC32E** £18-18-0. For record or radio reproduction. Output to 3, 6, 15 ohms. H.P. and L.T. supply for feeder. £9-18-6.

MODEL AC18E, 6-valve unit with p pull output of 18+ watts, separate mike stage and separate mike and gram inputs, 2 faders and tone-control, feedback over 3 stages. Input volts, mike .003, gram 3v, £14-14-0. **MODEL AC32E** £18-18-0. For record or radio reproduction. Output to 3, 6, 15 ohms. H.P. and L.T. supply for feeder. £9-18-6.

MODEL AC4C (A.C.) or **MODEL UC4C** (D.C.A.C.) 3 valve 4 watt amplifier chassis for records, etc. Output to 3 ohms. £5-9-6. All units are carriage paid. As supplied to hundreds of domestic and industrial users since 1945. Stamp for fuller details.

For use with the above amplifiers. Sold separately if desired, Rothermel D104 Crystal Microphone. £5-5-0. Acos 22-1, 22-2, £6-6-0. Collaro Record Players (A.C. only) with motor, turntable pick-up and auto-stop. Magnetic. £6-9-6; Crystal, £6-15-6.

SPEAKERS, Rola 10in., 35/-; 8in., 30/-; Gramplan 12in., £7. Goodmans 12in., £8-12-6. Microphone cable, 1 1/2 yd. Stylus needles play 6,000 records, 6/6. Jack plugs, 1/9 each.

COILS, Denco L.M. wave, T.R.F. with reaction, 6/6; Wearite "P" coils, 3/- each; Weymouth "H." 3/6 each; Weymouth I.F.s, 15/- pair; Wearite standard, 10/- each; Miniature, 10/6 each.

TRANSFORMERS, ETC., 2 x 350v., 0-4-5v., 2a., 0-4-6v., 4a., 19-6; ditto, 2 x 250v., 18-6. Speaker Transformers, 8V to 3 ohms, 4/3; 6V p/p to 3, 8, 15 ohms, 19/6. IS4 354 Miniature type, 5/3.

CHOKES, 60 m.a., 15 hv., 300 ohms, 5/3; 100 m.a., 20 hv., 400 ohms, 16/6; 150 m.a., 10 hv., 200 ohms, 16/6; 80 m.a., 10 hv., 180 ohms, 13/6.

VAR. CONDENSERS, Solid dielectric, .0003 or .0006, 4/- each.


FIXED CONDENSERS (only 1951 stock offered), 2-8, 4/9; 8-16, 7/3; all 500v. 50 mfd., 30/-; 25 mfd., 25/-; 25 mfd., 25/-; .0001, .0002, .0003, 8d.; .0005, .001, .002, .005, 9d.; .01, .05, 1 mfd., 10/6.

MISCELLANEOUS, 6K7, 6J7, 6J5, all 7/6; 1S5, 1S4, 354, 1T4, 1T5, all 9/6 each; 3a. droppers, 800 ohms, 4/6; 2a., 1,000 ohms, 4/6. B7C bases, 9d. Linecord, 3a. 60 ohms, ft., 7d. ft. All goods new. Post paid over £1. C.W.O. or C.O.D.

Speed-up
SOLDERING
with



SOLDERGUNS

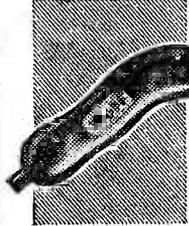

TYPE 21



TYPE 31

TYPE 71

TYPE 41

TYPE 61

Only Wolf Solderguns have all these time and money saving advantages—

Off-straight Easy-grip Handle • Perfect Control • Low Current Consumption • Models for every purpose from Fine Instrument to Heavy Industrial Soldering • Localised Heat • Maintains Correct Heat • Quicker Heat-up

The Bennett College

"I GUARANTEE YOU TUITION IN ANY OF THESE SUBJECTS UNTIL YOU HAVE REACHED DIPLOMA STAGE AT NO EXTRA COST"



Text Books are FREE to STUDENTS of THE BENNETT COLLEGE
You study at your own pace with your own Special Tutors.

Aviation (Eng. & Wire), Civil Service, Commercial Subjects, Draughtsmanship, Engineering, Gen. Cert. of Education, Mathematics, Plastics, Radio Service Eng., Salesmanship, Telecommunications, Television, Wireless Telegraphy, Works Managers and many other subjects

YOU CAN START A BENNETT COLLEGE COURSE FOR 30/- ONLY
and monthly payments of 15/-.



I am satisfied that no better system is possible. I say this about The Bennett College methods because of the long and unceasing line of successful students who have passed through the hands of our personal Tutors. The advantages to YOU of The Bennett College Training are immense. You wonder if I am over-stating the case? I am not. I am too proud of the College's tradition for sincerity and truth. I can help you—will you let me?

To the Governor, Dept. L104, The Bennett College, Sheffield, England.

I would like to have (at no cost) your prospectus and particulars of

NAME


ADDRESS

AGE (if under 21)

(Please write in Block Letters)


AUTOMATIC SOLDERING

Win new efficiency and economy with Wolf Automatic Soldergun. Its auto-feed, trigger solder-feed action and perfect balance make it indispensable to all modern assembly.


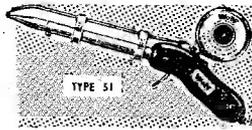


TYPE 51

SOLDERING IRONS

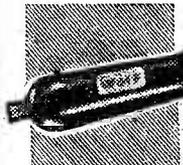

TYPE 22

  

For all who, for special reasons, prefer the conventional straight type handle. Identical as regards elements and bits to Wolf Solderguns but with round hard wooden handle with heat deflecting skirt.



ELECTRIC SOLDERGUNS & SOLDERING IRONS

★ Obtainable from all high class stockists and ironmongers
WOLF ELECTRIC TOOLS LIMITED - PIONEER WORKS
HANGER LANE - LONDON - W.5 Telephone: PERIVALE 5631-4



HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an I.C.S. Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television include the following:

Complete Radio Engineering, Radio Service Engineers Radio Service and Sales, Advanced Short-Wave Radio Elementary Electronics, Radar, Radio and Television Technology.

And the following Radio Examinations:
British Institution of Radio Engineers
P.M.G. Certificates for Wireless Operators
City and Guilds Telecommunications

Write today for our FREE "Radio" booklet, which fully describes the above I.C.S. Courses. Generous Discount granted to members of H.M. Forces.

International CORRESPONDENCE SCHOOLS

Dept. PW23, International Bldgs., Kingsway, London, W.C.

C. & W. ELECTRONICS TEST INSTRUMENTS

20 Range Multimeter M.M.2.
A.C./D.C. Volts from 25v. to 2,500v. at 4,500 Ω /v.
Basic Movement 20 μ A.
Scale Length, 3in.
D.C. current from 10 μ A to 1 amp.
Resistance from 1 ohm to 5 megohms.
Power and D.E.S.
1st Grade Accuracy on all ranges.
Complete with Test-prods and instructions.
£8/0.

Signal Generator S.2.
Range 100 kc/s. to 70 mc/s.
400 c.p.s. Audio. Int. & Ext. Mod.
Ladder, and fine Attenuator.
Direct Reading Frequency Dial.
Grey Crackle finish.
Complete with R.F. & A.F. leads. £8/0
12 months' guarantee on all instruments.
Send S.A.E. for leaflets.

C. & W. ELECTRONICS, 61, CHURCH STREET
OSWESTRY, SALOP

SPARKS' DATA SHEETS

Recognised as the Safest, the Simplest and the Finest Tested and Guaranteed Radio Constructional Radio Sheets.
JUST RELEASED!

THE "MIDDY"

A Two-Valve of Outstanding Performance on Medium- and Long-waves. All-dry batteries. Compact and Simple to Build. Tested under Stringent Conditions in Dorset. Speaker reproduction on both "Third" wavebands: "Light" ditto: Regional and Continental Stations plus the additional thrill of "Ship-to-Shore" Transmissions. The "Middy" is a Set which will set a Standard.

BE READY FOR POWER CUTS. Have a "Stand-by" Set handy. The "Middy" is ideal for this, for the Bedside, the Den, your Caravan or Yacht, or Camping.

FULL-SIZE DATA SHEET with instructions 3/2d.

REMEMBER SPARKS IS NOTED FOR A SQUARE DEAL. My Tested Designs range from a Crystal Set to a 9-valve Quality Radiogram. Send Stamp for List.

COMPONENTS SUPPLIED

L. ORMOND SPARKS (P)

42A, HIGH STREET, SWANAGE, DORSET

G2AK This Month's Bargains G2AK

All types of Osmor, Weymouth, Denco and Wearite Coils always in stock.

MIDGET SPEAKERS. W.B., 2 $\frac{1}{2}$ in., 16/6; Phillips, 3in., 15/-; W.B., 5in., 16/-; Elac, 6 $\frac{1}{2}$ in., 17/6; P. & P., 1/-.

TEST PRODS. for test meters. Red and black, 4/6 pair. ELAC FOCUS UNITS, for triode and tetrode tubes. P.M. type; List, 30/-. Our price, 20/-. post free.

T.V. TUBE MASKS, brand new, new ratio, 15/- each, post free.

SELENIUM RECTIFIERS, 250 v. 60 m.a. D.C. output. New, 7/6 each.

MORSE PRACTICE SETS, with double-action buzzer, output for 'phones, excellent key, require only 4 $\frac{1}{2}$ v. battery. As new, 7/6. P. & P., 1/-.

MIDGET OUTPUT TRANSFORMERS for personal portables, 6/- Standard pen., 5/6. Mike trans. for M.C. mikes, 2/-; for carbon, 1/3 each.

XTAL DIODES, 3/9 each. Germanium diodes, 5/6 each.

MICROPHONES. Carbon inserts, 2/6 each. M.C., No. 7, 3/11. Loud hailer, 7/6.

AVO MULTIPLIERS, 4,800 volt, for model 40, 5/-, post 9d.

POTENTIOMETERS. 20 k. and 25 k. W.W. 5 w., 2/- each. Carbon, 50 k., 100 k., 1 meg. and 2 meg., 1/6 each. 500 ohm H.D. toroidal, 3/6 each.

TWIN FEEDER. 300 ohm H.D. Twin, 5d. yd. Standard K25 300 ohm, 9d. yd. K24 150 ohm, 9d. yd. Coax. T.V. cable, 1in., 1/3 yd. Packing and postage on cables, 1/6.

SPECIAL VALVE OFFER. Kit of 4 midget 1.4 v. valves, 1 each 1S5, 1R5, 1T4 and 1S4, 30/- or 8/6 each, separately. Postage free on all orders over £1 except where specifically stated. PLEASE PRINT YOUR NAME AND ADDRESS.

CHAS. H. YOUNG, G2AK

All Callers to 110 Dale End, Birmingham

CENTRAL 1635

Mail Orders to 192 Holloway Head, Birmingham.
MIDLAND 3254

MATCHBOX RADIO RECEIVERS

FULLY ASSEMBLED RECEIVER. Tunes B.B.C. Long and Medium Waves. Fitted with station selector switch and non-linear impedance unit. Price, 15/-, post free.

KIT OF PARTS. Fully illustrated instructions and kit containing everything necessary for building the matchbox receiver. Price, 11/-, post free.

INSTRUCTIONS ONLY. Full step-by-step instructions, working drawings and theoretical wiring diagram. Price, 3/-, post free.


JOHN O'BEIRNE (W),

137, COTHAM BROW, BRISTOL, 6

ORDERS BY POST ONLY

GRAM MOTORS


& PICK-UPS for MICRO-GROOVE RECORDS

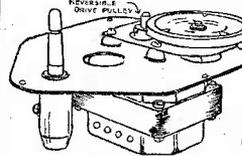

B.S.R. MU-10 motors for 33 & 78 r.p.m. Speed change by reversing drive pulley. 10in. turntable. 100-250v. £3.18.7

MU-14 de luxe model with ROTACAM instant speed change for 33, 45 & 78 r.p.m. £5.14.3

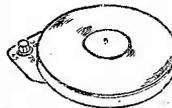ACOS GP-20 pickups, standard £2.11.5
GP-19 LP microgroove head only £2.34



Frith
RADIOCRAFT
69-71 CHURCH GATE-LEICESTER
PHONE 58927

News from the Trade


Hadley Coin-operated Radio Equipment

THIS new coin-operated radio system is specially designed for Hotels, Holiday Camps, Hostels, Nursing Homes, Block of Flats, etc. Programmes are relayed to attractive room units from a central control.

The user merely puts sixpence in the slot and selects his programme from a choice of two or more. Normally, managements arrange to give 24 hours listening for sixpence, but the cancellation routine can be varied as required.

Maximum volume is controlled centrally, thus ensuring that users of room radio will not disturb others.

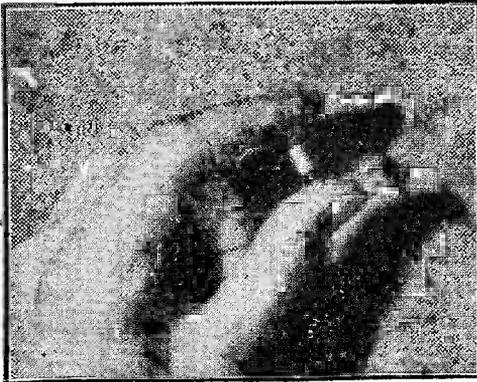The complete system is available on Rental



One of the new Westinghouse crystal rectifiers.

terms or can be purchased outright.—**Hadley Sound Equipments, Ltd., Cape Hill, Smethwick, Staffs.**

Westinghouse Germanium Crystals

THE Westinghouse Brake and Signal Company have introduced a wide range of germanium crystal rectifiers. These are of hermetically sealed ceramic construction and are only $\frac{1}{8}$ in. long by $\frac{3}{16}$ in. diameter. The range of types covers peak working voltages up to 100 volts and forward currents of 50 mA.

These crystal rectifiers are suitable for detectors, limiters, instruments and general purposes, the self capacity of all types being approximately 1 pF.

Each crystal rectifier is mounted on a colour-coded card giving the rating particulars. A leaflet, M.R.14 supplement 5, is available showing typical characteristics of all types and includes a tabulated list showing which type to select for each of the sixteen applications for which these germanium crystal rectifiers are particularly suitable.—**Westinghouse Brake & Signal Co., Ltd., 82, York Way, King's Cross, London, N.1.**

Regentone Price Changes


WE are asked to point out that the Auto "99" has been increased in price to 47 guineas, and the 3-speed version is now 53 guineas instead of 50 guineas as originally quoted.—**Regentone Products, Ltd., New Factory, Eastern Avenue, Romford, Essex.**

Southern Radio

A NEW edition of the popular illustrated catalogue No. 8 is now available from Southern Radio. This is a well-produced 50-page edition and is fully illustrated, covering all the well-known makes of component in alphabetical order. Copies are available to readers at 9d. post free from **Southern Radio & Electrical Supplies, 85, Fisherton Street, Salisbury, Wilts.**

Winel Record Cases

THE satisfactory storage of a large number of gramophone records often presents a problem, and unsatisfactory methods lead to warped or scratched discs. Messrs. Elwin have for years specialised in the manufacture of boxes of all types and have produced a wide range of record storage boxes ranging from small carrying cases suitable for picnics up to large units capable of holding 100 records. Separators and a large index card are provided and it is a simple matter to select any desired disc when required. In addition record albums are also available and designed to hold

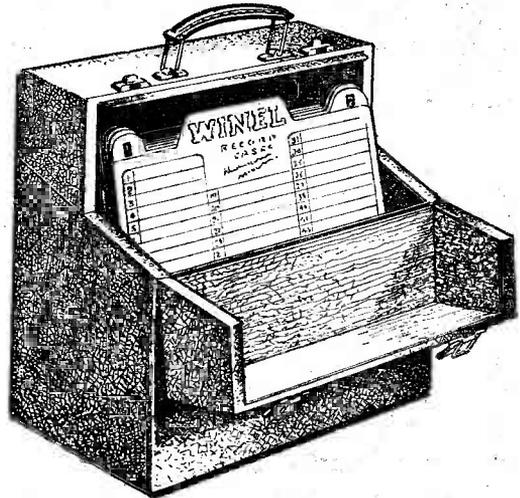

A record case from the Winel selection.

expensive discs in such a manner that not only are they satisfactorily protected, but the outward appearance of the albums is in keeping with the contents. Illustrated above is the Pyramid portable case designed for 50 records in two sections of 25. It is available in four colours, black, blue, red and green and for either 10in or 12in. recdrds.—**Henry Elwin Ltd., Plumtre Street, Nottingham.**

Osmor—Phone Change

OSMOR RADIO PRODUCTS, LTD., of Bridge View Works, Borough Hill, Craydon, Surrey, wish to inform customers and the trade that their telephone number has now been changed to Craydon 5148/9.

SURPLUS SILICON CRYSTALS

DETAILS OF POPULAR TYPES NOW AVAILABLE

By E. G. Bulley

THE reader may or may not be aware that these crystals are available on the surplus market. The types that seem to be in abundance are the CV101 and CV102, although other types of silicon crystals are available but are not so plentiful.

However, these crystals are to be had at reasonable cost and this does, therefore, enable the amateur to experiment in another field without much outlay.

The silicon crystal can more or less be compared with the thermionic diode as they have a fairly low resistance in the forward direction and a high resistance in the reverse direction. This perhaps can be clarified by remembering that as in a valve diode, the valve conducts on one half cycle, and does not conduct on the other half. This phenomena is similar to the forward and reverse direction of the crystal, respectively. As a point of interest the silicon crystal has more or less a negligible transit time, thus enabling them to be used at very high frequencies, an advantage over the thermionic diode.

Construction

The basic construction of crystals of this class consists of a silicon crystal or flake and a contact, the latter usually known as "the whisker," and this is made from pure tungsten or some suitable alloy. Both these electrodes are, however, found enclosed in a low-loss ceramic body.

The whisker is usually secured to the threaded portion of the crystal, but this naturally depends upon the crystal in question and its design.

Details

In crystals of this nature, there are, however, important parameters in their actual design, an important one being the diameter and shape of the whisker. This can be fully appreciated by the reader when he realises that the correct contact pressure against the silicon crystal is necessary to enable the crystal to function properly.

An essential requirement in silicon crystals is that of good conductivity, and this is ensured by either silver or gold plating the metal parts. The plating of such parts also prevents corrosion which must be avoided at all costs, otherwise the crystals will cease to function entirely or operate incorrectly.

Silicon crystals that are available on the surplus market lend themselves admirably to the experimenter for use in experiments on radio frequency and video detection, rectification and frequency conversion.

They are extremely useful in various measuring devices that the amateur may care to construct, such as field strength meters, etc. However, these are beyond the actual scope of this article, and various circuits utilising the crystals have already appeared in this journal, and will, no doubt, appear in future issues.

It is as well to mention, however, that crystals can be burnt out if they are not operated within their ratings, especially if they are subjected to a signal strength of excessive quantity. Another point of interest to the amateur is that the contact point of the whisker sometimes fuses, whereby the actual area of contact is increased and this in turn greatly effects the crystal.

Care

Crystals of this nature should be handled with care, remembering of course, that any mechanical knock will no doubt damage the crystal. One will note, that they are supplied in a lead cover, and this is for the sole purpose of safeguarding the crystal from stray R.F. fields which would do untold damage to the crystal. It is advisable, therefore, that the amateur should store such crystals in the lead cover when not in use.

Advisory Committee Formed

THREE Associations whose interests include matters relating to the development and production of radio communication and radar measuring instruments have collaborated in the formation of a joint committee which will advise their respective Councils on such subjects. The three Associations are the Radio Communication and Electronic Engineering Association, the Radio and Electronic Component Manufacturers Federation and the Scientific Instrument Manufacturers Association.

Membership

Membership of the joint committee, which is known as the Joint Advisory Committee on Radio Communication and Radar Measuring Instruments, is open to any member of the three Associations who is concerned with the development or production of this class of measuring instrument. The joint committee will be in a position to consider both commercial and technical questions brought to its notice by members themselves, Government Departments and other external bodies. It is particularly expected that the provision of this single channel for consultation with Government Departments on matters of common interest will prove convenient both to the Industry and to the Government.

Address

The joint committee, which is not another trade association, is administered from the offices of the Radio Communication and Electronic Engineering Association, 59, Russell Square, London, W.C.1 (telephone: Museum 6905); the Committee Secretary is the Assistant Secretary of the R.C.E.E.A.

● A speaker for the constructor's every need

Type	Cone dia.	Flux Density (Gauss)	Pole dia.	Gap length	Flux face	Total Flux	Speech coil Impedance (Ohms)	Handling Capacity (Watts)	PRICES	
									With Trans. £ s. d.	Without Trans. £ s. d.
*S.2.57	2½"	7,000	.375"	.033"	.093"	5,285	3	.3	—	18 6
*S.3.57	3½"	7,000	.625"	.035"	.125"	11,500	3	2	—	19 6
S.507	5"	7,000	.75"	.040"	.125"	14,000	3	2.5	1 8 9	1 1 0
*S.607	6"	7,000	.75"	.040"	.125"	20,000	3	3	1 11 9	1 2 6
S.607	6"	7,000	.75"	.040"	.125"	20,000	3	3	1 13 9	1 4 6
S.810	8"	10,000	1"	.043"	.187"	39,500	3	5	2 3 0	1 12 6
S.912	9"	12,000	1"	.043"	.187"	47,400	3	7	2 7 3	1 16 9
S.1012	10"	12,000	1"	.043"	.187"	47,400	3	10	3 3 0	2 4 6
S.12135	12"	13,500	1.5"	.050"	.25"	106,000	15	15	10 0 0	9 0 0

Further details of these speakers and of the famous Concentric-Duplex models gladly sent on request.

* All chassis material is of Mazak 3 except those marked with an asterisk which are of Drawn steel



Stentorian

LOUDSPEAKER CHASSIS

WHITELEY ELECTRICAL RADIO CO. LTD. MANSFIELD NOTTS

**BUILD YOUR OWN
MODERN RECEIVER
for
HALF the normal cost**

You're SURE to get it at
STERN'S
ESTABLISHED 25 YEARS

**SOME POPULAR
CIRCUITS for the
HOME CONSTRUCTOR**

- * **A MIDGET 4 STATION "PRE-SET" SUPERHET. RECEIVER** for A.C. mains. Designed to receive any three stations on Medium Waveband and one on Long Wave by the turn of a Rotary Switch, no Tuning being necessary. The set can be supplied either as a Complete Kit of Parts, or by purchase of the Components separately. The Complete Assembly Instructions, showing the Wiring Diagram and Component Layout and Point to Point connections, together with a Component Price List available for 1/6.
- * **A 4-VALVE T.R.F. BATTERY PORTABLE "PERSONAL" SET**, available as a Complete Kit of Parts or by purchase of the Components separately. The complete price details, including an individual Component Price List, are included in our set of Assembly Instructions, which is obtainable for 9d. In addition, these detailed Assembly Instructions also show the complete circuit, with a Practical Component Layout, which in themselves make the assembly of the set quite simple.
- * **A MIDGET 4-VALVE SUPERHET. PERSONAL SET**, covering Long and Medium Wavebands and designed for Mains or Battery operation. This receiver is designed to operate on A.C. mains or by an "All-dry" Battery; either method is selected by means of a Rotary Switch. It is so designed that the Mains Section is supplied as a separate section which may be incorporated at any time. The set, therefore, can be made either as an "All-dry" Battery Personal set or as a Midget Receiver for Combined Mains/Battery operation. The set can be supplied either as a Complete Kit of Parts or by purchase of the Components separately. The Assembly Instructions which include Wiring Diagram and Practical Component Layouts, are available for 1/9. This also includes a separate Components Price List.

- * **THE MIDGET A.C. MAINS 3-VALVE RECEIVER**, as designed and published by "Wireless World" covering Long and Medium Wavebands. Cost of all Components to build this set is £4/17/9. A reprint of the complete Assembly Instructions, including Practical Layouts, is available for 9d.
- * **THE "WIRELESS WORLD" MIDGET A.C. MAINS 2-VALVE RECEIVER**. We can supply all the components including Valves and M'Coil Speaker, to build this set for £3/10/0. Reprint of the original Assembly Instructions and Circuit may be obtained for 9d.
- * **THE "SUMMER ALLDRY" BATTERY PORTABLE**, as published in the June issue of "Practical Wireless." We can supply from stock all of the Components to build this Midget 3-Valve Receiver. A reprint of the complete article and circuits, including Practical Layout and Component Price List is available for 1/-.
- * **A COMPLETE KIT OF PARTS** to build a MIDGET "All-dry" BATTERY ELIMINATOR, giving approx. 69 volts and 1.4 volts. This eliminator is suitable for use with 4-valve Superhet. Personal Sets. It is easily and quickly assembled and is housed in a case size 4 1/2 in. x 1 1/2 in. x 3 1/2 in. Price of Complete Kit, 42/6. In addition we can offer a similar complete kit to provide approx. 90 volts and 1.4 volts. Size of assembled unit 7 in. x 2 1/2 in. x 1 1/2 in. Price 47/6.
- * For £6/5/0. A Complete Kit of Parts, including Drilled Chassis and Valves, to build a 6 to 8 watt **PUSH-PULL AMPLIFIER** for operation on A.C. Mains. Incorporates Tone Control and is suitable for use with any type of pick-up. The complete set of Assembly Circuits, including Practical Layouts, is available for 9d.


* Send 9d. P.O. for our NEW STOCK LIST, showing many KITS OF PARTS for Sets and Battery Chargers and "hundreds" of Wireless Components. When ordering please cover cost of postage and packing.

STERN RADIO LTD., 109 & 115, FLEET STREET, E.C.4.

Telephone :
CENTRAL 5814 & 2280

THE MODERN BOOK CO.

Reference Data for Radio Engineers, by W. L. McPherson. 7s. 6d. Postage 6d.
Wireless Servicing Manual, by W. T. Cooching. 12s. 6d. Postage 4d.
The Royal Signals Handbook of Line Communication, Volume 1. 20s. 0d. Postage 1s.
Television Receiving Equipment, by W. T. Cooching. 18s. 0d. Postage 6d.
The Radio Amateur's Handbook, by The American Radio Relay League. 24th Edition. 22s. 6d. Postage 1s.
Radio Engineering, Edited by R. C. Norris. 15s. 0d. Postage 9d.
Sound Reproduction, by G. A. Briggs. 2nd Edition. 10s. 6d. Postage 6d.
Theory and Design of Valve Oscillators, by H. A. Thomas. Volume VII. 36s. 0d. Postage 6d.
A Handbook of Telecommunication, by B. S. Cohen. 36s. 0d. Postage 6d.
Radio Servicing Theory and Practice, by A. Marcus. 35s. 0d. Postage 1s.
Television and Radiogram, by W. I. Flack. 6s. 6d. Postage 4d.
Amplifiers, by N. H. Crowhurst. 3s. 6d. Postage 3d.
Radio Valve Data, by 'Wireless World'. 2nd Edition. 3s. 6d. Postage 3d.
R.S.G.B. Amateur Radio Call Book. Autumn, 1951. 3s. 6d. Postage 3d.
 We have the finest selection of British and American radio books in the country. Complete list on application.
19-23 PRAED STREET (Dept. P. 12), LONDON, W.2. PADDINGTON 4135.

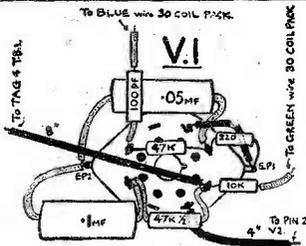

This is a small reproduction of a simple sub-assembly from one of our series of *unique, LIFE-SIZE, "Easy-as-A-B.C." Construction Blueprints*. If YOU could wire this unit then you can make any of the **GUARANTEED CIRCUITS** given in our "HOME CONSTRUCTOR'S HANDBOOK", knowing that failure is impossible! The latest issue of our famous book is **AGAIN ENLARGED** to contain the following twelve **FULL-PAGE** circuits, with descriptions, illustrations, full parts lists, and a host of useful information, formulae, etc.
 ●3 Valve, 3 wave FEEDER.
 ●4 Valve, 3 wave FEEDER (with "hi-fi" switching).
 ●5 Valve, 3 wave A.C. SUPER.
 ●5 Valve, 3 wave A.C./D.C. SUPER.
 ●Feeder amplifier and Power Pack.
 ●6 Valve, 3 wave A.C. SUPER.
 ●6 Valve, 3 wave A.C./D.C. SUPER.
 ●SIGNAL TRACER.
 ●4 Valve BATTERY SUPER.
 ●5 Watt AMPLIFIER.
 ●10 Watt High Quality AMPLIFIER.
 ●SIGNAL GENERATOR.
 All for the nominal price of 2/6!
SEND NOW for YOUR copy, obtainable ONLY from
RODING LABORATORIES
 694, Lea Bridge Road, London, E.10.
(Mail office W.D.)

MODERN ELECTRICS LTD.

Decca 3-speed A.C. gram units, complete £7 3s. 4d.
Dual PICK-UPS for above, for L.P. and standard recordings... £3 19s. 2d
Cosmocord G.P.20—we still have a small stock of these famous PICK-UPS, price... £3 11s. 5d.
G.P.19 Spare Heads—L.P. and standard for the above £2 3s. 4d.
GARRARD, PLUG-IN type HEADS, for 65A and 70A.
GARRARD ADAPTORS to convert older models.
E.M.I. TAPE £1 15s. 0d. (High Coercivity).
Soundmirror TAPE £1 5s. 0d.
Recording TAPE, by G.E.C. £1 10s. 0d.
Recording TAPE, by DUREX £1 15s. 0d. (per 1,200ft. reel.)
Just released—"MAGNETIC RECORDING," by Chief Engineer, Brush Development Co. The most comprehensive publication on Tape and Wire recording. 26/- post free.
MODERN ELECTRICS LTD.
 164, Charing Cross Rd., W.C.2
 TEMPLE BAR 7587.
 Export enquiries welcomed.

HIGHSTONE UTILITIES

Soldering Irons, streamlined iron, with curved Pencil Bit, 200/250 v. 50 w., 10/- Standard Iron, with adjustable bit, 200/250 v., 60 w., 11/- Heavy Duty Iron, 150 w., 14/6, all post 6d. Magneto, small ex 2in. meters, 1/- each, post 3d. Telephone Hand Generator with handle, 7/6, post 1/6. Bell, 3/6, post 6d.
Crystal Sets, which are fitted with a permanent crystal detector. Why not have a set in your own room—10/6, post 6d. De Luxe receiver in polished oak cabinet, 18/6, post 1/- Spare Permanent Detectors, 2/- each. When desired separately, 3/6. With clips and screws, 2/10, post 3d.
Headphones, in good order, 5/6; better quality, 7/6. New Headphones, 10/- a pair. Balanced armature type (very sensitive), 12/6 a pair, all post 6d. New Single Earpieces, 3/6. Bal. armature type, 4/6; ex-R.A.F. earpieces, 2/-, post 4d. All headphones listed are suitable for use with our crystal sets. Hand Microphones, with switch in handle, and lead, 4/- Similar instrument, moving coil, 7/6, post 6d.
Sparking Plug Neon Testers, with vest pocket clip, 3/6, and with gauge, 3/6, post 3d. EX-R.A.F. 2-Valve (3-valve) Amplifiers, can be used to make up a deaf aid outfit, intercommunication system, or with crystal set, complete with valves and fitting instructions, 20/-, post 1/6. Ditto, less valves, 10/- Wooden box to hold amplifier, 2/- extra.
Meters, 10v., 2 1/2in. Rectifier (a.c.) in wooden carrying case, 14/6 (15v., 2 1/2in. m.c., 9/6; 150v., 2 1/2in. m.c., 10/- 3,500v., 2 1/2in. m.c., 20/-; 6,000v., 3 1/2in., m.c., 47/6; 15,000v., 2 1/2in., m.c., double reading, 8/- 2.5 amp. 2in., T.C., 5/-; 4 amp., 2 1/2in. T.C. in case with switch, 7/6. Meter Movements, Units containing two 500 microamps. 5/- All meters post extra. Money refunded if not completely satisfied.
HIGHSTONE UTILITIES.
 58, New Wanstead, London, E.11.
 Letters only. New Illustrated List sent on request with 1ld. stamp and s.a.e.

YOU can become a first-class RADIO ENGINEER

We are specialists in Home-study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

T. & C. RADIO COLLEGE

---Post in unsealed envelope, 1 1/2d. postage---
To: R. Heath Bradley, T.C.R.C. 36, Northfield Road Ringwood, Hants.
 NAME.....
 ADDRESS.....
 P.119.

"YOU CAN RELY ON US"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES
VALVES—6SH7, 6/6; EF50, 7/6; 12SG7, 6/-; 12SR7, 6/6.
SWITCHES—1 pole 18-way, 2/6; 4 pole 3-way, 3/6; 3 pole 4-way, 3/6; 2 pole 6-way, 3/6; 6 pole 3-way (W Change for Superhet with R.F. stage), 4/6.
I.F. TRANSFORMERS—RS/GB, Semi-Midget, 466 kc/s., 12/6 pair. Wearite Midget M400B, 465, 21/- pair; Weymouth P4, 15/- pair; M800 Wearite Midget, 10/6 each.
COILS—All Wearite "P" Coils stocked, 3/- each. TRF matched pair, MW/LW with reaction, 7/6. (No. 2 coil O.K. for "Summer Portable"). Weymouth CS3W3, 11/6 pair. CT2W2, 9/6 pair.
SPEAKER TRANSFORMERS—Super Midget for personals, 154, 359, D192, etc., 5/-; Mains Midget 12/6. Standard type, 48 : 1, 4/6, 60 : 1 and 30 : 1, 4/6. Push-pull 6V6 to 2-3 ohms, 8/6.
I.F. FILTERS—Aerial, 465 kc/s. Filters complete, 6/8. Not surplus.
CERAMIC TRIMMERS—30 pf., 50 pf., 9d. 100 pf., 1/-, 250 pf., 1/7, 500 pf., 2/-, 750 pf., 2/8.
TWIN GANGS—0.005 uF. Complete with rubber-mounted feet and slow motion driver, 10/6.
MIDGET TWIN-GANG, 10/6.
SPEAKERS—W. B., 2 1/2in., 17/3. Plessey, 5in., Lightweight, 15/-; R. and A., 6 1/2in., P.M., 12/6. Stockists of Haynes, Weymouth, Wearite, Viewmaster, Easy-butt Televisor. Don't forget postage, chaps, and write for Catalogue 10 and Bargain Valve List. Price 6d.

RADIO SERVICING CO.
 444, WANDSWORTH ROAD, CLAPHAM, LONDON, S.W.3
 Telephone: MACaulay 4155.
 77, 77A, 166, 169 Buses; S.R. Station, Wandsworth Road.

Programme Pointers

A MONTHLY CRITIQUE BY MAURICE REEVE

THE British have long been noted as watchers of games—as distinct from a nation playing them. Whether on the bowling green, the cock-fighting alley or the fisticuff ring, round which the squire, the parson and the fraternity would foregather largely as an excuse to guzzle and bet, to our own day which witnesses no fewer than a hundred and fifty thousand gathered at Hampden Park to watch the local Rangers and Celtic play for the honours of Scottish soccer, or scarcely fewer at Twickenham, Wembley or Lord's—multitudes watch whilst a handful act. As the years slip by, fewer and fewer take part, only to succumb to the ease of the ringside seat or the chair by the radio, which provides the biggest audience of the lot.

It is not unnatural, therefore, that the wireless, which has gathered unto itself most of man's and woman's activities and served them up for us as good, bad and indifferent entertainment, should have grasped games in its maw, and particularly those which it can play itself in its studios, and which our fathers and mothers—or was it our grandfathers and grandmothers?—were so fond of playing in their own drawing-rooms and parlours. Little did they imagine that long after their bustles and dundreary whiskers were old-fashioned even at Madame Tussaud's, their descendants would gather round microphones in millions listening—not watching, even, but just listening; eavesdropping, one might almost say—to unseen teams playing modern versions of their old loved games of Consequences, Question and Answer, and many another.

“One Minute, Please”

For many years now these parlour games—notably Twenty Questions, Any Questions and various quizzes—have been favourite items in radio entertainment. And not unjustly, more especially when compared with some other alternatives we are given to choose from at round about their hours. They have now been joined by a new one, “One Minute, Please,” on Tuesdays at nine-thirty. I would like to wish it, at the outset, a prosperous career. Built on the same lines as Twenty Questions, with a “keeper of the password” instead of Norman Hackforth's voice, it gives rather more opportunity for personal initiative than its forerunner, of which Gilbert Harding and others have not been slow to take advantage. (It should suit Anona Wynn and Richard Dumbleby admirably, though I hope as many new names as possible are kept for it.) What a wealth of fun can be extracted from both trying to find, and to dodge, the password in sixty seconds of solo oratory! Gerard Hoffnung is a distinct acquisition to this type of programme. Ian Messeter, deviser and producer, and Roy Plonley, introducer, are to be congratulated.

“The Big Show”

This must have been one of the most keenly anticipated programmes ever put over the air; it must also have had one of the biggest audiences.

I thought that it was a first-class affair and, if strengthened in a couple, alas! of British, places, would be really top notch. The first, and major, reaction to it which I experienced was a consciousness of its vast superiority to the average B.B.C. “variety” programmes which are inflicted on us with such soul-destroying regularity. Admitting that it was in all probability a much more costly affair than could be afforded every Saturday night, it did serve to prove that not only is there an awful lot of dead wood—dead from the neck down and the feet up—in our native variety, but that the presentation and general arrangement of what good we have can be greatly smartened up.

Variety

“Music Hall,” alas, is back. The recent inclusion of, or prefix of the adjective “Festival” to its title did little to raise its general level of banality and raucousness. According to its first de-festivalised presentation, it will return to its unhonoured level. I did think, and was led to believe, it was to be abolished, but the wish was, presumably, father to the thought. There is, of course, always the remedy of not listening to it which, now that I have done my duty and reported on it, I shall take.

Plays

What is a masterpiece? Presumably, something which, in its own particular genre, cannot be improved upon. When they are presented to us in other than their original media, a certain lessening of their original greatness is almost inevitable.

Ibsen's “Ghosts,” a play, was presented to us in a radio version, also a play of Lance Sieveking's, and this suffered least damage. Hardy's “Tess of the d'Urbervilles,” a novel, suffered in its conversion to a play, “from the novel” by Ronald Gow rather more harm. This was probably because its original texture is more delicate and refined metal than the rugged Northern work. Both are imperishable masterpieces and received most excellent treatment at the hands of all who handled them. Aileen Mills brought out much of the adorable Tess's sweet femininity—the major portion cannot be extracted from the original Hardy prose—as did Griselda Hervey in the totally different type of woman, Mrs. Alving, of “Ghosts.” The Ibsen play made the better radio, as the particular Hardy qualities of illusiveness and imagery are not so essential, qualities difficult to produce over the air.

Music

Much good music has been wafted across to us: some magnificent Beecham programmes, an excellent series of Schumann recitals by that very fine and experienced Schumann player, Moiseiwitsch, and a bright and breezy production of the original Hammersmith Lyric “Beggar's Opera.” What a priceless treasure house of native genius this is. Whilst the wonderful things from Edinburgh would require an article all to themselves,

Beating the Electron

A NOVEL DEMONSTRATION BY MULLARD

AWAY from the main stand at the National Radio Exhibition was a baize-covered table with a golden ball lying invitingly in the middle. Over the top of the table there was a message, "Can you Beat the Electron?"

Visitors approaching the table looked at the golden ball and, after overcoming their initial shyness, made a frantic grab at it. But the electron was too quick for them. Some visitors tried to capture the golden ball by means of a stick or an umbrella, but they always failed. Directly the hand or any other object approached the golden ball it very rapidly withdrew to the bottom of a deep hole let in the table top.

The "Can you Beat the Electron?" exhibit was designed by Mullard, Ltd. Although intended as a display unit, it nevertheless illustrated in a most effective way some of the possibilities that electronic techniques have in protection systems.

To explain the basic principle of operation of the protection device employed in this demonstration, it is useful to recall the first valve radio receivers which came into use immediately after the crystal sets. With these early receivers strange howls and screeches would often come from the loudspeaker whenever the hand came near the tuning knob. This form of interference was due to the electrical capacitance set up between the hand and the sensitive tuning circuit, thus causing the reaction circuit to oscillate. In recent years this effect has been "tamed" and utilised in a number of interesting electronic devices. In the display unit referred to above, the electrical capacitance between the golden ball and earth changes when the ball is approached by any person or object. By means of an electronic circuit, this capacitance change is converted into an electric current which is used to operate a relay; and the relay, in turn, is used to set in motion the necessary mechanical protection mechanism. The whole cycle of operation is so

rapid that in the demonstration the golden ball disappeared from view at a speed faster than the hand can move.

The capacitance electronic detector, or the capacitance relay as it is sometimes called, besides finding many applications in protective systems, has



Two excited schoolboys, visiting the National Radio Exhibition, try to get the golden ball.

innumerable possibilities in other fields. The detecting element may take the form of any insulated metal object, but is usually in the form of a rod, a small ball or a plate. These detecting elements can be used to detect both large and small objects. For example, it is possible to detect cars or people at a distance several feet away from the detecting element even if a plate of glass or a dry plaster wall intervenes. On the other hand it is equally as easy to detect and count at rates of several hundred a second, such small objects as beans, buttons, etc.

The principle of capacitance change may also be used for such varied applications as measuring movements of the order of a few millionths of an inch; controlling the level of water in boilers; and measuring the thickness of materials, e.g., cigarette papers, plasters, and so on.

News from the Clubs

THE MIDLAND AMATEUR RADIO SOCIETY

Publicity Representative: B. H. T. Oliver (G3DJQ), Cleeve Lodge, Nether Whitacre, nr. Coleshill, Warwickshire.

AT the annual general meeting held on September 18th, it was fitting that, for the forthcoming year during which the Society celebrates its 21st anniversary, Mr. C. H. Young (G2AK) should be elected president. He is a founder member of MARS and has held a licence for 25 years. The Society also honoured Messrs. Butler and Rhodes by electing them as vice-presidents in appreciation of the valuable service they have rendered over many years.

WARRINGTON AND DISTRICT RADIO SOCIETY

Press Officer: Mr. Frank E. Loxham, "Fulwood," Heath Road, Penketh, nr. Warrington, Lancashire.

THE Warrington and District Radio Society has now moved headquarters to The King's Head Hotel, Winwick Street, Warrington, and will hold meetings on the first and third Tuesdays in every month. A full programme for the winter session has been compiled, including talks on two-metre transmission and reception by G. Leigh (G2FCV), "Negative Feedback," by N. Atkins (G3EXG), "The Thermionic Valve," by Messrs. Mullard, Ltd. (with film-strips), etc.

The annual dinner and social of the Society will be held at the Fir Grove Hotel, Latchford, nr. Warrington, on Friday, November 30th, 1951, and tickets may be obtained from the hon. secretary of the Society, Mr. S. Wood (G3EZ), 51, Henshall Avenue, Latchford, Warrington, and, as the tickets are limited, early application is advisable.

DUDLEY AND DISTRICT SHORT-WAVE RADIO SOCIETY

Hon. Sec.: J. Anderson, 15, Langley Avenue, Coseley, Bilston, Staffs.

THE inaugural meeting was held Tuesday, September 18th, the proceedings being conducted by Mr. G. Pennington. As a result of an election, Mr. J. Anderson and Mr. G. Doodey were chosen as secretary and treasurer respectively. Newcomers will be made particularly welcome.

LEICESTER RADIO SOCIETY

Hon. Sec.: L. Milnthorpe (G2FMO), 3, Winster Drive, Thurmanston, nr. Leicester.

THE first meeting of the winter session was held on October 1st at the clubroom, Holly Bush Hotel, Belgrave Gate, Leicester, and it was pleasing to see the room filled to capacity. The films, "Cathode-ray Oscilloscope" and "Power Lines" were shown and followed, to the amazement of the members, by a short comedy film.

Full details of membership and future activities of the Society can be obtained from the Hon. Sec. (above).

"DEMOBBED VALVES" MANUAL



2.9

POST FREE

giving equivalents of British and American Service and Cross Reference of Commercial types, with an appendix of B.V.A. Equivalents and comprehensive Price List. We have still some valves

left at PRE-BUDGET rates which actually sold at the old price. There is a space free for YOU on our mailing list.

CONDENSER TESTERS and Rectifier Units. Plugs straight into A.C. mains, 200/240 v., and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete, 3/9/6. Post 1/-.

EMISCOPIES, C.R.T. Type 4/1. 3in. brand new, only 1/7/6, post 2/6. Pen 4/6, new, 8/- only, post 1/-. PM 12m equiv. 6/- only, post 1/-. OZ4, 9/6; 1G6, 5/9; 3Q5, 1/1/6; 6AB7, 9/6; 6B8, 10/6; 6C6, 9/6; 6J7, 8/6; 6L6, 12/6; 6N7, 11/6; 6SC7, 9/9; 6SJ7, 9/9; 6SQ7, 11/6; 12SG7, 8/6; 7/6, 8/6; 954, 6/6; AC6 pen, 8/-; ATP4, 5/-; EF6, 11/6; EL50, 8/-; FC13, 10/6; MS pen, 7/6; Pen B4, 14/6; Pen 36c, 15/-; Pm 22A, 6/1-, post 1/-. Ask for Full List, 10,000 valves in stock.

TELEVISION. "The De Luxe Home Built Televisor and Radiogram" Design and Construction, 6/9 post free.

PLESSEY 3 speed mixer, auto change unit for 7, 10 and 12in. Records, £23-13-0.

SERVICE SHEETS, the one you require enclosed if available in a dozen, our choice, 10/6.

Speaker matching **TRANSFORMERS,** Ex-Gov. Surplus, guaranteed, 2/-, post 6d.

AMPLION TEST METER. 1,800 ohm per volt on all D.C. and A.C. ranges, 10 v., 100 v., and 500 v. D.C. and A.C. 50 mA. and 500 mA. D.C. Resistance up to 200,000 ohm. (3,000 ohm centre scale), with self-contained battery, 5,000 volt range with a separate H.T. test prod (9/6 extra). Supplied with test prods. Multi-colour scale easily readable, £5.

(Kindly mark envelope PW12.)

RADIO BULLS VALVES
246, HIGH ST., HARLESDEN, MID

R.1155 COMMUNICATIONS RECEIVER. We have been fortunate in obtaining a quantity of BRAND NEW UNUSED SETS, which are now becoming scarce. This famous ex-E.A.F. Bomber Command receiver covers 5 wave ranges: 18.5-7.5 mc/s, 7.5-3.0 mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s, and is easily and simply modified for normal mains use, full details being supplied. All sets aerial tested before despatch. IN MAKER'S ORIGINAL TRANSIT CASES: ONLY £11 19/6 (carriage 10/6). A factory-made power pack with output stage, which operates the R1155 immediately, can be supplied for £5.5/-.

BATTERY SUPERSEDER. Will save battery users pounds. Operates from a 2-VOLT ACCUMULATOR and delivers constant H.T. of 67 volts at 4.7 m.a., 130 volts at 13-25 m.a., and 1.4v. L.T. if required. American made, and originally intended for Weite-talkie equipment, this unit is easily adapted for use with any battery set, and fully illustrated details are supplied. ONLY 60/- (postage, etc. 2/-).

I.F. STRIP TYPE 194.—An easily modified I.F. Strip recommended for TV constructors who want good results at moderate cost, or for those who have built televisors but are having trouble in the vision or sound receivers. This 6-stage strip measures 18in. x 5in. x 5in., and contains 6 valves VR65, 1 of VR92, and 1 of VR53 or VR56. Mod. data supplied. BRAND NEW. ONLY 45/- (postage, etc. 2/6).

RECEIVER R.1355.—The unit specified for "Inexpensive Television." Complete with 8 valves VR65, and 1 each 5U, 4G, V1200, VR92, and a copy of "Inexpensive TV" which gives full constructional details. ONLY 55/- (carriage, etc. 7/6).

10-VALVE 14-METRE SUPERHET ZC8931.—For long-distance TV results. Valve line-up is 6 of VR65, 2 of VR92, and 1 each VR136 and VR137, and the 12 mc/s 6-stage I.F. Strip gives tremendous amplification with ample bandwidth of 4 mc/s. Easily modified. Full details supplied. BRAND NEW IN MAKER'S CARTONS. ONLY 59/6 (carriage 5/-).

6046/6050 AMPLIFIER.—An ideal unit for conversion into a high-gain TV pre-amplifier, full details being supplied. Complete with 2 valves EF50. ONLY 22/6 (postage, etc. 1/6).

R.F. UNIT, TYPE 24.—For use with the R.1355 Receiver for Sutton Coldfield TV (mod. data supplied), or as a pre-amplifier for Protector Television, December, 1950. ONLY 17/6 (postage 1/6).

SECTIONAL TELESCOPIC AERIAL, comprising 16 sections each 16in. in length, and colour-coded for ease of assembly. Complete in web case. BRAND NEW. ONLY 9/6 (postage 1/-).

WALKIE-TALKIE CHASSIS, TYPE 38.—A beautifully made chassis, ideal for the enthusiast, or as a source of components. As used by the Forces, with the exception of certain transmitting components removed by the Ministry of Supply. ONLY 9/6 (postage 1/6).

HEADPHONES DLR NO. 2.—Low-resistance phones fitted with solid type headband, and 6ft. lead terminating in jack plug. As used on type 19 receiver, etc. BRAND NEW. ONLY 6/6 (postage 1/-).

MURHEAD SLOW-MOTION DRIVE.—A really precision product of this famous maker's, 3in. in diameter with edge marked 0-100. Complete with cursor. BRAND NEW IN MAKER'S CARTONS. ONLY 8/6 (postage 1/-).

CONDENSERS.—Paper, metal cased.—1 mfd. 3,000 volts, 4/6; electrolytics (cans unless stated): 8 mfd. 450v., 2/6; 8 x 8 500v., 4/9; 8 x 16 450v., 5/9; 16 500v. cardboard, 6/-; 16 450v. can, 5/6; 16 x 16 500v., 7/-; 24 350v. cardboard, 4/6; 25 25v., 1/6; 32 250v., 2/9; 50 12v. can or card., 1/-; 32 x 16 50v., 1/6. Postage 1/-, please, on orders under £1. Cash with order please, and print name and address clearly. Amounts given for carriage refer to inland only.

U.E.I. CORPORATION

The Radio Corner

138 Grays Inn Rd., LONDON, W.C.1
Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Stn.) and 5 mins. by bus from King's Cross.

LONDON CENTRAL RADIO STORES

PHILCO RADIOS RECONDITIONED

LARGE TABLE MODEL in light walnut, large circular dial. Size 16in. x 16in. x 10 1/2in. Very selective. 115/-.

DE LUXE MODEL with Bronze speaker grill. Size 17in. x 14in. x 10 1/2in. 132/-.

ALL-WAVE DE LUXE TABLE MODEL. Large Circular dial. Two-speed tuning. Takes normal or dipole aerial. Size 18 1/2in. x 20in. x 9 1/2in. 174/-.

CATHEDRAL MODEL, in light or dark oak. Receives all British and European stations with great clarity. Size 19in. x 14in. x 10in. 110/-.

STANDARD TABLE MODEL. Square cabinet in light or medium oak. An absolute gift. Very few of these available. Size 18in. x 14 1/2in. x 10in. 95/-.

ALL TYPES have pick-up sockets. Supplied in A.C. or A.C./D.C. cover voltages 200-260v. Take extension speakers and are tested before despatch. Have 5 valves.

The Circuits are of high gain I.F. value which in turn drives an output valve, usually delivering about 4 watts of audio to the speaker. All sets will take one or more extension speakers.

NEW NIFE ACCUMULATORS, 2.5v. 2 amp. for 8 hrs. 4 1/2in. x 1 1/2in. Flat, 6/6. 9d. post, etc.

MAP READING TORCH. Magnifying lens, 3in. diameter, in bakelite case, with dimmer switch. Takes two U.2. batteries, 22/6, less batteries.

EVERLASTING NEW INERT CELL ACCUMULATORS. No acid or charging required; great many uses for them, 1.5 volts. Size 2in. x 2in. x 5 1/2in., 2/9 each; 3 for 7in. 1/- for postage.

UNISELECTOR SWITCHES. 3 Bank Wipe, 19/6; 4 Bank Full Wipe, 37/6; 6 Bank Wipe, 27/6.

2-VOLT VIBRATORS. Type R76C. 7-pin self-rectifying. Output 200v. at 60 M.A. Made by Electronic Laboratories, Inc., 7/6.

MALLORY, Type 650, 6-volt 4-pin. American base, 7/6.

MALLORY, Type G.629C. 12-volt 4-pin. American base, 7/6.

PHOTO ELECTRIC CELLS. Type CV143. Small infra-red image glass converter tube, 50-100v. Suitable for all purposes, 14/6.

N.B. We cannot enter into correspondence regarding these cells. Carriage charges relate to inland only.

WE WANT TO BUY RADIO EQUIPMENT — AMPLIFIERS — TAPE RECORDERS — TELEVISION TEST EQUIPMENT — COMPONENTS

LONDON CENTRAL RADIO STORES

23, LISLE STREET, W.G.2
Phone/Grams: GERrard 2969

ALPHA OFFERS.

VALVES BRAND NEW AND BOXED

Table listing various valve types and their prices, including 6F8G, 12H6, 4D1, etc.

MOULDED MICA CONDENSERS

.00027, .0001, .0002, .0003, .0005, 5/8 doz. .01, .001, .003, .002, .005, 7/- doz.

VOLUME CONTROLS

1, 1, 2 Meg. 100K. Ohms. With switch, 4/3 each. 25K, 50K, 1, 1 and 1 Meg. Double Pole Switch, 5/- each.

MAIL ORDERS ONLY. C.W.O.—C.O.D. DELIVERY BY RETURN. POSTAGE EXTRA.

ALPHA RADIO SUPPLY CO.,

5/6 Vices Chambers, Victoria Square, Leeds 1

TEST METERS (M.c.). 7 Ranges, 1.5 v., 3 v., 150v. 6 mA., 60 mA., 5,000 ohms, 25,000 ohms, 2 1/2 in. dia., case 6 1/2 in. x 4 1/2 in. less batteries, 24/6, post 1/6. TR9 RECEIVERS. Less valves, 5/6, post 2/6. 6/5G, Brand New. Boxed 5/-, Unboxed 3/6. RL155 COMMUNICATION RECEIVERS. Complete with Valves, Tested and Guaranteed. 28 10s. Carriage 10/-.

STAN WILLETTS, 43, Spon Lane, West Bromwich, Staffs.

RADIO G200 ANNOUNCES

VALVES.—VR78, VR92, 2/6. CV66, 2X2, 12SH7, 6SH7, 6H6, 12H6, HVR2a, TT11, Pen220a, VY2, 6AC7, 6L7, 5/-, 6N7gt, 6N7g, 6SQ7, 6J7g, AC67P, Pen46, 6AC7, 6J5, 6D6, 1625, 6K6, ELS, 12SG7, 3B7/1291, 6J7, 6K7, 6K7G, 6K7GT, VR103, KTW61, KTW62, 6V6gt, KTW63, 1C5gt, 6C4, 12SR7, 6/9, 8012, 6Q7Z, DH63, 10/5.

Type 6 and 6A units complete with VCR97 and all valves as new. Price 59/6, plus 5/- carriage.

ARTHUR HOILE 55, Union Street, Maidstone, Kent Phone 2812.

WALTON'S OF WOLVERHAMPTON

VALVES! VALVES! VALVES!

We are clearing very large stocks of slightly soiled valves at very special prices. Send S.A.E. to-day for full list. Here are a few examples.

All at 5/-.—EF36, EF39, EL32, EK32, KT44, VU120A, 12SH7, 12SJ7, 12J5, 6J5G, 6J5GT, 6SH7, 6K7G, 6SK7GT, 6SL7GT, 6BR8, 1A5G, 1G6G, 3D6, 1LD5, 1LN5, 7C5, 7B6, 7C7, PM2, KT2, 215SG.

All at 7/6.—5U4G, 807, 1625, 2A3, 6A3, 6SF5, 6N7; and many others.

Hurry—send your order to-day, to-morrow may be too late.

WALTON'S WIRELESS STORES, 48, STAFFORD STREET, WOLVERHAMPTON

Quixo Radio Cell Tester advertisement with image of a tester and 'RUNBAKEN MANCHESTER' logo.

SPECIAL OFFER

OF NEW AND GUARANTEED VALVES 1L4, 3Q4, 3A4, 7/6 each, or one of each type for 1/6, post free. The 1L4 and 3Q4 are similar to 1T4 and 3S4 respectively, but are actually superior in that they have a higher mutual conductance, and have a maximum screen voltage of 90 instead of 67 1/2; base connections of 1L4 are identical to 1T4, and those of 3Q4 are identical to 3S4. The 3A4 will give an output of up to almost three times that of either the 3S4 or 3Q4. Also a few 6J6, 20/-; EY51, ECL80, EBL21, ECH42, UBL21, UCH21, X145, 18/6; EF80, 17/6; EBL91, X78, 6/4; UAF32, UP41, UL41, 15/-; W77, DH7, N87, UBC41, 10/2 1/2; 6AK5, 10F3, 10FD11, 10P13, 12/6; EFL1, UY21, UY40, 11/6; 1R5, 174, 155, 3S4, EF22, EB91, 10/-; 6AG5, 6AJ5, 8/6; 6C4, 7/6; 9092, 6/-.

ELECTRAD RADIO 69 HIGH ST., BELFAST, N.I.

TR 1196 RECEIVERS advertisement with details on conversion data and contact information for Bold & Burrows.

NORMAN H. FIELD

68, HURST ST., BIRMINGHAM 5 MAIL ORDER DEPT. 64-65 Church Lane, Wolverhampton

At 10/-: 6K3, 6K8C, 1622, 12SG7, 1610, PEN46, 12SL7, 6KR8T; At 9/-: 6F7, 6L6G, 807, 5Z4, ARP6, At 8/6: VU39A, At 7/8: 7R7, 7/7, 6X5/GT, 1L48/GT, 6K7, 6J7, VL150, 6C5/GT, 6F8, 6C6/GT, 1A5/GT, 7C7, VR119, 6Y7/G, 1E7G, 7C6, 5U4G, ARP22, TP25, 6Z4, 3Q5/GT, 8V6/GT; At 7/-: 6B8, 6BR8G, 1G6/GT, 6K7G, MH4, VR53, EF39, VR55, EBC38; At 6/6: 6AB7, 6D6, VT22A, RK34, 2C34, 1625; At 5/6: 6S5T, 6N7, 6N7/GT, 6R7, 6R7/GT, 12C8, 12A6/GT, 12SG7, 6SA7, 6C5/GT, 6L7, 12J5, 6J7, 6K6, 6SH7/G, VR81, RF50, 3D6, 6SK7, 6C5/G; At 5/-: 6ACT, 6J5, 12SK7, 6SK7GT, 2A3, VU133, 2V3G, AR8, HL23DD, ARP12, VP23; At 4/6: 6J5/G, 6J5/GT, 12SH7, 6SH7GT, 12H6, 9D2, VL20, ARP1, 215SG, A, 4, 5, 6H6; At 3/6: BR872, VR58, EF39; At 3/3: 2X2, VU11, HL2, VR21, VR56, P61; At 2/6: VR65, SP61, VR65A, VR54, SP41, EB34; At 1/9: 7193.

1155 D.F. LOOP AERIALS 8/6 CRYSTALS, 500 Kcs. 7/-

ROTARY CONVERTERS. Approx. 6v. input D.C. to 220 volts D.C. 80ma ideal for portable rigs, and Car Radio. As New. 12/6 THREE IN ONE TRANSFORMERS. 6/- Postage 1/5.

- 1. Use as P/P Modulation Transformer PIP 21's to single 211-100 watts. Makes Ideal Output Transformer P/P 6L6 or 807 to match High Impedance Relay Speakers, and as,
2. 230 v. 50 cycles Input 150-0-150 at 100 ma. Output. Useful for H.T. Elimination and Low Voltage Power Supply. Can also be used 300 v. Half Wave at Lower Current, and as,
3. 230-115 v. AUTO Step/Up or Step/Down Mains Transformer 75 watts rating. U.S.A. Manf. Fully Shrouded. Please Add Something for Postage.

VALVE BARGAINS

Table with 5 columns of valve types and prices: 6K8, 6K7, 6B8, 6V6, 5Y3, 6C5, 6F6, 7/6, 9/6, 1R5, 174, 155, 1S4, 3V4, 9/6, 9/6, 9/6, 10/6

All new, boxed and guaranteed. U14 9/0 35L6 10/6 MU14 9/0 6SN7 12/6 6J7 9/6 12K8 11/6 VR91 8/6 6AM6 11/6 6H6 4/6 2K7 10/6 5U4 10/6 EC91 10/6 6C5 7/6 2A6 10/6 U19 10/6 A791 9/0 and hundreds of others. Lists 2/6.

CLEARANCE OFFER. Soiled VR91, tested O.K., 4/6 ea.; 5 for 1/1 post free. V. Con. 1, 1 meg. w. sw. 4/-; Conds. 8/450, 2/0; 16450, 3/4; 8-16450, 5/-; 25/25, 1/9; .0001, .001, mica, 5/6 doz. Trans. 6V, 14 a., 12, 16, 50 0350 v. 5 v. and 6 v. 10/6. Speakers 1/4trns. 3in. 11/6; 5in., 13/6, etc. O-p.ut Trans. 4/9; midget. 3/9. Coax. cable, 80 ohms, 1/- yd. Moore solder, 3/6 reel. OCT. V.H.PAX., 4/6 doz. Post 6d. 1/1 FREE.

T.R.S 71 Meadvale Rd., E. Croydon Callers. 307, Whitehorse Rd., W. Croydon. THO 1665.

VALVES!

A—Original cartons. B—Used and Boxed. Type A B Type A B Type A B. 2X2 4/0 4/3 6Q7GT 13/1 11/6 EC58 — 5/- 6B4 7 6/- 6R7 10/- — BL32 — 8/- 6C4 7/6 7/7 6K7GT — 6/9 HL23DD 12/6 6F8G 9/6 — 8V6GT 12/8 10/- KT66 — 9/6 6J5 6/9 — 6B34 — 7/6 KT263 — 8/6 6J5GT 6/6 — 12H6 — 2/9 KT263 — 3/2 6J7G — 6/6 807 — 9/6 Pen383 9/6 8/6 6K6GT 8/6 — 954 3/6 — TH228 — 12/6 6R7 7/9 6/9 7193 3/6 — VL128 — 9/- 6N7G 7/8 — EA50 — 3/8 VL128 10/6 — 6C7G 6/9 — EB34 — 2/8 VT11 9/6 — SP41 ex-equipment, soiled, but tested, 2/6.

ELECTROLYTICS!

20 mfd. 50 v., 1/3. 8-16 mfd. 350 v., 3/3 25 mfd. 25 v., 1/9. 22-16 mfd. 350 v., 5/8 30 mfd. 100 v., 9d. 22-32 mfd., 350 v., 5/9 100 mfd. 50 v., 1/9. 22-32 mfd., 450 v., 7/- 8 mfd. 40 v., 2/8. 16-16 mfd. 600 v., 4/9. "ELAC" 5in. P.M. LOUDSPEAKERS. Makers' cartons, a quality job only 14/9 (post 1/-). Send S.A.E. for current list. Orders over 1/1 post free. Otherwise please add 6d. MAIL ORDER ONLY.

REED & FORD, 2A, Burrely Road, Ainsdale, Southport.



The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

High Fidelity

SIR,—I refer to the letter on the quest for high fidelity written by G. Harding, of Wembley, in the October issue of PRACTICAL WIRELESS.

When the question of high fidelity arises, it is strange how often another very important point is forgotten.

I built an outfit which was supposed to give wonderful results and was complete with twin speakers and a cross-over system. I was assured by the manufacturers that my 12in. speaker could give response up to 8,000 cycles, and that above that figure would be the responsibility of the little speaker.

It occurred to me that I might be able to demonstrate to my friends the improvement made by a cross-over system and twin speakers, and with this in mind I fitted a switch which made the outfit work on the 12in. speaker alone or could switch in the twin arrangement.

When everything was in working order, it was noticeable that little difference could be detected. Some adults said there was a slight improvement but not much, and only a small boy declared that it was a distinct improvement with the twin arrangement.

Some time later I read a book describing the functioning of the human ear. There I read that only young people could hear the squeak of a bat as it flew, because the average adult ear could hear only up to 10,000 cycles.

That being so, it is quite pointless to involve oneself in the expense of attempts to reproduce sound up to 15,000 or even 20,000 cycles when the average adult ear can hear only up to 10,000.

It is equally obvious that the average adult will believe that an instrument is reproducing faithfully if it can handle sounds within the range of his ear.

The "hi-fi" instruments are undoubtedly masterly instruments, but as useful as an infra-red lamp to augment a motor car's headlamps would be to the unaided human eye.—ERNEST D. PURDY (Glasgow).

SIR,—Mr. Harding's letter in the October issue is a very inviting one and he may be interested in the views of a professional musician who is very interested in high quality professionally and from the technical side as well.

The £200 speakers are just fads of a few people who will never be satisfied with anything. I have several friends possessing such units and I judge my results on what they think as much as anything.

In most cases the host insists you stand on a certain square foot in his room with the head at an awkward angle.


But all that is what you could call ultra high quality. There is a high quality of reproduction, very useful and not particularly expensive to attain.

The standard set by commercial manufacturers is appallingly low with their single pentodes, small iron content output transformers and speakers with minute magnets. But if you extract each one of their weaknesses and reinforce it reasonably the results, in my opinion, will justify the extra expense. The effect of replacing any one item at a time gives results any layman will applaud. Replace them all and the result is justifiably called high quality, but not by any means original quality.

Far too much money goes into the tuning side of the ordinary set to allow any quality in the L.F. side for ordinary regional listening. Redistribute the expense to cover quality and you are hardly out of pocket except for the speaker. My own set-up is a standard triode push-pull amplifier with some 10 db negative feedback, a medium quality transformer and speaker and a large baffle, the results from which have pleased many distinguished musicians.—D. BRAIN (1st French Horn BBC Welsh Orchestra, Soloist L.S.O.), (Swansea).

Tone Controls

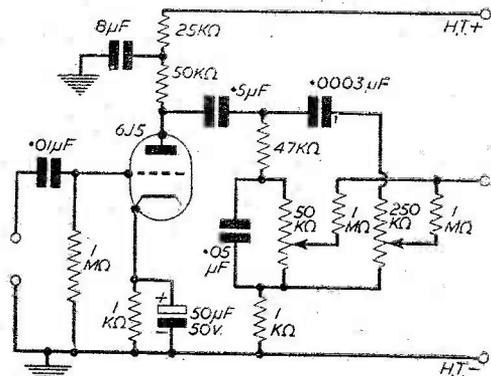SIR,—I very much enjoyed reading W. J. Delaney's article on tone controls, and although most of it is really useful, the circuits Fig. 5 and 6 are much too elaborate for the results obtained.



Tone control circuit suggested by Mr. A. Waterworth.

Now here is a tone control circuit which I would like you to publish, which I have been using for the past ten years with good results.—A. WATERWORTH (Burnley).

P.D. or E.M.F.

SIR,—Concerning the notes on potential difference and electro-motive force in the series "On Your Wavelength"; when a voltmeter is connected across the terminals of, say, a Daniell cell which forms part of a complete circuit whose other components are a rheostat, for varying the current, and an ammeter, all in series, it is found that the potential difference of the cell, which is the quantity measured by the voltmeter, decreases with increasing current. In other words, the potential difference is not a constant.

However, the electro-motive force in question is an invariable quantity, and is equal to the value of the potential difference when no current is flowing. A purist would assert that it is not possible to obtain a value of electro-motive force by means of a voltmeter, for, strictly speaking, any voltmeter takes some current.

I concede that for practical purposes the two terms can be—and in many text-books are—taken as synonymous, but that does not alter one iota the fact that there is a basic difference.—GEOFFREY PENNINGTON (Birmingham).

Battery Receivers

SIR,—Judging from what I saw at the National Radio Exhibition this year, the manufacturers seem to be under the impression that 95 per cent. of the listening public are connected to mains electricity supplies.

Most makers included a so-called A.B.C. portable in their range, but even so, who can undertake any serious listening on such devices as these, not to mention frequent and costly replacement of larger type H.T. batteries?

My own opinion is that it would pay some manufacturer to woo the 30 per cent. or so battery set users by producing something on the lines of the Ekco "Connoisseur," using perhaps lower consumption valves driven by a vibrator power supply. They might even consider supplying a small wind-driven generator to keep the battery trickle-charged!

Failing to arouse the interest of the radio industry, it may be that PRACTICAL WIRELESS might consider publishing details of an installation on the lines mentioned.—A. C. HEATH (Aldermaston).

Alternative I.F. Couplings

SIR,—With reference to Mr. D. Grant's letter in your October issue, whilst sympathising with him regarding his inability to obtain quality from a superhet or selectivity from a "hi-fi" T.R.F., may I point out that a method of reception superior to either is available?

I refer to the "Synchrodyne" invented by Dr. Tucker. This combines extreme selectivity with infinite-range quality. Should your correspondent not be familiar with this type of receiver, I will be pleased to let him have details.

Concerning Mr. G. Harding's letter re high fidelity,

whilst agreeing that much of the BBC's transmitted material is of execrable quality, it must be admitted that quite a number of programmes are of first-class quality, and for these alone it is well worth while acquiring the finest quality equipment one can afford. This does not necessitate paying £200 for a loudspeaker. One of the world's finest costs £10.—HAROLD STRIPE (Surrey).

T.R.F. versus Superhet

SIR,—I note Mr. Grant's comments in the October issue, but a point which I think is often overlooked is that a T.R.F. is the amateur's receiver and the superhet is the manufacturer's receiver. How many amateurs can line-up a superhet properly? Even assuming the I.F.'s are peaked by the makers, how can you adjust padders, etc., to ensure that the oscillator gives, at the minimum, three-point tracking—unless you have a signal generator? And how many amateurs have a signal generator? On the question of quality, the T.R.F. scores every time and more than one manufacturer has, on the market to-day, a tuner for use with high-quality amplifiers, in which a switch is provided so that when the "local" is received the circuit is changed-over from a superhet to a T.R.F.—H. WATTS (N.W.9).

Half-wave Rectification

SIR,—Half-wave rectification for H.T. is now much used. Even with voltages of only 200 volts or so (output), the use of a transformer is good, for reasons constructors will appreciate. But no manufacturer seems to make a transformer for such use: they all make tapped secondary transformers for full-wave rectification. One can of course use a tapped-secondary model, and waste half the secondary winding, but a simpler transformer for half-wave rectification would save space and would presumably be somewhat cheaper.—MALCOLM MACKENZIE (W.2).

A.C. Pre-set Two

SIR,—With reference to the theoretical circuit of this receiver in the November issue I note that a figure has been wrongly placed in the switch connections below the circuit. On the right-hand switch section, to which the 250 pF condenser is connected, the figure 3 against the right-hand contact point should be transferred to the centre of these three contacts.—ERIC LARNACH (Leeds).

Ex-Service Equipment

SIR,—Mr. Bradley has, apparently, discovered something which I suspected for a long time. I had, in fact, spoken to several friends about this matter and as it happened one of these had served during the war and for shortly after in the R.A.F., and he confirms that equipment is often marked for examination by coloured labels and in some cases by dabs of coloured paint, but otherwise there is nothing to distinguish them from serviceable or usable equipment. In fact, he confirms that it is even possible for equipment to be delivered by a manufacturer to a service equipment centre and to be disposed of before it has even been checked—although the factory may have checked it.—G. DAWSON (N.16).

L.R.S. CASH or EASY TERMS

Immediate Delivery Limited Stock

ARMSTRONG

ALL-WAVE CHASSIS

Model EXP 73. Cash £25/12/4, or £7/15/0 with order and 10 monthly instalments of 40/-.
Model RF 103. Cash £28/16/0, or £8/15/0 with order and 11 monthly instalments of 40/-.
Model RF 104. Cash £34/12/10, or £11/10/0 with order and 13 monthly instalments of 40/-.
Passenger carriage 10/- extra, payable with deposit.

GOODMAN'S LOUDSPEAKERS
Axiom 150. Cash £10/5/6, or £3 with order and 9 monthly instalments of 30/-.
Audium 60. Cash £2/12/6, or £2/5/0 with order and 7 mthly. instal. of 20/-.

W. B. CONCENTRIC DUPLEX LOUDSPEAKERS

The unit for the Connoisseur. Each unit constitutes two separate loudspeakers, concentrically mounted and having its own speech-coil, gap and diaphragm. Should not be confused with the twin-cone type.
10in. Model. Cash £7/7/0, or £2/0/0 with order and 6 monthly instalments of 20/-.
12in. Model. Cash £18/18/0, or £5/5/0 with order and 8 monthly instalments of 40/-.
Both the above complete with transformer and Cross-over Network.

The NEW REMINGTON CONTOUR 6 ELECTRIC SHAVER is now in stock. 50/- deposit (returnable) for TEN DAX'S FREE TRIAL. Illustrated leaflets on all the above available on request.

THE LONDON RADIO SUPPLY COMPANY
BALCOMBE, SUSSEX
Est. 1925

Best Buy at Britain's

COMMUNICATIONS RECEIVER TYPE R.1155. In Brand New condition and in perfect working order, £11.19.6, plus 10/6 carriage and packing in transit box. To those not familiar with the set full technical details can be supplied for 1/3, post paid.

R.1155, POWER PACK AND OUTPUT STAGE. Assembled in a neat black case size 8 1/2 in. x 6 in. x 4 in., enables the receiver to be operated direct from A.C. mains. Price £3.19.6, carriage paid.
'SCOPE BARGAIN. Erskine Lab. Ltd. Oscilloscope Type 1/B. Ready for use on 200/220 volts A.C. mains, complete with valves and C.R.T. in black metal case with carrying handle. Brand new and boxed with circuit. Special Bargain price Only £10.10.0, plus 5/- carriage.
SYLVANIA RED EF50's (VR91). Brand new at 8/6 each. British types (tested) 5/- each.

BLOCK CONDENSERS. 10 mfd. 1,000 v. test. 3 for 10/6 post paid.
U.H.F. ANTENNA. 22.5 cms. Brand new and boxed. 5/- each post paid.
B.I. ELECTROLYTIC BLOCK CONDENSERS. 8 mfd. 500 v. working. Three for 9/- post paid.
MULTIPLE BLOCK CONDENSERS. 8 x 16 x 4 x 4 x 6 mfd. all for 45/0 worth working. Price 4/9, plus 9d. post, or two for 10/- post paid.



CHARLES BRITAIN (RADIO) LTD.

11, Upper Saint Martin's Lane, London, W.C.2. TEM 0545
Shop hours, 9-6 p.m. (9-1 p.m. Thursday)

— OPEN ALL DAY SATURDAY —

— YOU READ MUSIC? —

Then how about making yourself an electronic organ. Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.
Write NOW for free booklet and further details to C. & S. 10a, Duke Street, Darlington, Durham.

SUPACOILS

If you wish to build radio receivers or equipment for profit or pleasure you MUST get our latest **Constructor's Handbook**, full of circuits and radio information for the constructor. Price 2/- only, or forwarded FREE with orders of 20/- or more.

- ★ **COILS.**—A complete range of High Q variable iron-dust cored coils in wave-lengths 10-30, 16-50, 30-75, 75-200, 190-350 and 800-2,000 metres: Aerial H.F. Oscillator. —As recommended for the Practical Wireless 9 valve All-wave Superhet and P. W. Car Radio, 3/- each.
- ★ **COIL KITS.**—For building your own Superhet Coil Packs. From 18/-.
- ★ **T.R.F. COILS.**—Air-cored L. & M. wave on one former—Aerial and H.F. 3/- pair.
- ★ **T.R.F. COILS.**—Iron-cored—M. wave only. Litz wound grid coils, Aerial and H.F. 7/- pair.
- ★ **I.F. TRANSFORMERS.**—Our popular variable iron-dust cored I.F. Transformers are still only 16/6 pair, ready aligned to 465 kc/s.
- ★ **DIALS.**—Extensive range always in stock, including the J.B. Spin Wheel Tuning Assembly at 27/6.
- ★ **COMPONENTS.**—Highest quality—lowest prices.

Stamp for complete catalogue.
SUPACOILS MAIL ORDER OFFICE,
98, Greenwich Avenue, London, E.17

OUTSTANDING OFFERS

Control Unit.—Ex R.A.F. type 88a, Ref. 10L137. Brand New. Mahogany case with sloping Grey Enamel Panel, size 12in. x 7in. Red and Green Calling lights. RTWT Switch. Send/receive switch. Sidetone Control. 1 mike, 2 telephone and 1 key jack sockets. Interior chassis size L. 11in. W. 8in. D. 1 1/2in. Components include VT20 (220P) valve, 3 L.F. transformers. Various first grade resistors and condensers. Outlet cable of 10-way 3in. screened lead (detachable) terminating in 10-way Jones Plug. 2 additional outlets terminating 1 with miniature 2-pin socket and 1 with standard jack plug. Overall size of case, Base 12in. x 5in., Top, 12in. x 4in. Height, 7 1/2in. A magnificent control unit for your Amateur Radio Station. The price is only 25/-, carr. paid.

G.E.C. Ex Govt. Transmitter Receiver. MR Series. 10 valves comprising one DET19, one L63, one H63, one D63, three KTW63, one KT63, 2 EF50. Grey Enamel case, size 10 1/2 x 8in. x 7in., weight 22 lbs. The whole in brand new condition. Valves Guaranteed. (Value of valves exceeds £10 at to-days prices.) We regret we have no circuit data of this set and are offered for value value only. Outstanding bargain at £3 19s. 6d., plus 5/- packing and carriage. Satisfaction Guaranteed.

H.P. RADIO SERVICES, LTD.,
55, COUNTY ROAD,
LIVERPOOL 4.

Tel.: Aintree 1445. Estb. 1935

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.P.
SHEPHERDS BUSH, LONDON, W.12
Telephone: SHEpherds Bush 1729

RECTIFIER UNITS TYPE 45 or 141. Incorporating a metal rectifier, this unit was designed to supply the H.T. voltage for the transmitter T1154. Input is 200/250v. A.C. mains 50 cps. Output is 1,200v. smooth D.C. at 200 mA. The whole is housed in a metal ventilated case, approx. 16in. high x 18in. x 8in., and weighs about 100lbs. PRICE £8-19-6, carriage 15/-.

ACCUMULATORS 2/12 VOLTS.—Assembled in a metal case 8 1/2 x 8 1/2 x 6in., with carrying handle that folds flat when not in use. Rated at 12v. 14 amp.-hours. Connections from each cell terminate to a threaded stem so that it is quite easy to rearrange connections to supply, say, 2v. or 6v. with, of course, a proportionate increase in amp.-hour capacity. In unused condition but outside of cases may be a little store-soiled. PRICE 26/-, carriage 4/-.

P10 TYPE EQUIPMENT RACKS. Standard 19in. centres. Height 5ft. 3in. Strongly made from 3/16in. angle iron. PRICE 30/-, carriage 5/-.

INDICATOR UNITS TYPE 6.—Contain C.R. tube VCR97, 4 VR91s, 3 VR54s, etc. An admirable unit to convert to an Oscilloscope, full data for this purpose being supplied with each unit. (Data separately 1/6 inc. post.) Also specified for several T.V. designs. Condition is as new supplied in maker's transit case. PRICE 85/-, carriage 7/6.

POWER PACK/OUTPUT STAGE.—A unit to operate the R.1155 Receiver direct from A.C. mains 200/250v. 50cps. and to provide for a speaker output. Assembled in an enclosed ventilated metal case approx. 10 x 7 x 6in. Employs 5Z4 rectifier and 6V6 output valves. Fitted with all leads and plugs, clearly marked for immediate connection without any alterations to Receiver. PRICE £5-7-6, carriage 3/-.

ALPHA OFFERS

- SPEAKERS.** All 2 to 3 Ohms.
 - 3 1/2" ELAC .. 12/6 3" PLESSEY .. 12/9
 - 5" GOODMANS .. 13/6 8" PLESSEY .. 13/6
 - 5 1/2" TRUVOX .. 13/6 10" PLESSEY .. 30/9
 - 10" ROLA .. 32/6 10" GOODMANS .. 32/6
 - 12" TRUVOX .. 65/- 8" M.E. 600 ohms .. 15/9
- METAL RECTIFIERS**
 - 12 v. 5 amp. .. 1/- each 2 volt 1 amp. 5/- each
 - 300 v. 80 mA. 5/9 .. 280 volt 60 mA. 5/3
 - Double 200 volt 30 mA each section mounted on bracket .. 4/- pair
- VALVE HOLDERS**
 - Paxolin International Octal, British 5 and 7 pin. All at .. 5/- doz.
 - Amphenol International Octal .. 7/-
- MAINS TRANSFORMERS**
 - 3-way Mounting Type, Primary 200-220-240 v. Secondaries, 350-0-350 v., 80 mA, 0-4 v. 5a; 0-6 v. 3 v. 4a; 0-4-5 v., 2a. 16/- each
 - N.R. Type Sub-chassis Mounting, 350-0-350 v. 80 mA. 5 v. 6.3 v. .. 18/6
 - Chassis Mounting Type, 350-0-350 v., 120 mA. 5 v. and 2 6.3 v., Secondaries Wax Dipped built to Government Standards 25/6
 - Quallrad, Fully Shrouded, Two-way Mounting, Primary 210-250-250 v. Secondaries, 250-0-250-0 mA, 6.3 v. 2 6.3 v. 2.5 .. 18/6
 - N.R. Type Sub-chassis Mounting 350-0-350 80 mA 4 v. 4 amp. 4 v. 2 amp. .. 18/6
- FILAMENT TRANSFORMERS**
 - Rely Two-hole Fixing, Primary 210-240 v., Secondary 6.3 v., 1.5 a. .. 8/6
 - Rely Type, as above, Secondary 4.3 v., 3 a., 10/6
 - Ellison Fully Shrouded, Primary 200-220-240, Secondary 0-4 v.-6.3 v., 4 a. .. 17/6
- WIRE WOUND VOLUME CONTROLS**
 - 5 ohms, 200 ohms, 500 ohms, 1 K ohms, 10 K ohms, 20 K ohms, 25 K ohms, 50 K ohms. .. 2/9
 - Midget type, 6 ohms, 400 ohms. .. 2/-
- IGRANIC JACK SOCKETS**
 - Heavy Duty Cooker Switch 30 amp. 4 positions .. 4/-
 - Bias Condensers, 25 mfd. 25 v. .. 1/3 each
 - BIG Ceramic Valveholders and Screw Retainer .. 10d.
 - Fully Shrouded Output Transformer, 2 ratios .. 1/9

See on other advert. Post orders only. C.W.O. or C.O.D. Please include postage, 3d. in stamps for list.
ALPHA RADIO SUPPLY CO., 5/6 Vines Chambers, Victoria Square, Leeds, 1

**A further selection of
ELECTRADIX
BARGAINS**

HYDRAULIC PUMPS. High pressure, for Bakelite shaft, etc., 2in. inlet and outlet spline shaft 2in. long, flange mounting, weight 5lbs., 45/-, packing and postage 2/-.

ROTARY CONVERTERS. D.C.I.A.C., 24 volts/230 volts, 100 watts, 75/-, carr. 5/-; 110/230 volts, 200 watts, £10.10.0, carr. 10/-; 230/230 volts, 200 watts, £12.10.0, carr. 10/-.

Starters for larger sizes 25/- extra. Send for leaflet.
THE DEM CONTINUITY TESTER in wood box, 6 1/2in. x 3 1/2in. x 2 1/2in., new, totally enclosed, with carrying strap and contact switch. A portable testing set for all electrical circuits. 7/6, post 1/-.

LIGHTING PLANTS. D. C. Briggs and Stratton, as new, 350 watts, 12/15 volts with Switchboard and Tank, tested and ready for use, £25. 550 watt Lyon Norman, with Switchboard and Tank, £30. 500 watt water cooled Pelaphone, 50/70 volts 10 amps., £45. Larger sizes available. Send for list.

MORSE KEYS. A.M. type, precision balance on bakelite base, 2/6, post 9d. Morse Practice Set, comprising A.M. Key twin coil buzzer, wired with space for battery, 7/6, post 9d. Practice Buzzer, adjustable note in metal case, 2/6, post 6d. Tiny Townsend Wavemeter type, plat. contacts high note, adjustable, 5/-, post 6d. G.P.O. twin coil open type, 2/6, post 6d.

Please include postage for mail orders.

ELECTRADIX RADIOS
214, Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

RADIOELECTRON
22, Frances Street,
Scunthorpe, Lincs.
NEW GOODS ONLY

CONDENSERS.—450 v.w. 1 mfd. 2/9; 2.3/3; 4.3/2; 8.3/4; 16.4/6; 8.3.6.8; 8.16.7/6; 16.16.10/6; 500 v.w. 8 mfd. 4/-; 16.6/9; 8.3.7/-; 8.16.8/6; 25 x 25 v. 2.3/3; 25 x 50 v. 2/3; 50 x 12 v. 2/3; 50 x 30 v. 3/6; Tubulars, 500 v.w. up to .01, 10d.; .02, 6d.; 11d.; .05, 1. 1/1; .25, 1/9; .5, 2/10; Moulded Mica, up to .0003, 10d.; to .01, 1/6; Sil. Mica, up to 80 pf., 9d.; to 8 k. pf., 1/-.

VOLUME CONTROLS.—Lge. 6sds., all values, 3/6; with SW, 5/3; D.P. SW, 6/-; Semi. Midg. Type, 4. 1. 2, med. 5/-; with SW, 7/-; D.P. SW, 8/-; Wire Wound, less SW, 1 K to 80 K, 6/6; 100 K, 7/8.

RESISTORS.—All Values, 1 w., 5d.; 1 w., 7d.; 1 w., 9d.; 2 w., 1/2; Wire wound, 5 w. up to 2 K, 2/-; 3 K, to 50 K, 2/6; 10 w. up to 12 K, 2/9; 20 w. up to 12 K, 4/-; Mains droppers, 2 adj. taps, 2 a., or 3 a., 2/6 yd. Linecord, 3 way, 2 a., or 3 a., 2/6 yd.

TERMS.—Orders up to 10/- post 6d., up to 21 6d. Over post free. List. 4d. Cash with Order. Please PRINT your name and address on all correspondence.

RADIO UNLIMITED

ELM ROAD, LONDON, E.17 Phone KEY 4813

Brand new goods—Return of post.

Condensers.—450v. w. 4 fmd. 2/-, 8 2/6, 16 3/-, 8 x 16 4/6, 16 x 16 5/6, 32 x 32 7/6, 500v. w.: 8 3/6, 16 4/6, 25 x 25v. 1.6, 50 x 50v. 2.3, 1.35v. 9d., 1.500v. 1/-, All Pils. 9d.

VOLUME CONTROLS.—Long Pin. diam. spin. All values, 3/-, SP/switch 4.6. "Amplion" guaranteed semi-midgert type. All values, 4/-, SP/sw 6/9, DP/sw 6/6.

VALVES.—13-000 actually in stock. 6X7, 6K8, EF39, EK32, EF36, 6N7, SP81, 6B8, 6SK7, 12SK7, 12A6, 12J5, EF8, 6/6 each. EL32, 6/7, KT6W1, 6/6; 7/6 each. 607, 5Y3, 6V6, 5Z4, EF91, EB91, 1L5, 1S5, 3S4, 1T4, 6SN7, 6SL7, 5U4, 6L6, 10/- each.

SPEAKERS.—Special "One Month" Offer. 3in. 5 Ohms 11/-, 3 1/2in. 11/6, 5in. 11/6, 8in. 14/6, 10in. 28/-, All new, guaranteed.

MANUALS.—Audio handbook, "Amplifiers," 3/9.



Amongst Webb's many activities we have a varied stock of TECHNICAL BOOKS

We list here a few of the titles in stock.

VALVE MANUALS — OSRAM 5/-, EDISWAN 2/-, MULLARD 5/-, BRIMAR 4/-.

Radio Valve Data (Wireless World) 3/6.

TELEVISION — "Electronic Engineering" Home Built Televisor—London 2/6; Birmingham 4/6; De Luxe 6/6.

Television Circuits (Haynes Radio), 2/6.

HIGH FIDELITY—Sound Reproduction (G. A. Briggs), 2nd Edition 10/6—246 pp. on Loudspeakers, L.S. Cabinets, Recording and Reproduction in general.

Pianos, Pianists and Sonics (G. A. Briggs), 10/6. 192 pp. on Sound and Sound Reproduction.

High Quality Audio Amplifiers (Wireless World), 2/6. Five popular circuits.

Amplifiers (N. H. Crowhurst), 3/6. 64 pp. on design and trouble-shooting—a very useful book.

SERVICING—Testing Radio Sets (J. H. Reynner), 22/6. 215 pp. of practical and theoretical tests.

Wireless Servicing Manual (W. T. Cocking), 12/6. 296 pp. The Radio Serviceman's Guide.

Radio Servicing Equipment (E. J. G. Lewis), 25/-, 371 pp. Excellent training for examinations.

GENERAL—Foundations of Wireless (M. G. Scroggie), 7/6. 358 pp. One of the best for the practical beginner.

Radio Circuits (W. E. Miller), 5/-, An excellent beginner's circuitry explanation.

Classified Receiver Diagrams (E. M. Squire), 10/6. 164 pp. A very useful reference book.

The Oscillograph and its Applications (Phillips), 5/-, 49 large pp. Practical applications.

The Gas-filled Triode (G. Windred), 2/6. Specialised applications.

Wireless World Guide to Broadcasting Stations, 2/-, Call sign metres and frequencies.

Television Interference (R.S.G.B.), 2/-, How to cut out TX trouble.

"Amateur Radio" Receivers, 3/6. Practical construction of S.W. receivers.

R.S.G.B. Amateur Call Book, 3/6. "Electronic Engineering" F.M. Receiver, 4/6.

Op-Aid (A.S.W.P.), 1/6. Operating help for listener and transmitter.

The Radio and Telecommunications Engineers' Design Manual (Blakey), 15/-, 142 pp. Advanced theoretical.

Radio Engineering (Vol. 1) (E. K. Sandeman), 45/-, 775 pp. Combined textbook for beginners and reference book for engineers.

Photo Cells in Industry (W. Summer), 3/-, 97 pp. Specialised information.

The Electron Microscope (D. Gabor), 4/6, 106 pp. Practical expositions.

Plastics in the Radio Industry, 2/6, 56 pp.

RADIO SUPPLY CO.

15, Wellington Street, Leeds, 1

BRAND NEW GUARANTEED GOODS

TERMS.—C.W.O. or C.O.D. over £1. Postage 1/3 extra on orders under £3.

R.S.C. MAINS TRANSFORMERS Fully interleaved and impregnated. Primaries 200-250 v. 50 c/s. Screened.

HALF SHROUDED DROP THROUGH 250-0-250 v. 70 m.a., 6.3 v. 2 a., 5 v. 2 a. 12/11
350-0-350 v. 70 m.a., 6.3 v. 2 a., 5 v. 2 a. 14/11
350-0-350 v. 90 m.a., 6.3 v. 3 a., 5 v. 2 a. 19/9
350-0-350 v. 100 m.a., 6.3 v. 4 v. 3 a., 21/9
350-0-350 v. 150 m.a., 6.3 v. 4 a., 5 v. 3 a., 27/11

FULLY SHROUDED UPRIGHT 250-0-250 v. 60 m.a., 6.3 v. 2 a., 5 v. 2 a., Midgert type 21-3-3in. 16/11
350-0-350 v. 70 m.a., 6.3 v. 2 a., 5 v. 2 a. 18/9
350-0-350 v. 100 m.a., 6.3 v. 4 v. 3 a., 23/9
250-0-250 v. 100 m.a., 6.3 v. 6 a., 5 v. 3 a., 26/9

For R1355 Conversion 26/9
350-0-350 v. 100 m.a., 6.3 v. 4 v. 3 a., C.T. 0-4-5 v. 3 a., 28/9
350-0-350 v. 150 m.a., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a., 31/-
425-0-425 v. 200 m.a., 6.3 v. 4 v. 3 a., C.T. 6.3 v. 7 a., C.T. 0-4-5 v. 3 a., Suitable Williamson Amplifier, 48/9

OUTPUT TRANSFORMERS, Push-Pull 10-12 watt to match 6V6, 6L6, P24, etc., to 3-5-8 or 15 ohm Speaker, 15/11
15-18 watt for 6V6, 6L6, etc., to 3 or 15 ohms 21/9

Williamson type exact to author's spec. 79/6
SMOOTHING CHOKES—80 m.a., 12 h. 350 ohms, 5/8; 90 m.a. 10 h. 100 ohms, 5/9; 100 m.a. 10 h. 100 ohms, 7/8; 200 m.a., 5 h. 100 ohms, 7/6; 50 m.a. 50 h. 1,500 ohms, Suitable Williamson Amplifier, 8/9.

SPECIAL OFFERS, Mains Trans. (Ex-B.M.I.) 200-250 v. primary, sec. 300-0-300 v. 70 m.a., 6.3 v. 3 a., 4 v. 2 a., 10/11, 220-240 v. primary, sec. 6.3 v. 1.5 a. 5/8, R.A. 8in. M.E. Speakers, field 600 ohms, speech coil 3 ohms, 12/9.

FULL LIST 4d. SPECIAL LIST FOR TRADE 4d. FOR EX-GOVT. ITEMS SEE CLASSIFIED ADVT.

H.A.C. SHORTWAVE H.A.C. EQUIPMENT

Noted for over 13 years for . . . S.W. Receivers and Kits of Quality.

Improved designs with Denco coils: **One-Valve Kit, Model "C" Price, 25/-, Two "E" "50/-**

All kits complete with all components, accessories, and full instructions. Before ordering, call and inspect a demonstration receiver, or send stamped, addressed envelope for descriptive catalogue.

"H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 11, Old Bond Street, London, W.1.

RADIO COMPONENTS EAST STREET, DARLINGTON

LOUDSPEAKER SEPARATORS. As previously advertised.

Model A, kit of parts, 18s. 6d.
" " built and tested, 22s. 6d.
Model B, kit of parts, 32s. 6d.
" " built and tested, 41s. 6d.

SCRATCH FILTER. For fitting to pick-up or amplifier to eliminate scratch, 17s. 6d.

WHISTLE FILTER. For insertion in loudspeaker leads to eliminate 9 Kc/s. whistles, 35s.

All parts in stock for **VIEWMASTER and ELECTRONIC ENGINEERING** Televisors. (No lists.)

Tel.: 4393.



Impressions on the Wax

Review of the Latest Gramophone Records

MOZART'S essentially ensemble opera, "Cosi fan Tutte," provides many attractive duets and trios, of which His Master's Voice have recorded important excerpts from Acts 1 and 2. The latest recording, *H.M.V. DB21120*, completes the series that was recorded by the actual Glyndeboune Opera Company and Glyndeboune Orchestra under their conductor, Fritz Busch. For this record we have one of the best of the soprano solos, performed by Sena Jurinac. The aria is a rondo, and greatly enhances the delights of the second act.

"La Boutique Fantasque" (The Fantastic Toyshop) has been recorded on *Columbia DX1785-7* by Efreim Kurtz, directing the Royal Philharmonic Orchestra. Produced as a ballet by the Diaghilev company in 1919, it is based on a collection of miniatures which Rossini wrote during his retirement.

Another recording from the ballet is Delibes' "Sylvia," which appears on *Parlophone PW8000-1*. This is the first issue of a new series of ballet music which Parlophone will release at regular intervals. Apart from the universally-known Pizzicati, there are other delightful numbers—such as the Huntresses' fanfare and the Valse lente—that make up this suite. It is played by the Royal Opera House Orchestra, Covent Garden, under the direction of Hugo Rignold.

Haydn's "Toy Symphony" was specially written for children, using their own particular weapons as part of the orchestra. The toy instruments used were the cuckoo, rattle, triangle, nightingale, quail, drum and trumpet, and these have the display passages, while the strings have the *ripieno*—the parts played by the whole orchestra. All the toy instruments come out with stereoscopic clearness in this recording by George Weldon, conducting the Philharmonia Orchestra on *Columbia DX1784*.

The Hallé Orchestra, under the baton of Sir John Barbirolli, give a first-class rendering of Bizet's "L'Arlesienne" on *H.M.V. DB9656-7*. This music is part of 27 items which Bizet was commissioned to compose for a Paris production of Daudet's "The Maid of Arles."

Vocal

Discovered by H.M.V. five years ago, Boris Christoff, the Bulgarian bass, now records two items that are often heard, but which require the ability of a front rank singer to be heard at their best. They are the "Song of the Flea" and "Song of the Volga Boatman," which he sings on *H.M.V. DB21305*.

Another equally famous bass is Owen Brannigan,

who sings Sterndale Bennett's famous ballad, "Leatin'" and Leslie Stuart's "Bandolero" on *Columbia C4110*. This singer is reputed to have one of the finest bass voices in Great Britain to-day.

Following Kirsten Flagstad's recent recording of Grieg's songs, she sings two more this month—"Ved Runclarne" (Return to Rundarne) and "Guten" (The Youth) on *H.M.V. DA1992*. Although this singer has announced her retirement from the operatic stage, she will still be seen in person upon the concert platform.

Variety

As a successor to the late Albert Sandler in the direction of the Palm Court Orchestra, Tom Jenkins has filled a difficult position with striking success. "Waltzing thru' Filmland," which he plays on *H.M.V. C4116*, is a medley of tunes from films arranged by Dennis Gonnin.

Lester Ferguson's latest for Parlophone brings together two renderings that have made this young tenor popular in the British entertainment world. The song on the first side is an English version of the tune, "Si tu partais" (If you go), which was heard in the film "Night Without Stars." On the reverse side of *Parlophone R3441* he sings "Love Calling Me Home."

For the first time Dinah Shore and Betty Hutton team with Tony Martin and Phil Harris to offer their version of a comedy song, "The Musicians," on *H.M.V. B10137*. The same quartette are on the reverse side with an equally amusing number from Walt Disney's "Alice In Wonderland" called "How D'ye Do and Shake Hands."

The vocal and instrumental ability of the Tanner Sisters and the Hedley Ward Trio are combined this month in a novelty number called "Jing-a-Ling, Jing-a-Ling" on *H.M.V. B10140*. The coupling is "Bon-bon Chocolate and Chewing Gum."

Dance Music

Joe Loss and his Orchestra continue with their "Dancing Time for Dancers" series with "The Valentino Tango" and a waltz, "Longing For You," on *H.M.V. BD6108*. Another record for dance tempo devotees is supplied by Victor Silvester and his Ballroom Orchestra with "Lullaby of Broadway" (quick-step) and "In a Shanty in Old Shanty Town" (waltz), on *Columbia FB3619*.

Finally, two catchy novelties from America, "Shanghai" and "Kissin' Bug Boogie," have been recorded by Sid Phillips and his Band, on *H.M.V. BD6107*.

Editorial and Advertisement Offices:

"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them, if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

BOOKS

R.S.G.B. "Amateur Radio" publications: Transmitting Licence, 32pp., 1/6; Service Valve Equivalents, 32pp., 1/3; Transmitter Interference, 32pp., 1/6; Simple Transmitting Equipment, 52pp., 2/3; Microwave Technique, 68 pp., 2/3; Receivers, 96pp., 3/9; Valve Technique, 104pp., 3/9; V.H.F. Technique, 96pp., 3/9; R.S.G.B. Bulletin, current issue, 1/6. Five recent issues, 2/6. Prices include postage. **RADIO SOCIETY OF GREAT BRITAIN**, 28, Little Russell St., London, W.C.1.

ALIGNMENT PEAKS. Second edition, 5,000 superheterodyne alignment peaking frequencies, 4/9 post free. The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free. Membership and examination data, 1/- post free. Secretary, I.P.R.E., 20, Fairfield Road, London, N.8.

BRITISH SHORT WAVE LEAGUE is devoted to the interests of amateur radio enthusiasts. Publishes 12-page "BSWL Review," monthly (members only). Offers many services and activity departments. World wide membership. Founded 1935. Apply for details to: **BRITISH SHORT WAVE LEAGUE**, 55, Victoria St., London, S.W.1. (Abbey 2384.)

ALL MAGAZINES.—We can arrange subscriptions to any British or foreign wireless and TV magazine. Send to-day for our free booklet giving details and prices. **WILLEN LTD.**, (Dept. 40), 101, Fleet St., London, E.C.4.

IDEAL FOR XMAS GIFTS.—"Personal Portables." Get your copy of the second edition No. 5 complete circuits and data, 2/8, from **BRAD-BOOKS**, Sennen, Penzance, Cornwall. And "A Portable Television" is better still, of course, at 3/2, post paid.

RECEIVERS & COMPONENTS

FAMOUS TRANSMITTER Receivers, complete with 9 valves, not guaranteed, but much cleaner than our previous stocks; post paid 20/-; consisting of 2 parcels. Trade enquiries invited. We have numerous component parts for amateur and professional. A few parcels left, 50 new, 50 used. Resistors, 6/6, 8 mfd. Ally Condensers, damaged cases, 1/3. **AUTOREX MOTORS**, New Whittington, Chesterfield.

MAKE THESE RECEIVERS.—Concise books of instructions, 1/6 ea., for TRF 2WB £5/10/-, MSS S'het £6, LMS S'het £6/5/-, complete with cabinet and valves. Thousands of components available: TRF coils, 5/3 m.; 1 x 350v. tub., 2/9 doz.; 1 x 50v. tub., 4/6 doz.; EF50, 4/9; VU11, 3/6; CV73 3/6. 3d. stamp for latest list. **SUSSEX ELECTRONICS LTD.** (W), Princes St., Brighton.

"WILTON" Battery D.x.5 Chassis Receiver: first grade Al. panels, 16 gauge, any size; send s.a.e. **WILTON RADIO**, 30, Giants Grave Rd., Neath.

MIDDLEBROUGH.—Denco and Viewmaster TV Kits, C.R. Tubes, Coil Packs, Valves, etc.; send for free lists to **PALMERS**, 114, Waterloo Road. (Phone: 3096.)

EVERYTHING for radio constructors. Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH**, 98, West End Road, Morecambe. Quick service.

2V. TRIODES, soiled, 1/-; Case and Chassis, 2/-; 1/250. 4d.; 7193. 1/9; small pf's, 3d. S.A.E. list. Post extra. **ANNAKIN**, 25, Ashfield Place, Otley, Yorks.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

EDe'S STUDIOS, Chelsea, offers real bargains in used radio spares stripped from Ekco Radio chassis; all components are tested before despatch. Mains Transformers, 350-0-350v. 80 m.a., 4v. 4a., 4v. 2a., 210-250v. prims., with fixing feet, 10/6, incl. post. Rola energised Speakers, 2,500 ohm, field, 8in., with trans. and baffle, 10/6, incl. post; 2,000 and 5,000 ohm, field, less trans., 8in., 8/6, or with damaged cones, 3/6; 400 ohm, with trans., 9/6. Chokes, 400 ohm, 60 mfd., 2/6. Pentode speaker trans., 2/6; i.f. trans., 1/0 k/cs, 3/6 pr.; 110 k/cs osc. coils, with diag., 2/- ea.; 2-wave band pass aerial coils, with switch, trimmer and diag., 4/- ea. 3 gang 0005 tuning condenser, with SM drive and drum with trims, 4/6; 0005 tuning cond., with trims, SM drive, dial and large knob, 5/-; these tuning conds. have one sect. with cut-away vanes for 110 k/cs. Twin HF hum suppressor chokes, 2/- ea.; 0.2 amp. mains droppers, 800 ohm, with fixing rod and voltage tap, 2/-; knobs, 3in. spindle, 1 large, 1/- per set of 3; volume controls, 4 meg., with switch, 1/6; toggle switches, d.p. on/off, 1/-; Resistors, 1 and 1 watt, 1/6 per doz. (our selection); round type Ekco cabinets, 10/-. Special offers: Reconditioned Ekco receivers, round type, AC/DC, bakelite cabinets, 4 valves, plus rec., covering medium- and long-wave bands, complete with valves and tested; only £3/17/6, plus 6/- carr. Philco 5-valve superhet, completely reconditioned and tested, in light oak or dark oak cabinets, Cathedral model for AC or AC/DC mains, £4/10/-, plus 6/- carr. Ekco AC 57, or AC 67, complete but less valves, 35/-, plus 5/- carr. Ekco AD 67, universal, complete but less valves, 30/-, 5/- carr. Terms: C.W.O. or C.O.D. over £1. Please add enough for post. **EDe'S STUDIOS**, 255, Fulham Rd., Chelsea, S.W.3. (Phone: FLAXman 5587.) Nearest Tube: Sth. Kensington.

YOU ARE INVITED to call and hear the wonderful new "Symphony" range of N.R.S. Audio Amplifiers with their three channels giving independent control of treble, middle and base. 5-watt model 9½ gns., 10-watt model (now with push-pull triode output) 15 gns. If you cannot call, send two 2d. stamps for full catalogue and bargain supplement. **Decca A.C. Gram Motors** for 33½ or 78 r.p.m., £4; ditto with switch for 33½, 45 and 78 r.p.m., £7/3/4. Decca Pickup to match with Acos hi-fi crystal cartridge for 78 or L.P., 53/-; or with both interchangeable heads, 84/6; postage 1/6. Acos G.P.20 Pickup with std. or L.P. head, 71/5; or with both heads, 114/9; postage 1/6. Record Player Cases, 15½ x 13½ x 7in., beautifully covered in brown leatherette, sprung carrying handle, uncut, motorboard, while they last, only 57/6. Bass Reflex Cabinet Kits, give superb bass response and crystal-clear top (4in. patent timber). Fully cut, practically fall together, only screwdriver reqd.; 8in. speaker model 2ft. 6in., high x 1ft. 3in. wide x 1ft. deep, fitted felt and deflector plate, 85/-; 10in. speaker model, 97/6; 12in. speaker model, 107/6; carr. 7/6. Available ready built, 7/6 extra. Full catalogue 5d. **NORTHERN RADIO SERVICES**, 16, Kings College Road, London N.W.3. (PRImrose 8314.)

SOUTHERN RADIO'S Wireless Bargains.—Walkie-Talkie (Transmitter-Receiver), Type 38, Mark II, complete with 5 valves, throat microphone, headphones and aerial, 7 m.a. amateur band suitable for field use, powerful superhet receiver; modulated transmitter; guaranteed ready for the air, less batteries, £3/10/-, R.3515 Television Units, complete with 21 valves, 6 stage 14 mc/s I.F. strip; ideal for T.V. conversion; brand new in original wooden cases, £3/10/-. Luffra Hole Cutters, adjustable from ¼in. to 3¼in. for use on wood, metal, plastic, etc., 5/9. Luffra Fly Cutters, 14/6. Lionel "Bug" Keys, genuine U.S. automatic Morse key, Type J36; few only, £3/7/6. Throat Microphones, magnetic type, complete with long lead and plug, 4/6. Control Cables for Command Receivers, B.C. 453/4/5, 14ft., with adaptors, 9/6. Condensers, 100 assorted tubular and mica, all new useful sizes to 2 mfd., 15/- 100. Resistances, 100 assorted new to 3 watts, 12/6 100. Hand Generators, 6 volts at 5 amps, with crank, 21/-. Plastic Transparent Map Cases, 14in. by 10½in.; ideal for maps, charts, display, photographs, etc., 5/6. Star Identifiers, with Hydrographic Office modifications, A-N Type 1, complete in case, 5/6. Moving Coil D/C Motors, brand new, 2in. 0-2 m.a., 0.5 m.a., 0-30 m.a., 0-20 volts, 9/6 ea. Westcoaters, Type WX8 and W112, 1/- ea., 11/- doz. Valves, brand new 805 U.S.A. in original cartons, each 32/6. **SOUTHERN RADIO SUPPLY LTD.**, 11, Little Newport St., London, W.C.2. (GERrard 6653.)

CONDENSERS. Condensers, Condensers for every use and occasion, including many high-voltage types for television and transmitting. It will pay you to send s.a.e. for Component Lists to **E. LYNCH**, 133, St. James Rd., Blackburn.

WALNUT RADIOGRAM CABINETS. Stamp details. **E. WISKER**, 501, Hale End Rd., Higgs Park, E.4.

SPOTLESS SURPLUS.—Mains trans. ex-E.M.I., 300-0-300v, 6V-4A, 5V-2A, 100 M/a, 23/-, post 2/-; Pent Out/trans., 3/6; C/tpd. P. Pull, 6/6; Chokes, 8H.70 M/a, 6/-; 6½in. P.M. Spkrs., 11/6; Valves, VR101 7/6, EL32 7/6, 6Q7G 10/6, EB33 8/6, 6K7G/GT 6/6, 6K7M 7/6, EP91 10/-; 12 valves, all values, 3/-; W/sw 4/6; Condensers, 4mf., 450v 1/6, 8/2; 8 x 16 4/4; 16 x 16 4/9; 32 x 32 6/6. Special. Fresh stock, 16 mfd. 450v. 4 for 10/6. D. P. STRANGE, 52, Pendlestone Rd., London, E.17.

RADIO SUPPLY CO., 15, Wellington St., Leeds 1.—All goods guaranteed. Brand new ex-Govt. Valves, D, 1/3; EA50, 2/9; MS/Pen., 4/6; KT, 4/9; 12SG7, 12SG7, 5/9; 6C6, 6/6, 6C5, 6/11; 6K7G, 6J7G, 6N7GT, KTZ4, 7/6; EF50 (VR91), 7/9; KT66, 8/11; EF39, 8/6; VP4B, 8/9; Pen.46, MHL6D, 1R5, 6X5GT, 5U4G, 9/6; 1S4, 9/11; 6V6G, 10/6; 5Y3G, 6Q7G, 10/11. E.H.T. Rects., VU120A (2v.), 2/9; VU133 (4v.), 3/3; Acorns, 954, 956, 2/9; SP61, 2/11. Selenium Rectifiers (ex new equipment), 120v., 40 m.a., H.W., 3/6; 150v., 60 m.a. (new), 3/11; 0-10-120v., F.W., 60 m.a., 4/9; 680v., 30 m.a., 6/9; 2/Av., 3 a. (new), 1/3. Ex-Govt. Smoothing Chokes, 60 m.a., 10h., 350 ohms, 3/11; 80 m.a., 10h., 250 ohms, 4/6; 100 m.a., 8-10h., 100 ohms (trop.), 4/3. Block Condensers, 4mf., 600v., T.C.C., 2/9; 0.5mf., 3,500v., 1/9. Receiver Units, less valves, R1124, 10/9; type T1, 7/6. Mnfs. surplus, 2 Gangs (0.005mf.), 5/9. Terms: C.W.O. or C.O.D. over £1. Post 1/3 under £3. List 4d.

VAR. CONDENSERS: Twin. 0005. 5/4; with drive. 6/1; single. 0005. 3/6; 4 gang. 0005. 8/6; 3 gang 25pF. 3/6; 2 gang 75pF. 4/1; single 2/1; 2 gang 50pF. 4/1; single. 1/6; Butterfly 50pF. 2/6. Trimmers/padders. from 100pF to 750. 9d. each. Mains Trans.: New, std. inputs 50c. Outputs, 250v 60ma., 6v and 5v. 15/6; 230v (S.E.) 20ma., 6v 1A, 12/1; 350v 80ma.; Univ. L.Ts. 18/1; similar. 250v. 18/1. Mains Dr. pp. 2A. 1k. 3A 800U. 4/6 each; 3A 3r Linecord (80u p.f.t.). 1-yd. Condensers, block Bmf. 440VAC wkg., 5/1; 8 mfd. 1KV wkg. (Aero-vac); 8/6; 4 mfd. 750vW. 3/1; Sprague tub. .01 1KV. 6d.; 5 350v. 8d. Williamson Amplifier Manuals. 2/1; Eddy-stone S.W. Manual, 2/1; Ediswan Valv. Manual, 9d.; Fuseholders, single 6d., twin 8d.; Panel, single. 1/1; Fuse Clips, 3d. pr. Fuses 1 1/2 in. cartridge, 4d. each; Terminals B/Lee, black, insulated, 9d.; I.F.T.s, canned, new, 10/13mcs 2/1; 7mcs 1/6; Coilformers, 2in. x 3/4 in., 4 for 1/1; Morse keys, small, brass. 2/6; Vibrapacks, Malory, 12v. synch. 150v 30ma. 12/6; Vibrators, 2v synch. 7pin UX. 6/1; Cable, 5 core rubber, 2yd. lengths. 1/6; 3 core screened, 10ft. lengths. 2/6; Spindle couplers, brass, cone-tina or insulated, 9d. each; Eddy-stone type, 1/3; Chokes, RF 4 pie Rx. 9d., TX 1/1; Muirhead Dials (black), 7/6. Lists available, 1/4. s.a.e. Terms: C.W.O. carr. paid over 10/-. S.A.E. enquiries, please. W. A. BENSON, 308, Rathbone Rd., Liverpool, 13.

R. F. UNITS, type 24 and 24 mod 27, 15/- ea.; R. F. with 6 universal valves, 30/-; Metal Rectifiers, 12v 1A. 1/6; 6. Delia Switches with 7-day clockwork movement, 21/-; Choro Horse lighting sets, 13-15v 300 watt. 1/6/10/- ea.; Elecs., 8 x 16mfd. 450v. 4/-; Valves 9001 7/6, 8AK5 10/6, others from 1/6. We still have plenty of Government surplus bargains in stock. Send S.A.E. for list. Also Lenses and Prisms and general optical gear. Booklet "How to use Exc. Gov. Lenses and Prisms," 2/6. H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

AERIALS, 75ft. 1/1, 15ft. 3d. 465 Kcs., iron-cored I.F.'s, 5/6 pr. .001. .01. .005 Mica. 4d. List 23d. CARTER'S, 67, Bell Lane, Marston Green, Birmingham.

THE CHALLENGER, MKI Amplifier and Acoustic Chamber. Connoisseur reproduction, 4 6/7s, 2 6/6s. 1 5/4d. 40-15,000 cycle response; circuit and data sheets; 5/-, post paid. TURNER, 14, Upton Grove, South Yardley, Birmingham.

HANNEY OF BATH offers: Eddy-stone 740 Receivers at the old price of £35/10/-; Acos GP20 Pickups, standard or LP, 7/1/5, heads only 43/4; WB Stentorian Speakers, complete range, as advertised; ETA 4-station tuning unit, 47/4; Osrom "Q" Coilpacks, type HO 52/-, H.F. stage, 2/18; Wearite "P" Coils, all ranges, 3/- each; Denco type "C" T.F.R. Coils, 1/- pair. All Components ex-stock for WW, EE, PW, PT and Viewmaster Televisors. L'don, B'ham and Holme Moss. We have stocks of the following Cathode Ray Tubes: Mazda CRM91, CRM121A, CRM121B, CRM123; Muirhead MW22-14, MW22-16, MW22-17, MW22-18, MW31-16, MW31-17, MW31-18; G.C. 6504A; Ferranti T12/44; Brimar CFB. We pay carriage on all tubes and guarantee safe delivery. (No c.o.d. on tubes.) Send 3d. stamp for our lists; new goods only; no surplus. C.W.O. (preferred), or c.o.d. (no c.o.d. under £1). Cash refunded on goods out of stock if necessary. L. F. HANNEY, 77, Lower Bristol Rd., Bath. (Tel.: 3811.)

MAGSLIP Transmitters from 10/-, Ideal for distant control of radio receivers, antenna direction, indication, etc., etc. Stamp for details. **ENGINEERING FACILITIES, LTD.,** 29, Rea St., Birmingham, 5.

TAPE RECORDINGS, ETC.

MAGNETIC SOUND Recording Wire, stainless steel, temporary wood, spools, approx. 1 1/2 hours running time at 2ft. per sec.; 14/- per spool. A. SMART, 40, Grange Rd., Halesowen, Worcs.


TAPE RECORDING—The new Line-A-Tone Recording Panels, 3 speeds, 3 1/2 in., 7 1/2 in. and 15 in. per sec. by push-button control. Freedom from wow, fast rewind. £20. The Line-A-Tone Recording Unit, incorporating the above, complete with microphone, tape, etc., in attractive walnut cabinet, £28. All accessories supplied. Order now. Delivery good. **MORECAMBE SOUND SERVICE,** Seaload Works, Cross, Cop. Morecambe.

REPAIRS AND REWINDS

VACUUM CLEANERS and Gram. Motors repairs cur speciality. Armature rewinds, new bearings and commutators fitted, also transformers rewound, speakers repaired. Competitive prices. Trade enquiries invited, 7 days c.o.d. service. Send s.a.e. for price lists to: A.D.S. Co. (V.E.M. Dept.), 261-3, Lichfield Rd., Aston, Birmingham, 6, Est. 1935.

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE,** 34a, Billington Road, Oxford.

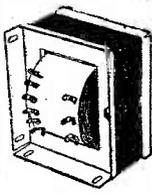Mains Transformers UPRIGHT - DROP THROUGH - AS ILLUSTRATED.
Two Types Only. Guaranteed.
No. 1: 250-0-250V., 60 mA., 0.4-6.3V., 5 amp. 0.4-5V., 2 amp. No. 2: Same, but 350v. Both 15/- post 1/3 for 1 to 3
HILLFIELDS RADIO,
8, Burnham Road, Whitley, Coventry.



COIL for summer A.D. portable 4/9. T.R.F. Coils for all-dry 3-band 3, 6, 6, 50 mfd. 12 v. 1-, 3in. Speaker P.M. 14/-, P.C. Valve-H 9d., Rubber Condensits, 6d. doz., Interference Suppressor ex H.A.F. 6/-, 50pF Trimmers 4d., 50+50pF trimmers 7d., L. & M.W. Padders 1/6, I.F.T.s 45c kc. iron-cored high "Q" 1/16 pair. LMS Hidget Coil Packs 27/6, 2 mfd. 450 v. 1/-, Mail order only.

T. G. HOWELL,
29, McWILLIAM RD., BRIGHTON, 7

AUTOMATIC SWITCHES

(reconditioned)
All types of clockwork and electric switches all reconditioned as new and guaranteed from 35/-

Write to:—
TIMESWITCHES for illustrated details.
GEORGE STREET, NORTH SHIELDS, NORTHUMBERLAND.

Amateur Radio Enthusiasts
THE INCOMPARABLE GLOBE-KING
SINGLE VALVE S.W. RECEIVER
● WORLD - WIDE RANGE 11-100 METRES ● CRYSTAL CLEAR NOISE-FREE RECEPTION ● ELECTRICAL BAND - SPREAD TUNING ● EXTREMELY LOW RUNNING COSTS
Catalogue Free. Stamp for postage
JOHNSONS (RADIO)
46, FRIAR STREET, WORCESTER

GOVERNMENT HEARING Aid Components—Crystal Microphones, 12/6; Crystal Inserts, 10/-; Transformers, 2/6; Potentiometers, 1/6; Cordage 4-wire, 3ft. 9in. long, 1/-; Panels, partly wired, 6d.; Lapel Clips, 4d.; Plugs, 2 or 3 pin, 3d.; Sleeving, 3ft. long, 3d.; Knobs, Handles, etc. Orders over 42d post free. F. R. BARRETT, 7, Upper Kent St., Leicester.

CONDENSERS, brand new, 1/500v tubular, 4/6 doz., post 4d. S.A.E. list bargains. MELHUISS, 315, Ewell Rd., Tolworth, Surrey.

SELENIUM Photo-Electric Cells, 40 x 22mm, 7/6; all standard Photo-cells in stock. Photo-electric Exposure Meter Kits, 37/6 and 42/6; s.b.c. Neon Indicator Lamps (90v), 15/- per dozen. G.R. PRODUCTS, 22, Runnymede Avenue, Bristol, 4

SYNCHRONOUS MOTORS, 200-250v, A.C., 50 cycles, clock type, 12/6 each, 1/- postage; suitable for model engineers. UNIVERSAL ELECTRICAL, 217a, City Rd., London, E.C.1.

EX W.D. unused Fluorescent Lighting tubes for 12 and 24 volt D.C. input, 230v. A.C. output; Rotary Converter, Choce, P.F. Condenser, Leak Transformer for 85-watt. Sodium Lamps. The whole enclosed in metal box, £5, to clear. A. J. PHILPOTT, Fountain Square, Fenton, Stoke-on-Trent.

EDUCATIONAL

TELEVISION—The Gothic Television School, devoted exclusively to training in Television, prepares students to Brit.I.B.E. and R.T.E.B. examination standards. Correspondence course prospectus from the Registrar, Gothic Television School, 13, North Avenue, London, W.13.

THE INSTITUTE of Practical Radio Engineers have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.F.R.E. Service, entry and progressive exams. Tuition fees at pre-war rates are moderate. The Syllabus of Instructional Text may be obtained, post free, from the SECRETARY, Fairfield Road, Crouch End, N.8.

MERCHANT NAVY and Air Radio. Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses. S.A.E. for prospectus from Director, THE WIRELESS SCHOOL, 21, Manor Gardens, Holloway, London, N.7. (Estd. 30 yrs.) (Phone: ARC 3694.) Students deferred from Military Service.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc., on "No Pass—No Fee" terms. Over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook—Free. B.I.E.T. (Dept. 242a), 17, Stratford Place, London, W.1.

SEE THE WORLD...—600 Radio Officers required. Send 2d. stamp for prospectus to Britain's leading college. We train most in shortest period at lowest cost. **WIRELESS COLLEGE,** Colwyn Bay.

WIRELESS—Postal Course in theory for Amateur Transmitting Licence, complete with text-book at moderate fee; also instruction at school for P.M.G.'s Certificates to become Radio Officers in Merchant Navy at good salaries. Recognised by Ministry of Education. Apply B.S.T., LTD., 179, Clapham Road, London, S.W.9. (Est. 1906.)

2-VOLT BATTERY SUPER-HET. 6-9 mc/s. Chassis taken from the No. 18 Tx/Rx. Tested and ready for use, 32/-.

TR1196 CIRCUIT AND CONVERSION DATA, 1/3.

New IN34 CRYSTAL DIODES, 5/6.

P.M.SPEAKERS. W.B. 2 1/2 in., 14/6; 6 1/2 in., 16/6; 8 in. with trans., 21/6.

MULTIMETERS. 2 1/2 in. Supplied as kits with black bakelite cases, 6 x 4 1/2 x 1 1/2 in. and resistors for D.C. ranges 0-3, 0-30, 0-150, 0-300, 0-600v. and 60mA. Scale also reads OHMS 0-5,000 with 1 1/2 v. battery, 24/6.

MOVING-COIL MICROPHONES with switch, 6/6. Trans. to match, 5/-.

6v. VIBRATOR PACK in black steel case, 7 1/2 x 5 1/2 x 3 1/2 in. Output 200v. 40mA., 22/6.

SELENIUM RECTIFIERS. H.W. 250v. 120mA., 8/6. F.W. 6 or 12v. 4A., 26/-; 6-12 or 24 F.W. 2A., 8/6; F.W. 6 or 12v., 1A 5/6.


ARMY CARBON MICROPHONE, with switch, 4/6. Trans. to match, 3/6.

TRANSFORMERS. 200-240 volts, tapped 3-4-5-6-8-9-10-12-15-18-20-24 and 30 volts at 2 amps., 21/3 Post Paid.

100/120v. AC/DC or 240 DC MOTORS. 1 1/6 h.p. 5/16 in. spindle at each end. 5 1/2 in. x 3 1/2 in., price 32/-, or fitted with 2 1/2 in. grindstone, medium or fine, 36/-.

All Carriage Paid. Money back Guarantee if returned within 7 days, unused.

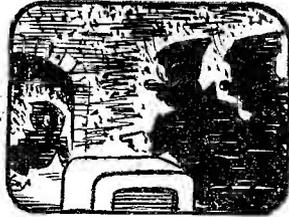THE RADIO & ELECTRICAL MART
253b, Portobello Road, London, W.11.
Phone: Park 6026.



The "Fluxite Quins" at Work
"Fixing our aerial's all right,
With solder and good old FLUXITE,
But why" EH cried
"Should our lad decide
To fall down the chimney to-night!"

See that **FLUXITE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, from 1/- upwards. **The FLUXITE GUN** puts FLUXITE where you want it by a simple pressure. Price 2/6, or filled 3/6.

FLUXITE
SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1/6 each.
FLUXITE Ltd., Dept. W.P.,
Bermondsey Street, London, S.E.1.

FIRST-CLASS RADIO COURSES . . .
GET A CERTIFICATE!
QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

FREE GUIDE
The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches)**, etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES
NATIONAL INSTITUTE OF ENGINEERING
(Dept. 461), 148, HOLBORN, LONDON, E.C.1

MORSE CODE Training




COURSES for BEGINNERS and OPERATORS, also a **SPECIAL COURSE** for passing the G.P.O. Morse Test for securing an **AMATEUR'S TRANSMITTING LICENCE.**
Send for the **Candler BOOK OF FACTS** It gives details of all Courses.

THE CANDLER SYSTEM CO.
(Dept. 5LO), 52b, Abingdon Road, Kensington, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

TRANSFORMERS

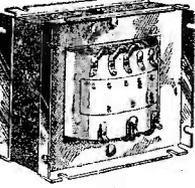M.T.1.—250-0-250 v. 80 mA; 0-4 v. 5 a.; 6.3 v. 3.6 a. 0-4.5 v. 2 a.
M.T.2.—Same as M.T.1. but 350-0-350 v.
M.T.3.—30 v.; 2 a.; tapped every 3 volts. All primaries tapped for 200 to 250 v.



M.T.4. Auto 0-10-120-200-230-250v. 100 watts. Examine what you buy. From component dealers or write to us if unobtainable. The maximum price for these transformers is **22/-** each.

THE DOUGLAS COIL CO.,
BRINKLOW, RUGBY.

SAMSONS
SURPLUS STORES

SPECIAL OFFER. E.C.C. Ltd., 80 watt Light-weight PETROL CHARGING SETS. Output 18v. 4.5A, 24v. 80 watt. Brand new. Complete with spares and tool kit. Price £22.10.0. Carr. 10/-.

36ft. AERIAL MASTS. R.A.F. type 50. Complete kit consists of 9 tubular steel sections, length 4ft., diameter 2ins. Set of pickets, top plates, guys and all fittings. Brand new in canvas carrying bags. Ideal for TV, aerial masts. £6.10.0. Carr. 7/6.

WILLARD BATTERIES. 12v. 85 AH in solid vulcanised rubber. Size 12 1/2 in. x 7 in. x 10 1/2 in. Brand new. £6.10.0. Carr. 6/-.

MASTER VOLTMETERS. 0.20v. A.C. Moving iron 6in. mirrored scale, made by Metro Vickers. 22/6. Carr. 1/6.

CRYSTAL LAPEL MIKE INSERTS. Very sensitive. 12/6. Postage 6d.

80 Ohm CO-AXIAL CABLE. 11/- per yd. Postage 9d. up to 10 yds.

169/171, Edgware Road, London, W.2.
Tel.: Pad. 7851.

125, Tottenham Court Road, W.1.
Tel.: Eus. 4982.

Hundreds of Bargains for Callers.
All orders and enquiries to our Edgware Road branch, please, which is open all day Saturday.

DUKE & CO.

RADIO CONTROL UNIT, 12/6 including speaker, 3 1/2 in. tweeter, 25 Resistances, including wirewound L.F. Trans., various conds.; 2 instrument type fuses, 8 International octals ceramic, 3 Acorns ceramic, 7 vibrators, 7 relays with multi-contacts, 2 Coax. connectors, Wire and all the usual parts, etc. Clean chassis and cabinet of pleasing appearance. Ideal amplifier or receiver, etc. Post 2/- extra.
JUST IN—CLOCKWORK MECHANISM, 8/6 each. Beautifully made in solid brass, small but each piece is engineering perfection. TYPE R.M.C.B. 4551. We shall give you more information later, as we understand these make first-class clocks, exposure timers, regulators, etc. Just the job for the Amateur Mechanic with ideas.

No. 18 SHORTWAVE SUPERHET, 15/6. Free instructions for conversion to All-wave and Circuits. Diagrams included. Note Set with 11th alteration makes first-class portable or car radio. I.F.'s 485. Change over to P. Coils for Medium Wave. Less valves. There are only a very limited number of these sets and our previous supplies were quickly sold out.

NIGHT RECEIVERS. In bakelite plastic cabinet, wall or desk, 4 valves. T.R.F. Universal or A.C. for only £5-12-6. Or assembled 35/- extra. New and improved circuits. An amateur can build this set with practically no knowledge. The only set now available at this price. Post and packing 2/6.

AERIALS, 7/- only. 12ft. in 3 sections, 4ft. each. Tubular copper-plated steel. Carr. 2/-. **AERIAL BASES,** Rubber, with fitting to take 12ft. aerial, 1/6 plus post 10d. **MICRO SWITCH, 3/6** each. Also mercury minors 3/6 each.

NICKEL CHROME WIRE. 50 yds. spool of .014 wire for only 4/6, or 25 yds. .032 same price. These prices are a fraction of to-day's prices (if you can buy it).

Money back guarantee. Cash with order, please. Or C.O.D. Stamps only for Lists. 621, Romford Road, Manor Park, E.12. Phone GRA 0677 for postal service. Personal shoppers 219, Ilford Lane. I.L.F 0265, Essex.

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

- Blueprints, 1s. each.
1937 Crystal Receiver ... PW71*
The "Junior" Crystal
Set PW94*

STRAIGHT SETS

Battery Operated

- One-Valve : Blueprints, 2s. each.
The "Pyramid" One-
valver (HF Pen) .. PW93*
Two-valve : Blueprints, 2s.
The Signet Two (D &
LF) PW76*
Three-valve : Blueprints, 2s. each.
Summit Three (HF Pen,
D, Pen) PW37*
The "Rapide" Straight
3 (D, 2 LF (RC &
Trans)) PW82*
F. J. Camm's "Sprite"
Three (HF, Pen, D,
Tet) PW87*
Four-valve : Blueprints, 2s. each.
Fury Four Super (SG,
SG, D, Pen) PW34C*

Mains Operated

- Two-valve : Blueprints, 2s. each.
Selectone A.C. Radio-
gram Two (D, Pow) PW19*
Three-valve : Blueprints, 2s. each.
Double - Diode - Triode
Three (HF Pen, DDT,
Pen) PW23*
Four-valve : Blueprints, 2s. each.
A.C. Fury Four (SG, SG,
D, Pen) PW20*
A.C. Hall-Mark (HF
Pen, D, Push-Pull) .. PW45*

SUPERHETS

- Battery Sets : Blueprints, 2s. each.
F. J. Camm's 2-valve
Superhet PW52*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprint, 2s.
Simple S.W. One-valver PW88*
Two-valve : Blueprints, 2s. each.
Midget Short-wave Two
(D, Pen) PW38A*
Three-valve : Blueprints, 2s. each.
Experimenter's Short-
wave Three (SG, D,
Pow) PW30A*
The Perfect 3 (D, 2 LF
(RC and Trans)) .. PW63*
The Band-spread S.W.
Three (HF Pen, D
(Pen), Pen) PW68*

PORTABLES

- Four-valve : Blueprint, 2s.
"Imp" Portable 4 (D,
LF, LF, Pen) .. PW86*

MISCELLANEOUS

- Blueprint, 2s.
S.W. Converter-Adapter
(1 valve) PW48A*

TELEVISION

- The Practical Television Receiver,
(3 sheets) 10/6

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

- One-valve : Blueprint, 2s.
B.B.C. Special One-
valver AW387*
Two-valve : Blueprints, 2s. each.
A modern Two-valver .. WM409*

Mains Operated

- Two-valve : Blueprints, 2s. each.
Consoelectric Two (D,
Pen), A.C. AW403

SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.
The index letters which precede the blueprint number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.
Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprints, 2s. each.
S.W. One-valver for
America AW429*
Two-valve : Blueprints, 2s. each.
Ultra-short Battery Two
(SG, det Pen)... .. WM402*
Four-valve : Blueprints, 3s. each.
A.W. Short-Wave World-
beater (HF Pen, D, RC,
Trans) AW436*
Standard Four-valver
Short-waver (SG, D,
LF, P)... .. WM383*

Mains Operated

- Four-valve : Blueprints, 3s.
Standard Four-valve A.C.
Short-waver (SG, D,
RC, Trans) WM391*

MISCELLANEOUS

- Enthusiast's Power Am-
plifier (10 Watts) (3/-) WM387*
Listener's 5-watt A.C.
Amplifier (3/-) .. WM392*
Harris Electrogram
battery amplifier (2/-) WM399*
De Luxe Concert A.C.
Electrogram (2/-) .. WM403*

HINTS COUPON

This coupon is available until Dec-
3rd, 1951, and must accompany all
Practical Hints.
PRACTICAL WIRELESS, DEC., 1951.

USEFUL XMAS GIFT



Novelty battery radio in coloured plastic cabinet only 6in. high, with built-in moving coil speaker, 2-gang tuning condenser, volume control and ON/OFF switch, all wired up ready to operate as soon as valves are fitted.

Valves required are three of type 1Y4 and one of 354. Price 49/6 each, postage and insurance 2/6 extra. Don't delay—send your order to-day.

5-VALVE SUPERHET CHASSIS
A.C. mains operated, completely wired, aligned and ready for immediate operation. Covers long, medium and short wavebands with gram input. Really first class receiver using Parneck mains transformer, Eric resistors, Hunt and Wingrove condensers, etc. Overall size 8 1/2 in. x 1 1/2 in. x 1 1/2 in. Pull vision dial, size 6 in. x 8 in. Complete brand new chassis with valves and 8 in. speaker, only £10 10s., plus 7/6 carriage and insurance.

TV UNIT UNIT, TYPE RDF1

As suggested by "Practical Television," October, is suitable for a home-built Television, but with the complete set of 14 valves instead of 11, e.g., 5 of 5P61, 2 of 6P1, 3 of 6A50 and 1 each of CV65, BB31, EC63, 5Z4. Price 49/6 plus 5/- post.

Many more Government Units in stock—send 6d. for our latest list



PRECISION EQUIPMENT

WHY PAY HIGH PRICES FOR COIL PACKS

If you use our parts, these literally fall together, and our publication "Making Coil Packs," price 1/6 each, describes a simple method of alignment without using a signal generator, and gives circuits of many typical receivers.

PRICE LIST OF PARTS



Set of 6 coils, covering the 3 standard long, medium and short wavebands, price 9/6. Punched metal chassis, 1/9. 6-bank trimmer assembly, 3/-. Midget wave-change switch, 4/-. Tag panel, condensers, etc., 1/9.

When complete, your coil pack will look like this.


A PLAN FOR FAULT FINDING

TEST 1

Connect a link from grid of receiver output valve to grid of "I.F./A.F." output valve. If results are obtained, the faulty component must be either R15, C15, output valve or loudspeaker. If no results, then proceed to Test 2.

TEST 2

Connect grid of receiver D.D.T. valve to grid of "I.F./A.F." D.D.T. valve, if results then faulty part must either be E13, C22, R16, R11, C19 or V3. If no results, go on to Test 3. The plan of which the above is an extract explains how our I.F./A.F. Amplifier will replace the stages of a faulty receiver one by one, and thus narrow suspected components down to about six. With it the novice can fault find with the same confidence as the expert. Also the I.F./A.F. Amplifier will enable the user to quickly (a) trace intermittent, obscure and multiple faults, (b) align and calibrate coil packs, superhet tuners, etc. (c) hook-up an emergency receiver or amplifier. Our Do Luxe Model contains a standard mains transformer (thus permitting mains isolation) and is complete with drilled chassis, valves, I.F. transformers, and all parts required to make up a superhet (less coil pack stage and speaker). Price in kit form is £6 10s. 0d. or ready made up £7 10s. 0d. with instruction manual and fault finding plan, carb. & packing 3/- extra. Instruction Manual available separately, 2/6.

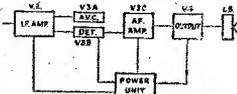

TV UNIT

194 STRIP

Also described in the October "Practical Television," contains 8 valves and really does give superior results. Price 45/-, plus 2/6 postage.

SPARES

CARBON RESISTORS

Standard Tolerance 1 watt 4d. each, 1 watt 6d. each, 1 watt 6d. each. All standard values in stock.

CONDENSERS

Mica and paper, values up to of mfd., 350-450 v. working, 6d. each.

VOLUME CONTROLS

Standard size, long spindle with switch, 4/- each, less switch, 3/- each. Midget type, long spindle with switch, 5/9 each, less switch, 4/- each.

ELECTROLYTIC CONDENSERS

1 mfd. 450 v.	1/3
2 mfd. 350 v.	1/3
2 mfd. 450 v.	1/6
4 mfd. 450 v.	1/6
8 mfd. 150 v.	1/6
8 mfd. 450 v.	2/6
8 mfd. 500 v.	3/3
16 mfd. 350 v.	2/9
16 mfd. 450 v.	3/6
16 mfd. 700 v.	7/6
32 mfd. 350 v.	2/9
8 mfd. x 8 mfd. 350 v.	3/-
8 mfd. x 8 mfd. 450 v.	3/9
8 mfd. x 16 mfd. 350 v.	4/9
16 mfd. x 16 mfd. 450 v.	6/-
24 mfd. x 24 mfd. 200 v.	4/6
32 mfd. x 32 mfd. 150 v.	4/9
32 mfd. x 32 mfd. 450 v.	6/9
100 mfd. x 100 mfd. 150 v.	5/6
10 mfd. 25 v.	1/6
25 mfd. 25 v.	1/6
25 mfd. 50 v.	2/-
50 mfd. 12 v.	9d.
50 mfd. 50 v.	2/3
250 mfd. 25 v.	2/6

152-153, Fleet Street, E.C.4.

Windmill Hill, Ruislip, Middx.

AVOID DELAY.
SEND LETTERS TO
RUISLIP ADDRESS
TO DEPT. V.

CLYDESDALE

Bargains in Ex-Services Radio and Electronic Equipment

COMMAND RECEIVER CC/CBY 46129

U.S.N. version of the BC-453 for that Sharp channel "Q-Fiver," range 550-1900 Kcs. with 6 valves, 3 138K7, 12K8, 12SR7, three gang tuning cond., etc., etc. Dim.: 11 x 5 1/2 x 5 ins., finish black, less dynamotor.

CLYDESDALE'S PRICE ONLY

70/-

POST PAID

Circuits of BC-453 available at 1/8.
R3547 CHASSIS LESS VALVES

Probably the greatest breakdown valve of any of the Radar receivers. Contains a removable 45 mcs. I.F. strip, 24 v. reversible motor, with 700:1 gearing, relay, pots, resistors, condensers, valveholders, etc. Chassis enclosed in metal case. Dim.: 18 x 13 x 7 1/2 ins.

CLYDESDALE'S PRICE ONLY

39/6

CARRIAGE PAID

NEW LIST No. 8

Giving details and illustrations of ex-services items and cancelling all previous lists and supplements.

Now Ready—Price 1/6

Price credited on first purchase of 10/- or over.

STILL AVAILABLE

S-40-B (P40) V.H.F. Tx. Chassis, P-40 Receiver Unit with valves	Each £1: 7: 6
Each £3: 19: 6	
Jefferson-Travis UF 2 1/2 Tx. Chassis	Each £2: 0: 0
Jefferson-Travis UF 1 Vibrator Pack	Each £1: 5: 0
Command Transmitter Chassis	Each 15: 0
Command Modulator Unit BC 456	Each 18: 0

As previously advertised.
TX and T/H partly stripped by M.O.S.

STAINS PROPPER

Vitreous enamel construction, 707 ohms, tapped at 110 ohms. Capable of handling 90 watts. Dimensions 3 1/2 x 1 1/2 in. diam.

CLYDESDALE'S PRICE ONLY

2/6

POST 3d.

B7G VALVEHOLDERS

These are of Paxolin construction. 9d. each, Post 3d.

Order direct from:

CLYDESDALE SUPPLY CO. LTD.

2, Bridge St., Glasgow, C.5. Phone: SOUTH 2 708/9
Visit our Branches in Scotland, England and N. Ireland.

SUCCESS?

In Radio, Television, and Electronics, there are many more top jobs than engineers qualified to fill them. Because we are part of the great E.M.I. Group we have first-hand knowledge of the needs of employers, thus our Home Study courses are authoritative and based upon modern industrial needs. Alternatively, our courses will prove equally valuable to you in furthering your hobby.

POST THIS COUPON NOW

E.M.I. INSTITUTES, Postal Division, Dept. 32, 43 GROVE PARK ROAD, CHISWICK, LONDON, W.4.

Please send, without obligation, your FREE BROCHURE. (I have marked the subjects which interest me.)

Mechanical Eng. Electrical Eng. Draftsmanship.
 Radio. Television. Production Eng. Automobile Eng. Aeronautical Eng. General Cert. of Education (Metric). Civil Service.

Also courses for A.M.I. Mech.E., A.M.I.C.E., A.M. Brit. I.R.E., A.F.R.Ae.S., CITY and GUILDS EXAMS. in Mech. Eng., Elect. Eng., Telecommunications, etc.

Other Subjects

NAME

ADDRESS

E.M.I. INSTITUTES—The College backed by an Industry