

ALIGNMENT OF FRAME AERIALS




Vol. 30 No. 569

MARCH, 1954

EDITOR:  
F.J. CAMM

# PRACTICAL WIRELESS

*More about the -*

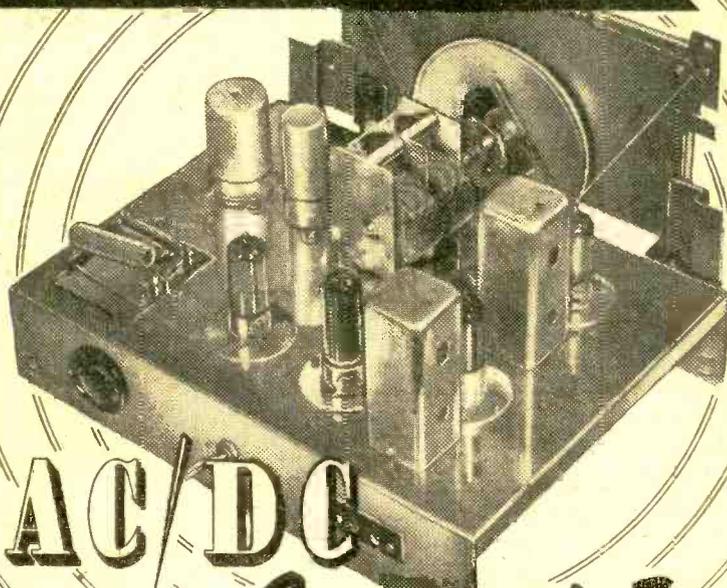

**AC/DC**

**Coronet Four**

IN THIS ISSUE:

MODIFYING TESTMETER TYPE "E"  
IMPROVING SUPERHET  
PERFORMANCE  
A CONDENSER ANALYSER


SURPLUS DOUBLE DIODE  
PENTODES  
THE "P.W." FULL-COMPASS  
ELECTRONIC ORGAN

# 2 New MODELS

~~ACOS~~ quality crystal  
microphones at a  
reasonable price

**MIC 33-1:** A crystal hand or desk omni-directional microphone for the high quality public address and tape recording field, incorporating a specially designed acoustic filter giving a response flat from 30 to 7,000 c.p.s.


RETAIL PRICE £2-10-0d.

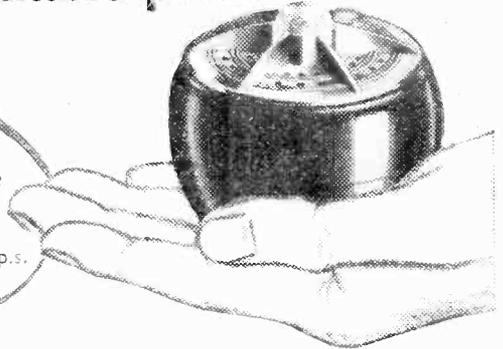

Ideal for tape and disc recording,  
P.A. and amateur radio.

**MIC 35-1:** A general purpose hand microphone of robust construction with substantially flat response from 50 to 5,000 c.p.s. Suitable for recording apparatus. Public Address equipment etc.

RETAIL PRICE £1-5-0d.

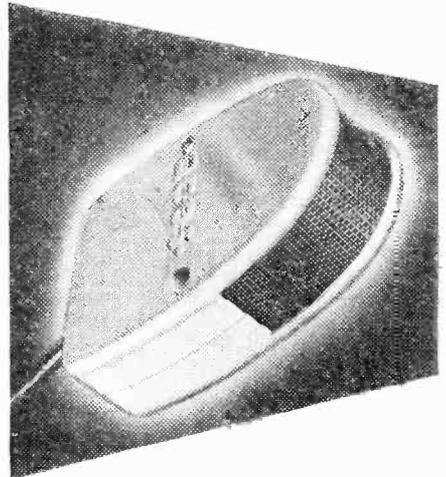

*always well ahead*


*ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.*

**COSMOCORD LIMITED • ENFIELD • MIDDLESEX**
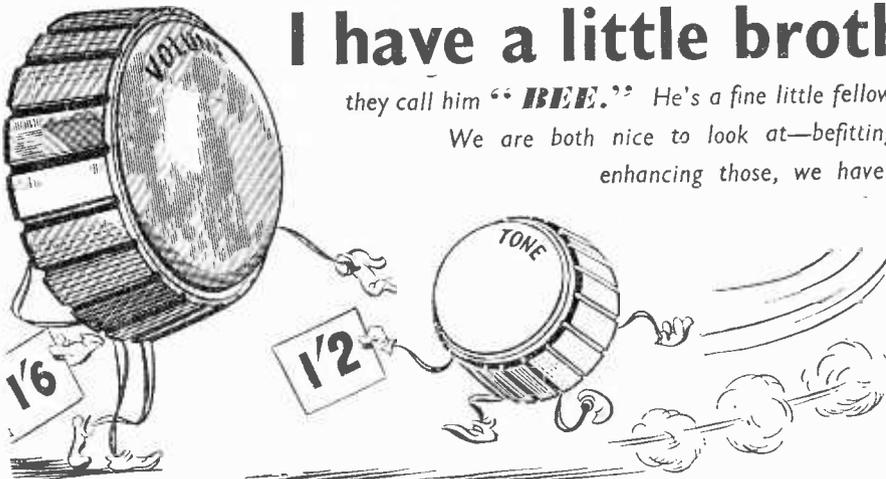
# I have a little brother—

they call him “**BEE.**” He’s a fine little fellow, just like me!

We are both nice to look at—befitting any set enhancing those, we have already met!



**YOU CAN OBTAIN US NOW FROM YOUR LOCAL COMPONENT STOCKIST**

The complete range of control knobs you’ve been waiting for! 16 special **GOLD FILLED** inscriptions that will meet the demand of every radio, T/V, tape recorder or amplifier enthusiast—beautifully made and designed to enhance the appearance of every commercial or amateur constructed set.  
 Sizes: Type “A” 1 1/8” dia. Type “B” 1 1/8” dia. Both types are 3/8” deep.

**AN ENGRAVING FOR EVERY PURPOSE—**  
**RADIO:** “Volume,” “Tuning,” “Wavechange,” “On-Off,” “S.M.L.-Gram,” “Radio-Gram,” “Tone,” “Vol./On-Off.”  
**TELEVISION:** “Focus,” “Contrast,” “Brilliance,” “Brightness,” “Brilliance/On-Off.”  
**AMPLIFIER:** “Bass,” “Treble” (plus any of above).  
**TAPE RECORDER:** “Record-Play” (plus any of above).  
**AVAILABLE IN WALNUT OR IVORY.**  
**PRICES:** Type “A,” 1/6 each; Type “B,” 1/2 each.  
 Plain knobs can also be supplied at 1/- and 10d., respectively


If in difficulty please write to:

**Uncles, Bliss & Co., Ltd., 139 · Cherry Orchard Road · East Croydon · Surrey**      Telephone: **CROYDON 3379·6390**
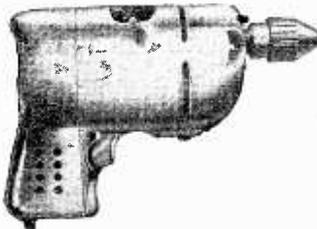
## BE PREPARED! Save TIME and MONEY with these PROFESSIONAL AIDS.

Speed the job with this **BLACK & DECKER** 1/2 in. Electric Drill.


**32/6** with 12/6 monthly order for 8 months  
**CASH PRICE, £5.19.6**



Present-day service demands a high-resistance meter. The **PULLIN “100”** is 10,000Ω per volt and has resistance ranges reading up to 1,000,000Ω on internal batteries. 4 1/2 in. meter in handsome diecast case.

**£3.17s.** with order and £1 monthly for 9 months.

**CASH PRICE £11.11.0.**

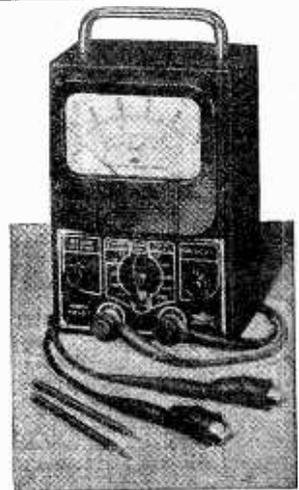

Full lists of other high grade equipment free on request.

EASY PAYMENT ORDER BLANK  
 To: **Frith Radiocraft, Ltd., Leicester**

DATE.....

No. of Pa'mts

Please supply.....  
 for which I enclose £ : : Deposit and agree to pay  
 further monthly payments of £ : : commencing on the first day  
 of next month

P.W. Mar. 54      SIGNED (usual signature).....

NAME IN FULL (CAPITALS).....

ADDRESS .....

State if Householder  If over 21  Occupation.....

**Frith RADIOCRAFT Ltd.** PHONE 58527  
 69-71 CHURCH GATE · LEICESTER

# CLYDESDALE *prices slashed*

**R1155 RECEIVER UNIT**  
Communications, D.P. and "ham." 20, 40, 80, 5 ranges 18-7.5 Mc/s., 7.5-3 Mc/s., 1,500-900 kc/s., 500-200 kc/s. and 200-75 kc/s. Complete with 10 valves, S.M. drive, M.E. tuning, B.F.O., etc. In metal case 16 1/2 x 9 x 9 in. External Power Supply required. Used, good condition. In Transit Case. ASK FOR **£8.19.6** CARRIAGE PAID P/H1916

ALSO AVAILABLE  
R1155, as above, but loose stored.  
ASK FOR **£5.19.6** CARRIAGE PAID P/H893

**T1154 TRANSMITTER UNIT**  
Medium-high powered for C.W.-M.C.W. R.T. 3 ranges 10-5.5 Mc s., 5.5-3 Mc s., 500-200 kc s. Complete with 4 valves, etc., in metal case 11in. x 16 1/2in x 3 1/2in. External Power Supply required.  
ASK FOR **39/6** Each CARRIAGE PAID P/1E3A

ALSO AVAILABLE  
T1154 as above, but less valves.  
ASK FOR **15/-** Each CARRIAGE PAID P/1E5B

**VISUAL INDICATOR TYPE 1, Ref. 10Q 2**  
Dual reading left right D.P. meter for R1155, 3 1/2in. Scale overall dim.: 3 1/2in. x 2 1/2in. In used condition.  
ASK FOR **12/6** Each POST PAID P/H362A

**POWER UNITS FOR T1154 R1155 UNITS**  
Each a Motor Generator Unit, smoothed, etc., in metal case 16 1/2 in x 7 1/2 in x 6 in  
LOOSE STORED

Types 33 or 33B, Input 24 v. D.C. 16A. Output 1.20 v. D.C. 200 mA.  
ASK FOR **42/6** Each CARRIAGE PAID P/1E7A

Types 35A, Input 18 v. D.C. 12 A. Outputs 7.2 v. D.C. 13 A. and 225 v. D.C. 110 mA.  
ASK FOR **£1.0.0** Each CARRIAGE PAID P/1E8A

**TRANSMITTER TUNING UNITS**  
Each having Vernier tuning dial, Variable Capacitor, Tank Coil unit on ceramic former, Ceramic Switch, etc., etc. In metal cabinet 17 1/2 in. x 7 1/2 in. x 8 in., finish black. Unused, but externally soiled, scratched and dented, due to being Loose Stored.  
TU.7B, Range 4,500-4,200 kc s. Ask for P H29.  
TU.8B, Range 6,200-7,700 kc s. Ask for P H30.  
TU.9B, Range 7,000-10,000 kc s. Ask for P H467

EITHER UNIT **10/-** Each CARRIAGE PAID 2/- EXTRA

**IFF RECEIVER R3103 Ref. No. 10DB 505.2**  
Contains: Motor Generator Input 12 v. 3.8 a. Output 480 v., .04 a. D.C. with gearbox operating a switching mechanism to detune the receiver at time intervals. Data available for converting to 250 v. 50 c/s use as motor.  
Plus: 4 VR65A (SP41), 2 VR62 (EA50), 2 CV6 (Det. 20) Valves, etc., etc.  
Metal Case, dimensions: 12in. x 12in. x 8in. Weight 24 lbs.  
ASK FOR **19/6** Each CARRIAGE PAID P/H951

**26 WATT OUTPUT TRANSFORMER**  
Parmeko type AF5081 1A. (Mfg. Surplus.) Primary: 6,630 ohms C.T. Sec's 3.5, 5, 7.5 or 10 ohms. Dimensions: 3 1/2 in. x 2 1/2 in. x 2 1/2 in. Fully shrouded. Weight 3 lbs.  
ASK FOR **19/6** Each POST PAID P/H565.

Order direct from:—  
**CLYDESDALE SUPPLY 2, BRIDGE STREET CO. LTD. GLASGOW - C.5**  
Phone: South 2706/9 Branches in Scotland, England and Northern Ireland

**BC-456 SPEECH MODULATOR UNITS**  
Part of SCR-274-N "Command Equipment." (U.S.A. Made)  
Complete with valves 1625, 1215 and VR150/30, transformers, relays, etc., less dynamotor. Overall dim.: 10 1/2 x 7 1/2 x 4 1/2 in. Loose stored.  
ASK FOR **17/6** Each CARRIAGE PAID P/E92

Available. BC-456 as above, in orig. carton.  
ASK FOR **27/6** Each CARRIAGE PAID P/E12A

**GLASS DOME INSULATOR**, with threaded Terminal Top and Metal Lead-through Rod. Dome dim.: 2 1/2 x 1 1/2 in. high. Lead-through projects 6 1/2 in. Overall length 9 1/2 in.  
ASK FOR **2/-** Each POST 3d. P/H151

**CERAMIC AERIAL SPREADER** individually boxed.  
Length overall 11in., between centres 9 1/2 in.  
ASK FOR **1/-** per pair POST 3d. P/H718

**BLACK PLASTIC CHAIN AERIAL INSULATORS**  
Comprising 3 links, 3 1/2 in. long, 1 1/2 in. wide, each link. Total length 7 1/2 in. A.M. ref. 10A J275.  
ASK FOR **9d.** per pair POST 3d. P/H525

## "YOU CAN RELY ON US" Some of Our Surplus Bargains—

**VALVES**

KT241	4/6	9D2	7/-	MSPEN (7)	
1T4	7/6	1R5	8/6		5/-
6K89	9/-	6BE6	10/-	1S4	8/6
12K8GT	3/-	EB34	3/6	12BB6	7/-
757	8/6	524G	7/6	6K7GT	7/6
6K7G	7/6	3A4	7/-	EL41	7/6
PT25H	5/-	2524	12/6	50C5	7/6
807	9/6	5Z3	8/6	2525	12/6
3524	8/6	6V6G	7/6	EL81	8/6
EB41	10/-	U78	8/6	6X5G	7/-
R3	9/-	76	6/-	VU39A	8/-
6C5	7/6	12A6	7/-	8NTGT	7/-
2A3	5/-	6AM5	8/-	77	6/6
EF50	6/-				

**ECONOMY VALVE SUGGESTIONS**  
3D3, 5/-, Is an excellent 1.4 v. loctal base O.P. valve. 6U5, 6/-, Is a 6.3 v. international octal based magic eye (will replace Y63, VU103, etc.). 6BW6, 7.6, Is the 6V6 in miniature B8A base. VU39A, 9/-, Replaces nearly all 4 v. 4-pin rectifiers. (Ideal for repair work.) 12J3, 4/6 Is an octal 12 v. triode—useful for detector valve in TRF, using 15 a. chain.

We Have Some Excellent EF50 at Bargain Offer.  
Price—6 for 27.6. (All Seals Perfect.)

**ELECTROLYTICS**

2 mfd., 350 v.	1/3	8-16 mfd., 450 v.	5/-
4 mfd., 350 v.	1/6	8-3 mfd., 500 v.	4/6
8 mfd., 350 v.	2/6	16-24 mfd., 350 v.	5/6
8 mfd., 450 v.	2/6	25 mfd., 25 v.	1/6
16 mfd., 350 v.	2/6	30 mfd., 12 v.	2/-
32 mfd., 350 v.	3/6	30 mfd., 50 v.	2/-
16 mfd., 450 v.	4/6	60-200 mfd., 275 v.	8/6

**MICA MOULDED CONDENSERS**  
.0001, .0002, .0003, 50 pf., 5 pf., 75 pf., 6d. each. .01, .005, 8d. each.

**TUBULAR CONDENSERS**  
.001, .002, .004, .005, .01, .02, .05, .1, 6d. each. .25, 350 v., .5, 350 v., 1.6 each.

**VOLUME CONTROLS**  
2,500 to 2 mg., 2/9 each, with switch, 4 3/8.

**SPEAKER TRANSFORMERS**  
48 : 1, 4/6. 30 : 1, 4/6. Midgest for 3S4, DL32, 5/-.

**BARGAIN SPEAKER**  
Plessey 5in. mains energised 1,000Ω, with matching transformer. 15. - New and Boxed. 6in. Elac P.M. Boxed, 15. -

**SPANNERS**  
Set of 2, 4, 6BA, 1/-, 4BA box spanner, 6d., 6 for 2-3. Miniature 12 v. 5 m.a. Instrument or bias rectifier, 1/- each. (Two for full wave.)

**GERMANIUM CRYSTALS** G.E.C., 3.6 each. .0005, twin gang condensers (standard size), 7.6. .0005 twin gang complete with drive and drum, 10. -

**RESISTANCES**  
1 w., 1 w., 4d. each. 1 watt, 8d. All Valves in 10 ohms to 10 mg. standard range.

**NEW PRODUCTS**  
(Additions to Catalogue No. 12.)  
Tyana Soldering Irons, 16.9.  
The New Henley Instrument Iron, 18.9.  
A New Good Quality EHT Oscillator Coil, 6 to 18 kv. Complete with circuit (mounting for rectifier, fixing, etc.). Price, 29.6.  
**TV POWER TRANSFORMER**—350-0-350 v., 250 m.a., 6.3 v. at 8 a., 5 v. at 3 a., 6.3 v. and 2 v. at 2 a., 87.6.

**L.T. METAL RECTIFIERS**  
12 v. 2 a., 6 v. 2 a., 10/6. 12 v. 3 a., 6 v. 3 a., 12/-, 12 v. 4 a., 6 v. 4 a., 14/-, 12 v. 6 a., 6 v. 6 a., 18/6. 12 v. 1 a., 7.6. All full wave. 6 v. 1 a. C. tapped, 5. -

**PUBLICATIONS**  
Williamson Amplifier, 3.6. Wireless World Valve Data, 3.6. A Modern Crystal Set, 6d. Midgest A.C. Mains Receiver, 6d. BSR, Elac Haynes, 5/-, TV Faults, 5. - How to Make Radio Gadgets, 5. - Send stamped addressed envelope for our surplus list.

**STOP PRESS**—We now have a range of high stability 2 per cent. precision resistors, 1 w. 100 ohms to 2.2 mg. (These are extremely accurate.) Price 1.6 each.

In addition to the above we stock all new proprietary components:—Denco, Allen, Osamor, Wearite, Weymouth, Bulgin, Belling Lee, T.C.C., Hunts, Colvern Lab., Ediswan, Goodmans, Garrard, BSR, Elac, Haynes, Jackson, etc., etc. 5 and 10 w. wire-wound resistors, silver micas, plugs and sockets, instruments, 281 types of T.C.C. condensers, 187 types of Hunt's condensers, wide angle coils and equipment, midgest resistors, Erie resistors, etc., etc.

We make a point of keeping a range of condensers, resistors, etc., for your convenience.  
A Catalogue (250 illustrations, 70 pages) is available price 1/-, NOTE: This does not contain any surplus components or units. Please add sufficient post and packing fee to avoid delay, etc.

# RADIO SERVICING CO.

82, SOUTH EALING ROAD, LONDON, W.5.

Open  
Saturday 6 p.m.  
1 o'clock Wed.

EALING 5737

Next Door to South Ealing Tube—65 Bus.

# HENRY'S


We have over 20,000 American and B.V.A. valves in stock.

ALL VALVES NEW AND GUARANTEED.

**SETS OF VALVES**  
Ten EF50 (Ex-Brand New Units) 5/- each 45/- Set

6K9G, 6K7G, 6Q7G  
5Z4G, 6V6G, (or KT61) ... 37/6 ..  
1R5, 1S5, 1T4, 1S1 (or 3S1 or 3V4) ... 30/- ..  
TP25, HL23 DD, VP23, PEN25 (or QP25) ... 25/- ..  
6K9G, 6K7G, 6Q7G, 25AG, 2Z5 or 25Z6 ... 37/6 ..  
12K8CT, 12K7GT, 12Q7GT, 35Z4GT, 35LGT or 50LGT 37/6 ..  
12S4GT, 12S1K7GT, 12SQTGT, 35Z4GT, 35LGT or 50LGT 37/6 ..  
PX25, KT33C, KT69, GU50 ... 10/6 each  
PX25's Matched Pairs ... 25/- pr.  
TEN 6AM6 (EF91) 30/-

**CRYSTAL MICROPHONE INSERTS**

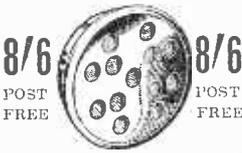

Ideal for tape recording and amplifiers. No matching transformer required.

**RECORDING TAPE (E.P.C.)**

600 feet Reels ... 10/-  
1,200 feet Reels ... 17/6

0Z1A	7/-	6K7G	6/6	12S4GT	8/6	EBC33	8/6	KT81	8/6
1G9	6/6	6K7M	7/6	12SQTGT	8/6	EF35	6/6	KT86	12/6
1R5	8/4	6K8G	9/-	12SQT	7/6	EF39	6/6	GU50	12/6
1S1	8/-	6K8CT	9/-	12SH7	7/6	EK32	6/6	XP2V	4/-
1S5	8/-	6L6G	8/6	12S7T	8/6	EF91	9/-	NH (1.5)	4/-
1T4	8/-	19Z2	11/-	12SK7	8/6	EL32	7/6	VU111	4/-
1A7GT	10/-	8U5	7/6	12SR7	7/6	EF50	8/6	VU133	4/-
1C5	8/-	6U6G	7/6	14A7	8/6	EF50 (Red)	8/6	VU120 A	4/-
1L.N5	8/-	6L7	7/6	25Z9GT	8/6	EF50 (Syl)	10/-	SD9	7/6
2X2	8/-	6N7GT	7/6	25Z5	8/6	EF50 (E.A. Units)	8/6	CV68	6/-
3V4	8/-	8Q7GT	8/6	35Z4GT	8/6	SP2	8/6	VR150 30	8/6
3S1	8/6	8X5GT	8/6	25A6	8/6	VT3	8/6	CK510AN	3/-
5Z4	8/6	6R7	8/6	36L5	8/6	DD12A	8/6	QP25	6/6
6A7G	8/6	6X5G	8/6	50L6GT	8/6	DK40	9/-	ACCPEN	6/6
6A7C	6/6	8S8GT	8/6	42	8/6	UL11	9/-	ACCPEN	6/6
6A8G	7/6	6SH7M	7/6	78	8/6	UY11	9/-	PEN25	12/6
6A8C	8/6	6SK7GT	7/6	33	8/6	1D1	4/-	VR150 30	8/6
6A11J	9/-	6S17GT	9/-	36A4	15/-	8D2	4/-	PEN15	7/6
6B3	7/6	6S8GT	9/-	3001	6/-	9D2	4/-	QP25	6/6
6C4	8/6	6S8GT	10/-	4002	6/-	1D2	10/-	SP61	4/-
6C5GT	5/-	6SS7	7/6	8032	6/-	R4	8/6	SP11	4/-
6C6	6/6	6V6GT	7/6	9001	6/-	D41	5/-	HL23 DD	6/6
6D3	6/6	7C5	8/6	909J	6/-	D42	5/-	V123	6/6
6P8G	8/6	7A7	8/6	931	6/-	D31	5/-	V141	7/6
6QAG	6/6	7C7	8/6	951	6/-	KT2	5/-	U22	8/6
6H6GT	5/-	7H7	8/6	954	6/-	U32	8/6	ATP4	4/-
6H6M	8/6	7B7	8/6	1200A	7/6	U17	10/-	TTP2	8/6
6J5GT	5/-	7S7	10/-	1741	37/6	U19	10/-	TH23	10/-
6J5M	8/6	12A8	7/6	191A	50/-	Y63	8/6	41MP	7/6
6J6	9/-	12C8	7/6	EA5	2/-	P2	4/-	42SP	6/-
6AK5	9/-	12H6	7/6	EA5	2/-	P2	4/-	215SG	4/-
6I7G	6/6	12K7GT	8/6	EF51	8/6	MU11	8/6	MS PENB	4/-
6J7M	8/6	12K8GT	8/6	(VR120)	6/-	PX25	12/6	VT301	7/6
6K6	9/-	12Q7GT	8/6	EB31	3/6	KT33C	10/-		7/6

**R.F. UNITS**

RF24 20-30 mc/s 15/- post free  
RF25 40-50 mc/s 19/6 post free  
RF26 50-65 mc/s 45/- post free  
RF27 65-85 mc/s 45/- post free  
ALL BRAND NEW WITH VALVES

**CATHODE RAY TUBES :**  
VCR7. Guaranteed full picture. 40 - carr. 2/-  
3BP1. Suitable for 'scopes and Tel. 25 - carr. 3/-  
MU - METAL SCREEN for VCR97. 10/-  
VCR139A (ACR10), 35/- Erard new.

**VCR517C Blue and White**  
6 in. Tube. This Tube replaces the VCR97 and VCR517 without alteration and gives a full Blue and White picture. Brand new in original crates. 35 - carr. free.

**No. 38 WALKIE-TALKIE TRANS-RECEIVER** complete with Throat Mike. Phones, Junction Box and aeriad rods in canvas bag. Freq. range 7.4 to 9 mc/s. All units are as new and tested before dispatch. As supplied to Overseas Police Forces. 24.10.0.

**"182A" INDICATOR UNIT** - Complete with VCR517 and Screen. 3-EP50, 4-SP61 and 1-5U4G. 9 w.w. w/controls. Ideal for TV or 'Scope. Brand New (less relay). In original cases. 67/6 plus 7/6 carr.

SEND POSTAGE FOR NEW 1954 COMPREHENSIVE 23-PAGE CATALOGUE : CONTAINING COMPONENTS & EX. GOVT. BARGAINS.

Please add postage up to £1. 1/- : £2 or over 2/-.  
Open Mon.-Fri. 9-6. Thurs. 1 p.m.

5 HARROW ROAD, PADDINGTON, LONDON, W.2

TEL : PADDINGTON 1003/9, 0401.

**NEW!**

## EXPERIMENTAL OUTFITS

### LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM £1 A MONTH

**POST THIS COUPON TODAY**

Please send me your FREE book on Practical Courses:

I am interested in.....

To: E.M.I. INSTITUTES, Dept. 32X, 43 Grove Park Road, Chiswick, London, W.4.

NAME.....

ADDRESS.....

**EXPERIMENTAL OUTFITS:**

**RADIO 1** — A course in basic principles.


**RADIO 2** — Instruction and equipment from which you build a Radio Receiver.

**TELEVISION** — Instruction and equipment for building a Television Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.
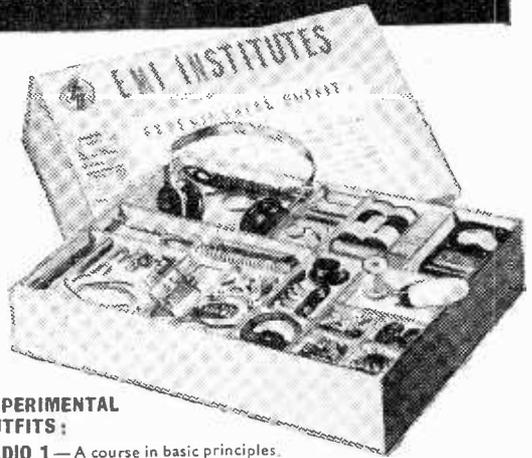
## E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation.



# PREMIER RADIO COMPANY

(Regd.) B. H. MORRIS & CO., (RADIO) LTD.


OPEN TILL  
6 P.M. SATURDAYS

207, EDGWARE ROAD, LONDON, W.2

Telephone:  
AMBASSADOR 4033  
PADDDINGTON 3271/2
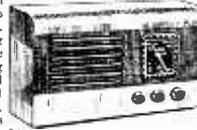
### BUILD A PROFESSIONAL LOOKING RADIO SET AT LESS THAN HALF TO-DAY'S PRICE

We can supply all the parts to help you. Drum (2 1/2 in. diam.), 1/6. (Driving head 1/6. Double pointer 4d. Spring 3d. Nylon Cord (yard) 6d. Dial Front Plate 2/6. Eng. raved Glass Dial, 180-350 and 800-2,200m. With station names, new wavebands ... 1.6  
T.R.F. Coils, 180-350, 800-2,200 metres, pair ... 5/6  
Punched chassis 3-valve plus rectifier T.R.F. Cabinet, Bakelite, in Walnut or Ivory or Wooden in Walnut finish ... 17.6  
Packing and Insurance ... 2/6  
**SEND 1/6 FOR EASY TO FOLLOW POINT-TO-POINT DIAGRAMS AND CIRCUIT DIAGRAM** which shows how YOU can build the Receiver illustrated above.



**THE COMPLETE KIT** to construct a 3-valve plus rectifier T.R.F. Receiver for use on 200-250 v. A.C. mains can be supplied at **£5.15.0**, plus 2/6 packing and carriage.  
Each kit is complete in every detail, nothing has to be made or improvised. Easy to follow point-to-point diagrams are supplied making construction very simple. The Dial is illuminated and the Receiver housed in its Cabinet size 2 1/2 in. x 5 in. x 6 in. presents an attractive appearance. The valve line-up is: 717A—H.P. Pentode, VR110—Detector, ATP4—Output and Metal Rectifier.



Waveband coverage is for the medium and long bands. Choice of 3 Cabinets: Bakelite in Walnut or Ivory or Wooden (Walnut finish).


### PREMIER MAINS TRANSFORMERS

All primaries are tapped for 200-220-250 v. mains 40-100 cycles. All primaries are screened. ALL Ts are centre tapped.

SP175B, 175-0-175, 50 mA., 4 v. @ 1 a. 4 v. @ 2-3 a. ... 25/-  
SP201B, 200-0-200, 120 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a. ... 28/-  
SP250A, 250-0-250, 100 mA., 5 v. @ 2-3 a. @ 2-3 a. @ 2-3 a. ... 29/-  
SP311, 300-0-300, 150 mA., 4 v. @ 1-2 a. 4 v. @ 2-3 a. 4 v. @ 3-6 a. ... 30/-  
SP352, 350-0-350, 150 mA., 5 v., 2-3 a. 6.5 v. @ 2-3 a. 6.5 v. @ 2-3 a. ... 30/-  
SP375A, 375-0-375, 250 mA., 6.3 v. @ 2-3 a. @ 2-3 a. @ 2-3 a. 5 v. @ 2-3 a. ... 55/-  
SP501, 500-0-500, 150 mA., 4 v. @ 2-3 a. ... 47/-  
SP501A, 500-0-500, 150 mA., 5 v. @ 2-3 a. @ 2-3 a. @ 2-3 a. @ 2-3 a. ... 50/-  
SP623A, 625-0-625, 200 mA., 6.3 v. @ 2-3 a. @ 2-3 a. @ 2-3 a. 5 v. @ 2-3 a. ... 67/6  
SP623B, 625-0-625, 200 mA., 6.3 v. @ 4 a. 5 v. @ 2 a. ... 19.6  
350-0-350, 80 mA., 6.3 v. @ 4 a. 5 v. @ 2 a. ... 19.6  
200-250-250, output 3 v., 50 v. @ 2 a. ... 17/6  
Mains Transformer, sub chassis mounted, 350-0-325, 70 mA., 5 v. @ 2 a., 6.3 v. @ 2-5 a. ... 19.6
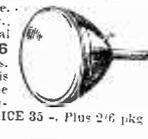
### C.R. TUBES ALL BRAND NEW

VCR 516 9in. Blue picture. Heater Volts 4, Anode 4 Kv. in Manufacturer's original Carton. PRICE **£3.19.6**  
Type 57. pkg., carr., ins.  
VCR 517C 6 1/2 in. picture. This tube is a replacement for the VCR971 and VCR517. Guaranteed full size picture. PRICE 35/- Plus 2/6 pkg. carr. ins.



### VALVES WIDE RANGE OF ALL TYPES

Please write for details.

**WILLIAMSON AMPLIFIER KIT**  
A complete kit of parts for the construction of the latest version of this famous amplifier, complete with valves, output and mains transformers.

**15 Gns.**  
Plus 7/6 pkg., carr. and ins.  
**WILLIAMSON AMPLIFIER TRANSFORMERS** (To specification)  
The Output Transformer 3.8 ohms sec., £4 4/-  
The Mains Transformer, PREMIER SP425A, 23/7/6.

E.H.T. Upright for VCR 97 tube, 2,500 v. 5 mA. 250-2 v., 1-14, 2-0-2 v., 2 a. ... 67/6

### I132A RECEIVER UNITS

11 valve Superhet receiver, covering 100 to 124 Mc, using four V85, two V153, and VR66, VR67, V70, VR54, and VR57 valves. Fitted with Tuning meter, slow-motion drive, R.F. and L.F. Gain Control, etc. (Built-in R.F. amp., frequency changer, oscillator, mod. stab., 3-L.F. amps., E.F.C. Det., First audio and output. Brand New with circuit diagram.  
PRICE 59/6 plus 7/6 pkg., carr., ins.

### CRYSTAL HAND MICROPHONE

High impedance. Excellent frequency response, light weight. Gives very high quality results when used with tape recorder, amplifiers for any type of P.A. equipment.  
Complete with screen lead and plug. Plus 1/6 Pkg. & Carr. Price 29/6.



TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. OVER £1. Please add 1/- for Post; Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

## REAL HIGH FIDELITY at modest cost . . .

### • Manufacturer-to-Consumer policy saves you one-third cost! •

**No. 1 "SYMPHONY" AMPLIFIER** is a 3-channel 5-watt Gram/Radio Amplifier with astonishingly flexible tone-control. You can lift the treble, the bass, or—and here is the unique feature—the middle frequencies to suit your own ear characteristics and the record or radio programme being heard. It is thus possible to arrange the frequency-response of the amplifier to a curve equal and opposite to the resultant curve of the other items in the chain so that what finally registers in the brain is as per original. This flexibility of control is far more important than mere nominal linear response of the amplifier, as the pickup, speaker, etc., are not linear. Independent Scratch-Cut is also fitted and special negative-feedback circuit employed. The Amplifier can accommodate a wide variety of records from old 78's to new LP's. Input is for all types of pickup of 0.2v. output or more and there is full provision (and power) for Radio Tuner. It is available to match 2/3 or 15 ohms speakers. Price £10 gns. (carriage 5/-). Fitted in Portable Steel Cabinet 35/- extra.

**No. 2 "SYMPHONY" AMPLIFIER** as above but with 10-watt Push-Pull triode output and triodes throughout. Woden mains and output transformers and choke. Output tapped 3, 7.5 and 15 ohms. Competes with the most expensive amplifiers on the market yet costs only 15 gns (carriage 5/-). Fitted in Portable Steel Cabinet 2 gns. extra.

**"SYMPHONY" AMPLIFIERS WITH REMOTE CONTROL.** Both the above model Amplifiers are available with all

controls on a separate Control Panel with up to 4 feet flexible cable which simply plugs into the amplifier. Enables the Amplifier proper to be sat in the bottom of a cabinet whilst the controls are mounted conveniently higher up. Extra cost 2 gns.  
**"SYMPHONY" AMPLIFIERS for DECCA MAGNETIC PICKUPS.** Same as Standard models but specially designed for these famous pickups or heads. The pre-stage and bass-compensation network is switchable so that the amplifier can be used with other pickups also. Prices: No. 1 £12/7/6; No. 2 17 gns.; carriage 5/-.  
**GARRARD 3-SPEED GRAM UNIT MODEL "T."** With turnover Magnetic Pickup Head or turnover Astatic Crystal Head £10, post and pack, 2/6.  
**MODEL "TA"** as above but fitted with the latest Radio Show High-Fidelity Aco HGP35 Pickup Heads (one for Std. and one for L.P.). Price £12/3/9, post and pack., 2/6. Heads only 43/- each, post 1/-.  
**MODEL "TB"** As above, but with two separate Decca XMS Heads, £13/7/6, post and pack, 2/6. Or with two separate Aco GPI9 Mk. 2 Heads, £12/10/0. Or with Garrard Head for fibres (78) and Aco GPI9 Mk. 2 for L.P., £12/5/0. Post 2/6.  
**GARRARD 3-SPEED AUTO-CHANGERS** Model RC90 in de luxe rexine-covered Portable Case £23/1/-. Or: fitted with Garrard Magnetic Turnover Head £25/3/5. Or fitted with two separate Aco high-fidelity HGP35 Heads, £27/7/-. Carriage in all cases 7/6.  
**"SYMPHONY" BASS REFLEX CABINET KITS** 30 in. high, consist of

fully-cut 3/4 in. thick, heavy, inert, non-resonant patent acoustic board, deflector plate, felt, all screws, etc., and full instructions. 8 in. speaker, model, 85/7/6; 10 in. speaker model, 97/6; 12 in. speaker model, £57/6. The design is the final result of extensive research in our own laboratory and is your safeguard of optimum acoustic results. Carriage 7/6. Ready built, 10/6 extra, also available fully finished in figured walnut veneer. 8" £10/10/-, 10" £11/-, 12" £11/10/-. Treble baffle to match, 45/-.

**STANDARD PORTABLE RECORD PLAYER CASES**, strongly constructed of 3/4 in. thick ply, rexine-covered, measure internally 15 in. by 12 1/2 in. by 6 1/2 in. Uncut motorboard. Will take any of the Garrard, Decca, B.S.R. or Collaro single-record units. Makes a de luxe Player. Price 57/6. Post 2/6.

**ILLUSTRATED CATALOGUE AND SUPPLEMENT.** Our new catalogue just published will save all those considering the purchase of radio or record-reproducing equipment much time, trouble and money. Send two 2d. stamps for your copy now! Our CHIEF ENGINEER will be pleased to afford TECHNICAL ADVICE where required.


### NORTHERN RADIO SERVICES

16, KINGS COLLEGE RD, LONDON, N.W.3.  
Phone: PR11mrose 8314.  
Tubes: Swiss Cottage and Chalk Farm. Buses: 2, 13, 31, 113, 187.

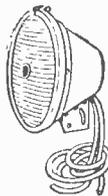**AMPLIFIERS**

57/6. A.C. or A.C./D.C. 3 valve, ideal for pick-ups or microphone. 4 watts output. Post 1/-.  
 77/6. 4 valve, push-pull type. 7 watts output. Post 1/-.  
 9/6. Brand new (ex W.D.), unused. Contains EF36, 2 transformers, 400 ohm relay, volume control, various condensers, resistors, etc. Case measures 5in. x 5in. Post 1/6. Less valve 4/9.

**ICHOBS.** 1/-. Radio and TV. Not engraved. Beautifully designed. Perspex rimmed. Latest type.



**SPOT LIGHTS**

8/9. Butler's new but ex W.D. 8in. dia., 6 1/2in. deep. Post 1/3.

**SIDE LIGHTS.** 1/9. Fitted with Infra-red glass, but easily changed for clear or red. Post 9d.

**CRYSTALS, GERMANIUM.** 1/9. With 3 FREE circuits. Brand new by B.T.H. Long wire ends, post 6d. Also crystal-set coils at 1/-. drawings FREE. Make a set for the children.

**INSULATING TAPE.** Brand new and wrapped. 1 lb. rolls, 1in. wide. List price 3/6, our price 1/6.

**TRANSFORMERS.** Car Radio trans., 5/9. 6 or 12 v. Post 2/-. O.P. trans., 1/9. Salvage, tested. Post 6d. Microphone trans., 3/9. Ex W.D., new condition. In fully shielded case. Post 9d. Pick-up trans., new, ex W.D. Unused. E.M.I. type. Fully shielded. 3/9. Post 1/-.  
**WONEY BACK GUARANTEE**  
**DUKE Electronics**  
 621 ROMFORD RD. LONDON, E.12.  
 Tel: GRA 6677  
 CWO or COD

**WONEY BACK GUARANTEE**  
**DUKE Electronics**  
 621 ROMFORD RD. LONDON, E.12.  
 Tel: GRA 6677  
 CWO or COD

**TV TUBES**

£5 12in., £3 9in. Most makes Picture shown to callers. Seconds, not ex W.D. Carriage and Insurance 15/6 extra.

**SPEAKER CABINETS.** 12/6. Ex British Relay Wireless. 8in. baffles fitted. Volume control position provided. Repolished walnut or oak. Post and packing 2/6.

**MOTORS.** 17/6. 12-24 v., 18 ct. gold brushes. Flexible shaft, as new. ex W.D. Post 2/6.

**ROTARY CONVERTER.** 12/6. Ex W.D., New. Input 24 v., output 200 v., at 50 mA. Post 2/6.

**POWER SUPPLY UNIT.** 47/6. Ex No. 19 set. Z.A. No. 3103. New. 12 v. in., two H.T. output at 275 v., and 500 v. Post 2/6.

**VIBRATORS.** Ex W.D., brand new. Z.A. No. 20709. £5 12/6. Carriage paid.

**BURGLAR ALARMS.** Brand new self-contained unit, made by Truvox. Consists of bell, and trip device mounted in metal cover. Works off 4 volt battery. SPECIAL OFFER, 5/9, post 1/3.

**METERS.** New and boxed. Moving coil movement, giving full and half scale deflection at 100 micro-amps. 2in. scale in 2 1/2in. square mounting. SPECIAL PRICE. 12/9. Post 1/6.

**RECTIFIERS**


3/9. Brand new, selenium. Type I.T. and T. REC. 1. Approx. rating 100 V., 40 mA. Post 6d.  
 8/9. 250 v., 60 mA. Salvage, guaranteed. Also seconds, used but guaranteed. 5/8. Post 1/2.  
 11/9. T.V. type. 300 v., 250 mA. Salvage, guaranteed. Post 1/3.

**AERIAL RODS.** 3d. each. Copper plated steel. Interlock to any length. Post on 12/6.

**MICRO SWITCHES.** Latest American midget. 220 v. 5 amps. Measures 1 1/2 x 1 1/2 x 1 1/2in. 3/6 each, post 4d.


**RADIO-TELEPHONES.** £8/17/6 each. 53-75 Mc/s. Model UF/1. Write for full details.

**RADIOGRAM CHASSIS FROM £10/17/6**

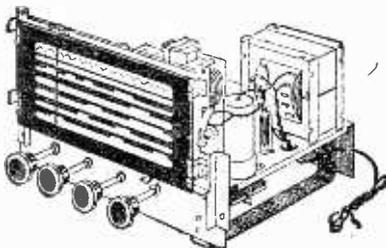

Latest show, brand new. 6 wave-band (illustrated). 15 gms. with 6-position tone control. 3-waveband (B3) at 12 gms., £10/17/6 (X9), similar to above by another manufacturer. All models have 5 valves (latest miniatures), flywheel tuning, neg. feed-back, gain switch, ex. sp. and P.U. sockets. Post 3/6.

SEND STAMP FOR 1954 CATALOGUE

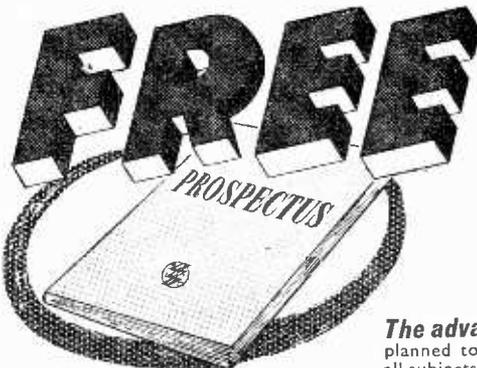

**POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES**

**PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME**

City and Guilds Grouped Certificates in Telecommunications; A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

**The advantages of E.M.I. training.** ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

**NEW LEARN THE PRACTICAL WAY.**  
 With many of our courses we supply actual equipment. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art. etc.

**Courses from £1 per month**

**POST THIS COUPON TODAY**

Send without obligation your FREE book.  
 E.M.I. INSTITUTES, Dept. 32K  
 43 Grove Park Road, London, W.4.  
 Phone: Chiswick 4417/8.

NAME .....  
 ADDRESS .....  
 SUBJECT(S) OF INTEREST .....

**EMI INSTITUTES**  
 The only Postal College which is part of a world-wide Industrial Organisation.

# ...more than you BARGAIN FOR!

The overwhelming reception you get when you fit one of these really powerful units in compact form, is more proof that OSMOR "Q" Range Coilpacks provide quality and performance right out of proportion to their midgest size and modest cost. They have everything that only the highest degree of long practised technical skill can ensure extra selectivity, super sensitivity, adaptability. Size only 1 3/4" x 3 3/4" x 2 1/4", with variable iron-dust cores and polystyrene formers. Built-in trimmers. Tropicalised. Prealigned, receiver-tested and guaranteed. Only 5 connections to make. All types for Mains and Battery superhets, and T.R.F. receivers. Ideal for the

reliable construction of new sets, also for conversion of the 21 Receiver, TR1196, Type 18, War-time Utility and others. Send to-day for particulars!

**SEPARATE COILS** A full range is available for all popular wavebands and purposes. Fully descriptive leaflet and connection data available. Just note these "plus points":  
 Only 1in. high. Packed in damp-proof containers. Variable iron-dust cores. Fitted tags for easy connection. Low loss Polystyrene formers.



4/-  
EACH

## With **OSMOR** Lines—you're on the right lines

A spotlight on another of the "specials" in the OSMOR "Q" coil range.

45 K/c. Tape Recorder Oscillator Coil

### Type QT 8

A centre tapped wave-wound coil as illustrated, for TRUVOX and Similar tape-decks. Single screw fixing. Fitted tags.



7/6  
each

TWO for the Price of ONE!

### The NEW OSMOR CHASSIS CUTTER

An inexpensive but invaluable tool of entirely new design. Cuts two hole sizes with any one reversible punch and die; and can be operated with a spanner or tommy bar. Blanks easily removed. For use on Steel up to 18 s.w.g.; Brass and Dural up to 16 s.w.g. Aluminium and Copper up to 14 s.w.g.



P. Pat. 113241/33

Type	Hole Sizes	Illus.	Price List on Request
1	1in. x 1 1/2in.	}	}
2	1in. x 1 1/4in.		
3	1in. x 1 1/8in.		
4	1 1/2in. x 2in.		

Tommy Bars available

### The OSMOR "JIFFY PUNCH"

for cutting smaller holes neatly and quickly with one blow of a light hammer.



P. Pat. 113241/53

Type	Hole Size	Illus.	Price List on request
A	1/2in.	}	}
B	3/8in.		
C	1/4in.		

For use on Steel up to 20 s.w.g. Brass and Dural up to 18 s.w.g. Aluminium and Copper up to 16 s.w.g.

(Dept. P45) 418, BRIGHTON ROAD, SOUTH CROYDON, SURREY. 'phone CROYdon 5148/9

### DIALS

Type A GLASS DIAL ASSEMBLY (as illus.), measuring 7 in. x 7 in. (9 1/2 in. x 9 1/2 in. overall) mounts in any position on or above the chassis and works with any type of drive. Choice of two 3-colour scales—G1 (L.M.S) or G2 (M.S.S.). Price complete, 24/6. P. & P. 1/6. Pulley assembly for right-angle drive if required, 1/9. Escutcheon 4/6.



### METAL DIALS

Overall size 5 1/2 in. sq., Printed Area 4in. sq. Cream back-ground, 3-colour. Type M1, L.M.S. waves. M2, L.M. waves. M3, M. & 2/S waves. Price 3/6 each. Pointer, 1/6. Drum, Drive, Spring and Cord 6.0. use with both types of dials, 3/2.

**FREE!**

Send 5d. (stamps) for fully descriptive literature including The really efficient 5-valve Superhet Circuit and practical Drawings, 6 valve ditto. 3 valve (plus rectifier) T.R.F. circuit, Battery portable superhet circuit, Coils and Coilpack leaflets, Chassis Cutter leaflet, and full radio and component lists, etc., etc.

We keep stocks of many radio components for use in published circuits, including:

### "PRACTICAL WIRELESS"

Coronet "FOUR," Beginners' Superhet, Modern High Power Amplifier 2; Attaché Case Portable; R1155 Converter; A.C. Band-pass 3; Modern I-Valver; 3-Speed Autogram, etc., etc.

### "WIRELESS WORLD"

No Compromise T.R.F. Tuner Midget Mains Receiver. Sensitive 2-Valve Receiver; Television Converter. (Special coils in cans available), etc., etc.

11.F.s. 465 kc. Permeability-tuned, with flying leads. Standard size 1 1/2 in. x 1 1/2 in. x 3/4 in. For use with OSMOR coilpacks and others, 14/6 pair. PREALIGNED, 1/6 extra.



### OSMOR "JAR-RACK"

Keep those small components—etc., neatly stored yet visible by using an OSMOR "JAR-RACK" (if you're a generous husband you'll buy one or two for your wife's larder, she will appreciate the extra space they make!) Hold: 1 lb. jam jars with or without lids. Easily removed, cannot fall out... just the thing for the tidy "HAM" or Radio Dealer.

Type 1 for wall-fixing, 6/9 each, holds 8 jars. (Jars are not supplied but are easily obtained.) Length 24in., enamelled olive green. Type 2 (as illustrated) for screwing under a shelf, 5/9 each, holds 6 jars. Length 18in., enamelled green. Post and packing, 1/- (either type).

### OSMOR "Station Separator"

Aerial plugs in here	Type	Metres
1	1	141-250
2	2	218-283
3	3	267-341
4	4	319-405
5	5	395-492
6	6	455-567
7	7	1450-1550 known "wave trap"
8	8	410-550k/c

This is a device on the well-known "wave trap" principle, which will reject an undesired signal when inserted in the aerial lead. Easily tuned to eliminate any one Station within the ranges stated. Fitting takes only a few seconds. Sharp tuning is effected by adjusting the brass screw provided. Post 1 Complete with full instructions—nothing to add.

Dear Reader,

We can't mention all our products here but shall be glad to receive your enquiries for Chassis, Tuning Condensers, Switches, Volume Controls, and all other Radio Components. If it's top quality components and a speedy, courteous service you are looking for—try Osmor. We really shall do our best for you.

## Osmor Radio Products Ltd.

(Trade Enquiries Invited)

# Practical Wireless

EVERY MONTH  
VOL. XXX, No. 569, MARCH, 1954

Editor: F. J. CMM

22nd YEAR  
OF ISSUE

## COMMENTS OF THE MONTH

By THE EDITOR

### THE BATTERY CORONET FOUR

THE two versions of the Coronet Four so far produced have been for A.C. and A.C./D.C. We have not overlooked those who are still compelled to operate battery receivers and they will welcome the news that, in next month's issue, we shall commence publication of constructional details for the Battery Coronet Four. It will make use of the same major components, the circuit being virtually unchanged, except for those modifications necessary to adapt it for battery operation. Some of the components will, of course, have different values but readers may like to commence to collect those parts such as the tuning unit, tuning dial, etc., common to the three versions of the Coronet Four. Whilst we are dealing with battery receivers, those still operating the old Fury Four will be glad to know that the modern version of this famous receiver is now in an advanced stage and constructional details will follow the battery version of the Coronet.

### CAR RADIO—NEW M.O.T. LICENCE REGULATION

EVERY application form for a Road Fund licence for a motor car contains a new question which must be answered. Applicants are asked whether their car is equipped with radio and, if so, whether a BBC licence has been obtained for it. This new quiz has been interpreted by some as an unwarranted interference with the liberty of the subject and that the M.O.T. has exceeded its powers in imposing it. Some, indeed, have refused to answer the question, but the M.O.T. say they are well within their rights in insisting upon the question being answered, and that failure to answer the question would entitle them to withhold the licence. We have taken legal advice on the matter and we are informed that it is a case which is arguable at law. We hope, therefore, that a test case will be brought to settle the problem. It is our view that the M.O.T. has arrogated unto itself powers which it does not possess, wide though its existing powers are, to make regulations without reference to Parliament. We must be particularly careful, even in small things, to hang on to the liberties left to us, otherwise we shall become a police state. It is not the business of the licensing authority to act as detectives for the Post Office.

Carried to extremes, one may be asked before a TV licence is installed whether one has a

refrigerator, a vacuum cleaner, electro-medical or other electrical apparatus capable of causing interference with TV, and if so whether such apparatus is fitted with suppressors!

### VACANCIES IN THE R.A.F. RADAR REPORTING UNIT

THE Royal Auxiliary Air Force, No. 3700 (County of London) Radar Reporting Unit for the first time for some years now needs recruits owing to over rapid expansion. This unit is the only one in the London area which trains radar operators. It is a mixed unit, and whilst a knowledge of radar is not necessary a basic idea of radio is most useful in training responsible operators to man the radar defences of this country.

Much of what this unit does is, of course, screened by security, but briefly it trains radar operators and mechanics to operate and maintain the aircraft early warning system so vital to this country's survival in the unhappy event of future hostilities. Both men and women volunteers are required. For evening training periods the pay is now 3s. 6d. to 4s., according to rank for a two-hour period, plus 2d. per mile travelling allowance. Full details are available from The Officer Commanding, No. 3700 (County of London), Radar Reporting Unit, 23, Bridford Mews, London, W.1.

There must be many hundreds of readers of this journal who could help in this important work which is both pleasant and interesting and provides free training of value in civil life.

### OUR BLUEPRINT SERVICE

WE often receive letters from readers complaining that components for some of our receivers are difficult to obtain. During the past two years we have removed a number of receivers from our blueprint list because of this and replaced them with designs of a more modern type. We have here a difficulty, however, because we also receive letters from constructors who have, during the years, accumulated large numbers of components which are no longer made and asking for designs incorporating them. We are, therefore, retaining in our list certain of these older designs, where modification to suit modern components would not occasion any difficulty. In general, whenever we produce a design we also produce a blueprint for it, but we are unable, of course, to control the supply of components. We are always delighted, however, to help readers by suggesting alternatives.—F.J.C.

# ROUND the WORLD of WIRELESS

## Broadcast Receiving Licences

THE following statement shows the approximate number of sound receiving licences issued during the year ended November, 1953. The grand total of sound and television licences was 13,216,644.

Region	Number
London Postal	... 1,670,288
Home Counties	... 1,455,467
Midland	... 1,280,992
North Eastern	... 1,666,324
North Western	... 1,298,559
South Western	... 1,020,934
Wales and Border	... 650,316
Total England and Wales	9,042,880
Scotland	... 1,111,360
Northern Ireland	... 216,177

Grand Total ... 10,370,417

## The Cup Final

WHILE many League clubs are still battling through the early rounds of the F.A. cup competition, the BBC have already reached an agreement with the Football Association to broadcast on sound and television the whole of the final match from Wembley Stadium on May 1.

## "Romance of Radar"

MR. E. J. DOHERTY recently gave a talk to children at the Sir John Cass College, Jewry Street, Aldgate, the subject of his lecture being "The Romance of Radar."

In his demonstrations he used a whistle to show the effect its echoes had on the radar screen of an oscillograph.

## Radar Equipment for French Air Force

THE French Embassy in London have placed an order in excess of £100,000 with E.M.I. Factories Ltd.

This order is on behalf of the French Air Ministry, who will shortly take delivery of 100 Airborne Navigational Aid Equipments, including spares and test gear. These are Rebecca Mark IV medium range homing devices which, used in conjunction with

ground beacons, enable aircraft to be directed accurately to particular sites.

Rebecca Mark IV was developed by E.M.I. in conjunction with the British Ministry of Supply and is produced by E.M.I. Factories Ltd.


## "Laurence Olivier Presents"

BEGINNING on February 2 the Light Programme presents a series of sixteen weekly half-hour programmes under the title

are Orson Welles, who will be heard in Pushkin's "The Queen of Spades"; Sir Ralph Richardson in Conrad's "The Tale"; Michael Redgrave in "The Overcoat," by Gogol, and Robert Donat and Rene Asherson in Stevenson's "The Sire de Maletroit's Door."
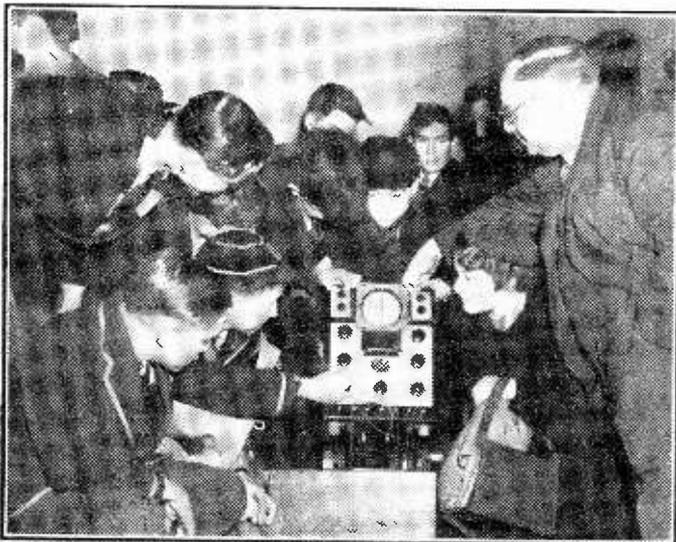
## Himalayan Expedition

IN conjunction with Marconi's Wireless Telegraph Co., Ltd., Auto Diesels Ltd., of Uxbridge,



Mr. Doherty shows his young audience the oscillograph at his recent lecture at the Sir John Cass College, Aldgate.

"Laurence Olivier Presents." These are dramatised short stories in most of which Sir Laurence will appear as actor and host, although, in some cases, the star part may be given to an actor of world renowned fame. The programmes are produced by Harry Alan Towers with special music composed by Sidney Torch. Among the stories which will be heard are "The Purse," by Balzac; Robert Louis Stevenson's "Markheim" and "Dr. Jekyll and Mr. Hyde"; "The Canterville Ghost," by Oscar Wilde; Dickens' "Bardell Versus Pickwick," and H. G. Wells' "The Country of the Blind."

The guest artists so far chosen

are loaning small generating sets for working the portable radio equipment of the Himalayan expedition financed by the *Daily Mail*, which left London early in January. The sets will operate at an altitude of 20,000 ft. in temperatures of -40 deg. to -60 deg. Under these conditions the engine-generator will be required to provide an output of 200 watts at 12-15 volts D.C. and will work direct into the motor-generators on the radio equipment.

## Daventry Transmitter

THE BBC announces that the Third Programme transmitter at Daventry, working on 464

metres (647 kc/s), has now resumed transmission on full power. This will have improved reception, especially for the more distant listeners. Further adjustments to the aerial system are being made to reduce the fading which is experienced at night time in the more remote areas.

**Wireless Saved the Eiffel Tower**

IT is now revealed that the Eiffel Tower would long ago have disappeared had it not been for wireless, despite the fact that for generations it has been one of the greatest attractions of the city.

The 50th anniversary of the wireless station on the Eiffel Tower has recently been celebrated. It was first a purely military post, created in 1903 by General Ferrié, then a captain in the Engineer Corps.

One of the chief workers was not forgotten during the celebrations, Raymond Braillard, chief of the Eiffel Tower station early in the century. He was responsible for the first radio programme.

One of the functions of the Eiffel Tower to-day is to broadcast the midday and other time signals to all shipping crossing the Atlantic.

**B.E.A.M.A. Appointment**

**MR. E. S. WADDINGTON**, F.S.E., A.M.(s.a.), I.Mech.E., M.Inst.W., Associate, I.E.E., Associate (s.a.), I.E.E., of Philips Electrical Limited, Industrial Products Department, has been re-elected vice-chairman of the Arc Welding Plant Section of British Electrical and Allied Manufacturers' Association.

**Appointment of I.P.R.E. Officers**

AT the Annual General Meeting of the Institute of Practical Radio Engineers, Group Captain (Ret.) V. H. Whatling and Mr. C. H. Gardner were elected honorary vice-presidents of the Institute. Mr. C. H. Gardner, a past President, was also appointed liaison officer between the Institute and other interests in the radio industry.

**Change of Address**

THE Glasgow District Office of Edison Swan Electric Co. Ltd. has moved into new premises at 167, St. Vincent Street, Glasgow. Telephone number Central 0687/8/9 as before.

From January 5th, 1954, all

departments, including the Cathode Ray Tube Service Depot (new telephone number Central 2206), have operated from this address.

**Obituary**

WE regret to announce the death of Mr. C. F. Cogswell, A.C.A., secretary of Philips Electrical Limited, on Monday, December 28th, at his home in



*The late Mr. C. F. Cogswell*

Hayes, Kent, after a long illness. Mr. Cogswell, who was 55, leaves a widow and two sons. He joined the company (then known as Philips Lamps Limited) as secretary in December, 1928, and became secretary of many of the Philips Subsidiary Companies and also a director of several of them. During the 1914-18 war he was a pilot in the R.F.C.

Although he always preferred to keep in the background, his unflinching sense of justice and constant preoccupation with the welfare of the employees earned the respect of all of them, and the loyal affection of those who were privileged to know him well.

**Philips Radio Crusade**

ONE hundred dealers, whose efforts to re-establish the popularity of sound radio in their particular area have proved the most outstanding, will sail from London for the Mediterranean on 22nd May as the guests of Philips Electrical Ltd.

This is the date upon which the new 28,000 ton P. & O. Liner S.S. "Arcadia" begins her maiden Mediterranean cruise. Ports of call on this 13-day cruise will be Ceuta, Naples and Barcelona, and the

vessel is due back at Southampton on 4th June.

**Best Radio Student**

THE Bronze Medal of the City and Guilds of London Institute for the best student in Great Britain in the 1953 Intermediate Radio Servicing Examination has been awarded to John McCubbin, 306, Todd Street, Glasgow, E.1.

McCubbin, who is employed by Messrs. James Anderson & Son (Glasgow) Ltd., is a student in the radio technology classes at Allan Glen's Further Education Centre, Glasgow. He is now in the fourth year, studying for the Radio Trades Examination Board, Final Certificate.

This is the first time the bronze medal has gone to Scotland.

**Roadmen Directed by Radio**

BIRMINGHAM Corporation is considering the use of radio as a means of directing Council roadmen from one job to another.

To give the idea a trial, an experimental radio telephone system has been installed in a city engineer's department tower wagon for three months. Roadmen, it is hoped, will be able to move from repair job to repair job much more quickly if given instructions immediately by radio, time being an important factor during bad weather conditions.

It is understood that the only other town to carry out similar tests is Southport in Lancashire.

**B.I.R.E.**

THE following meetings will be held during February, 1954:

London Section.—Wednesday, February 17th, 6.30 p.m., at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1.—"Electronics in Film Making," W. D. Kemp and B. R. Greenhead (High Definition Films Limited).

North-eastern Section.—Wednesday, February 10th, 6 p.m., at Neville Hall, Westgate Road, Newcastle-upon-Tyne.—"Some Aspects of Micro-wave Aerial Design," J. Bilbrough (Microwave Instruments Limited).

West Midlands Section.—Tuesday, February 23rd, 7.15 p.m., at Wolverhampton and Staffordshire Technical College, Wulfruna Street, Wolverhampton. Details from the Local Secretary, Mr. R. A. Lampitt, A.M.Brit.I.R.E., 20, Northfield Grove, Merry Hill, Wolverhampton.

# Modifying the Testmeter Type "E"

DETAILS FOR ADAPTING THE METER TO TEST A.C. VOLTAGES

By B. L. Morley

SOONER or later the amateur constructor feels a real need for a reliable testmeter giving a range of A.C. and D.C. volts, D.C. current and direct measurement of resistance in ohms.

Unfortunately, such instruments are rather expensive and are beyond the pocket of many; but there is a very useful instrument on the ex-Government market which meets most of the requirements mentioned above and is available for a very reasonable price.

This meter is known as the Testmeter Type "E" and has been made by the Avo company.

The instrument can be bought for as little as 49s., and it has the following D.C. ranges:

D.C. volts	D.C. current
0-2 v.	0-20 mA.
0-20 v.	0-100 mA.
0-200 v.	0-200 mA.
0-1,000 v.	0-2 amps.
	0-20 amps.

Resistance readings: 0-10,000 ohms.

It also incorporates a switching device which multiplies the D.C. voltage ranges by two, thus giving 0-4 v., 0-40 v., 0-400 v. and 0-2,000 v.

The instrument uses a small 1.5 v. cell for the resistance range, the battery being housed within the case. A U10 battery can be used for this purpose.

of A.C. volts, and this is probably the reason for its being rather neglected by the amateur.

It is possible to modify it for A.C. voltages by the inclusion of rectifiers in the circuit. Undoubtedly, the best method is to use a bridge rectifying circuit across

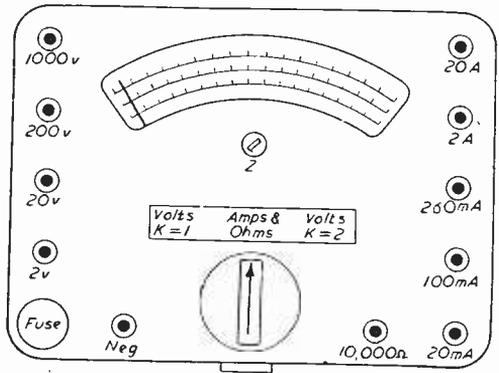


Fig. 1.—Face panel of the meter.

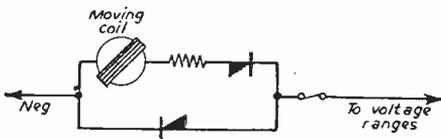


Fig. 2.—Basic circuit.

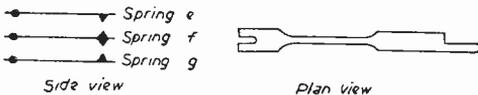


Fig. 3.—Details of the three spring contacts required.

The scale is marked 0-40, 0-20, 0-10 amps and volts, and 0-5,000 ohms, and infinity on the resistance range. (Fig. 1.)

Normal voltage ranges require a total current of 1 mA for full-scale deflection and therefore give a figure of 800 ohms per volt. This figure puts it well above many other meters classified as "inexpensive," and enables quite accurate readings to be taken.

One important feature it does not possess is a range

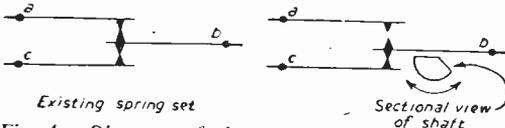


Fig. 4.—Diagram of the existing contacts in the switch.

Fig. 5.—A sectional view of the cam.

the moving coil. However, such a method would involve a complicated switching device and would be rather difficult to mount within the narrow confines of the case.

A more simple solution to the problem was sought which could be undertaken even by the novice with the aid of a few simple tools.

It was decided to use crystal diodes in a straightforward rectifying circuit as shown in Fig. 2, and while some efficiency is lost on the A.C. ranges, it was considered that the simplicity of the scheme coupled with the ease of modification justified the use of the circuit.

The loss in efficiency on the A.C. range is just under 10 per cent.; this means that 1/10th must be added to the reading given by the meter. For example, if the meter reads 200 v. on A.C., then the actual voltage is 220 v. The D.C. readings are unaffected.

The parts necessary for the modification are given below. The only tools needed are a pair of pliers, soldering iron and a 1/16th inch drill.

### PARTS

- Two crystal diodes type CG4 (B.T.H.).
- One spring contact set (see text).
- Odd length of wire, solder and insulation tape.

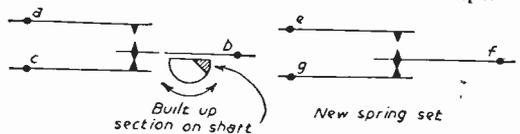


Fig. 6.—Showing the shape of the cam to be built up. Fig. 7.—Diagram of the new spring set arrangement.

The spring contact set may need some explanation. What is required is three spring contacts such as are used in ex-Government and ex-G.P.O. relays. Fig. 3 shows in detail the types required.

**Modifying the Switch**

The major modifications of the meter are to the



Fig. 9.—Mounting the new spring contacts.

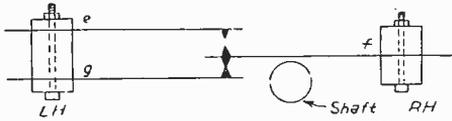


Fig. 10.—Plan of the new springs in position.

switch which is marked "Volts K=1," "Amps and Ohms," "Volts K=2."

Fig. 4 shows a diagram of the existing contacts in the switch. With the switch on "Volts K=1" position the contacts a and b are made. When the switch is in either of the other two positions the contacts b and c are made, the contacts a and b being open.

The operation of the contacts is brought about by the cam formation of the ebonite shaft of the switch.

Fig. 5 shows a sectional view of the cam, the switch being in mid-position (amps and ohms); it will be seen that if the shaft is rotated to the right the cam will operate the spring set so that a and b are closed and b and c are open. This is when the switch is in the "Volts K=1" position.

Further examination will show that if the shaft is rotated to the left instead of to the right, then b and c will remain closed and a and b will stay open.

Now the first requirement of our modification is to arrange that if the shaft is rotated to the left (K=2), then a and b springs close and b and c open.

To do this a cam must be built up so that it is shaped as shown in Fig. 6. The method of doing this will be explained later. It will be observed that under these conditions rotation of the shaft either to the right or to the left will operate the spring set.

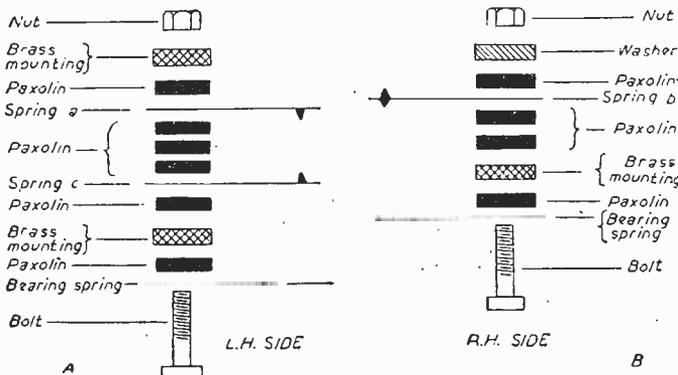


Fig. 8.—Semi-exploded view of the existing spring mounting.

An additional spring set is required made up from the parts mentioned previously. They function in a similar manner by operation of the shaft of the switch.

The new spring set arrangement is shown in Fig. 7. It is required that springs f and g are closed, f and e being open when the switch is in K=1 and also the "Amps and Ohms" position, and for f and e to be

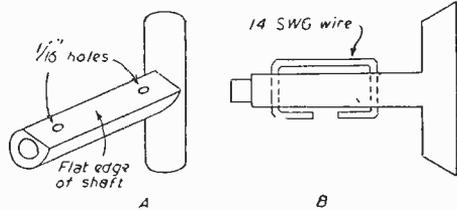


Fig. 11.—Fitting the new "cam."

closed while f and g are open when the switch is in the K=2 position.

A summary of the required spring operations is given below :

Position of switch	Spring set	Position of contacts
K=1	X	a & b made, b & c open
"	Y	f & g made, e & f open
Amps and ohms	X	a and b open, b & c made
"	Y	f & g made, e & f open
K=2	X	a & b made, b & c open
"	Y	f & g open, e & f made

Fig. 8 gives a semi-exploded view of the existing spring set mounting. The new springs are fitted on the same mounting above the existing ones.

Two bolts are provided for holding the springs, and it will be necessary to undo partially the top bolt on both left-hand and right-hand mountings so that the new springs can be slipped in.

An insulating tube is already fitted over the bolt, and each new spring will have to be cut slightly so that it can be inserted between the paxolin leaves, the top edge of the spring being level with the top of the paxolin strips (Fig. 9). The top bolts are then tightened so that the new springs are held firmly in position.

It is important to note that the dome contacts of the springs must be opposite each other, as shown in Fig. 10.

There should be no difficulty in getting access to the spring sets as the back of the meter can be easily removed by undoing the four brass retaining bolts.

It may be found easier to mount the springs if the switch is removed. To do this release the split pin, take off the washer, and then gently pull the switch out from the front of the meter.

**Modifying the Shaft**

The shaft is now modified, to enable the "cam" operations to be made as the pointer of the switch is moved.

It will be found that when the switch is in the K=2 position a flat side of the shaft is facing the moving spring arm. This flat section must be formed into a cam so that spring b and spring f are both operated when the switch is moved to K=2.

The simplest method found was to drill a  $\frac{1}{16}$  in. hole  $\frac{1}{8}$  in. from the two ends, on the flat portion on which it is desired to make the cam. A short piece of 14 s.w.g. wire was then bent and worked through the holes, as shown in Fig. 11. This provided enough lift to operate the springs.

The wire is withdrawn and the shaft reinserted into the meter: the wire can then be reinserted into the holes and bent as shown in the figure. The washer and split pin at the retaining end of the shaft can be replaced. Note that the wire lies along the

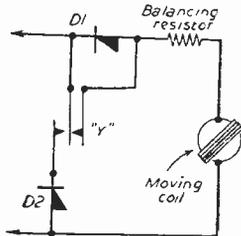


Fig. 12.—The theoretical circuit.

length of the shaft (flat side) so that both springs b and f are lifted when the switch is in K=2 position. The springs can be adjusted so that the contacts are made and broken in accordance with the plan given previously.

**Wiring**

The meter can now be wired. Fig. 12 shows the theoretical circuit. When the switch is in the K=1 or the amps/ohms positions, the diode D1 is short-circuited and the diode D2 is out of circuit. When the switch is operated to the K=2 position the short-circuit is taken off D1 and D2 is connected across the meter.

Fig. 13a shows the part of the circuit wiring which

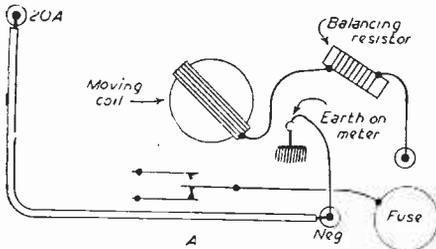


Fig. 13a.—The part of the wiring to be altered.

requires alteration, and Fig. 13b shows the crystals wired in, the heavy lines denoting new wiring, the light lines denoting existing wiring remaining *in situ*.

Only the actual wires associated with the modification are shown.

It will be found that the crystals can be fitted among the other components, as shown in Fig. 14. D2 should be covered with insulation tape, but D1 can be left bare.

All new wires should be insulated. Do not allow the soldering iron to linger when soldering the wires to the diodes or the material enclosing them will be melted.

**Testing**

All that remains to be done is to mark the front of the meter. By the side of K=1 put "D.C." and by the side of K=2 put "A.C."

The meter can now be tested by putting the switch to K=1 and testing a D.C. voltage, and then switching to K=2 and testing an A.C. voltage.

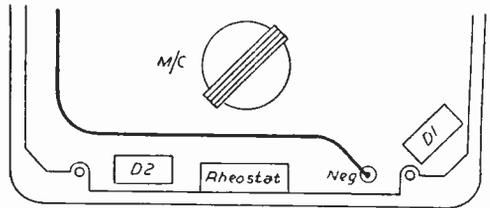


Fig. 14.—The position of the crystals.

Note that the K=2 no longer operates on the D.C. side so that the multiply-by-2 facility has been lost. The meter now reads A.C. instead of D.C. multiplied by 2 and the loss will not be found inconvenient as existing D.C. ranges are adequate for all normal purposes.

Remember that all A.C. voltages are multiplied by 2 so that the full ranges of the meter are now:

D.C. volts	A.C. volts	D.C. mA.	
0-2 v.	0-4 v.	0-20 mA.	0-10,000 ohms
0-20 v.	0-40 v.	0-100 mA.	
0-200 v.	0-400 v.	0-200 mA.	
0-1,000 v.	0-2,000 v.	0-2 amps.	
		0-20 amps.	

Note that the less the current consumed by the meter the greater the accuracy. As an example with the meter under test a more accurate reading was obtained on the 0-2,000 v. scale when testing 350 v. A.C.

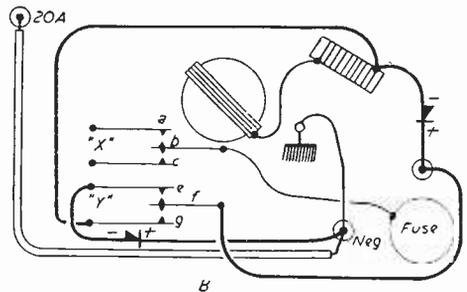


Fig. 13b.—New wiring denoted by heavy lines.

It would be unwise to test A.C. voltages greater than 1,000 v. on the meter because of the possibility of breakdown in the insulation.

**NEWNES RADIO ENGINEER'S POCKET BOOK**

By F. J. CAMM

5/-, or by post 5/3

Obtainable from booksellers, or by post from George Newnes, Ltd. (Book Dept.), Tower House, Southampton Street, Strand, W.C.2.

# Improving SUPERHET

SOME HINTS FOR MODIFYING EXISTING RECEIVER CIRCUITS IN ORDER TO OBTAIN BETTER STABILITY AND IMPROVED RESULTS


By K. C. Ireland, A.R.I.C.S.

**T**HIS article has been written for the beginner and young enthusiast bearing in mind that these amateurs are unlikely to have access to test instruments.

Many newcomers to radio consider the superhet difficult to understand and for this reason adopt the policy of leaving it alone. Do not be deterred, on this account, from experimenting with this type of set, as you will find much that is fascinating.

The writer first became acquainted with the superhet many years ago and gained his introduction to the subject via a publication written by the Editor of this journal. I suggest the beginner obtains a book on the subject and digests the general principles of its functioning. He will realise that there is nothing too difficult either in its fundamentals or construction that the average amateur cannot understand or tackle. He will probably also realise, having once grasped the underlying principles, that the circuit has tremendous potential amplification and that if this could be used to the full a very efficient receiver would result. I do not propose to delve into the theory of the superhet in this article but go right on to the practical side of improving an average type of set of this class.

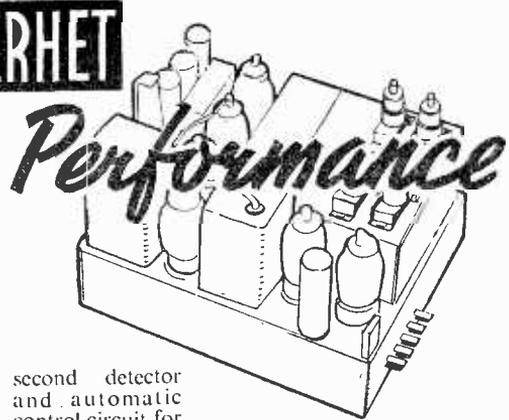Let us take as our example the normal five-valve superhet of commercial design built, say, about 12 years ago. This will have a frequency changer valve, intermediate amplifying stage, second detector and automatic volume control stages in one valve and a pentode output stage. Sometimes there is a first audio A.F. valve incorporated with the



second detector and automatic control circuit for volume control.

We will also assume that our set is operated from A.C. mains, and therefore the fifth valve will be a rectifier to supply smooth D.C. current for the anodes and screens of the amplifying valves.

The designer of such a commercially built set is catering principally for the average listener rather than the enthusiast, and absolute stability and ease of operation are important factors which he must take fully into account when deciding between high efficiency or docility.

One way of achieving this stability is to use ample screening in all the "hot" circuits, and although this may produce the desired result as far as stability is concerned high performance may be sacrificed by providing capacity losses between screens, i.e., earth and leads carrying minute voltages often at high frequencies (I am referring now to short-wave reception).

My policy is to omit screening wherever possible in those stages of the receiver carrying H.F. currents and to obtain stability without sacrificing efficiency, without screens, if this can be arranged. I believe in ample screening on the audio stages where losses from screening do not arise.

Let us assume that our receiver suffers from the following defects:

1. Modulation hum.
2. Overall high hum level.
3. Lack of sensitivity on the short waves.
4. Quality of reproduction is flat and uninteresting.

I will deal with numbers 1 and 2 first and 3 and 4 in a stage-by-stage analysis of what can be tried to improve each valve and its associated circuits.

### Stage-by-Stage Analysis

It will be appreciated that no single set will require all these refinements that I am suggesting but they are based on notes made on a number of sets over the past years.

**1. Modulation hum.** The elimination of this annoying trouble is fortunately a comparatively simple matter. The hum is mostly apparent when tuning through a powerful short-wave transmission and can be recognised by the fact that it is tunable with the signal. It is due to poor voltage regulation modulating the oscillator anode voltage. An almost certain cure is the provision of smoothing at the source of H.T. supply and a .1  $\mu$ F. condenser

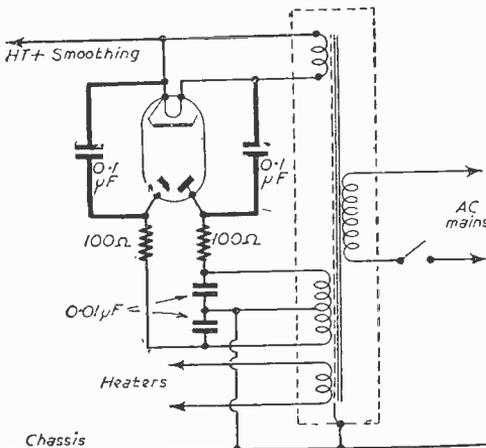


Fig. 1.—The heavy lines show the modifications to be made to avoid modulation hum.

connected across each anode and heater of the rectifier. At the same time include R.F. stoppers and filter condensers as shown in Fig. 1. The latter refinement is not necessary for the removal of modulation hum. The R.F. stoppers should have a resistance of about 100 ohms and be of about 3-watt rating. All condensers should be rated for 1,000 volt working to ensure complete safety for the rectifier.

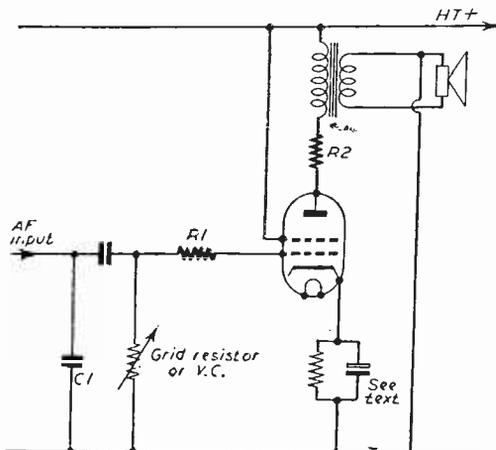


Fig. 2.—H.F. stoppers are shown here at R1 and R2.

2. *Removing hum.* A lot of time can be spent eliminating this trouble. I remember one set which defied all efforts. Increasing the capacity of the smoothing condensers had little effect. Wiring a further choke in series with the existing one only decreased the available voltage to the valves. It had been noticed that even with the volume control at minimum the hum persisted and it was apparent that the mains transformer, rectifying valve, mains energised speaker or output stage must be suspect. Changing the L.S. and rectifier did not improve matters.

It was decided to remove the mains transformer and examine this. On taking off the half-shroud cover it was noticed at once that a number of the top layers of the windings were loose and, in addition, the whole of one winding could be moved slightly on the core. It was now apparent that the hum was caused through magnetic induction vibrating the windings, and this was being transmitted to the speaker in the form of a 50-cycle hum. The transformer was heated in front of the fire and coated with pitch (obtained from old H.T. batteries). Bolts and nuts holding core laminations were tightened in a vice and the transformer refixed in the set mounted on hard rubber washers. As these insulated the core from the chassis, a stout earthing wire was connected to two of the mounting bolts and really well soldered to a large tag bolted through the chassis. No further trouble was experienced.

If the mains transformer, speaker, smoothing choke and condensers are of good quality and adequate size (electrically), there is little risk of hum if only one audio stage is used. There is greater risk with two, and care should be taken amply to decouple the anode of the first stage and all leads to signal grids and volume-control well screened and earthed.

I also believe in earthing the metal frame of the loudspeaker, particularly when a mains energised speaker is used; there is always the danger of stray currents from the field causing puzzling hum.

Now let us see what can be done with regard to faults No. 3, i.e., lack of sensitivity, and No. 4, poor quality reproduction. It is usual to find in sets built about 1940 that the tag group board system of wiring has been used. It obviously helped mass production on a conveyor belt. But if you examine a set wired in this manner you will find that many long leads (a potential source of hum) have to be employed to get from widely separated components to the group board. Examine your set and decide which of the boards can be dispensed with by wiring from point-to-point and then deal with these stage by stage through the set.

Secondly, provide each valve with its own stout earthing connection; this will facilitate the rewiring. It is usually quite a simple matter to use a holding-down bolt as the anchor point.

In Fig. 7 I have shown a typical group board applicable to the R.F. pentode of the I.F. amplifier. Note, even in a simple example, how many less joints there are to solder and the smaller space occupied by the components when point-to-point wiring is adopted and leads are shorter and more direct. Do make certain, however, that the contact between chassis and anchor tag is perfect; a number of poor earthing points will give rise to all manner of curious effects in the superhet.

Thirdly, provide each valve with its own H.T. feed back to the smoothed output from the rectifier. A common coupling point can cause instability. I appreciate that this suggestion may conflict with suggestion No. 2 about short connections, but much can be achieved with a little forethought before wiring. [A separate H.T. line will do much to reduce the risk of interstage interference

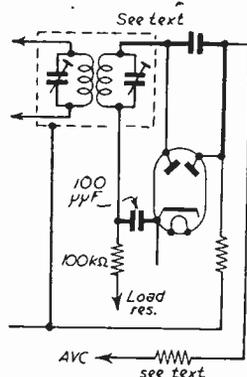


Fig. 3.—I.F. stoppers fitted in the second detector stage.

and break-through. It also has the advantage of enabling the correct voltage to be applied to the electrodes of the valve without upsetting others and to decouple where required, although it is not usual for a simple superhet to require heavy decoupling.

### Stage by Stage

I will now deal with the circuit stage by stage, commencing with the rectifier and working back to the aerial. I feel that it is better for the beginner to carry out modifications in this order as he will be working on familiar ground when dealing with the rectifier and audio stages, as these do not differ from those used in a straight circuit. By working this way he will be better able to assess the value of improvements when he reaches the more intricate circuits, confident that the output stages are stable.

**Rectifier (Fig. 1)**

The suggested refinements for this stage were discussed earlier in these notes and I do not think it necessary to go beyond this. If the speaker is mains energised it will probably be fitted with a hum-bucking coil. Try shorting this out; it may improve the bass response, but generally little will be gained as this coil has a very low resistance.

**Output Stage (Fig. 2)**

The additions that can be made to this circuit are shown in Fig. 2 and consist of a grid-stopper of 5,000 ohms to prevent any residual I.F. voltages from reaching the grid of the output valve and causing instability. R2 can be added as an anode stopper against parasitic oscillation. Remember, this resistance must carry the full anode current and must be capable of doing this without overheating. A resistor rated at three watts will be suitable for most valves likely to be found in the average receiver.

I will not deal with tone controls as it is most likely that the set will be fitted with one, either variable or fixed, and this can remain. C1 can be added as a precaution to by-pass to earth any I.F. voltages which may get as far as this; a value of .0001  $\mu$ F is suitable.

Providing a negative feedback system to the audio stage is very useful in securing stability and for improving general overall response, but there is little scope with only one audio stage of including this. There is insufficient gain available to offset the amount which must be tapped off to provide the feedback voltage. You might care to try omitting the output bias condenser, as by so doing a proportion of the available A.F. voltage is made common to anode and grid circuits which gives in effect a simple feedback system.

Some readers may consider all these refinements unnecessary in a low-power amplifier of simple design, I feel, however, that they are particularly necessary where amplification is confined to one stage, for the reason that on many occasions the set will be working at full gain and, therefore, in its most dangerous condition (in so far as risk of instability is

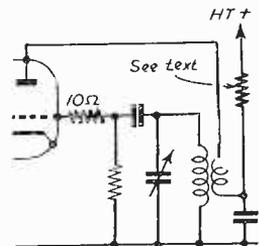


Fig. 5.—Modifying the oscillator section of the frequency changer.

concerned). In a high-gain amplifier, with two or more stages of amplification, the necessity of running at full gain rarely arises.

**Second Detector (Fig. 3)**

This operation is usually performed by one diode of a dual purpose valve, and there is little that can go wrong or that can be improved. There might be a slight risk of instability and if not already fitted try an I.F. stopper of 100,000 ohms in series with the load resistance with a small, fixed condenser of about .0001  $\mu$ F as by-pass to cathode for any I.F.

voltages. No screening should be necessary on this stage in a well-designed set.

**Automatic Volume Control Stage (Fig. 3)**

A.V.C. will aid stability generally over the circuit, but does impose a damping effect. To offset this try reducing the value of the diode coupling condenser (as low as 20 pF can be tried). This will reduce the damping on the I.F. transformers and so increase volume and also improve transient notes. At the same time increase the value of the A.V.C. filter resistance from the usual  $\frac{1}{2}$  megohm or  $\frac{1}{2}$  megohm to

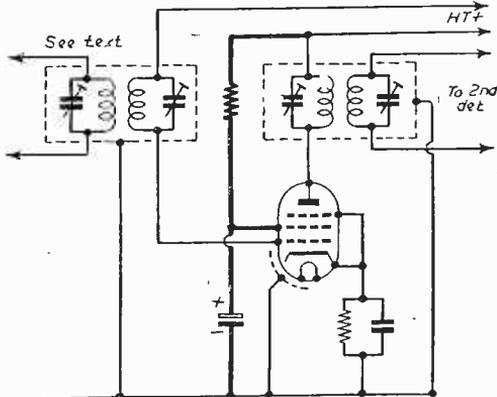


Fig. 4.—Decoupling the screen-grid of an I.F. stage.

1 megohm or even more. This higher value may reduce the overall damping effect of the A.V.C. circuit and thereby increase efficiency.

**Intermediate Frequency Amplifier (Fig. 4)**

This is one of the "hot" circuits. It has two functions to perform: to provide the high amplification of the R.F. signals passed to it from the frequency changer and at the same time control selectivity. Practically all the R.F. amplification is carried out by this valve, and if efficiency is to be maintained care should be taken to see that none is lost or wasted. Some screening is essential here, but let us see what can be done to reduce this to a minimum and at the same time keep the stage stable and under control.

If the valve is metallised I have found it better to scrape this from the glass and completely screen the valve in a metal can, not forgetting to provide a few ventilation holes at top and bottom. My experience is that the metallising tends to flake from the glass under heat and age and provide poor contact and worse screening. Do not enclose a metallised valve in a can; it will over-heat.

Make the flying lead from the I.F. transformer to the signal grid as short as possible, and try an unshielded lead here—there is no reason why a well-designed set should become unmanageable by reason of the omission of the screened lead. If you find screening of this lead is necessary, make the signal carrying wire as thin as possible and thus reduce to a minimum the losses to earth due to the capacity effect of the screen. If the screen of the R.F. pentode is not decoupled try doing so using a 20,000 ohm resistance as a basis for experiment with a .1  $\mu$ F

condenser to earth. The voltage drop caused by the resistor may help stability in this stage.

### Frequency Changer and Oscillator (Fig. 5)

I will deal with these as one stage partly for convenience and also because the beginner will probably think of them that way, as the two stages are combined in one valve performing two distinct operations, i.e., as a generator of local oscillations and as a mixer of these oscillations with the signal oscillations received via the aerial and tuning coils.

If the oscillator section of the valve oscillates too

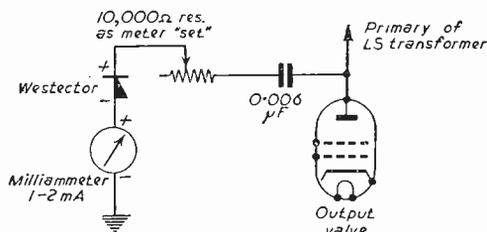


Fig. 6.—A simple output meter.

hard, or not sufficiently, then sensitivity will be poor—so give some attention to the oscillator anode voltage; experiment with a variable resistance in the anode lead and adjust this to give a nice control over the whole of the band. When you are satisfied, the variable resistance can be substituted by a fixed resistor of the correct value. I have found a voltage of about 70-80 suitable for a valve of the TH4 type.

It is as well to provide a small resistor (10 ohms) soldered direct to the oscillator grid pin socket as a precaution against instability on the short waves.

Make certain that all leads to the oscillator section are short and stout enough to be unaffected by vibration. Powerful signals from a loudspeaker situated in the same cabinet as the chassis can start vibrations of sufficient intensity to cause the oscillator to "spill over."

If the lead from the aerial socket to the wave-change switch is screened, omit the screen. This lead will often be carrying small voltages at high frequencies when screening will cause losses. I think it better to rely on the screening provided to the I.F. stage where losses will be lower because the frequencies carried by this stage are lower.

### Simple Alignment and Trimming

Accurate alignment of the superhet is essential for high efficiency, particularly on the short waves. Very often a slight adjustment of the trimmers will make a marked difference to the performance. No elaborate test gear is required, in fact it can be done by ear without any visual aids; but I have found a small output meter on the lines shown in Fig. 7 very useful and interesting. A milliammeter, small Westector, condenser and variable resistance are all that are required. If room can be found on the front of the cabinet these can be wired permanently into circuit and will form a useful tuning indicator.

We will assume that our set is working on all wavebands and that there are no serious defects in its performance. Connect a normal aerial to the set, and with volume at maximum and wave-change switched to medium band tune in a weak but constant signal at the low end of the dial. Adjust

each trimmer on the I.F. transformers for maximum reading on the meter. Commence with the secondary of the second transformer and work back to the primary of the first. Do this two or three times and satisfy yourself that you cannot get a higher reading. When this has been done tackle the oscillator trimmers.

Keep to the medium band and adjust the oscillator trimmer for maximum reading; do this a number of times on the one station, remembering that each adjustment of the trimmer will necessitate retuning the set slightly. Any small discrepancies between the dial reading and the correct frequency of the station can be ignored. Now tune to a known station at the top of the dial and note the reading—if the error approximates to the other you can be reasonably sure that the oscillator tracking is accurate. Try adjusting the trimmer on this new station and note any improvement by reading the meter. Now go back to the first station and check the dial reading. If this has remained steady give a final adjustment here. If the dial settings are not seriously out I am in favour of sacrificing accurate dial readings for maximum results.

The simple procedure outlined above is usually sufficient to provide good signals over the whole of the medium band. Trimming of the long-wave band is similarly carried out. The oscillator trimmer settings, however, will not be so sharp. Endeavour to get a station at each end of the band. This is not always easy as the number of stations is limited, but it is satisfying to know that the set is tracking accurately right through the band.

Alignment of the short-wave band is rather trickier, the oscillator tuning will be very sharp and care must be used not to miss the point of maximum meter reading.

Again use stations of known frequency, one at each end of the dial to commence with, and checking with

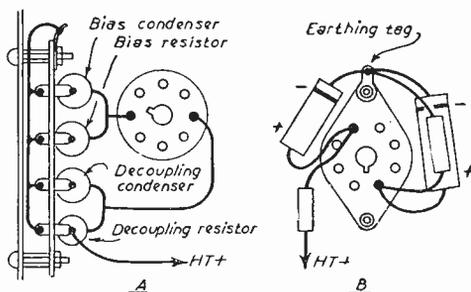


Fig. 7.—Typical wiring arrangements discussed by the author.

other known frequencies between these points. One point to watch on this band: if a station comes in at two points choose the one with the highest frequency (or lowest wavelength). This is because the oscillator frequency is normally arranged higher than the signal frequency in order to keep the frequency ratio between top and bottom of the tuning range as low as possible.

Do not use a metal screwdriver when adjusting any trimmers; the added capacity of metal and fingers will seriously upset your adjustments. I have found a piece of hardwood, chisel-pointed at one end, quite satisfactory.



# TRANSMITTING TOPICS

## MAINS TRANSFORMER MODULATION

By O. J. Russell, B.Sc.(Hons.), (G3BHJ)

THE cost of modulation transformers capable of handling reasonably high audio powers often causes speculative glances to be cast at a mains transformer that the enthusiast may have lying around. Surely if a good transformer could be impressed for modulation service, then the cost of a standard modulation transformer, might be saved? This is often by no means an unimportant consideration, as money saved in one direction may very well be spent on some other necessity. Some notes on possibilities of economy in this direction may accordingly be of interest.

In some cases, first-class results may be obtained with a mains transformer, but it must be clearly understood that there are certain limitations. A great deal depends on the mains transformer design and as modulation conditions are rather different from the original purpose of the transformer, it is as well to pick a really substantial transformer even if only a moderate audio power is to be used. The writer has heard of high-power transmitters using mains transformers successfully, and up to 60 watt carrier levels no trouble should be experienced. Naturally, of course, one would hardly go out and buy a new transformer for such work, it is more suggested as an idea for utilising any "spare" transformers. Resourcefulness and improvisation is the hallmark of the true amateur, and the writer has known of several amateurs successfully employing mains transformers in modulators. The writer himself has often employed this dodge, and to date has never actually purchased a genuine modulation transformer, despite several years of 'phone operation.

The simplest "mains transformer" modulation circuit is shown in Fig. 1. This actually employs the voltage tappings on the mains input side as an auto-transformer. It is, in fact, a somewhat refined version of the Heising system of choke modulation. The refinement consists of the fact that the mains voltage tappings enable some control over the matching of modulator to power amplifier to be effected. Thus, with the usual mains voltage taps of 200v., 220v. and 240v., we can, by selecting tap positions, have stepped up or stepped down ratios of 1 to 1, 1.1 to 1 and 1.2 to 1. This allows of matching load impedances up to 1.44 to 1, either up or down. While it is unlikely that an exact match will be obtained in this way, it does enable a much

better match than the simple Heising choke control system. One attraction is that a faulty transformer, that still has an intact primary, may be used in this way if the fault is only due to a break in some other winding.

Using a single 6L6 as the modulator valve, the writer has used this system to modulate an 807 PA running with inputs of up to 25 watts with good reports. In fact, recently good quality reports were received when using plain Heising modulation without the benefit of the better matching that is available with the tapped system.

It should be noted also that, with this system, it is absolutely necessary to operate the audio modulator valve in Class A. However, it is possible to parallel modulator valves to get increased audio power, but if this is done a difficulty arises. First the H.T. requirements for, perhaps, an 807 valve are for H.T. at some 600 volts or so for the R.F. stage. However, the use of, say, 6L6 valves in the modulator to give some 11 watts of audio requires on reference to the Class A conditions for the 6L6 some 350 volts of H.T. It may be necessary, there-

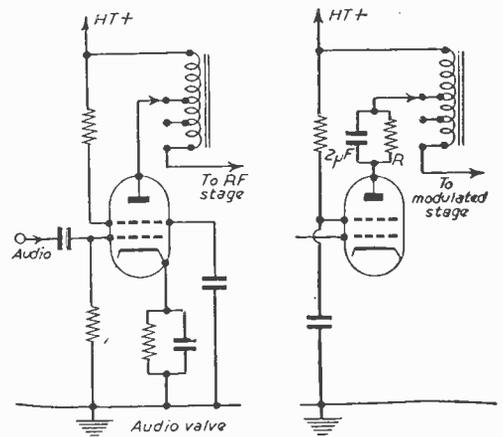


Fig. 1 (left).—The tapped primary winding of a mains transformer enables some degree of load matching to be effected.

Fig. 2 (right).—A dropping resistor R, by-passed by a condenser, enables the modulator valve to run at reduced H.T. volts.

fore, to cut down the H.T. to the 6L6s. This can be done with a resistance by-passed as in Fig. 2.

### Higher Powers

There are more troubles, for there is a second difficulty to consider. If we parallel up the audio valves, we automatically halve the load required if we use two valves, or, if we use three or four audio stages, we shall then require a third or a fourth of

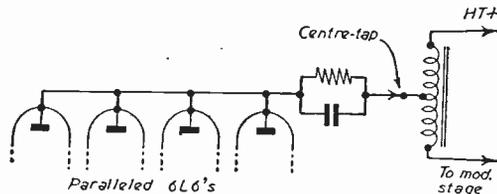


Fig. 3.—Paralleled modulator valves enable higher power output. The centre-tapped high voltage secondary enables a match to be made. A centre-tapped choke is also suitable in such a circuit.

the load resistance required for one valve. We shall have doubled, tripled or even quadrupled the audio power available, so that if matching can be achieved, we shall be able to modulate correspondingly high R.F. inputs to the P.A. stage. Ideally, four paralleled 6L6s would modulate some 90 watts of R.F. input to a P.A. stage. This is so attractive an idea that the arrangement shown in Fig. 3 merits attention. In order to obtain the high step-up necessary to match the low load required by four paralleled audio tubes to the relatively high load of a Class C R.F. stage, the H.T. windings of a centre-tapped H.T. secondary of a mains power transformer are suggested. This will give a voltage step-up of 2 to 1, and hence a load resistance step-up of 4 to 1.

To take a specific case, suppose our P.A. stage is a pair of 807s running at 140 mA. at 600 volts, which is an input of 84 watts. This represents a load impedance of  $\frac{600}{140} \times 1,000\Omega = 4,300\Omega$ . As a single 6L6 gives 11 watts of audio and requires a load impedance of just  $4,200\Omega$ , then four 6L6 tubes paralleled will give 44 watts of audio and require a load of one-fourth of  $4,200\Omega$ . However, by using the step-up circuit of Fig. 3, we can just nicely match four 6L6s into  $4,200\Omega$ . The actual match to a P.A. representing  $4,300\Omega$  will, for all intents and purposes, be perfect. Moreover, 44 watts of audio will ideally modulate an 88 watt P.A., so in fact, this gives us a little audio in hand.

The only snag likely to arise is the possibility of parasitics in the paralleled 6L6s, and this can be dealt with by the use of parasitic suppressing resistors of some  $10,000\Omega$  taken directly to the grid pin of each 6L6 and an anode stopper resistance of  $100\Omega$  in each anode lead. The four tubes will draw some 200 mA., so that a fairly husky power pack is needed. However, with nearly 100 watts input to the P.A., adequate power supplies are needed. Moreover, as the audio valves operate in Class A, the regulation of the power pack can be very poor without affecting results. Furthermore, the inputs can be scaled down for lower powers, and the number of 6L6 tubes in parallel altered, so as to adapt conditions for various R.F. power levels.

It should be noted that the matching difficulty

is the reason why the conventional push-pull arrangement cannot generally be used with a mains transformer. With the usual high voltage secondaries, the effect is a large step-down to the primary side, so that one would not match a conventional P.A. stage of high load resistance value. If a transformer with the usual primary and a centre tapped secondary rated for perhaps 120-0-120 volts is available, this would provide a fair match from a push-pull audio stage to an R.F. stage connected to the primary. However, husky transformers having relatively low voltage centre-tapped secondaries are not very common. Accordingly, methods that have been suggested here are necessary to obtain effective use of the more usual mains transformers as modulation transformers.

A final application of the mains transformer in a practical modulator is also useful. Certain audio amplifiers with high power output are often advertised as surplus. Some of these may have perhaps  $500\Omega$  impedance outputs. It is often possible to match this  $500\Omega$  output with a mains transformer to an R.F. stage. Thus, if the  $500\Omega$  output is connected to the 200 volts primary of a 350-0-350 secondary transformer, this gives a step-up in voltage of 3.5 to 1, and consequently a load step-up of  $(3.5)^2$  to 1, that is, 12.3 to 1. Accordingly, the  $500\Omega$  output is thus matched to  $6,150\Omega$ . In this way, such amplifiers may be matched approximately to a P.A. stage. To quote an example, G2BFQ is one station successfully employing this subterfuge.

Another possibility is the use of a filament winding to match a  $5\Omega$  or  $10\Omega$  output of an audio amplifier to the primary of a mains transformer so that it will

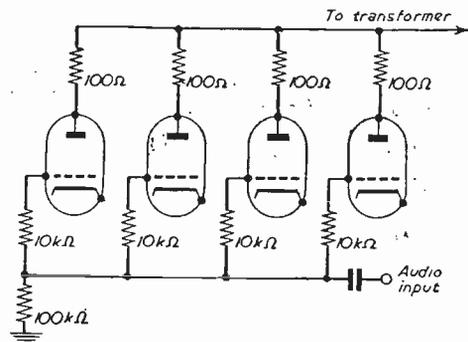


Fig. 4.—Anode and grid stoppers are desirable precautions in the use of paralleled modulator valves.

match into a P.A. stage. Various possibilities exist of this nature, so that a little thought may often enable an efficient modulator to be improvised at little cost. This is often more satisfying than taking the easy way out. Also, in emergency, the ability to improvise speech equipment may be useful when the "genuine" transformer gives up.

### NEWNES SHORT-WAVE MANUAL

6/- or 6/5 by post from

GEORGE NEWNES, LTD. : : Tower  
House, Southampton Street, London, W.C.2.


Constructors everywhere are amazed!

AT THE EXCELLENCE OF  
THE "TELE-VIEWER"

5 CHANNEL TELEVISOR  
A Design of a Complete 12in. SUPERHET T.V. RECEIVER

HUNDREDS SOLD IN 4 MONTHS  
SIMPLE DIAGRAMS MAKE CONSTRUCTION EASY

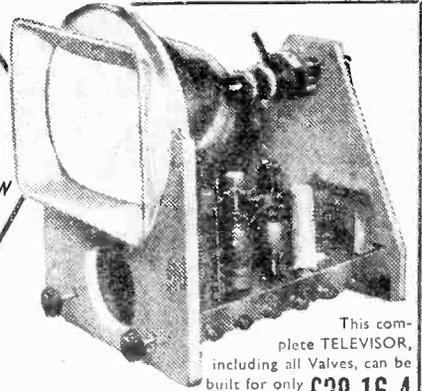PERFECT FRINGE AREA RECEPTION  
BETTER RECEPTION AT HALF COMMERCIAL COST



This complete TELEVISOR, including all Valves, can be built for only £28-16-4 (plus cost of C.R.T.)

- Here are some features which combine to make this such a fine receiver:
- 1. The Superhet circuit easily tuned to any of the five channels, i.e., LONDON, SUTTON COLDFIELD, HOLME MOSS, WENVOE and KIRK-O-SHOTTIS. (The extreme ease of tuning is accomplished by the provision of pre-aligned I.F.T.s.)
  - 2. A lifelike, almost stereoscopic, picture quality made possible by the following factors:
    - (a) Excellent band width of I.F. circuits. (b) A really efficient video amplifier. (c) C.R.T. Grid modulated from low impedance source. (d) High E.H.T. voltage (approx. 10 kv.)
  - 3. The picture brilliance is also much above the average and enables comfortable viewing with normal room lighting or daylight.
  - 4. FIRM picture "HOLD" circuits (Frame-Line) ensure a steady picture, free from bounce or flicker even under the most adverse conditions met with in "fringe" areas and excellent "interlace" ensures the absence of "liney" effect.
  - 5. Negative feedback is used in the audio frequency circuits which provide 2/3 watts of High Quality Sound.
  - 6. Entire receiver built on two chassis units, each measuring 14 1/2 in. x 6 1/2 in. x 3 1/2 in.
  - 7. Rigid C.R.T. mounting enables entire receiver to be safely handled with tube in position.
  - 8. All pre-set controls are mounted on side of chassis enabling all adjustments to be carried out whilst facing the C.R. Tube. As no hire purchase terms are available the receiver can be bought in five separate stages (practical diagrams and circuits are provided for each stage) thus enabling hire purchase interest rates to be avoided.

We can supply A New 12in. C.R.T. at the specially reduced price of £12/19/6 Carr. & Ins. 15/- extra.

Complete set of ASSEMBLY INSTRUCTIONS is now available. price 5/-. The instructions include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. A CABINET WILL ALSO BE AVAILABLE.

**STERN RADIO LTD.**  
109 & 115, FLEET STREET, E.C.4.  
Tel. : CENTRAL 5812-3-4

**OSRAM VALVES**      **G.E.C.**      **CATHODE RAY TUBES**  
**BARRETTERS**  
**GERMANIUM DIODES**

**GUIDE TO NEW TYPES**


The following notes are a convenient reference to new types introduced during recent months

**VALVES**

- Z309** Short base high slope R.F. pentode video amplifier. Slope 15 mA/V. Heater 12.6V 0.3A or 6.3V 0.6A. Base: B9A.
- Z719** Short base R.F. pentode. High input impedance. Slope 7.4 mA/V. Heater 6.3V 0.3A. Base: B9A.
- N329** Output pentode for sound and frame time base output stages in transformerless television receivers. Heater 16.5V 0.3A. Base: B9A.
- U43** Miniature wire-in television EHT rectifier. Indirectly heated P.I.V. 17 kv. Heater 6.3V 90 mA.
- Z729** Low hum, low microphony A.F. pentode for use in early stages of high gain amplifiers. Hum level 1.5 μV. Heater 6.3V 0.2A. Base: B9A.
- N727/6AQ5** Beam tetrode. Heater 6.3V 0.45A. Direct replacement for American 6AQ5. Base: B7G.
- W727/6BA6** Variable-mu R.F. pentode. Heater 6.3V 0.3A. Direct replacement for American 6BA6. Base: B7G.
- X727 6BE6** Heptode. Direct replacement for American 6BE6. Base: B7G.
- U709** Full wave, indirectly heated 350V 150mA rectifier. Heater 6.3V 0.95A. Base: B9A.

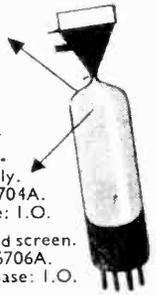**CATHODE RAY TUBES**

- 7201A** 14" rectangular all-glass tube. Flat aluminised screen, Grey filter glass face. Heater 6.3V 0.3A. EHT 10.8-14kv. Base: B12A.
- 7101A** 12" circular tube. Aluminised screen. Maintenance type only. Direct replacement for 6703A and 6704A. Heater 6.3V 0.3A. EHT 6-8kV. Base: I.O.
- 7102A** 12" circular tube. Aluminised screen. Direct replacement for 6705A and 6706A. Heater 6.3V 0.3A. EHT 7-10kV. Base: I.O.



**BARRETTTER**

- 305** Barretter. 0.3A. Voltage range 40-90V. For the regulation of heater current in transformerless television receivers. Base: E.S.

**GERMANIUM DIODE**

- GEX34** High level vision and sound detector and sound noise limiter. Direct replacement for GEX44/1 (discontinued). Colour code red/orange/yellow.

# G2AK This Month's Bargains G2AK

**NOISE LIMITERS.** Plug in type, no rewiring required. Three positions. Brand new in cartons, 15/- each. P. & P. 1/-.

**TEST METER.** 7 ranges as follows: 1.5 v. 3 v. 150 v. 6 ma., 60 ma., 5,000 ohms, 25,000 ohms, 2 1/2 in. Dia. scale M.C. meter. Rotary selector switch, Black bakelite case, 6 x 4 1/2 x 4 1/2, fitted with removable lid, also provision for internal batts, ranges can be easily extended. Bargain Price, 30/- plus 1/6 post.

**MULTI-METER BASIC UNIT.**—400 Microamp. F.S.D., scaled 8 ranges A.C./D.C. volts, HI and LO ohms, complete with rectifier made by Triplett, U.S.A. Only 32/6, post free.

**SHADED POLE MOTORS** for tape recorders or gram. units. With voltage tapping plate 200/250 volts, 3-hole fixing. Our price 12/6 ea. or 21/- pair. Post and pkg. on either, 1/6.

**SPECIAL TRANSFORMER OFFER.**—Pri. 115, 210, 240 v. Secs. 260/260 v. 100 mA., 6.3 v. 3 A. and 6.3 v. 1 A. for 6X5 rectifier. Universal mounting. Few only, 17/6 ea., post free.

**CRYSTAL HAND MICROPHONES.** High quality, very sensitive. Chrome finish, complete with screened lead and standard jack plug. Our price only 25/- ea. Few only.

**Special Valve Offer.** Kit of 4 midget valves 1.4 v., 1 each 1S5, 1R5, 1T4 and 1S4, 30/-, or 8/6 ea. separately. 807's, 12/6 ea. or 2 for 22/6. Most of the 1.4 v. B7G range available at 8/6 ea.

**L.T. Transformers.** 230 v. Primaries. 12 v. 1.5 A., 12/6; 6.3 v. tapped at 4 v. 1.5 A., 8/-; 6.3 v. 2.5 A., 12/6; 6.3 v. 6 A. and 5 v. 4 A., 25/-.

**Twin Feeder,** 300 ohm 150 watt rating, 6d. yd. Minimum quantity, post free, 20 yards; otherwise, P. & P. 1/6.

**Germanium Diodes, B.T.H.,** 2/-; G.E.C., 2/6 ea.

**Deaf-Aid Crystal mike units,** 12/6 ea.

**V.H.F. FANS.** Air space Co-axial Cable, 150 ohm, good to 600 Mc/s; normal price, 3/11 per foot. Our Price, 20 yard coil, £1. Very limited quantity available.

Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

**C. H. YOUNG, G2AK**

All orders: 110 Dale End, Birmingham 4 (CEN 1625) Mail Orders: 102, Holloway Head, Birmingham 1 (MID 3254)

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING

There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

- T/V TECHNOLOGY
- ADVANCED SHORT-WAVE RADIO
- RADIO ENGINEERING
- RADIO SERVICE ENGINEERING
- RADAR
- ELEMENTARY ELECTRONICS

I.C.S. will also coach you for the following examinations:—

**B.I.R.E.;** **P.M.G.** Certificate for Wireless Operators; **Radio Servicing Certificate (R.T.E.B.);** **C. & G.** Telecommunications, etc., etc.

**DON'T DELAY—WRITE TO-DAY** for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful. Reduced terms for H.M. Forces.

Dept. 170D, I.C.S., 71, Kingsway, W.C.2.

**INTERNATIONAL CORRESPONDENCE SCHOOLS,** (Dept. 170D), International Buildings, Kingsway, London, W.C.2.

Please send booklet on.....

Name..... Age.....

(Block letters, please)

Address.....



## SOUTHERN RADIO'S WIRELESS BARGAINS

**TELESONIC 4-Valve Battery Portable.** Complete with Hivac Valves. In Metal Carrying Case. Simply converted to Personal Portable. £2, including conversion Sheet.

**TRANSMITTER RECEIVERS.** Type "38" Mark II. BRAND NEW. Complete with 5 Valves. Headphones. Aerial and Three Microphones. £4/15/- per Set. Less Batteries. **TYPE "18" Mark III.** Complete with all valves but less Batteries and Attachments. **READY FOR USE. £7/17/6** Carriage Paid.

**ONE HUNDRED ONLY Type "38" Mark II TRANS-RECEIVERS.** Used but Complete with all Valves and contained in usual Carrying case. Ready for Use. **LESS ATTACHMENTS. 30/- per Set.**

**RECEIVERS RI09. 8-VALVES.** Vibrator Pack for 6-volts. In Metal Case with built-in Speaker. 1.8 to 8.5 Mcs. **NEW. £7, Carriage Paid.**

**CRYSTAL MONITORS, TYPE 2.** NEW IN TRANSIT CASE. Less Crystals. 8/-.

**BOMBSIGHT COMPUTERS. Ex-R.A.F. NEW.** Contains GYRO, MOTORS, REV. COUNTERS, GEAR WHEELS, ETC., ETC. Ideal for MODEL MAKERS, EXPERIMENTERS, Etc. £3/5/- each.

**LUFBRA HOLE CUTTERS.** Adjustable 1/4 to 3/16 in. Improved High Speed Type. 6/6. For Metal, Plastic, Wood, etc., use.

**RESISTANCES.** 100 Assorted Useful Values. Wire-ended. 12/6 per 100.

**CONDENSERS.** 100 Assorted Values Mica and Tubular, etc. 15/- per 100.

**PLASTIC CASES.** 14in. by 10 1/2 in. Transparent. Ideal for Maps, Photos, Display, etc. 5/6.

**STAR IDENTIFIERS.** Type I A-N. Covers both Hemispheres. In case, 5/6.

**WESTECTORS.** Wx6 and W112, 1/- each.

**CONTACTOR TIME SWITCHES.** Complete in sound-proof case. 2-impulses per sec. Thermostatic Control, 11/6.

**REMOTE CONTACTORS** for use with above, 7/6.

**MORSE TAPPERS.** Ex-Government, 3/6. Heavy Duty Types, 8/6. Complete Morse Practice Sets with Buzzers, 6/9.

ALL LINES PREVIOUSLY ADVERTISED STILL AVAILABLE.

Full List of RADIO BOOKS, 2/6.

**SOUTHERN RADIO SUPPLY LTD.,** 11, LITTLE NEWPORT STREET, LONDON, W.C.2. GERrod 6653.

## VINER'S VALVE BARGAINS

SP61		2/6		SP41	
FA50	2/-	ML6	4/-	2X2	7/-
VR116	2/6	DI	2/6	FB34	2/-
Pen220	2/6	7193	2/6	VU133	2/6
VR91 (EP50)	2/6	HI,2K	2/6	VR21	2/6
		ECC31	7/-	ECC32	7/-
EP36	4/-	EP54	5/-	EP39	5/-
EC52	5/-	EC54	5/-	EK32	6/6
IT4	7/-	IS4	7/-	IS5	7/-
SUIG	8/6	SZ4	8/6	VU39	8/6
U10	9/-	U22	7/6	MU2	8/6
6J5	5/-	6J5(M)	6/-	6SK7	6/-
6K7	6/-	8SN7	10/-	8Q7	8/6
6N7	7/6	6L6	10/-	8Q7	6/-
6X5	7/6	6V6	8/6	6AG5	8/6
12SJ7	4/6	12H6	4/6	APT4	4/-
7475 (Stab)	6/6	5130	5/-	CV188 (Stab)	TT11
RL32	5/6	ML14	8/6	VC73	4/6
954	3/-	CV63	4/6	PEN46	5/-

RS24 RF UNITS RF25

BRAND NEW £1 MINT CONDITION

**CONDENSERS ELECTROLYTIC.** B.E.C. Hunt, etc. W.E. 450 v. wkg. 8 mfd., 2 G. 8+8 mfd., 3 G. 15+16 mfd., 4 G. **DUBBLER DRILLKIT.** 500 v. wkg, 15 mfd., 3 G. 32 mfd., 5 G.

**MAGNETIC PHONE EARPIECES.** R.A.F. type, 2/- each.

**METERS.** M.C. 30, 50, 100, 300, 150, 500, mA., all 5 6 each. 3.5 kv. M.C., 9/6.

**NEONS.** Min. B.C. 230 v., 2/- each.

**COAXIAL CABLE.** 10 1/2 in. dia., 8d. per yard.

**TR9 RECEIVER.** Complete with valves, 15/-, less valves, 6/-.

**CANADIAN 48 SET.** Receiver less valves, £1. Tx. £1. R1225 Receiver chassis 10 mc. I.F., less valves, 6/-.

**NO. 38 SET.** New, complete with valves, 38/-.

## VINER'S (Middlesbrough)

Radio Electrical  
26, EAST STREET, MIDDLESBROUGH  
Tel.: (MID) 3418.



# On Your Wavelength

— By Thermion —

## How Many Battery Set Users ?

I AM glad to learn that this journal proposes to produce a battery version of the Coronet so that all readers may enjoy listening to this latest of our receivers especially designed to celebrate our 21st Birthday. Whenever a blueprint is mooted, the problem always arises as to whether it should be for a mains or a battery receiver; and if the former, whether it should be A.C. or A.C./D.C. We cannot, for obvious reasons, give three blueprints, and the matter is usually decided by the relative number of queries received on the three types. I readily concede that this may not always lead to a right decision. It may be that battery sets are so reliable that there is no occasion to ask a query concerning them.

From trade statistics it is plain that the demand for battery receivers is diminishing as the country becomes more and more within the scope of the grid. However, whichever decision is arrived at, it disappoints those in favour of the other two classes. It proved to be so in the case of the Coronet. We had the usual crop of queries from those unfortunates whose houses are still wired for D.C. and from those others equally unfortunate who are without electricity altogether. Of course, a solution could be found in a mains-battery design, but the disadvantages of that from a constructor's point of view are obvious. In fact, we have had very few enquiries for mains/battery receivers and a comparatively small number for D.C. receivers. It is only fair, however, that all sections of readers should be satisfied and would-be Coronet operators still tied to accumulators and dry batteries will read in the next issue of our battery Coronet Four, which makes use of most of the key components of the mains versions. You may therefore start gathering the parts together.

## The Fury Four

THE new edition of the Fury Four is well advanced and will follow the Coronet. That famous receiver made history. It was announced to the world by means of large-scale advertisements in all the national newspapers and the entire front page of the *Daily Mail* was secured to carry our advertisement relating to the free gift blueprint.

My Fury Four is still operating, although I have made additions and it is now housed in a radiogram cabinet. It was the mains versions, of course, that I built. Except for the change of a valve or so and a condenser, it has given me trouble-free service.

In the early days of this journal we received some complaints that we dealt with too many battery receivers. Now the position is reversed!


## Another Liberty to Go ?

THERE was a lively discussion in the office the other day concerning the new clause in the application form for Road Fund Licences which calls upon the applicant to state whether his car is fitted with a radio set and if so whether he has taken out a licence for it. My contribution to the discussion was that if the M.O.T. is undertaking the work of collecting licence fees for the BBC it could happen that we may not be able to purchase a radio licence unless we can prove we have paid the dog licence. This tendency to take away our liberty by a process of gradualness, so that we scarcely notice it, needs to be watched. We have lost a large number of our liberties since 1939. I have examined the powers conferred upon the Minister of Transport in relation to his authority to make regulations without reference to Parliament and I can find nothing therein which gives him power to act as a tax collector for radio licences, which have nothing whatever to do with the Ministry of Transport. There have been protests from all over the country regarding this matter, but the M.O.T. blandly states that it is acting within its rights without quoting its terms of reference. I for one do not accept their statement and I hope that some motorist will make a test case of it. Here is a case for the R.A.C. and the A.A. It should be no concern of any Government department to probe into the affairs of another. I do not have to tell the milkman before he issues a supply that I have paid my grocer's bill and am therefore a good business risk!
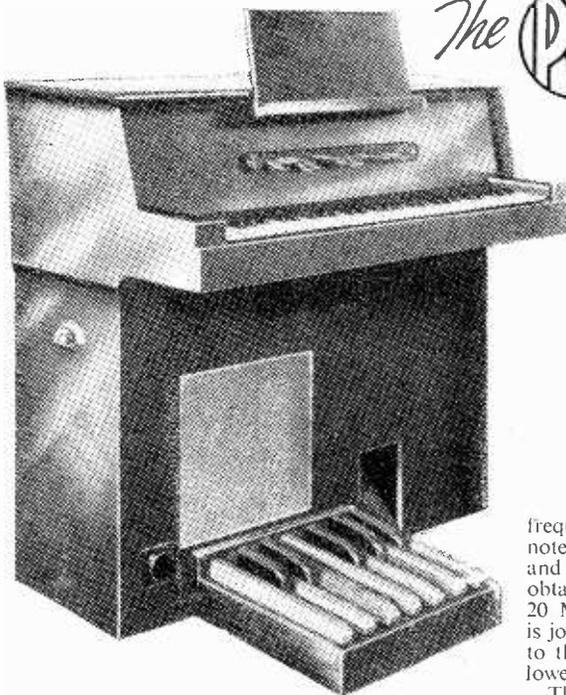
## Should I be Sacked ?

A READER from Northern Scotland, who says that he has taken our journal from its first issue, and who incidentally is in favour of more battery receivers being described herein, in a postscript asks the editor to sack me. Just like that! He disagrees with my views and so would prefer to see me plodding my penurious way as Fleet Street paragraphist instead of, as he thinks, besmirching these pages with views which are unpalatable to him. My fans must rally round. Strange to say, the Big White Chief just tossed the letter over to me with the wry comment that he proposed to do nothing about it and would I like to reply to it? I have done so with the polite suggestion that it has taken him 21 years to express his view! Perhaps the remoteness of his demesne is responsible for the remoteness of his views. How hard is the task of a contributor! If he is outspoken he is too forthright. If he dons the velvet glove he is not sufficiently outspoken. Anyway, the views I have are not formed lightly and I shall continue to express them with the same vigour as hitherto whilst space is allotted to me for that purpose. I do not expect all to agree with me.

Not so long ago a keen Scotch nationalist objected to a criticism in this journal of Lord Reith who, in this reader's eyes, could do no wrong.



The **PW** FULL-COMPASS  
*Electronic*  
**ORGAN**

This Month Details are Given of the  
Connections for the Main Busbars  
and Stop-key Circuits

By W. J. Delaney (G2FMY)

(Continued from page 98 February issue)


frequency of the note C one octave below the lowest note on the keyboard. Only 12 notes are employed, and the correct proportion of the two notes is obtained by linking the two relative notes through a  $20\text{ M}\Omega$  resistor (or two  $10\text{ M}\Omega$  joined in series). It is joined from the top of the group of three resistors to the centre of the two right-hand resistors on the lower 12 as shown in Fig. 25.

The turned-up ends of the lower resistors on the distribution strip have now to be connected together in groups of 12, all the right-hand resistors being joined, then the centre ones, and finally the lower ones. This will leave 14 separate busbars, one of which is the pedal bus (that joined to the right-hand resistors of the lower dozen). The busbars are now to be joined to single busses, the linking being by means of a  $1\text{ M}\Omega$  resistor, which, in conjunction with a small condenser, form click filters. The complete circuit of this part of the instrument is given in Fig. 22. Note carefully that the single octave busbars are shown as viewed from the front of the instrument. If a mistake is made in the wiring of the outside pair of resistors in each group it will not matter much as when the instrument is tested it will readily be apparent and will merely call for a change-over of the 4ft. and 16ft. leads to the stop key switches. The single collector busbars are connected to the stop

AT the end of the keyboard the earthing strip is taken round to the common earthing point.

The leads are then attached to the tops of the groups of resistors on the distribution strip, making certain by means of the colour code that the top note (f1) on each socket is taken to the top octave, and proceeding down the strip so that all the octaves will be of the same coloured leads and the notes will run in correct sequence. The four chassis provide the 60 notes—the top C not being used if one is fitted to the keyboard. Whilst connecting these leads to the distribution strip the pedal circuits may be completed.

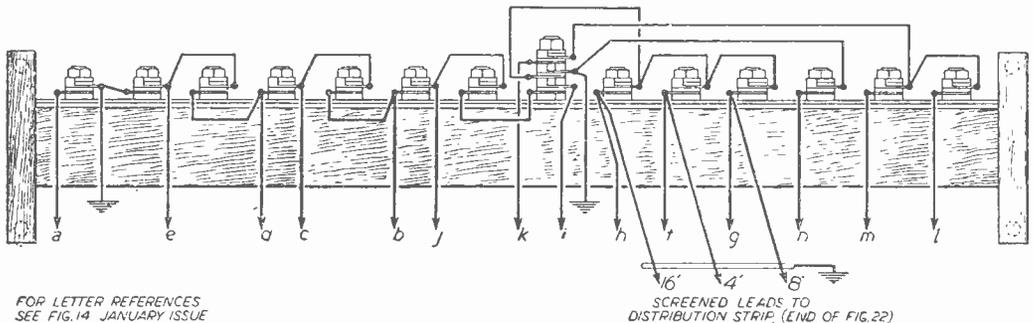For the single octave pedals beat notes are produced by mixing a tone with its fifth. Low C on the strip, for instance, has a frequency of 64 c.p.s., whilst the G above it has a frequency of 96 c.p.s. If these are mixed in the correct proportion the "difference frequency" of 32 c.p.s. is produced, and this is the



FOR LETTER REFERENCES  
SEE FIG. 14 JANUARY ISSUE

SCREENED LEADS TO  
DISTRIBUTION STRIP (END OF FIG. 22)

Fig. 23.—Details of connections to the stop-key switches.

keys, short screened leads being soldered to the centre immediately opposite the relative stops, a hole being made in the vertical screening box to permit the leads to pass through. The linking of the separate octave busses should also be carried out in screened leads to prevent interaction with one another, the screening box round the entire distribution strip taking care of hum.

**Stop Keys**

The stop keys or tone switches should now be wired, the full arrangement being shown in Fig. 23. The small pre-amp should be placed on the cover over the keyboard, and the extending screened multi-cables, shown in Fig. 14 of the January issue, should be joined to the keys as indicated, noting carefully the lettered references. The screening should extend as far as possible, although, due to the spacing between the stop keys, two or three inches of un-screened lead must remain here and there. This will not introduce any trouble, however, and when finally connected the linking wire should be soldered to the screening as near to the stop keys as possible, this linking wire being taken to the "string" switch (extreme left viewed from the rear) and thence across to the screening covering the three screened leads from the distribution strip to the other earthed points on the stop keys, and so on to the earthed socket on the keyboard (socket "A" in Fig. 14). The signal-light holder should be attached to the end of the stop key mount and two leads attached to it, one lead going to the common earthing wire and the other to the other 6.3-volt heater socket. Note that the volume control has an earth connection also, and this should be of the type having a metal

covering which can be soldered, or fitted with a soldering tag, and it should be earthed to the common earthing wire just mentioned. A soldering tag should also be attached to the metal front of the stop key assembly and earthed so that the volume control is screened. With some volume controls it may be found desirable to make a small metal box to fit round over it, but this will only be found on test.

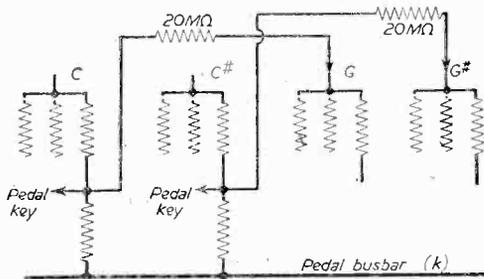


Fig. 25.—Details of circuit for obtaining the pedal notes.

**Hum**

This part of the wiring is very important and is the only point where hum can be introduced. Screening must, therefore, take place at every available exposed point (except for a maximum of three inches which is unavoidable in the case of some wiring to the stop keys), and if possible one single wire should be used between the socket "A" and the pilot lampholder, all screened leads and earth points being taken to it by the shortest possible route. Again, reference is made to the illustration at the foot of page 679 of

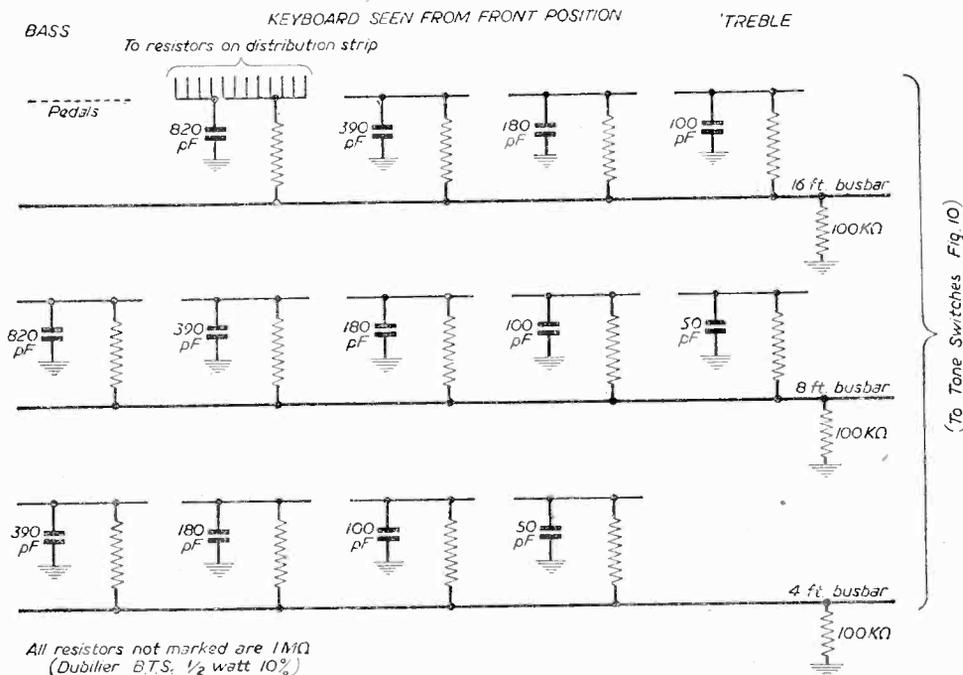


Fig. 22.—Details of main and octave busbar connections—with click filters.

the November issue. A lid covers the box containing the distribution strip but was removed for the purposes of the photograph. On the right of the strip the dozen leads on top carrying the 20 MΩ resistors for the bass section may be seen. The mains plug "X" in Fig. 19 should be attached to about 2ft. of ordinary 5-amp lighting flex and is later inserted in a socket linked with the normal mains supply to the organ. The 1 μF condenser should be of the standard

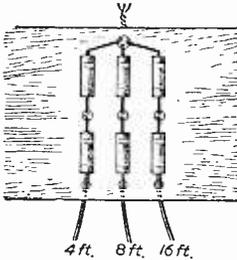


Fig. 24.—Connections to the divider network for the main outputs.

Mansbridge or paper type and should be rated at 500 volt working. A surplus condenser, tested for power factor, etc., was used here.

#### Pedal Clavier

A further 12-way screened lead (or separate screened leads) is now attached to the centre of the pedal resistors on the distribution strip and taken down to a 12-way socket, if the organ is to be portable. If portability is not required the leads may be taken straight down and attached to a Bulgin 12-way socket, type V.H.80, mounted on the front of the main body of the organ as shown in the illustrations. Connections to the 12 pins are arbitrary, but they

must be sorted out when attaching the leads from the actual pedals to the 12-pin plug (Bulgin type P.245) so that each goes to its correct note. A Jones 12-way plug and socket (surplus) were used in the original model to couple the two sections of the 12-way cable as this was intended to be portable. Again, the screening must be earthed. The actual pedals may be made from stout timber to any desired style, the original being 1in. hardwood, hinged with ordinary brass hinges at the front end, and a single strip of 3/4in. phosphor-bronze strip being run right across the rear wooden supporting strip. At the top of each pedal a short contact was screwed so that when in the rest position the contact was touching the long strip. The latter was earthed by soldering a long flex lead taken through the hole in which the expression pedal is mounted, and a clip at the end enables this to be attached to the chassis of the amplifier. This saves using a 13-position socket which is not available (12 connections for the notes plus the earth connection). A strip of felt along the upper strip prevents the pedals from being noisy, and a three-inch spring is mounted in a hole drilled in the lower part of the wooden framework and into each pedal. Any desired form of springing and mounting may be used here, and there is nothing to prevent the constructor from making a radial pedal board similar to the standard and using long pedals if desired. At the moment, however, no increase beyond the 12 notes may be made. Experiments are being undertaken with a view to using a full standard pedal clavier, but the same principle of "beat notes" does not work out, and calls for extra components.

#### Amplifier

All that now remains is the power amplifier, and this will be described in the next and final instalment.

(To be concluded)

## Mullard Filmstrips

A SERIES of twenty filmstrips, covering the two final years in the Ordinary National Certificate Course in Electrical Engineering, has recently been produced by the Technical Publications Department of Mullard, Ltd. It is understood that these filmstrips are the first of their kind to be produced to cover a specific course of study. Although prepared primarily for the assistance of lecturers and teachers in technical training establishments, many of the strips will undoubtedly be found suitable for senior science classes in grammar schools and for staff and apprentice training.

In producing this new series of filmstrips the Mullard Company have had the advice and assistance of an advisory panel composed in the main of teachers in technical colleges. The strips were made and will be distributed by Unicorn Head, Visual Aids, Ltd.

Teaching notes are provided with each strip. In preparing these notes no attempt has been made to produce "potted" text books or to impose on the lecturer any preconceived method of exposition. In general, the notes are confined to brief statements of the principles illustrated and to short descriptions of the apparatus shown.

The majority of the illustrations are either in the

form of diagrams, graphs and the like to illustrate principles and methods of construction; or drawings and photographs showing equipment under construction, examples of modern apparatus and typical installations. In selecting the diagrams, care has been taken to avoid the obvious and those of the simpler type that can be easily drawn on the blackboards.

The complete list of filmstrips in the series are as follows:

- |  |   |
|--|---|
| E21—Magnets and Magnetic Materials.            | E30—Filament Lamps.                                       |
| E22—Secondary Cells.                           | E31—Discharge Lamps.                                      |
| E23—D.C. Machine Construction.                 | E32—Photometry.   |
| E24—Armature Windings.                         | E33—Indicating Instruments—Fundamentals and Construction. |
| E25—Armature Reaction.                         | E34—Energy Meters.  |
| E26—Commutation.                               | E35—Alternating Currents and the Alternator.              |
| E27—D.C. Motors—Applications and Control Gear. | E36—Vectors.  |
| E28—Thermionic Valves—the Diode and Triode.    | E37—Transformers.   |
| E29—The Cathode Ray Oscilloscope.              | E38—Rectification.  |
|  | E39—Power Distribution Systems and Equipment.             |
|  | E40—Underground Power Cables.                             |

# ALIGNMENT OF FRAME AERIALS

OVERCOMING GANGING DIFFICULTIES IN PORTABLE RECEIVERS  
By R. A. Hill

**M**OST constructors appear to regard circuits employing frame aerials as either "stumbling blocks" or causes for spending much time and patience. If the steps described below are followed, with the aid of only an additional .0005 tuning condenser and an external aerial, it is possible to line up the aerial and oscillator sections quickly and accurately.

Although the example used here shows a single-wound oscillator coil and 1R5 battery valve, the principle applies to all types of superhets whether or not they use mains or battery valves, and single or double wound oscillator coils, with or without cores, the cores simply replacing the trimmers.

**Method**

Position the tuning scale and complete all wiring of the circuit with the exception of the aerial section of the frequency changer as shown in Fig. 1. It is assumed that the I.F.T.s are aligned as most types can be purchased aligned ready for use. Solder a 10 kΩ resistor from signal grid to earth, attach the aerial to the grid and switch on. The oscillator section can now be aligned.

On M.W. adjust C1 on H.F. end of scale, using a suitable station, e.g., Light Programme, 247 metres, and then C3 to position North Regional or a similar station on the other side of the scale. Repeat until no further adjustment is necessary and the stations are in their correct positions.

Do the same for the L.W., using C2 and C4. Most constructors obtain the best results on 1,500 metres, as this is usually all that is required of the L.W. especially for small portables.

**Aerial Section Alignment**

Now we come to the second stage, the alignment of the aerial section.

From the writer's experience, rectangular-shaped frames proved more successful than square or round shapes. The number of turns depends upon the gauge of wire and size of frame, but for M.W. wind on an average size former about 20 turns of 28 gauge wire, remembering that it is easier to take off than add on.

Remove 10 kΩ resistor used in previous stage and connect frame in its usual place, leaving the aerial connected to the grid, not forgetting to connect the appropriate section of the 2-gang tuning condenser, as shown in Fig. 2. Then disconnect the oscillator section of the tuning condenser, substitute the .0005 mentioned before (this gives independent control over the two circuits) and tune with this condenser any station on the waveband. Swing gang condenser to give maximum volume. When the frame aerial is correctly adjusted, maximum volume will be obtained when the scale pointer indicates the station tuned. If maximum volume is obtained with pointer at higher frequency, then turns will have to be removed and vice versa.

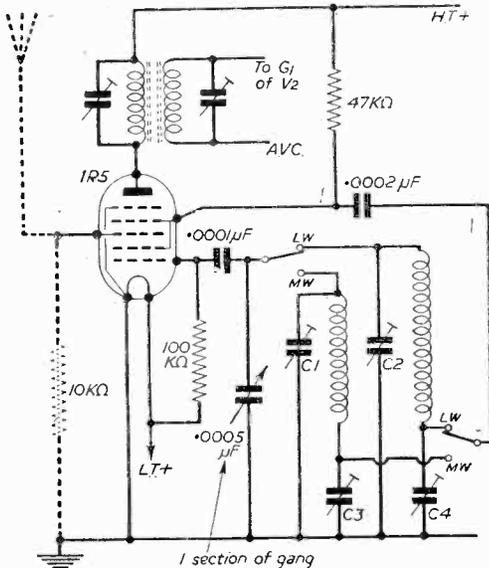


Fig. 1.—Alignment of the oscillator stage.

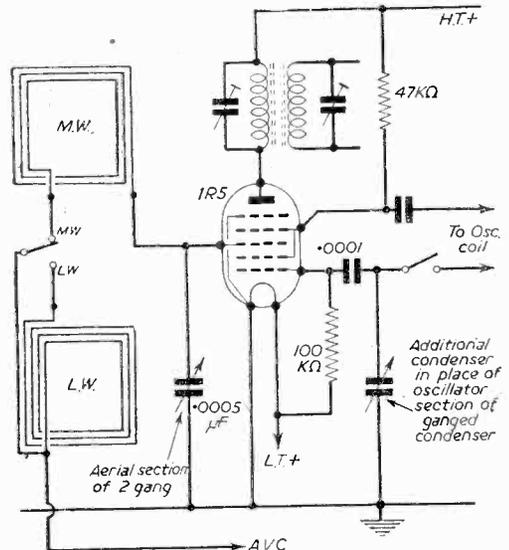


Fig. 2.—Tuning of the frame aerial.

### Avoid Stray Capacity

Stray capacity must be avoided by placing the frame aerial in the position it will finally occupy and keep the connecting leads short. Remove the external aerial and, remembering that the frame aerial is directional, check several stations to see that maximum volume is obtained in the correct positions.

Finally, remove single condenser and reconnect gang section and the set will be aligned. A very slight adjustment of the trimmers C1 and C3 may be necessary when all connections are made to obtain maximum volume, but care must be taken not to adjust incorrectly.

### Summary

In conclusion, although the preceding instructions seem lengthy, it is hoped that it can be followed by the beginners in wireless who are making their first portable. For the more advanced constructors, I have tabled in note form below the various steps:

1. Solder 10 k $\Omega$  resistor from signal grid to earth of F.C. and attach aerial.

2. On M.W., adjust C1 and C3 to give correct positions of stations.

3. Replace oscillator section of tuning condenser by separate tuning condenser, remove 10 k $\Omega$  resistor, and connect frame aerial, tuning condenser (as original circuit, but add external aerial). Tune a station with oscillator condenser and adjust frame aerial turns to give maximum volume when this station is indicated on tuning scale. Remove aerial when nearly correct and work on pick-up of frame aerial. Repeat for L.W.

4. Remove separate condenser and reconnect as with original circuit, adjusting C1 and C3 for final adjustments if necessary.

To those who wonder why an external aerial is necessary, the reason is that until the two circuits are nearly matched, the pick-up is so small that it makes it very difficult to hear the station being tuned. Home Service stations are easily identified when different regional items are being broadcast; a point which can be misleading especially at a time like this.

## Obtaining Bias in A.C./D.C. Amplifiers

A Novel Way of Obtaining Bias in High Power or Medium Power Amplifiers where the H.T. Voltage is Limited to That of the Mains

By J. S. Kendall

**D**.C. mains supplies to universal amplifiers present a problem that for a long time has been rather difficult to overcome. It is that of obtaining bias and yet keeping up the H.T. voltage. It must be remembered that there are voltages dropped across the rectifier and the smoothing choke. The design of highly efficient British valves for the output circuit have both increased the power output and reduced the bias voltage required. An example of this is the Mullard UL41 which gives 1.35 watts output with 100 volts anode and screen but requires only -5.7 volts bias. On the other hand, the International type 25A6 gives only 1 watt with the same anode voltage. This valve, however, requires a bias of -16 volts. Again the first valve requires 29 mA, whilst the second requires 22 mA, meaning that whilst less bias is required for the first valve the voltage dropped across the rectifier and the smoothing choke is increased. We would therefore seem to be moving in a vicious circle.

One way of getting the power from universal circuits has been by placing the output valves in parallel. Referring back again to the manufacturer's figures, the output of a pair of UL41 in push-pull with 170 volts anode and screen will give 9.0 watts for 10 per cent. distortion, but if the voltage is raised to 200 volts the output will be increased to 12.5 watts. In the first of these two figures the bias is taking 12 volts of the voltage applied, whilst in the second it is 15 volts. If this bias voltage did not have to be taken out of the cathode circuit there could be a still higher power output. One obvious way to get over this would be to use batteries, but if these are not in first class condition they will soon cause the output valves to be damaged due to passing an excessive anode current.

One method, however, that is now coming into use is the use of a D.C. supply rectified from an R.F. oscillator. Mullard Ltd. have recently published a new circuit in which an H.F. oscillator of 2 Mc/s is used. The circuit, whilst being quite useful, is not easily adapted for various other circuits. A suitable

circuit is given in Fig. 1, in which the oscillator valve is a UL41, with a UY41 for the rectifier, a 7475 being used as a reference voltage.

The coil used is a Wearite P type B.F.O. which will oscillate at about 500 kc/s with a 100 pF condenser shunting it; this latter component should be of high quality as it has to stand quite a high voltage. The potentiometer in the screen circuit is to reduce the drive power of the valve; on 110 mains the full voltage will be required, whilst on 230 volts the power will have to be reduced so that not too much power is wasted. The adjustment of the oscillator is correct when the 7475 stabiliser tube is glowing steadily.

The required output voltage can be obtained then by calibrating the potentiometer direct in volts, which can be done quite simply with a linear wire-wound pot. Each volt takes about 3 degrees, the complete 240 degrees of rotation giving 50 volts—the 50K fixed resistor will have to be a close tolerance resistor as 50K is not a preferred value.

The unit is one that is quite useful in the districts where the mains are D.C., and if required can be made up as a separate unit.


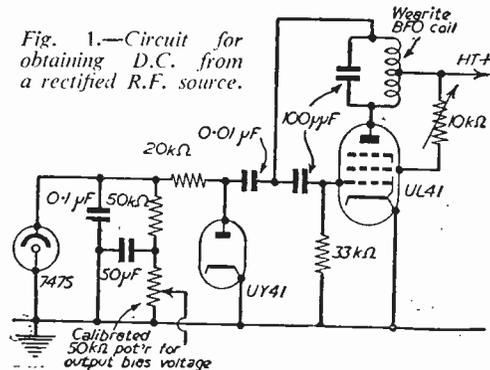


Fig. 1.—Circuit for obtaining D.C. from a rectified R.F. source.
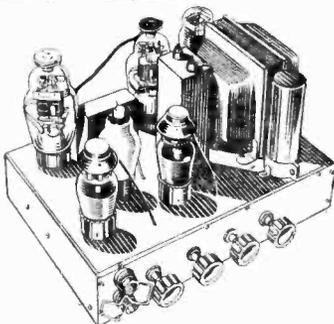
### R.S.G. 25 WATT QUALITY AMPLIFIER

We firmly believe our All "Push-Pull" Quality Amplifier to be by far the best value in amplifiers offered to-day. The volume of its high fidelity reproduction is completely controllable, from the sound of a quiet intimate conversation to the full, glorious volume of a great orchestra. Its sensitivity is so high that in areas of fair signal strength it can be operated straight from a crystal receiver. Entirely suitable for standard or long playing records in small homes or in large auditoriums. For electronic organ or guitar or for garden parties or dance bands. The kit is complete to the last detail, and includes easy to follow point-to-point wiring diagrams.

Outputs for 3 or 15 ohm speakers. Twin volume controls with twin input sockets allow SIMULTANEOUS INPUTS for BOTH MICROPHONE and GRAM, or TAPE and RADIO. SEPARATE BASS and TREBLE CONTROLS, giving both LIFT and CUT. FOUR NEGATIVE FEEDBACK



LOOPS with 15 db in the main loop from output transformer to voltage amplifier. Frequency response +3 db. 50-20,000 c.p.s. HUM and DISTORTION LESS THAN 0.5

per cent. measured at 10 watts, comparing favourably with most highest priced amplifiers. Six B.V.A. valves. Marconi/Osram KT series output valves. A.C. only. 200-250 v. 50 c.c.s. input. 420 v. H.T. LINE. Paper reservoir condenser. Compact chassis. Matched components. Size 14 x 10 x 9in. Available in kit form at the amazingly low price of 9 guineas. Plus carriage 5/- . Or ready for use 50/- extra.

### R.S.G. 8-10 WATT "PUSH-PULL" HIGH-FIDELITY AMPLIFIER A3.

Complete with integral Pre-amp. Tone control stage (as All amplifier), using negative feedback, giving humproof individual bass and treble lift and cut tone control. SIX Negative Feedback Loops. Completely negligible hum and distortion. Frequency response +3 db. 20-20,000 c.p.s. Two independently controlled inputs. Six B.V.A. valve. A.C. mains 200-250 v. input only. Outputs for 3 or 15 ohm speakers. Kit of parts complete in every detail. £7/19/6. plus 5/- carriage, or ready for use. 45/- extra.

**BATTERY SET CONVERTER KIT.** All parts for converting any type of Battery receiver to All Mains. A.C. 200-250 v 50 c.c.s. Kit will supply fully smoothed H.T. of 120 v 90 or 60 v at up to 40 mA, and fully smoothed L.T. of 2 v at 0.4 to 1 a. Price, complete with circuit, wiring diagrams and instructions, only 49/6. Or ready to use. 7/9 extra.

**PERSONAL SET BATTERY SUPERSEDER KIT.** A complete set of parts for construction of a Unit (boxed in Metal Case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v 50 c.c.s. Outputs 90 v 10 mA and 1.4 v 250 mA, fully smoothed. For 4-valve receivers. Price complete with circuit. Only 35/9. Or ready for use. 42/6. Size of unit 5 x 4 x 1 1/2 ins.

**H.T. ELIMINATOR AND TRICKLE CHARGER KIT.** Input 200-250 v A.C. Output 120 v 40 mA, fully smoothed, and rectified supply to charge 2 v acc. Price with steel case and circuit. 29/6. Or ready for use. 7/9 extra.

**BATTERY CHARGER KITS**  
For mains 200-250 v 50 c.c.s.  
To charge 6 v acc. at 2 a. 25/6.  
To charge 6 or 12 v acc. at 4 a. 21/6.  
To charge 6 or 12 v acc. at 4 a. 49/9.  
Above consist of Transformer, full wave rectifier, fuses, fuseholders and steel case. Any type assembled and tested. 6/9 extra.

#### EX-GOVT VALVES (NEW)

Each	Each	Each
JT1 8/9	6SK7Met 7/9	25Z4 9/6
1R5 8/9	6SJ7Met 7/9	25LGT 9/6
1S5 8/9	6X4G 9/11	32V4GT 10/6
3S4 9/9	6SN7CT 11/9	38LGT 9/11
5Y3C 9/9	6V6G 8/9	UY41 8/11
5U4G 10/6	6V6GT 8/9	EF36 4/11
5Z4G 9/6	6X5GT 8/9	EB91 8/9
6AL5 9/9	8D2 2/11	MU11 9/6
6F6G 7/8	8Y7 6/11	BF91 9/9
6AM6 9/9	9D2 2/11	MU11 9/6
6J5G 5/11	12A6 7/9	MS/Pen 5/9
6J7G 7/6	12KTGT 10/6	SP4 5/9
6KTG 6/11	12Q7GT 10/6	S261 2/9
6K6G 11/9	15D2T 5/9	VU120 2/11

**ELECTROLYTICS** (Current production. Not ex-Govt.)

Tubular Types		16/UF 450 v		2/9	
8/UF 350 v	1/9	24/UF 350 v	2/11	32/UF 350 v	2/11
8/UF 450 v	1/11	32/UF 350 v	2/11	32/mfd 450 v	4/9
8/UF 500 v	2/9	32/UF 500 v	6/11	40/UF 450 v	4/11
16/UF 350 v	2/3	40/UF 450 v	4/9	8/UF 350 v	3/9
16/UF 450 v	2/9	8/UF 450 v	3/9	8-16/UF 450 v	3/11
24/UF 350 v	3/6	8-16/UF 450 v	4/6	16-16/UF 450 v	4/11
32/UF 350 v	3/6	16-32/UF 350 v	4/11	32-32/UF 350 v	4/11
32/UF 25 v	3/6	32-32/UF 450 v	5/11		
50/UF 12 v	1/3				
50/UF 50 v	2/3				

**WILLIAMSON AMPLIFIER KIT.** All parts to Author's spec. Only 14 guineas.

**A PUSH-PULL 3-4 watt HIGH-GAIN AMPLIFIER FOR £3 12/6.** For mains input 200-250 v 50 c.c.s. Complete kit of parts including circuit, point to point wiring diagram, and instructions. Amplifier can be used with any type of Feeder Unit or Pick-up. This is not A.C. D.C. with "live" chassis, but A.C. only with 400-0-400 v trans. Output is for 2-3 ohm speaker. (We can supply a suitable 10in. unit by Rola at 29/6.) The amplifier can be supplied ready for use for 25/- extra. Carv. 9/6. Full descriptive leaflet. 7d.

**BRAND NEW COLLARO 3 SPEED AUTOMATIC RECORD CHANGERS.** Type RC3321, complete with P.U. (2 plug-in crystal heads). Mains input 200-250 v. Limited number at only 29/15/0.

**COLLARO SINGLE SPEED RECORD PLAYER UNITS.** Type AC914, with Crystal Pick-up. Mains Input 200-250 v A.C. Brand New. Only £3.19.6. plus carr 5/-

**P.M. SPEAKERS.** All 2-3 ohms. 6in. Goodmans. 14/11. 8in. Plessey. 15/9. 10in. Plessey. 18/6. 10in. R.A. 29/6. 10in. Rola with trans. 31/6. 12in. Truxov. 49/9.

### R.S.G. MAINS TRANSFORMERS (FULLY GUARANTEED)

Intertraced and impregnated. Primaries 200-250-250 v 50 c.c.s. Screened TOP SHROUDED DROO THROUGH

250-0-250 70 mA. 6.3 v 2.5 a	12/11
250-0-250 70 mA. 6.3 v 2 a, 5 v 2 a	14/11
350-0-350 80 mA. 6.3 v 2 a, 5 v 2 a	17/9
350-0-350 80 mA. 6.3 v 2 a, 4 v 2.5 a	14/11
250-0-250 100 mA. 6.3 v 4 a, 5 v 3 a	23/9
300-0-300 100 mA. 6.3 v 4 v 4 a, c.t. 0-4-5 v 3 a	23/9
350-0-350 100 mA. 6.3 v 4 v 4 a, c.t. 0-4-5 v 3 a	23/9
330-0-330 150 mA. 6.3 v 4 a, 5 v 3 a	29/11
350-0-350 150 mA. 6.3 v 2 a, 6.3 v 2 a, 5 v 3 a	29/11

**FULLY SHROUDED UPRIGHT**

250-0-250 v 60 mA. 6.3 v 2 a, 5 v 2 a. Midget type 21-3-3in.	18/9
350-0-350 v 70 mA. 6.3 v 2 a, 5 v 2 a	18/9
250-0-250 v 100 mA. 0-4-6.3 v 4 a. 0-4-5 v 3 a	25/9
250-0-250 v 100 mA. 6.3 v 6 a, 5 v 3 a. For R1355 conversion	29/9
300-0-300 v 100 mA. 0-4-6.3 v 4 a. 0-4-5 v 3 a	25/9
350-0-350 v 100 mA. 0-4-6.3 v 4 a. 0-4-5 v 3 a	25/9
350-0-350 v 150 mA. 6.3 v 4 a, 4 v 3 a	33/9
350-0-350 v 150 mA. 6.3 v 6 a, 6.3 v 3 a, 5 v 3 a	45/9
350-0-350 v 250 mA. 6.3 v 6 a, 4 v 2 a, 0-2-6 v 2 a, 4 v 3 a, for Elc-tronics Frnz. Television	67/6
425-0-425 v 200 mA. 6.3 v 4 v 4 a, C.T. 6.3 v 4 v 4 a C.T. 0-4-5 v 3 a. Suitable Williamson Amplifier, e.c.c.	49/9
Economy Quality Amplifier type	49/9
450-0-450 v 250 mA. 6.3 v 6 a, 6.3 v 6 a, 5 v 3 a	65/9

**ELIMINATOR TRANSFORMERS**  
Primaries 200-250 v 50 c.c.s. 120 v 40 mA 7/9  
90 v 10 mA. 8-0-8 v 250 mA. ... 8/11

**EX-GOVT SMOOTHING CHOKES.**  
250 mA 10 H 50 ohms ... 17/6  
250 mA 20 H 250 ohms. trop. ... 14/9  
200 mA 20 H 300 ohm. trop. ... 12/9  
150 mA 6-10 H 150 ohms tropicalised 7/9  
100 mA 7-10 H 100 ohms ... 7/9  
100 mA 5 H 100 ohms, tropicalised ... 3/11  
60 mA 5-10 H ... 3/9

**COAXIAL CABLE.** 75 ohms. 1 in. 84 yard. Twin Screened Feeder. 94 yard

**CHASSIS.** 16 s.w.g. Undrilled Aluminium Receiver Type 6 x 3 1/2 in. 2/6; 7 x 4 1/2 in. 3/3; 10 x 5 1/2 in. 5/9; 11 x 6 1/2 in. 3/3; 12 x 3 1/2 in. 3/9; 16 x 8 x 2 1/2 in. 7/6; 20 x 8 x 2 1/2 in. 8/11; Amplifier type (4 sided). 12 x 8 x 2 1/2 in. 7/11; 16 x 8 x 2 1/2 in. 10/11; 14 x 10 x 3 in. 13/6; 20 x 8 x 2 1/2 in. 13/6.

**SILVER MICA CONDENSERS.** 5, 10, 15, 20, 25, 30, 35, 40, 50, 100, 120, 150, 200, 230, 300, 400, 500, 1,000, 1,000 mfd. 2,000 pfd. (VOLUME MFD.) 5d. each. 3/9 doz. one type.

**VOLUME CONTROLS** with long (2 in.) spindles, all values, less switch 2/9. with S.P. switch. 5/9.

### R.S.G. MAINS TRANSFORMERS (FULLY GUARANTEED)

Intertraced and impregnated. Primaries 200-250-250 v 50 c.c.s. Screened TOP SHROUDED DROO THROUGH

250-0-250 70 mA. 6.3 v 2.5 a	12/11
250-0-250 70 mA. 6.3 v 2 a, 5 v 2 a	14/11
350-0-350 80 mA. 6.3 v 2 a, 5 v 2 a	17/9
350-0-350 80 mA. 6.3 v 2 a, 4 v 2.5 a	14/11
250-0-250 100 mA. 6.3 v 4 a, 5 v 3 a	23/9
300-0-300 100 mA. 6.3 v 4 v 4 a, c.t. 0-4-5 v 3 a	23/9
350-0-350 100 mA. 6.3 v 4 v 4 a, c.t. 0-4-5 v 3 a	23/9
330-0-330 150 mA. 6.3 v 4 a, 5 v 3 a	29/11
350-0-350 150 mA. 6.3 v 2 a, 6.3 v 2 a, 5 v 3 a	29/11

**FULLY SHROUDED UPRIGHT**

250-0-250 v 60 mA. 6.3 v 2 a, 5 v 2 a. Midget type 21-3-3in.	18/9
350-0-350 v 70 mA. 6.3 v 2 a, 5 v 2 a	18/9
250-0-250 v 100 mA. 0-4-6.3 v 4 a. 0-4-5 v 3 a	25/9
250-0-250 v 100 mA. 6.3 v 6 a, 5 v 3 a. For R1355 conversion	29/9
300-0-300 v 100 mA. 0-4-6.3 v 4 a. 0-4-5 v 3 a	25/9
350-0-350 v 100 mA. 0-4-6.3 v 4 a. 0-4-5 v 3 a	25/9
350-0-350 v 150 mA. 6.3 v 4 a, 4 v 3 a	33/9
350-0-350 v 150 mA. 6.3 v 6 a, 6.3 v 3 a, 5 v 3 a	45/9
350-0-350 v 250 mA. 6.3 v 6 a, 4 v 2 a, 0-2-6 v 2 a, 4 v 3 a, for Elc-tronics Frnz. Television	67/6
425-0-425 v 200 mA. 6.3 v 4 v 4 a, C.T. 6.3 v 4 v 4 a C.T. 0-4-5 v 3 a. Suitable Williamson Amplifier, e.c.c.	49/9
Economy Quality Amplifier type	49/9
450-0-450 v 250 mA. 6.3 v 6 a, 6.3 v 6 a, 5 v 3 a	65/9

**ELIMINATOR TRANSFORMERS**  
Primaries 200-250 v 50 c.c.s. 120 v 40 mA 7/9  
90 v 10 mA. 8-0-8 v 250 mA. ... 8/11

**EX-GOVT SMOOTHING CHOKES**  
250 mA 10 H 50 ohms ... 16/9  
250 mA 20 H 250 ohms. ... 11/9  
200 mA 20 H 300 ohms ... 6/11  
150 mA 6-10 H 150 ohms ... 5/6  
100 mA 7-10 H 100 ohms ... 4/11

**F.H.T. TRANSFORMERS**  
2,500 v 5 mA. 2.0-2 v 1.1 a. 2.0-2 v 1.1 a. For VCR97, VCR517, ACR2X, etc. ... 35/-  
5,000 v 5 mA 2 v 2 a ... 39/6

**OUTPUT TRANSFORMERS**  
Midget Battery Pentode 66: 1 for 3S1, etc. ... 3/9  
Small Pentode 5,000  $\Omega$  to 3  $\Omega$  ... 3/9  
Standard Pentode 5,000  $\Omega$  to 3  $\Omega$  ... 4/9  
Standard Pentode 7,000  $\Omega$  to 3  $\Omega$  ... 4/9  
Tri-ode ratio 40 mA. 30 : 1. 45 v 30 : 60 : 1. 30 : 1. Class B Push-Pull ... 5/6  
Push-Pull 10-12 watts 5V6 to 3  $\Omega$  or 15  $\Omega$  ... 15/9  
Push-Pull 10-12 watts to match 6V6 to 3-3  $\Omega$  or 15  $\Omega$  ... 16/9  
Push-Pull 15-18 watts to match 6L6, etc. to 3  $\Omega$  or 15  $\Omega$  Speaker ... 22/9  
Push-Pull 20 watts, sectionally wound, 6L6, KT66, etc. to 3, or 15  $\Omega$  47/9  
Economy Quality Amplifier type ... 47/9  
Williamson type exact to Author's spec. ... 85/-


Terms C.W.O. or C.O.D. NO C.O.D. under £1. Post 1/1 extra under £1. 1/9 extra under £3. Open 9 to 5.30; Sats. until 1 p.m. List 6d. Trade List 5d. S.A.E. please with all enquiries.

# RADIO SUPPLY CO. 32, THE CALLS, LEEDS, 2

# PRATTS RADIO

1070 Harrow Road, London, N.W.1.0

Tel. LADbroke 1734.

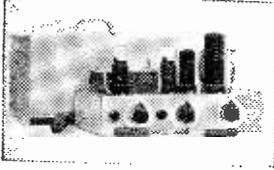

(Nr. Scrubs Lane)  
**AMPLIFIERS** College  
 General Purpose Units.  
 Model AC10E. (as illustrated) 10 watt 4 valve Unit  
 Neg. Feedback. Separate  
 Mike stage and Separate  
 Mike and Gram Inputs. 2  
 Faders and Tone Control.  
 £10.7.6. Model AC15F.  
 6 Valve Unit with F/P Output  
 of 14.15 Watts. Separate  
 Mike Stage and Separate  
 Mike and Gram Inputs. 2  
 Faders and Tone Control.

Feedback over 3 stages. £14.14.0. Model AC32E. Spec. as AC15E but with larger output stage of 32 watts £19.15.0. Model U10E. D.C./A.C. Mains. P/P Output of 10 watts. Spec. as AC15E. £12.19.6. All the above Amplifiers are Complete with Metal Cases. Chrome Handles and Outputs match 3, 8 or 15 ohm Speakers. Input volts for stated outputs, average Gram 5 volt, Mike .006 volt. All A.C. Models have H.T. and L.T. Output sockets for Tuning Units. All Amplifiers have sectionalised O/Transfrs. wound on super Silcor laminations.

**QUALITY AMPLIFIER CHASSIS FOR RECORDS, ETC.**  
 Model Q9C. 6 Valve Unit with Bass and Treble Controls. Williamson 18 section O/Transfr. and P/P Output of 9 watts. Input switching for Radio, L.P. Std. Adjustable Neg. Feedback. H.T. and L.T. for Tuner. £13.19.6.

**FULL RANGE OF PLAYERS, MOTORS, ETC. (LIST AVAILABLE).** **MIKES, PICK-UPS, SPEAKERS AVAILABLE.**  
**REV-ER.** Amplified Record Reproducer in rexine case with handle. 3 speed Single Player. Amplifier and Speaker. Beautifully finished. B.S.R. Unit, £14.14.0. or £4.18.0 and 12 monthly payments of 17/11.

**QUALITY SPEAKERS, W.B. H.F. UNITS.** 6in. 50/6; 8in. 60/6; 9in. 67/-; 10in. £3/13.6. Goodman's Audion 60, £8.12.6. (57/6 dep. and 12 payments at 10/6); Axion 150, £10.7.6 (69/2 dep and 12 payments at 12/8).

**RADIO CHASSIS, 3VL.** L. M. S. Wbands. 8in. dial illuminated. "E" series Valves. 8in. Speaker. £10.5.0 (dep. 68/4 and 12 payments at 12/6).

**B.S.R.** 3-speed, single-player in rexine case, 9 gns. (deposit 63/- and 12 payments at 11/6).  
**B.S.R.** Monarch 3-speed mixed autochanger with rexine case, 16 gns. (deposit, £5.12.0 and 12 payments at 20/6).  
**ALL GOODS ARE BRAND NEW. WE NEVER CHARGE CARRIAGE.**


Stamp for Lists (state interest). All goods can be inspected at our Showroom. Nearest stations: Kensal Gn. and Willesden Jen.

# DIRECT FROM THE MANUFACTURER

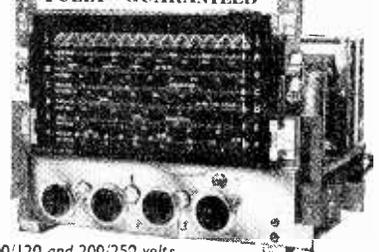**DULCI RADIO/RADIOGRAM CHASSIS**

Built to Highest Technical Standards  
**FULLY GUARANTEED**

All chassis 11 1/2 in. x 7 in. x 8 in. high. Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs. 3 tone positions for radio and gram.



For A.C. Mains 100/120 and 200/250 volts

- Model B3.—Long, Medium, Short 5 Valves. Output 3 1/2 watt **£12/12/0**
- Model B3.—Plus Push Pull Stage 6 Valves. Output 6 watt **£15/15/0**
- Model B3.—Double Feature with P.Pull & R.F. Stage. 7 Valves. Output 6 watt **£18/18/0**
- Model B6.—Six Wavebands, Med. Leng. 4 Short. (3 Bands spread.) 5 valves. Output 3 1/2 w. **£15/15/0**
- Model B6.—Plus Push Pull Stage 6 Valves. Output 6 watt **£18/18/0**
- Model B6.—Double Feature with P.Pull & R.F. Stage. 7 Valves. Output 6 watt **£23/2/0**

**ALL PRICES TAX PAID**

Escutcheon for 9in. x 5in. dial, 49/9 extra. Matching speakers P.M. type 3 ohms, 6in. or 10in. available. Chassis sent under money back guarantee conditions against remittance. Free particulars from the manufacturers.

**THE DULCI CO. LTD.,**  
 99 VILLIERS RD., LONDON N.W.2. Telephone: Willesden 7778

## THE FAMOUS BENNETT COLLEGE

can help your career through personal postal tuition

- in any of these subjects:
- Accountancy Exams. ★ Aircraft Eng. & Radio ★ Architecture ★ Auditing ★ Book-keeping ★ Building ★ Carpentry ★ Chemistry ★ Civil Service ★ Commercial Art ★ Commercial Arithmetic ★ Company Law ★ Costing ★ Draughtsmanship ★ Electric Wiring ★ Engineering (Civil); Electrical; Mechanical; Motor; Steam; Structural ★ Jigs, Tools & Fixtures ★ Journalism ★ Locomotive Eng. ★ Languages ★ Mathematics ★ Mining ★ Modern Business Methods ★ Plumbing ★ Police ★ Press Tool Work ★ Quantity Surveying ★ Radio ★ Salesmanship ★ Secretarial Exams. ★ Shorthand ★ Surveying ★ Telecommunications ★ Television ★ Textiles ★ Works Management ★ Workshop Practice

and GENERAL CERTIFICATE OF EDUCATION  
**SUCCESS WILL BE YOURS**

As a Bennett College Student your own Personal Tutor will coach you until you qualify, at your pace, with no time wasted. You will learn quickly, easily.

**SEND TODAY FOR A FREE PROSPECTUS**

TO THE BENNETT COLLEGE (DEPT. C.104), SHEFFIELD

Please send me your prospectus on..... (Subject)

NAME .....

ADDRESS .....

.....AGE (IF UNDER 21).....


PLEASE WRITE IN BLOCK LETTERS

## BUILD THIS AMAZING RADIO

POWERFUL! PERSONAL! PORTABLE!

- Selective tuning.
- Acorn low drain valve.
- Loud clear tone.
- Long range.
- No earth.
- Short aerial, 2ft.
- Welded steel case.
- Easy to assemble.
- All parts for this set are sold separately.

FOR **30/-**  
 POST FREE

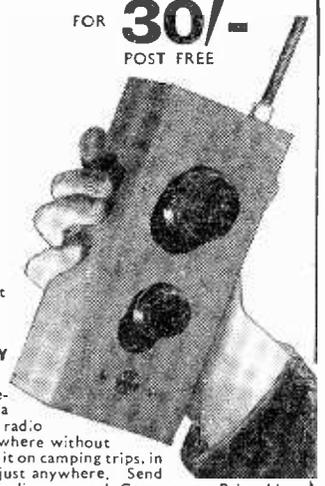

**MAIL ORDER ONLY**

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere. Send 2/- for layout, Wiring diagram and Component Price List.

**R. C. S. PRODUCTS (RADIO) LTD.,**  
 11, OLIVER ROAD, LONDON, E.17

# The Beginner's Guide to RADIO



The Eleventh Article of a Series Explaining the Fundamentals of Radio. This Month Condensers are Further Considered By F. J. CANN

I HAVE already briefly touched upon electrolytic condensers, but it is necessary now to explain in greater detail how they work.

The main advantage is the relatively large capacity obtainable for small physical dimensions. They differ radically from other types. We have seen that a condenser is a device for storing electrical energy and that in its simplest form it consists of two metal plates separated by a layer of insulating material, such as ebonite, glass, waxed paper or air. We have seen that an electric current is in reality the movement of small particles called electrons and that a condenser acts as a sort of electron reservoir. If we apply the poles of a battery, which is in effect a kind of electron pump delivering electrons at its negative pole and receiving them back at the positive pole, to the plates of the condenser, then one plate will acquire an excess of electrons and the other a deficit. The amount of electrons which can be "poured" into one plate of a condenser or drain from the other constitutes the "charge." The amount of the charge produced by unit pressure (1 volt) is a measure of the capacity of the condenser. We know that the capacity of a condenser is usually measured in microfarads and that the capacity is controlled by three things: the effective area of the plates, counting both sides; their distance apart and the nature of the dielectric. The larger the area of the plates the larger will be the capacity, and the closer they are placed together the more the capacity will increase. Actually the capacity does not vary directly with the distance between the plates, but is inversely proportional to the square of the distance. Thus, if the distance is halved the capacity becomes four times as great, and vice-versa. It is known that some dielectric materials give a larger capacity for a given size and distance apart of the plates than do others. This is called the *dielectric constant*. That of air is taken as unity, whilst most other substances show a higher figure. If two plates are fixed a certain distance apart in air, providing a capacity of, say, 1 microfarad and a piece of ebonite is slipped between them it will be found that although the plates are still the same size and distance apart, their capacity has increased two or three times. If in place of the ebonite a piece of ruby mica is used the capacity may increase as much as eight times. Thus, the dielectric constant of mica is eight. The dielectric, therefore, is of great importance in considering the efficiency of a condenser, for if it is a poor insulator the electrons collected on one plate will slowly leak through to

the other side and so the condenser will become discharged. A good condenser will hold its charge for some considerable time. In the timebase of TV receivers it is necessary to control the time of charge and discharge.

If a condenser is momentarily connected across a high-tension battery and then removed, it should be possible on joining the two terminals of the condenser together after several hours to get quite a fat crisp spark.

### Dielectric Strength

Apart from a condenser's ability to retain its charge and hence to give back as much energy as is put into it, there is the question of the *dielectric strength*. If the plates are very close together and the voltage (pressure) of the charging current is very high, it is possible for the insulation between the plates to break down altogether. This is a common fault with some of the cheaper receivers. A spark jumps between the plates cutting its way through the dielectric and so the condenser is completely discharged. Dielectric strength, therefore, is of great importance, especially in the power circuits of mains sets. Of the various substances used as dielectrics, mica has the greatest dielectric strength, paper is next and air lowest of all. Thus, the chief qualifications of a fixed condenser are good insulation and high dielectric strength. In some cases, more especially when used in H.F. circuits, a condenser must also be *non-inductive*. This means that it must in no way have the properties of a tuning coil. It must have no *inductance*. You may often see condensers marked

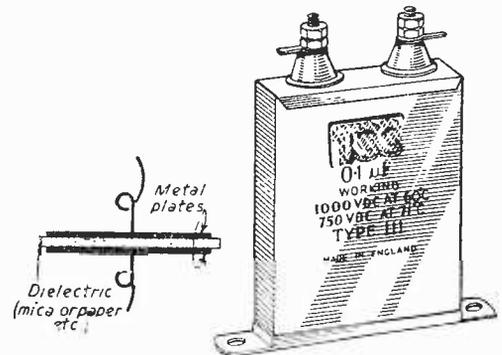


Fig. 46.—Principle of a fixed condenser and a typical "paper" type fixed condenser.

"non-inductive." How it is possible for a condenser to act like a tuning inductance may not at first be very clear, but if you consider the ordinary paper condenser you will see the reason. This type consists of two long strips of metal foil separated by layers of paper. The two strips form the plates and the paper the dielectric. In order to make the condenser compact, the whole thing is rolled up into a little bundle with the paper between the foil. Obviously the strips now form small coils and if the connection to each strip is taken from one end only, they will act as miniature tuning coils. The remedy for this consists

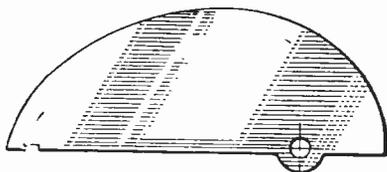


Fig. 47.—The popular "square law" condenser plate shape. (See last month's issue.)

in making contact with each turn of the foil. This is done by arranging for the foil strips to protrude slightly from the sides of the bundle—one strip to one side and one to the other. These are pressed over and coated with solder so that all the turns of each strip are connected together.

Now condensers of this type are very efficient and quite compact in sizes up to 1 or 2  $\mu\text{F}$ , but above this capacity they become rather bulky. Clearly there is a practical limit to the thinness of the foil employed, and also the paper dielectric cannot be reduced in thickness beyond a certain limit, otherwise it will be liable to puncture.

This is where the electrolytic condenser steps in. If you compare the size of that shown in Fig. 49 with the equivalent paper condenser you will see the considerable saving in space effected by the electrolytic type. There are also other advantages, such as its self-healing properties, but we will deal with those while describing the principle and construction of the condenser.

Electrolytic condensers are of two types—"wet" and "dry." They are both much the same in appearance, as will be seen from the two typical examples illustrated in Fig. 48, but whereas the former contains a liquid as the electrolyte, the latter employs a paste, jelly, or some absorbent material soaked in a solution.

The construction of an electrolytic condenser is somewhat similar to that of a dry cell. Fig. 49 represents it diagrammatically. It consists of a centre electrode of aluminium surrounded by the electrolyte (liquid or paste) and an outer metal case. The centre electrode forms one "plate" of the condenser and the liquid (or paste) the other. How a liquid can take the place of a plate is more easily understood if you remember that the liquid employed is a conductor of electricity—it is not an insulator like oil. Now, if the aluminium rod in the centre is one plate and the liquid surrounding it is the other, where does the dielectric come in? Well, actually when the unit is first assembled there is no dielectric. This has to be "formed." This is done by connecting the centre electrode to the positive pole of a battery or other source of current and the outer case to the negative pole. The current from the battery flows from one electrode to the other through the electrolyte, and in doing so gradually deposits a very thin film of alu-

minium oxide on the centre electrode. This film has a very high resistance, and the thicker it gets the more the current is reduced until a point is reached when only the smallest current passes; in other words, the film is to all intents and purposes an insulator. The condenser is now "formed" and consists of two plates (the centre aluminium rod and the electrolyte) separated by a dielectric consisting of the newly-formed film of oxide.

In practice the centre electrode is not a simple aluminium rod, but assumes more complex shapes. This is in order to increase its effective area. Two typical anodes are shown in Fig. 50. In each case a sheet of aluminium foil supported by an aluminium rod is used.

#### D.C. Only

You notice that I mentioned the *centre* electrode as being connected to the positive pole when the condenser is formed. This polarity must also be observed when it is connected in circuit. If it is connected the wrong way round, so that the centre electrode becomes negative and the container positive, then the film will pass into solution and the condenser will cease to function. Of course, this fact limits the use of the condenser to direct current circuits. It cannot

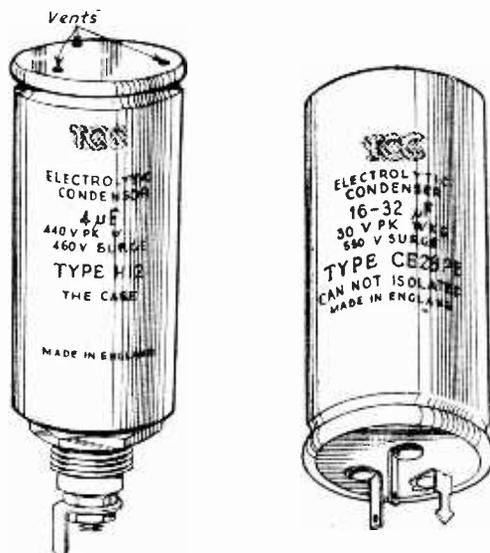


Fig. 48.—A standard type "wet" and a "dry" electrolytic condenser.

be used in alternating or high-frequency circuits, for in such cases each electrode becomes alternatively positive and negative. Any degree of ripple can be imposed on the D.C., providing it is not great enough to cause a reversal of polarity, that is to say, that so long as there is a polarising D.C. voltage it does not matter what form the current takes.

In mains receivers where condensers are used for smoothing, filter and decoupling circuits, the electrolytic condenser is ideal. It is easy to arrange for the anode to be connected to the positive line. In fact, with the many types of electrolytic condenser the container is fitted with a locking nut for securing the condenser to the chassis by the one-hole-fixing method, and so if a metal chassis is used, connection

is automatically made between the negative electrode and the earthed chassis. The positive connection is then taken to the centre terminal, which is screwed on the end of the anode and is, of course, below the chassis. In others, a soldering tag takes the place of the screwed end, and the condenser is mounted by means of a special clip.

With electrolytic condensers the insulation properties are not quite so good as with the ordinary type, as there is always a very slight leakage of current owing to the film of oxide not being such a good insulator as some substances. In the circuits mentioned above, however, this is of small consequence.

One great advantage of the electrolytic condenser is that it is "self healing." Should the film puncture owing to a sudden increase in voltage, the condenser will not be rendered useless. When the voltage drops again the puncture will seal up. This property is, naturally, of great importance in mains sets where the breakdown of a smoothing or filter condenser would put the whole set out of commission. (A punctured dielectric with an ordinary condenser means the destruction of the condenser.)

Since this basic electrolytic condenser was produced there have been many improvements. As an example, the production of really efficient "dry" and "semi-dry" types is very noticeable. With these types much ingenuity has been shown in the matter of the electrolyte and the design of the electrodes. Of course, the advantages of the dry type over the aqueous are obvious when it is remembered that with wet types a small vent hole is necessary. However carefully this is designed, there is always the possibility of some of the electrolyte being spilt if it is of a liquid nature. The advantages of the latest electrolytic condensers are: small leakage current (a fraction of a milli-ampere in most cases), quick recovery after a period of rest (when first used after standing idle for some time

all electrolytic condensers take a larger current than normal for some seconds), and low internal resistance. This means a low power factor. The power factor is really a measure of the efficiency of a condenser. An ideal condenser would have a power factor of zero. Modern electrolytic condensers can be brought down to about 5 or 6 per cent.

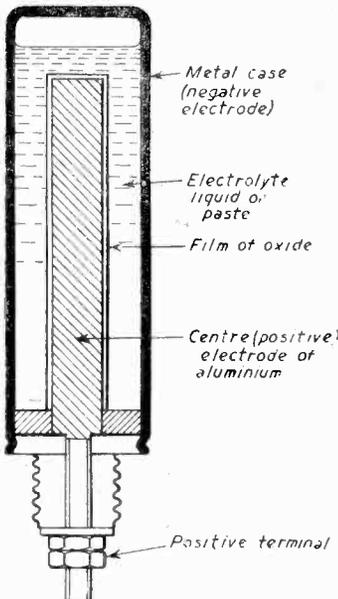


Fig. 49.—Details of construction of a typical "wet" electrolytic condenser.

more cumbersome *superheterodyne*. Most receivers today are superhets and it is a system of circuitry concerned with selectivity. In the older style of tuning circuits, with which we have been concerned up to the present, sharp tuning is not possible and it will be found in some cases that two or more stations can be heard

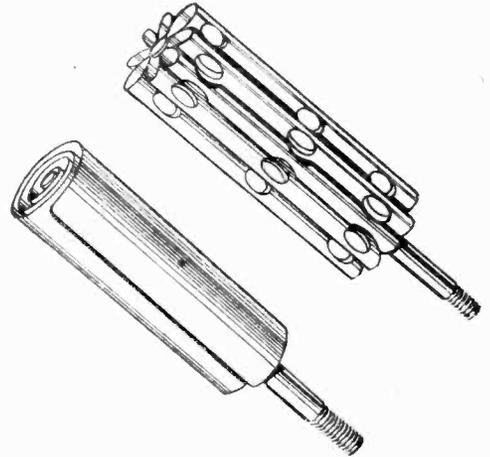


Fig. 50.—Two typical anode designs used in electrolytics.

at the same time, due to the closeness of their wavelengths. In the early days of radio when comparatively few stations were operating, the problem did not occur; but now that the broadcast band is crowded with stations having wavelengths only a few metres apart, it is necessary to design the tuning circuit so that overlapping does not occur. The superhet principle provides the solution. In brief, it consists of receiving a station at one particular wavelength or frequency and changing it to another by means of a frequency changer stage and an intermediate-frequency transformer. In brief, the superhet is a method of obtaining high selectivity by converting a received signal into a different and lower frequency and then amplifying this new frequency. The signal is detected, the frequency changed, amplified by two or more high-frequency stages, again detected and then passed to the I.F. stage or stages.

The intermediate-frequency transformer consists of two coils of wire coupled together and tuned, by pre-set condensers or metal cores, to the intermediate frequency, and connected between the intermediate frequency valves.

In the ordinary tuned radio frequency or "straight" receiver each tuned H.F. circuit operates at the carrier (original) frequency of the signal being received. If, for example, a 300 metre or 1,000 kc/s station is received in the aerial circuit, the oscillations will remain at 1,000 kc/s in every circuit right up to the detector. It is, of course, necessary for every H.F. circuit in the receiver to be variably tuned to allow for the reception of signals of various carrier frequencies. In a superhet, however, only a certain number of the tuned H.F. circuits are variably tuned, and operate at the carrier frequency of the signal. These circuits (there may be only one, of course) come first, counting from the aerial.

(To be continued)

**The Superhet**

The word "superhet" is an abbreviation of the

**L**AST month attention was drawn to the fact that the actual wires shown in the wiring diagram were "squared up" by the artist in order to make the layout and wiring clear. In actual practice some wires and even some components will come above each other and in such a condition the wiring would be impossible to follow. The main point to watch is that the components should be as near as possible to the positions actually shown, whilst the wiring should be made as direct as possible, cutting wire-ended components down as required to reduce the length of the lead. For instance, the  $.05 \mu\text{F}$  condenser seen immediately below the coil unit and above the  $.1 \mu\text{F}$  condenser has one lead cut to about  $\frac{3}{8}$  in. and is soldered direct to the earthing bus-bar, whilst the other lead is cut to a similar length, and to it are attached one lead from a  $1 \text{ M}\Omega$  resistor and the brown lead from the coil unit. The lead from the  $1 \text{ M}\Omega$  resistor should be twisted round the lead on the  $.05 \mu\text{F}$  condenser, and the brown coil lead soldered when the coil unit is placed in position. Wherever two or more leads are found at one point the correct procedure, to avoid damaging a component by the application of excessive heat, is to twist the leads together temporarily as the various parts are placed in position and finally, when all the wires at a given point are in position to undo them, loop them neatly, all through a single-loop formed in one of the leads, and then apply solder and a hot iron, when all will be joined in the same time as it would normally take to make a single connection. The loop should be permitted to fill with the molten solder and a good, sound connection will result.

#### Instability

Reverting to the question of the position of actual wires, it is possible, due to running leads in some positions, to introduce instability into almost any receiver. Grid and anode leads of each stage, as well as the anode lead of one stage and the grid lead of another stage, should never run close together or parallel. One model which has been constructed from the details given last month did, in fact, have this trouble and it was found to be due to the run of the yellow lead from I.F.T.2 to the anode tag of V2. The artist has shown this, for clarity, running round on the left-hand side of the valveholder, and if this is followed and it is found that the receiver does suffer from instability (which may not necessarily arise) the lead should be shortened and run round the other side of the valveholder—beneath the  $1 \text{ M}\Omega$  resistor and  $680 \text{ k}\Omega$  resistor, which incidentally was not mentioned in the list of parts given last month. This is also a  $\frac{1}{2}$  watt component.


#### Testing

When the wiring has been completed it should be very carefully checked against the wiring plan or blueprint, one of the most important checks being that made with a resistance meter between chassis and the H.T. positive line. If you do not have a resistance meter a simple meter, say reading to  $1 \text{ mA.}$ , in series with a 1.5 volt cell, will serve, and there should be no indication of any current reading from any point on the H.T. line to chassis, nor from any point on the H.T. line to the heater circuit. An upward flick of the needle may occur when the

# THE AC/DC Co

THE UNIVERSAL VERSION OF OUR LATEST REC


(Continued from page 77 February issue)

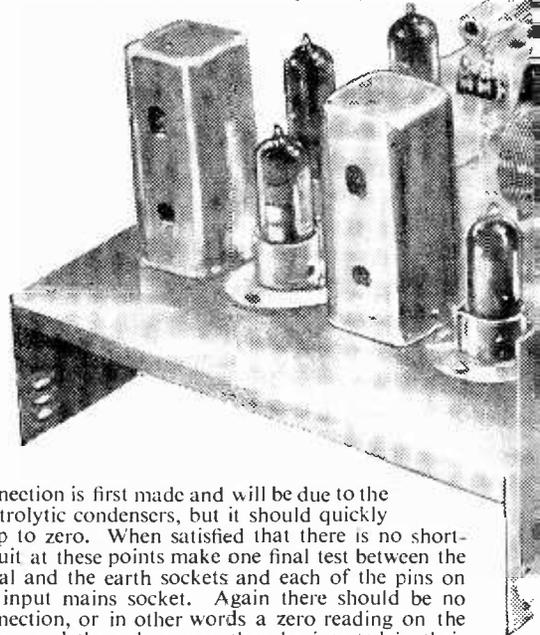

connection is first made and will be due to the electrolytic condensers, but it should quickly drop to zero. When satisfied that there is no short-circuit at these points make one final test between the aerial and the earth sockets and each of the pins on the input mains socket. Again there should be no connection, or in other words a zero reading on the meter, and the valves may then be inserted in their appropriate valveholders.

If your mains are between 200 and 230 volts, the  $200\Omega$  resistor joined in series with the  $1,000\Omega$  resistor may be omitted, or alternatively a short length of wire may be connected between the switch and the junction of these two resistors—short-circuiting the  $200\Omega$  resistor. On mains from 230 to 250 volts the  $200\Omega$  resistor must be included. Leaving the chassis inverted the mains lead may now be plugged in and the set switched on. With the centre knob in its mid-way position (this has three positions, short, medium and long) the tuning knob should be turned until the local station is heard, the volume control being adjusted to keep a suitable level of sound. At this stage a voltage test may be made to make certain that everything is satisfactory, and the table on the right shows the readings obtained on the prototype when connected to 240 volts A.C. mains. The tests were made with a meter having a resistance of  $10,000\Omega$  per volt, and thus if a meter with a lower resistance is employed the readings will differ slightly. They give an indication, however, as to the approximate voltages which should be found. One of the most important readings is that across the  $1,000\Omega$  series heater resistor. The current taken by

# ronet Four

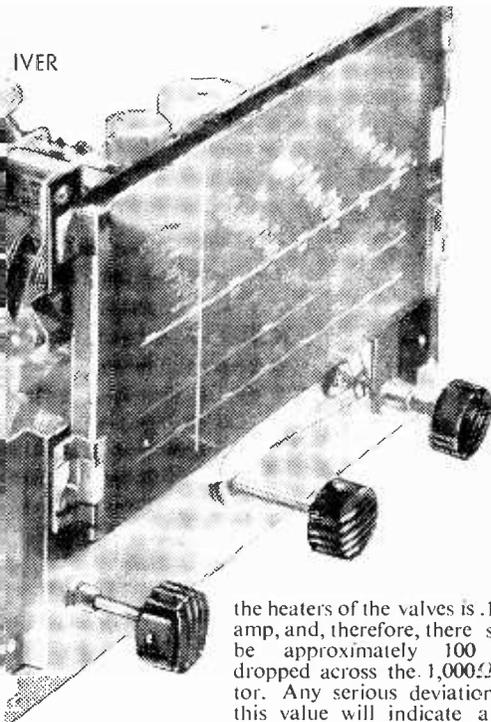

the heaters of the valves is .1 of an amp, and, therefore, there should be approximately 100 volts dropped across the 1,000 $\Omega$  resistor. Any serious deviation from this value will indicate a fault in the heater circuits and an attempt should be made to correct

it. The shunting of the resistor by the meter will affect its value, and again a high-resistance meter must be used.

### Tonal Quality

It will be noted that a .01 $\mu$ F condenser is shown connected by broken lines across the loudspeaker connections. This may be added by the constructor according to taste. If, without it, it is found that the tone is rather too shrill the condenser will lower it, and various values may be tried to suit the type of cabinet or room acoustics. The condenser may be joined direct across the transformer connections on the loudspeaker.

### Warning

Remember that on no account should any direct earth connection come into contact with the chassis. Also, as the chassis is in direct connection with one side of the mains the greatest care must be taken in handling the receiver and the knobs which have been specified have deeply recessed grub-screws, and therefore if alternatives are used care should be taken to see that the grub-screws are well sunk below the surface of the knob, and if not they should

be covered with wax (Chatterton's Compound) to avoid contact being made.

### Components and Adjustments

With every design which we publish a number of queries arise from readers who wish to use different parts, or make amendments to the published circuit. We cannot, of course, give instructions for making any modifications to the design as published, but there are certain small points which arose in the A.C. version and which are also applicable to this model which can be dealt with at this stage. First, with regard to the specified parts. The whole feature in this particular design is the removal of the necessity for trimming or lining up, and therefore the heart of the set is the tuning pack, the ganged condenser, the I.F. transformers and the tuning dial. All of these items are "matched" and pre-aligned, so that not only is the necessity for lining-up abolished, but the tuning dial will record correctly the various stations which may be tuned in. At one time all coil manufacturers made coils to a given inductance value, and it was thus possible to produce a tuning scale which would suit any coil, provided that you used a standard condenser with plates of a certain pattern. Modern coils differ, however, and the use of the iron core, which is now so common, varies the inductance, so that the user may adjust the core and obtain a different inductance value, the result of which will be to vary the frequency at different settings of the tuning condenser.

This difficulty is accentuated in the case of a multi-coil unit, and in a superhet a further complication arises due to the setting of the oscillator section. The particular coil specified, however, is tested by the manufacturers in a circuit, and the various trimmers and cores adjusted so that it lines up on the dial mentioned, and also gives maximum performance at all settings of the condenser on the three wavebands. If, therefore, you use any other coil unit, alternative variable condenser or dial, the combination will have to be separately lined up, and unless you have a good signal generator this is not a simple matter.

### Stray Capacities

The coil unit is provided with coloured leads, and the layout has been arranged to accommodate these leads without lengthening and to provide the minimum of stray capacities which could affect the tuning. Therefore, an alternative layout should not be adopted, unless this fact is borne in mind. The I.F. trans-


V1	A	210 v.
	S.G.	125 v.
	Triode A	210 v.
V2	A	210 v.
	S.G.	125 v.
V3	A	220 v.
	S.G.	210 v.
	C	14 v. (25 v. range)
Across 1,000 $\Omega$ series heater resistor=		100 v.

formers specified for this model are known as type "U" and differ from those used in the A.C. version in that the latter has a top grid lead to suit the different type of valve which was employed. The type "U" components have all leads projecting from the bottom, but the original transformers may be used, provided that they are modified as mentioned on page 76 of last month's issue. This modification will affect the stray capacities in this part of the circuit and will call for a slight readjustment of the lower trimmer to even things up, and it should be carried out on a station somewhere about the centre of the dial on the medium-waveband. Keep the signal very weak by means of the volume control and adjust the trimmer very slightly. Remember that the A.V.C. action will tend to mask the adjustments and a little care is necessary; rechecking on two or three stations will, however, serve to confirm the adjustment which is made. On the type "U" components no adjustment is necessary.
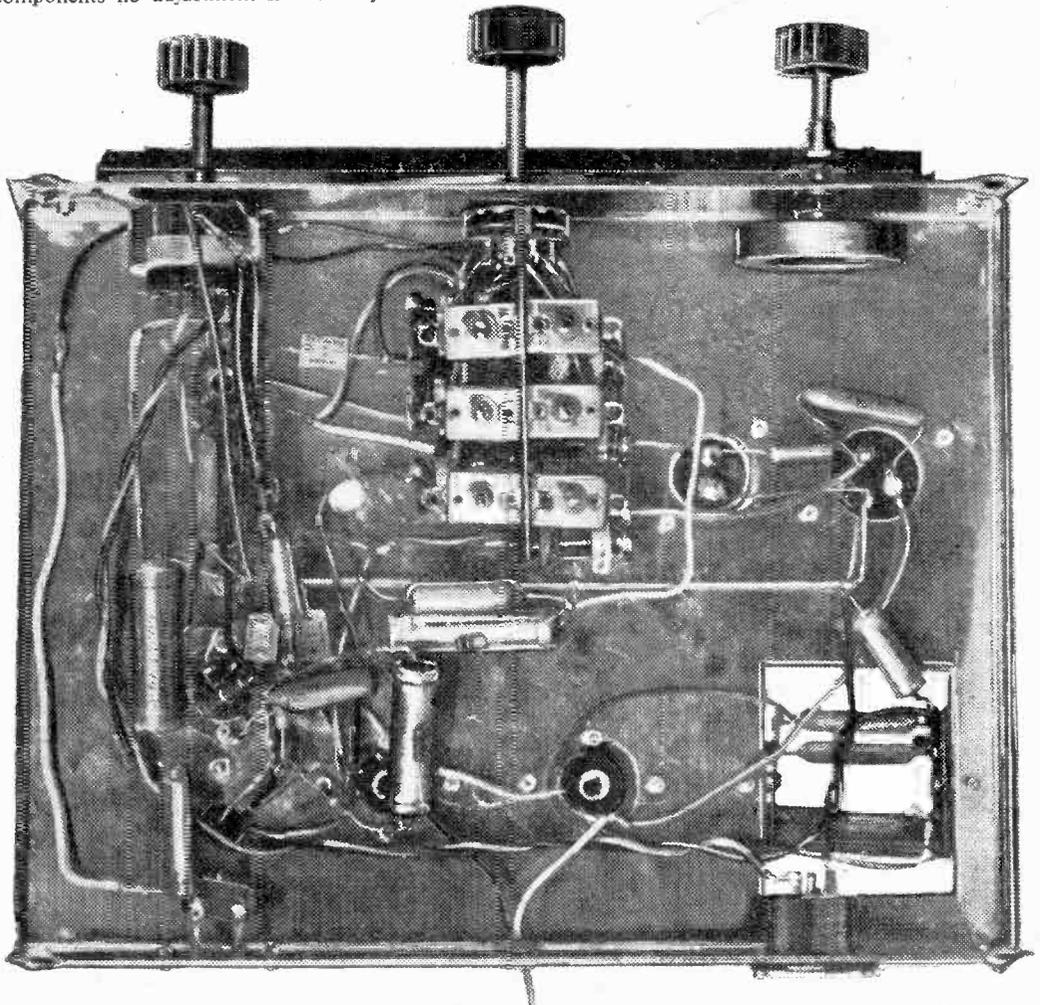
#### Components

With regard to the remaining components, alternatives are permissible, provided they are of suitable or equivalent types. For instance, the resistors may be of any make, provided they are of similar working voltages and more or less similar physical dimensions. With regard to the 20 M $\Omega$  resistor which is specified it will probably be found that in certain makes this is not available as a standard—perhaps only in a higher tolerance rating. It is, of course, quite permissible to use two standard 10 M $\Omega$  components connected in series to obtain this value, which is not so critical that the tolerance variation of two components will not affect results.

With regard to the loudspeaker, the model specified when used in a cabinet of the type illustrated gives a very good standard of reproduction, bearing in mind the output volume which is delivered. A better loudspeaker or a larger one will not necessarily give better reproduction unless the audio circuit is modified.




*This view of the underside of chassis shows the actual wiring positions and may be compared with the wiring diagram given last month.*

**EX-A.M. RECEIVER TYPE R1155.**



Brand new and unused. 5 Frequency ranges: 12.5-1.5 Mc s; 7.5-3.0 Mc s; 1,500-600 Kc s; 500-200 Kc s; 200-75 Kc s. Supplied in maker's original wood transit case. LASKY'S PRICE, £11/19/6. Complete. R.1155 Receivers. Second hand, aerial tested. £7/19/6. Carriage and packing 12/6 per unit extra, including 10, which will be refunded on return of packing case.

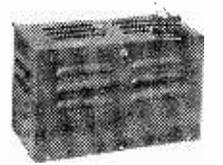**FULLY ASSEMBLED POWER PACK AND OUTPUT STAGE FOR R1155 RECEIVERS.**



For use on 200-250 volt A.C. mains. Wired and complete with valves. In steel case black crackle finished, size: 12 x 5 1/2 x 7 in. LASKY'S PRICE, 79/6. Carriage 5/- extra. Power pack as above, complete with 6in. loudspeaker. PRICE £25/5/0. Carriage 5/- extra.

**SPECIAL C.R.T. OFFER**

Brand new and unused 12in. ion trap type television cathode ray tubes, 6.3 volt heater, 7-9 KV. E.H.T. 35 mm. neck. Black and white picture. By famous manufacturer. By PERFECT. £12/19/6. Carriage and insurance 15/- per tube extra.

**TELEVISION SELENIUM RECTIFIERS**

The very latest "Sentercell" S.T.C. range.  
K/40, 3.2 kv. .... 6/-  
K/35, 3.6 kv. .... 8/2  
K/30, 4.0 kv. .... 8/8  
K/300, 4.0 kv. .... 14/8  
K/160, 12.8 kv. .... 21/6

**MAINS TRANSFORMERS**

All 200-250 v. 50 c.p.s. primary. Finest quality, fully guaranteed.  
MBA/3. 350-0-350 v. 80 mA. 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans. Price, 18/-.  
MBA/6. 325-0-325 v. 100 mA. 6.3 v. 3 a., 5 v. 2 a. With mains tapping board. Price, 22/6.  
MBA/7. 250-0-250 v. 80 mA. 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. Price, 18/-.  
MBA/8. SPECIAL OFFER. Drop through type. 235-0-235 v. 60 mA. 6.3 v. 3 a., 12/6.  
A/T/3. Auto transformer. 0-10-120, 200-230-240 volts. 195 watts. Price, 17/6.

**P.M. FOCUS MAGNETS**

35mm. With vernier adjuster. Triode 15/-, Triode 17/6. Less vernier. All types 12/6. 38mm. Wide angle, with vernier and picture shift control. 25/-.

**CRYSTAL DIODES**

Glass type. Wire ends, 1/6 each.

**LINE FLYBACK E.H.T. TRANSFORMER**

Output 7.9KV. E.H.T. with heater winding for EY51. 19/6.

6V6	...	7/6	VALVES. 10,000 IN STOCK AT THE LOWEST POSSIBLE PRICES. SOME EXAMPLES.
35Z4	...	9/-	
6AM3	...	7/6	
6H8	...	2/6	
EF50, Red	...	9/-	
New Sylvania	...	10/-	

**SPECIAL OFFER, 4 Valve + 1 each 1R5, 1T4, 1S5 and 3S1.**

**LASKY'S PRICE 30/- POST FREE.**

1S4	...	7/6	1A5	...	9/-	6J7	...	6/6	EF39	...	7/6
3S1	...	9/-	12K8	...	8/6	0Z4	...	6/-	12K7	...	10/6
1T4	...	7/6	12Y7	...	8/6	KT2	...	3/6	6L6	...	10/6
1R5	...	7/6	6AL5	...	9/-	6K8	...	8/6	EA50	...	2/6
1S5	...	7/6	6K7	...	4/6	U50	...	7/6	EBC33	...	7/6
1C5	...	7/6	1D5	...	8/6	ECH35	...	13/6	6L5	...	10/-

**"DINGHY" AERIALS, WITH REFLECTORS**

Umbrella type, with wire mesh reflector. Complete with setting up instructions. Mast not supplied. Ex. American Air Corps. Ideal for short-wave reception.

**LASKY'S PRICE, 5/- POST FREE.**

**R.1132.A RECEIVERS**

Supplied in maker's original wood transit case. Frequency coverage 100-124 Mc.s. 11 valves: 1 VR65, 1 VR66, 4 VR53, 2 VR54, 1 6J5, 1 V570, 1 VR37. Large tuning scale with slow motion drive. 0.5 mA. tuning meter, R.F. and L.F. gain controls, jack sockets for line and phone. Totally enclosed in metal case, grey enamelled with plated handles. Size: 18 x 10 x 11in. Supplied with all valves, also circuit and calibration chart.

**GRADE 1. Brand New 79/6.**

**GRADE 2. Soiled 49/6.**

**GRADE 3. Secondhand 39/6.**

**CAR RADIO SPECIAL**

Partly Assembled Car Radios.



Small size case, only 12 x 6 x 4in. Will fit most cars. For either 6 or 12 volts, depending on vibrator. Chassis supplied with 5 octal valveholders, medium wave aerial and oscillator coils. Output transformer, volume control, sundry resistances and condensers, dial and knobs. Case finished in pleasing shade of brown crackle. Dial calibrated 150-550 metres. LASKY'S PRICE, 69/6. Carriage 5/- extra. WRITE FOR FULLER DETAILS. Other chassis in various conditions of completion are available for personal callers only. **CIRCUIT** for 5-valve car radio, using above chassis. PRICE 1/6. We can supply a set of valves that will suit this car radio. All either GT. or metal. One each as follows: 6SA7; 6R7; 6V6; 0Z4; 6K7. PRICE 32/6 THE SET.

**HEARING AIDS**

By well-known Manufacturer. In metal case, size: 2 1/2in. x 4 1/4in. x 1in. Complete with batteries and 3 sub-miniature valves, earpiece and cord. Only two controls: volume and on/off. Fitted with internal crystal micr. phone. **MADE TO SELL, FOR 22 GNS. LASKY'S PRICE, 99/6** Postage 3/6 extra. Ready for use. Perfect working order. Slightly soiled but new and unused. A few hearing aids available, less earpiece, cord and batteries. PRICE 50/- Carriage 2/6 extra.

**CONDENSERS**

Electrolytic Cans.	
16 mfd. 500 v.w.	3/6
24 mfd. 350 v.w.	3/11
32 mfd. 500 v.w.	5/11
60 mfd. 350 v.w.	3/6
64 mfd. 450 v.w.	4/11
8+8 mfd. 450 v.w.	3/11
8+16 mfd. 450 v.w.	3/11
8+24 mfd. 450 v.w.	3/11
16+8 mfd. 500 v.w.	4/6
16+24 mfd. 450 v.w.	4/11
16+32 mfd. 450 v.w.	4/6
20+20 mfd. 275 v.w.	2/-
32+32 mfd. 350 v.w.	3/11
60+100 mfd. 350 v.w.	7/6
250 mfd. 350 v.w.	4/11

**MANY OTHER TYPES IN STOCK**

Send us your requirements.

**THE NEW ACOS MICROPHONE**

A general purpose hand mic. of robust construction, with almost flat response from 50 to 5,000 c.p.s. Suitable for recording equipment, P.A. etc. PRICE 25/-.



**BAFFLE RADIO CABINETS**



Pleasing design, complete with drilled chassis, dial, drum drive and back. Finished in satin mahogany veneer, natural polish. Outside dimensions: 17 1/2in. wide, 11 1/2in. high, 3in. deep. LASKY'S PRICE, 36/- Carriage 2/- extra. Circuit and component list for 4 valve T.R.F. set available.

**METAL RECTIFIERS**

6 and 12 volt F.W. Bridge.	
2 a.	9/-
3 a.	9/11
4 a.	12/-
6 a.	19/6

**S.T.C. SENTERCELL RECTIFIERS**

RM.1	3/10
RM.2	4/3
RM.3	5/-
RM.4	18/-

**LOUDSPEAKERS**

First Quality. All 3 ohm speech coil. Less output trans.  
3in. .... 14/6 6in. .... 15/-  
4in. .... 10/6 8in. .... 15/-  
5in. .... 13/6 10in. .... 17/6

Now available, 12in. Goodmans heavy duty. 15 watts. 15 ohms.

LASKY'S PRICE, £5/19/6. Carriage 3/6 extra.

**SPECIAL PURCHASE STAINLESS STEEL RECORDING WIRE**

1hr. Reels	6/11.
1/2hr. Reels	12/6.
1hr. Reels	25/-.

**COLLARO 3-SPEED AUTO CHANGERS**



Brand new and unused, in maker's original carton. Finished in cream. Fitted with high fidelity studio pick-up (turnover crystal), type GP 20. LASKY'S PRICE, £9/19/6. Carriage Free.

**I.F. TRANSFORMERS**

465 Kc.s. Iron dust cores in cans, midge type. Size: 1 1/2in. x 1 1/2in. Price 8/6 per pair. WEARITE TYPE 550. 445-520 Kc.s. 8/6 per pair. WEARITE TYPE 500. 450-470 Kc.s. 8/6 per pair.

**GRAM MOTORS.**

Shaded pole, synchronous. For 200 250 v. 50 c.p.s. mains. Rim drive. Many Uses. 9/6 each.

**LASKY'S RADIO**

Lasky's (Harrow Road), Ltd., 370, Harrow Road, Paddington, London, W.9


Telephone: CUNningham 1979-724. All Dept.s, MAIL ORDER AND DESPATCH DEPARTMENTS 485-487, HARROW ROAD, PADDINGTON, LONDON, W.9. Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs. half day 1 p.m. Postage and packing charges (unless otherwise stated) on orders value £1-1s. 0d. extra; £5-2s. 0d. extra; £10-3s. 0d. extra; over £10 carriage free unless specifically stated otherwise. All goods fully insured in transit.

## HOME RADIO OF MITCHAM

Announce an entirely  
**NEW CONSTRUCTORS**  
**3 VALVE SHORT-WAVE RECEIVER**

for A.C. mains

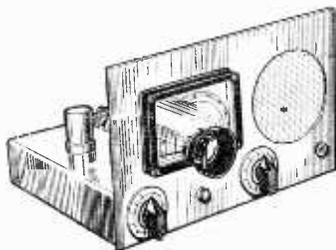Sensitive T.R.F. circuit using 3 EF50 valves and the latest



Eddystone plug-in short wave coils. Complete short-wave coverage from 10 metres to 180 metres. Medium wave coil also available. This fine easily assembled set will bring the thrill of

exploring the world to your fireside. Every component is standard and we can supply separately or as a complete kit. Chassis and front panel have all major holes punched ready for assembly. Join the happy band of short-wave listeners and send for the full constructional details of model JB.3. to-day.

Price 1/3, post paid. Available only from :

### HOME RADIO

187, London Road, Mitcham, Surrey. MIT: 3282.

Open until 6.30 p.m. every day. (Weds., 1.0 p.m.).


## JUST ARRIVED



The NEW
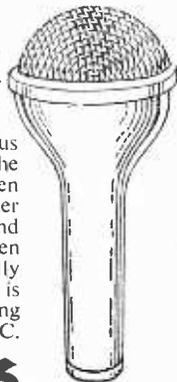
### 'Coronation' De Luxe HIGH FIDELITY CRYSTAL MICROPHONE

This latest RONETTE production uses the vacuum sealed DX12 crystal cartridge, as incorporated in the famous "Coronation" microphone. The Coronation De-luxe has been designed to give even greater sensitivity, with a wide range and flat frequency response between 30-13,000 c/s. The beautifully polished cream Urea housing is supplied with a long connecting flex, finished in white P.V.C.



only **59/6**



E & G Mail Order Supply Co.

The Radio Centre

33, Tottenham Court Rd., London, W.1

## SPARKS' DATA SHEETS

Constructional Sheets of Guaranteed and Tested Radio Designs.

IF YOU WANT A REALLY EFFICIENT PORTABLE

It will pay you to send a stamp for full details of my Latest Design.

### THE "ECLIPSE"

All-Dry Battery Superhet Portable.

A Tried, Tested & Guaranteed Design of the Personal Portable Type. Neat & Compact enough to be taken anywhere but not so small that it is difficult and fiddly to make.

COMPLETELY SELF-CONTAINED. Highly Efficient and Right up to Date.

The above is in addition to the

### 30 GUARANTEED DESIGNS

already available. Have you had a copy of my Latest List? It not a S.A.E. or a 2jd. stamp will bring one by return.

COMPONENTS AND DRILLED CHASSIS SUPPLIED.

L. ORMOND SPARKS (P), 48A, HIGH STREET, SWANAGE, DORSET.

## "ADCOLA" SOLDERING INSTRUMENTS

Regd. Trad. Mark



(British, U.S. and Foreign Patents)  
 Regd. Design No. 800302

For Wireless and Television Assembly

The advanced design of the Adcola Instruments meets the modern requirements of Television, Telecommunication and Radar Engineers

SUPPLIED FOR ALL VOLT RANGES FROM 6/7v. to 230/250v.

3/16in. dia. Bit. Standard Model	...	...	25/6
1/4in. dia. Bit. Standard Model	...	...	28/-
3/16in. dia. Detachable Bit. Model	...	...	33/6

Sole Manufacturers :

## ADCOLA PRODUCTS LIMITED

GENERAL OFFICES & WORKS : CRANMER COURT, CLAPHAM HIGH STREET, LONDON, S.W.4. (MACaulay 4272)

HERE IS RADIO'S SIMPLEST & CHEAPEST VALVE SET!

## THE "COCOA-TIN SPECIAL"

This receiver, as the name indicates, is constructed from scrap materials such as odd pieces of bakelite and plywood, screws, discarded cocoa tins, etc., found around the house and in the junk box. Two circuits are available, a single-valve for use with headphones, and a two-valve for loudspeaker reception. The original one-valve set, apart from the valve, cost less than 5 - to build; the loudspeaker set can be constructed by the addition of another valve and a few simple components. Both sets work from small dry batteries, cover long and medium waves, and require only an indoor aerial. They give results equal to sets built in the orthodox manner. Full instructions for building both sets, including point-to-point wiring diagrams—

PRICE 3/6 POST FREE

This offer is confined to Great Britain, Irish Republic and Northern Ireland.

RADIO DESPATCH SERVICE

137, COTHAM BROW, BRISTOL, 6. Orders by post only

## REP HIGH GAIN COILS



Dual Range Miniature 2/6 with Crystal Set Coil Circuit

Dual Range Coil 4/- with 2 Mains and with Reaction 2 Battery Circuits

Matched Pair Dual Range 8/- pair With Battery and T.R.F. Coils with Reaction Mains Circuits

- All coils wound on low loss formers.
- Individually tested and guaranteed.
- Post 3d. on all orders.
- Trade supplied.

RADIO EXPERIMENTAL PRODUCTS, LTD.  
 33, MUCH PARK ST., COVENTRY

# A Condenser Analyser

A COMPACT AND VERSATILE INSTRUMENT FOR TESTING THE INSULATION PROPERTIES OF ALL KINDS OF PAPER AND MICA CONDENSERS, AND RE-AGEING ELECTROLYTICS

By H. R. Singh

## The Electrolytic Condenser

**I**N an electrolytic condenser the dielectric consists of a very thin layer of oxide on an aluminium foil electrode, created by passing direct current from aluminium to the solution. Contact with the solution is made by another piece of aluminium foil or the outer case of the condenser. The oxide layer is not too stable and tends to de-form if the condenser is stored for any length of time. Thus, if an electrolytic is taken from stock and put straight into a receiver, the excessive leakage current may overload the rectifier section. Even if that section withstands the additional load, the heat produced in the electrolytic may, after a time, cause breakdown and damage. With the very high capacitors used in A.C./D.C. type television receivers, these risks are present in even greater degree. It can be said that whereas reformings of electrolytics before insertion into radio sets is highly desirable, where television receivers are concerned it is an essential safeguard.

## Mode of Operation

The instrument is designed to operate from A.C. mains supplies and provides a range of D.C. voltages which are coupled through current limiting resistors to the condenser under test. The current is thereby limited to a safe value which can be maintained until the electrolytic has re-aged, should it be necessary. At the same time, the voltage drop across the charging resistor is applied to a neon lamp. When the current is high, the voltage causes the neon to glow. As the current and voltage fall, the neon begins to flash and,

finally, when leakage has reached the normal amount, the neon goes out.

## Circuit

The circuit (Fig. 1) consists basically of a half-wave rectifier with switch-selected input voltages from a tapped mains transformer secondary, together with switches for selecting rectified input voltage, rectifier load resistor, reservoir capacitor and the various series charging resistors. A neon capacitor circuit gives visual indication of operation of the instrument.

The rectifier consists of a series of selenium half-wave rectifiers MR<sub>1</sub>, MR<sub>2</sub>, MR<sub>3</sub>, and MR<sub>4</sub>. Its input A.C. voltage, obtained from the mains transformer "T," is adjusted in steps between 125 and 550 volts by means of taps on the secondary selected by SW.1. Rectified output is developed across load resistors R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub>, and R<sub>4</sub> selected by SW.3 across which is connected the reservoir capacitor C<sub>1</sub> selected by SW.4. Switch SW.2 selects half-wave D.C. output and delivers it through the neon indicator network comprising R<sub>5</sub>, C<sub>2</sub> and 110 volt neon N, and the series charging resistors R<sub>7</sub>, R<sub>8</sub>, and R<sub>9</sub> selected by SW.5 to the test condenser. Switch SW.5 in position 1 connects R<sub>6</sub> across the test capacitor to discharge it.

Fig. 2 "A" shows the discharge resistor in circuit and "B" the simplified circuit of the whole system and corresponds to switch positions 2 to 8. Circuit diagram Fig. 2 "B" without discharge resistor R corresponds to switch position 9. Switches 1 to 5 are ganged together and termed the "Selector Switch."

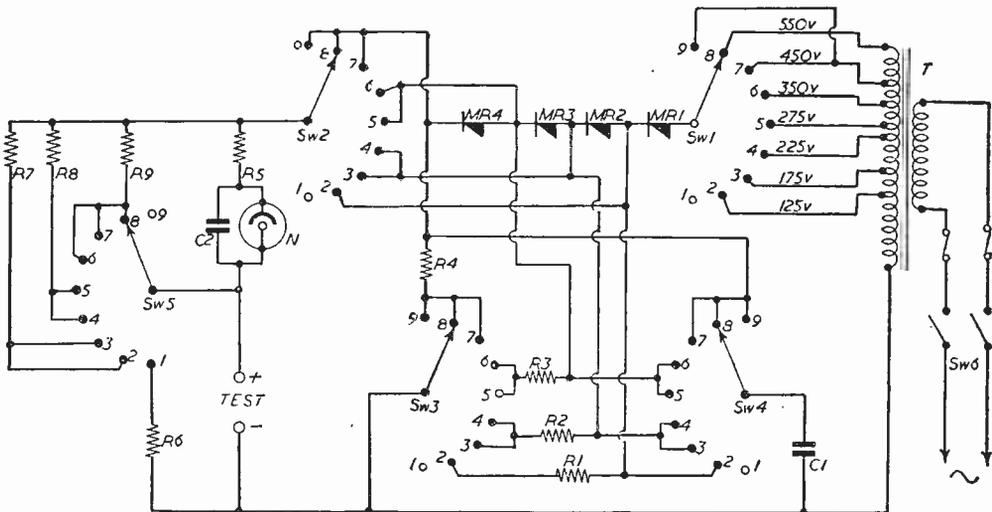


Fig. 1.—Theoretical circuit of the instrument.

**Operating the Instrument**

The instrument is quite straightforward to use. A pair of test leads should be made up terminating in crocodile clips at one end and red and black banana plugs at the other. These leads should be inserted into their respective sockets on the instrument panel, the selector switch set to position 1, and the unit switched on. In this position the discharge resistor  $R_6$  is brought into circuit and removes the danger of receiving a shock when the clips are used to make connection. In all other positions a voltage is impressed on the clips between 100 and 550 volts depending on the setting of the switch arm.

**Checking Insulation**

(Applicable to mica and paper condensers only.) Connect the test leads across the terminals of a condenser whose insulation is desired to be tested and rotate the selector switch to position 9. A good condenser or one with a high insulation should retain its charge for a long period, and the neon indicator which is in series with this condenser and the 450 volt

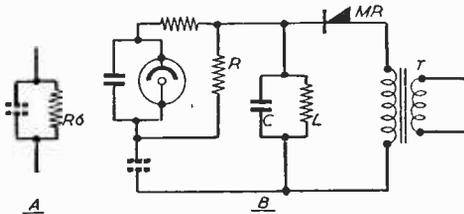


Fig. 2.—“A” shows the discharge resistor in circuit and “B” the simplified circuit of the whole system.

high tension system, should glow only once for a very brief period. This glow is due to the stress or initial charging current of the condenser. A deep momentary glow indicates a condenser of high capacity, and a weak glow a condenser of low capacity. A condenser having poor insulation will be indicated by frequent flashing of the neon, the rate of flashing depending on the loss insulation. Quantitatively, the insulation properties of the condenser can be determined from the formula  $R = 100.N$ . Where

$R$  = insulation resistance in megohms.

$N$  = number of seconds per flash.

Immediately a test has been made the selector switch should be returned to position 1 to allow the condenser to discharge.

**Re-aging Test**

To re-age electrolytic condensers that have been in store for any length of time, the procedure is to connect the condenser to the instrument test leads with due regard to polarity. Select the lowest voltage range and switch the instrument on. In most cases, particularly if the condenser is an old one, the neon indicator will be found to flash quite frequently. After a short period the flashing will have completely ceased and the insulation improved considerably. Select the next higher voltage and allow the flashing to subside. Continue in this way until the working voltage of the component is reached. Here the condenser is left to stand for at least an hour after the flashing has ceased or prolonged itself considerably. It is then discharged and taken out of circuit.

It may sometimes be found that a condenser will not reform satisfactorily at its correct working voltage. In such a case nothing else can be done and the component either rejected as a bad specimen or incorporated into a circuit where the working voltage is low and considered satisfactory for its working.

**Construction**

The layout of components in the construction of this unit is not critical, and as most constructors will have quite a number of spare parts it was decided not to give constructional details of the metalwork. It is stressed, however, that the panel layout should be so arranged as to present an all-round symmetrical appearance.

A dial should be made out of white Bristol board and fitted to the selector switch. Position 1 should be marked “DIS” to indicate discharge, while positions 2 to 8 should indicate the appropriate voltages present at those switch settings. This can best be done by connecting a multirange voltmeter to the test terminals and rotating the selector arm. Indian ink should be used to mark the dial which can afterwards be protected with a piece of 1/16in. thick clear Perspex. Position 9 should be marked “INS” to indicate insulation.

In concluding it must be pointed out that three components need special consideration and these are:

- (1) The neon lamp, which must be either a Phillips or Mazda type 110 volt S.B.C.
- (2) The mains transformer, which will have to be ordered specially and have good insulation.
- (3) The selector switch; this must be a robust component for the contacts to withstand the range of voltages specified under continuous use.

**COMPONENT LIST**

- $R_1 = 25k. 1 \text{ watt.}$
- $R_2 = 47k. 2 \text{ watt.}$
- $R_3 = 70k. 2 \text{ watt.}$
- $R_4 = 100k. 3 \text{ watt.}$
- $R_5 = 247k. \frac{1}{2} \text{ watt.}$
- $R_6 = 5k. 1 \text{ watt.}$
- $R_7 = 247k. 2 \text{ watt.}$
- $R_8 = 100k. 2 \text{ watt.}$
- $R_9 = 47k. 3 \text{ watt.}$

- $C_1 = 2 \mu F. 600 \text{ volt.}$
- $C_2 = 0.25 \mu F. 350 \text{ volt.}$

- 1 Mazda 110 volt S.B.C. Neon Lamp.
- 2 Banana plugs, black and red.
- 2 Sockets to suit above.
- 2 Crocodile clips.


- SW.1 } Yaxley type, single pole—9 way
- SW.2 } each section
- SW.3 } All ganged together.
- SW.4 }
- SW.5 }
- SW.6 = D.P. on/off Toggle Switch.

- MR.1 } = S.T.C.
- MR.2 }
- MR.3 } Type RM.1.
- MR.4 }

- 2 Fuses 1 amp., with holders.
- 1 Neon lamp holder.
- 1 Mains transformer, with Secondary tapped at 125 v., 175 v., 225 v., 275 v., 350 v., 450 v., 550 v., at 15 MA.
- 1 Small pointer knob.

**WIRELESS COILS, CHOKES AND TRANSFORMERS**  
8th Edition now ready. Price 6/- by post 6/4.

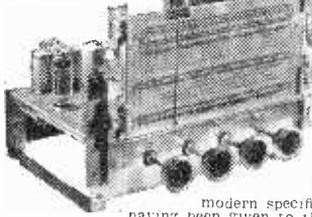**A COMPLETELY ASSEMBLED "ALL-WAVE" SUPERHET CHASSIS**



**MODERNISE YOUR OLD RADIOGRAM FOR**



We offer this Autochanger complete with Model B.3 3-waveband as advertised together with 10in. p.m. Speaker for £23 plus 10/- carr. and ins. or with BSPP Model for £26-/- plus 10/- carr. and ins.

**MODEL B.3. - A 5-valve 3 waveband Superhet Receiver for operation on A.C. mains 100-120 volts and 200-250 volt employing the very latest miniature valves. It is designed to the most modern specification, great attention having been given to the quality of reproduction which gives excellent clarity of speech and music on both Gram and Radio, making it the ideal replacement Chassis for that "old Radiogram," etc.**

**Brief specifications: - Model B.3. - Valve line up, (E)B6, 6BA6, 6AT6, 6B6, W3X4. Waveband Coverage, Short 16-50, Medium 187-550, Long 900-2,000 metres. Controls (1) Volume with on/off; (2) Tuning (Hywheel type); (3) Wave change and Gram; (4) Tone (3 position switch operative on Gram and Radio). Negative Feedback is employed over the entire audio stages. Chassis size, 11in. x 7 1/2in. x 8 1/2in. high. Price, complete and READY FOR USE, excluding speaker, £12 12/-. (Carr. and Pkr. 7/6 extra.)**


**MODEL B.3. P.P. - This model is the B.3. Receiver but incorporates two 6BV6 VALVES in PUSH-PULL, resulting in really excellent quality reproduction up to approximately 6 watts. Price £15 15/-. (Plus 7/6 carr. and ins.)**

**A 4-VALVE QUALITY "PUSH-PULL" 6-8 watt AMPLIFIER for A.C. mains.**



Incorporating Negative Feedback, Filter Input Circuit and employing 6V6s in Push-Pull. A simple arrangement is provided to enable either a magnetic-crystal or lightweight pick-up to be used, and is suitable for use with Standard or long-playing records. A tone control is incorporated, and the 10-watt output transformer is designed to match 2 to 15 ohm speakers. The overall size of the assembled chassis is 10in. x 8in. x 7 1/2in. high, and full practical diagrams are supplied. Price, including drilled chassis and valves, of complete kit, £8 17 6. Price of assembled chassis, supplied ready for use, £8 12 6. Full descriptive leaflets are available separately for 1/-.

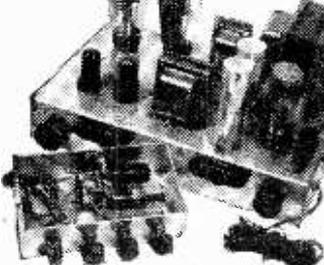**COMPLETE KIT for 12 WATT HIGH FIDELITY "Push-Pull" AMPLIFIER**



Designed for A.C. mains 200 to 250 volts, employs 6 valves plus rectifier, with negative feed-back, and comprises a main amplifier chassis and a remote controlled Pre-amplifier and Tone Control Unit, incorporating four controls—bass, treble, main volume or mixing control, and a radio, gram, microphone selector switch. This control unit measures only 7 x 4 x 2in. The measured frequency range of the amplifier with this unit shows an excellent response from 14,000 cycles down to 20 cycles, the bass and treble control allowing independent control of gain at both ends of the frequency range from zero to a gain of 50. It can be seen, therefore, that ample correction is provided to suit any type of pick-up with any type of recording, input voltage for maximum output is 70 mV. 6.3 volts at 2 amp., and 30 mA. H.T. is provided for tuning unit, and Control Unit, including drilled chassis and radio, gram, microphone selector switch. This control unit measures only 7 x 4 x 2in. The measured frequency range of the amplifier with this unit shows an excellent response from 14,000 cycles down to 20 cycles, the bass and treble control allowing independent control of gain at both ends of the frequency range from zero to a gain of 50. It can be seen, therefore, that ample correction is provided to suit any type of pick-up with any type of recording, input voltage for maximum output is 70 mV. 6.3 volts at 2 amp., and 30 mA. H.T. is provided for tuning unit, and Control Unit, including drilled chassis and radio, gram, microphone selector switch.

etc. Price of complete kit, Amplifier and Control Unit, including drilled chassis, valves, 6SNT and 6B5, £3 16 9. Complete assembly data is available separately for 1/3. Completely assembled and ready for use at £17. Please add 7/6 carr. and insurance. **THIS AMPLIFIER COMPARES WELL WITH THE WILLIAMSON AND SIMILAR DESIGNS AT A FRACTION OF THE COST.**

**A DUAL CHANNEL PRE-AMPLIFIER and TONE CONTROL UNIT**

This comprehensive PRE-AMPLIFIER and TONE CONTROL UNIT provides full control of Bass and Treble in conjunction with a main Volume Mixer Control. Can be used with any Amplifier and any Pick-up, the range of frequency control provided by the unit affording ample compensation for all types of Pick-up and all natures of recordings, i.e., English, American and Long-Playing, without recourse to pick-up correction. The extreme flexibility of the Bass and Treble Controls is such that the level of Bass and Treble can be set to suit any conditions, irrespective of the volume output of the Amplifier.

The Unit measures only 7in. x 4in. x 2in., including self-contained Power Supply, and can be accommodated either on or away from the main Amplifier, i.e., in the front panel of a Cabinet or any other position. Price, including drilled chassis, valves, 6SNT and 6B5, £3 16 9. Complete assembly data is available separately for 1/3. Completely assembled and ready for use, £5 5/-.

**The COLLARO Model A.C. 514 Record Player**



This receiver is of the very latest design covering both Long and Medium Wavebands, and includes the modern BVA miniature valves. The line up being 12BA6-12AT8-12A6-25W4. It incorporates Permeability Tuned Coils thus ensuring excellent selectivity and sensitivity. The overall size of the complete chassis including Speaker is 10 1/2in. x 4in. x 6in. An attractive Bakelite/Ivory finished Cabinet, size 11 1/2in. x 5 1/2in x 6in. is available for 16 6/- (plus 2/6 carriage and insurance).

£3/19/6 (Plus 5/- Carr. and Ins.)

RIM DRIVE 78 r.p.m. complete with the COLLARO Plug in type MAGNETIC HEAD and 10 inch TURNABLE. These are COMPLETE BRAND NEW UNITS for A.C. Mains 200-250 volts.

**A GENUINE SPECIAL OFFER! THE COLLARO 3RC/521**

**3-SPEED AUTOCHANGE UNIT**



£9/17/6

- (plus 7/6 carr. and Ins.)
- Normal price £13/10 0
- With separate Crystal-heads for STANDARD and L.P. Records.
- Incorporating Pick-up Weight Adjustment.
- Will autochange on 7in., 10in. and 12in. Records not intermixed.
- Minimum baseplate size 13in. x 12in. with height above 4in. and below baseplate 2in.
- Brand new in maker's cartons, complete with mounting instructions.

**"PERSONAL SET" BATTERY ELIMINATOR**

A complete kit of parts to build a Midget "All-dry" Battery Eliminator, giving approx. 69 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet receiver requiring H.T. and L.T. voltage as above or approx. to 69 volts. The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4in. x 1 1/2in. x 3 1/2in. Price of complete kit with easy-to-follow assembly instructions, 42 6. In addition we can offer a similar COMPLETE KIT to provide approx. 50 volts and 1.4 volts. Size of assembled Unit 7in. x 2 1/2in. x 1 1/2in. Price 47 6.

**We have a large selection of AUTOMATIC RECORD CHANGERS AT GREATLY REDUCED PRICES!!**

These units are all by the leading manufacturers and include MIXER and NON-MIXER types. All are brand new in Makers' original cartons. Send S.A.E. for full particulars.

**!! SPECIAL OFFERS !!**

- BAKER'S 12in. P.M. 15 ohm 15 watt speaker, £4/12/6
- TRIVON 12in. P.M. 23 ohm 10 watt speaker, £2/9/6 (Plus 1/3 carriage and insurance.)

**A COMPLETE 4 VALVE T.R.F. CHASSIS**

including a 5" P.M. SPEAKER and VALVES for only

£6/9/6 (plus 7/6 carr. and ins.)



**IMPROVED "MAXI-Q" CHASSIS MOUNTING COILS**



- 1 & 2 Former Mounting-Bush and Nut completely moulded in coloured polystyrene enables easy identification on both sides of chassis. No corrosion possible as in normal types of metal bush or mounting lugs. Coil can be made vibration proof and locked forever by slight application of polystyrene varnish ("DENFIX") to thread before assembly.
3. Adjustable Iron Dust Core, simplifying receiver alignment.
4. Litz windings on L.F. ranges.
5. The terminal spalls are tinned copper and form an integral part of the former.
6. Dimensions: Former length 1 1/2 in. Dia. 1 in. 0 B.A. Fixing.

The following Colour Code identifies the coils:

**BLUE:** Grid coil with aerial coupling winding. For R.F. or Mixer. Range 1-5. 3 1/11 each. Range 6-7. 3/9 each.  
**YELLOW:** Grid coil with coupling for reaction or R.F. anode. Straight detector or mixed following R.F. Range 1-5. 3 1/11 each. Range 6-7. 3/9 each.

**GREEN:** Grid coil with reaction and coupling winding (6 pin). Range 1-5. 4/9 each.  
**RED:** Superhet Osc. 465 Kc's. Range 1-5. 3/11 each. R. 6-7. 3/9 each.

**WHITE:** Superhet Osc. 1.6 Mc's. Prices as RED.  
 (Note: Ranges 6 and 7 Red can be used for various I.F.'s: no "White" coils are made for these ranges.)


RANGE	1	2	3	
Mc/s	.175 .525	.515 1.545	1.67 5.3	
Metres	1700 370	580 194	180 57	
RANGE	4	5	6	7
Mc/s	5.15	10.5 31.5	30 50	45/78
Metres	60 20	28 9.5	10/6	6.6/8.8

Complete Technical Information on the coils-DTB.1. 1/6. Formers of the above coils complete with core, any colour, 2/2 each.

SEND 9d. FOR GENERAL CATALOGUE.

**DENCO (CLACTON) LTD.,** 357/9, Old Road, Clacton-on-Sea, Essex.

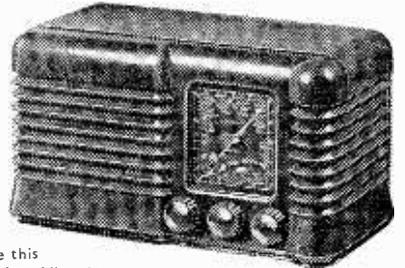**"ATOMIC"**  
**All-Mains Set for 90/-**



Using only screwdriver, pliers and soldering iron.

YOU can make this attractive 3-Valve All-mains Set (2 Wavebands). Send only 90/-, plus 3/- Carr. & Ins., and Complete Parts including Valves, Ready-to-Use Chassis, Moulded Cabinet and full, illustrated Instructions will be sent by return. YOU CAN MAKE MONEY MAKING THESE SETS FOR FRIENDS—they're simple to CONSTRUCT, astonishing VALUE.

- Send for Point-to-Point Wiring Diagram and List of Parts: 1/- POST FREE.
- Screwdriver, Pliers and Soldering Iron, only tools required.
- All parts sold separately.
- Money Back Guarantee.
- No Radio knowledge required.

**Norman H. Field,** Tel: MIDLAND 3619  
 68 HURST STREET, BIRMINGHAM 5

**VALVES YOU CAN TRUST!**

A—Makers' cartons. B—Unsealed and Boxed.

A	B	A	B	A	B
6AG5	10/6	6K7C	6/-	EA50	2/-
6AK5	9/6	6K7C	6/-	EB34	2/5
6AM6	7/9	6Q7	6/-	EB91	3/6
6P06	8/9	6Q7	11/6	EB94	8/6
6H6	4/6	6R47	5/9	EB94	8/6
6A5	6/6	6SK7	6/9	EP92	10/6
6J50T	5/-	6SK7	9/6	EP92	7/9
6J6	10/6	6V6	9/6	EP92	6/6
6J7C	6/6	6V6	7/9	EP92	6/6
6K4CT	7/6	12116	2/9	RV41	2/3 1/9
6K7	7/9	80	8/9	VU111	3/-

Any valve sent C.O.D. at makers' price.  
**SPECIAL:** Metal GKT, store solder, 5/-.  
**COAX 7fd. YD.:** Standard TV type (75/80Ω), approx. 1/4 in. dia., standard coat, limited stock.  
**JONES PLUGS & SOCKETS,** less cover, 10-wap. 10d. pair.  
**SLEEVING:** Green, 1 mm. (bore), 1 1/4 yd. Best quality. (Red and Blue, 2 mm.; Yellow, 1.5 mm.; Black, 1 mm., 2d. yd.)  
**6 MFD. 2,000V. TEST:** Metal block, 3/9, 1/- post.  
**0.25 MFD. 500V.:** Metal tubular, 6 for 2/-.  
 Post free on orders over £1.  
**REED & FORD, 2A, BURNLEY ROAD, AINSDALE, SOUTHPORT**

**MICROGRAM AMPLIFIERS**

**£3.19.6 P. & P.**  
 2/6d.

**SOUND VALUE**

Fits inside your record player leaving room for speaker. Dimensions 10in. x 3 1/2in. x 2 1/2in. 4 watts quality output. Suitable for all speakers and with standard or L.P. pick-ups. Built-in power pack for 200-250 v. A.C. only. Valves 6J7 and 6V6 available at 20/- per pair extra, if required. Other models with neg. feedback, etc.  
 6d. stamp for illustrated details.

**ELECTRO-ACOUSTIC LABS**  
 TAIN—ROSS-SHIRE, SCOTLAND

**NEW GOODS ONLY**

T—Tubular Type. C—Can. Clip Fit.  
**CONDENSERS.**—Electric. 450v. wkg. T. 8 mfd. 2/8; T. 16. 4/2; C & T. 8-3. 4/6; C. 16-24. 8/3; C. 16-32. 9/5; T. 64. 9/9; C. 61-100. 21/-; 500 v. wkg. T. 1 mfd. 8/-; T. 2/8; C. 4. 2/-; C. 8. 2/9; C. 16. 5/3; C. 32. 7/6; C. 8-8. 6/9; C. 8-16. 7/6; C. 16-16. 8/3; T. 25 x 25 v. 1/11; T. 25 x 50 v. 2/3; T. 50 x 12 v. 2/-; T. 50 x 25 v. 2/3; T. 50 x 50 v. 3/-; C. 100 x 50 v. 3/5; C. 32-32 x 50 v. 1/3.  
**TUB. PAPER.**—500 v. wkg. up to 500s. 80/- to 00s. 94/-; to 04. 11d.; .05 and .1. 1/1; .2 and .25. 1/6; .5. 2/3.  
**SIL. MICA,** 500 v. wkg. up to 100 pf. 9d.; to 500 1/-; to 1,000. 1/2; 2,000 and 3,000. 1/2.  
**VOL. CONTLS.**—Lg. Spdls. all values. 2/- with SW. 5/-; with DP. SW. 5/9.  
**RESISTORS.**—Carb. all Std. values. 20% tol. watt. 4d. w. 5d.; 1 w. 7d.; 1 w. 11d.; W. Wound. 3 w. to 5 K. 1/9. 5 w. to 5 K. 2/-; 5 w. to 50 K. 2/6; 10 w. to 30 K. 2/8.  
 Terms: Orders up to 10/- post 6d., up to £1. post 9d., over P free. Cash with order.  
**RADIOLECTRON,** 22, Frances St, Scunthorpe, Lincs

**EX-GOV'T. VALVES.**—Tested. EA50, EB34. 2/-; SP61. VU111. 2/6; EF36. 3/9; EF3E. EF50. EF54. EC52. VU39A. 4/6.  
**DROPPERS.**—Slider. 1,000 ohms. 2 a. 750 ohms. 3 a. 4/9; Min. 4 v. Buzzers. 2/6.  
**CONDENSERS.**—8 450. 1/6; 32 350. 2/3; 16 x 16 275. 2/6; 16 x 32 275. 2/11; 32 150. 1/6.  
**VOL. CONTROLS.**—Lrg. Sp. 1 M. 2/6; S.P. Sw. 3/6; D.P. Sw. 5/6; 1 in Sp. D.P. Sw. 3/6; Wirewound 20 K. 25 K. 1/9.  
**METERS.**—2 1/2 in. 0-15 volts A.C. D.C. 8/6.  
**UNIVERSAL SHUNTS.**—High accuracy wirewound shunts for extending the range of 1 milliamp. or 500 microamp. meters of any internal resistance. Only one simple adjustment to make, no calibrating meter being required. Boxed, with instructions and one year's guarantee. 5 Range Model. 11-. 550s (1 mA.), covers 1. 5. 20. 100 and 500 mA. 551 (1 mA.), covers 2. 10. 50. 200 and 500 mA.  
**VUEWMASTER** Sound Vision Chassis. 24 to 67 1/2 G. assembled, aligned and tested. Stamp for lists. Postage extra under £2.  
**MASSEY,** 58, WAKEFIELD AVENUE, HULL.

**H.A.C. SHORT WAVE EQUIPMENT**

Noted for over 18 years for...  
 S.W. Receivers and Kits of Quality.

Improved designs with Denco coils:  
**One-Valve Kit, Model "C"** Price, 25/-  
**Two " " " " "E" " " " "** 50/-

All kits complete with all components, accessories, and full instructions. Before ordering call and inspect a demonstration receiver, or send stamped, addressed envelope for descriptive catalogue.

**"H.A.C." SHORT-WAVE PRODUCTS**  
 (Dept. TH), 11, Old Bond Street, London, W.1.

**Television, Radio, Record CABINETS MADE TO ORDER**

ANY SIZE OR FINISH  
 CALL OR SEND DRAWINGS FOR QUOTATION

**B. KOSKIE**  
 (DEPT. C.)

72-76 Leather Lane, Holborn, E.C.1

Phone: CHAncery 6791/2

# Unorthodox Anti-fading Receiver

SOME NOVEL CIRCUIT ARRANGEMENTS FOR ISOLATED OR REMOTE AREAS

By Wm. Nimmons

**I**N the February, 1947, issue of this journal there appeared an article on a "Two-Programme Receiver" by the present writer. To recapitulate, the receiver was something of a compromise: it attempted to do two things at once, (a) to provide the ordinary loudspeaker reception from a number of stations, and (b) to provide an alternative station on headphones so that anyone who wished could concentrate on a serious talk or lecture on the headphones while others in the same room could indulge in jazz or light music.

The method by which this was achieved was as follows: a wavetrapp was inserted in the aerial lead, but instead of the energy being allowed to go to waste, the top end of the wavetrapp winding was taken to the grid of a detector valve. That is, when the wavetrapp was tuned to the desired station (from the point of view of the listener to the lecture) the energy circulating in the wavetrapp was utilised for that purpose. At the same time, this did not interfere in the least with the reception of other stations on the loudspeaker, as is customary with the insertion of a wavetrapp in the aerial lead of a receiver.

Since then another use for this wavetrapp-in-the-aerial method of reception has occurred to the writer. There are areas in the country which do not enjoy uninterrupted continuity of reception. Such an area is the east coast of Co. Down, and there are others. The main obstacle to good reception in Co. Down appears to be the encroachment or "mingling" of the wave from the Northern Ireland station and that from the North region. As these are on the same wavelength there appears little that can be done to counteract the fading.

But in other parts of the country there is fading pure and simple. As several stations carry the same programme it occurred to the writer: why not tune the wavetrapp to one station, and what may be described as the main part of the set to another station? The combined outputs of the two stations would (theoretically) emerge as a signal twice as great as any one of them, and could be fed to an amplifying or output valve in the usual way. Since, for distances in this country, the reception would be practically instantaneous, there would be no echo or other untoward effect.

Since the two stations are carrying the same programme, and since it would be unlikely for both stations to fade at the same time, there would appear to be a great advantage in this method of reception. Even if one station faded

completely, it would give a ratio of good reception of 1/2: in other words, the strength of the signal would only fade to half of its former value, which is a diminution scarcely to be noticed at loud volume levels and which would ensure continuity of reception.

## The Circuit

Accordingly, a set was made up, details of which can be seen in Fig. 1. It will be seen that the first part of the circuit (nearest the aerial) is in reality a wavetrapp, but with the difference that instead of ending with a coil and condenser it goes on to include a leaky-grid detector, together with its associated H.T. equipment.

Following on the wavetrapp, we have the standard leaky-grid detector consisting of a second coil and condenser feeding a detector valve which has the usual H.T. circuit. Both valves are provided with reaction to sharpen the tuning and increase signal strength, the reaction being provided by a differential condenser together with an H.F. choke in each anode circuit.

The method of coupling to the output valve is simple and effective. Both outputs (of the detector valves) are taken via a .5  $\mu$ F condenser to the same terminal of the primary of a parallel-feed transformer, the other side of which goes to the earth line. Thus, the combined outputs are fed through the primary of the transformer, the secondary of which behaves in the normal manner.

The circuit is a little tricky to tune at first, since we have no means of knowing which station is "coming through." However, by fitting a switch

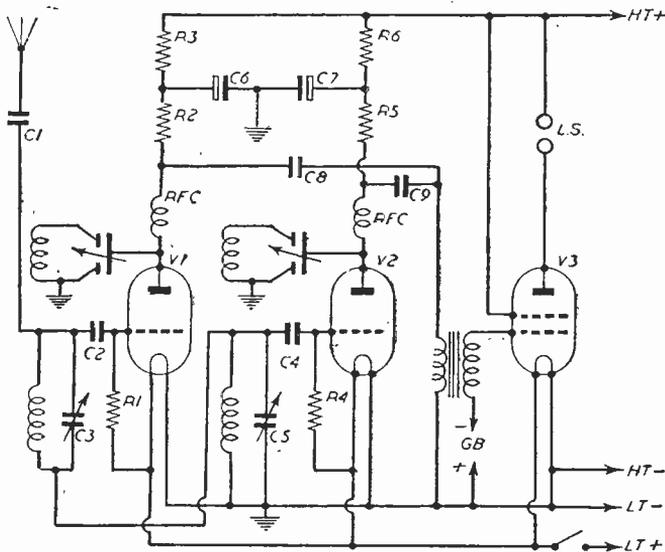


Fig. 1.—A simple dual-channel receiver.

in the filament legs of the two detector valves, and cutting out each in turn, the appropriate station may be tuned in. If one station is stronger than the other, this station should be tuned on the wavetraps, since this will prevent spreading on the other dial.

It was felt, however, that Fig. 1 as it stands was not very satisfactory from the point of view of anyone experiencing fading from a particular station. For one thing, fading occurs at extreme ranges, and the plain detector valve is not much use at such ranges. At least one stage of high-frequency amplification would be necessary.

**Adding H.F.**

This resulted in Fig. 2. Here we have the wavetraps at A, B being the orthodox main circuit. A is the wavetraps followed by an H.F. valve instead of the plain detector, with the detector following. The coils,  $L_1$  and  $L_2$ , behave like a wavetraps, and may be the usual dual-range coil, although the medium-wave winding only is shown.  $L_3$  and  $L_4$  are similar. The two detector valves are provided with reaction, and the method of passing on the signals to the output valve is similar to that of Fig. 1

As an experimental receiver, this set-up presents some curious features. It is as well that we should be clear just what we are trying to do before we start tuning the arrangement. We have to set A (and, of course, its associated tuning condenser in the grid circuit of the following detector valve) so that it absorbs energy from a particular station, this station being one of two we have selected as carrying the same programme. If it carries a

different programme from the station selected by B then both will go forward together!

They will, in fact, be conveyed via the two .5  $\mu\text{F}$  condensers to the primary of the transformer, and hence be amplified by the output valve. As such a cacophony is useless from the programme point of view steps should be taken to ensure that the two halves of the set are carrying the same programme.

For this reason, it is nearly always impossible to receive foreign programmes on the dual system. It is, of course, possible to cut out the wavetraps by bridging it with a switch; the set then behaves like any other 3-valver, and it is possible to receive foreign broadcasts.

But for general use, in the manner in which the set is designed, it is usually only possible to receive the Home, Light and Third programmes. This can be done by selecting for, say, the Home Service, two stations as far apart as possible on the dials, and tuning one in on the wavetraps and the other on the main tuner. The Third Programme is the one most likely to be affected by fading, and fortunately the two wavelengths are well separated. As the Light Programme is also transmitted on the long waves it is not so liable to fading; but if a medium and a long-wave station are received the medium-wave station should be received on the wavetraps. The reason for this will become obvious when we see that if the long-wave winding were interposed *before* the medium-wave winding it would seriously interfere with the functioning of the latter.

There are some points worth mentioning with regard to the tuning. The first is that if we tune in the wavetraps to a powerful station and then leave it and transfer our attention to the main tuner, we may get something of a shock. The station seems to spread all over the dial! What is happening is that the signal is being carried forward quite independently of the main tuning, but such is the power of habit that we consider the tuning of this section hopelessly unselective. However, by tuning the main section to the same programme on another station we have achieved our object!

The second curious point about the tuning is that all stations are displaced upwards on the main tuner—that is, the tuner nearest the earth in Fig. 2. This is surprising, since the interposition of a wavetraps does not usually displace the position on the dial of stations to which it is not tuned. Be that as it may, the fact remains that all stations are displaced upwards by


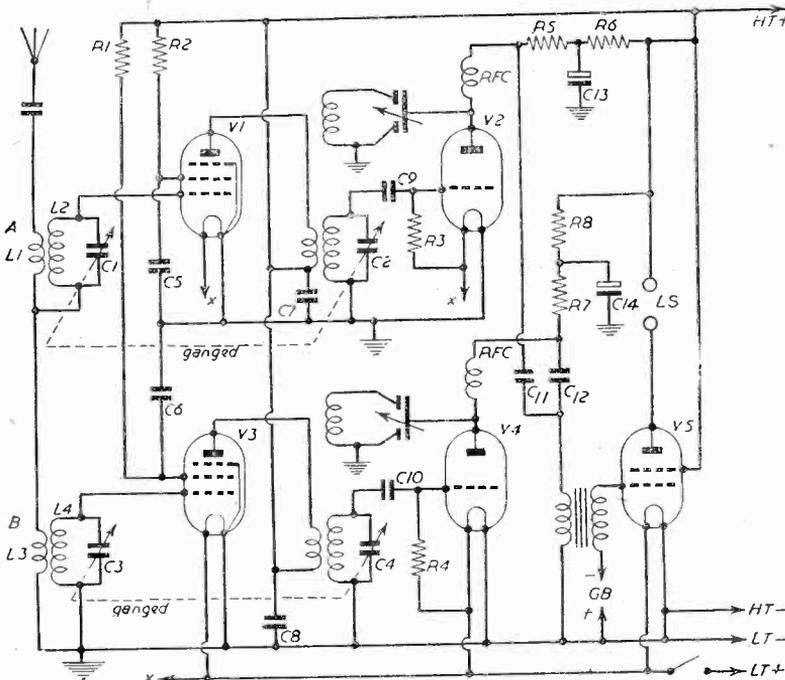


Fig. 2.—A more comprehensive receiver. The wavetraps circuit is associated with V1.

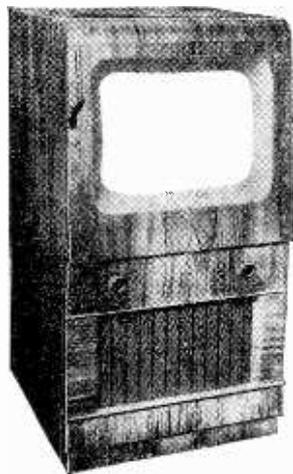

# “Superior 15”

## SOME QUESTIONS ANSWERED—

### QUESTION

*Can I expect sound and pictures equal to factory made sets?*

*Is it robust and likely to go for long periods without trouble?*

*Why is it so much cheaper than any other big picture televisor?*

*Does it look like a home-made set?*

*How about soldering? Is it difficult like repairing a kettle or saucepan?*

*Is aligning the set difficult?*

*Will the Elpreq “Superior 15” receive all B.B.C. stations?*

*What happens if I cannot get my televisor to work once I have finished?*

### ANSWER

The picture compared favourably with any set at the Radio Show.

Yes, because all parts are standard size and proved types.

The reason is because you assemble it yourself and thus save labour and other costs.

No, because it isn't really home made, it is simply assembled from factory made parts, just as are all so-called “factory made” TV models.


Soldering radio parts is simplicity itself.

No, the coils are all specially designed which “pre-align” them and you have only to follow the simple directions to ensure receiving the perfect picture. No instruments are necessary.

Yes, and all constructors will be notified of the modifications that will be necessary when Commercial TV starts.

You send for a service form which you complete and then our engineer will indicate your trouble. Alternatively, for a nominal charge, we will take your chassis and make it perfect.

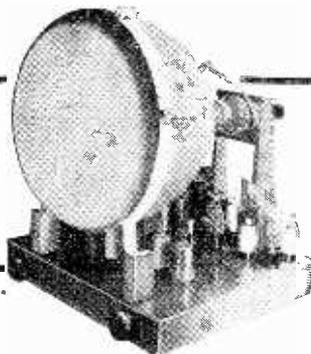**UP TO THE  
MINUTE BIG  
PICTURE T.V.**



**ONLY £37. 10  
OR £12. 10  
DEPOSIT**

### —MORE QUESTIONS ANSWERED

#### QUESTION

*What is the cost?*

*Are Hire Purchase terms available?*

*Are there any guarantees?*

*Are cabinets available?*

*How much is the data and can I have it on approval?*

*How can I order?*

#### ANSWER

All components, valves and Cosor 15in. cathode ray tube cost £37-10-0.


Yes, the deposit is £12-10-0, the balance is spread over 12 months.

You are covered by two guarantees, one covers the components and the other ensures that you will get perfect results.

The illustrations show the cabinets which are available. The Console costs £11-10-0 and the Super corner model £18-0-0. H.P. terms again are available.

The data costs 7/6, but providing you keep it clean and in good condition you can return it within 7 days if you think you cannot make the televisor (7/- will be refunded to you).

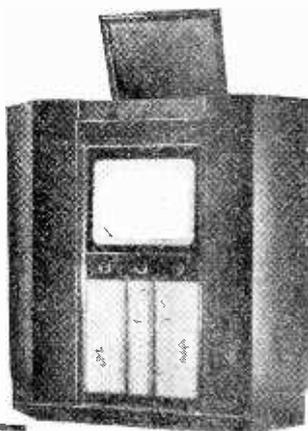An order form is enclosed with the 7/6 data, which you can complete and post to us.



### —As Demonstrated at the National Radio Show

## ELECTRONIC PRECISION EQUIPMENT LTD.

Post orders should be addressed to: — **ELPREQ HOUSE (Ref 7.), HIGH STREET, WEALDSTONE, MIDDX.**

42-46, WINDMILL HILL, RUISLIP, MIDDX.  
Phone: RUISLIP 5780.  
Half-day, Wednesday.

Personal shoppers however should call at: —

152-153, FLEET STREET, E.C.4.  
Phone: CENTRAL 2533.  
Half-day, Saturday

29, STROUD GREEN ROAD, FINSBURY PARK.  
Half-day, Thursday.

**Best Buy at Britain's**

**TELEVISION RECTIFIERS.** 3in. long. 2in. dia. 235 volts A.C. input. Type A—Output 300 mA. at 13.6. Type B—Output 300 mA. at 14.6. BRAND NEW. Postage 1/ extra.

**RF26 and RF27 UNITS.** Brand new and boxed. RF26 for 50-85 Mc.s. and RF27 for 65-85 Mc.s. Either type ONLY 45/- plus 2/- post.

**10mF. CONDENSERS.** paper block. 1,000 volt test. 600 v. working. New and boxed at 3 for 10.6.

**R1139A complete.** brand new receiver for 100-124 Mc.s. Easily altered for other frequencies. With 11 valves and circuit, only 45/- plus 7/6 cart.

**R1155.** Brand new at £11.19.6. A few soiled at £7.18.6. All these sets are tested prior to despatch. Carriage 10/- extra. Send 1/3 for circuit and data.

**R1155 POWER PACKS.** Three types available—£4.10.0. £5.5.0 and £6.10.0. Send S.A.F. for details. Packs are guaranteed six months.

**A2074** contains standard mains transformer 315-0-315 v. 70 mA. 6.3 v. 2 A. and 5 v. 2 A. (Admiralty rating), paper smoothings, 10 Hy. choke and countless other components. All in steel case 11in. x 6in. x 18in. and in mint condition. BARGAIN PRICE £7.6. plus 9/- cart.

**EF50 Sylvania** at 8/6 for British EF50 at 6/6. VT501 (TT1) at 5/-. Postage extra. **100 MICRO-AMP Meter** 3in. range, panel mounting. Brand new at 42/6 each.

**METAL RECTIFIERS—NEW.** 6 or 12 volts. 1 Amp. at 7.6. 2 Amp. at 11.3. 3 Amp. at 12.6. 4 Amp. at 15/-. These are fullwave bridge type.

**CHOKES.** 5 Hy. 309 mA. 500 ohms, potted, chassis mounting. Beautiful job, only 12/8 new boxed. 30 Hy. 150 mA. 300 ohms, universal mtz., 10/6 each.



**CHARLES BRITAIN (RADIO) LTD.**

11, Upper Saint Martin's Lane, London, W.C.2. TEM 0545  
Shop hours, 9-6 p.m. (9-1 p.m. Thursday)  
OPEN ALL DAY SATURDAY

**5 in 3**

Free leaflet tells how range extender gives 3 octaves from 30 valve electronic keyboard. Imitates whole orchestra. Is simply built from simple instructions. Get your free copy now. . . .

**C & S, 10 Duke St., Darlington, Co. Durham**

**SPECIAL OFFER**

**GUARANTEED EX-W.D. VALVES**

6V6G, 6T, 5U4G, 6FG, Y63-6A8, EF53, at 8/6. 6K7M, 6SA7M, 6Y4, 6Y5, 6AG5, at 7/6; 6K7G, 6U5M, at 6/6; EF50, 12Y4, at 5/-; 6J5G, VU12A, at 4/6.

**E.H.T. TRANSFORMER.**—5.6 Kv. with U22 Rectifier, 37/6 Plus 2/- P.P.

**FRAME TRANSFORMER.**—Ratio 10 to 1. MATCHES ALLEN or DENCO wide angle Def. Coils, size 3in. x 3in., 10/- P.P. 1/-.

**AIR-SPACED FIL TRANSFORMERS.**—In 230, out 2v. 2 a., 11/6; in 230, out 6.5v. 2 a., 15/6; in 230, out 2v. 3v.-6.3v. 2 a., 24/-.

**HUNDREDS OF BARGAINS IN RADIO AND TV COMPONENTS.** Send stamp for list.

**JACKSON'S RADIO SUPPLIES**

163, EDGWARE ROAD, LONDON, W.2.

**SOUND MASTER**

and **P.W. CORONET FOUR COMPONENTS ALWAYS IN STOCK**

Separate price lists for these and constructor televisions available on request

**J. T. FILMER,**

MAYPOLE ESTATE, BEXLEY, KENT  
Tel.: Bexleyheath 7267

**COPPER WIRE**

ENAMELLED		TINNED	
S.W.G.	2 ozs. 4 ozs.	2 ozs. 4 ozs.	
16	1/4 2/-	1/4 2/-	
17	1/4 2/1	1/4 2/1	
18	1/4 2/2	1/4 2/2	
19	1/4 2/3	—	
20	1/5 2/4	1/5 2/4	
21	1/5 2/5	1/6 2/5	
22	1/6 2/6	1/6 2/6	
23	1/7 2/7	1/7 2/7	
24	1/7 2/8	1/7 2/8	
25	1/8 2/9	1/8 2/9	
26	1/8 2/10	1/8 2/10	
27	1/9 2/11	1/9 2/11	
28	1/9 3/-	1/9 3/-	
29	1/10 3/1	1/10 3/1	
30	1/10 3/2	1/11 3/5	
31	1/11 3/3	2/- 3/1	
32	1/12 3/4	2/1 3/8	
33	2/- 3/5	2/2 3/10	
34	2/- 3/6	2/3 4/-	
35	2/1 3/7	2/4 4/2	
36	2/1 3/8	2/6 4/5	
37	2/2 3/10	2/7 4/8	
38	2/3 4/-	2/9 4/11	
39	2/4 4/2	2/10 5/2	
40	2/5 4/4	3/- 5/6	

POSTAGE EXTRA.

POST ORDERS ONLY PLEASE.  
Send stamp for comprehensive lists.

**CRYSTAL SET**

INCORPORATING THE SILICON CRYSTAL VALVE

Adjustable Iron Cored Coil.

**RECEPTION GUARANTEED**  
Polished wood cabinet. 15/-, post 1/-  
A REAL CRYSTAL SET, NOT A TOY

**POST RADIO SUPPLIES**  
33 Bourne Gardens, London, E.4

**VALVES**

NEW AND BOXED—ALL GUARANTEED.

Send 21d. Stamp for Full List.

6F33	9/6	12AT7	9/6	7F7	8/6
12AX7	9/6	6BE6	9/-	X78	11/6
354	9/6	12BA3	9/-	6CH6	9/-
EL81	7/6	6AU6	9/-	12AU7	12/6
6C4	6/6	6BR7	12/6	GT1C	10/6
6AG5	6/6	12BE6	9/-	KT33C	9/6
EA401	8/6	12AT5	10/-	EL32	6/6
6N7	6/6	5Y6	9/6	EF36	5/-
6SF5	7/6	6BA6	9/-	UF41	9/6
6L7	5/6	6AK5	8/6	EF92	6/6
6F7	7/6	6J6G	8/6	1L4	6/6
6I6	7/6	6CH2	10/6	Q21	7/6
6BW3	9/-	18BT	11/8	12SK7	6/6
6J4	14/6	18BTA	12/6	CV284	9/6
6SA7	7/6	5R4G	12/6	CV286	10/6
6SK7	7/6	HL2JDD	9/-	CV287	11/6
6SN7	9/-	V23	6/6	85A2	13/6
6SL7	8/6	ECC33	7/6	6V6	8/6
6AT6	9/-	TP25	12/6	EX91	7/6

Postage 9d. on orders under £2.

**ELECTRAD RADIO**

5, DONEGALL STREET, BELFAST, N.I.

**WATERLOO RADIO**

**METAL RECTIFIERS.**—Bridge 12v. 2 amp. 11/3; 3 amp. 12/6; 4 amp. 15/-; 5 amp. 23/6. Half-wave 125v. A.C. input. RML 60 mA. 3/9; RME 100 mA. 4/3; RML3, 125 mA. 5/3; RMA, 250v. 275 mA. 15/6.

**VALVES.**—6AM6, 6CH6, 6BA8, 6BE6, 6BW7, 12BE6, 6G6, 6D6, 3A4, 1U5, 1T4, 6AL5, W7, N18, 6B3, 50C5, 1S5, 12AX7, 7/6 each, 3 for 20/-; 6K8gt, 12K8gt, 1R5, 5763, VR150/30, 9BH7, 9/6 each.

**CHARGER TRANSFORMERS.**—Input 200-250v. 50 c.p.s. A.C. to charge 6 or 12 volts at 1.5 amps. 12/5; 3 amps. 21/6; 6 amps 29/3. 1 post 1/-.

**LOUDSPEAKERS.**—3in., 4in., 5in., 14/6; 6in., 15/0; 8in., 10in., 22/6. Post 1/-.

**GERMANIUM DIODES.**—2/- each.

35, Tenison Way (Waterloo Bridge Roundabout), London, S.E.1.

**FREQUENCY CRYSTALS.** 5.8 to 8.5 Mc/s in 25 Kcs. steps. 5/6 and 8/-. List supplied.

**SPECIAL OFFER.** New and boxed ARP12 VP23 valves. 5/6 each, 4 for £1.

**FISHING ROD AERIALS** 12ft., Set 3. 7/6. Mounting Base. 3/6.

**0-5 AMPMETERS.** 2 in. square M/c. 11/-  
**GERMANIUM DIODES.** 3/9.

**P.M. SPEAKERS.** 8in., 20/-; 5in., 14/6; 6in., 16/6; 10in., 27/6. Leading makes.

**SELENIUM RECTIFIERS.** F.W. 6 or 12v. 4 A., 22/6; 6 A., 30/-; 3 A., 14/6; 100 mA. 3/6; 1 A., 8/6; 24v. 2 A., 30/-; 250v. 100 mA. H.W. 9/-; 80 mA., 6/6; 250v. 275 mA., 17/6.

**TRANSFORMERS.** 200-240 volts, tapped 24-5-8-8-9-10-12-15-18-20-24 and 30 volts at 4 A., 21/6. One year guarantee.

**M/C MICROPHONES AND TRANSFORMERS.** 15/6.

**EX-W.D. PHONES.** Low Resistance. 8/6.

**MINIATURE VALVES.** New. 5001, 6062, 9003, 7/6; 6AG5, 1S4, 1S5, 1T4, 1R5, 10/6; 6AL5, 8/8; 12AT7, 6AM6, DH77, 6AT5, EF91, EF92, EX51, 6BE6, 11/6.

**NEW VALVES.** 35Z4, 35L8, 25Z4, 25L6, 42, 80, 11-/-; 6B3GT, 6K7GT, 6V6GT, 50L6, 42, 80, 11-/-; 6B3GT, 11/26, 12/6.

**MULTIMETER KIT.** 2 1/2 in. M/c calibrated meter. D.C. 0-300, 0-300-150-200 and 600, 0 A., 0-80. Black ebonite case. Also reads 0-5,000 ohms with 11v. battery. 25/6.

**V. VIBRATOR UNITS.** Output 250v., 60 mA., 22/6. Complete in steel case.

**TR1106.** Transmitter Section. New and complete. 4.8 Mc/s. Easily converted. Less valves. 15/-; with valves, £2.

**FREESTYLE TELEPHONE CARBON MICROPHONES.** 3/-, Throat Microphones with cord and plug, 4/-.

ALL POST PAID IN U.K.  
**THE RADIO & ELECTRICAL MART**  
253b, Portobello Road, London, W.11.  
Phone: Park 6026.

**TESTOSCOPES Mains Tester**

For high and low voltage testing—1-30 and 100-650 volts A.C. or D.C.

Write for interesting leaflet 29F.

**RUNBAKEN-MANCHESTER**

**TELEKIT SUPPLY**

**VOLUME CONTROLS.**—1, 1 and 1 meg., long spindles 2/6. Complete kit of parts (including valves) for tube, re-record/playback 4 watt amplifier, £9. **VIBRATORS.**—12 v., 4-pin, 5/-; **TUBULAR CONDENSERS.**—05 pF at 3,500v., 2/6

**VALVES NEW & SURPLUS. GUARANTEED.**

CV181	6/-	6AC7, 12A6,	1207	8/6	
VR1	7/6	55H7 (soiled)	12CW6	6/-	
6AT9	7/6	5/- each.	15D2	4/6	
6B7	8/6	6X4	6/6	EF50	5/-
6K7	4/-	6A8	8/6	6AM6	6/6
6Z4	6/-	6B9	6/-	1L4	5/6
OD8	4/-	6BE6	7/-	12S9 (soiled)	4/6
1T4	6/6	6B46	7/-	5/-	
1S5	6/6	6J3	5/-	12AT7	7/-
3V4	6/6	6AL5	7/6	6BW6	8/-
7S7	6/-	7H7	6/-	6CH6	8/6
1L5 (soiled)	3Q4	7/6	W77	7/6	
	5/-	12K3	8/-	AL60	4/6

Send your enquiries for Radio, TV and Electrical Goods to: Chantry Lane Works, Chantry Lane, Bromley, Kent. Phone: Rav. 5845.

**TELETRON SUPER INDUCTOR COILS.**

Miniature dust core types. Dual Wave TRF pre-aligned 7/9r Types. HAX Triple wound for crystal diodes. Q100. Gain 33. No overlap. 3/5/Het. coils AE and OSC. All Bands. 6/9r. 1E7's 12/6 pr., etc. Stamp for list and coupon.

**THE TELETRON CO.**  
286, Nightingale Road, London, N.9.

about 10 degrees on the condenser scale.

The use of an entirely separate L.T. battery to supply  $V_1$  and  $V_2$ , with no connection whatever to earth, did not cure this curious fault. Bearing in mind that this is a purely experimental receiver, with a considerable amount of experimental work still to be done on it, it is possible that the application of a bias to valves  $V_1$  and  $V_2$  will materially increase the "normality" of the receiver. This can be done by breaking the connection to earth at the bottom of  $L_3$  and  $L_4$  (in Fig. 2) and connecting the slider of a potentiometer to the bottom of  $L_3$ , one side of the potentiometer going to the earth line and the other to a negative bias. The junction of the slider and the earth line should be spanned by a .1  $\mu\text{F}$  condenser.

When this is done the application of bias will be made to valves  $V_1$  and  $V_2$ .

Would not an ordinary double-diode-triode with automatic volume control do all that is necessary?

The answer is that on the fringe areas of the

transmission the fluctuations in signal strength are so great, and moreover are accompanied by distortion, that the average automatic volume control system is quite inadequate to deal with them. By having the set tuned to a station which is behaving normally, however, the fading station is masked by the overwhelming strength of the sound one.

For those with an itch to experiment, Fig. 2 should give ample scope. Fig. 3 is a rather different type of circuit. In this there is no wavetrapp circuit, but the first two valves are duplicated and their outputs fed to the single output valve in the manner with which we are familiar. It will be seen that in this case two separate aerials are required.

As will be seen in Fig. 3,  $V_1$  and  $V_2$  form one part of the receiver, and are intended to tune in one of the stations; while  $V_3$  and  $V_4$  form another part and are intended to tune in the other station. Both stations are combined in the output, and if only one fades at a time the output will be only at most 50 per cent. down.

LIST OF COMPONENTS

Fig. 1.—C1, .0001  $\mu\text{F}$ ; C2, .0001  $\mu\text{F}$ ; C3, .0005  $\mu\text{F}$ ; C4, .0001  $\mu\text{F}$ ; C5, .0005  $\mu\text{F}$ ; C6, 2  $\mu\text{F}$ ; C7, 2  $\mu\text{F}$ ; C8, .5  $\mu\text{F}$ ; C9, .5  $\mu\text{F}$ ; R1, 1 megohm; R2, 30 K $\Omega$ ; R3, 20 K $\Omega$ ; R4, 1 megohm; R5, 30 K $\Omega$ ; R6, 20 K $\Omega$ .

Fig. 2.—C1, .0005  $\mu\text{F}$ ; C2, .0005  $\mu\text{F}$ ; C3, .0005  $\mu\text{F}$ ; C4, .0005  $\mu\text{F}$ ; C5, .1  $\mu\text{F}$ ; C6, .1  $\mu\text{F}$ ; C7, .1  $\mu\text{F}$ ; C8, .1  $\mu\text{F}$ ; C9, .0001  $\mu\text{F}$ ; C10, .0001  $\mu\text{F}$ ; C11, .5  $\mu\text{F}$ ; C12, .5  $\mu\text{F}$ ; C13, 2  $\mu\text{F}$ ; C14, 2  $\mu\text{F}$ ; R1, 100 K $\Omega$ ; R2, 100 K $\Omega$ ; R3, 1

megohm; R4, 1 megohm; R5, 30 K $\Omega$ ; R6, 20 K $\Omega$ ; R7, 30 K $\Omega$ ; R8, 20 K $\Omega$ .

Fig. 3.—C1, .0001  $\mu\text{F}$ ; C2, .0001  $\mu\text{F}$ ; C3, .0005  $\mu\text{F}$ ; C4, .0005  $\mu\text{F}$ ; C5, .0005  $\mu\text{F}$ ; C6, .0005  $\mu\text{F}$ ; C7, .1  $\mu\text{F}$ ; C8, .1  $\mu\text{F}$ ; C9, .1  $\mu\text{F}$ ; C10, .1  $\mu\text{F}$ ; C11, .1  $\mu\text{F}$ ; C12, .1  $\mu\text{F}$ ; C13, 2  $\mu\text{F}$ ; C14, .0001  $\mu\text{F}$ ; C15, .0001  $\mu\text{F}$ ; C16, .5  $\mu\text{F}$ ; C17, .5  $\mu\text{F}$ ; C18, 2  $\mu\text{F}$ ; R1, 100 K $\Omega$ ; R2, 100 K $\Omega$ ; R3, 5 K $\Omega$ ; R4, 5 K $\Omega$ ; R5, 1 megohm; R6, 1 megohm; R7, 30 K $\Omega$ ; R8, 20 K $\Omega$ ; R9, 30 K $\Omega$ ; R10, 20 K $\Omega$ .


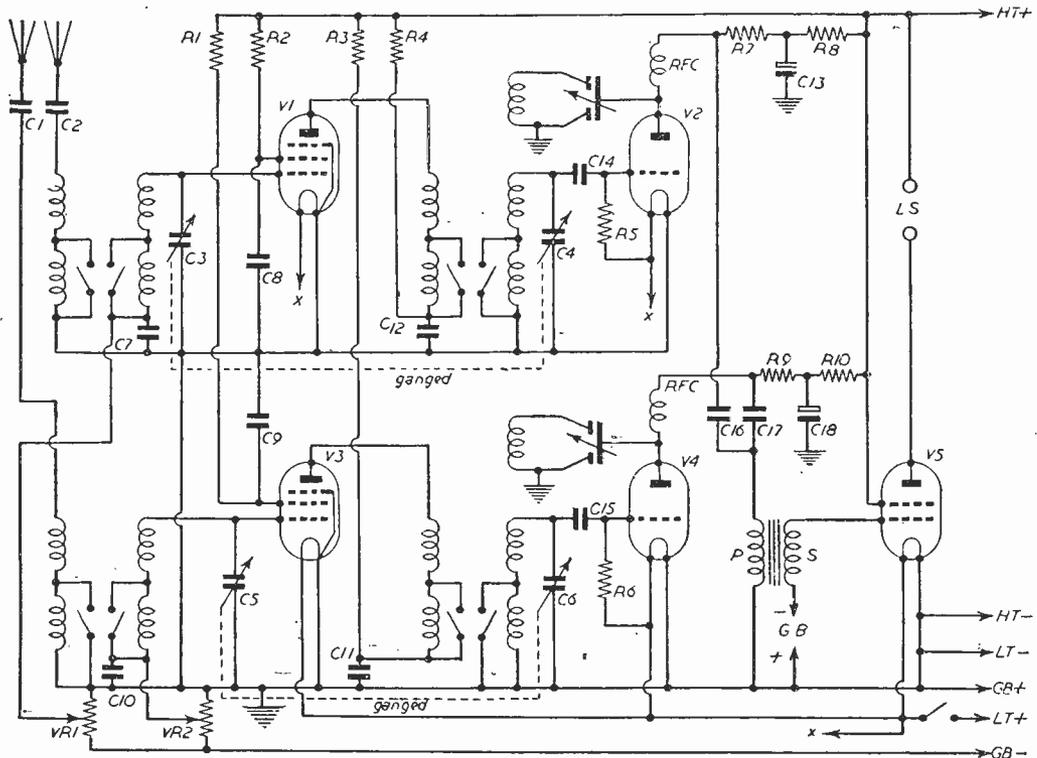


Fig. 3.—Another type of dual-channel receiver.

# Programme Pointers

By MAURICE REEVE

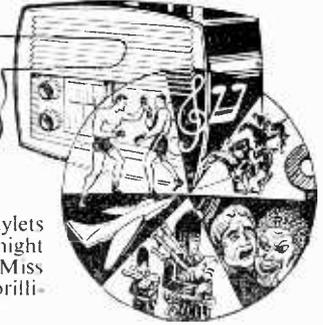

## Drama

THERE is nothing quite like Shakespeare as radio material, so far as the spoken word is concerned. This is so universal in its embracement, so colourful in its idiom and so powerful in its appeal, that, given first-class delivery—which it invariably gets on the BBC—it is bound to succeed. As with Beethoven's music—which, alas, has usually to carry the heavy cross of annotation and explanation, meticulously and boringly repeated at each performance—no descriptive notes are necessary: the genius of the work is self-evident; its message stands forth four square.

Two notable examples were offered us last month, each from opposite ends of the poet's vision. High tragedy in "Othello" and fairy comedy in "The Dream," the latter being particularly attractive by virtue of Mendelssohn's incomparable incidental music in full, beautifully played by the Royal Philharmonic Orchestra under John Hollingsworth.

Very long casts must receive a general congratulation with special tributes to Joan Hart as Desdemona and Sir Ralph Richardson as Bottom the Weaver.

Marlowe's "Dido, Queen of Carthage" was also well worth doing. Unlike the works of Shakespeare, it must have been new territory to many listeners as it was to their contributor, who had hitherto only read it. Pamela Brown and Sebastian Shaw headed a notable cast, one and all of which vividly portrayed the famous tragedy.

"Anna Christie" was revived—I hardly know why, especially as it was played just before the author's death. Joan Millar was the star who chose it in the Wednesday evening series. She occasionally lost her assumed American veneer in her moments of highest passion of which there are not a few.

"The Hanging Judge" was Boris Karloff's choice in the same series. An exciting piece in which, after sentencing a man to death early on, the "double life" of the judge, Sir Francis Brittain, is gradually revealed. It reminded me of Robert Hitchen's much more exciting novel, "The Paradine Case." "Hanging Judge" is by Raymond Massey, from a novel by Bruce Hamilton. So characteristic is Boris Karloff's voice, and so well known from years of film fame, that I am sure I should have recognised it without the aid of *The Radio Times*. This was the last piece put on by the late Sir Godfrey Tearle.

## Comedy

"Once in a Lifetime," a story of the early days of Hollywood by G. S. Kaufman and Moss Hart, is a very clever and witty satire on some of the nit-wits who manage to do well for themselves in such industries as film making, but it lacked snap and sparkle in production. One thought of Harry Green in "Fifty Fifty" with regret.

Diana Churchill broke new ground with her Wednesday night "choice," Noel Coward's brilliant

triple bill of playlets with the title "To-night at Eight-thirty." Miss Churchill was most brilliant and versatile.

## "What Do You Know?"

The noises which emanate from musical instruments, either solo or in combination, are largely pleasant or unpleasant according to taste, and sometimes to context. But surely there can only be one opinion of the "musical interpolation" of that very entertaining show, "What Do You Know?", and that is, hideous. Furthermore, it is quite unnecessary.

## Success of Buchanan

Jack Buchanan makes a most likeable and entertaining "Master of Ceremonies" in the "Forces Show." His suave and urbane sophistication, helped by his faultless technique and long experience, are most agreeable. Furthermore, each time I have heard this show, he has been provided with a very good script.

## Beecham Concerts

Two magnificent Beecham concerts adorned the past month, one with the BBC symphony orchestra and the other with his own Royal Philharmonic. No fewer than three Beethoven symphonies were in the two programmes, the third, sixth and seventh, a feast from Sir Thomas, who doesn't give us too much Beethoven. The finale of the seventh restored our faith in the classic masterpieces and convinced one that, given the right kind of performance, they can never become hackneyed.

This may be the best place to mention "Eugene Onegin," originally a "master" short story of Pushkin, then an opera of Tschaiakowsky—one of his best works—and now "dramatised for broadcasting" by Wilfred Grantham. I liked it very much. The sad story of how the dissipated young Onegin turned away from Tatiana when she was literally throwing herself at him, only to find later, to his cost, that, when happily married and with a family, he truly loved her but was spurned for his intrusion, came over very effectively. As with many "operised" stories, "Carmen," for example, nothing quite compensates for a much loved and very familiar score.

## "Much Binding"

As I feared, the new "Much Binding" flags a bit and doesn't maintain its original momentum. The idea of a newspaper increasing its circulation from nine to 10 copies stales. Apparently, it stays at 10, an idea that can't last for ever, but the weekly features from Sam Costa, Maurice Denham and Dora Bryan keep up a good average of wit and fun.



**COMMUNICATIONS RECEIVER R.1155**  
The famous ex-Bomber Command Receiver known the world over to be supreme in its class. Covers 5-wave ranges 18.5-7.5 mc/s, 7.5-3.0 mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s, and is easily and simply adapted for normal mains use, full details being supplied. Aerial tested before despatch these are BRAND NEW AND UNUSED IN MAKERS' ORIGINAL TRANSIT CASES. ONLY £11/19/6.

A few used receivers, also tested working before despatch, are available at £7/19/6. A few of the R.1155 N model can also be supplied. This is the latest version which covers the Trawler Bands, and in addition is fitted with ultra slow motion tuning. Used, but tested working before despatch. ONLY £17/19/6.

A factory made Power Pack. Output Stage and Speaker contained in black cracked cabinet to match the receiver, can be supplied at ONLY £5/10/0. Operates receiver immediately.

**DEDUCT 10 - IF PURCHASING RECEIVER & POWER PACK TOGETHER.**  
Please add carriage costs of 10/6 for Receiver, and 5/- for Power Pack.

**POWER PACK TYPE 3.** Used by the Services with the R.1132A receiver. A standard 19in. rack mounting job to match the receiver, this is for 200/250v, 50 cycle mains with output of 250 v. D.C., 100 ma. and 6.3 v. 4 amps. Is fitted with H.T. current meter and voltmeter, and is a really superb unit, which can be used for a variety of sets. Tested working before despatch.

**ONLY 90/- (Carriage, etc., 5/-)**  
**100 MICROMETER SPEAKERS.** 2in. Circular Flush Mounting. Widely calibrated scale of 15 divisions marked "Yards," which can be re-written to suit requirements. These movements are almost unobtainable to-day, and being BRAND NEW IN MAKERS' CARTONS are a snip. ONLY 42/6  
**INDICATOR 62A.** A two deck chassis job, this contains VCR97 tube with Mumetal screen, 12 valves EP50, 4 of SP61, 3 of EA50 and 2 of EB34. IN NEW CONDITION IN MAKERS' TRANSIT CASES. ONLY 99/6 (carriage, etc., 10/0).

**TRANSFORMERS.**—Manufactured to our specifications and fully guaranteed Normal Primaries, 425-0-425 v., 200 ma., 4.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a. ONLY 50/-; 350 v. 0-350 v. 160 ma., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a. ONLY 42/6; 250 v. 0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a. ONLY 32/6; 350 v. 0-350 v. 150 ma., 6.3 v. 5 a., 5 v. 3 a. ONLY 32/6. The above are fully shrouded, upright mountings. 5.5 kv. E.H.T. with 2 windings of 2 v. 1 a. ONLY 72/6; 7 kv. E.H.T. with 4 v. 1 a. PLEASE ADD POSTAGE.  
**POSTAGE FOR EACH TRANSFORMER.**

**E.H.T. TRANSFORMER FOR VCR97 TUBE.**—2,500 v. 5 ma., 2-0-2 v. 1-1 a. 2-0-2 v. 2 a. (post 1/6). 37/6.

**PYE 45 MCS. STRIP.**—Ready made for the London vision channel, and easily modified for other stations as per details published in our "Practical Television" Complete, with 6 valves EP50 and 1 EA50. BRAND NEW. ONLY 70/- (postage, etc., 2/6).

**RECEIVER R3118.**—A further supply of the very popular unit we sold out a few months ago. Ideal for conversion to TV, having a built-in A.C. Mains Power Pack for 130-240 volts. Is tremendously powerful, employing 7 I.F. stages of 12 mc/s with 4 mc/s band-width, and has 16 valves; 5 of V665, 4 of V662, 2 of VR33, and 1 of V663. VR137, P61, 5Z4 and Y63 "Magic Eye." In new condition. ONLY 97/6 (carriage, etc., 7/6).

**PM SPEAKERS.**—5in. Rola with transformer, 17/6; 10in. LECTERNA with transformer, 27/6; 12in. GOODMANS, 15 ohm speech coil, less transformer, 99/6. All speakers BRAND NEW AND UNUSED. Postage 2/- each, please.

**TR1196 TRANSMITTER SECTION.**—In perfect condition, less valves. ONLY 12/6 (post, etc., 2/6).

**ROTARY POWER UNITS Type 104.**—Input 12 v., output 230 v. 65 ma. and 6.3 v. 2.5 a. Fully filtered and smoothed and noise suppressed. Ideal for car radio, etc. BRAND NEW. ONLY 15/- (post, etc., 2/6).  
C.W.O. Print name and address clearly. Amounts given for carriage refer to inland only.

### U.E.I. CORPORATION,

138, Gray's Inn Road, London, W.C.1  
(Phone: TERMINUS 7937)

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Green Lane Station) and 5 mins. by bus from King's Cross.)



## Magna Cartridge



Completely Tropicalised. Tested under extreme conditions of Heat and Humidity (125° F. with 95% humidity) without deterioration and loss of output.

- Output comparable to Crystal Pick-ups.
  - Cantilever Stylus Protecting Records and eliminating Needle-talk and surface noise.
  - Stylus easily replaceable.
  - Will fit three-speed record changers and units.
- No. 200. Price £110.0. P. Tax 9/6. Now available as a complete Pick-up. No. P.200. Price £25.0. P. Tax 14/6. For full technical details write to:

**ERWIN SCHARF**

49-51a, De Beauvoir Road, London, N.1  
Telephone: CLISSOLD 3431.

## W. B. SUPPLIES

100, Oldham St., Manchester, 4

Tel.: Central 2424

**VALVES.**—EA50, 2-; VS2, 2-; VR51-26; VT81, 2 11; EF50, 4 6; 6 v. 6 G.I. 6 11; EF55, 8 6.

**SPEAKERS.**—5in. P.M., 11 6.  
**GERMANIUM DIODES.** 19 ea.; 2 for 3-.

**YAXLEY TYPE SWITCHES.**—2-pole, 6-way, 1-pole 10-way, 11-bole 7-way, all at 2/3; 4-pole, 3-way Midget, 1 6.

**HIGH VOLTAGE CONDENSERS.**—01 mfd. 4 kv., .02 mfd., 5 kv., .03 mfd. 2.5 kv., .05 mfd. 3.5 kv., 2- each

**COAXIAL CABLE.**—23ft. lengths, with 2 Pye plugs, 3/11.  
**HEADPHONES** suitable for crystal sets, 12/6.

**COIL FORMERS.** 1in. with iron dust cores, 6 6 doz. (9d each).

**TRANSFORMERS.**—Input 230 v., output 75 v., C.T. 600 mls., 250 v. C.T. 10 mls., 4 v. 5 amp., 4 v. 1.5 amp., 10/-

**1 MEG POTS,** with switch, 2-; 5,000Ω. 1ess switch, 1/6.

**SMOOTHING CHOKES.**—60-60 mls., 2-.  
**RELAYS** 765Ω, 4 make 1 break, 2,000Ω 1 make, 2 break, 2/3.

**EPICYCLIC (Slow Motion) Drive** with knob and pointer, 2/6.

**V.C.R. 138.**—Scope tube, 3in., 30-.  
**AIR GUNNER'S CONTROL UNIT.**—Type 229, containing 2 toggle switches, 2 push switches, 2 pots, 1 Yaxley, 1 G.P.O. type switch, 3 knobs, epicyclic drive, indicator lamp, etc., 3/5.

**CRYSTAL SET COILS** with 4 tappings, 1 6.

**RECTIFIERS.**—12 v. 2 amp., 12 6; 250 v. 10 mls., 7 6.

**VIBRATORS.**—12 v. 4-pin, 5/-.  
**5 V. VIBRATOR PACKS.**—Output 90 volts, 5 11 complete

**CONDENSERS.**—8 mfd. 500 v. screw cans 5  
**TOOL ROLLS.**—Very useful, 2/4.  
**RHEOSTATS.**—250 Ω. Totally enclosed, 2-.

# WEBB'S RADIO

are proud to present the  
**NEW EDDYSTONE**

## "840"

AC/DC Communications Receiver

Fulfills a long-felt want for an efficient long range receiver to work from D.C. or A.C. mains.

**VALVES.**—SEVEN, plus metal rectifier.  
**TUNING.**—FOUR BANDS 30.6 mc/s to 1.4 mc/s and 205 to 620 metres.

**FEATURES.**—Accurate calibration—great stability—high sensitivity—B.F.O.—internal loudspeaker—built like a battleship for utmost reliability.

### £45.0.0.

(Available under Webb's Extended Payment Scheme. Deposit £15.00 and 12 payments of £2.15.0)

**THE EDDYSTONE "840"** is available from stock at Webb's Radio.

HAVE YOU HAD YOUR COPY OF WEBB'S NEW 52-PAGE CATALOGUE?

It costs 1/- post-free, including registry for our unique information service.



14, SOHO ST., OXFORD ST., LONDON, W.1

Tel: GERARD 2089

SHOP HOURS

9 a.m. - 5.30 p.m. Sats. 9 a.m. - 1 p.m.

# The L-C Circuit, "Q" and the Power Factor

A SIMPLE EXPLANATION OF SOME OF THE PRINCIPAL FACTORS IN CIRCUIT DESIGN

By F. E. Apps

**I**N every radio and television set there are many circuits consisting of a coil or coils and a fixed or variable capacitor, either in parallel with or in series with the coil. For the set to work efficiently it is necessary that these circuits be adjusted or tuned to the correct frequency, but it is not this alone that determines whether the set is efficient. There are other factors that have a great effect upon this efficiency. One of these factors is the "Q" of the coil. This "Q" could be called, and is, in fact, a term that expresses the "goodness" of the coil.

## "Q"

The losses that occur in a coil may be due to several causes. One is due to the D.C. resistance of the coil, which will vary greatly, and in some cases—that of a short wave coil, for instance—be very small indeed. There is also the loss occasioned by the coil's proximity to metal objects, such as screening plates or the chassis. This loss is due to the electromagnetic field set up around the coil by the R.F. in it, inducing current in the adjacent metal and thus losing energy by it.

To refer to the D.C. resistance loss again: it should be noted that in the case of multi-turn coils this resistance is usually kept down by using "Litzen-draht" wire, which is a wire made up of many strands of fine wire insulated from each other, offering a much larger surface area for the H.F. currents to travel over than would be the case of a single strand wire of the same cross-sectional area.

Note that H.F. currents do not penetrate the wire as D.C. does but only travel on the surface. Where a coil, such as an I.F. coil, appears to have lost efficiency it may often be traced to the fact that some of these strands have broken away at the soldered joint, thus lowering the amount of surface area and increasing the H.F. resistance of the coil.

Insulation resistance of the coil and the coil-former will naturally affect the coil's efficiency. This may be due to poor or worn insulating material on the wire itself, or poor material of which the former is made, especially if this material is liable to absorb moisture from the atmosphere.

From the foregoing it can be seen that there are quite a few factors that affect a coil, or rather the "Q". Thus we can formulate that the "Q" of a coil is the ratio of the purely reactive impedance of the

coil to the HF resistance of the coil, i.e.,  $Q = \frac{\omega L}{R}$ .  
So much for the coil part of an L-C circuit.

## The Capacitor and the Power Factor

The losses that occur in a capacitor are fewer than in the coil, but they can have an effect on the efficiency of the circuit that can be serious. This is especially so in the higher frequencies. One, of course, is insulation resistance, meaning the dielectric resistance which should be very high for efficiency, 100 megohms being a reasonable lowest reading allowable. There is also resistance to ground and resistance at points

of contact to the plates. All of these resistance tests may be very high and the condenser apparently quite efficient, but this is not always the case. In capacitors whose dielectric is some other substance than air, as in trimmers, padders, etc., another factor arises.

The dielectric of a capacitor is under a state of strain due to the continual charging and discharging of the plates, and should the material of which the dielectric is composed be of a poor or unsuitable composition this strain will affect its atomic structure and loss of energy will occur in the form of heat. This will in turn affect the insulation resistance and eventually cause breakdown. This is the reason why in condensers in a circuit that are subjected to heavy fluctuations of current, as in a television time-base circuit, it is usual to specify mica dielectrics.

These losses, if they occur, will affect the phase relationship between current and voltage which should, in a perfect capacitor with nothing else in the circuit other than capacity, be 90 deg. Thus we classify a condenser by the effect it has on this relationship. This is called the Power Factor and is stated as  $\cos \theta$  or as the ratio between true power and the apparent power in the circuit by the phase angle  $\theta$  between current and voltage. If in a capacitor the

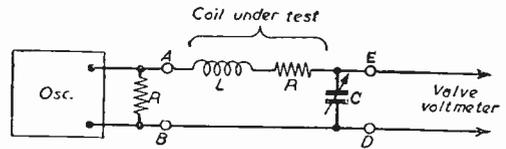


Fig. 1.—Theoretical circuit of an average "Q" meter.

phase angle  $\theta$  between current and voltage is 90 deg. then  $\cos \theta$  or the Power Factor is zero.

## The L-C Circuit

Here we have both inductance and capacity with, maybe, some H.F. resistance, which may occur in either coil, capacitor, or both. We take the complete circuit and estimate its efficiency or goodness, and state that as the "Q" of the circuit. This can be measured accurately and the instrument used is known as a "Q" meter.

Essentially it consists of a means of generating an oscillation that will correspond with the L-C value of the circuit under test, a meter to measure the output of an oscillator across a standard resistor, means of applying same output to the circuit under test, and a valve voltmeter to measure the voltage obtained. If the applied voltage across R be adjusted to, say, .1 volt and the voltage across the coil under test be 10 volts, then as  $V_1 = IR$  through the resistor and  $V_2 = I\omega L$  through coil,

$$\frac{V_2}{V_1} = \frac{\omega L}{R} = Q$$

Therefore  $Q = 100$ .

Notice that the voltage applied is kept low and R is also low, so that impedance of output is negligible. The voltage must be taken on a valve voltmeter, as it has a very high input impedance and thus any stray

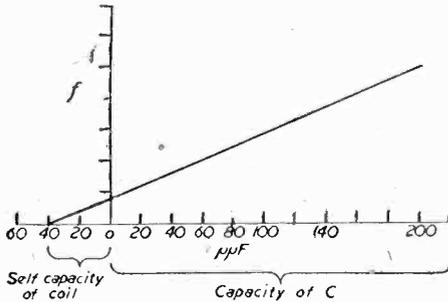


Fig. 2.—A graph of various readings at different frequencies on a "Q" meter in checking the self-capacity of a coil.

capacity, etc., across the test terminals have negligible effects. The oscillator portion of the "Q" meter

must have an accurately adjustable attenuator and calibration.

In the theoretical diagram of an average "Q" meter (Fig. 1), L and R represent the coil under test.  $R_1$  is the standard resistor of low value which is purely ohmic; C is adjusted until  $V_0$  is maximum, whose value is observed on the valve voltmeter. Points A and B are points for observing  $V_1$  and points E and D for observing  $V_2$ . Output from the oscillator should not be high otherwise the reading of  $V_2$  will be too great for the valve voltmeter if the "Q" is high.

There are other purposes to which a "Q" meter can be put. As C is an air dielectric condenser of very low loss indeed a check may be made on other small condensers such as trimmers, padders, etc., by placing them across C at points C and D and reading the difference in "Q" on the valve voltmeter.

It is sometimes necessary to check the self-capacity of a coil, when it will not tune to a given frequency that should be in its range, with a given trimmer capacitor. This can be done on a "Q" meter by taking various readings at different frequencies. One can then plot a curve on graph paper and check the residual capacity of the given coil when capacity of C equals zero (see Fig. 2).

## News from the Clubs

### COVENTRY AMATEUR RADIO SOCIETY

Hon. Sec. : K. Barber, 1, Charterhouse Road, Coventry.

THE Society have been successful in obtaining accommodation for their exclusive use at 9, Queen's Road, Coventry. The club station has been installed there and operates under call-sign G2ASF on the 160, 80-, 40-, 20- and 10-metre amateur bands.

### BRIGHTON AND DISTRICT RADIO CLUB

Hon. Sec. : T. J. Huggett, 15, Waverley Crescent, Brighton.

THE Annual General Meeting of the above club took place on January 5th, 1954.

The following officers were elected :

Hon. Sec. : T. J. Huggett.

Chairman : Mr. R. Langridge.

Vice-Chairman : Mr. E. Bannister.

Hon. Treasurer : Mr. W. Pitfield.

The club transmitter G3EVE is on the air the second Tuesday in every month, on 80 metres.

Meetings are held at 7.30 p.m. every Tuesday at the Eagle Inn, Gloucester Road, Brighton.

### CHESTER AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : E. Yates, G3ITY, 38, Durham Road, Blacon, Chester.

THE new year began well with a large attendance at the first meeting of the year—on the 5th January—when an auction sale was held.

On the 12th January a very interesting lecture was given on an all band transmitter portable, by B. O'Brien (G2AMV), Regional Representative.

The sixth Annual General Meeting was held at the Tarron Hut Y.M.C.A., Chester, at 7.45 p.m. on Tuesday, 19th January.

The monthly news letter is available to all interested on application to the club secretary.

### SOUTHEND AND DISTRICT RADIO SOCIETY

Hon. Sec. : J. H. Barrance, M.B.E., 49, Swanage Road, Southend-on-Sea, Essex.

THE first of a series of up-to-date lectures by expert experimental researchers in the field of radar, transistors, electro-chemistry etc., was held recently in the Queen's Road Laboratories of the Municipal College, when Mr. T. Gray, of Marconi's, Chelmsford, unfolded the marvels of radar to a large appreciative audience. These were well rewarded for having braved the weather.

The talk was illustrated by epidiascopic projection, operated by Mr. S. T. Smith, M.B.I.R.E., and included a composite radar picture of the Spithead Review.

In pointing out the possibilities and limitations of radar, Mr. Gray explained how, in some respects, in the detection of distant objects, radar was superior to the human eye, while in others it was inferior.

### CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec. : C. H. Bullivant, 25, St. Fillans Road, London, S.E.6.

ALTHOUGH no meeting was held on Christmas Day, a net was organised on Top Band by G3DIC and most of the licensed members of the Society had their equipment tuned to 1925 kc/s at 10.30 a.m. Christmas morning. Some of our SWL members visited stations operating in the net whilst others had their own receivers running to listen-in on the proceedings.

On December 18th, D. Reed gave an interesting talk describing his record player and home built amplifier. His talk was illustrated with excerpts from both LP and standard 78 r.p.m. recordings. January 1st again attracted a large gathering for a junk sale when, as usual on these occasions, much equipment changed hands.

Meetings are held every Friday at the Society's H.Q., 225, New Cross Road, S.E.14, and a warm welcome awaits new members both young and old.

### STOKE-ON-TRENT AMATEUR RADIO SOCIETY

Hon. Sec. : K. H. Parkes, G3EHM, 159, Belgrave Road, Longton, Stoke-on-Trent, Staffs.

MEETINGS are held each Thursday night in our headquarters, M at the rear of the Cottage Inn, Oakhill, Stoke-on-Trent, Staffs.

Lectures are being arranged on tape recorders, modulators, transistors and T.V.I. suppression. Members are asked to make full use of our workshop and refreshment facilities are now adequate.

Prospective members are cordially invited to attend any Thursday night. Application forms can be obtained from the secretary.

### B'HAM & DISTRICT SHORT WAVE SOCIETY

Hon. Sec. : Mr. Yates, 67, Regent Road, Handsworth.

AT the Annual General Meeting, the main business of the evening was the electing of officers for the coming year.

In view of the retirement of the society's president, Mr. Burton, G.2.BON, has now been elected to this position, and will also be chairman again for the coming year.

The following members will be officers of the society for the coming year also : vice-chairman, Mr. Frearson ; treasurer, Mr. Shirley ; hon. secretary, Mr. Yates.

Committee members : Mr. Neal, Mr. Burdett, Mr. Button.



### FOR SETS OF VALVES

Ten VR91 (EF50) Valves Ex. Brand new units. C/- each, 45/- set.  
 6K56, 6K76, 6Q76, 5Z46, 6V86, 37 6 set.  
 6K56, 6K76, 6Q76, 5Z46 or 37 6 or 35 6 set.  
 6K56, 6K76, 6Q76, 25A66, 25Z46, 37 6 set.  
 12K66, 12K76, 12Q76, 35Z46T, 35L66T or 50L96T, 37 6 set.  
 Ten 6AM6 (EF91), 75/- set.

### MAINS TRANSFORMERS

3-way Mounting type.  
 M.T.1. Primary 0-240-250-250 v.  
 Secondary 250-250-250 v. or 240-250-250 v.  
 4 amps, 5 v. 2 amps with tap at 4 v. on filament winding. Price 17/6 each.  
 M.T.2. Primary 0-240-230-250 Secondary 250-0-250 v. 80 mA.  
 6.3 v. 1 amp, 5 v. 2 amps. Both filament windings tapped 4 v. Price 17/6 each.  
 M.T.3. Low Voltage Transformer. 20 v. 2 amps, with tappings at 3-4-5-6-8-9-10-12-15-18-20-24 volts. Price 17/6 each.

### SPECIAL OFFER Co-Axial Cable

Best quality Grade "A" cable, solid 1 022 70-ohms, 7 1/2 pair. Best quality Grade "A" cable, stranded 7 0078 8 1/2 pair. Best quality Grade "A" cable, air spaced 1 056, 1-yd.

### SOLDERING IRONS

964 Nylon oval bit type, 19/- each.  
 968 Nylon pencil bit type, 19/- each.

### HEADPHONES

Type CLR Low Resistance Head-phones 120 ohms, 7 6 pair. Type DHR A. Super Quality Headphones, 13 9 pair. Headbands, wide type, 1/8 each.

## VALVES

0Z4	6/-	6J5GT	5/8	8D2	2/9
1A5GT	6/6	6J5M	6/6	8E2	2/-
1C6GT	6/-	6J7G	6/6	8E3	4/8
1L4	7/6	6K7G	6/-	8E6	3/6
1R5	7/9	6K7M	6/6	9D2	3/-
1R4	7/9	6K7GT	6/6	9D6	6/-
7A5	7/9	6K8M	8/8	9D6T	6/-
1T4	8/-	6K8GT	8/8	9D6T	6/-
1U5	10/-	6K8GT	9/-	9D6	6/-
220V5G	6/9	6J6	8/8	10C1	11/-
2X2	5/-	6L6G	8/-	10F9	11/-
3A4	9/-	6L7M	7/6	10L1D11	11/-
3Q4 (N18)	9/-	6L7	7/6	12A6	6/6
3D6	5/-	6P26	10/-	12AU7	9/-
3E1	8/6	6Q7G	9/-	12AT7	9/-
3V4	8/-	6Q7GT	9/-	12CS	8/6
4D1	2/-	6R4ZGT	8/6	12H6	6/6
42	8/-	6S8T	7/6	12J5	9/-
5U4G	8/6	6SH7	8/6	12K7	8/6
5Y3G	8/-	6S7GT	8/6	12K8GT	8/6
5Z3	8/6	6SK7	8/6	12S6T	5/6
5Z4G	8/6	6SL7	8/-	12SH7	5/6
6A7	8/6	6SN7GT	9/-	12S7	7/6
6AN7	10/6	6SN7	8/-	12SK7	7/6
6AC7	6/6	6U5G	8/-	12SK7	7/6
6AA7	7/6	6V8A	2/6	12S9T	9/-
6AK5	9/-	6V9GT	7/6	12Q7	9/-
6AL5	9/-	6X4	8/6	12D2	10/6
6AM6	8/-	6X5GT	7/6	12D11	10/6
6AT6	10/-	6X5A	7/6	25A6G	9/-
6AM5	9/-	7B7	8/6	25L6GT	8/6
6B6	9/-	7B7	8/6	25Z46	8/6
6BE6	11/6	7C5	8/6	25Z46T	8/6
6C4	8/6	7C6	8/6	35A6T	8/6
6C5GT	7/6	7H7	8/6	35A6	8/6
6C6	6/6	7T7	8/6	35Z46T	8/6
6C9	8/-	7R7	8/-	50L96T	8/6
6D1	7/6	7S2	8/-	50L96T	8/6
6D6	7/6	7Q7	8/6	ATP4	6/6
6E6A	7/6	7Q7	8/6	AC6PEN	5/6
6E8A	7/-	7Y4	8/6	CV6	6/6
6E6A	6/6	75	10/-	CV71	1/-
6H6	4/6	80	8/6	DH14A	9/-
6V6	5/-	807	8/6	EH149	2/-

### GOODMANS 12"

Goodmans 12in. heavy duty loudspeaker 15 speech coil, £4.19.6. (A super job).  
 Truxov Model EX11 Lightweight Type 12in. loudspeaker, 49/6 each.

- 4 Position Rotary Switch, 30 amp. .... 3/6
- Battery Charger Bulb Clips 465 Ke. I.F. Transformers, per pair .... 6/6
- Isotax Valve Holders, Pyralin Condenser Clips, all sizes .... 3/6
- 2 Ratio Output Transformer 1 1/2 in. .... 1/11
- Conso-dia. Bell Transformer, 3 v., 3 A., 9 v., 1 amp. .... 7/6
- Resistor Choke 20H, 250  $\Omega$  50 mA. .... 6/-
- H.F. Pole Wound Chokes, 1000, 10000, 100000, 12 v., 1 1/2 in. T X Tube .... 1/-

### RECEIVER 1132A

Contains EK32 : 4 EF39 : 6H6 : 6J5 : 3SP01 : P61 in good condition. Fitted with tuning meter. Slow motion drive calibrated dial complete with circuit diagram, 47.6 each. Carriage and packing, 7.6.

### GUARANTEED NEW AND BOXED

2.9	EF841	11/-	1F22	8/-
2.9	EL32	11/6	1F10	9/-
4.8	1X42	13/-	1F41	11/6
3.6	6H35	10/6	1F81	10/-
3.6	EF80	11/6	1UB41	9/6
6/-	EB41	11/-	1UCH42	12/6
6/-	6V180	11/6	1UF41	12/-
6/-	EF36	8/6	1UY41	10/-
6/-	EF34	10/-	1EF39	6/6
11/-	EF80	11/6	1EB34	2/6
11/-	EZ40	11/-	1EBC33	7/6
11/-	EM31	9/-	1EF30	6/6
6/6	EFY91	9/-	8P61	3/9
9/-	EX51	13/-	8K32	3/6
9/6	EZ41	11/-	8P41	3/6
8/-	FC13	9/-	PH1	3/9
5/-	HD14	10/-	EF50	6/-
6/-	HH3	7/9	EP50 Syl	6/-
9/-	HD30	8/-	EA50	2/-
9/-	HL23DD	8/-	VH116	4/-
5/6	HE12DD	8/-	DD14	4/-
5/6	KT2	5/6	EF8	6/6
7/6	KT35C	10/6	EP54	7/-
7/6	KT74	8/-	EE52	5/9
6/6	KP66	10/-	VH150 30	9/-
7/6	KT71	7/6	EL32	6/-
8/6	KW61	7/6	ET11	6/-
9/-	KZ41	6/6	VP23	8/6
4/-	KZ53	5/6	VC39	8/6
10/6	MH4	5/-	VU111	3/8
9/-	MS PEN	9/-	VU20A	2/8
8/6	OM9	9/-	VU133	3/9
9/-	PEN25	8/6	VU14A	3/9
8/6	PEN46	8/6	V4A	(Circuitgram)
8/6	PEN20A	4/6	PL53	8/6
8/6	PL58	13/-	W77	10/-
8/6	PL82	11/6	W81	8/6
6/6	PY82	11/6	X65	10/-
5/6	PY80	11/6	X66	11/6
6/6	PY81	11/6	Y61	9/-
1/-	QZ22B	7/6	Y61	9/-
9/-	QZ21	7/6	Y61	9/-
2/-	TP22	9/-	Atlas	4/6

### WIRE WOUND VARIABLE RESISTORS

Colvern CLR92 1K, 1.9 each.  
 Polar 500, 1.9 each.  
 Colvern 5, 200, 10K, 20K, 25K, 50K, 50K, 2.4 each.  
 Colvern CLR84, 10K, 25K, 20 1.3 each.  
 Ex-Government Vol. Controls  
 500, 600, Double 1,500, 10K, 20K, 25 K, 50K, 100K, 150K, 200K, 1 meg., 2 meg., 1 meg., 2 meg. All 1/2 each.

### LOUDSPEAKER UNITS

3in. Plessey Round Type for Portables ... 12/0  
 Elac. 3 1/2in. square type. 2 to 3 ... 13/6  
 5in. Units by Elac. ... 12/3  
 Truxov 6 1/2in. Wafer Speaker, only 1 1/2in. deep ... 20/-  
 8in. Units by Plessey and R. & A. ... 15/-  
 Lectra 10in. 2 to 3 1/2 ... 18/6  
 Rola Celestion 10in. ... 25/6  
 12in. Truxov BX11 Lightweight Extension Loudspeaker in mottled bakelite case, suitable for bedrooms or kitchens etc. Plessey Mains Energised 8in. Unit, 1,500 Field ... 21/-

### REPAIR YOUR OWN LOUDSPEAKERS

Speaker Cone replacements available as follows.  
 CA8Z 5in. Rola 5Z types, and other midgets with tin pole piece ... 4/- ea.  
 CA6P 6 1/2in. Philco, R. & A. ... 4.6 ea.  
 CA8Z. Rola 8Z New Plessey. This cone will suit most modern receivers with an 8in. Speaker ... 5/- ea.  
 CA8Z 6 1/2in. Rola 6Z. ... 4.6 ea.  
 CA8P Philco, R. & A. ... 5/- ea.

### MOULDED BAKELITE CASE CONDENSERS

.0001 mfd. 4 kv., 1/- each.  
 .25 mfd., 4 kv., 1.6 each.  
 .1 mfd., 1,000 v., 1/- each.  
 Screened Microphone cable with outer P.V.C. 7 0076, 1/- yd.  
 .00035 mfd. 2-gang Condenser, complete with trimmers and dust cover, 8.3 each.  
 Dial Bulbs M.E.S. Types. 6.3 v., .15 a., 6 1/2. each.  
 6.3 v., .3 a., 8 1/2. each.  
 M.B.A.T. Types  
 6.5 v., 3 a., 6 1/2. each.  
 6.5 v., 3 a., 5 1/2. each.  
 50-amp Rotary Switch 4-position, complete with knob, 4/- each.

### HALF-WATT 1mA. PENCIL RECTIFIERS


K3 25-605 v. ... 5/8  
 K3 10-4 kv. ... 7/6  
 K3 45-1,140 kv. ... 8/2  
 K3 50-1,200 kv. ... 8/8  
 K3 60-1,5 kv. ... 9/8  
 K3 100-2,570 kv. ... 14/8  
 Standard S.T.C. Rectifiers. ... 3 11 ea.  
 RM1 125 v. 60 mA. ... 4.3 ea.  
 RM2 125 v. 80 mA. ... 6 ea.  
 RM3 125 v. 100 mA. ... 6 ea.  
 RM4 125 v. 250 mA. ... 16/- ea.

### HAND MICROPHONE by "REGENT"

complete with screened lead and plug-Crystal inter, nickel chrome plated head. Listed at 2 gas. Our price, 21/- each.
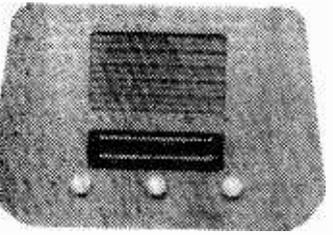
### \*\*\* "SWAN" RADIO CABINET \*\*\*

Build a Radio in this up-to-date Cabinet. A modern looking Radio Cabinet complete with drilled chassis : dial drive and drum : back plate : dial : spring : pointer : size 15 1/2 in. x 11 in. x 5 in. Price 38.6 ea. Post and Packing 2/-.



We can supply a circuit diagram with all instructions for constructing a Medium wave band radio receiver to operate on Long and Medium wave bands for 1.6. The complete kit can be supplied for £6.6/-. Plus Packing and Post 2.6.

J.B. Drives, Etc.  
 SLS Spin Wheel Drive ... 27/6  
 Airplane Drive ... 13/-  
 Full Vision Drive ... 13/-  
 Square Plane Drive ... 12/9  
 SLS RV Drive ... 26/6  
 Send for catalogue of drives, condensers, etc

Enamelled Copper Wire on 1 1/2 lbs. Reels  
 14 S.W.G., 1.4 32 S.W.G., 2.2  
 16 S.W.G., 1.4 30 S.W.G., 2.3  
 18 S.W.G., 1.6 24 S.W.G., 2.4  
 20 S.W.G., 1.7 26 S.W.G., 2.6  
 22 S.W.G., 1.8 28 S.W.G., 2.8  
 24 S.W.G., 1.10 40 S.W.G., 2.11  
 26 S.W.G., 1.10 44 S.W.G., 3.3  
 28 S.W.G., 2-

**TERMS :-**  
 Cash with order or C.O.D. Postage to be added to orders as follows : 9d. up to 10/- ; 1/6 up to 20/- ; 1/6 up to 40/- ; 2/- up to £5. MAIL ORDER ONLY.  
 Send 6d. in stamps for comprehensive, illustrated catalogue.

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."

# ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

**NOW READY**  
Complete building instructions for the

# DISCOTAPE

to convert your gramophone into a high fidelity  
**TAPE RECORDER**

Written in non-technical language with clear, stage-by-stage diagrams. Price 3/6—refundable on purchase of kit. Send for your copy now!

**THE DISCOTAPE KIT** comprises the Erase and Record Reels, their mounting sockets and platform, main drive capstan, take-off/take-up spindles, driving belts, and complete ancillary mechanical parts ready for mounting on your gram. platform, converting it into the playing desk, plus all components, from the punched and drilled chassis down to the last nut, for a small (5in. x 5in.) easy-to-build oscillator/pre-amplifier unit which plugs into your radio receiver, using it as the main amplifier. Does not preclude use of gram, or receiver for normal purposes.



The perfect Kit for the home Constructor. Simple to build—simple to operate. THE DISCOTAPE enables you to have a gram, and Tape Recorder in ONE unit.

Price, complete Kit, £12  
Retailer enquiries invited.

**N.E.A.L. ACOUSTICS LTD.**  
COURT STREET, LEAMINGTON SPA.

# YOU can become a First Class RADIO ENGINEER

We can train you to earn good money in your spare time or start a radio business of your own. Our Home-Study Courses are easy to understand and the fees are very reasonable. Post coupon now and we will send you full details in plain sealed envelope.

## T. & C. RADIO COLLEGE

Post in unsealed envelope, 1½d. postage  
To: T. & C. RADIO COLLEGE  
36, Northfield Road,  
Ringwood, Hants.

NAME .....  
ADDRESS.....

P3/54

# THE CORONETS

NATURALLY, THE RODING RL30 TUNING UNITS WERE CHOSEN FOR THESE SUPERB RECEIVERS SINCE RELIABILITY, OPTIMUM PERFORMANCE AND FIRST-TIME SUCCESS ARE THE ESSENTIALS FOR HOME-CONSTRUCTION.

G. K. of Harrow writes: "The set (Coronet) is absolutely brilliant and is equal to anything I have ever heard."

Ensure YOU get the same results as the designer by using these guaranteed parts which we can supply:

- COIL PACK RL30, 49/9.
- RL IF TRANSFORMERS, Type U, 16/- pr.
- 1B SL8 ASSEMBLY, 27/6.
- 1B .0005 2-GANG, 14/- (or £5.5.11 if ordered together)
- Aligned, sealed and matched as specified for this receiver. Also

½ meg. v/c. w/sw. 7/6; ready punched chassis, (Univ.), 12/6; B8A and B9A v/holders, 1/- each; P350 connector, 3/9; Knobs, 11d. ea.; WB speaker, 48/6; transformer, 8/6; NEW MULLARD Valves, UCH42, 21/3; UBF80 19/11; UL41, 17/3; UY41, 13/11 (£3.12.4 set of 4); Resistors, 10 w., 2/3 ea.; 5 w., 1/10 ea.; 1 w., 8d. ea.; ½ w., 6d. ea.; Condensers, CE27LE, 11/6; CE26L, 4/9; 50 mf., 2/9; Paper tub., 1/- ea.; 100 pf., 9d. ea.; Sundries: socket strip to screened flex, inclusive, 7/8; Cabinet, £3; Solder, 9d. length or 5/- carton; Elec. clips (2) 4d. ea. C.W.O. or C.O.D. (cabinet C.W.O. only). Postage to £3 1/-, to £5 1/6, over £5 2/- C.O.D. charges extra.

All parts in stock for "CORONET AC. 4"  
Send for list.

OUR FAMOUS "HOME CONSTRUCTORS HANDBOOK" (1954 EDITION) CONTAINING 15 LARGE BLUEPRINT CIRCUITS, WITH FULL PARTS LISTS, INFORMATION, etc. GIVEN FREE WITH ORDERS FOR "CORONETS" OVER £3. OR A COPY WITH CURRENT CATALOGUE CAN BE OBTAINED FOR THE NOMINAL PRICE OF 2/6. 50 GLOSSY ART PAGES PACKED WITH USEFUL INFORMATION!

Obtainable only from  
**RODING LABORATORIES**  
(DEPT. P3)  
BOURNEMOUTH AIRPORT,  
CHRISTCHURCH, HANTS.

# LEWIS RADIO Co. for Cabinets

Send 1/- for our latest illustrated catalogue of ALL types of cabinets, chassis, Auto-changers, Speakers and Armstrong chassis.

We make Cabinets to Individual Specification.

## Chassis

Send for free leaflet on our latest 5-valve 3 waveband Superhet radio Radiogram Chassis.

## Amplifiers

Send for details of our domestic type amplifiers. 5 and 4½ watt.

## Tape Recorders

The latest 2 speed model at 48 gns. now available.

—120, GREEN LANES—  
**PALMERS GREEN, LONDON, N. 13**

■ BOWes Park 6064 ■

VALVES			
All Valves	Guaranteed	24 Hours Service	
PY82	9/6	Y63	8/6
6X5	8/6	425PT	6/-
694	2/-	35Z4	9/6
EA50	2/-	35L6	9/6
SP41	3/6	2X2	4/6
SP61	3/6	425P-T	6/6
MSPEN	5/-	1P2	4/6
VR137	4/-	KT21	4/6
80	9/6	HF4101	5/6
6C5	8/6	DDL4	5/6
706	9/6	6C5	8/6
6K7	5/6	IT4	8/-
ET50 (5yl)	7/-	1R5	8/-
VR115	4/6	1S5	8/-
5Z4	8/6	6V6	8/-
YU39	8/6	6KR	9/6
6Q7	9/-	EF39	8/6
		GSN7	9/6
		6L6	10/6
		7B7	9/6
		707	9/6
		50L6	8/6
		5U4G	8/6
		807	8/6
		ECL30	11/6
		EF80	11/6
		12KR	9/6
		12KT	9/6
		KP3C	10/6
		EB81	7/6
		EF91	9/-
		41MTL	6/-
		ARF 12	9/-
		12Q7	9/6

- \* G.E.C. crystal diodes, 2/-.
- \* Pvc plus and sockets, 6d. pair.
- \* Chokes, 10 henry 150 m.a., 5/8, plus 1/- post.
- \* Co-axial Cable, 80 ohm per ft., 8d. yd. (not W.D.). Post 1/- per 12 yds.
- \* Twin Transparent Flex, 18/6 per 100 yds.
- \* IML 2 1/11; RM2 S.T.C. 4/6; RM4. 15/-
- \* Earth V.C. WIS, 1 meg.-1 neg., 4/-
- \* FIL. TRANSFORMERS.—6.3 v. at 1.5 amps. Tapped at 200, 220, 240, 6.9, plus 9d. Post.
- \* STANDARD O.P. Primary Current 50 m.a. D.C. Secondary Current 2-3 ohms. Impedance 5,000 ohms. Ratio 40-1. 5.9, plus 6d. post.
- \* MIDGET TELEPHONE Transformers. approx. 100-1. 1.3, post 3d.
- \* REGENT Hand Mike (Crystal). Complete with screened lead and jack plug. 21.2.6.
- \* FUSES, 1 1/2in. length. 1 A., 1.5 a., 2 a., 3 a., 5 a., 3.6 dz.
- \* CODED CONDENSERS SPECIAL
- \* RESIST.—01, .01, .001, .002, .005, 3/6 dz.
- \* JACK SOCKETS, Two hole fixing. 6d.
- \* MAINS DROPPERS.—One hole fixing. 2 a.-1,000 ohms. 3.-750 ohms. 4/6.
- POSTAGE 9d. up to 10/-, 1/- up to 20/-, 1/6 up to 40/-, 2/- up to 45/-

**REX RADIO, 37, LOUIS STREET, LEEDS, 7.**  
Catalogue 6d. Mail Order Only.

# Surplus Double Diode Pentodes

DETAILS OF EX-SERVICE VALVES, WITH BASE CONNECTIONS

By E. G. Bulley

VALVES belonging to this classification are complex in structure and are similar in construction to the double-diode-triode, with the exception that the amplifier section is a pentode instead of a triode. However, the application of such valves is the same as that of the double-diode-triode, that is to say they are so designed as to perform simultaneously the functions of detection, amplification and automatic volume control.

Now, as in the case of the double-diode-triode the pentode also has a single cathode structure. The emitting surface on the sleeve is in two sections, one for the diodes and the other for the pentode unit. Both sections of the valve are internally screened as in the case of the double-diode-triode.

The diode sections in these valves can be used independently, one for A.V.C. and the other for

detection. They can, however, be used in conjunction with each other, either in parallel or in a full-wave rectifier circuit. The former will give nearly twice as much A.V.C. voltage for a given carrier as for the latter type of circuit. Nevertheless the latter does not require so good a carrier frequency filtering as the former. Furthermore, by utilising the valves under discussion it is possible to dispense with an intermediate stage, although one can, if one so desires, use them in the conventional R.F. and I.F. pentode circuits.

TABLE 1.

U.S.A. Type	Vh.	Ih	Va	Vs.	Gm.	Impedance K $\Omega$	Remarks
VT189	6.3	.5	250	100	1.3	700	1.H
VT68	6.3	.3	300	125	1.1	600	1.H
VT 93A	6.3	.3	300	125	1.3	600	1.H
VT169	12.6	.15	300	125	1.3	600	1.H
British NR87	4.0	2.0	250	250	9.0		1.H
VT 162	6.3	.3	250	125	1.1	600	1.H

### Typical Circuit

An important feature of these valves is that the pentode section can be used as an output pentode if the valve has a high slope. A

typical circuit showing the valve being used as such is shown in Fig. 1. This circuit provides delayed A.V.C. with diode detection feeding a high-slope output pentode.

It is as well to mention, however, that R.F. voltages should be prevented from being fed to the control grid of the pentode. The most satisfactory way of doing this is to include an R.F. choke between the diode load resistor and the diode anode. In

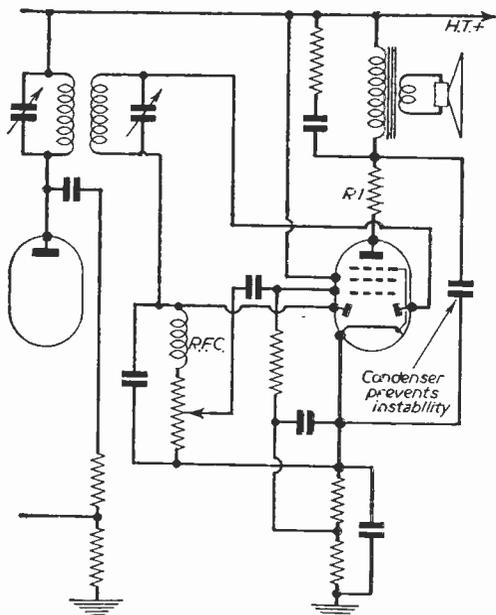


Fig. 1.—Circuit showing how double diode pentode can be used as an output pentode.

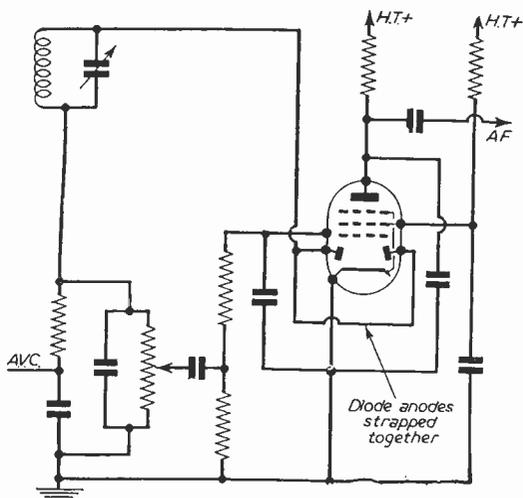


Fig. 2.—Basic circuit showing half-wave detection, A.V.C. and fixed bias amplifier.

addition, one can include a condenser between the anode and the cathode of the pentode. R1 in Fig. 1 is an anti-parasitic resistor, and should be assembled as near to the anode pin as possible.

When such valves as shown in Fig. 1 are used, it is advisable to keep the anode and screen voltages as high as possible without exceeding the maximum ratings of the valve.

Fig. 2, however, is a basic circuit, wherein the double-diode-pentode is used as a half-wave detector with A.V.C. and an amplifier with fixed bias.

Surplus valves that are available today at very reasonable prices are enumerated in Table 1. These valves should

prove extremely useful to the experimenter and newcomer to radio. The basing details of such valves are also shown in Table 2.

TABLE 2.

	1	2	3	4	5	6	7	8	Tc	Remarks
VT189	H	A	D1	D2	G2	G1	K & G3	H	—	Local
VT68	H	A	G2	D1	D2	K & G3	H	—	G1	7 Pin Base (U.S.A.)
VT 93A	—	H	A	D1	D2	G2	H	K & G3	G1	Int. Octal
VT169	—	H	A	D1	D2	G2	H	K & G3	G1	Int. Octal
VT162	H	A	G2	D1	D2	K & G3	H	—	G1	American 7 Pin
NR87	D1	A	D2	H	H	K & G3	G2	—	G1	British 7 Pin

## New Radar Plotting Device

THE Marconi International Marine Communication Co., Ltd., now has available a new plotting device to assist in the proper appreciation of the radar "picture" observed on the P.P.I. The plotter, known as the Marconi-Harrison "Locator-graph," has been designed following extensive enquiries (made with the co-operation of shipowners) among navigators as to the desirability of such an adjunct to the marine radar set—enquiries which indicate that a need exists for a simple and handy computer of this nature.


Plotting on the "Locator-graph" is carried out with an ordinary pencil on a sheet of transparent plastic material about 12in. square. The pencilled marks can be erased by an indiarubber when no longer required. A circular scale graduated from 000 deg. to 359 deg. is engraved on the underside of the transparent plastic to serve as a bearing ring, and beneath this is a rotatable ivory disc engraved with equally-spaced horizontal and vertical lines, ten concentric circles, and a radial bearing line. The "Locator-graph" is mounted on a thin duralumin base plate, forming a light yet rigid instrument easily held in the hand and not susceptible to distortion in extremes of temperature or humidity. The entire instrument is completely non-magnetic and may therefore be used in close proximity to compasses; it is also entirely self-contained and can be employed anywhere on the bridge.

In use the "Locator-graph" enables the navigator to record in fully visual form the changing positions of radar responses from other ships and above-water objects as they appear on the P.P.I., instead of having to rely on memory or on bearings and distances jotted down on paper. By plotting consecutive echo positions he can calculate another vessel's course and speed, estimate her point of nearest approach, and, by observing any departure from her line of relative motion, take any action which may be advisable to avoid any danger of collision.

The advantages of these facilities will be obvious. The plot can be made quickly and accurately without recourse to chart-work, and when made it can be carried away from the radar set and shown anywhere on the bridge if consultation should be necessary.
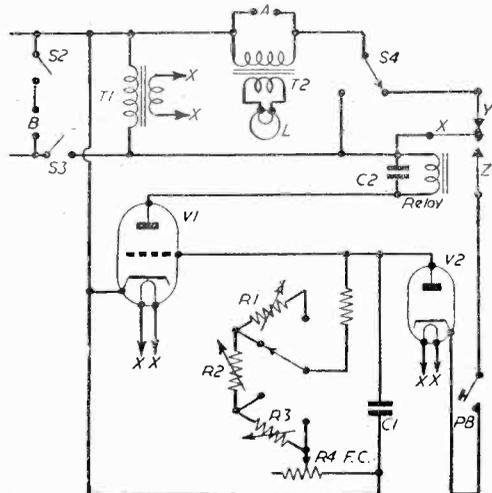
## An Electronic Timer

IN our February issue we gave a description of a useful accessory known as an Electronic Timer. Several readers on examining the circuits given with this article discovered that in the Fig. 4 diagram a short-circuit would arise when the push-button switch was operated. The draughtsman was, unfortunately, responsible for joining up two points, and thereby introducing the offending lead. A corrected diagram is given below, from which it will be seen that the short length of horizontal line between the cathode of V2 and the condenser C1 should be omitted. This was apparent to most readers, but for the benefit of those who are making the instrument and were not clear as to the correction needed, the amended diagram is given. In reply to those readers who wished to have details for modifying the time constant or other modifications we can again only repeat our standard reply to such requests—we are sorry but we cannot give individual modifications.



Corrected diagram of the Timer.

Great Britain's Valve Mail-Order House

**TAYLOR** Montrose 7-range Multi-meters. A.C./D.C. 50/-  
8 amp. precision M1 movement. 0.6-30-150-300 volt. 0-30 mA — 300 mA. Post 1/-.

**DARIO VALVE** at lower prices and one year guarantee. Ask for list.

**MIKE** Connects to radio or gram. Talk over your own radio, room to room. Easy to fix. Two mikes make 2-station house phone in your own home. Order-to-day. **12/6** Post 1/0.

**Q-MAX** Chassis Cutters and Keys. 1/4in. 1/2in. 1 1/4in. 1 1/2in. 1 3/4in. 1 7/8in. 1 9/16in. 2 1/2in. 3 1/8in. 3 1/2in. 3 3/4in. 4in. square. 2 1/4in. All prices incl. keys. **POST**

**ROD** Antennas. 1ft. sections, interlocking and extending, copper plated steel. BARGAIN! **2/6** dozen.

**SERVICE SHEETS** The one you require enclosed if available in a dozen assorted of our best choice. **10/6**

**HEADPHONES** High resistance light weight S. G. Brown make at 30/- and 27/- also special type, Brand New 14-0. Or ex-Govt. Low resistance. **6/-** Post 1/6

**SOLDERING IRON.** • The perfect Small Soldering Iron. • Adjustable Bit. • Easy to Handle. • Weight approx. 4 oz. • Heating Time 3 min. • 40 watt Economy Consumption. • **16/9**

**TYANA TRIPLE IRON.** Complete with detachable BENCH STAND. The smallest high-power soldering iron. Length only 8 1/2in. ; adjustable long bit dia. 3/16in. ; mains voltages 100,110, 200/220, 230 230. **19/6**

**B.T.H. GERMANIUM CRYSTAL DIODE.** Complete with Blueprint and operation instructions. **3/-**

**NEOFLEC CONDENSER TESTERS AND RECTIFIER UNITS.** Plugs straight into A.C. mains. 200/240 v., and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete. Supplies are becoming limited. **39/6** Post 1/-

**ENGLISH ELECTRIC TUBES** T.901 16in. for Magnavision view Supervisor. Telemek and Viewmaster. T.901a 16in. will replace in Ferguson, Bush, Peto-Scott, Philco and Sobell sets. **£22.4.10**

**EASY TERMS** ON ALL TAYLOR METERS. Terms up to 10 months and very near Cash Price. Please ask for full List, Terms and Proposal Form.

**SPECIAL VALVE OFFER**

01A	2/-	202STH	8/-
1B4	3/-	210VP	7/-
1LN5	7/-	EF6	17/6
2A6	2/-	KT241	5/-
2A7	3/-	MSPEN	5/-
2B7	3/-	P215	5/-
6AB7	2/-	PM12M	3/-
6J7	5/-	TP22	6/-
12A	2/-	VPI3C	7/-
12SF5	6/-		Post 9d.


A "BURNING" Question

**Blowlamp or Electrostrip ?**  
Unique Electric Paint Stripper outdates & outstrips Blow-lamp. No smell, no mess, cost 1d. per hour. One year guarantee. Unique. **37/6** Post 1/3

Kindly mark envelope P.W.3

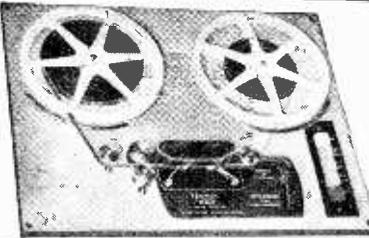**TRUVOX TAPE DECK MARK III**

Cash **£23.2.0**  
Deposit **£7.14.0**  
and 12 monthly payments of **29/-**



Deposit **10/-** monthly

Electric Paint Sprayer **75/-** Free Post 2/-



**Six Tools in One**


Punches, Bends and Shears Metal Strip. Rod & Angle. Every Handy man, Mechanic and Service Engineer needs one! 10,000 used! Unique! Order TO-DAY. Reduced from **20/-** **10/-**



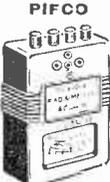**DEMOBbed Valves "Manual"**

Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of R.V.A. Equivalents and Comprehensive Price List. We have still some Valves left at very old Budget Rates (33 1/3%) which are actually sold at the old price. (1951 rate.)

**RADIO BULL VALVES**  
246, HIGH ST., HARLESDEN NW10



All-in-one Radiometer A.C./D.C. Tests everything in a Radio. Complete with Test prods. **29/6** Post 1/6

**Instantaneous! SOLDERING GUN 63/-**

Note these special features  
Instant Heating  
Ample Capacity for one-turbid listening on Crystal  
Temperature Control At the finger-tip  
Slender Bit Can be bent to shape to reach corners  
Automatic Feed Of molten solder by magnetic induction  
Fully Guar. for 12 months.

Ex Gov. Guar. "DEMOBbed"



double-headphones for undisturbed listening on Crystal Battery and Mains Set. **7/6** Post 1/6.

**VALVES FROM 2/-**

As advertised last month. We have still some left. Please enquire by return. Also for any other types.

**GORDONS TOOL KIT**



A handy kit of tools (Set No. 307BA). The set comprises five spanners covering B.A. sizes from 6 to 9. 4 1/2in. midjet adjustable pliers with slim bead head and a 2in. electrician's turn screw with plastic high-insulation handle. The tools are of chrome-vanadium steel, chrome-plated and polished, and packed in a clear plastic wallet with window panels. **22/-**

**CONDENSERS**

Wire Ends	Price
2 m d 450 v. ...	2/6
4 .. 450 v. ...	2/6
8 .. 500 v. ...	2/6
16 .. 500 v. ...	2/9
25 .. 25 v. ...	1/3
50 .. 50 v. ...	2/3

Cans  
8 / 8 m.d. 500v. 3/6  
8 x 16 .. 500v. 4/8  
16 x 16 .. 500v. 5/9  
16 x 24 .. 350v. 5/9  
16 x 32 .. 275v. 6/6  
16 m.d. Govt. Surplus 175 v. 1/- Post 6d.

**Contemporary**

Speaker FABRIC attractive colour and design. Special offer. 2-per square foot. Send 6d. for large sample.

AC/DC Neon Tester Type 400, **11/3**


**144** Useful Parts for itadio and Electrical Handyman. Separately packed per B.A. size. Screws, Washers, Nuts, Tags, etc., etc. Standard Handy Kit. **8/-**



**SOLDER** melts with a match. A tin/lead solder containing cores of Ersin flux sufficient for 100 average 1/- joints.

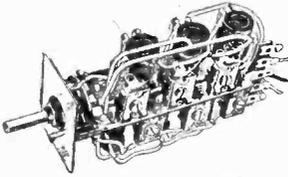**ELPICO TAPE AMPLIFIER**

Model AC/54  
Cash Price **£16. 16. 0**  
or Deposit **£5.12.0** and 12 monthly payments of **22/-**. Can be used for recording plays back and erase with any tape unit. Case to fit. **£4.15.0**.  
**MICROPHONES LUSTRAPHONE**  
Model C51/2. High Imp. Crystal **£5.15.0**.  
Model LX55 Crystal **£2.10.0**. Rothermel 2AD56. High Imp. Crystal. **£3.3.0**.




**THE 30 COIL PACK**  
for your  
**CORONET FOUR!**  
**FREE**

full details for building this super pack for a super set given FREE with each copy of our new Handbook The "HOME CONSTRUCTOR" (price 2/6 only), which also contains FULL WIRING DETAILS for building NINE first-class superhets together with circuits of TRF Receivers, 10-watt Quality Amplifier, Crystal Set, etc., Soldering, Metal-working, Constructional and Servicing Notes, Resistance Code, Useful Data, etc. Complete with fully illustrated catalogue. Obtainable from Radio dealers and stationers, or in case of difficulty send direct to SUPACOILS, 21, Markhouse Rd., London, E.17.

Selenium Rectifiers for Home Charging—6 or 12 volt. 2; Amp., 10/-, 4 Amp., 15/- Aluminium TV Tube 3/6. & 3/6. dia. 7d. & 8d. ft. Co-axial Cable. 50 ohm, 9d. yd., 75 ohm, 10d. yd. Twin Feeder, 75 ohm, 6d. yd., 300 ohm, K25, 9d. yd. Screened 1/3 yd. Condensers. .0005 mfd., 3 gang New & Boxed, 7/6. Valves. EF50 7/6, ECC35 8/6, EC54 4/6, & 6K7M 5/9. Orders over £2 Carr. Paid. Under 1/3. Send 6d. for 24-page Catalogue. Visit our Shop, open 8.30-6, inc. Sats. Tel.: St. Albans 5951.

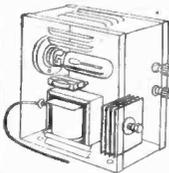**BOLD & BURROWS (G3HEO),**  
12-18, Verulam Road (A5),  
St. Albans, Herts.



**"AUTOMAT" CHARGER KITS**  
No. 2 kit as shown, built in one hour, simple, fool proof, troublefree. All new material with full guarantee, and ample rating. No. 2 kit, 12/14/3. 3 amp. Westinghouse selenium rect., 65 watt trans., halhath bulb for 2v., 6v. 12v. charger, 46/-; case, screws, grommets, 12/6 extra, post 2/-. No. 1 kit, similar but 2 amp. rectifier, 45 watt trans., ballast indicator bulb for 2v., 6v., 12v., charger, 38/6; case 12/6; post 1/10. Eliminator kit, trans., H.T. rect., 2v. 4 amp. trickle rect, condensers case, for 120v. 20 mA eliminator 37/6 P.P. 1/10.

**CHAMPION PRODUCTS,**  
43, Uplands Way, London, N.21.  
Phone: LAB 4167.

**LYONS RADIO LTD.**

3, GOLDHAWK ROAD, Dept. M.P.,  
SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEPherds Bush 1729

**POWER UNITS TYPE 285**

Input : 230v. A.C. mains. 50 cps.  
Output : E.H.T. 2 kV., D.C. 5 mA.  
H.T. 350v. D.C. 150 mA.  
L.T. 6.3v. 10 A. 6.3v. 5 A. A.C.

Originally used as a ground supply unit for operating R1355 receiver and Type 62 Indicator units. Contains valves VU120, 5U4 and VR91, with metal-cased smoothing condensers and constructed in the usual first-class manner associated with ex-A.M. equipment. Housed in metal-cased unit approx. 18 x 12 x 9 in., with fuseholders and input/output plugs on front panel. In new and unused condition.  
Price only £410/-, carriage 12/6.

**A.C. VOLTMETERS.**—Switchboard pattern. 6in. dia. M.I. type, calibrated at 50 cps. from 90v. to 170v. Price 19 6, post 2/-.

**SLYDLOK FUSEHOLDERS.**—5 amp size. 3 for 6 6, 6 for 11 6.

**MORSE CODE TRAINING SETS.**—Valve-operated oscillator sets which give a true representation of actual listening conditions. The circuit employs 2 valves ARF12 (VP23) with facility provided for selecting one of three differently pitched notes. All controls are on front panel and include volume, and terminals for headphones and two morse keys. The sets are housed in wooden instrument cases with circuit diagram in hinged lid. Power requirements : 60-120v. H.T. and 2v. L.T. Price, including valves 25/-; carriage 3 6. Optional extras : L.R. Phones, 5 9; Morse Keys, 2 6. Carriage free with above.

**UNLIMITED**

Battery Charger Transformer. 2 v., 6 v., 12 v. at 1.5 Amp. with Circ. 12/6.  
Metal Rectifiers. 12 v. at 2 Amp. 8/9.  
L.T. Transformer. Tapped, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 v., 19 6.

**AMPLIFIERS**  
"DEFESCO" AC2, Audio Amplifier. Two-valve plus Rec., 191 watt A.C. Mains. Complete Kit, incl. valves, 59 6.  
Wired and Tested, incl. valves, 75/-.  
"DEFESCO" AC5 PP, Push-pull amplifier, five-valve, A.C. Mains. V. & T. controls. Complete kit, incl. valves, £7.19.6.  
Wired and tested, incl. valves, £8.19.6.  
Descriptive leaflets on request.

"SNP LINE" Rev. counters, 9909, with Solinoid & battery, 5/6. Post free.  
ELM ROAD, LONDON, E.17. (Key 4813)

**STAN WILLETTS**  
43 SPON LANE, WEST BROMWICH STAFFS. Tel.: WES. 2392.

**VALVES—BRAND NEW—Guaranteed**  
6V8GT, 7 6, 6P8G, 5 9, 6K7G, 5 9, 5U4G, 7 6, E132, 5 9; 59/- doz, 83/- doz, 15/- doz, 2C34, BK34, 1 9, 18/- doz, 6A6G, 6 9; 78/- doz, 3D6, 1 11, EA50, 1 9; 18/- doz, 35L6, 9 6, 807, 7 6, N37, 7 6, W37, 5 9, SP61, 3 6. Post 6d.  
1T4, 1R5, 1S5 3S4, brand new, 27 9 set of 4, 7 6 each, post 6d.

**ROTARY SLIDING VANE BLOWER.**  
7 c. ft. per min. at 10lb. per sq. in. at 1,200 r.p.m. Brand new, 15/-, post 2/-.

**GERMANIUM XTAL DIODES.** type GEX34, brand new, 1/9; 15/- doz, post 3d.  
Complete set of parts for CRYSTAL SET construction, 2 wave band, less phones, 9 6, post 6d.

**WANTED**  
VALVES. C.R.T. GOOD PRICE PAID.

**Just Published**  
**RADIO CONTROL OF MODELS**

by G. Sommerhoff

This book gives circuits (some for the first time) and constructional data of radio control gear for model aircraft, model power boats, sailing yachts and cars. Not only are the simplest and cheapest methods shown, which would be very suitable for the beginner, but also the more complicated methods, so affording the opportunity of improving existing equipment. 3s. 6d., postage 3d.

**Basic Electronic Test Instruments,** by R. P. Turner. 32s. 0d., postage 9d.

**Electronic Gadgets for the Constructor,** by E. N. Bradley. 3s. 6d., postage 3d.

**Practical Wireless Encyclopaedia,** by F. J. Camm. 21s. 6d., postage 1s.

**Telecommunications Principles,** by R. N. Renton. 37s. 6d., postage 1s.

**Radio Data Charts,** by R. T. Beatty, revised by J. McG. Sowerby. 7s. 6d., postage 6d.

**Radio Valve Data** compiled by *Wireless World*. 3s. 6d., postage 3d.

**THE MODERN BOOK CO.**

Britain's largest stockists of British and American technical publications.

19-23 PRAED STREET,  
LONDON, W.2.  
(Dept. P.3)

Please call or write for our new catalogue.  
Phone: PADdington 4165. Open all day Saturday.

**ASTRAL RADIO PRODUCTS**  
(T. C. HOWELL)

**OUTSTANDING BARGAIN.**—Midset I.P.F.'s, 465 kc/s iron cored, 13/16in. square x 1 1/2 in. high. Brand New High "Q." 6/- pair, postage 6d.

**T.R.F. Coils** as used in original model 3-Band All Dry 3 (April '53 issue P.W.). 6/6 pair, postage 6d.

**Dual-Wave H.F. Coil** as used in original models: Summer All Dry Portable, Modern 1 and 2 Valve, etc., etc. 4/3 each, post 6d.

**"K" Type Coils** as used in original model A.C. Band Pass 3 3/3 per coil. Osc. and S.W. band also available, postage 6d.

**M.W. Frame Aerial.**—Litz wound, very high gain, on bakolin, size approx. 5in. square 5/- each, post 6d.

**STANDARD T.R.F. COILS** J. & M.W. 5/6 pair boxed post 6d.  
See separate advert. for details of our new publication "Home Radio."

139, The Ridgway, Woodingdean, Brighton, 7.

**J. B. SERVICE (BEXLEY-HEATH) LTD.,**

Mail Order Dept.,  
5, MAYPLACE ROAD WEST,  
BEXLEYHEATH, KENT  
Phone: Bexleyheath 1000.

**SILVERED MICA CONDENSERS.** Brand new, 5pF, 20%, 6d. each; 240pF, 330pF, 820pF, 1500pF, 1650pF, 5%, 9d. each; 510pF, 2%, 1 - each; 240pF, 1%, 1 3 each. Midset Ceramic, 8pF, 10%, 18pF + - 5pF, 9d. each.

**GRADE 1 HIGH STAB RESISTORS.** 470 ohms, 5%, 1 watt, 1/- each.

**NEW RETAIL SHOP NOW OPEN:**  
44, CHURCH ROAD,  
UPPER NORWOOD, S.E.19  
Phone: Livingstone 6222.

# OPEN TO DISCUSSION

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## TV Interference

SIR,—I have never seen fairer comment than that which appears in your January editorial and I heartily congratulate you.

My only regret is that it will not come to the notice of the many misguided TV owners who seem to have been persuaded that 90 per cent. of their troubles are due to privately-owned motor-cars, though the truth is almost the reverse.

Further to the examples you quote, it is on record that a radio service van was recently driven away from a house, creating a veritable snowstorm on the screen of the receiver which had just been serviced!

—C. N. COURTNEY (Barking).

## Radio-controlled Models

SIR,—How pleased I was to see Mr. G. Paish's letter in your last issue of PRACTICAL WIRELESS asking for a section on radio-control although why only in the summer I do not understand. The summer may be the time for operating the models, but winter evenings are when they are made.

Radio control has so many varied possibilities and is so relatively unexplored except by a few who do not publish their ideas, that I feel it would offer your excellent magazine even more variety, and certainly gain the appreciation of those readers whose interests lie deeper in "applied radio" as opposed to "pure radio." C. L. YOUNG (Southampton).

## The Amateur Transmitter

SIR,—Here are a few brief replies to points raised by Mr. H. Cole and Mr. C. Roberts in reply to my letter in your October issue.

1. The question of Parliamentary voting is one which concerns the people of this country only; the allocation of radio frequencies affects other countries and is primarily decided by the Atlantic Conference, and not by the British Post Office.

2. Amateur stations have been known to interfere with essential service stations; this can easily occur if the service station is listening to a weak signal which the amateur cannot hear.

3. Crystal control is just as liable to cause interference as any other method of control: it is fairly obvious that Mr. Cole is not aware of the different ways interference can arise and this is a very strong reason for not giving him a licence!

4. Radiation from model control transmitters is a matter of yards, not of miles, owing to the low aerial, of an inefficient type, and high frequency.

5. I did not say that a licensed amateur never interferes with other services; my point was that he is less likely to do so than another with no knowledge of transmitter theory, and that if interference is brought to his notice, he will know what to do about it.

6. If Mr. Roberts cannot read morse, how can he possibly distinguish between the Continental commercial stations on 80 metres and British amateurs? It is a comparatively rare thing to hear a British amateur operating badly, but the less said the better about some of the commercial stations. Some of the amateur bands are shared with other services, and amateurs are allowed to use them "subject to non-interference with other services" (terms of licence).

7. I have never yet heard a licensed British amateur operating on an unauthorised frequency, but I have heard it done by an operator whom I knew to be a pirate (subsequently caught and heavily fined!). How does Mr. Roberts know that the 4.2 Mc/s. offender was not a pirate, and how did he measure the offender's frequency so accurately?—V. G. P. WILLIAMS, G3FYY (London, N.W.2).

## Coastal Radio Beacons

SIR,—I was delighted when I saw the article on "Coastal Radio Beacons" in the December issue.

I suggest you follow up with a small article each month on the other radio navigational aids. Could your technical department issue a set design to cover the following conditions: (1) all dry; (2) cover shipping and radio bands; (3) Long range. It need only be on headphones; (4) minimum of controls; (5) Incorporate a D/F loop aerial, if possible.

The set would then be a very handy set to have at sea. Time checks with the "pips" could be taken for navigational work, weather forecasts, etc., for general safety, and if a D/F loop aerial is possible, radio navigation can be used.—W. A. ANDERTON (Nelson).

## Reader's Appeal

SIR,—I should like to appeal to any reader who has any circuit or handbook of the 358 ex-government communications receiver to be kind enough to loan it to me.

I have one of these receivers minus coil units, and I wonder if any of your readers have successfully used other coils?—J. WALWYK (Hounslow).

*Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.*

## Radio-controlled Models

SIR,—Your correspondent, G. Paish (Devon) (Feb. issue, p. 122), who is asking for information on audio frequency tone modulated radio controlled models, may find the following to be of interest.

Anon, "Radio-Craft," Jan. 1946, p. 242, Radio Target Planes.

Anon, "Wireless World," Sept. 1951, p. 342, Radio Telecarriers.

Bruinsma, A. H., "Remote Control by Radio" (Philips Technical Library).

Chantrill, John J., "Newnes Practical Mechanics," July 1949, p. 299, and Aug. 1949, p. 338, Radio Controlled Model Battleship.

Honest-Redlich, G., "Radio Control for Models" (Harborough Pub. Co.), pp. 39-46, R.F. Circuits, Modulated Carrier; pp. 73-80, Special Intergear for Modulated Carriers.

Hunt, Peter, "Radio Control for Model Aircraft," (Harborough Pub. Co.), p. 53, Audio Frequency Control.

Osborne and Dunn, "Radio-Craft," Oct. 1947, p. 20, Ploughing by Radio.

Queen, I., "Radio-Craft," Jan. 1945, p. 212, A Radio Robot Convoy.

Rayer, F. G., "Newnes Practical Mechanics," Feb. 1953, p. 86, Radio-Controlled Boat Mechanism.

Safford jr., Edward L., "Model Control by Radio" (Radcraft Publications, Inc.), p. 22, Resonant Relays and Reeds; p. 30, Bandpass-Band Elimination Filters; p. 32, Band Rejection Filters; p. 33, Discriminators; pp. 59-63, Tone-Operated Receivers; pp. 64-69, Tone Modulated Transmitters.—JACK POTTER (Whitley Bay).

## Noise and the R1155

SIR,—Being an owner of a R1155 I feel that all this changing of valves in the receiver to try to cut down the noise level is unnecessary. With a good aerial, cut for the frequency it is receiving on, the noise level will drop considerably. The R1155 which I possess is about a year old and apart from removing the D.F. parts and putting in an output stage the set has never been modified and the signal-to-noise ratio is extremely good. The aerial I use is a 132ft. long wire. Admitted, the bandwidth on the 55 is not very good, but apart from that it is an excellent receiver.—M. KELFITT (Leicester).

## D.C. Supplies

SIR,—I learn from statistics supplied by the British Electricity Authority that there are over six million homes supplied with Alternating Current and something less than half a million with Direct Current. Further, it is hoped, economic conditions permitting, to transfer all D.C. supplies to A.C. (240 volts) within the next five years.

I have much sympathy with the "D.C. Brigade" but I feel that with these figures in mind there is

little justification for PRACTICAL WIRELESS designers confining themselves to A.C./D.C. type circuits.

My own experience is, and I fancy that it will be generally conceded, that the "Universal" type of receiver does not give the same performance as the A.C. only type. The increased safety factor due to mains isolation and lesser heat dissipation alone must weigh heavily in favour of this type of circuit, apart from the higher voltages available and simpler arrangement of valve heater wiring. I deprecate the trend towards "Universal" television circuits and imagine that these are prompted more by pricing than technical considerations and must ultimately lead to inferior results and more frequent servicing.

Surely your best course is to continue the present policy of designing fundamentally for A.C. and also producing a universal version, as with the recent "Coronet." I would suggest that D.C. only circuits would be rather a waste of time; although cheaper to produce than their A.C. counterparts. Direct Current is on the way out, even if somewhat slowly. PRACTICAL WIRELESS circuits have a reputation for longevity, and conversion of supplies to A.C. might well take place before the useful life of a D.C. receiver was spent!—FRANK H. COWLES (Southall).

SIR,—I am now 59 years of age and my newsagent will confirm you that I have for many years taken your Wireless and Television monthlies. Many times I have found them interesting and helpful, but only when you have catered for D.C. or A.C./D.C. We have a good area with D.C. and many more would welcome more A.C./D.C. circuits.—F. C. MACKIE (Gateshead).

## Use of the 6N7G

SIR,—With reference to the letter signed "Dreamer, Manchester," in the January issue of PRACTICAL WIRELESS, it may be of interest to report my own experience.

I modified my existing quality amplifier, which had been using a triode-connected KT63 output valve (driven by an L63) and replaced the KT63 with a 6N7G. Although this was, for myself, an expensive modification, I thought it was worthwhile because I then had 10 watts of very good quality output from the amplifier. Before modification, with only 5 watts, there was an excessive quantity of H.T. current wasted which is now being used by the 6N7G.—A. BLAKEMORE (Derby).

## R1132A

SIR,—I should like to contact a reader who has bought and modified an ex-R.A.F. R1132A. My receiver operates well except for a loud hum, not due to smoothing, and the 6V6 output valve gets too hot to hold after about five minutes.

I wonder if any of your readers has experienced the same trouble and if he would write to me?—R. PINCHES (Plymouth).

Editorial and Advertisement Offices: "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4383. Telegrams: Newnos, Rand, London. Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. We give no warranty in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

# BARTON'S (Radio) LIMITED


(Dept. PW), 42 TOTTENHAM CT. RD., LONDON, W.1.

Telephones: LANGHAM 1151/2
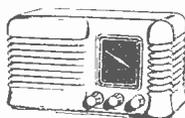
## BUILD YOUR OWN RADIO!



We can supply all the parts (including valves, 5in. moving coil speaker, cabinet, chassis, and everything down to the last nut and bolt) to enable YOU to build a professional-looking radio. The chassis is punched and drilled ready to mount the components. There is a choice of any of three attractive cabinets 12in. long 5in. wide by 6in. high, as follows: either Ivory or brown bakelite, or wooden, finished in walnut.



Complete and easy-to-follow point-to-point and circuit wiring diagrams supplied.

### MODEL I. T.R.F. RECEIVER

This is a 3 valve plus metal rectifier TRF Receiver with a valve line-up as follows: **6K7 (HF), 6A7 (DET) and 6V6 (Output).** The dial is illuminated and when assembled the receiver presents a very attractive appearance. Coverage is for the Medium and Long Wave bands. Operates on 200/250 volts AC Mains.

Plus 2/6 Packing. **£5.15.0**  
Carriage, Insur.

### MODEL 2. SUPERHET RECEIVER

This is a powerful midget 4 valve plus metal rectifier Superhet Receiver with a valve line-up as follows: **6K8, 6K7, 6Q7, 6V6.** The dial is illuminated and coverage is for the Short Wave bands between 16-50 metres, the Medium Wave bands between 190-540 metres, and the Long Wave bands between 1,000-2,000 metres. Operates on 200/250 volts AC mains.

Plus 2/6 Packing. **£7.19.6**  
Carriage, Insur.

**T.R.F. RECEIVER** We can supply this Receiver ready built at **£6.19s. 6d.** plus 3/6 p.c. **ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR**

**NOTE:** We would respectfully suggest to those interested in building these receivers that **OUR** circuit diagrams be compared with those of other firms. Intending constructors can then judge for THEMSELVES which Instruction Booklet is the most comprehensive. Instruction Booklet and priced Parts List for either of the above receivers available separately at 1/- This money will be refunded if circuit diagram is returned as NEW within 7 days. When ordering please state Model No.

### BATTERY CHARGER KIT

Incorporates metal rectifier. Transformer is suitable for AC mains 200/250 volts. Charges either 12, 6 or 2 volt accumulator at 1 amp. Complete with circuit diagram. Price **£2 6s.** plus 1/6 post and packing.

### MAINS TRANSFORMERS

Type LP1.	250-0-250, 60 mA.	6.3 v. 3 amp. 5 v. 2 amp. Fully shrouded	22 9
.. LP1.	275-0-275 v. at 80 mA	0.4 6. 3 v. at 4 amps. 0.4 5 v. at 2 amps	22 6
.. LP6.	350-0-350, 80 mA.	6.3 v. 5 amp. 5 v. 3 amp. Half shrouded.	28 -
.. LP6.	350-0-350.	120 mA. 6.3 v. 5 amp. 5 v. 3 amp. Fully shrouded	29 6
.. LP7.	425-0-425, 150 mA.	6.3 v. 5 amp. 5 v. 3 amp. Fully shrouded	37 6
.. LP3.	C.T. 5 v. 3 amp. Fully shrouded	52 6	
.. LP10.	430-0-430, 200 mA.	6.3 v. 4 amp. 6.3 v. 4 amp. 5 v. 3 amp. F.S.	55 -
.. LP11.	350-0-350, 150 mA.	6.3 v. 5 amp. 5 v. 3 amp. Fully shrouded.	44 6
.. B12.	350-0-350, 150 mA.	6 v. 3 amp. 4 v. 3 amp. 30 v. 0.5 amp. incorporates voltage adjustment panel tapped 200 210 v., 220 230 v., 240 250 v. Semi-shrouded drop through type	21 -
.. B13.	250-0-250, 80 mA.	6.3 v. 4 amp. 5 v. 2 amp. Universal Upright mounting	23 6
.. B14.	350-0-350 80 mA.	6.3 v. 4 amp. 5 v. 3 amp. Universal Upright mounting	23 6
.. B15.	General Purpose Step-down Transformer. Tapped 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v. Total Output 30 v. at 2 amp. 20 v. at 3 amp.		

All the above are plus 1/6 post & pkg.

### METAL RECTIFIERS

S.T.C.	R.M.1. 125 v. 60 mA.	4 6
	R.M.2. 125 v. 100 mA.	5 -
	R.M.3. 125 v. 125 mA.	6 -
	R.M.4. 250 v. 250 mA.	18 -
E.B.T. PENCIL RECTIFIERS	K3/50. 4 Kv.	8 8
	K3 100. 8.5 Kv	14 8

### METAL RECTIFIERS (FULL WAVE)

12 v. 1 amp. (Bridge Type), 7 6 ; 12 v. 2 amp., 11/3 ; 12 v. 3 amp., 12 - ; 12 v. 4 amp., 15 -.

### METAL RECTIFIERS BRAND NEW!

300 v. 75 mA. may be used in series or voltage doubling to give any required voltage. 7 11, plus 6d. post/pkg.

### RESISTORS (CARBON)

1 and 1/2 watt, 3d. each. 1 watt 5d. each. All preferred values from 10 ohms to 10 megs.

### ELECTROLYTIC CONDENSERS BRAND NEW!

8 mfd. 150 v. ....	1 C	25 mfd. 50 v. ....	1 6
8 mfd. 150 v. ....	2	20-20 mfd. 275 v. 2	3
8-8 mfd. 450 v. 3 6		25 mfd. 25 v. ....	1 6
8-16 mfd. 350 v. 3 11		50 mfd. 50 v. ....	2 -
16 mfd. 450 v. ....	3 6	8-16 mfd. 350 v. 3 11	
32 mfd. 500 v. 4 11		4 mfd. 450 v. ....	1 6
50 mfd. 12 v. ....	1 6	32-32 mfd. 370 v. 3 11	

### AUTO TRANSFORMERS

Tapped 10 v., 120 v., 200 v., 230 v., 250 v. 100 w. 22/-  
All the above are plus 1/6 post & pkg.

### MICROPHONE TRANSFORMERS

Ratio 100 : 1. Has innumerable uses. 1/11 plus 6d. post/packing.

### THE NEW ACOS 35-1

Crystal mike, output level—55db. Ref. iv./dyne cm., 25/- plus 6d. post. & pkg.

**WE CARRY VAST STOCKS OF RADIO TELEVISION AND ELECTRICAL COMPONENTS—We invite your enquiries.**

**TERMS OF BUSINESS:**  
Cash with order (or C.O.D. Post items only); all orders for small items totalling over £2 post free unless otherwise stated.

## Announcing a NEW 4 watt AMPLIFIER KIT

This is a 3 valve 3 stage Amplifier for use with Gramophone, Microphone or Radio. **Valve line-up is as follows—6N17, 6V6, 5Z4.** Negative feed-back. Tone control. Voltage adjustment panel incorporated. 4 watts output. For operation on A.C. Mains 200/250 volts. The complete Kit, includes every item down to the last nut and bolt, drilled and punched chassis, and comprehensive point-to-point wiring circuit diagram.

**ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR**



**PRICE £4.19.6** Plus 2/6 PACKING, CARRIAGE & INSUR.

The Output Transformer supplied is for use with a loudspeaker of 3 ohms impedance and we would suggest that the output of the completed amplifier justifies the use of one of the latest W.B. H.F. Speakers which can be supplied as follows: 8in., 60 6; 5in., 67 -; 10in., 73 6. All plus 2 6 pkg., carr., insur.

Circuit Diagram only, available separately at 1/-.

To those who require this Amplifier ready-built we can supply it at **£5.19.6**, plus 3 6 pkg., carr., ins.

### LOUDSPEAKERS

**THE LATEST RANGE OF W.B. H.F. SPEAKERS**

Incorporating the NEW Composite Cone  
W.B. 6in. H.F., 10,000 lines, 3 ohms. **£2 10 6**  
W.B. 8in. H.F., 10,000 lines, 3 ohms **£3 0 6**  
W.B. 9in. H.F., 12,000 lines, 3 ohms. **£3 7 0**  
W.B. 10in. H.F., 12,000 lines, 3 ohms. **£3 13 6**  
(Also available 15 ohms imped.)


TRUVOX 12in., 2-3 ohms. SPECIAL OFFER.	47/6
WHARFEDALE BRONZE 10in. Flux Density, 10,000 lines 6 w. 15 ohms	£4 12 8
WHARFEDALE GOLDEN 10in. Flux Density 13,000 lines 8 w. 15 ohms	£7 13 3
WHARFEDALE GOLDEN/CSB 10in. Flux Density 13,000 lines, 5 w. 15 ohms	£8 6 7
WHARFEDALE SUPER 8cs. AL 8in. Cloth Suspension, Flux Density 13,000 lines, 4 w. 10 ohms	£6 13 3
WHARFEDALE SUPER 5/CS AL 5in. Cloth Suspension, Flux Density 13,000 lines 10 ohms	£6 13 3
WHARFEDALE W12.CS 12in. Cloth Suspension, Flux Density 13,000 lines, 10 w. 15 ohms	£9 15 0
WHARFEDALE W12 12in. Flux Density 13,000 lines, 15 w. 15 ohms	£9 5 0
GOODMANS 8in., Axion 101 H.F., 15 ohms 5 w. peak A.C.	£6 12 0
GOODMANS 12in., Axion 150 twin cone H.F., 15 ohms 15 w. peak A.C.	£10 5 6
GOODMANS 12in., Audiom 80 H.F., 15 ohms, 15 w. Peak A.C.	£8 12 6

All the above plus 2 6 pkg., carr., ins.

**QUALITY GOODS • MONEY BACK GUARANTEE • PROMPT DESPATCH**
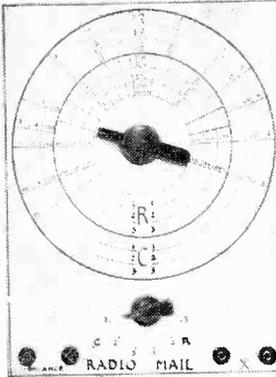
# RADIO MAIL

DEPT. F,  
4, RAYLEIGH STREET,  
NOTTINGHAM



## TEST GEAR IN KIT FORM

**NO** CALIBRATING  
OR METAL WORK  
**JUST ASSEMBLE  
AND USE**

## RES/CAP. BRIDGE

SIX DIRECT  
READING RANGES  
500 pf—50 mfd  
10 ohms—5 megs

**31/6** P. & P.  
1/6

## INDUCTANCE BRIDGE 42/6

Five direct reading ranges. 50 micro/Hy—100 Henries.

**R.M. TWIN MULTI-OHMER 25/-** P. & P.  
1/6  
Our latest product, becoming tremendously popular with all classes of radio men. Send for details.

## I.F. ALIGNER 17/6

Tunes over 465 Kc/s range of I.F. freqs. Fully screened. Pre-tuned.

## AUDIO FREQUENCY BRIDGE 38/6

Measures all audio frequencies from 40 to 16,000 cycles in three ranges. Direct reading.

Cash with order or C.O.D. Stamp for illustrated leaflets.

# WE PAY TOP PRICES

FOR  
AMERICAN SURPLUS ELECTRONIC EQUIPMENT  
Any Quantity or Condition

## LOOK AT THESE EXAMPLES

For equipment in good condition

- SCR291, complete £350
- Receiver R54 APR1 with all tuning units ... £135
- Transmitter RT4336 ... £110
- Receiver RC348R £25
- Frequency Meter TS175 ... £80
- Test Set TS27 ... £25
- Scanner RC91 ... £100
- Test Set TS13 ... £100

- Tranceivers. ARCI, ARC3, SCR522, TCS, BC800, RT/APN2.
- Indicators, ID6B/APN1, ID17/APN3, ID18/CPN2, BC1151, BC1152, BC1159, MG112, 1-81A, 1-82A.
- Test Sets, Any unit with prefix "TS." 1E19, BC638, 1-208, DC1001, BC1142, CM3.
- Synchroniser, BC1149.
- Power Units, RA31, RA42, RA59, RA62, RA88, RA90, MG149, PE93, FE158, DM28.
- Tuning Units, TN17, TN18, TN19, TN54.
- Control Gear, BC1150, BC1145, JB91, JB95, JB93, JB102, PN31, PN32.
- Antenna Gear, BC223A, RC94, AS27, AT1, AN101.
- Mountings, FT237, FT247A.

We pay similar Remarkable Prices for:

- Scanners, Any type, any condition.
- Receivers, R11U/APR5, R89B/ARN5, R65/APN5, R15/CPN2, BC349.
- Transmitters, CPN2, T11/APN3, BC1139, TDE.
- R5/ARN7, R13/APN3, BC1147A, ART13, TDQ.

• And almost every American made unit even if not mentioned above.

Phone us immediately, transfer charge.

• Deal with the firm that has been established for twenty-five years and which is by far the largest buyer of Ham Equipment.

### ALTHAM RADIO CO.

JERSEY HOUSE, JERSEY STREET, MANCHESTER, 4  
Telephone: Central 7834/5/6

# FREE To AMBITIOUS ENGINEERS!

This 144-page Book

Have you sent for your copy?

## 'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses, in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

--- FREE COUPON ---  
Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

## WHICH IS YOUR PET SUBJECT?

Mechanical Eng.  
Electrical Eng.  
Civil Engineering  
Radio Engineering  
Automobile Eng.  
Aeronautical Eng.  
Production Eng.  
Building, Plastics,  
Draughtsmanship  
Television, etc.

## GET SOME LETTERS AFTER YOUR

NAME!  
A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.P.E.  
A.M.I.M.I.  
L.I.O.B.  
A.F.R.Ae.S.  
B.Sc.  
A.M.Brit.I.R.E.  
CITY & GUILDS  
GEN. CERT.  
OF EDUCATION  
etc., etc.

NAME .....  
ADDRESS .....

Subject or Exam.  
that interests me  
British Institute of Engineering Technology,  
409B, College House, 29-31, Wright's Lane,  
Kensington, W.8.

# BIET

# SOUND MASTER SERVICE

The Sound Master is an entirely new Portable Tape Recorder which has been produced especially for the Home Constructor by the designer of the famous View Master Television.

Full constructional details are now available.

INSTRUCTION ENVELOPE,  
6/6d. post free.

WRITE NOW for our fully detailed price list.

We carry full stocks of all items needed for the Sound Master and can offer a  
**RETURN OF POST SERVICE.**  
**FULL HIRE PURCHASE FACILITIES**  
AVAILABLE on complete or part kits.

## WATTS RADIO

(Weybridge), LTD.,

8, Baker Street, Weybridge, Surrey.

# Smith's of EDGWARE ROAD

COMPONENT SPECIALISTS SINCE BROADCASTING STARTED

Invite all those interested in

## ELECTRONIC COMPONENTS

to send for particulars of their

## New Mailing List Scheme

Price-lists also available for:

- "Viewmaster" Television
- "Teleking" Television
- "Magnavision" Television
- "Soundmaster" Tape Recorder
- "Coronet" A.C. Four.

**H. L. SMITH & CO. LTD.**  
287/9 Edgware Road, London, W.2.

Tel.: Paddington 5891. Hours: 9 till 6 (Thursday 1 o'clock).  
Nr. Edgware Road Stations, Metropolitan and Bakerloo.

## HANNEY of BATH offers:— VIEWMASTER IN EASY STAGES

Constructor's Envelope 7.6. Stage 1, 62.3; two 43.3; three, 25.1.8; four, 9.10; five, 21.0.4; six, 27.7.3; seven, 64.0. Complete pre-amp kit (less valve), 32.2.

WB100 (sound and vision chassis), 18.6; WB101, 6.7; WB102, 18.6; WB103, 42.7; WB103A, 52.6; WB104, 15.6; WB105, 47.2; WB106, 25.6; WB107, 32.6; WB108, 33.3; WB109, 1.2 or 3 (state tube type), 22.6; WB110, 10.0; WB112, 21.6; WB Console conversion kit, 35.0; WB300 pre-amp chassis, 17.6; Westinghouse Rectifiers, 14A66, 20.4; 14D36, 11.7; WX3 and WX6, 3.9 each; 36EHT100, 29.5; 36 EHT50, 26.1; 36EHT35, 23.8; K3 100, 14.8; K3 50, 8.9; K3 45, 8.2. T.C.C. Condensers, 27.10 (any condenser supplied separately). Morganite pots, 5.0 each; Manganite resistors, 35.3. Colvern pots, 22.6; or CLR901 3.3 each and CLR4089 22.6.4. Belling-Lee 1.707, 8.8. Puses, 61. ea. h. Wearite Coils (with L.O. L'don and Belfast 22.0. Wenvoe and Pontop Pike 28.0. H. Moss, K.O.S, B'ham and Brighton, 30.0. Pre-amp coils 4 - pr. any channel).

**TELEKING.** Constructor's Envelope, 6.0; Coils, 44.6; Chassis kit, 50.0; T.C.C. kit, 27.4.3; R.H.I. kit, 21.0; Allen Components, L.O.308, 40.0; F.O.305, 21.0; D.C.300, 39.6; F.C.302, 31.0; G.L.16 and G.L.18, 7.6 each; B.T.314, 15.0; S.C.312, 21.0; A.T.310, 30.0; O.P.117, 9.0; Dubilier Resistor-pot, kit, 61.6.

**SOUNDMASTER.** Constructor's Envelope 6.6. W.B. Kit £11 13.2; 3 Collaro Motors 25.15.0; Lab. resistors pots, 48.6; T.C.C. condensers 82.0; Wearite kit, 27.0; Bulein kit 70.0; NSF switches 35.6; Brenell tape desk, unassembled 21.13.0; W.H. cabinet, 26.6; Mulard Valves 25.18.2; Lustraphone C51Z mike 25.15.0. Stand extra 10.6.

### P.T. SUPER VISOR

TCC Condenser kit, 28.6.4; Erie resistor kit, 54.4; 4 w/w pots, 26.0; 7 Erie carbon pots, 35.0; Allen coils, 44.6; Allen DC 300C, 39.6; G.L.16 and G.L.18, 7.6 each; S.C.312, 21.0; F.C.302, 31.0; O.P.117 output trans., 9.0; Denco WA F.M.A.I. 21.0; WA.L.O.T.I. 42.0; Denco chassis kit, 51.6; Westinghouse WX.6, 3.10; WG.4A, 7.6; LW.7, 26.8; English Electric polystyrene mask, 42.0; perspex filter, 18.6; anti-corona ring, 10.10; Tube sheath, 6.2; T.501 tube, inc. carriage and insurance, 22.14.10; Elac IT 8 ion trap, 5.0.

Send diff. in stamps for our GENERAL LIST, which contains details of components for Viewmaster, Teleking, Magnavision, Super Visor, Lynx, Coronet Four, Williamson Amplifier, Soundmaster, etc., etc. Please add postage to orders under £2.

## L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH. Tel: 3811

## The solder for all HOME TELEVISION CONSTRUCTOR SETS

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60 40 High Tin Television and Radio Alloy. The size 1 Carton contains 55 feet of solder, costs 5/.



## Ersin Multicore Solder


In case of difficulty in obtaining supplies, please write to:  
MULTICORE SOLDERS LTD, MULTICORE WORKS, MAYLANDS AVE., HEMEL HEMPSTEAD, HERTS. • Boxmoor 3636 (3 lines).

## Armstrong

Specialists in high quality radio for over 20 years offer to the enthusiast their
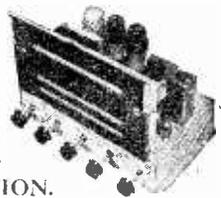
## 2 outstanding new models

which still further substantiate their name for PERFECTION.



**FC.38** 8 valve Superheterodyne chassis, giving 8 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls. WAVE RANGE: 16-50 metres, 190-550 metres and 1,000-2,000 metres. PRICE: £23 13s. including tax.

**RF.41** 10 valve Superheterodyne chassis, giving 10 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls, also a highly sensitive R.F. stage before the mixer. WAVE RANGE: 12-90 metres, 190-550 metres and 800-2,000 metres. PRICE: £31 19s. 8d. including tax.

Both High Class Chassis at an economical price giving AMAZING Realistic Radio and Record Reproduction from the modern records. Money back guarantee on every chassis supplied.

## ARMSTRONG WIRELESS & CO. LTD.

WALTERS ROAD, HOLLOWAY, LONDON, N.7.

Telephone: NOrth 3213/4.

**RECEIVERS & COMPONENTS**

**EVERYTHING** for radio constructors. Condensers, Coils, Valves, Resistors, etc. Send stamp for list. SMITH, 98, West End Road, Morecambe. Quick service.

**LARGE QUANTITY**, ex-equip., working perfect with any Coil Pack. 465KCS IFTs, dust iron core, bench superhet tested, pr. 4/6, p.p.; doz. prs., 42/-, p.p.; Var. Cond., all lin. spindles and 500 pf. p.gang, Single 1/6; Superhet Twin. 3/6; 4 gang. 2/6 (post 1/-); brand new and Tested. 1/350, 2/6 doz., 20/- gross; Tropic .01/1000, 1/350, 1/500, 3/6 doz. 30/- gross; 32/F/450. 4in. x 2in. diam., 1/9 ea., 18/- doz.; BTG (1R), ceram V/holder, 8d. ea., 6/- doz., 60/- gross; packing free; post extra, s.a.e. full list. **THE RADELECTRIC CO.** (Prev. Radio Services), Lr. Bullingham, Hereford. (Phone: 4857.)

**PRESELECTORS**, Receivers, Transmitters, Amplifiers, etc.: equipment constructed to specification; all types of radio communications equipment serviced; collect and deliver London area. Send stamp for latest list. **RADIOCRAFT LTD.**, 25, Beardell St., London, S.E.19. (Tel.: GP. 5585.)

**BRAND NEW**, "Goodmans" Output Transformers, made for 6V6s in P.P., 6/6 each; "Polar", .0005 mfd. Tuning Condensers, standard spindles, 4/6 each; new and boxed Hand Mics., tried and tested on tape recorders with perfect results, reduced from 22/2/- to 29/6 each; brand new 6SH7s in original boxes, 5/- each; M/C Meters 0-500 mA 2in. diam. 7/6 each; Miniature 0-30pf air-spaced Trimmers, normally 2/6, our price 9d. each, or 7/6 doz.; Meter Switches, 6 pole, 5 way 13 banks, 2 pole, 5 way each bank, 5/- each; Ceramic 5-pin U.X. Bases, 9d. each. Don't forget our now famous Chassis Service." If you are not on our mailing list, write for details and our new 1954 free list. **SERVIO RADIO**, 156-8, Merton Rd., Wimbledon, S.W.19. (LIBerty 6252.)

**TRANSFORMERS**, EMF. input 110/245v. output, 350/0/250v., 120ma. 6v. 4a. 4v. 2a. Drophthru, 18/- (p. paid) Octal (baseboard mounting) Valveholders, 3/- doz.; Meters, 2in. sq., 5ma. or 100ma. 7/-; Bat. Amplifier, with valve QP21, etc., 7/6; with EF36, relay and trans., etc., 7/6; Pots, w. w.d., 20k. 10w. 3in. dia., 3/6; EHT Filter Boxes, with 15kV ceramic conds., 500pf and 750pf and chokes, 5/6; LI/HT Filters, D.C., with 4 conds. and 4 dust chokes, 2/6; Responder, 4790, 10 valves, 160/220mes, 30/- (5/- carr.); postage extra. Cash with order; immediate delivery. s.a.e. for list/enquiries. **W. A. BENSON**, 308, Rathbone Rd., Liverpool, 13.

**OSMOR** for really efficient coils, coil packs, and all radio components, as specified for many "Practical Wireless" circuits. See our advert. on page 134 of this issue for free circuit offer, or send 5d. stamp to address below. **OSMOR RADIO PRODUCTS, LTD.** (Dept. PC3), Borough Hill, Croydon, Surrey. (Tel.: Croydon 5148/9.)

**VALVES**, PT.15, 5/-; ML6, 4/-; Meters, 3.5 A. (TC), 100ma (MC), 4/-; Oil Thermometers 0-100°C, 6A/683, 9/-; Oil Pressure Cages, 150lb./sq.in., 6/-; RF Chokes, 8.8 MH, 1/6; 1.5 MH, 6d.; post extra; free lists. **ANNAKIN**, 25, Ashfield Place, Olley, Yorks.

**RATES**: 5/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Lower House, Southampton St., Strand, London, W.C.2.

**MIC PLUGS** in P.U. sockets, 5/6; small M/R O P Trans., 2/6; new 6V6GT, 7/6; 6Q7GT, 5Z4, 9/-; Bargain list 6d. **CARTERS**, 578, Washwood Heath Rd., B'ham, 8. (EAS 3017.)

**CHASSIS**, 4 sided, 18 s.w.g., aluminium, 9 x 7 x 2in., 4/6, plus 6d. postage; special sizes, prices in proportion; Valve Holes 3in., others 2in. each (send sketch). **WOOD AND TOY**, 51, Whinfield Rd., Claines, Worcester.

1 M.A. f.s.d., m.c. Meters, £1; repairs; instruments, 3, Downsway, Southwick, Sussex.

**WANTED**, Trophy Battery 3 or similar, "Stansfield", Sudbury, Suffolk.

**RADIO SUPPLY CO. (LEEDS) LTD.**, 32, The Calls, Leeds 2. Ex-Gov. Transmitter Receivers type, TR9, complete with all valves, 47/6, plus 5/- carr. M/C Meters, 0-5 amps, 11/9; Selenium Rectifiers, F.W. Bridge types, 6 12v. 1a. 5/9; 6/12v. 2a. 9/9; 6/12v. 4a. 13/9; H.T. types, 250v. 50 ma., H.W., 5/9; 250v. 100 ma., H.W., 7/9; M.E. Speakers, all 2-3 ohms, 6in. Rola, 600 ohm field, 11/9; 10in. R.A. field, 600, 1,000, or 1,500 ohms, 23/9; ex-Govt. C.R.T.s, VCR517, 7/6; carr. 5/-; ex-Gov. 02mfd, 5,000v. 1/9; 02mfd, 8,000v. 1/11; unused Accumulators, 2v. 16 A.H., with non-spill vents, 5/9; top-shrouded main Trans. Primary, 220/240v. 50 c/s, secs. 250.0-250v. 70 m.a., 6.3v. 3a. 12/11. All goods guaranteed; c.w.o. or c.o.d. over £1; postage under £1 1/1, under £3, 1/9.

**BARGAIN PARCELS** of Radio Parts, 5/-, retail value more than £2. Stamp for particulars. List of surplus. **ELLETT**, Meppershall, Shefford, Beds.

**ELECTROLYTICS**, capacity, voltage, size, type of mounting; price post paid: 8, 450v. 1 x 2, clip, 2/-; 50, 12v. 3 x 1 1/2, tag, 1/6; 150, 25v. 4 x 1 1/2, clip, 2/-; 250, 12v. 4 x 1 1/2, wire, 2/3; 350, 25v. 1 x 2 1/2, clip, 2/6; 16 + 16, 450, 1 1/2 x 2, clip, 4/-; 40 + 40, 275v. 1 1/2 x 2, clip, 3/3; 24 + 24 + 16, 350/425v. 1 1/2 x 2, clip, 4/9; 60 + 200, 275/350v. 1 1/2 x 4, clip, 6/6; 4, 150v. 3/4 x 1 1/2, clip, 1/1; 500, 12v. 1 1/2 x 2 1/2, clip, 2/-; 8, 350v. 3/4 x 2, clip, 1/9; 100 + 175, 275/350v. 1 1/2 x 4, clip, 6/6; 32 + 32, 350/425v. 1 1/2 x 2, clip, 5/-; 8 + 16, 450/525v. 1 x 2, clip, 4/-; 2, 450/525v. 3/4 x 1 1/2, tag, 2/-; 350v. 3/4 x 1 1/2, tag, 1/3; 1,000, 6v. 1 x 2 1/2, clip, 2/9; 6,000, 6v. 1 1/2 x 3, clip, 4/9; 8, 450v. 1 x 2, clip, 1/9; all alicans, some with sleeves, all voltages wkg., surge where marked. new stock guaranteed. **RADIO CLEARANCE LIMITED**, 27, Tottenham Court Road, London, W.1. (Telephone: Museum, 9188.)

**GOVERNMENT SURPLUS**, 26-page List, Radio and Electrical Equipment; price 6d. **A. T. SALLIS**, 93, North Road, Brighton, Sussex.

**"LITTLE WONDER"** single-valve Loudspeaker Receiver! Send 1/- P.O. for "Easy-Build" diagrams and instructions. **JOHNSONS (RADIO)**, 46, Friar St., Worcester.

**WALNUT** Radiogram Cabinets of distinction; stamp details. **R. SHAW**, 63, Fairlop Rd., E.11.

**ALTHAM RADIO CO.** pay highest prices in the trade for all American equipment, including Test Sets, Transmitters, Receivers, etc. **JERSEY HOUSE**, Jersey Street, Manchester, 4. (Tel.: Central 7834-5-6.)

**GOLD SPRAYED**, expanded metal Speaker Fret, 12in. x 12in., 4/6; 12in. x 9in., 3/6; 8in. x 6in., 1/6. Special sizes up to 24in. x 24in. at 1d. per sq. inch. Add 1/- towards cost of postage and packing. Lightweight magnetic Pick-ups, complete (by Goldring), 30/-, including p. & p. **SHARP'S (RADIO)**, 252, Chapel St., Salford, 5.

**EDUCATIONAL**

**SEE THE WORLD** as a Radio Officer. Short training period; low fees; scholarships, etc., available. Boarding and day students. Send 2d. stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

**WORLD TRAVEL** and adventure in the Merchant Navy. Young Men 15 years upwards, required for training in Marine Wireless and Direction-finding at sea. (Trainees in fourth-year registration Groups are eligible for Deferment of Military call-up.) Immediate sea-going positions on completion of training. Suitable candidates will be entered as Officers and must be prepared to sail to all parts of the world. Courses: Full or Part-time, also by Correspondence. Recognised by Ministry of Education. Scholarships available. Boarding and modern canteen facilities; low training fees. Send 1/- P.O. (stating age and height, etc.) for complete prospectus to: **OVERSEAS HOUSE** (Dept. 14), Brooks Bar, Manchester, 16. (Tel.: MOSS-Side 2047.)

**WIRELESS**.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **B.S.T. LTD.**, 179, Clapham Rd., London, S.W.9.

**MERCHANT NAVY** and Air Radio.—Here is an opportunity to train as a Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses. Estd. 30 years; s.a.e. for prospectus from Director. **THE WIRELESS SCHOOL**, 21, Manor Gardens, London, N.7. (Tel.: ARC, 3694.)

**FREE!** Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast, or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the College operated by Britain's largest electronic organisation; moderate fees. Write to **E.M.I. INSTITUTES**, Postal Division, Dept. PW28, 43, Grove Park Road, London, W.4.

**THE INSTITUTE** of Practical Radio Engineers Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

**BOOKS**

**BOOKLETS:** "How to Use Ex-Gov. Lenses and Prisms." Nos. 1 and 2, price 2/6 each. Ex-Gov. Optical lists free for s.a.e. H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

**AMERICAN MAGAZINES**—One year Audio Engineering 28/6; specimen copy, 3/-; High Fidelity, 43/-; Popular Science, 28/6. Free booklet quoting others. WILEN, LTD. (Dept. 40), 101, Fleet Street, London, E.C.4.

**I.P.R.E. TECHNICAL PUBLICATIONS.** 5,500 Alignment Peaks for Super-heterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy The Practical Radio Engineer, quarterly publication of the Institute, 2/-; membership and examination data 1/-; Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

**SITUATIONS VACANT**

*The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.*

**MINISTRY OF SUPPLY** at Malvern urgently requires skilled Instrument Makers, Toolmakers, Universal Millers, Precision Fitters, Centre Lathe Turners, Sheet Metal Workers, Aircraft Engine Fitters, Airframe Fitters, Radar Electronic Instrument Fitters, to serve as Research and Experimental Mechanics (Special). Rate of pay for 44-hour, 5-day week, on entry as a Research and Experimental Mechanic (Special) is 139/4, plus merit pay of 26/-. There are prospects of advancement to higher rates of merit pay. Hostel accommodation available immediately and housing accommodation may be available within a reasonable period for successful married applicants. Apply, giving full particulars of apprenticeship, training (including Forces' training), qualifications and experience, to DIRECTOR, R.R.E., St. Andrew's Road, Malvern.

**A.M.I.MECH.E.**, A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook, free. B.I.E.T., (Dept. 242B), 29, Wright's Lane, London, W.8.

**AIRCRAFT** Radio Mechanics skilled in workshop practice or aircraft installations to work at Stansted Airport, Essex; hostel accommodation available; minimum hourly rates 3/9. Write to the PERSONNEL MANAGER, 7, Berkeley St., W.1.

**CITY AND GUILDS** (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. B.I.E.T., (Dept. 242A), 29, Wright's Lane, London, W.8.

**T/V AND RADIO.**—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc. on "no pass—no fee" terms. Over 95% successes. Details of exams, and home training courses in all branches of radio and T/V; write for 144-page handbook—free. B.I.E.T. (Dept. 242G), 29, Wright's Lane, London, W.8.

**CONDENSERS.**—100 mfd. 25 v., 1/9 each. Dubilier BR 850 8 mfd. 500 v., 2/6. TCC Micro pack 25 mfd. 25 v. CE32c, 1/9 each. Dubilier BR505, 50 mfd. 50 v., 2/- each. BEC 16 x 16 mfd. 450 v., 3/- each. B.I. .02 mfd. 1,000 v., 7d. each.

**WIRE WOUND VARIABLE RESISTORS.**—Colvern CLR902 1K., 1/9 each. Polar 500., 1/9 each. Colvern 5,200, 10K., 20K., 25K., 30K., 50K., 2/4 each. Colvern CLR801, 10K., 25K., 20, 1/3 each.

**MOULDED MICA CONDENSERS.**—All wire ends 0001, .0003, .0004, .0005, .01, .001, .005, .00027, .0008, .00005, .003, 4/6 doz.

**EX-GOVERNMENT VOL. CONTROLS.**—500, 600, Double 1,500, 10K., 20K., 25K., 50K., 100K., 150K., 200K., 1 meg., 1/2 meg., 1 meg., 2 meg., all 1/2 each.

**HALF WAVE 1 M/A. PENCIL RECTIFIERS.**—K3/25, 665 v., 5/8; K3/40, 1 Kv, 7/6; K3/45, 1,140 Kv., 8/2; K3/50, 1,260 Kv., 8/8; K3/60, 1.5 Kv., 9/8; K3/100, 2,550 Kv., 14/8.

**ENGRAVED KNOBS.**—1 1/2 in. dia. for 1 in. spindles, available Cream or Brown as follows: "Focus," "Contrast," "Brilliance," "Brightness," "Brilliance On/Off," "Wavechange," "On/Off," "Tuning," "Volume," "S.M.L. Gram.," "Bass," "Vol. On/Off," "Radiogram," "Tone," "Trebble," "Record-Play." Price 1/6 each. Plain knobs to match, 1/- each.

**TERMS:** Cash with order or C.O.D. Postage and packing charges extra, as follows. Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; 45 add 2/- unless otherwise stated. Minimum C.O.D. fee and postage, 2/3. Illus. Cat. available, send 6d. in stamps. MAIL ORDER ONLY.

**ALPHA RADIO SUPPLY CO.,** 5/6 Vinces Chambers, Victoria Square, LEEDS, 1.

**ASTRAL RADIO PRODUCTS**  
**READY NOW—Our New Publication "Home Radio,"** a 32-page booklet giving fullest details of constructing from a crystal set to 3-valve, fully illustrated and set out in the simplest form enabling the beginner to construct with ease. All components are available and list of suppliers is included. These 4 circuits were originally published in "Hobbies Weekly" and from correspondence received have been a great success. Price of booklet 2/-. Postage 2d. See page 184.

**COVENTRY RADIO**  
189, DUNSTABLE ROAD, LUTON  
Tel.: Luton 2677

**COMPONENT SPECIALISTS SINCE 1925**  
All B.V.A. and Tunstam valves in stock.  
**EDDYSTONE COMMUNICATION SETS AND COMPONENTS**

Short Wave Components Catalogue, Ed. T.C.C., Hunts & Dubilier Condensers. Welwyn and Erie Resistors. Lab/Morganite, Erie, Dubilier, Colvern and Ampion Potentiometers. Denco, Osrom, Wearite and Weymouth Coils and Packs. Eddystone, Denco, Wearite and Weymouth I.F.S. Woden and Elstone Transformers. Elac, Goodmans, Plessey, Rola, Celestion Speakers. Avo and Taylor Test Meters. E.M.I., Scotch Boy and Grundig Recording Tapes. Valradio Vibrator Converters.

**Special Offer.**  
Ready Punched 5-Valve Chassis. Size 12 1/2 x 8 1/2 complete with attractive glass lid 11 x 4 1/2. Reflector Plates, Pointer and Pulleys. Price 12/6 plus 1/- postage.

These are some of the components we stock. Send for our 50-page Component Catalogue, price 6d.

**REAL BARGAIN CLEARANCE,** all new goods, e.g., 4v LMS Wave S/het, £3/10/-, incl. valves, coil pack, etc.; A.F. Oscillator, sine/sq. atten. o/p, 20-200kc/s, only £4/10/-; IOW Quality Ampfr., high gain, perfect, £2; Tape Recorder Ampfr. Osc., offers over £7; numerous other smaller items. S.A.E. for list in confidence. "CLELAND," Ashtead, Surrey.

**TAPE RECORDING**

**HOME-MADE** Tape Recorder, complete with Radio, etc. (faulty), 500v power pack, mains distribution board; cheap. Box No. 243, C/O PRACTICAL WIRELESS.

**THE CHALLENGER,** a new compact Tape Deck, taking 600ft. reels, size only 1 1/2 in. x 7 in., best quality heads, price £8/18/- complete. Send stamp for details to: E. W. A., 266, Warbreck Drive, Blackpool.

**VALVES**

**6V6G AND GT,** matched in pairs, new, boxed, 17/- per pair; p. and p. 1/-; R. J. COOPER, 32, South End, Croydon, Surrey.

**NEW VALVES WANTED,** small or large quantities, 3Q4, 6V6, 5Z4, ECL80, EF80, EY51, PL81, PY82, KT61, 6L6G, VR150 30, 5K4, 80, etc. Prompt cash. WM. CARVIS, 103, North Street, Leeds, 7.

**RADIO UNLIMITED** offer new boxed Valves: 1T4, 1S4, 1S5, 1R5, 3S4, 3V4, 6F6, 6V6, 6X5, 6Y5, 6SK7, 12SK7, 6SQ7, EF91, EB91, 6J6, all at 7/6 each; 5Z4, 5U4, 5Y3, U14, 12K7, 12K8, 12Q7, 35L6, 25L6, 35Z4, 25Z5, 25Z5, 6AT6, 8/6 each; 1L4, 3A4, 1P2, 12J5, SP41, SP61, EP36, 9D2, AR8, 6K7, ARP12, ARP4, 6H6, D63, all at 4/6 each; 6K8, 6Q7, 6L6, KT66, 25A6, KT61, 9/6 each. Stamp full list. RADIO UNLIMITED, Elm Road, London, E.17. (KEY 4813.)

**VALVES,** over 3,000 in stock: 2D21, EC91, 12AU7, 6BR7, 6CH6, 6VW6, 6SN7, 9/-; EL91, 6P33, 12AT7, EY94, 7/-; EF91, 6J6, 12AX7, 6/6; 6AL5, 6C4, EAC91, EF92, 5/6. SKILLMAN, Franchise St., Weymouth.

**"VIEWMASTER" VALVES,** exact to specification, guaranteed, new and boxed, set of 12, £6 2/6; post free: 6AM6, EF91, 6F12, 277, 8D3, W77, EF92, 6C4, L77, 6AM5, EL91, 12AX7, 7/9; any 8 for 56/-; EB91, 6AL5, 6X5GT, EF39, HVR2A, 6/9; 1.4v miniatures, 1S5, 1R5, 1T4, 3V4, 3S4, 1S4, DK92, DF92, DL93, 7/6; any 4 for 27/6; 6V6G, 6V6GT, 6F6G, KT63, U22, EBC33, EF50, 20D1, 7B7, 7C5, 7C6, 7H7, 7S7, 7/6; 524G, 5U4G, 5Y3GT, U50, MU14, 7Y4, 12AT7, 12AU7, ECC81, 1CSGT, DL35, U78, 6A7, DH77, 6AT6, 6J6, 6A8G, 25Z5, 25Z6GT, 25L6GT, 35L6GT, 50L6GT., 35Z4GT, 80, 6X4, 6BA6, 6BE6, 6BW6, EC91, Pen 46, FV82, 6LD20, 807, 8/6; PL38, EL38, 22/6; PZ50, GZ32, 6U4GT, U08, 17/-; DK32, 1A7GT, E42, 6P25, EL33, N78, 15/-; U25, EBF80, U6F60, UF42, UAF42, U37, R16, UCH21, UBL21, ECH35, 13/6; EY51, U16, PL83, N39, 1H5GT, DAC32, 1N5GT, DF39, 3Q5GT, DL33, CY31, ECC91, 12/-; X65, PL81, PL82, PY81, 11/-; ECL80, EF80, 6F1, 10C2, 6F15, 6C9, 10P1, 10P3, UCH42, EAF42, R10, 10/6; EF80, EL41, ECH42, EBC41, UBC41, UF41, 10LD11, 10P9, U309, U319, KT39C, 10/-; 25Z4G, 25A6G, 6K6G, 6K8GT, 6Q7GT, 12K8GT, 12J7GT, 12K7GT, 12Q7GT, 6SN7GT, UY41, U14, UY41, EP41, EZ40, EAC91, U09, U040, 9/-; 6K67, 6K7GT, EP8, 3A4, KF35, KL25, 6/-; all new and boxed; postage 4d. per valve extra. READERS RADIO, 24, Colberg Place, Stamford Hill, London, N.16. (STA. 4587.)

# ALFRED PADGETT

40, MEADOW LANE  
LEEDS, II

Est. 20 Years

## COLLARO GRAM. MOTORS

Variable speed, centre drive. Not to be confused with rim drive. Complete with Turntable, 37/6.

## CO-AX. CABLE

1/2 in. Not ex-W.D. 80 ohm, 6d. per yd., 20 yds. 8/6.

## 12-24 VOLT D.C. MOTOR

Size: 2 1/2 in. x 2 in. x 1 1/2 in. With spindle, 3/8 in. x 3/8 in. dia. Just the Motor for Model Makers or Model Railways, 12/6.

## VALVE SCREENING CANS\*

Complete with Base and Cover, 6d. each.

## INTER-VALVE TRANSFORMERS

3.5-1 Ratio. 6d. each.

## MINE DETECTOR

Amps. with HR Phones and 3 ARPI2 valves. New, 25/-

Amateur Radio Enthusiasts  
THE INCOMPARABLE

## GLOBE-KING

SINGLE VALVE S.W. RECEIVER  
● WORLD-WIDE RANGE 11-100 METRES ● CRYSTAL-CLEAR NOISE-FREE RECEPTION ● ELECTRICAL BAND-SPREAD TUNING ● EXTREMELY LOW RUNNING COSTS  
Catalogue Free Stamp for postage.

JOHNSONS (RADIO)

46, FRIAR STREET, WORCESTER

# LOOK!

- NO AERIAL ● NO EARTH
- FITS IN THE POCKET ● SELF-CONTAINED BATTERIES

These are features of the "TWIN" ONE-VALVE POCKET SET

which you can build using our clear drawings and instructions. The receiver is designed around the famous "twin" valve now available as a British all-dry midget type. The aerial and batteries are self-contained, and the receiver is small enough to fit in the jacket pocket. The set can be used indoors or out, giving powerful headphone reception of many stations on the medium waveband. It can also be adapted for long waves. Fully illustrated instructions and point-to-point wiring diagram.

Price **3/6** Post Free

This offer applies only to Gt. Britain, Irish Republic, and Northern Ireland.

## SWIFT RADIO,

102, BATH ROAD, WILLSBRIDGE, NR. BRISTOL

# FIRST-CLASS RADIO COURSES . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

## FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-promoting qualifications as A.M.Bric.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**  
Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES—

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 461), 148, HOLBORN, LONDON, E.C.1


# TAPE-DISC

SERVICE

Have your favourite tape-recording made into a gramophone record. 1 1/2 d. stamp for free literature to . . .

H. R. McDermott, 10, Duke Street, Darlington, Co. Durham

## Fidelia

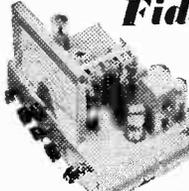

HAND BUILT RADIO UNITS

THE FIDELIA MAJOR 10

Hand built high quality radiogram chassis at economic price. 10 valve, model 1 illustrated, £32-8-4. De-luxe 8 valve model £24-6-6. 7 valve £21-12-0. 5 valve £23-18-4.

Technical data sheets free.  
Electro Acoustic Developments, 2, Amburst Road, Telcombe Cliffs, Sussex.

# MORSE CODE Training

Send for the Candler BOOK OF FACTS

It gives details of all Courses which include a Special one for securing Amateur Licence. CANDLER SYSTEM CO. Dept. 510 52b, Abingdon Road, London, W.9. Candler System Co., Denver, Colorado, U.S.A.

# EVERYTHING FOR VIEWMASTER & SOUNDMASTER

ELECTROLYTICS.—450v. wkg. (Gtd. New Stock), 4 mid. 1/6. 8 mid. 2/-. 16 mid. 3/-. 8-8 mid. 3/6. 8-16 mid. 4/-. 16-16 mid. 4/6. P.M. LOUD-SPEAKERS (3-ohms), 3in. 13/6. 5in. 14/6. 6in. 15/6. 8in. 18/6. 10in. 22/6. GERMANIUM CRYSTAL DIODES 3/6. B.I.C., 0.1 mid. 3 kv. TV Condensers, 10/6. H.R. HEADPHONES, 18/6. SOLON Miniature SOLDERING IRONS, 19/6. 6in. SOLDERERS (for VCR7), 17/6. 10 h. 50 mA. SMOOTHING CHOKES, 5/6. 9in. Old Aspect CREAM RUBBER MASKS, 5/6. WEARIFE COILS, 3/-, ALL CHASSIS, 2 1/2 in. deep, 6in. x 4in. 4/6. 8in. x 6in. 6/-. 10in. x 7in. 7/-. 12in. x 8in. 9/-. 14in. x 8in. 13/-. 16in. x 9in. 14/-. ELAC FOCUS RINGS, R17/Mk. II 28/6. R20/Mk. II 30/-. R25/Mk. II 32/6. TRANSFORMERS (Mains Input, Standard Primaries), 250-0-250v. 50 mA. 0-4.6-3v. 4 A. 0-1-5v. 2 A. 19/6; Ditto but 350-0-350v., 19/6; 250-0-250v. 100 mA. 6.3v. 3.5 A. 5v. 2 A. 26/6; Ditto but 350-0-350v. 26/6. MAINS TRANSFORMERS for PRE-AMPLIFIERS, TEST-GEAR, etc. PRIMARY, 230-240v. SECONDARIES, 0-250v. 30 mA. (for 250v. from a half-wave rectifier) and 6.3v. 1 A. Price new and guaranteed, 14/9.

ORDERS UNDER £1 please add 1/- P. & P. Orders £1 and over please add 1/9.

FOR INSTANT SERVICE—WRITE

**CITY & RURAL RADIO**  
101, HIGH ST., SWANSEA, GLAM.  
Telephone: Swansea 4677.

## Quizz Radio Quiz Test

Accurately tests High, Low and Grid Bias Batteries. Write for leaflet 29 M.



**RUNBAKEN MANCHESTER!**

## BENTLEY ACOUSTIC Corp., Ltd.,

38, Chalcut Road, N.W.1. PRImrose 9090.

OZ4	5/6	6SHT	4/6	80	8/-
1A5	5/-	6S7J	7/6	85A2	10/6
1G9	6/-	6SK7	6/6	210LF	2/-
1L4	6/-	6SL7	7/6	807	7/6
1LD5	4/-	6SN7	8/6	5763	8/6
1LN5	4/-	6V6	7/-	EB91	5/6
1T4	6/6	6X5	7/-	EF39	10/6
2A3	6/6	7B7	7/-	EF91	6/-
2X2	4/6	7C5	7/-	EF91	7/6
3D6	2/-	7C6	7/-	EL91	7/6
5U4G	7/6	7C7	8/-	FP33	10/-
5Y3	7/6	7H7	8/-	EC33	8/-
5Z4	8/-	7Q7	8/-	EM34	10/-
6A9	8/-	7R7	8/-	HL2	2/-
6B8M	5/6	7S7	7/-	MVSPen	6/6
6CD6	11/-	7Y4	8/-	MH4	5/-
6CH6	6/6	12AT7	7/-	MU12	8/-
6C6	6/6	12AU7	10/-	6X4	7/-
6J7G	6/6	12AX7	7/-	VR53	5/-
6D6	5/6	12BE6	7/-	VR55	7/-
6H6G	2/-	12C8	7/-	VR57	7/-
6HM6	3/-	12L5	5/6	GUSY63	5/6
6L5G	5/-	12K7	8/-	UAF12	13/-
6K8	6/6	12K9	8/-	UBL21	13/-
6R7G	5/-	12Q7	8/-	UCH21	13/-
6R7G	5/-	12SK7	6/-	UCH42	10/-
6K8	8/-	12SQ7	8/-	6AM6	5/6
6L5G	8/6	25L6	8/-	6BA6	7/-
6SA7	8/6	35L6	7/6	6BE6	7/-
6SA7	7/6	50L6	8/-	6BW6	7/-
6SG7	7/6	75	8/-	9D2	2/9

**SPECIAL OFFER.** New Philips Superhet Coils. 4 Wave Band. Aerial and Oscillator in Two All Cans. Complete with Circuit. 7/6 pr. Post Extra. Min. C.O.D. Charge 2/3. Refund Guarantee. S.A.E. Free List.

Practical Wireless

**BLUEPRINT SERVICE**

**PRACTICAL WIRELESS**

*No. of  
Blueprint*

**CRYSTAL SETS**

- 1/6d. each
- 1937 Crystal Receiver ... PW71\*
- The "Junior" Crystal Set ... PW94\*
- 2s. each
- Dual - Wave "Crystal Diode" ... PW95\*

**STRAIGHT SETS**

Battery Operated

- One-valve : 2s. each.
- The "Pyramid" One-valver (HF Pen) ... PW93\*
- The Modern One-valver ... PW96\*
- Two-valve : 2s. each.
- The Signet Two (D & LF) ... PW76\*
- 3s. each.
- Modern Two-valver (two band receiver) ... PW98\*
- Three-valve : 2s. each.
- Summit Three (HF Pen, D, Pen) ... PW37\*
- The "Rapid" Straight 3 (D, 2 LF (RC & Trans)) ... PW82\*
- F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ... PW87\*
- 3s. each.
- The All-dry Three ... PW97\*

- Four-valve : 2s. each.
- Fury Four Super (SG, SG, D, Pen) ... PW34C\*

Mains Operated

- Two-valve : 2s. each.
- Selectone A.C. Radiogram Two (D, Pow) ... PW19\*
- Three-valve : 3s. 6d. each.
- A.C. Band-Pass 3 ... PW99\*
- Four-valve : 2s. each.
- A.C. Fury Four (SG, SG, D, Pen) ... PW20\*
- A.C. Hall-Mark (HF Pen, D, Push Pull) ... PW45\*

**SUPERHETS**

- Battery Sets : 2s. each.
- F. J. Camm's 2-valve Superhet ... PW52\*
- Mains Operated : 3s. 6d. each.
- "Coronet" A.C.4 ... PW100\*
- AC/DC "Coronet" Four ... PW101\*

*No. of  
Blueprint*

**SHORT-WAVE SETS**

Battery Operated

- One-valve : 2s. each.
- Simple S.W. One-valver ... PW88\*
- Two-valve : 2s. each.
- Midget Short-wave Two (D, Pen) ... PW38A\*
- Three-valve : 2s. each.
- Experimenter's Short-wave Three (SG, D, Pow) ... PW30A\*
- The Perfect 3 (D, 2 LF (RC and Trans)) ... PW63\*
- The Band-spread S.W. Three (HF Pen, D (Pen), Pen) ... PW68\*

**PORTABLES**

- 1s. 6d.
- The "Mini-Four" All-dry (4 valve superhet). \*

**MISCELLANEOUS**

- 2s. each.
- S.W. Converter-Adapter (1 valve) ... PW48A\*
- (2 sheets), 7s. 6d.
- The P.W. 3-speed Autogram. \*
- The P.W. Electronic Organ (2 sheets), 7s. 6d. \*

**TELEVISION**

- The Practical Television Receiver, (3 sheets), 10/6
- The "Argus" (6in. C.R. Tube), \* 2/6
- The "Super-Visor" (3 Sheets) 7/6\*

**AMATEUR WIRELESS AND WIRELESS MAGAZINE**

**STRAIGHT SETS**

Battery Operated

- One-valve : 2s.
- B.B.C. Special One-valver ... AW387\*

Mains Operated

- Two-valve : 2s. each.
- Consoelectric Two (D, Pen), A.C. ... AW403

**SPECIAL NOTE**

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W.M. to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of  
Blueprint*

**SHORT-WAVE SETS**

Battery Operated

- One-valve : 2s. each.
- S.W. One-valver for American ... AW429\*
- Two-valve : 2s. each.
- Ultra-short Battery Two (SG, det Pen) ... WM402\*
- Four-valve : 3s. each.
- A.W. Short Wave World-beater (HF Pen, D, RC Trans) ... AW436\*
- Standard Four - valver Short-waver (SG, D, LF, P) ... WM383\*

Mains Operated

- Four-valve : 3s.
- Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ... WM391\*

**MISCELLANEOUS**

- Enthusiast's Power Amplifier (10 Watts) (3/-) WM387\*
- Listener's 5-watt A.C. Amplifier (3/-) ... WM392\*
- De Luxe Concert A.C. Electrogram (2/-) ... WM403\*


**QUERY COUPON**

This coupon is available until Mar. 4th, 1954, and must accompany all Queries, sent in accord with the notice on page 185. PRACTICAL WIRELESS, .. Mar 1954

**CABINET** as illustrated, 11 1/2 x 6 1/2 x 5 1/2 in. Walnut or cream, complete with T.R.F. chassis, 2 wave-band scale, station names, new waveband, backplate, drum, pointer, spring, drive spindle, 3 knobs and back. 22/6. P. & P. 3/6.

As above with Superhet Chassis, 23/6. P. & P. 3/6.

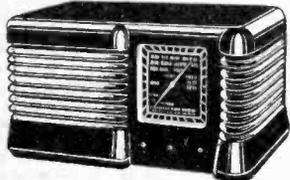As above complete with new speaker to fit and O.P. trans. 35/- P. & P. 3/6 with Superhet Chassis, 36/- P. & P. 3/6.



Used metal rectifier, 230 v. 50mA. 4/6; gang with trimmers, 6/6; M. & L. T.R.F. coils, 5/-; 3 obsolete Ex Govt. valves, 3 v/h and circuit, 6/6; heater trans., 6/-; volume control with switch, 3/6; wave-change switch, 2/6; 4 v. h. f. id. 4/6; bias condenser, 1/-; resistor kit, 2/-; condenser kit, 4/-.


**M. & L. Superhet Coils** with circuit, 6/6; iron cored 465 IP's, 7/6; min. gang, 5/6; volume control with switch, 4/-; wave-change switch, 2/6; heater trans., 7/6; 4 v/h, 1/6; 4 obsolete Ex Govt. valves, metal rectifier and Xtal diode with circuit, 14/6; 25 x 25 mfd., 1/-; 16 x 16 mfd., 3/3; condenser kit (17), 7/6; resistor kit (14), 3/6.

Used 4 valve plus metal rec. A.C. mains, 230 250 superhet. Valve line up 6K8, 6K7, 6Q7 and 6R6. Medium wave in mahogany cabinet, size 22 x 14 x 10 1/2 in. These have been checked and are in first-class working order, and have a first-class performance, 6 1/2 in. P.M. speaker, P. & P. 5/- £3 19/6.

Used 5 valve A.C. mains 200/250 3-waveband superhet. Complete in outstanding walnut cabinet, size 22 x 14 x 10 1/2 in. Valve line up, 6K8, 6K7, 6R8Q, 6R6 and U60 rec., 8 1/2 in. P.M. speaker. In first-class working order, £7 19/6. P. & P. 12/6. We have a few of these in A.C./D.C., price as above.

**All dry A.C. mains battery unit**, 200 250 v. Metal case size 8 x 5 x 3 1/2 in. by famous manufacturer. Incorporating Westinghouse metal rectifiers, 3 500 mfd., 16 2 1/2 mfd., mains trans., 3 smoothing chokes, output 90 v. 10 mA., 1.4 v., .25 amp. P. & P. 2/6, 39/6.

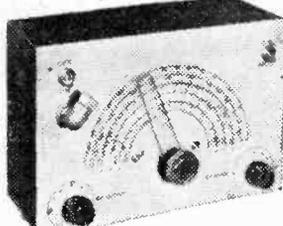**COMPLETELY BUILT SIGNAL GENERATOR**, Coverage 110 Kc/s-320 Kc/s., 200 Kc/s-900 Kc/s., 900 Kc/s-2.75 Mc/s., 2.75 Mc/s-9.5 Mc/s., 9.5 Mc/s-25 Mc/s., 17 Mc/s-50 Mc/s., 25.5 Mc/s-75 Mc/s. Metal



case 10 x 6 1/2 x 4 1/2 in., size of scale 6 1/2 x 3 1/2 in., 2 valves and rectifier, A.C. mains 230 250 v. Internal modulation, 400 c.p.s. to a depth of 30%. Frequency calibration accuracy plus or minus 1%. Modulated or unmodulated R.F. output continuously variable 100 milli-volts. Post and packing 4/-, £4 5/0. 34/- deposit, three monthly payments of £1.

Terms of business: Cash with order. Dispatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 1/- up to 10/-, 1/6 up to £1. and 2/- up to £2. All enquiries and list, stamped addressed envelope.

**High impedance plastic recording tape** by famous manufacturer. 1,200 feet complete on spool, 17/6. P. & P. 1/6. 600 feet 8/- P. & P. 1/6.

**Amplifier Case**, black reline covered, leather carrying handle, chrome plated corners, rubber feet, felt lined, detachable lid. External dimensions 13 1/2 x 13 1/2 x 9 1/2 in. 21/- P. & P. 2/6.

**Pr. 200 250 v.**, secondary 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volt at 2 amps., 13/-.

**Drop thro'** 230-0-230, 200 mA., 6 v. 5 amps., 5 v. 3 amps., 27/6.

**Heater Transformer**, Pri. 230-250 v. 6 v. 11 amp., 6/-; 2 v. 2 1/2 amp., 5/-; 2.4 or 6 v. at 2 amps., 7/6; 2 v. 2 1/2 amp. and 6 v. 0.6 amp. E.H.T. insulated, 8/6. P. & P. each 1/-.

**R.I. MAINS TRANSFORMERS**, chassis mounting, feet and voltage panel. Primaries 200 250.

300-0-300 60 mA. 6.3 v. 1 a., tapped at 4 v. 6.3 v. 2 a. tap 4 v., 13/6.

350-0-350 75 mA. 6.3 v. 3 a. tap 4 v. 6.3 v. 1 a., 13/6.

350-0-350 70 mA. 4 v. 5 a. 4 v. 2.5 a. C.T. 2/- P. & P. on the above transformers 2/-.

500-0-500 125 mA. 6.3 v. C.T. 4 a. 6.3 v. C.T. 2 a. 5 v. C.T. 2 a., 27/6.

500-0-500 120 mA. 4 v. C.T. 4 a. 4 v. C.T. 4 a., 27/6.

500-0-500 250 mA. 4 v. C.T. 5 a. 4 v. C.T. 5 a., 4 v. C.T. 4 a., 39/6.

P. & P. on the above transformers 3/-.

32 mfd., 350 wkg. .... 2/-

16 x 21 350 wkg. .... 4/-

40 mfd., 200 wkg. .... 1/3

40 mfd., 450 wkg. .... 3/6

16 x 8 mfd., 500 wkg. .... 4/6

16 x 16 mfd., 500 wkg. .... 5/9

8 x 15 mfd., 450 wkg. .... 3/9

32 x 32 mfd., 350 wkg. .... 4/-

32 x 32 mfd., 350 wkg. and 25 mfd., 25 wkg. .... 6/6

25 mfd., 25 wkg. .... 11/-

250 mfd., 12 v. wkg. .... 1/-

16 mfd., 300 wkg. wire ends .... 3/3

32 mfd., 200 wkg. wire ends .... 1/6

8 mfd., 350 v. wkg. tag ends .... 1/6

50 mfd., 25 v. wkg. wire ends .... 1/9

100 mfd., 350 wkg. .... 4/-

100 + 200 mfd., 350 wkg. .... 9/6

16 x 16 mfd., 350 wkg. .... 3/3

Ex Govt. mfd. 800 v. wkg. size 3 1/2 x 1 1/2 or .... 2/6

60 + 100 mfd., 280 v. wkg. .... 7/-

16 + 32 mfd., 350 wkg. .... 6/-

50 mfd., 180 wkg. .... 1/6

60 mfd., 220 wkg. .... 2/6

8 mfd., 150 wkg. .... 1/6

100 mfd., 280 wkg. .... 8/6

50 mfd., 12 wkg. .... 11/-

32 + 32 mfd., min., 275 wkg. .... 4/-

50 mfd., 50 wkg. 8 mfd., wkg. wire .... 1/9

Miniature wire ends moulded 100 pf., 500 pf., and .001 ea. .... 7d.

Partridge fully shrouded mains transformer, input 200 250 secondary 350-0-350 175 mA. 6.3 v. 7 amp., 5 v. 3 amp., p/p 3/3-35.

Partridge fully shrouded pushpull transformer, PRI 6,000 ohms, SEC 15 ohms, p/p 2/-, 20/-.

Partridge fully shrouded choke, 15 Hen. 180 mA., p/p 2/-, 15/-.

Partridge fully shrouded choke, 5 Hen. 120 mA., p/p 2/-, 8/6.


**CONSTRUCTORS' PARCEL**, comprising chassis 12 1/2 x 8 x 2 in. cad. plated 18 gauge, v.h. 1F and trans. cut-outs, backplate, 2 supporting brackets, 3 waveband scale, seven length station names. Size of scale 11 1/2 x 4 1/2 in. drive spindle, drum, 2 pulleys, pointer, 2 bulb holders, 5 paxolin international octal valve holders, 4 knobs, and pair of 465 IF's, 16/6. P. & P. 1/9.

**AS ABOVE**, but complete with 16 + 16 mfd. 350 wkg. and semi-shrouded drop thro' 250-0-250 60 mA., 6 v. 3 amp. Pri. 200-250, and twin-gang 31/6. P. & P. 3/-.

**5in. M.F. field coil** 750 ohms with O.P. trans., 17/6. P. & P. 1/-.


**Germanium crystal diode**, 2/3, post paid.

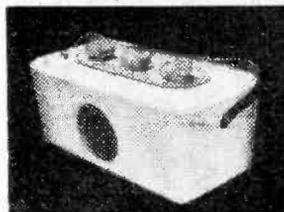**BATTERY CHARGER KIT**, comprising metal case 5 x 4 1/2 x 4 1/2 in. trans. 230 250 v. and metal rec. Will charge 6 or 12 v. battery at 1 amp., 19/6. P. & P. 2/6.



**PERSONAL PORTABLE CABINET** in cream-coloured plastic, size 7 x 4 1/2 x 3 in. Complete 4-valve chassis. Scale and 3 knobs. Takes miniature 90 v. and 7 1/2 v. batteries, 9/- P. & P. 1/6.

**3in. P.M. SPEAKER** to fit above, 10/- Miniature output transformer, 5/- Miniature wave-change switch, 1/6. Miniature 1-pole 4-way selector, Volume and ON, 1/6. 4 BTG valveholders, 2/4. Midget twin gang 1in. dia., 1in. long and pair medium and long-wave T.R.F. coils 1in. long x 1in. wide: complete with 4-valve all-dry mains and battery circuit, 8/6. Condenser Kit, comprising 11 miniature condensers, 3/6. Resistor kit, comprising 15 miniature resistors, 4/6. The above receiver (less valves and batteries) could be built for approximately 51/- P. & P. 2/6. Valves to suit above 10/- ea. Point to Point Wiring Diagram 1/-.

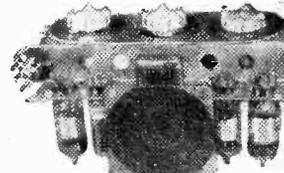

View of chassis as it would look when assembled with valves inserted.

**Extension speaker cabinet**, in contrasting walnut veneers, size 15 x 10 1/2 in. Will take 8 or 6in. speaker, 17/6. P. & P. 2/-.

**Volume Controls**, Long spindle less switch, 50K, 500K, 1 meg., 2/6 each. P. & P. 3d. each.

**Volume Controls**, Long spindle and switch, 1, 1 1/2 and 2 meg., 4/- each; 10 K, and 50 K, 3/6 each. 1 and 1 meg., long spindle, double pole, switch, miniature 5/- P. & P. 3d. each.

**Standard Wave-change Switches**, 4-pole 3-way, 1/9; 5-pole 3-way, 1/8. Miniature 3-pole 4-way, 4-pole 3-way, 2/6.

**Valveholders**, Paxolin octal, 4d. Moulded B7C, 7d. Moulded B7C, 7d. Octal amphenol, 7d. Octal pax., 4d. Mazda Amphenol, 7d. Mazda pax., 4d. B7A, B7A amphenol, 7d. BTG with screening can, 1/6. Duodecal paxolin, 9d.

**Trimmers**, 5-40 pf., 5d.; 10-110, 10-250, 10-450 pf., 10d.

**Twin-gang .0005 Tuning Condensers**, 5/- With trimmers, 7/6.

**Midget .00037 dust cover and trimmers**, 8/6.

**P.M. SPEAKERS**

	with less trans.	trans
3in. ....	13/6	19/6
5in. ....	16/6	12/6
6in. ....	16/6	12/6
8in. ....	18/6	15/-
10in. ....	18/6	19/6

Post and packing on each of the above, 1/6 extra.

**Truvox BX11** 12 in. P.M. 3 ohm speech coil 45/- P. & P. 3/6.

**Crystal pick-up with Sapphire Trailer Needle**, with volume control, 23/- P. and P. 1/-.

**D. COHEN, 23, HIGH STREET, ACTON, W.3.** (Opposite Granada Cinema)

Hours of Business: Saturdays 9-6 p.m. Wednesdays 9-1 p.m. Other days 9-4.30 p.m.