

● A FRONT DOOR INTER-COM SYSTEM ●

# PRACTICAL <sup>1/3</sup>

DECEMBER  
1956

EDITOR: F.J. CAMM

# WIRELESS





## PRINTED CIRCUIT F.M. TUNER

The circuit is based on the 912 Tuner and may be used to feed any amplifier

The T.C.C. Printed Circuit F.M. Tuner is now offered to the home constructor and enables an outstanding performance to be obtained, both in sensitivity and quality. The F.M. Tuner has already achieved a well deserved reputation for its extremely high sensitivity, and its excellent performance. By using a printed circuit these features are assured, the I.F. and R.F. amplifiers being extremely stable at maximum gain and results being consistent on all tuners.

The printed circuit is produced on a high-grade laminate board on which are also printed

the aerial coil and the R.F. coupling coil. These coils do not require tuning and further simplify the assembly and alignment. The sensitivity of the average F.M. Tuner is of the order of  $10\mu\text{V}$ . for an output of 2v. at the ratio discriminator.

All components are mounted on the top of the printed panel with the exception of the oscillator coil and its associated condensers which are mounted beneath the panel. This has been done to maintain a high order of stability for the oscillator and thereby prevent drift.

The power supply for the tuner is intended to be on a separate chassis and is connected to the tuner by means of flexible leads. For all technical details of the F.M. Tuner, reference should be made to the 912 F.M. booklet.

Printed Circuit and complete set of Condensers **£4.4.7**

### THE TELEGRAPH CONDENSER CO. LTD

SPECIAL PRODUCTS DIVISION : NORTH ACTON · LONDON · W.3 · Telephone : ACOrn 0061


## HIGH FIDELITY AT REALISTIC COST!

See and hear these and all other W.B. lines at our London Office (109 Kingsway, W.C.2) any Saturday between 9 a.m. and 12 noon.



Ready to assemble Cabinets from £5. 10. 0

TV and Record Storage Cabinets £9. 14. 3 & £10. 4. 9

H.F. 1012. 10" Hi-Fi Unit  
£4. 19. 9

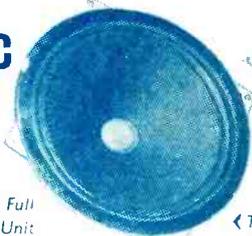

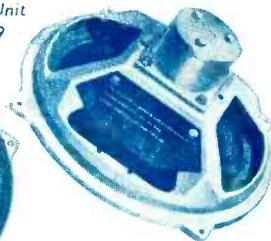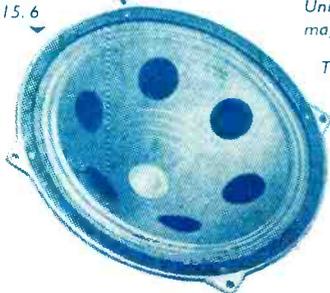H.F. 1214. Full Range 12" Unit  
14,000 gauss  
£9. 15. 6




T.816. Special 8" Mid-Range and High Frequency Unit. 16,000 gauss magnet. £6. 10. 0



Tweeter Units  
£4. 4. 0 & £12. 12. 0

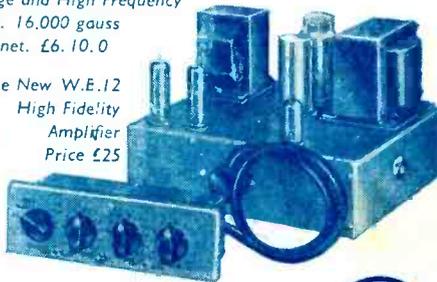
The New W.E.12 High Fidelity Amplifier  
Price £25



Details of all the outstanding W.B. products on request

WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS



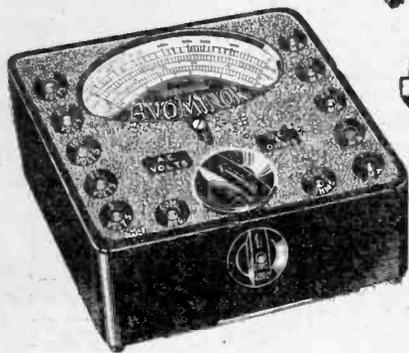

**MODEL 1**

**D.C. VOLTAGE :** 0 to 500 volts.  
**A.C. VOLTAGE :** 0 to 500 volts.  
**D.C. CURRENT :** 0 to 500 mA.  
**RESISTANCE :** 0 to 20,000  $\Omega$ .  
 Total resistance of meter: 200,000  $\Omega$ .  
**SENSITIVITY :** 400  $\Omega$ /V.

**MODEL 2**

**D.C. VOLTAGE :** 0 to 1,000 volts.  
**A.C. VOLTAGE :** 0 to 1,000 volts.  
**D.C. CURRENT :** 0 to 500 mA.  
**RESISTANCE :** 0 to 200,000  $\Omega$ .  
 Total resistance of meter: 4 M $\Omega$ .  
**SENSITIVITY :** 4,000  $\Omega$ /V.

Write for a free copy of the latest Comprehensive Guide to "Avo" Instruments.

# 'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark.

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set.

## The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance; 22 ranges of readings on a 3-inch scale.

Size: 4 1/4 ins. x 3 1/2 ins. x 1 1/2 ins.  
 Nett weight: 18 ozs.

List Price: £12 : 0 : 0

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

## The D.C. AVOMINOR

is a 2 1/2-inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4 1/4 ins. x 3 1/2 ins. x 1 1/2 ins.  
 Nett weight: 12 ozs.

Complete as above  
 List Price: £5 : 5 : 0

Sole Proprietors and Manufacturers:—  
**AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.**  
 Avocet House, 92/96, Vauxhall Bridge Rd., London, S.W.1. VICTORIA 3494 (9 lines)

# BEGINNERS!— BUILD AN "EASY-TO-MAKE" RADIO



107/6

Total building cost including choice of beautiful walnut veneered cabinet or ivory or brown bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple easy-to-follow diagrams. This terrific new circuit covers all medium and long waves with optional negative feedback, has razor-edge selectivity, and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple easy-to-follow plans—in fact, everything! All parts sparkling brand new—no junk! Every single part tested before despatching. Uses standard octal-base valves: 6K7G high-frequency pentode feeding into 6J5G anode-bend detector triode, coupled to 6V6C powerful output beam-power tetraode, fed by robust rectifier. For A.C. Mains, 200-250 Volts (low running costs—approximately 18 Watts!). Size 12in. x 6in. x 5in. Build this long range powerful midget NOW! All parts and set of plans, £5.7.6. (Post and packing 3/6.) Priced Parts List, 2/-.

LOOK!



BUILD THIS POCKET RADIO FOR ONLY 37/6

AT LAST! In response to many requests we now present the **DOUBLE TRIODE "SKYPOCKET"**, a beautifully designed precision **POCKET RADIO**. No radio knowledge needed!—**EVERY SINGLE PART TESTED BEFORE DESPATCH**; our simple, pictorial plans take you step-by-step. This set has a remarkable sensitivity due to painstaking design. Covers all medium waves 200 to 550 Metres. Size only 5 1/2 in. x 3 in. x 2 in. In Strong, Transparent case with panel, cover and ivoryine dial. A really personal-phone, pocket-radio WITH **DETACHABLE ROD AERIAL**. Self-contained all-dry battery operation. Average building time 1 hour. Total Building Cost—including Case, Double Triode Valves, etc., in fact, everything down to the last nut and bolt—**ONLY 37/6**, with plans. Postage, etc. 2/- C.O.D. 1/6 extra. (Parts sold separately. Priced Parts List, etc. 1/6.) Demand is certain to be heavy—so **SEND TODAY!**



47/6

Build this exceptionally sensitive **WIND-TRIODE** radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 3 in. Covers all Medium and Long waves—uses one only all-dry battery. H.T. consumption only 1 to 1.5 mA. Ideal for Bedroom, Garden, Holidays, etc. Many unsolicited testimonials, Mr. Norton, of Oxford, writes: Yesterday evening on the Medium waveband, I counted 32 separate stations; I am very pleased with the set, which is well worth the money. Total building cost—Everything down to last nut and bolt—47/6 (Postage, etc. 2/-) with full set of clear, easy-to-follow plans (For Headphone Reception). Cost of Extra Valve, Speaker, Parts, etc. 38/6. All these fit inside Case or parts sold separately. (Priced Parts Lists, 2/-)

**CONCORD ELECTRONICS (Dept. PWD), 69, PRESTON STREET, BRIGHTON, 1**

Orders despatched by return of post. Cheques accepted. Cash on delivery 1/6 extra. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Callers welcome. Shop hours: 9 a.m. to 8 p.m. 1 p.m. Thursdays.

**THE SKYSEARCHER**

An all mains set for 19/6



This is a 2-valve plus-metal rectifier set useful as an educational set for learners, also makes a fine second set for the bedroom, workshop, etc. All parts, less cabinet, chassis and speaker, 19/6. Post & ins. 2/6. Data free with parts or available separately 1/6.

**MINIATURE MOTOR**



Size only 2 1/2 ins. long by 1 1/2 ins. diameter—American made—laminated poles and a motor—intended for 28 volt. D.C. but O.K. on lower D.C. voltages and A.C. mains, through step-down transformer—price 10/6. Post, etc., 2/6.

**MULTI-METER KIT**


Parts suitable for making a multi-meter to measure volts, milliamps and ohms. Kit containing all the essential items including moving-coil meter, resistors, range selector, calibrated scale, etc., in only 15/-, plus 1/- post and packing.




**INSERT MICROPHONE**

Ref. No. Mic 253-A, a really beautifully made magnetic mike of little over 1/2 in. in diameter. Price 3/6, post free.

**THERMOSTATS**

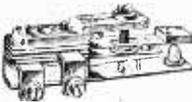

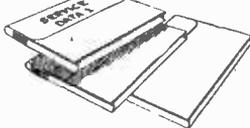
Useful for the control of a pilot process such as converters, glue-jets, vulcanisers, hot plates, etc. Adjusted to operate over the temperature range 50-550 deg. F. 14 amp. 3/6; 5 amp. 8/6; 2 amp. 6/6; 15 amp. 15/6.



**SERVICE DATA**

100 service sheets, covering British receivers which have been sold in big quantities and which every service engineer is ultimately bound to meet. The following makers are included: Aerodyne, Alba, Bush, Cossor, Ekco, Ever-Ready, Ferguson, Ferranti, G.E.C., H.M.V., Kolster Brander, Liffen, McMichael, Marconi, Mullard, Murphy, Philco, Philips, Pye, Ultra. Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price 2/1 for the complete folder.

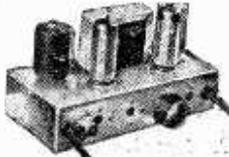**PRODUCTION INCREASED — CIRCUIT IMPROVED—PRICE REDUCED**



**3-speed Gramophone Motor**

Latest rim drive 3-speed motor with metal turntable and rubber mat. Small mod. makes speed easily variable for special effects and dance work.

**Hi-Fi Pick-up**

Using famous Cosmoord Hi-G turn-over crystal. Separate sapphire for each speed. Neat bakelite case with pressure adjustment. Special ship offer this month. The two units for 24/10/-, plus 5/- post and insurance, or made up on board as illustrated 25/10/-, plus 5/- post.


**3 & 4 Speed Gramophone Auto-Changer**

Latest types by all famous makers are invariably in stock at competitive prices. B.S.R. Monarch, Garrard, etc. Latest models from 27/15/-, plus 5/- carriage and insurance.



To-day's best value in Band III Converters suitable for your T.V. or money refunded. Complete ready to operate. 49/6 non mains, or 69/6 mains, post and insurance, 3/6.

**RECORD PLAYER 24/10/0**

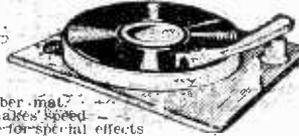

South London Branch.—For the benefit of callers south of London we have opened a branch at 266, London Road, Croydon.


**The "CRISPIAN" Portable Radio**



A 4-valve truly portable battery set with very many good features as follows: Ferrite rod aerials, low consumption valves, superhet circuit with A.V.C. ready-built and aligned chassis if required, beautiful two tone cabinet covered with C.I. Rexline and Tygan. Guaranteed results on long and medium waves anywhere. All parts, including speaker and cabinet are available separately or if all ordered together the price is 27/15/- complete, post and ins. 3/6, ready-built chassis 30/- extra. Instruction booklet free with parts or available separately price 1/6.

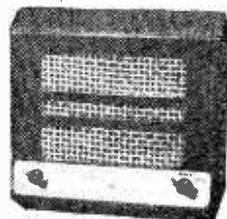**OFFICE INTERCOM.**

This is a 2-station "master" unit comprising an A.C. mains operated push-pull amplifier with built-in P.M. speaker which acts as microphone or loudspeaker depending on whether switch is set to "talk" or "listen." Complete in polished cabinet ready to work. Price, complete with one sub and 100ft. twin wire, 28/19/6, plus 3/6 carriage and insurance. Sub stations 19/6 each.



**ELECTRIC BLANKET WIRE**

Waterproof P.V.C. covered, so blanket washable. 161 ohms per foot—1/6 per yard. 14 yards, ideal for average blanket, 2/1 post free.

**HUGE MINISTRY PURCHASE**

R.1155—yours for 22 down

Frequency 75 kc/s to 18 mc/s—10 valves—metal case—robust receiver—most over 160 to make—will give years of service, very little used. Price 210 or 514 units of 22. Carr. & transit case 15/- cr.




**ENGINEERS 1" MICROMETER**

Brand new and perfect—invaluable to engineers, apprentices, model makers, students, etc. Only 10/- post free.

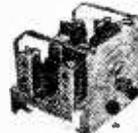**5-VALVE SUPERHET YOURS FOR ONLY 21 DOWN**

Chassis size approx. 5 1/2 x 7 1/2 x 8 1/2. First-class components, A.C. mains operation. Three waves of medium and two shorts. Complete with five valves, ready to work. New and unused. Cash price 25/19/6, or 6 payments of 21/- (carr. and ins. 7/6).



**MAINS-MINI**

Uses high-efficiency coils, covers long and medium wavebands and fits into the neat white or brown bakelite cabinet—limited quantity only. All the parts, including cabinet, valves, in fact, everything, 24/10/0, plus 3/6 post. Constructional data free with the parts, or available separately 1/6.

**W.D. CIRCUIT DETAILS**

Diagrams and other information extracted from official manuals. All 1/6 per copy, 12 for 15/-, American Service

A.1134	R.109
BC.348	76 receiver
BC.312	76 receiver
R.103A	R28/ARCS
B.C.342	R1110/A
RA-1B	RA-1B
R-208	AR8D
R-1155	AN/APA-1
R-1124A	76
R-1132A R-1481	R.T.18
R-1147	CAY-4C-AAM-
R-1228A	RADAR
R-1062	A.S.B.-3
R-1355	Indicator 62A
B.C.1206-A B	Indicator A.S.B.3
B-455-A (or-B)	Indicator 62
B-454-A (or-B)	Indicator 65K
B-453-A (or-B)	R.F. unit 24
Transmitter T1154	R.F. unit 26
Fifty-eight walkie talkie	R.F. unit 25
Frequency meter	R.F. unit 27
B.C. 221	Wireless No.19
	Demobbed valves


**PUSH PULL OUTPUT TRANSFORMER**

Potted Midrect type standard matching. Ref. No. 866. Size 1 1/2 in. x 1 in. x 2 1/2 in. Price 8/6 post free.

**PUSH PULL INPUT TRANSFORMER**

Potted Midrect type Ref. No. 4558. Size 1 in. x 1 in. x 1 1/2 in. Price 6/6 post free.

**"CHIMELITE"**

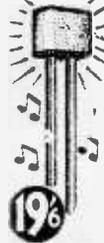

It is a hall light as well as a double chime and you can make it in a couple of evenings for the total cost of only 19/6 including instructions, post, etc. 2—data available separately price 2/-.

**FLUORESCENT LIGHTS**



These are a complete fluorescent lighting fitting. Built-in ballast and starters—stove enamelled white and ready to work. Ideal for the kitchen, over the work-bench, and in similar locations. Single 40. 4ft. 3in. long, uses a 40-watt standard tube. Price, 39/6 complete with tube. Carriage and ins. 5/6. Twin 20. uses two 20-watt standard tubes. Price, 29/6 less tubes. Carriage and ins. 4/6.



**MULLARD AMPLIFIER "510"**

A Quality Amplifier designed by Mullard. Power output exceeds 10 watts. Frequency response almost flat from 10 to 20,000 C.P.S. For use with the Acos "Hi G" and other good pick-ups. Made up and ready to work for £12.10/-, plus 10/- carriage and insurance.



**CONNECTING WIRE**


P.V.C. covered in 100ft. coils—2/9 a coil or four coils different colours. 10/- post free.

**12in. T.V. CABINET—15/-**



We are offering these at not much more than the cost of the plywood they contain. If not wanted for T.V. many useful items can be made—record storage cabinet, H.F. loudspeaker case, book case, etc., etc. Price 15/- carriage 3/6.

**THE UNI-T.V.**

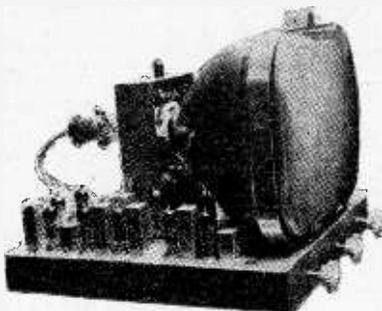

Undoubtedly the most up-to-date television for the home constructor. You can build all or only part and the set when finished will be equal to a factory-made equivalent. What other constructor T.V. has all these features?

- ★ Made up units if required.
- ★ All miniature valves.
- ★ Metal rectifier.
- ★ No expensive transformer.
- ★ 13-channel circuitry.
- ★ Multi-vibrator time bases.
- ★ Ferroxcube, E.H.T. and scan coils.
- ★ 34.37 Mc/s I.F.
- ★ Suitable for any modern 12, 14 or 17in. tube.
- ★ Modern contemporary cabinet if required.

The building cost (less tube) is only £31.10.0. plus 10/- carriage and insurance. All parts guaranteed 12 months. Full information and data free with parts or available separately price 3/6.

**THE STATESMAN**




**THIS IS ON OFFER AT APPROX. HALF COST TO MAKE.**

An impressive costly looking cabinet originally designed for T.V. but simple modification makes the cabinet suitable for radio-gram amplifier, tape recorder, or reflex speaker—size 23in. wide, 22in. deep and 57in. high. Limited quantity at £8.15/- each. Carriage 12/6.

South London Branch.—For the benefit of callers south of London we have opened a branch at 286, London Road, Croydon.

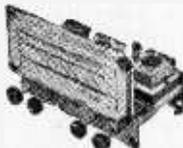**THE CLEVELAND ORGANTONE**

5 valve superhet covering Long, Medium and Short waves. Miniature valves—Low loss coils—permeability-tuned I.F.S.—full A.V.C.—variable negative feedback—gram. position—4 watts output—particularly fine tone. Price £11.10.0. Carriage and insurance, 7/6.




**CHASSIS ASSEMBLY**




Three-colour 3-waveband scale covering standard, Long, Medium, and Short wavebands, scale pan, chassis, punched for standard 5-valve superhet, pulley driving head springs, etc., to suit. Scale size 1 1/4 x 3 1/2 in. Chassis size 15 x 5 in. x 2 1/2 in. deep. Price 15/- plus 1/6 post. Note.—This is the one that fits our 47.6 table cabinet.

**HIGH VOLTAGE TESTER**

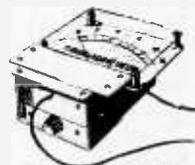

An instrument that will measure voltages up to 10,000 but which draws no current from the source, will probably be a valuable addition to your workshop equipment. It can be made entirely from odds and ends. Booklet giving full instructions, plans, etc., 2/6 post free.

**"SNIPERSCOPE"**

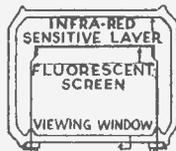

"Cat's eye" used for seeing in the dark. Will work burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Price 5/- each. Post and ins. 1/- . Data will be supplied with cells if requested.

**DON'T BE CAUGHT LIKE THIS**



**CAR STARTER CHARGER KIT**

All parts to build 6- and 12-volt charger which can be connected to a "flat" battery and will enable the car to be started instantly. Kit comprising the following:

Mains transformer.....	19/6
5-amp. rectifier.....	17/6
Regulator Stud Switch.....	3/6
Resistance Wire.....	2/6
Resistance Former.....	2/6
Mains on/off Switch.....	1/-
0.5 amp. Moving Coil Meter.....	9/6
Constructional Data.....	1/6
or if bought all together price is	£2.6.
plus 2/- post and packing.	

**ELECTRONIC PRECISION EQUIPMENT, LTD.**

Post orders should be addressed to E.P.E., LTD., Dept. 5, 123, Terminus Road, Eastbourne. Post enquiries to Eastbourne with stamped envelope, please.


42-46, Windmill Hill, Luton, Beds.	152-3, Fleet Street, E.C.4.	29, Strand Green Rd., Finbury Park, N.4.	249, Kilmarn High Road, Kilmarn. Ayr, Ayr.
Phone: RU1SLIP 5780	Phone: FLEet 2833	Phone: ARChway 1049	MAIda Vale 4921.
Half day, Wednesday.	Half day, Saturday.	Half day, Thursday.	

*For a regular  
smooth response curve*


**You need a PHILIPS**

**dual-cone  
loudspeaker**

Made in Holland

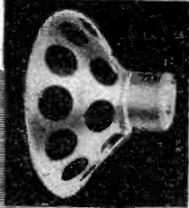

A special dual-cone design distinguishes Philips high fidelity speakers, resulting in energy transmissions almost independent of frequency. This ensures that, in an ordinary room, sound pressure within an angle of 90 degrees varies by not more than six decibels; while the excellent spatial distribution of acoustic energy—even at the highest frequencies—is obtained by Philips choice of coupling factor between high-range and low-range cones.

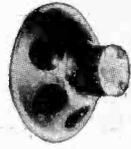

The small cone acts as a high note radiator for frequencies above 10,000 cycles and as a diffuser for frequencies below 10,000 cycles from the large cone. The large cone itself acts as a low note radiator below 10,000 cycles, and as a reflector for the high notes above this frequency. The distribution of sound over the entire frequency range is thus much wider than on a normal loudspeaker. These loudspeakers have a very smooth response curve combined with a low resonance frequency.

**N.B.** Any of these speakers may be used on their own or with another suitable loudspeaker using a crossover unit.

The Philips dual-cone loudspeaker comes in two sizes: 8" and 12", price 6½ gns. (tax paid) and 10 gns. respectively. There is also a single-cone loudspeaker, available in the same two sizes: price £6.2s. 6d. (tax paid) and £10.0s. 0d. respectively.

For full details write to:




**PHILIPS ELECTRICAL LTD**  
Musical Equipment Dept. • Century House  
Shaftesbury Avenue • London • WC2

(PR436)

**THE SUPERIOR BUREAU**

**PRICE 16½ Gns.**  
Plus 25/- carriage

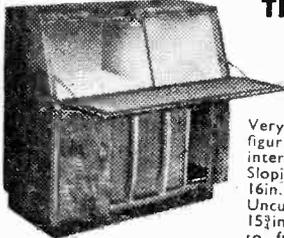


Very elegant in highly figured walnut veneer with internal panels in sycamore. Sloping radio panel size 16in. long x 10½in. high. Uncut motorboard size 15½in. long x 13½in. back to front. Lid panelled in beige leatherette. Two large storage cupboards. Speaker chamber large enough for 12in. speaker, overall cabinet size 35in. high, 34in. long, 16½in. deep.

**BAKELITE CABINET**

Ideal for midget construction. Available in Walnut or Green. Size 12in. long, 7in. high, 5½in. deep. Complete with handle, back, dial and two knobs.

**PRICE 15/6**  
Plus 3/-  
p.p.

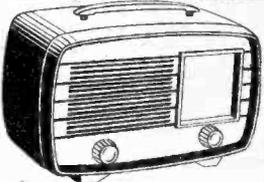


**THE SUPEREX "55" BATTERY PORTABLE**

Four valve superhet covering L. and M. waves. Attractive two-colour attache case size 10½in. x 8½in. x 4½in. Large elliptical speaker.

**PRICE £7-15-0** Plus 4/- postage and packing. SEND 1/6 FOR FULL BUILDING INSTRUCTIONS.

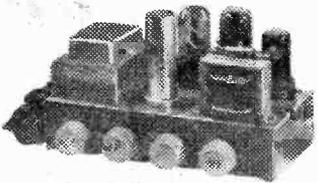**S.R. 3-4 WATT AMPLIFIER**

**PRICE £5.15.0** Plus 3/6 postage and packing.



High quality three valve three watt amplifier for A.C. Mains 200/250 volts. Four controls give a wide tone variation. 3 ohm speaker output. Chassis fully isolated. Valve line-up: 6SG7, 6V6, 6X5. Bronze finished chassis size 8in. x 4in. x 5in. high. Supplied built and tested, and guaranteed for twelve months (90 days valves).

**THE COMPACT BUREAU**

**12 Gns.**  
Plus 20/- carriage.



A well-designed cabinet veneered in highly figured walnut. Outside dimensions 29½in. long, 16in. deep and 32in. high. Sloping control panel on right hand side approximately 13in. x 10½in. Removable base board size 13½in. x 13in. on left-hand side. Large storage compartment located in side cabinet above baseboard.

**PERSONAL SHOPPERS WELCOME**

SHOP OPEN : 9 a.m. to 6 p.m. Monday to Saturday ; 1 p.m. Thursday.  
TERMS : Cash with order or C.O.D. (U.K. and N. Ireland only)

**Superior Radio supplies**

**37 HILLSIDE, (HARROW ROAD) STONEBRIDGE, NW10 - Elgar 3644**



# SPECIAL OFFER 12 VALVES for 18/-, Post 2/-.

LIMITED STOCKS—ORDER NOW.

These are NOT the usual 2X2, EB34 types offered. A good selection of obsolete and older type valves—of great interest to all constructors and service men.

## ARE YOU BUILDING THIS POPULAR KIT?

Modern Portable. A.C. 'D.C. Mains' Battery Receiver. Four valves, DK96, DL96, etc. 2 Waveband Superhet. In an attractive Lizard Grey case, size 8 1/2 in. x 8 1/2 in. x 4 1/2 in. Full Kit of Parts down to last nut and bolt.



**£9.9.0**

Or if you prefer you can build the battery version first for £7/17/6 and add the mains components later. Post extra on Kit, 3/-.

Full Circuit Diagram. Shopping List, and Point-to-Point Wiring Diagram, 3/-.

**CHOKES**

250H, 250 ohms, 60 M/A. Clamp construction, each.....	6/-
10H, 200 ohms, 90 M/A. Clamp construction, each.....	9-3
10H, 200 ohms, 150 M/A. Clamp construction, each.....	13/-
10H, 300 ohms, 40 M/A. Midget Clamp construction, each.....	5-3

**TRANSFORMERS FOR BATTERY CHARGERS**

230 v. Input tapped 6-12 v. 1 amp., each.....	13-6
230 v. Input tapped 6-12 v. 3 amp., each.....	18/-


We have large stocks of Saxley Type Switches. ALL BRAND NEW. With long bearing spindles. Various numbers of Switch and Wafer Combinations. To clear at the **SPECIAL PRICE**, 8/- per dozen. Post 1/6.

**TRANSFORMER MTS**  
Small mains transformer suitable for TV converters, etc. Primary 230 v., Secondary 250 v., 40 M/A and 6.0 v., 15 amp. Price 15/6 each, postage 1/6.

**WESTINGHOUSE RECTIFIERS**  
Type 14A86, 13/6 each.

**OUTPUT TRANSFORMERS**

Multi Ratio Type, each.....	6-6
Midget for 384 Output, each.....	4-6
Standard 5,000 ohms, each.....	4-6
Standard 19,000 ohms, each.....	4-6

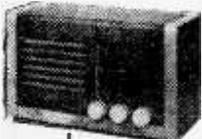

## ALPHA 3 VALVE T.R.F. KIT

£5.10.0

- ★ Easy to Build.
- ★ Valves 6J7, 6K7, 6V6GT plus metal rectifier.
- ★ Walnut cabinet.

Full instructions, point-to-point wiring diagram. Circuit diagram and full shopping list 1/- . All components may be purchased separately.

**CONDENSERS**

BEC 100 MFD 25 v.....	1/9
BEC 500 MFD 12 v.....	1/9
TCC 25 MFD 25 v.....	1/3
DI'ILLIER 100 MFD 12 v.....	1/9
BEC 50 MFD 50 v.....	2/-
TCC 25 MFD 50 v.....	1-8
TCC 50 MFD 25 v.....	1/9
TCC 250 MFD 12 v.....	1/9
BEC 250 MFD 25 v.....	1/8
TCC 50 MFD 50 v.....	1/-
BEC 250-250 MFD 6 v.....	1/6
DI'ILLIER 50-12 MFD 12 v.....	1-9

**VOLUME CONTROLS**  
Type with Single Pole Switch. 5K ohms; 10K ohms; 20K ohms; 50K ohms; 100K ohms; 2 meg.; 1 meg.; 1 meg.; 2 meg. All 3/6 each.

**DUAL VOLUME CONTROL**  
With Double Pole Switch 500K ohms and 500K ohms. Price 6/9 each.

**TYANA SOLDERING IRONS**  
Lightweight 40-watt iron, with easily replaceable elements and bits, 200/250 v., price 16/9 each.

**TURNOVER CRYSTAL PICK-UP CARTRIDGES**  
Aston Type HOP37-3c. Long-playing and standard with stylus (as used in latest radiograms). Price 15/6 each.

**PURETONE TAPE**  
1,200ft. Reel, Plastic Spool. 12/6 each.

**VIBRATOR UNIT**  
12 volt Vibrator Unit by Mallory, complete with vibrator, 17/6 each. Aerialite Band III Aerials, 5 element, 702 x 11. An array with universal 1in.-2in. masthead bracket, suitable channels 8, 9 and 10. Price 41/-, carriage 4/6. Aerialite Coaxial outlet boxes at 4/6 each. Aerialite Coaxial plugs and sockets at 1/1 each.

**COIL FORMERS**  
Aladdin Coil Formers 1in. complete with Iron Dust Cores, each..... 6d.  
Aladdin Coil Formers 1in. complete with Iron Dust Cores, each..... 6d.  
Ceramic Coil Formers 1in. dia. 1in. long 4 Ribs, each..... 4d.  
Dynamo Coil Formers 2in. dia. 2 1/2 in. long. These have been removed from R.A.F. Beau Approach equipment and are in some cases complete with Trimmers, each..... 8d.

**CHARGER RECTIFIERS**—All Full Wave

12 volt 1 amp., each.....	5-3
12 volt 2 amp., each.....	8-6
12 volt 3 amp., each.....	13-9

**TSL FERROMAGNETIC AERIAL ROD**

A length of Ferrite Rod with full instructions for winding Medium or Medium and Long Wave Internal aerials. 6/- each.

**SPECIAL OFFER**  
Anti-ferre Aerial Type CD4 Indoor with full instructions, etc., 13/6 each. Carriage Paid.

Our **NEW 1956-57 Illustrated Catalogue** is now ready. 44 pages of interesting reading. Send 1/- for your copy.

**HEATER TRANSFORMERS**—All 250 v. Input.

2 volt 1.5 amp., each.....	5-6
2 volt 2.0 amp., each.....	8-3
4 volt 1.5 amp., each.....	5-6
4 volt 2.0 amp., each.....	10-6
5 volt 2.0 amp., each.....	10-6
6.3 volt 1.5 amp., each.....	5-6
6.3 volt 2.0 amp., each.....	9-6
12 volt 1.5 amp., each.....	5-6

**CONDENSERS. TELEVISION ELECTROLYTICS**

100 MFD 450 v. TCC, each ...	2
60-120 MFD 300 v. BEC, each	5
100-200 MFD 275 v. BEC, each	5
60-250 MFD 275 v. BEC, each	5

**PUBLICATIONS**

No. 134—F.M. TUNER CONSTRUCTION by W. J. May	each
★ Easy to Build, Point-to-Point Wiring ★ Super High Fidelity Response ★ 32 Pages	
★ All Components for this Circuit available ex stock... 2/6	
No. 138—HOW TO MAKE AERIALS FOR TV (Band 1 and 3) and V.H.F. (Band 2) Data for all Channels. Ten different designs for local and fringe areas.....	2/6
No. 135—ALL DRY BATTERY PORTABLE CONSTRUCTION. ★ Simple and cheap to build ★ Point-to-point wiring ★ Dual Penic serial for high sensitivity... 2/6	
No. 100—A COMPREHENSIVE VALVE GUIDE, Book No. 1. No. 121—A COMPREHENSIVE VALVE GUIDE, Book No. 2 (Characteristics and Base Connections).....	5-
No. 103—RADIOFOLDER "A" The Master Colour Code Index for Radio and Television.....	1/6
No. 114—RADIOFOLDER "E" An inexpensive Tape Recorder.....	2/6
Please include 4d. postage per copy.	

**CRT ISOLATION TRANSFORMERS**

NR9A 2 v.; NR9B 4 v.; NR9C 6.3 v.; NR2D 10.8 v.; NR9I 13.3 v. Price 10/6 each, all for use on receivers with own transformer.	
NR14 Input 230/240 v., output 2-24-21-21-3 volts at 2 amps., 17/6 each.	
NR12 Input 220/240 v. Multi output 0-2-4-6-3-7-3-10-13 volts. 25% and 50% BOOBT, 21/- each.	
NR15 Input 220/240 v. Output 2 v., with 25% and 50% BOOBT. Price 17/6 each.	

**LOUD SPEAKERS**  
All PM Types less Transformers

Each	
3 1/2 in. Square Type Elec. Speaker.....	19/6
5 in. Types by Elec., Lectrom, Celestion, etc.....	17/6
6 1/2 in. Types by Goodmans, Rola, R. & A.....	18/6
8 in. Types by Goodmans, Plessey, R. & A.....	19/6
10 in. Types by R. & A., Celestion, etc.	25/6
12 in. Plessey Lightweight.....	35/-
Elliptical Speakers, Goodmans, 4 in. x 7 in.....	19/6
Mains Energised Units 6 1/2 in. x 8 in. ohm field.....	19/6
Post extra, 2/-.	

**ALPHA RADIO SUPPLY CO.**

5/6 VINCES CHAMBERS  
VICTORIA SQUARE  
LEEDS 1.

**TERMS:** Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. All single valves postage 6d.

**MAIL ORDER ONLY**

# R.S.C. BATTERY CHARGING EQUIPMENT

## ASSEMBLED CHARGERS

6 v. 1 amp ..... 19/2  
 6 v. or 12 v. 1 amp. .... 25/9  
 6 v. 2 amps. .... 29/9  
 6 v. or 12 v. 2 amps. .... 38/9  
 6 v. or 12 v. 4 amps. .... 56/9  
 Above ready for use. Carr. 2/9.  
 With mains and output leads.

## HEAVY DUTY KIT

12 v. 30 amp. Suitable for Garage or firm with a number of vehicles.  
 Mains input 200-250 v. 50 c/s.  
 Outputs 12 v. 15 amp. twice.  
 Consists of Mains Trans. 2 Metal Rectifiers. 2 Meters, 4 Fuses, 4 Terminals, 2 Rheostats and circuit. Only 9 gns., carr. 15/-.

## BATTERY CHARGER KITS

Consisting of: Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse holders, Grommets, panels and circuit. Carr. 2/6 extra.  
 6 v. or 12 v. 1 amp. .... 22/9  
 6 v. 2 amps. .... 25/9  
 6 v. or 12 v. 2 amps. .... 31/6  
 6 v. or 12 v. 4 amps. .... 49/9

## BATTERY CHARGER KIT

Consisting of F.W. Bridge Rectifier 6/12 v. 5 a. Mains Trans.; 0-9-15 v. 6 a. output and variable charge rheostat with knob. Only 45/9.

## ASSEMBLED CHARGER

6 v. or 12 v. 2 amps.  
 Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready for use. With main's and output leads. Double Fused. Only Carr. 3/6. **46/9**

All for A.C. MAINS 200-250 v., 50 c/s. Guaranteed 12 months.



Assembled 6 v. or 12 v. 4 amps. Fitted Ammeter and variable charge selector. Also selector plug for 6 v. or 12 v. charging. Double fused. Well ventilated steel case with blue hammer finish. **69/9**

Ready for use with mains and output leads. Carr. 3/6.

# R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and impregnated. Primaries 200-230-250 v. 50 c/s. Secondary TOP SHROUDED DROP THROUGH  
 250-0-250 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a. .... 16/9  
 350-0-350 v. 70 mA, 6.3 v. 2.5 a. .... 16/9  
 350-0-350 v. 80 mA, 6.3 v. 2 a, 5 v. 2 a. .... 18/9  
 250-0-250 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a. 22/9  
 300-0-300 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a. 22/9  
 350-0-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a. 22/9  
 350-0-350 v. 100 mA, 6.3 v. 4 a, C.T. 0-4-5 v. 3 a. .... 23/9  
 350-0-350 v. 150 mA, 6.3 v. 4 a, 5 v. 3 a. .... 29/9

## FULLY SHROUDED UPRIGHT

250-0-250 v. 60 mA, 6.3 v. 2 a, 5 v. 2 a. Midget type 21-3-in. .... 17/6  
 350-0-350 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a. .... 19/9  
 250-0-250 v. 100 mA, 6.3 v. -1 v. 4 a, C.T. 0-4-5 v. 3 a. .... 26/9  
 250-0-250 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a. for R1355 conversion. .... 31/-  
 300-0-300 v. 100 mA, 6.3 v. -1 v. 4 a, C.T. 0-4-5 v. 3 a. .... 26/9  
 350-0-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a. 23/9  
 350-0-350 v. 100 mA, 6.3 v. 4 v. 4 a, C.T. 0-4-5 v. 3 a. .... 27/9  
 300-0-300 v. 130 mA, 6.3 v. 4 a, 6.3 v. 1 a. for Mullard 510 Amplifier. .... 35/9  
 350-0-350 v. 150 mA, 6.3 v. 4 a, 5 v. 3 a. 33/9  
 350-0-350 v. 150 mA, 6.3 v. 2 a, 6.3 v. 2 a, 5 v. 3 a. .... 35/9  
 425-0-425 v. 200 mA, 6.3 v. 4 a, C.T. 6.3 v. 4 a, C.T. 5 v. 3 a. Suitable Williamson Amplifier, etc. .... 49/9  
 450-0-450 v. 250 mA, 6.3 v. 6 a, 6.3 v. 6 a, 5 v. 3 a. .... 69/9

## FILAMENT TRANSFORMERS

All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/6; 12 v. 3 a. or 24 v. 1.5 a. 17/6.

## SMALL POTTED MAINSTRANS.

Removed from New Ex-Govt. units. Primary 0-200-230-250 v. Secs. 250-0-250 v. 60 mA, 6.3 v. 2 a. 5 v. 2 a. Size 31 x 41 x 3in. .... **11/9**

## E.H.T. TRANSFORMERS

2,500 v. 5 mA, 2-0-2 v. 1.1 a, 2-0-2 v., 1.1 a for VCR37, VCR517, etc. .... **36/6**

## ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s ..... 14/9  
 120 v. 40 mA, 5-0-5 v. 1 a. .... 15/9  
 90 v. 15 mA, 4-0-4 v. 500 mA. .... 9/9

## CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries :  
 0-9-15 v. 11/9; 0-9-15 v. 3 a. 16/9;  
 0-3-5-9-17 v. 3 a. 17/9; 0-3-5-9-17.5 v. 4 a. 18/9; 0-9-15 v. 5 a. 19/9; 0-9-15 v. 6 a. 22/9.

## SMOOTHING CHOKES

250 mA 5 H 100 ohms ..... 12/9  
 150 mA 7-10-250 ohms ..... 11/9  
 100 mA 100 H 200 ohms. .... 8/9  
 80 mA 10 H 350 ohms ..... 5/6  
 60 mA 10 H 400 ohms. .... 4/11

## OUTPUT TRANSFORMERS

Midget Battery Pentode 66; 1 for 3S4, etc. .... 3/9  
 Small Pentode, 5,000 $\Omega$  to 3 $\Omega$  ..... 3/9  
 Small Pentode 7/8,000 $\Omega$  to 3 $\Omega$  ..... 3/9  
 Standard Pentode, 5,000 $\Omega$  to 3 $\Omega$  ..... 4/9  
 Standard Pentode, 7/8,000 $\Omega$  to 3 $\Omega$  ..... 4/9  
 Multi-ratio 40 mA, 30-1.45-1.60-1.90-1. Class B Push-Pull Push-Pull 10-12 watts 6V6 to 3n or 15n ..... 5/6  
 Push-Pull 10-12 watts to match 6V6 to 3-8 or 15n ..... 16/9  
 Push-Pull 15-18 watts, 6L6, KT66 ..... 22/9  
 Push-Pull 20 watts, sectionally wound 6L6, KT66, etc., to 3 or 15n 47/9  
 Williamson type exact to spec. .... 85/-

FOR CALLERS ONLY. WE HAVE MANY CLEARANCE LINES BOTH SMALL AND LARGE, INCLUDING SMALL NUMBER OF 1954 and 1955 AMPLIFIER KITS

## MANUFACTURERS' SURPLUS MAINS TRANSFORMERS.

250-250 v. 50 c/s. Fully shrouded upright mounting 425-0-425 v. 150 mA, 6.3 v 3 a, 5 v. 3 a. 29/11, post 2/9. Wearite 325-0-325 v. 100 mA, 6.3 v. 2.5 a, 5 v. 2 a. 19/9. Drop Through Chassis type 250-0-250 v. 70 mA, 6.3 v. 2.5 a, 10/9.

EX-GOVT. TRANSFS., 230/250 v. 50 c/s 480 v. 200 mA, 6.3 v. 5 a, 25/9; 300-0-300 v. 150 mA, 4 v. 3 a. 9/9; 0-16-16-20 v. 35 a. 69/6, carr. 7/6.

## EX-GOVT. SMOOTHING CHOKES

250 mA, 5 H 50 ohms ..... 12/9  
 150 mA, 10 H 100 ohms ..... 11/9  
 150 mA, 6-10 H 150 ohms. Drop. .... 6/9  
 100 mA, 10 H 150 ohms Tropicalised. .... 3/11  
 L.T. type 1 amp. 2 ohms ..... 2/9

## EX-GOVT. METAL BLOCK (PAPER CONDENSERS)

4 mfd. 500 v. 2/9; 4 mfd. 1,000 v. 4/9; 4 mfd. 1,500 v. 5/9; 8 mfd. 500 v. 6/9; 8 mfd. 500 v. 4/9; 10 mfd. 500 v. 5/9; 4 mfd. 400 v. plus 2 mfd. 250 v. 1/11.

## EX-GOVT. ELECTROLYTICS.

Removed from unused equipment. 8-16 mfd. 550 v. 1/3; 400 mfd. 6V, with clip, 1/9; 50 mfd. 50 v., with clip, 9d.

## EX-GOVT. VALVES (NEW)

1T4	7/9	6F6G	7/9	6AT6	7/9
1S5	7/9	EF39	5/9	ECC83	9/9
351	8/9	6V6GT	6/9	EF80	7/9
5Y3G	8/9	6X5GT	7/9	EF91	6/9
5U4G	8/9	6L6G	11/9	EF95	4/9
524G	8/9	807	7/9	EL32	3/9
6K7E	5/9	12A6	7/9	EL91	5/9
6K8G	9/9	15D2	4/9	KT44	8/9
6S7GT	9/9	5Z4G	9/9	KT66	11/9
6SL7GT	9/9	25Z4G	4/9	SP61	2/9
6SN7GT	9/9	MH4	4/9	35Z4	8/9

## EX-GOVT. UNIT REFL.

Brand new, cartoned. Complete with 14 valves, including 5Z4, E.H.T. rectifier. Trans. Choke, etc. Only 29/9, carr. 7/6.

## ELECTROLYTICS (current production)

NOT EX-Govt. Can Types

Tubular Types		Can Types	
8 $\mu$ F 450 v. ....	1/9	8 mfd. 600 v. 2.11	
8 $\mu$ F 500 v. ....	2/6	16 mfd. 500 v. 3/9	
16 $\mu$ F 350 v. ....	2/3	16 mfd. 350 v. 1/11	
16 $\mu$ F 450 v. ....	2/9	16 $\mu$ F 450 v. ....	2/9
16 $\mu$ F 500 v. ....	3/9	32 $\mu$ F 350 v. ....	2/11
32 $\mu$ F 350 v. ....	3/9	32 mfd. 450 v. ....	4/9
32 mfd. 500 v. ....	5/9	100 mfd. 450 v. ....	4/9
25 $\mu$ F 25 v. ....	1/3	8-8 $\mu$ F 450 v. ....	2/9
50 $\mu$ F 12 v. ....	1/3	8-16 $\mu$ F 450 v. ....	2/11
50 mfd. 25 v. ....	1/6	16-16 $\mu$ F 450 v. ....	3/11
50 $\mu$ F 50 v. ....	1/9	32-32 $\mu$ F 350 v. ....	4/9
100 mfd. 12 v. 1/9		32-32 $\mu$ F 450 v. ....	5/9
100 mfd. 25 v. 2/3		60-100 mfd. ....	350 v.
6,000 mfd. 6 v. 3/9		64-120 mfd. 350 v. ....	7/9
		100-200 mfd. ....	350 v.
		275 v. ....	6/9

Many others in stock.

## HUNTS MOLDSEAL CONDENSERS.

.005 mfd. 400 v., .01 mfd. 400 v., .04 mfd. 500 v., 5/6 doz. (one type); 1 mfd. 350 v., 8d. ea.; .25 mfd. 500 v., 1/3; .5 mfd. 500 v., 1/8 ea.

# R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all'dry battery eliminator. Size 51 x 41 x 2in. approx. Completely replaces batteries supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s. is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9. or ready for use, 46/9.



Type BM2. Size 8 x 5 1/2 in. Supplies 120 v., 90 v., and 60 v., 40 mA and 2 v. 0.4 a to 1 amp. Fully smoothed. Therefore completely replacing both H.T. batteries and L.T. 2 v. accumulators. When connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. Accumulator. Complete kit of parts with diagrams and instructions 49/9. or ready for use 59/6.

## H.T. ELIMINATOR AND TRICKLE CHARGER KIT.

Input 200-250 v. A.C. Output 120 v. 40 mA. Fully smoothed and rectified supply to charge 2 v. accumulator. Price with louvred metal case and circuit, 29/6. Or ready for use, 8/9 extra.

**SPECIAL OFFERS** 8-8 mfd. 450 v. small can electrolytics in lots of six, 1/6 ea. Small .0005 mfd. 2 Gangs, 4/9 ea.

**T.V. CABINETS.** Leading manufacturers surplus. Attractive designs. Walnut veneered with doors for 15, 16, or 17in. Tube, £3-19-6. Carr. 7/6.

## EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet. 6in. 2-3 ohms, 29 6. 8in. 2-3 ohms, 35/9. Very limited number.




**VOLUME CONTROLS** with long (1in. diam.) spindle, all values less switch. 2/9; with S.P. switch, 3/9; with D.P. switch, 4/6.

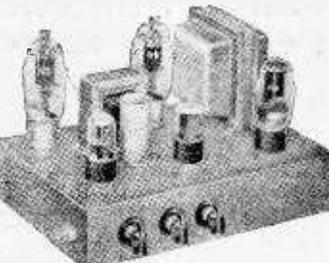**R.S.C. A8 ULTRA LINEAR 12 WATT AMPLIFIER**

NEW 1956 Model High-Fidelity Push-Pull Amplifier with "Built-in" Tone Control, Pre-amplifier, High sensitivity. Includes 5 valves (807 outputs). High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE** Lift and Cut. Frequency response 3 db. 30-3,000 c/s. Six negative feedback loops. Hum level 71 db. down. ONLY 70 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

**£7-15-0**  
 For STANDARD or LONG-PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, GUITARS, etc. **OUTPUT SOCKET** with plug provides 300 v. 20 mA. and 6.3 v. 1.5 a. For supply of a **RADIO FEEDER UNIT**. Size approx. 12.9-7in. For A.C. mains 200-250 v. 50 c/s. Outputs for 3 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value at **£7/15/-**, or factory built 45/- extra. Carriage 10/-.  
 If required louvred metal cover with 2



carrying handles can be supplied for 17/6. Additional input socket assembly Vol. Control so that two different inputs such as Gram and "Mike" or Tape and Radio can be mixed, can be provided for 13/- extra. Guaranteed 12 months.

**TERMS** on assembled two input model. **DEPOSIT** 25/6 and nine monthly payments 22/4. **HIGH-FIDELITY MICROPHONES and SPEAKERS** in stock. Keep cash prices or H.P. terms if supplied with amplifier.

**R.S.C 30 WATT ULTRA LINEAR HIGH-FIDELITY AMPLIFIER A6**

A highly sensitive Push-Pull, high output unit with self-contained Pre-amp and Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response  $\pm$  3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, and separate Bass and Treble controls. Minimum input required for full output is only 30 millivolts so that **ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE**. The unit is designed for **CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS**, etc. For use with **Electronic ORGAN, GUITAR, STRING BASS**, etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDES L.T. and H.T.** for a **RADIO FEEDER UNIT**. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has outputs for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions.

If required cover as for A8 can be supplied for 17/6. **ONLY 9 GNS.** An extra input with associated vol. control so that two separate inputs such as Gram and Mike can be mixed, can be provided for 13/- extra. The amplifier can be supplied, factory built with 12 months' guarantee, for 50/- extra. **TERMS** for assembled two input model: **DEPOSIT** 28/9 and 9 monthly payments of 28/9.

**P.M. SPEAKERS.** All 2-3 ohms, 5in. Goodmans, 17/9. 7 x 4in. Elliptical Goodmans, 10/6. 6in. Plessey, 16/9. 8in. Plessey, 16/9. 8in. Rola, 19/9. 10in. Plessey Heavy duty, 28/9. 10in. R.A. 28/9. 12in. Plessey, 29/11. 10in. W.B. "Stentorian" 3 or 15 ohms type HF1012 10 watts, high-fidelity type. Highly recommended for use with any of our amplifiers, £4/10/9. 12in. Plessey, 15 ohm 10 watts, 3 gns.

**PLESSEY DUAL CONCENTRIC 12in. 15 ohm HIGH-FIDELITY SPEAKER** with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.) providing extraordinarily realistic reproduction when extra used in car, AB or similar amplifier. **£4/10/9**. Price complete, only 25/17/6.

**M.E. SPEAKERS** 2-3 ohms, 8in. R.A. Field, 600 ohms, 11/9.

**COAXIAL CABLE** 75 ohms, 4in. 8d. var. Twin Screened Feeder, 11d. yard.

**SELENIUM RECTIFIERS**

6/12 v. 1 a.	5/9	6/12 v. 1 a. H.W.	2/9
6/12 v. 2 a.	8/9	H.T. Types H.W.	
6/12 v. 3 a.	11/9	150 v. 40 mA.	3/9
6/12 v. 4 a.	15/9	250 v. 50 mA.	4/11
6/12 v. 6 a.	19/9	250 v. 80 mA.	6/9
6/12 v. 10 a.	25/9	250 v. 150 mA.	9/9
L.T. Types H.W.		300 v. 250 mA.	12/9

**R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER**

For 200-250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5. Complete kit with diagrams, £3/15/- Assembled 22/6 extra. Carr. 3/6.

**THE SKYFOUR T.R.F. RECEIVER** A design of a 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. It consists of a variable-Mu high-gain H.F. stage followed by a low distortion anode bend detector. Power pentode output is used. Valve line up being 6K7, 5P61, 6F6C. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-point wiring diagrams, instructions and parts list. 1/9. This receiver can be built for a maximum of £4/10/6 including attractive Brown or Cream Balcalite or Walnut veneered wood cabinet 12 x 6; x 6 1/2 in.

**R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER**



A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads, in addition to all other types of pick-ups and practically all mikes. Separate Bass and Treble controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down. 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape Deck preamplifier. For A.C. mains input of 200-250 v. 50 c/s. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with green crackle finish and point-to-point wiring diagrams and instructions. Exceptional value at only 24/15/-, or assembled ready for use 25/- extra, plus 3/6 carr.

**R.S.C. TA1 HIGH QUALITY TAPE DECK AMPLIFIER.** For ALL Tape Decks with High Impedance, Playback and Erase Heads, such as Lane, Truxco, etc. (Unit can now be supplied for use with latest Use ONLY Colloredo Tape Transcriber: refer to TA1C.) For A.C. Mains 230-250 v. 50 c/s. **11 GNS.**

Positive compensated identification for recording level by Magic Eye. Recording facilities for 15, 74 or 31in. per sec. Automatic equalisation at the turn of a knob. Linear frequency response of  $\pm$  3 db., 50-11,000 c.p.s. Negative feedback equalisation. Minimum microphony and hum. High output with completely effective exposure and distortionless reproduction. Sensitivity is 15 millivolts so that any kind of crystal microphone is suitable. Only 2 millivolts minimum output required from recording head. Provision is made for feeding a P.A. amplifier. Unit can also be used as a gram-amplifier requiring input of 0.75 v. R.M.S. Carriage 7/6. Illustrated leaflet 6d.

**PICK-UPS.** Colloredo high-fidelity high impedance magnetic type. Only 31/6. Brand New.

**SUPERHET FEEDER UNIT** Design of a high quality Radio Tuner Unit (specially suitable for use with any of our Amplifiers). A Gridle Pentode F changer is used. Pentode I.F., and double Diode Second Detector. Delayed A.V.C. Ac. Grid F.C. Coupling is by bottom end condenser Coupling giving freedom from alignment changes when Ae. of varying lengths and capacity are used. Both Frequency Changers and I.F. valves are A.V.C. controlled from the very low distortion Double Diode so arranged that very high Percentage modulation of the transmitter can be handled without distortion. The Feed for the delayed A.V.C. is arranged so that A.V.C. distortion is avoided. The Ch. Sw. incorporates Gram position. Controls are Tuning, W. Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 0.6-7in. high. Simple alignment procedure. Point-to-point wiring diagrams, instruction and priced parts list with illustration, 2/6. Total building cost, £4 15/-. For descriptive leaflet send S.A.E.

**GARRARD 3-SPEED MIXER AUTO-CHANGER RC110.** Current Model. Brand new, cartoned. Provision for taking 10 records. Fitted High-Fidelity turnover pick-up head with dual sapphire point stylus for Standard or Long-playing records. Very limited number at only 28/17/6. Carr. 5/6. Or deposit 3 gns. and four fortnightly payments of 1 gns.

**B.S.R. MONARCH 3-SPEED MIXER AUTO-CHANGER.** For standard 200-250 v. 50 c/s. mains. Autochanges on all 3 speeds. Plays Ten mixed 7in., 10in. and 12in. records. Separate sapphire stylus for L.P. and 78 r.p.m. High-fidelity type crystal pick-up. Minimum baseboard size needed 14 x 12 in. x 5 1/2 in. high. Brand new, cartoned, at £7.15/-, carr. 3/6.

**B.S.R. TUB 3-SPEED SINGLE RECORD PLAYING UNITS** for 7in., 10in. or 12in. records at 33, 45, or 78 r.p.m. Supplied with high-fidelity crystal pick-up with dual sapphire point turnover stylus for standard or long-playing records. Only £4/13/6. plus 3/6 carr.

**LINEAR 4-5 WATT QUALITY AMPLIFIER.** Size only 6 x 5 x 5 1/2 in. high. Designed for use with B.S.R. or Garrard Autochanger. Fitted separate Bass and Treble controls, Vol. Control and mains switch. Latest type Miniature B.V.A. valves used. For 200-250 v. A.C. mains. Ready for use. Sensitivity 45 m.v. for full output. Power supply available for T.R.F. or Superhet. Feeder Unit. CHASSIS IS NOT ALIVE. Suitable for most microphones and all types of pick-ups. Built to high standards and attractively finished. Full manufacturer's guarantee. Only 6 gns.

Terms: C.W.O. or C.O.D. NO C.O.D. under £1. Post 1/9 extra under £2: 2/9 extra under £5. Open 9 to 5:30; Sats. until 1 p.m. Catalogue 6d., Trade List 5d. S.A.E. with all enquiries.

**RADIO SUPPLY CO. 32, THE CALLS, LEEDS, 2.**



UNDOUBTEDLY THE BEST VALUE YET OFFERED

# Stern's "fidelity" Tape Recorder

ASSEMBLED & READY FOR USE **£43**

(Plus £1.10.0 Carr. and Insurance. £1 is refunded when packing case is returned to us.)  
Terms £21.10.0 deposit and 12 monthly payments of £1.10.10 or £11.0.0 deposit and 9 months of £3.18.3.


IMMEDIATELY AVAILABLE TO MAIL ORDER CUSTOMERS

!! HOME CONSTRUCTORS !!  
YOU CAN BUILD IT YOURSELF FOR **£40**

The Truvox Tape Deck and the Quality Amplifier are supplied tested and ready for use. The actual assembly of the Recorder is simple and only involves a few connections (a connection chart is supplied for this purpose). The items illustrated and described form the complete equipment and each are available for sale separately.
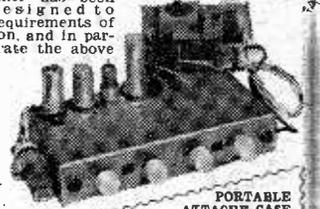
### MODEL TRI/F QUALITY AMPLIFIER

This amplifier has been expressly designed to meet the requirements of enthusiasts for fidelity reproduction, and in particular to CORRECTLY operate the above TRUVOX DECK. It is supplied complete with a matched Elliptical 3 ohms P.M. Speaker. It incorporates an efficient Tone Control arrangement and has a Magic Eye Level Indicator (Operative on Record). It can also be used as a general purpose Amplifier for high quality reproduction of gramophone records direct from a Gram Unit. Price £14.14.0.




PORTABLE ATTACHE CASE

Neat, compact and attractively finished. It contains 1 in 5 concealed pockets for Mike, Mains Lead and reel of tape.
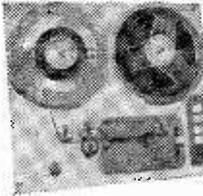
### TRUVOX TAPE DECK MODEL Mk. 111/TR7/u

This is Truvox's new "small" design being only 14in. x 13in. The whole instrument is built to close engineering limits resulting in the minimum of "wow" and "flutter" values. It will play the NEW PRE-RECORDED TAPES and takes all standard tapes up to 1,200ft.



SEND S.A.E. FOR DESCRIPTIVE LEAFLET INCLUDING PRICE DETAILS & H.P. TERMS

### SCOTSBOY MAGNETIC RECORDING TAPE

Supplied complete with a 1,200ft. reel of Scotsboy Tape. Price 35/-.

### MODEL MIC33/1 ACOS CRYSTAL MICROPHONE

A highly sensitive Mike which accurately matches the input arrangement of the Amplifier. Price £2.10.0.

## STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4

Tel.: FLEet 5812-3-4.

# WEYRAD

"H" TYPE COILS—FOR MANUFACTURERS, SERVICE ENGINEERS AND INDIVIDUAL CONSTRUCTORS

A low-priced, soundly-designed Range of Coils, providing continuous coverage from 12 to 2,000 metres in 6 Bands.


The coils are supplied in individual aerial, H.F. transformer and oscillator versions for each band. Iron dust cores are adjusted by means of a threaded brass stem with a screwdriver slot which permits fine adjustment of inductance without the danger of damage to cores. Circuit connections are made to 4 tags at the end of the former. Single 6 B.A. mounting.

"H" type coils are recommended for many popular circuits including the "Practical Wireless" AC/DC 3-valve Superhet and are widely used for servicing and conversion purposes.

RETAIL PRICE ..... 3/9 EACH.

ILLUSTRATED FOLDER ..... 3d.

A.M./F.M. RECEIVER BOOKLET ..... 2/6.

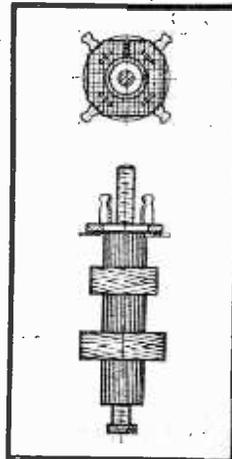

### RANGES :


- Band 1—800-2,000 mtrs.
- Band 2—250-800 mtrs.
- Band 3—190-550 mtrs.
- Band 4— 90-250 mtrs.
- Band 5— 33-100 mtrs.
- Band 6— 16 - 50 mtrs.
- Band 7— 12 - 37 mtrs.

Coils are coded according to type and range :  
HA 1 = Band 1 aerial.  
HO 3 = Band 3 oscillator

## WEYMOUTH RADIO MANUFACTURING CO., LTD.

CRESCENT STREET, WEYMOUTH, DORSET

# Build yourself a 75gns Radiogram for

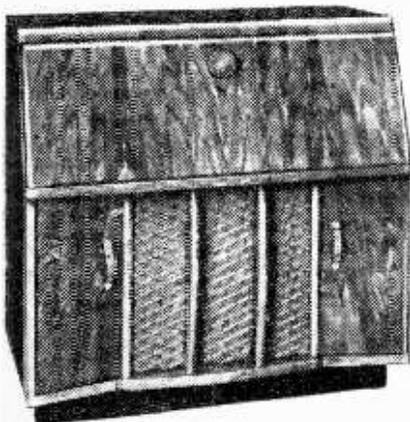

**£54-7-6 only**

**CABINET CAT. NO. CAB/03**

A magnificent Bureau-type Cabinet of the very highest quality in specially selected Walnut veneered exterior. Light Sycamore interior with Resine lining to match. Outside dimensions: length, 34in., depth 17½in., height 33in. Sloping control panel on right-hand side approx. 16in. x 10½in. Removable baseboard on right side approx. 16½in. x 15in. *Packing and carriage 25/-.*

CASH **£17.6.6**  
Or on Credit Terms.

**CHASSIS CAT. NO. CR/AFM49,FP**


9-valve Superhet with F.M./V.H.F. Band (4 wavebands). Push-pull output. Slow-motion tuning drive. Full provision of Automatic Volume Control. Sockets provided for Aerial, Earth, Gram, Pick-up and Extension Speaker. Connections provided to Gram. Motor controlled by Chassis On/Off switch. The tone-controls have been given an extra wide range to embrace all types of recordings. A.C. 200/250 volts 50 cycles only. *Packing and carriage 15/-.*

CASH **£27.6.0**  
Or on Credit Terms.

**AUTOMATIC RECORD CHANGER**

CAT. NO. R.C.A. The latest multi-speed changer incorporating 16 r.p.m. for "talking-books" and arrangement for manual control. Fitted with high-fidelity Crystal Turnover Pick-up Head. A.C. mains 200/250 volts 50 cycles only. *Packing and carriage 12/6.*

CASH **£9.15.0**

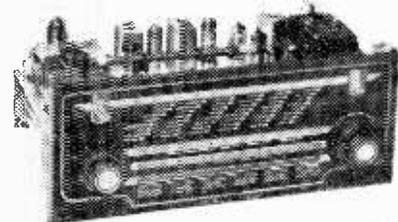

**CABINET CAT. NO. CAR-02 ★**

A well-designed Bureau-type Cabinet in a medium size. Veneered in a highly figured Walnut. Outside dimensions: length 29½in., depth 16in., height 32in. Sloping control panel on right-hand side approx. 15in. x 10½in. Removable baseboard on right-hand side approx. 13½in. x 12in. Large record compartment inside the cabinet, located at the top on left-hand side.

CASH ONLY **12 Gns.**  
*Packing and carriage 20/-.*

**OTHER CHASSIS**

CAT. NO. CR/A. 5-valve Superhet, 3 wavebands. **12 Gns.** *Packing & carr. 12/6.*

CAT. NO. CR/AFM47. 7-valve Superhet with F.M./V.H.F. Band (4 wavebands).

**23½ Gns.**  
Or on Credit Terms.  
*Packing and carriage 15/-.*

**★ F.M. TUNERS ★**

CAT. NO. FMT/A. Complete Unit in Cabinet with Magic-eye tuning. **16½ Gns.**  
Or on Credit Terms. *Packing and carriage 12/6.*

CAT. NO. FMT/B. Chassis only excluding magic-eye. Unboxed, 11½in. long x 5½in. overall depth x 4in. high. **CASH £13.15.0**  
*Packing and carriage 12/6.*

★ **LOUDSPEAKERS, GRAM, AMPLIFIERS, TAPE-RECORDER** equipment, etc., available at keenest prices. Send for large illustrated Catalogue.

**ALL FULLY GUARANTEED.** Generous extended credit terms on orders exceeding £15. Dealers supplied at full discounts.

All enquiries (excluding Northern Area) to:

Northern enquiries only (not Scotland & N. Ireland) to:

**DOMESTIC**

**MAYLIT LTD**

**DIRECT SALES LTD.**

90 JUDD ST., LONDON, W.C.1. TER. 9876

**3 MARLBOROUGH RD., ALTRINCHAM, CHESHIRE**

Telephone enquiries: ALTRINCHAM 4045

# About these Hi-g heads . . .

11 Carr Street,  
Cougee,  
Sydney,  
Australia.

Dear Sirs,

"- will track with ease all present day records". So reads your ad. for the new Hi-g Heads. "We will soon see about that", I said. The first test for this new L.P. Head was Decca's Brahms Fourth - always very difficult to handle I found on the old head. The shock I received was enough to put me to bed for a month - where was all that distortion? Where was all that groove jumping? Having recovered my strength and secretly suspecting it was just a fluke, I tried the Swan Lake - also another jumper - and then in a determined effort to prove you wrong, on went the Symphonie Fantastique and Rite of Spring.

At this stage the neighbours and family were seriously alarmed at sundry cries issuing from my room - they need not have worried - they were cries of pure joy. I had seriously considered installing expensive magnetic Pick-ups - of which I knew very little - but this will obviously be quite pointless now.

"- will track with ease all present day records" to which I say, "blessed be the name of Acos Hi-g"


Yours with relief,  
(Sgd ) Cliff Davidson.
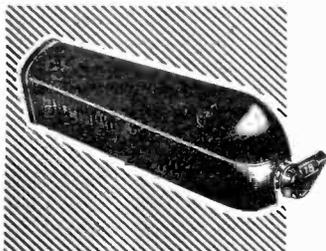
## Over to you, Mr. Davidson



.. that is what Mr. Davidson has written — and we didn't go to Australia to prompt him! His letter sums up what many others have expressed. It really does pay to use ACOS Hi-g pick-ups — both from the point of view of reproduction and of longer record life.

**FREE** The subject of Hi-g cannot be adequately explained in an advertisement, so we have produced an interesting booklet— "The ABC of Hi-g". May we send you a copy?



*always well ahead*

ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.

**COSMOCQRD LTD., Eleanor Cross Road, Waltham Cross, Herts.**

Telephone: Waltham Cross 5206

# PRACTICAL WIRELESS

EVERY MONTH  
VOL. XXXII, No. 600, DEC., 1956

EDITOR: F. J. CAMM

24th YEAR  
OF ISSUE

COMMENTS OF THE MONTH

BY THE EDITOR

Editorial and Advertisement Offices: "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363. Telegrams: Newnes, Rand, London. Registered at the G.P.O. for transmission by Canadian Magazine Post.

## Car Radio

THE demand for car radio receivers continues to increase and the number of cars now fitted with them is 300,000.

Great interest was shown in the car radio receivers exhibited at the Radio Show. We still think, however, that there is considerable room for improvement, for in spite of careful suppression of electrical apparatus on the car itself, interference from trams, electrical railways and other public transport is still severe. Although the Government has made a move towards the compulsory suppression of domestic electrical apparatus causing interference, it has left the major causes of it alone.

### V.H.F.

SINCE Wrotham opened in May, 1955, no fewer than 450,000 V.H.F. sets have been sold and the demand increases daily. There can be no doubt that this is the answer to interference-free reception of very high quality, and in the course of a few years the system must inevitably oust the older one.

### RADIO FILM SHOW

WE recently witnessed some excellent films dealing with transistors, valves, and cathode-ray tubes and their methods of manufacture. These films were so interesting that we made the suggestion to the producers that they should be shown to a wider audience, and, accordingly, the films are to be shown at the Caxton Hall (Great Hall Site) on Thursday, February 21st, 1957. Admission will be free, but by ticket. There will be an interval for refreshments. Readers wishing to attend this film show should send in requests for tickets immediately. Address your letters to "Film Show," PRACTICAL WIRELESS, address as on this page. The meeting will commence promptly at 8 o'clock in the evening.

There is bound to be a large demand for

seats, and accommodation is limited. Please, therefore, apply early.

### BLUEPRINTS—PRICE INCREASE

OWING to a rise in cost of producing blueprints, we are compelled, as from this issue, to increase the price of each by 6d. This is the first price increase since our Blueprint Service was inaugurated over 20 years ago. We have deferred increasing the price until rising costs left us with no alternative.

### BINDERS FOR VOL. 31


ON page 689 of this issue we give details of the new arrangements for binding this journal. We are supplying a loose-leaved binder in which readers can insert their copies month by month, without having to wait for the completion of the volume before they can have them bound in the ordinary

way. When the volume is completed the index can, of course, be inserted. This method will prevent copies becoming mutilated or misplaced. The covers are in black cloth, lettered in gold, and are grease- and water-proof.

Volume 32 will be completed with our issue dated February, 1957, as owing to the printing strike we did not publish two issues. Indexes will, of course, be available at 1s. 3d.
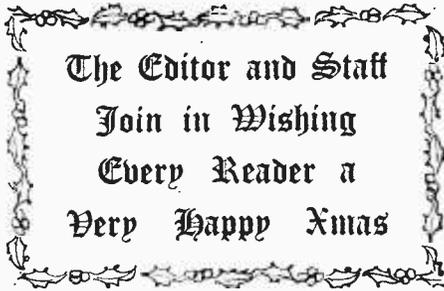
### TWO NEW HANDBOOKS

TWO new handbooks have recently been published from the offices of this journal: "The Home Electrician" (206 pp., 147 illustrations) deals with the installation, overhaul and repair of all domestic electrical apparatus. It costs 12s. 6d., or 13s. 2d. by post. "The Elements of Mechanics and Mechanisms" (432 pp., 481 illustrations) deals with the natural forces, laws of motion, thermodynamics, hydraulics, etc., and gives hundreds of examples of particular mechanisms. It costs 30s., or 31s. 3d. by post.—F. J. C.



The Editor and Staff  
Join in Wishing  
Every Reader a  
Very Happy Xmas

OUR NEXT ISSUE, DATED JANUARY, 1957, WILL BE PUBLISHED ON DECEMBER 7th

# Round the World of Wireless



By "QUESTOR"

## Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of August, 1956, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London Postal	1,291,963
Home Counties	1,288,706
Midland	1,001,448
North Eastern	1,303,831
North Western	992,843
South Western	819,041
Wales and Border Counties	514,358
Total England and Wales	7,212,190
Scotland	927,197
Northern Ireland	205,757
Grand Total	8,345,144

## New British Standards.

THE following new Standards are announced:

Thin vulcanised fibre sheets (including leatheroid), for electrical purposes (B.S. 2768 : 1956).

Basic characteristics of radio service selection and intercommunication systems for civil aircraft (B.S. R.2 : 1956).

Copies of these British Standards may be obtained from the Sales Branch, British Standards Institution, 2, Park Street, London, W.1, price 3s.

## F. R. W. Stafford Resigns

F. R. W. STAFFORD, M.I.E.E., has resigned from Belling and Lee, Ltd., where he has served for many years as technical manager, to become a consulting radio and electronic engineer on his own account.

Mr. Stafford, who is well known to the technical Press for his many contributions on aerials and interference suppression, has been intimately associated with the technical side of the industry for 33 years. His work has included domestic radio, telecommunications, radar and general applications of electronics.

He was the originator of G9AED, the first U.K. Band III pilot television transmitter.

Mr. B. H. Douthwaite, A.M.I.E.E., has joined Belling and Lee, Ltd., with effect from October

1st last, taking up the appointment as administrative head of the research and development activities of the company.

## V.H.F. in the West

THE BBC's Very High Frequency sound broadcasting station at North Hessary Tor, South Devon, has now been brought into service and transmits the West of England Home Service on 92.5 Mc/s; the Light Programme on 88.1 Mc/s and the Third Programme on 90.3 Mc/s, each with an effective radiated power of 60 kW. The transmissions are horizontally polarised. This new station is on the same site as the BBC's North Hessary Tor Television Station.

The V.H.F. service will be further extended in the West Country when the installation of additional transmitters is completed later at the BBC's V.H.F. station at Wenvoe, near Cardiff. The Wenvoe station, which at present transmits the Welsh Home Service, will then transmit in addition the

West of England Home Service and the Light Programme and will provide good reception in North Devon, Somerset, and parts of Dorset, Wiltshire and Gloucestershire.

## R.N.V.R. (Wireless) Reserve

YOUNG men who join the Royal Naval Volunteer (Wireless) Reserve may, when qualified, be issued by the Admiralty with a complete radio transmitter and receiver, together with a G.P.O. Transmitting Licence. This equipment can be used in their own homes, on Naval wavelengths, to enable the volunteers to keep in practice by communicating with other naval units. One of the radio stations issued under this system was the main feature of an exhibition of hobbies recently held at Cheltenham Town Hall.

## Radio Aids British Harvest

RADIO is speeding an important part of Britain's 1956 harvest. In the fields of Yorkshire and Lincolnshire harvesters are speaking over two-way short-wave radio, keeping in touch with a central control point and calling in men, machines and transport as required.

This new development is being



R.N.V.R. Telegraphist E. Fowles seen explaining the working of one of the Admiralty issued radio stations to possible R.N.V.R. recruits at the hobbies exhibition at Cheltenham. Young men who qualify before National Service are guaranteed entrance to the Navy when called up.

used by Batchelors Peas, Ltd., now at the peak of their garden pea harvesting season. The crops from many thousands of acres have to be brought in within six short weeks.

Lt.-Col. Maurice W. Batchelor, chairman of the company, said, "We have installed two-way radio in our agricultural representatives' cars and fitted it at our vining stations. A control office has been set up at headquarters in Sheffield.

"The peas are separated from the pods mechanically at the vining stations, and when a particular field is ready for cutting our fieldman radios the station, warning it of the variety and quantity of the crop to expect."

#### Servicing Examination Results

THE Radio Trades Examination Board and the City and Guilds of London Institute have now published the results of the Radio and Television Servicing Certificate Examinations for 1956.

Entries for both these examinations showed an increase over the figures for 1955, particularly in the Radio Servicing Certificate Examination, for which 822 entries were received, representing an increase of 55 per cent.

The number of successful candidates in the Radio Servicing Certificate Examination was 322. In addition, 185 candidates were referred in the practical test. In the Television Servicing Certificate Examination, 60 candidates were successful and 51 were referred in the practical test.

The next Radio Servicing Certificate Examination will be held on 7th, 9th and 18th May.

The next Television Servicing Certificate Examination will be held on 13th and 15th May and 22nd June.

#### Scottish Radio Show

THE Radio Industry Council has announced that the Scottish Radio and Television Exhibition will be held at Kelvin Hall, Glasgow, from May 22nd to June 1st, 1957.

The exhibition will be the first to be organised by the radio manufacturers since television began in Scotland and will precede by a few months the opening of the first Scottish commercial television station.

The only previous exhibitions held in Scotland by the radio manufacturers were at Kelvin Hall in 1933, 1934 and 1935. The

Scottish Radio Retailers' Association, however, have organised two very successful exhibitions since the war at St. Andrew's Hall, Glasgow.

#### BBC Presents Scholarships

THE BBC are presenting one or two research scholarships each year, valued at £385 per annum, to

University graduates in electrical engineering or physics who obtain good honours degrees, giving them the opportunity to work for a higher degree at any University in the United Kingdom, not necessarily at the one where they graduated. The scholarships are for two years in the first instance with the possibility of extension in suitable cases, if necessary. The scholarships are limited to male British subjects normally resident in the United Kingdom. The only condition applying to the subject for research is that it must be in those fields of telecommunications or physics which have an application to sound or television broadcasting.

The Corporation has given one research scholarship only this year and that was to Mr. P. C. J. Hill, who graduated at Birmingham University with first-class honours in electrical engineering. Mr. Hill will conduct his researches in the Department of Electrical Engineering at the Imperial College of Science and Technology, under the supervision of Dr. D. Gabor.

#### Weather by Phone

WITH reference to the illustration published on page 445 of our September issue, we are asked to point out that the number to dial for the weather reports is WEA 2211.

#### Ear Radio

IT is reported from America that a transistor radio has been produced small enough to be worn in the ear, and so cheap to produce that they can be discarded in three or four weeks when the battery is exhausted. Mr. Glen Schmidt, of the company making these radio sets, said they would cost just over



This Marconi engineer is standing on the site of a V.H.F. multichannel radio station at Kuh-i-Sefid, 16 miles from Arak in Iran. Not far away the temperature can exceed 120 deg. F. in the shade. In all, 84 Marconi multi-channel equipments Type HM.181 together with a considerable quantity of telephone carrier equipment are being installed along the National Iranian Oil Company's new 60-mile oil pipe-line from Abadan to Teheran. This picture was taken when the survey team traversed the route selecting suitable sites. Kuh-i-Sefid ("The White Mountain") is 10,000ft. in height. The site shown (8,000ft.) is immediately above a valley which is often rendered impassable by snow, and was chosen so as to enable the radio signals to be shot along and through the valley in one hop.

9s., and each would be tuned to a single station. They would be colour-coded to indicate to which station they were tuned.

#### BBC's New Norwich H.Q.

THE BBC has acquired premises known as St. Catherine's Close, All Saints' Green, Norwich, for use as a sub-regional studio centre.

# A Versatile Valve Voltmeter


ANOTHER INTERESTING SERVICING AID AND ACCESSORY FOR THE EXPERIMENTER'S WORKSHOP

By J. Hillman

**T**HIS is a combination instrument which can measure ohms, D.C. volts or A.C. volts, and additionally is particularly useful for measuring grid voltage, high resistances, as well as insulation testing. Its input resistance on D.C. is 60 M $\Omega$ . The instrument is self-contained and can be used to measure from 0.05 ohms up to 750 megohms on its resistance range. On the voltage ranges from 0.1 volt up to 1,200 volts the meter is 20 M $\Omega$  per volt.

Provision is made for changing the polarity of the output leads without removing them from the testing points.

The scale of the meter may seem a little unusual, because it is marked 0-3 and 0-15, but the writer is of the opinion that these markings are more useful than the usual commercial ones of multiples of 10. The majority of voltages requiring to be measured in servicing sets occur in the ranges 1.5 to 2.5, 100 to 150, and 250 to 300, and with a meter scale of 3, 150 and 300 the readings occur in that part of the scale where the meter is more accurate. With most com-

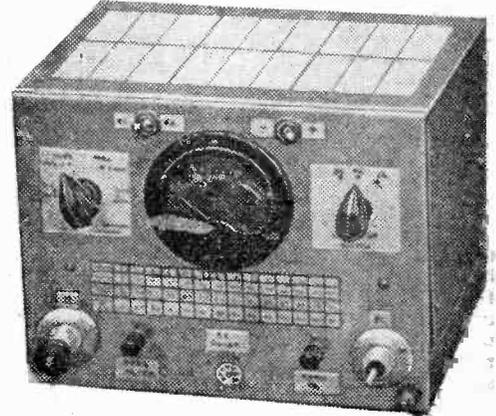

mercial instruments these readings come either half way or right at the very end of the scale.

If the reader does not desire the above scales, but prefers the commercial type scale, no alteration is needed to the instrument as the scale can be 0-2 and multiples of this, i.e., 2, 10, 20, 100, 200, 400. The initial setting up is the same.

For those who wish to use the scale I recommend

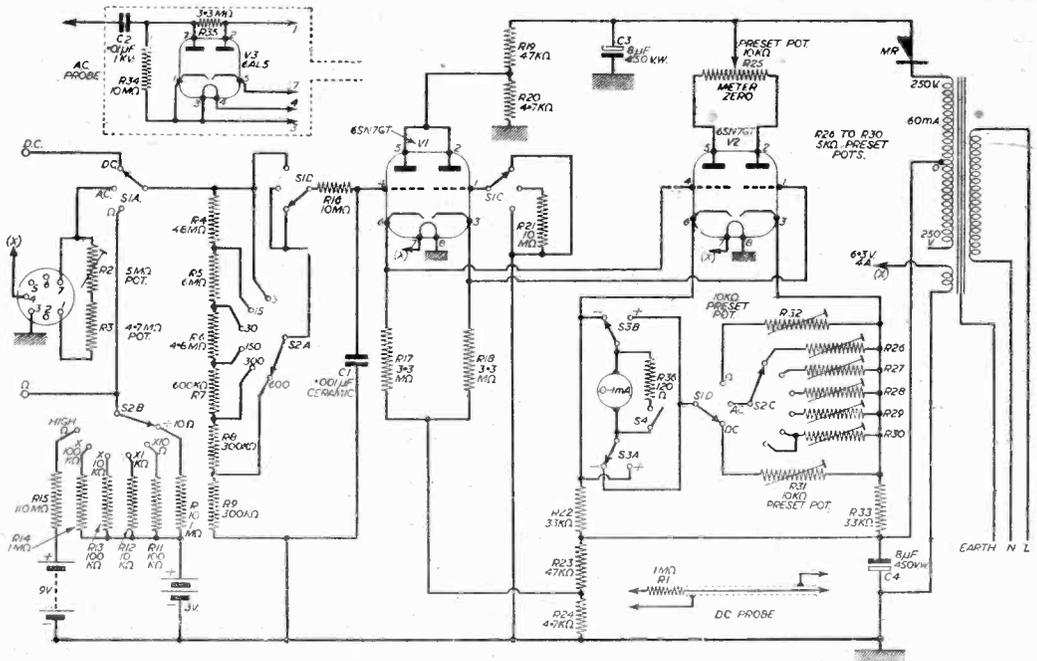



Fig. 1.—Theoretical circuit of the Meter. R and C details are given and the remaining components are listed on page 664.



The 3-volt battery is a twin cell, and connection is made to it by flexible leads and crocodile clips, whilst the 9 volt battery is a grid bias battery, using flexible leads and wander plugs to make connections to it.

The mains transformer is mounted on top of the chassis and the heater wiring run along the top of the

remaining end to take a small grommet as in Fig. 8. Into this a piece of 4 B.A. threaded rod is secured by means of nuts either side of it, and the end of the rod is filed to a point, a piece of insulated sleeving threaded over it so as to leave just the tip bare. A lead is soldered to the end of the rod and goes to C2. The valve, valveholder and R34, R35 and C2 are all wrapped in polythene strip and pushed inside the condenser case and flexible leads (four coloured ones) are brought out and twisted together for about 3ft. and termin-

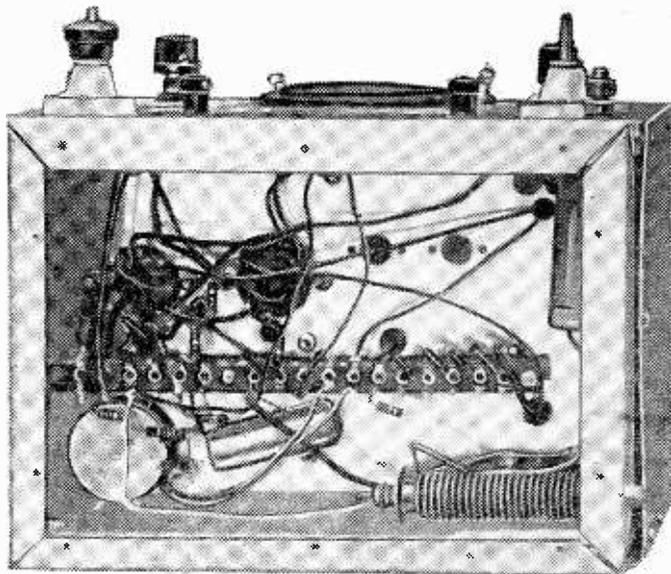


*A view of the underside of chassis.*

chassis to a grommet at V1 valveholder. The insulated terminal of the stand-off bracket is made from an accumulator terminal with the brass stud cut off, and a hole drilled and tapped 2 B.A.

#### A.C. Probe

The A.C. probe is made from an old electrolytic condenser case. One end (the terminal end) is sawn off and the inside removed and a hole drilled in the

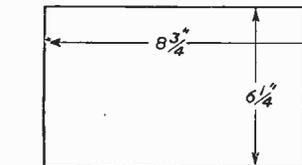

*Fig. 6.—Bottom cover plate.*

ated in a B7G plug. If 7/33 flex is used quite a light lead results.

#### D.C. Probe

The D.C. probe consists of a length of coaxial cable as in Fig. 9, one end terminated in a porcelain insulator to which is bolted a length of 4 B.A. rod filed to a point at one end, and with sleeving over it and the other end terminated in two spade terminals. One point to note is that R1 is fitted inside the porcelain insulator of the D.C. probe, and its purpose is to minimise any effect on the external circuit under test, so that no matter what range is used there is always 1 megohm resistance between the meter and the external circuit.


R21 must be efficiently earthed and this is done by connecting it to chassis at a convenient point to the switch, and also by running a direct earth wire from it to the heater earth. This is important, as on A.C. it may cause erratic readings if not properly earthed.

No on-off switch is fitted, as the mains lead can then be kept well away from the front panel, but one could easily be fitted if required.

The S2 switch should have widely spaced contacts, the one used by the writer was made up from two ex-government 2-P six-way wafer switches; if,

#### MISCELLANEOUS COMPONENTS

- Meter 0-1 mA. 2 1/2 in.
- 2 Int. octal valveholders.
- 2 B7G valveholders.
- 1 B7G plug.
- 1 SPST toggle switch.
- 1 DPDT toggle switch.
- 1 3P 6 w. w/c switch.
- 1 4P 3 w. w/c switch.
- 2 stand-off insulators.
- 1 OBA Earth terminal.
- 2 spade terminals.
- 4 crocodile clips.
- 1 metal rectifier 250 v. 60 mA.
- 1 mains transformer, 250-0-250 v. 60 mA, 6.3 v. 4 a.
- 2 wander plugs.
- 1 Yard coaxial cable.
- Rubber grommets as required.
- Connecting wire as required.
- 7/33 PVC flex coloured as required.
- 4 BA and 6 BA nuts, bolts and washers as required.
- 2 pointer knobs.
- Self-tapping screws as required.
- 1 tag strip.
- 3-core flexible mains lead.

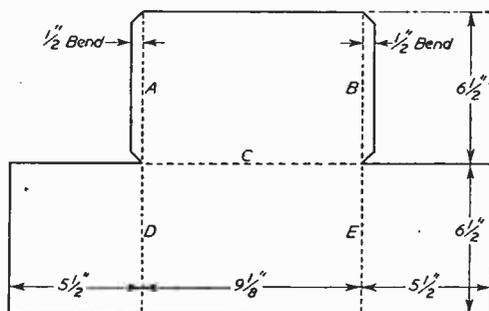

*Fig. 5.—Top cover details.*

however, a ceramic switch is available this will be better still.

**Marking**

The panel should be marked as in Fig. 10, using pieces of paper cemented to the panel and marked in

and then with the D.C. probe connected, set S2 to three volts, S1 to D.C., S3 to + and adjust zero meter control to bring pointer to zero. Now connect the end of D.C. probe to a standard voltage. The more accurate the voltage the more accurate will the meter be. The standard used by the writer was a 2 volt accumulator charged and allowed to stand for a day, then its reading checked on a 1,000Ω per volt meter was 2.2 volts. R31 D.C. on the potentiometer bracket is now set to give this reading on the meter; the probe is next disconnected from the battery and the meter zero used again to zero the pointer, and this procedure is carried on until no further change in reading is noted. The rest of the ranges on D.C. should now be checked and should be found correct.

The polarity reversing switch S3 should now be checked, and there should be no difference between the readings in the positive and negative positions. Should the readings differ try changing the 6SN7 valves. Meter doubling switch S4 can now be adjusted by trial and error to give twice scale reading in ×2 position.

For A.C., set S1 to A.C., S3 to A.C., S2 to 15 volt range, and use balancing potentiometer R2 to get meter to zero and to give R25 its range to zero meter. For 3-volt range the scale would have to be calibrated separately as the scale is not linear, and as the writer is of the opinion that this range is of little use in practical servicing the first range to be cali-

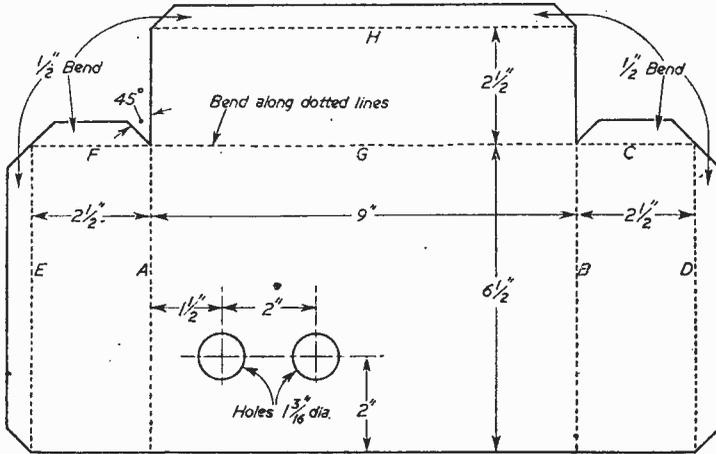


Fig. 3.—Chassis bending and drilling data.

with Indian ink, and then smeared over with cellulose cement when dry. The potentiometer bracket is also marked as in Fig. 11. The resistance chart is shown in Fig. 10A and this is the average readings; a more accurate and detailed chart is cemented on the top cover for more exact readings, and each range can then be shown.

**Calibration**

First allow the meter to warm up for an hour or so

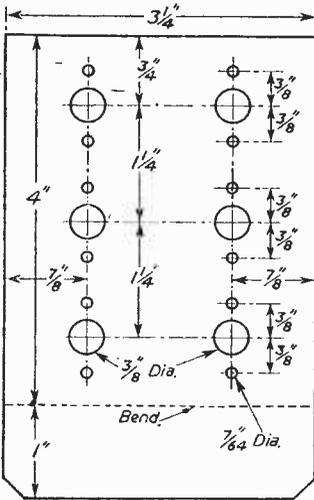


Fig. 7.—Drilling and bending details of the potentiometer bracket.



Fig. 8.—The A.C. probe.

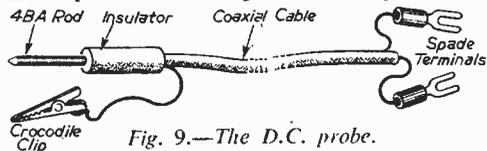


Fig. 9.—The D.C. probe.

brated is the 15-volt one. By using a 6.3 volt mains transformer connect A.C. probe to its terminals and adjust R26 to give correct reading on scale and using meter zero each time until no difference in off and on readings is obtained. Similarly with 30 volt use R27; 150 volts use R28; 300 volts use R29; 600-volts use R30; using two 6.3 volt heater transformers phased to give 13 volts for the 30 volt range. Use a battery eliminator transformer 150-0-150 for the rest of the ranges, and use the mains as a check voltage on the 300-volt and 600-volt range.


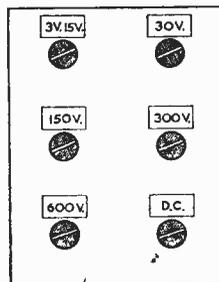


Fig. 11.—The potentiometer bracket.

For resistance calibration set S1 to Ω, S2 to ÷10Ω range, S3 to Ω and zero ohms at one end of scale, then switch S1 to A.C. and zero meter and S1 to Ω and zero ohms until meter

reads correctly zero at each end of scale. Now switch to A.C. to prevent running battery down, whilst making preparations for calibration. One point to note is that the zero ohms adjuster adjusts the scale at maximum and this is at the maximum reading of the meter unlike ordinary ohm meters. For the first range use a large battery charging one ohm variable resistor so that by counting the turns on it the one ohm can be sub-divided into decimal fractions of an ohm. Connect the resistor with fairly heavy flexible leads and switch S1 from A.C. to ohms each time a reading is taken, and then allow a minute or so for the battery to recover before proceeding with the calibration. Do not keep the switch S1 in the ohms position longer than is necessary to take the reading, as at this low resistance a heavy current tends to flow. For the other ranges use the zero ohms R32 in conjunction with the zero meter for each range and use  $\pm 10$  per cent. resistors to calibrate the meter, noting the readings for each division on the scale. By using two or more resistors in parallel the

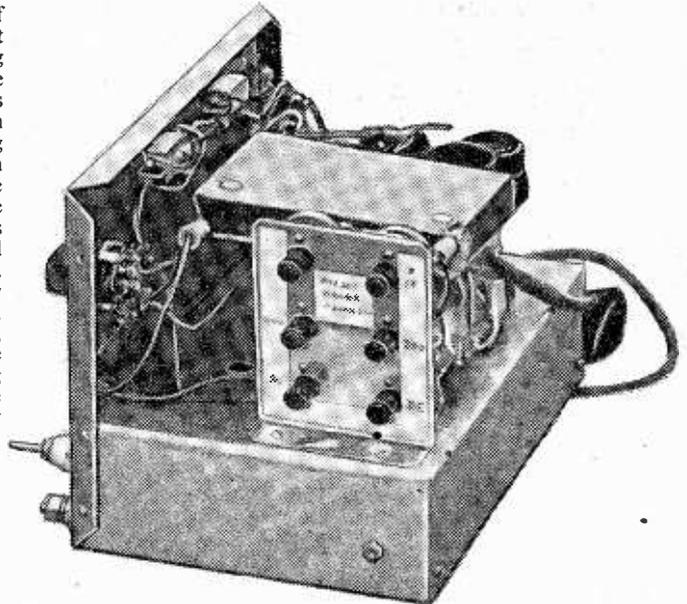

Three-quarter rear view of the instrument.

Range ... ..	1	2	3	4	5	6	7	8	9	10	11	12	13	14
$\Omega$ ... ..	1	2	5	8	10	15	20	30	40	50	60	125	150	270
All others ...	.82	1.8	2.7	3.3	4.7	6.8	8.2	12	15	18	27	33	56	100
High $\Omega$ M $\Omega$ ...	2.7	6.8	8.2	12	15	25	32	40	50	68	90	100	200	370

Fig. 10A.—The Resistance Chart.

lower readings can be calibrated, e.g., for 5 ohms use two 10 ohms resistors in parallel, and for 4 ohms use three 12 ohm resistors in parallel. The normal 10 per cent. range extends to 22 M $\Omega$  and by using a

number of these in series the range can be calibrated up to about 264 M $\Omega$  which is when 12 resistors are used in series. For higher calibration points 50 M $\Omega$  resistors may be used if available. The writer

used 5-watt carbon ex-government ones, which are not very accurate, but then accuracy is not essential at these high values as this range is used more for insulation testing. As a substitute for high resistances a piece of soft wood can be used which can be measured on the scale already calibrated and then resistors added in series to calibrate the higher readings.

One last point regarding the wiring to the mains transformer; use three-core flex for the mains lead and put the earth wire to the screen of the mains transformer, but do not connect this to the chassis, as otherwise when checking voltages above earth potential the lead will short the H.T. to earth in the circuit under test.

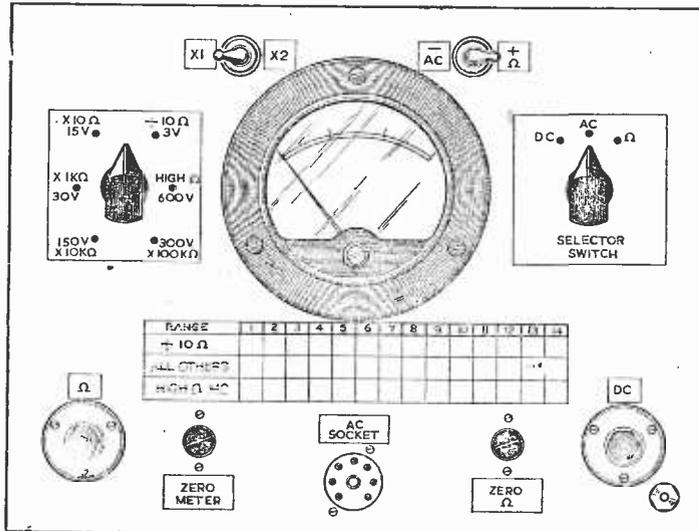


Fig. 10.—Details of the front panel.

**A NEW HANDBOOK**  
 The Home Electrician By F. J. Camm  
 206 pages, 147 illustrations 12/6, or  
 13/- by Post from  
 Book Dept., George Newnes Ltd., Tower  
 House, Southampton St., Strand, W.C.2

# A Beginner's SHORT-WAVE THREE

AN A.C.-OPERATED  
SHORT-WAVE RECEIVER

By

V. M. Meadows

(Concluded from  
page 614, Novem-  
ber issue.)



IT should be noted that the variable condenser CA should *not* be earthed to the panel or chassis at any point: if it were, then it is obvious that all the signals derived from the aerial would simply go straight to earth. The condenser should be mounted to the panel and chassis front drop by means of two insulated washers, these being of paxolin, and a short length of tubing, either of the same material or of rubber.

Before fitting the condenser into position ensure that the hole into which it is to be fitted is larger than that normally required for the condenser bush alone. Then, placing one of the paxolin washers over the bush, place the condenser into position. From the front of the panel slide over the condenser bush the short length of paxolin or rubber tube, following this with the remaining insulated washer and the normal fixing nut.

### Wiring the Circuit

It is best to commence the wiring by connecting up the power supply section of the circuit. In this manner the heater wiring may be so carried out that all the heater leads are placed near the chassis deck. Assuming that the specified components are being used (see component list) wiring may now commence, but before doing so a few words about this may not come amiss, especially to the beginner reader about to construct his first receiver.

It is a good plan for readers building this receiver to use various colours of PVC wire for differing portions of the circuit, this being of considerable help when tracing possible faults if and when they arise. The following colours have been used in the prototype: Red for H.T. +; White for the tuned circuits; Black for earthed wiring and Green for the audio connections.

All the individual components should be suspended with their respective wires, but, at the same time, these should be reasonably taut and securely anchored to the valve tags, etc., before soldering. The use of insulated sleeving over the component wiring, after having been cut to the required length, especially where they are carrying H.T. potential, is to be

thoroughly recommended. In this manner H.T. shorts to the chassis, etc., are avoided.

The component wire ends, when cut to the correct length, should be thoroughly tinned *before* soldering into position, this being extremely important if dry joints and consequently bad connections are to be avoided.

### Power Supply (V3)

Having mounted the mains transformer in such a manner that the two thick green wires protrude through the grommet nearest the rear chassis wall, looking at the underside of the chassis, solder one of these green covered wires to the earthed tag of the five-way tag strip mounted above the rectifier valve-holder. Solder the other green wire to tag 1 of V1. Before soldering these two wires, however, the enamel covering over the copper wire should first of all be removed by scraping with a knife or old razor blade, the bare copper then being thoroughly tinned before finally securing as outlined above.

These two wires are the 6.3 volt heater leads, and reference to the circuit diagram of Fig. 1 will enable a clearer understanding of the mains transformer colour code as used in the Ellison type MT162.

The thin blue and red wires coming through the same grommet as the green heater leads should next be cut short, the ends being separately bound with insulation tape so that no possible contact with each other or the chassis can possibly occur. These

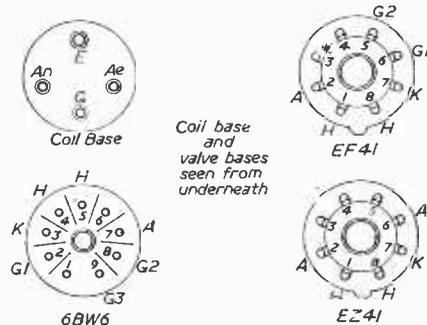


Fig. 7.—Details of valve base connections.

should then be tucked away neatly between the L.F. choke and the chassis wall.

The thin green wire is next soldered to the five-way tag strip, that tag nearest the rear chassis wall being used for this purpose. The thin black wire should now be soldered to the next tag of the same strip.

Proceeding now with the wires coming through the other grommet, solder the white and the yellow wires to the centre tag of the five-way tag strip, this particular tag being that bolted to the chassis wall and therefore at earth potential. These two wires should be brought along between the L.F. choke and the chassis side wall.

Next, dealing with the two thick systoflex-covered red wires, cut these short and securely tape them with insulation tape separately. Having completed this, tuck them away between the L.F. choke and the chassis wall. These are the 5-volt heater leads, not required with the particular type of rectifier that we are using.

The two thin red PVC covered wires should now be brought along between the L.F. choke and the chassis wall, one being soldered to tag 6 of V3 valveholder and the other to tag 2 of the same valve. (See circuit diagram.)

The next step is to bring in the mains lead. A suitable length of twin flex should be fed through the grommet on the rear wall of the chassis. Bare both ends of this flex and solder these to the switch tags on the rear of the potentiometer, one to each tag, of

course. At a point near the five-way tag strip, cut one of these leads only and bare both severed ends. Solder one of these to the same tag already holding the thin green wire from the mains transformer, and the other end to that tag already containing the thin black wire from the transformer. At the other end of the mains lead fit a suitable mains plug.

Dealing next with the valveholder of V3, solder tag 1 to the central metal spigot and join this to the earthed tag previously fitted under one of the holding bolts. Next, with a suitable length of black PVC wire, join tag 8 of V3 to tag 4 of V2, taking the connecting wire as close to the chassis deck as possible and along the chassis rear wall. From tag 7 of V3 take a short length of red-covered PVC wire to the tag of C9, and from there to one tag of the L.F. choke (it does not matter which one). From the other tag of the L.F. choke, connect to the tag of C8, and from there to a free tag of the strip situated on the rear chassis wall. From this latter tag take a short length of PVC wire to one side of the speaker transformer primary winding.

This completes the wiring of the power stage. Note should be taken of the fact that the five-way tag strip mounted above the rectifier valveholder is of the type having the central tag *only* bolted to the chassis. If another type should be used the main point to be noted is that only the white, yellow and one thick green wire coming from the mains transformer should

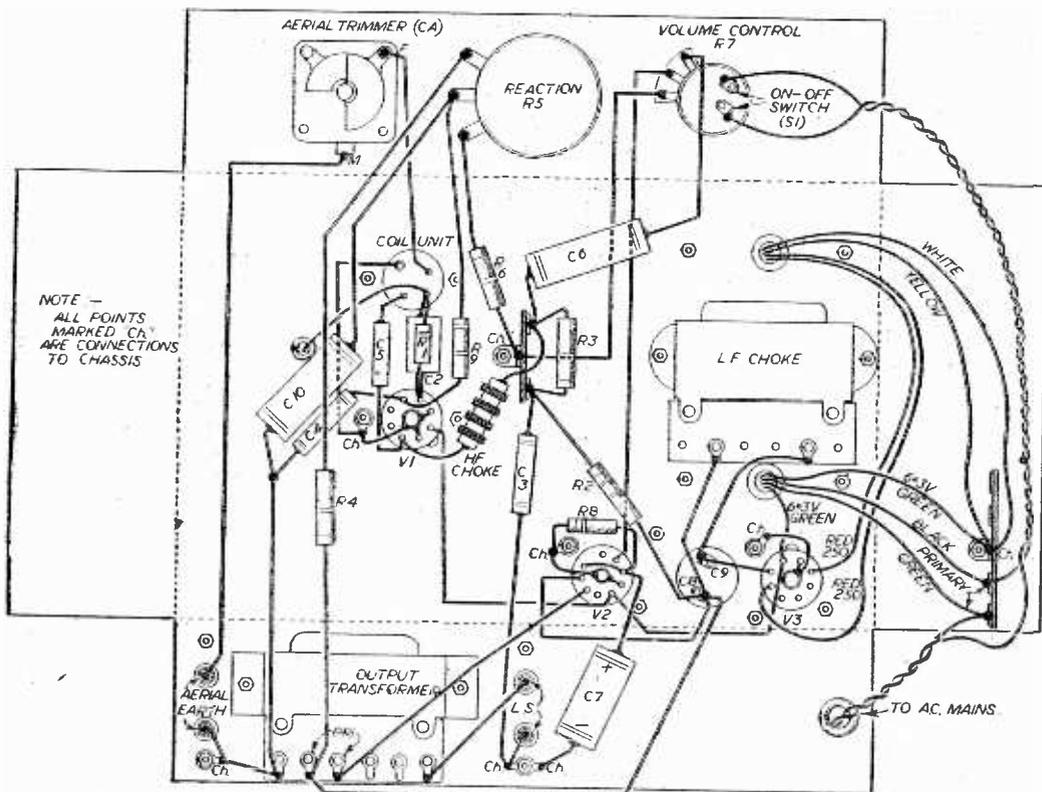


Fig. 6.—Below chassis wiring details.

be earthed. All the others should be soldered to free tags, i.e., not connected to the chassis in any way.

### Output Stage

Dealing with this stage next, this being the easiest way in which to wire the receiver, connect tag 4 of V2 to tag 1 of V1. As this is the heater lead, position the PVC covered wire as closely as possible to the chassis deck, taking the wire midway between the two respective valveholders. By means of a short length of bare wire, connect tag 5 of the valveholder (V2) both to the centre metal spigot of the valveholder and to the earthed solder tag fitted under one of the fixing nuts.

From tag 3 of V2 solder one end of R8, the other end of which is connected to the earthed solder tag. To fit C7, first solder the negative end to the solder tag fitted on the holding bolt of the speaker output terminal strip contained on the rear chassis wall. (Note: The negative end is coloured black.) Having done this, solder a short length of bare wire to the positive end of the condenser and connect the other end of this wire to the cathode of V2, i.e., tag 3. Now join tags 3 and 9 of the valveholder by means of a short length of PVC wire.

From tag 8 connect a length of wire to the connecting tag of C8. From tag 7 join to the other side of the output transformer primary winding. Dealing with the output transformer secondary winding, connect one end to the earthed tag contained on the aerial/earth paxolin strip and the remaining end to one of the tags of the speaker output strip. The remaining free tag of this latter strip should now be soldered to the earthed tag fitted under this strip.

Dealing next with the grid circuit, connect tag 2 of V2 direct to the centre tag of the potentiometer R7. The left-hand tag of R7, looking at the component from the rear, should be connected to the earthed fixing tag of the three-way paxolin strip shown mounted in mid-chassis. The right-hand tag of R7 should next be wired to the negative end of C6, the other end of which should be connected to the tag of the three-way tag strip just mentioned. The tag nearest the front of the chassis is best for this last connection. To this same tag connect one end of R3 and the R.F. choke. The other end of R3 should now be soldered to the third tag of the strip, i.e., nearest the rear of the chassis. From this last mentioned tag connection should now be made to the positive end of C3, the other end of which is

next soldered to the earthed tag situated on the rear wall of the chassis. From the positive end of C3 join one end of R3, the other end of which is connected to the solder tag of C8.

This has now completed the output stage wiring and part of the detector circuit. Before proceeding farther, a careful check should be made, both with these instructions and with the circuit diagram of Fig. 1, to ensure that no possible errors in respect of the wiring exist.

### Detector Stage

This stage is the "heart" of the receiver, and careful attention to layout is essential if the maximum results are to be achieved. Constructors are urged carefully to study the under-chassis view of the receiver and obtain a clear idea of the layout before proceeding with the actual wiring of the circuit.

It is best to commence by wiring up the earthed portions of the valve and the associated components. Thus, with a length of bare wire, connect tags 8 and 7 of V1 to the central metal spigot of the valveholder, and from there connect this to the earthed tag fitted under one of the holding nuts of the valveholder itself. From this same earthed tag take a length of bare wire to the earth connection of the coil holder—this being that tag greater in diameter than the others.

Connect to tag 2 of V1 the free end of the R.F. choke and one end of C5, the other end of this latter component being now connected to the reaction winding tag of the coil holder (see inset to Fig. 1 or, where new coils are purchased, the leaflet enclosed). To tag 6 of V1 solder one end of C2 and R1. It is best to cut these to length and to solder the connecting wires together, at both ends, before finally

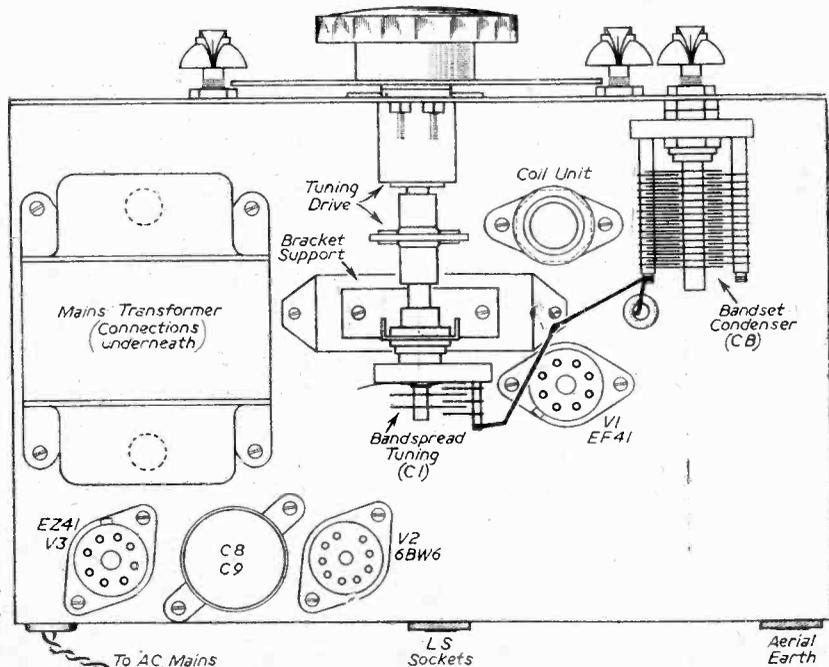


Fig. 5.—Above chassis wiring and layout details.

connecting them into circuit. The other ends of both C2 and R1 should then be connected to the grid winding tag of the coil holder. To tag 5 of V1 solder one end of R9 and C10 (positive end). The other end of R9 is then soldered to the centre tag of the potentiometer R5. The remaining end of C10 is next taken to the earthed side of the speaker transformer secondary winding.

To the right hand tag of R5, looking at the rear of the component, connect one end of the resistor R4, the other end of which is connected to the H.T. connection of the output transformer. To the centre tag of R5 add one end of C4 (positive), the negative end of which is soldered to the earthed side of the output transformer secondary winding. To the left-hand tag of R5 connect one end of R6, the other end of which is soldered to the earthed tag of the 3-way tag strip mounted on the chassis deck.

From the grid winding tag of the coil holder, connect a suitable length of PVC covered wire and, feeding this through the chassis via the rubber grommeted hole, connect the other end to C1. From this latter connection take a length of wire to CB, the bandspread condenser.

From the aerial winding connection of the coil holder connect a length of wire to the variable condenser CA, the aerial control; solder this wire to the static plate connection. From the other side of this condenser, i.e., the rotor or moving vanes connection, take a length of wire direct to the aerial input solder tag mounted on the rear wall of the chassis. The earth socket tag associated with the aerial input socket should now be soldered both to the earthed solder tag fitted under one of the holding nuts attached to the aerial/earth paxolin strip and also to the earthed end of the output transformer secondary winding.

The wiring of the receiver is now complete and, having again made a check of the instructions, together with Fig. 1, the constructor may proceed with testing the receiver before inserting the valves V1 and V2.

### Testing the Receiver

In order to test the receiver, insert V3—the rectifier—and connect the power lead to the mains. Switch on and read the H.T. voltage at the junction of C8 and the L.F. choke. This should be around 320 volts depending on which make of meter is used—assuming, of course, that one is to hand. Having done this, insert V1 and V2, the speaker, aerial and earth. The various voltage readings which one would expect are then given in Fig. 1. The conditions under which these voltages were obtained have already been given.

### Operating the Receiver

Having selected the coil appropriate to the range of frequencies over which it is desired to tune, rotate the Bandsset condenser until a signal is heard. Advance the reaction control until the point of oscillation is passed—heard as a rushing sound in the speaker—bring the control back until this oscillation just ceases and then adjust the aerial condenser for the maximum signal. The A.F. gain control will, of course, have to be at maximum setting in order to obtain a sufficient volume of audio signal. Generally speaking, once the aerial condenser CA has been set for best results with a particular coil no further

adjustment of this control will be necessary; each coil having its own setting so far as this condenser is concerned.

### The Finishing Touches

In order that the completed receiver may present a pleasing appearance, both to the owner and others, the front panel should be treated with a good coat of paint. That used in the prototype was black hard-gloss enamel paint which is readily available from the local branch of the popular stores.

The various control panels and wording are those available under the trade name "Panel-Signs"—available at most radio shops; those shown on the photographs are from Set No. 1.

### Conclusion

The receiver has been air tested over a period of some months and it has produced good results throughout that time. Comparatively simple to construct, it is a good receiver for the beginner or as a stand-by receiver for the more advanced.

## B.I.R.E. Premium Awards

THE Council of the British Institution of Radio Engineers has recently announced the award of Premiums for papers published in the Brit.I.R.E. Journal during 1955.

### The Clerk Maxwell Premium

(The senior Premium for the most outstanding paper in the Journal) to E. M. Bradley, B.Sc., and D. H. Pringle, Ph.D., for their paper on "The Theory and Design of Gas-discharge Microwave Attenuators." Dr. Pringle is, and Mr. Bradley was, with the Electronics Research Laboratory of Ferranti Ltd.

### The Heinrich Hertz Premium

To R. Filipowsky, Dr. Ing., for his paper on "Electrical Pulse Communication Systems." Dr. Filipowsky is at present with the Westinghouse Electric Corporation, Baltimore.

### The Louis Sterling Premium

To D. R. Coleman, D. Allanson and B. A. Horlock, for their paper on "The Development and Design of an Underwater Television Camera." Messrs. Coleman and Allanson are at present with Pye Ltd., and Mr. Horlock was formerly with that company.

### The Marconi Premium

To Sin-Pih Fan, M.S., Ph.D., for his paper on "The Magnetron Beam Switching Tube: its Operation and Circuit Design Criteria." Dr. Fan was formerly with the Burroughs Research Centre, Paoli, Pennsylvania, and has now returned to China.

### The Leslie McMichael Premium

To D. J. Fewings, B.Sc., and S. L. Fife, for their paper on "A Survey of Tuner Designs for Multi-channel Television Reception." Mr. Fewings is with Marconi's Wireless Telegraph Company, and Mr. Fife is with the English Electric Company.



# KT88

## A NEW AUDIO OUTPUT VALVE WITH AN ANODE DISSIPATION OF 35 WATTS



An addition to the well-ried and popular range of G.E.C. Audio Valves, of which the KT66 has set a standard in its class the world over, the new G.E.C. KT88 is now available to meet conditions of use requiring higher power.

### POINTS ABOUT THE KT88

**1** The KT88 is a beam pentode with aligned grids for maximum efficiency.

**2** 50 watts output is available from a pair connected in the ultra linear circuit with auto bias and an H.T. line voltage not exceeding 500.

**3** 100 watts output is available from a pair connected in the ultra linear circuit with fixed bias and an H.T. line voltage not exceeding 560.

**4** 25 watts output is available from a pair triode connected with auto bias and an H.T. line voltage not exceeding 500.

**5** The mutual conductance of the KT88 is 11 mA/V.

**6** An all glass ring seal replaces the conventional pinch seal giving increased strength, higher rating and reduced dimensions.

**7** The valve is mounted on an international octal base and has a heater rating of 6.3 volts., 1.8 amps.

*Full particulars of these valves can be obtained from the G.E.C. VALVE & ELECTRONICS DEPT.*

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2



AM FM GANG CONDENSER

## precision built components

AM/FM GANG CONDENSER Type L.E.A.F.

A.M. section C swing 532 pF

F.M. section 12 pF swing.

Robust construction and wide air gap in F.M. sections, to ensure stability.

Price 21/6

it's reliable . . . if it's made by Jackson

Write for fully illustrated catalogue



**JACKSON BROS.**  
**(LONDON) LIMITED**

KINGSWAY, WADDON, SURREY

Telephone : CROYDON 2754/5

Grams : WALFILCO SOUPHONE

LONDON

# RADIO COMPONENTS — RETURN-OF-POST SERVICE

Details of some of the items from our extensive stock of Radio and Television components are given below. All items are usually held in stock and all orders are normally dealt with on the day they are received.

## OSRAM 912 PLUS AMPLIFIER

INSTRUCTION MANUAL, 4/-. PRICE LIST Free.

RESISTORS. Lab. Kits. Main Amplifier. only 33/4. Includes the three potentiometers. Passive Unit, 6/9. Pre-amplifier, 14/6.

TCC CONDENSERS. Main Amplifier, 55/-. Passive Unit, 12/9. Pre-Amplifier, 18/9.

All resistors and condensers are available separately. Full details in list.

OUTPUT TRANSFORMERS. Partridge P3591A, 99/-. Gilson WO710, 52/6. Whiteley, 32/-.

MAINS TRANSFORMERS. Partridge H300/110 (P3591B), 75/-. Elstone MT912, 40/6. Whiteley, 78/-.

SMOOTHING CHOKES. Partridge C10/135, 33/6. Whiteley, 18/9.

SWITCHES. Specialist Switches. Main Amplifier, 14/ the pair. Passive Unit, 11/6. Pre-Amplifier, 10/6.

CHASSIS. Drilled. Whiteley, steel, gold finish, 34/8. Denco, plain aluminium, 14/6.

PANELS. Main Amplifier only. Tele-Radio, 14/3. Denco, 6/6. Drilled for Passive or Pre-Amp., Denco, 7/6.

VALVES. 2729, Osram, 24/4; alternative, 15/-. B309, Osram, 19/6; alternative, 10/-. N709, Osram, 16/- each; alternative, 1/28 each. U709, Osram, 11/10.

COMPONENTS by Bulgin, Belling Lee and all other items are always in stock. Full details are given in our free price list.

COMPLETE KITS. Main Amplifier only.

Kit A. Complete Kit with Partridge Transformers and Choke, Whiteley Chassis and new Osram Valves, £25.5.0.

Kit B. Complete Kit with Partridge Transformers and Choke, Denco Chassis and alternative valves, £21.17.0.

Kit C. Cheaper Kit with Elstone Mains Transformer, Gilson Output Transformer, Whiteley Choke, Denco Chassis and alternative valves, £19.17.0. Remember that these kits are really complete.

PASSIVE UNIT if required with the above kits, £2.13.0 extra.

PRE-AMPLIFIER if required with the above, £4.15.0 extra with Osram Valve or £4.6.0 extra with alternative valve.

G.E.C. METAL CONE SPEAKER, always in stock at £9.5.0.

CREDIT TERMS. Complete or part kits can be supplied on Credit Terms. Please state exact requirements and we will send a quotation.

## MULLARD 510 AMPLIFIER

INSTRUCTION MANUAL, 3/6. PRICE LIST Free.

RESISTORS. Lab. Kits. MA10/56. All resistors and potentiometers for the Main Amplifier only. R1-R39, 39/-. MA10/PA/B. All resistors and potentiometers for Main Amplifier, Pre-Amplifier Version B. R2-R22, R27-R29, R31-R54, 57/6. MA10/FAA for Pre-Amplifier Version A only. R31-R46, 16/10.

CONDENSERS. TCC Kits. Main Amplifier, 45/-. Our alternative Kit for Main Amplifier, 30/-. TCC Kits for Pre-Amplifiers, Version A, 15/-. Version B, 24/3.

CHASSIS. Denco. Aluminium ready drilled. Main Amplifier with base plate, 19/6. Pre-Amplifiers, Version A, 8/6. Version B, 12/6.

PRINTED PANELS. Denco. Main Amplifier, 6/6. Pre-Amplifiers, Version A, 1/6. Version B, 2/6.

OUTPUT TRANSFORMERS. Partridge P3667 (tapped for 6 k and 8 k load), 52/6. Elstone OT6 (6 k), 45/-. Elstone OT8 (8 k), 45/-. Ellison OP67 (8 k), 40/-. OP67A (6 k), 40/-. Gilson WO696A (8 k), 47/6. WO696B (6 k), 47/6.

MAINS TRANSFORMERS. Elstone MT/510 Main Amplifier only, 36/-. Elstone MT/510 for amplifier when Pre-Amplifier or FM Tuner are used, 42/6.

VALVES. EF86, Mullard, 24/4; alternative, 15/-. ECC83 Mullard, 19/6; alternative, 10/-. EL84 Mullard, 16/9; alternative, 12/6. E280 Mullard, 11/10. E281 Mullard, 11/10.

COMPONENTS by Bulgin, Belling Lee and all other items always in stock. Full details are given in our free list.

COMPLETE KITS. Main Amplifier only. Note—These kits include the MT/510 Mains Transformer. If the pre-amplifier or FM Tuner are to be used the MT/MU Transformer is required.

Elcon Plugs and Sockets will also be required and the price of these and the difference on the transformer must be added to the kit.

Kit A. Complete kit with TCC Condensers, Mullard Valves and Partridge Output Transformer, £16.6.0.

Kit B. As Kit A, but with alternative valves and condensers, £13.16.0.

Kit C. As Kit B, but with Ellison Output Transformer, £13.4.0.

PRE-AMPLIFIER KITS. Version A with Mullard Valve, £5.4.0. With Alternative valve, £4.15.0. Version B with Mullard Valve, £6.19.0; with alternative valve, £6.10.0.

PRINTED CIRCUIT ITEMS. All in stock.

Chassis. Special TCC Printed Circuit Panel, 22/6. Denco Metal Frame to support the TCC panel with small chassis for Power Unit, 15/-.

Condensers. TCC Special Kit, 45/-. Valve Holders. Special Printed Circuit type, 1/- each.

## RECORD CHANGERS

BSR MONARCH. UA8. FOUR SPEED. £7.19.6d. Credit Terms. Deposit £13.10d. and seven monthly payments of £13.8d. Other makes available at special prices. Send for details.

## CONDENSERS AND RESISTORS

We carry a wide range of these and fully detailed lists are available free.

### CRYSTAL SET COMPONENTS

COILS. Teltron HAX Coil, 3/-. Specially made for use with Crystal Diodes. CRYSTAL. Suitable Crystal Diode, 2/6. TUNING CONDENSER. .0005 mfd., 3/10. CHASSIS. Small metal chassis fitted with tuning scale and sockets, 2/9. TUNING KNOB, 1/-.

### TRANSISTORS

MULLARD. OC70, 21/-. OCT1, 24/-. OC72 Matched Pairs, 60/- a pair.

S.T.C. T1 (3X 300N), 40/-. T12 (3X 301N), 45/-. T13 (3X 302N), 50/-. T14, 18/-. T15, 21/-. T16, 24/-. T17, 21/-. T18, 24/-. T19, 21/-. T20, 24/-. T21, 21/-. T22, 24/-. T23, 24/-. T24, 21/-. T25, 24/-. T26, 21/-. T27, 24/-. T28, 21/-. T29, 24/-. T878, 21/-. T879, 24/-. T880, 21/-.

# An Electronic Metronome

ANOTHER INTERESTING TRANSISTORISED ACCESSORY

By P. Cheetham

**W**ORTH building if only to demonstrate the versatility of the transistor, this circuit can be completed in an hour from the contents of the average spares-box, plus one 10-transistor. There is no point in using a valuable low-noise, high-alpha transistor in this circuit: one which does not come up to scratch in other respects will still be perfectly satisfactory here.

The transformer may be any standard output transformer with a low resistance primary; in fact, the one actually used was a push-pull type which had one half of its primary burned out, the remaining half having a resistance of 180 ohms.

Using a 2½ in. speaker, it is possible to build the metronome of a size which fits easily into the pocket, but the larger the speaker, of course, the louder will be its tone, although, again, it is quite unnecessary to use a first-class speaker for it has only to croak like a death-watch beetle and not sing like a nightingale. The prototype model used a speaker with a badly damaged cone repaired with Sellotape, yet it worked quite well.

## Constructional Details

The three-ply case is 3¼ in. square and 1½ in. deep (inside measurements) with a 2¼ in. diameter hole for the speaker. An excellent grille can be found by attacking the old civilian respirator with a tin-opener, and all components, including a deaf-aid battery, may be glued into the case once the loud-speaker has been bolted down. The transistor is best left supported only by its springy leads, and these leads should not be cut, for there is always the danger of overheating when making the soldered joints, but it is advisable to thread half their lengths with sleeving as a safeguard against short circuits.

## Switching Arrangements

By the use of two potentiometers, it is possible to have a "low" and "high" range, and with switches connected as shown in the circuit diagram, the sub-miniature (deaf-aid) potentiometer serves as the main on/off switch and low speed control. Any other 1 MΩ control with switch would serve here, but as these are available at a shilling only, and occupy no space at all

inside the case, it seems pointless to use anything else.

When the ½ meg. control is switched on, the low speed control is shorted out and by continuing to turn, any high-speed setting may be chosen. Meanwhile the slow speed setting has remained undisturbed and it is only necessary to switch off the high-speed control in order to return immediately to these low-speed clicks.

## LIST OF PARTS

250µF 25 VW Condenser.  
100K ¼ watt Resistor.  
1 Meg. Potentiometer with Switch.  
½ Meg. Potentiometer with Switch.  
2½ in. Loudspeaker.  
Speaker Transformer (low resistance primary).  
Junction Transistor (any type).

## Calibration

The speed of the clicks depends not only upon the time constant of the C.R. circuit but on the voltage of the battery, so the latter should be chosen to cover the ranges desired. The value of the capacitor may be increased or reduced, as long as its working voltage is not likely to be exceeded, but not much is gained by changing the values of the resistors shown. The 100 K fixed resistor is for limiting the current flow through the transistor to a safe value, and any attempt to increase the value of the potentiometers may lead to inaccuracies due to leakage paths set up by moisture, etc.

The operating voltage should be chosen from the table on page 674 and the scales calibrated by comparison with a pendulum or a stop-watch.

Incidentally, with only 1½ volts, the metronome becomes an excellent tunable A.F. oscillator!



Front and rear views of a unit made up from the circuit described here.

Battery volts	Total range
22½	5 per min. to 3 per sec.
18	10 per min. to 4 per sec.
12	20 per min. to 5 per sec.
6	1 per sec. to 10 per sec.
3	15 per sec. to 200 per sec.

Current consumption in all cases is less than ½ mA so deaf-aid batteries may be used.

### Uses

The finished instrument is far more versatile than its name suggests and has been in regular use in a technical college laboratory for counting slowly oscillating phenomena (pendulums, pistons, springs) by synchronising the speed of the clicks with that of the movements, and scaling off the period of oscillation on the metronome. The exceptionally sharp and clearly defined clicks produced when working voltages are not too low, lead to the most accurate readings,

and also enable the metronome to be used in the photographer's dark-room for counting off seconds.

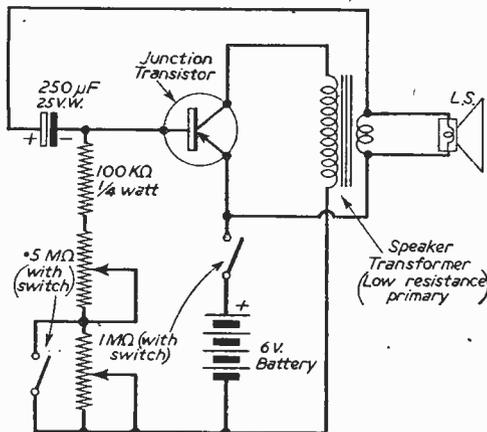


Fig. 1.—Theoretical circuit of the Metronome.

## News from the Clubs

### THE WARRINGTON AND DISTRICT AMATEUR RADIO SOCIETY

Press Sec.: R. Dyke, 22, Stetchworth Road, Walton, Warrington, Lancs.

THE Society meets at 7.30 p.m. at the Royal Oak Hotel, Bridge Street, Warrington, on the first and third Thursday of each month. In addition to the usual lectures, etc., it is proposed to hold a series of talks on radio theory up to the standard of the R.A.A. Visitors and prospective new members will always be welcome at any of the meetings.

### TORBAY AMATEUR RADIO SOCIETY

Hon. Sec.: L. H. Webber, G3GDW, 43, Lime Tree Walk, Newton Abbot.

AT the September meeting, which was held under the chairmanship of G2GK, heartiest congratulations were extended to blind member George Western, who has succeeded in obtaining his full licence G3LFL. Two other members are waiting for their licences.

A new member to the district was also welcomed in Cliff Stagg, G3KPW, whose address is 3, West Street, Ashburton, Devon.

A junk sale will be held at the November meeting and members are asked to bring their unwanted spare apparatus for disposal.

### CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: C. H. Bullivant, G3DIC, 25, St. Fillans Road, Catford, London, S.E.6.

AT the Annual General Meeting held on September 14th, the following officers were re-elected: J. Lambert, G3FNZ, chairman; N. Moore, hon treasurer; C. Bullivant, G3DIC, hon. secretary; C. Hatfull, G3HZI, and W. Martin, G3FVG, committeemen. One of the major decisions taken during the meeting was the setting up of an emergency fund into which a certain amount of money will be placed each year. The object of the fund is to ensure that the Society will have a reserve to fall back on during possible lean years. Ultimately it is hoped to have sufficient funds to obtain a permanent club room.

Forty-three members and friends were present at the Junk Sale held on September 28th.

November Diary: 9th and 23rd—Constructional evening and ragchew; 16th—"Progress of the Avometer," by Mr. J. A. Thomas; 30th—Junk Sale.

Meetings are held every Friday at 7.30 p.m. at the club rooms, 225, New Cross Road, S.E.14. Details of membership can be obtained from the Hon. Secretary.

### PLYMOUTH RADIO CLUB

Hon. Sec.: Cyril Teale, G3JYB, 3, Berron Park Road, Peverell, Plymouth.

THE Club now have an 1154TX and WS36 for "20," "15" and "10" and BC348 receiver.

Visits to the local power station and local BBC stations are arranged. Lectures are also arranged.

Next meetings are November 13th and 27th, December 11th, 8th January, 7.30 p.m., at Virginia House Settlement, Barbican.

### THE BRADFORD AMATEUR RADIO SOCIETY

Sec.: F. J. Davies, 39, Pullan Avenue, Eccleshill, Bradford, 2.

THE syllabus for the coming winter is now out and the club will be pleased to let anyone interested have a copy.

The club meets on alternate Tuesdays at 7.30 p.m. at Cambridge House, 66, Little Horton Lane, Bradford, and holds Morse instruction there from 7.0 to 7.30 before the meetings.

### CRAY VALLEY RADIO CLUB

Hon. Sec.: S. W. Coursey, G3JJC, 49, Dulverton Road, New Eltham, S.E.9.

AT the November meeting of the club to be held at Station Hotel, Sidcup, Kent, Tuesday 27th, 8.0 p.m., Mr. L. Clinch will talk on "Natural Sound in the Home." He will show by means of demonstrations of home-built equipment how amateurs can make the most of the high quality transmissions and recordings that are available to the public today.

Visitors, particularly those interested in recent audio developments, are cordially invited to the meeting.

### SPEN VALLEY AND DISTRICT RADIO AND TELEVISION SOCIETY

Hon. Sec.: J. Stubbs, 5, Manor Street, Hartshead Moor, Cleckheaton, Yorks.

THE 1956-57 season of the above society opened on September 19th with a social evening. Other meetings in future include: November 14th—Visit to MRG Bradford. 7.0 at works. Limited number.

Officials for 1956-57: President, G3GJV, H. Brooke; Vice-president, G80K, P. Dennison; Treasurer, Mr. L. A. Metcalfe; Joint Secs.: G3KNA, J. Stubbs, and G3JJC, J. Charlesworth; Committee: G3KRL, J. Schofield, G3JQC, G. Hawkesworth, G2CGR, G. Crossley.

Anyone wishing further information regarding the above society please write to the Hon. Sec. Meetings are held Wednesday fortnightly.

### THE SLADE RADIO SOCIETY

Hon. Sec.: Mr. C. N. Smart, 110, Woolmore Road, Erdington, Birmingham, 23.

FOURTH quarter's programme:—November 9th, "Microwave Techniques," by Mr. T. J. Hayward, G3HHD (member), of the R.A.F. School of Radio. Generation, transmission, reception and uses of microwaves. November 23rd, Annual General Meeting. December 7th, "The Labgear LG300 Transmitter," by Mr. S. R. Kharbada, of Labgear (Cambridge) Ltd. December 21st, "Fun and Games," presented by Messrs. L. H. Blackwell and G. L. Turner (members).

The club station (G3JBN) at the Church House is available every day of the week for the use of members. Instructional and constructional classes are held on every Tuesday and Wednesday evening. The "Slade Net" will be on the air on the following Friday evenings: November 30th and December 28th.



# On Your Wavelength

BY THERMION

## BBC Pronunciation

I HAVE recently taken the BBC to task for permitting their announcers to adopt their own methods of pronunciation, in opposition to common usage. One announcer is now referring to "conference" and "confident." There is not one English dictionary in the whole world which gives such a pronunciation. You will remember that I tackled them some years ago over "Raif" for "Ralph." I know many men with such a Christian name and not one of them is known as "Raif." Then there was that frightful word "cumbat," again a pronunciation not to be found in an English dictionary. To-day these BBC announcers with their supercilious, snobbish Kensington shop-girl type of pronunciation have produced "humage" (homage). In my view the BBC has no authority to mess about with etymology and pronunciation in this way. What is wrong with pronouncing the word as the dictionary says? Learned savants have given their lives to standardising pronunciation, and the BBC now wishes to set it all at naught by introducing BBC English. Imagine the confusion this is causing among those who teach English in our universities, colleges and schools, and consider how it is confounding foreigners over here learning English. They are taught how to pronounce one way at school and hear it pronounced over the air in another. Some years ago the BBC set up a committee to decide upon pronunciation where there were alternative pronunciations. It is true that, instead of having a committee composed entirely of English men of letters, we had to have a Scotsman and a Welshman to teach us how to pronounce English! I should have thought that the BBC would have been more concerned that their artistes pronounce words properly, especially singers. Take this gem from Doris Day's programme: "When the rad, rad rarbin carms barbarbarbin' alarn." Every night one hears "yeou (you), trew (true), larv (love)." Nearly all of the vocalists who sing "parpular sarns" endeavour to ape the pronunciation of the negro. For example, "Ahm (I am) gawn (going) barse (boss)." No doubt you can think of many hundreds yourself. The BBC does nothing about that. I agree that in general BBC London announcers speak better English than is heard from the Scottish, Welsh or Irish stations, whose announcers are still full of dialect and have never studied an English dictionary, but the BBC must really not invent a pronunciation of their own.

## Hot Gospelling on the Air

I AM glad that the BBC does not permit commercialised hot gospelling on the air as does Radio Luxembourg. This station regularly spawns into the ether a lot of jargon with quotations from the Bible in the high-speed hot gospelling perfervid style of W. Graham. I was listening in the other evening to one of these hot gospellers quoting disconnected passages from the Bible and accusing the whole human race of being sinners and in an accusatory

tone, interspersed with hymns not to be found in the British hymnal, and then—could it be?—it was, the maestro himself, W. Graham, who spouted for a considerable time in the same accusatory tone about clouds, punctuated with a lot of well-known quotations about clouds. There was one quotation about clouds, however, which he omitted, and it seems apropos. I refer to that rhyme from Tennyson's "Revenge," which goes "He vanished like a cloud upon the silent summer heaven." It was apropos because he was promptly faded from my set. The fact is that this hot gospelling has become a highly profitable business and W. Graham has begot a large number of disciples all endeavouring to copy the style of the master. They shout, rave, rant and quote and at the end of it have said nothing. I wonder that Radio Luxembourg permits such trash to spoliolate the ether.

## Servicing Printed Circuit Receivers

THE replacing of a defective component in a printed circuit receiver is not so simple as one might suppose. The soldering of components into a printed circuit is a special technique and it is recommended by two companies that the defective component should not be unsoldered but cut out. One manufacturer recommends the following equipment for servicing printed circuits. A small, pointed soldering iron of 35 watts, soft wire brush, 60/40 resin core solder, diagonal wire cutters, long-nosed pliers, thin-bladed knife, polystyrene dope, and acetone as a solvent for it. The defective component should be cut out so as to leave as much of its lead wires as possible. Next clean the wires of the new component and form the ends into small loops, slip these over the old wire ends and apply a soldering iron. If the old wires are too short the defective component should be cut in half in order to retain the extra length of wire inside it.

If in some cases this practice cannot be adopted, carefully heat the joint, using as little heat as possible, brush the solder away and then release the component. After the new component has been soldered in, the area should be brushed over with the dope to protect against short circuits. Make quite sure that solder does not bridge gaps between conductors. If a break occurs in the printed circuit foil this can, of course, be bridged with solder.

## Valve Prices

I AM glad to see that the valve manufacturers who have exercised their monopoly, in my view, far too long, have at last agreed in view of the Monopolies Commission, to reduce their prices. All valves and TV tubes are priced extortionately as far as the public is concerned. Manufacturers, of course, obtain them at specially low prices, which is but a tithe of what the retailer charges you when you want a replacement valve. Whilst I do not altogether agree that monopolies are bad things, in this case, they have not worked in the public interest.



A CONTEMPORARY  
DESIGN FOR THE HANDYMAN

By R. J. Applin

(Concluded from page 595 November issue)

# Making A Radiogram Cabinet

WHEN the main panels have been cut a chamfer may be worked on the front edge as for the bottom member, working from top to bottom.

Next a full length mitre must be accurately cut along the top edge, and a similar stopped mitre 6in. wide at the front of the bottom edge.

This being done and the panels being an accurate fit when placed in position, they may be fixed with glue—applied to the framing and held in position for drying by clamps similar to those shown in the drawing.

The panels must be fixed to allow  $\frac{1}{2}$ in. projection beyond the back of the framing to cover the edges of the plywood back panel.

The last of the panelling, the top, may now be applied.

As will be seen on examination of the drawing, the lid is not in the centre of the cabinet, there being a 3in. wide panel one side and a 9in. wide panel the other.

This means that the record player, when in position, is partially hidden but is definitely not inaccessible.

The two small side panels and the lid in one piece are cut to an overall length of 36in. and a width of 16 $\frac{1}{2}$ in.

A full length 45 deg. chamfer is next worked on to the front edge in the same way as the other panels and it is then cut into the required three lengths.

A mitred edge is cut on each of the small end panels to fit accurately with that cut on the sides. These two members may then be glued and cramped into position, re-using the cramps employed for the side panels, and left to dry.

The accuracy required when cutting the two mitred edges running along the top of the cabinet cannot be over-emphasised as a shoddy joint here cannot possibly be disguised.

The lid may next be prepared and fixed into position.

A rebate  $\frac{3}{8}$ in. wide by  $\frac{3}{16}$ in. deep is cut into either edge of the lid on the underside to accommodate a strip of brass which is fixed in position with counter-sunk brass screws at 3in. centres.

This metal strip is necessary to stop the lid from warping.

With the brass strips fixed into position the lid may be fastened with a 24in. brass piano hinge.

The hardwood edging may now be applied around the metal fret of the front panel. On the original this was made from 1 $\frac{1}{2}$ in. by  $\frac{3}{8}$ in. splayed black walnut, mitred at angles and glued into position to the edge of the plywood; held by wedges whilst drying.


This provides a very simple and effective way of finishing off the fret panel—the dark wood contrasting with the light chestnut cabinet.

The two panels remaining to be constructed are the fascia to the radio and the motor board.

They are both cut from  $\frac{3}{8}$ in. thick birch-faced plywood and made to fit exactly between the framing.

A panel of the required size must be cut from the fascia to provide a "window" for the tuning dial.

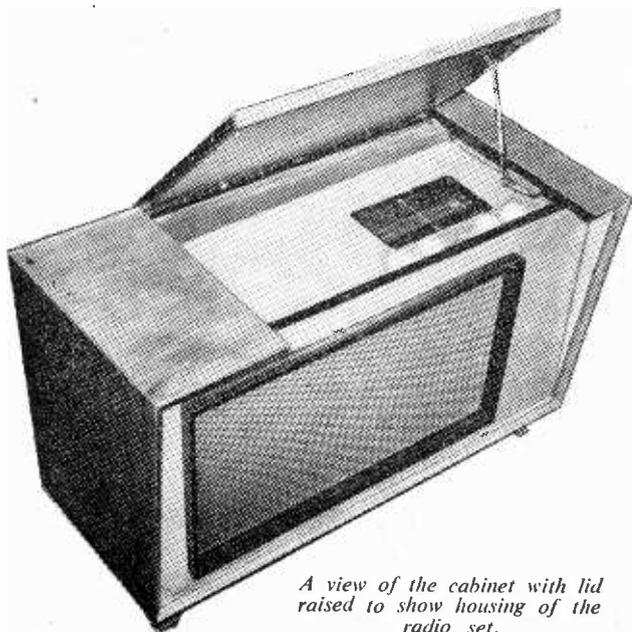The rounded corners to this panel are achieved by first drilling a  $\frac{3}{8}$ in. diameter hole in each corner of the piece to be removed and then cutting the remainder with a fine saw.



A view of the cabinet with lid raised to show housing of the radio set.

The edges to this opening are at this stage filled with sealer and given three coats of black cellulose lacquer—an application which provides a professional touch to the finished article.

When this has been done a panel of  $\frac{1}{4}$  in. thick clear Perspex may be cut, allowing a lap of  $\frac{1}{2}$  in. all round, and glued to the back of the opening using Perspex cement as an adhesive.

down with fine sandpaper to provide a surface to receive the polish.

Before the polishing is commenced a black cellulose finish is given to the two edges of the top panelling which are exposed when the lid is raised, together with the front edge.

These three edges must be given a preliminary application of several coats of grainfiller to provide a perfect base for the cellulose—this applying particularly to the front edge where it is necessary to disguise the joint between the chestnut inner panel and the  $\frac{3}{8}$  in. thick plywood outer fret.

When the cellulose is perfectly dry a polish may be applied to the rest of the cabinet.

A well-known brand of commercial french polish should be chosen and in the case of the original a clear polish was used to preserve the colour of the woods.

Several coats of polish should be applied with a brush, rubbing down the surface between each coat with fine sandpaper and gradually building up a good enough surface to receive the final coat.

A linen pad filled with cotton wool may now be used to work up a fine finish on the cabinet, the method of working with the polisher being best left to the discretion of the individual.

It will be found easier to polish the motor board and fascia panel before fixing, and these may then be secured from the underside by the use of small brass angle brackets fixed to the framing as shown.

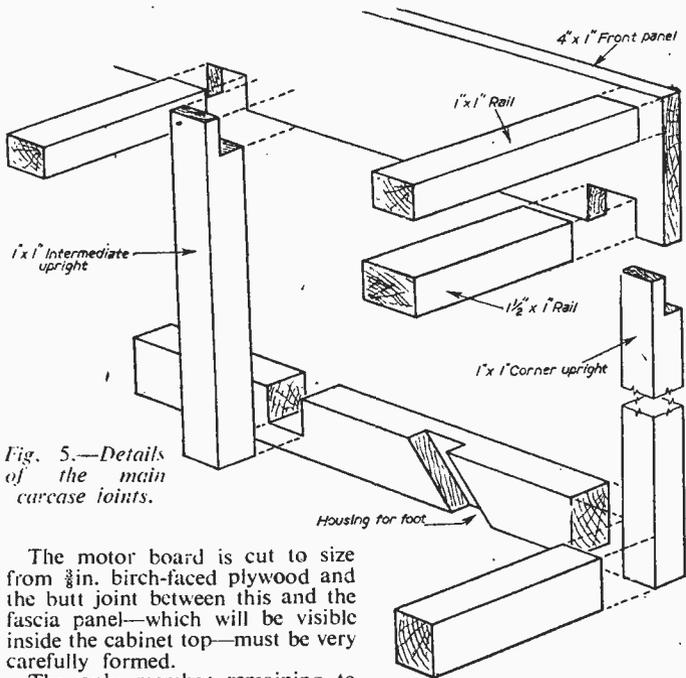


Fig. 5.—Details of the main carcase joints.

The motor board is cut to size from  $\frac{3}{8}$  in. birch-faced plywood and the butt joint between this and the fascia panel—which will be visible inside the cabinet top—must be very carefully formed.

The only member remaining to be made is the plywood back panel. This is cut from  $\frac{1}{4}$  in. thick plywood to fit between the rebates formed by the projecting bottom, side and top panels. Several slots or louvres are cut in this panel near the top to provide an exit for the cooling air to the radio and further holes are provided to allow the earth, aerial and power leads to enter the cabinet.

This panel may then be secured in position to the framing using small brass cups and screws.

Having completed the structure of the cabinet it is now necessary to prepare the cabinet to receive a polish.

The first operation is to work over the entire cabinet with coarse and then fine sandpaper in order to remove any scratches present and to provide a perfectly smooth surface.

When this has been done an application of grain-filler must be given to all surfaces to be polished, and then left to dry thoroughly; after which it must again be rubbed

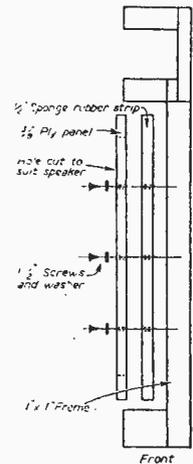
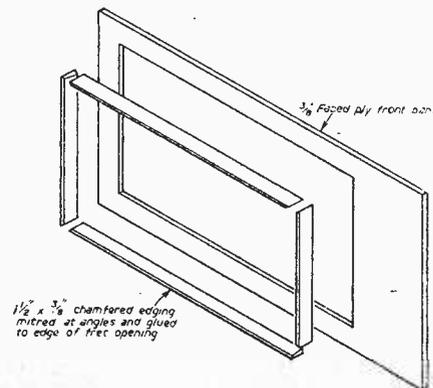
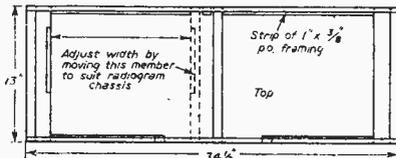


Fig. 6.—Baffle, front and further constructional details.

When the polishing has been completed a stay may be fixed to the lid in the open position.

The bottom of the stay-member is fixed to a small block of wood which may be glued and screwed to the underside of the top panel in an appropriate position.

The cabinet itself is now complete and all that remains to be done is the installation of the radio chassis, speaker and gram turntable.

The unit used in the original is a commercially produced radiogram chassis coupled with a 10in. speaker.

The speaker was mounted on a  $\frac{3}{8}$ in. thick panel of plywood which was fixed to the inside framing with cups and screws and two strips of sponge rubber as shown in the detail.

The front ends of the chassis were bent to provide two fixing lugs as shown, and the chassis was dropped into position between two rebated cross-members and screwed into position. Two small felt pads being provided to give a cushioning effect.

However, the methods adopted for fixing the radio components will necessarily differ, and it is hoped that the above methods as used on the original may be of some assistance.

If these constructional notes are followed through systematically in the order suggested, no difficulty will be experienced in producing a finished cabinet

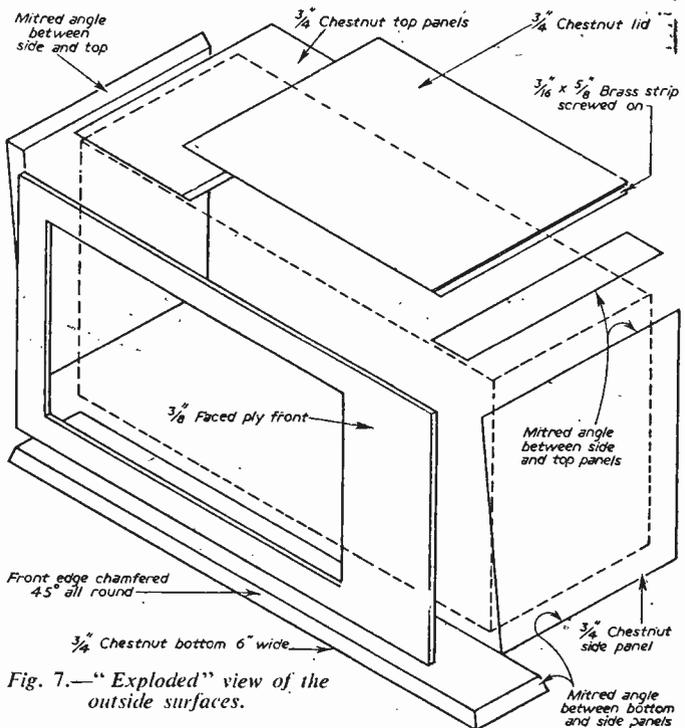


Fig. 7.—“Exploded” view of the outside surfaces.

which will hold its own with anything a modern furniture manufacturer will produce, and which will provide many years of trouble-free service.

## B.R.V.M.A. Statement

CHANGES in the constitution and trading practices of the British Radio Valve Manufacturers' Association, having effect from September 1st, 1956, are announced in the following statement issued to the Press on October 4th.

“It will be known that the Association abandoned its ‘stop list’ and allied provisions some years ago and it has now discontinued all arrangements for collective resale price maintenance on the part of the manufacturers. This has been made necessary by the Restrictive Trade Practices Act which, in effect, prohibits this practice. It will in future be for each individual manufacturer to maintain the prices of his own valves and tubes if he so desires.

“Hitherto ‘B.V.A. Prices’ have been fixed by agreement of all manufacturers who are members of the Association. This policy has also been abandoned. From knowledge of the structure of the industry, however, and in view of the present period of recession with continually rising costs, it will be appreciated that although prices are no longer to be fixed by agreement it does not follow that the prices of comparable valves and tubes will necessarily vary between one manufacturer and another in the immediate future.

“In coming to the decision to abandon collective fixing of prices, the Association has had in mind that if this practice were to be continued it would in all

probability have to be justified in the very near future before the Restrictive Trade Practices Court in the light of the narrow economic criteria set out in the Act. The practice of fixing prices by agreement is not in the present state of the industry of the same degree of importance as it has been in the past or as it may well be in the future.

### PRACTICAL TELEVISION NOV. ISSUE NOW ON SALE PRICE 1/3d.

The current issue of our companion paper describes how to make a Simple Valve Voltmeter which is an invaluable instrument in the service workshop or experimenter's den.

There is also an explanatory article on Bandwidth, and further notes on the methods of using an Oscilloscope. The Servicing article in the November issue deals with the Regentone 14T and similar models, whilst a general article describes the various portable television receivers which are now on the market. These include the Ekco, which is designed for battery as well as mains operation, and may thus be driven from a car battery. Our contributor “Icônos” recently paid a visit to the Manchester ITA centre and an illustrated article on this branch of the independent network is also included in the issue.

Problems Solved, Correspondence, and Number 8 of the Beginner's Guide to Television, dealing with Colour Television, completes this issue.

# PREMIER RADIO COMPANY

B. H. MORRIS & CO. (RADIO) LTD.

OPEN TILL  
6 P.M. SATURDAYS

(Dept. P.W.) 207, EDGWARE ROAD, LONDON, W.2

Telephone :  
AMBASSADOR 4033  
PADDDINGTON 3271-2

## BUILD THESE NEW PREMIER DESIGNS

### 3-BAND SUPERHET RECEIVER

MAY BE BUILT FOR **£7.19.6** Plus 3/- Pk. & Carr.

2 Band T.R.F. Receiver may be built for £5.15.0 plus packing & post 3/-. These two receivers use the latest type circuitry and are fitted into attractive cabinets 12in. x 6 1/2in. x 5 1/2in. in either walnut or ivory bakelite or wood. Individual instruction books 1/- each, post free.



### ALL-DRY BATTERY PORTABLE RADIO RECEIVER

MAY BE BUILT FOR **£7.8.0**

Plus 3/- Pkg. & Postage

4 Miniature valves in a superhet circuit covering medium and long waves. Rex fine covered cabinets 11 1/2in. x 10in. x 3 1/2in. in contrasting colours, wine with grey panel. Instruction book 1/6 post free, which includes full constructional details and list of priced components.



### 4-WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** Plus 2/6 Pkg. & Carr.

Valve line-up 6SL7, 6V6 and 6X5, FOR A.C. MAINS 200-250 VOLTS. Suitable for either 3-ohm or 15-ohm Speakers. Negative feedback. Any type of pick-up may be used. Overall size 9in. x 7in. x 5in. Price of Amplifier complete, tested and ready for use, £5.5.0 plus 3/6 pkg. and carr.



A STEEL CASE IS NOW AVAILABLE, COMPLETE WITH ENGRAVED PANEL, 15/6 EXTRA.

### MULLARD AMPLIFIER KIT


*Why not make the Best!*

All the components for model 510. PLUS preamplifier on one chassis (total six valves) may be purchased for £12.12.0, plus pkg. & post 7/6, or preamplifier and tone control in a separate unit, £14.14.0 plus pkg. & post 7/6.

NOW SUPPLIED WITH ULTRALINEAR OUTPUT TRANSFORMER

Send for the Premier WIDE ANGLE TELEVISOR booklet. 3/6 post free.

### COMPACT GRAM AMPLIFIER

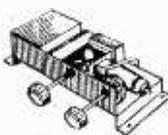

Suitable for any type of Pick-up. Volume and tone control fitted with knobs. Overall size 7 1/2in. long x 3 1/2in. wide x 2 1/2in. high. Complete and ready for use.

**£2.19.6**

Plus packing & postage 2/6.

### GRAM UNITS

B.S.R. 4-Speed Autochanger, £8.15.0 plus 5/- pkg. & post.  
B.S.R. TUB 3-Speed £4.12.6 plus 2/6 pkg. & post.

### A NEW TAPE RECORDER

CREDIT TERMS DEPOSIT **£5**

and 8 monthly payments of £4.18.6

H.P. TERMS 1 DEPOSIT **£20**

and 12 monthly payments of £1.17.1

Cash price £40 plus packing and carriage 2/- Case finished in Brown and Antique Fawn. Size 15in. x 12 1/2in. x 7 1/2in. with the very latest type Continental fittings. For A.C. mains 200-250 volts, 50 cycles.

SEND FOR LEAFLET

## data for AUDIOPHILES\*

EF86



ECC83



EL34



GZ34



EL84



EZ81



Audiophiles all over the world are demanding Mullard audio valves for their high quality sound equipment. And who can blame them when they know that the Mullard World Series of Audio Valves is the finest in the world. Fill in the coupon below for free data on Mullard World Series Audio Valves.

\* Audiophile—Enthusiast for high quality sound reproduction who is satisfied with nothing but the best.

This popular book is available now from most dealers, price 3 6d. It contains designs and full constructional details of the new Mullard EL34 High Quality 20 Watt Amplifier, a Mullard Band II F.M. Tuner, pre-amplifiers for the Mullard EL34 Amplifier and for the popular Mullard 5 Valve 10 Watt Amplifier, together with other useful technical information.



## Mullard WORLD SERIES AUDIO VALVES



Mullard Ltd., Publicity Division, Mullard House, Torrington Place, London, W.C.1.

### COUPON

To Mullard Ltd., Publicity Division

Please send me, free of charge, leaflets on the Mullard World Series of Audio Valves, and details of "High Quality Sound Reproduction".

NAME .....

ADDRESS .....


# BAND 3 T/V CONVERTER—185 Mc/s - 199 Mc/s

Suitable for London, Birmingham and Northern Transmissions

£2-5-0 post free.

A highly successful unit (W/World circuit), incorporating variable oscillator tuning, Midget BVA valves, etc. Chassis size 7 x 4 x 2 1/2 in. Thousands already in use. Suitable for most types of T/V sets. TRF or Superhet. Kit of parts 45/-, Blueprint 1/6, Power pack kit 30/-, Switch kit (Band 1—Band 3 Ae switching),

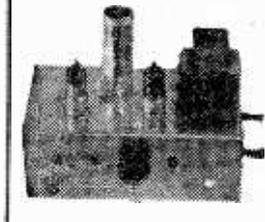6/6—all Post Free. Wiring and aligning of above 20/- extra. Full range of Band 3 aerials in stock. Adaptors from 7/6 per set. Indoor dipoles 6/6. Outdoor with cables, 13/9. Band 1—Band 3 crossover, filter unit, 7/6. Variable attenuators 6 db—36 db, 7/6. BBC Break-through Filter, suitable for BBC pattern rejector, 8/6.



## Volume Controls

Log. ratios, 10,000 ohms — 2 Megohms. Long spindles. 1 year guarantee. Midget Eddie-wan type. No. S.N.P.S.W. D.P.S.W. 3/-, 4/-, 4/9  
Linear Ratio, 10,000 ohms — 2 Megohms. Less switch, 4/- each. Coax plugs, 1/2. Coax sockets, 1/4. Compilers 1/3. Outlet boxes, 4/6.

## 80 ohm COAX

STANDARD 1/4 in. diam. Polythene insulated. GRADE "A" ONLY  
**8d. yd.** SPECIAL — Semi-air spaced polythene. 80 ohm Coax 1/4 in. diam. Stranded core. Losses cut 50%.  
**9. yd.**



## ALL-WAVE RADIOGRAM CHASSIS 3 WAVEBANDS, 5 VALVES

S.W. 16 m.—50 m. LATEST MIDGET S.W. 200 m.—350 m. B.V.A. M.W. 200 m.—2,000 m. SERIES  
Brand new and guar. A.C. 200/250 v., 4 pus. W/C sw. Short-Medium-Long (4 min. P.U. socket. High Q. 1st core coils. Latest circuit technique, delayed AVO and neg. feedback. O/P 4 watts. Chassis size, 13 1/2 x 5 1/2 x 2 1/2 in. dia. 10 in. x 4 1/2 in. hor. or vert. station names. Walnut or ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost.  
Chassis isolated from mains. **BARGAIN PRICE £9.15.0**  
Carr. and ins., 4/6.  
7 or 10 in. speakers to match.  
7 Valve De Luxe, push-pull vers.0, 7 watt output, £12.10.0. Carr. & ins. 5/-.

**BARGAIN VALUE IN AUTO CHANGERS**  
3 speed auto change mixers for 7 in., 10 in. & 12 in. records. Lightweight Xtal P.U. with turnover Duo-point sapphire stylus for Hi-Fi reproduction. Latest models—Modern styling. All brand new, boxed and guar. A.C. 200/250 v. only.  
Latest 4 speed COLLARO auto-changer with Studio 'O' pick-up, 10 gm. 4 speed GARRARD auto-changer, 91 gm. All suitable for above Radiogram chassis.

**ALUMINIUM CHASSIS**—18 a.w.f. Plain, un-drilled, folded 4 sides and riveted corners lattice fixing holes. Strong and soundly constructed with 24 in. sides, 7 in. x 4 in.; 4/8; 8 in. x 6 in.; 5/8; 11 in. x 7 in.; 6/8; 13 in. x 9 in.; 8/8; 14 in. x 11 in.; 10/8; and 18 in. x 16 in. 8 in., 16/8.  
**SPECIAL OFFER**—Goodmans 12 in. P.M. Speaker Audiom 50, Brand new, boxed and guar. FEV ONLY. £4/10/-, Carr. 3/-.  
**REMISTORE**—CZ1 for 3A heater chains, 3/6. £2/2 for 15a., or 2a., 2/6. C23 (Pilot Lamp), 1/8

**NEW VALVES GUARANTEED**  
1R5, 1T4 7/6; 6DAF96 10/-; 6CH81 12/6; 6DZ4 18/-; 185, 184 7/6; 6DP96 10/-; 6CL80 12/6; 6K200 11/-; 384, 3V4, 8/-; 6DK96 10/-; 6EP41 10/6; 6MT74 8/6; 6Z4 8/6; 6DL96 10/-; 6EF50 10/-; 6PC84 12/6; 6AT8 8/6; 6E450 2/-; 6EF50 10/-; 6CF90 12/6; 6H6 10/6; 6EB01 7/6; Equip. 5/6; 6CF92 12/6; 6H6M 3/6; 6BC41 10/6; 6EP90 10/6; 6CL83 12/6; 6K7 6/6; 6BC33 8/6; 6EP85 10/6; 6PL1 12/6; 6K8 9/-; 6CC83 12/6; 6EP86 13/6; 6PL2 10/-; 6Q7 8/6; 6C84 13/6; 6EP89 10/6; 6PL3 12/6; 68N7 9/-; 6CX35 13/6; 6EP91 8/6; 6Y90 11/-; 6V6 7/6; 6EP90 12/6; 6EL41 11/6; 6Y81 12/6; 6X4 8/6; 6CF92 13/6; 6EL84 12/6; 6PY2 10/-; 6X3 8/-; 6CH42 10/6; 6Y51 12/6; 6U5 12/6

and hundreds of others at Bargain Prices.  
**SPECIAL PRICE PER SET**  
1R5, 1T4, 185, and 284 or 3V4 ... .. 27/6  
6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5 ... .. 35/-  
**SPEAKER PRET.**—Expanded Bronze anodised metal 8 in. x 8 in., 2/3; 12 in. x 8 in., 3/-; 12 in. x 12 in., 4/3; 12 in. x 16 in., 6/-; 24 in. x 12 in., 8/6, etc.

## ELECTROLYTICS ALL TYPES NEW STOCK

25/25 v., 50/12 v.	1/9	Can Types, Clips, 3d. ea.	5/6
50/50 v., 4/500 v.	2/-	8 + 8/450 v. W.C.C.	4/6
100/25 v., 2/450 v.	2/-	8 + 16/450 v. Hunt's 5/4	
8/450 v. B.E.C.	2/6	16 + 16 + 16/350 v.	5/6
8/500 v. Dub.	2/6	16 + 16/450 v. T.C.C. 5/6	
8 + 4,500 v. Dub.	4/6	16 + 32/350 v. B.E.C. 5/-	
8 + 16/450 v. T.C.C.	5/-	32/350 v. Dub.	4/6
16 + 16/450 v. B.E.C.	3/6	32 + 32/450 v. T.C.C. 6/6	
16 + 16/450 v. T.C.C.	5/6	60/350 v. T.C.C.	6/6
32/350 v. Dub.	6/6	60/100/350 v.	11/6
32/500 v. Dub.	5/-	100 + 250/275 v.	12/6
50 + 50/350 v. B.E.C. 6/6		100 + 200/275 v.	12/6

## I.F. TRANSFORMERS—465 kc/s

Brand new ex-manufacturer's midget I.F.T. size 2 1/2 in. x 3 in. x 1 1/2 in. dust core tuning. Litz wound coils. High Q. Bargain offer, 7/6 pair.

## MAINS TRANSFORMERS—Made in our own Workshops to Top Grade spec. Fully interleaved and impregnated. RADIO AND AMPLIFIER

TYPE—250 v. 60 ma. P.V. sec., 5 v. or 6.3 v. 1 a. Isolation 2 1/2 a. set Htrs. 2 1/2, etc. G.T.T. HTR. ISOLATION TYPE.—Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1.25:2 v., 4 v., 6 v. or 12 v., 10/6 ea. Ditto with mains primaries 200/250 v., 12/6.  
TYPE.—To designers spec. Viewmaster, 55/-, Mullard Amp, 35/-; Osram, 9/2, 35/-. HEATER TRANS.—Prim. 220/250 v., 6.3 v. 1 1/2 a. or 4 v. 2 a., or 12 v., 75 or 16 v., 5 a., 7/8; 6.3 v. 3 a. or 5 v. 6 a., 18/8 L.F. CHOKES.—10 H. 65 ma., 5/-; 15 H. 100 ma., 10/8; 14 H. 120 ma., 10/8; 20 H. 150 ma., 14/8; Simplex, 10/8; Soundmaster, 10/8. OUTPUT TRANS.—Standard pentode, 4/8; ditto tapered P.M. 4/8; small pentode, 3/8; Midget battery pentode (184, etc.), 4/8.  
**SOLE SOLDERING IRONS** (200-220 v. or 230-250 v.) 25 watt. instrument type, 21/-; 65 watt. Fossil Bit Type, 26/8; 85 watt. Oval Bit Type, 25/-; comprehensive stock of spares available.

**LOUDSPEAKERS**—P.M. 3 OHM 5 in. Celest., 17/6; 5 in. Celest., 18/8; 7 x 4 in. Goodmans's Electrical 12.6; 5 in. Elec., 20/-; 8 in. Goodmans's special, 21/6. Min. N. and A., 25/-; 12 in. Plessey, 35/-; Min. N.E. 2 k. ohm field, tapped O.P. trans., 24/6; 34 in. Elec., 17/6.  
**SCOTCH TAPE, EMITAPE, etc.**, 1.200ft., 30/-; Long playing, 1.800ft., reel, 45/-; Paper tape, good quality 1.200ft., 12.6. Reels only, 5 in., 3/8, 7 in., 4/3

**TWIN-FEEDER**, 80 ohms, 6d. yd.; 300 ohms, 8d. yd. **TWIN SCREEN FEEDER**, 80 ohms, 13 yd.

**50 OHM COAX CABLE**, 8d. per yd., 1/4 in. dia. **TRIMMERS**, Ceramic, 4 pf.—70 pf., 9d.; 100 pf., 1/3; 250 pf., 1/6; 600 pf., 1/9. **PHILIPS Beehive Type**—2 to 8 pf. or 3 to 30 pf., 1/3 each. **RESISTORS**—Pret. values 10 ohms 10 megohms.


**CARBON WIRE-WOUND**  
20% Type, 1 w., 3d.; 5 w., 25 ohms—1/3  
1 w., 5d.; 1 w., 6d.; 10 w., 10,000 1/8  
2 w., 9d.; 15 w., ohms 2/-  
10% Type, 1 w., 9d.; 5 w., 15,000—1/8  
5% Type, 1 w., 1/-; 10 w., 33,000 2/-  
1% Hi-Stab. 1 w., 2/-; 10 w., ohms 2/3  
**WIRE-WOUND POTS**  
Pre-Set Min. T.V. Type  
Knurled Slotted Knob  
All values 25 ohms to 30 K., 3/- ea. 50 K., 4/-  
Ditto Carbon Track  
50 K. to 2 Meg., 3/-.

**CONDENSERS**—Mica or S. Mica. All pref. values. 3 pf. to 680 pf., 6d. ea. Ceramic types, 2.2 pf. 5,000 pf. as available, 8d. each. Tubulars, 450 v., Hunts and T.C.C., 0005, 0017, 005, 01 and 1,350 v., 2d., 02, 05, 1,500 v. Hunt's T.C.C., 1/-; 250 Hunts, 1/8; .5 Hunts, 1/9; 1,500 v. T.C.C. (8impex), 3/6; .001, 6 kv., T.C.C., 8/6. .001 20 kv. T.C.C., 9/6.

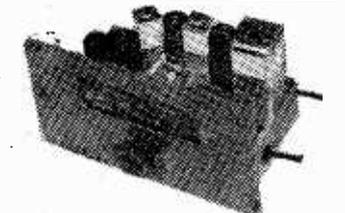**STANDARD 3 WAVEBAND COIL PACK**, Size 2 1/2 in. x 1 1/2 in. depth, 4 pos. switching, Long, Med., Short, (Grand). Dust-core coils prealigned for 465 Kc/s I.F. Complete with trimmers, ready to use. A very sensitive and efficient Coil Pack. **Manufacturer's Surplus. Bargain Offer, 27/6.**



**3 SPEED COLLARO RECORD PLAYER**  
Complete with amplifier and speaker (as illustrated) A.C. 200-250 v. Bargain value—KIT PRICE ONLY £12.10.0, carr. and ins. 5/-.  
**UNIT PRICES**—Cabinet, etc., £33.0.0, carr. 3/6. Amplifier and 6 in. speaker, wired and tested, £3.12.6, carr. 2/6. 3 speed Collaro Gram unit with Studio Hi-Fi pick-up, £25.19.6, carr. 2/6.



**P.M. TUNER-UNIT** (87 mc/s—105 mc/s), by Jason. As tested and approved by Radio Constructor. Complete Kit of parts to build this modern highly successful unit, drilled chassis and J.B. dial, coils and caps, BVA miniature valves and all components, except, for only 28/10/0, post free. **SUPERIOR TYPE GLASS DIAT** (as illustrated)—Calibrated in Mc/s and edge lit by 2 pilot lamps, 12/6 extra. Illustrated handbook with full details, 2/- post free.

# TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188).  
50 yards Thornton Heath Station. Buses 130A, 133, 159, 166 & 190

Listed above are only a few items from our very large stock. Send 3d. stamps today for Complete Bargain list.  
Hours: 9 a.m.—6 p.m. 1 p.m. Wed. OPEN ALL DAY SAT.

Terms C.F.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 1lb. 7d., 1lb., 11l., 31s., 10s., 2s., 10lb., 29s.

# Hard Valve Model Control Receivers

CIRCUITS FOR THE EXPERIMENTER USING MODERN MINIATURE VALVES

By F. G. Rayer

THE simpler type of model control receiver uses a "soft," or gas-filled, valve. This has the great advantage of small size, good range, and ease of adjustment. Unfortunately, however, this type of valve is expensive, and has a relatively short life. Circuits for hard, or vacuum, valves are therefore worth using when circumstances permit—that is, when a little extra weight can be carried, when great range is not important, and when the more careful adjustment necessary can be undertaken. In such circuits valves of small type, including the 1S5, 1T4 and 1S4, and hearing-aid miniatures, can be employed, their life being the same as in ordinary broadcast receivers. The resultant equipment is particularly suitable for boats used on small sailing ponds, where the extra size is unimportant, and working is at relatively short distances.

A normal type of super-regenerative circuit is shown in Fig. 1, resembling that used with a gas-filled valve. Such a circuit will operate successfully with a 1T4, 1S4, or similar type, but is very critical to adjust. At no time can a range anything like so great as with a gas-filled valve be achieved, though short-range working can be obtained.

Quenching and regeneration have to be adjusted

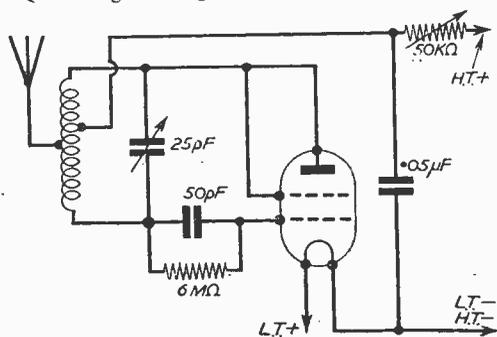


Fig. 1.—Super-regenerative one-valver.

carefully, with a meter in series with the relay (which is wired to the H.T. positive lead in the usual way). A wide range of H.T. voltages can be used, and the battery voltage will govern the setting of the 50K potentiometer. The H.T. tap on the coil will usually require to be about three and a half turns from the anode end, if the coil consists of 13 turns of 20 S.W.G. wire, self-supporting, 1in. in diameter. The position of this tap, and the aerial tapping, greatly influence oscillation. Aerial damping should be such that the valve only goes into oscillation with the 50K potentiometer near zero value.

The current dip will be less than with a gas-filled valve, so that a careful setting of the relay is also

required. It is helpful to use a transmitter running at the maximum permitted output, to facilitate adjustments and improve range.

## Diode Detector

A short-range circuit extremely easy to set up is shown in Fig. 2. When a signal is present, the rectified output of the diode develops a voltage across the 10 megohm leak, thereby changing the valve anode current, which operates the relay. A valve such as the 1S5 will have a change in anode current of about .3 mA, for a change in grid voltage of .5 volt, with suitable standing bias, and this is ample to operate a relay.

To tune this circuit, a microammeter is wired in parallel with the 10 megohm leak, and the 25 pF condenser adjusted for maximum reading. The grid bias voltage is then arranged so that a satisfactory change in anode current arises when the transmitter is keyed. The anode current can be arranged to increase or decrease, when a signal is received, according to the way the diode is connected. The relay is then adjusted in the accustomed manner for

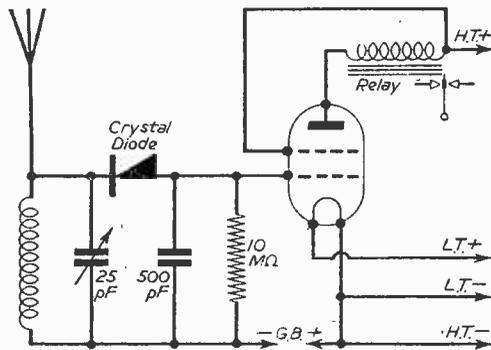


Fig. 2.—A diode-valve circuit.

maximum sensitivity over the current values present.

The range of this circuit naturally depends upon the transmitter and aerials, but with a sensitive relay a useful range can be achieved for boats on a pond of the kind usually found for model sailing.

## Modulation Control


The circuits described only require the usual unmodulated signal. If modulation can be provided, additional methods of working become feasible. Those using various modulation tones, with tuned reed relays, will be familiar to model-control builders, but it is also possible to use one tone, of any frequency, so that the receiver will take the place of the gas-filled triode type.



# A FRONT DOOR INTER-COM SYSTEM

AN INTERESTING COMBINED MIKE, LOUDSPEAKER AND DOOR RELEASE MECHANISM FOR A BLOCK OF FLATS

By K. V. R. Bowerman

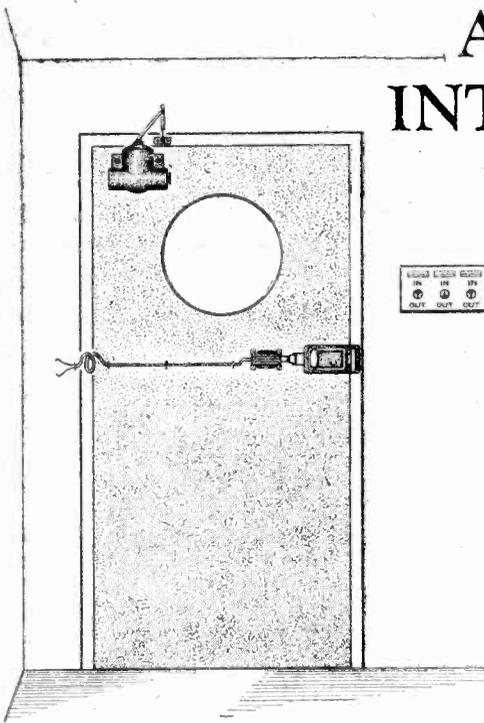

**T**HE installation to be described is suggested for use in small blocks of flats (or houses converted into two or three flats) of the type that share a single street door and have no porter in attendance.

The installation comprises four sections :

(1) *A front door unit.* This has a bell-push corresponding to each flat ; a signal lamp for each bell-push ; a 3in. loudspeaker and an electrically-operated bolt (see later).

(2) *A relay unit,* containing two main relays (common to all flats) and one further relay individual to each flat (total of 5 P.O.-type 200-500 ohm relays for a 3-flat installation).

(3) *A simple two-stage amplifier,* using one 6J7 valve, one 6V6 valve and a metal rectifier.

(4) *The flat units.* These each have a 3in. speaker, two push-buttons, one toggle switch and a bell or buzzer.

## The System

A caller presses the bell-push corresponding to the flat which he wishes to enter. The bell or buzzer starts sounding in this flat and continues to sound until the answerer operates a switch on the local unit. The answerer then presses his "press-to-speak" button and asks the caller his business : he releases the "press-to-speak" button and the caller is able to reply via the front door speaker. If the answerer is satisfied as to the identity of the caller and wishes him to enter, he again presses the "press-to-speak" button, tells his caller to push open the door, and then presses the door-lock release. This operates a solenoid which withdraws a spring bolt and allows the front door to be pushed open. The act of pushing the door open restores all circuits to normal and a

door-closing spring shuts the door. The spring bolt automatically locks as the door closes. If a flat is to be left unoccupied, the tenant, on his way out, operates a switch (marked "IN" or "OUT") near the front door. If, when the switch is in the "OUT" position, a caller pushes the bell-push corresponding to the empty flat, the buzzer does not operate. Instead, a panel reading "OUT" is illuminated next to the name of the tenant.

When one flat is in communication with a caller at the front door, the speakers in the other flats are muted, thus ensuring privacy. With this installation, the necessity for descending and ascending flights of stairs every time there is a caller is eliminated. How does the tenant get back ? He uses his ordinary cylinder lock key.

## The Circuit

The circuit is best understood by following, on the circuit diagram (Fig. 1), the complete cycle of events described above.

(1) Caller pressed bell-push for Flat 1 (PB7). RY1 is energised by the 6-volt rectifier MR2 via door switch and lamp LP1. LP1 is a 6-volt 0.3-amp. cycle lamp bulb. RY1 passes only a few milliamps and therefore the bulb does not light. RY1 closes contacts RY1A, RY1B and RY1C. The first two pairs of contacts bring the remote speaker SK1 into circuit ; RY1C shorts out PB7 and LP1, thus locking relay RY1 in the energised state. Buzzer (or bell) B1 is effectively in parallel with the relay coil and will therefore start sounding and will continue to do so as long as the relay is energised and switch SW1 is closed.

(2) Answerer operates SW1, silencing the buzzer by

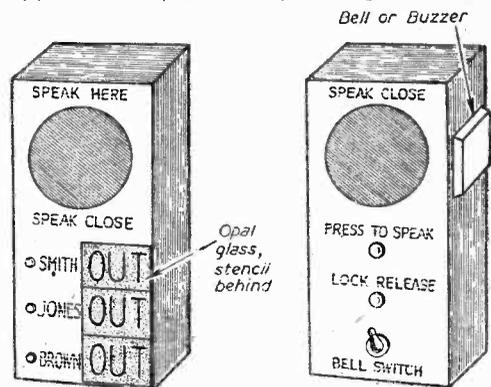


Fig. 2.—Details of the front door (left) and the room units (right).

breaking its connection to line 4. He then presses push-button PBI (a "press-to-speak" button) and this operates relay RY4 by joining line 2 (L.T. negative) to line 3, which is connected to one end of the coil of RY4. The other end of this coil is joined to

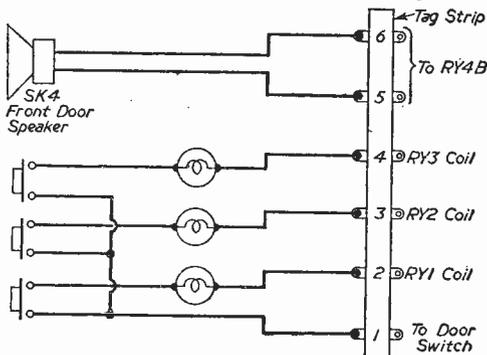


Fig. 4 (b)—Door unit wiring.

L.T. positive. When RY4 operates, the two change-over contacts RY4A and RY4B join speaker SK1 to the input transformer (T1) of the amplifier, and speaker SK4 (at the front door) to the output transformer (T2). The answerer's speech is thus amplified and can be heard by the caller.

(3) Answerer releases PBI. This causes RY4 to release and allow contacts RY4A and RY4B to change back to the "rest" position. Speaker SK4 then becomes the "microphone" feeding T1, and SK1 is fed by the output transformer T2. The caller can thus talk back to the answerer, who, when satisfied, pushes PB2. This joins line 2 (L.T. negative) to line 5 (one side of RY5 coil). The other side of the coil is connected to L.T. positive. Contacts RY5A and RY5B close. Contacts RY5A put a short across lines 2 and 5 and the relay thus "locks on." Contacts RY5B (heavy duty) feed A.C. at mains voltage to the electric bolt solenoid (see later). The bolt is thus held "open" as long as RY5 is energised.

(4) Caller pushes door open and breaks the door switch. This disconnects L.T. positive, RY1 falls off and with it all other relay circuits including the electric bolt. The whole installation is thus restored to normal. The door-closing spring closes the door and the de-energised spring bolt latches automatically.

(5) Should the tenant be out, he will have switched SW4 to the "OUT" position. This shorts out RY1, and when PBI is pushed by the caller a direct connection exists between lamp LP1 and the L.T. supply. This lamp is arranged to

light up behind a small opal glass panel beside the bell-push reading "OUT" (see Figs. 2 and 3).

(6) A tenant returning to the building inserts his key into the existing cylinder lock, which although modified (see later) to operate electrically, still functions normally when operated by hand.

The equipment and wiring for each flat is similar and may be repeated for any number of flats.

**Construction**

We will take separately each section as outlined at the beginning of this article.


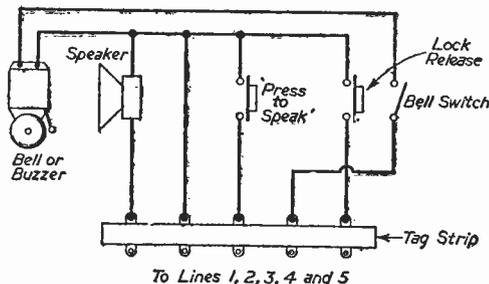


Fig. 4 (a)—Flat unit wiring.

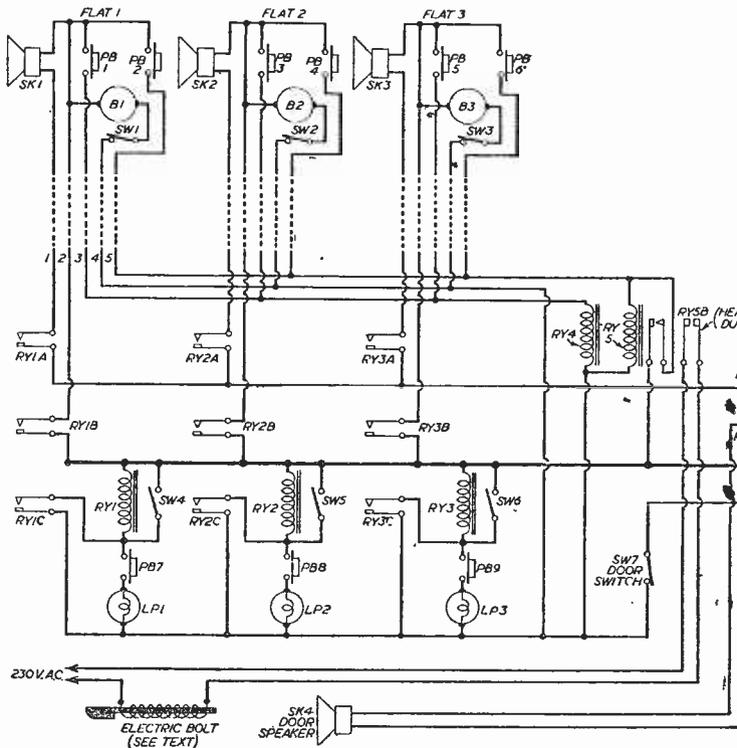



off to weaken it slightly. The spring must be stretched again, after cutting, to its original length. This modification in no way alters the normal function of the cylinder lock.

Other types of lock must be modified according to design, and readers will no doubt be able to adapt the idea to suit the particular lock in use. If a separate ready-made electric bolt is installed, then a car ignition switch of the cylinder lock variety could be used to complete the electric bolt circuit and so enable tenants to enter the building in the normal way. For safety the solenoid should be enclosed in a wooden cover.

The door switch can be very simple. Two strips of springy brass could be attached, one to the door and one to the lintel, so that they are in contact when the door is closed and separate as the door opens. An alternative (and possibly more elegant) method would be to mount a push-button or micro-switch in the door jamb at the hinged side so that it is kept pressed when the door is shut and is released as the door opens.

**The Relay Unit**

Parts required :

5 type 3,000 P.O. relays (200-500 ohm coils)

- RY1—3 pairs of "make" contacts (normally open).
- RY2—3 pairs of "make" contacts (normally open).
- RY3—3 pairs of "make" contacts (normally open).
- RY4—2 sets of "changeover" contacts.
- RY5—1 pair of "make" contacts (normally open).
- 1 pair of heavy duty "make" contacts (normally open).

3 toggle switches (SPST).

These relays are best mounted within the amplifier case and they may be grouped together for ease in wiring on a strip of paxolin (see Fig. 7). They are

normally used for automatic telephony and special racks are provided in the exchange for mounting them. There is no need to be elaborate in this case, however, and the writer has found the method (indicated in Fig. 7) of fixing by thin metal strips passed over the relay coils to be entirely satisfactory. The bolts and nuts securing the metal brackets should be tightened just sufficiently to hold the relay lightly but firmly. Wiring is shown in Fig. 4 (c).

Note that switches SW4, SW5 and SW6 are on flying leads so that they can be positioned on a separate block near the front door.

**The Amplifier**

Parts required :

Valves—1 6J7 (V1) ; 1 6V6 (V2).

Transformers—1 mains transformer, 250-0-6.3 (2 amps.); 1 metal rectifier, 250 volts; 1 metal rectifier (selenium), 6-12 volts, 2 amp., for L.T. relay supply.


Resistors : (½ watt) 100 K $\Omega$ , 47 K $\Omega$ , 1 K $\Omega$ , 250 $\Omega$  ; (2 watt) 1 K $\Omega$ , 100 $\Omega$ , Pre-set 1 meg. pot. (log scale).

Condensers : .01  $\mu$ F ; .5  $\mu$ F (500 v.w.) ; 2 25  $\mu$ F (25 volt w.) electrolytic ; 1 32 ; 32  $\mu$ F (350 volt. w.) electrolytic.

Chassis, screening can, screened leads, solder tags, etc.

The amplifier is so straightforward that Fig. 1 speaks for itself. The only unusual feature is the transformer input. This can be any output transformer with a primary of reasonably high impedance and a secondary of 3 ohms. A ratio of approximately 100 : 1 should be aimed at. But you can, in fact, use a twin of T2, which is suitable for matching a 6V6 to a 3-ohm speaker (40 : 1), but this will give slightly reduced volume. T1, of course, is connected in reverse, the 3-ohm secondary being used as a primary. This has been done so that the long lines to the speakers in the flats can be at low impedance to minimise hum pick-up and capacity effects. A certain

(Concluded on page 689)

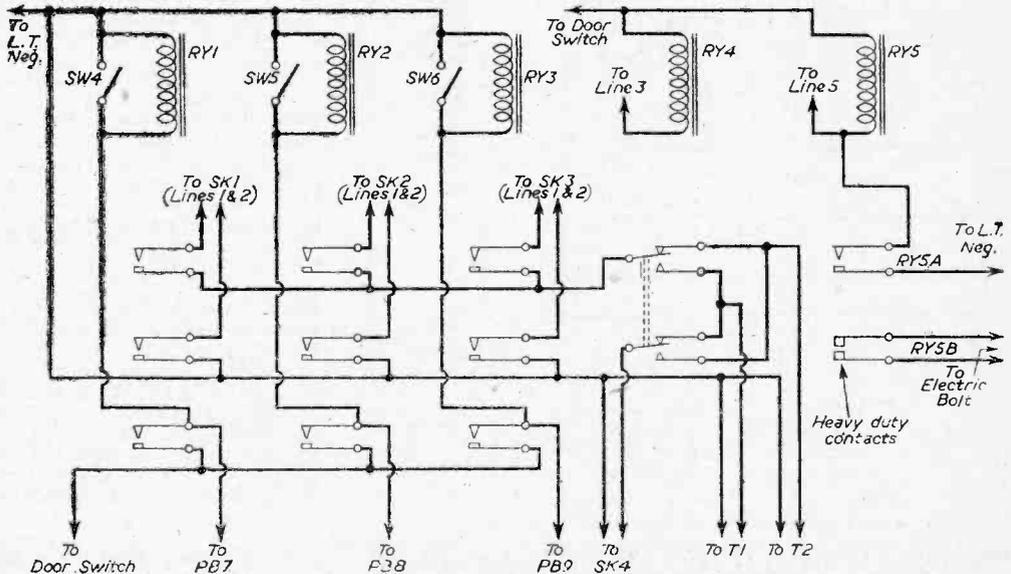

—Complete relay unit wiring.

**C.R.T. ISOLATION TRANSFORMER**

Type A. Low leakage windings. Ratio 1: 1.25 giving a 25% boost on secondary.  
 2 v., 10/6; 4 v., 10/6; 6.3 v., 10/6; 10.8 v., 10/6; 13.3 v., 10/6.  
 Ditto with mains primaries, 12/6 each.  
 Type B. Mains Input 220/240 volts. Multi Output 2, 4, 6.3, 7.3, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50% respectively. Low capacity, suitable for most Cathode Ray Tubes. With Tag Panel, 21/- each.  
 Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 220/240 volts. Output 2-21-21-24-3 volts at 2 amps. With Tag Panel, 27/6 each.  
**NOTE**—It is essential to use mains primary types with T.V. receivers having series-connected heaters.

**TRIMMERS**, Ceramic, .30, .50, 70 pf., 100 pf., 150 pf., 1/3; 250 pf., 1/6; 500 pf., 750 pf., 1/9.  
**RESISTORS**. All values. 10 ohms to 10 meg., 1/4 w., 4/4; 1/2 w., 6d.; 1 w., 8d.; 2 w., 1/-.  
**HIGH STABILITY**, 1/2 w., 1% 2/- Preferred values 400 ohms to 10 meg.  
**WIRE-WOUND RESISTORS** (1/3 10 watt) 25 ohms—10,000 ohms ..... 1/2 15 watt) ..... 2/6  
 15,000 ohms—50,000 ohms, 5 w., 1/9; 10 w., 2/3.  
**KNOBS**, GOLD ENGRAVED.—Walnut or Ivory, 1/4in. diam., 1/6 each. Not engraved, 1/- each.

**12/6 PURETONE RECORDING TAPE**

1,200 ft. on standard lifting 7" Plastic reels. Brand new, boxed, 12/6.  
 Spools 5" metal, 1/6, 7" plastic, 4/3.


**O.P. TRANSFORMERS**. Heavy Duty 50 ma., 4/6. Multitap, push-pull 6/6. Tapped small periods, 3/9.  
**L.F. COKES** 15/10 H. 60/45 mA., 6-3; 10 H. 120 mA., 10/6; 15 H. 150 mA., 12/6.  
**MAINS TRANS.** 350-0-350, 80 mA., 5 w., tapped 4 v. 4 a., 5 v. tapped 4 v. 2 a., ditto 250-0-250, 21/-.  
**HEATER TRANS.** Tapped period, 200/250 v. 6.3 v. 11 amp. 7/6; Tapped sec. 2, 4, 6.3 v., 11 amp., 8/6.  
**VCR97 TESTED FULL PICTURE**, 8/2.  
**COPPER PLATED AERIAL RODS**, 1/2 x 12in. push fitting, 3/- doz., p. & p. 1/-.  
**ALADDIN FORMERS** and core, 1in., 6d.; 2in., 10d.  
**FORMERS** 5957/3 and Cans TV1, 2. 3in. sq. x 2 1/2in. and 1in. sq. x 1 1/2in. 2/- each with cores, with cores.  
**TYANA**—Midnet Soldering Iron, 200/240 v. or 220/230 v., 16/9. Soton Instrument Iron, 24/-.  
**MIKE TRANSF.** 50:1, 1.3/9 ea.; 100:1, 1.10/6.  
**MAINS DROPPERS**, 3 x 1 1/2in. Adl. Siders, 3 amp. 7/0 ohms, 4/3; 2 amp., 1,000 ohms, 4/3.  
**LINE CORD**, 3 amp., 40 ohms per foot, 2 amp., 100 ohms per foot, 2 w., 6d. per foot, 3 w., 7d. per foot.  
**LOUDSPEAKERS P.M. 3 OHM**.  
 5in. Goodmans, 17/8. 7in. x 4in. Goodmans, 22/6.  
 3 1/2in. square, Elic, 21/8. 10in. R. & A., 20/-.  
 4 1/2in. Goodmans, 18/3. 10in. R. & A., 20/-.  
 8in. Tweeter, LS175, 12/6. 12in. Plessey, 30/6.  
 Min. M.E. 2.5 k. or 2 k. field, tapped O.P. transf., 24/6.  
**CRYSTAL DIODE**, G.E.C., 2/-; Crystal Book, 1/6.  
**GEX34 4/-**. Handbook of German Circuits, 2/6.  
**HIGH RESISTANCE PHONES**, 4,000 ohms, 15/9 pr.

**CRYSTAL MIKE INSERT** by Acos, precision engineered. Size only 1 1/2 x 3/16in. Bargain Price 6/6. No transformer required.

**SWITCH CLEANER** Fluid, squirt sprout, 4/3 tin.  
**TWIN GANG TUNING CONDENSERS**, .0005 mfd. midget, less trimmers, 6/6; .0005 standard-size with trimmers, 9/6; less trimmers, 8/6; ditto, soiled, 2/6; .0005 mfd. 3-gang, 7/6.  
**SPEAKER FRET**.  
 Expanded metal, Silver, 1 1/2in. x 9/16in., 2/- each.  
**TAPEMASTER RECORD PLAY HEAD**, 45/-.

**VALVES**

A SMALL SELECTION FROM OUR STOCKS			
All Boxed	1/6	New & Guaranteed	
8/6	5/6	EA50	6/6
1R5	6/8	954	GA15
1T4	6/8		12A77
1R5	PF50	2/6	6B4
384	Equip.	E1148	6K7G
3V4	SP61	EB34	EB91
5U4	SP41	3/6	HVR2
6AM6	EP92	3/6	(near)
6AT6	PN46	6/6	6SK7
6B7	7/6	7/6	EP80
6K6	6B66	GV6G	EL42
6NL7	6BVG	6X1	HVR2A
6SN7	6P6	6X5	PN25
6V6GT	6K74T	807	U22
EP830	UF41	EP70	VI23
8v1/2 Red			
EP91	EY31	U25	PL51
			3524
			947

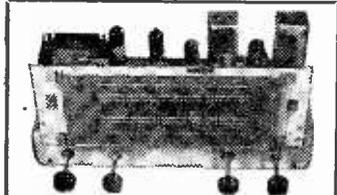


**ALL WAVE RADIOGRAM CHASSIS**

**THREE WAVEBANDS FIVE VALVES**  
 M.W. 16 m.—50 m. LATEST MULLARD  
 A.C. 200/250 v. 4-way Switch; Short-Medium-Long-Gran. A.V.C. and Negative feedback 4.2 watts. Chassis 1 1/2 x 5 1/2 in. Glass Dial 10 x 4 1/2 in. horizontal or vertical available. 2 Pilot Lamps, Four Knobs, Walnut or Ivory. Aligned and calibrated. Chassis isolated from mains. T.S.L. Tweeter Supplied Free!  
**10 gns.** Carr. & Ins., 4/6.  
**TERMS**: Deposit £5.0 and six monthly instalments of £1.  
**MATCHED SPEAKERS FOR ABOVE CHASSIS**  
 8in., 10/6; 10in., 25/-; 12in., 30/-.

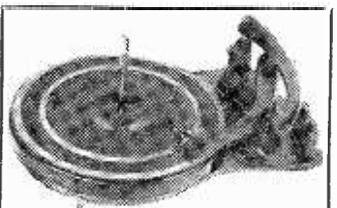**R.C.S. SCOOP**

Collaro Auto-changer RCS51 for 78 r.p.m. 10in. and 12in. records. Brand new in maker's boxes! High impedance lightweight Pick-up with sapphire needle, will match any Amplifier or Radio. Less than half price.  
**5 gns.** Carr. and Ins., 5/6.



**£7-19-6**

Terms: Deposit £4 and six monthly payments of 15/6.  
 Brand new Plessey 3-speed Autochanger Mixer. Xtal Head with Dupont sapphire stylus. Board required 1 1/2 x 12in. Height 5 1/2in. Walnut Veneered Playing Desk 10/6 extra.

**EXCEPTIONAL OPPORTUNITY**

**COLLARO** 4-speed Single Record Player, including heavy weight turntable and lightweight Pick-up with Turnover Xtal mounted on baseplate. Auto-stop fitted.  
**OUR PRICE, 6 gns.** carriage 4/-.

**ALLDRY UNIT POWER PACK**

Replaces Battery B114, etc., 40 v. tubes 1 1/2 in. Size 4 1/2 in. x 1 1/2 in. 4-pin Socket. Same as battery. Only 1/- a year to run on A.C. 200/250 v. FAMOUS MAKE. LIST PRICE, 65/- OUR PRICE, 39/6. Ready for use.  
**B.S.R. MONARCH** 3-speed Motor and Turntable with selecting switch for 33, 45 and 78 r.p.m. records, 100-120 v. and 200-250 v. A.C. 50 cps. Also B.S.R. MONARCH Lightweight Pick-up with Acos Xtal turnover head, separate Sapphire stylus for L.P. and Standard records, SPECIAL OFFER, THE TWO 1/4.12.6, post 2/6.  
**T.V. PRE-AMP (McMICHAEL)**, Tunable Channels 1 to 5. (With Amplify Output of your Band 3 converter) Midget size. High Gran. Pricing Model, B.V.A. Valve. Full instructions. Ready for use. (H.T. 200 v., L.T. 6.3 v., .3 amp. required.) BRAND NEW, 25/- each.  
**MAINS POWER PACK** for above, 25/- extra.  
**SUPERSET COIL PACK**, 27/6. Miniature size 2 1/2 in. x 2 1/2 in. x 1 1/2 in. HIGH "Q" Dust coated coils. Short, Medium, Long Gran. Switching. Single hole fixing. Complete with connection diagram and 5 valve circuit.

**TELETRON BAND III CONVERTER**

For London, Midland and Northern Transmissions.  
 Suitable all T.V. makes. T.R.F. or Superhet. Ready wound coils, two EF80 valves, all components, punched chassis, circuit-diagram, wiring plans, COMPLETE KIT for mains operation 200-250 v. A.C. £3.10.0.  
 AS ABOVE LESS POWER PACK. Requires 200 v. 20 ma. H.T. 6.3 v. .6 a. L.T. ... £2.5.0  
 Mains Transformers to above Spec. ... 10/6  
 Min. Westinghouse Rect. ditto ... 8/6  
 B.E.C./I.T.A. Aerial crossover unit ... 7/6  
 Punched and drilled chassis ... 3/6  
 Larger chassis for Mains Model ... 8/-  
 Teletron Coilset with plans ... 15/-  
 Full plans and circuit details ... 6d.

**Volume Controls 80 ohm CABLE COAX**

Long spindles. Guaranteed 1 year. Midget. 10,000 ohms to 2 Meg. Stranded core. 9d. yd. No sw. S.P.F.S.W. 1/2 P.S.W. Larger chassis for Mains Model ... 15/-  
 Lin or Log Taps. ... 8d. yd.  
**COAX PLUGS ... 1/- DOUBLE SOCKET ... 1/3**  
**SOCKETS ... 1/- OUTLET BOXES ... 4/6**  
**BALANCED TWIN FEEDER, yd. 6d. 80 or 300 ohms. DITTO SCREENED per yd. 1/-.** 80 ohms only.  
**WIRE-WOUND POTS, 3 WATT. Pre-set Min. T.V. Type.** All values 25 ohms to 50 K., 3/- ea. 50 K., 4/- (Carbon 50 K., 2 to 1, 3/-).  
**WIRE-WOUND 4 WATT. Pots, 2 1/2in. Spindles.** Values, 100 ohms to 50 K., 5/6; 100 K., 6/6. CONDENSERS. New stock. .001 mfd., 7 kv. 1/4", 5/6. Ditto, 20 kv., 9/6; 100 pf. to 500 pf. Mica, 6d.; Tantalum, 200 pf. to .01 mfd., 9d.; .05, 1.1, 1.2, 2.5, 3/6, 5, 1/9, 1/359 v., 6d.; 1,000 v., 1/3; 1 mfd., 2,000 volts, 4/-.  
**CERAMIC CONDS.** 500 v., .3 pf. to .01 mfd., 10d. SILVER MICA CONDENSERS. 10%, 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3. DITTO 1/6, 1.5 pf. to 500 pf., 1/9; 315 pf. to 3,000 pf., 2/-.

**I.F. TRANSFORMERS 7/6 pair**

46 Kes Slur tuning Miniature Can., 2 1/2 in. x 1 1/2 in. High Q and good bandwidth. By Pye Radio. Data sheet supplied.

**NEW ELECTROLYTICS. FAMOUS MAKES**

TUBULAR	TUBULAR	CAN TYPES	
1/275 v. 2/-	100/25 v. 2/6	8 + 16/500 v. 5/6	
2/450 v. 2/3	8 + 8/300 v. 4/6	16 + 16/500 v. 6/6	
4/450 v. 2/3	16 + 16/500 v. 4/6	25 + 20/450 v. 5/6	
8/450 v. 2/3	6/-	32 + 32/350 v. 4/6	
8/500 v. 2/9	CAN TYPES	32 + 32/450 v. 6/6	
16/450 v. 3/6	Chips	50 + 30/350 v. 7/6	
16/500 v. 4/-	16/450 v. 3/6	64 + 120/275 v. 7/6	
32/450 v. 5/6	32/350 v. 4/6	100 + 200/275 v. 7/6	
25/25 v. 1/9	64/50 v. 5/6		12/6
50/25 v. 1/9	50/25 v. 3/6	1,000 + 1,000/6 v. 1/6	
50/50 v. 2/-	18 + 16/450 v. 5/6		6/6
50/50 v. 2/-	16/450 v. 3/6	16/500 v. 3/6	
		SEMI-RECTIFIERS, E.P. TYPE, ELY-	
		BACK VOLTAGES, K/R25 2 kv. 5/-; K/R40 3.2 kv. 7/-; K/R45 3.6 kv. 7/6; K/R50 4 kv. 8/6;	
		K/R100 8 kv. 14/6; MAINS TYPE, R.M1, 125 v., 60 mA., 9/-; R.M2, 100 mA., 6/-; R.M3, 120 mA., 8/-; R.M4, 250 v., 275 mA., 16/-.	
		<b>PANEL LAMPS</b> (Neon) 230 v., A.C./D.C., 3/6.	
		<b>COILS</b> Weirite, "P" type, 3/- each. Osornor Midget "Q" type adj. dust core, 4/- each. All ranges.	
		<b>TELETRON, L. &amp; Mel. T.R.F.</b> with reaction, 3/6.	
		<b>BERFORD RO AERIALS</b> , M.W., 8/9; M. & L., 12/6.	
		<b>TELETRON T.R.F. COILS</b> A/H/F, 7/- pair.	
		H.E. COKES ..... M.H. 3/- each.	

**ALUMINIUM CHASSIS**

18 s.w.g. drilled with 4 sides, riveted corners and lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 6in., 5/6; 11 x 7in., 6/9; 13 x 6in., 8/6; 14 x 1 1/2in., 10/6; 15 x 1 1/2in., 12/6; 18 x 16 x 3in., 16/6.

**FULL WAVE BRIDGE SELENIUM RECTIFIERS**

2, 6 or 12 v. 1/2 amp., 6/9; 2 1/2, 11/3; 4 1/2, 17/6.  
**CHARGER TRANSFORMERS**, Tapped input 200-250 v. for charging at 2, 6 or 12 v., 1/4 amp., 13/6.  
 1/4 amp., 21/6.  
**BERNARDS VALVE MANUALS I & II**, 5/- each.  
**VALVE and TV TUBE equivalents books**, 5/-.  
**ACID HYDROMETER**. New Ex Gov. Unavailable. Packed in metal case 7 x 1 1/2in. dia., 4/6.  
**WAVECHANGE SWITCHES**.  
 5 p. 4-way 2 waf. long spindle ..... 6/6  
 2 p. 2-way, 3 p. 2-way, short spindle ..... 2/6  
 2 p. 4-way, 4 p. 2-way, 4 p. 3-way, long spindle ..... 3/6  
 3 p. 4-way, 1 p. 12-way, long spindle ..... 3/6  
**VALVE HOLDERS**. Fax. Int. Oct. 4d., EF50, EA60, 6d.; B12A, CR12, Eng. and Amer. 4, 5, 6, 7, 8, 9, 10, 11. MOULDED STAND and Int. Oct. 6d.  
**BTG, B8A, BRG, B9A, 8d.** with can, 1/6.  
**VCR97 2/6**, B9A with can 2/6. CERAMIC, EF50, BTG, B9A, Int. Oct. 1/-, BTG with can 1/9.  
**BLACK CRACKLE PAINT**, air drying, 3/- tin.

We have no connection with any other firm. Please address all Mail Orders correctly as below.  
**RADIO COMPONENT SPECIALISTS 307 WHITEHORSE RD., WEST CROYDON**  
 OPEN ALL DAY—(Wed. 1 p.m.) 10 page list 3d.  
 Tel. THO 1665. Buses 133 or 68 pass door. 48-hour postal Service, P. & P., 1/- £2 orders post free. (Export Extra) C.O.D. Service 11/6

**Still only 5 connections**  
**Smaller in size**  
**many plus' features**

*The New*  
**Q-pack**  
FROM 42/-

**FREE**

CIRCUITS & WIRING DIAGRAMS

AMAZINGLY ROBUST

**JIFFY PUNCH**

FERRITE ROD AERIALS

For cutting smaller holes neatly with one blow of a light hammer

HOLE	RETAIL
in. 6/6	
in. 7/6	
in. 8/9	

HIGH "Q" M.W., 8/9  
M. & L.W., 12/9

**CHASSIS CUTTER**

HOLE SIZES	RETAIL
1 in. x 1 1/2 in.	19/6
1 in. x 1 1/4 in.	18/9
1 in. x 1 1/8 in.	22/6
1 1/2 in. x 2 in.	27/3

**BAND III Converter**

Kit £3.5.0  
Ready wired £4  
Postage and packing 3/-

**BAND I FILTER**

Rejects B.B.C. from I.T.A. aerial. Suitable for all makes.

10/- inc. instructions

Fitted in 2 minutes

**OSMOR NEW ASSEMBLY DIAL**

Calibrated for Osmor Coils

Coil-packs 24/6

Bronze Finish Escutcheon 4/-

**POTTED COILS HIGH "Q"**

Simple press home fixing


Entirely New Design

**STATION SEPARATOR**

Price 10/-

Send 7d. in stamps for circuits, wiring diagrams, coil-pack leaflets, components, lists chassis drawings templates, price lists.

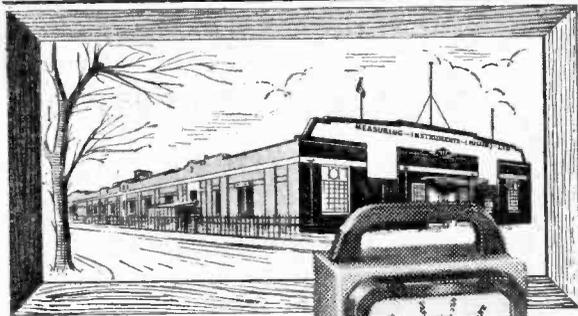**OSMOR RADIO PRODUCTS LTD.** P.W.5 418 Brighton Road, South Croydon Surrey. Telephone Croydon 5148/9.



## Background to Reliability

Behind the world-wide popularity and reliability of the Pullin Series 100 Multi-Range Test Set, with its 21 ranges from 100 microamps to 1,000 volts and sensitivity of 10,000 ohms per volt, are the considerable research, manufacturing, development and service resources of M.I.P., one of the great Pullin Group of Companies.



**MEASURING INSTRUMENTS (PULLIN) LIMITED**  
Electrin' Works, Winchester Street, Acton, London, W.3.  
Tel. : ACORn 4651 & 8801 (5 lines)

## Get your Pullin Series 100 Multi-range Test Set ON EASY TERMS

Here's a grand opportunity for the amateur radio-man or the service engineer. We will send your Pullin Test Set by return of post, post free, on receipt of £2.10.0 deposit. Thereafter, you pay nine monthly payments of £1.4.6. The cash price is £12.7.6. **WRITE TO-DAY TO FRITH RADIOCRAFT—ADDRESS BELOW (right).**

<input type="checkbox"/>	TICK HERE
<input type="checkbox"/>	Please send descriptive leaflet.
<input type="checkbox"/>	Please supply 1 Pullin Series 100 Test Set. I enclose 50/- deposit and promise to pay 9 further monthly payments of 24/6.
SIGNED .....	
ADDRESS .....	
IF OVER 21.....OCCUPATION.....	

**POST TO**  
**FRITH RADIOCRAFT LTD**  
69-71 CHURCH GATE LEICESTER  
& 28 HIGH ST NEWPORT PAGNELL Bucks

amount of hum pick-up is inevitable with this installation, but if the input and output circuits of the amplifier are fully screened; as indicated, hum will be reduced considerably and should not interfere with the intelligibility of speech. A screening can should be used for the 6J7, and both transformers should be well screened. The grid leads to both valves should also be screened. R1 is a pre-set volume control which should be adjusted to the most convenient level and left there. The casing of this component should also be well earthed.


**The Flat Units**

- Parts required :
- 3in. speaker (3-ohm).
- Bell or buzzer.
- 2 push buttons.
- 1 toggle switch (SPST).
- 5-way tag strip.
- Expanded aluminium for speaker fret.

These units can be constructed on similar lines to the front door units (see Fig. 2). A smaller wooden box may be used, and the speaker can be mounted directly behind the plywood front. The buzzer (or bell) unit could be mounted on the side of the box. Wiring is shown in Fig. 4 (a).


The amplifier and relay unit can be housed in a suitably ventilated wooden box, and should be placed

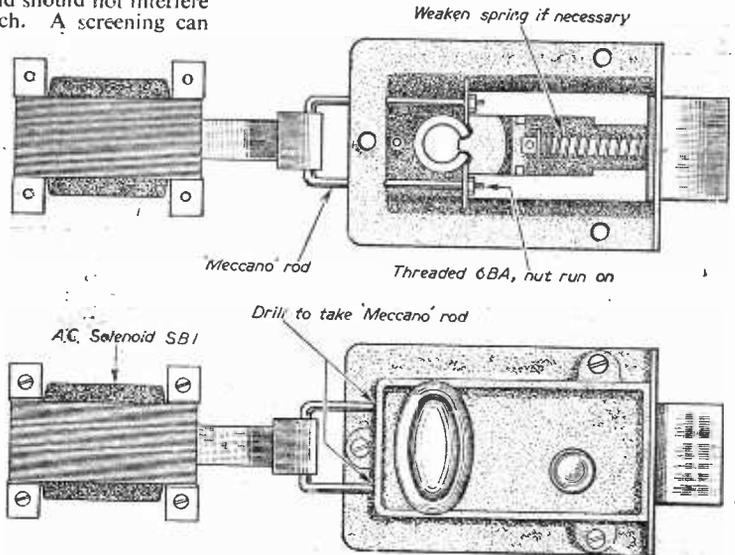on a shelf near the front door, high enough to be out of reach of children. It could equally well go in the "cupboard under the stairs," if there is one. The



Figs. 5 and 6.—Cylinder lock modifications.

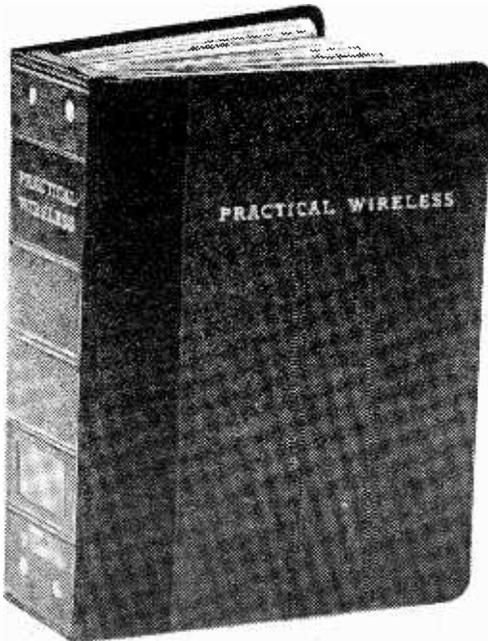important things are, first, to leave a hole for a screwdriver so that any necessary adjustments can be made to VR1; secondly, to place SW4, SW5 and SW6 in a prominent position on a switch block near the door, plainly marked "IN" and "OUT".



# Self-Binders


FOR

## "PRACTICAL WIRELESS"

AS a service to our readers we have arranged for self-binders to be supplied in which they may preserve the copies of this journal. Copies can be inserted as received, and you do not therefore have to wait for the completion of the volume. You secure the same all-time protection as with ordinary binding. The self-binders are in black waterproof and greaseproof cloth, attractively lettered in gold. This system avoids copies becoming damaged or mislaid. The Easibinder opens flat at any page of any separate edition and gives quick reference facilities. When the volume is complete, our annual index, published at 1s. 3d., should be inserted.

They cost 10s. post free. Orders should be sent to PRACTICAL WIRELESS (Binding Dept.), George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

# Programme Pointers

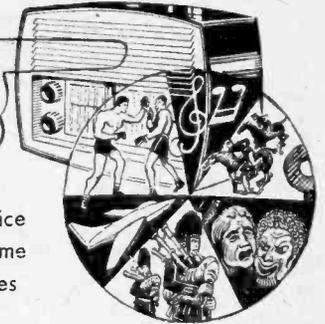

A RECENT letter in the Press gives me the opportunity of raising again the subject of signature tunes. The gist of the correspondent's complaint was this: that before the BBC asks radio listeners to tone their sets down when they are near open windows in the fine weather, they should study more carefully the quality of the music being disseminated and which is evidently calculated, if too strident and rasping, to destroy the quiet and sociable amenities of neighbours. In other words, how the rock 'n' roll can I have my Sunday nap when the Joneses' set is blaring away like it always does when I'm at home!

The logic that prompted the letter is transparently clear. The poorer the "music," the more unacceptable it will be: the better, the less. Granted that Mozart himself may at times be an intruder and that radio is, like Government, of the people, by the people, for the people, it cannot be denied by any sane, if unsophisticated, person that some of the so-called signature tunes, together with the "effects" that punctuate many popular programmes, are so truly awful and hideously unrelated to anything in the shows they summon us to, that we wonder a deputy to the Lord Chamberlain wasn't long ago appointed to control them.

With one exception, not one is even skilfully written; nor does it bear the slightest relation to the character of the show it precedes. I recently mentioned the accompanying noises to the new—and good—programme, "Curiouser and Curiouser": it is difficult to imagine whether it could be any worse emanating from the window next door or the next room under one's own roof.

The exception to this padded cell fitted with the ravings of musical madmen is, of course, the theme-song prefacing "The Archers," a graceful piece, arresting to those who may not know it, and wholly in character to the programme to which it has been attached.

Note.—The letter I have referred to naturally comprises more than signature tunes: the writer refers to the whole hotch-potch of miscellaneous fare under the generic title of "entertainment," such as "Round and About" encompasses on Saturday afternoons.

## Letters

The series, on Sundays, of letters addressed by practitioners in various callings such as music, authorship, medicine, etc., to young people about to seek their fortunes in those professions, was interesting and instructive to the layman listener like myself. Whether the aspirant to a consulting room in Harley Street, chambers in Lincoln's Inn or the writer of a book selling a hundred thousand copies before publication did, I wouldn't know. I should think he most probably did. But it would be deeply interesting if someone in each subject were engaged to make a reply!

So long as there are an England and a Scotland,

Our Critic, Maurice  
Reeve, Reviews Some  
Recent Programmes


so long will the story of the tragic rivalry of Elizabeth the First and Mary Stuart be sought by dramatists, novelists and historians. It has every possible ingredient: so many, in fact, that a writer has to select certain ones to avoid what might turn out to be an incurable attack of indigestion. The German poet-dramatist Schiller, in his "Maria Stuart"—brilliantly done on the Third—lays the emphasis on the political rather than the romantic, and on the treachery of the Earl of Leicester in particular. Margaret Rawlings, perhaps, sounded too beautiful as Elizabeth, and Barbara Jefford not quite enough so. But they made an excellent pair of two totally different and contrasting women. Marius Goring was excellent as the double-dyed scoundrel Leicester. A long cast all added to a first-rate production by Julius Gellner. The translation was by Joseph Mellish. Again there were some truly abominable "musical" interspersions, this time by Roberto Gerhard. Had it woken me up from next door whilst having my Sunday "post prandial" in the sun, the neighbour—to speak in under-statements—would have heard expressions of my annoyance. The Greeks have a word for it.

## The Promenades

The close of this year's Promenade Concerts coincided with the announcement of the coming retirement of Sir Malcolm Sargent as chief conductor. Fortunately, this will not affect his appearances at next year's Proms. Few more colourful personalities than Sir Malcolm's have adorned our concert platforms. For this reason alone we hope his baton will wave as often as ever, because not for many years has the world of music known so few "characters."
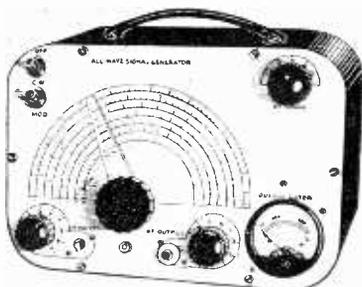
## Edinburgh Festival

As usual many splendid things came from the Edinburgh Festival: so many, in fact, that I am only going to name one (next year I must consider devoting a whole article to this opulent occasion). Many of the symphonies, sonatas, quartets, etc., performed there are to be heard all the year round. At Edinburgh they are usually done by slightly more celebrated virtuosi and with more reverence and swank than we are used to in mundane London. My special mention is for Strauss' "Salome," done by the Hamburg State Opera Company. Based on Oscar Wilde's play, it is a sumptuous work, even when there is nothing to look at. And it is not to be heard every day. It seemed to be beautifully performed and it came over excellently.




**COMPLETELY BUILT SIGNAL GENERATOR**

Coverage 120 Kc/s-230 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-9.5 Mc/s, 8 Mc/s-28 Mc/s, 16 Mc/s-56 Mc/s, 24 Mc/s-84 Mc/s. Metal case 10in. x 6 1/2in. x 4 1/2in. Size of scale 6 1/2in. x 3 1/2in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%. £4/19/6 or 34/- deposit and 3 monthly payments 25/- P. & P. 4/8 extra.

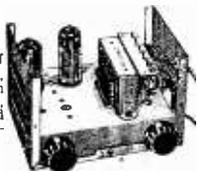**COMMERCIAL TELEVISION CONVERTER SUITABLE ANY T.V. ALL CHANNELS**

**NO ALTERATIONS TO SET**  
Complete with built-in power supply, 230-250 v. A.C. mains. Crackle finish case 5 1/2in. long, 3 1/2in. wide, 4 1/2in. high. Incorporating gain control and band switch. Illustrated with cover removed.



**£3.19.6** Plus P. & P. 2/6.

- Heater transformer. Pri 230-250 v. 6 v. 1 1/2 amp. 6/-.
- Extension Speaker cabinet in polished walnut, complete with 8in. P.M. P. & P. 3/-. 24/6.
- 8in. P.M. Speakers, removed from chassis, fully guaranteed. All by famous manufacturers. P. & P. 1.6. 12/6.
- Volume Controls. Long spindle less switch, 50 K., 500 K., 1 meg., 2/6 each. P. & P. 3d. each.
- Volume Controls. Long spindled and switch. 1, 1 and 2 meg., 4/- each. 10 K. and 50 K., 3/6 each. 1 and 1 meg., long spindle, double pole switch, miniature, 5/-.
- Standard Wave-change Switches. 4-pole 3-way, 1/6; 5-pole 3-way, 1/6. Miniature 3-pole 4-way, 4-pole 3-way, 2/3. 2-pole 11-way twin wafer, 5/-. 1-pole 12-way single wafer, 4/-.
- 1,200 ft. High Impedance recording tape on aluminium spool, 12/6 post paid.
- Polishing attachment for electric drills. Quarter-inch spindle, chromium-plated, 5in. brush, 3 polishing cloths and one sheep-skin mop, mounted on a 3in. rubber cup. 12/3. P. & P. 1/6. Spare sheep-skin mops, 2/6 each.

**COLLARO RC54**

3-speed automatic changer, will take 10 records mixed. Studio 'O' pick-up. £7.9.6 P. & P. 5/-. A.C. mains 200/250v.

**GARRARD RC/110**

3-SPEED AUTOMATIC MIXER CHANGER



Will take 10 records, 7in., 10in. or 12in. mixed, turnover crystal head, brand new, current model. A.C. mains 200/250 v. (List price £14.10/-)

**£7.19.6**


P. & P. 3/6.

**RADIO & T.V. COMPONENTS (Acton) LTD.**

23, HIGH STREET, ACTON, LONDON, W.3

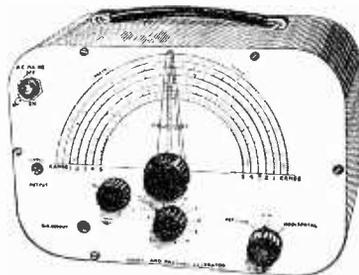**SIGNAL & PATTERN GENERATOR**

Coverage 7.6 Mc/s-210 Mc/s. in five bands, all on fundamentals, slow-motion tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1%. A.C. mains 200-250 v.



**£6.19.6**

P. & P. 5/6.

Or £3 deposit and 3 payments of 30/-.

**3-speed TRANSCRIPTION MOTOR BY FAMOUS MANUFACTURER**

Complete Kit of parts comprising accurately balanced precision made heavy turntable with rubber mat, large constant speed condenser, starting motor, base plate. Can be assembled in half-an-hour. A.C. Mains 200/250 v. Fully Guaranteed. Parts sold separately.



**£6.19.6**

Post paid.

- P.M. SPEAKERS, 6in., closed field, 13/6. 8in. closed field, 20/6.
- 10in. closed field, 25/- 12in., 25/- 3in., 16/6. P. & P. on each 2/-.
- Valveholders. Paxolin octal, 4d. Moulded octal, 7d. EF50, 7d. Moulded B7G, 7d. Octal amphenol, 7d. Octal pax, 7d. Mazda Amph., 7d. Mazda pax., 4d. B8A, B9A amphenol, 7d. B7G with screening can, 1/6. Duodecal paxolin, 9d.
- Twin-rang .0005 Tuning Condensers, 5/- With trimmers, 6/6.

**AC/DC MULTI-METER KIT**




Comprising 2in. moving coil meter, scale calibrated in AC/DC volts, ohms and milli-amps. Voltage range AC/DC 0-10, 0-100 and 0-500. Milli-amps 0-10, 0-100. Ohms 0-1,000 and 0-10,000. Front panel, range switch, wire wound pot. (for ohms zero setting) two toggle switches, resistors and meter rectifier. Complete in case, grey hammer finish. **19/6** Plus P. & P. 1/6

Point to point wiring diagram 1/- free with Kit.

Potato & Vegetable Peeler, by famous manufacturer, capacity 4 lbs. complete, with water pump. All aluminium construction, white stove-enamelled finish. Originally intended for adaptation on an electrical food-mixer, can easily be converted for hand operation. 39/6. P. & P. 3/-.

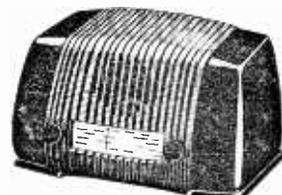**T.R.F. KIT in PLASTIC CABINET**

3 valve plus metal rectifier, A.C. mains 200-250 v. Medium and Long waves. In pastel blue or brown. Valve line-up: 2 VR65s and VT52. Size 15 1/2in. long by 9in. high by 7in. deep.



**£3.19.6** P. & P. 4/6.

Point to point wiring diagram 1/6 free with Kit.

Where post and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.



# FOR VALVES—GUARANTEED NEW AND BOXED

071	5/6	0C4	7/-	7H7	8/6	26L1	12/6	EM80	11/-	PY80	10/-	VR92 (EA50)	VU39
1A5GT	8/-	6C5GT	6/8	7C5	8/-	20P5	12/6	EV51	11/8	PX81	10/-	VR105/30	(MU12/14)
1A7	11/6	6C6	6/6	7C6	8/-	25L4GT	9/6	EV81	12/-	PX82	8/-	VR116	MU64 (U12)
1C2 DK92	9/6	6C9	10/6	7H7	9/-	23V5	9/6	EV91	8/-	Q121	6/9	VR136	8/-
1C3GT	9/6	6C10	7/6	7H7	9/-	25V30	9/9	EZ40	10/-	RP230	3/11	VR137	5/6
1B3GT	10/6	6C11	7/8	7H7	9/6	25Z11	9/-	EZ41	11/-	V22	8/-	VR150/30	8/-
1LD5	5/-	6C12	7/6	7H7	9/6	25Z5	9/6	EZ80	10/-	V25	8/-	VP23	6/6
1N5	10/6	6C13	12/-	75	10/8	25Z6GT	9/6	E1148	2/-	V25	13/6	VR21	6/6
1A3	7/6	6C14	14/-	80	8/6	35L4GT	9/-	FW4,500	13/-	V301	11/6	V25 (EL52)	8/6
1S3	7/6	6C15	14/-	85A1	5/-	35Z4GT	8/6	GZ82	12/6	VAF42	11/8	VT501 TT11	11/8
1T4	7/6	6C16	14/-	85A1	5/-	35Z5	9/-	H230	5/-	VAF41	9/-	Y63	7/6
1L5	7/6	6C17	14/-	85A1	5/-	35Z6	9/-	HL230D	8/-	VB41	10/-		
2X2	4/6	6C18	14/-	85A1	5/-	35Z7	9/-	HR210	3/11	VB41	10/-		
3D6	5/-	6C19	14/-	85A1	5/-	35Z8	9/-	KL56	8/6	VCF42	11/6		
304	9/6	6C20	14/-	85A1	5/-	35Z9	9/-	KT2	5/-	VF41	10/-		
3Q3	9/6	6C21	14/-	85A1	5/-	35Z10	9/-	KT26	10/-	VF41	11/-		
384	7/6	6C22	14/-	85A1	5/-	35Z11	9/-	KT46	15/-	VF41	10/-		
3V4	8/6	6C23	14/-	85A1	5/-	35Z12	9/-	KTW43	8/6	VR31	2/9		
4D1	3/-	6C24	14/-	85A1	5/-	35Z13	9/-	KTZ41	6/-	VR33 (EP39)	8/6		
42	8/6	6C25	14/-	85A1	5/-	35Z14	9/-	LP220	3/11	VR34 (EP34)	8/6		
5K4CY	9/6	6C26	14/-	85A1	5/-	35Z15	9/-	MH4	7/6	VR35 (EP35)	2/-		
5U4G	8/6	6C27	14/-	85A1	5/-	35Z16	9/-	MS/PEN 7 Pin	5/-	VR35 (EP35)	2/-		
5Y3GT	8/6	6C28	14/-	85A1	5/-	35Z17	9/-	N78	12/6	VR36 (EP36)	7/6		
5Z4G	8/6	6C29	14/-	85A1	5/-	35Z18	9/-	P61	3/9	VR37 (EK32)	6/-		
6A7	12/6	6C30	14/-	85A1	5/-	35Z19	9/-	P215	3/11	VR37 (EK32)	6/-		
6A81	10/6	6C31	14/-	85A1	5/-	35Z20	9/-	PC205	5/-	VR38 (EP38)	8/6		
6A27	6/6	6C32	14/-	85A1	5/-	35Z21	9/-	PCN48	7/6	VR39 (EP39)	8/6		
6A25	5/6	6C33	14/-	85A1	5/-	35Z22	9/-	PEN220A	4/-	VR65 (SP61)	3/-		
6A55	5/6	6C34	14/-	85A1	5/-	35Z23	9/-	PC284	10/-	VR65A (SP41)	3/-		
6A56	6/6	6C35	14/-	85A1	5/-	35Z24	9/-	PCF80	9/-	VR66 (PGU 3/9)	3/9		
6AK7/GAG7	8/6	6C36	14/-	85A1	5/-	35Z25	9/-	PCF82	12/6	VR91 (EP50)	4/-		
		6C37	14/-	85A1	5/-	35Z26	9/-	PCF83	12/6	VR61	6/-		
		6C38	14/-	85A1	5/-	35Z27	9/-	PCF84	12/6				
		6C39	14/-	85A1	5/-	35Z28	9/-	PCF85	12/6				
		6C40	14/-	85A1	5/-	35Z29	9/-	PCF86	12/6				
		6C41	14/-	85A1	5/-	35Z30	9/-	PCF87	12/6				
		6C42	14/-	85A1	5/-	35Z31	9/-	PCF88	12/6				
		6C43	14/-	85A1	5/-	35Z32	9/-	PCF89	12/6				
		6C44	14/-	85A1	5/-	35Z33	9/-	PCF90	12/6				
		6C45	14/-	85A1	5/-	35Z34	9/-	PCF91	12/6				
		6C46	14/-	85A1	5/-	35Z35	9/-	PCF92	12/6				
		6C47	14/-	85A1	5/-	35Z36	9/-	PCF93	12/6				
		6C48	14/-	85A1	5/-	35Z37	9/-	PCF94	12/6				
		6C49	14/-	85A1	5/-	35Z38	9/-	PCF95	12/6				
		6C50	14/-	85A1	5/-	35Z39	9/-	PCF96	12/6				
		6C51	14/-	85A1	5/-	35Z40	9/-	PCF97	12/6				
		6C52	14/-	85A1	5/-	35Z41	9/-	PCF98	12/6				
		6C53	14/-	85A1	5/-	35Z42	9/-	PCF99	12/6				
		6C54	14/-	85A1	5/-	35Z43	9/-	PCF100	12/6				
		6C55	14/-	85A1	5/-	35Z44	9/-	PCF101	12/6				
		6C56	14/-	85A1	5/-	35Z45	9/-	PCF102	12/6				
		6C57	14/-	85A1	5/-	35Z46	9/-	PCF103	12/6				
		6C58	14/-	85A1	5/-	35Z47	9/-	PCF104	12/6				
		6C59	14/-	85A1	5/-	35Z48	9/-	PCF105	12/6				
		6C60	14/-	85A1	5/-	35Z49	9/-	PCF106	12/6				
		6C61	14/-	85A1	5/-	35Z50	9/-	PCF107	12/6				
		6C62	14/-	85A1	5/-	35Z51	9/-	PCF108	12/6				
		6C63	14/-	85A1	5/-	35Z52	9/-	PCF109	12/6				
		6C64	14/-	85A1	5/-	35Z53	9/-	PCF110	12/6				
		6C65	14/-	85A1	5/-	35Z54	9/-	PCF111	12/6				
		6C66	14/-	85A1	5/-	35Z55	9/-	PCF112	12/6				
		6C67	14/-	85A1	5/-	35Z56	9/-	PCF113	12/6				
		6C68	14/-	85A1	5/-	35Z57	9/-	PCF114	12/6				
		6C69	14/-	85A1	5/-	35Z58	9/-	PCF115	12/6				
		6C70	14/-	85A1	5/-	35Z59	9/-	PCF116	12/6				
		6C71	14/-	85A1	5/-	35Z60	9/-	PCF117	12/6				
		6C72	14/-	85A1	5/-	35Z61	9/-	PCF118	12/6				
		6C73	14/-	85A1	5/-	35Z62	9/-	PCF119	12/6				
		6C74	14/-	85A1	5/-	35Z63	9/-	PCF120	12/6				
		6C75	14/-	85A1	5/-	35Z64	9/-	PCF121	12/6				
		6C76	14/-	85A1	5/-	35Z65	9/-	PCF122	12/6				
		6C77	14/-	85A1	5/-	35Z66	9/-	PCF123	12/6				
		6C78	14/-	85A1	5/-	35Z67	9/-	PCF124	12/6				
		6C79	14/-	85A1	5/-	35Z68	9/-	PCF125	12/6				
		6C80	14/-	85A1	5/-	35Z69	9/-	PCF126	12/6				
		6C81	14/-	85A1	5/-	35Z70	9/-	PCF127	12/6				
		6C82	14/-	85A1	5/-	35Z71	9/-	PCF128	12/6				
		6C83	14/-	85A1	5/-	35Z72	9/-	PCF129	12/6				
		6C84	14/-	85A1	5/-	35Z73	9/-	PCF130	12/6				
		6C85	14/-	85A1	5/-	35Z74	9/-	PCF131	12/6				
		6C86	14/-	85A1	5/-	35Z75	9/-	PCF132	12/6				
		6C87	14/-	85A1	5/-	35Z76	9/-	PCF133	12/6				
		6C88	14/-	85A1	5/-	35Z77	9/-	PCF134	12/6				
		6C89	14/-	85A1	5/-	35Z78	9/-	PCF135	12/6				
		6C90	14/-	85A1	5/-	35Z79	9/-	PCF136	12/6				
		6C91	14/-	85A1	5/-	35Z80	9/-	PCF137	12/6				
		6C92	14/-	85A1	5/-	35Z81	9/-	PCF138	12/6				
		6C93	14/-	85A1	5/-	35Z82	9/-	PCF139	12/6				
		6C94	14/-	85A1	5/-	35Z83	9/-	PCF140	12/6				
		6C95	14/-	85A1	5/-	35Z84	9/-	PCF141	12/6				
		6C96	14/-	85A1	5/-	35Z85	9/-	PCF142	12/6				
		6C97	14/-	85A1	5/-	35Z86	9/-	PCF143	12/6				
		6C98	14/-	85A1	5/-	35Z87	9/-	PCF144	12/6				
		6C99	14/-	85A1	5/-	35Z88	9/-	PCF145	12/6				
		6C100	14/-	85A1	5/-	35Z89	9/-	PCF146	12/6				

Packing and Postage—6d. per valve. SAME DAY SERVICE

**DUAL VOLUME CONTROL**  
With Double Pole Switch 500K ohms and 300K ohms. Price 6/6 each.

**TYANA SOLDERING IRON**  
Lightweight 40-watt iron, with easily replaceable elements and built 200/250 v. price 18/6 each.

**TURNOVER CRYSTAL PICK-UP CARTRIDGES**  
Acos Type HGP37-3e. Long-playing and standard with stylus (as used in latest radiograms). Price 18/6 each.

**PURETONE TAPE**  
1,500ft. Reels, Plastic Spool, 12/6 each.

**VIBRATOR UNIT**  
12 volt Vibrator Unit by Mallory, complete with vibrator, 17/6 each.

Mail Order only. For terms see our Advertisement on Page No 653



5/6 VINCES CHAMBERS  
VICTORIA SQUARE  
LEEDS 1.

## ENTHUSIASTS WHO KNOW SPECIFY



**THE DULCI RECORD PLAYER**  
Latest Model B.S.R. 4-speed Auto-changer. With turnover Crystal pick-up, spring-mounted on an attractively finished metal Plinth.  
**£10.10.0 (Tax paid)**



## MODEL GA4 HIGH FIDELITY AMPLIFIER

Very latest design Amplifier. With 3-position selector for Amp. LP and 78 RPM. With control panel on fly leads for any position fixing. Rotatable mounted transformer for hum elimination.  
**Price £9.9.0. (Tax paid)**  
Leaflets sent on request.

Full trade facilities available.

**THE VERY LATEST PRODUCTION**  
A Powerful Pre-Amplifier for the Collaro Tap Transistor correctly compensated for all 3 speeds. Manufactured and fitted to the Deck by ourselves. Specification and prices available.

**THE DULCI COMPANY LTD.**  
95 Villiers Road, London, N.W.2 Tel: WIllesden 6678

## SOUTHERN RADIO'S WIRELESS BARGAINS

**TRANSRECEIVERS.** Type "38" (Walkie-Talkie). Complete with 5 Valves. In Metal Carrying Case. Ready for use. Less external attachments. 30/- per set. ATTACHMENTS for use with "38"

**TRANSRECEIVER + HEADPHONES, 15/6; THROAT MICROPHONE** with Lead & Plug. 4/6; **JUNCTION BOX, 2/6; AERIAL 2/6.**

**TRANSRECEIVERS.** Type "18" Mark III. TWO UNITS (Receiver & Sender) contained in Metal Case. Complete with Six Valves, Microammeter, etc. LESS EXTERNAL ATTACHMENTS. 44/10/-.

**TRANSMITTERS.**—T.1154—Complete all valves, etc., etc. Perfect order. 3 frequencies. 42/7/6 in transit case. Delivered U.K.

**RECEIVERS.** Type "109." 8-Valve S.W. Receiver with VIBRATOR PACK for 6 Volts. Built-in Speaker. METAL CASE. 65.

**BOMBSIGHT COMPUTERS.** Ex-R.A.F. BRAND NEW. A Wealth of Components. GYRO MOTORS, REV. COUNTERS, GEAR WHEELS, etc., etc. Ideal for Model Makers, Experimenters, etc. 63.

**LUFBA HOLE CUTTERS.** Adjustable 1/4in. to 3/4in. For Metal, Wood, Plastic, etc. 7/-.

**RESISTANCES.** 100 ASSORTED USEFUL VALUES. Wire Ended, 12/6 per 100.

**CONDENSERS.** 100 ASSORTED. Mica, Metal Tubular, etc. 15/- per 100.

**PLASTIC CASES.** 14in. x 10 3/4in. Transparent. Ideal for Maps, Display, etc. 5/6.

**STAR IDENTIFIERS.** Type I A-N. Covers both Hemispheres. in Case. 5/6.

**CONTACTOR TIME SWITCHES.** In Sound-proof Case. Clockwork Movement. 2 Impulses per sec. Thermostatic Control. 11/6.

**REMOTE CONTACTORS** for use with above, 7/6.

**MORSE PRACTICE SET** with Buzzer on Base, 6/9. Complete with Battery, 9/6. **MORSE TAPPERS, Srd. 3/6; Midget, 2/9.**

**METERS & AIRCRAFT INSTRUMENTS.** Only need Adjustment or with broken Cases. TWELVE INSTRUMENTS, including 3 brand new Aircraft Instruments. 35/- for 12.

**CRYSTAL MONITORS.** Type 2. New in Transit Case. Less Valves, 8/-.

Postage or Carriage extra. Full List of RADIO BOOKS, 23d.

**SOUTHERN RADIO SUPPLY LTD.**  
11, LITTLE NEWPORT ST., LONDON, W.C.2. GERrard 6653

# MATCHED CRYSTALS

HOW TO BALANCE A PAIR OF CRYSTALS FOR AN F.M. CIRCUIT

By A. M. St. Clair

**M**OST of the F.M.-V.H.F. units designed for, or by, the amateur constructor make use of a ratio detector, embodying a pair of so-called "matched crystals." In commercial apparatus we usually find a double-diode valve. It is worth examining, therefore, the relative merits of the two methods. Let us first look at the pair of matched crystals, without specifying at the moment precisely what is meant by the term "matched."

Crystals (usually germanium diodes) need no heater supply; they eliminate a valveholder from the chassis; they are compact, which is not only an advantage in itself, but enables the discriminator wiring to be made neater and more efficient; and the absence of heater wiring means the elimination of a danger spot which, in the case of the valve, often leads to the unwanted distribution of I.F. ninth harmonic all over the chassis.

Against all this the valve appears able to offer only a slightly increased detection efficiency and a much higher reverse resistance. Since neither of these considerations is of the first importance in the application being considered, and since a pair of crystals may be purchased at a lower cost than that of a suitable valve, we may well ask where the snag is. And, of course, it resides in that word "matched."

The writer was recently engaged on a design which called for a ratio discriminator, using crystals, and giving a really Hi-Fi performance. This occurred at the time of the last radio show, and he therefore repaired to Earls Court and made a round of several of the manufacturers offering germanium diodes, seeking information on the subject of matching procedures. Although one representative claimed that all the crystals produced by his firm under a certain type number were, in fact, matched, subsequent investigation proved this to be untrue. As for the rest, the consensus of opinion was: "Not really a recommended application." So, thrown back on his own

devices, he returned to his bench, where the following method was worked out.

### Difficulties

First let us consider the difficulties. Supposing we try the obvious thing, matching forward and reverse resistances. Suppose, further, that we try to do this by means of a meter. To see what is likely to happen, look at Fig. 1. This shows the voltage-current curve of a typical germanium diode. Looking at the forward characteristic, let the voltage applied by the meter to the crystal be  $V$ . This brings us to the point B on the curve, and the current passed is therefore  $I$ . The meter thereupon indicates a resistance of  $V/I$  ohms, corresponding to the slope of the line OB. But the true resistance of the crystal, working at a mean applied voltage  $V$ , with an A.C. signal which is not too large, i.e., which does not drive it into serious non-linearity, corresponds to the slope of the curve at the point B, which is the same thing as the slope of the tangent line AB. The correct reading should thus be (volts difference between A and V)/ $I$  ohms. The ohm-meter method fixes a point on the characteristic curve, but tells us nothing about the slope of the curve. Hence, a pair of crystals matched by this method will probably have curves similar to those shown in Fig. 2. A meter which has  $1/5$  of a volt across its terminals when passing 1 mA from its internal battery will read each as 200 ohms, while the actual dynamic resistances at the point B are 50 ohms for curve X and 150 ohms for curve Y. The differences actually encountered may not be so great as these, which have been chosen for clarity in the diagram, but they are big enough to invalidate the ohm-meter method.

Now before the "experts" dash off to design methods for measurement of dynamic resistance at the working point, or for displaying the whole characteristic on the C.R.T., let me point out a few

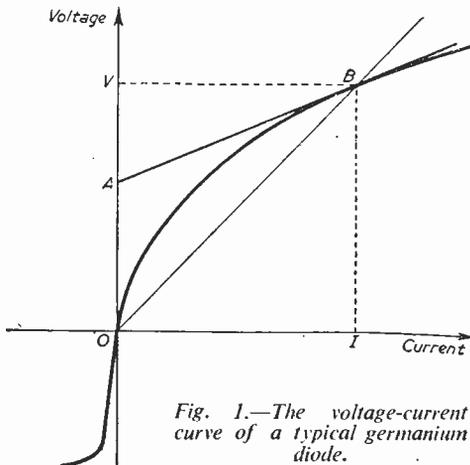


Fig. 1.—The voltage-current curve of a typical germanium diode.

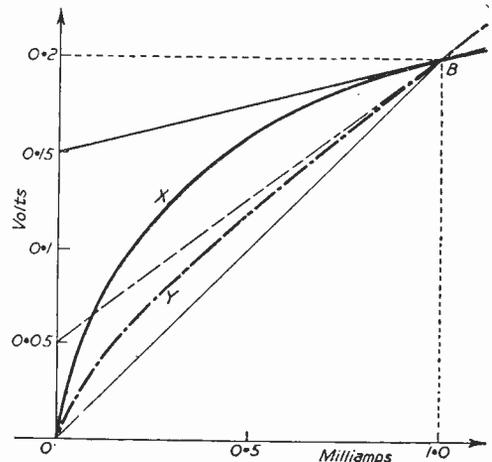


Fig. 2.—Curves for a test pair of crystals.

other things. First, when using a ratio discriminator the "working point" of the crystals is not easy to define. In Fig. 3, which shows the relevant portions of a ratio discriminator, the crystals are seen to be partially backed off by the electrolytic condenser C. Where there is no limiter, or where the final I.F. amplifier is worked as a semi-limiter (the normal practice), the voltage across this condenser will vary with signal strength, and the operating point of the crystals with it. Hence you may find that a pair of crystals which are balanced for the Third Programme are quite otherwise on the Light. And even if you do go to the trouble of designing a jig for matching characteristic curves, you may still find that you have not achieved a perfect match in operation. From a variety of reasons for this two should be mentioned

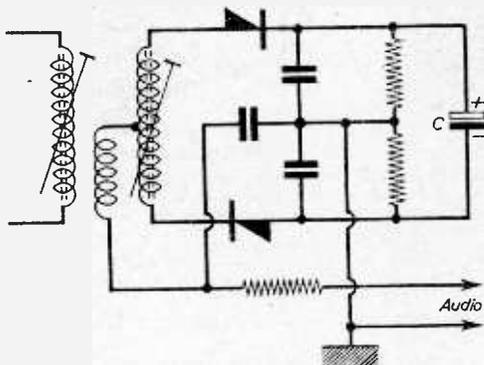


Fig. 3.—A ratio discriminator.

First, in most F.M. discriminators the output is basically the difference between two quantities of the same order of size; hence small variations in the nature of these quantities may produce large variations in the nature of the output; and, secondly, the presence of the electrolytic condenser in the ratio discriminator introduces complexities into the mode of operation of the crystals, one of which is the increase of audio voltage across them to a degree sufficient to affect their performance. (Crystal matching is much less critical in the Foster-Seeley discriminator.)

What is required, then, if we are to avoid making a very large number of measurements on each crystal, is a "performance match," accomplished under something like working conditions. Let us suppose, first of all, that we have a perfectly matched pair of crystals; that is to say, it is impossible to tell them apart by any electrical test. It is obvious that the performance of a discriminator using these crystals will be quite unaffected if we interchange them, so that each is wired in the position previously occupied by the other, and this quite independently of any considerations of accuracy of balance in the discriminator itself. Thus, if we interchange the crystals in a discriminator, the degree of misalignment caused is an indication of the mismatching of the crystals. It is too severe a check in the case of the ratio discriminator, however, and a better method of proceeding is as follows.

### The Procedure


Disconnect the electrolytic. Insert a pair of crystals. (It is as well in performing these tests to provide some form of simple spring clip for the crystals. It not only

facilitates the work, but it avoids too much soldering and unsoldering of the crystals, which is likely to impair them.) Adjust the discriminator for zero audio output, as in the normal procedure for alignment. Interchange the crystals. Leaving the discriminator adjustments unchanged, reset the signal generator to obtain an audio null once again. Note the change required, write it on a piece of paper and attach the paper to either one of the crystals. The other crystal remains in the discriminator and provides the "base line" for the tests. Identify it with a spot of red paint or in some other unmistakable manner. Make no further adjustments on the discriminator or on the unit of which it is a part; for the rest of this test only the signal generator is adjusted. Insert a fresh crystal in the position vacated by the one you have just tagged, and adjust the signal generator again for null. Note the reading. Reverse the crystals, readjust for null, note the reading. Tag the crystal with the two readings. Repeat for all the available crystals. In this way all the crystals except the red spot reference one will have two readings attached. (The second reading of the first crystal is the original balance point, which should of course be the correct I.F.—usually 10.7 Mc/s.) These readings should be identified according to the side of the discriminator on which they were obtained, e.g., a given crystal might be marked "Right, 10.72 Mc/s; Left, 10.64 Mc/s." To obtain markings for the "red spot," find the crystal which has the least difference between its two figures, and use these figures. If you have no crystal whose figures are within 0.02 Mc/s, then you have no crystal which will match well with the "red spot," and it should be left out of further consideration.

Now arrange the crystals in order according to their markings. If they are arranged with reference to, say, the right-hand figures, then the left-hand figures should also be reasonably closely ordered. If this is not so, then either an error has been made or an unfortunate choice of a poor reference crystal. If you set the crystals in order of right-hand figures as they come off the first test you will be able to spot discrepancies here, before too much effort has been wasted. Select a pair of crystals having reasonably similar figures to each other. (The exact meaning of "reasonably similar" will, of course, depend largely on the number of crystals you are working with.) Place them in the discriminator. Adjust the signal generator to the correct I.F., and the discriminator for correct balance (audio null). Interchange the crystals. The readjustment required on the signal generator to restore balance should be small compared with those needed in the first part of the testing. If it is not, try another pair of crystals—change only one if you have several with closely corresponding figures. When you have found a suitable pair, leave the discriminator in balance and reconnect the electrolytic. Readjust the discriminator transformer secondary to restore balance, if necessary. If only a trivial adjustment is necessary the pair is matched.

Starting with about a dozen crystals you may hope for perhaps two well matched pairs. The remainder are not necessarily bad crystals—you just do not happen to have suitable mates for them. The larger the number you start with, the higher will be the percentage yield, and the more rigorously will you be able to interpret closeness of readings and "triviality" of adjustments. The more you have, the more pairs you get, and the better the pairing.

# RISF *Quality reproduction*

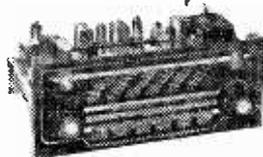


## RADIO AND RADIOGRAM CHASSIS

Designed to the highest standards. General specifications applicable to all models: 200/250 volts A.C. 50 cycles. Horizontal multi-coloured glass dial. Slow motion tuning. Full Automatic Volume Control. Negative feed-back from output transformer secondary. Aerial, Earth, Gram, Pick-up and Extension Speaker sockets provided. Connections provided to Gram. Wide range tone controls for all types of recordings.

**WESTFIELD.** 5-valve superhet. 3 wavebands. **12 Gns.**  
Packing & Carriage 12/6.


**MANSFIELD.** 7-valve superhet. 4 wavebands, including F.M./V.H.F. Band. **23½ Gns.**  
Packing & Carriage 15/-.

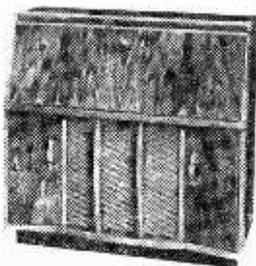**HEATHFIELD.** 9-valve superhet. 4 wavebands, including F.M./V.H.F. Band. Push-pull output. **26 Gns.**  
Packing & Carriage 15/-.


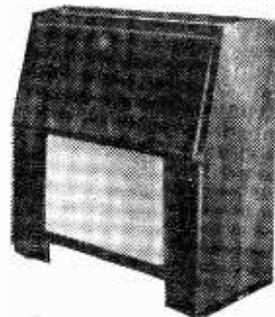
## THE APEX CABINET

High quality Bureau-type cabinet in selected Walnut veneered exterior with Light Sycamore interior and matching Rexine lining. Dimensions: Width, 34 ins. Depth, 17½ ins. Height, 33 ins. Sloping control panel on right-hand side, 16 ins. x 10½ ins. approx. Removable baseboard on right side, 15½ ins. x 15 ins. approx. **16½ Gns.**  
Packing & Carriage 25/-.



## THE EXCEL CABINET


Medium size, high quality Bureau-type cabinet in highly figured Walnut veneer. Dimensions: Width, 29½ ins. Depth, 16 ins. Height, 32 ins. Sloping control panel on right-hand side, 13 ins. x 10 ins. approx. Removable baseboard on right side, 13½ ins. x 13 ins. approx. Record compartment inside cabinet. **15 Gns.**  
Packing & Carriage 15/-.

## AUTOMATIC RECORD CHANGERS ★

Latest-type four-speed auto-changer, incorporating 16 r.p.m. for "talking-books" and arrangement for manual control. Fitted with high-fidelity H.G.P. 37. Crystal Turn-over Pick-up head. A.C. mains 200/250 volts. 50 cycles only. **£9.15.0.**  
Packing & Carriage 12/6.

Latest Garrard R.C. 88 Model fitted with G.C.2 Crystal Turn-over Pick-up head. A.C. 200/250 volts. 50 cycles. **£13.0.0.**  
Packing & Carriage, 12/6.

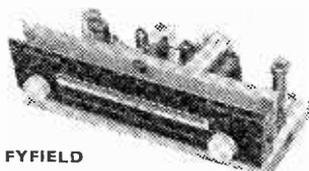★ **LOUDSPEAKERS, Gram Amplifiers, etc.**  
Available at keenest Prices



## FYFIELD

F.M./V.H.F. Tuner in chassis form suitable for building into existing Radiograms or Receivers. **£13.15.0**  
Packing & Carriage, 12/6.

## F.M./V.H.F. TUNERS

These tuners are designed for maximum sensitivity and best signal to noise ratio. Eminently suitable for fringe-area reception. High stability capacitors are used at all critical points and drift is less than 20 kilocycles on any part of the band. 200/250 volts A.C. 50 cycles only




## CHESTERFIELD

F.M./V.H.F. Tuner Unit with automatic Magic Eye tuning, fitted in high-grade dark Walnut cabinet. Self-powered and completely self-contained. **16½ Gns.**  
Packing & Carriage, 12/6.

**ALL FULLY GUARANTEED**

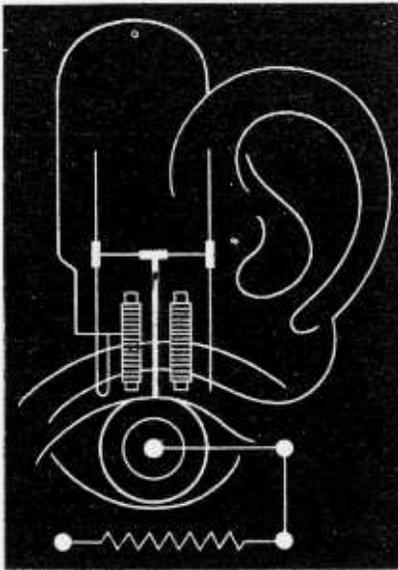**COMPLETE CATALOGUE AVAILABLE ON REQUEST**

**RADIO INSTRUMENT SUPPLY FACTORY**  
STATION ROAD · HAROLD WOOD · ESSEX · INGREBOURNE 2935



## SMITH'S FOR TECHNICAL BOOKS

Books on radio theory, practice and maintenance for the beginner and books on new developments in circuit design, new components, methods of application, and the established text books can be obtained through your local Smith's shop or book-stall. Books not in stock at the branch can be quickly obtained from Head Office.

★ Your stationery and printed matter can also be supplied through our local branch.

## W. H. SMITH & SON

FOR BOOKS ON ELECTRONICS

Head Office: STRAND HOUSE, LONDON, W.C.2

## It's NEW . . . .

### The "GOOD COMPANION"

A winner in appearance and performance, you can make this fine Battery Set in your leisure time

**Portable**

- ★ 4 VALVE SUPERHET
- ★ MEDIUM AND LONG WAVES
- ★ EQUAL TO PROFESSIONAL SET
- ★ NEW "FAULTLESS TECHNIQUE"
- ★ ONLY 7 Gns.

Pliers, screwdriver and soldering iron plus our NEW Construction Technique enables "Stage by Stage" building without any confusion by the "FAULTLESS METHOD."

**YOU CANNOT GO WRONG!  
GUARANTEED TO WORK!**

Write today for the "KNOW-HOW" on the GOOD COMPANION Battery Portable. Full Instructions and "FAULTLESS TECHNIQUE." ONLY 1/6 POST FREE.

"BEGINNERS SUPERHET" . . . a 5 Valve Superhet for ONLY 139/6 plus 2/8 Post and Packing.

METEOR III TRF . . . a 3 Valve set with a BIG output at ONLY 109/6 plus 2/8 Post and Packing.

Send TODAY for "KNOW-HOW" and Diagrams on any (or BOTH) of the above. ONLY 1/- each Post FREE.

**NORMAN H. FIELD (Electronics)**

Dept. P.W., 68, HURST STREET, BIRMINGHAM 5  
Birmingham's Largest Constructors' Store.

**COMMUNICATIONS RECEIVER R.1155.**—The famous Bomber Command Set. Covers 18.5-7.5 Mc/s, 7.5-3.0 Mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s. 'B' Model with super slow motion tuning. ONLY £10.10.6, tested working before despatch and supplied with 14-page booklet which gives technical information, circuits, etc. (available separately 1/3).

**A.C. MAINS POWER PACK OUTPUT STAGE**, in black metal case. Enables receiver to be operated immediately by just plugging in. Supplied WITH built-in speaker £5.5.0 or LESSER speaker, £4.10.

DEDUCT 10/- IF PURCHASING RECEIVER & POWER PACK TOGETHER.

Add carriage costs of 10/6 for receiver, 5/- for power pack.

**AMERICAN "COMMAND" RECEIVERS.**—Huge purchase from the Air Ministry. These famous compact receivers which can be used for a variety of purposes are offered at ridiculously low prices while stocks last. Complete with 6 metal type valves, 1 each of 12S3, 12SR7, 12A6, and 3 of 12SJ7, in aluminium case size 11" x 5 1/2" x 5". Used, but in very good condition, although cases may be somewhat dented. Circuits supplied. First come first served. Choice of models, BC455 (6-9 mc/s), £5/-, BC454 (3-6 mc/s), 27/6, BC453 (100-550 kc/s, the renowned "Q" Flyer), 59/6, and a few of the 1.5-3.0 mc/s. model 65/- (Carriage, etc., 3/-).


**COLLINS TCS TRANSMITTERS.**—Special offer of these famous American Transmitters. Frequency range 1.5-12.0 mc/s. in 3 bands. Employs 7 valves, 2 of 1625 in P.A. Stage, 1625 buffer and 1625 modulator Stage, 3 of 12A6 in oscillator stage. Radio telephone or radio telegraph. Provision for VFO or Crystal Control, 4 crystal positions. Has plate and aerial current meters. In BRAND NEW CONDITION, ONLY £12.10.0. Matching receivers available £8.10.0, or THE PAIR £20. (Carriage 10/- each.)

#### CLASS D WAVEMETER

Another purchase of this famous crystal-controlled wavemeter which has been repeatedly reviewed and recommended in the "R.S.G.B." Bulletin as being suitable for amateur transmitters. Covers 1.0-0.1 mc/s, and is complete with 100/1,000 kc/s crystal, 2 valves ECH35, two 6-volt vibrators and instruction manual. Designed for 6 v. D.C. operation, but simple mod. data for A.C. supplied. BRAND NEW IN MAKER'S TRANSIT CASES, ONLY £5.19.6. Transformer for A.C. modification, 7/6.

**U.E.I. CORPORATION** 138, Gray's Inn Road, London, W.C.1. (Phone: FERminus 7927)  
Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station), and 5 mins. by bus from King's Cross.

# Servicing Radio Receivers

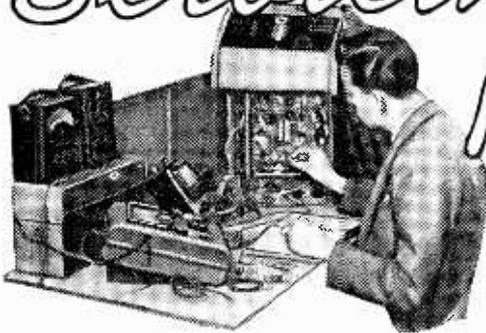

KOLSTER-BRANDES MODEL FB10FM

By Gordon J. King, A.M.I.P.R.E.

**T**HIS is a small transportable receiver for reception of the V.H.F.-F.M. transmissions only, and can also serve as an efficient F.M. adaptor for coupling to the audio circuits of more elaborate radios and radiograms or act as an F.M. tuner in front of an A.F. amplifier or record reproducing unit.

It features an inbuilt power unit for A.C. mains only, contains four valves, plus metal rectifier, and is housed in a plastic cabinet of contemporary design. It is of very similar appearance—using the same kind of cabinet—to the Kolster-Brandes "A.M. only" transportable—Model FB10.

As the receiver was first released in 1955, it has not been in the field long enough to exhibit so-called "stock faults" and consistent characteristics which generally show up after three or four years' service. Nevertheless, it was considered desirable to use this somewhat simple model to introduce to our readers the current trend in the design of commercial F.M. receivers. A knowledge of this model may also be of assistance to the many readers who have requested information for converting their existing receivers for the reception of F.M.

*This is the final article in the present series. Next year a new series will commence and will include combined A.M./F.M. models, and receivers using transistors.*

## The Circuit

A complete circuit of the receiver/adaptor is shown at Fig. 1. As will be seen, the first valve VI is a double-triode; section A is used in the form of an earthed-grid R.F. amplifier, while section B is arranged as a self-oscillating frequency changer. This mode is truly representative of the R.F./frequency changer stages of almost all commercial receivers, whether for both systems or just F.M. With combined receivers, however, this double-triode "front-end" is generally built into a small metal case.

The dipole signal is applied to the cathode of the R.F. amplifier triode across L2 by way of the small coupling coil L1. The resistors and capacitors in L1 circuit simply isolate the aerial from the receiver chassis which, as will be seen, is connected to one side of the mains supply. The grid of VIA is con-

nected directly to chassis, and the amplified dipole signal occurs across the R.F. coil L3 in the anode circuit.

Since the impedance at the cathode of VIA is extremely low, L2 is heavily damped by this low impedance and also by the dipole. It thus responds over the entire F.M. band (Band II) and needs no variable tuning. L3, however, being in a much higher impedance circuit, needs to be tuned for optimum response over the band, and this is achieved by C1 section of the tuning gang.

L5 is the oscillator coil, which is tuned over the band by C2 section of the gang. Feed-back coupling is secured by coil L4 in the grid circuit of V1B. The signal across L3 is coupled to the grid of V1B at the junction of two capacitors across L4. These two capacitors in conjunction with the inter-electrode capacitances of V1B and the capacitor on the "earthy" side of L4 form a bridge circuit of somewhat delicate balance.

When the balance is achieved, there exists very little or no oscillator voltage at the junction of the two capacitors across L4. Such a bridge circuit is a salient feature of all F.M. "front-ends," since it precludes feed-back of the oscillator signal, via the R.F. stage to the aerial. This avoidance of oscillator

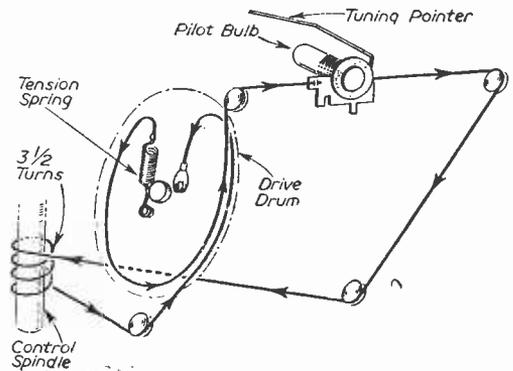


Fig. 4.—Details of the dial drive.



# COMPLETE KITS OF PARTS for the "HI-FI" ENTHUSIAST

The MULLARD "5-10" MAIN AMPLIFIER



This is the very latest design and needs no recommendation from us. Our Kit is complete to Mullard's specification, including the latest GILSON ULTRA LINEAR OUTPUT TRANSFORMER and the entire MULLARD Valve line up. ALL SPECIFIED COMPONENTS are supplied. **PRICE OF COMPLETE KIT OF PARTS £11.10.** (Plus 5/- carr. & ins.)

The full SPECIFICATION and PRACTICAL BUILDING INSTRUCTIONS for these Units are available for 1/6 each. SPECIAL PRICE REDUCTION. We supply the two complete Kits—Mullard 5-10 and "fidelity" Preamplifier—for £16.16.0. We also supply both fully assembled and ready for use for £19.19.0.

STERN'S "fidelity" PRE-AMPLIFIER-TONE CONTROL UNIT.

"A design for the music lover"



Briefly it has inputs for all types of MICROPHONES, HIGH and LOW GAIN PICK UPS and a RADIO TUNING UNIT. It incorporates, (a) GRAM EQUALISING CONTROL, (b) STEEPCUT FILTER, (c) Continuously variable BASS and TREBLE CONTROLS and a variable OUTPUT CONTROL which enables its use with any type of Amplifier. **PRICE OF COMPLETE KIT OF PARTS £6.6.0.** (Plus 5/- carr. and ins.) WE ALSO OFFER IT ASSEMBLED, READY FOR USE, £8.



STERN'S 'HIGH QUALITY' 8-10 WATT AMPLIFIER

Has power supply for Radio Tuning Unit.


**PRICE OF COMPLETE KIT OF PARTS (Plus 5/- carr. & ins.) £7.10.0.** SUPPLIED ASSEMBLED and READY FOR USE. **£9.10.0.** Proved one of the most popular models yet offered to the HOME CONSTRUCTOR. Provides excellent reproduction up to 8 watts, employing 6V6's in push pull, incorporating negative feedback. Provides for use of both 3 and 15 ohm speakers.

## MODERNISE YOUR OLD RADIOGRAM

The NEW ARMSTRONG PB.409 A.M., F.M. Radiogram Chassis

"A chassis for those who want the highest quality."

- A 9 Valve line up employing the latest MULLARD preferred-type Valves.
- Provides complete coverage of the V.H.F./F.M. Transmissions plus the Short, Medium and Long Wavebands.
- Has Push-Pull Output, with Negative Feedback, for 6 watts peak Output.
- Quick Action "Piano Key" Selectors and separate Bass and Treble Controls.
- Has "Magic Eye" Tuning Indicator.
- Two Gram Inputs are provided, one for Crystal Pick Ups and the other for Magnet types.
- Dimensions 13in. x 9 1/2in. x 8in. high. Dial size 1 1/2in. x 5 1/2in.

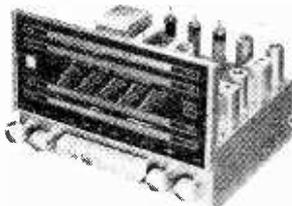

PRICE £29.8.0.

(Plus 6/- carriage and insurance.) TERMS: (a) Hire Purchase: Deposit £7.7.0 and 9 monthly payments of £2.14.0. H.P.: £17.14.0 and 12 monthly payments of £1.7.3. Send S.A.E. for illustrated leaflet.

- ★ THE LATEST A.M., F.M. RADIOGRAM CHASSIS.
- ★ A NEW 4-SPEED AUTOCHANGER.

## COMPLETE YOUR RADIOGRAM WITH ONE OF THESE LATEST 4-SPEED RECORD PLAYERS

We offer the PFB409 and :-  
★ The Collaro Model 456 for £39.7.0. Terms : Deposit £9.16.9 and 9 monthly payments of £3.12.2 or H.P. Deposit £19.13.6 and 12 monthly payments of £1.16.6.  
★ The B.S.R. MONARCH for £37.7.0. Credit : Deposit £9.7.0 and 9 monthly payments of £3.8.7. H.P. : Deposit £18.14.0 and 12 monthly payments of £1.14.8.  
Each of these Players has the Manual Control Position. (Carriage & Insurance on above combinations is 10/- extra.) Recommended Speakers for this very high quality equipment are (a) W.H. Stentorian 8in. H.F.E. £4.3.6. (b) W.H. Stentorian 10in. HF1012, £4.19.8.

## RECORD PLAYERS THE VERY LATEST MODELS GREATLY REDUCED PRICES

★ TRANSCRIPTION UNITS. ★ 3 and 4 SPEED AUTOCHANGERS. ★ AUTOCHANGERS WITH MANUAL CONTROL POSITION. Send S.A.E. for ILLUSTRATED and DESCRIPTIVE LEAFLET.

### STERN'S "F.M." TUNING UNIT

A 5-valve Tuner incorporating the latest Mullard Permeability Tuning Heart and a "Magic Eye" Tuning Indicator.


PRICE ASSEMBLED & READY FOR USE: £14.10.0.

(Plus 7/6 carriage and insurance.) TERMS: (a) Hire Purchase: Deposit £7.5.0 and 9 monthly payments of 18/4. (b) Credit: Deposit £3.12.6 and 9 monthly payments of £1.6.7.

THE COMBINE A.M.-F.M. UNIT is precisely similar in appearance to the above and incorporates 7 valves. It provides complete coverage of F.M. Transmissions and MEDIUM WAVEBAND giving a good selection of foreign stations.

PRICE £18.18.0

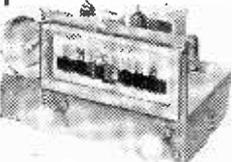(Plus 7/6 carr. & ins.) TERMS: (a) Hire Purchase: Deposit £9.9.0 and 10 monthly payments of £1.1.0. (b) Credit: Deposit £4.15.0 and 9 monthly payments of £1.4.7.




## AN EXCEPTIONAL "CASH ONLY" OFFER £7.19.6.

(Plus 5/- carr. & ins.)
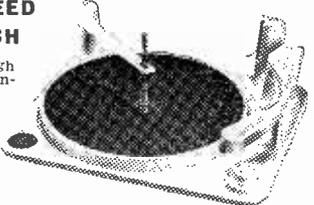
### THE NEW 4-SPEED B.S.R. MONARCH


- Complete with High Fidelity Crystal "Turnover" Head which incorporates separate stylus for L.P. and 78 r.p.m. records. ● A "MIXER" Unit that will autochange on 7in., 10in. and 12in. records of same speed.
- Incorporates the Manual Control position.



(a) The "COMPACT 5-2" A Two-stage high sensitivity Amplifier having SEPARATE BASS and TREBLE CONTROLS and designed to give up to approx. 5 watts with very pleasing quality. PRICE £5.15.0. (Plus 5/- carr. & ins.)

(b) The "COMPACT 5-3" A Three-stage version of the "5-2" model but in this case having an additional stage and incorporating Negative Feedback. PRICE £6.16.0. (Plus 5/- carr. & ins.)

### STERN'S "COMPACT 5" AMPLIFIERS

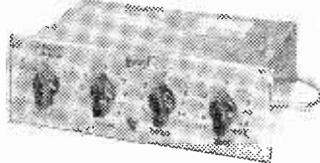


Expressly developed for very high quality reproduction of Gram. Records and particularly suitable for high quality reproductions of the F.M. transmissions. Two models are available: A separate POWER SUPPLY UNIT to operate with these amplifiers is available for £2.10.0. Has additional supply available for Radio Tuner, etc.

### CALLERS ONLY

We have in stock various Kits of Parts including F.M. Tuners, A.M. F.M. Tuners, Midget Battery Portable, Mains Units, etc. etc.

STERN RADIO LTD. 109 & 115 FLEET STREET, LONDON, E.C.4.

Telephone: FLEET 5812/3/4

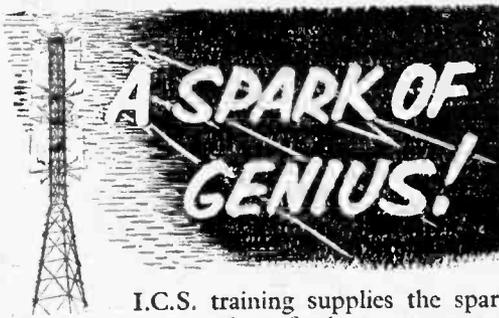

I.C.S. training supplies the spark you need to further your career. The Courses I.C.S. offer are practical and up-to-date, they recognise the present emphasis on Frequency Modulation, and can help you attain one of the many well-paid posts that exist today in the radio world. Prepare yourself now, at home and in your own time, with the expert help of I.C.S. tutors. The cost of an I.C.S. Course is moderate and includes all books.

Among the I.C.S. Courses available are:

- FREQUENCY MODULATION ENGINEERING
- T/V ENGINEERING
- RADIO SERVICING
- RADIO ENGINEERING
- RADAR ENGINEERING
- BASIC ELECTRONICS
- INDUSTRIAL ELECTRONICS
- ELECTRONIC ENGINEERING

Complete the coupon below and post it to us today for further details of the Course which interests you. Write to: Dept. 170E, I.C.S., 71 Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS  
 DEPT. 170E, INTERNATIONAL BUILDINGS, KINGSWAY, LONDON, W.C.2.

Please send FREE book on .....

NAME..... AGE.....  
 (Block letters please)

ADDRESS .....

OCCUPATION ..... 12/56

**INTERNATIONAL  
 CORRESPONDENCE SCHOOLS**

# ADCOLA

PRODUCTS LIMITED  
 (Regd. Trade Mark)

## SOLDERING EQUIPMENT

### ILLUSTRATED

3" Detachable bit type (List No. 64)

Protective Shield (List No. 68)

Catalogues sent FREE

Telephones:  
 MACaulay 4272 & 3101



British and Foreign Pats.

Reg. Designs, etc.

Head Office, Sales:

**ADCOLA PRODUCTS LTD.**

Clapham Road, St., London, S.W.4

TUBES  
**T.V. GUARANTEED £5**  
 6 months


17" Rectangle £7. 10. 14" Rectangle £5. 10  
 16" 15" 14" Round £5

PLEASE NOTE.—A 15" or 14" T.V. tube can be fitted in place of a 9" or 12" with little or no alteration. 15 1/2 ins. carr. on each tube. 12" round type and smaller sizes please enquire and give alternative, if possible, as heavy ordering may cause delay in delivery.
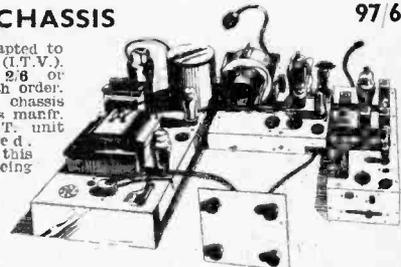
### T.V. CHASSIS

97/6

Easily adapted to Band 3 (I.T.V.). Drawing 2/6 or FREE with order. Complete chassis by famous manf. R.F. E.H.T. unit included. Owing to this chassis being in 3 separate units (power, t. base and s/ vision inter-connected), it is easily fitted to table or console model. This chassis is less valves and tube. Ins. and carr.: London 6/1, state B.B.C. Channel—Provinces 10/-. Our E5 tube fits this chassis. Catalogue on request for cheap valves, Channels 1-3 or 4-5; many clients have successfully converted to 14 and 15" tubes. I.F.'s are 16.5—19.5 mc/s vision high. I.T.V. channel 6-13 easily converted.



REMEMBER SATURDAY OPEN ALL DAY

**DUKE & CO.**

621, Romford Rd., Manor Park, London, E.12

GRA 6677-8.

anode circuit across the second I.F. transformer I.F.T.2. This is a fairly conventional stage, and one to which we have become accustomed in A.M. sets. The wide bandwidth is maintained due to the damping effect of the valves and circuits at 10.7 Mc/s. This second I.F. transformer is often referred to as the "discriminator transformer," for it is this, in this set anyway, which feeds the F.M. discriminator.

Here the discriminator is in the form of the popular ratio detector, comprising double-diode V3 A/B and associated resistor and capacitor. The circuit is of the unbalanced variety, and the audio signal is taken from across the 300 pF capacitor in the tertiary winding of the transformer. For those readers who require a full description of the working of the ratio detector, reference should be made to PRACTICAL WIRELESS, November, 1955, under the article entitled "Understanding F.M. Discriminators."

It will be seen that the two diodes are connected in series across the centre-tapped secondary of the transformer, and that the circuit is completed through the resistor-capacitor parallel combination. This section forms a time-constant and serves to endow the detector with the feature of amplitude limiting, since the time-constant is relatively large compared with the duration of a pulse of amplitude interference. The A.F. load consists of the volume control R1; and from this is fed the required level of A.F. to the grid of the triode section of V3(V3C).

Valve V3 is, in fact, one of the new range developed primarily for use in F.M. receivers. It features three diodes and a triode. Usually, the diode shown earthed in V3C section is used as the A.M. detector diode in combined sets. It serves no useful purpose, however, in the circuit under discussion.

The triode acts as an A.F. amplifier in conventional mode. The amplified A.F. appears across the 470K resistor in the anode circuit, and is coupled by way of the 0.02  $\mu$ F capacitor to the control grid of the output pentode V4.

The output transformer and associated circuitry is rather interesting. The primary of the transformer is tapped as a means of neutralising hum in the output stage. It will be seen that the output of the metal rectifier is connected to one side of the primary, and that H.T. for the rest of the receiver is picked up from the tap; the other side, of course, connects to the anode of the output valve in the usual manner. There are two secondary windings. One is the normal one for driving the loudspeaker, while the other is a spare which is connected to the adaptor output terminals, and it is from here that the signal is taken for operating a separate A.F. amplifier when the adaptor facility is required.



Switches S3, S4, S5 and S6 are ganged and form the receiver/adaptor switch (see Figs. 2 and 3). When the receiver is operated on its own internal loudspeaker switches S3, S4 and S5 close and S6 opens. In the "adaptor" position of the control, however, S3

opens and reduces the H.T. voltage by introducing an extra 220-ohm resistor in the H.T. feed; S4 opens and introduces negative feed-back by disconnecting the 50  $\mu$ F electrolytic capacitor in the cathode of V4; S5 opens and disconnects the loudspeaker; and S6 closes and connects a dummy load L6 in place of the loudspeaker across one of the transformer secondaries.

Tone correction and de-emphasis is provided by the 0.01  $\mu$ F capacitor and series connected 1 K resistor across the primary of the output transformer. Considerably enhanced response occurs in the "adaptor" position owing to the introduction of negative feed-back in the output stage.

H.T. is provided by the metal type rectifier MR1 (type 18RA2N1151), and smoothing is aided by electrolytic unit comprising C3, C4 and C5. It will be noted that an auto mains transformer is employed and that one side of the mains is connected to receiver chassis. The chassis, therefore, might well be live to earth. Switch S1/S2 is the on/off switch and is ganged to the volume-control R1.

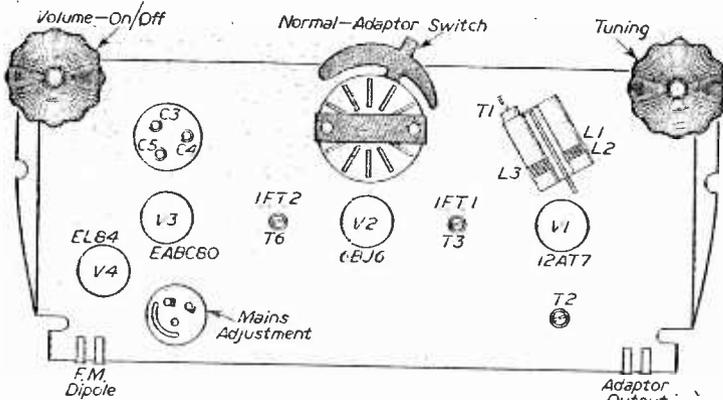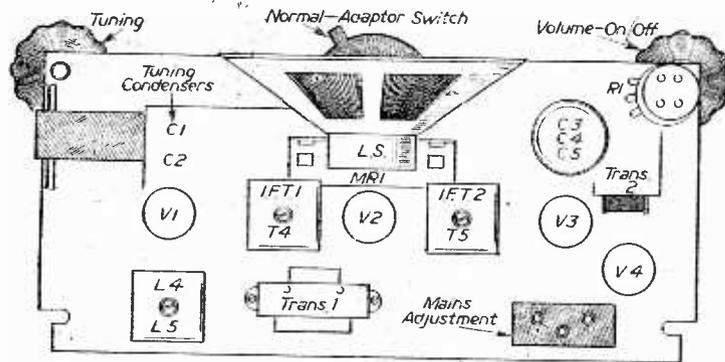It should be mentioned that some earlier versions adopted a valve type EZ80 rectifier in place



Figs. 2 (top) and 3 (lower).—Top and bottom chassis details.

of the currently used metal rectifier. Also, instead of an EL84, a 6AM6 valve was used in the output stage.

Sufficient output is available from the adaptor sockets to drive fully the A.F. stages of most "A.M. only" receivers and audio amplifiers. When the adaptor facility is utilised it is often necessary to attenuate the signal by means of resistor pads to prevent overloading and to maintain a correct match. It is general practice to connect the adaptor signal to the pick-up sockets of radios and radiograms. Stand-off resistors can be used to prevent the adaptor, where permanently connected to a radiogram, from shunting the pick-up signal.

Fig. 4 illustrates the tuning drive system. Nylon drive-cord should be used when replacement becomes necessary, and a total length of about 40in. is required.

### Alignment

Optimum performance is achieved only when the circuits are accurately aligned, and this applies particularly to I.F.T.2. For best results the use of a wobblulator and oscilloscope are required. Details of this method of alignment are given in the March, 1956, issue of PRACTICAL WIRELESS.

The method outlined, though not as accurate as the wobblulator/oscilloscope method, often serves.

A D.C. voltmeter should be connected across the 39 K resistor in the ratio detector diodes circuit, with the positive side of the meter to the chassis connection. With a 10.7 Mc/s unmodulated signal applied to the control grid of V2, trimmer T5 should be adjusted for maximum voltage reading. It is desirable, initially, to unscrew trimmers T5 and T6 until they are half-way out of their formers.

The signal should now be transferred to point one

on the circuit, and trimmers T3 and T4 adjusted for maximum voltage reading. With the signal very loosely coupled to the first stage, by connecting the "live" generator lead to a nearby earth point, trimmers L5, L3 and L4 should be adjusted, in that order, for maximum voltage reading. It may be necessary to put in a larger signal than hitherto for these adjustments.

The voltmeter should now be removed from across the 39 K resistor, and in its place should be connected two accurately matched series-connected resistors. A microammeter should be connected between the junction of these resistors and point two on the circuit.

A 10.7 Mc/s unmodulated signal should again be connected to point one on the circuit and trimmer T6 very carefully adjusted for zero reading on the microammeter, which will occur midway between a negative-going and positive-going indication. Since T6 was initially unscrewed for the previous adjustments, it will have to be screwed in correspondingly to reach the point of balance.

Before making any of the foregoing adjustments, the mains should be connected to the set so that the chassis is on the neutral line. The "live" side of the generator should also be connected via a capacitor of 0.001  $\mu$ F. It is also desirable to connect the "earthy" side of the generator to the chassis through a similar capacitor.

Adjustments of T1 (the R.F. coil) and T2 (the oscillator coil) are best made on an actual transmission, preferably on the "Third Programme." The receiver tuning should be adjusted so that the cursor coincides with the scale frequency of the local Third Programme, and T2 should be very carefully adjusted until the signal is accurately tuned. T1 should then be adjusted for maximum sensitivity

## Scratch Filters

IT is quite possible that many readers will have shared my difficulty in obtaining details of a unit, simple in construction but at the same time efficient, to eliminate that old "bugbear" of record scratch so evident with the older 78 r.p.m. recordings.

Briefly, the equipment used by the author consists of a Collaro 2010 transcription unit fed into a Leak TL/10 pre-amp with the main amplifier output to a two-speaker system consisting of Wharfedale W12/CS and Super 8/CS/AL.

The circuit described (Fig. 1) gives excellent results with far less "top" cut than any other arrangement tried to date. Providing the unit is

kept not less than 2ft. 6in. from the mains transformer, etc., no increase in hum will occur.

By means of the trimmer condensers "cut off" frequency is variable between 5-10 Kc/s. For maximum efficiency the two trimmers should be adjusted to have approximately the same capacity, and this can be achieved with very little effort, and once set seems to give good results with a large number of recordings. The choke should have an iron core and inductance of 5 Henries and a suitable component may be obtained from Osmor Radio. The switch used by the author is a four-bank Yaxley type obtained for 1s. 6d. from a radio shop dealing in ex-Government gear. It is, of course, important to see that the switch has a sufficiency of terminals.

In accordance with the usual practice for such equipment, all leads should be screened to prevent hum and for added efficiency the unit could be mounted into a metal box which would, of course, completely screen the switch mechanism and wiring.

The second arrangement (Fig. 2) is simpler and cheaper, and considering these factors gives good results.—L. SHELDON.

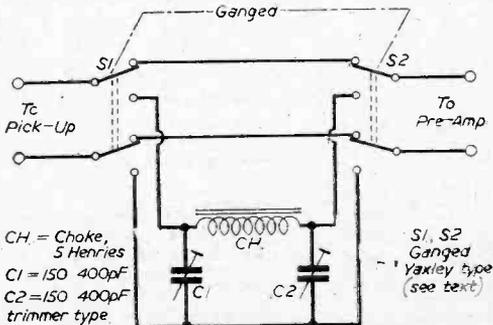


Fig. 1.—One of the filters referred to.

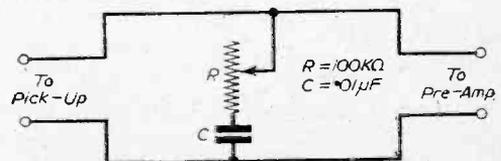



Fig. 2.—A simple and cheaper arrangement.




# HOME RADIO OF MITCHAM

have all the parts in stock for the MULLARD

## F.M. TUNER

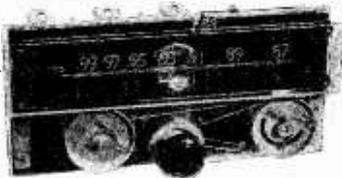

## 5 VALVE 10 WATT Quality Amplifier

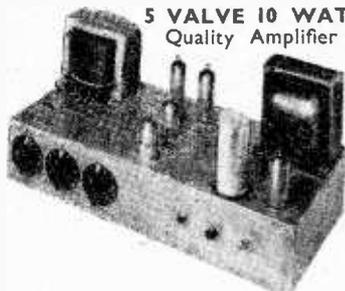

Full constructional data of both these units with wiring diagrams, parts lists, including separate pre-amplifier if required, in the "High Quality Sound Reproduction" book, price 3/6 (plus 4d. post).

Ready punched chassis	...	...	12/-
JB SL15 drive assembly	...	...	25/6
Magic eye. escutcheon	...	...	2/6
JB 101 variable condenser	...	...	10/9
Complete set of resistors	...	...	15/6
Complete set of ceramicons	...	...	41/6
All DENCO coils and I.F.'s.			

Ready punched chassis complete with screens and base plate	...	...	19/-
Complete set resistors	...	...	25/-
Complete set condensers	...	...	from 33/-
Output transformers	...	...	from 37/6
Mains transformers	...	...	from 36/-
All BULGIN parts in stock.			

We can supply detailed price lists for these home constructor kits and also the OSRAM 912 PLUS and BEGINNER'S SHORT WAVE 3 free on request.

**HOME RADIO (MITCHAM) LTD., 187, London Road, Mitcham, Surrey MIT 3282**

## More "Gladstone" Bargains

Special. 1-V. gram. amplifier, metal rect., 6 $\frac{1}{2}$ in. speaker, gain-on-off, tone, mains trans., on baffle with Tygan front. N709 valve; all for £3 carr. paid. Ditto in Rexine carrying case with 4-speed auto-changer with turnover head. £15.10.0 carr. pd. A.M./F.M. chassis 6 v. and magic eye; with o.p. trans. £19.19.0.

3 Waveband A.M. chassis 5 v. with o.p. trans., £9.19.6 (7/6). Midget 5 v. A.C./D.C. A.M. Chassis, with 5in. speaker. £5.19.6 (7/6).

Valves included in all of above (not ex-Govt.).

3-speed mixer autochangers. Collaro £8.

Chokes : 25 H 100 mA. 200 $\Omega$ , 7/6; 35 H 200 mA. 160 $\Omega$ , 10/6.

B.S.R. gram motor 200-240 v. with pick-up, £4.5.0 (5/-). D.C. to A.C. Converter 200-250 input 220 v. 50 c.p.s.

25 W. output converts your A.C. motor for D.C. mains, £4.4.0 (6/-). Collaro mixer changer in cream carrying case, £12.19.6 (6/-). Battery charger 200-240 v. in 2 v. in 2 v. 12 v. 1-amp., 29/- (2/6).

"All-dry battery" eliminator for 4 low consumption valves (200-240 v.) 90 v. 12 m.a. 1.4 v. 125 m.a., 45/-(2/-). Few only: ex-NAAFI A.C./D.C. radios. 15-55 m., 200-550, 800-1,900 m., tone, gram. input, will take up to 8 ext. speakers; 10 w. output with all valves, in working order. Made by Magneta, Ltd. Price £8 (carr. 7/6).

Please add postage on orders less than 20/- small items

Open Saturdays. Carriage charges in brackets

**GLADSTONE RADIO,**  
82B, HIGH ST., CAMBERLEY, SURREY.

## TECHNICAL TRADING Co.

AMERICAN SCR522 TRANSCEIVERS, complete all valves, including two 832's, £4. carr. 6/- THROAT MIKES, 2/8. SINGLE HEADPHONES, with headband, new, 2/6. DISTRESS TRANSMITTERS, all dry, with dipole telescopic aerial, weight 1lb., 12/6. VOLTAGE ADJUSTER PANELS, 200/250 v., 6d. DOUBLE FUSE HOLDERS with 5 amp. plug, 9d. INDICATORS, TYPE 95, VCR97, 16 valves, 39 6, carr. 6/- 10/20 WATT 12-VOLT AMPLIFIERS, high gain push pull, ideal cars, compact, untested, £4/10/-, carr. 6/- TAPE RECORDER CASES,—Blue rexine, hinged Baffle locks, carrying handle, size 16in. w. x 12in. d. x 9in. h.—15/-, carr. 3/6. DITTO, beige, de luxe, surplus famous make, 45/-, carr. 4/- "TECHTRAD" SUPERHEAT COILS, polystyrene formers, high finish. Consisting Med. and Long (both aerial and osc.) Wave Coils with full instructions, 7/6. Pair Quality Midget I.F.S. 2/6. Or both items, 15/6. No. 22 SETS, 16 valves, £4/15/- ALUMINIUM CHASSIS.—8in. x 4in. x 1 $\frac{1}{2}$ in., 3/-; 8in. x 5in. x 1 $\frac{1}{2}$ in., 3/6; 8in. x 6in. x 2 $\frac{1}{2}$ in., 4/9; 8in. x 10in. x 2in., 5/9. Post 9d. 8in. P.M. SPEAKERS.—Top Mikes, 12/6. Ditto, tested ex. eqpt., 8/6. 7 x 4 Ellipticals, 18/- Post 13. CHOKES, 15H, 150 mA., 9/6. RE-CORDING TAPE.—Well known make, 1,200ft. Reels, Big Purchase enables us to sell at 16/- reel. Post 9d. AND VALVE TESTERS, £9. F.M. RECEIVERS,—Consisting 6-valve sensitive chassis, latest miniature valve, 7 x 4 Elliptical speaker, beautiful cabinet. Listed £20, our price £11 complete, carr. paid. CONSOB DOUBLE BEAM SCOPES, very good condition, £18.

SPECIAL BARGAIN! 12 v. 4 amp. rect., 9/6 ea., £5 doz. Full wave iron selenium heavy compact type.

Standard 3 Gang .0005 CONDENS., lin. sp. boxed, 3/6.

GEBESCOPE 16 mm. TALKIE PROJECTORS at far below market price. Reget sound projectors at £29 sold out. But we have obtained a quantity of the dearer 1 $\frac{1}{8}$  inch soundless projectors with built-in push/pull amplifier, separate heavy 12in. speaker, A.C./D.C. 110/250, complete for mains operation, tested, good condition, £33. Mint condition, £38.

ALDIS SIGNAL LAMPS, w/case, ex. cond., 25/- CONDENSERS—Latest ceramic, 10, 20, 50, 900, 1,000, 3,000 pf. 5 - doz., post 6d. LATEST ELECTROLYTICS,—100 mfd., 6 vw., 1 $\frac{1}{2}$ ; 8 mid., 250 vw., 1/3; 16" 16, 350 vw., 3.- RESISTANCES,—1 w.—2 w., 47 0-1m $\Omega$ , 2/- doz., 10-100 AMPHENOL VALVE HOLDERS.—Octal, B5A, B7C, B9A, B9C, 6/- doz. B9A w/cscreen, 1/3. 12-20Z. W.V. PRESET POTS.—500 $\Omega$ , 1K, 2K, 2.5K, 5K, 10K, 20K, 25K, 2/- ea. EB34, 1/6. SP61A, 2/6; SP61, 3/-; SP210, 3/6; 6AK5, 6J5G, 4/-; 6J6, 6J7G, 6F92, PEN20, 5/-; 6AG5, 807, EL91, 5/6; 6K7M, VR150 30, 6/-; 6C4, 6F6G, 6K6, 6/6; ECC81, 8/-; 12AT, U22, 5/6; 6F3, 9/6; 615, 39/- Postage 1/- in £1 (1/9 in £1 Speakers/Trans.), minimum 6d. No. C.O.D. 1,000 OTHER BARGAINS AT  
**350/352, FRATTON ROAD, PORTSMOUTH**  
PORTSMOUTH'S RADIO, TV AND TOOL SHOP





# NEW! THE PRACTICAL WAY

of learning **RADIO · TELEVISION · ELECTRONICS**  
**AMATEUR S.W. RADIO · MECHANICS · PHOTOGRAPHY · CARPENTRY · ETC.**



**DO IT YOURSELF!**  
**IN YOUR OWN HOME — IN YOUR OWN TIME**

An entirely new series of courses designed to teach Radio, Television and Electronics more quickly and thoroughly than any other method. Specially prepared sets of radio parts are supplied and with these we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio receivers, etc.

Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business—these Practical Courses are ideal and may be yours at very moderate cost.

With these outfits, which you receive upon enrolment and which remain your property, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to designing, testing and servicing of Complete Radio and Television Receivers.

Photograph of E.M.I. factories at Hayes—our industrial background.



An Educational Organisation associated with the E.M.I. group of Companies including:  
 "HIS MASTER'S VOICE", COLUMBIA, etc.

**OTHER COURSES WITH PRACTICAL EQUIPMENT INCLUDE :** RADIO (Elementary and Advanced) · TELEVISION MECHANICS · ELECTRICITY · CHEMISTRY PHOTOGRAPHY · CARPENTRY.

Also Draftsmanship · Commercial Art · Amateur S.W. Radio · Languages · Simple Electrical Repairs in the Home · Painting and Decorating · Etc · Etc.

With these outfits, you are given instructions that teach you the basic principles in the subject concerned.

**NEW TELEVISION COURSE** including a complete set of equipment dealing with the design, construction and servicing of a high quality television receiver.

**COURSES** (with equipment) also available in many other Engineering subjects.

**COURSES FROM 15/- PER MONTH**



To E.M.I. INSTITUTES,  
 Dept. 32, 43 Grove Park Road,  
 London, W.4.

NAME .....

ADDRESS .....

SUBJECT(S) OF INTEREST  
 DEC. (We shall not worry you with per:cn l visits) K76

# TWO OUTSTANDING JASON F.M. KITS

QUALITY DESIGNS • EASY TO BUILD

## JASON F.M. TUNER

Ease of building and complete stability characterise this outstandingly successful Jason design. It uses four Z77/EF91 valves and has a useful range of at least 60 miles from the transmitting station. A fringe-area version is also available. The book of the Jason F.M. Tuner (Data Publications), price 2/-, gives complete building and operating instructions. Chassis supplied ready punched. 0.5v. output suits all high-fidelity amplifiers. Power pack kit also available. Detailed price list, etc. on application.



Complete kit of quality components less valves, **£5.5.0.**

Fringe-area version (less valves), **£6.0.0.**


Power-pack kit, **£2.1.9.**

## FROM LEADING STOCKISTS EVERYWHERE

In case of difficulty please write direct to the makers

### JASON MOTOR & ELECTRONIC CO.,

## JASON "ARGONAUT" MW/FM TUNER UNIT

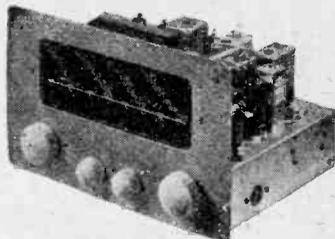

## FOR BUILDING AS A TUNER OR RECEIVER

For those wishing to enjoy selected reception of overseas transmissions as well as the superlative quality of F.M., the Jason "Argonaut" will be found ideal. It is recommended particularly for ambitious builders, and may be built as a tuner-unit, or self-powered unit with quality output stage. The chassis accommodates either version, F.M. sensitivity—15 microvolts; Switching and wiring are absolutely straightforward. Supplied with chassis, dial and tuning condenser ready mounted. Centre front-panel holes are blocked by easily removed plastic discs. All parts (less valves) to build tuner, **£10.10.0.** All parts (less valves) to build as complete receiver, self-powered, **£11.10.0.**

32B, CRICKLEWOOD LANE, LONDON, N.W.2  
Phone: SPEdwell 7050

## The Tape Recorder for YOU



Easy to operate with single knob control. Very wide frequency range with high quality output and may be used as a separate amplifier. Complete with crystal desk microphone and one hour spool of tape and fitted in cornerless simulated pigskin suitcase with continental gilt fittings—for operation on 110 v.-250 v. A.C. Mains.

# 40 GNS.

or 9 monthly payments of £5. 3. 0.

E. & G. MAIL ORDER SUPPLY CO. The Radio Centre, Museum 6667.  
33, Tottenham Court Road, London, W.1.

## CONSTRUCTORS build these at DOWN-TO-EARTH PRICES

### PERSONAL PORTABLE RADIO

# 30/-

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere.

Send 2/- for layout, Wiring diagram and Components Price List.

## 1v SHORT-WAVE RADIO

- ★ Covers 10-100 metres.
- ★ World-wide reception.
- ★ Low drain valve.
- ★ Picture diagram and instructions for beginners.
- ★ Assembling time 1 hr.

# 30/-

This 1 valve S.W. receiver can be built from our list of components for 30/-, including valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required. All components can be purchased separately and are colour-coded so that the beginner can build this set quite easily.

Post and Packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE.

Send 2/- for specification, wiring diagram, layout and price list to:—  
**R.C.S. PRODUCTS (RADIO) LTD**  
OLIVER ROAD, LONDON, E.17. Mail order only.

# A COMPACT H.T.—L.T. UNIT FOR PERSONAL RECEIVERS

AN ALL-DRY BATTERY MAINS REPLACEMENT UNIT

By L. Baker

**T**HE purpose of this unit is to provide the L.T. and H.T. supplies for the average "Personal" receiver. There must be many of these type receivers in use as bedroom sets and for occasional listening. The writer's own model is an R.C.A. type with miniature B7G valves in a superheterodyne circuit. As the cost of batteries for this set was rather prohibitive, it was decided to make a small unit to provide the necessary supplies, namely, 90 volts H.T. and 1.5 volts L.T. In order that the set should retain its portable qualities it was decided that the unit should be as small as possible and should fit inside the set with no alterations to the wiring of the set itself, and be so arranged that it could be removed and substituted by the normal batteries at any time. The unit described proved to be satisfactory in every way, and indeed, after long periods of use gave no trouble.

In size it is comparable to the average 20 packet of cigarettes. The case which was made of 1/16in. aluminium is shown in Fig. 2. Basically, it will be seen that the case (which also serves as chassis) is a flat rectangular tray 4 3/4 in. long by 3 1/2 in. wide by 1/2 in. deep. A lid to suit the above dimensions was made from the same material and this lid covers the components when in use. The 3/16in. tabs at the sides serve to hold on the lid, which is screwed to the tabs by means of small 1/4 in. woodscrews. The aluminium should be cut to the dimensions shown in Fig. 2, and before bending it holes should be drilled for the mounting clips of C1 and C2, also C3 and C4. The hole for the output socket should also be made before bending, as also the mounting holes for T1, CH1, the H.T. rectifier, the L.T. rectifier, and variable resistor R1 should be drilled while the aluminium is flat. As the components to be used will differ slightly, it is not possible to lay down hard and fast drilling dimensions. It will be a help, of course, to mark out the space for components (4 3/4 in. by 3 1/2 in.) before bending the material, and in this space position the actual components to be used. In this way the case or chassis can be drilled with enough accuracy to suffice. Having completed the drilling, the chassis may then be bent to shape and the components mounted inside.

## The Mains Transformer

This unit is specially wound to suit the power supply. In the writer's model the basis of this was an old bell transformer which was stripped down and the bobbins used to accommodate the new windings. The same core was used which consisted of a number of E. and I. pieces. The primary was wound on its own bobbin and consisted of 1,320 turns of 36 s.w.g. enamel wire. The start or inside wire was passed through the cheek of the bobbin and anchored to a tag strip, which was held on to the transformer core by one bolt which was originally used to hold the laminations together. Every 200 turns of wire was insulated by a thin layer of empire tape, and when the

final layer was wound the whole bobbin of wire was given a coat of shellac. The end wire was passed through the cheek again and soldered to another tag on the strip already mentioned. The winding for the H.T. was wound next: This was also on its own bobbin and consisted of 850 turns of 36 s.w.g. wire. This was not insulated at intervals, but instead wire with a single silk covering was used. The wire was passed through the cheek of the bobbin as before, leaving some 5in. protruding to reach its required anchor points. The final secondary for the L.T. was then wound and this consisted of 30 turns of No. 20 s.w.g. wire enamel, also in its own bobbin with long, protruding ends as before. The final unit was dipped in shellac to bond it tightly together and prevent buzz.

## The Choke

This was made from the core stampings of a discarded miniature audio choke. All wire was stripped off, the bobbin retained. On the bobbin were placed 200 turns No. 20 wire, long ends left protruding for connection purposes. The choke also was given a coat of shellac. When wiring up the unit, pieces of sleeving were used over all wires protruding from ends of choke and transformer to insulate them from the chassis and components.

## The H.T. and L.T. Rectifiers

In the writer's model these units were both rescued from ex-W.D. equipment. The H.T. rectifier is a small half-wave unit about 1/2 in. long and fins of about

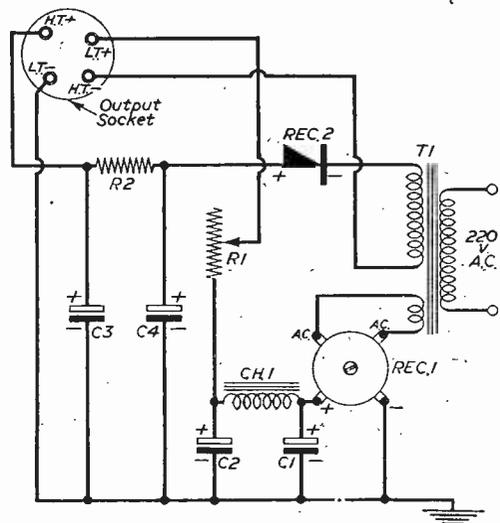


Fig. 1.—Theoretical circuit of the unit.

in. It was rated at 25/30 mA max current. This is more than adequate for the H.T. requirements of the average personal receiver. It was mounted by single hole fixing. No doubt readers will have to hand other metal rectifiers of slightly different shape, these should work just as well provided they are small enough to be accommodated in the case and they are known to be in good condition. The L.T. unit was a full-wave type and rated at 4/8 volts at 1 amp. max. It was found that the consumption of the L.T. portion of the writer's set was .25 amp., and therefore the output of the rectifier for L.T. was adequate. It was noted also that the consumption of the average personal receiver using B7G valves was almost the same. The valve complements of several sets were checked and it was found the valve line-up

for H.T. + and - and L.T. + and - go to the correct positions. Use soldered connections only, and wire earth connections directly to the case where shown on circuit diagram in Fig. 1. It will be seen that the H.T. negative output of the unit does not go to the chassis but is taken direct to the output socket. This is in order to provide for the automatic bias system of the receiver. The H.T. negative usually goes to earth via the bias resistor in the receiver proper.

#### Adjustment and Operation

Having completed wiring and checked for mistakes, etc., it would be as well to check with the ohmmeter between various points to see that no short-circuits will occur. If all is in order, with the unit *not* connected to the receiver check for the various voltages.

The no load outputs should be approximately 120 volts H.T. and approximately 3 or 4 volts L.T. If an old valve of the B7G type with good filament is to hand it is advisable to connect its filament across the L.T. output and measure the voltage on load. The voltage should now drop quite a bit. For this test turn the slider of R1 so that all the resistance is in circuit, then with voltmeter connected across the socket holding the valve, check that the L.T. voltage can be varied by adjustment of R1. If the voltage can be reduced to 1 volt or so all is in order. If not, recheck wiring and especially check and replace the L.T. rectifier. Having completed this test return R1 to its setting with all the resistance in circuit and connect the unit to the receiver. With meter across L.T. output and the set switched on, adjust R1 until exactly 1.4 volts show on the meter. Check again with

the meter the H.T. voltage on load. This should now be in the region of 80 or 90 volts. It should not be more than 90 volts, if it is increase the value of the carbon smoothing resistor by the required amount to drop it to 90 volts. This completes adjustments. The set should now play normally with little or no trace of hum. If hum is present try changing about the leads to the mains plug. If it still persists all condensers should be checked, especially the L.T. smoothing and H.T. smoothing condensers.

It will be noted that no switch has been included in the unit. In order to switch off, therefore, the A.C. has to be switched off at the wall socket or by removing the plug. If desired a small toggle switch could be included in the unit, or if the unit is to take a permanent place in the set the switch on the set itself could be used removing all connections from it and wiring them in the permanently "on" position. Then using screened lead, wire in the switch to the primary of the transformer primary lead.

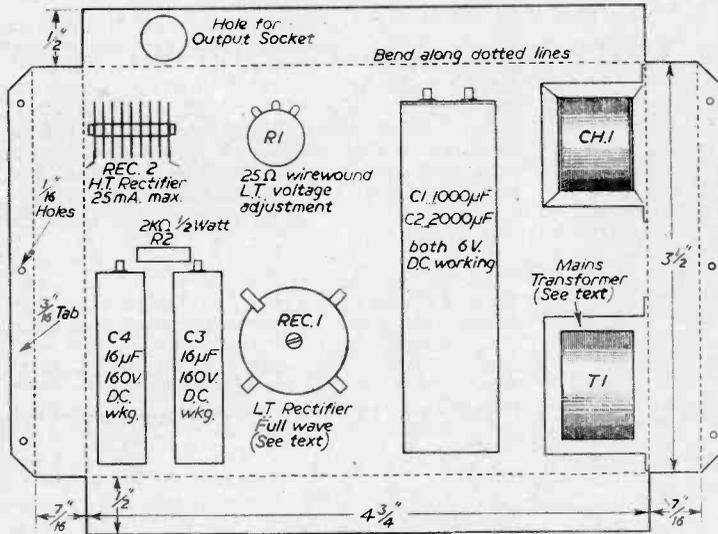


Fig. 2.—Layout and component values.

was usually DK92, DF91, DAF91, DL92. The filament of this set-up requires 1.5 volts at .25 amp. Many other sets will have a similar consumption; however, to provide for a slight adjustment the variable resistor R1 is included in the output from the L.T. rectifier. In the rectifier used by the writer there were actually only three connections to it, the fixing bolt being the negative side of the output rectified current. To simplify the diagram, Fig. 1, and the pictorial diagram, Fig. 2, four connections are shown. By way of warning it is extremely important to observe the polarity of both rectifiers and those which clearly show the cathode or positive terminal should be used. On no account should dubious units be used, especially in the L.T. circuit as damage to the valves could result.

#### Wiring

This is simple and straightforward. All wires should be well insulated, especially the wires from the transformer and choke. The output socket was taken from an old H.T./L.T. battery for the receiver and in the completed unit it should be carefully checked that the output of the unit should be taken to the correct lugs on the socket so that the receiver plug

### WIRELESS COILS, CHOKES AND TRANSFORMERS

8th Edition.

Price 6/-. by post 6/9.

# LASKY'S RADIO




## AMAZING OFFER!

Brand New, Perfect, 16in. C.R. Tubes at almost One-Third of List Price. Gives large black and white picture 11in. x 14in. Call or send for full details. Listed at £23.9.10.

**LASKY'S PRICE £8.9.6**  
Carr. & Insur., 2/6.
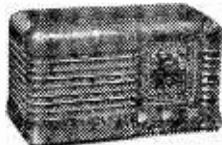
## INEXPENSIVE RADIO YOU CAN EASILY BUILD

Unbeatable Value in Parcels for the Home Constructor



CAN BE BUILT FOR **£5.10.0**

Carr. & Pkg. 2/6

**PARCEL No. 2.** Contains everything to build a T.R.F. 3-valve Set for 200/250 A.C. mains, medium and long wave. Uses 6K7G, 6J7, 6V6 and metal rectifiers. With your choice of Cabinets, see below:

● Neat Plastic Cabinet, walnut or ivory finish; or attractive Wood Cabinet, walnut veneer. Size: 12 x 6 1/2 x 5 1/2 in. deep. State which required.

**INSTRUCTION BOOK** for either above sets, 1/- post free.

**CABINETS ONLY**, plastic or wood. 17/6. Carr. 2/6. All Components available separately.

CAN BE BUILT FOR **£7.19.6**

Carr. & Pkg. 2/6



**PARCEL No. 1.** Contains everything to build a 4-valve superhet for 200/250 A.C. mains, long, med. and short wave. Uses 6K8, 6K7, 6Q7, 6V6 valves. With your choice of Cabinets, see below.

## NEW BATTERY PORTABLE FOR HOME CONSTRUCTION ON PRINTED CIRCUIT

CAN BE BUILT FOR **£7.7.0**

Carr. & Pkg. 3/6.

19 Star Features make this the finest Portable radio ever offered to the home constructor. Extremely simple to build, the printed circuit eliminates wiring errors. Send for CIRCUIT DIAGRAM, assembly data, all instructions and shopping list, 1/6 post rec.



## GARRARD RC.110 3-SPEED MIXER AUTO-CHANGERS

Brand new in maker's cartons. Complete with turnover crystal pick-up. Cream/Brown enamel finish. Limited number only. List £14.13.0.

**LASKY'S PRICE**

**£7.19.6** Carr. 3/6.

Cabinets available.



## LASKY'S (HARROW ROAD) LTD.

42, TOTTENHAM COURT ROAD, W.1.  
Telephone: MUSeum 2605.  
370, HARROW ROAD, PADDINGTON, W.9.  
LADBroke 4075 and CUNningham 1979.  
Open all day Saturday, early closing Thursday.

All Mail Orders to Harrow Road, please.

## Beginners can easily

# BUILD THIS FRYING-PAN RADIO

NO RADIO KNOWLEDGE WHATEVER NEEDED!

Can be built by anyone in an evening using our step-by-step, easy-to-follow plans. Total building cost including mirror finish frying-pan and everything down to the last nut and bolt only 79/6, Post Free. It is a REAL ALL-ELECTRIC RADIO with normal size speaker, etc. Exceptionally sensitive circuit covering all Medium and Long Wavebands, RECEIVES "HOME," "LIGHT," "LUXEMBOURG," "A.F.N.," etc., etc., really beautiful tone due to "wall-baffle" effect. Size only 9in. Diameter, 2in. Deep, and handle 7in. Long. Hangs anywhere—IDEAL FOR KITCHEN, BEDROOM, ETC. (Mains lead passes unnoticed through the hollow handle.) AMPLIFIED VOLUME. RUNNING COSTS ONLY 1d. FOR 75 HOURS! Weight only 3 1/2 lbs. For A.C. Mains 200 to 250 Volts. Robust design and should last a lifetime. EACH PART TESTED BEFORE DESPATCH, AND YOU CAN'T FAIL BECAUSE OUR EASY-TO-FOLLOW PLANS TAKE YOU STEP-BY-STEP. BUILD ONE OF THESE AMAZING LOW-PRICED SETS—NOW! Total building cost including full set of plans 79/6 Post Free. (Parts may be bought separately. Parts Lists 2/6.) LIMITED QUANTITY. Send Cheque or Postal Order Today! Please cross Postal Orders. (C.O.D. 2/- extra.) BUILD ONE FOR YOUR MOTHER OR WIFE!



ONLY **79/6**

POST FREE

(Dept. PW2) 60 PRESTON STREET, BRIGHTON, 1

**Concord Electronics**

## FREE TO AMBITIOUS ENGINEERS!

This 144-page Book

Have you sent for your copy?



'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

FREE COUPON

Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME .....  
ADDRESS .....  
.....  
.....  
Subject or Exam. ....  
that interests me .....  
British Institute of Engineering Technology,  
409B, College House, 29-31, Wright's Lane,  
Kensington, W.8.

## WHICH IS YOUR PET SUBJECT?

Mechanical Eng.  
Electrical Eng.  
Civil Engineering  
Radio Engineering  
Automobile Eng.  
Aeronautical Eng.  
Production Eng.  
Building, Plastics,  
Draughtsmanship  
Television, etc.

GET SOME LETTERS AFTER YOUR

NAME!  
A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.P.E.  
A.M.I.M.I.  
L.I.O.B.  
A.F.R.Ae.S.  
B.Sc.  
A.M.Brit.I.R.E.  
CITY & GUILDS  
GEN. CERT.  
OF EDUCATION  
etc., etc.

# BIET

**1355 RECEIVER**  
Complete with 11 valves, 3-SP61, 6U4C, VU120, VR82. As specified for "Inexpensive Television." In absolute new condition. 27/6. Carr. 5/-.

**TRANSISTOR SQUARE WAVE GENERATOR**  
This arrangement comprises an emitter-couples multi-vibrator, and provides a square waveform with excellent transient characteristics. The output provides two basic tones and a large number of harmonics spreading through the a.f. spectrum. Ideal for signal tracing. Complete Kit with 2 Transistors Components and Circuit 25/-.  
As Per "P.W." Nov. issue.

**"R.F. 26" F.M. CONVERTER UNIT 88 100 Mc/s.**  
This well-known R.F. 26 Unit is now adaptable for F.M. reception using 2 I.F. stages and separate local Oscillator and tuned by a Multirad graduated Vernier drive. Can be converted at low cost of 92/6. Send 1/6 for 8-page Descriptive booklet containing full wiring instructions, circuits and aout diagrams.

**62A INDICATOR UNIT**  
Containing VCR97 with Mu-Metal Screen. 21 Valves: 12-EF50, 4-SP61, 3-EA50, 2-EB34. Plus Pots, Switches, H.V. Cond., Resistors, Multirad S.M. Diode, Double Deck Chassis and Crystal. BRAND NEW ORIGINAL CASES. 67/6. Carr. 7/6.

# TRANSISTORS

**JUNCTION TYPE (Red Spot) OFFERED AT LESS THAN HALF-PRICE**

Designed for A.F. application up to 800 kc/s and is suitable for use in Radio Control, Signal Tracers, Local Station Receivers, Oscillators, Transistor Voltmeters, Microphone Pre-Amplifiers, etc.

**10/-**

(Tested and complete with Data and Circuits)

N.B.—These transistors may be used in place of Mullard OC71 or similar Transistors.

**R.F. TRANSISTORS (Blue-Spot), 1.6 Mc/s. 15/- each.**

**TRANSISTOR SIGNAL TRACER**

This Circuit is designed for Audio, R.F., and I.F. Frequency and is ideal for the Serviceman for checking all types of Sets including T.V. Powered by 6 volt Dry Battery. Miniature in construction. Complete Kit with 2 Transistors, Components and Phones with Circuit. 42/6.

**TRANSISTOR PUSH-PULL AUDIO AMPLIFIER (100 Milliwatts Output)**

Build this Push-Pull Amplifier which is ideal for Crystal or Magnetic Pick-up Application. Baby Alarm, Microphone Amplifier, etc. Powered by 6 volt Dry Battery lasting for months. Complete Kit of Parts including 4 Transistors and all Components with Circuit (less Speaker) 24.10.0.

**"TELETRON" PORTABLE TRANSISTOR SUPERHET**

We offer all the Components including 4 Transistors, I.F.T.'s, Trans. 2 Gang miniature condenser, Ferrite Rod, 3in. p.m. Speaker, V/C and resistors and condensers to build this Receiver for 28.10.0 Or as above with Push-Pull Output, 6 Transistors and 6 x 4 elliptical Speaker, 29.00.0 (All components sold separately. Send for shopping list and circuits.) Or with 2 Mullard OC72s (matched) and 6 x 4 High Resistance Push-Pull Speaker. Output 200 Milliwatts, 210.10.0.

**TR 1196 TRANSMITTER**  
Transmitter section comprising EL32, EF50, VT501, Relay, etc.. 12/6. P.P. 2/6.

**R.F. UNITS**  
RF24 complete with valves, 10/-.  
RF25 complete with valves, 12/6.  
RF26 complete with valves, 25/-.  
Brand new. Carr. 2/6.

**MINIATURE I.F. STRIP TYPE "873" 9-72 MEG.**  
Brand new miniature I.F. Strip size 10 1/2 in. x 2 1/2 in. high. Valve line-up: 2-EF92, 3-EF91 and EB91. With circuit. Price (less valves) 7/6. With Valves, 42/6. P. & P. 1/6. This I.F. Strip is part of above equipment.

**CATHODE RAY TUBES**  
VCR138A WITH SCREENS... 21in. £1 15 0  
VCR139A. 24in. C/R Tube. Brand new in original cartons (carr. free) £1 15 0  
VCR197. Guaranteed full TV picture (carr. 2/-) ... £2 0 0  
VCR517C. Guaranteed full TV picture ... £1 15 0  
**M.U.M.E.A.I. SCREENS** for VCR97 or 517. P.P. 1/6 ... 10 0  
6in. ENLARGER for VCR97 or 517 ... P.P. 1/6 ... 17 6  
VCR97. Slight cut-off. Carr. 2/- ... 15 0  
3BP1. Brand new ... £1 10 0

# HENRY'S (RADIO LTD.)

5, HARROW ROAD, PADDINGTON, LONDON, W.2.

TEL.: PADDINGTON 1008-9, 0401

## VALVES • SAME DAY SERVICE

**All Guaranteed New and Boxed**  
1.4v. midget. IR5, 1S5, 1T4, 1U5, 384, DA9F1, DF91, DK91, DL92, DL94; any 4 for 27/6.

1A7G12/8	6V8GT	7/-	DH77	8/6	EY51	10/6	
1C5GT11/6	6X4	7/-	DK32	12/6	EZ40	8/-	
1H5GT	6X5GT	6/9	DK92	9/6	EZ41	8/-	
	11/6	7/8	DK96	8/6	EW40	8/6	
1N5GT	7C5	8/-	DL33	11/6	EW40	8/6	
	11/6	7/6	DL35	11/-			
1R5	8/6	7H	8/-	DL96	8/6	GZ32	12/6
1S5	7/3	7S7	8/-	EAB8C0	KT33C	10/0	
1T4	7/3	7Y4	8/-		KT63	7/6	
3A5	6/6	10C1	12/6	EAC91	9/6	MU14	8/6
3Q5GT11/6	10C2	10/-	EAF4210/6	N7	6/6		
384	7/9	10F1	10/-	EB91	8/9	N78	14/6
3V4	8/6	10LD11	8/6	ECB33	7/6	PCC84	8/6
5U4C	8/-	11/8	EB4C1	10/-	PCF80	7/6	
5Y3GT	7/6	10P14	13/6	EBF80	9/6	PCF8211/6	
5Z4G	9/-	12A7	7/6	EC40	12/6	PEN36C	
6AK5	5/-	12U7	8/6	EC83	9/6		18/-
6A5	6/9	12J7GT	8/6	ECB83	9/6	PEN45	20/-
6AM6	7/6	9/6	EC91	6/-	PEN46	6/6	
6AQ5	7/6	12KTGT	8/6	ECF80	12/6	PL81	11/9
6AT6	8/6	8/6	ECF8213/6	PL82	9/6		
6BA6	7/6	12K8C	8/6	ECF8510/3	PL83	9/6	
6BE6	7/6	14/6	ECH44	10/-	PY80	9/6	
6BW6	7/6	12Q7GT	10/-	PY81	9/6		
6C9	10/-	8/6	ECH81	8/6	PY82	7/9	
6F1	13/-	14S7	14/6	ECL80	10/-	PZ30	18/-
6FG6	6/6	20L1	10/9	EF37A	9/-	U50	7/6
6F13	13/-	19/6			U50	7/6	
6F15	13/-	25L6GT	9/6	EF39	6/-	U78	7/6
6J6	6/-	9/6	EF40	12/-	UAF42		
6K7G	5/-	25Z4G	9/6	EF41	9/6		10/6
6K7GT	6/-	36L8GT	9/6	EF42	12/-	UBC41	8/6
6K8C	7/9	35Z4GT	6/6	EF43	7/6	UCHZ2	
6K8CT	9/8	50L6GT	9/6	EF80	9/6		10/3
6L18	11/6	B36	15/6	EF85	8/6	UF41	9/6
6Q7GT	9/6	CL33	14/-	EF86	12/6	UF41	10/0
6SN7GT	7/9	DAC3211/6	8/6	EF91	7/6	UY41	8/6
		DAP36	8/6	EF92	8/6	W77	12/6
6U4T	7/9	DF90	6/6	EL41	10/6	X79	12/6
		DF33	11/6	EL84	10/6	Y63	12/6
6V6G	7/-	DF96	8/6	EM34	10/-	Z77	7/6

Postage 5d. per valve extra.

## WHY WASTE TIME FIT QUALITY COMPONENTS

Catalogue 1/-  
Parts for the following: Manual  
Osram "912" Plus Amplifier ... 4/-  
Mullard 10-watt Amplifier ... 3/6  
The Coventry  
2-watt Amplifier ... }  
4-watt Amplifier ... } 1/-  
6-watt Quality Amplifier ... }  
The Coventry A.M. Tuner Unit ... }  
Denco F.M. Tuner Unit ... 1/6

Complete Component Price Lists will be supplied with each Manual

## COVENTRY RADIO

EST. 1925  
109, DUNSTABLE ROAD, LUTON, BEDS.  
Phone: Luton 2677

## Morse Code operating ... as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.  
Send 2yd. stamp for Payment Plans and Full Details of all Courses.  
CANDLER SYSTEM Co. Dept. 510 52b, Abingdon Road, London, W.8. Candler System Co., Denver, Colorado, U.S.A.

## BENSON'S BETTER BARGAINS

**BO624A.** (8CR322). New condition, with 10 valves; 100/150 mc/s. Less valves and relays. 50/- (Rail 5/-). VALVES: 4-SP61, 6C4, 6A4G, 9001, 9002, 6SNT, 6AM6, EL91, VR99, VR102, 3A3, 128K7M, 12A6, 807E, KT33C, 12N17, EF54, 6A47, TTU1, EC52, 6K7GT, 6NH7M, 6AC7, Pen46; at 4/-: EF99, RK34, KEYS, Morse, large, covered, 10/8; small 2/6 (p. 3/-). R.X.S. 112/114 (TR1987), with 3EF91, 2/EL11, 5 gang tuner, new, 37/8, less valves, 8/8. Circuit 1/-.  
**MOTORS:** Gram., 230 v. Induction, 78 r.p.m. with governor (Garrari), 30/- (post 2/9); SYNCH. 230 v. geared to 1 r.p.m. final, new, 32/8. Synch. 100 v. 3,000 r.p.m. 10VA., 10/-.  
**SUPPRESSORS,** radio interference. ex-A.M., 5/6 (post 2/-). BRAND NEW R.F. 26, 27/8; RF24, RF25, 10/8 (postage 2/6).  
**AERIAL RELAYS** (co axial) 6/6 12/24 v., 7/8. DYNAMOTORES (type 3-1) 12 v. to 250 v. 55 mA. and 6.3 v. 2.5 A. 10/6. Filters for these, 2/6.  
**EDDYSTONE** 12 v. to 150v. 75 mA., cased, 15/-, 11 v. to 300 v. 200 mA., cased, 15/- (carr. 8/6).  
**CLOCKWORK** Contactors, 2 impulses per sec., 8/6. U.S.A. type, small, 9/6. THERMISTORS, U.S.A., new, 2/6. METAL RECTIFIERS: 600 v. 30 mA., 6/-, 500 v. 50 mA., 10/6, 1,000 v. 30 mA., 7/8. R1355 IF strips only, new, with valves, 25/- less valves, 12/6 (post 2/6). WAFER SWITCHES, 1 pole 11 way 2 Bank, 3/6. 4 P. 3 W., 4 P. 2 W., 1 P. 6 W. 3 B. 2/6. IF AMPLIFIER 178, 15.0 m.c/s., with valves, 15/6 (postage 2/6). RELAYS, 6 v. 2 break, 1/6. I.F.T.'S 10/13 mc/s. cabled, new, 1/3. R1165 Coils, new, 12/6. HEADPHONES, L.R. super lightweight HS 40 B, 17/6. VIBRA-PACKS: Military 12 v. to 250 v. 50 mA., 2/6. reversible, 18/6. 6 v. to 280 v. 75 mA. smoothed, filtered, 25/- 2 v. to 480 v. and 150 v. (dual vibrator) smoothed, filtered, 30/- (post each 3/-). List and enquiries, S.A.E. please. Terms C.W.Q. Postage extra. Immediate despatch. Callers and post: W. A. BENSON (P.W.), 138, Rathbone Road, Liverpool, 15. SEP 6853. Callers: SUPERADIO (Wohapel LTD.), 116, Whitechapel, Liverpool, 1. RGF 1130

**READERS RADIO**  
24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587

# Open to Discussion



*The Editor does not necessarily agree with opinions expressed by his correspondents*

## S.W. Listeners

**SIR**,—In reference to the letter by H. F. Barker, of Reading, printed in your "Open to Discussion" feature.

I agree that the S.W. listener is not fully catered for in most of the large radio societies; I agree that these societies are of value to the S.W. listener, but not in the practical sense.

I have found that in most local radio societies the S.W. listener is way out of the picture if in the company of licensed operators, and sits in the background whilst the hams talk of their Q.S.O.s.

In my opinion this is the reason why so many are dropping out of our hobby of S.W. radio.

The answer to this problem would, indeed, be to issue a novice licence, using low power and XE1 controlled, and providing the S.W. listener can prove that he is a genuine experimenter and that he can find a licensed operator to inspect the novice station to see that things are in order, etc.

This, in my opinion, is the only possible way for many S.W. listeners making the grade. Many inexperienced operators are using mobile nets in commercial fields, so why not the genuine novice experimenters?—L. G. HUTTON, M.S.M.(P.) (G5229) (Birmingham).

## Radio Alarm Clock

**SIR**,—With reference to your article by John Williams, August issue, on "Radio Alarm Clock", may I be permitted to say that ingenious as the clock contact arrangements may be they make the construction of this piece of equipment unnecessarily tedious for the service that the contacts are capable of giving.

A well-tried arrangement is the fitting of an insulated metal strip to the rear of the clock; this forms one contact, the alarm winder and case the other, as this rotates when the alarm rings. The metal strip stops the winder when the alarm spring pressure has put it under tension. (To reset, wind alarm half a turn.)

This completes the time switching with much more robust contacts than the foil. This switch is placed in the neutral line, of course. Now, for those with the qualms about the almost full mains voltage appearing across the clock contacts, when the master switch is over to alarm.

All that is required is a relay and a means of energising it (one is produced commercially, 4.5-volt battery operation) by either a battery or small transformer. The relay can be mounted inside the set and the clock left to switch the energising side

of the relay, the main contacts breaking one lead to the set transformer, etc., or double pole switching if the relay has contacts available.

With the reasonably heavy contacts on the relay, the bed lamp-radio cum tea brewer, etc., really becomes a possibility, without blowing a hole in the foil each time the contacts open and close, and the accompanying electrical interference.—

D. C. RAYNER (Electrical Engineer, Leeds).

## Correspondents Wanted

**SIR**,—I am 16 years old and interested in electronics. Through your columns I would like to get in touch with pen friends with similar interests. If many reply I will

file and forward letters to enable as many as possible in similar circumstances to correspond together.—RICHARD C. HARDWICK (Abbeylands, Sherborne, Dorset).

**SIR**,—I would be glad to hear from anyone who would like to correspond with me, as I have no one to help me over my technical matters. I have built sets of my own and am 17 years of age.—M. KING (47, Whitwell Road, Broxtowe, Nottingham).

## "Transmitting Topics"—November, 1956

**SIR**,—On reading through this article we note that the author, Mr. O. J. Russell, mentions that data on the 807 valve is not available. We should like to point out that full operating conditions and data may be obtained for the Brimar 807 valve on application to our Valve Application Department, —G. C. Fox (Valve Application Department), S.T. and C., Ltd., Footscray, Sidcup, Kent.)

## Amateur Results

**SIR**,—Recent remarks about the early detector and low frequency receivers induced me to unearth some old components and build a medium wave version of the "Perfect Three," blueprint No. 63. This type of set possesses an odd kind of fascination; perhaps because of its being capable of giving good results, in spite of its simple nature! It is good, strong and clear on the Home and Light, and distant stations can be obtained on the 'phones.

A five-to-one universal transformer and a Lissen H.F. choke are large and weighty items: I had to make the plywood chassis 4 in. deep. I used a two-gang .0005 with the tuners joined, and an old .0001 vernier, with long handle. Noting the admonition to use thick wire, I made up coils of 17, 28 and 15 turns of 26-gauge on a ribbed 3 in. ebonite former. The coil ends are joined to plug-in pins, which plug in to a

*Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.*

seven-pin valve holder. This makes an ideal base. An ordinary output transformer is used and an 8in. Celestion speaker.

With this simple old set some of that hypnotic spell, well known to the early pioneers, returns! Then home building was universal; it swept America and Europe—the commercial set was almost unknown! The "influence," was even more potent than is that of television to-day! There were, however, a great many beautifully made components on the market. They possessed terminals and screws for joining and fastening. With them it was easier to construct sets than it is with the tag-ended components available to-day!—A. TROWBRIDGE (Staines).

#### The R.1155

SIR,—I note in PRACTICAL WIRELESS that there have been several queries with regard to the R.1155. Having carried out instruction on these Rx's while in the R.A.F. I can clear up a few points:

Range	RX1155, 1155A, B, C, D, E, F, M	R1155L and 1155N
1 H.F.	18.5 to 7.5 Mc/s	18.5 to 7.5 Mc/s
2 H.F.	7.5 to 3.0 Mc/s	7.5 to 3.0 Mc/s
2A H.F.	Not applicable	3.0 Mc/s to 1,500 kc/s
3 M.F.	1,500 kc/s to 600 kc/s	1,500 kc/s to 600 kc/s
4 M.F.	500 Kc/s to 200 kc/s	500 kc/s to 200 kc/s
5 M.F.	200 kc/s to 75 kc/s	Not applicable

I.F. 560 kc/s. Bandwidth 4.3 kc/s at 6 db. attenuation.

L.O. freq. 560 kc/s above incoming signal freq.

#### VALVES

V1, V2—D.F. switching	Triode hex. VR99A (X65 or X66)
V3—R.F. amplifier	Vari- $\mu$ pentode VR100 (KTW62 or KTW61)
V4—Freq. changer	T.H. VR99 (X65 or X66)
V5, V6—I.F. amps.	Vari- $\mu$ pent. VR100 (KTW62 or KTW61)
A.V.C. and B.F.O. V7, V8—2nd detector Visual meter switching limiter and output	VR101 double-diode- triode. MHLD6
V9—Visual meter switching.	Double triode VR102 BL63
V10—Tuning indicator	VJ103 Y61 or Y63

The VR99A and VR99 were being replaced with VR1581 (ECH35).

The frequency of the B.F.O. is 280 kc/s  $\pm$  3 kc/s.

The second harmonic is used to prevent the B.F.O. from being locked by the incoming I.F. signal.

I hope these few facts will come in useful to readers.—D. B. SMITH (Nottingham).

#### Training Courses

SIR,—The radio and television servicing course now running at Wesley Institute is intended for new entrants to the industry, and also for amateurs who wish to solve their home problems. Students wishing to take less advanced examinations can be catered for. Details are as follows:

1. Evenings: Wednesdays, probably to be expanded to Mondays also (7 p.m. to 9 p.m.).
2. Fee: 20s. per one evening per session; 27s. 6d. per two evenings the session, ending July, 1957.
3. The instructor is employed in the research department of a well-known firm in the industry.

Wesley Institute is just off the Harrow Road, at Stonebridge, N.W.10.—E. N. FENNELLS, B.Sc.(Econ.), F.R.G.S., L.C.P. (Head of Institute).

#### Amateur Tracking of "Mouse"

SIR,—Your correspondent, Mr. A. P. Buchanan, in reference to operation "Mouse," has written an interesting and thought-provoking letter.

Although some of us cannot hope to keep pace with the technical side of such matters, an article should prove of much interest to all types of readers and from the humblest amateur upward we are brought nearer to these great projects by the advent of the Great Magician—radio.

May I remark, if it is not out of place, to those who are modellers in any way, that many of the small fittings and gears as used in radio cannot be excelled for use in modelling, especially as radio apparatus demands such a high standard of workmanship and quality generally.—M. K. HUGGARD (Co. Wicklow).

## Bought All Your Christmas Presents Yet?

No? Then here's an idea. Why not send your friends who are radio enthusiasts a gift you'd be delighted to receive yourself—a year's subscription for PRACTICAL WIRELESS? For twelve whole months your gift will bring them repeated pleasure, and each new issue will be a renewed reminder of your good wishes.

But the days are flying—you must order now to ensure that first copies arrive before Christmas. Simply send your friends' names and addresses with your own and remittance to cover (an annual subscription for PRACTICAL WIRELESS—12 issues, including postage—costs 18s. Od.) to Subscription Manager (G.2), George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. An attractive Christmas Greetings Card, made out in your name, will be sent to announce your gift.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."



## RECEIVERS &amp; COMPONENTS

**ELECTROLYTICS**, capacity, voltage, size, type of mounting, price post paid. 1,000 + 1,000, 6v, 1 x 3, clip, 3/3; 1,000 + 2,000, 6v, 1 x 3, 3/9; 100, 12v, 1/2 x 1 1/2, tag, 1/9; 500, 12v, 1/2 x 1 1/2, W/E, 2/-; 2,000, 12v, 1 1/2 x 2, W/E, 3/6; 10, 25v, 1/2 x 1 1/2, W/E, 1/3; 25, 25v, 1/2 x 1 1/2, W/E, 1/3; 50, 25v, 1/2 x 1 1/2, W/E, 1/3; 100, 25v, 1/2 x 1 1/2, W/E, 2/-; 1,000, 25v, 1 x 3, clip, 4/-; 3,000, 25v, 1 1/2 x 4 1/2, 5/6; 5,000, 25v, 1 1/2 x 4 1/2, clip, 6/6; 5,000, 50v, 1 x 3, clip, 3/9; 2,500, 50v, 1 1/2 x 4 1/2, clip, 6/6; 5, 150v, 1/2 x 1 1/2, W/E, 1/3; 8, 150v, 1/2 x 1 1/2, tag, 1/3; 40 + 40, 1 x 2, clip, 2/9; 200, 250v, 1 1/2 x 3, clip, 3/6; 100, 275-350v, 1 1/2 x 3, clip, 3/-; 16 + 16, 275v, 1 x 2, clip, 3/-; 32 + 32 + 32, 1 1/2 x 2, clip, 4/3; 16 + 8 + 4, 1 x 2, lug, 3/-; 200 + 250 + 250, 275v, 2 x 4 1/2, clip, 8/6; 60 + 250, 275/350v, 1 1/2 x 4 1/2, clip, 6/3; 16 + 16 + 8, 350/425v, 1 1/2 x 2, lug, 4/3; 32 + 32 + 8, 350/425v, 1 1/2 x 3, clip, 5/-; 16 + 16, 350v, 1 x 2, clip, 3/6; 32 + 32, 350v, 1 1/2 x 2, clip, 4/-; 2, 350v, 1/2 x 2, tag, 1/-; 100, 350/425v, 1 1/2 x 3, clip, 4/-; 50 + 50, 350/425v, 1 1/2 x 3, clip, 4/6; 100 + 200, 350v, 1 1/2 x 4 1/2, clip, 7/6; 8 450v, 1 x 2, clip, 1/9; 20 + 10, 450v, 1 x 3, clip, 4/-; 8 + 8, 500v, 1 1/2 x 2, clip, 4/-; Photoflash Types, 1,000 mf, 200v, 1 1/2 x 4 1/2, clip, 12/6; all all cans, some with sleeves, all voltages, wkg., surge where marked, new stock, guaranteed. Television Chassis, cadmium plated steel, size 13 x 13 x 2 1/2 in., complete with 13 valveholders (9-B9A Pax, 1-B9A Cer., 2-B7G Cer., 1-Int. Oct. Ampl.), 20 various tag strips, cut away for metal rec. line trans., etc., 9/11 each, post paid; front and rear tube mounts to fit above chassis, 3-pair, post paid. P.M. focus Magnets, wide angle, tetrode tube, fully adjustable 9/11, post paid. Scanning Coils, wide angle, with mounting lugs, 19/6, post paid. Vision I.F.s (2nd, 3rd and 4th), freq. 34 mc, slug tuned, size 13/16 x 13/16 x 2 1/2 in. can. set of 3, 5/6, post paid. T.V. Rectifiers, H.W., 250v, 350mA, 2 1/2 in. fin. x 1 in. long, 12/6, post paid. Mains trans., 250-0-250v, 120mA, 6.3v, 2.5A, 6.3v, 0.6A, Pri. 0-110-125-150-205-225-245v, 17/-, post paid. 1000 W/W Pots, 3w, lin. spindle, 2.6, 8 mf, 600/750v, Paper Conds., 4, 2 in. x 4 1/2, 6/6. **RADIO CLEARANCE LIMITED**, 27, Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

**MAKING YOUR OWN?** Telescopes, Enlargers, Projectors, or, in fact, anything using lenses. Then get our booklets "How to use Ex-Gov. Lenses & Prisms," price 2/6 ea. Comprehensive lists of optical, radio and scientific equipment free for s.a.e. **H. W. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

**OSMOR** would like you to have Free Practical Wiring Diagrams of the latest published circuits with full lists of components required. Send 7d. (stamps) to **OSMOR RADIO PRODUCTS LTD.**, 418, Brighton Rd., Sth. Croydon. (Croydon 5148.) (See advert., page 688.)

**LOUDSPEAKERS** repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Bullingdon Rd., Oxford.

**SERVICE MANUALS/SHEETS.** Tel./Radio for hire, sale and wanted. S.A.E. enquiries. **W. J. GILBERT (P.W.)**, 24, Frithville Gardens, London, W.12.

**RATES:** 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1 - extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

**AMERICAN RADIO** Plans and Devices. Now available. Hundreds of new and startling devices you can make. Only designs of this type available in UK. Receivers, walkie-talkies, amplifiers, recorders, magic eye alarms, etc., etc. Full lists, data, illustrations. Free for stamp. Send to-day.—A.P.S. (PW), Seageford, King's Lynn.

**ENGRAVING.** Amateurs and trade surplus can be undertaken by getting in touch with **A. G. ENGRAVING**, now at 292, Aislefield Rd., London, S.W.18. (BAT 9897.) (Engravers to well-known makers of Electronic Equipment used by the Aircraft Industry. A.W.R.E., etc.)

**TELEVISION**, 9in. Models, £6/10/-; 12in. Models, £15; all makes working; carriage paid. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

**SEVERAL EARLY MODELS** 9in. Television, complete and mostly working, £5/5/- each; carriage paid. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

**PANL**, the air-drying black crackle paint, 3/6 per 1/8th pt. can. **G. A. MILLER**, 8, Kenton Park Cres., Kenton, Middx.

**ALL TYPES** of new radio valves wanted, small or large quantities; cash payments. **R. H. S. LTD. (W.)**, 155, Swan Arcade, Bradford, 1.

**OSMOR NEWS.** F.M. Switch-tuned Coilpack. Circuits and full information available shortly on request. **OSMOR RADIO PRODUCTS LTD.**, 418, Brighton Road, S. Croydon.

**B.S.R.** Monarch 3-speed Autochange Units, new, in maker's sealed carton, guarantee, complete with instructions, template, suspension springs, £9/15/-; carriage paid; immediate delivery. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

**SEND TO-DAY** for our stock list of T.V. and Radio Bargains, C.R.T.s, Valves, Speakers and all Components. We are the cheapest people in the trade. All goods sold by us are guaranteed. **VIDEO ELECTRONICS (LONDON) LTD.**, Dept. P.W., 16/22, Bacon Street, London, E.1.

**POWER PACKS**, 19in., rack mounting, ex-W.D., type 3, 200/250 input, 225v at 100 ma and 6.3v at 3a out., fully smoothed, 2 meters, set tested, £3/2/6 each, plus 7/6 c. and p. **LAWRENCE**, 131, Waddington Ave., Coulsdon, Surrey.

**THE HIWAYMAN.** A new super Portable Radio for the home constructor; all-dry, 4-valve superhet with Ferrite rod aerial, easy wiring diagrams and instructions, 1/6 (post 3d.). **RADIO EXPERIMENTAL PRODUCTS LTD.**, 33, Much Park St., Coventry.

**GUARANTEED TELEVISION**, 12in. models, first-class picture, 5-channel, £30 each; carriage paid. **THE GRAMOPHONE SHOP**, 19-21, Brockley Rise, Forest Hill, S.E.23.

**MIDDLESBROUGH.** Largest stocks on N.-East coast, Radio, TV components. FM Kits. Gram Cabinets. Tape Decks, Leak Amplifiers, Valves, etc. Callers only. **PALMERS**, 106, Newport Road. (Phone: 3096.)

**TAN IN 24 HOURS.** Super-Ionic Sunray Lamps, ultra-violet infra-red combined; automatic exposure; controlled emission; all mains; listed £7/10/-, our price 80/-, S.A.E. brochure, Dept. 14. **SCIENTIFIC PRODUCTS**, Cleveleys, Lancs.

**MAINS TRANSFORMERS**, ex equipment, guaranteed, prim. 230v, 50c. sec. 250v, 30 m/a, 6.3v 1.5a, 5v 2a, 7/- each, post 1/-, **HERMES RADIO**, Glazebury, nr. Manchester.

**EX A.M. HIGH TENSION BATTERIES.** All perfect and guaranteed. Hundreds of satisfied customers to date: 90 x 7 1/2 v 6, 60 x 1 1/2 v 4 1/2, 90/1 1/2 High Cap. 10/8, 64 x 86 x 2 1/2 v 10/6. Special offer due to further bulk purchase. Plenty to go at. Midget 120v 2/3, 6 for 11/-, 12 for 20/-; 22 1/2 v 2/- ea., 6 for 10/-, 18-doz., 67 1/2 (BIOI), 4-, 6 for 20/-, 30/- doz.; 30v, 1/9, 6 for 8/-, 14-doz. All inc. p. & p.; s.a.e. for list. **DIGGINS**, 129, Radnor St., Hulme, Manchester, 15.

**AMERICAN MAGAZINES.** Year's subscription "Audio" 35/-, "High Fidelity" 50/-. Specimen copies 4/- and 5/- each. Catalogue free. **WILLEN LTD.** (Dept. 40), 9, Drapers Gardens, London, E.C.2.

## FOR SALE

**CAR CIGARETTE LIGHTERS**, 6 or 12 volt, 7/6, post free. **WHITSAM ELECTRICAL PRODUCTS**, 18, Woodrow Close, Perivale, Middlesex.

**CANDELABRUM**, 19.9, ideal Xmas gift. 3 light lounge fitting, with flex and lamp holders, 3 shades in glass or plastic. P. and p. 2/9. Transformers, 3/9, 350-0-350v, 12v, 4v, htrs.; Prim. 100-250v, make ideal auto trans. p. and p. 2/3. Transformers, 3/9, 280-0-280v, 6v at 2.5 amp, 5v at 2a, 4v at 2a; p. and p. 2/3. O.P. Transformers, 1/3, 2.5 ohms, std.; p. and p. 9d.; 12/6 doz.; p. and p. 2/-, **DUKE & CO.**, 621, Romford Rd., Manor Pk., E.12. (GRA 6677.)

## WANTED

**TRANSMITTER/RECEIVER** Stations TR-194, TR-195, TR-196, ARC-1, ARC-3 and Wireless Sets 62, 7. **GILFILLAN & CO. LTD.**, 7, High Street, Worthing. (Tel.: 8719.)

## VALVES

**WANTED.** Valves EY51, ECL80, KT61, 6U4GT, PL81, 3524, etc., etc. prompt cash. **WM. CARVIS LTD.**, 103, North Street, Leeds, 7.

**ALL TYPES** of Valves required for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcoet Road, N.W.1. (PRImrose 9090.)

## EDUCATIONAL

**BUILD YOUR OWN T/V** and learn about its operation, maintenance and servicing. Qualified engineer-tutor available whilst you are learning and building. Free Brochure from **E.M.I. INSTITUTES**, Dept. PW58, London, W.4. (Associated with H.M.V.)

**A.M.I.Mech.E., A.M.Brit.I.R.E.,** City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook, free. B.I.E.T. (Dept. 242B), 29, Wright's Lane, London, W.8.

**WIRELESS.**—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **BST: LTD.** 179, Clapham Rd., London, S.W.9.

**THE WIRELESS SCHOOL.** Day, Evening and "Radiocerts", Postal Courses; s.a.e. for prospectus. **THE DIRECTOR**, 21, Manor Gardens, London, N.7.

**FREE!** Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit.I.R.E. City and Guilds, R.T.E.B., and other Professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to **E.M.I. INSTITUTES**, Dept. PW28, London, W.4.

**WIRELESS.** See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus, **WIRELESS COLLEGE**, Colwyn Bay.

**MERCHANT NAVY** Wireless School, Overseas House, Brooks' Bar, M/cr 16.

**T/V and RADIO.**—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc., on "no pass—no fee" terms. Over 95% successes. Details of exams, and home training courses in all branches of radio and T/V; write for 144-page handbook free. **B.I.E.T.** (Dept. 242G), 29, Wright's Lane, London, W.8.

**ASTRAL RADIO PRODUCTS**

**'HOME RADIO,'** 32 page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d. **TRF COILS.** Specified for 'Bedside Push-button 4', 'All Dry 3 Band, 3', 'Push-button 4', etc., 6/6 pr. post 6d. Push-button Unit with modification data 7/- **DUAL WAVE HF Coil.** Specified for 'Summer All Dry Portable', 'Modern 1 Valve', 'Modern 2 Valves', 'B 7 G Battery Miniature', etc., 4/3, post 3d. **IFT's Miniature,** 1" x 1 1/2" x 2 1/2" in cans. Extra high 'Q'. Special offer, 8/6 pr., post 6d. **K COILS.** 'AC, B' pass 3', 3/3 each, post 6d. **FRAME AERIALS.** M.W., 5/-, post 4d. **H.P. CHOKE** (Osmor Q.C.1), 6/9, post 4d. **Crystal Set Coils.** L. & M.W., 2/6, post 3d. **82, Centurion Road, Brighton**

**INCORPORATED** Practical Radio Engineers home study courses of Radio and TV Engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. "The Practical Radio Engineer" journal, sample copy 2/-. 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet, 1/-. All post free from the **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

**CITY AND GUILDS** (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. **B.I.E.T.** (Dept. 242A), 29, Wright's Lane, London, W.8.

**VACANCIES FOR SKILLED CRAFTSMEN IN GOVERNMENT SERVICE AT CHELTENHAM**

Experienced in one or more of the following:—

1. Maintenance of radio communication receivers.
2. Sub-assembly lay-out, wiring and testing of radio type chassis.
3. Cabling, wiring and adjustment of telephone type equipment.
4. Fault finding in and maintenance of, electronic apparatus.


**BASIC PAY:** £8 11s. 4d., plus up to £2 10s. merit pay, assessed at interview and based on ability and experience.

Opportunities for permanent and pensionable posts.

Five-day week, good working conditions, single accommodation available.

Apply to: **Personnel Officer G.C.H.Q. (FOREIGN OFFICE)** 53, Clarence Street, Cheltenham.

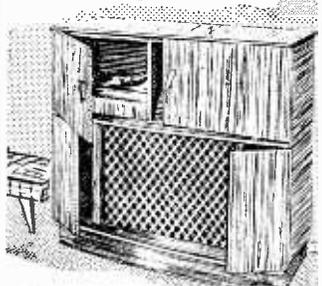**CABINETS and HI-FI EQUIPMENT**  
We can supply any Cabinet to your own specification.



**"The Continental"** (unpolished) £24-15-0

Polished to specification £28.15.0. This elegant Cabinet is the latest in our range. Designed in the continental style, solidly constructed and finished in selected mahogany veneers.

Available in dark, medium, light, high gloss or contemporary finish. We can also supply and fit this or any cabinet with the latest Hi-Fi amplifiers, tuners, transcription units, record changers, speakers, etc.

Send for comprehensive illustrated catalogue of cabinets, chassis, autochangers, speakers, etc., all available on easy H.P. terms.

**LEWIS RADIO COMPANY**  
120 (P.W.2) GREEN LANES, PALMERS GREEN, LONDON, N.13.  
Telephone: BOWes Park 6064.

**GALPIN'S Electrical Stores**

Send for Free List for Small Power Transformers, Electric Light and Slot Meters, Volt, Amp and Milliampmeters, etc.. Transformers made to order.

Radio Bargains for Visitors.

OPEN ALL DAY SATURDAY.

**408 HIGH ST. LEWISHAM LONDON S.E. 13** (Nr. Station Lewisham Junc.)

**1-Finger Pianists**

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

**G & S, 10 Duke St., Darlington, Co. Durham**

**F M and HI-FI Components**

**DENCO F.M. TUNER** circuits 1s. 6d.  
**RADIO CONST'R. F.M.** 2s. 0d.  
**MULLARD AMPLIFIERS** " 3s. 6d.  
**G.E.C. 912 PLUS AMPLIFIER** " 4s. 0d.  
**G.E.C. F.M. PLUS TUNER** " 2s. 6d.

Separate price lists available on request to **J. T. FILMER MAYPOLE ESTATE, BEXLEY, KENT.** Tel. Bexleyheath 7267.

**ANNAKIN'S BARGAINS**  
A.C. Motors, Synch. small. Gears down to 11 r.p.m. New. Only 13/- 110v. only. **Main: Transformer,** tapped 200-250 v. To suit above motor. (Also has 6 v. windings.) New, 10/-.

**RF27** Units with 3 valves. Damaged dials. £1. Headphones, single, low res., and head-band, 8/- New. Boxed. **Unit with two CV181 (9D6) valves,** midjet relay, 4 Rotary switches, ww potm., 4 transformers. Soiled. Cheap at 16/6. All above cart. free. Money Back Guarantee. **25, ASHFIELD PLACE, OTLEY, YORKS**

**BROOKS (RADIO)**

4 Charles Street, Morecambe, Lancs.

Tested—VALVES—Guaranteed

1A7	11/-	6X4	7/6	EF80	10/6
1C5	9/6	6X5	6/6	EF86	11/-
1N5	9/6	7B7	8/6	EL41	10/6
1R5	7/6	7C5	8/6	EM34	10/6
1S5	7/6	7C6	8/6	EY51	12/6
1T4	7/-	7S7	8/6	EZ40	8/6
1U4	7/6	7Y4	8/6	EZ80	8/6
3S4	7/6	12K7	8/6	PCB34	11/6
3V4	8/-	12K8	9/-	PCF82	12/-
5U4	8/6	12Q7	8/6	PL81	11/6
5Y3	7/6	25Z4	8/6	PL82	9/6
3Z4	8/6	35L5	8/6	PL83	12/-
6AL5	6/6	35Z4	8/6	PY80	9/6
6AM6	8/6	80	8/-	PY81	10/-
6AT6	8/-	EABC80	10/-	PY82	9/-
6BA6	8/6	EAF42	10/-	PY83	11/6
6BE6	8/6	EBG41	10/6	UYC41	9/6
6K7	8/6	EBP80	10/-	UYC42	11/-
6K8	8/6	ECC81	11/-	UF41	10/6
6Q7	9/-	ECC82	11/-	UL41	10/6
6SN7	8/6	ECC83	11/-	UY41	8/6
6V6	8/6	ECH42	11/-	UY31	8/6
		ECL80	11/-		

Plus 6d. per valve P. & P.

**BAND II. AERIALS.**—5-element loft-type. 45/6. 5-element mast attachment, 51/6.

**AERIAL X-Co-ax** for Band 3 lead-ins.. 10/4. yd. Solderless Co-ax Plugs, 1/3 each.





**PULLIN**  
SERIES 300.  
**TEST METER**  
A.C./D.C. 10000 DIV  
21 RANGES  
100µA to 1000V  
COMPLETE IN THE LIST  
WORKS WITH TEST LEADS  
CLIPS AND LEADS  
FULLY GUARANTEED

SENT POST FREE FOR £2. 10. 0 AND  
NINE FURTHER MONTHLY PAYMENTS  
OF £1.4.6. CASH PRICE £12.7.6.

**FRITH RADIOCRAFT LTD**

10-17, CHURCHGATE, LEICESTER. PHONE 55927  
28 HIGH STREET, NEWBURY, RAGBELL, BUCKS. PHONE 237

**SPARKS' DATA SHEETS**

Constructional Sheets of Guaranteed Tested Radio Designs.

**FOUR NEW DESIGNS**  
The "SEAFARER" - A "hot" One-valve for batt. operation. Iron dust-core coil. M/L waves. Very efficient. Ideal for beginner or as a good "stand-by" Set. D. Sheet with full instructions, 3/-, post free.  
The "SEAFARER" - 2-V. batt. operation. M/L waves plus FULL TRAWLER band. Iron dust-core coils. Good speaker sizes. A really little Set. D. Sheet, 3/-, post free.  
The "STAR" - 2-V. batt. operation. A powerful little Set for good reception of M/L stations. Iron dust-core coil. Simple but very efficient. D. Sheet, 3/-, post free.  
**TO ALL D.X. 2 OPERATORS**  
Convert your D.X. 2 to a 3-V. T.R.F. unit with a specially designed Add-on H.F. model. D. Sheet, 3/-, post free.  
**SEND 2d. STAMP FOR DETAILED LIST.**  
**L. ORMOND SPARKS (P),**  
Valley Road, Corfe Castle, Dorset



**POWER UNIT 285.** 240 v. input. Output 2,000 v. 5 mA., 350 v. 200 mA., 6.3 v. 17 amps. Double choke and condenser smoothed, complete with 5U4, VU120, EF50, 59/6.

**MIDGET REVERSIBLE MOTORS.** P/M type, size 2in. x 1 1/2in. with 1/2in. spindle. Operates from 4.5-24 v. D.C. Brand new, 8/6 each.

**MODULATOR TYPE 67.** Contains complete A.C. mains power pack, input 230 volts A.C. Output 350 v. 120 mA. and 6.3 v. 5 amp. Choke and condenser smoothed uses 5Z4 rectifier. 11 other valves, 5 SP61, 1 VR116, 2 EB34, and 3 EA50. Brand new, 49/6.

**BLOWER MOTORS.** Small type, 12/24 v. D.C. Brand new, 12/6

**CRYSTAL MIKE INSERTS,** 4/6 each. 300 ft. copper aerial wire, 3/6 reel.

**BUZZERS.** 3 v. D.C. Brand new, 2/6.

**AMERICAN ROTARY TRANSFORMERS.** Input 12 v. D.C. Output 250 v. 80 mA., 22/6. Input 6 v. D.C. Output 250 v. 80 mA., 22/6.

**FERRITE RODS.** 8in. x 5/16in., 2/-.

**CRYSTAL DIODES,** 10d.

**R.E.P. - DUAL RANGE COIL,** 2/6. 0.0005 mfd., variable, 3/6.

**HIGH RESISTANCE PHONES.** Brand new, 12/6 pr.

**MODULATION TRANSFORMERS.** Collins type, P/P 807, 20 watts, 12/6. Ditto for TA-12, 12/6.

**AR.88 WAVECHANGE SWITCHES,** Brand new and boxed, 17/6.

**AMERICAN HEADPHONE ADAP. TORS,** high to low impedance, 1/3.

**465 KC/S B.F.O. UNITS.** Brand new and complete with 155 valve, 8/6.

**GARRARD GRAM MOTORS.** 200/250 v. A.C. Adjustable speed 0.45 r.p.m. Complete with turntable, 22/6.

**ROTARY CONVERTERS.** Input 24 v. D.C. Output 230 v. A.C. 50 cycles, 100 watts. Brand new, 92/6 each.

**FIELD TELEPHONES.** DON. MK. 5. Complete and working, 39/6 each.

**METER SWITCHES.** 1 pole 12 way, 8 bank, 7/6.

**COMMAND RECEIVERS.** Brand new with valves and circuit. Trawler band model, 1.5-3 mc/s., 75/- each.

**COMMAND TRANSMITTERS.** Complete with valves and crystal, 2.1-3 mc/s., 29/6; 4.5-3 mc/s., brand new, 29/6.

**SMOOTHING CHOKES.** All new and unused. 20 h. 175 mA., 10/6; 8 h. 250 mA., 10/6; 9 h. 100 mA., 7/6; 8 h., 100 mA., 8/6; 15 h. 60 mA., 5/6; 30 h. 20 mA., 3/6; 8 h., 50 mA., 5/6.

**CHARGER TRANSFORMERS.** 200/250 v. input. For 6 or 12 v. 1 amp., 9/9; 2, 6 or 12 v. 2 amp., 14/3; 2, 6 or 12 v. 4 amp., 16/6.

**METAL RECTIFIERS,** full wave and bridged for above, 1 amp., 7/6; 2 amp., 11/3; 4 amp., 14/3.

**RHEOSTATS.** Slider type, 14 ohms, 4 amp., 7/6; 1 ohm, 12 amp., 6/6; Rotary type, 8 ohm, 2.5 amp., 7/6; 90 ohm, 0.74 amp., 7/6; 200 ohm, 0.35 amp., 5/6.

**DEAF AIDS.** Complete with 3 sub-miniature valves, crystal mike, tone and volume controls, etc., 19/6. Earpieces to match, 3/6. Leads, 1/-; Spare 1 meg. pots., W/switch, 1/-; Tone control switch, 1/-; Valves, CK505, 2/6.

**HOURS OF BUSINESS:** 9 a.m.—6 p.m., Thursday, 1 p.m. Open all day Saturday. Please print name and address clearly and include postage or carriage on all items.

**Broadcast in Your Own Home**



The New Highly Sensitive Microphone incorporating a specially wound transformer designed to match any Radio or Radiogram, mains or battery. Hours of amusement at a party, good fun for all the family. Suitable for baby alarms and many other purposes. Not a toy but a guaranteed working instrument. Full instructions enclosed. Made to sell at 2/-.

**OUR PRICE 15/-** POST FREE.

Trade supplied

**E. CLAPSHAW**

369, Alexandra Rd., Muswell Hill, London, N.10.

**H.A.C. SHORT WAVE EQUIPMENT**

Noted for over 18 years for S.W. Receivers and Kits of Quality.

Improved designs with Denco coils - One-Valve Kit, Model "A" Price 25/- Two "B" " " " " 50/-

All kits complete with all components, accessories, and full instructions. Before ordering call and inspect a demonstration receiver or send stamped, addressed envelope for descriptive literature.

**"H.A.C." SHORT-WAVE PRODUCTS**

Dept. TD, 11, Old Bond Street, London, W.1.

**NEW BOOKS**

- Beginners' Guide to Radio, by F. J. Camm, price 7/6, postage 6d.
- Radio Valve Data, new edition, by Wireless World, 4/6, postage 6d.
- Radio Servicing, Vol. 1, Basic Electro-technology, by G. N. Patchett, 5/-, postage 6d.
- Electronic Novelties for the Constructor, by Bradley, 5/-, postage 6d.
- F. M. Plus tuner for the G.E.C. 912 Plus Amplifier, 2/6, postage 3d.
- Brimar Valve and Teletube Manual, No. 6, 5/-, postage 6d.
- Radio Servicing Pocket Book, by Molloy, 10/6, postage 6d.

**UNIVERSAL BOOK CO.**

12, Little Newport Street, London, W.C.2 (Adjoining Lisle Street)

**GRAM-PAK AMPLIFIERS**


Complete £3.19.6 P. & P. 2/6

This midget 4-watt amplifier fits neatly into any record player leaving ample room for speaker, 7" x 2 1/2" x 1 1/2". Suitable with any speaker and all modern crystal 3-speed pick-ups. For 200-250 v. A.C. Perfect, distortionless, quality guaranteed.

**ACCESSORIES:**  
BSR crystal turnover P.U., £1.14.6.  
7" x 4" elliptical speakers, 19s. 6d.  
BSR 3-speed player unit with above P.U., £4.12.6d.

The complete outfit ready for your cabinet, £9.10.0 post free.  
6d. stamp for details of this and other models.

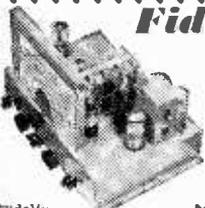**ELECTRO-ACOUSTIC LABS.**  
TAIN: ROSS-SHIRE: SCOTLAND



**Fidelia**  
HAND BUILT RADIO UNITS

THE FIDELIA MAJOR 10

Fidelia AM/FM models give reception of V.H.F. high quality transmissions plus normal wavebands. Major AM/FM 12 valves, £44. De-Luxe AM/FM 11 valves, £33/12/-, F.M. Tuner, £14/3/-. Data sheets free.  
Electro Developments, 2, Anhurst Road, Telcombe Cliffs, Sussex

**T.C.R.C.**

POSTAL COURSES

**RADIO TELEVISION MATHEMATICS**

Backed by 23 years' success

Write for free booklet W

**T/C RADIO COLLEGE**

DUART HOUSE, ASHLEY ROAD, NEW MILTON, HANTS.

# Taylor

## JUNIOR UNIVERSAL METER



### Model 120A

A small 19-range instrument ideal for the enthusiastic amateur. Sensitivity is 1,000 o.p.v. A.C. and D.C. Accuracy: 2% D.C.; 3% A.C.

#### RANGES

Volts D.C.: 0-.25-10-50-250-500-1,000-2,500.

Volts A.C.: 0-10-50-250-500-1,000-2,500.

Milliamps D.C.: 0-1-10-50-500-5,000.

Resistance: 0-2,000 ohms, 0-200,000 ohms. Can be extended to 20 megohms. Automatic overload protection fitted to meter movement.

**PRICE £9.15.0. PROMPT DELIVERY**

**CREDIT TERMS:** Nine monthly payments of £1.44.

**TAYLOR ELECTRICAL INSTRUMENTS LTD.**

Montrose Avenue, Slough, Bucks.

Telephone: Slough 21381. Cables: Taylins, Slough

## G2AK This Month's Bargains

Don't miss this one!

### CRYSTAL HAND MICROPHONES

As illustrated, in silver hammer case with polished grille, handle and 4 feet screened lead. ONLY 21/-.

**12 V. MINIATURE ROTARY TRANSFORMERS.** Output 360 v. 30 mA. Cont. or 310 v. 70 mA. intermittent. Only 4 1/2 in. x 2 1/2 in. overall. Ideal for car radio, mobile TX, etc. Only 21/- . Post 2/-.

**HEADPHONES.** H.R. Type 4,000 ohms, very sensitive. Only 12/6 pr. Post 1/6. C.L.R. type (low res.) 8/6. Post 1/6.

**AMERICAN BREAST MIKES,** swivel head, push to talk and lock-on switch. Excellent job. Only 12/6. Post 1/6.

**BRITISH BREAST MIKES** complete with pr. of H.R. 4,000 ohm phones in wooden carrying case. New W.D. stock, unrepeatable at 17/6. Post 2/-.

**AERIAL WIRE.** Copper, 7/25 stranded: 140ft., 10/-; 70ft. 5/-; Hard Drawn 14g.: 140ft., 17/-; 70ft., 8/6. P. & p. 2/-.

**GLASS INSULATORS.** 1/6 each. Small shell ditto. 4 1/2d. each or 4/- doz. plus postage.

**CONDENSERS.** 8/F 600 v. Trop. 750 v. normal condensers. NEW, ex W.D. stock, 5/6, p. & p. 1/6.

**New TCC Type III.** 8 mfd. 1,000 v. D.C. wk'g. (List over £3). OUR PRICE 10/6, p. & p. 1/9.

No C.O.D. on orders under £1.

**PLEASE PRINT YOUR NAME AND ADDRESS**

**CHAS. H. YOUNG LTD.**

Dept. 'P' 110, Dale End, Birmingham 4. (CEN 1635)

Train for a wonderful  
future in -

# ELECTRONICS

Train to meet the need for pioneers in this  
expanding field.

Every day the demand for the expert in electronics grows. Radio, television, radar and the whole field of industrial automation are rapidly expanding, and the trained specialist assures for himself a well-paid career in this quickly developing profession. Here is your opportunity to enter for

### 1-year course

Full-time day course in the Principles and Practice of Radio and Television. Mainly designed for the training of Radio and Television Servicing Engineers. Next course, commencing May 22nd, is already fully booked. Enrolments for following course, commencing September 11th, now being accepted.

## The E.M.I. College of Electronics

Dept. 32, 10, Pembridge Square, London, W.2.

Telephone: BAYswater 5131/2

The College associated with a world-wide electronics industry, including "His Master's Voice," Marconiphone, Columbia, etc.

## ALL THESE FINE BARGAINS ARE AT

### The Walk-around Shop

**MORSE SIGNALLING LAMPS** (Aldis type) 5in. dia. with sighting arrangement, 2 handles, keying switch, and 2 yds. cable. In wood Carrying Case, price 10/-, plus 3/- p.p.

**WAVEMETER TYPE W1310.** Coverage 155 to 230 Mc/s. continuous, complete with testprod. Input 230 v. 50 cycles. New condition. £3/10/-, plus 7/6 carr.

**TYPE 62A INDICATORS.** Ideal for conversion to oscilloscopes. T.V. units, etc. Containing YCR97, 12 VR91 (EF50), 2 VR54 (BB34), 3 VR92 (EA50), 4 CV118 (SP61). Slow-motion dial. 13 pots and scores of useful components. Size 8 1/2 x 11 1/2 x 18in. In wooden packing case, £3, carriage 7/6.

**DESYNN TYPE Antenna or Beam Position Indication System.** This comprises a Transmitter unit and Indicator which will operate on 12 or 24 volts D.C. and will indicate with instantaneous and smooth pointer movement. The Transmitter is a specially designed potentiometer and will operate the Receiver on a simple three wire system and the receiver in this instance is calibrated in gallons, but dial could be easily altered to indicate a 360 deg. sweep. Transmitter and Receiver with full instructions. Price 12/6, p.p.

**EAR PIECES.** 2,000 ohm C.H.R. or balanced armature type, low resistance. Single units. 3/6 each, plus 6d. p.p.

**MINIATURE I.F. STRIPS.** Size 10 1/2 x 2 1/2 x 3 in. Frequency 9.72 Mc/s. 2 EF92s and 1 EF91. I.F. amps EB91, DET/AGC, EF91, AGC, Amp. and EF91 Limiter. Circuit supplied. Price 8/-, less valves. Post paid.

**AN/APNI TRANSDUCER.** This Unit consists of Magnet, and Coil which is attached to an aluminium diaphragm suspended freely and perforated to prevent air damping. Mounted on a ceramic cover, which sits over the diaphragm, is a form of 2-gang capacitor which has a swing from 10-50 pF. The above unit is used as part of Wobulator described on page 252 of the June "Wireless World." Price 7/6, p.p.

**I.F. AMPLIFIER UNIT.** 460 kc/s with IT4. Brand New and Boxed. Fully screened in-plug-in box; size 2 1/2 in. x 1 in. x 4 1/2 in. Price, with circuit, 10/- ea., plus 1/- p.p.

**PROOPS** Dept. 'P', 52 Tottenham Court Road,  
**BROS. LTD.** London, W.1. LANgham 0141

Shop Hours: 9-6 p.m. Thursday: 9-1 p.m. Open all day Saturday;

## Practical Wireless

# BLUEPRINT SERVICE

### PRACTICAL WIRELESS

*No. of  
Blueprint*

#### CRYSTAL SETS

2/- each	
1937 Crystal Receiver ...	PW71*
The "Junior" Crystal Set ...	PW94*
2/6 each	
Dual-Wave "Crystal Diode" ...	PW95*

#### STRAIGHT SETS

##### Battery Operated

One-valve : 2/6 each	
The "Pyramid" One-valver (HF Pen) ...	PW93*
The Modern One-valver ...	PW96*
Two-valve : 2/6 each	
The Signet Two (D & LF) ...	PW76*

3/6 each	
Modern Two-valver (two band receiver) ...	PW98*

Three-valve : 2/6 each	
Summit Three (HF Pen, D Pen) ...	PW37*

The "Rapid" Straight 3 (D, 2 LF (RC & Trans)) ...	PW82*
---------------------------------------------------	-------

F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ...	PW87*
---------------------------------------------------	-------

3/6 each	
The All-dry Three ...	PW97*

Four-valve : 2/6 each	
Fury Four Super (SG, SG, D, Pen) ...	PW34C*

##### Mains Operated

Two-valve : 2/6 each	
Selectone A.C. Radiogram Two (D, Pow) ...	PW19*

Three-valve : 4/- each	
A.C. Band-Pass 3 ...	PW99*

Four-valve : 2/6 each	
A.C. Fury Four (SG, SG, D, Pen) ...	PW20*

A.C. Hall-Mark (HF Pen, D, Push Pull) ...	PW45*
-------------------------------------------	-------

#### SUPERHETS

Battery Sets : 2/6 each	
F. J. Camm's 2-valve Superhet ...	PW52*

Mains Operated : 4/- each	
"Coronet" A.C. 4 ...	PW100*
AC/DC "Coronet" Four ...	PW101*

*No. of  
Blueprint*

#### SHORT-WAVE SETS

##### Battery Operated

One-valve : 2/6 each	
Simple S.W. One-valver	PW88*

Two-valve : 2/6 each	
Midget Short-wave Two (D, Pen) ...	PW38A*

Three-valve : 2/6 each	
Experimenter's Short-wave Three (SG, D, Pow) ...	PW30A*

The Prefect 3 (D, 2 LF (RC and Trans)) ...	PW63*
--------------------------------------------	-------

The Band-spread S.W. Three (HF, Pen, D, (Pen). Pen) ...	PW68*
---------------------------------------------------------	-------

#### PORTABLES

2/-	
The "Mini-Four" All-dry (4-valve superhet)	

#### MISCELLANEOUS

2/6 each	
S.W. Converter-Adapter (1 valve) ...	PW48A*

The P.W. 3-speed Autogram ...	(2 sheets), 8/-*
-------------------------------	------------------

The P.W. Monophonic Electronic Organ (2 sheets), 8/-	
------------------------------------------------------	--

#### TELEVISION

The "Argus" (6in. C.R. Tube), 3/-*	
------------------------------------	--

The "Super-Visor" (3 sheets), 8/-*	
The "Simplex" ...	3/6*

The P.T. Band III Converter	1/6*
-----------------------------	------

*All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94 are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.*

### AMATEUR WIRELESS AND WIRELESS MAGAZINE

#### STRAIGHT SETS

##### Battery Operated

One-valve : 2/6	
B.B.C. Special One-valver ...	AW387*

##### Mains Operated

Two-valve : 2/6 each	
Consoelectric Two (D, Pen). A.C. ...	AW403

#### SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W.M. to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No of  
Blueprint*

#### SHORT-WAVE SETS

##### Battery Operated

One-valve : 2/6 each	
S.W. One-valver for American ...	AW429*

Two-valve : 2/6 each	
Ultra-short Battery Two (SG, det Pen) ...	WM402*

Four-valve : 3/6 each	
A.W. Short Wave World-beater (HF Pen, D, RC, Trans) ...	AW436*

Standard Four-valver Short-waver (SG, D, LF, P) ...	WM383*
-----------------------------------------------------	--------

##### Mains Operated

Four-valve : 3/6	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ...	WM391*

#### MISCELLANEOUS


Enthusiast's Power Amplifier (10 Watts) (3/6)	WM387*
-----------------------------------------------	--------

Listener's 5-watt A.C. Amplifier (3/6) ...	WM392*
--------------------------------------------	--------

De Luxe Concert A.C. Electrogram (2/6) ...	WM403*
--------------------------------------------	--------
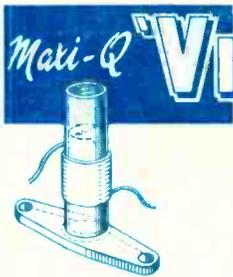
#### QUERY COUPON

This coupon is available until Dec. 6th, 1956 and must accompany all Queries, sent in accord with the notice on our "Open to Discussion" page. PRACTICAL WIRELESS, Dec. 1956.



# Maxi-Q 'VIEW MASTER' T.V.

## 3 STATION TUNER AND MODIFICATION COMPONENTS

### MODIFICATION COILS

Coils for the Modification of the T.R.F. "View Master" into an I.F. Unit for use with the 3 Station Tuner. The packet contains all Coils complete with Iron Dust Slugs. PRICE 20/-.

SWITCH KIT: Fine Tuner, Coil Mounting Plates, Tag Panel, Earthing Wire and Copper Foil for the 3 Station Tuner. PRICE 27/-.  
Fine Tuner sold separately at 4/-.

NOW AVAILABLE: The "Practical Television" reprint booklet giving full details of the complete conversion, price 2/9, post paid, or GIVEN FREE to all customers making one purchase of the three complete kits.

Available from all reputable stockists or direct from Works. Send 1/- in stamps for GENERAL CATALOGUE covering full range of components.

**DENCO (CLACTON) LTD.,** 357/9 OLD ROAD, CLACTON-ON-SEA, ESSEX.

STOP PRESS: MAXI-Q F.M. TUNER UNIT assembled and valued at £9/19/6, inc. P.T. Power Pack at £3.  
Mullard Tape Recorder, Amplifier Chassis, Type A or B, 31/6 each. Power Pack Chassis, 11/6.

*Trace the Trouble in a Trice*

**PIFCO**  
**ALL-IN-ONE RADIOMETER**

- \* Circuit Test
- \* L.T. & H.T. Tests
- \* mA Test
- \* Valve Test

Use the PIFCO All-in-One RADIOMETER for the practical testing of all types of radio and electrical apparatus. You can carry out continuity and resistance tests, check H.T., L.T., and G.B. voltages, also Household Appliances, Car Lighting Systems, Bell Circuits, etc. May be used on A.C. or D.C. mains.

Obtainable from your local dealers.

Write for informative folder to:—

**PIFCO LTD., WATLING ST., MANCHESTER 4**  
and 36-37, UPPER THAMES ST., LONDON, E.C.4

ONLY **32/6** COMPLETE

## MAKE SOUND JOINTS SIMPLY BY USING Multicore

### ERSIN MULTICORE

Contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON

5/-

### HANDYMAN'S CARTON

Suitable for 200 average joints. 6d.



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

### ARAX MULTICORE

#### FOR METAL FABRICATION

(Not wire-to-tag joints)  
Contains 2 cores of Arax flux. Flux residue is easily removed with water.

SIZE 8 CARTON

5/- Handymans Carton 6d.



### HOME CONSTRUCTORS 2/6 PACK

In addition to the well-known Home Constructors Pack (containing 19ft. of 18 s.w.g. 60/40 alloy) a similar pack is now available containing 40ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits



### BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruded flex 3/6 each



## MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3638)