


• A HI-FI A.M. RECEIVER •

PRACTICAL 13

WIRELESS

JUNE
1958

EDITOR: F.J. CAMM

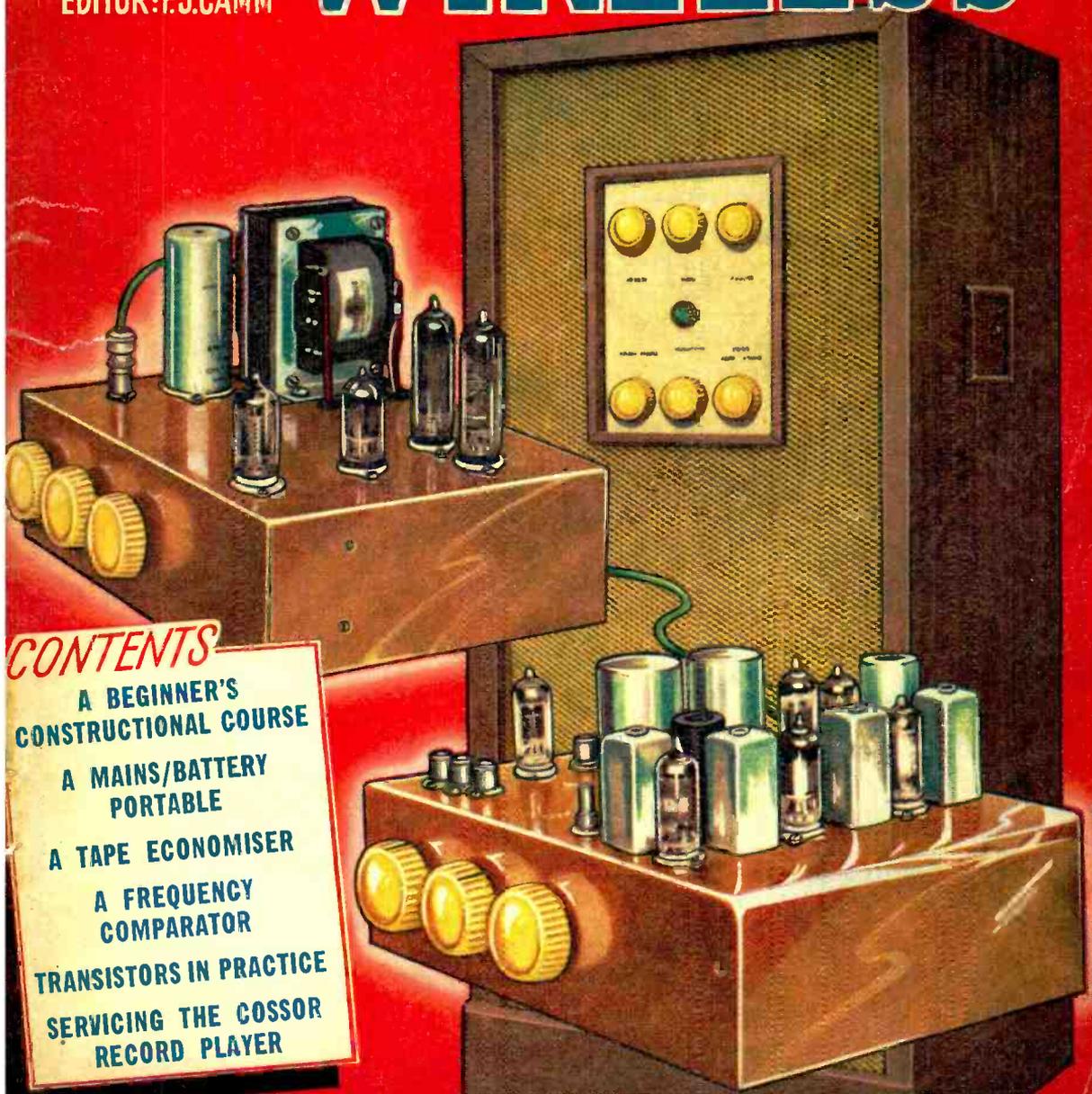

CONTENTS

- A BEGINNER'S CONSTRUCTIONAL COURSE
- A MAINS/BATTERY PORTABLE
- A TAPE ECONOMISER
- A FREQUENCY COMPARATOR
- TRANSISTORS IN PRACTICE
- SERVICING THE COSSOR RECORD PLAYER

Supreme in Service

'MICROMITE'

DRY ELECTROLYTIC CONDENSERS



These small but high quality electrolytics have proved so popular that the range has been greatly extended. The use of high-gain etched foil electrodes keeps size and weight down, making the condensers suitable for suspension wiring. Conservatively rated; long shelf life ensured; green plastic insulating sleeving prevents short-circuits.

Capacity in μ F.	Peak Wkg. Volts	Surge Volts	Dimns. in Ins.		Type No.	List Price Each
			Length	Diam.		
50	12	15	1 1/2	1/8	CE87B	2/9
25	50	60	1 1/2	1/8	CE88DE	3/-
1	350	400	1 1/2	1/8	CE86L	2/6
8	350	400	1 1/2	1/8	CE99LE	3/3
16	350	400	2	1/8	CE91LE	4/-
32	350	400	2	1/8	CE93LE	6/-
4	450	550	1 1/2	1/8	CE99PE	3/3
8	450	550	1 1/2	1/8	CE90PE	3/6
16	450	550	1 1/2	1/8	CE92PE	5/-
32	450	550	2	1/8	CE94PE	7/6



THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION : NORTH ACTON · LONDON · W.3 · Telephone : ACOrn 0061

The makers of the world famous H.F.1012 announce a speaker that will achieve even greater success



Stentorian **H.F.1016**

- ★ 10" Die Cast Chassis ★ 16,000 gauss magnet
- ★ 10 watts handling capacity
- ★ Patented Stentorian Cambric Cone
- ★ Universal Impedance Speech Coil (instantaneous matching at 3, 7.5 and 15 ohms.)
- ★ 30-15,000 c.p.s. frequency response
- ★ 35 c.p.s. bass resonance

Incorporates a very powerful magnet assembly and is noteworthy for its brilliant transient response when mounted in a bass reflex cabinet. May also be used with Stentorian T.10 Tweeter Unit as an outstanding two-speaker system at remarkably low cost.

£8 (inc. P.T.)

Hear it at all leading Hi Fi dealers; write our London office (109 Kingsway, W.C.2) for name of nearest stockist, and leaflets on all W.B. products. The complete range is demonstrated at this address every Saturday, 9 a.m. to 12 noon.



WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS

EMI "HIS MASTER'S VOICE" MARCONIPHONE · COLUMBIA


Announce NEW PRACTICAL WAY OF LEARNING AT HOME

NEW — completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.

NEW — experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course.

Radio and television courses, with which specially prepared components are supplied, teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern Radio and T/V equipments.

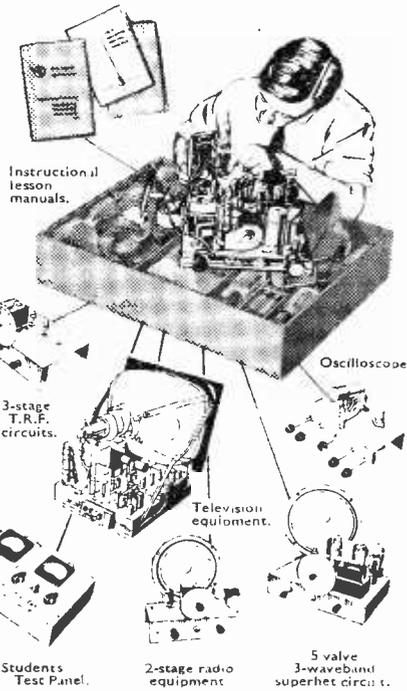If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure giving full details. There is no obligation whatsoever.



Courses with Equipment
RADIO · SHORT WAVE RADIO
TELEVISION · MECHANICS
CHEMISTRY · PHOTOGRAPHY
ELECTRICITY · CARPENTRY
ELECTRICAL WIRING · 'HI-FI'
DRAUGHTSMANSHIP · ART etc.

E.M.I. Factories at Hayes England.



EMI INSTITUTES

Fill in for **FREE BROCHURE**
 E.M.I. INSTITUTES, Dept. 32 X, London, W.4.

Name _____ Age _____ (If under 21)

Address _____

I am interested in the following subject(s) with _____
 without equipment _____

(We shall not worry you with personal visits)

FREE

BLOCK CAPS PLEASE

JUNE, 58

IC107

The only Home Study College run by a World-wide industrial organisation

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250 v., 50 c.p.s. Guaranteed 12 months.

ASSEMBLED CHARGERS
 6 v., 1 amp. 19/9
 6 v. or 12 v., 1 amp. 27/9
 6 v., 2 amps. 29/9
 6 v. or 12 v., 2 amps. 36/9
 6 v. or 12 v., 4 amps. 56/9
 Above ready for use. Carr. 3/6 With Mains and output leads.

SELENIUM RECTIFIERS
F. W. BRIDGE TAPES
 612 v. 4 a. 411 L.T. Types H.W. 1.11
 612 v. 2 a. 9/9 2.4 v. 1 a. 1.11
 612 v. 2 a. 11/9 6.12 v. 3a. H.W. 2.9
 612 v. 4 a. 14/9 H.T. Types H.W. 3.9
 612 v. 6 a. 19/9 150 v. 40 mA. 3/9
 612 v. 6 a. 25/9 250 v. 50 mA. 5/9
 612 v. 10 a. 25/9 250 v. 80 mA. 7/9
 612 v. 15 a. 35/9 250 v. 250 mA. 11/9

BATTERY CHARGER KITS
 Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse-holders, Grommets, panels and circuit. Carr. 2/9 extra.
 6 v. or 12 v. 1 amp. 22/9
 6 v. 2 amps. 25/9
 6 v. or 12 v. 2 amps. 31/6
 6 v. or 12 v. 4 amps. 53/9

ASSEMBLED CHARGER
 6 v. or 12 v. 2 amps.
 Fitted Ammeter and selector plug for 6 v. or 12 v. Louvered metal case, finished attractive hammer brush. Ready for use. With mains and output leads. Fused. Double. Only Carr. 19. **49/9**

Assembled 6 v. or 12 v. 4 amps.
 Pitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvered steel case with stoved blue hammer finish. Fused. Ready for use with mains and output leads. Carr. 16. Credit Terms: Deposit 30/- and 4 monthly payments, 13/-



R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c.p.s. Screened.
TOP SHROUD DROP THROUGH
 250-0-250 v. 70 mA. 6.3 v. 2a. 5 v. 2a. 16/9
 350-0-350 v. 80 mA. 6.3 v. 2a. 1 v. 2a. 18/9
 250-0-250 v. 100 mA. 6.3 v. 4a. 5 v. 3a. 23/9
 300-0-300 v. 100 mA. 6.3 v. 4a. 5 v. 3a. 23/9
 350-0-350 v. 100 mA. 6.3 v. 1a. 5 v. 3a. 23/9
 350-0-350 v. 100 mA. 6.3 v. 4a. C.T. 0-4-5 v. 3a. 23/9
 350-0-350 v. 150 mA. 6.3 v. 4a. 5 v. 3a. 29/9
FULLY SHROUDED UPRIGHT
 250-0-250 v. 60 mA. 6.3 v. 2a. 5 v. 2a. 17/6
 Midjet type 21-3-3in. 25/9
 250-0-250 v. 100 mA. 6.3 v. 5a. 5 v. 3a. 26/9
 250-0-250 v. 100 mA. 6.3 v. 6a. 5 v. 3a. 26/9
 For R135 conversion. 31/-
 400-0-400 v. 100 mA. 6.3 v. 1a. 5 v. 3a. 26/9
 500-0-500 v. 100 mA. 6.3 v. 4a. 5 v. 3a. 26/9
 300-0-300 v. 130 mA. 6.3 v. 4a. 8.3 v. 1a. 26/9
 For Mullard 510 Amplifier. 35/9
 350-0-350 v. 150 mA. 6.3 v. 4a. 5 v. 3a. 33/9
 350-0-350 v. 150 mA. 6.3 v. 2a. 6.3 v. 2a. 3 v. 3a. 35/9
 425-0-425 v. 200 mA. 6.3 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3a. Suitable Williamson Amplifier, etc. **40/9**

EX-GOVT. SMOOTHING CHOKES
 250 mA. 20 H 200 ohms 12/9
 250 mA. 5 H 50 ohms 19/9
 150 mA. 10 H 100 ohms 11/9
 150 mA. 6-10 H 150 ohms Trop. 6/9
 120 mA. 12 H 100 ohms 9/9
 100 mA. 5 H 100 ohms 31/1

CHARGER TRANSFORMERS
 All with 200-250 v. 50 c.p.s. Primaries:
 0-9-15 v. 11 a. 11/9; 0-9-15 v. 3 a. 16/9;
 0-9-15 v. 5 a. 19/9; 0-9-15 v. 6 a. 23/9.

SMOOTHING CHOKES
 250 mA. 5 H 100 ohms 12/9
 150 mA. 7-10 H 250 ohms 11/9
 100 mA. 10 H 200 ohms 8/8
 80 mA. 10 H 350 ohms 9/9
 60 mA. 10 H 400 ohms 41/1

OUTPUT TRANSFORMERS
 Midjet Battery Pentode 8E1 for 384, etc. 3/9
 Small Pentode 5,000Ω to 3Ω 3/9
 Small Pentode 7,000Ω to 3Ω 3/9
 Standard Pentode 5,000Ω to 3Ω 4/9
 Standard Pentode 7,000Ω to 3Ω 4/9
 10,000Ω to 3Ω 4/9
 Push-Pull 10-12 watts 6V6 to 3Ω or 15Ω 15/9
 Push-Pull 10-12 watts to match 6V6 to 3-5Ω or 15Ω 16/9
 Push-Pull 6L84 to 3 or 15Ω 16/9
 Push-Pull 15-18 watt. 6L6, KT68 22/9
 Push-Pull 20 watts, sectionally wound 6L6, KT68, etc. to 3 or 15Ω 47/9

MAINS TRANSFORMERS
 Manufacturers surplus. Primaries 200-250 v. 50 c.p.s. 375-0-375 v. 150 mA. 6.3 v. 4 a. C.T. 6.3 v. 1 a. Fully shrouded. 22/9.
 325-0-325 v. 100 mA. 6.3 v. 2.5 a. 5 v. 2 a. Drop through type. 18/9. Postage on either type 2/9.

FIlament TRANSFORMERS
 All with 200-250 v. 50 c.p.s. primaries 400 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 4 a. 8/11; 6.3 v. 6 a. 8/12; 3 a. or 2.4 v. 1.5 a. 17/6.
JUNCTION RESISTORS
 Brand new R.F. Type 17 6. A.F. 7 6.
VOLUME CONTROLS with tone (in. diam.) spindle all values less switch, 2/9, with S.P. switch, 3/9; with D.P. switch, 4/6.
H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Input 200-250 v. A.C. Output 120 v. 40 mA. Fully smoothed and rectified supply to charge 2v. accumulator. Price with louvered metal case and circuit, 29/6, or ready for use. 8/9 extra.

ELIMINATOR TRANSFORMERS
 Primaries 200-250 v. 50 c.p.s. 15/9
 120 v. 10 mA. 0-5 v. 1 a. 19/9
 90 v. 15 mA. 4-0-4 v. 500 mA. 9/9

THE SKYFOR T.R.F. RECEIVER.
 A design of a 3-valve Long and Medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. It consists of 3 audio band detector. Power pentode output is used. Valve line-up 6K7, 8P61, 6V6G. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-point wiring diagrams, instructions and parts lists. 19. Maximum building cost 24/9 6. Including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 s. 6d. extra.

EX-GOVT. DOUBLE WOUND STEP UP STEP DOWN TRANSFORMERS.
 10-0-100-230-220-240 v. to 5-0-75-115-135 v. or REVERSE. 80-100 watts. Only 12/9, plus 2/9 post. 10-0-100-230-220-240 v. to 0-9-110-122-136-148 v. or REVERSE. 200 watts 35 s. plus 7/6 carr. Both 50 c.p.s.

EX-GOVT. MAINS TRANSFORMER.
 Primary 0-110-120-200-210-220-240-250 v. 20 c.p.s. Secs. 275-0-275 v. 100 mA. 6.3 v. 7a. 5 v. 3a. Govt. rating. 22/9. Following with 240-250 v. primaries, 400-0-400 v. 200 mA. 5 v. 3 a. 5 v. 2 a. 19/9; 230-0-230 v. 100 mA. 12.6 v. 1.5 a. 5 v. 2 a. 11/9; 12.6 v. 3 a. 5 v. 3 a. 9/9. Postage 2/9 on any type.

EX-GOVT. CASES. Size 14-10-8 1/2 in. high well ventilated, black crackle finished, undrilled cover. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER FOR CORDLESS PORTABLE AMPLIFIER. Only 9/9, plus 2/9 postage. Size 8 1/2 x 13 1/2 x 6 1/2 ins. with undrilled well ventilated cover, finished in stoved grey enamel. Suitable for charger or instrument case. 7/9, plus 2/9 post.

EX-GOVT. VALVES (NEW)

1R5	7/9	615	5/9	ECC91	4/9
1T4	7/9	6U6	4/9	EF80	7/9
1S5	7/9	6V6G	4/9	EB12	4/9
354	8/9	6X4	6/9	EF91	8/9
5Y6G	8/9	6X5GT	8/9	EL32	3/9
5U4G	8/9	6L6G	11/9	KT44	8/9
5Z4G	8/9	807	7/9	KT61	9/9
6KT6	5/9	12A6	4/9	EZ90	6/9
6S17GT	6/9	15D2	4/9	EL84	10/6
6SL6GT	8/9	35Z4GT	8/9	FW4500	9/9
6SN7GT	8/9	MH4	4/9	FW4500	9/9
6AT6	7/9	ECC83	9/9	SP61	2/9

SPECIAL OFFERS: Electrolytes. 32-32-32 mid. 250 v. Dubilier small cans 12/9 ea. 150 mid. 450 v. 3/9. Small .0005 mfd. 2-gang. 4/9 ea. Westinghouse Rectifiers 250 v. 250 mA. 7/9. CO-AXIAL CABLE. 75 ohm. 1/4 in. 8d. yd. Twin-Screened Feeder 11d. yd.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-diy battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c.p.s. is available. Suitable for all battery portable receiver, requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9, or ready to use. 46/9.



VERS normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions. 49/9, or ready for use. 59/6.

MINIATURE MOTORS. 21 28 v. D.C. or A.C. made by Hoover Ltd., Canada. Size only 2 1/2 x 1 1/2 in. Spindle 1 1/2 in. long, 1/4 in. diam. Brand New. 9/9.


HEADPHONES. Brand new. Low resistance. Only 6/9 pr.

EX-GOVT. 50 WATT SPEECH AMPLIFIERS. For normal 200-250 v. A.C. mains. Complete with hand mike with good length of lead and all valves. Ready for use in wood transit cases. Only 9 Gns., carr. 15/-.

TANNOY RE-ENTRANT 8 WATT SPEAKERS. For use with above. 27/6 ea.

EXTENSION SPEAKERS
 Ready for use in walnut veneered cabinet.
 8 in. 2-3 ohms. 29/11.
 8 in. 2-3 ohms. 35/9.
 Very limited number.

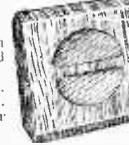EX-GOVT. METAL BLOCK PAPER CONDENSERS.
 4 mid. 350 v. 2/6; 4 mid. 1,000 v. 4/9;
 8 mid. 500 v. 4/9; 10 mid. 500 v. 3/9.



R.S.C. A8 ULTRA LINEAR 12 WATT AMPLIFIER

High-Fidelity Push-Pull Amplifier with "Built-in" Tone Control. Precision stages, high sensitivity, includes 5 valves, 400 outputs. High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condenser of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE** "Lift" and "Cut" Frequency response 18 db., 30-20,000 c/s. 5% negative feedback. Hum level 71 db. down. **ONLY 70 millivolts INPUT** required for **FULL OUTPUT**. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

For **STANDARD** or **LONG - PLAYING RECORDS**. For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS**, etc. **12-T SOCKET** with plug provides 100 v., 20 mA. and 6.5 v., 1.5 a. For supply of **RADIO FEEDER UNIT**. Size approx. 12.8-7in. For A.C. mains 200-250 v., 50 c/s. Outputs for 3 and 15 ohm speakers. Kit or assembled. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value at **£7 15-0** of factory built 45 - extra Carriage 10 -.

£7-15-0

U. required hatched metal cover with 2

COLLARO RC64 3-SPEED AUTO-CHANGERS with Studio pickup Brand new. For 110 v., 50 c/s. A.C. mains. Price with 110 v. 200-250 v. A.C. Trans. only 7 Gns. Carr. 5-6.

COLLARO CONQUEST 4-SPEED AUTO-CHANGERS with high fidelity Studio Pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c/s. A.C. mains. Our price **£9 19-6**. Carr. 5-6. Credit Term. Deposit 3 gns. and 9 monthly payments of 21-6.


COLLARO 4-SPEED SINGLE PLAYER with separate pick-up, as fitted RC457. For 200-250 v. A.C. mains. **£4 12-6**. Post 3-9.

1G3 MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with above or any other single or auto-change units. Output for 2-ohm speaker. For 200-250 v., 50 c/s. A.C. mains. Overall size 6 x 3 1/2 x 2 1/2 in. Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 55-9.

SUPERHET FEEDER UNIT. Designed of high quality Radio Tuner Unit, especially suitable for use with any of our Amplifiers. Delayed A.V.C. employed. W.Ch. Sw. incorporates Gram position. Controls are Tuning, W.Ch. and Vol. Only 250 v., 15 mA. H.T. and L.T. of 6.3 v., 1 amp. required from amplifier. Size of unit approx. 9-6-7in. high. Simple alignment procedure. Point-to-point wiring diagrams, instruction and priced parts list with illustration. 2-6. Total building cost, **£4 15 -**. For descriptive leaflet send S.A.E.

LINEAR 145 MINIATURE 4.5 WATT QUALITY AMPLIFIER. Suitable for use with Collaro, B.S.R. or any other record-playing unit, and most microphones. Negative feedback 12 db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v., 50 c/s. Output for 2-ohm speaker. Three miniature Mullard valves used. Size of unit only 6-5-5in. high. Output for 2-ohm speaker. Guaranteed for 12 months. Only **£3 19-6** plus 10% A.E. for illustrated leaflet. Credit Terms. Deposit 2-6 and 5 monthly payments of 22-6.


LINEAR "DIATONIC" 10-14 WATT HIGH-FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER. For 200-250 v., 50 c/s. A.C. mains. Valve line-up ECC83, ECC83, EL84, EL84, 6Z61 miniature Mullard. The unit has built-in contained Pre-amplifier, Tone Control, Bass, and separate Bass and Treble Controls. Independent "Mike" and Gram input sockets are provided. Size is only 9-7-6in. Output Matchings for 3 and 15 ohm speakers. Only 12 Gns. or Deposit 2-9 plus 10% A.E. and 9 monthly payments of 26-9. Send S.A.E. for leaflet.

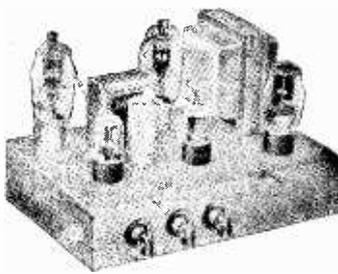

carrying handles can be supplied for 18-9. Additional input socket with associated Vol. control so that two different inputs such as Gram and "Mike" or Tape and Radio can be mixed, can be provided for 13 - extra. Guaranteed 12 months. **TERMS** on assembled two input model: **DEPOSIT 25-6** and nine monthly payments 25-6.

R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home. Small club, only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads, in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down. 15 db. of negative feedback is used. H.T. of 200 v., 25 mA. and L.T. of 6.3 v., 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v., 50 c/s. Output for 2-ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate with Blue hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only **£4 15 -**, or assembled ready for use 25 - extra, plus 3-6 extra, or Deposit 2-6 and 5 monthly payments of 22-6 for assembled unit.

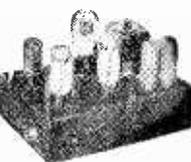

LINEAR 145 HIGH QUALITY TAPE DECK AMPLIFIER. With "built in" power pack and output Ready for Use. **ONLY 12 GNS.** Truly Astonishing Collaro, Carr. 7-6. Brennell, etc. For A.C. Mains 200-250 v., 50 c/s. Linear frequency response of 3 db., 50-11,000 c/s. Negative feedback equalisation. Illustrated leaflet Cd.

SENSATIONAL OFFER STAR GALAXY 4-SPEED MINOR AUTO-CHANGER. A precision manufactured unit with a motor which virtually eliminates "wow" and rumble. Playing Deck size 11 x 10in. Depth below baseboard 2in. Above 5in. Fitted pick-up with dual sapphire tipped stylus. For 200-250 v. A.C. mains. A once in a lifetime opportunity. Only Brand new cartoned. **£3-19-6** Carr. 3-9

TERMS: C.W.O. or C.O.D. NO C.O.D. under £1. All goods supplied subject to terms and guarantee as detailed in current catalogue. Open 9 to 5-30; Sat. until 1 p.m. Catalogue 6d. Trade list 5d. S.A.E. with all enquiries.

R.S.C. 30 WATT ULTRA LINEAR HIGH-FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response 3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 6Z61 output valves. All components are chosen for reliability. 81A valves are used. EF86, EF83, ECC83, 807, 6Z61. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that **ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE**. The unit is designed for **CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS**, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT**. An extra input with associated Vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v., 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover as for

£10-19-6

As can be supplied for 19-9. The amplifier can be supplied, factory built with 12 months' guarantee, for **£13.10. TERMS: DEPOSIT 3-6** and 9 monthly payments of 31 -.

R.C.A. 2C WATT RE-HEARNT SPEAKERS. 15 ohms or 700 ohms matching. For Outdoor work. Only 8 GNS. **P.M. SPEAKERS**. All 2-3 ohms, suitable for use with 1G3, 1A5, A5, or A7 amplifiers. 5in. Goodman's, 17-0-7 in. Elliptical Elac., 19-9. 6in. Goodman's, 17-9. 8in. Rola, 19-9. 10in. R.A., 27-9. 10 x 6in. Elliptical Goodman's, 29-9. 12in. Plessey, 29-11. 16in. W.B., Stenorian 3 or 15 ohms type HP1012 10 watts, hi-fidelity type. Recommended for use with our A8 Amplifier. **£4 10-9**. 12in. Plessey 3 ohms 10 watts. 12,000 lines, 56-6

PLESSEY DUAL CONCENTRIC 19in. 15 ohms HIGH FIDELITY SPEAKER (12,000 lines) with built-in tweeter (completely separate elliptical speaker with choice, condensers, etc.), providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price complete, only **£5 17-6**.

M.E. SPEAKERS 2-3 ohms, 8in. R.A. Field, 800 ohms, 11-9.

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER

For 230-250 v., 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5. Complete Kit with diagrams. **£3 15 -**. Assembled 22-6 extra. Carr. 3-6.



AM/FM RADIOGRAM CHASSIS HIGH QUALITY 6-8 WATT PUSH-PULL OUTPUT

For 200-250 v. Mains. Long wave. Medium P.M. and Gram. Complete with 4 B.V.A. valves. Guaranteed 12 months. Only 22 GNS. Or Deposit **£2 12 -** and 5 monthly payments of 22-12.

Post 19 extra under £2 - 2-9 extra under £5. All goods supplied subject to terms and guarantee as detailed in current catalogue. Open 9 to 5-30; Sat. until 1 p.m. Catalogue 6d. Trade list 5d. S.A.E. with all enquiries. **(LEEDS) LTD., MAUDE ST., (opp. Parish Ch. School) LEEDS, 2**

RADIO SUPPLY CO.

BEGINNERS!—YOU CAN BUILD THESE EASILY!


**YOU CAN BUILD THIS TINY
POCKET OR SHOULDER
RADIO FOR**



37/6!

(cigarette
shown for
size)

It's fun to build this "POCKETPAL" shoulder or pocket radio. So easy to build—it covers all the medium waveband with exceptional sensitivity and selectivity. Features a high efficiency pentode valve in well tested, powerful circuit. Personal phone ALI-DRY battery operation (batteries fit inside), slides over the shoulder—AERIAL IS INSIDE THE SLING LEAD!—or slips into pocket. Minisize 3" x 2" x 5". Built in about 90 minutes WITHOUT ANY EXPERIENCE, using our "STEP-AND-CHECK" INSTRUCTION MANUAL WHERE EVERYTHING YOU DO IS SPELLED OUT FOR YOU IN PICTURES SO YOU CAN'T GO WRONG! This "POCKETPAL" radio can be built for only 37/6, including Case, Valve, Manual, Nuts, etc. Post & Packing is 2/- (C.O.D. 2/-). PARTS SOLD SEPARATELY—shopping list, etc. 1/6. HEAVY DEMAND CERTAIN—DON'T PUT IT OFF—SEND NOW!

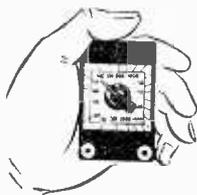

**BUILD
THIS
FOR
ONLY
35/-!**

It's fascinating to build this "fantabulous" "TOM-THUMB" transistor radio—only the size of a small cigarette packet, yet a marvel of clarity giving unexcelled transistor reception over all the medium-waves. Personal phone circuitry gives loud and clear tone. Can be built by absolute novice in 30 minutes providing endless listening pleasure the moment building is completed. Uses only one small 8d. penlight battery lasting months. Absolute beginners are assured of error-free building because of our SPECIAL INSTRUCTION MANUAL—WHERE EVERYTHING IS SPELLED OUT FOR YOU IN PICTURES—SO YOU CAN'T GO WRONG! It costs only 35/- to build the "TOM-THUMB" including Case, Transistors, Manual, Nuts, etc. Postage & packing amount to 2/- (C.O.D. 2/-). PARTS SOLD SEPARATELY—shopping list, etc. 1/6. EASY TO BUILD. THRILLING TO OWN—SEND AT ONCE!

**BUILD THIS
"MAINS"
"FRYING-
PAN"
RADIO
FOR ONLY
68/6!**



Build this "MAINS" "FRYING-PAN" SPECIAL, uses highly sensitive twin-triode valve circuit and normal size speaker. Covers all Medium and Long Waves giving amazing performance and tone. Costs only 1d. for about 75 hours' use. Excellent for KITCHEN, bedroom, garden hut, etc., etc. Robust design.

NO EXPERIENCE
NECESSARY
EVER REQUIRED
YOU CAN BUILD
IT!
MERLIN DESIGN
AND GET
PROFESSIONAL
RESULTS!
For A.C. Mains 200 to 250 Volts. LOADS OF FUN TO BUILD!—INSTRUCTIONS

ANYONE CAN FOLLOW. Can be built for 68/6d, including valve, speaker, step-by-step plans, etc. Postage and packing 3/- (C.O.D. 2/-). PARTS SOLD SEPARATELY—shopping list, etc. 1/6. WILL PAY FOR YOURSELF AGAIN AND AGAIN!—RUSH YOUR ORDER TODAY.

(NOTE: Complete range of components stock'd. regret no orders sent abroad, cheques gladly accepted. MAIL ORDER ONLY.)

MERLIN LABORATORIES (Dept. PW4), 167a PORTLAND ROAD, HOVE, SUSSEX

CABINETS AND EQUIPMENT



This popular Walnut Bureau Cabinet is veneered with the finest selected Walnut and beautifully polished. It is designed to accommodate any equipment with generous storage compartments.

Walnut £16-16-0
Natural Oak £18-18-0

This beautifully made cabinet is Oak veneered with Mahogany interior and is satin finished, also available in Walnut and Mahogany.

This cabinet can be fitted with any of the latest Hi-Fi units.

**CONTEMPORARY
£10-15-0**

We can supply and fit these or any cabinets with equipment. Fitting absolutely free.

- | | |
|--------------------------|----------|
| 5v. AM Chassis ... | £14. 5.0 |
| 5v. FM Tuner ... | £13.15.0 |
| 5v. Switch. FM. Tun. ... | £15.12.9 |
| 6v. AM/FM Chassis ... | £20.17.0 |
| 7v. AM/FM Chassis ... | £24. 6.6 |
| 8v. AM/FM Chassis ... | £23. 0.0 |
| 9v. AM/FM Chassis ... | £27. 6.0 |
| 10v. AM/FM Chassis ... | £37. 0.0 |

Send for comprehensive illustrated catalogue of cabinets, auto-changers, speakers, etc., all available on easy H.P. terms.

LEWIS RADIO

120 (P568), GREEN LANES, PALMERS GREEN, (Nr. Cock), LONDON, N.13. Tel. Bowes Park 1155/6.



Tape Decks

- | | |
|--------------------|----------|
| Motek K9 Tape Deck | 21 Gns. |
| Truvox Mk. IV Tape | 29 Gns. |
| Wearite Type C ... | £45. 0.0 |

Autochangers

- | | |
|--------------------|----------|
| B.S.R. Monarch ... | £8.15.0 |
| Latest Collaro ... | £9.19.6 |
| Garrard 120/4 ... | £12.17.2 |
| Garrard 88/4 ... | £17.18.8 |
| Garrard 98 4 ... | £19.17.0 |

Best Buy at Britain's

SANGAMO WESTON METER. 1 milliamp basic movement scaled 0-5, 0-100 volts. Brand New, recent manufacture. 3in. large. Clearly calibrated scale, complete with leads and prods. in canvas carrying case. Real Snip. 27/6. Post 1/6.

AMERICAN MULTIMETERS, by Precision, U.S.A. 400 microamps basic. A.C. and D.C. volts to 6,000 D.C., milliamps to 600. Ohms to 5 megs., 23 ranges in all. In polished wooden case, 7 1/2 x 5 1/2. Complete with leads, batteries and instructions. Tested and guaranteed. £9.10/6.

AVOMETERS.—31 range Universal meter, for A.C. and D.C. volts, A.C. and D.C. current and Ohms. Large easy-to-read 5 in. mirror scale. B.S.I. standard. Complete with batteries and guaranteed in first-class working order. £8/19/6. P. & P. 3/6.

MILLIARD GM4140 1 C. & R. BRIDGES.—2.1 Ohm to 10 Megohms in 4 ranges: 10 p.p.d. to 10 mF.d. in 3 ranges. For 50 c/s A.C. mains. In perfect working order. £7.10/- P. & P. 3/6.

WEE MEGGERS.—0 to 50 Megohms at 500 v. BRAND NEW in leather case. With leads and instructions. £12 10/- Ditto, but 100 v. £6 10/-

MINIATURE 373 LE STRIPS.—For F.M. tuner described in April and May P.W. Complete with 3 of EF91, 2 of EF92 and EF91. A fresh release enables us to offer these once again. BRAND NEW, with circuit, 42/6. OR less valves, 12/6. Post either, 2/6.

SPEAKERS.—3 Ohms, 6 1/2 in. diam. in grey wicker styled cabinet. 4 1/2 x 5 1/2 in. Complete with volume control and transformer for 600 Ohms line. Brand new. 27/6. P. & P. 3/6.

VIBRATOR PACK.—Input 6 v. D.C. Output approx. 100 v. at 30 m Amps. D.C. Fully smoothed and R.F. filtered. Size 6 1/2 x 5 1/2 in. Fitted with Mallory 623C vibrator. BRAND NEW. 12/6.

VIBRATOR PACK.—Input 6 v. D.C. Output 230 v. D.C. 100 m Amps Fully smoothed and R.F. filtered. Size 9 1/2 x 5 1/2 in. Complete with OZ4 and vibrator. Brand new. 25/-

MAINS ISOLATING TRANSFORMERS (Vortexion).—For testing A.C. D.C. sets in safety. 230 v. input, output 230 v. 100 watts. 22/6. P. & P. 2/6.

MAINS TRANSFORMERS.—Input 200-250 v. A.C. Outputs 275-0.275 v. 100 m Amps; 6.3 v. 7 Amps; 5 v. 3 Amps. (Covt. rating.) 4 x 4 1/2 x 4 in. high. Upright m.k. Brand new. 25/- P. & P. 2/6.

R.C.A. OUTPUT TRANSFORMERS.—Frt. push-pull 6L8's. Secs. 600 Ohms tapped at 15, 7.5 and 3 Ohms. Tertiary winding for NFB. Handles 2 Watts. Potted. Circuit of R.C.A. amplifiers supplied FREE. Brand new. 27/6.

AVOMINOR LEATHER CASES.—Brand new, with strap. 7/6.

PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS

CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martin's Lane, London, W.C.2

TEMPLE Bar 0545

Shop hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday

SPECIAL OFFER!!!

**SMALL
TYPE
ONLY**

EY51 10/6

**BRITISH
MADE**

EXPRESS SERVICE !!!
C.O.D. ORDERS RECEIVED BY 3.30 P.M., EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON. ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY.

FOR ONLY 6d. EXTRA PER ORDER WE WILL INSURE YOUR VALVES AGAINST DAMAGE IN TRANSIT. ALL UNINSURED PARCELS AT CUSTOMER'S RISK.

1A3	3/- 6AU6	10/6 6L18	13/- 12AH8	10/6 35/51	12/6 D42	10/6 ECC84	10/- FW4/800	PCF82	12/6	1UBC41	8/6				
1A5	6/- 6B4G	6/6 6N7	8/- 12AT6	10/6 35A5	11/- D63	5/- ECC85	9/6	12/6 PCL82	12/6	1UBF80	9/6				
1A7	15/- 6B7	10/6 6Q7G	10/- 12AT7	8/- 35L6GT	10/- D77	6/6 ECC91	5/6 GZ30	10/6 PCL83	17/6	1UBF89	10/6				
1D6	10/6 6B8G	4/6 6Q7GT	11/- 12AU7	7/6 35W4	8/6 DAC32	11/- ECF87	13/6 GZ32	12/6 PEN40DD		1UCC85	10/6				
1H5	11/- 6B8M	5/- 6R7G	10/- 12AX7	9/- 35Z3	10/6 DAF91	8/- ECF82	13/6 GZ34	14/-	25/-	1UCH42	11/6				
1L4	6/6 6BA6	7/6 6S7GT	8/- 12BA6	9/- 35Z4GT	10/6 DAF96	10/- ECH35	9/6 H30	5/-	PEN45	19/6	1UCH81	11/6			
1LD5	5/- 6BE6	7/6 6S7	10/6 12BE6	10/- 35Z5GT	9/- DAF33	11/- ECH42	11/- H63	12/6	PEN46	7/6	1UCL82	15/6			
1LN5	5/- 6B16	8/- 6S7GT	8/- 12E1	39/- 41MTL	8/- DF91	7/- ECH81	9/- HABC83		PL82	10/6	1UF41	9/-			
1N5	11/- 6BR7	11/6 6SH7	8/- 12J5GT	4/6 50C5	12/6 DF96	10/- ECL80	14/-		PL83	11/6	1UF80	10/6			
1R5	8/6 6BW6	9/6 6S17	8/- 12J7GT	10/6 50L6GT	10/6 DH63	10/- ECL82	14/- HK90	10/6	PM12	12/6	1UF85	10/6			
1S5	8/- 6BW7	8/- 6SK7GT	8/- 12K7GT	7/6 72	4/6 DH76	7/6 EF36	6/- HL23	10/6	PM12	6/6	1UF89	10/6			
1T4	7/- 6BX6	8/- 6SL7GT	8/- 12K8GT		7/6	8/- DH77	8/6 EF37A	8/-	HL41	12/6	1PM12M	6/6			
1U5	10/- 6C4	7/- 6SN7GT	7/6	14/- 78	8/6 DK32	15/- EF39	6/- HL133DD		PY80	9/-	1UL46	15/6			
2A7	10/6 6C5	6/6 6S57	8/- 12Q7GT	7/6 80	9/- DK91	8/6 EF40	15/-	12/6	PY81	9/-	1UL84	11/6			
2C26	4/- 6C6	6/6 6U4GT	14/- 12SA7	8/6 83V	12/6 DK92	12/6 EF41	9/6 HVR2	20/-	PY82	9/-	1UY41	8/6			
2D13C	7/6 6C8	12/6 6U5G	7/6 12SC7	8/6 85A2	15/- DK96	10/- EF42	12/6 HVR2A	6/-	PY83	9/6	1UY85	10/6			
2X2	4/6 6C9	12/6 6U7G	8/6 12SG7	8/6 150B2	15/- DL2	15/- EF50(A)	7/- KF35	8/6	QP21	7/-	1V1507	5/6			
3A4	7/- 6C10	12/6 6V6G	7/- 12SH7	8/6 220P	10/6 DL33	9/6 EF50(E)	5/- KL35	8/6	QP25	15/-	1VLS492A	£3			
3A5	12/6 6CH6	12/6 6V6GT	8/- 12S17	8/6 807	7/6 DL66	15/- EF54	5/- KT2	5/-	QS150/15		1VMP4G	15/-			
3B7	12/6 6D5	6/6 6X4	7/- 12SK7	8/6 956	3/- DL92	8/- EF73	10/6	KT33C	10/-		1VP217	12/6			
3D6	5/- 6E5	12/6 6X5GT	6/6 12SQ7	8/6 1203	7/- DL94	9/- EF80	8/-	KT44	15/-	1VQO4/7	15/-	1VP417	15/6		
3Q4	9/- 6F6G	7/- 6Z4/84	12/6 12SR7	8/6 4033L	12/6 DL96	10/- EF85	8/-	KT63	7/-	1R12	12/6	1VP13C	7/6		
3Q5GT	9/6 6F6GT	8/- 6Z5	12/6 12Y4	10/6 5763	12/6 DLS10	10/6 EF86	17/6	KTW61	8/-	SD6	12/6	1VP41	7/6		
3S4	8/- 6F8	12/6 6/30L2	12/6 14R7	10/6 7193	5/- DM70	8/6 EF89	10/-	KTW62	8/-	SP4(7)	15/-	1VR105/30			
3V4	9/- 6F12	7/6 7A7	12/6 14S7	17/- 7475	7/6 EA50	2/- EF91	7/6	KTW63	8/-	SP41	3/6		9/-		
5U4	8/6 6F13	13/- 7B7	8/6 19AQS	11/- 9002	5/6 EA76	9/6 EF92	6/6	KTZ41	8/-	SP42	12/6	1VR150/30			
5V4	12/6 6F16	9/6 7C5	8/- 19H1	10/- 9003	5/6 EABC80	9/-	EL32	5/6	KTZ63	10/6	SP61	3/6	9/-		
5X4	12/6 6F17	12/6 7C6	8/- 20D1	16/- 9006	6/- EAC91	7/6	EL41	11/-	L63	6/-	SU61	10/6	VT61A	5/-	
5Y3G	8/- 6F32	10/6 7H7	8/- 25L6GT	10/- AC6PEN	7/6 EAF42	10/6	EL42	11/6	LN152	14/6	TP22	15/-	VT501	5/-	
5Y3GT	8/6 6F33	7/6 7Q7	9/- 25Y5	10/6 AC/HL/	EB34	2/6	EL81	15/-	LZ319	10/-	U16	12/6	W76	7/6	
5Y4	12/6 6G6	6/6 7S7	10/6 25Y5G	10/- DDD	15/-	EB41	8/6	EL84	10/6	MH4	7/-	U18/20	12/6	W81	6/6
5Z3	12/6 6H6G	3/- 7V7	8/6 25Z5	10/6 AC/P4	8/-	EB91	6/6	EL91	5/-	MHL4	7/6	U22	8/-	X61	12/6
5Z4G	10/6 6H6M	3/6 7Y4	8/- 25Z4G	10/- AC/VP1	15/-	EBC33	7/6	EM34	10/-	MHL6	12/6	U31	10/-	X63	10/6
5Z4GT	12/6 6J5G	5/- 8D2	3/6 25Z6G	10/- AL60	10/-	EBC41	10/-	EMB0	10/6	M4	12/6	U43	10/6	X65	12/6
6A8	10/- 6J5GTG	5/6 8D3	7/6 28D7	7/- AP4	7/6	EBF80	10/-	EMB1	10/6	ML6	6/6	U45	10/6	X66	12/6
6AB7	8/- 6J5GTM	6/- 9D2	4/- 30	7/6 ATP4	5/-	EBF89	9/6	EY51		MU14	10/6	U50	5/-	XD(1.5)	6/6
6AB8	14/- 6J6	5/6 10C1	15/- 30C1	10/- AZ31	12/6	EC52	5/6	(Small)	10/6	OA10	12/6	U52	8/6	XFW10	6/6
6AC7	6/6 6J7G	6/- 10F1	19/6 30F5	8/- BL63	7/6	EC54	6/-	EY51		OA70	5/-	U76	7/6	XFY12	6/6
6AG5	6/6 6J7GT	10/6 10F9	11/6 30FL1	12/6 CK505	6/6	EC70	12/6	(Large)	12/6	OA71	5/-	U78	7/6	XF(1.5)	6/6
6AJ8	9/- 6K6GT	8/- 10F18	12/6 30L1	9/- CK506	6/6	ECC31	15/-	EY86	17/6	OC72	30/-	U107	11/10	XSG(1.5)	6/6
6AK5	8/- 6K7G	5/- 10LD3	3/6 30P12	13/6 CK523	6/6	ECC32	10/6	EZ35	6/6	P61	3/6	U251	15/-	Y63	7/6
6AL5	6/6 6K7GT	5/- 10LD11	16/9 30P16	10/- CV63	10/6	ECC33	8/6	EZ36	6/6	P15	10/6	U404	10/6	Z63	10/6
6AM5	5/- 6K8G	8/- 10P13	17/6 30PL1	19/6 CV85	12/6	ECC35	8/6	EZ43	8/-	PABC80	15/-	UABC80		Z66	20/6
6AM6	7/6 6K8GT/G	11/6 11E3	15/- 31	7/6 CV271	10/6	ECC38	8/-	EZ41	10/6	PCC84	9/-			Z77	7/6
6AQ5	8/6	11/- 12A6	6/6 33A/158M	CV428	30/-	ECC82	7/6	EZ80	9/6	PCC85	12/6	UAF42	10/6	Z719	8/-
6AT6	8/6 6L6G	9/6 12AH7	8/-	30/- DI	3/-	ECC83	9/-	EZ81	10/-	PCF80	10/-	UB41	12/7	Z729	17/6

TERMS OF BUSINESS :—CASH WITH ORDER OR C.O.D. ONLY. POST/PACKING CHARGES 6d. PER VALVE ; ORDERS VALUE £3 OR MORE POST FREE. MINIMUM C.O.D. FEE AND POSTAGE 3/-. EACH ADDITIONAL VALVE 6d. EXTRA. WE ARE OPEN FOR PERSONAL SHOPPERS MON.-FRI. 8.30-5.30. SATS. 8.30-1 P.M.

ALL VALVES, NEW, BOXED, TAX PAID, AND SUBJECT TO MAKERS' GUARANTEE. FIRST GRADE GOODS ONLY, NO SECONDS OR REJECTS. GOODS ARE ONLY SOLD SUBJECT TO OUR TERMS OF BUSINESS, OBTAINABLE FREE ON REQUEST. CATALOGUE OF OVER 1,000 DIFFERENT VALVES 3d.

METAL RECTIFIERS FOR RADIO AND TELEVISION. H1VAC MINIATURE AND SUBMINIATURE VALVES. We stock the full range of each of the above items. Full technical details and prices FREE on receipt of S.A.E.

BENTLEY ACUSTIC CORPORATION LTD.


THE VALVE SPECIALISTS

38 CHALCOT ROAD, LONDON, N.W.1

Primrose 9090

PLEASE ENQUIRE FOR ANY VALVE NOT LISTED. 3d. STAMP, PLEASE.


**Now Two Models
Turret Tuner**

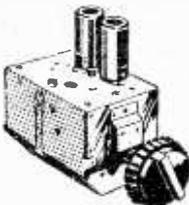

Brand new stock, not surplus, with coils for Band I and III, complete with valves. Model I I.F. output 33 mc/s. Series heaters. Model II, I.F. output 16-19 mc/s. Parallel heaters with circuit diagram, 7/9/6.

With knobs 3/6 extra, post and ins. 2/6.

14in. T.V. Cabinet

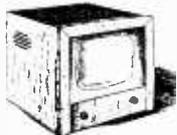


14in. T.V. cabinet of the latest styling — beautifully veneered and polished — limited quantity.

City-sale price 19/6 ea. Carr. and packing 3/6 extra. Masks 10/- extra.

Transistor Timer

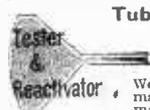All the parts for making transistorised Enlarging or Process Timer with constructional details. £2/10/-, plus 2/6 post and pkg.



Tube Tester and Re-Activator

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will re-activate them. Supplied complete with full instructions. Price £3, plus 2/6 post and ins.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0.5, 0.50, 0.100, 0.500, 1.000, A.C. volts 0.5, 0.50, 1.00, 0.500, 0.1.000. D.C. milliamps 0.5, 0.100, 0.500. Ohms 0.50,000 with internal batteries. 0.500,000 with external batteries. Measures A.C. D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price 19/6, plus 2/6 post and insurance.




Xaxley Switches

3-pole, 2-way	1/3
12-pole, 2-way	1/6
3-pole, 3-way	1/6
9-pole, 3-way	2/-
2-pole, 4-way	2/-
6-pole, 4-way	2/6
4-pole, 5-way	2/6
2-pole, 6-way	2/6
1-pole, 7-way	2/6
1-pole, 12-way	2/6
6-position shorting switch	2/-
Double-pole mains switch for attaching to Xaxley switches	1/6

Discount of 10%, allowed where a dozen of one type ordered. Special quotes 144 or over.

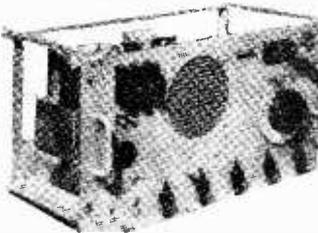**Short Wave Communications Receiver
R.208.**



This is a superb short wave receiver covering 5.30 to 30 metres (10 to 60 mc/s). Uses 6 valves. Has R.F. stage, 2 I.F. stages B.F.O., etc. Multi-head instrument driven by

two internal power packs, mains and battery vibrator pack. Complete with own P.M. speaker. Provision for phones and speaker muting. Complete in metal transit case; size approx. 24 x 18 x 12ins.; weight 70lb. Suitable A.C. mains 100-250 and 6 volt battery. In perfect condition, practically unused. Tested before despatch and guaranteed. Handbook free with each. Price £6.19.6. carriage and insurance 15/- or 10/- (plus 15/- carriage and insurance) deposit and 14 weekly payments of 10/-.

Geiger Counter

As described in "Practical Wireless" April issue. All the parts including the 20th Century tube type G24 and other specified valves and components but not the chassis or case. £5.7.6. plus 3/6 post and ins.


T.V. Pattern Generator

All the parts for the unit described in the April issue of "Practical Television," including valves and other parts but not the chassis or case. 45/-, plus 3/6 post and ins.

Response Curve Generator

All the parts to make the unit described in the April issue of "Practical Television," including valves and other parts but not the chassis or case. 5/-, plus 2/6 post and ins.

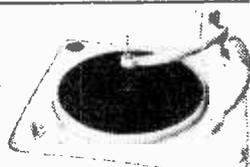**Yours for 10/-
down and 17
weekly pay-
ments of 10/- or
cash price
£8.10.0**



The latest, most up-to-date Record Player made by the famous B.S.R. company. Using Hi-Fi Crystal Pick Up and fitted with every modern device. Definitely a record changer which will give years of trouble-free music. Not surplus but the current model, price £8.10/- or 10/- deposit and 17 weekly payments of 10/-, carriage and insurance 5/-.

PUBLIC ADDRESS SNIP


Parmeko 12 watt output transformer, primary 4,000 ohms centre tapped, secondary 100 ohms (three suitable for 6-15 ohm speakers wired in series). Really massive transformer, weighs approx. 8 lb. Offered at a ridiculously low price of 17/6, plus 3/6 carriage and ins.

**The "GRISPIAN"
Portable Radio**



A 4-valve fully portable battery set with very many good features as follows: Ferrite rod aerials, low consumption valves, superhet circuit with A.V.C. ready-built and aligned chassis if required, beautiful two tone cabinet covered with I.C.I. rexine and Tygan. Guaranteed results on long and medium waves anywhere. All parts, including speaker and cabinet are available separately or if all ordered together the price is £7.15/- complete, or £6.8/9 with 8/6 U11 and £6.8/8 with 8/6 U74 9/6.

T.V. Service Sheets

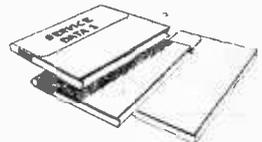

100 sheets covering the most popular post-war Televisions by leading makers—Cosor, Ekco, Ferguson, Eye, etc., etc. Give circuit diagram component values, I.F. frequencies etc., £1 post free.

Fluorescent Lights




These are complete fluorescent lighting fittings. Built-in ballast and starters—stove enamelled white and ready to work. Ideal for the kitchen over the work-bench and in similar locations. Single 40, 4ft. 3in. long, uses a 40-watt tube. Twin 20. Uses 2 20-watt standard tubes. Price for either type 39/6, with tubes. Carriage and ins., up to 150 miles 5/6, up to 250 miles 7/6.

Beginner's Superhet



All the components including metal chassis, valves, metal rectifier, coils, tuning condenser, etc., etc., required to build the "Beginner's Superhet" as described in the January issue, are available as a parcel. Price £3, plus 3/- post and ins.

Band III Converter

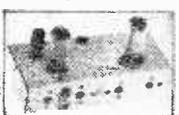

Available Wales, London, Midlands, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers, and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately 1/6.

Ex-Government Valves

Many types in stock. Here are some of the more popular ones:


1LD5	3/6	6N7	7/8	1625	10/6
1T4	7/6	6Q7	9/6	DDT4	8/6
2X2	4/9	6SA1	3/-	DDT13	9/6
3A4	7/-	6SJ7	9/6	DH79	9/6
5U4	8/-	6SK7	6/-	DL74	9/6
5Z4	9/6	6SL7	8/-	EF50	5/6
6AC7	6/6	6X6	9/6	EF80	8/6
6B8	4/-	7AT	9/6	EL50	10/6
6C4	6/6	7X7	9/6	H63	6/6
6C6	6/6	7Y4	8/6	HL4G	6/6
6D6	6/6	12SK7	6/-	HL13	9/6
6P6	7/6	25Y5	10/-	HL1320	9/6
6P8	9/6	25Z4	9/6	KT72	9/6
6GG6	6/6	25Z6	10/6	KTW61	4/6
6H6	2/6	41	9/6	KTW73	9/6
6J5	5/-	42	8/-	KTZ41	9/6
6J7	6/-	43	10/-	HL1320	9/6
6K6	7/-	73	12/6	PEN426	10/6
6K7	7/6	77	8/6	U12	8/6
6K8	9/6	78	8/6	U71	9/6
6L6	9/-	84	8/6	U74	9/6
		954	3/6		



CLOCK CASE


Also suitable for barometer or other instrument. Nicely polished. Price 4/6, post and packing 1/6.

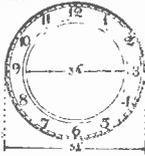Clock numerals to suit these cases etched on metal, 2/6.



Post and ins. if ordered separately.

F.M. Tuner

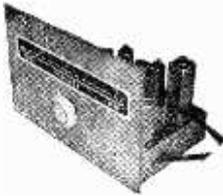

This is a high fidelity unit which although moderately priced has a performance equal to the highest priced. Its stability is very good and extremely good results have been received with the simplest of aerials as far away as Eastbourne. The unit is made up ready to work and has its own power supply for A.C. mains. Demonstration at all our branches. Price 12 gns. or 10/- down and 26 weekly payments of 10/- Post plus insurance 5/-.

You can build our TV in one evening

There are only 24 solder joints to make—suitable 14in. or 17in. tube, cost £20 10/-. We will gladly send full constructional details, and circuit diagram on receipt of 3/- which will be credited in full if you buy the kit.

Mains-Mini




Uses high-efficiency coils, covering long and medium wave bands and fits into the neat white or brown bakelite cabinet—limited quantity only. All the parts, including cabinet, valves, in fact, everything, £4 10/0, plus 3/6 post. Constructional data, free with the parts, or available separately 1/6.

500 Microamp Flush Mounting Moving Coil Meter 2in.

Brand New EX-Ministry, 17/6, plus 1/6 post and insurance.


Simplex Transistor Kit

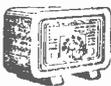Makes ideal bedroom radio, uses one transistor and one crystal diode. Complete less case 19/6, case 5/- extra, post and ins. 1/6.



Coil Pack Snip

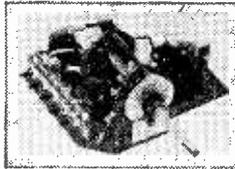
Covers the Medium Waveband 200-550 metres and two short wavebands 35-120 metres, and 13-42 metres, for 465 kc/s I.F. Extremely well made, supplied complete with diagram of connections, only 9/8, plus 1/6 post and insurance.



Power Transformer


100 v. 3-phase to 230 v. single-phase, 10 kVA oil filled, original cost probably around £100. In perfect working order, £25 each, ex. Eastbourne. Ditto, but smaller and not oil filled, 3 kVA., £12.

This Month's Snip

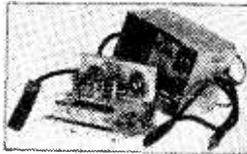

Breakdown unit contains: miniature relay, push-pull input transformer, push-pull output transformer, valveholders, condensers, resistors, useful bakelite enclosed hand switch which can also be used as foot switch.

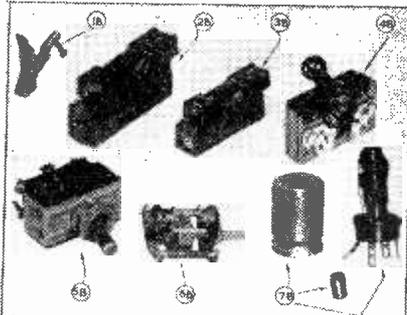
If mounted on base, all in really useful aluminium case with easily removable lid. Size approx. 5 1/2 in. x 4 1/2 in. x 3 1/2 in. Case is ideal for building Pattern Generator or similar instrument. Special snip price this month 5/6, plus 1/6 post and insurance.



- 1b. Crocodile clip for metering, etc. Has sharp point for piercing insulation without spoiling it. 8d. each or 7/- per dozen.
- 2b. 15 amp slydlok panel mounting fuse and fuse carrier. 2/6.
- 3b. 5 amp slydlok panel mounting base and fuse carrier. 2/-.
- 4b. Double pole 15 amp toggle switch, ex. equipment but unused. 1/8.
- 5b. 5 amp double pole change-over toggle switch (DP DT), ex. equipment but unused. 2/6.
- 6b. Air spaced trimmer 30 pF long 1/2 in. spindle. 2/3 each or 24/- per dozen.
- 7b. 1/2 in. coil former with dust core and can. 4/6 per dozen sets.

Super Sensitive (2,000 O.P.V.) Multimeter Kit

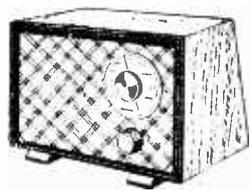17 ranges including D.C. volts to 1,000 volts, A.C. to 1,000 volts, D.C. millamps to 500, ohms to 2 meg., capacity and inductance. All the essential parts including metal case, selected resistors, wire for shunts, selected switches, calibrated scale and instructions, 32/6, plus 2/6 post and insurance.



The Skysearcher

This is a 2-valve plus-metal receiver set useful as an educational set for beginners, also makes a fine second set for the bedroom, workshop, etc. All parts, less cabinet, chassis and speaker, 19/6. Post and ins., 2/6. Data free with parts or available separately 1/6. 3-valve battery version also available at the same price.

All-Mains Amplifier



Powerful three-valve Mains amplifier ideal for dances, parties, etc. Complete less chassis, cabinet and speaker (available if required)—data 1/6 (free with parts). Price 19/6, plus 2/6 post and insurance.

Complete Walkie-Talkie for £1



This 38 Walkie-Talkie Radio Transmitter has a range of approx. 5 miles, just right for search parties, fire brigades, etc. Operates on dry batteries. Complete with five valves and in metal case. Size approx. 6" x 6" x 3 1/2". Unused but not tested or guaranteed. £1 only, plus 2/6 post and insurance.

Variable Rheostat



This is a heavy duty slider resistor rated at 25 amps, but easily capable of twice this load. Basic resistance is 4 ohms, but by the removal of one wire this becomes 3 ohms, alternatively it can be rewired to suit individual requirements. Adjustment is by rotating a bakelite knob which couples to a heavy duty slider, ideal for dimmer circuit. Price 8/3, post and insurance 3/6.

ELECTRONIC PRECISION EQUIPMENT, LTD

Post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66, Grove Road, Eastbourne, marked Department 7.

42-46, Windmill Hill, East-India, Middlesex. 68, Grove Road, Eastbourne, Sussex. 29, Stroud Green Rd., 266, London Road, Finsbury Park, N.4. Croymed. Phone: RUSLAP 5780. Half day, Saturday. Half day, Thursday. Half day, Wednesday. Phone: ARChway 1049. Phone: CRO 6538. Half day, Wednesday.

MAXI-Q
REGD.

COIL PACKS

CP.3 370pF and CP.3 500pF. These 3 waveband Coil Packs are available for use with either 370pF or 500pF tuning condensers. The coverages are : Long Wave 800-2,000 metres, Med. Wave 200-550 metres, Short Wave 16-50 metres. Designed for use with " MAXI-Q " glass scale type S2. Retail price of each unit : 32 - plus 12 9 P.T.—total 44 9.

CP.3 G. As above but with Gram position, suitable for use with 500pF tuning condenser : 39/- plus 15 7 P.T.—total 54 7.

CP.3 F. This Coil Pack is for use with a 500pF tuning condenser and covers the standard Long, Med. and Short wavebands with the addition of the band 50/160 metres. This covers the Trawler band, Aeronautical and the 80 and 160 metre Amateur bands : 49,- plus 19 7 P.T.—total 68 7.


CP.3F,G. As CP.3 F but with Gram position : 57,- plus 22 9 P.T.—total 79 9.

CP.4 L and CP.4 M. These compact 4-station Coil Packs are available for either 1 Long Wave and 3 Medium Wave stations (CP.4 L) or 4 Medium Wave stations (CP.4 M). They are fully wired and require only four connections for use with any standard frequency changer valve : 25/- plus 10/- P.T.—total 35 -.

CP.4 L G and CP.4 M G. As CP.4 L and CP.4 M but with provision for Gram position : 31,- plus 12 5 P.T.—total 43 5.

See Technical Bulletin DTB.9 for details of all Coil Packs, 1 6

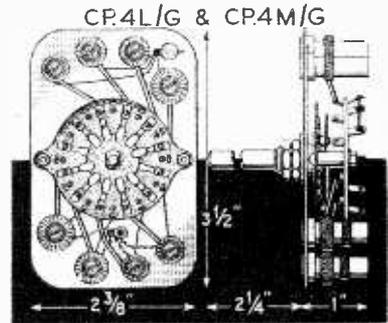GENERAL CATALOGUE covering technical information on full range of components 1/- post free.



DENCO (CLACTON) LTD. (Dept. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex

STOP PRESS.—TREBLE LIFT INDUCTOR FOR THE MULLARD TYPE " C " TAPE AMPLIFIER. Wound in ferroxcube pot core assembly. Price : 22 6 each.

Trading Terms for direct postal orders. C.W.O. plus appropriate postal charges. Please send S.A.E. with all enquiries.

EXCLUSIVE OFFER—

low voltage, halogen quenched

GEIGER—MUELLER TUBES at 55/- each.

A large contract purchase from famous manufacturer enables us to make an exclusive offer of these highly sensitive gamma counters. Straight from production, individually tested and fully guaranteed.

SPECIFICATION

- Effective length : 11.8 cm. Standard British 4-pin base.
- Background count : 90/min.
- Plateau : Minimum length 80 V. Slope 5% per 100 V.
- Working potential : 400-450 V.
- Current : 0.001 μ A to 1 μ A at 100 to 6,000 c/min.
- Response : exceeds 30,000 c/m.
- Dead time : 100 μ sec. at 6,000 c/m. Rise time : 5 to 10 μ sec. at 6,000 c/m.
- Temperature range : - 55 C. to + 60 C.
- Gamma efficiency : 1%.
- Stainless iron electrode.

COME TO PROOPS' for special component bargains such as transformers, rectifiers, relays, solenoids and valves and an endless variety of surplus equipment at keenest prices.

PROOPS Dept. P,
52 Tottenham Court Road, W.1.

BROS. LTD.

LANGHAM 0141

Hours :
9 to 6. Thursdays, 9 to 1 p.m.
Open all day Saturday.

EXPRESS ELECTRONICS

ROSEDENE LABORATORIES
KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW, TESTED AND GUARANTEED

1AC6	8/6	6BW6	7/6	12K7GT	8/-	E8B1	6/9	KT33C	9 6
1C1	7/6	6BW7	8/-	12KBGT12/6	E8C41	10/-	N17	7 6	
1C2	8/6	6CH5	7/-	12Q7GT	8/-	E8F80	9/6	N18	7 6
1C3	9/-	6C10	9/-	16A5	9/-	ECC35	7/6	N19	7/6
1F1	8/6	6D1	1/6	25L6GT	8/6	ECC81	8/6	PCC84	9/-
1F3	7/6	6D2	6/9	25Z4G	8/6	ECC82	7/6	PCF80	10/6
1FD1	8/6	6F12	6/-	35L6GT	9/-	ECC83	8/6	PCF82	10 6
1FD3	7/6	6F15	9/-	35W4	8/5	ECC84	10/6	PL82	9/-
1P1	9/-	6J5G	5/6	35Z4GT	8/-	ECC85	10/6	PY81	8 6
1P10	7/6	6J5GT	6/6	5763	13/6	ECF82	10/6	PZ30	17/6
1P11	7/6	6K7G	5/6	D77	6/9	ECH42	10/-	U52	8 -
1R5	7/6	6KR8T	9/6	DAF91	7/6	ECH81	8/-	U76	8 -
1T4	7/6	6L6G	10/6	DAF96	9 -	EFF37A	9/-	U78	7 -
1S5	7/6	6Q7GT	8/6	DF91	7/6	EFC39	5/-	UBC41	8/6
1U5	7/-	6SL7GT	7/6	DF96	8/6	EF41	9/-	UCH42	10/-
3Q4	7/6	6SN7GT	8/-	DH76	8/-	EF80	8/6	UF41	8 6
3S4	7/6	6V6G	7/6	DH77	7/6	EF91	6/-	UL41	10 -
3V4	7/6	6V6GT	7/6	DH142	8/6	EF92	5/6	UY41	7 6
5U4G	8/6	6X4	7/-	DH150	10/-	EL37	19/6	VW6	8 -
5Z4G	9/6	6X5GT	7/6	DK91	7/6	EL38	20/-	W142	8 6
6AL5	6/9	8D3	6/-	DK92	8/6	EL41	10/-	X17	7 6
6AM6	6/-	12AH9	10/6	DK95	9/-	EY51	12/6	X18	8 6
6AT6	7/6	12AT6	8/6	DL92	7/6	EZ35	7/6	X142	8 6
6BA6	7/6	12AT7	8/6	DL96	9/-	EZ40	8/-	X150	10 -
6BE6	8/-	12AU7	7/6	EAS0	1/6	EZ80	8/-	Z77	6 -
6BR7	10/6	12AX7	8/-	FABC80	8/6	EZ81	8/-	ZD17	7 6

MATCHED PAIRS

EL84 23/-, 6V6G and GT 17/-, 6BW6 13/- per pair.
Push Pull O.P. Transformers for above 3-15 ohm 14/6.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94	27/6
1R5, 1T4, 1S5, 3S4 or 3V4	27/6
6K8, 6K7, 6Q7, 6V6, 5Z4G	35/-
12K8, 12K7, 12Q7, 35L6, 35Z4	35/-

Postage and packing, 6d. Over £1 post free. C.O.D. 2/3

PREMIER RADIO COMPANY

Tel.: AMBassador 4033

B. H. MORRIS & CO. (RADIO) LTD.

Tel.: MUS. 3451

207 EDGWARE RD., LONDON, W.2 & 23 TOTTENHAM COURT RD., LONDON, W.1



The "Petite" PORTABLE

A completely new design with the all star features from the firm with 45 years of experience in the supply of designs for the home constructor.

MAY BE BUILT FOR

£7.7.0

Plus p. & p. 3/-

Batteries Extra. I.L.T. 10' (Type B126) or equivalent. L.T. 1/6 (Type AD35) or equivalent.


★ Size only 8in. x 8in. x 4 1/2in. ★ Instruction Book 1.5.

The New De-Luxe TAPE RECORDER TR3

for £6. 5. 0. DEPOSIT & 8 MONTHLY PAYMENTS OF £5.17.11 OR CASH 45 GNS.

Plus 21/- post & pkg.

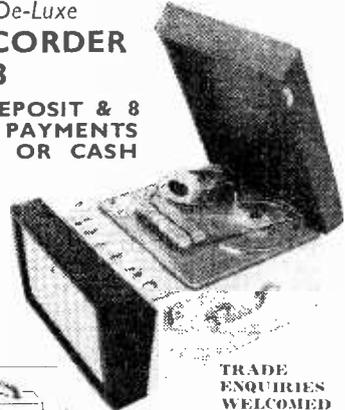Case finished in Red and Cream with gilt styling and fittings. Size 18 1/2 in. x 15 1/2 in. x 9 in. for A.C. Mains 200/250 v. 50 cycles.



TRADE ENQUIRIES WELCOMED

Build this New TAPE RECORDER KIT

for only

£38.15.0




This Kit comprises:

- 2-speed lane Mk. VI Deck..... £18 10-
 - Premier Tape Amplifier complete with separate plug-in-type power pack £14 --
 - 7 x 4 Elliptical Speaker £11 1/6
 - De-luxe Cabinet with gilt fittings and detachable lid £4 19/6
 - Reel of Scotch Boy 1.200ft. Tape and empty Spool £1 11/6
 - Latest Type ASCOS microphone £2 15-
- All the above sections can be purchased separately.

BUILD THE 1-VALVE BATTERY RECEIVER

As shown on B.B.C. T.V. This receiver contains a DAF96 valve and a pair of 4,000 ohm headphones, and is powered by a combined 6V and 1.5 volt battery. Price complete with headphones but less battery 45-. Send for free diagram.

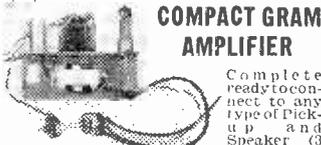2-VOLT 16 AD bakelite-cased ACCUMULATOR by Oldham. Dagenite, Exide. New and unused, unspillable. 7 1/4 x 4 x 2. Price 6 6, plus 1/6 p. & p.



COMPACT GRAM AMPLIFIER

Complete ready-to-connect to any type of Pick up and Speaker (3 ohms). A.C. Mains 200

250 v. Volume and tone control on 4-extended leads. 1 valve. Overall size 7 1/2 long x 6 1/2 wide x 3 1/2 high.

Plus packing and postage 2 6.

£2.19.6

PREMIER BATTERY ELIMINATOR, housed in two containers which are exactly the same size as AD35 and B126 Batteries. Kit 37/6 plus 2/- p. & p.



PUT IT TOGETHER YOURSELF

AND SAVE POUNDS

TOTAL COST ONLY

£9.19.6

Plus 5/- packing & postage.

Each Unit may be purchased separately as follows:—

- Amplifier Cabinet in maroon and fawn (size 13 1/2 x 11 x 6 1/2 in.)..... £2/10-
 - 1 Valve Amplifier £3/19/6
 - 7 x 4 in. Elliptical Speaker £1/1/6
 - B.S.R. TUB Turntable and Pickup £3/19/6
- This can also be supplied complete with the Latest Collaro 4-speed Junior Turntable and Pickup for only £4 12/6 plus 5/- packing and postage.
- If any of the individual items are purchased kindly add the postage as follows: Cabinet 3/-, Amplifier and Speaker 3/-, Turntable 2/6.

3-Band Superhet Receiver may be built for £7 19/3 plus pkg. & carr 3/-

4-WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** Plus 2/6 Pkg. & Carr.

Instruction Book 1/- post free. A steel case is now available, complete with engraved panel, for 15/6 extra. The amplifier may be supplied complete for £5.5.0 plus pkg. and post 3/6, or fitted in case at £6 plus pkg. and post 3/6.

8 WATT AMPLIFIER

This design includes 5 miniature valves of the latest types, an ultralinear output transformer suitable for Speakers of 3 and 15 ohms and a very attractive Perspex front panel with gold lettering, complete set of parts.

Postage & packing **£8.8.0**
5/- extra.
or £10.19.3 built and tested. Send 1/6 for Booklet.

Why not make the best!

MULLARD AMPLIFIER KIT

Now supplied with ultralinear output transformer.

All the components for Model 510, plus pre-amplifier, on one chassis (total six valves), chassis gold hammer finished. May be purchased for £12.12.0 plus pkg. and post 7 6. This version complete and tested £15.15.0. Or pre-amplifier and tone control in a separate unit £14.14.0, plus pkg. and post 7 6.

SPECIAL REDUCTION 2-BAND T.R.F. RECEIVER

MAY BE BUILT FOR **£5.10.0** Plus 3/- Pk. & Post.

These two receivers use the latest type circuitry and are fitted into attractive cabinets 12 1/2 in. x 8 1/2 in. x 5 1/2 in. in either walnut or ivory bakelite or wood. Individual instruction books 1/- each. Post free.

ADDRESS ALL MAIL ORDER ENQUIRIES TO: (Dept. P.W.) 207 EDGWARE RD., LONDON, W.2

Stern's "fidelity" TAPE RECORDERS



THEY INCORPORATE . . .
 ● Choice of the latest COLLARO or TRUVOX Tape Decks
 ● The Model HF TR2 "fidelity" AMPLIFIER
 ● ROLA CELESTON 10 x 6in. P.M. Speaker
 ● 1,200ft. reel EMI Tape
 ● ACOS Crystal Microphone

(Plus £1.10.0 carriage & insurance of which £1 is refunded on return of Packing Case.)

THIS POPULAR RECORDER IS OFFERED INCORPORATING EITHER . . .

★ The Latest COLLARO TRANSCRIPTOR DECK or
 ★ THE NEW TRUVOX MK IV DECK

- You WON'T BUY better value
- Truly "Hi-Fi" RECORDINGS are obtainable
- Call in and HEAR THEM or send S.A.E. for ILLUSTRATED LEAFLET.

PRICE INCORPORATING COLLARO DECK
CREDIT SALE . . . Deposit £12.8.0 and 9 Monthly Payments of £4.10.8.
 H.P. TERMS. Deposit £24.15.0 and 12 Monthly Payments of £2.5.11.

PRICE WITH TRUVOX DECK INCORPORATING REV. COUNTER . . . **£52.10.0**

CREDIT SALE. Deposit £13.2.6 and 9 Monthly Payments of £4.16.3.
 H.P. TERMS. Deposit £26.5.0 and 12 Monthly Payments of £2.6.8.



A TAPE PRE-AMPLIFIER and ERASE UNIT

STERN'S MODEL HF TR1—A completely assembled Pre-amplifier with

own Power Supply. Can be supplied correctly matched for use with Truvox or Collaro Decks and incorporates Recording Level Indicator and Monitoring facilities. Please send S.A.E. with any enquiry.

PRICE **£11.10.0** (Plus 5/- carr. and ins.)

SPECIAL REDUCTION WHEN PURCHASED WITH DECK.

"fidelity" TAPE AMPLIFIER HF/TR2 with Separate SMALL POWER SUPPLY UNIT £16.0.0

(Carr. and ins. 6/-)
 H.P. TERMS: Deposit £8 and 9 months of £1.
 CREDIT TERMS: Deposit £4 and 9 monthly payments of £1.9.4. When ordering please advise make of deck in use. Send S.A.E. for full details.



HOME CONSTRUCTORS. We can supply a COMPLETE KIT OF PARTS to build this TAPE AMPLIFIER for £12 (plus 5/- carr. and ins.). The Assembly Manual, Practical Diagrams, etc., are available for 2/6.

{Can be supplied to correctly operate with Collaro & Truvox Decks.}

HOME CONSTRUCTORS

BUILD YOUR OWN RECORDER . . . We offer

(a) The HF TR2 AMPLIFIER and POWER UNIT, both assembled, with the TRUVOX MK IV TAPE DECK. **£38.10.0**

ALTERNATIVELY the Amplifier and Power Unit as a KIT OF PARTS. **£35.0.0**

(b) The HF/TR2 AMPLIFIER and POWER UNIT, both assembled, with the TRUVOX TAPE DECK incorporating PRECISION REV. COUNTER. **£41.10.0**

ALTERNATIVELY the Amplifier and Power Unit as a KIT OF PARTS. **£38.0.0**

(c) The HF/TR2 AMPLIFIER and POWER UNIT, both assembled, with the COLLARO TRANSCRIPTOR. **£35.0.0**

ALTERNATIVELY the Amplifier and Power Unit as a KIT OF PARTS. **£31.10.0**

plus 12/6 carriage and insurance.

TO COMPLETE THE RECORDER . . . We offer

The Portable Carrying Case . . .

Acos Crystal Mike . . . Rola 10in. ALL **£9.0.0** (Plus 7/6 carr. & ins.)

x 6in. P.M. SPEAKER . . . 1,200ft. FOR Plastic Tape.

WE MAKE SPECIALLY REDUCED

PRICES FOR COMBINED ORDERS

ADD TAPE TO YOUR EXISTING AMPLIFIER . . . WE OFFER YOU

(a) The Model HF/TRIP TAPE PRE-AMPLIFIER together with the TRUVOX MK IV TAPE DECK. **£35.0.0**

(b) ALTERNATIVELY as in (a) above but Truvox Deck incorporating PRECISION REV. COUNTER. **£38.0.0**

(c) The Model HF/TRIP TAPE PRE-AMPLIFIER together with the COLLARO TRANSCRIPTOR Tape Deck. **£31.10.0**

PLEASE INCLUDE 12/6 to cover cost of carriage and insurance

HIRE PURCHASE and CREDIT SALE TERMS are available on all equipment (excluding Kits of Parts). Send S.A.E. for details.


NOTE.—The Collaro Transcripator is in short supply and there may be a delay in delivery. We will however book an order.

The Deck switches of the Transcripator have to be "wired-up." We will complete this wiring, for use with either the HF TR2 or the HF TRIP, for an extra charge of £1.

A Selection of RADIOGRAM CHASSIS enabling "MODERNISATION" of that OLD RADIOGRAM

ALL ARE THE LATEST AM-FM DESIGN

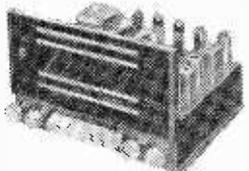- The Dulci Model H.3 **£20.17.0**
- The Dulci Model H.4 **£24.6.6**
- The Dulci Model H4/PP **£29.3.10**
- The ARMSTRONG PB 409 **£29.0.0**
- The ARMSTRONG AF 105 **£37.0.0**



We also have the latest FM or combined AM/FM RADIO TUNING UNITS.

- THE Dulci FM Tuner incorporating Power Supply **£17.10.3**
- The Dulci AM-FM Tuning Unit having own Power Supply incorporated **£20.17.0**
- The TSL FM Tuner incorporating Power Supply **£18.16.0**

The above are just a few examples—we have others. Send S.A.E. for full data on any chassis. Credit Sale and H.P. Terms are available.

"FRUSTRATED EXPORT ORDER"

The Corsor Model 527. X 4-Valve "All dry" Battery Transportable.

Offered **£6.15.0** Plus 5/- carr. & ins.

Consists of a 4-valve Superhet Receiver covering Medium Waveband 197-575 metres, and two Short Wavebands 13.6 to 136 metres. The new low consumption valves are incorporated and the whole is accommodated in an attractive robustly made case. Battery required is 90 volts and 1.4 volts (price 19/6) and is external to case.




STERN'S "F.M." TUNING UNIT

A 5-valve Tuner incorporating the latest Mullard Permeability Tuning Heart and a "Magic Eye" Tuning Indicator.

PRICE ASSEMBLED **£14.10.0**

READY FOR USE (Plus 7/6 carriage and insurance.)

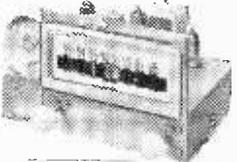TERMS: (a) Hire Purchase: Deposit £7.5.0 and 9 monthly payments of 18/4.
 (b) Credit: Deposit £3.12.6 and 9 monthly payments of £1.6.7.



HOME CONSTRUCTORS—You can build this unit for £10.10.0. Full Assembly Instructions are available for 1/6.

HOME CONSTRUCTORS—BUILD YOUR OWN "HI-FI" LOUDSPEAKER SYSTEM

WITH W-B'S WELL-KNOWN RANGE OF READY-TO-ASSEMBLE CABINETS. ALL ARE BEAUTIFULLY MADE AND FINISHED AND VERY EASILY ASSEMBLED. ONLY A SCREWDRIVER IS REQUIRED. THEY ARE PACKED FLAT IN CARTONS AND COMPLETE WITH SCREWS.

SEND S.A.E. FOR LEAFLET.

STERN RADIO

LIMITED (Dept. P.W.)

PLEASE SEND S.A.E. WITH ALL

1958 NEW LOOK MULLARD DESIGNS FOR THE "Hi-Fi" ENTHUSIAST
THE VERY POPULAR MULLARD "5-10" MAIN AMPLIFIER **MULLARD'S NEW 2-STAGE PRE-AMPLIFIER - TONE CONTROL UNIT** **THE NEW MULLARD "3-3" MAIN AMPLIFIER**



Undoubtedly the most successful amplifier yet designed, and used in conjunction with the new Mullard Pre-Amplifier, an undistorted power output of up to 10 watts is obtained. Thoroughly recommended to the "Hi-Fi" enthusiast who contemplates a very high quality home installation. In addition the versatility of the equipment makes it quite suitable for use in small halls, etc. We supply complete to MULLARD'S Specification with specified valves and components and including the latest PARMEKO Ultra-linear Output Transformer and the PARMEKO Mains Transformer which has power available to drive Radio Tuning Unit.


COMPLETE KIT OF PARTS **£10.00**
 Alternatively, we supply ASSEMBLED and TESTED **£11.10.0** (Carriage & Insurance 5/- extra.)
 This "5-10" with the latest PART-PRICE ULTRA-LINEAR OUTPUT TRANSFORMER for **£1.6.0** extra

Please enclose S.A.E. if ILLUSTRATED and alternatively, the COMPLETE ASSEMBLY MANUALS, containing component Price Lists and Practical Drawings, etc., are available at 1/6 each.

SPECIAL PRICE REDUCTIONS

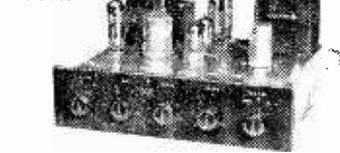- (a) THE COMPLETE KIT OF PARTS to build both the "3-3" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£12.10.0**
 - (b) THE COMPLETE KIT OF PARTS to build the "5-10" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£15.15.0**
- PRICES FOR THE "5-10" ARE SUBJECT TO £1.6.0 EXTRA IF THE PARTRIDGE TRANSFORMER IS REQUIRED.

THE NEW COMPLETE MULLARD "5-10" AMPLIFIER



Designed for a simple domestic installation with Genuine High Quality reproduction up to a maximum of 10 watts. Separate BASS and TREBLE Controls are incorporated with switched inputs for 78 and L.P. Records plus Radio Tuning Unit. We incorporate SPECIFIED COMPONENTS and NEW MULLARD VALVES. We also give the purchaser the choice of two of the best ULTRA-LINEAR OUTPUT TRANSFORMERS made—first the latest by PARMEKO LTD. and also the latest by PARTRIDGE (£1.6.0 extra). We also supply the PARMEKO MAINS TRANSFORMER, and this has extra power available to supply a Radio Tuning Unit. The Control Unit can easily be detached from the Amplifier Chassis for use in a remote position. COMPLETE KIT OF PARTS (PARMEKO Transformer) **£11.0.0**
 Alternatively, we supply ASSEMBLED AND TESTED **£13.10.0**
 Credit Sale, Dep. £3.7.6 and 9 Monthly Payments of £1.4.11. H.P. Terms, Dep. £6.15.0 and 8 Monthly Payments of 19/3. Send S.A.E. for ILLUSTRATED LEAFLET or 1/6 for the COMPLETE ASSEMBLY MANUAL.



A completely new design employing Two EF88 valves, and in particular designed to operate with the Mullard range of Power Amplifiers, but also perfectly suitable for other makes, etc.

- Briefly it incorporates:
- Equalisation for the latest R.I.A.A. characteristics.
 - Input for variable reluctance.
 - Magnetic Pick-Ups.
 - Input for Crystal Pick-Ups.
 - Input for Tape replay.
- (a) Direct from High Impedance Tape Head.
 (b) From a Tape Amplifier or Pre-Amplifier.
- Sensitive Microphone Channel.
 - Wide range Bass and TREBLE Controls.
 - Attractive Perspex front control panel.
 - Our Kit is strictly to MULLARD'S SPECIFICATION. **£6.0.0**

COMPLETE KIT OF PARTS Alternatively, we supply ASSEMBLED and TESTED (Carriage & Insurance 5/- extra.) **£8.0.0**

DESCRIPTIVE LEAFLETS are required; containing component Price Lists and Practical Drawings, etc., are available at 1/6 each.

THE NEW COMPLETE MULLARD "3-3"




Developed from the very popular 3-valve 3-watt Amplifier designed in the Mullard Laboratories. Our kit is complete to MULLARD'S SPECIFICATION including supply of specified components, valves and a PARMEKO OUTPUT TRANSFORMER. We also include switched inputs for 78 and L.P. records, plus a radio position. Extra power to drive a Radio Tuning Unit is also available. **£7.10.0** (plus 6/6 carriage and insurance).
 Alternatively supplied ASSEMBLED and FULLY TESTED **£8.19.6** (plus 6/6 carriage and insurance).

The complete specification is available for 1/6. Developed from the very popular 3-valve 3-watt Amplifier designed in the Mullard Laboratories. Our kit is complete to MULLARD'S SPECIFICATION including supply of specified components, valves and a PARMEKO OUTPUT TRANSFORMER. We also include switched inputs for 78 and L.P. records, plus a radio position. Extra power to drive a Radio Tuning Unit is also available.

THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION

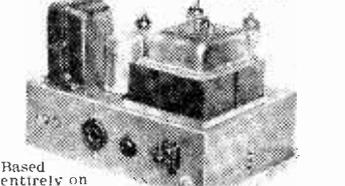The Portable Case will also accommodate almost any make of Autocharger and is attractively finished in Maroon and Grey Revene. WE ALSO SUPPLY SEPARATELY—
 (a) THE 2-Stage (plus Rectifier) AMPLIFIER **£42.8**
 (b) THE PORTABLE CARRYING CASE **£3.17.6**
 (c) P.M. SPEAKER **19/9**
 Carriage and Insurance 4/- extra.



Based entirely on the present very popular "3-3" model and designed to operate in conjunction with the new 2-stage PRE-AMPLIFIER (shown left) thus providing all the facilities associated with the more expensive "Hi-Fi" Equipment. We recommend it as the IDEAL HOME INSTALLATION where very high quality is desired at the lower volume level (up to 3 watts). We supply completely to MULLARD'S SPECIFICATION including the latest PARMEKO Output Transformer, specified Valves and Components. Has power available to drive a Radio Tuning Unit. COMPLETE KIT OF PARTS **£7.0.0**
 Alternatively, we supply ASSEMBLED and TESTED (Carriage & Insurance 5/- extra.) **£8.0.0**

NOTE ONLY NEW HIGH GRADE COMPONENTS and MULLARD VALVES are supplied with these Kits—We do NOT use "Surplus or Cheap" components.

- (a) The "3-3" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£15.0.0**
 CREDIT: DEPOSIT £3.15.0 & 9 Monthly Payments of £1.7.6 H.P.; DEPOSIT £7.10.0 & 9 Monthly Payments of 19/-
 - (b) The "5-10" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£18.18.0**
 CREDIT: DEPOSIT £4.15.0 & 9 Monthly Payments of £1.14.7 H.P.; DEPOSIT £9.9.0 & 12 Monthly Payments of 17/6
- When ordering include an extra 7/6 to cover Carriage and Insurance

RECORD PLAYERS

The Very Latest Models are in Stock. MANY AT REDUCED PRICES!!! TRANSCRIPTION UNITS, AUTO-CHANGERS, SINGLE RECORD PLAYERS

Send S.A.E. for ILLUSTRATED STOCK LIST A FEW CASH BARGAINS
 ● The latest BSR MONARCH 4 SPEED "MINOR" AUTO-CHANGER Entirely complete with Crystal Pick Up **£7.19.6**



● The latest COLLARO 4 SPEED "MINOR" AUTO-CHANGER — Complete with the Studio "O" Pick Up **£7.19.6**

(Also available with the low gain Studio "P" Pick Up for £8.15.0.)

● The latest COLLARO 4 SPEED SINGLE RECORD PLAYER complete with Studio "O" Pick Up **£6.19.6**

● The COLLARO "JUNIOR" 4 SPEED SINGLE RECORD PLAYER, complete with separate Crystal Pick Up **£4.10.0**

(This high output Crystal Pick Up is available separately for £12.6/- Carriage and Insurance on above Units 5/- ex.


SPECIAL CASH ONLY OFFER !!

This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER. ALL for **£8.7.6** ONLY (plus 7/6 carr. & ins.). The Amplifier consists of a 2-Stage design incorporating 3 modern B.V.A. valves and has separate BASS and TREBLE CONTROLS.



109 & 115 FLEET ST., LONDON, E.C.4.
 Telephone: FL Ees 5812/3/4.
CORRESPONDENCE

SIGNAL GENERATORS

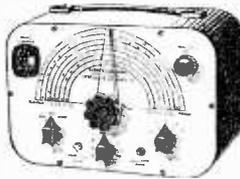


unmodulated i.f. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.


25/- deposit and 6 monthly payments of 21/6. Cash £8.19.6. Post and Packing 5/- extra.
Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6 1/2in. x 5 1/2in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 230/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%. Modulated or unmodulated R.F. output continuous variable 100 millivolts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

25/- deposit plus P. & P. 5/- and 4 monthly payments of 21/6. Cash £11.9.6 plus P. & P. 5/-.


Coverage 120 Kc/s. 84 Mc/s. Metal case 10in. x 6 1/2in. x 4 1/2in. Size of scale. 6 1/2in. x 3 1/2in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 20%. Modulated or unmodulated R.F. output continuous variable 100 millivolts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

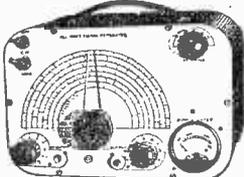

CONVERT TO I.T.A. FOR ONLY 25/- deposit plus P. & P. 5/- and 4 monthly payments of £15.6. Cash £5.17/- plus P. & P. 5/- ANY T.V. (except Philips Bristol area or Valley Area, Wales) WITHIN 35 MILES OF I.T.A. TRANSMITTER. ALL CHANNELS NO ALTERATIONS TO SET. Complete with built-in power supply. 200-250 v. A.C. mains. Crackle finish case 5 1/2in. long. 3 1/2in. wide. 4 1/2in. high. Incorporating gain control and band switch. Illus. with cover removed. Complete installation comprises: Converter. Wolsey 3-element I.T.A. outside or left aerial. 36ft. I.T.A. lead. two plugs. (Wolsey 5-element 10/- extra.) "CONVERTER" only £3/19.6 plus P. & P. 2/6.

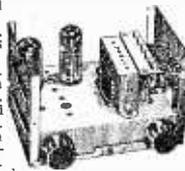

AC/DC POCKET MULTI-METER KIT

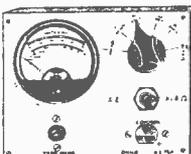

Comprising 2 1/2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range AC/D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot. for ohms 2370 setting. Toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus Built and tested P. & P. 1/6. 7/6 extra.

Point to point wiring diagram 1/- free with kit.

4-VALVE ALL-DRY SUPERHET PORTABLE KIT

Incorporating Ferrite rod aerial. Medium and long waves. In grey leatherette. Size 6in. x 7in. x 6in. Valve line-up: 1T4, 1R5, 1S5, 3V4. Complete kit of parts (less batteries). £5.19.6 Plus Post & Packing 3/6.



PORTABLE AMPLIFIER

Size 6 1/2in. long, 5 1/2in. high, 2 1/2in. deep. Will suit any type of crystal pick-up. Output approx. 2 watts. Incorporating ECC83 double triode. Cossor 142BT output pentode and contact-cooled rectifier. Fully isolated mains trans-49/6 Plus former for 230/250 A.C. mains. Base, treble, and P. & P. 3/6 volume controls. 5in. SPEAKER with O.P. TRANSFORMER purchased with the above. 18/6, plus P. & P. 1/6.

COLLARO MIXER 4-SPEED AUTOMATIC CHANGER

Model 457 Type "O" Pick-up. Size 12in. x 13 1/2in. Minimum clearance above baseboard 5in., below 2 1/2in., 10 records. A.C. mains. 230-250 v., turnover crystal head. Brand new, fully guaranteed (suitable for use with the above amplifier). £8.19.6 Plus or 25/- deposit, plus P. & P. 5/-, and 7 monthly payments of £15/0.

RADIO & T.V. COMPONENTS (Acton) LTD.
23 HIGH STREET, ACTON, LONDON, W.3

All enquiries S.A.E. Goods not dispatched outside U.K.

The new


MOTEK-K9

TAPE DECK

This superlative all British Deck with three speed control knob is designed to allow easy fitment and simplicity of operation. The many outstanding features place this Deck in a class alone.

Details on request Patents pending

Cost 21 gns

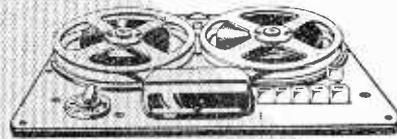

MODERN TECHNIQUES

Wedmore Street, London, N.19. Tel: ARCHWAY 3111

DHB 7315



"MY BENNETT COLLEGE TUTOR MIGHT HAVE BEEN IN THE ROOM"

PERSONAL POSTAL TUITION

WHAT CAREER DO YOU WANT?

- Architecture
- Building
- Carpentry
- Commercial Art
- Diesel Engines
- Draughtsmanship
- Electrical Eng.
- Electric Wiring
- Forestry
- Locomotive Eng.
- Machining Drawing
- Mechanical Eng.
- Motor Engineering
- Plumbing
- Quantity Surveying
- Radio Engineering
- Sanitary Science
- Surveying
- Telecommunications
- Television
- Wireless Telegraphy and Telephony
- Book-keeping
- English
- Geography
- Journalism
- Languages
- Mathematics
- Modern Business Methods
- Police Subjects
- Salesmanship
- Short Story Writing
- and many others

OR WHY NOT OBTAIN A QUALIFICATION?

- A.M.I.C.E.
- A.M.I. Mech. E.
- A.R.I.B.A.
- A.M.I. Struct. E.
- GEN. CERT. OF EDUCATION & R.S.A. Exams.
- A.M.J. Mun. E.
- A.H.S.E.
- A.A.C.A.
- A.C.W.A.
- A.C.I.S.
- A.C.E.S.
- A.R.I.C.S.
- A.A.I.

Every Bennett College student enjoys this friendly, intimate coaching right through his Course. A few of the Courses are listed opposite. Tell us your subject. We will send you The Bennett College Prospectus and the famous FREE book "Train your mind to SUCCESS". This will show you how you can advance to a better, finer future by Personal Postal Tuition. Fill in and post the coupon today.

BENNETT COLLEGE
(Dept. F.104 PT.) SHEFFIELD

Please send me the Prospectus on.....

..... and my free copy of "Train your mind to SUCCESS."

NAME

ADDRESS

TOWN

Age (under 21)

Please write in BLOCK letters

Post this coupon NOW!



VALVES
Guaranteed
All Tested
Before
Dispatch

AC6PEN 6/6	H30	5/-	UCF80	23/-	
AC7HI	HL23DD	8/6	UCH42	10/6	
ATP4	34/9	17/5	UCH81	11/6	
AZ31	3/6	KF35	8/6	UCL82	23/-
CBL31	24/4	KK32	23/-	UCL83	25/9
CCH35	24/4	KT24	5/-	UF41	10/6
CL33	20/2	KT33C	10/-	UF85	10/6
CY31	17/5	KT36	27/10	UF89	10/6
DAF96	10/6	KT55	13/6	UL41	10/6
DF96	10/6	KT66	15/-	UL44	27/10
DK96	10/6	KTW61	8/-	UL46	24/4
DL96	10/6	KTW63	7/6	UL84	11/6
DM70	8/6	KTZ41	8/6	UU6	20/11
EA50	1/6	ME91	7/6	UU8	17/10
EABCO8	10/6	MH4	7/6	UU9	8/6
EAC91	7/6	MH41	7/9	UY41	8/6
EAF42	10/6	N37	18/1	UY85	10/6
EB34	2/-	N78	12/6	VP28	3/6
EB41	9/6	OZ4	5/6	VP23	6/6
EB333	7/6	P61	3/6	VP41	8/6
EB341	10/6	PC84	10/-	VR105	30/-
EBF80	10/6	PCF80	13/6	VR116	4/-
EBF89	18/1	PCF82	12/6	VR150	3/-
EBL21	24/4	PCL82	14/6	VUI20A	9/6
EBL31	24/4	PCL83	14/6	VUI20B	6/6
EC91	7/6	PL38	27/10	VU39	6/6
ECC40	12/6	PL81	16/-	(MU12 14)	6/6
ECC84	10/3	PL82	9/6	6/6	8/9
ECC85	9/6	PL83	11/6	VUI11	2/6
ECF80	13/6	PX25	12/6	W77	8/6
ECF82	12/6	PY80	9/-	W729	13/6
ECH21	24/4	PY81	10/-	X65	12/6
ECH35	10/6	PY82	8/6	X78	22/3
ECH42	9/6	PY83	10/6	X79	11/6
ECH81	10/-	PZ30	20/11	Y63	9/6
ECL80	13/6	PEN4DD	23/09	Z309	9/6
ECL82	12/6		27/10	Z359	9/6
EF22	8/6	PEN25	5/-	Z759	9/6
EF36	6/-	PEN45	27/10	IA3	3/6
EF37A	12/6	PEN46	7/-	IA5GT	6/-
EF39	6/-	PEN46	7/-	IA7	12/6
EF40	13/6	PEN220A		IC2	11/6
EF41	9/9			IC5GT	12/6
EF42	14/-	PENA4	15/-	ID6	12/6
EF50	4/-	QP21	7/6	IH5GT	10/6
EF55	10/6	R16	27/10	IL4	6/6
EF80	9/6	R19	13/6	ILDS	3/6
EF85	9/-	SP41	3/-	IN5	10/6
EF86	13/6	SP61	3/-	IR5	8/-
EF89	10/-	SP220	3/11	IS4	10/6
EK32	8/6	T41	24/4	IS5	7/6
EL32	5/6	TH42	9/-	IT4	7/6
EL33	20/2	TP25	27/10	IU5	7/6
EL38	27/10	UI0	10/6	2C26	1/6
EL41	10/6	UI4(DW4)		2X2	4/6
EL42	12/-	500)	8/6	3A4	7/-
EL84	10/6	U22	8/-	3D6	5/-
FM34	10/6	U37	27/10	3Q4	9/-
EM80	10/6	U45	15/-	3Q5GT	9/6
EM81	11/6	U329	14/6	3S4	8/6
EY51	13/6	U403	17/5	3V4	9/-
EY86	17/6	U404	11/10	4D1	3/-
EZ40	9/-	U801	31/4	5R4G	9/6
EZ41	10/-	UABC80		5U4G	8/6
EZ80	8/9			5Y3G	8/-
EZ81	11/10	UAF42	10/6	5Y3GT	8/-
EZ90	8/-	UB41	9/6	5Z4G	10/-
E1148	2/-	UBC41	10/-	6A7	13/-
FW4,500	10/-	UBF80	9/6	6A8C	10/6
		UBC84		6AC7	6/-
GZ32	12/-		20/11	6AG5	5/6

6AK6	6/6	6X5G	7/-
6AL5	6/6	6X5GT	7/-
6AM6	9/-	6/30L2	12/6
6AQ5	7/6	7B7	8/6
6AT6	8/6	7C5	8/-
6AU6	10/6	7C6	8/-
6B4	5/-	7H7	9/-
6B8G	4/-	7Q7	9/-
6BA6	7/6	757	9/6
6BE6	8/-	7Y4	8/6
6BG6	24/4	8D2	2/9
6BH6	16/-	9D2	3/6
6B8J	9/-	10F1	27/10
6BR7	11/6	6/10	6/6
6BRV6	8/6	6/12AH3	11/6
6BV7	10/-	6/12AT6	10/6
6C4	7/-	6/12AT7	9/6
6C5GT	6/6	6/12AU6	10/6
6C6	5/-	6/12AU7	7/6
6C8G	5/-	6/12AX7	8/6
6CD6G	31/4	6/12BA6	9/6
6CH6	7/6	6/12BE6	10/-
6D6	5/-	6/12BH7	11/6
6F1	13/6	6/12CGT	8/6
6F6G	7/6	6/12HG6T	3/6
6F6M	7/6	6/12J5GT	4/6
6F13	14/-	6/12J7G	10/6
6F15	14/-	6/12K7GT	8/6
6G6G	4/6	6/12K8GT	10/6
6H6	2/6	6/12L7G	13/6
6H6GT	2/6	6/12Q7GT	8/6
6J5GT	5/6	6/12S7	1/6
6J5M	6/6	6/12S7	7/6
6J6	6/-	6/12S7	8/6
6J7G	6/6	6/12S7	8/6
6J7M	9/-	6/12SK7	6/-
6K6GT	7/-	6/12SL7	8/6
6K7G	5/-	6/12SN7GT	
6K7GT	7/-		17/6
6K7M	6/9	6/12SQ7	8/6
6K8G	8/6	6/1457	14/6
6K8GT	10/-	6/15D2	7/9
6K25	20/11	6/198G5G	
6L6G	9/-		24/4
6L7	7/6	20D1	16/-
6N7	7/6	20F2	27/10
6P23	27/10	20P1	27/10
6Q7GT	9/-	20P3	20/11
6QA7GT	8/-	20P5	20/11
6S7	7/6	25A6G	11/6
6S7H	6/-	25L6GT	10/-
6S7	8/6	25Y5	9/9
6S7G	6/-	25Y5G	9/9
6SL7GT	8/-	25Z4	9/6
6SN7GT	7/6	25Z5	10/-
6SQT	9/3	25Z6	10/-
6U4GT	14/-	30F5	12/6
6U5/6G5	8/6	30FL1	12/6
6U5G	8/6	30P4	21/7
6U7G	8/6	30P12	12/6
6V6G	7/-	30P11	12/6
6V6GT	7/-	35L6GT	9/6
6V6M	8/6	35W4	8/6
6X4	7/6	35Z4GT	8/-

35Z5GT	9/-	210DDT	4/6
42	8/-	210VPT	3/6
50C5	11/6	807	6/6
50CD6G		954	2/-
	31/4	955	4/9
50L6GT	8/6	956	3/6
75	11/6	9001	5/6
77	7/6	9002	5/6
80	8/6	9003	5/6
142BT	3/6	9004	5/6
185BT	34/9	9006	5/6

MAINS TRANSFORMERS

3 Way Mounting Type.

MT1
Primary: 200-220-240 v. Secondaries: 250-0-250 v. 80 m/A 0-6.3 v. 4 amp., 0-4 v. 2 amp. Both tapped at 4 v. 21.9 each.

MT2
Primary: 200-220-240 v. Secondaries: 350-0-350 v. 80 m/A 0-5.3 v. 4 amp., 0.5 v. 2 amp. Both tapped at 4 v. 21.9 each.

MT3
Primary: 200-220-240 v. Secondaries: 30 v. 2 amps. Taps at 3 v., 4 v., 6 v., 8 v., 9 v., 10 v., 15 v., 18 v., 20 v., 24 v., 21/9 each. Postage and Packing please add 2/- per transformer.

CHASSIS

Aluminium Undrilled with Reinforced Corners. Available in the following sizes — ea.

6in. x 4in. x 2in.	4/6
8in. x 6in. x 2in.	6/3
10in. x 7in. x 2in.	7/3
12in. x 3in. x 2in.	5/9
12in. x 5in. x 2in.	6/9
12in. x 8in. x 2in.	8/6
14in. x 3in. x 2in.	6/-
14in. x 9in. x 2in.	12/-
16in. x 6in. x 2in.	8/6
16in. x 10in. x 2in.	14/-

All are four-sided—ideal for radio receivers—amplifiers—power packs, etc.

WB "Stentorian"
Model HF 812 Die-cast chassis 84/6
Model HF 1012 Die-cast chassis 99/9

Universal speech coils.
Co-axial Cables, etc. yd.
Aerialite Aeraxial 597. semi-airspaced
Ashton Co-axial cable solid
Ribbon feeder (Flat) 300 ohms 6d. postage.

The Brayhead Turret Converter.—Comprehensive installation instructions, plug-in facilities for over 600 popular models of T.V. sets of standard I.F. ranges, £7.7.0 Illustrated leaflets available. Adaptors Price 7/6

SPECIAL PURCHASE
Bin. P.M. Speaker Units with Output Transformer removed from equipment, 11/6 each.

PUBLICATIONS

No. 138. HOW TO MAKE AERIALS FOR TV. (Band 1 and 3) and V.H.F. (Band 2). Data for all Channels. Ten different designs for local and fringe areas. each. 2/6.

No. 140. TELEVISION SERVICING FOR BEGINNERS. ★ 40 pages of Information. each 4/6

No. 142. MODERN TV CIRCUITS AND FAULT FINDING GUIDE. ★ Many interesting Circuits included. each 4/6

Reprint No. 5. TV FAULT FINDING. Profusely illustrated with Photographs taken from a Television Screen. each 5/-

Reprint No. 11. QUALITY AMPLIFIERS FOR A.C. MAINS. Articles describing a number of amplifiers selected for their quality of performance and ease of construction.

No. 127. AMPLIFIER MANUAL NO. 3. 3/6

No. 101. TWO-VALVE RECEIVERS 1/6

No. 99. ONE-VALVE RECEIVERS 1/6

No. 104. THREE-VALVE RECEIVERS 1/6

No. 96. CRYSTAL SET CONSTRUCTION 1/-

No. 146. HIGH-FIDELITY LOUDSPEAKER ENCLOSURES 5/-

No. 126. THE BOYS' BOOK OF CRYSTAL SETS WITH PRACTICAL CIRCUITS 2/6

All publications plus 4d. each 6d. postage.

LOUDSPEAKER UNITS

Make	Type	Size	Price
Plessey	Square	3in.	19/6 each
Lesconvia, Plessey	Round	3in.	17/6 each
Goodmans, Plessey	Round	6in.	18/6 each
Goodmans, R. & A.	Round	8in.	19/6 each
Plessey, R. & A., Elac	Round	10in.	25/6 each
Elac	Elliptical	7in. x 4in.	19/6 each
Elac	Elliptical	10in. x 6in.	25/6 each

All the above are PM units with 2 to 3 ohms speech coils.
RTC 12in. heavy duty 20 6in. Mains Energised
watts model 15 ohms Speaker 17 6
Speech Coil £5 5 0 Bin. Mains Energised Speaker £1 1 0



All have field coils of approx. 600 ohms.



103 LEEDS TERRACE
WINTOUN STREET
LEEDS 7

TERMS: Cash with order or C.O.D. Postage and Package charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. All single valves postage 6d. Personal Shoppers Monday-Friday 9 a.m. to 5 p.m. Saturday 10 a.m. to 1 p.m.

PRACTICAL WIRELESS

EVERY MONTH
VOL. XXXIV, No. 618, JUNE 1953
COMMENTS OF THE MONTH

EDITOR : F. J. CAMM

26th YEAR
OF ISSUE

BY THE EDITOR

MIDGETS

OUR recent editorial comments on the need for a really midget battery-operated personal receiver, light in weight, and easily carried in the pocket, has brought forth a large amount of correspondence and suggestions, and readers will be glad to know that we are now experimenting with a circuit which we feel will meet most of the conditions which have been named. It is obvious that high quality of reproduction cannot be expected, nor can the reader expect to receive a large number of stations. Such a receiver must essentially operate only on the medium-waveband and from low-voltage batteries. One or two readers have submitted tiny receivers which they have made themselves and we shall be describing one of these in an early issue. In the meantime, we shall still be glad to receive details of midget receivers which have actually been built and we should prefer constructors to send the receiver to us for test. We shall, of course, pay for all articles describing such receivers accepted for publication. One of the difficulties at present is to find suitable sources of components, and it would seem that some of these will have to be made.

ANOTHER "P.W." EVENING?

EVER since we organised that P.W. evening at Caxton Hall last year there has been immense demand from readers for a repetition of it with, of course, a different programme. We should be glad, therefore, if readers who would be interested in attending will drop us a card signifying their intentions.

THE RADIO SHOW

THIS year's Radio Show takes place at Earls Court from August 27th to September 6th. We can report up to the moment of going to press that there is no indication of any startling developments, and the mixture it would seem will be as before. It is good that there should not be too frequent changes in design. The motor trade tried the sales dodge of putting each year's model out of date at the end of the current year. This was always irritating to the purchasers. The trade has now adopted a more sensible plan of producing new models by series numbers and not designating them by the year of introduction. The radio trade in its earlier years followed this system, but found that it did not work. The public did not too readily take to the idea of scrapping a £50 radio set because the latest model had a different design of loudspeaker grille or a different tuning dial. New models every two or three years are tolerable. This year's show, therefore, may show price changes and, as usual, different designs of cabinet. The public will go to the Radio Show not only to see the manufacturers' products, but also the sideshows put on by the Services, the BBC and other associations. The Radio Show is a fascinating event for this reason alone. There will be improved catering arrangements and innovations to add to the comfort of the visitor. —F. J. C.

Our next issue, dated July, will be published on June 6th.

Editorial and Advertisement Offices :
PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1958.

Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - 19s. per annum.
Abroad - - 17s. 6d. per annum.
Canada - - - 16s. per annum.

CONTENTS :

	Page
Editorial	263
Round the World of Wireless	264
A Beginner's Constructional	
Course	266
New Radio Components	270
A Mains-Battery Portable	272
On Your Wavelength	276
Transistors in Practice	279
The Audio Fair—1958	283
Is a Pre-war Set Worth	
Servicing?	287
A Hi-Fi A.M. Receiver	289
A Tape Economiser	294
A Frequency Comparator	297
Transmitting Topics	301
Servicing Radio Receivers :	
Coscor Record Player	309
Programme Pointers	314
Open to Discussion	317
News from the Trade	321

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Round the World of Wireless



By "QUESTOR"

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of February, 1958, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London Postal	1,047,961
Home Counties	1,056,672
Midland	781,325
North Eastern	1,016,681
North Western	758,308
South Western	654,548
Wales and Border Counties...	406,725
Total England and Wales ...	5,722,220
Scotland	759,319
Northern Ireland	180,774
Grand Total	6,662,313

During February the number of combined television and sound licences throughout Great Britain and Northern Ireland increased by 96,476, bringing the total to 7,994,723. Sound only licences total 6,662,313 including 330,238 for sets fitted in cars.

Transistors in Explorer

COSMIC ray, meteorite and temperature information

now relayed to earth from the globe-girdling Explorer satellite is being gathered with the help of many tiny silicon transistors made by Raytheon Manufacturing Company.

Extremely rugged and reliable, the pea-sized Raytheon transistors are in the satellite's telemetering circuit that sends coded data to receiving stations on earth.

The transistors, Type 2N328, developed under Army Signal Corps contract, are the PNP design, made by the Raytheon-perfected fusion alloy process. This process permits a mechanically stronger assembly, allowing the transistor to withstand higher shock and vibration stress, both in the launching and orbit.

Other advantages for satellite use, in addition to the many inherent advantages of silicon transistors, are the 2N328's high electrical efficiency and ability to withstand sudden surges of voltage.

The silicon devices work well at temperatures ranging from minus 50 to plus 150 degs. Centigrade, or much higher than germanium. Likewise, silicon performs more uniformly at the predicted temperatures for which the satellite equipment was designed.

Retirement

THE retirement is announced of Mr. W. H. Grinsted, O.B.E., F.C.G.I., M.I.E.E.



Mr. Grinsted, O.B.E., etc., who has retired from Edison as reported here.


Director of Engineering of Siemens Edison Swan Ltd.

Mr. Grinsted was born at Slinfold, Sussex. He received his education at Collyers School, Horsham and at the Central Technical College (now Imperial College) London, where he held the Clothworkers' scholarship and won the Siemens Medal (awarded to the third year student heading the list in Electrical Engineering).

R.E.C.M.F.'s New Chairman

AT a meeting of the Council in London, Mr. K. G. Smith (N.S.F. Ltd.) was elected chairman of the Radio and Electronic Component Manufacturers' Federation in succession to Mr. Richard Arbib. Mr. Hector V. Slade (Garrard Engineering and Manufacturing Co. Ltd.) was elected vice-chairman.

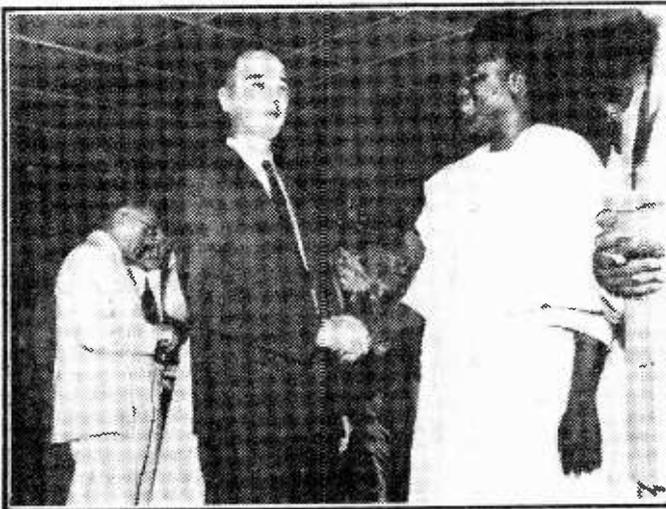Mr. K. G. Smith is technical and sales director of N.S.F. Ltd.



Mr. D. P. Young, Chief Installation Engineer, Marconi's, is seen receiving the congratulations of the Minister, Chief Akintola on the successful opening of the network referred to on the opposite page.



whose factories are at Keighley, Yorkshire and Liverpool. He is a native of South Africa but has lived in this country for over 30 years.

He is also a director of the Motor and Electronics Corporation, Ltd., of British Centralab, Ltd.

Linear Accelerator at Cheshire Hospital

A FOUR million electron-volt gantry mounted Linear Accelerator designed for super-voltage X-ray treatment of deep-seated tumours has been installed in the new Radiotherapeutic Unit of the Clatterbridge General Hospital, Bebington, Cheshire.

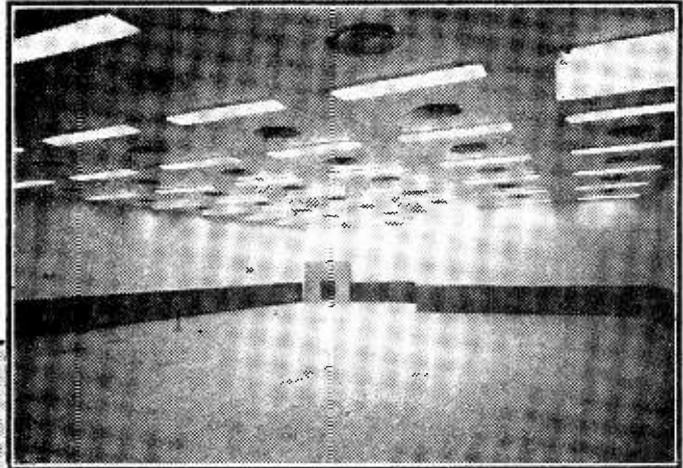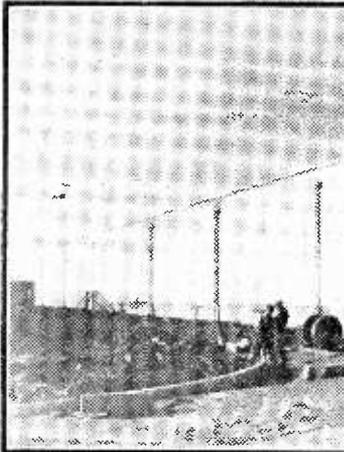The inaugural ceremony, performed by Lord Cohen of Birkenhead, took place on



Outside and inside views of the £300,000 factory at Swindon, which is to be devoted to the production of transistors. It has no windows, is dustproof and fully air-conditioned. It is owned by Senil Conductors, Ltd.

March 28th under the auspices of the Liverpool Regional Hospital Board.

The installation of this equipment represents a further stage in the programme for the provision of Linear Accelerators for deep therapy treatment at suitable hospital centres in Great Britain. Newcastle-upon-Tyne General Hospital was the first to be equipped under the programme. Other centres where Linear Accelerators have been installed are in Edinburgh, London and Manchester.

New Records for Radio Exports

EXPORTS of two items of radio equipment reached their highest monthly levels in February it is announced by the

Radio Industry Council. These were sound reproducing equipment, where the value in one month topped £1m. for the first time, and valves and tubes, where the value was £426,000. These figures compare with values of £793,000 for sound reproducing equipment in February, 1957.

and of £350,000 for valves and tubes in February, 1957.

The provisional value of exports of all items of radio equipment in February was £3.65m. This was slightly below the figure, £3.7m, for February, 1957 (but may exceed it when the full returns are known).

The total for the first two months of the year is now over £7.4m, compared with £6.9m, for the first two months of 1957, which was a record year.

World's Biggest Radio Multi-channel Link

THE largest radio telecommunications system of its type in the world was inaugurated recently in Nigeria

by the Nigerian Minister of Communications and Aviation, Chief the Honourable S. L. Akiintola, M.H.R. Marconi's Wireless Telegraph Company have been responsible for the construction of the whole system, which is capable of providing an ultimate capacity of over

50,000 channel miles. Marconi V.H.F. multi-channel equipment has been used at all the 14 terminal and 25 repeater stations.

With the completion of this scheme internal communications in Nigeria have made a significant advance. It is now possible to telephone from Lagos to many provincial towns whose local services have not previously been connected into a national network. The important centres now linked by first class trunk services include Lagos, Ibadan, Benin, Onitsha, Enugu and Kaduna.

Radios to Seven Countries

HUNGARY is to export a total of 14,000 radio sets to Cyprus, Yugoslavia, South Africa, Sweden, Czechoslovakia, Greece and Roumania this year from the Telephone Electrical Goods Factory, Budapest.

And railway safety equipment worth £600,000 will be exported to Czechoslovakia, and Yugoslavia, reports the newspaper *Népakarat*.

A Beginner's CONSTRUCTIONAL COURSE - III

A NEW SERIES WRITTEN ESPECIALLY FOR
THE AMATEUR

By E. V. King

3.—CONVERTING THE 2-VALVER INTO A 3-VALVE SET

WHERE the lead from C14 goes through the grommet scrape it clean and solder on R10 which is then earthed to chassis (Fig. 16). Solder on a few feet of lighting flex for the speaker. Fix C16 across the primary of the speaker transformer, i.e. the tags already going to anode and H.T.


Checking the Circuit

Again pencil out the theoretical circuit. Ink it in as each part is checked. Especially check the value of R9, beginners make many mistakes with the colour code. Then carry out a visual "round the clock" valve base check as follows: 1 to earth. 2 to earth via R9 and C11. 3 to TR2 and C16. 4 to pin 7. 5 to earth. 6 to earth. 7 to pin 7 V2, TR2 and pin 4 V3. 8 to pin 8 V2.

Testing the Detector With an Output Stage

The detector stage should not have been disturbed and should of course still be working. Connect everything up, note the mains is in the right way round and switch on. Note that both filaments light up. If not check the mains supply and filament circuits. Attach a good aerial (50ft. will give good volume at this stage) to the positions on the PA2 already detailed. In Fig. 22 these places are "Y" or "Red" of the PHF2 coil near V2. If the aerial is short it is best attached directly to the red tag of the coil via a small 500 pF safety condenser.

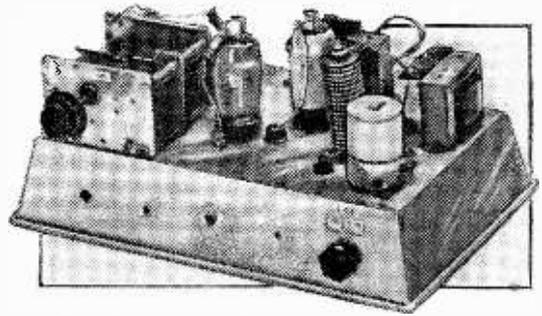Your receiver will now receive the local stations at good speaker volume. There should



only be a minimum of hum from the speaker and speech and music should be undistorted and clear.

If you do not get reception proceed as follows. Unplug V3 leaving all wiring in place. Attach headphones as already detailed and verify that the detector stage is working. If not then you must have disturbed the detector stage wiring or shorted the H.T. supply to earth. If the detector stage is working replace V3, remove the top cap clip and touch the top cap with a finger. Loud 50 cycle hum should be heard from the speaker, if not then the output stage is faulty. Check the valves by interchange into the detector stage (using phones). If the valves are all right thoroughly check all V3 wiring and the value of components.

If the directions have been carefully followed no troubles will arise. A student of 15 built one of these receivers from these instructions and only made one error which he quickly put right. His error, for some reason or other, was to short out R11 with a direct loop of wire between C12 and C13. The result, of course, was a terrific hum even when all top caps were in place!

Do not proceed to the next stage until your two valver is working perfectly as regards clarity and lowness of hum. There are some notes on hum at the end of this series.

Adding an H.F. Stage

If we fit an amplifier to increase the aerial signal then we shall get much more volume from the output stage. This volume is, of course limited, or distortion will occur on local stations. So the amplifier fitted must have a variable amplification factor. If the amplifier fitted is

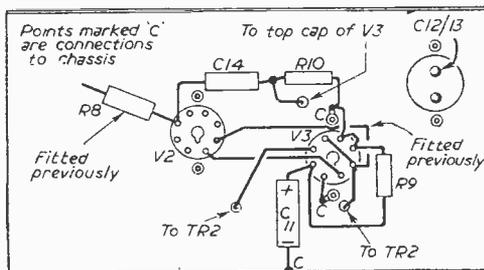


Fig. 16.—New wiring added when fitting V3 (view of underside of chassis).

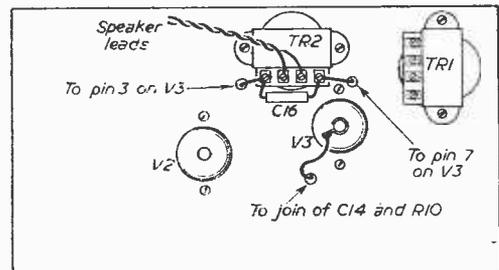


Fig. 17.—Additional wiring when V3 is fitted (top view of chassis).

tuned like the detector stage we shall have much increased selectivity. Stations near together on the dial will be separated with ease and distant ones received well provided fading troubles are not too bad (these are atmospheric in origin).

Preliminary Alterations to the Detector Stage

Fix another coil, a Wearite PHF2 this time, in the position shown in Fig. 19. Make sure the red tag is facing the top cap of V2 as shown. Now remove the end of C7 which is attached to the red tag of PA2 and attach it instead to the red tag of the PHF2 just added. Shorten the leads if necessary. Earth tag X of PHF2 and earth tag Z. Any suitable tag may be attached to chassis for this purpose. Take a short lead

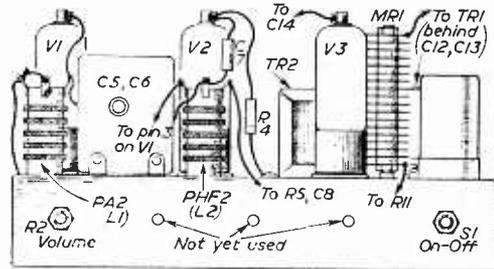


Fig. 20.—Side view of the receiver with this month's modifications.

from the red tag of this coil to the other gang (C6), that is the gang nearest the front of the receiver, making sure that the lead goes to the fixed vanes and not the moving ones.

Now try out the detector and output stage as before. It should work as before when the aerial is placed on the red tag of the new PHF2 coil. It should work, but with much reduced volume, in position on tag Y. This is in order. Do not proceed until the set is working with this new coil added. Any troubles which occur

must of course be due to the tuned circuit of coil and condenser and nothing else, for nothing else has been disturbed.

Wiring the H.F. Stage (Underneath)

Refer to Fig. 20 and fix the volume control in the correct position. Fix another Mazda

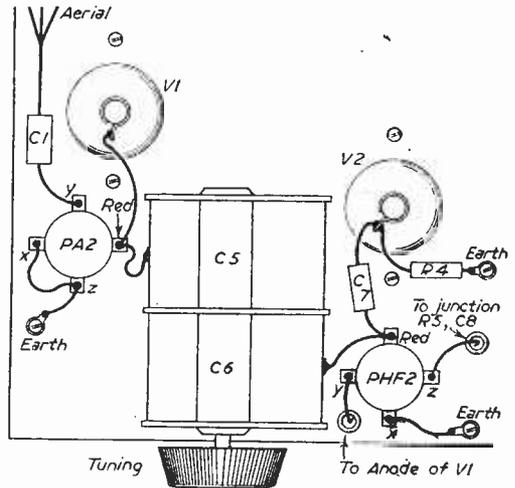


Fig. 19.—Top view of H.F. and detector stages.

Octal base for V1 in the same relative position as V2 and V3 (Figs. 1 and 21).

The theoretical circuit is given in Fig. 18, compare it with the diagram of the complete three-valver in Fig. 22. The under view of the practical layout is given in Fig. 21 and the top view in Fig. 19. The front elevation of Fig. 20 may also help the reader with the wiring.

Here is a suggested plan to follow. Take pin 8 of V1 to pin 8 V2. Take pin 7 on V1 to pin 7 on V2. This valve is then supplied with H.T. and L.T. Earth pin 1 to nearby tag. Earth pins 5 and 6 to the other tag. Suspend R1 in air between pin 2 and any earth (i.e. pin 6 would do). Fix C3 likewise. Take pin 3 to the Y tag of the PHF2 (detector stage). Remove the earth lead on the Z tag and instead take Z to C8 (other half of double 8-8 μF). Join C8 to pin 7 on V1 via R5. The H.T. supply is now decoupled. Take pin 4 to slider (centre tag) of the volume control and from there to earth (any suitable tag is fitted) via C2. One of the side tags of the volume control is earthed, the other is connected to junction R5 and C8 via R3 (more about this value later). Earth junction of R3 and volume control via C4 (this could be omitted in most cases without any effect). Check this with pencil and paper, and "round the clock"

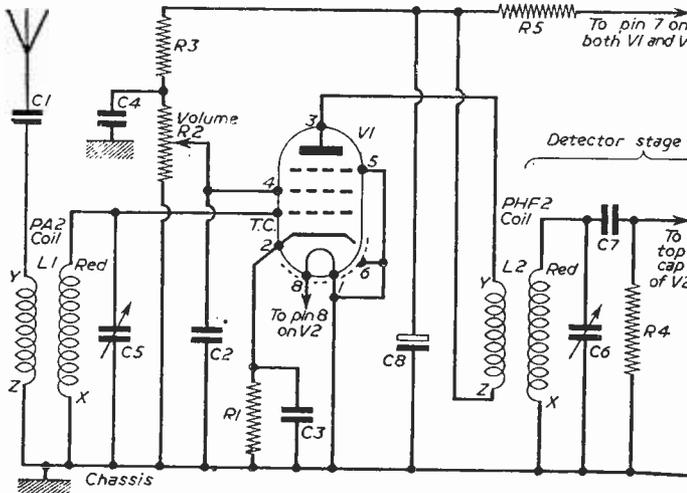


Fig. 18.—Theoretical circuit of H.F. stage.

again as follows: 1 to earth. 2 to earth via R1 and C3. 3 to Y of PHF2. 4 to R2 and C2. 5 to earth. 6 to earth. 7 to pin 7 V2. 8 to pin 8 V2. Now check for sure that your component values are correct.

Wiring the H.F. Stage (On Top)

The PA2 is now used. This should already have tags Z and X to chassis, and the red to the fixed vanes of the nearby gang C5. Make sure these leads are still attached. Now take

LIST OF COMPONENTS FOR OUTPUT STAGE (Fig. 15)

- C11—25 μ F 25v.w.
- C14—.01 μ F
- C16—.01 μ F
- R9—330 ohms
- R10—470k ohms
- Tr2—Standard speaker transformer
- V3—SP41 6I

a lead direct to the top cap connector of the new valve V1. The H.F. stage is now complete.

Testing the Complete Receiver

Fix up all leads making sure mains is in correctly. Observe that all valves light up. If not verify if the valve is faulty by changing them round, or if the filament circuit is faulty check the circuit Tr1, and pins 1 and 8 on each holder. Advance R2 and signals should be heard. A long aerial is not required. Advance R2 fully, if the set starts to oscillate this is in order. Do not leave it doing so, retard R2 until the oscillations clear (if there were any) and tune the gang condenser. Stations should be heard though probably with interference for the time being.

Trimming the Receiver

Have a look at the gang condensers and find the small auxiliary condensers which are called trimmers. A small screwdriver will be required to adjust these. Do them up tight and then undo

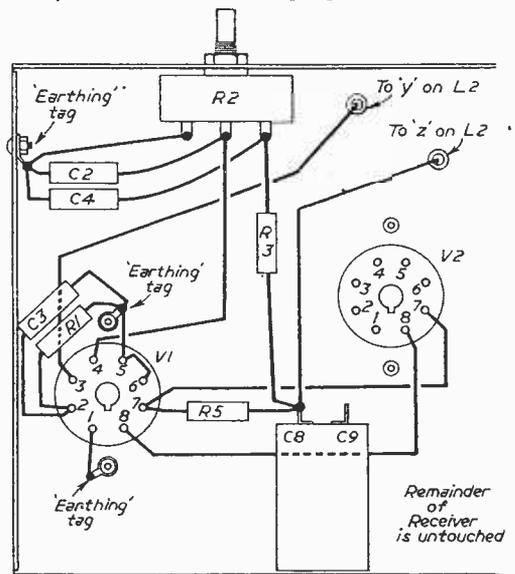


Fig. 21.—View of the underside wiring added to complete H.F. stage.

them both two complete turns. Now open the vanes and find a weakish station (i.e., Luxembourg, if you are not too near the south coast). Use R2 control as necessary, but do not let the receiver oscillate: if it does reduce setting of R2 slightly. Now adjust carefully the two trimmers


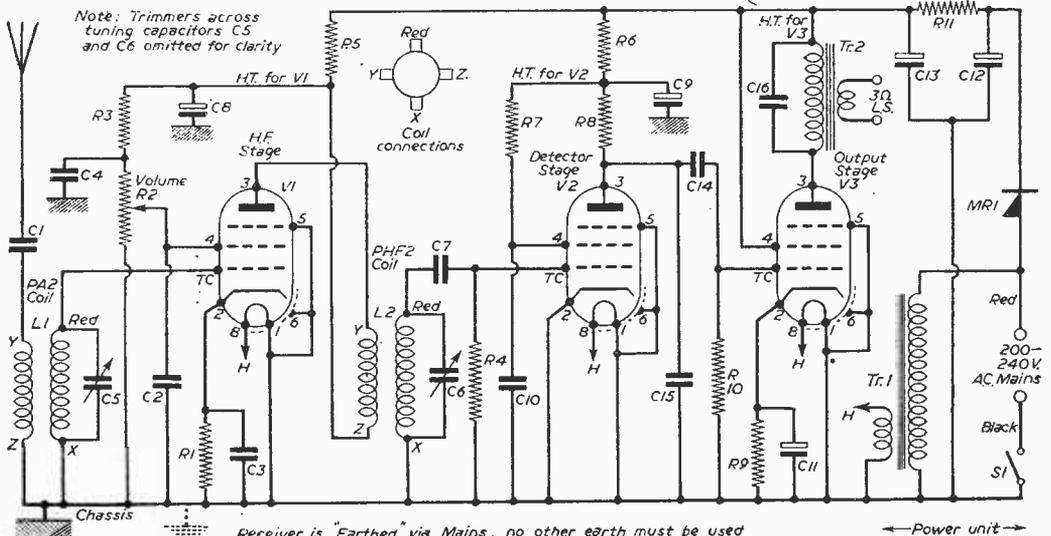


Fig. 22.—The theoretical circuit with this month's additions.

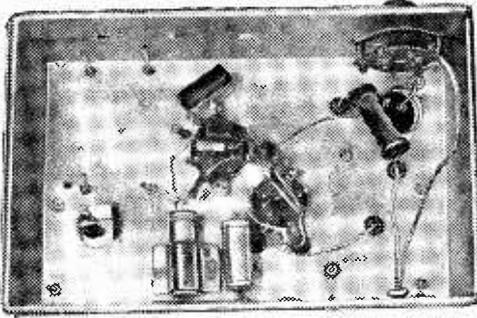

A view of the underside of chassis.

one at a time to receive your weak station at maximum volume. If the radio oscillates as you do this retard R2. With care you will get the station loudest at a certain setting of each trimmer and if each screw is moved the slightest either way the signal should be fainter. If this condition is not obtained you must experiment with one trimmer done up more than the other in the first instance.

All trimming is best done on the aerial it is intended to use with the receiver as the setting of the trimmer on C5 is affected by the capacity of the aerial. The author would like to repeat again that when finished the trimming should be such that a weak station on the high frequency end of the tuning is *peaked with each* trimmer.

(To be continued)

LIST OF PARTS

Here is a complete list of parts, with alternatives and their function in the circuit.

- C1—500 pF mica aerial series condenser fitted to safeguard someone fitting the aerial if the receiver were connected to mains the wrong way round. Incidentally, it will also save PA2 burning out if the aerial hit the gutter, etc., under similar conditions.
- C2—.01 μ F paper; 350 volts working. This is a screen decoupling condenser.
- C3—.01 μ F 350 v. bias condenser.
- C4—.01 μ F 350 v. decoupling condenser (optional, see text).
- C5 and C6—Twin gang 500 pF, each gang fitted with trimmers. Slow-motion drive an advantage. A three-gang may be used with the middle gang not used (one prototype will be seen in the photographs to have a three-gang in use). Insulated knob with sunken grub screws required. These condensers tune the two coil secondaries to the frequency required.
- C7—100 or 120 pF mica or ceramic. This is the grid condenser which stops a charge on the grid of V2 leaking instantaneously to earth via PHF2.
- C8 and C9—A double 8-8 μ F electrolytic condenser. Any value will do which is greater than 8, i.e., a 32-32 μ F will be just as good. The working voltage must be at least 250 v. and for safety order 350 v. condensers.
- C8 decouples with R5 the H.T. for V1, and C9 decouples with R6 the H.T. supply for V2.
- C10—.1 μ F paper 350 v. working, screen decoupling for V2.
- C11—25 μ F (between 12 and 50 is suitable), 25 v. electrolytic condenser. Do not use one with a higher voltage rating. This keeps the bias on V3 grid steady no matter what current is passing across R9.
- C12 and C13—Another double electrolytic, 16-16 μ F or larger, say, 32-32 μ F, 450 v. working. Do not use a lower working voltage than 350 v. C12 is the reservoir condenser for MR1 and C13 is the smoothing condenser working with R11.
- C14—.01 μ F mica or ceramic or Sprague type, 600 v. working. This couples the output from V2 anode to the grid of V3. It must be good or H.T. will get to the grid and ruin V3. Slight leakage would put a wrong bias on V3 grid and cause distortion.
- C15—100 pF mica or ceramic. This gives a H.F. by-pass to earth with practically no path for audio currents. It also helps with modulation hum troubles.
- C16—.01 μ F paper 450 v. working. A top cut capacitor for toning down the high note response of pentodes. It also helps to cut out medium wave heterodyne whistles during the evenings.
- (All resistors are $\frac{1}{2}$ watt unless stated otherwise.)
- R1—1,000 ohms (brown, black, red). This gives a bias on V1 grid. Bias varies with position of R2 as the current through the resistor thus varies.
- R2—1 megohm potentiometer. This is a true potentiometer between H.T. plus and minus. The voltage (and hence the amplification of the valve) on V1 screen grid is thus controlled by the slider.
- R3—220 k. (red, red, yellow), a resistor to stop the grid of V1 connected to R2 slider from becoming too positive. The value given is satisfactory, for greater sensitivity adjust as described later.
- R4—1 megohm (brown, black, green). Grid leak to allow the charge on the control grid of V2 to leak slowly to earth, otherwise the valve would cut off.
- R5—10 k. (brown, black, orange). Decoupling resistor for V1, works in conjunction with C8.
- R6—10 k. Decoupling resistor for V2, works with C9.
- R7—1 megohm. Screen H.T. dropper for V2 to get a suitable voltage on V2 grid for leaky grid detection.
- R8—470 k. (yellow, violet, yellow). Anode load for V2. The detected signal is developed across this resistor.
- R9—330 ohms (orange, orange, brown). Bias resistor for V3. This gives a voltage drop when the valve draws current, thus producing a negative bias for V3 grid (via R10).
- R10—470 k. (yellow, violet, yellow). Grid leak to give the proper bias to control grid of V3 and to stop it acquiring a charge.
- R11—3,000 ohms (5,000 ohms would do), 3 watts or larger wattage. This is the smoothing resistor in the H.T. circuit and works in partnership with C12 13. Large resistors are not usually coded, but if so it is orange, black, red.
- I.1—Wearite PA2 aerial coupling coil and tuned grid coil for V1.
- I.2—Wearite PHF2 anode coupling coil and tuned detector coil for V2.
- V1—SP41 SP61 (that is VR65a/VR65 ex-government) H.F. amplifier.
- V2—Ditto. Leaky grid detector.
- V3—Ditto. L.F. output stage.
- Three bases for the above valves. Mazda Octal. Three top caps to suit.
- TR1—Filament transformer, 4 v. 3 A. or 6 v. 2 A. (see text) from A.C. mains. Standard speaker transformer will do under some conditions.
- TR2—Standard speaker transformer or multi-ratio type (R.C.S.). This provides an anode load for V3 and matches the valve to the speaker.
- MR1—Metal rectifier. Any type supplying 30 mA or more and rated at 240 v. input will do. This rectifies the A.C. input to pulsating D.C., which is received by C12 (H.T.48 is a suitable type).
- SI—Mains on/off switch. Toggle type not suitable. Rotary type with insulated knob is required. One pole one way will do, or two pole one way can be used (see text).
- CHASSIS—See text.
- MAINS LEADS—Two core coloured cable with three pin plug, if possible.
- AERIAL—50 ft. or more for one-valver, 20 ft. or less for ordinary reception with 3 valves.

New Radio Components

DETAILS OF SOME OF THE EXHIBITS SEEN AT THIS YEAR'S R.E.C.M.F. SHOW

MANY of the new radio components which were exhibited at the Radio and Electronic Component Show at Grosvenor House and Park Lane House, London, were smaller, more robust and able to withstand higher temperatures than ever before.

The trend to miniaturise components continues, particularly for those to be used with the very small transistors now being manufactured, and also in connection with printed circuitry.

Components for use in guided weapons need to be sub-miniature, of extreme ruggedness and able to operate in high temperatures. Some of the new transformers and chokes are suitable for working in temperatures up to 200 deg. C. and even 250 deg. C. and there is an exploratory design suitable for 500 deg. C.

Certain components have also been designed to withstand the strong vibration and enormous acceleration due to high "G" values in guided missiles.

Improvements are to be found in even the more stereotyped components such as wafer switches and small relays, both sealed and unsealed.

Developments in ferrites and dust iron cores include the introduction of new materials with new properties, especially for memory devices for computers.



Made for the first time in this country are sintered glass preforms for glass-to-metal seals in hermetically sealed components. These are cheaper, less laborious to use and available with closer tolerances than the glass tubing they replace.

It would not be possible to deal with everything shown at the exhibition, so we pick out here a few of the more interesting items from the point of view of the constructor.

Travelling Wave Tube

The T.W.S.1. shown on page 271 is a convection-cooled travelling wave tube by the

Whiteley
speaker,
Model
HF.1016.

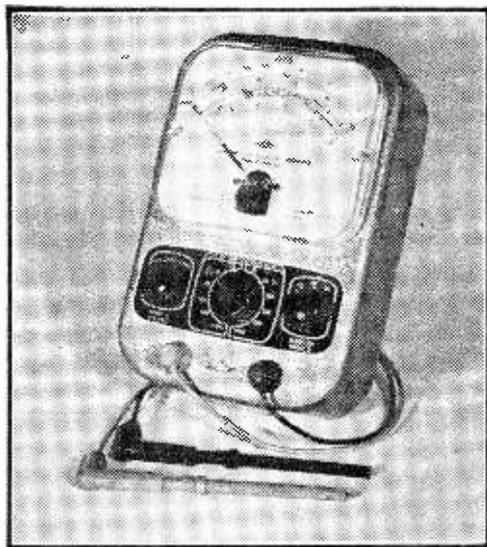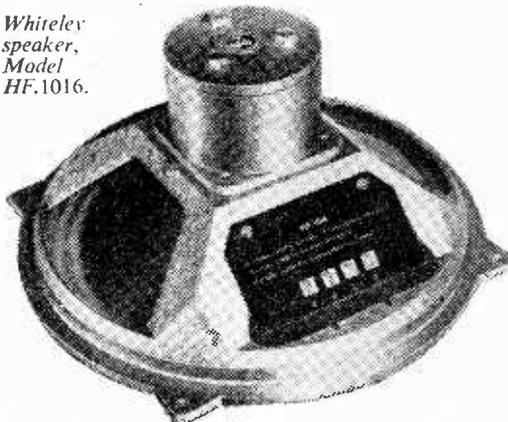


The New Series 100 Test Set by Pullin.

M.O. Valve Co., intended for use in the 1,500 to 3,000 Mc/s frequency range, and suitable for most broad-band amplifier and variable attenuator requirements. The tube is conservatively rated, and an output of 38w can be obtained with a power gain of 26 db.

Series 100 Test Set

The Pullen (Measuring Instruments Ltd.) test set shown above has been redesigned and has the following features:

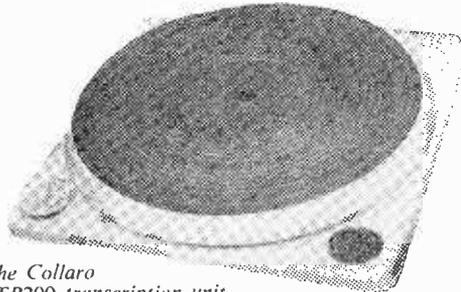
- (i) A new type diakon plastic cover is fitted to the meter, which gives a very wide angle of vision, and good illumination on the dial surface.
- (ii) An increased scale length is possible due to the use of the new cover, and re-arrangement of scales, giving an extra long ohms scale.
- (iii) The test set is fitted with a stand which makes it possible to use an instrument in a horizontal, vertical or an inclined position. This, it



*The Collaro
4TR200 transcription unit.*

will be appreciated, facilitates reading the instrument under difficult lighting conditions. The case has been re-styled in aluminium alloy and a finger recess for carrying is fitted instead of the protruding handle previously used.

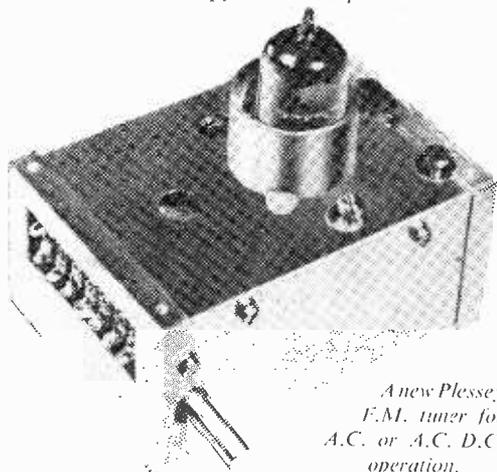(iv) The case is finished grey hammer enamel and an adjustable support is incorporated.



A new Plessey F.M. tuner for A.C. or A.C./D.C. operation.


(v) The meter has a 3in. mean scale length, rectangular pattern with knife edge pointer, 3 ohm scale and a sensitivity of 100 microamps for full scale deflection.

(vi) The test leads have been improved and they are fitted with retractable probes and a swivelling mechanism which enables the leads to be used in any position without risk of damage.

(vii) A special printed circuit has been designed for the majority of the wiring, which gives a much more rugged construction, facilitates service, and enables all components to be accessible when the back cover is removed.



Whiteley V.H.F./F.M. tuner.

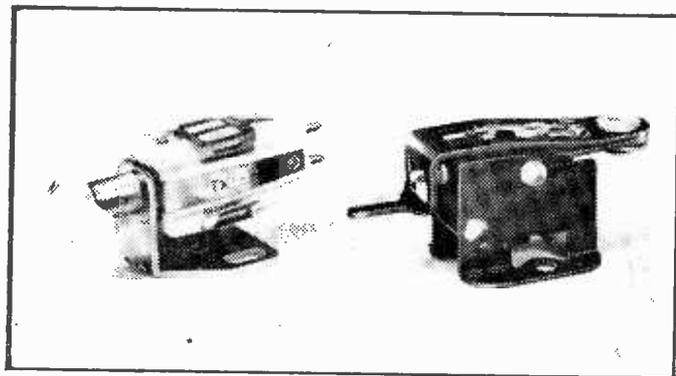


Collaro's TX.38 and a ceramic pick-up.

Whiteley Electrical

Amongst the well-known Whiteley (W.B.) apparatus were the 10in. High Fidelity Loudspeaker (Type HF.1016), incorporating power-fut 16,000 gauss magnet, cambric cone and tapped speech coil, handling capacity 10 watts, frequency response 30-15,000 c.p.s., retail price £8 including tax.

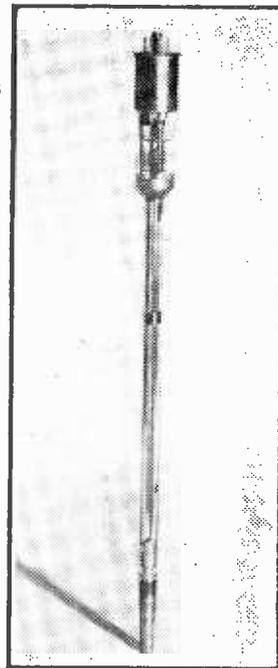Also there was a new model F.M. tuner with a circuit of advanced design. An important feature is the use of printed circuit techniques to ensure maximum electricity stability together with rigid mechanical structure thus ensuring freedom



The Travelling Wave Tube by M.O. Valve Co.

from drift. It is designed to receive frequency modulation signals in the band of 88-108 Mc/s and is therefore suitable for use in most parts of the world.

Plessey F.M. Tuner

Another tuner was shown by the Plessey company. This is for A.C. and A.C./D.C. operation, using a double triode valve as R.F. amplifier and mixer-oscillator. The frequency coverage of this unit is 87 to 101 Mc/s.

Collaro Products

Collaro Ltd. presented their new improved Tape Transcriber Mark IV, which incorporates several modifications to the previous design. Among the new features are the interconnected micro switch and fly-wheel brake. By means of these improvements both motors will be switched off and the fly-wheel instantaneously stopped when the "stop" button is operated. Any one of the six smaller knobs will then start the machine in either direction without subjecting the motors to excessive loading.


A Mains - Battery

THIS receiver was designed to be used by anyone, anywhere, at any time. It is a four-valve superhet using economy valves and readily obtainable cheap batteries. For the above reasons the set was built around an Ever-Ready B.126 90 volt H.T. battery and the popular 1289 4½ volt pocket-lamp battery (7½ volt L.T. batteries are notoriously expensive). The valves used are DK96, frequency changer; DF96, intermediate frequency amplifier; DAF96, detector, A.V.C. and A.F. amplifier; DL96, output pentode; a contact cooled metal rectifier is used for the mains supply together with a VR105/30 voltage stabiliser. Since the main circuit details are reasonably conventional, and therefore the power supply and switching are of more interest the receiver will be dealt with theoretically in two sections, although full practical details will be given.

The power supply section will be dealt with first and the circuit is given on page 274.

Power Supply

The power from the mains is rectified by MR. C8A being the reservoir condenser, R11 the dropper resistor, C88 and the VR105/30 smoothing and stabilising the output at 105 volts. Current from this supply flows through R9, the filament dropping resistor, and A/3, a 500Ω surplus relay, finally returning through a Brimistor type CZ10 and the filament chain if the set is switched on. The CZ10 is included to absorb the filament current, 25 mA, when the set is switched off, the voltage across it then being about 15 volts. With the set running, the voltage across it drops to 9.05 volts, and at this voltage it only passes about 2 mA. The current flowing through A/3 causes it to operate switching A1, 2 and 3 to the mains position. Pin 7 of the DL96 receives the mains supply of 9.05 volts which flows right through to pin 1 of the DK96 and the chassis. From there if S2 (part of the on/off switch) is closed it flows through R6, which provides part of the grid bias for the output valve, and back to the mains. About 1.1 volts is developed across R6 since the H.T. and L.T. currents flow through it on the mains position; also about 5½ volts are dropped across R4 and the first three valves, thus about 6½ volts bias is present for the output

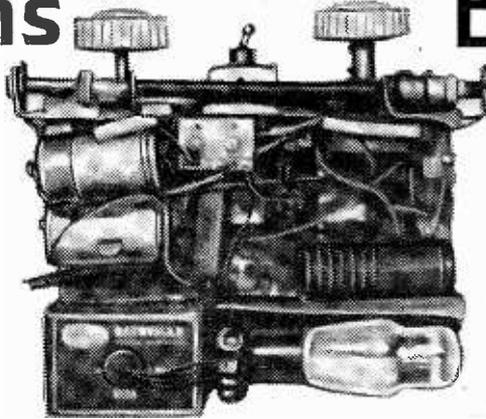

Portable

valve. The H.T. supply on mains is fed through A2 and R8 which drops the voltage to about 85 volts on the H.T. rail. When the mains is switched off or disconnected, the relay A3 is de-energised and A1, 2 and 3 change to battery, connecting pin 7 of the DL96 to chassis and earthing the negative L.T. battery tag through A3 and supplying the H.T. rail with voltage from the H.T. battery. The L.T. current now flows through S1 and is split, one half feeding R4 and the DL96, and the other half feeding the remaining valves in exactly the same way that the mains supply did. Only the output valve changes its working condition in that all the bias is now produced by R6, R13 and R7 carrying the H.T. current. R3 is used to by-pass the cathode current of the DL96 on mains supply, since the anode and screen currents must flow out of the filament and would, unless by-passed, overload the other valves. Similarly R5 by-passes the current from the DF96. The DAF96 cathode current is only about 0.1 mA and may safely be neglected. R2 by-passes the cathode current of the first section of the DL96 and the current through R1 on mains. On battery R1 and R2 are in parallel and by-pass the cathode current of the second section

An A.C./D.C. Set With Stabilised Power Supply
Enabling it to be Plugged in Anywhere Without
Adjustment Where 200-250 Volt Mains Exist.
Also Containing Automatic Switch-over from
Mains to Battery if the Power is Cut Off.

By G. Keating

which, it will be remembered, comes first on battery operation, because the current flow through the filament of this valve is reversed. As a result of these resistors the voltage is maintained at 1.3 volts per section on mains operation and is no greater than 1.5 volts per section on battery which is the operating conditions recommended by the manufacturers. The stabilised power supply ensures that the operating voltages are always correct whenever the set is operated from A.C./D.C. mains between 200 and 250 volts. If the supply voltage is below 200 volts at peak demand times then the stabiliser may flicker on and off, in which case R11 should be reduced in value to, say, 2 KΩ (a 15k 1w resistor connected in parallel, will achieve this temporarily). This can also be used when the rectifier falls in efficiency after very prolonged use. The relay deserves special mention, it is of 500Ω resistance and it closes at about 12 mA, so the 25 mA filament current is more than sufficient for reliable

operation. The original had a two-pole change-over switch, only fitted, so a bolt was mounted on the chassis in such a position that the armature just made contact with it when the relay was de-energised. As the mounting bracket was already insulated from the frame a wire from the frame to the negative terminal of the

for simplicity. Consequently it is wiser to wire in all components in Fig. 1 first, before wiring in the additional ones in Fig. 2. The signal is picked up by a dual wave Ferrite rod aerial tuned by C9A and applied to G3 of V1. The oscillator section of this valve is a conventional series fed, grid

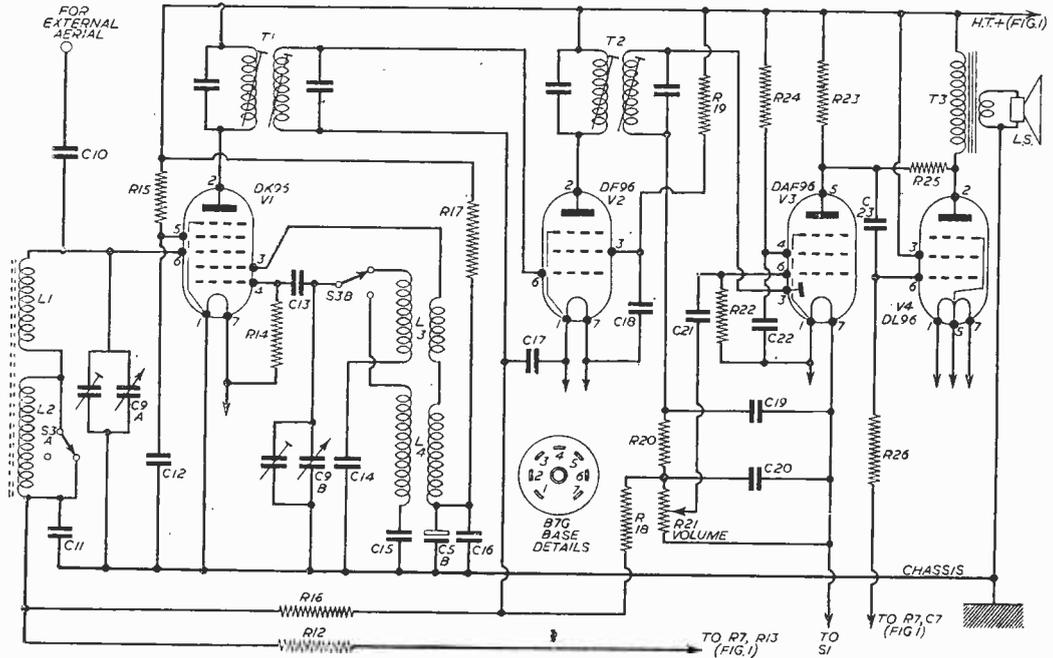


Fig. 2.—The receiver circuit. The mains section is shown on page 274.

L.T. battery provided contact A3. Of course, if a relay with a three-pole change-over switch was obtained, this modification would not be necessary. Any relay will do providing it will operate firmly and reliably on 25 mA. The value of R9 should be altered so that R9 and the relay A/3 total 3.4 KΩ resistance.

The Circuit

The remainder of the set will now be described and Fig. 2 gives the circuit diagram of this part. It should be noticed that most of the components already detailed in the power supply section will be omitted from Fig. 2

tuned circuit with separate coils for medium and long waves.

It will be observed that both the oscillator coupling windings are in series with the medium-wave section nearest to G2, the oscillator anode.

COMPONENTS FOR FIGURE 2

- * C5A—50 μF 150 v. }
- C5B—50 μF 150 v. } in the same can
- C9A) 500 pF twin gang midget
- C9B) with trimmers (2½ x 1½ x 2in.)
- C10—5 pF silver mica or ceramic
- C11—0.1 μF 150 v.
- C12—0.1 μF 150 v.
- C13—100 pF silver mica
- C14—470 pF silver mica
- C15—150 pF silver mica
- C16—0.1 μF 150 v.
- C17—0.1 μF 150 v.
- C18—0.1 μF 150 v.
- C19—100 pF ceramic
- C20—100 pF ceramic
- C21—10,000 pF ceramic
- C22—0.1 μF 150 v
- C23—10,000 pF ceramic
- R12—10 MΩ
- * R13—100 Ω
- R14—27 KΩ
- R15—100 KΩ
- R16—10 MΩ
- R17—27 KΩ
- R18—10 MΩ
- R19—39 KΩ
- R20—47 KΩ
- R21—2 MΩ volume control (with double pole switch)*
- R22—10 MΩ
- R23—2.2 MΩ
- R24—10 MΩ
- R25—15 MΩ
- R26—10 MΩ
- T1 and T2—Pair slug tuned midget HT's, 13/16 x 13/16 x 2in. maximum.
- T3—Radiospares miniature output transformer
- L1) Dual wave Ferrite rod aerial (Teletron used in
- L2) original but any should do). 8 x 5/16in.
- L3—Osmor QO8
- L4—Osmor QO9
- S3A) D.P. D.T. toggle switch
- S3B)
- L.S.—3 Ω loudspeaker (original was 5in. Celestion but a 7 x 4in. elliptical would suit). A high flux density type is strongly recommended.
- * See Fig. 1.

Because of this the coils should not be mounted too close together as mutual coupling will make adjustment of one coil core affect the other. With the layouts given, however, the coils are virtually completely independent of each other. C14 and C15 are the medium and long wave padding condensers; these particularly must be silver mica. It is desirable that all the condensers marked in

to the I.F. amplifier V2 and then through T2 to the detector, V3. It is rectified by the diode section and the audio voltage, having been freed from I.F. voltages by the filter R20, C19 and C20, is developed across the volume control R21. A 2 M Ω component was used in the original but 1 M Ω would be quite satisfactory if easier to obtain. The audio voltage is taken from

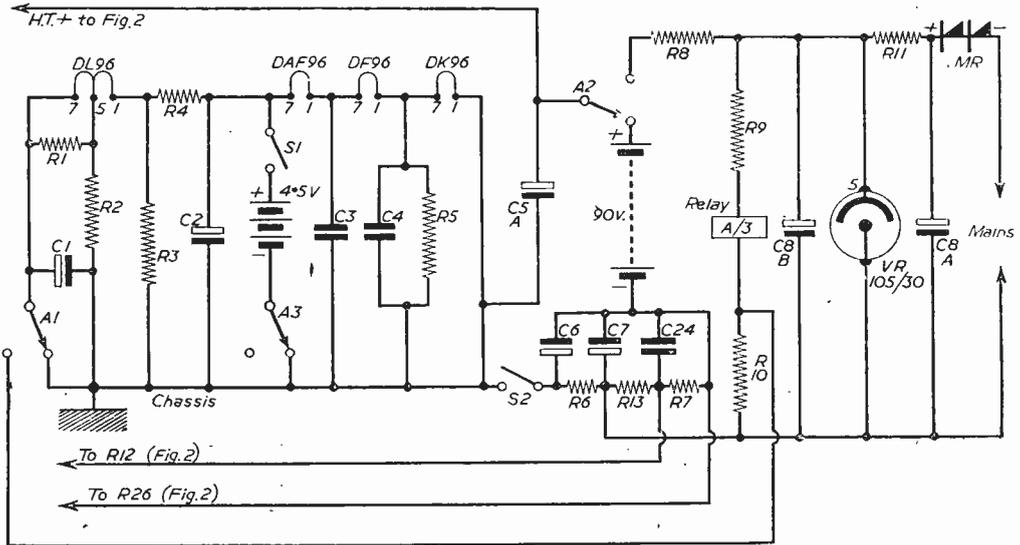


Fig. 1.—The power supply circuit.

the components list should be silver mica also. The reason for this is that ceramic condensers have a fairly large negative temperature coefficient, and since the set gets fairly warm when used from the mains these will cause serious and prolonged tuning drift. You have been warned! Moulded mica condensers are mostly unsatisfactory, solely because of their size. To continue with the circuit; the signal is now fed through T1 the first I.F. transformer at 465 kc/s,

the slider of R21 and fed through C21 to G1, the signal grid of V3. R22 is the grid leak, and R23 the anode load. From the anode of V3 the signal is fed through C23 to the output valve V4. The output transformer matches to a 3 Ω speaker and R25 provides sufficient negative feedback to reduce the distortion produced in the output valve. The tone has been found to be quite good although the high Q coils, which give excellent selectivity, naturally reduce the

COMPONENTS FOR FIGURE 1

- R1—680 Ω
 R2—2.2 K Ω
 R3—2.7 K Ω
 R4—56 Ω
 R5—680 Ω
 R6—33 Ω
 R7—560 Ω
 R8—2.2 K Ω
 †R9—2.5 K Ω 5 w. wire wound †390 Ω 1/2 w.
 R10—CZ10 Brimistor
 R11—2.5 K Ω 10 w. wire wound
 R13—100 Ω
 C1—25 μ F 25 v. (BEC, CE200)
 C2—25 μ F 25 v. (BEC, CE200)
 C3—0.1 μ F 150 v.
 C4—0.1 μ F 150 v.
 C5A—50 μ F 150 v. }
 *C5B—50 μ F 150 v. } in the same can
 C6—25 μ F 25 v. (BEC, CE200)
 C7—25 μ F 25 v. (BEC, CE200)
 C8A—8 μ F 275 v. }
 CB8—8 μ F 275 v. } in the same can

C24—0.1 μ F 150 v.

S1 and S2 ganged with volume control (R21)*

A/3 500 Ω relay (see text)

MR Electricx contact cooled 250 v. 85 mA half wave metal rectifier

† Two resistors in series

* See Fig. 2.

SUNDRY COMPONENTS


- 4 B7G valve holders
 Octal valveholder
 1 J.B. cord drive, standard type No. 4,690
 1 J.B. dial drum, 2 1/2 in. No. 4,030
 1 cord tensioning spring, No. 4,587
 2 tool clips
 1 plug to suit B.126, 3 pin
 Various nuts and bolts (mostly 6 B.A.)
 2 knobs to taste (original were A713 1 1/2 in. white, engraved "Vol/On-Off" and "Tuning")
 1 sheet of aluminium, 8 x 13 in. for main chassis
 Miscellaneous pieces for screens, mounting brackets, etc.
 Wire, solder, nylon drive cord, small pulley

treble response. As some people may prefer a further reduction in treble (what is usually called a mellow tone), it will not be amiss to show how this can be achieved. R25 the negative feedback resistor is omitted and a fixed condenser is wired across the primary of the output transformer. Another 10,000 pF ceramic

auxiliary outside aerial is used, and to minimise variations in volume, caused by the marked directive properties of a Ferrite rod aerial, when the set is being carried as a portable. The negative bias point referred to earlier is obtained from the bias supply for the output valve and is arranged to be the same on both battery and mains. (On mains it is the full mains bias, on battery it is just part of the full bias.)

Constructional Details

As every theoretical detail has been exhaustively dealt with the practical layout and dimensions will now be given. Despite all the refinements incorporated, it is remarkably compact; the measurements of the chassis being 8in. X 6in. X 5in., which includes both batteries and a 5in. loudspeaker; in fact everything except the cabinet and knobs. The chassis is made from sheet aluminium, as ready-made chassis are costly, and the wrong shape. The front panel

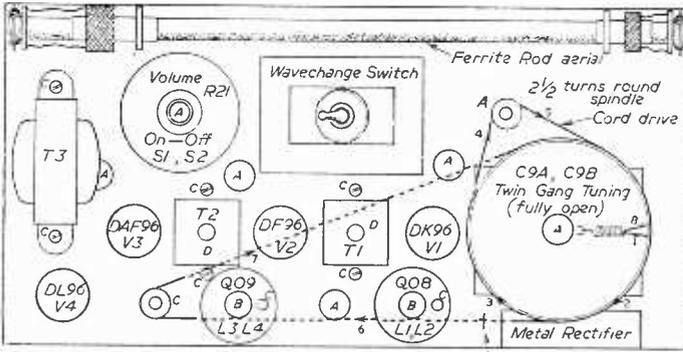

Panel drilling hole sizes
 A 3/8" dia. B... 5/16" dia C 1/8" dia. D. 13/16" square Valve holes 5/8" dia.
 Pointer (limit of travel 3 1/2")


Fig. 3.—Plan layout of the portable.

will probably be found suitable, although the value may be varied to suit individual taste. Since the bass response can be surprisingly good for this type of set, a 5in. loudspeaker of good quality is recommended. A high flux density speaker has the supreme advantage of giving more volume from the limited output power, and is strongly recommended. Cheap and midget speakers will be found disappointing from the point of view of both tone and volume. The A.V.C. system is a little unusual in that it consists of a potentiometer network between the positive filament pin of V3, and a negative bias point of approximately -1.2 volts to chassis. Three 10 MΩ resistors R18, R16 and R12 divide the majority of the standing voltage of 5.1 volts into three equal parts (the volume control divides a little but the amount is small). Thus at the junction of R12 and R16 the potential is about +0.5 volts to chassis and at the junction of R16 and R18 the potential is about +2.1 volts. These points are thus at about the same voltage as the middle of the filaments of V1 and V2 respectively and are thus suitable for the A.V.C. feed. Owing to this potentiometer, only one-third of the control bias is applied to V1 and only two-thirds to V2. Another useful feature is that about 1 volt delay exists owing to the biases being about mid filament potential and not negative filament potential. This stops weak signals decreasing the gain and improves sensitivity. A.V.C. is provided to stop strong signals from overloading the set if an


forms the basis of the set and carries almost all of the components. Slow-motion tuning and a dial are included.

No detailed layout diagram can be given owing to the extremely compact wiring, but the layout of all the larger components such as valves, tuning condensers, transformers, and controls will be given.

(To be continued)

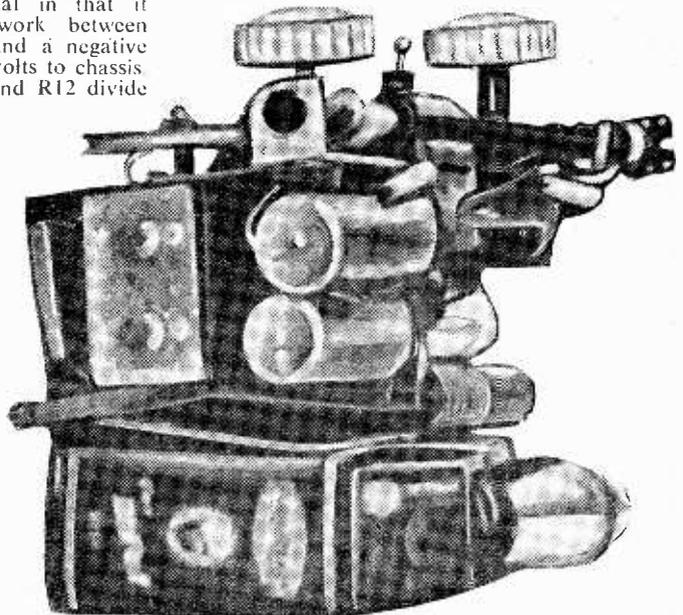

A general view of the set.

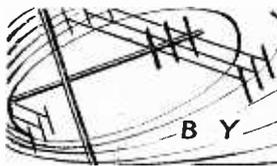

On Your Wavelength

BY THERMION

"Arrangements"

HAVE you ever noticed the high proportion of "arrangements" pumped into the ether by ersatz musicians today? A composer writes a piece of music and immediately someone wishes to "arrange" it, so that it sounds nothing like what the composer intended. Some of those who do the arranging are not genuine musicians and could not compose music. Music should be played as the composer wrote it. So many of these quack musicians batten on like limpets and barnacles to other people's work. The arrangement usually consists of a complete mutilation of the score so that the original theme is unrecognisable. Liszt was one of the pioneers of the arranging racket. He arranged a large number of other people's compositions. This is a form of musical piracy. If so-called musicians feel they are able to arrange, let them compose and arrange their own music.

The Voice of America

THE VOICE OF AMERICA HAM SHOW is heard weekly on Tuesdays at 4 p.m. Eastern Standard Time (2100 G.M.T.) and is directed to audiences behind the Iron Curtain. It is a 12-minute segment of the regular English language 30-minute programme called "Report from America" which is broadcast daily. As readers know, The Voice of America Programmes in Russian and other Iron Curtain languages are severely jammed, but broadcasts in English are free from jamming. Since English is the second language of a substantial part of the audience which The Voice of America is trying to reach, these broadcasts are regarded by the American authorities as extremely important. The commentator for Voice of America is Bill Leonard.

Three Exhibitions in One Week

IN April, no less than three comparatively small exhibitions were held on one week—the Radio Components Show, the London Audio Fair, and the Instruments, Electronics and Automation Exhibition. None of the industries which these three exhibitions represent is large enough to promote an exhibition on a national scale, with the possible exception of the last which held its show at the Olympia. The Radio Components Show was held in two parts at Grosvenor House and Park Lane House, London, and the London Audio Fair at the Waldorf Hotel. I still think that these exhibitions should be held under the same roof as the National Radio Exhibition at Earls Court. Each of the three industries represented are only component parts of a major industry. I know that they are more or less trade shows, but that is no reason why the public should not be permitted to examine the exhibits.

Luxembourg and Religion

I OBSERVE that the perfervid tub thumping, religious programmes are still being injected into the ether for five nights a week on 208 metres between the hours of 11 p.m. and midnight. There are usually four programmes of a quarter an hour every evening, and in all of them we are told what miserable sinners we are, backed up by lashings of miscellaneous and unrelated quotations from the Bible. All of these programmes emanate from America, where religion has become big business. They do not teach it—they sell it. The thinly-veiled appeals for sacrificial letters from listeners must bring in a large amount of money. You are offered free copies of periodicals and booklets. One such periodical is before me now. In it is a column on how to make your will. It includes the line "to the . . . organisation" just to make quite sure that you do not forget them when you die. There is a religious mania in America, and there are blatant advertisements in the newspapers. One religious quack advertises "For one dollar you will receive a guaranteed blessing within 48 hours." Steps are, I am glad to note, being taken to investigate some of these religious organisations, many of which are run by people who have had no religious training. Unfortunately, under the American constitution laid down by Abraham Lincoln, no law can be made which restricts religion in any way. Of course, Radio Luxembourg is a commercial station and the money of a religious organisation is as good as anybody else's. I recommend you to listen to some of these broadcasts and see if you agree with me. They do not ring true.

In America anyone can set himself up as an evangelist and millions of unthinking people may regard him as a trained parson. Some of these people are undoubtedly just making a business of it, and it seems a pity that they are aided in their efforts by being permitted to purchase programme time. Fortunately, it could not happen over here, but the ether knows no boundaries and large numbers of people do listen in to these foreign broadcasts. It is a thousand pities that our own Archbishop of Canterbury should have lent support to this form of insincere hot-gospeiling and, in view of the exposures of this religious quackery which have taken place in the American papers, I hope he is wiser now.

AMPLIFIERS: Design and Construction

17/6, or 18/6 by post from:

GEO. NEWNES LTD., Tower House, Southampton Street, Strand, London, W.C.2.

Speaking for BRITAIN

What does Operation Britain mean to us?



AT HOME AND ABROAD, too little is known or even remembered of the active part that Britain plays today. We feel it. We believe in it. But is this enough?

For what is Britain? She is neither more nor less than we, her people, make her. She is our united efforts; she is our pride; she is our energy, our wisdom and our talents.

Our fathers made her past, and our children will make her future. It is up to us to make her present, building on past achievements a foundation for that future. This means action—now, and by every single one of us.

Ours is a vital nation: and it is to tell of this vitality that we have formed Operation Britain, gathering together eminent men from

all parts of British life—experts in their own field of activity: labour, management, government—united by their belief in Britain's future.

At home, we must look beyond our British understatements, and seeing our real strength, build to greater strength. Abroad we must ensure that our achievements are assessed at their real worth to the world and the world's future.


Ours is a heritage no longer bounded by the seas: ours is a vital role in world affairs. It is only by knowing this, each one of us, aware of our real ability, that we can build towards the future that is our birthright—the world's birthright—a future that is bright with promise.

This is an "Operation Britain" Organisation advertisement

Write for details of corporate and individual membership of the organisation to:—

THE OPERATION BRITAIN ORGANISATION • 165 FLEET STREET LONDON EC4 • FLEET STREET 5011

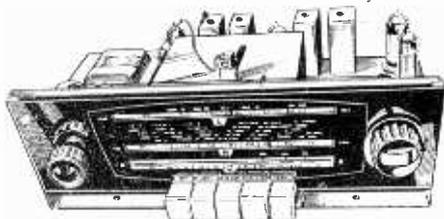WONDERFUL OFFER OF A.M.-F.M. CHASSIS BY FAMOUS MANUFACTURER



Why buy a F.M. Tuner at the same price?
 Only 150 available at £12.12.0 (P. & P. 8/-). UNUSED.
 Tapped input 200-225 v. and 226-250 v. A.C. ONLY.
 Chassis size 15" x 6 1/2" x 5 1/4" high: 7" x 4" Elliptical speaker included.
 Dial 14 1/2" x 4" in gold, red and deep brown.
 Pick-up, Extension speaker, Ae., E., and Dipole sockets.
 Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram.
 Covers 1,000-1,900 M.; 200-550 M.; 88-108 Mc/s.
 Aligned and tested. With all valves.
 Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85.
WORTH TWICE THE PRICE. Terms available. Cabinet to fit, polished, with back, 47/6.

HIGH GAIN BAND 3 T.V. CONVERTERS

NO ALTERATIONS REQUIRED TO YOUR SET
 RETURN OF POST SERVICE. All new goods.

Posted orders to Camberley, please. 3/- each extra post (4/- for 2). 2/- extra C.O.D.

Full instructions supplied. Can be fitted in 10 mins.; free from drift; fitted with co-axial plug; fully wired ready for use; with power pack, including metal rectifier; double wound transformer; 2 valves; mains on-off switch; fine tuner; B.B.C. to I.T.A. at turn of switch; 12 months' guarantee (B.V.A. valves 90 days). Terms available, one-third down and balance plus 7/6 in four equal monthly payments; postage with first payment. FOR ALL SETS EXCEPT EARLY PHILIPS.


AUTOMATIC RECORD CHANGERS are in short supply. Collaro CONQUEST turnover crystal pick-up, 4-speed mixer. A.C. mains 200-250 v., see illus. ALSO Collaro single player AC4/564, turnover crystal, pick-up with "T" head. £6/16 6 (3/6 p. & p.).



£8/10.0 (5/- p. & p.)

13 CHANNEL CONVERTER

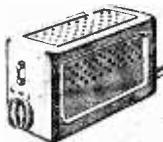Switch positions, off-I.T.A.-B.B.C. Valves PCF80 and PCC84. Moulded cabinet 8 1/2 in. x 4 1/2 in. x 6 in. Don't confuse with similar article being offered without power pack.



£5.5.0

Robust Band 3 AERIALS, for 1 in. to 2 in. diam. mast or for loft. 3-element, 27 -; 5-element, 35 -; 9-element, 55 -; carr. paid. Low Loss Co-Axial Cable, 8d. yard.

BATTERY ELIMINATOR for 4 LOW CONSUMPTION VALVES. 90 v. 20 mA. and 1.4 v. 250 mA., 35 - 42.6 p. & p.; 200-250 v. A.C. (size 5 1/2 in. x 3 1/2 in. x 2 in.).

GLADSTONE RADIO

82B, High Street, Camberley, Surrey. and 3, Church Road, Redfield, Bristol. Tel. 51207.

SOLDERING EQUIPMENT



PRECISION SOLDERING INSTRUMENTS for the ELECTRONICS INDUSTRY

- Comprehensive range
- Robust & Reliable
- Light weight
- Rapid heating
- Bit sizes 3/32 in. to 3/8 in.
- All voltage ranges 6/Tv. to 230 250v.
- Prices from 19/6

Illustrated is the 25w. 3/16 in. replaceable bit model with safety shield.

British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.10 sent free on request. Sole proprietors and manufacturers:


LIGHT SOLDERING DEVELOPMENTS LIMITED

106 George Street, Croydon, Surrey.
 Phone: CROYdon 8589 Grams: Litesold Croydon



Here's the new Handyman Workbench even better than before!

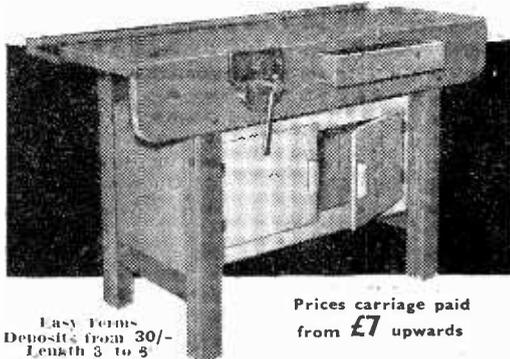As demonstrated on B.B.C. T.V.—now complete in every detail. Spacious tool cupboard, flush fitting drawer, "Woden" Bench Stop and Holdfast are obtainable as additional extras to the standard model. Made in solid hardwood throughout. Also latest model "Woden" Quick Release Woodworkers Vice type A.120 fitted as illustrated.



Easy Terms
 Deposits from 30/-
 Length 3 to 5

Prices carriage paid
 from £7 upwards

To: J. POWELL & SON LTD. (Dept. C)
 Pensnett, Brierley Hill, Staffs. Phone: Kingswinford 3036.
 Please forward illustrated folder and comprehensive price list.

NAME

ADDRESS

TRANSISTORS

in Practice

7.—AUDIO OUTPUT STAGES

By R. Hindle

(Continued from page 197, May issue)

THE receiver so far described will provide only low power output and the addition of an extra transistor in front of the circuit does not add to the power that the last transistor is capable of giving. The next development will be a power stage so that a speaker can be driven.

It will be realised that the variable resistor can no longer provide reaction because the secondary winding is no longer connected. It still has the effect of adjusting the working point of the detector transistor and it should be adjusted for best signal.

The neutralising winding of the inter-transistor coil must be connected the right way round or else instead of reducing the effective back coupling it will increase it. If the circuit is unstable, therefore, it could be that the coil connections are reversed and the first thing to try is the changing over of the two leads going to the neutralising winding. It may be found with some transistors that the amount of feedback without neutralising capacitor is insufficient to cause instability. Should this be so, the neutralising capacitor could be omitted and the winding once more connected for reaction, to give somewhat more gain. These are experiments that can be tried but it is suggested that in the first place the chassis should be made to work with the circuit as specified.

A series of batteries has been developed especially for transistor operation. The rather untidy hook-up used in the early stages of the development of this design has now given way to one of these neat and compact sources of power. Press-stud connectors are used for connecting to this battery, which is an Ever Ready type PP1, and as the studs are of different types it is impossible to reverse the connections. The type quoted is only 2½ in. × 2 in. × 2 in. and it provides 6 volts as needed for this design.

Do not forget, whilst working on this chassis after completion, that a transistor is wired into it, and take appropriate precautions when making any modifications to prevent heat from damaging the transistor.

It has already been pointed out that a transistor stage is always fundamentally a power amplifying stage. Each stage is driven by current, which involves the provision of power at the input stage and not merely a voltage as is the case with a valve, and it gives an amplified power version at its output suitable for driving a subsequent transistor stage. Inter-stage coupling is arranged for optimum power transfer rather than for optimum voltage transfer.

Whereas in a multistage valve amplifier all stages right up to the output stage require only low dissipation circuits (assuming Class A working; the driver stage of a Class B valve amplifier is more like the transistor case) a multistage transistor amplifier can be expected to be designed for successively greater dissipation stage by stage towards the output. This was seen in the two-stage audio amplifying circuit described in this series. The present purpose, however, is to deal with the final stage of the transistor amplifier—that which has the job of driving the loudspeaker.

As with valves, transistors can be operated in Class A, in which case the base bias is set so that the quiescent operating conditions (i.e., without a signal applied) are midway along the straight part of the collector characteristic, or in Class B in which case the transistor is biased back so that the quiescent state collector current is negligibly small. The Class A condition gives amplification with comparatively little distortion and either single output transistors or push-pull circuits can be operated in Class A. Class B, on the other hand, is fundamentally a distorting amplifier—in fact, a theoretically perfect Class B amplifier (if such were possible) would amplify only one half-cycle and would cut off the other half-cycle—and so for the purposes of audio operation two Class B transistors must be operated in push-pull, each amplifying one half-cycle only, but when the two outputs are combined in the output transformer there is, in effect, an amplified signal following both half-cycles of the input signal.

Class A

The maximum theoretical efficiency of a Class A stage in the case of either valves or transistors, is 50 per cent.; that means that no more than half the power drawn from the valve H.T. or transistor battery supply can be converted into an audio signal and any attempt to increase the drive beyond this

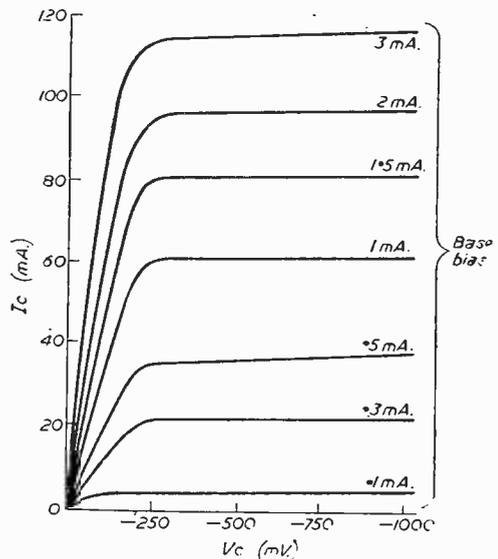


Fig. 39.—Low voltage collector characteristic—OC72.

point merely introduces distortion without increase of output. This may not seem so good, but in practice even such efficiency cannot be attained. The maximum of 50 per cent. efficiency involves three impossible assumptions:

1. That there is no loss in the collector load, i.e., that the voltage drop in the load under D.C. conditions is nil. This requires a transformer having a primary that has sufficient inductance for the purposes of loading the transistor but with zero D.C. resistance. This is impossible, of course, but fortunately the primary inductance needed by a

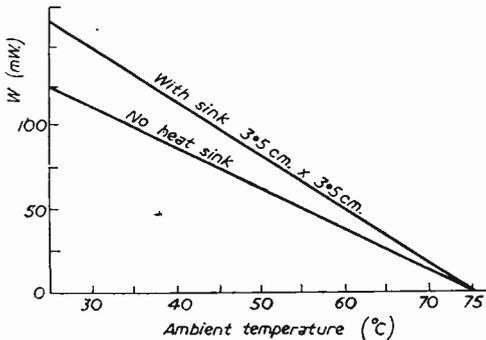


Fig. 40.—Dissipation characteristic—OC72.

transistor for a given frequency range is comparatively small and so it can be wound in a small volume and with low resistance.

2. That the transistor can be operated down to zero collector current. This cannot be so, either. There is a minimum level below which collector current cannot fall and this level is subject to variation with junction temperature; this minimum has been referred to before in this series and is known as $I_c(0)$.

3. That the transistor can be operated with a collector swing down to zero volts. An attempt to do this could run into gross nonlinearity, and consequently severe distortion, because the transistor current gain falls off rapidly as collector voltages fall at the lower end of the characteristic.

Fortunately, with regard to 2 and 3, the transistor can operate down to quite low collector currents and voltages and so, in fact, efficiencies reasonably close to the theoretical maximum can be achieved.

There are two possible approaches to the design of a Class A amplifier. Either the need is for the maximum power output that can be obtained from a small transistor of limited permissible dissipation or else the transistor is more liberally rated for the purpose in hand, in which case the choice of power output rests with the designer who can determine the power by the circuit constants. The object of the exercise, in both cases, is to adjust the base bias current until the appropriate collector current is obtained.

Taking the idealised case of a transistor in Class A giving the theoretical optimum efficiency of 50 per cent., and fearing in mind that the maximum dissipation of power in a Class A circuit takes place in the no signal, or quiescent, condition, it follows from the definition that the power output obtained will be a half of that dissipation. So, if the intention is to get the maximum audio from a given transistor, signal conditions can be put aside temporarily and

the D.C. conditions computed from the standard formula for power, i.e.:

$$W = I_c E$$

where W is the maximum dissipation, I_c is the collector current and E is the applied battery voltage. The unknown is, of course, I_c so by manipulation of the equation:

$$I_c = \frac{W}{E}$$

If, on the other hand, the limiting factor is the power needed and not the permissible maximum dissipation, the first thing to do is to convert this audio power figure into a dissipation figure, which as above simply means multiplying by two. Then the same formula applies, i.e.

$$I_c = \frac{2P_L}{E}$$

P_L being the maximum audio power required in the load resistance.

In practice, allowance has to be made for the deviations from theoretical maximum efficiency. This has the effect of reducing the audio power that can be drawn as has been stated, due to the fact that the collector cannot swing to zero volts. This requires that the quiescent collector current must be set somewhat higher than was previously indicated if the transistor is to operate about the middle of its characteristic and the new I_c is found by reducing the factor E used in the above equation by an amount equivalent to the forbidden "territory" of collector voltage caused by curvature of the characteristic. It is wise to err on the safe side here, so commonly a half a volt has to be allowed for. Thus the equation for quiescent collector current becomes

$$I_c = \frac{2P_L}{E - 0.5}$$

This increase in I_c is strictly necessary only if it is intended to operate the transistor over the whole of the straight part of the characteristic. If the transistor is to be operated well within its rating it is not likely to swing so far as the curved regions and so the adjustment need not be considered.

This does not really help the man aiming at the maximum power from his transistor, however. He must still begin his calculation from the maximum dissipation point of view which, of course, still involves the total voltage applied so again he must use

$$I_c = \frac{W}{E}$$

By equating these two alternative ways of defining I_c it can be seen to what extent power output in practice falls short of 50 per cent., i.e.,

$$\begin{aligned} \frac{2P_L}{E - 0.5} &= \frac{W}{E} \quad (= I_c) \\ 2P_L \cdot E &= W(E - 0.5W) \\ P_L &= W \frac{(E - 0.5)}{2E} \\ &= \frac{(E - 0.5)}{E} \quad 50\% \text{ of } W. \end{aligned}$$

The effective drop in efficiency from the theoretical maximum is thus less significant the higher the voltage applied and so it is clearly better to increase the audio power output taken from a transistor by increasing the voltage applied rather than by increasing the current drawn from the same voltage source.

Let us try some examples:—

If a $1\frac{1}{2}$ volt source were to be used the efficiency

when maximum power permissible is being drawn from a single transistor in Class A will be:—

$$P_L = \frac{1}{1.5} \cdot 50\% = 33\% \text{ of } W.$$

If a 6 volt system is in mind, such as the power supply used for the receiver developed in this series, or a car battery in the 6 volt range

$$P_L = \frac{5.5}{6} \cdot 50\% = 46\% \text{ of } W.$$

A 12 volt car system would provide only slightly higher efficiency though, of course, the current drawn would be halved because the voltage is doubled for the same dissipation. Actually

$$P_L = \frac{11.5}{12} \cdot 50\% = 48\% \text{ of } W.$$

Above, $\frac{1}{2}$ -volt was quoted as a safe limit of swing of the collector voltage, and to support this Fig. 39 gives the collector characteristic of the OC72 at low voltages. It will be seen that this limit errs on the side of safety so far as this transistor is concerned. Fig. 40 is given to show how dissipation varies with ambient temperature. It will be seen that at 75 deg. C. no collector current can be allowed because this is the limit of junction temperature and any dissipation would raise the junction temperature higher than ambient temperature. When ambient temperature is lower, the permissible dissipation is that which will raise the junction temperature to the limit. The curves illustrate the effect of fitting the transistor on to a small heat sink.

Circuit for Transistor Output Stage

The circuit of a Class A output stage is given in Fig. 41.

Now can be seen an additional cause of loss of supply voltage. This is the drop across the resistance in the emitter circuit. This resistance, and the transformer primary resistance, are generally arranged to drop around one volt, this being satisfactory from the point of view of stabilisation.

Variation in Supply Voltage

What has one to do about the variation in voltage that is bound to occur when a battery supply is used? Dry batteries lose voltage whilst in use but in the interests of economy they have to be used for a reasonable period of time. In the case of a car radio the accumulator may drop below the nominal value and also it will rise under charge, and the radio is likely to be used under either circumstance.

The method of approach again depends on whether the maximum possible output from a given transistor is needed or whether a predetermined output from a conservatively rated transistor is aimed at. In the case of a receiver operating from a dry battery the former is likely to be the case. The procedure is then to calculate the collector current for the maximum permissible dissipation at the peak battery voltage and one can do no more than tolerate the fall in dissipation—and of power output—until compelled by the inadequacy of results to replace the battery.

The car radio case is likely to take the alternative line. Very likely the transistor will be capable of giving more power output than it is decided to use (after all one does not take more out of the electrical system than necessary), so the thing to do is to calculate the collector current for the minimum output audio power likely to be acceptable at the lowest voltage likely to be encountered. An output of two

watts is reasonable, and a 12 volt system is not likely to fall below 11 volts at times when the radio is in use. Then, allowing half a volt for curvature of the characteristic and one volt voltage drop in the series resistance:—

$$I_c = \frac{2 \cdot 2}{10 \cdot 05} = .42 \text{ amps.}$$

and the base bias would have to be adjusted to give this value of collector current. This indicates a dissipation of $10 \cdot 42$, or 4.2 watts. The transistor chosen would have to be rated for a much higher dissipation than this, however, because the battery under charge when the car is running is likely to reach

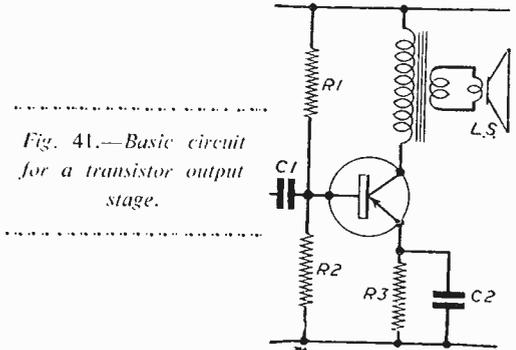


Fig. 41.—Basic circuit for a transistor output stage.

a voltage of 14. The base bias will increase in proportion as it is drawn from the same supply and will cause a similar increase in collector current. So now

$$I_c = \frac{.42 \cdot 13}{10} = .55 \text{ amps.}$$

and the dissipation $W = .55 \cdot 13 = 7.15$ watts.

This has been worked out allowing for the drop of voltage in the emitter lead, but without taking into account the effect of the stabilising circuits on the base current. Without such stabilisation it appears that a transistor capable of a dissipation about four times the audio power required must be used for a range of voltage supply to be expected in a car radio. Allowing for normal stabilisation things are not quite so bad, but even then a permissible dissipation three times the audio power acceptable as a minimum is desirable.

Load Resistance

The load to be applied to the transistor can be estimated, assuming the ideal transistor characteristics, which is near enough for the purpose, from the simple relationship of battery supply voltage and power output for which the circuit has been set up. Thus,

$$R_L = \frac{E}{I_c}$$

where E is the battery supply voltage and I_c is collector current. But as above

$$I_c = \frac{\frac{1}{2} P_{out}}{E}$$

so by substitution

$$R_L = \frac{E^2}{2 P_{out}}$$

From this it is interesting to compute the circumstances under which the normal speaker impedances of 3 ohms and 15 ohms match the transistor directly without a transformer. The 3 ohm speaker is not likely to be much use for domestic or car radio with-

out transformer because at a power supply of 6 volts it matches at an output of 6 watts, and for 12 volts it is higher, actually 24 watts. The 15 ohm speaker appears to be more hopeful because on a 6 volt circuit it matches for an output of 1.2 watts and on a 12 volt battery the matching output is almost 5 watts.

Thermal Runaway

It is with a power transistor that the dangers of thermal runaway are encountered. This phenomenon is due to the increase in temperature of the junction caused by the power dissipated. This increase in temperature itself increases the current flowing which in turn further increases the temperature. If the junction cannot easily lose the heat generated this feedback effect can build up until the transistor destroys itself. Even if conditions prevent self-destruction those conditions will cause distortion due to the resultant limitation of the current swing.

COMPONENT LIST FOR FIG. 41

- R1—4.7 K Ω
 - R2—1 K Ω
 - R3—33 Ω
 - C1—10 μ F 6 v. Daly H2 5/1
 - C2—100 μ F 6 v. Daly E2 49/1
 - TFR—Belclere BN1827
- } Dubilier $\frac{1}{2}$ Watt

Only in the small transistors is it wise to operate the transistor by itself. In other cases a heat sink is provided. This is effected by mounting the transistor in thermal contact (not necessarily in electrical contact) with a piece of metal and transistor manufacturers give guidance with regard to the amount of metal needed for various levels of dissipation.

The principle of design of the base circuit follows the lines of the audio circuits already described.

Where large audio outputs are sought, however, it has to be remembered that a comparatively large power has to be fed to the base and in this case it may be necessary to design the driver stage as a power amplifier rather than a current amplifier.

Design for an Output Stage

Now a low power Class A single-ended output stage suitable for addition to the receiver developed during this series of articles and following the circuit in Fig. 41 will be designed. This will not involve the complications of high power drive and the audio amplifier circuit as already described will drive it. This method of operation is not likely to be entirely satisfactory for permanent use because of its comparatively low output, but it is set up as a logical step in the process of design as it uses one of the two transistors to be used in the next step in Class B push-pull. In fact, if possible, it would be as well to buy a matched pair ready for the final design and use one experimentally in the present circuit before proceeding to the more complicated one. The transistor is actually a Mullard OC72 and it is operated from the six-volt battery already provided for the rest of the circuit.

The permissible dissipation of the OC72 is seen from Fig. 40 to depend on the maximum ambient temperature under which it will be called to operate. For such cases as car radios using larger transistors and where the receiver has to work in confined spaces, this factor has to be given great thought. In the present case, however, operating a well ventilated situation is assumed and a temperature not exceeding 35 deg. C. will permit a dissipation up to 100 mW. without heat sink. If the temperature is likely to exceed this the same design would be satisfactory except that the transistor would have to be mounted on a "sink." A loss of 1 volt in the emitter resistance and output transformer primary is assumed. The maximum possible output is needed, so

$$I_c = \frac{W}{E} = \frac{100}{5} = 20 \text{ mA}$$

(To be continued)

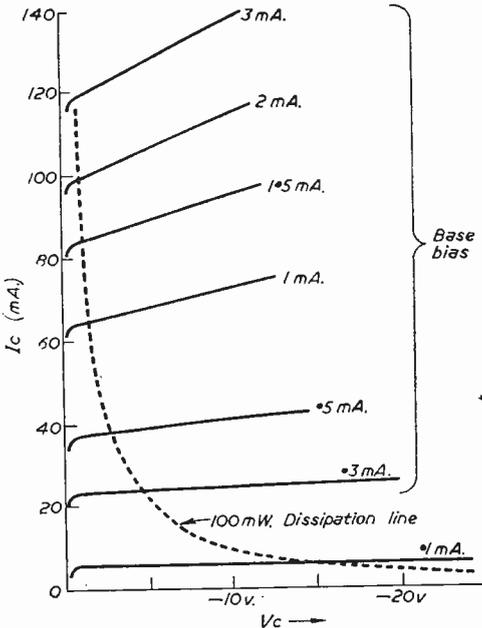


Fig. 42.—Collector characteristic—OC72.

PRACTICAL TELEVISION MAY ISSUE NOW ON SALE PRICE 1s. 3d.

Many old receivers are in use in which the circuit is of the "straight" type and which, therefore, do not lend themselves very easily to conversion for Band III reception. The best thing in such cases is to modify the video section making it conform to modern practice, and then to fit a two or three station tuner, or if preferred, one of the commercial turret tuners. How to do this is explained in the current issue of our companion paper PRACTICAL TELEVISION now on sale.

An improved Frame Sync circuit is described and will interest those who feel they would like better interlacing, whilst other articles in this issue deal with how to make a Skeleton Slot Aerial, Scanning and Synchronisation, a Mismatch Distributor, The Booster Diode, Tracing Obscure Faults and Servicing the KB LFT 50/60.

Also to be found in this issue are the usual features, Correspondence, Underneath the Dipole, News from the Trade, etc.

The Audio Fair—1958

DETAILS OF SOME OF THIS YEAR'S EXHIBITS

THIS year's Audio Fair was more comprehensive than last year's, and again depicted the many advances which have been made in Hi-Fi equipment. As usual the majority of apparatus on view consisted of amplifiers, pickups and associated gramophone equipment, loudspeakers and tape recorders. Many old friends were to be seen, as well as newcomers, and the various rooms which were reserved for demonstrations were, as usual, crowded to capacity. The following are some brief notes of some of the many items which were to be seen.

Scotch Boy Tape

For the first time the entire range of the 3M Company's "Scotch Boy" Magnetic Recording Tapes was on show.


The display of tapes featured the three "Scotch Boy" recording tapes on various spool sizes:

No. 111A Standard.—This has a standard brown oxide coating, on an acetate base, and is available in spools of 200, 600, 850, 1,200 ft. and other sizes for professional use.

No. 111V Super PVC.—Designed for extra strength and easy handling. With similar character-

istics to No. 111A and with the same oxide coating, it is intended for applications where the handling, winding and storage features of PVC are preferred. It is available in spools of 200, 600, 850 and 1,200 ft. and in other sizes for professional use.

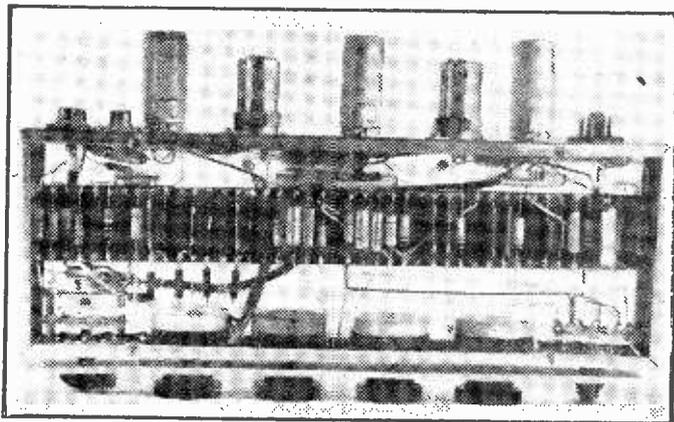No. 150 Extra Play is a polyester based type with a dark red oxide coating and offers 50 per cent. more recording time for the same reel size.




The use of tag boards is well illustrated in this G.E.C. pre-amp.—the "88-50."

because of the extra-thin backing. The "weather balanced" flexible superstrong polyester backing has outstanding mechanical properties over a wide temperature range and an extremely low rate of water absorption. It is available in spools of 300, 900, 1,275, 1,800, 2,400 ft. and 3,600 ft.

G.E.C.

Two new G.E.C. developments in high-quality loudspeaker technique—one a complete unit which will be marketed, and the other a design for home constructors—were shown.

A specially constructed 50w amplifier and pre-amplifier—the "88-50"—is shown on this page. Offering improved performance and control range, the two units have inputs for a radio tuner, a magnetic or crystal gramophone pick-up, a microphone or a magnetic tape replay head. The pre-amplifier gives full playback facilities from any known programme source, using simple and economic circuits. It is designed to give an output of 0.5 volts r.m.s. for maximum signal level, corresponding to the input required by the amplifier.

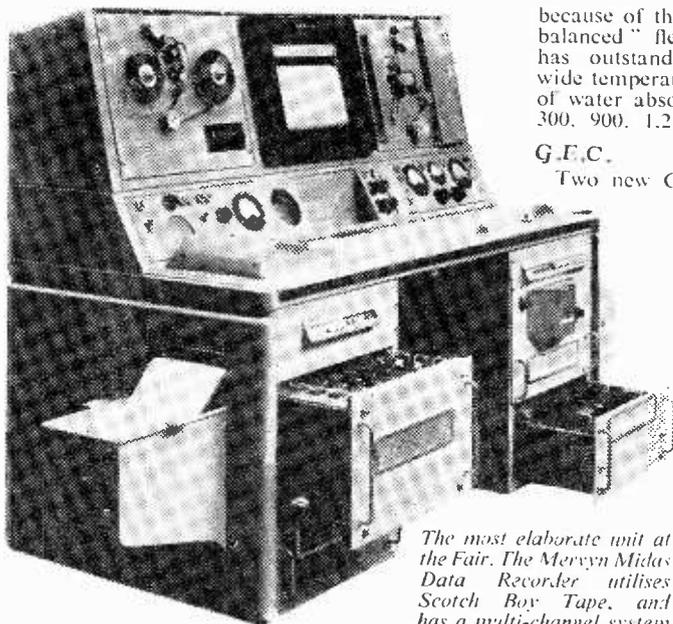

The most elaborate unit at the Fair, The Mervyn Midas Data Recorder utilizes Scotch Boy Tape, and has a multi-channel system of recording.

Mullard

The Mullard stand featured the universally available World Series audio valves, together with a range of alloy junction transistors for battery-operated audio amplifiers and pre-amplifiers.

The transistor range includes the OC16, an all-metal power transistor for the output stages of medium-power amplifiers; the OC72, which is available in matched pairs for push-pull output stages of low-power amplifiers; and the OC71 for use in pre-amplifier circuits.

W.B. (Whiteley Electrical)

The complete range of Stentorian High Fidelity Loudspeakers from 8in. to 18in. in diameter, as well as special loudspeakers from 1½in. upwards, fitted with the patented cambrie cone providing a quality of reproduction not otherwise obtainable except at many times the price, were shown.

The W.B.12 Quality Amplifier is available with either the "Standard" or "Major" Controls Units, embodying the most up to date designs and recently developed valves, and a special Whiteley output transformer. The Major Control Unit enables any pickup to be used with the W.B.12, and has a nine position selector switch in addition to separate treble, bass, "Filter," "Slope" and volume controls.

A further important addition is the W.B.6 combined amplifier and control unit, with 6 watts output, forming a compact unit size 11½in. × 7in. × 4in. It has a selector switch for a range

of inputs, full range bass and treble controls and separate volume control.

A new F.M. tuner was shown for the first time with a circuit of advanced design. An important feature is the use of printed circuit techniques to ensure maximum electrical stability, together with rigid mechanical structure, thus ensuring freedom from drift. The complete unit is housed in a sheet steel case designed to match the amplifier.

Collaro

Collaro Ltd. presented their Conquest Record Changer. This revolutionary 4-speed model is unique in that records of any dimension from 6in. to 12in. can be loaded and automatically played. There is no finger to be reset and no protrusions which might cause damage to records. The Conquest also has provision for manual play at all speeds, and automatically switches off after playing the last record. A double action cam is incorporated in the change speed control, thus eliminating all possibility of damage to the idler wheel if the speed control is operated while the machine is running. The record changer spindle is designed so that there is a gentle lowering of records from the stack, ensuring hundreds of playings without damage to the centre holes, and a sensitive velocity trip mechanism operates on all modern and most old records.

Another interesting exhibit was the new improved Tape Transcriber, Mark IV, which incorporates several modifications to the previous design.

Further Notes on the Geiger Counter

REVIEWING the many readers' enquiries about the Simple Geiger Counter described in the April issue, a few points have arisen which may be of interest.

First, the G-M tube G24 is obtainable from 20th Century Electronics Ltd., King Henry's Drive, New Addington, Surrey, and the price is 35/-, postage extra. This tube measures 270 mm. in length, but type G12 measuring only 145 mm. will work almost as well and can be neatly strapped to the side of the box. This tube also costs 35/-.

The type numbers of the batteries used (OL230 and OL250) are those intended for deaf-aid sets, and suitable equivalents are Ever-Ready B106 for H.T., and either D18 or D19 for L.T.

The rectifier K840 is made by Sentercel, and the apparently over generous ratings are due to the fact that the forward and reverse resistances were the primary considerations in the choice of this component. The valves CK505 AX may be obtained from Service Trading Co., 9, Little Newport Street, Leicester Square, London, W.C.2, at 2/6 each, postage extra. This firm also has most of the other components in stock.

Those having difficulty in obtaining the midget neon may be interested to learn that the majority of cheap mains "circuit testers" contain nothing more than one of these neons with a series resistor and test prods attached.

A minor printing error in the wiring layout omits the connection between the junction of C1 and R4 and the grids of V2 and V3, but reference to the circuit diagram will reveal the missing wire.

The Choke

A more detailed description of the home-wound ringing choke has been requested by some, but this is not critical with regard to resistance and number of turns. For example, the two prototype chokes were rapidly wound on an electric motor with 40 s.w.g. D.S.C. enamelled wire, and the resultant winding was loose and spongy in texture, whereas the Teletron product is neatly wound with enamelled wire which occupies only half the volume.

Any breaks in the wire occasioned during winding must be rejoined by soldering, and the joint well insulated by Sellotape or transformer paper. The end connections must be particularly well insulated from each other and the rest of the winding, or sparking-over may occur.

A reference was made to Government publications of use to those going prospecting for uranium on their holidays.

The following works can either be purchased from the "Geological Survey and Museum," Exhibition Road, South Kensington, London, S.W.7, or they can be seen in the library of the museum.

(1) Dines, H.G. "Metalliferous mining districts of South-west England" (Mem. Geol. Surv. G.B., H.M.S.O., 2 Vols.).

(2) Davidson, C. F. "Uranium Deposits in Great Britain."

(3) Ponsford, D. R. A. "Radioactivity Studies of some British Sedimentary Rocks."

Any public library should be able to obtain these for readers.



Our specialist buying knowledge and reputation ensure a square deal . . . and enable us to


offer the best for your money!

BAND 3 T/V CONVERTER—180 Mc/s - 205 Mc/s

Suitable for London, Birmingham, Northern, Scottish and Welsh ITA Transmissions.

Mk. 2 Model as illustrated. Latest Cascode circuit using ECC84 and EF80 valves giving improved sensitivity (+ 18 db) over standard circuits. Built-in Power supply AC 200-250 v. Dimensions only 6 1/2 in. x 3 in. Ht. 4 in. Simple and easy to fit—only external plug in connections, wired, aligned and tested ready for use. State Channel required. Guar. Bargain Offer—good results or full refund.

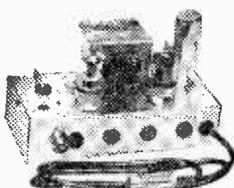only £3.19.6. Carr. & Pack. 2/6. Band 1, Bard 3 Change-over Switch and B.B.C. aerial socket, 8/- extra. **CONVERTER ACCESSORIES** Bard 1-Band 3 Cross-over Unit, 7.6. Var. Attenuators (db-36db), 6/9. BBC Pattern Filter, 8.6. Bard 3 Aerials—outside Single Dipole with 4 yds. co-ax., etc., 13/9. 3 Element Beam, 27.6. 5 Element, 35/-, etc.




Volume Controls

Log. ratios, 10,000 ohms - 2 Megohms. Long spindles. 1 year guarantee. Miglet Edison type. No sw. S.P. Sw. 1/4 P.Sw. 3/- 4/- 4/9 Linear Ratio, 10,000 ohms - 2 Megohms. Less switch, 8/- each. Coax plugs, 1.2. Coax sockets, 1.7. Couplers, 1.3. Outlet boxes, 4.6.

80 ohm COAXIAL

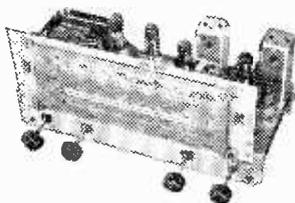STANDARD 1/2 in. diam. Polythene insulated. GRADE "A" ONLY. **8d. yd.** SPECIAL — Semi-air spaced polythene, 80 ohm Coax 1/2 in. diam. Standard core. Losses cut 50%. Ideal lead in. **9d. yd.**



ALL-WAVE RADIOGRAM CHASSIS

3 WAVEBANDS 5 VALVES LATEST MIDGET S.W. 16 m.-50 m. B.V.A. M.W. 200 m.-500 m. L.W. 800 m.-2,000 m. SERIES

Brand new and guar. A.C. 200-250 v., 4 pos. W.C. sw. Short-Medium-Long-Gran. P.T. socket. High Q dust core coils. Latest circuit technique, delayed AVC and neg. feedback. O.P. 4 watts. Chassis size 13 1/2 x 2 1/2 x 2 1/2 in. Dial 10 in. x 4 1/2 in. Hor. or Vert. station names. Walnut or ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost. Chassis isolated from mains. **BARGAIN 9j gns.** Carr. & ins., 4/6. PRICE 8 or 10 in. speakers to match, 20/- and 25/- 7 Valve De Luxe, push-pull EL41 version, 7 watt output, with H Duty Output Transformer, £12.10.0. Carr. & ins., 5/-.

NEW BOXED VALVES GUARANTEED

1R5, AT17 6, D196 9	EP41 10.6	PCF82 10.6
1R5, 1R4 7.6	DK36 9	EP80 10.6
3R4, 3V4 9	DL36 9	EP86 12.6
5Z4 9.6	6X5 10.6	EP91 9.6
6AT6 8.6	EAB/80 9.6	EL41 10.6
6K7 6.6	EB91 6.6	EL84 11.6
6K8 8.6	EB94 11.6	EM85 11.6
6Q7 8.6	EW83 9.6	EV51 12.6
6SN7 8.6	EC84 12.6	EV86 14.6
6V6 7.6	EC90 12.6	EL40 8.6
6X4 7.6	EC92 12.6	EZ80 8.6
6X5 7.6	EH42 10.6	EZ81 8.6
6Y5 9	EH81 10.6	MT14 8.6
6Y4 8.6	EL80 10.6	PCF84 10.6
DAP96 9	EL82 12.6	PCF80 10.6

SPECIAL PRICE PER SET

1R5, 1R4, 1R5, 1R4 or 3R4, or 3V4	27.6
DK36, D196, DAP96, DL36	35-
6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5	35-



RECORD PLAYER CABINETS

Contemporary style, rexine covered cabinet in mottled red with cream interior. Size 18 1/2 x 13 1/2 x 11 in., fitted with all accessories, including speaker, buffer board and plastic feet. Space available for all modern amplifiers and autochangers, etc. 1 unit record player mounting board 11 x 13 in.

Cabinet Price, **£3. 3. 0.** Carr. & Ins., 2/6.

2-VALVE AMPLIFIER Mk. 1.

200-250 v. A.C. Modern circuit with High Gain EL41 output and double wound Main Transformer, variable tone and volume controls, wired and tested with 6in. speaker and O.P. Trans. complete with knobs and drilled ready to fit Baffle Board in above cabinet. Only **£3.12.6.** Carr. & Pack. 2/6.

2-VALVE AMPLIFIER Mk. 2.

200-250 v. A.C. Specification as above but a higher fidelity and greater output (approx. 3 watts) is obtained by using latest Twin Stage Triode-coupled Valve 1Y1-82 and negative feedback Tone Control. Complete wired and tested as above **£3.19.6.** Carr. & Pack. 2/6.

SPEAKER FRET—Expanded Bronze anodised metal 8 x 8 in., 2 3/4; 12 x 8 in., 3/-; 12 x 12 in., 4/6; 12 x 16 in., 6/-; 24 x 12 in., 9/-, etc.

TYGAN FRET (Murray pattern) 12 in. x 12 in., 2/-; 12 x 15 in., 3/-; 12 x 24 in., 4/-, etc.

RECORD PLAYER BARGAINS


4 sp. BSR (TC9), 92.6. 4 sp. COLLARO JUNIOR, £4.10.0. 4 sp. GARRARD (4 S.P.), £7.15.0. AUTO CHANGERS.—4 sp. BSR (CANS), £8.10.0. 4 sp. COLLARO, £9.15.0. 1 sp. GARRARD (RC120 LH 2), £10.5.0. Carr. & Ins., 4/6. All above units are latest models and are fitted with modern styled 'Fairlight' Xtal. P.T. with turn-over head and twin sapphire stylus.

TV TUBES—RECONDITIONED

All Tested and Guarant. 6 months. **GENUINE OFFER**—all tubes Reconditioned and Re-wound and virtually as good as new. 12 in. Mullard, Mazda, etc., £6.10.0. 14 in. Mullard, Mazda (Rect.), £7.0.0. 17 in. Mullard, Mazda (Rect.), £9.10.0. Carr. & Ins. 12/6.

COMPREHENSIVE STOCKS—QUICK DELIVERY

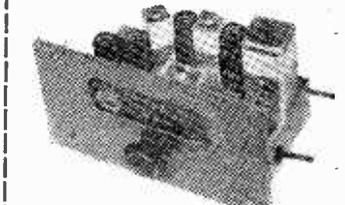I.F. TRANSFORMER—465 kc s. Brand new ex-manufacturer's midget I.F.T. size 2 1/2 in. x 1 1/2 in. dust core tuning. Litz wound coils, High Q. Bargain offer, 7.6 pair.



F.M. TUNER UNIT (87 mc—105 mc s) by Jason.

As described in Radio Constructor. Designer Approved kit of parts to build this modern highly successful unit, drilled chassis and superior type B. glass dial, coils, caps and all quality components, etc., for only 5 Gns., post free. Set of 4 specified min. valves, 20/-, post free. Illustrated handbook, with full details, 2/- post free. 2-day alignment service now available, 7.6 plus P.&P.

ELECTROLYTICS ALL TYPES NEW STOCK.

25-25 v. 50 12 v. 1.9	32-32 350 v. B.E.C. 5.6
50-50 v. 4 500 v. 2	Can Types, Clips 3d. ea.
100-25 v. 2 450 v. 2	8-4 450 v. T.C.C. 4.0
4-50 v. B.E.C. 2.3	8-16 450 v. Hunts 5.5
4-50 v. Dub. 2.9	16-16 450 v. T.C.C. 5.6
4-8 200 v. Dub. 4.0	32 350 v. Dub. 4
4-16 450 v. T.C.C. 5	32-32 275 v. Hunts 4.6
16-450 v. B.E.C. 4.6	32-32 150 v. T.C.C. 6.6
16-500 v. Dub. 4	250 350 v. B.E.C. 8.6
16-16 450 v. T.C.C. 5.6	60 350 v. T.C.C. 6.6
32 350 v. Dub. 4	60-16 250 v. 11.6
32-500 v. Dub. 5	60-60 275 v. 12.6
50-50 350 v. B.E.C. 6.6	100-250 275 v. 12.6

Many other types in stock.

TRANSFORMER & COIL WINDING CAPACITY AVAILABLE FOR PROTOTYPES & SMALL RUNS.



Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

RADIO COMPONENT SPECIALISTS (Est. 1946)


70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)
50 yards Thornton Heath Station.
Buses : 130A, 133, 159, 166 and 190.
Hours : 9 a.m.-5 p.m. 1 p.m. Wed. Open all day Saturday.
Terms : C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post. Pack up to 1lb. 7d., 1lb. 11, 5lb. 1, 6lb. 5lb. 2, 10lb. 2, 9.



PRECISION-BUILT COMPONENTS

JACKSON LGP GEARED DRIVE

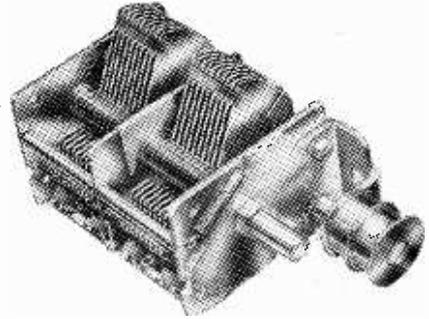This geared drive gives a 9in. pointer travel with only a $\frac{3}{4}$ in. diameter pulley. The LGP geared drive can be fitted to the standard range of L type condensers. Price LGP2 complete 18/9. LGP3 complete 24/-.



IT'S RELIABLE IF IT'S MADE BY JACKSONS!

Please write for illustrated catalogue.

JACKSON BROS. (London) LTD.

KINGSWAY · WADDON · SURREY

Telephone: CROydon 2754/5

FIRST-CLASS RADIO COURSES...

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches),** etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES—

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 461), 148, HOLBORN, LONDON, E.C.1.

BENSON'S BETTER BARGAINS

TRANSFORMERS: Input 230 v. 50 c. Outputs 629-550-375-0-375-550-629 v. 200 mA. and 250 mA. simultaneously available. . 5v. 3 A. twice. New, 24 lb. nett. £3 del'd. mainland. **SPEAKERS:** 5in. in case. 25/-, menced 18'6 (p.p. 2/6). **DRIVES:** slow-motion, Admiralty; 200:1 ratio, scaled 0-100. 5/6. Muirhead, 4in. dial (brass). 7/6. **RI155B.** Good condition, fully valved; tested, with "N" drive; handbook supplied. 27/10/- (rail 10/-). **TEST SET 127U (1058).** U.S.A. Micro-wave Frequency Meters; 375-725 mc/s. 3 valves, new, less bats. 27/10/- **CR100**—brand new; power transformers. 30/- **POWER UNIT.** 301: Input 200 250 v. Outputs: 250 v. 75 mA; 24 v. 1 A. D.C. and 6.3 v. 3 A. A.C. New, casel, with plugs, 45/- (p.p. 3/6). **COMMAND RECEIVERS,** brand new, 6 valves, med. wave (0-22.1.5 mc/s). 57/6; used 82/6 (post 3/6). Conversion data and circ., to CAR RADIO. 1/6. **I.F. STRIP 373,** new, with valves, 35/- **RELAYS,** coaxial, "P.G." 12 v., 10/-; set 3 plugs. 1/6. **VIBRAPACKS** 4 v. (C) to 250 v., 80 mA., 12/6; med. wave (0-22.1.5 mc/s). 22/6 (post 3/6). **VIBRATORS,** Mallory G629C 12 v. 4-pin, 7/6. **BRAND NEW R.F.26.20**—(post 3/-); **RF27,** good cond., 15/- **DYNAMOTORS** (post 3/6): 12 v. to 250 v., 65 mA. and 6.3 v. 2.5 A., 11/6; 6 v. to 250 v., 80 mA., 12/6; 11 v. to 210 v., 70 mA. and 13 v. smooth, filtered, casel, 15/-; "Command" type 28 v. to 250 v., 60 mA. (small), 10/6. **METAL RECTIFIERS:** 12 v. 1 A. bridge, 2/6; 270 v., 80 mA., HW, 5/-; 250 v., 100 mA., 4/-; 350 v., 80 mA., 6/-; 12 v. 4 A. Bridge, 12/6; 240 v., 30 mA., 3/6; 1,000 v. 30 mA., 7/6. **RI155 S.M. DRIVES "N"** type, new, 10/6. **TS350** with 1 mA. 3 1/2in. meter, valve TP25, casel., 30/- **METERS,** contain 2 separate micro-amp movements and 2 neons, new, 8/6. Cross-over needle (L/R). 100 μ A each section, good condition, 10 G. R.F. UNIT with 1EF93, 2 EF91, motor-tuned (20-35 mc/s), I.F. 15 mc/s, new, 30/- (p.p. 3/6). **CAMERA CONTROLS.** Type 35: a photographic timing device; 24 v. motors. New, 15/- (p.p. 3/6). Inert CELLS 1.5 v., 1.2. **CUT-OUTS** 50/285 "J" 24 v., 200 A., 10/- **LIST AND ENQUIRIES:** S.A.E. please 1 Ternus, C.W.O. Postage extra. Immediate despatch.

Callers and Post: **W. A. BENSON (P.W.)**
138, Rathbone Road, Liverpool, 15. NEP 6853
Callers: **SUPERADIO (W'chapel) LTD.**
118 Whitechapel, Liverpool, 2. ROY 1130

TV & RADIO TUBE TROUBLES

By S. Heller

23/- Postage 1/-

THE RADIO AMATEUR'S HANDBOOK. By A. R. R. L. 1958 ed. 32/6. Postage 1/9.

TELECOMMUNICATIONS PRINCIPLES. By R. N. Renton. 45/- Postage 1/9.

ELEMENTS OF TAPE RECORDER CIRCUITS. By H. Burstein & H. C. Pollak. 23/- Postage 1/-.

TRANSISTORS THEORY AND PRACTICE. By R. P. Turner. 16/- Postage 9d.

MAGNETIC TAPE RECORDING. By H. G. M. Spratt. 55/- Postage 1/-.

TRANSISTOR TECHNIQUES. Gernsback Lib. 12/- Postage 9d.

HIGH FIDELITY SOUND REPRODUCTION. By E. Molloy. 20/- Postage 1/-.

RADIO VALVE DATA. Compiled by "WW". 5/- Postage 8d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET, LONDON, W.2

Complete catalogue 6d. Phone: Paddington 4185. Open 6 days 9-6 p.m.

Is a Pre-war Set Worth Servicing?

SOME DATA ON OLD MODEL RECEIVERS AND THE PROBLEMS INVOLVED IN SERVICING THEM

By "Serviceman"

MOST service engineers have, in the course of their work, run up against this problem. I have had many of these sets brought to me for service, and it has been a difficult problem to decide whether to service them or to advise the owners to scrap them. In many of these cases, the reason for people wishing to have them serviced is because they like the cabinet, which has often, especially in the case of radiograms, been kept in a very good condition. Most of the pre-war cabinets were of good, sound timber and not the thin ply of which many present-day cabinets consist. Generally, when one informs the owners that the set is not worth the cost of the servicing and suggest they purchase a new one, they reply that having heard the new sets they cannot compare with their old one. This is mainly because they have become accustomed to the tone of their old set, which in the case of most of the pre-war sets, had a sharp topcut in the amplifier and loudspeaker, thus giving what they consider was a mellow tone. When they hear the later day models giving a lot of top, to which their ears are not accustomed, they consider them harsh and not pleasant listening. My method of dealing with these sets is not to have any hard and fast rules about them, but to judge each case on its own merits.

The Pros and Cons

In the case of people who I know cannot afford a new set, such as, for instance, old age pensioners, I do my best for them, if it is possible to put the set in order, with the chances of a reasonable further period of useful life, but I always inform them that owing to the age of the instrument I cannot guarantee that it will not break down again within 12 months.

In the case of people who can afford to purchase a new set, I point out that firstly the cost of servicing, including labour, new parts and valves, may be quite high and perhaps be more than the set is worth. Also I tell them that as all the component parts have already had a long life and to replace the lot would be out of the question, there would always be a possibility of one of these components breaking down within a short space of time after the set was serviced, and therefore no guarantee could be given. If they do not accept these conditions then I turn the job down.

Jobs to Reject

Should it be a case where they wish to retain the cabinet, then I suggest, if the set itself is in very bad condition, that a new chassis be installed in the cabinet. Care should be taken here to see that a chassis is chosen that does not necessitate cutting or drilling the cabinet for control spindle purposes.

Sets that are not worth while attempting to

service are those with the old type side contact valves. These valves are practically unprocurable and to try and replace with five- or seven-pin types means a considerable amount of time and trouble. The main reason is that the holes in the chassis for these side contact valveholders are considerably larger than for other types. This means plates being cut out for normal valveholders and fitted on the chassis.

Any sets using the old 4 volt heater type, especially the five-pin types, should be carefully considered. Some of these valves are impossible to obtain and to convert to a 6 volt range would not be an economic consideration.

Other types with the old large type band pass coils that have gone open circuit should be bypassed. Replacements for these coils are hopeless. Rewinding takes up too much time, and consequently the cost of servicing becomes excessive. Other sets that I suggest should be rejected are those with rubber-covered leads, where the rubber is either perished or in a bad state. To attempt to do this type of job means practically complete rewiring.

Points to Watch in Servicing Old Sets

It is advisable in all cases to renew the electrolytic condensers, and also the rectifiers, valve or metal type, but it should be pointed out that then the H.T. voltage will probably be higher than before. This means that the bypass and coupling capacitors will be subject to a greater strain and as they are old there is a liability of their breaking down. When these electrolytics and rectifiers are changed, the set should be put on a soak test and checks made on all resistors for temperature rise. At any sign of this occurring, change the bypass condenser concerned, as it is probably leaking, which is often the prelude to short circuiting. It is also advisable to check voltages on valves, which will, in most cases, show up any other likely near failures. Old A.C./D.C. sets are those to view with great suspicion, as the heat radiated inside these sets is often much greater than in A.C. sets and this causes greater deterioration of the components. Mains dropping resistors or line cords should always be replaced, as this is where the greatest heat comes from.

Remarks on Valve Changing

From the foregoing the reader can see that, unless it is being done as a personal favour, or if the owner does not mind the cost, it is not advisable to undertake these jobs. Even when the greatest care is taken and an extended soak test given, one cannot be sure that the repair will last for a reasonable time, without another breakdown.

It often happens with these sets, that a valve

has failed, and the correct replacement cannot be obtained, and a later type valve has been fitted with a base adaptor. Now it should be pointed out that, although the new valve is of the same type, has the same heater voltage and current, its characteristics are often considerably different. When fitting a valve of this description, always check up on anode, screen and cathode voltages. In the case of valves in tuned circuits, a slight alteration of trimmers may be necessary to allow for different inter electrode capacities of the old and new valves.

International Car Radio Rally

WHAT is believed to be the world's first International Car Radio Rally will commence on June 25th in Britain and 26th on the Continent. The main difference between this and other motoring rallies is the fact that participants will be given their instructions over the air from Radio Luxembourg. The prime qualification for entry, therefore, is that participants' cars must be equipped with car radio. Instructions will be broadcast at frequent intervals throughout the rally in English, Dutch, French and German on two wavelengths—208 and 1293 metres.

The rally is organised by the Regional Motoring Club of South Holland and the Luxembourg Motoring Club. It is open to entrants from Great Britain, France, West Germany and Belgium, Holland and Luxembourg.

Starting points are London, Amsterdam, Paris, Brussels, Luxembourg and Bonn. It is planned that British entrants will spend the night of the 25th at Dover, crossing the Channel the following morning. At Rheims they will join the main route, as will participants from Luxembourg and Paris. Those setting out from Amsterdam, Brussels and Bonn will have met at Eindhoven (Holland) and will join the main route at Dinant. A reception centre has been arranged at Chaudfontaine (Belgium) and the rally finishes at Luxembourg in the late afternoon of the 27th.

Passengers

In contrast with other international rallies, each car will be permitted to carry more than two passengers. The organisers stress that the rally is in no sense a test of speed and endurance and, while some simple skill and regularity tests will be included, they will not affect the nature of the rally as a tourist event involving moderate speeds and easy map-reading. Participants will, therefore, have plenty of opportunity of enjoying the splendid scenery through which they will pass. The 800 mile route covers some of the most beautiful parts of the Low Countries, the Ardennes, the Eiffel and Northern France.

On June 28th a winding-up party will be held and prizes will be presented. Among other attractions will be an entertainment provided by artistes of international standing.

Entries

British motorists wishing to take part are invited to apply for further particulars to Competitions Department, Royal Automobile Club, Pall Mall, London, S.W.1. The latest date for entry is June 7th.

Changing Loudspeakers

Many of the old sets had electrically energised speakers and replacements are out of the question. It therefore becomes necessary to fit a permanent magnet speaker. In this case an L.F. choke will be necessary, to act as H.T. smoother in place of the loudspeaker field coil. In fitting this make sure the inductance and also the current carrying capacity of the winding is sufficient. It is better to use as large a choke as space will permit than to use a small one that will overheat and perhaps burn out.

New Mullard Photo-cell

A NEW type of photo-electric cell which will enable the cost of many industrial control and detection devices to be reduced substantially will shortly be available in quantity for the first time in this country.

The new cell incorporates a specially constructed photo-sensitive element of cadmium sulphide, and is remarkable for its extremely high sensitivity: it is, in fact, some 20,000 times more sensitive than the conventional p.-e. cell.

Even from weak sources of light it will produce sufficient current to operate a large relay direct without the need for intermediate amplification. The electronic amplifier circuitry associated with most devices based on conventional photo-cells is therefore made unnecessary, with consequent savings in equipment costs, simplification of design, greater reliability and easier maintenance.

Furthermore, the cell will produce the current necessary to operate a relay with only a very low applied voltage. This is made possible by a special form of construction in which the resistance of the cadmium sulphide element is effectively reduced by an interdigital pattern of copper strips.

The cadmium sulphide cells will be mounted on standard valve bases identical with those of the present Mullard range of conventional cells. Thus, when existing equipments are modified, special head mountings or probes designed for specific installations can be retained.

Advance Performance Details

Typical performance figures for a Mullard cadmium sulphide cell with a photo-cathode of 1.8 square cm. effective area include the following:


From an illumination of 5ft.-lamberts, with a colour temperature of 1500 deg. K, the cell will produce approximately 20mA of current for an applied voltage of 10v. From the same illumination, but with a temperature of 2700 deg. K, the current is approximately 6mA. Within the limits of permissible power dissipation doubling the applied voltage gives a four-fold increase in current. Maximum dissipation is 1 watt at 25 deg. C and 200mW at 75 deg. C.

Dark current is extremely low: with 300v. applied to the cell it is not greater than 2.5 microamps at 25 deg. C.

Spectral response range is 4500 deg. A to 8000 deg. A, covering the entire visible spectrum and extending into the infra-red, with maximum response in the yellow/red region.

A Hi-Fi A.M. RECEIVER

THIS receiver was built primarily with the intention of providing a reasonably high quality reproduction of recorded music from both gramophone and tape, but a considerable amount of effort has been spent on providing a radio-frequency feeder to give results similar in quality to those obtainable from the gramophone. The feeder unit is the part of greatest interest in this series, as it sets out to overcome the disadvantages of Amplitude Modulation broadcasts on the Medium and Long waves.

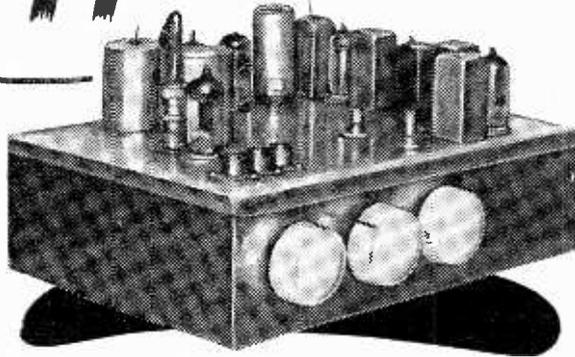

How to Make a Self-contained High-quality Receiver, Using a Mullard 5-10 Amplifier for the Output Section. Full Cabinet Constructional Details Will be Given in Subsequent Issues

By R. Couvela

quite a variety of answers to this, some of which are given below:

The principal disadvantage of F.M. is the limitations of the variety of programmes which may be received. The prototype of this series receives the Light Programme, the Home Service (any region), and Radio Luxembourg, but there is no reason for selecting these three except for personal preference. The coil-

Immediately, of course, the query is raised, why not use the new Frequency Modulation transmissions? There are

packs available give a wide range of choice of stations, and, by constructing the coilpack at

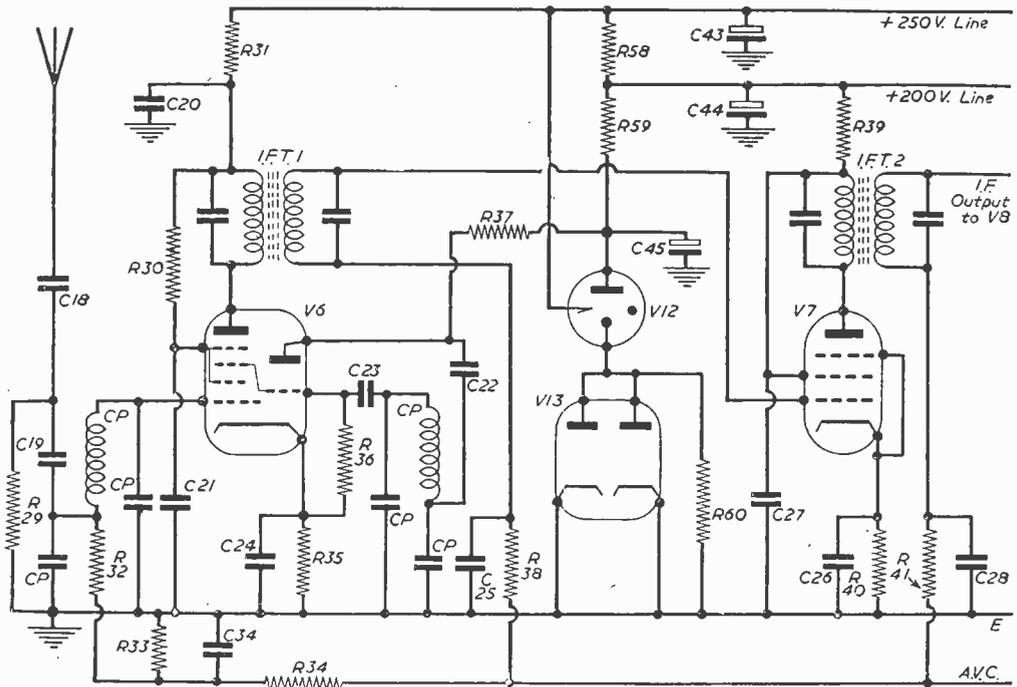


Fig. 1(a).—Circuit of the feeder section.


home, the constructor is not limited to three stations. In addition, of course, a variable tuning system could be installed by suitable modification of the constructional details.

Another disadvantage of F.M. is that only local stations can be received with ease (and quality), and this makes difficulties for "fringe areas."

The reader should from the first be clear that this receiver is not intended to satisfy the most stringent demands of the High Fidelity enthusiast, but rather to provide a unit which, while being well above the normal standard of quality, does not involve great expense or technical knowledge to construct.

The Circuit

The tuning of this receiver is carried out by an Osmor preset coilpack, of which there are several types available, to suit various requirements. When used with a conventional circuit, these coilpacks normally have adequate stability, but, as an added refinement, this receiver incorporates a stabilised H.T. supply for the oscillator section of the frequency changer. No previous stage is used, mainly because facilities are not available on the coilpack in use, but if it had been considered necessary, this difficulty could have been surmounted. The circuit has been found in practice to have adequate selectivity and sensitivity. The frequency changer and

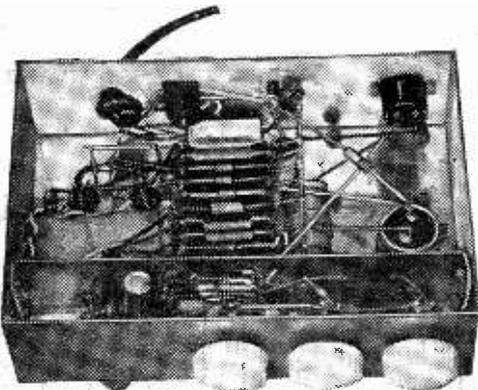


Underside view of the second unit, which includes the section shown in Fig. 1(b).

tuner sections are mounted in a separate compartment, screened from the rest of the set, and it should be noted that, due to the screening, it is not possible to operate the set without a short aerial.

In order to provide an output signal of more than average consistency of amplitude, especially when receiving Radio Luxembourg, it was considered necessary to amplify the A.V.C. supply.

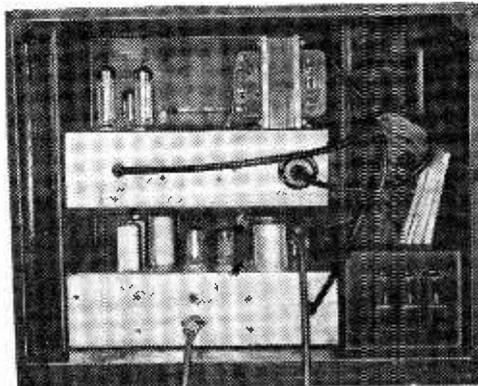In order to provide an adequate range of amplification values to make full use of the amplified A.V.C., two stages of variable-mu I.F. amplification have been used.




How the sections are housed in the upper part of the cabinet.

Following the detector stage the audio frequency signal is made available on a switch, in common with any other desired audio frequency signal, by which any one signal may be selected at will. A simple means is provided for regulating the amplitude of each signal, so as to allow them all to be adjusted to a similar level, to avoid the necessity of readjusting the volume control on changing from radio to gramophone, or vice versa.


It was thought desirable to fit a simple scratch filter at this stage, and this is performed by a single R.C. filter network. The filter is continuously variable for the sake of convenience, and is arranged to attenuate all frequencies above a fixed cut-off frequency at a rate of approximately six db per octave. The cut-off frequency may be fixed at any value between 2 kc/s and 20 kc/s by a knob on the front panel, the latter setting having no effect on the amplifier performance.

The signal is then passed to an unbiased cathode follower circuit, which enables the output of this unit to be connected to any one of the wide range of load values, as required.

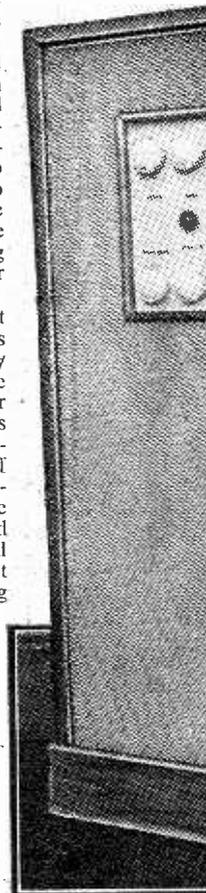In normal use, the signal is then passed down a coaxial lead to a Mullard 5-10, or similar high quality audio frequency amplifier. The output is by a Goodmans Axiette loudspeaker in a cabinet



The cabinet

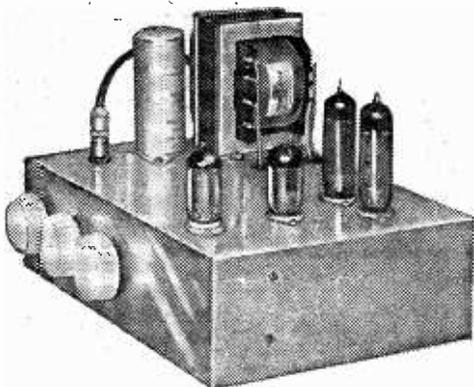

View of the second unit.

specially designed for it. This cabinet is integral with the housing of the main chassis.

The Cabinet

The complete unit is built into one cabinet, as it was intended that it should be used in a normal living-room, and numerous separate units are definitely frowned upon by non-technical observers under such circumstances. This requirement also demanded that the unit should be of attractive appearance, and as a result some considerable amount of planning went into the design of the cabinet in order to make it suitable for home construction whilst simultaneously fulfilling all other requirements, both technical and aesthetic.

The Feeder Unit

The circuit of the feeder unit is shown in Fig. 1(a) and should be mainly self-explanatory, but the following notes are intended as a comment on the design and function of the receiver, and also as an explanation of the few unconventional features. The treatment is stage by stage for easy reference, and, in order to save comment, the reason for not starting the numbering of the components at 1 is to avoid confusion with the reference numbers of components in the Mullard 5-10 booklet if you are going to use this in the complete set.

The Frequency Changer Stage


As has been stated earlier the tuning coilpack is an Osborn preset model, of which several versions are available, the prototype using type L.L.H. The circuitry of the coilpack has been included for easy reference, although the switching has been omitted for simplicity. The details of connections will be found in the instructions with the coilpack.

The valve, V6, is an Osram X.79, or equivalent. The hexode section is operated at an H.T. of 250 volts, decoupled by C20 and R31. An identical decoupling network is used on all stages. The H.T. supply to the anode of the triode is 150 volts stabilised: R37 is the anode load of the triode.

The aerial network, C18, R29, is intended to exclude 50 c/s signals from the aerial input, and thus eliminate modulation hum. In some areas, where this type of interference is common, R29 should be replaced by a R.F. choke, as recommended in the coilpack instructions.

Note that A.V.C. is fed to this section of the circuit at half the level used for the other stages. This is brought about by the potential divider R34, R33. The network R32, C34, is inserted to prevent stray signals from the A.V.C. line causing interference in the grid circuit of V6. An identical network is used on all stages. C19 is inserted to isolate the A.V.C. voltage from R32 from the earth on R29.

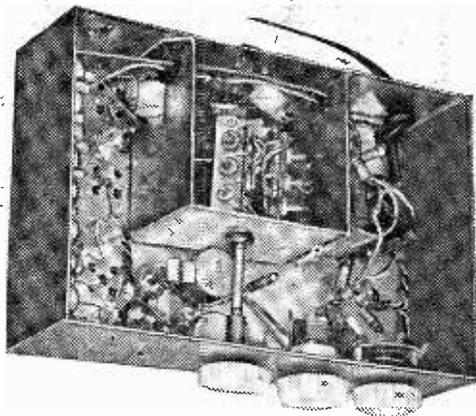The oscillator uses a straightforward Colpitts circuit, this arrangement being perfectly normal in this application. Grid bias, for this section is obtained in the usual manner for this arrange-




Underside view of the section shown in Fig. 1(a).

ment, C23, R36 providing the "leaky grid" circuit.

The anode signal output of the stage is fed via I.F.T.1 to V7. The I.F. is 465 k/c/s, and the I.F.T. is a Denco type I.F.T.11.

The I.F. Amplifier Stage

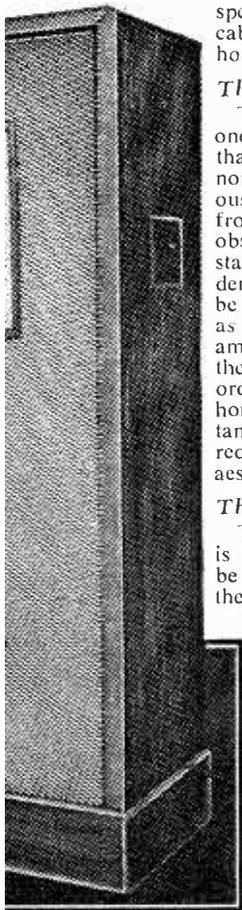The "earthy" end of I.F.T.1 is fed with A.V.C., via the filter C25, R38, which is included



ed receiver.

to eliminate stray signals and interaction. The other end is connected to the grid of V7, and it should be noted that, by careful design, both this lead and the anode lead have been reduced to half an inch in length. Care should be taken when drilling the chassis to orientate the valveholder correctly so as to maintain this condition. The stage is fed by a decoupled H.T. of 200 volts, and is perfectly conventional in circuitry.

The valve is a Brimar 9D6 (Osram W77) or equivalent. This is a variable-mu R.F. pentode, on a B7G base.

The output of this circuit is fed via I.F.T.2 to a similar stage acting as a second I.F. amplifier. The only difference in the circuit of V8 is that the A.V.C. supply signal is taken via a capacitor C30 from the anode, so no further comment is necessary.

The A.V.C. Amplifier Stage

This circuit is similar to the I.F. amplifiers, but is fed by an R.C. circuit, R44, C30. This stage, of course, has no A.V.C., so R44 is earthed. The valve is an Osram Z77 or equivalent, although another W77 will work just as well without modification. The H.T. is 200 volts, and the output is via I.F.T.4.

The A.V.C. Detector Stage

The circuit of the A.V.C. detector may appear confusing at first sight, but is, in reality, perfectly conventional.

As is normal, the signal is fed to the anode of a diode whose cathode is held at a positive voltage, decoupled by C35. The A.V.C. signal is then taken directly from this anode. It will be recalled that the circuit commonly used is similar, except that the cathode of the diode is also used as the cathode of the first audio frequency amplifier. The present arrangement is necessary here as a higher value of voltage delay is required due to the amplification of the A.V.C. signal. This voltage is obtained from the

VALVES			
V6	X79	Osram	Frequency changer B9A
V7	{W77	Osram	Variable-mu pentode B7G
V8	{9D6	Brimar	
V9	Z77	Osram	High-mu pentode B7G
V10	{D77	Osram	{Detector
	{6A15	Brimar	
V11	L77	Osram	Triode B7G
V12	QS 150/15	Osram	Stabiliser B7G
V13	{D77	Osram	Safety valve (see B7G
	{6AL5	Brimar	

potential divider R47. VR48, of which VR48 is used to control the voltage. The procedure of setting this potentiometer will be described later.

The valve, V10a, is half a 6AL5 (Osram D77 or other equivalent).

The Signal Detector Stage

This stage is not quite the same as the circuit commonly used, because we take advantage of the fact that the cathode has only one use (instead of three, as is usual), and employ the diode in a simpler circuit, after the fashion of a half-wave power rectifier. The valve, V10b, is the other half of the double diode used as the A.V.C. detector. The choice of which section to use for which purpose is entirely a matter of convenience, but the screen between the sections should be earthed.

After detection, the audio signal is passed to an amplitude control, VR49. The reason for this is that it may be found that the signal obtained from the radio is considerably greater

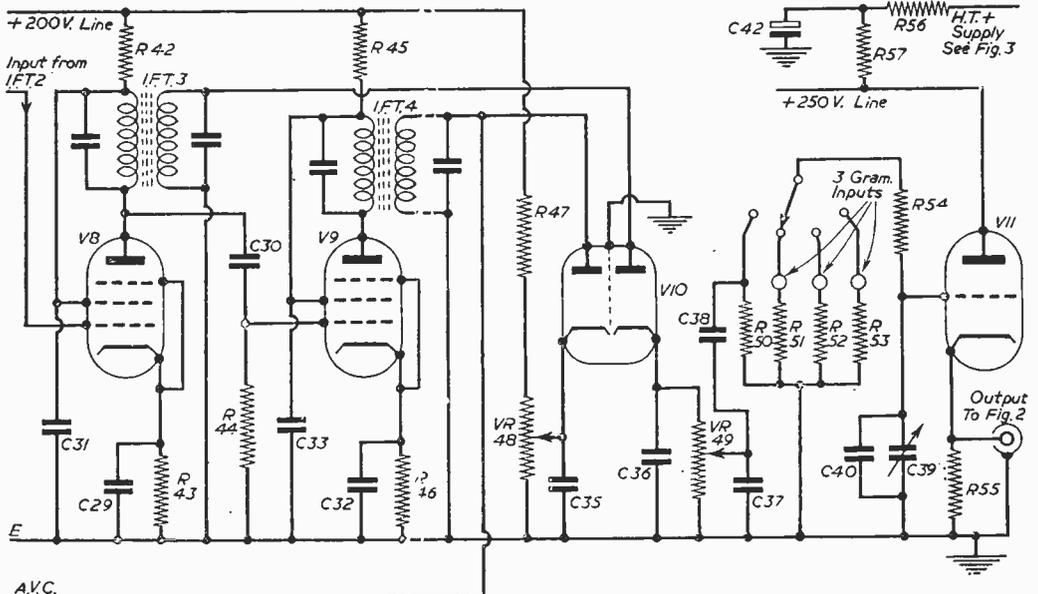


Fig. 1(b).—Circuit of the I.F.s and detector, with the first audio stage.

than that from the gramophone. in which case VR49 is used to preset the signal to a lower level in order to minimise the necessity for adjusting the volume control on switching from radio to gramophone and vice versa. This control is preset, and does not appear on the control panel. It is very useful, especially in reducing the wear on the main volume control, and the advantages gained by its insertion easily justify the slight extra expense.

In order to ensure that no R.F. component remains in the signal after this stage, the control VR49 is decoupled on both sides by C36, C37.

The "Gram-radio" Switch

When designing this receiver, it was thought that it would be useful to fit a number of audio frequency input sockets, from which signals could be selected at will by means of a switch.

but it is obviously superfluous to have any more than the two words "GRAM" and "RADIO" on the front panel. This will explain the apparent discrepancy between the diagrams. Further "Gram" channels are selected by turning the knob anti-clockwise, past the position marked.

It will be seen that each switch position has its own grid leak. There are two main reasons for this: first, to provide a load on the signal sources not in use, and to prevent the possible formation of static charges on the contacts, and secondly, to provide an internal arm of a potential divider, by means of which the gram or other external signals may conveniently be reduced in amplitude by the insertion of a series resistor. The reasons for requiring the latter are, of course, the same as those given for the insertion of VR49.

(To be continued)

LIST OF COMPONENTS

(The following items are required in addition to those needed for the Mullard Amplifier, Type 510.)

Resistors

All are 1/2 watt minimum rating except where otherwise specified.

Resistor	Resistance	Dissipation	Function
R29	10 k		Hum freq. decoupler
R30	33 k	1/2 W	Dropper for V6/G2-3
R31	2.2 k		H.T. decoupler
R32	220 k		A.V.C. line blocker
R33	220 k		A.V.C. potl.
R34	220 k		divider
R35	220 ohms		Cathode resistor, V6
R36	47 k		Grid bias resistor, V6t
R37	33 k	1/2 W	Anode Load, V6t
R38	220 k		A.V.C. line blocker
R39	2.2 k		H.T. decoupler
R40	220 ohms		Cathode resistor, V7
R41	220 k		A.V.C. line blocker
R42	2.2 k		H.T. decoupler
R43	220 ohms		Cathode resistor, V8
R44	220 k		Grid leak, V9
R45	2.2 k		H.T. decoupler
R46	220 ohms		Cathode resistor, V9
R47	150 k		H.T. potl. divider
VR48	50 k		H.T. potl. divider
VR49	250 k		Volume control
R50	1 M		Grid leak, V11
R51	220 k		} Grid leaks, V11
R52	220 k		
R53	220 k		} Scratch filter network
R54	150 k		
R55	220 k		Cathode load, V11
R56	1.5 k	3 W	} H.T. voltage droppers
R57	1.5 k	3 W	
R58	1.5 k	3 W	
R59	3.9 k	2 W	
R60	10 k	2 W	Safety resistor for V12 (see text)
R61	1 MΩ		Discharge resistor

Capacitors

Capacitor	Capacity	Voltage	Function	
C18	0.01		Hum freq. filter.	
C19	0.01		Isolating A.V.C. from earth	
C20	0.01		H.T. decoupler	
C21	0.01		Screen decoupler, V6	
C22	150 pF		Isolating osc. coils from H.T.	
C23	100 pF		Bias cap., V6t	
C24	0.01		Cathode decoupler, V6	
C25	0.01		A.V.C. decoupler, V7	
C26	0.01		Cathode decoupler, V7	
C27	0.01		H.T. decoupler	
C28	0.01		A.V.C. decoupler, V8	
C29	0.01		Cathode decouple, V8	
C30	390 pF		Coupling cap., V8/V9	
C31	0.01		H.T. decoupler	
C32	0.01		Cathode decoupler, V9	
C33	0.01		H.T. decoupler	
C34	0.01		A.V.C. decoupler, V10	
C35	0.01		Cathode decoupler,	
C36	390 pF		R.F. filter	
C37	390 pF		R.F. filter	
C38	0.05		Coupling cap., V10,V11	
C39	75 pF	} 450	Scratch filter	
C40	75 pF			
C41	300 μF (2 x 150)	} 450	Main reservoir	
C42	64 μF			
C43	120 μF			One Can
C44	32 μF			350
C45	32 μF	One Can	Smoothing	

(All Capacitors not otherwise specified should have minimum rating 250 V.W.)

Sundries

- Valvcholders: 1—B9A with skirt and screen, 1—B7G with skirt and screen, 6—B7G (screens not essential).

Coaxial sockets (Aerialite) qty., 5.

Single aerial socket.

3 7in. lengths of 6 B.A. screwed rod (see Part 3).

1-pole, 4-way switch.

3-way connecting block (for power inlet).

Aluminium for chassis, nuts, bolts, wire, grommets, knobs, etc.

Coils

All I.F.T.s are Denco I.F.T.11, 465 kc/s.

Note: Connection instructions are included in the carton, and these should be closely adhered to. Pin 4 of I.F.T.4 should be earthed.

Coilpack is Osmor "Switchpack" (any type) or home-constructed switch unit using standard coils.


N.B.—No special instructions available from this magazine. Connection instructions in carton.

A Tape Economiser

OBTAINING GOOD QUALITY SIGNALS AT LOW SPEEDS

By H. C. Parr

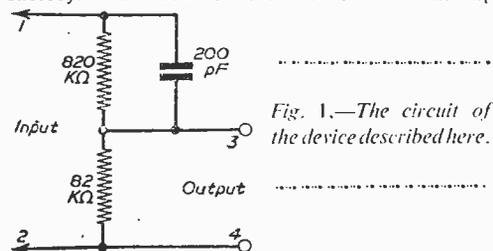EVERY owner of a tape-recorder giving tape speeds of $3\frac{1}{2}$ and $7\frac{1}{2}$ in. per sec. must have tried the effect of recording music at the slower speed, and if he is accustomed to the wide frequency range of modern V.H.F. broadcasting and L.P. records, he must have come reluctantly to the conclusion that results are barely satisfactory. The trouble is, of course, that the tape




output at this slow speed falls away rapidly at frequencies above about 1,000 cycles, and even with suitable compensation in the playback amplifier it is difficult to reproduce frequencies above about 5,000 cycles. The price one must pay for these frequencies is a doubling of the tape speed, and so of the running costs involved.

However, under certain circumstances to be mentioned later, it is possible to emphasise the upper frequencies while recording at $3\frac{1}{2}$ in. so as to make up for the loss of output compared with that at $7\frac{1}{2}$ in. and so obtain results identical with those normally achieved at the faster speed. Fig. 1 shows the circuit of a very simple device which does this. It can be built up in a few minutes on the type of socket pair which is used for the "extension speaker" or "gram" connection of a radio.

The Apparatus


Fig. 2 shows the appearance when completed.

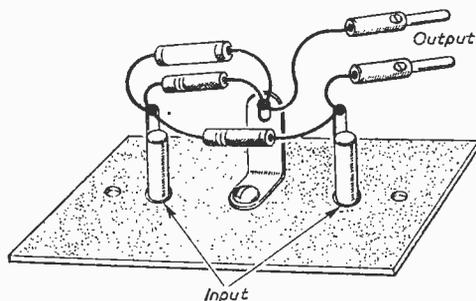

If desired a small wooden box can be made with one side open so that the sockets can be screwed on to it with the "works" inside, and a small hole for the leads to be taken through.

The appearance will then be as in Fig. 3.

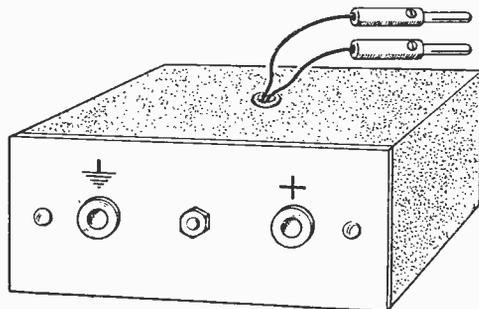The reader must suspect by now that there is some snag in expecting so simple a device to achieve so much, and he is not mistaken. The drawback is a reduction of 20 db in the available input, and so in general the device is useless when recording from a microphone, for the



resulting signal will not be strong enough to load the recorder fully. This does not apply when recording from the radio, whether the output be taken from the extension speaker terminals or direct from the tuner. The plugs shown in Figs. 2 and 3 are connected to the appropriate socket on the radio, and the output from the sockets shown is taken to the recorder through screened cable. If sufficient signal is not available when it is applied to the "radio" input, then the "microphone" input can be used.

Precautions

There are two precautions to be observed in using this device. Firstly, the terminals 2 and 4 must be connected respectively to the earthy side of the radio and recorder, or hum may be introduced. Secondly, since the purpose is to make the tape response at $3\frac{1}{2}$ in. equal to that at $7\frac{1}{2}$ in. the playback amplifier, if it provides compensation for both these speeds, should be switched to the " $7\frac{1}{2}$ " setting. If the switching is linked to the speed change mechanism some modification will be needed for the amplifier to be in the " $7\frac{1}{2}$ " setting while the tape runs at $3\frac{1}{2}$ in.

There will be no great difference in the behaviour of the recording level meter or magic eye, for in normal music the energy level is quite low at the frequencies involved.

The results at the slow speed, provided the recorder does not suffer from wow or flutter troubles, are then quite indistinguishable from those obtainable at $7\frac{1}{2}$ in. If the machine is used frequently for making permanent recordings from the radio, a considerable saving in tape costs will result.

AN ESSENTIAL "PIECE OF EQUIPMENT" FOR

RADIO & TV ENGINEERS


Technicians and Radio Amateurs

This new 2nd Edition provides in compact form all the information required by those engaged in design, maintenance, technical sales, operation and servicing of modern radio and TV transmitting and receiving equipment. It supplies the practical data, formulae, calculations and information you need, and which is often not obtainable without recourse to numerous references. For the technician and executive-to-be it is indispensable.

GRAMMED WITH FACTS, FIGURES AND DATA
WRITTEN BY 41 SPECIALISTS

Formulae & Calculations. Electron Optics & Colour TV. Materials. Studios & Equipment—*planning, lighting, camera tubes, etc.* Broadcasting Transmitters & Power Plant. Communication Transmitters—*design, components, marine, ground-to-air, mobile, international call signs, etc.* Amateur Radio Equipment—*licences, frequencies, H-F transmitter and receiver design, etc.* R.F. Transmission Lines. Waveguides. Broadcasting Receivers—*design, developments, V.H.F., etc.* TV Receiver Design—*frequency conversion, channel selection, V.H.F. Converters, colour TV, etc.* Commercial H.F. Radio Links. Broad-Band Radio Systems. Navigation & Radar. Aero Equipment. Industrial TV. Aerials—*vertical rod-inverted L-loop-aerials, V.H.F.—band III—car aerials, fundamentals, fringe equipment, etc.* Transistors. Crystal Diodes. Resistors. Capacitors. Inductors & Transformers. Microphones. Loudspeakers. Interference—*causes, etc.* Recording. Gramophone Mechanisms. Batteries & Conversion Equipment—*dry, storage, charger, vibrators, etc.* Measuring & Test Equipment. Radio & TV Installation & Servicing—*equipment, alignment, precautions, fault-finding, etc.* Projection TV—*tubes, adjustment, theatre, etc.* Quartz Oscillators & Frequency Allocations. Units & Symbols, etc. etc.

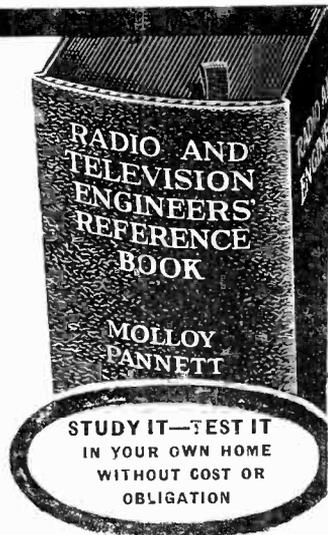BROADCASTING • COMMUNICATIONS • NAVIGATION • SERVICING



- 1,800 pages of technical data to meet your everyday needs.
- 46 main sections, written and compiled by leading authorities.
- 2,000 diagrams, tables, standard formulae, calculations, measurements.

3,260 cross - referenced index entries enabling wanted information to be found in an instant.

PROVE ITS VALUE—

FREE FOR 7 DAYS

POST TO - DAY

We cannot list above more than a small fraction of its invaluable contents — seize this opportunity to examine it freely in your own home. A "must" for the radio enthusiast.

To : George Newnes, Ltd., 66-69, Great Queen Street, London, W.C.99.
 Please send me Newnes RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK without obligation to purchase. I will either return the book within eight days or I will send the first payment of 7s. 6d. eight days after delivery, and then seven monthly subscriptions of 10s. until the sum of 77.6 has been paid. Cash price within eight days is 72.

Name

Address

Occupation

Your Signature (Or your parent's signature if under 21)

Place X where it applies.

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

RB2

Post coupon in 2d. unsealed envelope.

Tel. : Mitcham 6201
Open Daily to Callers

RST

All Valves Brand New and Fully Guaranteed

211, STREATHAM ROAD, MITCHAM, SURREY

STANDARD 24 HOUR EXPRESS MAIL ORDER SERVICE

Table listing various electronic components such as valves (6Z4, 1A7, 11D5, etc.), resistors, capacitors, and other parts with their respective specifications and prices.

METAL RECTIFIERS NEW AND GUARANTEED
Table listing metal rectifier models (RM1, RM2, etc.) and their specifications.

TERMS OF BUSINESS C.W.O. or C.O.D.
2/9 PACKING CHARGE ON ALL C.O.D. ORDERS. POSTAGE 3d. PER VALVE.

OBsolete VALVES A SPECIALITY
QUOTATIONS GIVEN ON ANY TYPE NOT LISTED.

REPANCO

HIGH GAIN TRANSISTOR COMPONENTS

STANDARD RANGE

Ferrite Slab Aerials Type FS2. Designed for Long and Medium Wave reception with transistor portable superhet receivers.
Combined I.F. Oscillator and 1st I.F. transformer Type OT1.
2nd I.F. Transformer (315 Kc/s.) Type TT2, 5/-.

MINIATURE RANGE

Ferrite Slab Aerial Type FS3. Medium Wave only. With fixing grommets. Size 3in. x 3/4in. x 5/32in., 7/6.
Oscillator Coil Type X08. Medium Wave only. Overall size 1/2in. dia x 1/2in. Enclosed in Ferrite pots, 5/-.
I.F. Transformer Type XT6. Suitable for 1st and 2nd I.F. 455 Kc/s. Size 1/2in. sq. x 1/16in., 10/-.
I.F. Transformer Type XT7. Designed for 3rd I.F.T. or detector I.F.T. 455 Kc/s. Size as XT6, 10/-.
Push Pull Interstage Transformer Type TT9. Ratio 1 : 1 C.T. Radiometal Core. Size 1/2in. x 1/2in. x 1/32in., 12/6.
Push Pull Output Transformer Type TT10. Ratio 8 : 1 C.T. Matched to 3 ohm speaker. Size as TT9, 12/6.

JUST RELEASED. "THE MINI-7" a new personal portable transistor receiver. Size 5 1/2in. x 3 1/2in. x 1 1/2in. Send 1/9 P.O. for instructions.

Mail Order and Trade: RADIO EXPERIMENTAL PRODUCTS, LTD. 33 Much Park St. COVENTRY Tel. : 40572

Wholesale Enquiries and Export: REPANCO, LTD. O'Brien's Buildings 203-269 Foleshill Rd. COVENTRY Tel. : 40594

'EMISTRUCTOR' HI-FI

- * ASSEMBLE THE UNITS
* LEARN AS YOU BUILD

At last! Here's YOUR opportunity to own a magnificent Hi-Fi—a complete hi-fi system in a beautifully-styled cabinet at two-thirds of normal price—plus all the extra satisfaction and fun of building it yourself!



CHOICE OF UNITS AVAILABLE: Superb contemporary style cabinet • 8 or 14 watt high quality amplifier (push-pull output with feed back) • 4-speed auto-change record player with compensation • High quality speaker system • Tape transistor with pre-amplifier • Record storage compartment • Instruction Manuals on assembly and on Hi-Fi sound reproduction. All equipment available on deferred terms.

EMI INSTITUTES
To: E.M.I. Institutes, Dept. H.F.32, London, W.4.
Please send, without any obligation, your free Brochure to:
NAME
ADDRESS
JUNE 58 IC122

A FREQUENCY COMPARATOR

A STANDARD method of comparing and checking frequencies in the laboratory is by means of Lissajous Figures on the screen of a cathode ray oscilloscope. For the experimenter, who does not possess an oscilloscope, or who has only one which is tied up in another part of the rig at the moment when he wishes to check on some frequencies, an alternative and simpler method is desirable. In this connection it is ironic to note that in the professional laboratory, where frequency standards are expensive and reliable, there is likely to be a sufficient number of C.R.O.'s for monitoring their accuracy; but that the amateur, whose oscillators and signal generators are likely to be home-made and distinctly sub-standard will seldom have more than one C.R.O., and quite often not even that. It is thought, therefore, that the instrument described in this article will be of great use both to the serviceman and to the home constructor.

In the first place, any such device, to be of value over a wide range of frequencies, must make use of the cathode ray tube in some form or another. No other device can offer the speed and freedom from inertia necessary for H.F. use. But fortunately, the cathode ray tube is available in a cheap and simple form perfectly suited to frequency measuring systems, a form requiring no EHT, no time-bases, no focusing devices, and no deflection arrangements. I refer to the "Magic Eye."

The Principle

Fig. 1 shows the principle of the device. The tube here is a 6E5. One frequency, f_1 is applied to the triode grid, and appears on the target grid via the amplifying section of the magic eye. The other frequency f_2 is applied to the target anode. If the two frequencies are approximately equal, this will result in periods when the target grid and anode are in-phase, alternating with periods when they are out of phase. The rate of alternation will be the beat frequency, the difference between f_1 and f_2 , and this will, of course, be clearly visible in the form of a regular flickering of the display. If we adjust the variable frequency to obtain zero beat, it is then equal to the comparison frequency.

This is simple enough, and quite useful. But the great usefulness of the principle in practice depends upon two further facts. The device works not only when $f_1 = f_2$, but also when $f_1 = kf_2$ (or when $kf_1 = f_2$), where k is any whole number from one up to ten or twelve; and every amateur has at least one good

frequency source, the 50 c/s mains. Hence, with the aid of a practical form of this instrument, we can use the mains to determine the accuracy of an audio oscillator in steps of 50 cycles up to 500 c/s; and hence, by means of a simple auxiliary oscillator, we can proceed up to 5,000 c/s, 50,000 c/s, etc. Likewise, from a single crystal oscillator, we can work downwards, in small enough steps to obtain excellent calibration, in checking a signal generator.

The Circuit

A suitable circuit, using a 6E5, is shown in Fig. 2. Here a triode is added to provide amplification for the f_2 signal. Any valve you have available in the spares box will do, and there is no need to work under linear conditions. A pentode may be used, either triode-strapped or otherwise. Far from needing linear amplifiers, this system works better when the distortion is high, particularly when beating against harmonics. It is for this reason that rectifiers are wired into the grid circuits. They are for the introduction of deliberate distortion in order to sensitise the apparatus to harmonics.

An Alternative

An alternative scheme is shown in Fig. 3, using an EM34 magic eye. In this version, the signals are mixed in the common anode load, and the beat is fed to the eye through a low-pass filter. This is advantageous where R.F. signals are being monitored, since no R.F. reaches the eye itself. The possible frequency range of this variation is limited only by the valve used in the earlier stage (mixer), and the style of wiring. Since this particular form of instrument is sensitive to ripple

A Simple Method of Frequency Checking Which Does Not Call for the Use of a Cathode-ray Oscilloscope. The Arrangement Described Here Makes Use of the Standard "Magic Eye" Tuning Indicator

By A. M. St. Clair

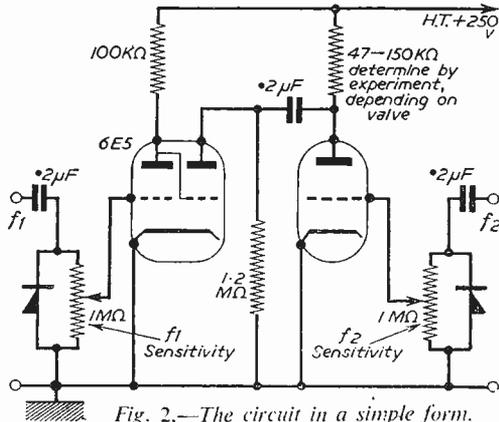


Fig. 2.—The circuit in a simple form.

and variations in the H.T. line, a neon stabiliser is included. This limits the H.T. on the mixer to the lit voltage of the tube used; this is preferably a 120 volt tube, but even an 85 volt one will serve. The value of R1 should be adjusted experimentally to a point where the neon is just stably lit, and this resistor should be heavy enough to carry the full neon current as well as

point. Advance the oscillator dial to a nominal 100 c/s. and repeat the process. Working in this way you will obtain an accurate point on the dial for every 50 cycles up to 500 c/s. Beyond that, another oscillator is required; but it does not have to be accurate or even calibrated. Of course, if you have a second oscillator also requiring calibration, it will serve, and each

oscillator will help in the calibration of the other. But if you have to build the auxiliary oscillator, keep it simple—a one-valve transformer coupled or R.C. job—because it does not even have to be stable for more than a few seconds on end.

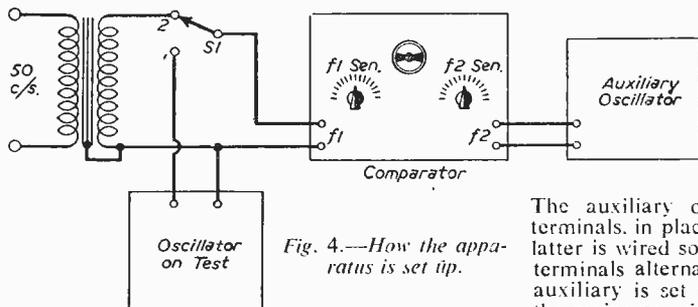


Fig. 4.—How the apparatus is set up.

the valve supply. Otherwise, the circuit, for the same reasons as given above—no linearity requirement—is singularly uncritical. If a stabilised power supply is available there is no need to include the neon stabiliser, in which case the double triode may be given the full source voltage, with an attendant increase in sensitivity.

Using the Unit

A word or two on how to use the equipment. Let us suppose that you have a home-built audio oscillator, such as has been often described in these pages, and that you wish to make an accurate calibration of its dial. Apply a voltage of about 2 to 5 volts A.C. derived from the 50 c/s mains via a suitable transformer to the f1 terminals. Apply the output of the oscillator to the f2 terminals. Adjust the output of the oscillator to a suitable level, and set it to a nominal 50 c/s as shown on the dial. A beat will be seen on the eye. Adjust the oscillator for zero beat, and mark the dial "50 c/s" at that

The set-up is as in Fig. 4. The auxiliary oscillator is wired across the f2 terminals, in place of the oscillator under test. The latter is wired so that it may be switched to the f1 terminals alternatively with the A.C. source. The auxiliary is set to 500 c/s by beating with either the mains or with the oscillator under test, which is now accurate at 500 c/s. With the switch in position 1, the oscillator under test is made to beat with consecutive harmonics of the auxiliary, giving accurate calibration points at 500, 1,000, 1,500, 2,000 c/s, and so on up to 5 or 6 Kc/s. If a finer division is required, the auxiliary oscillator will have to be set to a lower frequency, say, 100 or 250 c/s. To cover a wider range, the auxiliary should be modified to work at a higher frequency. Before each reading, immediately before, the switch should be set to position 2, and the auxiliary thus checked against the mains.

The proceedings for checking, either up or down, against a crystal standard, are exactly the same in principle. The comparator finds a very useful application, rather less laborious, in checking an oscillator against a known standard. Here, we merely beat the setting of the uncalibrated oscillator against the setting of the standard without using either harmonics or auxiliaries. Broadcast stations can perform useful service as "known standards."

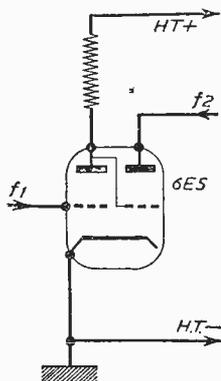


Fig. 1.—This circuit illustrates the principle of the arrangement described here.

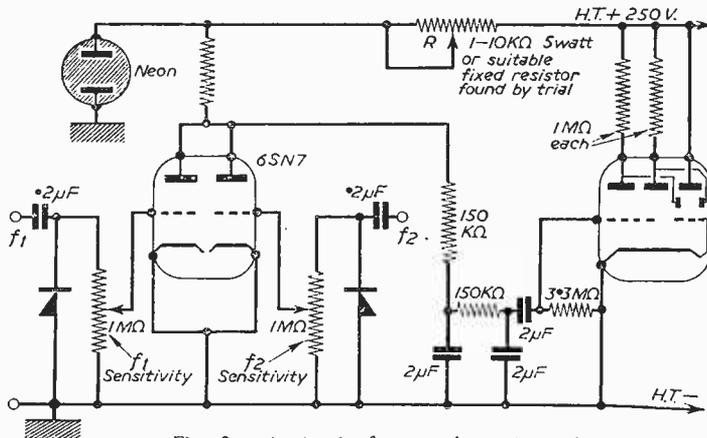


Fig. 3.—A circuit for an alternative scheme.

HOME RADIO OF MITCHAM

187 LONDON ROAD, MITCHAM, SURREY.


MIT 3282

London and Home Counties distributors for Panda Transmitters.

We are stockists for: EDDYSTON, PANDA, ARMSTRONG, DULCI, DENCO, J.B., STENTORIAN, REPANCO, TELETRON, GOODMAN'S, OSMOR, WHARFEDALE, GRAY-SHAW.


A NEW SPEAKER BY STENTORIAN

STRAIGHT FROM THE AUDIO FAIR

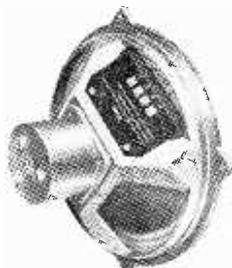


NO OTHER SPEAKER HAS ALL THESE FEATURES. 10in. Die-cast chassis. 16,000 gauss magnet. 10 watts handling capacity. Universal speech coil. 30 to 15,000 c.p.s. frequency response. 35 c.p.s. bass resonance. **PRICE £8.0.0.**

FAMOUS COSSOR AMPLIFIER AND SPEAKER KIT

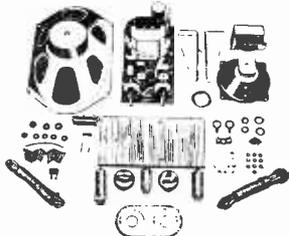

Model 562K. Contains all the components and material to build a 3-watt high quality amplifier complete with valves and two matched speakers. Easily constructed from detailed instructions. Printed circuit chassis. Delivery from stock. **PRICE £9.15.0** post paid.


START BUILDING THE AMAZING NEW MINI-7

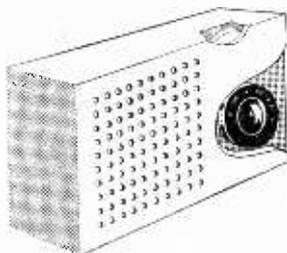

A 7 transistor superhet pocket portable with 2½in. speaker giving guaranteed results on its internal ferrite rod aerial. Can be easily assembled in four stages. Build one now ready for the holidays and amaze all your friends. **SEND NOW**—for full constructional details, point-to-point diagrams, wiring instructions and detailed price list, 1/9 post paid.

F.M. TUNER KITS

G.E.C. "F.M. PLUS" tuner. Fringe area high quality tuner with own power unit and specially designed for use with the "912 PLUS" amplifier but suitable for any Hi-Fi amplifier. Constructional data and price list 2/10. Also kits stocked for the famous JASON tuners. SWITCH TUNED version with a.f.c. and MANUAL TUNING version available. Full constructional data of either of these popular kits 2/4 post paid. Parts lists free on request.

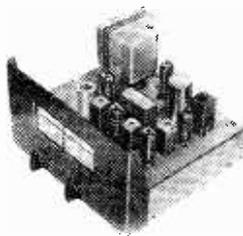

LOUDSPEAKERS

Brand new by famous makers. permanent magnet 3-ohm speech coil:

3½in. x 5in. 6½in. ...	17/6
7in. x 4in. elliptical ...	15/-
9in. x 5in. elliptical ...	25/-
8in. ...	21/-

Please add 2/- post on all speaker orders.

MULLARD '3-3' AMPLIFIER


Separate Bass and treble controls and suitable for gramophone, radio, or microphone inputs. Really amazing quality and performance. Ready wired, assembled and tested. **PRICE ONLY £8.8.0** post and packing 2/6.



PICK-UPS

Latest type lightweight crystal pick-ups with turn-over cartridge and sapphire stylus for standard and long playing records. **PRICE ONLY 3/6** (post 9d.).

CABINETS

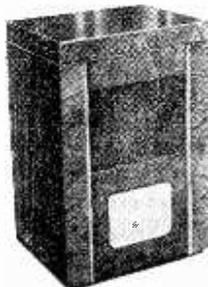

A full range of beautifully finished cabinets for speakers, record players, amplifiers, tuners, etc. Send 3d. stamp for fully illustrated leaflet including the new "Prelude" contemporary models. These cabinets are packed flat in cartons and can be quickly and easily assembled with only a screwdriver. Despatch by return. Carriage charge 3/6 (U.K. only).

SPECIAL MOTORISTS' AND CAMPERS' 3 COLOUR TORCHES

Long range focusing torches with novel device giving Red, Green, or White beam. Takes two U.2 batteries. Including bulb but less batteries **ONLY 5/-** post paid.

BATTERY PORTABLE KITS

TRANSEVEN 7-transistor portable with 7 x 4 speaker and low running costs from 7½ V. battery. Smart compact cabinet measuring 9in. x 7in. x 4in.

HIWAYMAN well tried 4 valve all-dry with ferrite rod aerial in straight-forward superhet circuit.

Full constructional data on either of these sets, 1/9 each post paid.

TRANSISTOR COMPONENTS

Full range of ARDENTE and REPANCO miniature components in stock and illustrated leaflets available on request.

IMPROVE YOUR COMMERCIAL TV.


High gain Band III pre-amplifier with own power pack. Amazing improvement. Easily assembled on ready punched chassis. Full data 1/6. Complete kit **£2.14.0** post paid.

THE LINEAR 'DIATONIC'

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

A special feature is the compactness of the unit. Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 9 x 7 x 6½ ins.

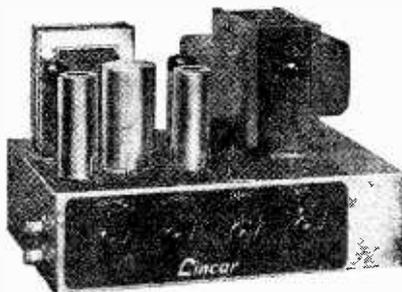In addition two high impedance input sockets are provided for microphone and gram, etc. Each input has its associated vol. control, live B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81, H.T. and L.T. power supply point is included for a radio tuner.



FREQUENCY RESPONSE
± 2 d.b., 30-20,000 c.p.s.

MAXIMUM POWER OUTPUT
In excess of 14 watts.
RATED OUTPUT 10 WATTS.

SENSITIVITY
Volume (1) 22 millivolts for rated output.
Volume (2) 220 millivolts for rated output.

TREBLE LIFT CONTROL
Continuously variable +6 d.b. to -13 d.b. at 12,000 c.p.s.

BASS CONTROL
Continuously variable +13 d.b. to -18 d.b. at 15 c.p.s.

HUM LEVEL
Referred to maximum output and including integral pre-amp - 60 d.b.

HARMONIC DISTORTION
0.19% measured at 6 watts.

NEGATIVE FEEDBACK
Total 32 d.b. including 24 d.b. in main loop.

Weight 12½ lbs. Power consumption 90 watts. For 200-230-250v. 50 c.p.s. A.C. mains.

Outputs for 3- and 15-ohm speakers. Chassis finish stoved Blue-Grey hammer.

HIGHEST QUALITY! Retail price
MAXIMUM RELIABILITY!
AT A PRICE YOU CAN AFFORD. Available through your local dealer, leading mail order firms, or direct from us. Send S.A.E. for descriptive literature.

12 GNS.

TRADE ENQUIRIES to

ELECTRON WORKS, ARMLEY LEEDS.

L45 MINIATURE 4/5-WATT QUALITY AMPLIFIER

Size only 6 x 5 x 5½ in. high. 12 d.b. Negative Feedback. Sensitivity 30 m.v. for full output. 3 Mullard valves. ECC83 Twin Triode. EL84 Power Output. EZ90 Rectifier. Separate Bass and Treble Controls. Mains switch incorporated in control. For 200-250 v. 50 c.p.s. A.C. Mains. An ideal unit for use with Gram, or "Mike". Output matching for 2-3 ohm speakers.

Retail Price **£5-19-6**

Also available: LG3 3-watt Gram Amplifier. 55/9. LT 45 Complete Tape Amplifier. 12 gns. "Conchord" 30-watt Amplifier. 15 gns.


LINEAR PRODUCTS LTD.

TELETRON TYPE FX. 25



Self-tuned, Dual-wave Ferrite Rod Aerial, 15/- each.

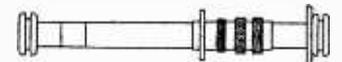Designed for use in pocket Transistor receivers. Descriptive folder with circuit-component layout, and wiring instructions for a three-Transistor regenerative receiver. Price 6d. NO aerial, caft or tuning condenser required. Operates speaker from 3 Penlight cells. All parts, including cabinet and chassis, available from component stockists.



Miniature Transistor IFTs & Osc coil for 315 kc/s, 6/6 ea. FRM/2 Transistor Ferrite Rod Aerial, 10/-. Available from component stockists. Stamp for complete lists and circuits.

THE TELETRON Co. Ltd.
266 Nightingale Rd., London N9
HOW 2527

CHASSIS

UNDRILLED ALUMINIUM CHASSIS

4 Sided Chassis	ca.
8in. x 4in. x 2½in. ...	6/-
8in. x 6in. x 2½in. ...	6/6
8in. x 8in. x 2½in. ...	7/-
10in. x 6½in. x 2in. ...	6/6
10in. x 8in. x 2½in. ...	7/6
11in. x 7in. x 1½in. ...	6/6
12in. x 8in. x 2½in. ...	8/-
14in. x 8in. x 2½in. ...	8/6
16½in. x 8in. x 2½in. ...	9/-

2 Sided Only	ca.
7in. x 4in. x 2in. ...	3/-
10in. x 8in. x 2½in. ...	4/9
16½in. x 8in. x 2½in. ...	6/9

One minute hole punches and screw-up type hole punches available from ¼ in. dia. to 2in. dia. in ¼ in. steps. Send for price list. Postage and packing charged extra 1/9. Send sketch of your requirements for prices by return to:

Oliver & Randall
LIMITED
40 Perry Hill, London
S.E.6

COPPER WIRE

ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED. RESISTANCE WIRES. 1 oz., 2 oz. & 4 oz. REELS. All gauges available. B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets. EBONITE AND BAKELITE PANELS. TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES. ALL DIAMETERS. Latest Radio Publications. SEND STAMP FOR LISTS.

SPECIAL OFFER

G.E.C., B.T.H. & WESTINGHOUSE
GERMANIUM CRYSTAL DIODES
1/- each. Postage 3d.

Diagrams and three Crystal Set Circuits Free with each diode. A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

CRYSTAL SET
INCORPORATING THE SILICON CRYSTAL VALVE
Adjustable Iron Cored Coil.
RECEPTION GUARANTEED
Polished wood cabinet, 15/-, post 1/6
A REAL CRYSTAL SET, NOT A TOY
POST RADIO SUPPLIES
33 Bourns Gardens, London, E.4

TRANSMITTING TOPICS

MODULATING WITH THE CLAMP TUBE

By O. J. Russell, B.Sc.(Hons.), G3BHJ



ONE of the reasons why the clamp tube is a permanent feature of the present-day transmitters is the fact that it may readily be used to provide modulation. This is in addition to its value and original purpose of providing a "safety" device that protects the P.A. valve from excessive dissipation when drive or bias fails.

To elucidate the mysteries of "series screen," "gating" clamp and similar modulators, it must be realised that they are all forms of screen modulation. Consider the simple transformer coupled screen modulator of Fig. 1. This may be simplified to the choke coupled modulator shown in Fig. 2. If the choke is replaced by a resistor, we get the basic "clamp tube" modulator of Fig. 3. Thus the clamp tube system is purely "resistance coupled" screen modulation. Viewed in this way, there would hardly seem to be any need to stress this. However, a legend seems to have arisen in which "clamp modulation" is regarded as having esoteric and wonderful properties quite unrelated to screen modulation, and presumably conferring mysterious and nebulous benefits not to mention greater efficiency, than ordinary "old fashioned" screen modulators.

The cautious reader may now in fact begin to suspect that "simplifying" screen modulation down to a resistance coupled version may mean a sacrifice of efficiency. This is in fact the case, and a simple clamp tube modulator is not as effective as a straightforward transformer coupled

screen modulator as shown in Fig. 1. Before considering this further, it is as well to consider the limitations and properties of screen modulation from first principles. Without repeating the "step by step" detailed arguments which the writer has previously given, the following points should be noted. Screen modulation is an "efficiency" method, and the simple forms suffer from the following limitation . . . that the actual R.F. carrier output is one-quarter of the carrier output that the P.A. valve is capable of giving under normal C.W. conditions at the same H.T. voltage. Due to efficiency considerations the maximum carrier output the P.A. valve is capable of giving at "all out" conditions is one-half that obtainable under C.W. conditions. To make this clear, if we have a P.A. stage running flat out at full anode dissipation at 100 watts under normal C.W. conditions, then with the same H.T. voltage under screen modulation conditions we shall only be able to run at 50 watts input, and at half the R.F. efficiency of normal operation. Hence our actual R.F. carrier output is that of a normal 25 watts P.A. stage. If we run under maximum possible dissipation and output, a substantial increase in H.T. voltage is necessary. Thus to take a familiar example, the humble 807 needs voltages of some 1,200 volts for "good" efficiency modulation. Below some 1,000 volts of H.T. the characteristics of the tube are not fully exploited. This is a far cry from the "simple low power rigs" that utilise "simple and economical" screen or clamp modulators. Thus some of the 10 watt topband rigs with clamp modulators are equiva-

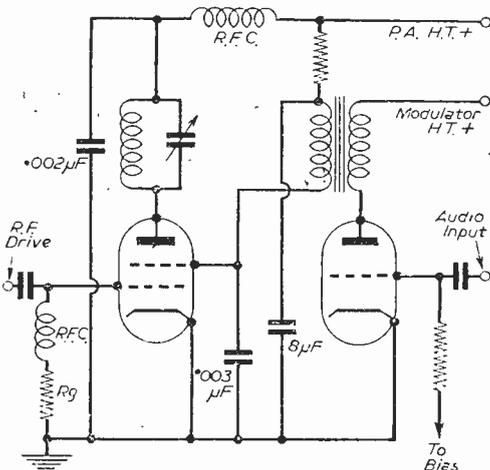


Fig. 1.—A conventional transformer coupled screen modulation circuit.

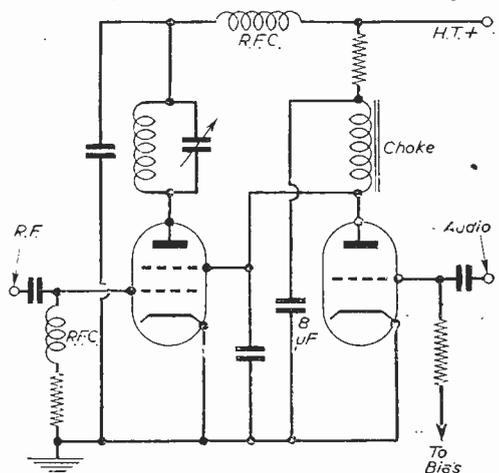


Fig. 2.—A choke coupled screen modulator.

lent to, say, 5 watt anode modulated rigs. Thus a 6V6 "clamp tube" might just as well be utilised as an anode modulator when it would be capable of directly anode modulating at least a 9 watt P.A. stage running at full C.W. efficiency.

Advantages

Considerations such as the above thus tend to deflate the much boosted value of "clamp tube" modulators for users of simple low power rigs. Thus the Tx running at 40 watt P.A. input under clamp modulation, is at best equivalent to a 20 watt P.A. stage, and if a 6L6 clamp tube is

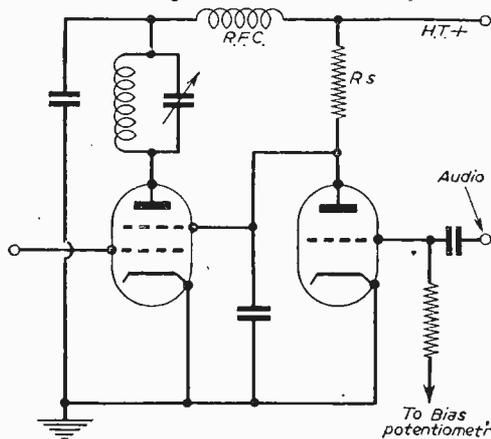


Fig. 3.—The conventional clamp tube modulator is, in effect, a resistance coupled screen grid modulator.

used that could modulate a 20 watt P.A. stage. What benefit is clamp tube modulation therefore, and surely it gives "better" results than that. At the risk of an explosion from the "defenders of clamp tubes," the efficiency figure for simple clamp tube modulators are as given. The chief advantage of the clamp tube modulator is that it is a simple system giving good speech with very simple audio equipment. To counterbalance the loss of carrier output, no separate modulator, powerpack and modulation transformer are required. Thus screen modulation systems merely require a small speech amplifier ahead of the clamp tube to provide clamp tube modulation. However, the fact that a simple system will provide good speech does not mean that a price is not paid in the form of loss of carrier. Moreover, the "efficiency" arguments indicate that the clamp tube system is hardly worthwhile for the low-power man, whereas a high-power C.W. rig can still run a respectable, though reduced, carrier output. An input of 150 watts clamp modulated, for example, equals a 75 watt anode modulated input... at least ideally. Thus, with high inputs, a clamp tube modulated rig can give a respectable amount of modulated carrier. Note, however, that there is a hidden fallacy to beware of. Just because one can run 150 watts of C.W. that does not mean that one can run 150 watts input of clamp tube modulated telephony. To be able to do that, the P.A. valve would have to be "over-sized," and capable of some 300 watts of C.W.

input. Thus the owner of a pair of 807's capable of just 150 watts of C.W. input would be able to run only about 75 watts of clamp modulated P.A. input. An amateur using an 813 in his P.A. stage, and with a power pack capable of some 2,000 volts output, could readily run an input of around 150 watts of clamp tube modulated input.

The above may seem to be discouraging to the amateur who has hoped that clamp tube modulation can automatically be applied to provide full modulation of his normal C.W. input. Unless his normal C.W. input is an unduly conservative one, both efficiency and power input must be reduced to obtain effective modulation. With this limitation, effective speech may be readily obtained. This leads us to consider how the amateur may "set up" his clamp tube modulator system for good modulation.

Satisfactory Circuits

As indicated, the audio input from a small speech amplifier (Fig. 4) is applied to the grid of the clamp tube. The circuit of Fig. 4 should be adequate to modulate the usual clamp tube circuits. It is best to adjust such systems by running the transmitter into some form of artificial load. According to the power level to be expected, a 12 watt car bulb or a 25, or 50 watt domestic light bulb should be tapped in across the aerial tuner in place of an aerial. Load up the full C.W. input with the clamp potentiometer turned for full carrier input, i.e., with the clamp tube fully cut off. This is the normal C.W. operation, and the electric lamp used as artificial load should be lit to full brilliance. With the receiver aerial removed, and the gain turned down, it should be possible to monitor the carrier. Alternatively a pair of phones and a germanium rectifier plus an R.F. pickup coil should enable the speech to be monitored. To adjust to approximately the correct clamp tube setting for modulation, turn the clamp tube bias potentiometer so that the clamp tube starts to conduct. This will be shown by the P.A. plate milliammeter falling back from its normal C.W. reading. Ruthlessly reduce the P.A. current input to half the normal C.W. current reading. This is a good position to start modulation tests. To attempt modulation, cautiously advance the audio gain of the speech amplifier feeding the clamp tube, and listen to the quality of the speech on the monitor. If good, clear speech is obtained, observe the lamp used as a load. This should flicker upwards in brilliancy on speech. If no noticeable flicker is obtained, the modulation percentage is quite low. If this low modulation percentage gives very loud headphone signals on your monitor, reduce the gain or pickup of the monitor so that speech is reproduced at a low level. To avoid confusion an assistant may be pressed into service to speak into the microphone, or even a broadcast programme may be utilised as the audio input, provided one is sure no radiation of R.F. from your transmitter is occurring. Finally, one should be able to get enough audio gain to produce noticeable flickering of the load lamp. However, watch the P.A. plate meter.

(Continued on page 305)

WHY PAY MORE! Visit our SELF SERVICE SURPLUS STORES

INDICATOR UNIT 277

Consisting of Fin. C.R. Tube, type VCR522, 6 valves; 4 EF50, 2 VR92. Incorporates Focus, Brightness and Gain Controls. Size, 7 1/2 x 5 in. Manufactured by Cossor. Only 65/-. P. & P. 3/6.

VIBRATOR POWER PACK. Input 12 v., output 150 v. at 100 milliamps. 2 bias packs 50 v. each. Complete with screen lead for battery. Completely smoothed. Brand new. Price 20/-. Postage and packing 3/6.

POCKET VOLT TEST METER Two D.C. ranges: 0-250 v. and 0-15 v. Complete with test prods. Brand New. Very limited quantity. ONLY 10/6. P. & P. 1/6.

CONVERTERS. Easily the most useful units released by the Ministry. Within minutes you can extend the frequency of any receiver to cover the following: R.F.26, 50-65 Mc/s, 20/- each. R.F.25, 40-50 Mc/s, 8/6 each. Complete with valves and circuit. 3/6 Postage on each.

500 MICROAMPS METER. 2in. circular calibrated 0-15 and 0-600 volts. New and boxed. 17/6. P. & P. 2/6.

BENDIX RECEIVER RA10. A-4 waveband superhet covering 150 Kc/s-10 Mc/s. Valves 6SK7 1st R.F. 6KB Mixer. 6SK7 1st and 2nd I.F. 6R7 2nd Det. 6C5 B.F.O. 6K6 output. Size 6 1/2 x 15 1/2 in. Easily converted to mains operation as described on page 453 of the September "Practical Wireless." £5/10/-. Carr. 7/6.


HIGH RESISTANCE HEADPHONES. 4,000 ohms. Brand new, 11/6 each. P. & P. 2/-.

COMPLETE HEADPHONE AND MICROPHONE ASSEMBLY. A must for every Constructor and "Ham." consists of moving coil, padded headphones and "press to talk" microphone. 10/-. P. & P. 3/6.

0-1 M.A. METER. 2in. square flush mounting. Brand New, 22/6. P. & P. 1/6.

WHEATSTONE BRIDGE. Consisting of four stud switches: 0-10 ohms, 0-100 ohms, 0-INF. Galvanometer centre zero F.S.D. 2.5 mA. Ranges easily extended. Housed in oak cabinet 16 x 7 1/2 x 6in. Complete with instructions, 40/-. P. & P. 4/-.

WALKIE/TALKIE SET

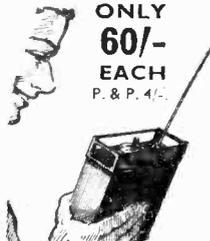

ONLY 60/- EACH P. & P. 4/-

consisting of transceiver covering 7.4-9 Mc/s. range approx. 10 miles. complete with 5 valves, headphones, microphone, junction box, & 6ft. telescopic aerial. Only requires 120 v. & 3 v. dry battery. These magnificent Walkie/Talkie sets (as used by H.M. Forces) are ideal for any application and can be operated with ease by young and old alike. **TWO FOR £6, POST FREE.**

COMMUNICATION RECEIVER R.1155

This magnificent receiver covers 5 ranges: 75-200 Kc/s, 200-500 Kc/s, 600-1,500 Kc/s, 3-7.5 Mc/s, 7.5-18.5 Mc/s. Fully tested before despatch. Complete with N type drive circuit and instruction booklet £8/10/-. Carr. 10/-.

UNSPILLABLE ACCUMULATORS

2 volts 16 A.H. Ideal for 6 and 12 volts supply, etc. Brand new original cartons. Size 4in. x 7in. x 2in. 5/6 each. P. & P. 2/6. 3 for 15/-. P. & P. 3/6. 6 for 27/6. P. & P. 5/-.

WIRELESS SET NO. 19

As described and recommended for Amateur use in April and May issues of "Practical Wireless." This famous Transmitter-Receiver incorporates "A" Set—TX/RX covering 2-8 Mc/s (37.5-150 metres). "B" Set—VHF TX/RX covering 230-240 Mc/s (1.2-1.3 metres) and intercom. amplifier. Complete with 15 valves, 500 microamp check and tuning meter, circuits and instruction book. (American manufacture.) In magnificent condition, 60/-. carr. 10/-.

ATTACHMENTS FOR ABOVE :

Variometers	20/-
Headphone and microphone assembly	13/6
Morse key assembly	4/6
12ft. aerial	7/6

Simple TWO-WAY TELEPHONE KIT



25/- P. & P. 3/6

Install your own intercom with this brand new kit consisting of 2 "press to talk" hand telephones, long life battery, 100ft. of cable and simple wiring details.

Ideal for garage, office, workshop, factory, farm, camping, and home. Will give endless hours of pleasure and has proved reliable under all conditions.

INFRA RED MONOCULAR

Ideal for night viewing, etc. Complete with push button power unit and focus lenses. Brand new in beautiful carrying case. Originally cost Govt. £40. Our Price, 25/-. P. & P. 3/6.

AMERICAN MIDGET ACCUMULATORS. 36 volts, lead acid type. 2/6 ea. P. & P. 1/-.

R.C.A. MAINS TRANSFORMERS. Input 110-240 v., output 345-0-345 v. at 150 mA., 6.4 v. at 4.5 amps., 5 v. at 2 amps. Brand new, fully shrouded. Limited quantity. Write now. Only 35/-. P. & P. 3/-.

R.T.-7/APN-1 ALTIMETER TRANSCIVER. Brand new complete with 14 valves: 3 12SJ7, 4 12SH7, 2 12H6, 1 VR150, 2 9004, 2 955. Famous Wobblulator Unit. Dynamotor, Relays 3,500 ohms and 6,500 ohms. A.F. amplifier. Receiver section covers 400-450 Mc/s. Transmitter sweeps 418 to 462 Mc/s. Ideal for model control work, etc. Only 35/-. carriage 10/-.

RELAYS. 6,500 ohms and 3,500 ohms. 8/- pair. Post paid.

SIGNAL GENERATOR AND WAVEMETER. Type W 1649. Frequency of Signal generator: 140 to 240 Mc/s. Accuracy: 0.5 Mc/s. Frequency of Heterodyne Wavemeter: 155-255 Mc/s. Accuracy ± 0.2 Mc/s. Containing VR135 and 4 VR91. 5 meg. crystal. Retractable aerial. Power requirements: 6.3 volts and 120 volts. Unit housed in copper-lined wooden case. Size 15 1/2 in. x 13 in. x 14 1/2 in., 45/-. Plus 10/-. P. & P.

LUMINOUS MAGNETIC MARCHING COMPASS. Pocket size. Brand new with instructions. Only 12/6. P. & P. 1/-.

MUIRHEAD VERNIER SLOW MOTION DRIVES. Scaled 0-180 deg. Ratio 25 to 1. 3in. dia. 10/6. P. & P. 1/6.

INDICATOR UNIT SLC No. 5. Ideal for conversion into an Oscilloscope using a 139A or ACR10 tube. Unit consists of 2 VR65, 1 VR66, various resistors, condensers and pots. Size 11 6 x 3in. Brand new, complete with modification circuit, 20/-. P. & P. 3/- each.

ARMOUR RECORDING WIRE. U.S.A. top quality on original reels. Length 3,700 yds. 10/-. P. & P. 1/6.



32A, COPTIC STREET, LONDON, W.C.1.
AND
87, TOTTENHAM CT. RD., LONDON, W.1.

All post orders and correspondence to:
(Dept. "P") 32A, Coptic Street, London, W.C.1.

ELECTRIC PAINT SPRAYER

New model for up and down spraying of all painting jobs in & out-doors, 3'-down & 8' up. 9/6 or Cash Price Reduction Offer at 67/6.



3/- down



Post 1/- **10/-**

.001-1" MICROMETER
Invaluable to engineers apprentices, model makers, Precision Instrument for Schools, Garages, Workshops, Students, Handymen, Engineers. Valuable Micrometer Bargain. also 2in. Model 14.6.

This New Blowlamp

Post 9d.
is 5 1/2 in. high, weighs only 7 ozs. and is sturdily made from solid brass tube. No working parts to go wrong. Ideal for tinning and sweating, silver soldering, paint stripping, glass bending and drawing. Uses methylated spirits only. **14/7**

MAJOR Model 6 times stronger Flame. 39/-

Chassis Cutters with Keys

The easiest and quickest way of cutting holes in sheet metal. The cutter consists of three parts: a die, a punch and an Allen screw. The operation is quite simple. Prices incl. key: Size in. 13/9; 1/2 in. 14/9; 1 in. 1 1/4 in. 17/6; 1 1/2 in. 1 3/4 in. 19/6; 2 in. 23/-; 2 3/4 in. 35/9; 3 in. 40/9; 1 in. sq. hole. 27/- Post 1/-.

All prices are with key.


PIFCO

All-in-one Radiometer A.C./D.C.
★ Circuit Test.
★ L.T. and H.T. Tests.
★ M.A. Test.
★ Valve Test.
Continuity and Resistance Tests. Complete with Test Leads. Post 1/- Guaranteed **32/6**



SERVICE SHEETS
The one you require enclosed if available in a dozen assorted of our best choice. **10/6**

NEW ALL-ELECTRIC COPING SAW

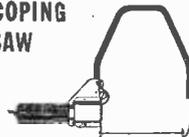

Cuts in Timber, Hardboard, Hurl and Soft Woods, Plastics, Fibrework, Asbestos and Soft Metals. High-speed action. Complete with 4 Standard Blades, 52/6, or 10/- down & 5 monthly of 13/- Post 2/6.

AVO Multimeter 19 Range Meter

£9.10 or 10/- down & 19 weekly payments of 10/-. Like all AVO meters it is a very fine instrument: it has a sensitivity of 10,000 ohms per volt and 19 most useful ranges as follows: D.C. volts 0-1,000 (seven ranges), A.C. volts 0-1,000 (five ranges), D.C. Current 0-1 amp. (5 ranges), Resistance 0-2 megs. (2 ranges) (complete with test leads), Immediate delivery.

COLLARO "Junior"

4-speed motor and pick-up with HGP59 cartridge. **92/6**

2 watt AMPLIFIER

with one EL84 and one Metal Rectifier. **52/6**
A Superior Unit

RADIO BULLS VALVES
246, HIGH ST. HARLESDEN ROAD

DEMOBbed VALVES 2/6 MANUAL

Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents, and Comprehensive Price List. We have still some Valves left at very old Budget Rates (93%) which are actually sold at the old price (1951). Also ready our new comprehensive BVA List.

SALE

of VALVES both RADIO and TV Types

As listed below

From

4/- to 21/-



1D5	10	42	12/-	PenA4	10/-
1L4	4	43	12/-	PenVA	10/-
6A7	15	45/5	15/-	Pen36C	10/-
6X7	7	70L7	21/-	Pen36C	10/-
6V6	8	75	12/-	Pen36C	10/-
25Y5	10	80	10/-	Pen36C	10/-
23A7	21	MX40	10/-	Pen36C	10/-

and full range of T.V. & Radio Valves. Post 1/-

Train for a Wonderful future in RADIO & TELEVISION ...

Radio and Television techniques are continually advancing and their applications ever increasing. These fields offer to the trained technician a career with an assured and remunerative future.

Here is your opportunity to enter for:—

1 YEAR COURSE Full-time day course in the Principles and Practice of Radio and Television. Designed for the training of Radio and Television Servicing Engineers and others similarly engaged in the Electronics industry. Next course commences September 9th, 1958; others in January and May, 1959.


The E.M.I. College of Electronics, Dept. 32, 10, Pembroke Square, London, W.2.
Telephone: BAYswater 5131/2.

The College is part of the E.M.I. Group... Britain's foremost electronic engineers... Pioneers of the world's first public television service.



MINIATURE COILS FOR TRANSISTOR RADIO CIRCUITS

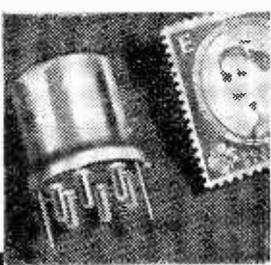These are the smallest screened coils available on the British market or the Continent.



DIMENSIONS Height (Excluding Lugs), 5,8".
Diameter (Top), 9/16".
Diameter (Base), 5,8".

- ★ Latest high-efficiency ferrite pot cores and litz windings
- ★ High Q for maximum gain and selectivity.
- ★ Coupling ratios carefully designed to match latest R.F. transistors. I.F. 460/470 Kc/s.
- ★ Low-loss moulded nylon formers.

THREE TYPES AVAILABLE:
List: 735 Oscillator Coil, List Price 11/3 each
736 1st or 2nd I.F. transformer, postage 6d. extra.
737 3rd I.F. transformer.

Connection diagram supplied.
DELIVERY: Ex Stock, C.W.O. or C.O.D. (1/6 extra).
Trade, Manufacturers, and Export enquiries invited

Orders and enquiries direct to the manufacturers:

CHANNEL ELECTRONIC INDUSTRIES Ltd.,
Components Division
DUNSTAN ROAD, BURNHAM-ON-SEA, SOMERSET. Phone 3167.

It will be found that with enough audio input, and with adjustment of the clamp tube bias control, the P.A. plate meter will kick strongly. This is an indication of incorrect bias setting, and not (as some imagine) a demonstration of "modulation." This warning is necessary, as some operators with a kicking meter gleefully quote "peak modulated input" readings from the "maximum kick height" and delude themselves into believing they are running very efficiently. Actually the kicks are a warning that adjustments are not right. If the meter kicks violently upward, adjust the clamp tube bias potentiometer so that the P.A. draws more current. If the P.A. stage is drawing too much current, the P.A. meter will kick downwards, and the bias control for the clamp tube should be adjusted so that the P.A. stage draws less current. Finally, with the P.A. stage adjusted for minimum kicking, if the audio input is increased too much, kicking will take place irrespective of the bias control setting. In general the P.A. meter kicking slightly upwards seems to be a favourite position for good modulation and efficiency. However, this position is not far from the original trial position obtained by turning on the clamp tube so that the P.A. input is around half the normal full C.W. input. Cautious adjustment on the above lines, coupled with monitoring the signal on a simple crystal monitor will reveal much more about clamp modulation than might be suspected. If a cathode-ray tube modulation monitor is available, the results will amaze those who imagine that a wildly kicking P.A. meter is a sign of a high modulation depth, as it will reveal a very lopsided modulation envelope. Moreover a cathode-ray modulation check will reveal that the modulation depth falls short of the 100 per cent. mark, no matter how much distortion is tolerated.

The fact that the modulation depth does not

exceed the 100 per cent. mark, or in fact with the simple clamp tube modulator falls far short of it, is even hailed as an advantage by some. The severe clipping that occurs with excessive audio input produces exactly the same pernicious effects as overmodulation, viz., splatter and spread. The clamp tube modulator merely provides these effects below the full modulation mark, in at any rate the simple circuits generally described. As these effects are clearly audible to

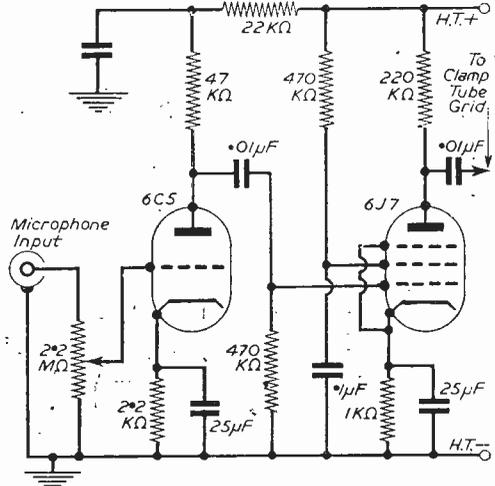


Fig. 4.—A simple two-stage speech amplifier preceding the clamp valve is adequate to give good modulation from a crystal microphone. The current taken need only be a few milliamperes at, say, 250 volts. The preamplifier may generally be fed from the transmitter power supplies without need for a separate power pack.

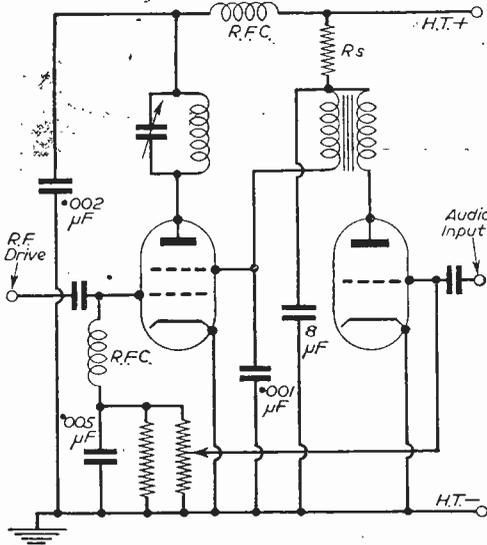


Fig. 5.—Transformer coupling combined with the conventional clamp valve permits of more effective screen modulation.

anyone with a monitor and a clamp tube modulated transmitter, the "advantage" of "not over-modulating" is largely illusory.

What is serious is the fact that one does not obtain full modulation with the simple clamp tube circuit. Even if the anode of the clamp tube could provide distortionless audio even when its anode swung down to zero volts, the carrier would still not be 100 per cent. modulated in a downward direction. This is because the screen must be swung appreciably negative to reduce carrier output to a full stop. With the generally used clamp tubes, an inspection of their triode characteristics reveals that generally the limit of reasonably distortionless swing in the negative direction is at a point where the screen and clamp anode are at a potential of around 50 volts positive. This seriously limits modulation depth ideally to some 66 per cent. in the downward direction for linear modulation. It is in fact why the "best" position of clamp bias adjustment is set so that there is a gentle upward kicking of the P.A. meter. By this means the upward or positive modulation is at its full level, with slight clipping of the negative peaks that would otherwise swing below the 50 volt mark. This somewhat increases distortion, but gives a somewhat higher effective modulation level.

Full Modulation

Once adjustments reach the "somewhat" class, they are obviously at the mercy of the individual temperament of the operator, and tend to lead to the wildly kicking plate meter of the man who thinks he is getting his money's worth of modulation if the meter swings violently. This poses the question of whether there is a clamp tube circuit that will modulate fully. This question is settled by combining classical transformer coupled modulation with the clamp tube principle as shown in Fig. 5. This circuit will behave precisely as a normal clamp tube controlled P.A. By using a small audio coupling transformer, say, a step-up ratio of around two to one, the screen may be supplied with ample power. Where a

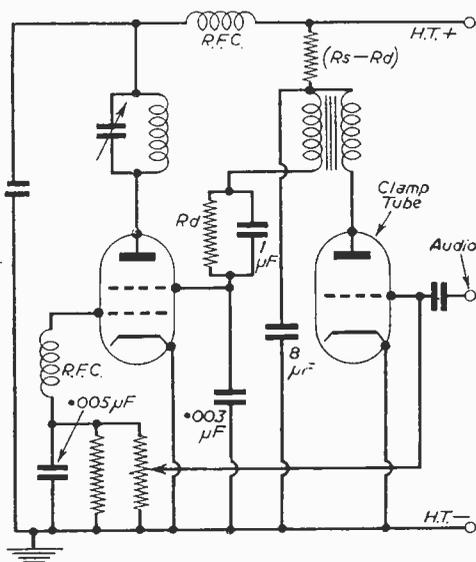


Fig. 6.—A small by-passed auxiliary dropper resistor (R_d) enables fuller modulation to be obtained. If R_d exceeds 1,000 ohms, the screen resistor should be reduced in value to compensate.

small amount extra of modulation depth is still needed, an auxiliary by-passed dropper resistance may be inserted in series with the screen feed, as shown in Fig. 6. This by-passed series resistor cannot be made too big, as it will result in an excessive drop of screen potential unless adjustments are made to the main screen dropping resistor value. If the resulting increase in "stand-by" current may be tolerated, it is quite practicable to use an auxiliary screen dropper resistor by-passed for audio, and obtain full screen modulation with purely resistance coupled clamp tube modulation. This is illustrated in Fig. 7, and is recommended as a simple improvement that may be readily applied to existing "simple" clamp tube modulator circuits.

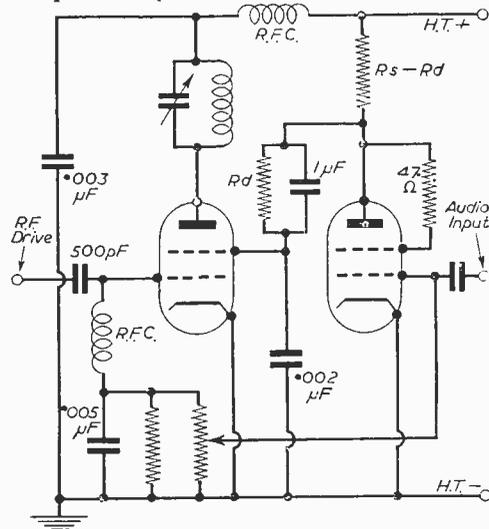


Fig. 7.—A by-passed auxiliary screen dropping resistor will enable even the simple clamp tube modulator to give deeper modulation. The clamp tube operates at a higher voltage than the P.A. screen, and is thus enabled to swing the screen volts to nearly zero volts. The auxiliary resistor should be a few thousand ohms.

News from the Clubs

EALING YOUTH RADIO SOCIETY

THIS club, whose main interests are: (1) Radio Construction, (2) Radio and TV Maintenance, (3) Amateur Radio Communication, would welcome new members. The meetings are held every Monday, 7.30 p.m. at the Brentside Centre (old Nursery School), Bordsars Road, Hanwell, W.7. The club is sponsored by the Ealing Youth Sub-committee, and is open to boys between the ages of 14 and 20 years.

BRIGHTON AND DISTRICT RADIO CLUB

Hon. Sec.: R. Purdy, 37, Bond Street, Brighton, 1.

MORSE classes and "Fundamentals" classes are held on all evenings where possible to fit in with the existing programme.

As always, visitors and prospective members are invited to "drop in." May fixtures are as follows:

Tuesday, May 6th—Mullard Sound Film on the manufacture of television cathode ray tubes entitled "Made for Life."

Committee meeting to arrange future programme.

Tuesday, May 13th—A talk by Mr. H. R. Henly, title to be announced.

Tuesday, May 20th—Mr. J. P. Clement, the "C.R.O."

Tuesday, May 27th—National Field Day. Final details to be arranged.

NORTHAMPTON SHORT WAVE RADIO CLUB (G3GWB)

Hon. Sec.: S. F. Berridge (G3ITW), 20, Ethel Street, Northampton.

OWING to altered domestic arrangements of the owner of the premises, meetings are still held at the Club Rooms, Allen's Pram Works, 8, Duke Street, Northampton, but on *Thursdays* instead of on *Fridays*. It is hoped to revert to the usual *Friday* meetings at the end of October. A No. 19 set is being prepared for portable operation during the summer months as "field days" are planned using the Club call-sign G3GWB P.

TORBAY AMATEUR RADIO SOCIETY

Hon. Sec.: G. A. Western (G3LFL), 118, Salisbury Avenue, Barton, Torquay.

THE Annual Dinner and Social held at the Oswalds Hotel,

Torquay, was attended by over 50 members, XYL's and visiting hams and proved a marked success. The President, W. B. Sidenham (G5SY), expressed his pleasure in having such a well attended function, this being responded to by the Acting Chairman, F. D. Cawley (G2GM), who in his brief review of Club activities commented favourably upon the large increase of members during the past year. He extended a warm welcome to the committee members of the Exeter R.S.G.B. Group, which included the county representative, B. Muaro (G3FLK).

RETURN-OF-POST SERVICE

JASON FM TUNER KIT

We can wholeheartedly recommend this tuner as being one of the most satisfactory of all the FM Kits. Construction is easy and results first class. Our Kit is really complete, the Instruction Book, all components, valves and small items such as wire, nuts, bolts and solder being included. Definitely nothing else to buy.

COMPLETE KIT, £6.19.6. Post free. Credit Terms. Deposit 19.6 and seven monthly payments of £1.0.0.

All parts are available separately and our fully detailed list is available free upon request. Instruction Book can be supplied for 2/- plus 3d. postage.

AMPLIFIERS

MULLARD 510 and GEC 912 PLUS

We carry full stocks for all versions of these popular Amplifiers and our price lists are available free.

NEW MULLARD

2 VALVE PRE-AMPLIFIER

Latest Mullard circuit for use with the 510 Amplifier. Booklet giving full details now available 1.3 post free. Complete Kit, including drilled chassis and control panel, £8.12.0. Credit Terms Deposit 19/- and seven monthly payments of 19/-.

NEW COSSOR AMPLIFIER KIT

2-valve amplifier ready built, supplied with valves, speaker and separate tweeter for home assembly on baffle or in cabinet. Complete instructions included. £9.15.0. Credit Terms. Deposit £1.9.8 and seven monthly payments of £1.6.6.

GRAMOPHONE EQUIPMENT

BSR MONARCH RECORD CHANGER. Latest four-speed model. £8.12.6. Credit Terms. Deposit, £1.4.6 and seven monthly payments of £1.4.0.

COLLARO "CONQUEST." Latest Collaro model with Studio Pick-up. £9.19.6. Credit Terms. Deposit £1.10.6 and seven monthly payments of £1.7.0.

SINGLE RECORD PLAYERS

GARRARD 4SP.—The latest Garrard four-speed player unit. Fitted with Garrard GC2 Crystal Pick-up. £8.1.9. Credit Terms. Deposit, £1.4.3 and seven monthly payments of £1.2.6.

COLLARO 4564.—Four-speed unit fitted with the well-known Studio Pick-up "O" or "P" £9.7.0. Credit Terms. Deposit, £1.9.8 and seven monthly payments of £1.6.6. Special Offer of the same unit fitted with "T" (High output) Pick-up only, £7.19.9. Credit Terms. Deposit, £1.5.6 and seven monthly payments of £1.2.0.

BSR T12.—Four speed motor with separate Pick-up fitted with BSR TC8 cartridge. £4.15.0. Credit Terms. Deposit, £1.5.0 and three monthly payments of £1.6.6.

COLLARO JUNIOR.—Four-speed motor with separate pick-up. The Pick-up is an ACOS model and is fitted with the HG P59 Cartridge. £4.13.6. Credit Terms. Deposit, £1.3.6 and three monthly payments of £1.6.6.

TRANSCRIPTION UNIT

COLLARO 4T 200.—4-speed with transcription pick-up. £19.10.0. Credit Terms. Deposit £2.12.0 and seven monthly payments of £2.12.0.

MULLARD TAPE AMPLIFIER TYPE "C"

THE MULLARD TAPE AMPLIFIER TYPE C is a new version of the Type B Amplifier. It comprises a recording amplifier and a play-back Pre-amplifier, and is intended to use an existing amplifier for play-back. It uses a Ferroxcube Inductor in the treble boost circuit and has a switch for the speed equalising circuits in place of the plug-in unit on the Type B Amplifier. The circuit gives details for use with Brenell, Collaro, Truvox and Lane Tape Decks.

INSTRUCTION MANUAL is available from us free of charge. Please send 4d. in stamps to cover cost of postage. **COMPLETE KIT** containing all components, control panel and sundries kit.

KIT A.—With alternative valves. £14.0.0.

KIT B.—With Mullard valves. £15.15.0.

All items available separately. Detailed list free.

POWER PACK KIT, £4.0.0. Items available separately. Send for list.

CREDIT TERMS.—Kit A. Deposit £2.1.6 and seven monthly payments of £1.17.6. Kit B. Deposit £2.7.0 and seven monthly payments of £2.2.0.

NEW JASON "MERCURY" FM SWITCHED TUNER KIT

This fine new switched tuner provides all three BBC programmes at the turn of a switch. The front end unit is supplied ready wired and tested. See our advertisement in December PRACTICAL WIRELESS or send for full details. Instruction book 2/3 post free.

COMPLETE KIT, £9.19.0 POST FREE

CREDIT TERMS. Deposit £1.10.0 and seven monthly payments of £1.7.0.

LATEST AVO TEST METERS

AVO METER MODEL 8 MARK II

The latest version of this finest of all test meters is now available from stock. 50 microamp movement (20,000 ohms per volt). Eight DC Voltage, Seven DC Current, Seven AC Voltage, Four AC Current and three ohms ranges. Fully detailed literature available free. Price £23.10.0. Credit Terms. Deposit £3.9.0 and seven monthly payments of £3.3.0. Leather carrying case, £3.0.0.

AVO MULTIMETER

A new and very attractive pocket size instrument at a modest price. Movement is 100 microamps (10,000 ohms per volt). Six DC Voltage. Five AC Voltage. Five DC Current and two ohms ranges. Descriptive leaflet available free upon request.

Price £9.10.0 Credit Terms. Deposit £1.8.0 and seven monthly payments of £1.6.0. Leather carrying case, 32.6.

TRANSISTORS

SURPLUS TYPES

RF Junction Type, Red Yellow Spot, 21 - AF Junction Type, Yellow, Green Spot. Pair in push-pull gives 250 mW, 10/- each.

MULLARD TYPES

OC79, 21 - OC71, 24 - OC72 Matched Pairs, 6/-.

All transistors post free.

CREDIT TERMS

Any of the above items can be supplied on Credit Terms. Details are as follows:—

SEVEN MONTHLY PAYMENTS. Deposit 3/- in the £ and balance plus a small service charge (10% of balance, but minimum charge 1d) payable in seven monthly payments.

THREE MONTHLY PAYMENTS. Deposit 6/- in the £ and balance plus a small service charge (5% of balance, but minimum charge 10/-) payable in three monthly payments.

TERMS OF BUSINESS.—Cash with order or C.O.D. Postage extra under £3. We charge C.O.D. orders as follows. Up to £1, postage and C.O.D. fee, minimum 28. Over £3 and under £5, C.O.D. fee only 15. Over £5 no charge.

WATTS RADIO (MAIL ORDER) LTD.


54 CHURCH STREET, WEYBRIDGE, SURREY. Telephone: Weybridge 4556

PLEASE NOTE. POSTAL BUSINESS ONLY FROM THIS ADDRESS.

ANNUAL HOLIDAYS—CLOSED FROM AUGUST 9th to 23rd.

YOU can build any of these at Low Cost!

A MINI TRANSISTOR RADIO

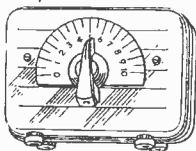

AN IDEAL PRESENT

A two-stage highly sensitive circuit uses a new super high gain transistor coil and mini tuning condenser. Gives remarkable performance. With step-by-step instructions. Beginners can't go wrong. Get your order in while prices are low. Send 2/- for wiring diagram and component price list.

Total building costs **37/6**

Includes Plastic case, mini components, Batteries etc. All parts sold separately.

Ideal for:


- ① Late night listening.
- ② Children's nursery, etc.

WORLDWIDE SHORT-WAVE RADIO

EXPLORE THE WORLD ON SHORT WAVES!


Can be built from our list of components which can all be purchased separately, covers 10-100 metres and is capable of receiving speech and music from all over the world. Price includes the famous 954 acorn valve and one coil covering 40-100 metres. Provision is made to increase to two or three valves and all components are colour coded. Send 2/- for point to point wiring diagram, layout and price list.

30/-

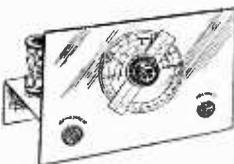

Post and packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE.

TRANSISTOR POCKET RADIO

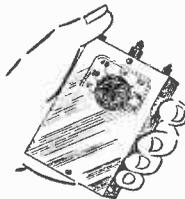

The ideal low cost transistor pocket radio for the beginner. The Two-stage circuit utilises the new R.C.S. VARILOOPSTICK transistor coil. A specially designed miniature .0005 tuning condenser permits the receiver to be in a case which fits in the palm of your hand. Works for months off small battery costing 7d. Can be built in 30 minutes. PRICE **30/-**

All components are sold separately, full construction data, including plan to parts for 2/-.

PERSONAL PORTABLE RADIO

THE SET FOR PERSONAL LISTENING

This little set was designed to give you a real personal portable radio that you can listen to anywhere without disturbing others. Use it on camping trips, in bed, in your office. Supplied with detachable rod aerial, it covers all the medium waves 200-500 metres. Average building time one hour. PRICE **30/-**

Send 2/- for specification, point to point circuit and parts price list.



R.C.S. PRODUCTS (RADIO) LTD., 11, OLIVER ROAD, LONDON, E.17. (Mail Order only)

HANNEY

offers

COSSOR 3 VALVE 3 WATT HI-FI AMPLIFIER KITS,

£9 - 15 - 0

CARRIAGE PAID

AVO MULTIMINOR

£9 - 10 - 0

Components for

- OSRAM 912 PLUS AMPLIFIER
- OSRAM 912 PASSIVE UNIT
- OSRAM 912 PRE-AMPLIFIER
- OSRAM F.M. PLUS TUNER
- MULLARD 510 AMPLIFIER
- MULLARD 510 "A" PRE-AMPLIFIER
- MULLARD 510 "B" PRE-AMPLIFIER
- MULLARD 3/3 AMPLIFIER
- MULLARD F.M. TUNER UNIT
- DENCO MAXI-Q F.M. TUNER UNIT

Manuals available:

912 PLUS AMPLIFIER—4/-; MULLARD HIGH QUALITY AMPLIFIER MANUAL (contains F.M. details)—3/6; DENCO F.M. TUNER—1/6.

Send 3d. postage, stating lists required. General Components list also available.

L. F. HANNEY

77, Lower Bristol Road Bath

EDDY'S (Nottm.) LTD.

Dept. P.W.

172 ALFRETON ROAD, NOTTINGHAM

THE BARGAIN OF THE YEAR
ACOS CRYSTAL TURNOVER PICKUPS (2 Sapphire Styli).
Brand New Boxed, 2/11 each. Postage 2/6 Extra.

DR. CECIL'S RADIO CRYSTALS, 6d. Each (List Price 1/6).

MAP CASES, 2/6 Each. Post 6d. Ideal for Service Sheet holders, Job Cards, Etc.

SINGLE PIECE THROAT MIKES, 1/- Each. Post 6d. Extra. Could be used for electrifying Musical Instruments.


MIDGET BATTERY ELIMINATORS. To convert all types Battery Portables (Please state make and model No.) to mains operation. 5/76 Each. Plus Post, etc., 2/6.
Smaller than H.T. Battery Alone.

AZ1	12/11	EL41	9/11	UBCH1	8/6	5Z4M	10/11	6V6G	5/11
AZ31	12/11	EL91	9/11	UBF3	9/6	5AG5	7/6	6X4	6/6
B31	12/11	EY85	15/11	UC42	8/11	5AQ5	7/6	6X5GT	7/11
CV31	12/11	EY23	8/3	UCF2	10/6	6AT5	7/6	10F1	15/11
DAF35	9/6	HY80	8/11	UF1	8/11	5B3C	2/11	10F9	11/6
DF35	9/6	KT33C	8/3	UF12	11/6	5BA5	6/6	12AH7	7/6
DK95	9/6	L83	6/6	UL41	9/6	5BJ5	7/6	12AT7	8/6
DL95	9/6	MU14	8/6	UL31	8/11	5FL1	13/11	12KT6	7/6
EBC41	9/3	OZ4	6/6	UY11	7/6	5F43	13/11	12Q7G	7/6
EBF40	9/6	PCC81	9/11	UY35	9/11	5F15	13/11	12SH7	5/6
ECC31	8/11	PCF3	12/6	VP21	7/6	5J5G	2/11	12SN7GT	
ECC35	8/11	PCL33	15/6	VTS2	2/11	RTM	9/6		19/11
ECH35	10/11	PEN33C	17/6	1C37T	10/6	5K7G	2/6	14S7	14/6
ECH42	9/11	PL39	9/11	1H3T	11/6	5K7M	7/6	18AQ5	9/6
ECH81	9/11	PL91	13/6	1N3GT	10/6	5K83	7/11	25A6G	12/11
FF49	13/11	PL92	9/6	1D1	10/6	5L9C	5/11	35A5	10/6
EF11	9/6	PL33	9/11	1R5	7/11	5P21	17/6	35W4	7/6
EF42	12/6	PY31	8/3	1S5	7/6	5Q7G	8/11	807	4/11
EF3	8/6	PY32	8/6	3Q3GT	9/6	5SN7GT		934	1/6
EF33	12/6	U25	13/6	5U4G	9/6		5/11	955	3/11
EF91	6/11	U33	13/6	5Z1G	6/11	6U4GT	13/11	959	2/11

Any parcel insured Surplus. New and against damage or Guaranteed valves. Post, etc., 6d. per Extra. All tested before Valve extra. Over 1/6ss in transit. 6d. All despatch before Extra. E3. Free.

S.A.E. WITH ALL ENQUIRIES

Servicing Radio Receivers

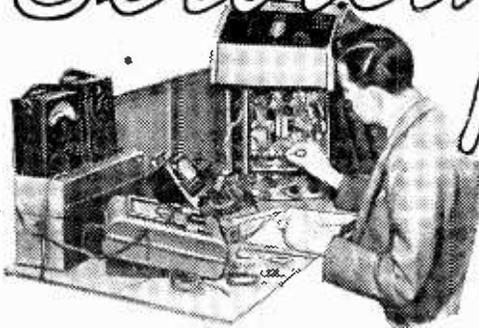

COSSOR TRANSISTOR RECORD PLAYER MODEL 544

By Gordon J. King, A.M.I.P.R.E.

AS an introduction to the commercial application of transistors, we deal this month with the Cossor Transistor Record Player (Fig. 1). While this instrument serves only as a record player and has no provision for the reception of radio signals, it represents admirably the way in which transistors are now used for the amplification of audio-frequency signals.

The full circuit is given in Fig. 2, from which readers will have little difficulty in following the signal path, in spite of the less familiar symbols of the transistors. From recent articles on the transistor, it will be recalled that, like a thermionic valve, a transistor requires a D.C. bias supply, and that the bias has to be arranged in the reverse direction between the collector and base.

In this sense, the transistor can be looked upon as two crystal diodes formed between the emitter and base and the collector and base (in the circuit at Fig. 1 the letters B, C and E around the transistor symbols represent base, collector

and emitter respectively). These three points are often likened to the electrodes of a triode valve as follows: collector and anode, base and grid and emitter and cathode.

The forward direction of current in the emitter-base circuit due to the biasing gives this circuit a lower resistance, while a relatively higher resistance is possessed by the collector/base circuit which is biased in the reverse direction. When the current in the base/emitter circuit increases, the current in the base/collector circuit also increases, but to a greater extent. Generally speaking, this action is promoted by the emission of so-called positive holes from the emitter to the collector circuit with a consequent lowering of the resistance of the base/collector circuit.

The signal is applied to the transistor, so as to cause variation of the negative current in the base/emitter circuit, which results in an equal or greater variation of current in the base

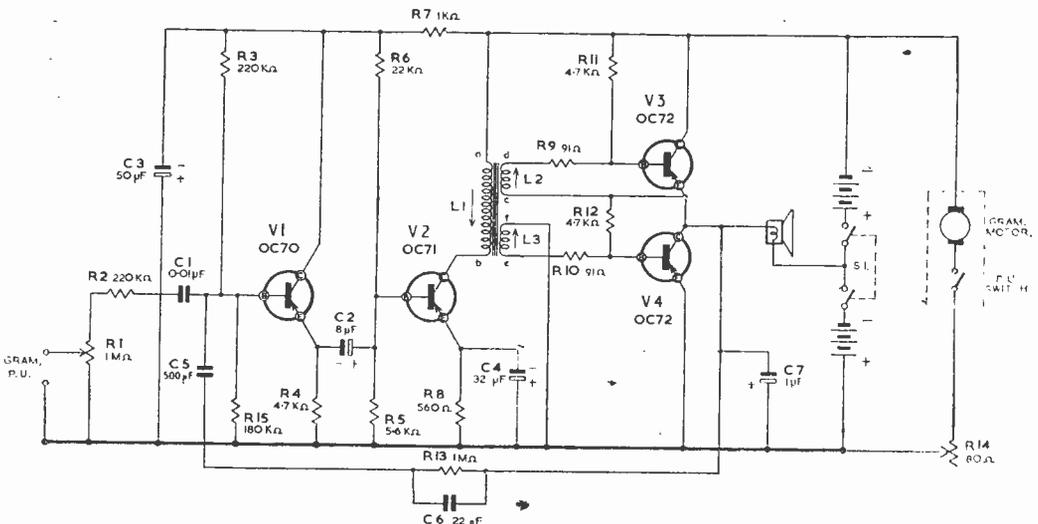


Fig. 2. Theoretical circuit of the record player.

collector circuit. Power gain is thus secured by reason of the *applied signal* causing a current change in a *low resistance* circuit while promoting a similar current change in a *high resistance* circuit. With these brief facts in mind we can investigate the Cossor circuit.

Circuit Description

The signal from the crystal pick-up is coupled to the base of the first transistor (V1) by way of the volume control R1 (note that in this case the slider of the control is connected to the pick-up and not to V1 as it would be with a thermionic valve), resistor R2 and capacitor C1. These serve as equalising and matching components from the pick-up to the transistor. The signal is thus applied to the base, which, as

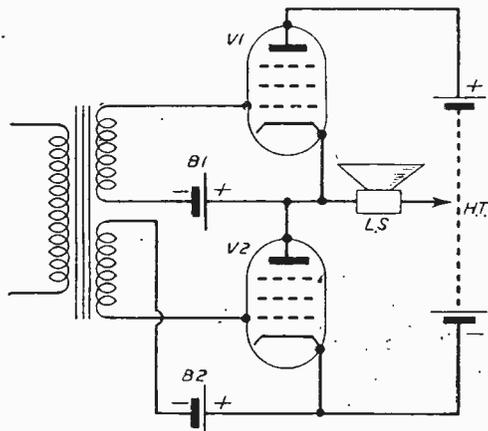


Fig. 3.—The single-ended push-pull output stage, using a tapped H.T. battery.

already mentioned, may be likened to the grid of a thermionic valve.

From the signal point of view, the collector of V1 is at chassis potential (via C3), and the output signal is taken from the emitter circuit. From the valve aspect, this means that anode is at chassis potential from the signal point of view, and that the signal is taken from the cathode. In other words, the stage is arranged in form analogous to the cathode-follower, and is usually referred to as a grounded-collector amplifier.

The advantage of this arrangement lies in the fact that it has a relatively high input impedance and can be matched into a pick-up circuit, for example, without calling for a transformer. Its output impedance is low, however, but this is often desirable as a matching artifice when the input impedance of a proceeding stage is fairly low, such as the input impedance of stage V2 in the Cossor circuit.

The second stage, in fact, consists of a grounded-emitter amplifier. Here the input impedance at the base is lower than the output impedance at the collector, and to avoid low frequency attenuation as the result of the low impedances involved coupling between V1 and V2 is made by way of an 8 μ F capacitor C2. It will be appreciated, of course, that this

stage has a distinct resemblance to a signal triode stage in which the cathode is grounded and the signal is taken from the anode.

The current variations in the collector/base circuit and the power produced by them is abstracted by the driver transformer, the primary winding being connected in the collector circuit of V2. The transformer is designed to drive the push-pull class "B" output transistors V3 and V4 to provide an audio output of some 300 mW with very little distortion.

The Output Stage

The output stage is worth investigation since it represents a fairly recent development (in valve circuits as well as transistors) which dispenses with the usual split-primary transformer in push-pull output stages. It is described by the curiously conflicting term "single-ended push-pull output."

Let us first look at the idea in terms of valves with which we are possibly more familiar. In Fig. 3 are shown the two output valves V1 and V2, but instead of being connected across the primary of a centre-tapped output transformer, they are effectively connected in series with the H.T. supply. The loudspeaker is connected between the anode/cathode junction and a centre voltage tap on the H.T. supply. On the face of it, it may appear that the loudspeaker is going to suffer a burn-out, but if the problem is considered a little more deeply it will become evident that the valves, H.T. and loudspeaker form a type of bridge circuit. This is, indeed, the case, and provided each valve is taking equal current, as governed by the matching and biasing, the circuit will be in balance and no current will flow in the loudspeaker speech coil. This is the static D.C. condition.

However, when the valves are driven alternately by the signal, the condition of balance will be disturbed in sympathy with the signal and the difference current will flow through the speech coil, thus causing it to operate precisely the same as if it were connected to the secondary of a conventional output transformer. One of the most expensive and distortion-producing components has by this means been eliminated, but since a transformer is not available for matching purposes, the impedance of the loudspeaker requires to be greater than that of a loudspeaker used with a conventional output stage. In this connection, the speech coil impedance necessary is half the optimum load of a single valve.

The circuit in Fig. 4 illustrates how the tapped H.T. supply can be avoided. Since the signal "sees" a low impedance over the whole of the H.T. battery, it matters little whether connection is made at a centre-tap or at one end. The out-of-balance D.C. is blocked by capacitor C.


The circuit at Fig. 2 shows clearly how the idea is extended to transistor circuits. Here a tapped bias source is adopted for V3 and V4. This is much a matter of convenience, though it does ease the balancing problem somewhat, since the tap is taken from the junction of two series-connected 4.5 volt batteries (Ever Ready AB28s

(Continued on page 313)

I GIVE PERSONAL ATTENTION AND ASSISTANCE WITH BUILDING!



WHY PAY MORE?

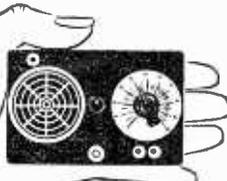

47/6 Build this exceptionally sensitive "SKYROMA" radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 1/2 in. x 3 in. Covers all Medium and Long waves—uses all-dry battery. (H.T. consumption only 1 to 1.5 mA., personal phone.) Ideal for Bedroom, Garden, Holiday, etc. Many unsolicited testimonials. Mr. Norton of Oxford writes: "Yesterday evening on the Medium waveband, I counted 32 separate stations: I am very pleased with the set, which is well worth the money. BUILD THE SKYROMA NOW!" Total building cost—everything down to last nut and bolt—47/6 (Postage, etc., 2/-) with full set of clear, easy-to-follow plans. (Parts sold separately. Priced Parts List, etc., 1/6.) C.O.D. 2/- extra.

AT LAST! In response to many requests we now present the "SKYPOCKET," a beautifully designed precision POKET RADIO. No radio knowledge needed—EVERY SINGLE PART TESTED BEFORE DESPATCH; our simple, pictorial plans take you step-by-step. This set has a remarkable sensitivity due to painstaking design. Covers all medium waves 200 to 550 Metres. Size only 5 1/2 in. x 3 in. x 2 in. in Strong, Transparent case with panel cover and dial. A really personal-phone, pocket-radio WITH DETACHABLE ROD AERIAL. Self-contained all-dry battery operation. Average building time 1 hour. Total Building Cost—including Case, Valves, etc., in fact, everything down to the last nut and bolt—ONLY 37/6, with plans, Postage, etc., 2/-. C.O.D. 2/- extra. (Parts sold separately. Priced Parts List, etc., 1/6.) Demand is certain to be heavy—SEND TODAY!



107/6 Total building cost including choice of beautiful walnut veneered cabinet or Ivory or Brown Bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple easy-to-follow diagrams. The terrific new circuit of the "OCEAN-DIPPER" covers all medium and long waves with optional negative feedback, has razor-edge selectivity, and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple easy-to-follow plans—in fact, everything! All parts sparkling brand new—no junk! Every single part tested before despatching. Uses standard octal-base valves. For A.C. Mains, 200-230 volts (low running costs—approximately 18 Watts). Size 12 in. x 3 in. x 3 in. Build this long range powerful midset NOW. All parts and set of plans, £5.7.6. (Post and packing 3/6.) Parts sold separately. Priced Parts List, 1/6. C.O.D. 2/- extra.

the Skypocket 37/6
COSTS ONLY 37/6 TO BUILD!

ONLY £8-10-0!

BRAND NEW—NOT SURPLUS! In maker's sealed cartons. Latest UA3 "Monarch" 4-speed record-player complete with High-fidelity turnover head. Type HGP 37-1. Capacity of 10 Records, plays 12 in., 10 in. and 7 in. intermixed in any order. 78, 45, 33 and 15 r.p.m. For A.C. mains 100 to 230 volts. Exclusive "mag-disk" selector gives quickest and quietest change over. With full instructions and fixing plans. Limited Quantity at £8.10.0 plus 4/6 Post, Packing, etc. **WHY PAY MORE!**



WE'VE DONE IT AGAIN! our design department in response to a great many requests have designed this "SKYPIXIE" Vest-Pocket TWO TRANSISTOR RADIO which gives a superb performance. It is highly sensitive. Size only 4 1/2 in. x 3 1/2 in. x 1 1/2 in., the weight under 7 ozs. Yet it is a THREE-STAGE receiver covering all medium waves, working entirely off a tiny "pen-light" battery, which costs 6d.—fits inside the case—and lasts many months. Uses personal phone and has push-button "MIXERS" On Off Switch. Every part tested before despatch! **SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS.** Total building cost including case, transistors, etc.—everything down to the last nut and bolt—ONLY 47/6 with plans, Postage, etc., 2/- C.O.D. 2/- extra. (Parts sold separately. Priced parts list, etc., 1/6.) As the building cost is absolutely "rockbottom" (it might increase later) DEMAND WILL BE VERY HEAVY—RUSH YOUR ORDER TODAY!

the Skypixie
TWO-TRANSISTOR RADIO
COSTS ONLY 47/6 TO BUILD!

BUILD TRANSISTOR SET THIS FOR 29/6!

VERY SPECIAL OFFER WHILE STOCK OF PARTS LASTS!—The "SKY-SMALL" Pocket two-stage transistor set, size only 1 1/2 in. x 3 1/2 in. x 4 1/2 in. Covers all medium-waves and works entirely off tiny "pen-light" battery which costs 6d. and fits inside case. All parts tested before despatch. Can be built for 29/6, plus 2/- post and packing, including Case, Transistor. **STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS,** nuts, bolts, etc. (C.O.D. 2/- extra.) Parts sold separately, priced parts list, etc., 1/6. **VERY SIMPLE TO BUILD.**

BUILD THIS Skyrroma 47/6 FOR ONLY

ONLY 95/-!

NEW in maker's sealed cartons!—limited quantity of "COLLARO" JUNIOR 4-speed record player units, exceptionally easy to fix, with lightweight pick-up, incorporating crystal turnover head and separate sapphire stylus for Standard and Long-Playing. With full instructions and fixing plans. Unbeatable price, 95/-, plus 3/6 Post, Packing, etc. C.O.D. 2/- extra. **RUSH YOUR ORDER NOW!—BEFORE IT'S TOO LATE!**



Sensational Offer!

150 ONLY!... The famous "Galaxy" Stear, 4-speed auto-change units in maker's sealed cartons. Advanced design, finger-tip stop, start and speed-change. A.C. mains 110 to 250 volts. Size 10 1/2 in. x 12 1/2 in. List price £13.15.0. **DIRT PRICE WHILE STOCKS LAST YOUR ORDER BEFORE WE SELL OUT!**



CONCORD ELECTRONICS

69, PRESTON STREET BRIGHTON

Dept. PWV

Orders receive prompt attention. Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no Orders sent abroad.

THE "WEYRAD" SIGNAL GENERATOR

AN INSTRUMENT OF HIGH ACCURACY AT LOW COST



- Coverage 100 Kc/s-70 Mc/s (on fundamentals).
- Accuracy better than $\pm 2\%$ on all ranges.
- Large, clearly calibrated scale.
- Modulated or C.W. output.
- 500 c/s A.F. source.
- S.G.M.I.—A.C. mains operation. Double wound, varnish-impregnated transformer, tapped 210/225/250 volts.
- S.G.B.I.—All dry battery operated.
- All components are by well-known manufacturers ensuring maximum reliability.
- Both types in quantity production.
- Illustrated leaflet available, price 2d.

WEYMOUTH RADIO MANUFACTURING CO., LTD.
CRESCENT STREET, WEYMOUTH, DORSET

FREE TO AMBITIOUS ENGINEERS!

This 148-page Book

Have you sent for your copy?



'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £20 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

--- FREE COUPON ---

Please send me your FREE 148-page "ENGINEERING OPPORTUNITIES"

NAME
 ADDRESS
 Subject or Exam
 that interests me
 British Institute of Engineering Technology,
 409 B, College House, 29-31, Wright's Lane,
 Kensington, W.8.

WHICH IS YOUR PET SUBJECT ?

Mechanical Eng.
 Electrical Eng.
 Civil Engineering
 Radio Engineering
 Automobile Eng.
 Aeronautical Eng.
 Production Eng.
 Building, Plastics,
 Draughtsmanship,
 Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
 A.M.I.C.E.
 A.M.I.P.E.
 A.M.I.M.I.
 L.I.O.B.
 A.F.R.Ae.S.
 B.Sc.
 A.M.Brit.I.R.E.
 CITY & GUILDS
 GEN. CERT.
 OF EDUCATION
 etc., etc.

BIET

THE SUPEREX "55" BATTERY PORTABLE

BUILDING COST £7.15.0


Plus 5/- P.P.

- 4-VALVE SUPERHET.
- LONG/MEDIUM WAVES.
- 7in. x 4in. SPEAKER
- B7G 1.4 v. VALVES.
- SIMPLE CONSTRUCTION.



SEND 1/6 FOR BOOKLET.

CHASSIS ASSEMBLY

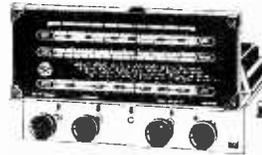

CONTAINING :
 DRILLED CHASSIS AND
 BACK PLATE, SIZE
 12 x 7 x 8in., GLASS DIAL
 L.M.S.G., DRIVE DRUM
 AND SPINDLE, KNOBS.
 PRICE 22/6 PLUS 2/6 P.P.

ALWAYS IN STOCK

RESISTORS, CONDENSERS, TRANSFORMERS, VALVES, AMPLIFIERS, AUTOCHANGERS, RADIO CHASSIS, SPEAKERS, CABINETS, PICK-UPS, SPEAKER FABRIC, RECORDING TAPE, MICROPHONES, ETC.

Shop Open : 9 a.m.—6 p.m. Early Closing : Thursday, 1 p.m.

SUPERIOR RADIO SUPPLIES LTD.

37, HILLSIDE, STONEBRIDGE, N.W.10
 PHONE : ELGAR 3644

or equivalents), which also serve to provide the required power for operating the Garrard Type BA1 record player by way of the speed control potentiometer R14.

As already mentioned, the two output transistors operate in class "B," or nearly so. In practice they pass a small quiescent current so as to reduce distortion as the result of transistor non-linearity. Potentiometer networks comprising R9, R11 and R10, R12 serve to bias the transistors in this way and also promote a small degree of negative feedback and damping of resonances formed by the transformer and transistor input capacitances. From our previous discussion, it will be clear that V3 and V4 are operated in the grounded-emitter mode.

Capacitor C7 smooths the effects caused by alternate "switching" of the output transistors, while resistor R13 and capacitor C4 form an overall negative feedback loop, giving some 10 dB of feedback at 400 c/s. and provide a lift in bass response due to the frequency selective nature of the circuit. Capacitor C6 is included to give enhanced stability at the higher frequencies.

Decoupling of the bias to V1 and V2 is secured by R7 and C3, as in ordinary valve circuits. The operating conditions of V1 are stabilised by R3 and R15 in conjunction with the emitter resistor R4, while the operating conditions of V2 are similarly stabilised by R6, R5 and R8.

Servicing Notes

As the operating conditions would be severely disturbed by shunting any network resistor by a resistor of relatively low value, and thus possibly result in permanent damage to a transistor, voltage checks within the circuit must be made with a voltmeter of, at least, 1000 ohms-per-volt sensitivity. Similarly, it is not desirable to make or break connection within the circuit with the amplifier switched on. For example, if a current check is required, the amplifier must first be switched off, the circuit broken and milliammeter

inserted. The amplifier can then be switched on and the measurement made. The same applies, of course, on re-connecting the circuit.

The total "no-signal" current of the amplifier should range between 3.8 mA and 4.2 mA depending on the condition of the batteries. This is made up by current in the potentiometers, 0.4 mA of collector current in V1, 2 mA of collector current in V2 (taken between point A on L1 and the negative line) and 150 μ A to 400 μ A of collector current in V3 and V4. The out-of-balance loudspeaker current should not exceed 50 μ A. Taken on a 20,000 ohms-per-volt instrument, V1 collector should register negative 8.25

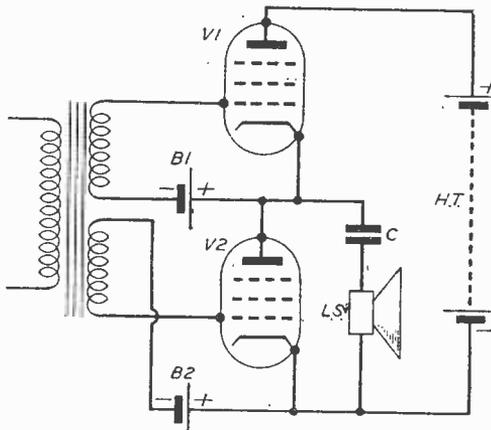


Fig. 4.—The H.T. tap can be avoided by the use of a coupling capacitor, C.

volts, V1 emitter negative 2 volts and V2 emitter negative 1.25 volts.

Transistors are very heat-conscious, and if overheated when operating are liable to destroy themselves in a very short time. They should thus be kept clear of soldering irons and other heat-producing devices. Soldering in and out of circuit should never be a prolonged process. A miniature low-power soldering iron is desirable, and even then a heat "sink" should be produced by a pair of long-nose pliers held tight on the transistor connecting lead, between the point of soldering and the transistor itself. Moreover, the transistor leads should not be bent close to the seal.

Inadvertently reversing the supply polarity will almost certainly destroy a transistor, and this should also be borne in mind when making *in situ* resistance checks with an ohmmeter. The negative terminal of most multi-range meters is usually in connection with the internal battery positive lead when used as ohmmeters—this is a point worth remembering.

When replacing components on the printed circuit, the faulty part should be snipped out so that sufficient connecting wire is available for the replacement part. The connecting leads of the new part should be tinned before attempting connection to the wire ends remaining above the board. In this way the heat period of soldering can be kept to a minimum.


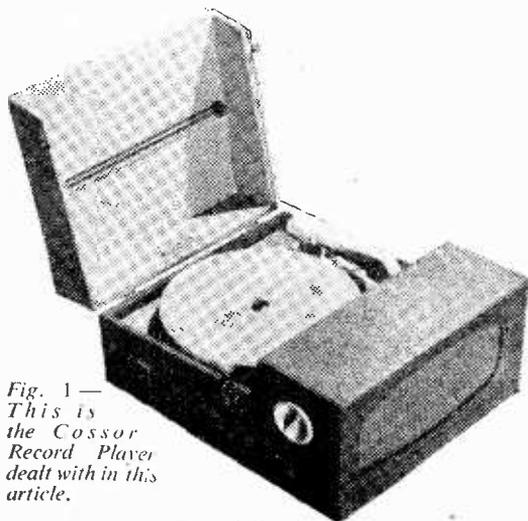


Fig. 1—This is the Corsor Record Player dealt with in this article.

Programme Pointers

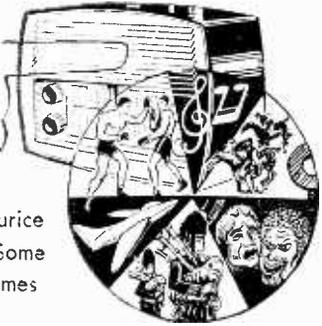

Our Critic, Maurice
Reeve, Reviews Some
Recent Programmes

ROMEO and Juliet, Paolo and Francesca, Antony and Cleopatra, Faust and Marguerite; and so on through hosts of others whose loves, invariably crowned with tragedy, have brought tears to millions of readers, theatregoers and opera audiences. Until we reach 1958, the age of Ron and Eth, the culmination of all earthly passion and desire, the *ne plus ultra* of trembling trepidity and the incarnation of inconsequential insipidity—desire under the aspidistra—whose saga of frustration and impotence pursues us weekly.

I have, of course, referred to those cerebral offsprings of Frank Muir and Denis Norden, radioed by Dick Bentley and Jimmy Edwards and so lugubriously impersonated by Wallas Eaton and June Whitfield.

Whither wendest them? How will they perish? Only Messrs. Muir and Norden know this. So far as we are concerned, they follow the pattern set by famous predecessors such as Dan and Doris Archer or Dr. and Mrs. Dale—also Peter Pan; they never grow up. So far as we can see into the future, they can only terminate their existence by consummating their love which would, of course, transfigure them completely. But Ron and Eth married—there would be crowds besieging Broadcasting House and the G.P.O. commanding fleets of auxiliary vans to carry the protest mail there: it would be unthinkable and unpardonable.

In the meantime may Eth's romantic illusions remain unshattered and Ron's frightening timidity be continued for some time to come.

Talking About Music

Antony Hopkins has made a name for himself as a conductor and broadcast critic which is wholly justified. His Sunday evening series, "Talking About Music," is quite delightful, very informative and equally refreshing to the novice or the devotee. Mr. Hopkins always has a happy smile ready and can illustrate passages on the piano with no mean dexterity. His programmes are most enjoyable.

Lady Godiva, ever since she rode the streets of Coventry in a costume that wouldn't pay a dividend for any silk or nylon merchant these days, has been a godsend to lyric writers, music-hall jesters and dealers in ribaldry generally. A few years ago a famous judge had cause to remark that when he was a boy it took a sheep to dress a woman but, when he was speaking, it only required a couple of silkworms. The learned judge lived four or five hundred years too late.

In "Scandal at Coventry"—specially written for radio—Clemence Dane treated the subject seriously and quite beautifully. The "ride," to the accompaniment of the slow clop/clop of hooves, sounded most effective and suggestive.

It provoked a thought: on television the scene would either have been produced in an inhibited or meaningless manner or completely excoriated, but in "blind" radio it remained undisturbed. Up radio!

Famous Trials

The Thompson-Bywaters murder trial was one of the most famous and exciting of all time. So it was natural that it would find a place in the "Famous Trials" series: No. 4, in fact. It made both a dramatic play and an historical documentary. Written by F. Tennyson-Jesse, commented on by Lord Birkett and produced by Nesta Pain, all the poignancy and futility of the wretched affair were made crystal clear, as was the savage brutality of sentencing Edith Thompson. Mary Wimbush played her with tragic simplicity and heartrending realism.

March 21st, 1918. That date means little or nothing to anyone younger than the present writer; not so much, perhaps, as Waterloo or Agincourt. But to those of his own generation it ushered in a period during which neither Lloyd George nor Haig themselves knew whether the first world war was not, after all, going to be lost. The programme, "The March Retreat" (the title seems something like a masterpiece of understatement), vividly recalled those pulsating days. I hope it is followed up by one which I style in advance "The Turn of the Tide and Victory." For it was less than eight months later that that frightful war was all over and "in the bag."

As there was nothing new to say about it, nothing new was sought. But, with the Fifth Army Commander himself taking part, plus several important participants, it was a stern reminder, well presented, of events which will for ever remain in the memories of those even remotely connected with it.

The Lyons

"Life With the Lyons" proceeds pleasantly if not always with perfect tranquility! They make a delightful family—they are, of course, very old friends now—and it is always a pleasure to pop in on them. The script maintains a reasonably high average with very few wholly dull sessions. Like "The Archers," they will never grow up; if they did, that would be that?

Brenell

TAPE RECORDING EQUIPMENT

The Connoisseur's Choice

Why are so many tape recording experts turning to the Brenell Deck? Is it because they want precision engineering, greater speed stability, the best value for money, freedom from troublesome gadgets, high quality materials, multiple speeds?

All these features are combined in Brenell Equipment, you can buy Brenell and know you have bought 'the Expert's Choice.'

Brenell have control during manufacture of all the essential parts—they are not merely "assemblers," and every part must conform to a critically high standard. Skilful design is followed up by high degree of craftsmanship in manufacture, resulting in equipment which is rightly held in the highest esteem throughout the world.

In the Mark 5 Tape Deck, all the proved features which have given Brenell its great reputation are retained, and new features make available TODAY the Deck of the FUTURE.

BRENELL MARK 5 TAPE DECK

4 Speeds 1½, 3½, 7½, 15 i.p.s.
3 Motors.
Up to 8" dia. spools.
Provision for Extra Heads (up to 4 in all)
Interlocked Switching
Safety Switch to Prevent Accidental Erasure.
Pause Control.
Digital Revolution Counter.
Fast Wind and Rewind.

TAPE PRE-AMPLIFIER T.P.2

Designed to suit any Brenell Deck, incorporates all the best features of the modern tape pre-amplifier.
Frequency correction for 3½, 7½ and 15 i.p.s.
Monitoring facilities via headphones.

Monitoring facilities via main amplifier equipment.

Head DE-MAGNETISING facilities.
Microphone input sensitivity 2.5 m.v. into 2 megohms for full modulation.
Radio/Pick-up input sensitivity 250 m.v. into 700K ohms for full modulation.
Erase and Bias oscillator 50 Kc/s.
Frequency response:
3½ i.p.s. 60 c/s—6,000 ± 3 db.
7½ i.p.s. 60 c/s—10,000 ± 3 db.
15 i.p.s. 60 c/s—14,000 ± 3 db.
Output to main equipment approximately 1 v. at 50,000 ohms.
Valves: EF86, ECC83, EL84, EM81.
Power requirements:
300 v. at 40 Milliamps. H.T. Supply.
6.3 v. at 1.5 amps. Heater.

POWER UNIT T.U.2

Powerful for use with Tape Pre-Amplifier.

BRENELL '3 STAR' PORTABLE TAPE RECORDER

This attractive tape recorder combines a deck and amplifier of outstanding quality with a large loudspeaker in a modern styled cabinet; delightful performance and appearance will make this recorder one of the most popular types available.

Salient features:

Push button deck control.
Interlocked switching.
Pause Control.
3 speeds 1½, 3½ and 7½ i.p.s.
Switched frequency correction.
Digital Revolution counter.
PRINTED CIRCUIT AMPLIFIER.
Separate Bass and Treble Controls.
Cathode Ray Type Recording Level Indicator.
Extension loudspeaker socket.
Monitoring facilities.

BRENELL ENGINEERING CO. LTD. IA DOUGHTY ST., LONDON, W.C.1, ENGLAND
Telephone: HOLborn 7358 and CHAncery 5809.

BE TRANSISTORWISE

and build these fine transistor kits



"RECO" TRANSISTOR ONE WITH TELESCOPIC AERIAL vari Q ferrite coil, personal phone, etc. Case size and layout now as "Reco" Two. Complete kit 37/6. p.p. 1/9. Pictorial wiring diagram, etc. 1/-.



"RECO" TRANSISTOR TWO
An amazing receiver which on test (50 miles from London) received Continental stations with only a few yards of aerial wire. The Home and the Third were received on built-in Vari "Q" ferrite aerial. All parts and plastic case, 1½in. x 4½in. x 4½in. 49/6. Personal phone free with kit or balanced armature output unit 4/6 extra. P.P. 2/3. Pictorial wiring diagram, parts price lists, etc. 1/-.



RECO "SPECIAL TRANSISTOR THREE
This fine receiver has, now been greatly improved with the addition of a handsome looking chromium plated telescopic aerial 1½in. closed, 48in. extended. Has sensitivity control and High Q Frame Aerial. Complete kit with choice of 6A4M5 5/- 12V7GT 10/6
6A4M6 7/6 12X7GT 7/6
6A4M5 7/6 22A6G 13/6
6A4M6 7/6 12Q7GT 7/6
6BA6 7/- 12Z3 7/6
6BE6 7/- 14ST 12/-
6BH6 9/- 19A05 7/6
6BL6 8/6 25L6GT 8/6
6BW6 7/6 25Z4G 8/6
6BW7 7/6 25Z6GT 9/-
8CD6G 25/- 35L9GT 9/6
9PG 6/6 35Z4CT 7/6
6K7G 4/6 35Z5GT 6/6
6K7GT 9/- 43 12/6
6K8G 9/6 50CD6G 12/6
6L18 12/6
6M7GT 7/- 50L6GT 8/6
6SL7GT 7/- AZ31 10/6
6SN7GT 7/6 130EF41 9/6

"Sonotone" miniature earphone or balanced armature output unit which, in areas of reasonable signal reception, can be mounted inside case. Case size 6½in. x 4½in. x 1½in. with red plastic ornamental unit cover. 77/6. Less telescopic aerial and with balanced armature output unit 65/-. Pictorial wiring diagram, parts price list, etc., 1/3.



"RECO" MIDDY TRANSISTOR THREE
Small in size big in performance. Ideal for invalids. Take it on holiday. Vest pocket size 4½in. x 3½in. x 1½in. In areas of reasonable signal reception receives local stations on built-in ferrite rod Vari "Q" aerial. Covers 130 to 500 metres. Complete with three transistors and pencil. Price including "Sonotone" miniature earphone with moulded ear insert and lead 65/-. Pictorial wiring diagram, parts price list, etc. 1/3. Overseas orders. Carr. 10/- extra.

RADIO EXCHANGE CO., Dept. P.W.
27A Harpur Street BEDFORD

VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. midtot, 1R5, 1S5, 1T4, 3S4, 3Q4, 3V4, DAF91, DF91, DK91, DL92, DK92, DL94; ANY 4 for 27/6

1A7GT	13/6	6U4GT	11/-	B33	15/-	EF42	11/6	PL81	16/-
1C5GT	13/-	6V8G	7/-	CL33	16/9	EF30		PL82	8/6
1D5	12/6	6V8GT	7/6	D77	5/6	EF35	8/6	PL83	10/6
1R5GT	11/-	6X4	7/-	DAC32	5/6	EF35	9/6	PY80	8/-
1R5	8/-	7B6	12/8	DAF96	8/6	EF80	7/6	PY81	8/-
1S5	7/6	7B7	8/-	DF33	11/-	EF31	7/3	PY82	8/-
1T4	7/-	7C5	8/-	DF96	8/6	EF92	5/6	PY83	8/6
3A5	10/6	7C5	8/-	DH76	7/6	EL33	16/9	PZ30	18/-
3Q4	7/6	7H7	8/-	DH7	7/3	EL38	22/8	R19	15/-
3Q5GT	9/6	7S7	9/-	DK32	13/6	EL41	9/6	SP41	3/6
3S4	7/6	7Y4	8/-	DK92	8/6	EL42	11/6	SP61	3/6
3V4	8/6	12A4H	8/-	DK96	8/6	EL84	8/6	U50	7/6
5U4G	8/-	12AT6	8/-	DL33	9/-	EM80	9/6	U76	7/6
5V4G	11/9	12AT7	7/6	DL35	13/-	EM81	10/-	U78	7/-
5Y3GT	7/6	12A7	8/-	EAB30	7/6	EY51	11/6	UABC80	9/-
5Z4G	9/6	12AX7	8/-	EAF42	9/6	EZ40	7/9	UBC41	8/6
6AL5	5/6	12BA6	8/-	E91	6/-	EZ41	9/6	UBF83	9/6
6AM5	5/-	12V7GT	10/6	EBC33	7/6	EZ80	7/6	UCC95	9/-
6AM6	6/6	12X7GT	7/6	EC41	9/6	EZ81	9/6	UCH42	9/-
6A4M5	7/6	12Z3GT	13/6	EBF80	8/6	FW4/500	11/6	UCH81	9/6
6A4M6	7/6	12Q7GT	7/6	ECC81	8/-	GZ32	11/-	UCL83	15/6
6BA6	7/-	12Z3	7/6	ECC82	8/6	KT33C	8/6	UF41	8/-
6BE6	7/-	14ST	12/-	ECC83	8/6	KT63	6/6	UF42	15/6
6BH6	9/-	19A05	7/6	EC94	8/6	MH4	8/-	UF89	9/-
6BL6	8/6	22A6G	13/6	ECC85	9/6	MU14	9/-	UL41	8/9
6BR7	8/6	25L6GT	8/6	ECF80	10/6	N18	7/6	UL44	22/6
6BW6	7/6	25Z4G	8/6	ECF82	9/-	PCC84	9/-	UL84	8/6
6BW7	7/6	25Z6GT	9/-	ECH21	16/9	PCF80	10/-	UR1C	12/6
8CD6G	25/-	35L9GT	9/6	ECH35	10/6	PCF82	10/-	UT21	14/6
9PG	6/6	35Z4CT	7/6	ECF42	9/-	PCL82	10/-	UY41	6/6
6K7G	4/6	35Z5GT	6/6	ECH81	8/-	PCL83	12/-	UY85	7/6
6K7GT	9/-	43	12/6	ECL80	10/-	PEN44	11/-	VP4B	14/6
6K8G	9/6	50CD6G	12/6	ECL82	12/-	PEN3C	14/6	VP41	6/6
6L18	12/6			EF37A	8/6	PE46	8/-	VP321	21/-
6M7GT	7/-	50L6GT	8/6	EF39	6/6	PL36	15/-	W76	7/6
6SL7GT	7/-	AZ31	10/6	EF41	9/6	PL38	22/6	W77	5/6
6SN7GT	7/6			130EF41	9/6			W78	7/6

1 Postage 6d. per valve extra. 277 7/3

Any Parcel Insured Against Damage in Transit 6d. extra.

READERS RADIO
24, COLBERG PLACE, STAMFORD HILL,
LONDON, N.16 STA. 4587

Open to Discussion



The Editor does not necessarily agree with opinions expressed by his correspondents

Improving the "Soundmaster"

SIR.—The following suggestions will be found to improve the performance of the Soundmaster tape-recorder considerably:

1. Increase the value of the screen resistors of V1 and V2 to 330k. The 33k resistors specified and supplied in the kit are incorrect and ruin the performance of the instrument. (The circuit diagram is correct.)

2. To prevent flutter and wow, especially with long-play tapes, the 500 ohm resistor in series with the take-off motor should be increased to at least 2k. (10w.). The tape will not spill and the resultant "slack" flutter is completely damped out by the pressure pads.

3. The pinch-wheel cam spring may be shortened by about $\frac{1}{16}$ in. to increase the pressure if there is any sign of slipping, though this should not be necessary.

4. The pressure pads should be applied as lightly as is consistent with good high-frequency response.—J. H. WHITELEY (G3AES) (Hull).

A Condenser Condition Tester

SIR.—Mr. J. Brown is apparently unaware of the excellent protection afforded by a metal rectifier shunted across a meter so as to give it a logarithmic scale, which is ideal for measuring the forming and leakage current of capacitors. The arrangement is shown in the accompanying circuit diagram. At very low voltages a metal rectifier has considerable resistance and makes little effect on the lower readings of the meter, but as the voltage is increased the resistance of the rectifier decreases and so shunts a greater proportion of the current away from the meter. Two half-wave metal rectifiers are used connected as shown in order to give protection in both directions, and the resistance in series with the meter is adjusted to get full-scale deflection at the current required.

A 1 mA meter shunted in this way can have a half-scale deflection of about 2 mA while reading 25 mA full scale, and for this a Westinghouse Type 2/6A rectifier, with its outside ends connected together, and a variable resistance of 2,500 ohms is suitable. Or the rectifier may be made up from an old copper-oxide one, using 6 discs for each section, no cooling fins being needed. A 5 mA meter can be used instead of the 1 mA, but the scale will be less open. The meter will need re-calibrating or a graph made,

and great accuracy cannot be expected since the resistance of the rectifier varies somewhat with temperature, but it is quite good enough for testing.

Using a single resistor (R13, Fig. 1, April issue) to limit the current on all ranges is very unsatisfactory because if it is of sufficient value for the higher ranges it will grossly reduce the current at lower voltages, with misleading results. It is therefore best to put a limiting resistor in each range, except the lowest ones where there is sufficient resistance in circuit already to limit it to 25 mA.


It is interesting to note that, using the circuit shown, a 5 mA meter can be made to read 1 amp, and yet have a half-scale deflection of under 15 mA. For this a Westinghouse L.T.-7A rectifier and resistance of about 130 ohms is required.—R. V. GOODE (Totland Bay).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

Intermittent Heater Circuit

SIR.—Occasionally an annoying fault occurs in A.C./D.C. sets which can prove difficult to trace. It is an intermittent heater, when the set has warmed up which results in all the valves having no heater current. The offending valve often will not show up when tested with no anode current taken, as it may not rise to the same temperature.

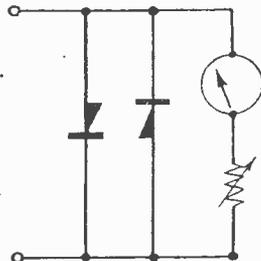By a sketch, it can be seen that if a heater becomes o/c in a series heater chain, then the full mains volts are developed across the faulty



Safeguarding a meter. See Mr. R. V. Goode's letter on the left.

heater because with no heater current flowing there can be no voltage drop across the other resistances.

If a voltmeter is placed across a good valve, then when the break occurs the heater volts will fall to zero.

Therefore to determine which is the faulty valve a voltage check is made on each heater.

when one rises as the fault occurs this is the valve concerned.--MONTY LIPPY (Islington).

Using Old Eliminators

SIR.—In reply to H. Young (Reading), he may be interested to know that I have been using an *old battery eliminator* as a very useful condenser leakage tester for many years. All that is needed is a neon lamp and holder and a bracket to fix it on top of the eliminator; then fix two flexible leads in the H.T. positive and negative sockets with the neon in series with one of them, and terminated in spring clips.

In use I find that condensers down to $.005 \mu\text{F}$ give a useful indication on first switching on. Leaky condensers are immediately revealed by a steady glow or continuous flashing. High value resistors, which may give no indication on an ohmmeter, may also be readily tested for continuity.


I hope the above hint may be useful to Mr. Young and other readers. —H. E. HOWARD (Bournemouth).

Tape Recorder Improvement

SIR.—Almost all tape recorders have at least two heads, record-play, and erase.

The record-play head is in use all the time, but the erase head stands idle when playing back, or recording additions to a previous recording. This is obviously a waste of perfectly good head, and the following notes show how it may be used as a monitoring head and for giving echo effects. The illustration shows the system used. The signal from the low-impedance erase

head is fed to a high gain transistor amplifier. The circuit shown gives a gain of about 300 and takes 0.8 mA from the 250v. supply. The output is suitable for feeding to a valve amplifier or to high-impedance headphones. Other types of transistor may be used if care is taken not to exceed their permitted voltage and current ratings. The spare contacts on most push-button tape decks can be arranged to give the switching arrangements S.

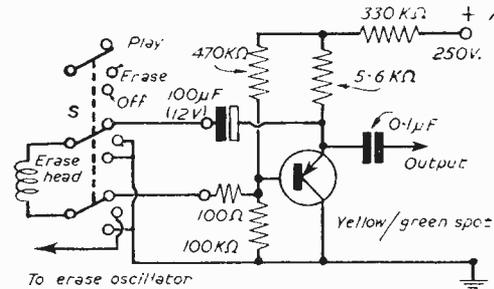

The tape recorder switching arrangement described by Mr. Dobson.

The quality of the output will depend on the erase head gap and the tape speed. Some top cut is inevitable with wider gaps. The device is most suitable for monitoring, when adding to recordings already on the tape, but interesting echo effects may also be obtained by feeding the monitoring signal from the erase head amplifier back to the record head.--J. DOBSON (Sheffield).

Aligning Alba Models 3211, 6221, 6231, 6241 and 6251

THE following are the trimming details for the alignment of the above receivers which were dealt with in our April issue.

Retune the generator to 154 Kc/s and the receiver to 1,950 metres and adjust L15 and L8 for maximum output. After tuning to 250 Kc/s (1,200 metres) and adjust CX6 and CX3 for maximum output.

Finally, the S.W. band: Tune the receiver to 50 metres and the generator to 6 Mc/s and adjust L13 and L6 for maximum output. Retune to 17 metres (17.65 Mc/s) and adjust CX4 and CX1 for maximum output. For best overall results the operations should be repeated for optimum tracking and sensitivity.

F.M. Alignment

Switch the receiver to F.M. and tune to the low-frequency end of Band II. Adjust the R.F. and oscillator trimmers C5 and C9 to the centre of their range. Connect a valve voltmeter between the junction of C7 and C8 on the F.M. tuner and adjust C10 for minimum reading, observing only the dip in meter indication which occurs when C10 is nearest its *minimum* value.

Connect a microammeter and series 200K resistor between pin 2 of V4 and chassis, with the positive

meter terminal to chassis, apply a 10.7 Mc/s unmodulated signal across L5 and adjust L18, L12 and L11 for maximum indication on microammeter. Make a note of this reading. Transfer negative meter connection to point "T" on circuit diagram and carefully adjust the core in L19 for a meter reading exactly half of that noted above. Repeat all the operations given in this paragraph.

Reconnect the negative meter lead to pin 2 of V4, inject a 10.7 Mc/s unmodulated signal to the tuner by way of a tight loop of wire around the ECC85 and adjust L4 and L5 for maximum indication on the meter. It is recommended that a check of the F.M. I.F. response is made at this point by detuning the generator 100 Kc/s either side of the 10.7 Mc/s (plus and minus 100 Kc/s) and checking that the reduction in meter indication is no greater than 40 per cent. (3 db).

Set the receiver tuning to the calibration mark at the low frequency of Band II, inject into the Band II aerial terminals a signal of 87.9 Mc/s, deviated at 25 Kc/s, and adjust C9 and C5 for maximum indication on an output meter connected to the extension loudspeaker sockets. Tune the receiver to 95 Mc/s and retune the generator to coincide. Adjust the spacing between C7 and C8 for calibration at this frequency.

Disconnect meter and signal generator, connect F.M. aerial and adjust C1 for optimum sensitivity. Seal all trimmers lightly with wax.

Wanted!


QUALIFIED MEN AND WOMEN

Industry and Commerce offer their best posts to those with the qualifications—appointments that will bring personal satisfaction, good money, status and security. As part of a modern industrial organisation, we have skilled knowledge of what is required and the best means of training personnel for present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed here. Write to us to-day for further information. There is no obligation of any kind.

PERSONAL & INDIVIDUAL TRAINING IN —

- | | | | |
|---------------------------------------|-------------------------|-------------------------------|-----------------------------|
| Accountancy | Draughtsmanship | Mathematics | Sales Management |
| Advertising | Economics | M.C.A. Licences | Sanitary |
| Aeronautical Eng. | Electrical Eng. | Mechanical Eng. | Engineering |
| A.R.B. Licences | Electrical Instal. | Metallurgy | Salesmanship |
| Art (Fashion, Illustrating, Humorous) | Electronics | Motor Eng. | Servo Mechanisms |
| Automobile Eng. | Electronic | Painting & Decorating | Shorthand & Typing |
| Banking | Draughtsmanship | Photography | Short Story Writing |
| Book-keeping | Eng. Drawing | P.M.G. Certs. | Short Wave Radio |
| Building | Export | Police | Sound Recording |
| Business | Gen. Cert. of Education | Production Eng. | Telecommunications |
| Management | Heat & Vent. Eng. | Production Planning | Television |
| Carpentry | 'Hi-Fi' Equipment | Radar | Time & Motion |
| Chemistry | High Speed | Radio | Study |
| City & Guilds Exams | Oil Engines | Radio Amateur (C & G) Licence | Tracing |
| Civil Service | Industrial Admin. | Radio Engineering | Transistors |
| Commercial | Jig & Tool Design | Radio & Television Servicing | Welding |
| Subjects | Journalism | Refrigeration | Workshop Practice |
| Commercial Art | Languages | | Works Management etc., etc. |
| Computers | Management | | |
| Customs Officer | Maintenance Eng. | | |

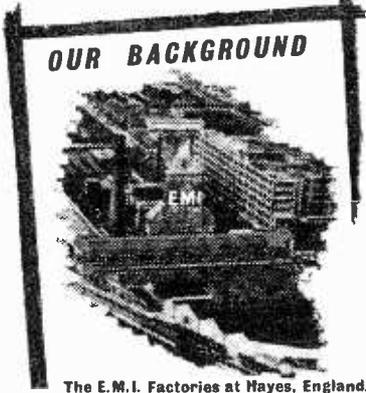Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Exams., R.T.E.B. Servicing Certificates, R.S.A. Certs., etc., etc. Moderate fees.




The E.M.I. Factories at Hayes, England.
The only Home Study College operated by a world-wide manufacturing organisation

EMI

INSTITUTES

NEW! Courses with PRACTICAL EQUIPMENT

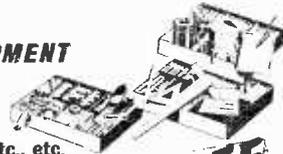in RADIO · TELEVISION · MECHANICS
CHEMISTRY · ELECTRICITY
DRAUGHTSMANSHIP · PHOTOGRAPHY etc., etc.



POST THIS TODAY

To :- E.M.I. INSTITUTES, Dept. 32K, London, W.4.

NAME _____ AGE _____
(if under 21)

ADDRESS _____

I am interested in the following subject(s) with/without equipment _____

FREE


BLOCK CAPS PLEASE

JUNE/58 (We shall not worry you with personal visits)

102

- Part of "His Master's Voice" Columbia, etc., etc.

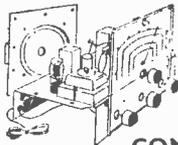STOCK CLEARANCE OF CHASSIS. TERMS AVAILABLE



SUPER CHASSIS, 99/6
5 valve octal set hot chassis, including R. speaker, 4 control knobs (Tone, Volume, Tuning, w. change sw.), 4 w. band with position for gram P.U. and extension speaker. A.C. Ins., Carr., 5/6.

**LOOK!
COMPLETE T.V. CHASSIS, 49/6**

Made by famous manufacturer. R.F. E.H.T. unit included. Drawings 2/6 or FREE with order. Chassis in 3 separate units (Power, s. vision, Timebase) inter-connected. These chassis can easily be fitted into existing console cabinets. Less valves and tube. Channel 12-2-55. Easily converted to L.T.A. Ins., Carr., 10/6.



HOME RADIO, 79/6
A.C. D.C. Universal mains. 5 valve octal set hot 3 w. band receiver, can be adapted to gram P.U. In an attractive wooden cabinet. 18" x 11 1/2" x 8 1/2". Ins., Carr., 7/6.

POPULAR RADIO OR RADIOGRAM CHASSIS, 39/6

3 w. band and gram. 5 valve s. hot. International circuit. Ideal table gram, but still giving high quality output. 4 knob control 8" P.M. speaker. 7.9 extra. Set of knobs, 2-. Chassis size 12" x 6" x 9". Less valves. Ins., Carr., 4/6




HEADPHONES, 1/9. Single earphone and band C.L.R. Ideal for crystal sets, extension on radio, etc. Post 1/3.
CHASSIS, 1/- each. 6 or 8 valve. Latest type midgeet valve design for A.M. or P.M. Brand new cadmium plated on heavy w.g. steel. Size 12 1/2" x 7 1/2" x 2 1/2". P. & P. 1/9. 4 for 4-. P. & P. 1/3-. 12 for 10-. Carr. 5/-.
INSULATING TAPE, 1/6. Finest quality 75% 1/2" wide. Post 9d. Closed Thursdays, 1 p.m. Open all day Saturday. Send for FREE 1958 Catalogue. Liverpool St. to Manor Park Station—10 mins.

DUKE & CO. (Dept. 4), 621/3, ROMFORD ROAD, MANOR PARK, E.12. Tel.: ILF. 6001/3

T.V. TUBES 17" £7.10.0 14" £5.10.0.

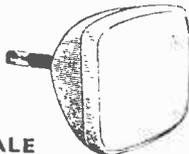
12 month guarantee. We still retain our high quality after 3 years. Set tested. Reconditioned. Shown working to personal shopper. "SPECIAL OFFER" of 14", 15", 16" round T.V. tubes at £5. Convert your 9", 10", 12" to these sizes. Full details in our catalogue on request.
12" T.V. 14 1/2" £5.8.26. 3 month guarantee on all round tubes. Ins., Carr., 15/6.



SPEAKER SALE

29 3/4" Extensions in cabinets. Complete, fitted with 8 P.M. speaker "W.B." or "Goodmans" of the highest quality. Standard matching to any receiver. (3-5 ohms). Plug and switch included. Money refunded if not completely satisfied. Ins., Carr., 3/6.
8" P.M. Speaker, 8/9. Ideal for kitchen and bedroom extension. Let the lady of the house enjoy that Radio or T.V. programme. Complete with (L.T.A. trans., 10-. P. & P. 2/9.

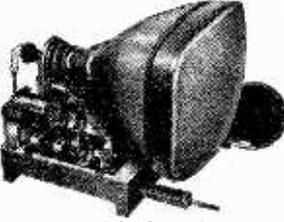17in. T.V. CHASSIS, TUBE & SPEAKER £19.19.6



Latest improved circuits, higher E.H.T. (brilliant picture), improved sensitivity (for greater range). Chassis easily adapted to any cabinet. 17" Rectangular tube on adapted chassis. Channels 1-5. Less valves. With all-channel Turret Tuner, 50.- extra. Chassis size: 14" x 11" deep. With 5 valves. 6SN7GT, 6V6, EY51, 2 6D2S, £21.19.6. With all valves including 6L6, EL38, 7 6F1's, £25.19.6. 12 months guarantee on tube, 3 months on valves and chassis. State B.H.C. channel and L.T.A. if TURRET TUNER ordered. Ins., Carr., 25/6.

14in. T.V. CHASSIS, TUBE & SPEAKER £13.19.6

As above, with 14" round tube. Guaranteed 3 months. With 5 valves, £15.19.6. With all valves, £19.19.6. All-channel TURRET TUNER, 50.- extra. Ins., Carr., 25/6.

Z & I AERO SERVICES LTD.,

Retail Shop: 85, Tottenham Court Road, London, W.1.
Tel.: LANGHAM 8109
Head Office: 14, South Wharf Road, London, W.2.
Tel.: AMBASSADOR 0151

ARR-3 F.M. RECEIVERS. Two R.F. stages, two I.F. stages, two Audio stages; Automatic Frequency Control; Frequency Range 62-70 mc/s. Easily converted to B.B.C. V.H.F. Band. Price complete with conversion kit, full conversion instructions and circuit diagram. ... £5.10.0 15 - p.p.

MARCONI CR-100 2 RECEIVERS fully overhauled and in perfect condition £27.10.0 20 - p.p.

MARCONI CR-150 RECEIVERS. 2-40 mc/s. dual superhet, perfect condition £50.0.0 20 - p.p.

COMMAND TRANSMITTERS. used, 4 to 5.3 mc/s or 5.3 to 7 mc/s 25 -
(callers only)

EDDYSTONE POWER PACKS. Mains operated:
Output 175V HT-6.3V LT 35 - 7/6 p.p.
Output 303V 200 mA HT-12V L.T. 49 6 - 7/6 p.p.


VALVES:

6U4G	7-	8A3	4-	6AC7	6-	6AG7	3/8
6AC7	10-	6AL5	4-	6AM6	4/8	6B4G	5/8
6BB	18-	6C4	6-	6P3A	5	6BU5	1/9
6J5	4/6	6J6	3/8	6K7	8-	EB01	5/-
EB03	7-	EP3A	5-	OD3	5/6	VR105-30	5/6
6N7	7-	6S17	7/6	6SK7	5/6	6SL7	7-
6SN7GT	7-	6S7	8-	6Z3	12-	90T	5/8
813	70-	955	1/6	900G	2/6	EA091	5-

METERS:

2 1/2" Rd. Plug-in 0-90-0-900 uA plain scale	12 6
2 1/2" M.C. A.C. Voltmeter 300V	20 -
3 1/2" Rd.F.I. M.C. 100-0-100 uA	55/-
3 1/2" Rd.F.I. M.C. 500-0-500 uA	40 -
3 1/2" Rd.F.I. M.C. 1 mA F.S.D	50 -
3 1/2" Rd.F.I. M.C. 0-120V, 200 ohms Volt	15/-
3 1/2" Rd. Mirror Scale Two-range Voltmeter, M.C. 5 100V, basic movement 1 mA, with leather case and prod's.	25 -
Cross pointer meter (L-R meters)	12 6

"ASPDEN" TAPE RECORDER KITS

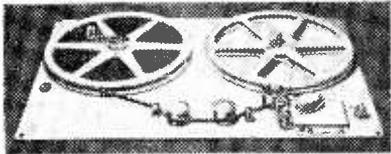

TAPE DECKS. 2-speed, twin track, easy to assemble kits with finest motor, Ferroxcube heads and full instructions.

MODEL 582 for 5in. spools, kit £8.5.0.

MODEL 782 for 7in. spools, kit £9.5.0.

Either model assembled and tested, 30.- extra.

AMPLIFIER kit. 2 1/2 watt, record, replay, 2 recording positions, neon indicator, etc., £5.18.0. Power pack kit for above, £2.18.6 (both without valves). Carr. and packing extra.

YOU CAN BUILD A QUALITY TAPE RECORDER

R.C.W. of Co. Durham writes:—
"... I have been using this equipment very successfully for some months now. Many people who have heard it have been staggered that such quality can be obtained for such a low price."

This tape deck and amplifier is being used in the Antarctic by an Expedition member.

Send stamp for full particulars to:—
W. S. ASPDEN Stanley Works, Back Clevedon Rd., BLACKPOOL, Lanes.

News from the Trade

SIGNAL GENERATOR

A NEW signal generator is announced by Radio & T.V. Components. Details are as follows:

Coverage 100 Kc/s.—100 Mc/s. on fundamentals and 100 Mc/s. to 200 Mc/s. on harmonics. Metal case 10in. × 6½in. × 5½in.. grey hammer - finish. Incorporating three miniature valves and metal rectifier. A.C. mains 200/250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent.; modulated or unmodulated R.F.. output continuously variable 100 milli-volts, C.W. and mod. switch. variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2 per cent. Price £6 19s. 6d. Or 25s. deposit and 6 monthly payments of 21s. 6d. Post & packing 5s. extra.—Radio & T.V. Components (Acton) Ltd., 23, High Street, Acton, W.3.

REDUCED BATTERY PRICES

THE Ever Ready Co. (G.B.) Ltd., have released the latest edition of their price list for batteries in form of a wall chart.


All types of radio, lighting, hearing aid, photoflash, electronic and transistor "power pack" batteries are listed. A special feature is the battery replacement list for radio receivers, gramophones and electronic equipment.

Convenient to be hung on wall or counter, and easy to read, the wall chart should be invaluable to Ever Ready dealers all over the country to whom supplies have been despatched.

"SOUND 777" PRICE INCREASE

OWING to the increase in the list price of the Collaro tape transcriber from £22 to £25, Tape Recorders Ltd., have found it necessary to amend the price of the "Sound 777" tape recorder from 40 gns. to 44 gns. list. They have also been faced with the additional rising costs of both labour and material and the total increases have been taken into consideration in fixing this new price.

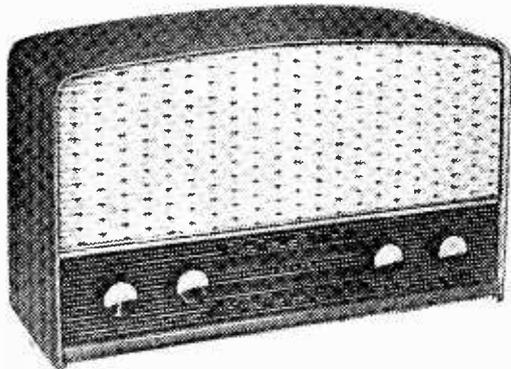The "Sound 777," even at the new price, is




The new Cossor A/M radio receiver.

still claimed to be the lowest priced 3-speed and fully automatic push button tape recorder in the world.—Tape Recorders (Electronics) Ltd., 784-788, High Road, Tottenham, N.17.

THE MOTEK K9 TAPE DECK

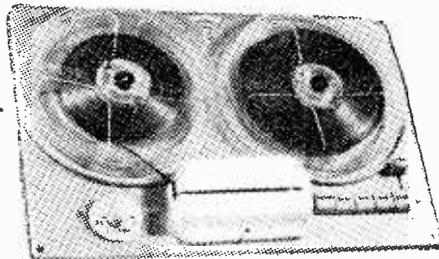WE again show this deck which, unfortunately, was incorrectly described in the caption in our April issue as The New Motor Tape Deck. The manufacturers, who submit each deck to exhaustive



The new Motek tape deck.

tests before despatch guarantee them for a period of 12 months and we understand that production of the MOTEK K9 is now in full swing to meet the ever increasing trade demand.—Modern Techniques, Wedmore Street, London, N.19.

NEW COSSOR A/M RADIO RECEIVER

A NEW A.C./D.C. receiver, with printed circuit construction and high sensitivity 8in. × 5in. elliptical speaker, has been released by Cossor Radio & Television Limited. The receiver, Model 571, operates on long and medium wavebands. An attractive tuning scale, with calibration in red and green, is admirably set off in a veneered wooden cabinet.


Three Cossor "multiple" valves and rectifier and internal Ferrodync rod aerial complete the specification of this attractive receiver which retails at £18 18s. (tax paid).—Cossor Radio & Television Ltd., Cossor House, Highbury Grove, London, N.5.

PHILIPS REDUCE PRICE OF "MUSETTE" PORTABLE RADIO

PHILIPS ELECTRICAL LTD., announce that the tax-paid price of their "Musette" battery portable radio receiver has been reduced from 12 gns. to 9½ gns. (List £7 4s. plus P.T. £2 15s. 6d.).

This reduction has been made possible by the adoption of new manufacturing techniques at the company's Croydon factory, the resultant savings in production costs being passed on to the public.

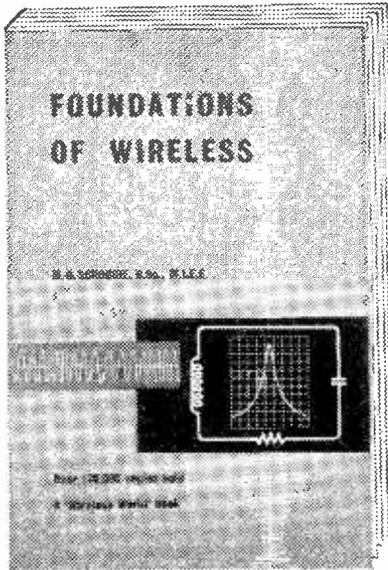Full rebates will be granted to dealers to cover stocks in hand. A window streamer and showcard are also being supplied.—Philips Electrical Limited, Century House, Shaftesbury Avenue, London, W.C.2.



NEW enlarged edition of a book that has already sold over 170,000 copies

Foundations of Wireless

7th Ed. by M. G. Scroggie B.Sc. M.I.E.E.

In an easy style, this book covers the whole basic theory, starting from the most elementary principles. It deals with receivers, transmitters, amplification, valves, transistors, aerials, power supplies, and other aspects of the subject. More emphasis is now made on f.m. and v.h.f., and cascode v.h.f. amplifiers, colour television, c.n.t. generators and transistor d.c. voltage raisers are included for the first time.


Published for 'Wireless World' by

Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1

15s net by post 16s 4d

from leading
booksellers

THE BARGAIN OF THE YEAR

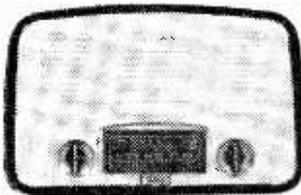

BEREK (EVER-READY) BATTERY RADIO

4 Mullard Valves

MW 200-550 m SW 20-75 m

Brand New in Sealed Cartons.

BELOW COST £5.19.6.

While they last.

CASH ONLY CARRIAGE PAID
Cancelled Export Order.

Not a kit. A factory built Super-sensitive All Dry Battery Receiver. Uses Ever Ready B136 or B103 obtainable everywhere.

H. P. RADIO SERVICES LTD.,

51, County Road, LIVERPOOL, 4.

Tel. : AINtree 1445. TELEX 62-244

: Established 1935

TV SPARES

41, CALL LANE,
LEEDS 1.

Tel. 28559.

We specialise in exact replacement components, e.g.

Mains Droppers for Ultra twin R5. 1,690Ω + 1,450Ω, 5/3; R7. 175Ω + 340Ω + 410Ω, 5/3. For Phillips: R1. 150Ω | 250Ω, 170Ω + 100Ω, 6/5. R3. 430Ω + 200Ω + 180Ω, 4/10, etc.

Line Output Transformers: LOP4 fits Pye V4, VT4, V7, VT7, 55/2. LOP6 fits FV2, FV4, 50 9.

TSL HI-STAB ½ watt Resistors. 10Ω to 10MΩ, 5d. each. 4/- per 12 mixed.

Crystal Diodes, 1/3. Red Spot Transistors. 7/6.

Service Sheets. 6 for 5/-. 12 for 9/-. P. & P. free. These are all mixed. No enquiries for sheets, they are sold just as they come

New type AVO Multiminor Meter, £9/10/-. P. & P. free by registered post.

Please enclose postage. No lists available yet.

LYONS RADIO

LTD.

Dept. M.P., 3 GOLDHAWK ROAD
SHEPHERDS BUSH, LONDON, W.12

Telephone: SHEpherd's Bush 1729

METERS.—All moving coil types, in brand new condition, all 2½" dia. First 3 flush panel mtg. last 2 projection mtg.

0/1mA.—PRICE 19/6. 0/500mA.—PRICE 10/6
Centre zero 200 0.200mA.—PRICE 8/6
0 500 micro-amps.—PRICE 17/6
0/50mA.—PRICE 9/6

UNIVERSAL MEASURING BRIDGES. Ex Gov. by Mullards, measure 0.1 ohms to 10 megohms and 10 pF to 10 mfd. Can also be used to calculate power factor, for percentage tolerance measurement and, with the use of external standards, inductance measurement. Operate from 100 to 250 v. 50 cps. A.C. mains. Supplied in good condition and working order with instructions. PRICE ONLY £7, post 3/6.


TRANSFORMER RECTIFIERS. Provide an output of 50 v. D.C. at 1 A. Trans. rating: Pri. 230 v. 50 cps. Sec. 63, 68 and 69 v. at 1.5 A., size 5 x 4 x 3½ ins. Rect.: P.W. bridge type 10 x 2½ ins. dia. PRICE the pair, 21/-, post 3/6.

AMPLIFIER UNITS TYPE A.1134A.—Two stage audio amplifiers which can be used for intercom. purposes, as a gram. amplifier and for use with crystal receiver, etc. Valves fitted are one each VR21 and VR35. Operate from 50 or 120 v. H.T. battery, 2 v. accumulator and 9 v. G.B. In neat metal cases, 7 x 5 x 4 ins. In new condition with connection details. PRICE ONLY 9/6, post 3/-.

FROM THE HOME OF HI-FI



High Fidelity at its finest

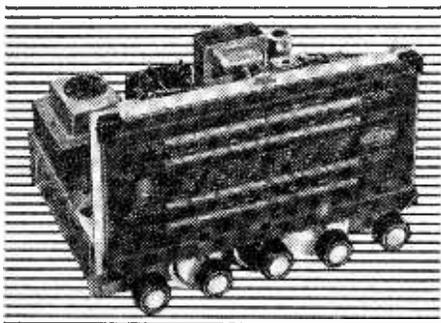

Model H4PP. (Illustrated) NEW! A complete Dulci High Fidelity radiogram chassis, combining sensitivity, selectivity and stability to delight the most discerning listener. Outstanding record and VHF reproduction, 4 wavebands. Ultra linear amplifier gives ample power output. Push-pull system, wide frequency response, bass and treble controls. Fits easily into any existing cabinet. The perfect chassis for modernising your radiogram.

AM/FM Model H4PP. Price **£29.3.10.** inc. P.T.

Model H4. AM/FM Radiogram chassis. 7 valve, 4 waveband superhet with FM (VHF). Magic eye tuning indicator. High sensitivity. Dial size 11 1/4" x 5 1/2". Sockets for speaker (3 and 15 ohm.) Mains sockets for motor. **£24.6.6.** inc. P.T.

Model H3. Three waveband model (inc. VHF), 6 valves. For 3 ohm. speaker. Chassis immensely sensitive and stable, giving highest quality reproduction. Wide range Tone Control, with pick-up, extension speaker and gram motor sockets. **£20.17.0.** inc. P.T.

Write for full details

DISTINCTLY



QUALITY PRODUCTS

THE DULCI COMPANY LTD. 97-99 VILLIERS ROAD LONDON N.W.2. TELEPHONE: WILLESDEN 6678/9

62AK: This Month's Bargains

HI-FI EQUIPMENT

AVAILABLE FOR IMMEDIATE DELIVERY. Amplifiers, speakers, pick-ups by Gramplan Leak Quad Rogers R.C.A. Spectona W.B. Wharfedale, etc.

VOLTMETERS. Dual range 0-5 v. and 0-100 v. voltmeters. M.C. 1,000 Ω/v . Ranges easily extended. With test prods and leads. Complete in solid leather carrying case, 6 1/2 in. x 5 in. x 2 1/2 in. A gift at 25/- post free.

100 Kc/s XTALS, by famous American makers. 3-pin based holder. New condition, worth £3.10.0. Only 25/- post free.

PLUG IN NOISE LIMITERS. 3 Position Limiting. No Rewiring. Best with H.R. Phones. Only 8/6. P. & P. 1/6.

HEADPHONES. H.R. Type 4,000 ohms, very sensitive. Only 12/6 pr. Post 1/6. C.L.R. type (low res.) 8/6. Post 1/6.

CHOKES. 2.5 mH, 120 mH pie-wound R.F. chokes. 2/- each. 3 or more post free.

AERIAL WIRE. Copper, 7.25 stranded: 140ft., 10/-, 70ft., 5/-. Hard Drawn 14g.: 140ft., 17/-; 70 ft., 8/6. P. & P. 2/-.
RIBBED GLASS 3in. AERIAL INSULATORS. 1/6 ea., or 6 for 7/6. P. & P. 1/6.

CONDENSERS. 8 μF 600 v. Trop. 750 v. normal condensers. NEW, ex W.D. stocks, 5/6. P. & P. 1/6

ABSORPTION WAVEMETERS, 3 to 35 Mc/s in 3 switched bands. Complete with indicator bulb. 17/6 post free.

CHAS. H. YOUNG LTD.


Dept. 'P' 110, Dale End, Birmingham, 4. (CEN 1635)

No C.O.D. on orders under £1.

Please Print Your Name and Address.

P.C.M. SWITCHED TUNER

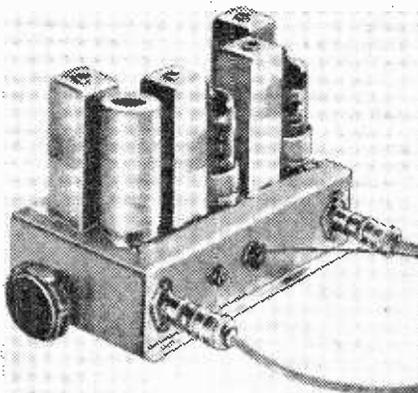(as described on P.205, last month's P.W.)
 SUPERB RECEPTION OF V.H.F.



This SWITCHED Tuner is a sensitive and entirely drift free unit fitted with the new DIOMATIC-FREQUENCY CONTROL which is 10 times as effective as a conventional reactance valve. DOUBLE VALVES are used throughout, enabling a SIX VALVE circuit to be constructed on a chassis 3in. x 5 1/2in. An included PRE-AMPLIFIER gives 10 volts output. All parts and valves £7.19.6; less valves £6.5.0. Coil set including Diomatic control circuit £2.10.0. Chassis and switch 10/6.

From C. & G. KITS, Dept. F.M., 285, Lower Addiscombe Rd., Croydon, Surrey.

RECEIVERS & COMPONENTS

MIDDLESBROUGH. Largest stocks on N.-East coast. Radio, TV components. FM Kits. Gram. Cabinets. Tape Decks, Leak Amplifiers, Valves, etc. Callers only. PALMERS, 106, Newport Road. (Phone: 3096.)

TELEVISIONS NEEDING ATTENTION. 9in.-10in. models, £4/10/- each. 12in. models, £6/6/- each. 15in. models and Philips Projection models £11/10/- each; immediate despatch, carriage paid. BARKERS, 325, Brockley Road, S.E.4. (TID 6752.)

VALVES from 1/6. Radio, T.V. Components; low prices. Lists 3d. J. PALMER, 32, Neasden Lane, N.W.10.

T.V. TUBES, 30/-, with cathode heater shorts; 15/- with burn; carr. extra; ideal for testing; good picture. Please enquire for types and sizes required. DUKE & CO., 623, Romford Road, Manor Park, E.12. (ILF 6001.)

F.M. AERIAL offers from manufacturers. Indoor Dipole, with mast and base, 12/6; "H" dipo, 22/6, post free. Send 1/- P.O. for our full T.V. Aerial Lists with illustrated parts catalogue and aerial data. Build your own aerials from our fully machined parts and save money. SKYLINE WORKS, Burnshall Road, Coventry.

PYE POWER TRANSISTORS, brand new 25/- each. A.C. R109 Power Packs, fully smoothed, 30/-; Receivers, 85/-, new, 10 watt Amplifiers, with Mullard 5-10 Preampifier Mixer, 3/15 ohms. out., £6/19/6; 12 volt 12 watt new Amplifiers, with Mike, maker's guarantee, 6 gms. 6-volt charger Transformers, with Rectifier, 12/6; 12 volt, 15/6. Send 3d. stamp for large list Transistor Components, Amplifiers, etc. TRAN-SISTOR TECHNIQUES, 175, East Dulwich Grove, London, S.E.22. (GIP 1275.)

TRANSISTORS, Red Spot, 7/6 post free.
VALVES.—6K7G, 4/6. EF36, EL32, 3/9.
CRYSTAL DIODES, 1/-, All post extra.

Leading Brands of Components Stocked. B.V.A. Valves at list prices.

PETHERICK'S RADIO SUPPLIES
9A, Westcombe, Bideford, N. Devon

SENTONS FOR SALES SERVICE AND SATISFACTION

ELECTROPTICAL SPEAKERS 7in. x 4 1/2in. 9,000 LINE Gauss flux density. 3.5 Ohms. 19.6, post 1/6.

WESTINGHOUSE METAL RECTIFIERS HALF WAVE, LW1 input 240 volts. Output D.C. nominal 270 volts. Output current 330 mA. 19.6, post 1/6.

MAIN TRANSFORMERS, PRIMARY 192-250 volts, SEC. 280-0-280 100 mA. 6.3 volts 3.7 amps. 6.3 volts 0.95 amps. Mounted panel and fuse holder 25/-, post 3/-.

V.I.F. TWIN GANG TUNING CONDENSERS WITH TRIMMERS, BALL BEARING DRIVE, 0 to 9.79 pF MINIA-TURE, 5/6, post 1/-.

V.I.F. AM-FM TWIN GANG TUNING CONDENSERS, AM 0 to 523 pF FM 0 to 10 pF. Ball Bearing drive, 2 gms. post 1/-.

The above items are only a few of the many lines that we have available at bargain prices. Send 3d. stamp to-day for latest lists. MONEY BACK GUARANTEE ON ALL COMPONENTS.

J. E. SENTON, LTD., 102, Gray's Inn Rd., Lond. N, W.C.1. Tel.: T2Rminus 0229-9

RATES: 5/8 per line or part thereof, average five words to line, minimum 9 lines, Box No. 1 - extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., Strand, London, W.C.2.

ANNAKIN

The Greatest Bargains ever offered: 1143 A. Rods, less valves and crystals: Receiver type 71.—3/6 ea., post 3/6. Transmitter type 50.—2/6 ea., post 3/6. Amplifier type 185.—3/- ea., post 3/6.

OTHER SNIPS
Test Oscillator G219.—Covers 1.4-22 Mc's in 5 bands. Smart dial, handswitch, attenuator and valve. Less batteries. In smart steel case. New. £1 ea., carr. 6/6.
Handsets No. 2.—Bakelite. L.R. phone and carbon mike, plug, cord. New, 12/6 ea., post 1/9.

Monitor Crystal 4A.—Calibrated 100-120 Mc's. B. Marconi. Has A.C. power pack, with 1-VU39, 2-VR91, 1-VR92, 1-VR68, 1-VR67, 1-VR51. A.F. modulated. A super job. Less crystals. Metal case. New, 55/- ea., carriage 7/6. Money-back Guarantee. Send S.A.E. for lists or enquiries. Above carriage, England/Wales.
25, ASHFIELD PLACE, OTLEY, Yorks.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

AMAZING OFFER.—Originally £10-£100 each. Ekco, Pye, H.M.V., Marconi, Philips, Murphy, etc., 9-10in. Televisions, complete, not working, 50/- each; carriage paid; immediate despatch; 12in., £5/5/-; 15in., £9; Philips 17in. Projection Televisions, £9/15/-; TOMLINS, 127, Brockley Rise, London, S.E.23.

METERS (NEW BOXED M.O.S.)
Ammeters. 6 in. round, switchboard mounting, moving iron, 50 cycles A.C., scaled 0-50. Price £4, postage 3/6.
Ammeters. 2 in. round, moving coil, complete with m.a. scale, 50 cycles movement, scaled 0-20. Price 10/6, postage 1/6.
Voltmeters. moving coil, 2 in. round, 10,000 ohms resistance, scaled 0-50. Price 10/6, postage 1/6.
Voltmeters. 2 1/2 in. round, moving iron, 50 cycles, scaled 0-20. Price 15/-, postage 1/6.
Voltmeters. 2 1/2 in. round, moving iron, scaled 0-500. Price 17/6, postage 1/6.
SPEED ELECTRICS. Eastwood, Notts.

P. HARRIS ORGANFORD DORSET

30ft. ONE PIECE WOOD POLES. 4in. dia. throughout, perfectly round, straight and smooth. Hollow and light yet very strong, made for radio. 35/- (special cheap rate). **INSTRUCTION MANUALS** (not photos). HRO, AR-88, AR-77, DST-100, No. 12 Sender, BC-221: all 27 s. **MODULATION TRANSFORMERS.** 85 watts audio, 40/- (7/6) 200 watts audio, 65/- (10/6). **TRANSFORMERS.** 4" x 12" Bendix, totally enclosed, 6ft. high x 22 x 2), standard rack width, £3 (20/-). **RACK SHELVES.** 12in. deep folding chrome and grey, 12/6 (4/-). **P.O. RACKS** 42 luxé channel sides, drilled both sides, 32/6 (2/6). **P.P.C. (P.P.S.)** 6ft., 90° (20/-); 8ft., 6in., 120° (30/-); 5ft., angle sides, 80° (15/-). **STEP DOWN TRANSFORMERS,** double wound totally enclosed, 23/115/-, 200 watts, 45/- (7/6). 1,000 watts, 100° (30/-). **RESONANT TUNING CIRCUITS** by Woden, 2H, 400 ma, 20/- (5/-). **TRANS-MITTER TRANSFORMERS,** 190/250v. Primary, 1,000-0-1,000v, 500 ma, 75° (10/-). **POWER UNITS,** 6v. D.C. input, 250v, 83 (20/-). **TRANSFORMER CHOKES** by Woden, 2H, 400 ma, 20/- (5/-). **TRANS-MITTER TRANSFORMERS,** 190/250v. Primary, 1,000-0-1,000v, 500 ma, 75° (10/-). **POWER UNITS,** 6v. D.C. input, 250v, 83 (20/-). **TRANSFORMER CHOKES** by Woden, 2H, 400 ma, 20/- (5/-). **VOLTMETERS,** 2 1/2in. flush 0-15 A.C./D.C., 15/- (2/6). **MILLIAMMETERS,** 2 1/2in. flush 0-30 or 0-100 mV/cm, 12/6 (2/6). **PRECISION AMERICAN CRYSTALS** for BC.221, octal base, 1,000 Kcs, 20/- (1/8). **UNUSUAL VALVES,** guaranteed 6L5 metal, 12/6 (1/-). AL-69, 40-12, 83-B, DA-41, all 20/- (1/-). **RIPE'S** high speed relays, 7/3 (1/6). **DEPT-2** descriptive List of over 1,000 different items available. Amount in brackets is carriage England and Wales.

"OSMOR NEWS." Fit an Osmor Band III Equaliser! Tunable Rejection Components lists for "P.W.", "Consult Car Radio", "P.W.", "The Chorister" and "R. Constructor". Beginner's S. Wave 1 Valver" on request OSMOR, 418, Brighton Rd., S. Croydon. (CRO 5148.)

UNREPEATABLE OFFER.—12in., 5 Channel T.V., £15; 14in., £22, good working order. C. EDWARDS, 1070, Harrow Rd., London, N.W.10. (Phone: LADbroke 1734.)

SURPLUS COMPONENTS, as new. P.M., L/S 8in., 15/-; 6in., 10/-; 5in., 7/-; all 2-3 ohm. O.P. Trans., 35 ohms, 7k ohms, or 12k ohms, 3/6 each; 485 Kc. I.P.T.S. Std. or midget, 5/- pair. Midget Tuning Cons., 300 pF, 5/- Please include postage. L. & E. 208, Queenstown Rd., S.W.8.

FOR LOWEST PRICES and bargain offers in FM, AM, radio, gram. and Hi-Fi Units, Tape Recorders, FM and TV Loit and Outdoor Aerials, Cabinets, etc., send 3d. stamp for illustrated details. Easy terms. All goods new and guaranteed. M. RICHARDS, Dunker, Carvoza Road, Truro, Cornwall.

SMART TALE, 0-100, 2in. x 2 1/2in. grey, for volume, tone, etc., 1/-, plus 3d. post. COTEN SUPPLIES, 10, Coten End, Warwick.

RESISTORS-CONDENSERS, 100 new wire-ended Resistors, 1, 2 watt, mixed, useful values, plus 25 new moulded Mica Condensers, 10/-, post free. Resistors only 8/-. Cash with order. WHITE, The Briars, Needing-worth, St. Ives, Hunts.

T.V. FILTER of unique design, easily fitted. Stops wire netting or patterning on your picture. Only 10/6. LAVO ELECTRICS, 8, Albert Terrace, Whitehaven, Cumb.

GUARANTEED TELEVISION, 12in. 5-Channel models, first-class picture, £26 each, carriage paid. T H E GRAMOPHONE SHOP, 19-21, Brockley Rise, London, S.E.23.

FM-AM CHASSIS

PUSH-PULL OUTPUT — 7 VALVES
HIGH SENSITIVITY — GRAM INPUT
7 x 5 FULL VIEW SCALE
AFC—AVC
ONLY 113

REL. SOUND PRODUCTS CO.
Marlborough Yard, N.19 Tel. ARC 5978
29 mins. West End

R.F.P. One valve chassis, 2/3, Coll. 4/- 3 Dial Plates, 2/3. 0005 Mid. Tuning, 3/10. 0093, 3/10. Instructions, 9d. Chassis 3D Transistor, 3/-, Instructions, 9d. Seven Transistor superhet portable Instructions 1/6.

TRANSISTORS, Audio, 10/-. R.F. 21/- **THREE** Waveband prealigned superhet coil pack, 28/-, plus P.T. 10/-.

T.R.F. coil set, 8/-. Superhet coil, pair 8/-, ALL coils complete with crystals. Connecting wire, stranded P.V.C. covered, 2d. yd.

Resistors, 6d.
TELETRON pocket 3 TRANSISTOR "COMPANION," Complete Kit, 89/6, p.p. 1/6.

ELECTRADIO

18, Broadlands Avenue,
Keynsham, Som.

SALE

SATISFACTION OR MONEY BACK GUARANTEE IF RETURNED WITHIN 7 DAYS

TRANSISTORS.—Red Spot L.F. (up to 80 kc/s); 7- Blue Spot (up to 16 Mc/s), 10- White Spot R.F. (up to 2.5 Mc/s), 14- Collins' T.C.S. Transmitters (store soiled), 1.5-14 Mc/s. £5.10.0; Receivers, ditto, £4.10.0 (£10 pair).

GUARANTEED T.V. TUBES!
(EX EQUIPMENT)

12in. (MW31-74, 331, etc.) £5. 5.0
14in. (MW33-24, CRM141, etc.) £4. 10.0
17in. (MW48-84, 415, etc.) £6. 10.0
17in. (CRM171 only) £5. 0.0
(All guaranteed 6 months) (carr. & ins. 12/6)

4 SPEED AUTO STAAR GALAXY

Modernise your radiogram or build a super record player. Famous Ultra-Modern Autochangers (as shown but less base) with latest Power Point or ACOS GP85 Light-weight turnover Sapphire Pickups. Beautiful Cream and Chrome finish. 10 Records taken of any size or speed. For all mains voltages (post 4/-).

£3-19-6! (listed approx. £13)



Above Autochanger mounted on stream-lined high-finish case, as shown, to make complete add-on Player, which will play any 10 Records through your Radio or Amplifier for all mains voltages.

£5-15-0

COMPLETE PLAYER in covered two-tone quality portable Case, with above Autochanger, excellent 3-valve Amplifier, 7-inch Speaker, beautiful reproduction (worth over £20).

13 Gns.

GUARANTEED RADIO VALVES.

BOXED, 24 HOUR SERVICE	
5J40	6 6E4K7G 6 - EB91 5 6E20 8 -
5Z40	9 - 6B8N7G 5 6EB23 7 - 1Z40 7 8 -
6X5	5 6B174T 12 6E32 5 - 1V32A 5 -
6A8	9 - 6V6C 6 - EB91 9 8 RTW3 6 -
6AL5	5 6E664T 6 6E22 9 - M11 9 -
6AM6	7 6E69W 6 6E081 8 - P61 2 6 -
6BY6	6 6E6X1 6 - EB92 8 6 PC84 9 -
6B59	6 6E6X5GT 5 - EB93 8 6 PC85 11 6 -
6C1	4 6E7 7 6E34 12 6 PC86 12 6 -
6C9	4 6E75 6 6E05 9 - PC82 11 -
6D6	11 - 12A7M 8 6E080 12 - PE25 5 -
6D6	4 6 12A7 8 - EB92 12 - PE25 13 6 -
6H5	2 - 12A7T 6 6E043 8 6 PL2 9 -
6H5	11 - 12A7T 6 6E043 8 6 PL2 11 -
6J5GT	4 - 12A7T 6 6E046 4 - PY80 8 6 -
6J5G	3 - 12A7T 7 6E047 7 - PY81 8 6 -
6J5H	5 - 12L64T 6 6E074 8 - PY82 9 -
6K74	4 6E524T 7 6E074 8 - PY83 8 6 -
6K74T	6 6E524T 7 6E074 8 - PY83 8 6 -
6K73	6 - 8 - 7 6E090B 4 6A44 2 6 -
6K8C	7 6E8 7 6E89 8 6 SP1 2 6 -
6L6	8 - 1207AM 3 6E85 7 - 122 7 6 -
6L7	6 6E1 9 6E89 8 6 T52 6 6 -
6R74	6 6E1 9 6E89 8 6 T52 6 6 -
6S47M	7 - C1C 9 6E95 8 6 UY11 8 -
6S47M	5 6 EA59 1 6E132 4 6 VP41 6 6 -
6S17M	7 - EB34 1 6E191 4 - 866A 11 6 -

S.A.E. FOR FREE LIST OF 500 SUPER SNIPS

All items less 5/-, and post free for a dozen or more.
Postage 1/- in £1 (1/3) in £1 Speakers (Trans.), Min. 6d. No C.O.D.
100 TELEVISION SET BARGAINS TO CALLERS AT

TECHNICAL TRADING Co.
350/352, FRATTON ROAD,
PORTSMOUTH

FOR SALE

AMERICAN MAGAZINES. Year's subscription "Audio" 35/-; "High Fidelity" 50/-, Spec. copies 4/- & 5/- ea. Cal. free. WILLEN LTD. (Dept. 40), 9, Drapers Gdns., London, E.C.2

TAN IN 24 HOURS.—Super-tone Sunray Lamps. Ultra-violet infra-red combined; automatic exposure; controlled emission; all mains. Listed £7 10/- our price, 83/- S.A.E. illustrated brochure. Dept. 100, SCIENTIFIC PRODUCTS, Cleveleys, Lancs.

EVERYTHING FOR THE AMATEUR. Write for our new List catering for home engineers, Hi-Fi Fans, Tape Recording Fans, etc., etc. Probably the most comprehensive in the trade. Price 1/-. R.H.S., 155, Swan Arcade, Bradford, 1.


RADIO SHOP (next to Empire Cinema), Normanton, Yorks.—Special offer: Co-axial Cable, 5d. yd.; 100yd. Coils, £1/18/-; "Labgear" Printed Circuit-Diplexers, 11/- each. Please add postage on Co-axial Cable, other goods post free. "Rezentone" brand new, guaranteed, 4-speed Auto-Changer, handy gram., list price 24 gns., our price 20 gns.; "Cyden" Band III Tuners, our price £7; "Brayhead" Tuner Tuners, our price, £6/15/-; Adaptors 7/6; "Collaro" 4-speed Auto-Changers, brand new, £8/15/-. No lists—mail order only. Please address mail orders to: 33, Beckbridge Estate, Normanton, Yorkshire.

VALVE CARTONS, plain white, from 12 to 100,000 "Off the shelf." Miniatures, 10/-; "G.T.s." 12/-; "G's." 14/- per 100, plus 2/- postage. May we quote you for any type of printed carton, all kinds of printing, catalogues, lists, etc.? Quotes and samples with pleasure. J. & A. BOXMAKERS LTD., 75a, Goodwin St., Bradford, 1.

TAYLOR MODEL, 67A Signal Generator: little used; £14/10/-. D. P. ROTH, 154, Lewisham Road, S.E.13.

MAINS FROM 12V. BATTERY.—Brand new American Dynamotor Unit in beautiful black crackle case; weighs about 38lb., but neat and compact—thousands of uses, no conversion required. In seconds makes marvellous, powerful 200/250 A.C./D.C. electric motor, electric fan, dynamotor (gives 250 volts at about 100 watts from 12-volt car battery); runs mains radios, bulbs, etc.; makes ideal rotary transformer, battery charger, etc.; continuous duty, quiet running, doesn't overheat; worth £25; our price, 30/-, with instructions, carriage paid. Satisfaction guaranteed. Send remittance with order. Dept. "A." SCIENTIFIC PRODUCTS, Manor Works, Cleveleys, Blackpool.

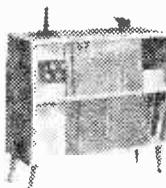CABINETS for SPEAKERS, PYE BLACK BOX & RECORDS.



Write for Catalogue

A. L. STAMFORD (Dept. U29),
20, College Parade, Salisbury Road,
London, N.W.6

WANTED

VALVES WANTED. ECL80, EY51, EY66, PL81, PCF80, and all Miniature Types, U25, 10C1, 10C2, 10F1, etc., 5Z4C, 6K8G, 6V6G. Brand new only. Prompt cash by return. R.H.S., 155, Swan Arcade, Bradford, 1.

WANTED. Transmitter T.59, Trans-receivers, TR.1520, 1934, 1935, 1936, 1987, Receivers BC.312 and type 100, P.S.U. type 381; Dynamotors DM.21 and DM.28, GILFILLAN, 7, High St., Worthing. (Tel.: 8719.)

URGENTLY REQUIRED, new Radio, Television, or Industrial Valves. Also old and obsolete types. Cash prices offered for any quantity. Write, call or phone: MIT 6202, 201, Streatham Road, Mitcham, Surrey.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.
103, North Street, Leeds, 7.

SERVICE SHEETS

SERVICE SHEETS for sale and hire. Radio T.V. S.A.E. enquiries, J. PALMER, 33, Neasden Lane, N.W.10.

SERVICE MANUALS/SHEETS. Tel. Radio for hire, sale and wanted. Mixed Manuals and Sheets. 12 for 10/-; s.a.e. enquiries, W. J. GILBERT (P.W.), 24, Pritchville Gdns., London, W.12.

ENGINEER has complete range new Radio TV Service Sheets, 3/- each; state Model No. required; c.w.o. L. BRENNER, 23, Meadowy Close, Burnet, Herts.

SITUATIONS VACANT

THERE IS a national shortage of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at The School of Marine Radio and Radar (A.S.F.), Hamble, Southampton. For details, apply Commandant, quoting A.12.

EXPEDITION TO ANTARCTICA.—Scientific Assistant (Ionospheric) required by the Falkland Islands Dependencies Survey for the operation and maintenance of special electronic Ionospheric recording apparatus at an Antarctic Base for 2 years. Commencing salary, according to age in scale, £400, rising to £540 a year, with all found, including food, clothing and canteen stores. Free passages. Liberal leave on full salary. Candidates, preferably single, and aged 21-28 years, must be of good education, of high physical standard, and experienced in the servicing of radio or radar equipment. Genuine interest in life at an Antarctic Base essential. Write to the CROWN AGENTS, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience, and quote M315 44623, PU.

(Continued overleaf)

PUBLIC APPOINTMENTS

MINISTRY OF TRANSPORT AND CIVIL AVIATION.—Trainee Communications Officers. Min. age 18. Morse, 20 w.p.m.; type or teleprint, 30 g.p.m.; elementary knowledge of radio. Pay whilst training £7/5/4 p.w. at age 18 and £10/0/6 (men) and £9/15/11 (women) at 25 or over; free meals and accommodation. After training salary £665 to £815; slightly lower for women and at certain stations. Apply: M.T.C.A. (ESB), Comm., Berkeley Square House, London, W.1.

EDUCATIONAL

11-4

EXAMINATION

Write for FREE 24-page GUIDE and Test, stating age of child, to: THE REGISTRAR (Dept. M8), Mercer's Correspondence College, 69, Wimpole St., London, W.1.

LEARN IT AS YOU DO IT we provide practical equipment combined with instruction in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to: E.M.I. INSTITUTES, Dept. PW47, London, W.4.

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook free and post free. B.I.E.T. (Dept. 242A), 29, Wright's Lane, London, W.8.

T.V. and RADIO.—A.M. Brit. I.R.E., City and Guilds, R.T.E.B. Cert., etc. on "no pass—no fee" terms. Over 95% successes. Details of exams, and home training courses in all branches of radio and T.V. write for 144-page handbook free. B.I.E.T. (Dept. 242G), 29, Wright's Lane, London, W.8.

OSMABET LIMITED

14, HILLSIDE ROAD, TOTTENHAM, LONDON, N.15.
TRANSISTOR P.P. amplifier, Mullard 6 v. 250 Mw. circuit, complete kit (less speaker battery), 90/-, circuit, etc., 1/6.
TRANSISTOR AMPLIFIER portable, the very last word, can be built for £15, circuit, etc., 1/6.
TRANSISTORS, tested guaranteed. Audio, 10/-, R.F. 8 Mc. 21/-.
TRANSISTOR midset electrolytics, 6, 8, 16, 32, 50 mfd., 6 v. all at 3/6 each.
TRANSISTOR TRANSFORMERS, for Mullard circuit, 16/- pair.
PRE-AMP, Band III ITV high gain, complete kit 50/-.
MULLARD 3-3 amplifier to spec., built, tested, £7.15.0.
RECORD PLAYER amplifier, 200/250 v. A.C. two stage built, tested, 50/-.
RECORDING TAPE, 1,200 ft., Scotch Box, 27/6. Puretone on metal reel, 12/6.
MAINS TRANSFORMERS, Midket 200/250 v. A.C. output 200 v. 25 mA, 6.3 v. 15, 10/6.
HEATER TRANSFORMERS, 200/250 v. A.C. 6.3 v. 1.5 a, 7/6, ditto 3 a. 10/6.
MULLARD 5/10 output trans. to spec., 8 K. 19/6.
CHARGER, 200/250 v. A.C., 0-12 v. 2 amp., 47/6.
COILS, TRF m/l, with circuit, 7/6 pair.
HEADPHONES, HR 4,000 ohms, new, boxed, 18/6.
ISOLATION CRT low capacity transformers, 1-1.25 (25% boost), 2 v., 4 v., 6.3 v. at 7/6 ea., ditto trans. Mains primary, 200/250 v. A.C. 2 v., 4 v., 6 v., 10 v., 13 v. at 10/6 each.
CHOKES, New, boxed, 65 mA, 5/6; 85 mA, 7/6; 150 mA, 13/6. Postage all orders. Trade and Mail Order.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M. Brit. I.R.E., City and Guilds, R.T.E.B., and other Professional Examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to: E.M.I. INSTITUTES, Dept. PW28, London, W.4.

THERE IS a national shortage of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at The School of Marine Radio and Radar (A.S.I.), Hamble, Southampton. For details, apply Commandant, quoting A.12.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

MISCELLANEOUS

THE TAPE RECORDER SPECIALISTS offer wonderful bargains in Tape. Famous British make. 7in., 1,200ft., 22/6; 5in., 650ft., 19/6; 5in., 650ft. (L.P.), 19/6; 5in., 600ft., 14/6; each plus p. & p. 1/6. Send now, only 500 reels available. Tape Recorders bought for cash; all makes stocked; no interest terms; free offers; specialised repair service. E. C. KINGSLEY & CO. (G.), 132, Tottenham Court Road, London, W.1. (EUSTON 6500.)

HOBBIES

STAMPS.—Wonderful offer. Great Britain Q.E.II. 2/6, 5/- and 10/- values, entirely free to genuine approval applicants enclosing 3d. postage. **WHITE**, Stamp Dealer, Dept. 49, Eastleigh, Hampshire.

BARGAIN OFFERS

ROTARY CONVERTERS. D.C./A.C. 200W, 24V., 11 amps input; 50-110-230V A.C. 50 c/s, S.P. output through transformer. Brand new, suitable for T.V. and tape recorders where mains are not available, £8/10/-, complete with transformer; carr. 10/- extra.

"5" METERS. 2" square flush panel mounting, suitable for AR88 or other receivers. New stock, 39/6, post 1/6.

MORSE PRACTICE SETS. Air Ministry Service type Morse Key, beautifully balanced and fitted with back and front contacts, heavy insulated knob, twin coil buzzer (adjustable note), all wired on base, with space for battery, 10/-, post 2/6. Morse Key only, 4/6, post 1/-, Practice Buzzer in bakelite case, 3/6, post 6d. Twin Coil Buzzer, 5/6, post 9d.

AUTO TRANSFORMERS. 200W., 50V. input, 110/230V. output, 55/-, post 2/6. 115V. input, 230V. 500W. output, £5, carr. 5/-, 115/230V. 10 KVA, £25, carr. 25/-.

ELECTRADIX RADIOS

Dept. P., 214 QUEENSTOWN ROAD, BATTERSEA, S.W.8. MACaulay 2159

COLLINS H.F. STATION 1.5 Mcs. to 12 Mcs. 4-Channel with Power Supply Units for 12 volt D.C., 24 volt D.C., 115 volt A.C. and 230 volt A.C. supply.

WIRELESS SET 10—with all ancillary equipment including Rotary Plus Vibe-pack Power Unit, R.F. Amplifier, etc.

WIRELESS SET 31—Manpack Walkie-Talkie 40-48 Mcs.

WIRELESS SET 53—Canadian Walkie-Talkie 6-9 Mcs.

WIRELESS SET 28—Walkie-Talkie 4-Channel 50-42 Mcs.

R.C.A. TRANSMITTERS CRV52092—60-80 Mcs Power Supply 115 volts A.C.

R.C.A. RECEIVERS CRV4068-A—60 Mcs. Power Supply 115 volt A.C.

MARCONI RECEIVERS B28/CR100—60 Kcs. to 20 Mcs (Gap 420-500 Kcs) 230 volt A.C.

HALLICRAFTERS RECEIVERS S-27 and SX38. Morse Keys 2 - each. Magstrip Hunters, 3 inch. 4/6 each.

We have a large variety of the following. Please ask for lists. Switches, toggle and waver. Fuses, various types and values. Jack Plugs and Sockets. Capacitors, fixed and variable. Ball-races. Potentiometers. Transformers, Rectifiers, Vibrator, sync and non-sync. Uniselectors. Relays. Carbon brushes for generators and dynamos.

H.P. or Credit Facilities on all goods.

R. GILFILLAN & CO., LTD.

7, High Street, Worthing, Sussex.

Tel.: Worthing 8719 or 30181.

FOR THE BEST VALUE
in TAPE RECORDERS

... we recommend the



55 GNS.

or 55/- deposit and 8 monthly payments of 137/6. Delivery after first payment.

NO INTEREST TERMS !!

4 watts output—3 hours playing time—3 speeds. Completely automatic operation. All other makes of Tape Recorders in stock.

Write for details to:—

The E & G RADIO CENTRE Ltd.
 33 Tottenham Court Rd., London, W.1.
 Telephone: MUSeum 6667

LASKY'S RADIO



COLLARO 4-SPEED MIXER AUTO-CHANGERS

Incorporating auto and manual control. Complete with Studio crystal p.u. and sapphire stylus.

R.C. 456. List £13.17.0.

Lasky's Price **£7.19.6.**

Latest R.C. 457 (Continental), **£8.19.6.** Post on either of above. 3/6.

COLLARO 4-SPEED SINGLE PLAYERS


"Junior," Motor and separate crystal p.u. **92/6** Post Free.

Motor only, **59/6**, post 2/6.

Pick-up only, **29/6**, post 2/6.

4/564, 4-spd. Single Player Unit with Studio crystal p.u. **£6.19.6.** Carr. 5/6.

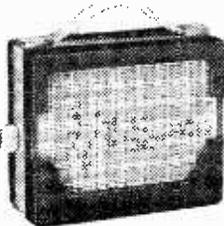LASKY'S FULLY TRANSISTORISED PORTABLE FOR HOME CONSTRUCTION



Entirely New! Note these Star features

- ★ Printed Circuit 6 1/2 in. x 2 1/2 in.
 - ★ 200 milliwatts p.p. output.
 - ★ Uses 7 Transistors and 1 germanium diode.
 - ★ Ferrite rod aerial.
 - ★ Fully tunable.
 - ★ Uses one 6 v. and one 1 1/2 v. battery. Very low consumption.
 - ★ Choice of 7 x 4 in. elliptical or 3 1/2 in. P.M. Speaker.
 - ★ Choice of cabinet.
- CAN BE BUILT FOR £9.19.6**
Circuit Diagram and building instructions. 1/6 post free. Carr. 3/6

BUILD THIS BATTERY PORTABLE

The printed circuit supplied makes construction easy and accurate and you can build this fine 4-valve, med. and long wave superhet portable in an hour or so. Performance equals ready-built sets costing pounds more!

FOR ONLY £7/7/-, plus 3/6 carr., you can build this Portable using all brand new components and valves, only batteries extra. Printed circuit, circuit diagram and full instructions supplied.

Circuit Diagram and building instructions 1/6 post free.

FOR ONLY

7 gns.

or as mains battery for only

9 Gns.



FOR ONLY £5/9/-, plus 3/6 carr., you can build this as a mains and battery Portable using our specially designed build-yourself Power Unit for 200-250 v. A.C.

LASKY'S (HARROW ROAD) LTD.

42, TOTTENHAM COURT ROAD, W.1. Telephone: MUSEUM 2605.
370, HARROW ROAD, PADDINGTON, W.9. LAD 4075 and CUN 1979.

Open all day SATURDAY. Half-day Thursday.

PLEASE ADDRESS ALL MAIL ORDERS TO HARROW ROAD.

FOUR-SIDED BLANK CHASSIS

Made in our own works from Commercial Quality half-hard Aluminium of 16 s.w.g. thickness (approx. 1/16") these chassis will carry components of considerable weight and normally require no corner strengthening.

THOUSANDS OF SIZES TO CHOOSE FROM!

We can now supply on the SAME DAY as your order is received the exact size to the nearest half-inch and in depths of 1", 1 1/2", 1 3/4", 2", 2 1/2", 2 3/4", 3", 3 1/2", 4" and 5".

—AT NO EXTRA CHARGE. Maximum length 17". To arrive at the cost of any chassis, you need only add twice the depth to the length and the width, multiply the two and refer to the table below.

Sq. Ins.	Price Post	Sq. Ins.	Price Post	Sq. Ins.	Price Post
18	3- 13	17 8	1- 16	336	13/- 19
48	4- "	20 8	9- "	368	14- "
60	5- "	240	10- "	400	15- "
112	6- "	272	11- "	432	16- "
144	7- "	304	12- "	464	17- "

Full particulars on request.

PANELS.—Cut to any size up to 3ft. x 3ft. at 4/6 per square foot. Postage should be added at the rate of 1/6 oz. for each 9 sq. ins.
H. L. SMITH & CO. LTD. (Metalwork Dept.)
287-289, EDGWARE ROAD, LONDON, W.2. PAD 5891

STEREO KITS FROM JASON



NEW DESIGNS FOR YOU TO BUILD

Be ready for stereo sound with a Jason Stereophonic Pre-amp. Two designs are offered. Model J.4-4 (8 valves) is for the more experienced constructor. It has sufficient gain to play off a tape head. This is the model as designed by Mr. H. Lewis York, and described in *Hi-Fi News*. Model J.2-2 (4 valves) is a somewhat simpler version of the original design, and less complicated to build. Both can be used for single-channel working.

MODEL J.4-4. Complete with drilled chassis, instructions, nuts, bolts, wire, etc., but without 8 valves **£16.10.0**

MODEL J.2-2. As above, but without 4 valves **£12.18.0**

J.2-2 can also be supplied built, **£18.18.0.**

JASON J.2-10 STEREO AMPLIFIER £37.10.0

FROM LEADING STOCKISTS, or in cases of difficulty:
THE JASON MOTOR & ELECTRONIC CO.

3-4(P) Gt. Chapel Street, Oxford Street, London, W.1
(Between Oxford Circus & Tottenham Ct. Rd. S.W. 1, Ltd.) Phone: GER. 0273; 4

TELEVISION TUBES

HIGH QUALITY TUBES FULLY GUARANTEED SIX MONTHS

3/16 MW 36-24	£8.10	CRM 121	} £9	CRM 171	} £12.10
4/14 CRM 141	£10.10	CRM 122		MW 43-64	
CRM 142		£12.10	MW 31-16	MW 43-69	
CRM 152			MW 31-74	4/15	

RECLAIMED 12"—£6; 14"—£5; 17"—£7.10
PRICES INCLUDE CARRIAGE AND INSURANCE


PRIME ELECTRICS (Dept. W/3)
36 QUEENSDALE ROAD, LONDON, W.11
(Near Shepherds Bush, Central Line) Telephone: PARK 1131
CALLERS: 10.30 to 3.0 (Except Wednesdays)

 <p>"Q Coils" Iron dust cores 4/- Amazing efficiency</p>	 <p>Potted 5/- Coils Superhet, T.R.F. modern technique</p>	<p>Coils for Colliaro Tape Officially recommended Transcriptor pre-amp. Bias oscillator 7/6</p>	<p>STATION SEPARATOR —A positive answer For either Home, Light or Third etc. 10/6</p>	<p>STOP! T.V. Patterning SIMPLE REMEDY 10/-</p>
<p>SCRATCH FILTER COIL 10/6 Whistle Filter 10/-</p>	<p>DUAL RANGE COILS T.R.F. S'HET) 7/6 ea.</p>	<p>OSMOR Mini-Magic F.M. Tuner Kit Complete £1-10-0</p>	<p>B.B.C. 1 VALVER Components 27/6 (Valve 10 - ex.) including diagrams</p>	<p>Also B.B.C. (T.V.) Filter Choke 7/6</p>
<p>FERRITE ROD AERIALS MW 8/9 M-L 12/9</p> 	<p>I.T.A. Converter To Hi-Fi T.V. FOR ALL SETS KIT Complete 65/- Very efficient! £4</p>	<p>Dial 24/6 complete ASSEMBLY</p> 	<p>The World on a 1 Valve Short Wave Coil & Circuit 6/-</p>	<p>Experimental & Development Dept.</p>
<p>Special Coils for HAMS DESIGNERS MANUFACTURERS</p>	<p>OSMOR Satellite Switch-tuned F.M. Dimensions 4 1/2" x 4 1/2" A completely stable drift-free unit for adding to existing radio or Hi-Fi amplifier. Circuit & wiring diagram on request.</p>			<p>F.M. COILS For Osmor C'ts & Many Designs</p>

Thank "Q" FREE! Send 1/- (stamps) for fully descriptive literature AND OSMOR DESIGNS—5-Valve S'Het, Miniature dirco, Battery and Battery/Main Receiver, Mains T.R.F. S'Het and T.R.F. Freders, Band 3 Converters, F.M. Tuners, Wiring Diagrams, Chassis Templates, Coil and Coilpack information and price lists and information on circuits in "Wireless World," "Practical Wireless," "Radio Constructor," Full Circuits included. See also classified Adverts. on page 324.

OSMOR (Dept. P.W. 23) **418 BRIGHTON ROAD SOUTH CROYDON, SURREY CROYDON 5148/9**

CRYSTAL CALIBRATOR

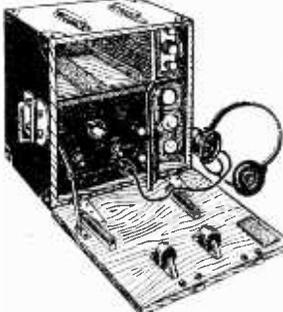

Just the job for the ham or short wave enthusiast. Check points every 10, 100, and 1,000 kc/s. Contains 1,000 kc/s crystal, 6 valves in multi-vibrator circuit, accuracy plus or minus 0.025%. Brand new. Size 12 in. x 8 in. x 7 in. Complete in transit case with all accessories including phones and spare valves. **£3.19.6.** plus 5/- carr.

FIELD'S RADIO, 85, SNOW HILL, Birmingham, 4.
Please print your name and address. Phone: Cent. 3136.

"D I Y"

Yes! You can **DO IT YOURSELF** with the aid of our **RADIO HOME CONSTRUCTOR'S HANDBOOK**. Over 100,000 enthusiasts already have earlier issues of this famous publication which gives full parts lists, circuits, etc., of many receivers, tape recorder, oscilloscope, feeder unit, communications set, hi-fi amplifiers, power pack, crystal set, etc. (incl. "P.W." Coronets). It is also packed with data, construction, soldering and servicing hints, facts, formulae, colour code, etc. Our latest "Easy-as-A-B-C" FULL SIZED P-P Construction sheets are available FREE with orders so that even the beginner gets professional results first time! This claim is confirmed by many hundreds of genuine testimonials received. Send 3/- to-day for your copy. (Worth much more!)

NOWHERE IS THERE A BOOK SO VALUABLE TO THE NOVICE CONSTRUCTOR AND EXPERT!

RODING LABORATORIES
Hurn Airport, Christchurch, Hants

TRANSISTORS ARE OUR SPECIALITY
ALL PRICES ARE POST PAID

Red Spot, 7.6. Red Yellow, 21 - White Spot, 13.6. Green Yellow, 10 - Also, Mullard & Mazda Types, Crystal Diodes, 1.3.
The New "Mini-Seven" Circuit, 1.6.
"Transeven" Portable Circuit, 1.5.
KIT now ONLY £10.12.6.

ELECTROLYTICS—GUARANTEED
15 - 18 mfd. 450 v., 150 mA. 2 1/2" x 1. 4.3
16 mfd. 450 v. 150 mA. 1 7/8" x 1. 2.4 each.
8-8 mfd. 450 v. 100 mA. 1 1/2" x 1. 2.9.
8-16 mfd. 450 v. 100 mA. 1 1/2" x 1. 2.9.
50 mfd. 50 v. 1.6. 25 mfd. 25 v. 1.3.
Resistor: All Values 10, 5 watt, 6d. ea.

TERMS: C.W.O. or C.O.D. (over 25).
FULL COMPONENT LIST, 6/-.

OAKFIELD RADIO
44 OAKFIELD ROAD, STOCKPORT

AC/DC MULTIMETER 45/-

March Offer repeated. 50 only left. Build this fine Multimeter. Ranges: 3, 15, 60, 150, 600 v. D.C.; 15, 60, 150, 600 v. A.C.; 6, 60, 600 mA D.C. Ohms to 2M. 1,800 ohms per scale 0-15 and 0-600. Three range 1%. Shunt. G.E.C. meter rectifier. Two 1 1/2" wire wound, five 1 1/2" High Stab. Carbon. Two 10% Resistors. WW pot. Two switches. Circuit and instruction books. Definitely no adjustments to make, all shunts, etc., ready made, just wire up. 45/- post free.

G.E.C. (Salford) Bridge-Type Instrument Rectifiers, 1 mA or 500 μ A type, 6.6, post 6d.
Watt Meter Moving Coil 21 m-ter, 0-3 watts linear scale, 3 ohms impedance, for audio power measurements at secondary of O.P. trans. 15/- post 1/6.
Shunt for 1 mA 100 ohm Meter.—Range 0-100, 1,000 mA. 1% accuracy. 8.6, post 6d.

Lists available. S.A.E. with enquiries please.

PLANET INSTRUMENT CO.
25, DOMINION AVE., LEEDS 7.

The Radio Amateurs Handbook, A.R.R.L. 1958. 32.6 postage 1/9.

Belmar Valve and Tele. Tube Manual No. 7.6 - postage 9d.

High Fidelity Loudspeaker Enclosures by Babani. 5 - postage 6d.

World Radio Handbook 1958 by Lund Johansen. 13.6. postage 9d.

Elementary Telecommunications Practitioner by J. R. C. Smith. 12.6. postage 1/-.

Foundation of Wireless by Scroggie. New Edition. 15/- postage 1/-.

Radio Upkeep and Repairs by Witts. New Edition. 15/- postage 9d.

We also have a full range of Slide Rules and Drawing Instrument Sets. Send for list.

UNIVERSAL BOOK CO.
12 Little Newport Street, London, W.C.2
(adjoining 115c Street)

Train for a wonderful future in ELECTRONICS...

Every day the demand for the expert in electronics grows. Radio, television, radar and the whole field of computers and automation are rapidly expanding and the trained specialist assures for himself a well-paid career in this quickly developing profession. Here is your opportunity to enter for:—

3 YEAR COURSE TELECOMMUNICATIONS—Entrance standard G.C.E. Ordinary level or equivalent. This course trains students to become Assistant Development Engineers. It covers the City and Guilds' Full Technological Certificate in Telecommunications Engineering. It also includes theoretical and practical instruction on Computers (Digital and Analogue), Process Control and Automation. Next course commences September 9th, 1958.

1 YEAR COURSE Full-time day course in the Principles and Practice of Radio and Television. Designed for the training of Radio and Television Servicing Engineers and others similarly engaged in the Electronics industry. Next course commences September 9th, 1958; others in January and May, 1959.

The E.M.I. College of Electronics, Dept. 32, 10 Pembroke Square, London, W.2. Telephone: Bayswater 5131 2
The College is part of E.M.I. Group... Britain's foremost electronic engineers... Pioneers of the world's first public Television Service.

THE E.M.I. COLLEGE OF ELECTRONICS



1A67

The "TYANA" Standard Soldering Iron



- Adjustable Bit.
- Weight approx. 4 oz.
- Heating Time 3 min.
- 40 Watt economy Consumption.
- Standard Voltage Ranges.

Replacement Elements and Bits
always available.

"DIPLOMA" HEADPHONES



Lightweight
High Resistance (4,000
ohms). Complete
with cord. 17/6

Ideal for CRYSTAL SETS and also for
use with TAPE RECORDERS.

KENROY LIMITED

152/297 UPPER ST., ISLINGTON,
LONDON, N.1.

Telephone: Canonbury 4905-4663

WIRING ACCESSORIES

Return of Post Service. Lowest possible
prices consistent with high quality. Money
back guarantee.

PVC Cable Flat Twin Twin with E. 3 Core

1.044	£2. 9. 2	£3. 1. 9	£3.10. 5
1.029	£3. 5. 7	£3.17.11	£4.18. 5
4.036	£4. 9. 6	£5. 2.11	£6.11. 4
7.029	£5.12. 6	£7. 0. 7	£8. 4. 7

TRS CABLE

1.044	£2.10. 0	£3. 1.10	£3.10. 3
1.029	£3. 3.11	£3.16. 4	£4.19. 4
3.033	£4. 3. 5	£5. 1. 7	£6. 5. 6
7.029	£5.10. 5	£6.16.11	£7.18.10

Prices per 100 yds. All sizes stocked. Supplied in 25, 50, 75 or 100 yd. lengths. 7.029 and above cut to length—no cutting charge. Carriage paid on all orders over £2. Full range of accessories available. Send for complete lists.

F. HUNT & CO.
STEPCOTE HILL, EXETER
Phone: Exeter 56687

ASTRAL RADIO PRODUCTS

"HOME RADIO." 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d.
TRF COILS. 7/- pr., post 6d. DUAL WAVE HF Coil with REACTION. Specified for "Summer All Dry Portable."
"A.C. Double Triode 1," etc., 4/6, post 3d.
H.F.S. Miniature 1" x 1 1/2" x 2 1/2" in cans. Extra high "C." Special offer, 9/- pr., post 6d.
COIL PACKS. L.M.S. 3/6, post 1/-.
Crystal Set Coils. L. & M.W. 2/6, post 3u.
82 Centurion Road, Brighton

Build your own POCKET RADIO

A.L. PARTS NECESSARY TO BUILD YOURSELF A COMPLETE 5-TRANSISTOR POCKET RADIO (Size less than 5 1/2" x 3 1/2" x 1 1/2") CAN BE SUPPLIED FOR AS LITTLE AS £9.18.2. (MEDIUM WAVE) or £10.6.8. (LONG AND MEDIUM WAVES). Send now for free price list and/or 3/- for instruction booklet.

Components available include:
Miniature 3 ohms. Loudspeaker 27/6.
Jackson O.O. Twin Gang with intersection screen ... 10/6.
Oscillator and I.F. Coils ... 8/-.
Output transformers matching single OC72 to 3 ohms ... 10/-.
Battery packs to give 9 volts from 1 1/2 volt s im-pen-light cells 5/-.
(Also available to give 3, 6 or 12 volts.)

Resistors ... from 4d.
Capacitors ... from 6d.

Special Offer—Transistor Radio Batteries (1.5 v.) Size 1 1/2" x 1 3/16". 3d. each.

Mail Orders Only.

S. E. C. Ltd.

9-11 Menmouth St., London, W.C.2.

1-Finger Pianists

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

**C & S, 10 Duke St., Darlington,
Co. Durham**

Morse Code operating ... as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.

Send 3d. stamp for Payment Plans and full details of all Courses.

CANDLER SYSTEM CO. Dept. 510
52b, Abingdon Road, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

VALVES—Guaranteed

EA50	2-SP61	6-1D5	8/6	8/6
EB41	7.6-TT11	3.6-1L5N5	5-8U5	7/6
EB91	6-VR18	5-4D1	4-8U5(UX)	
ECC33	8.6-VR21	4-8AK5	7-6	8/6
EP36	4.6-VR65	3.6-8A1.5	6-6U7	5-
EP37	7.6-VR65A	3.6-8B6	7-7D3	8-
EP39	5-6VR01	4-8B36	7-7D3	7/6
EP50	5-VR137	4-8B6	5-8D2	4/6
EP80	8.6-VT20	3.6-6BW6	6-6R22	5-
EL42	5-VT50	3.6-6CSM	6-8D6	5-
024	5-VT51	4-8D2	6-12BAG	7/6
PAJ	4-VT111	2-6B35	6-12B26	6-
PEN45	5-WT7	5-6J6	6-12K7	8/6
PY31	11.6-XP1.5	3.6-6KTG	4-615D2	6-
SP41	9-XSG1.5	6-6KTG	5-618	7/6
SP41	10-	4-6SA7	8-20D1	12-
SP41	4-Z132	6-6GSN7GT	20P4	15-

Postage 6d. per valve, orders over £1 post free. (Also all components) TV Tubes, Perfect Condition (callers only) MW22 16. MW 22 18. £4.0.0 each. Also all Transistor Components.

TELEKIT SUPPLY

104 High Street, Beckenham, Kent. Phone: BEC 3720

Fidelia HAND BUILT

Fidelia Range includes: AM/FM chassis models from our new 8 valve at £25 to our 12 valve at £44.

V.H.F. Tuner Units, £12 to £20.

High Fidelity amplifiers, £18 to £30. Full details willingly on request. (6d. for postage is appreciated.)

ELECTRO ACOUSTIC DEVELOPMENTS
2, Amhurst Road, Telscombe Cliffs, Sussex

RES/CAP. BRIDGE 35/-

Checks all types of resistors and condensers.

Easy to Build Up. Easy to Use. READY CALIBRATED

Stamp for details of this and other kits. RADIO MAIL (Dept. PA)
Raleigh Mews, Raleigh Street, Nottingham

TRANSISTOR SUPPLIES

TRANSISTORS, I.F.: 7.6; R.F.: 13.6 and 18-; Mullard OC71, 24; OC72, 30; Matched pairs OC72, £3. Diodes, 1.6; Mullard, 5-; Brimar, 7.6. MORCO TRANSISTOR and Diode Kit for transistor and diode circuits, 3-; TRANSISTOR TRANSFORMERS, interstage, 8.6; Driver Push-Pull, 8.6; Push-Pull output, 8.6. ELECTROLYTICS for transistor circuits, 8 uF, 2-; 15 uF, 2-; 30 uF, 1.6. FERRITE ROD ASSEMBLY, Long, medium wave and coupling coil for MORCO CIRCUIT, 13.6. LOUD-SPEAKER, sensitive P.M. 5in., 18.6; output transformer for same, 5-. HEADPHONES, L.R., 8.6; H.R., (4,000 ohm-), 17.6. TRANSFORMERS, MULLARD CIRCUIT, 20-; Bargain Lines—Balanced inserts as miniature speakers, 5-; Trimmers 100, 270, 750H, 1.9; Var Condenser, air, 0003 3-; Bins, speakers with output trans, 16.6; Sub-Miniature Transistor Transformers, 8.6; Super Coax, semi-air, 1-; ordinary coax 6d. yd.; Crystal Inserts, 4.6; Two High Resistance Earpieces, Band and Flex to assemble own H.R. Phones, 8-; Limited Stocks, Morse Keys, 2.6.

Terms: C.W.O. postage extra. Excess refunded. Send 9d. stamps for transistor circuits and list.
MORCO EXPERIMENTAL SUPPLIES
(Props.: Moores (Sheffield), Ltd.)
8 & 10, GRANVILLE ST., SHEFFIELD, 2
Tel.: 27461.

Constructors! Build the

"PIXIE-PAK"

Pocket-sized Loudspeaker Set

This receiver is designed for cheapness, ease of construction, and guaranteed reception. Using transistors and the minimum of components and the minimum of components, it is powered by small torch cells, and contained in a pocket-sized plastic case.

Covering long and medium wavebands it provides loudspeaker reception in most districts without an aerial or ear. In poor reception areas a short indoor aerial is sufficient.

Send stamped, addressed envelope for free illustrated folder, component layout, full description, and price list.

This offer applies only to Great Britain and Northern Ireland.

CENTRAL RADIO SALES

CENTRAL CHAMBERS, SMALL ST. BRISTOL, 1

SPARKS' DATA SHEETS

THE "SEAFARER"

Battery Two-valve offering New Interests and Thrills on Trawler, Ship-to-Shore, Aeronautical and 80-180 m. Amateur Bands Plus normal Med. and Long waves. A great little Set. Data Sheet, etc. etc. 3.3. All Components and Chassis available.

L. ORMOND SPARKS (P), VALLEY ROAD, CORFE CASTLE, DORSET

COVENTRY RADIO

Component Specialists since 1925

We have now trebled the size of our premises in order to supply a larger range of Components, Amplifiers and Hi-Fi Equipment.

Send your enquiries to:

189-191 Dunstable Road, Luton, Beds.

New Telephone No.: LUTON 7388-9

FM and Hi-Fi Components

DENCO F.M. TUNER circuits	1s. 6d.
RADIO CONST'R. F.M.	2s. 0d.
MULLARD AMPLIFIERS	3s. 6d.
G.E.C. 912 PLUS AMPLIFIER	4s. 0d.
G.E.C. F.M. PLUS TUNER	2s. 6d.

Separate price lists available on request to J. T. FILMER 82, DARTFORD RD, DARTFORD, KENT. Tel. Dartford 4057.

All material offered below guaranteed new and perfect. Money refunded if dissatisfied.

METERS, a.supp. D.C. M.I. 2 1/2m. P.I. Red., 11.6. 7.4 amp. D.C. M.I. 1 1/2m. P.I. Red., 12.6. 1 m.A. M.C. 2 1/2m. P.I. Red., 22.6. 200 m.A. M.C. 2 1/2m. P.I. Red., 9.6. 25 v. D.C. M.I. 2 1/2m. P.I. Red., 7.6. 200 v. A.C. M.C. 2 1/2m. P.I. Red., 22.6. 250 v. A.C. m.c. 2 1/2m. P.I. Red., 25 v. each. P. & P. 1.0 each. 1.5 each.

VEEDER REVOLUTION COUNTER, 6-ohms, induct. red. motor drive, full inside small unit. New, 8.6 each. P. & P. 2.7.

U.S.A. RELAYS, 27 volt miniature, 4 pole change over, 5.6 each. P. & P. 2.4.

MURHEAD, PRECISION ROTARY STD SWITCHES, 2 banks, each bank 24 position, heavy duty contacts, 12.6 each. P. & P. 1.6.

HIGHEST QUALITY DIAMOND REPLACEMENT STYLUS with 6 months guarantee. Please specify type of your record player. £3.0.0 each, including P. & P. and postage.

SLIDER RESISTANCE HEAVY DUTY, 70 ohms, 2 barrels with gear drive 2 1/2 amp. Price 22.6. P. & P. 3.0.

PHOTO MULTIPLIER, Type 501A, for Alfa counter, 10m. scanning, spectroscopy, etc., £2.5- each. P. & P. 1.0.

TELEPHONE HANDSETS, sound power, our will work by simple connection without batteries, 22.6 each. P. & P. 1.2.

TELEPHONE HANDSETS, 1.8 A. Similar to P.O., with switch, carbon insert, 12.6 each. P. & P. 1.6.

ARMOUR RECORDING WIRE, U.S.A. Top quality on original reels, length 47m yards, 17.6. P. & P. 1.6.

HEADPHONES, Audio ohms, impedance, 15 v. B.R. M.C. No. 1, Brown, 12.6. H.S. 100 I.R. 1.8 A., min. ear pads, 15-. P. & P. on above 1.6 each.

MICROPHONES, Throat, British, magnetic, 4.6. Throat, carbon, 1.8 A., 3.6. No. 8 carbon with switch, 7.6. Type 18, ex. o.v. mask, 3.6. P. & P. on above 1.2 each.

AUTO. TRANSFORMER, step up, step down, 110 v.-200-220-240 v. Fully shrouded, 60 watt type, £2.2- each. P. & P. 1.6. 200 watt type, £3.3- each. P. & P. 1.6. 1,000 watt type, £4.4- each. P. & P. 1.6.

200 250 v. A.C. MOTORS, New 1.80 hp, 2.4 Jives, direct 6,000 r.p.m., induction 300 r.p.m., 22.6 each. P. & P. 2.6.

MORSE PRACTICE SET, Wooden base, tap, adjustable, buzzer, battery clips and terminals, 8.6 each. P. & P. 2.

MORSE KEYS, Sanyo Service patt., 2.6 each. P. & P. 1.0.

NEON LIGHT, 250 v. A.C. M.B. Clear, 1.9 each. P. & P. 1.0.

NEON PANEL MOUNTING INDICATOR LIGHTS, with 4-pin leads, chrome bezel, 200 250 v. Red, clear and green, 3.0 each. P. & P. 6d.

ULTRA VIOLET BULB, A.C. 10 v., 12 v., 36 watt, 5.6 each. P. & P. 1.6.

RADIAL STUD SWITCH, 90 segs, 20 sp. Complete with handle and housing, 5- each. P. & P. 2.0.

CONTACTOR TIME SWITCH, two impulses per second, in sound proof box, 11.6 each. P. & P. 1.0.

MURHEAD Veeder Drive, sealed motor, deg. ratio 41:1, die sing, as fitted to RF 251 sets, complete with lampholder. In manufacturer's original packing, 8.6 each. P. & P. 1.6.

INFRA-RED TELESCOPE, complete with 4 section zooming tube, image converter tube and full optical system. Brand new, complete with 100x carrying case, 17.6 each. P. & P. 6.

HIGH-SPEED RELAY, Siemens, 2 bobbins, 1,000 ohms each, 10.6 each. P. & P. 1.0.

WHEATSTONE BRIDGE UNIT, 4-terminal switches, 60-0-60 ohm, 1.5 ohm, 1.5 ohm, 1.5 ohm, 1.5 ohm, 2.5 m.A. In oak carrying case 16 x 7 1/2 x 4 in., 40- each. P. & P. 3.6.

MINIATURE 24 v. D.C. REVERSIBLE RECORDER MOTORS, 3000 rev. motor and right angle gear drive, 300 x 100 x 40m, 12.6 each. P. & P. 2.0.

REVERSED AND VIGNOLES Condit Testing Units Meter, pattern 'S', complete testing tools, instruction book, etc., two ranges 5 and 30 ohms, £4 17/6 ea. P. & P. 2.0.

SCOTCH ROY 1,200 ft. plastic tape on plastic spool, 25- P. & P. 1.0.

SIEMENS CONTACT COOLED RECTIFIERS, H.W. 125 v., 80 m.A., 4.3. 250 v., 50 m.A., 7- 250 v., 55 m.A., 8.6. Bridge 250 v., 75 m.A., 11-. 250 v., 60 m.A., 17.6. P. & P. 1.0.

TOGGLE SWITCHES on off 8 P., 1.9; change-over, 2.6; D.P.D.P., 3.9. P. & P. 1.0.

COLLARO Crystal Microphones, 37.6. P. & P. 1.0.

SERVICE TRADING CO.

Personal callers: 9 LITTLE NEWPORT STREET, LONDON, W.C.2.

All mail orders: Dept. P., 47 HIGH STREET, KINGSTON-ON-THAMES.

EXCLUSIVE OFFER OF THE R. 107

THE ARMY'S FINEST COMMUNICATIONS RECEIVER

Just purchased from the Ministry of Supply, this magnificent 9 valve 3 Wave-band receiver gives World Wide Reception over a coverage of 1.2-17.0 Mc/s (18-25 metres), taking in several important Amateur Bands, Shipping Band, and part of the Medium Wave Band, including the B.B.C. Light Programme, sensitivity is 1 micro-volt on CW, and 2-6 micro-volts on RT. The controls include a Bandwidth Switch ("Wide" or "Narrow"), choice of A.V.C. and B.F.O., Audio Filter, R.F. Gain, Aerial Trimmer. Has built-in Output Stage with Internal Speaker, which can be switched out to use Headphones. Uses normal international Octal Valves. Incorporates A.C. Mains Power Unit for 100-250 volts, and Vibrator Pack for 12 volts D.C. in Grey Metal Case size 24" x 13" x 17". These sets are used, but in very good condition, thoroughly checked and aerial tested before despatch.

COMPLETE, READY TO SWITCH ON

£8-19-6

(Carriage 20) England and Wales, rest of U.K. extra
S.A.F. for Illustrated Leaflet.

COLLINS T.C. TRANSMITTERS. Special offer of these famous American Transmitters. Frequency Range 1.5-12.0 Mc/s in 3 bands. Employs 7 valves, 2 of 1625 in P.A. Stage, 1625 buffer and 7925 modulator stage, 3 of 12A6 in Oscillator stage. Radio Telephone or Radio Telegraph. Provision for VFO or Crystal Control 4 Crystal positions. Has Plate and Aerial Current meters. IN BRAND NEW CONDITION. ONLY 412.10.0 (carriage, etc., 15-).

COMMUNICATIONS RECEIVER R.1155.—The famous Bomber Command Set Covers 18.5-7.5 Mc/s, 7.5-3.0 Mc/s, 1,500-600 Kc/s, 500-200 Kc/s, 200-75 Kc/s. Late Model "B" fitted with Super Slow Motion Tuning. Slightly used, but in First-class Condition, aerial tested before despatch. 14-page booklet supplied giving circuits and notes, etc. (or available separately 1/3). ONLY 27 19 6 (carriage 10 6).

A.C. MAINS POWER PACK & OUTPUT STAGE.—In black metal case. Enables receiver to be operated immediately by just plugging in. WITH built-in speaker. £5 5-. LESS speaker. £4 10- (carriage 5-).

6 V. VIBRATOR PACKS. Output approx. 130 v. at 30 mA. Fully filtered and smoothed. Complete. ONLY 12 6.

R1155 SUPER SLOW-MOTION TUNING ASSEMBLY. As used on all late model 1155s. Easily fitted to "A" sets, etc. ONLY 12 6.

EHT TRANSFORMERS. 5.5 kV. (Rect.) with 2 v. 1 a., 79 6. 7 kV. (Rect.) with 2 v. 1 a., 89 6. 2.5 kV. (Rect.) with 2-0-2 v. 1.1 a., 2-0-2 v. 2 a. (for VCR97 tube, etc.), 42 6 (postage 2- per trans.).

POCKET VOLTMETERS.—Read 0-15 volts and 0-300 volts A.C. or D.C. BRAND NEW AND UNUSED. ONLY 18 6.

CRYSTALS. British Standards 2-pin 500 kc/s, 15-. Miniature 200 kc/s and 465 Kc/s, 10- each.

ROLA 6 pin. P.M. SPEAKER. Mounted in grey crackled metal cabinet 9 in. x 9 in. x 1 in., with volume-control. Ideal for use with receiver, or as extension. BRAND NEW. ONLY 27 6. (Post 2 6).

MAINS ISOLATING TRANSFORMER. Manufactured by Vortexion. Fully shrouded. Will provide true 1:1 ratio from nominal 230 v. Primary. Rated at 100 watts. BRAND NEW. ONLY 22 6. (Post 2 6).

HARRIS ELECTRONICS

(LONDON) LTD.

138 Gray's Inn Road, London, W.C.1.


(Phone TERMINUS 7937)

Please include carriage costs on ALL items.

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross)

The VIKING tape recorder

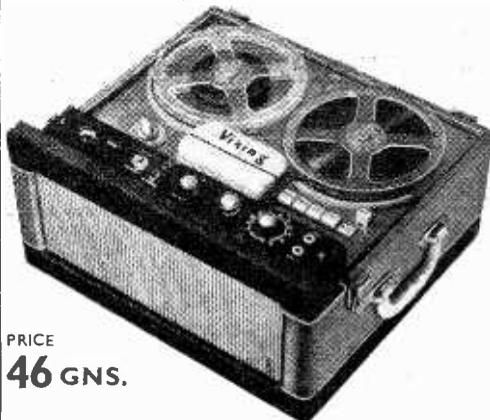Uses the MOTEK K9 deck. 3-speeds, "Pause," counter. Hatfield oscillator. Switch for Amplifier. 2 inputs. Vol. control scale. Unique method of super-imposing recording. Accessibility for service. C.C.I.R. linked equalisation. Detachable lid.



PRICE

46 GNS.

Send now for leaflet to:—

HATFIELD RADIO

78, STROUD GREEN ROAD, LONDON, N.4

Tape specialists since 1952.

REPANCO HIGH GAIN COILS

Dual Range Crystal Set Coil. Type DRX1	...	2/6
Dual Range Coil with Reaction. Type DRR2	...	4/-
Matched Pair Dual Range T.R.F. Coils. Type DRM3 pair	...	8/-
Pair Dual Range Superhet Coils. Type SH4 pair	...	8/-
Miniature Iron Dust Cored Coils. Type "R" — Range		
800-2,000m.	RA1 RHF1 RO1	
190- 550m.	RA2 RHF2 RO2	
70- 230m.	RA3 RHF3 RO3	each 3/3
15- 50m.	RA4 RHF4 RO4	
Ferrite Rod Aerial. Dual Range Type FR1	...	12/6
Miniature I.F. Transformers. Type MSE (465 Kc/s) pair		12/6
Standard I.F. Transformers. Type TCG (465 Kc/s) pair		13/6

EASY-TO-BUILD TRANSISTOR RECEIVERS

Repanco "Three Dec."—A new dual range radio with band pass tuning using a crystal diode and 3 transistors. Easy wiring plans and instructions. 1/- post free.

Repanco "Transven."—Latest portable superhet 7 transistor receiver with preset tuning for 4 stations. Easy wiring plans and instructions. 1/9 (post free).

Repanco "Mini-7." The amazing new Pocket Transistor Radio. Size only 5 1/2 in. x 3 1/2 in. x 1 1/2 in. A seven transistor Superhet circuit fully tunable over medium wave. Uses 3 White Spot and 4 Red Spot transistors. Attractively housed in a plastic case. Comprehensive plans and component price list 1/9 (post free).

RADIO EXPERIMENTAL PRODUCTS LTD.

33 MUCH PARK ST., COVENTRY

Tel. 62572.

Practical Wireless

BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

- 2/- each
- 1937 Crystal Receiver ... PW71*
- The "Junior" Crystal Set ... PW94*
- 2/6 each
- Dual - Wave "Crystal Diode" ... PW95*

STRAIGHT SETS

Battery Operated

- One-valve : 2/6 each
- The "Pyramid" One-valver (HF Pen) ... PW93*
- The Modern One-valver ... PW96*
- Two-valve : 2/6 each
- The Signet Two (D & LF) ... PW76*
- 3/6 each
- Modern Two-valver (two band receiver) ... PW98*
- Three-valve : 2/6 each
- Summit Three (HF, Pen, D, Pen) ... PW37*
- The "Rapide" Straight 3 (D, 2 LF (RC & Trans)) ... PW82*
- F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ... PW87*
- 3/6 each
- The All-dry Three ... PW97*

- Four-valve : 2/6 each
- Fury Four Super (SG, SG, D, Pen) ... PW34C*

Mains Operated

- Two-valve : 2/6 each
- Selectone A.C. Radiogram Two (D, Pow) ... PW19*
- Three-valve : 4/- each
- A.C. Band-Pass 3 ... PW99*
- Four-valve : 2/6 each
- A.C. Fury Four (SG, SG, D, Pen) ... PW20*
- A.C. Hall-Mark (HF, Pgn, D, Push Pull) ... PW45*

SUPERHETS

- Battery Sets : 2/6 each
- F. J. Camm's 2-valve Superhet ... PW52*
- Mains Operated : 4/- each
- "Coronet" A.C.4 ... PW100*
- AC/DC "Coronet" Four PW101*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : 2/6 each
- Simple S.W. One-valver ... PW88*
- Two-valve : 2/6 each
- Midget Short-wave Two (D, Pen) ... PW38A*
- Three-valve : 2/6 each
- Experimenter's Short-wave Three (SG, D, Pow) ... PW30A*
- The Prefect 3 (D, 2 LF (RC and Trans)) ... PW63*
- The Band-spread S.W. Three (HF, Pen, D (Pen), Pen) ... PW68*

MISCELLANEOUS

- 2/6 each
- S.W. Converter-Adapter (1 valve) ... PW48A*
- The P.W. 3-speed Autogram ... (2 sheets), 8/-*
- The P.W. Monophonic Electronic Organ (2 sheets), 8/-

TELEVISION

- The "Argus" (6in. C.R. Tube), 3/-*
- The "Simplex" ... 3/6*
- The P.T. Band III Converter 1/6*

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94, are pre-war designs kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

- One-valve : 2/6
- B.B.C. Special One-valver ... AW387*

Mains Operated

- Two-valve : 2/6 each
- Consoelectric Two (D, Pen), A.C. ... AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : 2/6 each
- S.W. One-valver for American ... AW429*

- Two-valve : 2/6 each
- Ultra-short Battery Two (SG, det Pen) ... WM402*

- Four-valve : 3/6 each
- A.W. Short Wave World-beater (HF, Pen, D, RC, Trans) ... AW436*

- Standard Four-valver Short-waver (SG, D, LF, P) ... WM383*

Mains Operated

- Four-valve : 3/6
- Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ... WM391*

MISCELLANEOUS

- Enthusiast's Power Amplifier (10 Watts) (3/6) WM387*
- Listener's 5-watt A.C. Amplifier (3/6) ... WM392*
- De Luxe Concert A.C. Electrogram (2/6) ... WM403*

QUERY COUPON

This coupon is available until June 6th, 1958, and must accompany all Queries sent in accord with the notice on our "Open to Discussion" page. PRACTICAL WIRELESS, JUNE 1958

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEAIGHT & SONS, Rymer Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (A/S) LTD, South Africa and Rhodesia: CENTRAL NEWS AGENCY, LTD. Subscription rate including postage for one year: Inland 15s., Abroad 17s. 6d. (Canada 18s.). Registered at the General Post Office for the Canadian Magazine Post.

SPUTNIK-SPECIAL

SHORT-WAVE RECEIVER 10-60 MC/S (5-30 Metres) RECEPTION SET TYPE 208




Complete with 6 valves, 2-6K8G, 2-EF39, 6Q7G and 6V6G. Internal mains power pack and 6 v. vibrator pack. Built-in 6in. speaker. B.F.O. and R.F. stage. I.F. freq. 2 Mc/s. Provision for phones and muting and 600 ohms. Combined input 100/250 v. A.C. and 6 v. D.C. All sets in new condition and air tested. £6.19.6. Carr. 15/6.

BE PREPARED TO LISTEN TO THE SATELLITES.

"EAVESDROPPER" THREE TRANSISTOR POCKET RADIO

(No Aerial or Earth required)
Variable tuning on medium waves. Total cost as specified, including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit and plastic case. All items sold separately. Full practical layout diagrams. 70/- post free. With balanced armature earpiece, 73/6. With Min. Hearing Aid, 86/-.

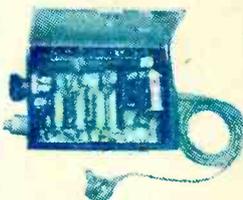**"HOMELIGHT" TWO TRANSISTOR PERSONAL PORTABLE**

Variable tuning. We can supply all components, including two Transistors, Diode, Resistors, Condensers and Miniature Hearing Aid and plastic case, size 4½ x 2½ x 1½ in., and 3 v. battery for 50/-. Practical layout.

All items sold separately.

"TRANSISTOR-8"

Push-Pull Portable Superhet. CAN BE BUILT FOR £11.10.
This Portable 8 Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set.

TEN STAR FEATURES



- ★ 8 Specially selected Transistors.
- ★ 250 Milliwatts Output Push Pull.
- ★ Medium and Long Waves.
- ★ Internal Ferrite Rod Aerial.
- ★ Elliptical Speaker.
- ★ Drilled Chassis 8½ x 2½ in.
- ★ Point-to-Point Wiring and Practical Layout.
- ★ Economical. Powered by 7½ v. battery.
- ★ Highly sensitive.
- ★ Attractive lightweight contemporary case.

COMBINED PORTABLE CAR RADIO

Two sets for the price of one.

We can supply all these items including Cabinet for £11.10.0. P.P. 2/6. All parts sold separately. Circuit diagram and shopping list free.

Car Radio Conversion Components. 8/- extra.

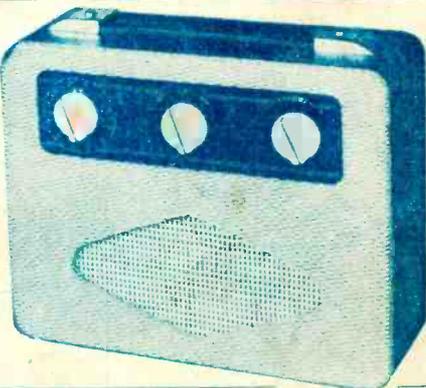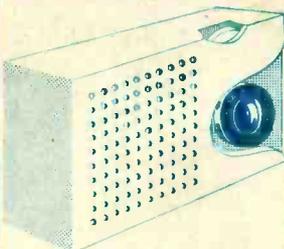**MINI-7 POCKET TRANSISTOR PORTABLE**

Size 5½ x 2½ x 2½

- ★ Seven selected Transistors.
- ★ Push-Pull Output
- ★ Internal Ferrite aerial.
- ★ Drilled chassis.
- ★ Practical layout
- ★ Medium Wave
- ★ Long Wave 10.6 extra.
- ★ Attractive plastic case.

Send 1/6 for Instruction Booklet and Prices.

ULTRA SENSITIVE!
ECONOMICAL!
HIGHLY SELECTIVE!

MAY BE BUILT FOR £9.19.6

This Superhet is superior in performance to most commercial Transistor sets and costs less than half the price.

All components as specified can be supplied at an inclusive price of £9.19.6. P.P. 2/6.

Send 1/6 for Instruction Booklet and Prices.

HENRY'S (RADIO) LTD.

5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2.

Opposite Edgware Road Station
OPEN MONDAY to SAT. 9-6.


PADDINGTON 1008/9
THURS. 1 o'clock

TRANSISTORS

JUNCTION TYPE P-N-P. (British Manufacture.)
Red-Spot, 800 kc/s Audio Frequency ... 7/6
White Spot, 2.5 Mc/s R.F. and I.F. Amp. ... 15/-
Red-Yellow, 1.5 to 8 Mc/s R.F. and I.F. Amp. ... 21/-

MINI-TWO TRANSISTOR MINIATURE POCKET RADIO

The smallest Transistor set offered on the market. Variable tuning. Drilled chassis, plastic case 3 x 2 x ¾ in., Miniature Hearing Aid, 2 Transistors and all components including 1½ volt battery, circuits and full practical layout diagrams. All components sold separately. Total cost 47/6 complete.

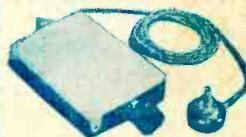**TRIPLETT A.C./D.C. POCKET TEST-METER, TYPE 666H**

15 ranges 1000 ohm p. volt
A.C./D.C. 10/50/250/1000/5000 volts.
Milliamps 0-10/100/500 m/a.
OHMS 0-300/250,000 ohms.

£5.10.0.

"373" MINIATURE 9.72 Mc/s I.F. STRIP.

The ideal F.M. Conversion Unit. Complete with 6 valves: 3-EF91, 2-EF92, and EB91. I.F.T.s, etc. With circuit and conversion data.

12/6 (less valves)
42/6 (with valves)

Postage 2/6 on either type.

HUNDREDS OF BARGAINS AVAILABLE IN TRANSISTOR COMPONENTS, VALVES, ETC. SEND 6d. for 28-PAGE CATALOGUE