


PRACTICAL WIRELESS

OCTOBER 1963

2¹/₂


AN A.F./R.F. SIGNAL GENERATOR

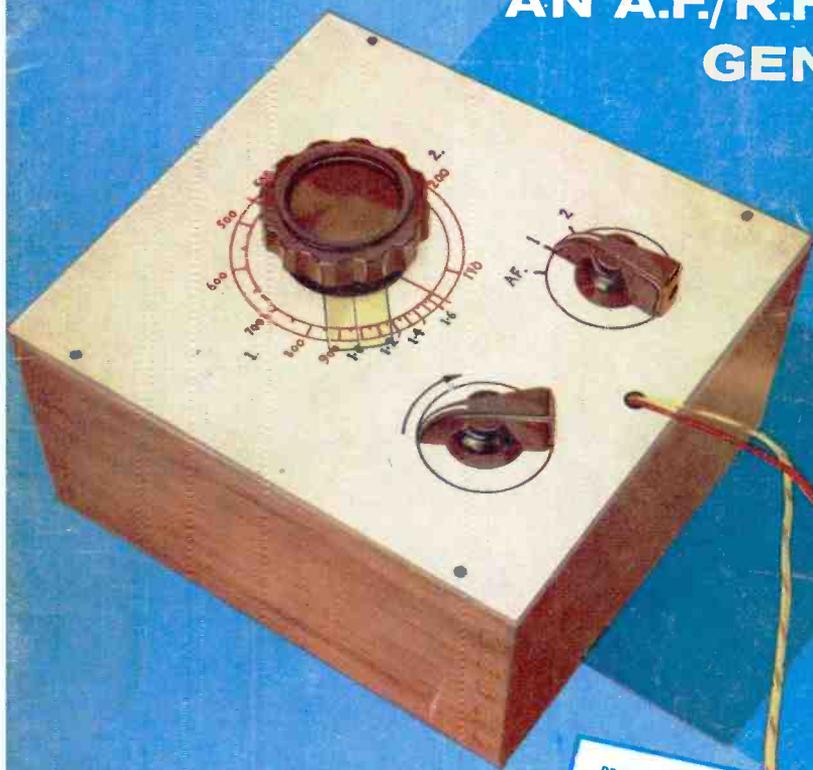Two-Transistor
Circuit
Tuning Range
170kc/s-16Mc/s



FREE inside!
**OHM'S LAW
CALCULATOR**

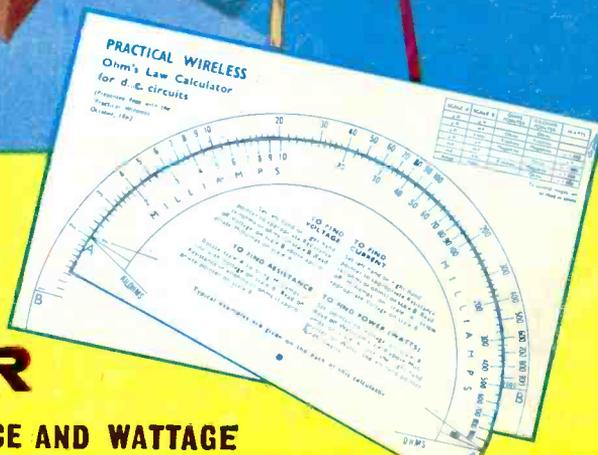FOR CURRENT, VOLTAGE, RESISTANCE AND WATTAGE



ADCOLA
PRODUCTS LIMITED
(Incorporated in England)

SOLDERING INSTRUMENTS AND EQUIPMENT

DESIGNED FOR
THE AMATEUR'S
RADIO STATION

ILLUSTRATED

List No. 70. $\frac{1}{8}$ " BIT
IN
PROTECTIVE
SHIELD
List No. 68

APPLY DIRECT
FOR
CATALOGUE
TO
Sales and
Service Dept.

**ADCOLA
PRODUCTS
LTD**
**ADCOLA HOUSE
GAUDEN ROAD,**


Telephones
MACaulay 4272 & 3101



LONDON, S.W.4


Telegrams
SOLJOINT LONDON SW4

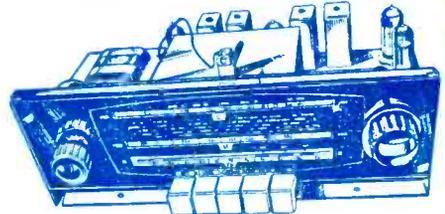BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.13.0 (Carriage Paid)



A.C. ONLY. Chassis size 15 x 6 $\frac{1}{2}$ x 5 $\frac{1}{2}$ in. high. New manufacture. Dial 14 $\frac{1}{2}$ x 4in. in 2 colours, predominantly gold. Pick-up Ext. Speaker. Ae. E., and Dipole Sockets. Five push buttons—OFF, L.W., M.W., P.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.: 200-300 M.: 88-98 Mc/s. Valves E280 rect.; ECH81, EP89, EAC80, EL84, ECC85. Negative feed-back circuit. Speaker and Cabinet to fit chassis (table model), 47/8 (post 5/). 10 x 6in. ELLIPTICAL SPEAKER. 25/-, to purchasers of this chassis. TERMS: (Chassis) £3.10.0 down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. yd. Circuit diagram 2/6

PUSH-PULL AMPLIFIER £5.5.0

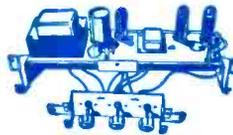

(6/- Carr.)
Brand new 200/240 A.C. mains. Bass, treble and vol. controls. With valves E280, ECC83 and 2-E84 giving full 8 w. Chassis 12 x 3 $\frac{1}{2}$ x 3 $\frac{1}{2}$ in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel". Stereo version 2 x 4 w., same price. Fixed panel. Tone & Vol. Controls

SPECIAL OFFER

3-valve Amplifier on chassis as for Push/Pull amplifier above. 2 concentric controls for on/off, volume, bass, treble. E280, ECC83 and ECL82. Mains and output transformer—3 ohm. 200-250 v. A.C. input. Suitable for guitar, telephone amplifier (pick-up coil required, 12/- extra), record player, microphone, etc., etc. Special offer while stocks last, ONLY £3. (6/- P. & P.)

TAPE RECORDER AMPLIFIER



Type TR3. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel. 13 x 1 $\frac{1}{2}$ in. height 5 $\frac{1}{2}$ in. overall. Front to back 5 $\frac{1}{2}$ in. Vol. and on/off tone. Mike radio and ext. speaker jacks. Valves magic eye, ECC83, ECL82, E280. Mains trans. Ready to bolt to B.S.I. Deck. Complete with switch wafer wired. Our Price ONLY £8.15.0 (6/- Packing and Carr.). Also available for Collaro Deck at 5/- extra.

NOTE THESE LOW PRICES

6-TRANSISTOR KITS AND SETS

All brand new parts. Rexine and Vynair Cabinets. Different colours. All holes drilled in printed circuit boards. Full M.W. and L.W. coverage. Car aerial socket. Alignment service, 17/8, inc. return post. All parts supplied separately. Built in 2 $\frac{2}{3}$ hours. 500 mW. output. Booklet 2/6, refunded on purchase of kit.

SUPERHET CIRCUITS

THE "SCALA"

THE "MILAN"



"Scala" Kit £4.19.6. (Post 4/-). Size 8 $\frac{1}{2}$ x 2 x 5 $\frac{1}{2}$ in. high and 3 $\frac{1}{2}$ in. speaker: or fully built £7.10.8.



"Milan" Kit £5.17.6. (Post 5/-). Size 9 x 3 $\frac{1}{2}$ x 7 $\frac{1}{2}$ in. 8 x 2 $\frac{1}{2}$ in. speaker: or fully built £7.5.

100 mF. + 200 mF. ELECTROLYTIC. New 275 v. (350 v. surge). 4in. x 1 $\frac{1}{2}$ in. dia. 5/- each. (Post 1/-).


ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH.

Terms Available on Items over £5. Send 6d. (stamps will do) for 20-page illustrated catalogue. Delivery by return C.O.D. 2/- extra.

ALL ITEMS GUARANTEED 12 MONTHS VALVES 3 MONTHS

GLADSTONE RADIO

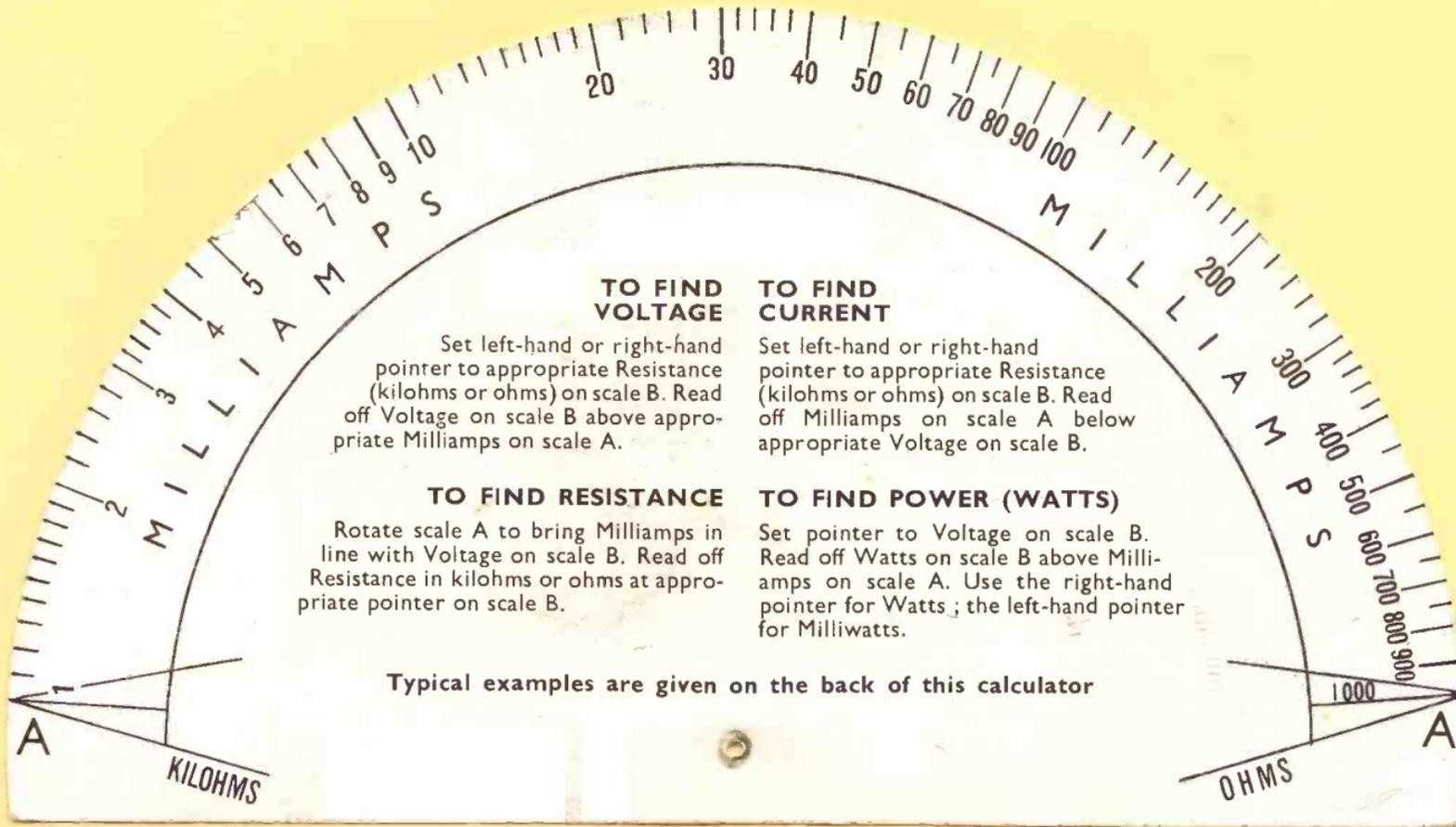"SCALA", CAMP RD., FARNBOROUGH, Hants
Farnborough 3371 CLOSED SATS



TO FIND VOLTAGE

Set left-hand or right-hand pointer to appropriate Resistance (kilohms or ohms) on scale B. Read off Voltage on scale B above appropriate Milliamps on scale A.

TO FIND CURRENT

Set left-hand or right-hand pointer to appropriate Resistance (kilohms or ohms) on scale B. Read off Milliamps on scale A below appropriate Voltage on scale B.

TO FIND RESISTANCE

Rotate scale A to bring Milliamps in line with Voltage on scale B. Read off Resistance in kilohms or ohms at appropriate pointer on scale B.

TO FIND POWER (WATTS)

Set pointer to Voltage on scale B. Read off Watts on scale B above Milliamps on scale A. Use the right-hand pointer for Watts; the left-hand pointer for Milliwatts.

Typical examples are given on the back of this calculator

TO FIND VOLTAGE

$$V = I \times R$$

Set kilohms at left-hand pointer, or ohms at right-hand pointer. Read volts above the milliamps scale.

Example : 10 mA is passing through a 2 kilohm resistor. Set left-hand pointer to 2 (kilohms); reading off 10 (milliamps) on Scale (A) gives the voltage drop as 20V (Scale B).

TO FIND CURRENT

$$I = \frac{V}{R}$$

Set kilohms at left-hand pointer, or ohms at right-hand pointer. Read current below volts.

Example : 30 volts is dropped across a 300 ohm resistor. Set right-hand pointer to 300 (ohms). Reading down from 30 (volts) on Scale B, the current is shown as 100 mA.



OHM'S LAW MEMORY AID

The relationship between voltage (V), current (I) and resistance (R) is given at a glance in the left-hand triangle. Wattage (W), current and voltage are similarly indicated in the other triangle.

Place finger over the *unknown* factor and the formula is given by the relationship of the two uncovered characters.



TO FIND RESISTANCE

$$R = \frac{V}{I}$$

Set volts above milliamps and read either kilohms at left-hand pointer or ohms at right-hand pointer.

Example : Current is 20 mA and voltage 60 V. Set Scale A so that the 20 (mA) is lined up with 60 (V) on Scale B. Reading left-hand pointer gives resistance as 3 kilohm.

TO FIND POWER (Watts) $W = I \times V$ or $I^2 R$

Set right-hand pointer to volts (Scale B), when the wattage is read off above the milliamps on Scale A.


Example : Voltage applied is 250 V; current drawn is 20 mA. Set right-hand pointer to 250. Reading above 20 (milliamps) on Scale A, gives 5 (watts) on Scale B. To find milliwatts proceed as above but use the left-hand pointer.

PRACTICAL WIRELESS

Ohm's Law Calculator

for d. c. circuits

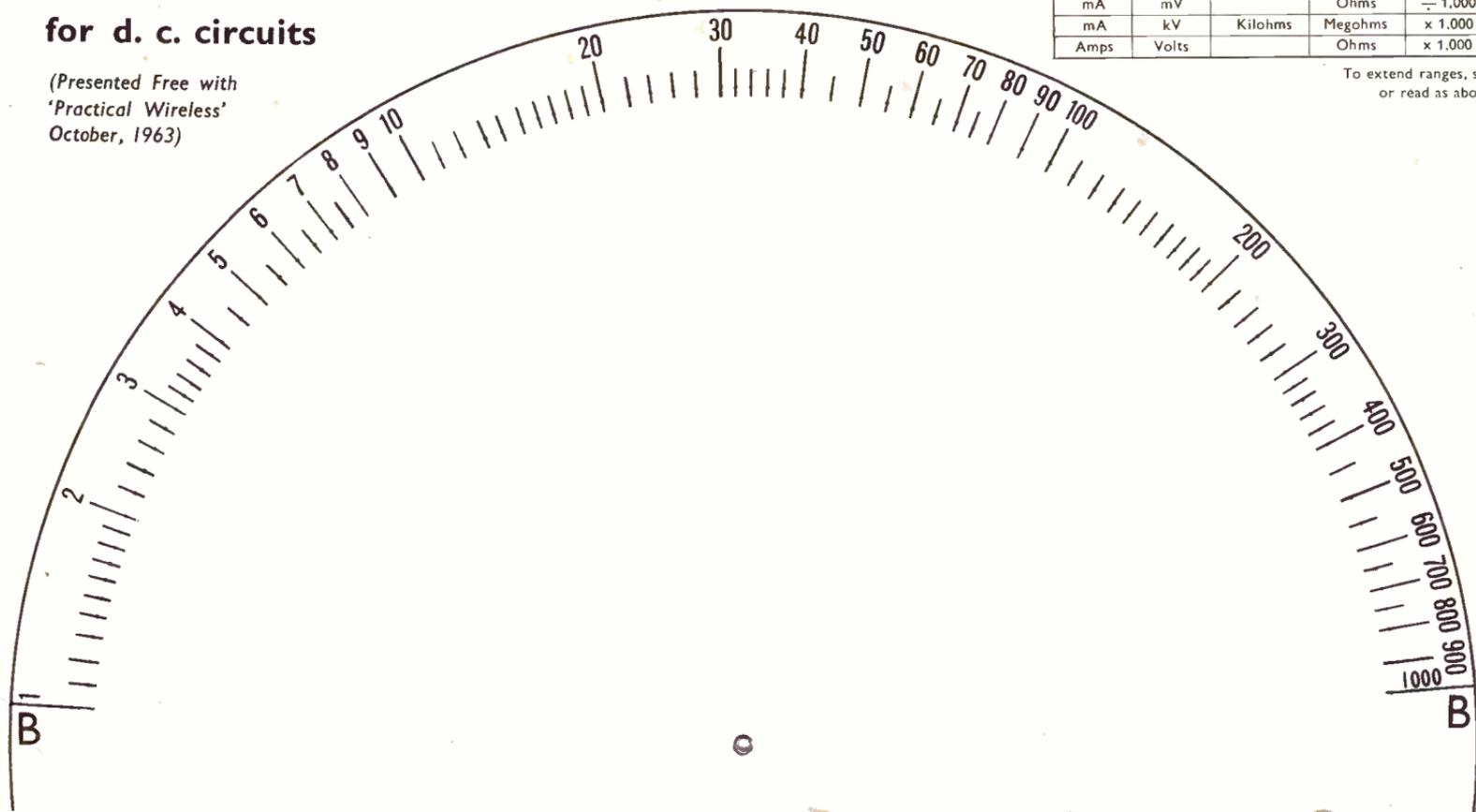(Presented Free with
'Practical Wireless'
October, 1963)



SCALE 'A'	SCALE 'B'	OHMS POINTER	KILOHMS POINTER	WATTS
μ A	μ V		Ohms	
μ A	mV	Ohms	Kilohms	
μ A	Volts	Kilohms	Megohms	$\div 1,000$
μ A	kV	Megohms		x 1
mA	mV		Ohms	$\div 1,000$
mA	kV	Kilohms	Megohms	x 1,000
Amps	Volts		Ohms	x 1,000

To extend ranges, set
or read as above

PRACTICAL WIRELESS


Ohm's Law Calculator

for d. c. circuits

(Presented Free with
'Practical Wireless'
October, 1963)

SCALE 'A'	SCALE 'B'	OHMS POINTER	KILOHMS POINTER	WATTS
μ A	μ V		Ohms	
μ A	mV	Ohms	Kilohms	
μ A	Volts	Kilohms	Megohms	$\div 1,000$
μ A	kV	Megohms		$\times 1$
mA	mV		Ohms	$\div 1,000$
mA	kV	Kilohms	Megohms	$\times 1,000$
Amps	Volts		Ohms	$\times 1,000$

To extend ranges, set
or read as above

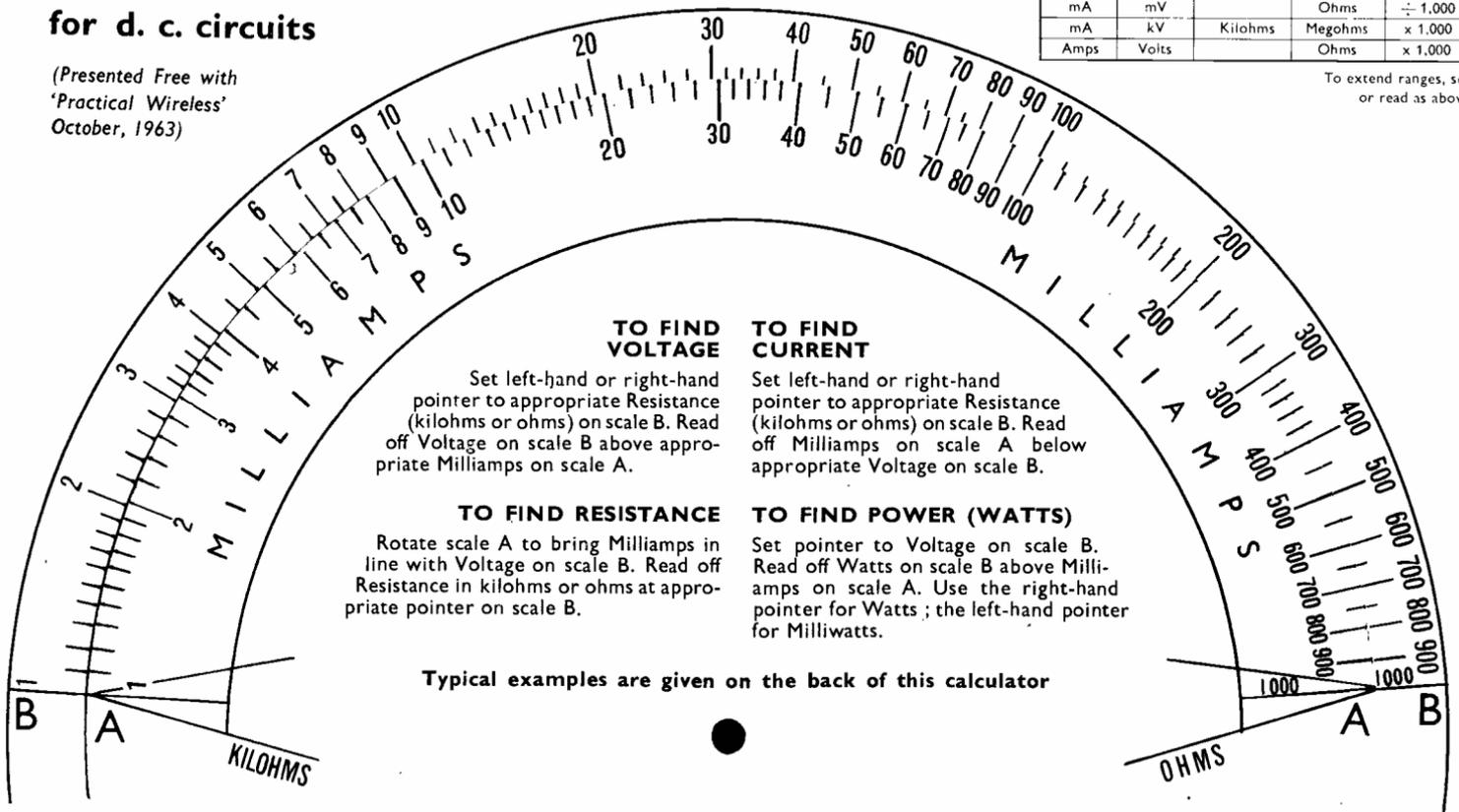

TO FIND VOLTAGE

Set left-hand or right-hand pointer to appropriate Resistance (kilohms or ohms) on scale B. Read off Voltage on scale B above appropriate Milliamps on scale A.

TO FIND CURRENT

Set left-hand or right-hand pointer to appropriate Resistance (kilohms or ohms) on scale B. Read off Milliamps on scale A below appropriate Voltage on scale B.

TO FIND RESISTANCE

Rotate scale A to bring Milliamps in line with Voltage on scale B. Read off Resistance in kilohms or ohms at appropriate pointer on scale B.

TO FIND POWER (WATTS)

Set pointer to Voltage on scale B. Read off Watts on scale B above Milliamps on scale A. Use the right-hand pointer for Watts; the left-hand pointer for Milliwatts.

Typical examples are given on the back of this calculator

R.S.T. VALVE MAIL ORDER CO.

Tel: MITcham 6202
Open Daily to Callers

211a STREATHAM ROAD, MITCHAM, SURREY.

All Valves Brand New and Fully Guaranteed — Obsolete valves a speciality.
Quotations given on any type not listed. Send S.A.E.

Special 24 Hour Express Mail Order Service

AC2/PEN 19/6	ECC85 7/6	EY83 12/6	PCC85 9/6	TDD4 12/6	UU6 17/6	6A8GT 13/6	6P25 10/6	12Q7GT 6/6
AC2/PEN DD 21/-	ECC88 12/6	EY86 7/-	PCC88 12/6	TDD13C	UU8 15/-	6AC7 6/-	6P28 12/6	12SA7 8/6
AC/TP 29/-	ECC91 3/-	EY91 3/-	PCC89 8/6		UU9 7/6	6AK5 5/-	6Q7 9/6	12S17 8/-
AC/VPI-5-7	ECF80 7/6	EZ35 6/-	PCF80 9/1	TH41 20/-	UYIN 12/6	6ALS 4/-	6Q7G 6/6	12SK7 6/-
AZ1 15/-	ECH21 21/6	EZ40 7/-	PCF82 7/-	TY86F 12/6	UY21 15/6	6AMS 5/-	6Q7GT 8/6	12SL7 8/-
AZ31 13/6	ECH35 10/-	EZ80 6/-	PCF86 12/6	U10 9/1	UY41 7/6	6AM6 4/-	6SA7 7/-	12SN7 10/-
B35 9/-	ECH42 9/6	EZ81 6/-	PCL82 9/1	U12 9/1	UY85 6/6	6AQ5 6/6	6SCT 8/6	12SQ7 12/-
CIC 10/-	ECH81 7/6	EZ90 5/-	PCL83 10/-	U14 9/1	VMS4B 12/6	6AT6 6/-	6SF5 10/-	14H7 10/-
CCH35 20/-	ECH83 8/6	E1148 2/-	PCL84 7/-	U22 8/-	VP4 15/-	6AU6 9/-	6SG7 7/-	14R7 10/-
CL33 12/6	ECL80 7/6	FC2 15/-	PCL85 9/-	U25 11/-	VP4A 15/-	6BA6 6/-	6SH7 6/-	14S7 16/-
CY1 15/-	ECL82 9/6	FC2A 17/6	PCL86 12/6	U26 10/-	VR105/30 7/6	6BE6 6/-	6SK7 5/6	19AQ5 8/-
CY31 10/-	ECL83 10/6	FW4/500 9/1	PENA4 19/6	U31 9/1	VR150/30 7/6	6BG6G 15/-	6SL7GT 6/-	20D1 10/-
D77 4/-	ECL86 9/6	FW4/800 9/1	PENB4 17/6	U35 17/6	W61 11/-	6B16 6/-	6SN2GT 5/6	20D2 21/-
DAC32 9/6	EF6 21/-	GZ30 10/6	PEN4DD 22/6	U37 17/6	W76 5/-	6BQ7A 12/6	6SQ7 8/6	20F2 17/6
DAF91 5/6	EF9 21/-	GZ32 10/6	PEN4VA 17/6	U47 11/-	W77 4/-	6BR7 10/6	6U4GT 10/-	20L1 22/6
DAF96 7/6	EF22 14/-	GZ33 19/3		U50 7/1	W81 6/-	6BS7 12/6	6U5G 7/6	20P1 15/-
DCC90 12/6	EF36 4/-	GZ34 13/6	PEN36C 20/-	U52 4/-	W81M 6/-	6BW6 8/-	6V6G 4/6	20P3 24/-
DF33 9/6	EF37 8/-	GZ37 19/3	PEN45 20/-	U78 4/6	X61M 10/-	6BW7 8/-	6V6GT 8/-	20P4 20/-
DF91 4/-	EF37A 8/-	HAB8C8010/6	PEN45 10/-	U145 10/6	X65 12/6	6C4 3/6	6X4 4/6	20P5 20/-
DF92 7/6	EF39 4/-	HL41 8/6	PEN45DD 25/-	U191 13/6	X76 12/6	6CSG 6/6	6XSGT 8/6	25A6 8/-
DF96 7/6	EF40 15/-	HL92 8/6	PEN46 5/-	U251 15/-	X76M 12/6	6C9 12/6	6Y30L2 10/-	25L6 8/-
DH63 6/-	EF41 8/-	HL133DD 9/6	PEN453DD 20/-	U281 15/-	X78 26/-	6CD6G 27/6	7B5 12/6	25Y5G 8/-
DH77 7/-	EF42 10/-	HN309 25/-	PEND4020 20/-	U282 19/6	X79 40/9	6CH6 10/-	7B6 10/-	25Z4 7/6
DK32 11/-	EF50A 3/1	IW4/350 10/-		U301 17/-	X81 10/-	6CW4 16/-	7B7 8/6	25Z5 8/6
DK91 6/-	EF50E 3/1	IW4/500 10/-	PL33 15/-	U329 15/-	Y61 10/-	6D2 4/-	7C5 8/6	25Z6 8/6
DK92 7/6	EF80 5/-	KT33C 8/-	PL36 12/6	U339 13/6	Y63 10/-	6D6 5/6	7C6 8/6	27SU 19/6
DK96 7/6	EF85 5/-	KT33C 8/-	PL38 21/6	U403 10/-	Z63 7/6	6E5 10/6	7D5 15/-	30C1 9/-
DL33 8/6	EF86 8/-	KT36 17/6	PL38 21/6	U404 10/-	Z66 10/-	6F1 10/6	7D6 15/-	30C15 12/6
DL35 10/-	EF89 9/-	KT61 9/6	PL81 9/1	UAF42 8/6	Z77 4/-	6F6 6/9	7D8 15/-	30F1 10/6
DL91 8/-	EF91 4/-	KT66 15/-	PL82 8/1	UB1 7/6	Z152 5/-	6F12 4/-	7H7 6/-	30L1 8/6
DL92 6/-	EF92 5/-	KT76 10/-	PL83 7/6	UBC41 8/6	OZ4 5/-	6F13 10/-	7R7 10/-	30L15 11/-
DL93 7/-	EF95 10/-	KT81 15/-	PL84 8/1	UBC81 10/-	IA7 11/-	6F14 10/-	7S7 10/-	30P4 18/-
DL94 7/6	EF98 10/-	KTW61 8/-	PL820 18/-	UBC80 8/-	IC5 10/-	6F15 12/6	7Y4 6/6	30P12 10/-
DL96 7/6	EF183 10/6	LN152 8/-	PM24M 13/6	UBF80 8/-	ID5 8/6	6F19 12/6	8D3 4/-	30P16 9/-
EA50 2/-	EF184 10/6	LN209 11/6	PX4 15/-	UBF89 7/6	ID6 10/-	6F23 10/6	9BW6 12/6	30P19 17/6
EABC80 5/-	EC32 8/6	LN309 12/6	PX25 25/-	IHS 9/6	IL4 5/-	6F25 16/6	10C1 12/6	30P11 11/6
EAC91 4/-	EL3 21/6	LZ319 12/6	PY31 15/-	IL5 9/6	IL5 9/6	6F26 13/6	10C2 17/6	30P13 11/6
EAF42 9/6	EL32 4/6	MKT4 17/6	PY32 12/6	IR5 6/6	IN5 9/6	6F33 5/6	10F1 10/6	30P14 16/6
EB34 2/6	EL33 10/6	MS4B 17/6	PY33 10/6	IR5 6/6	JIS 5/6	6H6 2/-	10F9 12/6	35A5 15/-
EB41 5/-	EL34 14/-	MVS/PEN 17/6	PY80 7/6	IS5 5/6	6J5 5/6	6I5G 4/6	10P13 15/-	35L6GT 8/6
EB91 4/-	EL35 10/-		PY81 7/6	IT4 4/-	6J5GT 5/6	6K 4/-	10P14 19/-	35W4 7/6
EB93 21/-	EL37 17/6	MVS/PENB 17/6	PY82 6/9	IU5 5/9	6J7 7/6	6K8 9/6	10P15 23/6	35Z3 15/-
EB93 21/-	EL38 17/6		PY83 8/-	2P 22/6	6I7G 5/6	6K8G 5/6	12A6 6/6	35Z4 7/6
EB94 8/6	EL41 9/6	MU14 9/1	PY88 10/-	UCL83 13/6	6I7GT 7/6	6K8G 5/6	12A8 9/6	35Z5 8/6
EB98 10/6	EL42 9/6	MX40 15/-	PY80 10/-	UCL83 13/6	6K7G 7/6	6K8G 5/6	12AT6 7/6	41STH 22/6
EBF80 8/-	EL81 12/6	N18 8/1	PZ30 15/-	UF42 7/6	6K7G 2/6	6K8 9/6	12AT7 5/6	42 12/6
EBF83 8/-	EL84 6/9	N37 14/-	Q595/10 10/-	UF80 7/1	6K7GT 7/6	6K8G 5/6	12AU6 17/6	50C5 10/-
EBF89 8/-	EL85 10/-	N78 22/6	Q5150/15 10/-	UF85 7/6	6K8 9/6	6K8G 5/6	12AU7 5/6	50CD6G 30/-
EBL1 21/-	EL90 8/6	N108 15/-	R2 10/-	UF86 12/6	6K8G 5/6	6K8G 5/6	12AX7 5/6	50L6 8/6
EBL21 21/-	EL91 4/-	N309 18/-	R16 17/6	UF89 6/6	6K8G 5/6	6K8G 5/6	12BA6 7/6	75 8/6
ECC35 8/-	EL95 10/-	N339 30/-	R19 16/-	UL41 8/-	6K8G 5/6	6K8G 5/6	12BE6 7/6	78 7/6
ECC40 15/-	EM80 8/6	N369 10/6	R20 16/-	UL44 20/-	6K8G 5/6	6K8G 5/6	12B7 10/6	80 7/6
ECC81 5/-	EM81 8/6	OD3 9/1	R20 16/-	UL46 14/6	6K8G 5/6	6K8G 5/6	12C8 8/6	85A2 12/6
ECC82 5/-	EM84 9/6	OZ4 5/6	R20 16/-	UL84 6/6	6K8G 5/6	6K8G 5/6	12CGT 4/6	185BT 30/-
ECC83 7/-	EM85 10/-	P2 10/-	SP41 3/6	UL85 7/6	6K8G 5/6	6K8G 5/6	12K2GT 5/6	807A 6/6
ECC83 7/-	EY51 7/6	PABC80 13/-	SP61 3/6	UM80 10/6	6A7 9/1	6K8G 5/6	12K8GT 10/-	807B 5/6
ECC84 8/6	EY81 8/6	PCC84 8/1	T41 15/-	URIC 15/-	6A8G 8/6	6K8G 5/6		

COMPLETE VALVE LIST FREE WITH ORDER

METAL RECTIFIERS

RM1 7/6	14A86	23/-	16RD 2-2-8-1	12/- (FC142)
RM2 8/-	14A97	26/-	16RE 2-1-8-1	10/-
RM3 10/-	14A100	28/-	18RA 1-1-8-1	5/-
RM4 17/6	14RA 1-2-9-2	21/- (FC301)	18RA 1-1-16-1	7/- (FC116)
RM5 19/6	14RA 1-2-8-3	25/- (FC31)	18RA 2N-1-8-1	12/-
	16RC 1-1-16-1	10/-	18RD 2-2-8-1	16/- (FC124)

BRAND NEW TRANSISTORS

OC44 6/-	OC74 6/-	OC81D 6/-
OC45 7/-	OC75 6/-	OC82 8/-
OC71 5/-	OC77 6/-	OC82D 6/-
OC72 8/-	OC81 6/-	

SILICON RECTIFIERS

400 volts 350 mA 8/- each

SETS OF VALVES

IR5, IS5, IT4, 3S4, 3V4 Set of 4, 19/-
DAF91, DF91, DK91, DL92, DL94 Set of 4, 19/-
DAF96, DF96, DK96, DL96 Set of 4, 26/6

SURBITON PARK RADIO LTD.

FOR POST HASTE—POST FREE SERVICE

MARTIN RECORDKITS

HALF TRACK

B.S.R. TD9 Monardek. Latest model, 5 1/2 in. spool	£9.90
Deposit £1.00 and 9 monthly	£11.00
Tape Amplifier for B.S.R. Deck, printed circuit ready wired with EOC88, ECL82, EM85 and EZ80. Complete with all plugs, sockets, panels knobs etc. The whole amplifier mounts on to the deck making a self-contained unit	£8.80
Deposit £1.00 and 9 monthly	£11.00
Case with 7 x 5 in. speaker, two-tone grey	£4.40
Complete Kit as above, with Tape and Microphone	£22.00
Deposit £2.40 and 12 monthly	£11.60
Collaro Studio Deck. Very latest model, 3 speeds, 7 in spools	£10.19.6
Deposit £1.20 and 8 monthly	£11.7.3
Tape Amplifier for Studio Deck, with ready wired printed circuit, control and input panels, mains and output transformers, knobs, plugs, screws etc., EP86, EOC88, EM84, EZ81 and 2-EL84, 3 watta output. Magic eye, Radio and hio, inputs Ex 1/8 socket, Tone and Monitor controls. Can be used as amplifier	£11.11.0
Deposit £1.40 and 12 monthly	£19/-
Case for above, with 9 x 5 in. speaker, two-tone grey	£5.50
Complete Kit, with Tape and Microphone	£29.00
Deposit £2.18.0 and 12 monthly	£28.2
Building instructions available at 2/6 each kit (returned if kit bought).	

JASON F.M. TUNERS

FMT1, complete with 4 EP14 valves	£6.12.6
Deposit £1.0.6 and 6 monthly	£12.0
FMT2, less power, complete with 4 EP80 valves	£7.17.6
Deposit £1.0.6 and 7 monthly	£12.6
FMT2, with power, complete with 4 EP80 and 1 EZ80	£9.15.0
Deposit £1.0.0 and 9 monthly	£11.8
FMT3, Fringe complete with valves, less power	£9.12.6
Deposit £1.0.6 and 9 monthly	£11.4
FMT3, with power, complete with all valves	£11.10.0
Deposit £1.7.6 and 9 monthly	£14.9
JTV/2, switched P.M. and TV sound, self powered, all valves	£13.7.6
Deposit £1.13.0 and 12 monthly	£15.3
Mercury II, as JTV/2 but less power, all valves	£11.2.6
Deposit £1.4.6 and 8 monthly	£11.7.3
Instruction book is included in all kits, but otherwise 2/6 and 3/6.	

AMPLIFIERS (MONO)

Linear L45 3 watt, 3 valve	£5.19.6
Linear Distante, 12 watt, suitable Mic or Guitar	£12.12.0
Linear Concord, 30 watt, ideal Guitar amp, with case	£18.00
Deposit £1.16.0 and 12 monthly	£19.10
Dulci GA5, integrated amp. and P.A., 5 watt, ECL86 valve	£13.2.6
Deposit £1.8.6 and 12 monthly	£11.6
Dulci DPA15, 15 watt with 2 valve pre-amp	£25.4.0
Deposit £2.10.8 and 12 monthly	£21.11
Tripletone Hi-Fi Major with pre-amp. Guitar or Mic.	£15.18.9
Deposit £1.15.3 and 12 monthly	£16.1
Leak TL/12, 10 watt Main amp. only	£18.13.0
Deposit £2.0.6 and 12 monthly	£11.11
Leak Variatone III pre-amplifier	£15.13.0
Deposit £1.11.6 and 12 monthly	£16.1
Quad, 15 watt Main amplifier only	£22.10.0
Deposit £2.5.0 and 12 monthly	£11.7.3
Quad pre-amplifier, Mono	£19.10.0
Deposit £1.19.0 and 12 monthly	£11.2.3

AMPLIFIERS (STEREO)

Dulci AC202, Integrated	£12.12.0
Deposit £1.7.0 and 12 monthly	£11.0.8
Dulci GA505 Integrated	£18.18.0
Deposit £2.0.6 and 12 monthly	£11.11
Cadet Mk. 2 watt, 4 tube amplifier, 4 ECL86 valve	£26.15.0
Deposit £2.13.8 and 12 monthly	£24.3
Leak Stereo 20 Main amplifier	£30.9.0
Deposit £3.4.8 and 12 monthly	£210.3
Leak Variatone III, stereo pre-amplifier	£25.0.0
Deposit £2.12.0 and 12 monthly	£21.6
Quad 22 Stereo Control Unit	£25.0.0
Deposit £2.10.0 and 12 monthly	£21.0
For Quad Main Amplifiers see Mono section above.	

QUARTER TRACK

B.S.R. TD9 Marriot heads, L series	£11.11.0
Deposit £1.4.0 and 12 monthly	£19/-
Tape Amplifier, as over, but quarter-track	£9.9.0
Deposit £1.0.0 and 9 monthly	£11.0
Case, two-tone grey with speaker	£4.4.0
Complete Kit, with tape and microphone	£25.0.0
Deposit £2.10.0 and 12 monthly	£21.6
Collaro Studio Deck, Marriot X series heads	£17.17.0
Deposit £1.17.6 and 12 monthly	£19.6
Tape Amplifier, as over but quarter track	£12.12.0
Deposit £1.7.0 and 12 monthly	£10.8
Case, with speaker, two-tone grey	£5.5.0
Complete Kit, with tape and microphone	£35.0.0
Deposit £3.10.0 and 12 monthly	£21.8.2
Tape Pre-amplifier for Collaro Studio Deck, with power supplies, EAC88, ECL82, EZ80 and EZ85. Radio and Mic sockets, gives an equalized output of 400mV	£28.8.0
Half Track	£11.0
Deposit £1.0.0 and 8 monthly	£9.9.0
Quarter Track	£11.0
Deposit £1.0.0 and 9 monthly	£11.0
TAPE HEADS	
M.S.S. Quarter track Record/Playback and Erase Set	£8.8.0
Bradmatic Half track Record/Playback head only	£11.2.6
Bradmatic Half track Record/Playback and Erase as Studio Set	£11.9.6
Collaro pressure sensitive 2 1/4 speed deck ball track	£32.11.0
Deposit £2.5.0 and 12 monthly	£21.4.0
Brenell Mk. 5 Tape Amplifier with power pack	£26.0.0
Deposit £2.12.0 and 12 monthly	£23.2

RADIO TUNERS

Armstrong T3C V.H.F. Tuner, self powered	£17.19.0
Deposit £1.19.8 and 12 monthly	£19.5
Armstrong 8T3 Mk. 2 A.M./F.M. Tuner, self powered	£26.12.0
Deposit £2.13.0 and 12 monthly	£24.2
Armstrong AP208 A.M./F.M. Radio chassis base and treble controls, P.I., inputs etc.	£21.4.0
Deposit £2.0.0 and 12 monthly	£14.10
Armstrong Jubilee Mk. 2 A.M./F.M. push-pull output stage	£26.8.0
Deposit £2.16.8 and 12 monthly	£26.11
Armstrong Stereo 55 A.M./F.M. Radio chassis, with stereo gram	£29.18.0
Deposit £2.9.8 and 12 monthly	£29.5
Armstrong Stereo 12 Mk. 2 A.M./F.M. Radio chassis, stereo gram and push-pull output stages	£40.8.0
Deposit £4.0.8 and 12 monthly	£36.11
Brass esutchon available for AP208 and Jubilee Mk. 2	7/6

GRAMOPHONE UNITS

Garrard SRP10 with GCR cartridge, Mono, single player	£26.11
B.S.R. UA14 with TCR cartridge, Mono 4 speed changer	£26.18.6
Deposit £1.0.0 and 6 monthly	£18.3
Garrard Autoaim, Mono GCR cartridge, 4 speed changer	£26.18.6
Deposit £1.0.0 and 6 monthly	£18.3
Garrard AT8 Automatic de Luxe, GCR Mono cartridge	£11.9.0
Deposit £1.8.8 and 9 monthly	£14.9
Phillips AG1018 Stereo cartridge, will change 7 in. records	£12.12.0
Deposit £1.7.0 and 12 monthly	£10.8
Decca Derram Arm and Plug-in Shell	£5.5.0
Decca Transcription Cartridge	£4.14.6
Decca Derram Auto Cartridge	£3.13.6
Goldring GL58 with arm, less cartridge	£15.19.8
Deposit £1.19.0 and 12 monthly	£16.6
Goldring "48" Transcription, 60 rpm	£17.14.0
Deposit £1.19.0 and 12 monthly	£19.0
Goldring GL55, as 0158 but less pick-up arm	£18.1.7
Deposit £1.7.7 and 12 monthly	£11.6
Garrard 4H/F with Mono GCR cartridge	£17.0.0
Deposit £1.14.0 and 12 monthly	£18.2
Garrard Lab Type "A" transcription auto-changer, Mono GCR	£19.14.9
Deposit £1.19.6 and 12 monthly	£11.2.9
Garrard 301	£20.12.2
Deposit £2.3.2 and 12 monthly	£11.4.0
Garrard 301 Strobe	£22.0.0
Deposit £2.4.0 and 12 monthly	£11.6.6

LOUDSPEAKERS

Goodmans Ariette 8	£5.6.7	Goodmans Ariom 201 12 in. Unit	£10.7.0
Goodmans Ariom 10	£6.5.11	Deposit £1.1.0 and 8 monthly	£15.8
Goodmans 5K/20/EL	£7.0.0	Goodmans Ariom 10 1 1/2 in. Unit	£14.10.0
Wharfedale Super 8/RS/DD	£6.14.2	Deposit £1.9.0 and 12 monthly	£14.0
W.B. HF1012 10 in.	£4.7.3	Wharfedale W12/EG 12 in. 15 watt Guitar speaker	£10.10.0
R.T.C. 12 in. Unit, 15 watt	£5.6.0	Deposit £1.1.0 and 12 monthly	£17/6
R.T.C. Hi-Fi Master	£8.3.0	Wharfedale Super 10/RS/DD 10 in. high quality unit	£10.18.0
Goodmans XO 5000 cross-over	£1.19.0	Deposit £1.3.8 and 12 monthly	£17/11
		Wharfedale RS/12/DD 12 in. 15 watt Hi-Fi speaker	£11.10.0
		Deposit £1.7.8 and 9 monthly	£14.8


48 SURBITON ROAD, KINGSTON UPON THAMES, SURREY

Established over 30 years

Telephone KIN 5549

We pay all postage and insurance. All orders despatched same day. Money refund guarantee
Hours: 9 a.m.—6 p.m. (1 p.m. Wednesday). We do not close for lunch. Open all day Saturday

INCREASE YOUR KNOWLEDGE

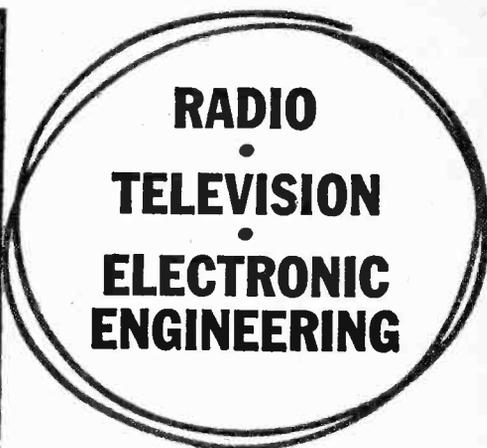

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING, INDUSTRIAL TELEVISION, RADIO AND TELEVISION SERVICING, RADIO SERVICE AND SALES, VHF/FM ENGINEERING, ELECTRONICS, COMPUTERS AND PROGRAMMING, ELECTRONIC TECHNICIANS, SERVOMECHANISMS, TELEMETRY, COLOUR TV, INSTRUMENTATION, AND PRINCIPLES OF AUTOMATION.

ALSO EXAMINATION COURSES FOR:

A.M.Brit.I.R.E.; City and Guilds Telecom. Technicians, C. & G. Radio and T.V. Servicing (R.T.E.B.), and P.M.G.'s Certificates. C. & G. Radio Amateurs' Certificates.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet radio receiver, Signal Generator and High-quality Multitester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Course opens a new world to the keen Radio amateur.

THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialised knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

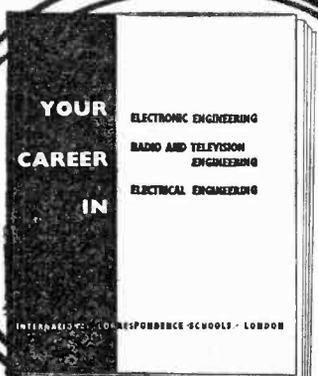You will receive the FREE ICS Prospectus listing the examinations and ICS technical course in radio, television and electronics. PLUS details of over 150 specialised subjects.



PLEASE SEND FREE BOOK ON _____

NAME _____

ADDRESS _____

OCCUPATION _____ AGE _____

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEXT HOUSE, PARKGATERD, London SW11

10.63

PORTABLE TRANSISTOR RADIOS

BACKED BY SUPER AFTER SALES SERVICE

ROAMER SEVEN Mk. III

● 9 stages—7 transistors and 2 diodes.

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 17 metres. Push-pull output for room filling volume from rich toned heavy duty 5in. speaker. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Air spaced ganged tuning condenser ensures wonderful station selection. Simulated hide case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP9 battery available anywhere.)


5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification

Total cost of parts now only

£5.19.6 P. & P 5/6

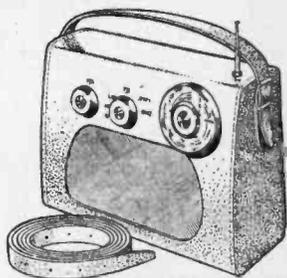Parts Price List and easy build plans 3/-.



MELODY SIX

"... amazed at volume and performance... has really come up to my expectations." S. G., Stockton on Tees.

● 8 stages—6 transistors and 2 diodes.

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push-pull output. Wonderful reception of B.B.C. Home and Light, 239, and many Continental stations. Handsome leather look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2 in. approx., with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only

£4.9.6

P. & P. 3/-.

Parts Price List and easy build plans 2/-.



TRANSONA FIVE


● 7 stages—5 transistors and 2 diodes.

Fully tunable over medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic speaker, etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in. with red speaker grille. (Uses 1289 battery available anywhere).

Total cost of all parts now only **42/6**

P. & P. 3/6.

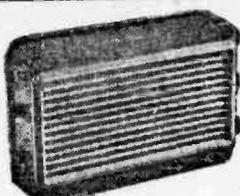Parts Price List and easy build plans 2/-.



TRANSONA SIX NEW!


● 8 stages—6 transistors and 2 diodes.

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade powerful magnet 3in. speaker makes listening a pleasure. Push pull transformers for ample power. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear.

Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere). (Carrying strap 2/- extra).

Total cost of all parts now only **59/6** P. & P. 3/6

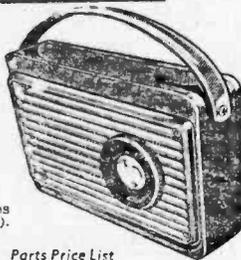Parts Price List and easy build plans 1/6



POCKET FIVE

● 7 stages—5 transistors and 2 diodes.

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round super-sensitive Ferrite Rod Aerial and fine tone 2 1/2 in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/2 x 3/4 in. (Uses PP4 battery available anywhere).

Total cost of all parts now only **42/6**

P. & P. 3/-.

Parts Price List and easy build plans 1/6



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler band. The ideal radio for home, car or can be fitted with carrying strap for outdoor use. Completely portable—has built in aerial for wonderful reception. Special circuit incorporating 2 R.F. stages, push pull output, 3in. speaker (will drive larger speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6

Parts Price List and easy build plans 2/-.




ROAMER SIX

● 8 stages 6 transistors and 2 diodes.

Listen to stations half a world away with this 5 waveband portable. Tunable on Medium and Long waves, Trawler Band and two Short waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 6 1/2 x 4 1/2 x 1 1/2 in.

Total cost of all parts now only **£4.19.6** P. & P. 3/6.

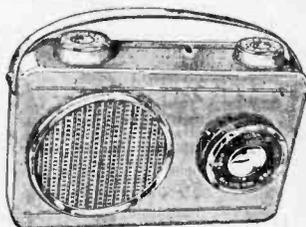Parts Price List and easy build plans 3/-.



Radio Exchange Co.

27 HARPUR STREET, BEDFORD

Phone 2347 ● Opposite Co-op. ● 10-1 p.m. Sats.

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at prices stated.

THE R.S.C. BASS-MAJOR 30 WATT GUITAR AMPLIFIER


A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

Eminently suitable for bass guitar and all other musical instruments

- ★ Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 3in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v. to 50 c.p.s. A.C. mains operation.
- ★ Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

39¹/₂ Gns.

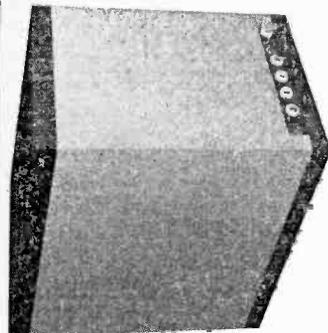Send S.A.E. for leaflet.
OR DEPOSIT of £4.3.0 and 12 monthly payments of £3.9.11. Carr. 17/6.



R.S.C. JUNIOR GUITAR AMPLIFIER
5-watt high quality output. Separate bass and treble "cut" and "boost" controls. Sensitivity 15 m.v. Two high impedance inputs. 10in. loudspeaker. Handsome, strongly made cabinet (size 14 x 14 x 7in. approx.) finished in attractive and durable polychrome. 200-250 A.C. mains operation. **£8.19.6** OR DEPOSIT £1 and 9 monthly payments of £1. Carr. 7/6.

LINEAR TREMOLO/PREAMP. UNIT
Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket of amplifier. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect), Volume and Switch. Three sockets are for two inputs and Foot Switch. **ONLY 4 Gns.**

R.S.C. SENIOR Guitar Amplifier
14 watt high-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-up can be used at the same time. Two loudspeakers are incorporated, a 12in. high flux 14 watt bass unit, and a 6 x 4in. elliptical for treble. Cabinet is well made and finished as Junior Model. Size approx. 15 x 13 x 9in. **Only 16 Gns.** Carr. 10/-

Send S.A.E. for leaflet.
OR DEPOSIT 37/- and nine monthly payments of 37/-.



R.S.C. B20 BASS GUITAR AMPLIFIER

A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains. **Send S.A.E. for leaflet.**

29¹/₂ Gns Or Deposit £3.2.0 and 12 monthly payments of 56/10. Carr. 17/6.

EX. GOVERNMENT ACCUMULATORS. Size 7 1/4 x 2 1/2. 2 v. 16 A.H. brand new, 6/9 each, 3 for 15/6.

EX. GOVT. SMOOTHING CHOKES. 200 mA, 3-5 H, 50 ohms. Parmeko 8/9; 150 mA, 10 H, 50 ohms 9/9; 80 mA, 20 H, 900 ohms 5/9; 120 mA, 12 H, 100 ohms 9/9; 50 mA, 50 H, 1,000 ohms 6/9; 100 mA, 10 H, 100 ohms 6/9; 60 mA, 5-10, 50 ohms 2/11.

COMPLETE POWER PACK KIT, 1911. Consisting of Mains Trans., Metal Rectifier, Double electrolytic, smoothing choke chassis and circuit. For 200-250 v. A.C. mains. Output 250 v., 60 mA, 6.3 v. 2 a.

R.S.C. POWER PACK, 39/9. Louvred metal case only 8 x 5 1/2 x 2 1/2ins. Stove enamelled. For 200-250 v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA, fully smoothed and 6.3 v. 2 a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

R.S.C. BABY ALARM or INTER-COMM. KIT. Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20-£30. Only 89/6 carr. 5/- or assembled ready for use 6 £22.



EX. GOVT. SELENIUM RECTIFIERS 12v 15 AMP 19/9 (BRIDGE) F.W. ONLY

DERBY NOW OPEN AT 26 Osmaston Road THE SPOT

TRANSISTOR SALE. Mullard OC71 3/9, OC45 4/11, OC44 4/11, OC72 4/9, OC81 4/11, OC171 8/9, Ediswan XA101 3/9, XB102 3/9, XA112 3/9, XB113 3/9, XB104 3/9, XC101A 3/9. Postage 6d. for up to 3 Transistors.

D.C. SUPPLY KIT, 12 v. 1 a. consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses, Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 29/11.

SELENIUM RECTIFIERS
F.W. BRIDGE 24 v. 2 amp. 14/9
6/12 v. 1 a. 3/11 24 v. 20 amp. 89/9
6/12 v. 2 a. 6/11 H.T. TYPES H.W.
6/12 v. 3 a. 9/9 150 v. 40 mA. 3/9
6/12 v. 4 a. 12/3 250 v. 60 mA. 3/11
6/12 v. 6 a. 15/3 250 v. 60 mA. 4/11
6/12 v. 10 a. 28/9 250 v. 80 mA. 5/11
6/12 v. 15 a. 35/9 250 v. 75 mA. F.W. (Bridge), 10/11. 250 v. 50 mA. F.W. (Bridge), 8/11. H.W. 250 v. 60 mA. 5/11.

HI-FI 10-WATT AMPLIFIERS. Brand New Complete **£7.19.9** Carr. 5/6.

Manufacturers' discontinued Model. Push-Pull output. Latest high efficiency valves. Dual separately controlled inputs for "Mike". Separate Bass and Treble Controls. High sensitivity. Output for 3 or 15 ohm speaker. Guaranteed tested and in perfect working order.

HUGE PURCHASE OF BRAND NEW 24v. 20 Amp. F.W. (BRIDGE) SELENIUM RECTIFIERS. each **49/9**

R.S.C. (Manchester) Ltd.

LEICESTER 32 High St. Half-day Thursday
BIRMINGHAM 6 Gt. Western Arcade (Opp Snow Hill Sta) No half-day

SHEFFIELD 13 Exchange St. Castle Market Bldgs. Sheffield Half-day Thursday

HULL 51 Savile St. Hull

LIVERPOOL 73 Dale St. Liverpool 2 Half-day Wednesday

BRADFORD 56 Morley St. (above Alhambra Theatre) Bradford

MANCHESTER 8-10 Brown St. (Market St.) Manchester 2 No half-day

LEEDS 5-7 County (Mecca) Arcade, Briggs, Leeds. No half-day

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

R.S.C.(Manchester)
Ltd.MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1.
Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

LEICESTER

32 High St.

Half-day
Thursday

BIRMINGHAM

4 Gt. Western
Arcade
(Opp Snow Hill
Sta) No half-day

SHEFFIELD

13 Exchange St.
Castle Market
Bldgs. Sheffield

Half-day Thursday

HULL

51 Savile
St., Hull

Half-day Thursday

LIVERPOOL

73 Dale St.
Liverpool 2

Half-day Wednesday

BRADFORD

56 Morley St.
(above Alhambra
Theatre) Bradford

Half-day Wednesday

MANCHESTER

8-10 Brown St.
(Market St.)
Manchester 2

No half-day

LEEDS

5-7 County
(Mecca) Arcade,
Leeds

No half-day

FANE HEAVY DUTY HI-FI SPEAKERS

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice coil Assemblies. 122/10 20w., 5 gns. 122/10A 20w., 6 gns. 122/12 20w., 6 gns. 122/12A 20w., £7.19.6. 122/14 22w., 9 gns. 122/14A 22w., 10 gns. 122/17 25w., 11 gns. 122/17A 25w., 12 gns. 15in., 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 152/12 20w., 12 gns. 152/12A 20w., 13 gns. 152/14 27w., 14 gns. 152/14A 27w., 15 gns. 152/17 35w., 16 gns. 152/17A 35w., 17 gns. "A" indicates dual cone type. 30-17,000 c.p.s. Send S.A.E. for leaflets. Terms available.

R.S.C. 30-WATT ULTRA LINEAR

HIGH FIDELITY AMPLIFIER A10
A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Gain level 70 db down. Frequency response +3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 607 output valves. All components are chosen for reliability. Six valves are used EF86, EF89, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts. Has ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT.
An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains, and has output for 3 and 15 ohm speakers. Complete Kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. Separated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months guarantee, for 14 gns. Send S.A.E. for leaflet.

11 Gns.

Carr. 10/-

TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9. Suitable microphones and speakers available at competitive prices.

WE STOCK ARMSTRONG, DULCI, LINEAR, ROGERS, LEAK and JASON EQUIPMENT GOODMANS, W.B. and FANE SPEAKERS**GARRARD AND GOLDRING T/ABLES**

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, W/Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 63 v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7in. High simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts list with illustrations. 2/6. Total building cost £4.15.0. S.A.E. for leaflet.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 and 90 v. This includes low consumption types. Complete kit with diagrams. 39/9, or ready to use, 46/6.



kit of parts with diagrams and instructions. 49/9, or ready for use, 59/6.


P.M. SPEAKERS. 10in. W.B. "Stentorian" 3 or 15 ohms type HF 1012 10 watts, hi-fidelity type. Recommended for use with our A10 Amplifier. £4.7.6. 12in. R.A. 3 ohms 10 watts (12,000 lines). 59/6.

TWEETERS. R.A. 3 ohm 19/9. 15 ohm 25/9.

R.A. 12in. DUAL CONE 3 ohm 8 Watt Speakers. Ideal for Stereo. Only 39/9 ea.

Jason FMTI V.H.F./F.M. Radio Tuner design. Total costs of parts including valves. Tuning dial. Escutcheon, etc. £7.19.6.

LINEAR L65 MINIATURE 4/5 WATT QUALITY AMPLIFIER. Suitable for any record playing unit, and most microphones. Negative feedback 12 db. Separate Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 3-ohm speaker. Mullard valves EZ80, ECC83, EL84. Size only 7 x 5 x 5in. High. Guaranteed 12 months. Only £5.19.6. Send S.A.E. for leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

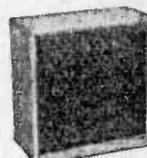12in. 10 WATT

HIGH QUALITY LOUDSPEAKER in walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/-. Terms: Deposit 11/3 and 9 monthly payments of 11/3.

12in. 20 WATT HI-FI LOUDSPEAKERS IN CABINETS. Size 18 x 18 x 10in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6. For larger types see page 477.

LINEAR L64 GRAM AMPLIFIER High quality. Separate Bass and Treble controls. Handsome appearance. Completely enclosed. Black/Gold Frontplate 5 gns.

R.S.C. 4.5 WATT A5 HIGH-GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads. In addition to all other types of pick-ups and practically all "mikes", there are separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down 15 db. of Negative feedback is used. I.T. of 300 v. 25 mA and L.T. of 63 v. 1.5 A. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes full punched chassis (with baseplate) with Blue Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assemble ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.



230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes full punched chassis (with baseplate) with Blue Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assemble ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

NOW OPEN AT 26 Osmaston Road THE SPOT DERBY

R.S.C. GRAM AMPLIFIER KIT. 3 watts output. Negative feedback. Controls Vol. Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.

THE SKYFOUR T.R.F. RECEIVER
A design of a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, SP61, 8V6C. Selectivity and quality excellent. Simple to construct. Point-to-point wiring diagrams, instructions and priced parts list. 1/8. maximum building costs £4.18.6. Inc. attractive walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

MULTI-METERS. CARY M1. Sensitivity 2,000 ohms per volt. A.C. and D.C. 54/-.
A.10. Basic Meter sensitivity 155 micro-amps A.C. and D.C. ranges £4.17.6.
B.20. Sensitivity up to 10,000 ohms per volt A.C. and D.C. £6.10.0. 30,000 ohms per volt, with overload buzzer. £8.19.6.

R.S.C. JUNIOR HI-FI REPRODUCER. The very latest Goodman Axiote 8 High Fidelity loudspeaker (retailing at approx. 3 gns.) fitted in a specially designed Bass Reflex cabinet. Size 12 x 18 x 10in. Acoustically lined and ported and finished in polished walnut veneer. Matching impedance 15 ohms. Frequency range 40-15,000 c.p.s. Power handling 6 watts. 8 gns. nominal. Ideal for Stereo. Carr. 4/6 Limited number.

8 Gns.

R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL. Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £3.18.6.

STANDARD MODEL. As above but for 12in. speakers. Size 20 x 15 x 13in. For vertical or horizontal use. £5.19.6. Suitable legs with brass ferrules. 19/6 per set of 4.

R.S.C. CORNER CONSOLE CABINETS

Polished walnut veneer finish. Pleasing design. **JUNIOR MODEL.** Size 20 x 11 x 8in. for 8 x 5in. or 10 x 6in. speakers. £2.9.6.
STANDARD MODEL. Size 27 x 18 x 12in. for 8 or 10in. speakers. £4.11.9.
SENIOR MODEL. Size 30 x 20 x 15in. for 12in. Speaker. Suitable Speaker systems below. Only 7 gns.



AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/-. Or Senior 15 watt. 7 gns. Carr. 7/6.

AUDIOTRINE EQUIPMENT CABINETS

Size 36 x 15 x 18in. Beautiful walnut veneered finish. Elegant contour design. Robust construction. Uncut, removable baseboard. Depth above Only 12 gns. baseboard 5/- Carr. 15/-.
Terms: Dep. 29/9, and 9 monthly pymts. 29/9.



AUDIOTRON HI-FI TAPE RECORDER KIT 25¹/₂ Gns. Carr. 17/6.

REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN AN HOUR. Incorporating the latest Collaro Studio Tape Transcriber. The audiotone High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable carrying Cabinet with latest attractive two-tone polychrome finish. Size 14 1/2 x 15 x 9 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. TERMS. Deposit £2.13.9 and 12 monthly payments of 44/-. Cash price if settled in 3 months.




ONLY 3 PAIRS OF SOLDERED JOINTS MAINS

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram. as in A.10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, E281. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response +3 db. 30-30,000 c/s. Six negative feedback loops. Hum level 60 db. down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for STANDARD or LONG PLAYING RECORDS. FOR MUSICAL INSTRUMENTS such as STRINGS, BASS, LEAD and RHYTHM GUITARS, etc. OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a RADIO FEDER UNIT. Size approx. 12 x 9 x 7 in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only 8 Gns. Carr. 10/- for factory built 5/- extra. If required louvered metal cover with 2 carrying handles can be supplied for 18/9. TERMS ON ASSEMBLED UNITS. DEPOSIT 2/9 and 9 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing Cabinets. Speakers, Microphones, etc. with cash and credit terms.

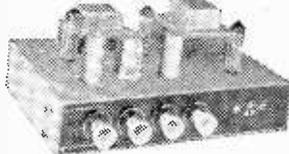

LINEAR TAPE PRE-AMPLIFIER. Type LP/1. Switched Negative feedback equalisation Positions for Record (11m., 31m., 71m. and Playback. EM84 Recording level Indicator. Designed primarily as the link between a Collaro Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. Only 9 gns. S.A.E. for leaflet.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. 8 Gns. Carr. 10/- Full constructional details and price list 2/6. Carr. 10/- Kit can be supplied assembled ready to use for 59/6 extra.



SENSATIONAL STEREO OFFER

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Sensitivity 130 mV. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 18/9 extra with above only.

SOLDERING IRONS. 230-250 v. 30 watts. First quality. For Radio work. 18/9. Spare elements and bits available.

HEAVY DUTY CHARGER KIT. 6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-230-250 v. F.W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panels, Plugs, Fuses, Fuseholder and circuit. 59/9. Carr. 4/6.

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250v., 50 c/s. Guaranteed 12 months.

Assembled 4-5 amps 6/12 v. Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvered steel case with stoved blue hammer finished. Fused and ready for use with mains and output leads. Carr. 5/-. Terms: Deposit 13/3 and 5 monthly payments 13/3 6/12 v. 3a., all facilities as above. Only 59/9. carr. 3/9.

ASSEMBLED 6/12 v. 2 amps. Fitted Ammeter, Bridge and selector plug for 6 v. or 12 v. Louvered metal case finished attractive blue hammer blue. Fused, ready for use with mains and output leads. Carr. 3/9 49/9 Carr. 27/9 6/12v. 1 amp. 27/9 Less meter.

BATTERY CHARGER KITS Consisting of Mains Transformer, Bridge, Selenium Rectifier, well ventilated steel case. Fuses. Fuse-holders. Grommets, panels, Heavy Duty Clips, circuit. Carr. 3/6 extra. 6 v. or 12 v. 1 amp. 22/9 As above, with Ammeter 28/9 6 v. 2 amps. 19/9 6 v. or 12 v. 2 amps. 25/9 6 v. or 12 v. 2 amps, inclusive of Ammeter 35/9 6 v. or 12 v. 4 amps. 45/9 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector 52/9

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primary 200-230-250 v. 31 c/s. Screened TOP SHROUDED UPRIGHT 200-250-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a. 17/9 250-0-250v. 100mA. 6.3v. 2a. 5v. 2a. 18/9 250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. 21/9 250-0-250v. 100mA. 6.3v. 3.5a. C.T. 19/9 250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 25/9 300-0-300v. 130mA. 6.3v. 4a. 6.3v. 1a. for Mullard 510 Amplifier. 29/9 300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 28/9 350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 28/9 425-0-425v. 200mA. 6.3v. 4a. 5v. 3a. 49/9 FULLY SHROUDED UPRIGHT 250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3 v. 2a. Midget type 11 8 x 3 in. 17/11 250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 27/9 300-0-300v. 100mA. 6.3v. 4a. 5v. 3a. 27/11 300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v. 1a. for Mullard Amplifier 33/9 350-0-350v. 100mA. 6.3v. 4a. 5v. 3a. 27/11 350-0-350v. 150mA. 6.3v. 4a. 5v. 3a. 35/9

FULLY SHROUDED (continued) 425-0-425v. 200mA. 6.3v. 4a. C.T. 5v. 3a 55/- 425-0-425v. 200mA. 6.3v. 4a. C.T. 6.3v. 4a. C.T. 5v. 3a. 59/9 450-0-450v. 250mA. 6.3v. 4a. C.T. 5v. 3a 69/9 OUTPUT TRANSFORMERS Midget Battery Pentode 66 : 1 for 354, etc. Small Pentode. 5000 Ω to 3 Ω 4/6 5000 Ω to 15 Ω 4/6 Following types for 3 and 15 Ω speakers: Standard Pentode 7/8,000 Ω to 3 Ω 5/9 Standard Pentode 7,000 Ω to 3 Ω 5/9 Push-Pull 3 Ω 5/9 Push-Pull 6 watts. EL84, or 6V6 to 3 Ω or matched to 15 Ω 9/9 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5 to 15 Ω 19/9 Following types for 3 and 15 Ω speakers: Push-Pull 10-12 watts 6V6 or EL84 18/9 Push-Pull 15-18 watts. 6L6, KT66 22/9 Push-Pull Mullard 510 Ultra Linear 28/9 Push-Pull 20 watts, sectionally wound, 6L6, KT66, EL34, etc. 49/9

MIDGET MAINS Primaries 200-250 v. 50 c/s. 250 v. 60 mA. 6.3 v. 2a. 11/9 250-0-250 v. 60 mA. 6.3 v. 2a. 12/11 Both above size 2 1/2 x 2 1/2 x 2Hns. FILAMENT TRANSFORMERS All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2a. 7/6; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/6; 12 v. 1.5 a. twice. 17/6. SMOOTHING CHOKES 150 mA, 7-10 H 250 ohms. 11/9 100 mA, 10 H 200 ohms 8/9 80 mA, 10 H 350 ohms 5/9 60 mA, 10 H 400 ohms 4/11 CHARGER TRANSFORMERS All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. 1a. 12/9; 0-9-15 v. 2a. 14/9; 0-9-15 v. 3 a. 18/9; 0-9-15 v. 5a. 19/9; 0-9-15 v. 6 a. 23/9; 0-9-15 v. 8 a. 28/9 AUTO (step up/down) TRANS. 0-110/120-230/250 v. 50-80 watts. 13/9; 250 watts. 39/9; 150 watts. 27/9. MICROPHONE TRANSFORMERS 120 : 1 high grade, clamped. 7/6.

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090
NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK

ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM DISMANTLED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED," BUT HAVE A SHORT AND UNRELIABLE LIFE

0A2	5/-	4BK8	9/3	6U7G	6/0	20P4	13/9	ACBPEN6/-	F.ABC280	6/-	EL35	13/6	KTW61	5/-	QP25	5/-	U43	6/3	AF118	20/-
0B2	6/-	4BB7	25/-	6V6G	3/0	20P5	14/8	AC1PEN	EAC09	3/8	EL37	12/6	KTW62	8/6	QR150/169/8	4/-	U45	15/6	AF127	13/-
0Z4G	4/8	4B86	7/6	6V8GT	6/0	25A8G	7/8	17/8	EACF42	7/8	EL41	7/6	KTW63	5/9	R12	5/8	U46	13/6	BY13	12/6
1A3	2/6	6B7W	5/-	6X4	4/-	25L0GT	6/0	AC1PEN	EBA1	4/9	EL42	7/9	LE3	3/-	R17	17/6	U62	4/9	GD8	5/6
1A5	5/-	4B86	4/-	6X5	4/8	25U4GT11/2	2/-	AC1PEN	EBB1	2/8	EL43	8/9	LN162	6/-	R18	14/6	U76	4/9	GT102	8/6
1A7GT	5/8	6C4	2/3	6Y6	6/-	25V5G	8/-	AC80/VM	EBB2	2/8	EL44	8/9	LN162	6/-	R19	7/6	U78	4/9	GT108	8/6
1C1	4/9	6C6	4/-	7B6	9/-	25Z4G	7/-	AC1PEN	EBB3	2/8	EL45	8/6	LN309	8/9	R19	7/6	U78	4/9	GT108	8/6
1C2	6/9	6C8	3/-	7B7	7/8	25Z4G	7/-	AC1PEN	EBB4	2/8	EL46	8/6	LN319	10/6	R20	8/6	U84	4/7	GT108	8/6
1C3	6/9	6C8	3/-	7C5	10/0	25Z5G	8/-	AC1PEN	EBB5	2/8	EL47	8/6	ME1	16/10	64/-	U90	17/6	GT111	8/6	
1C5	6/9	6C9	11/6	7C8	7/8	25Z6GT	8/-	AC1PEN	EBB6	2/8	EL48	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1C6	10/6	6C10	7/9	7D3	21/-	27V	23/8	AC1PEN	EBB7	2/8	EL49	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1D5	7/-	6C12	6/8	7D5	15/6	28D7	7/-	AC1PEN	EBB8	2/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1D6	9/9	6C17	12/6	7D6	15/6	30C1	10/-	ATP4	EBF63	8/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1P1	6/3	6C82	21/6	7D8	18/-	30C15	10/-	AC1PEN	EZ31	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1P2	2/9	6C16	5/-	7B7	5/8	30P6	6/-	AC1PEN	EZ31	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1P3	2/9	6C16	5/-	7B7	5/8	30P6	6/-	AC1PEN	EZ31	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1P4	2/9	6C16	5/-	7B7	5/8	30P6	6/-	AC1PEN	EZ31	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
1P5	1/5	6D1	1/6	7B7	14/-	30P12	12/6	B36	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1P9D	3/9	6D3	17/6	7Y4	5/-	30L1	5/8	B163	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1L6	6/9	6D6	3/-	8D2	2/6	30L15	10/-	C14	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1E8GT	6/3	6B2G	14/3	8D3	3/0	30P4	12/3	C10	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1U4	2/9	6E5	6/-	8B5G	13/6	30P12	7/8	C11	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1LLA6	16/10	6F1	6/8	9D2	3/-	30P16	6/-	CCH35	13/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1LD5	4/3	6F5	6/3	9D7	12/3	30P19	12/3	CK506	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1LND5	4/3	6F5	6/3	9D7	12/3	30P19	12/3	CK506	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1P8GT	6/8	6F6GT	7/6	10C2	10/6	30P13	9/6	CL3	11/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1L1	6/3	6F8	5/-	10D1	7/-	30P14	13/3	CV6	2/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1P10	4/9	6F11	17/9	10D2	11/8	35A5	20/9	CV8	10/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1P11	5/6	6F12	3/3	10F1	10/-	35L0GT	8/-	CV271	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1A5	3/9	6F6	4/-	10F2	10/6	35L1	10/6	CV271	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1R4	5/9	6F14	25/11	10F18	10/0	35Z3	16/4	CV1C	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1R5	3/9	6F15	9/6	10LD3	6/9	35Z4GT	4/9	CV31	8/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
172	24/11	6F16	7/6	10LD11	10/9	35Z5GT	4/9	D1	1/3	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
174	2/9	6F17	12/6	10P13	8/6	408U	15/8	D11	1/3	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1U4	7/6	6F18	13/6	10P14	8/6	408U	15/8	D11	1/3	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
1U5	6/3	6F19	9/9	11D3	17/6	42	10/-	D43	4/3	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
2A7	10/6	6F23	9/6	11D5	17/6	43	10/-	D43	4/3	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
2026	3/-	6F24	11/6	11E1	15/-	50A5	21/10	D77	2/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
2D190	7/6	6F28	5/-	11E3	17/6	50B5	7/6	D77	2/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
2E21	5/8	6F30	7/6	10B6	7/6	50C2	9/3	DAF91	3/9	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
2P	23/3	6F32	4/-	12A5	16/8	50C160/40/9	DAF96	6/3	ECF80A	20/-	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6	
2X3	3/-	6F33	3/8	12AC6	13/6	50L6GT	7/6	DC090	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3A4	4/-	6G6	2/6	12AD6	15/2	52KU	14/8	D14	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3A5	6/9	6B6	1/6	12AE6	13/3	53KU	14/8	D14	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3B7	5/-	6G5	3/8	12B7	12/6	53KU	14/8	D14	12/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3D6	4/-	6J5GT	4/3	12A7B	9/6	75	5/8	DDT25	7/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3Q4	6/9	6J6	3/8	12A7B	9/6	75	5/8	DF33	8/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3Q5	7/3	6J7G	4/9	12A7T	4/7	77	6/-	DF66	15/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3B4	4/9	6J7GT	7/6	12A7B	9/6	77	6/-	DF66	15/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3V4	6/8	6J8	12/6	12A7T	4/7	80	6/8	DF91	2/9	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
4D1	4/-	6K6	5/6	12A7B	9/6	85	15/-	DF96	6/3	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
3R4G	9/-	6K7G	1/6	12A7X	4/9	83V	18/5	DF97	7/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
574	8/-	6K7GT	4/8	12B4B	6/6	85A1	5/6	DE90	15/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
4G4	4/3	6K8	6/6	12B4B	6/6	85A1	5/6	DE90	15/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
5V4G	7/6	6K8GT	7/9	12B4B	6/6	85A1	5/6	DE90	15/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
5Y3GT	4/6	6K20	13/6	12E1	17/-	90AV	6/7/8	DE77	4/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
5Y4	9/6	6L1	9/6	12RHGT	1/6	90C9	37/8	DEH1	25/11	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
5Z3	19/5	6L6G	6/8	12J5GT	2/6	90C9	42/-	DEH1	25/11	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
5Z4G	7/6	6L8	12/6	12K17	7/6	90C11	37/8	DEH1	25/11	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
630L3	8/6	6L7GT	6/8	12K5	17/6	150B2	18/6	DK32	8/9	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6A7	9/-	6L17	12/6	12K9GT	3/9	150C2	5/-	DK40	18/3	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6A8G	7/-	6L18	7/6	12K0KT	9/6	151	13/-	DK91	4/9	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6A87	4/-	6L19	9/9	12K7GT	3/8	152BT	34/11	DK92	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6A8T	3/-	6L20	6/6	12K8	7/6	152BT	34/11	DK92	6/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6A95	2/9	6L13	7/6	12K4T	4/7	180T	10/8	DL33	7/3	Armer.	2/8	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6
6A97	6/-	6L120	12/6	12M07	3/6	301	20/-	DL35	6/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6A95	8/6	6N7GT	5/-	12M87	3/6	302	10/8	DL36	6/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6AK5	5/-	6P1	18/6	12M7	5/6	303	10/8	DL36	6/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6AK8	19/6	6P25	9/-	12M87	5/6	304	18/-	DL36	6/6	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6AK8	6/-	6P28	18/6	12M87	5/6	305	13/6	DL37	15/2	EL50	8/6	ME1	16/10	64/-	U91	17/6	GT111	8/6		
6AL5	2/3	6P28	11/6	12M87	5/6	306	13/6	DL37	15/2	EL50	8/									

Newnes Great Profit Maker!

COMPLETE IN 6 VOLUMES

- Guarantees Quicker Servicing and Satisfied Customers



Radio & TV Servicing

DATA FOR MODELS RIGHT BACK TO 1956

Here is all the technical information you need for quicker repair work now and for years ahead! The set provides full servicing data and specialist repair methods for the popular models marketed by 70 principal makers and companies—current models and back to 1956. It is essential to the shrewd repair man because people are keeping their sets longer. If you have never before examined this famous reference work now is your opportunity. See it for a week on free examination without obligation to buy.


TELEVISION • RADIO • RADIOGRAMS • CAR RADIOS
TAPE RECORDERS • RECORD REPRODUCERS

DATA FOR ALL THESE MAKES—Alba, Ambassador, Argosy, Armstrong, Baird, Beethoven, Berec, Brayhead, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, Emerson, E.M.I., Emisonic, English Electric, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Portogram, Pye, Radiomobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Sony, Sound, Spencer-West, Stella, Stereosound, Strad, Ultra, Vidor, Walter, Webcor. Includes special 50-page supplement of older models.

PLUS 2 YEARS' FREE POSTAL ADVISORY SERVICE

More than 4,000 Circuits and Component Layout Diagrams • 2,250 Popular Models

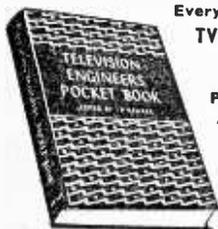Use it **FREE** for 7 days to prove its value



Every purchaser receives a Free copy of
TV ENGINEERS POCKET BOOK
(Value 12/6)

272 PAGES : OVER 200 PRACTICAL ILLUSTRATIONS

An invaluable companion to your set for on-the-spot repairs

Concise information on installing, fault-tracing and repairing, servicing equipment, alignment, etc.

Hurry - Post Coupon To-day

George Newnes Ltd., 15-17 Long Acre, London, W.C.2.
Send me Newnes RADIO AND TELEVISION SERVICING (in 6 volumes) and TV ENGINEERS POCKET BOOK without obligation to purchase. I will return them in 8 days or send 15/- deposit 8 days after delivery, then twenty monthly subscriptions of 15/-, paying £15/15/- in all. Cash price in 8 days is £15.

If you are under 21 your father must complete this coupon. If married woman your husband must complete.

Full name _____ { Mr. / Mrs. / Miss }
(BLOCK LETTERS)
Address _____

Occupation _____

Signature _____

Tick ✓ where applicable

The address on left is—

My Property	<input type="checkbox"/>
Rented unfurnished	<input type="checkbox"/>
Parents' Home	<input type="checkbox"/>
Furnished Accom.	<input type="checkbox"/>
Temporary Address	<input type="checkbox"/>

(RV)533/76



GO TRANSISTOR WITH SINCLAIR

BOOKS • CIRCUITS • TRANSISTORS • EQUIPMENT

THE WONDERFUL SINCLAIR RANGE OF TRANSISTORS

M.A.T.'s

MICRO-ALLOY TRANSISTORS

MATs give extremely high power gains at all levels of collector current and voltages, and at frequencies from A.F. to 100 Mc/s. They may be used in place of ordinary transistors to give greatly improved performance in any circuit.

- MAT 100 High gain low level type 7/9
- MAT 101 Extra high gain, low level type 8/6
- MAT 120 High gain, medium and high level type 7/9
- MAT 121 Extra high gain, medium and high level type 8/6

★ NEW FOR V.H.F. AND U.H.F. THE ADT.140

This new Sinclair transistor, only $\frac{1}{4}$ " high x $\frac{1}{4}$ " dia., is specially designed for F.M. and T.V. applications and for V.H.F. and U.H.F. transmitters and receivers. Made by the alloy-diffused process, the ADT.140 has a typical alpha cut-off frequency of 400 Mc/s. Power gain is 15dB at 100 Mc/s and 9dB at 200 Mc/s.

Price 15/-



THREE IMPORTANT BOOKS

Each of these books is crammed with invaluable information, tested circuits and layout diagrams for receivers and equipment using MATs and the new ADT.140.

- "22 Tested Circuits using Micro-Alloy Transistors" 5/6 post free
- "Tested Short Wave Receivers using MATs" 5/6 post free
- "Tested Superhet Circuits for Shortwave and Communication Receivers, using MATs" 6/6 post free

Special Offer to "Practical Wireless" readers ALL Three Books for

15/-


Post free

NOW—THE SINCLAIR MICRO INJECTOR — Fascinating to build

Smaller, more versatile, covers 1 Kc/s to 30 Mc/s

PERFECT FOR FAULT FINDING AND SERVICING ALL RECEIVERS AND AMPLIFIERS

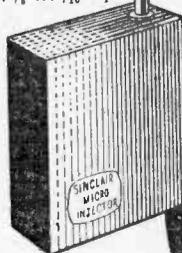Size of Case only $1\frac{1}{4}$ " x $1\frac{1}{10}$ " x $\frac{1}{2}$ "



SINCLAIR MICRO INJECTOR

TRACE THAT FAULT



Using two MICRO-ALLOY TRANSISTORS the Sinclair Micro-Injector is a precision sub-miniature instrument which generates and injects a test signal into any part of a receiver or amplifier at any frequency from 1 Kc/s to 30 Mc/s. By this means the location of any fault can be rapidly found.

The Sinclair Micro-Injector is powered by a 6d. standard battery which will last for about 6 months. Its size is $1\frac{1}{4}$ " x $1\frac{1}{10}$ " x $\frac{1}{2}$ " excluding the probe which is $\frac{3}{16}$ " long, by far the smallest instrument of its kind available. Assembly is extremely simple and will take even a beginner only half an hour. Clearly illustrated building instructions are provided together with operating instructions.

Total cost including all parts, MAT Transistors, printed circuit board, plated probe, and case in royal blue with gold trim.

27/6


SINCLAIR MICRO AMPLIFIER OUTPERFORMS AMPLIFIERS 20 TIMES LARGER

This fantastically small, powerful amplifier is smaller than a 3d. piece. With a frequency response from 30 to 50,000 c/s \pm 1 dB, and power gain of 60dB (1,000,000 times) it becomes a valuable tool in the hands of the keen experimenter as well as providing an excellent sub-miniature hi-fi amplifier with an output suitable for any earpiece or even loudspeaker. With MAT Transistors, brand new micro-miniature quality components and micro-printed circuit.



28/6

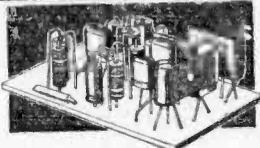★ WITH DETAILED INSTRUCTIONS, APPLICATIONS, DATA AND CIRCUITRY.




FREE with every amplifier, circuits showing how to use it with low and high impedance pick-ups, microphones, tapeheads in various radio circuits, transmitter circuits, in guitar amplifier, as a mono or stereo hi-fi system, intercom, etc.
BUILT AND TESTED **59/6**

SINCLAIR TR.5 COMBINED PRE-AMPLIFIER AND HALF-WATT POWER AMPLIFIER

- Embodies the latest circuitry techniques to produce a perfectly clean half watt of audio power even from very low output sources such as low-impedance tape recorder heads, pick-ups and microphones. Each amplifier is supplied ready built and unconditionally guaranteed.
- CIRCUIT—5 matched transistors and temperature compensating diode in a transformerless complementary-symmetry configuration.
- POWER OUTPUT—500 mW undistorted into a 16 ohm speaker.
- SENSITIVITY—0.5 mV.
- POWER GAIN—80 dB (100 million times).
- FREQUENCY RESPONSE—50 c/s to 20 Kc/s \pm 3dB.
- SIZE—2 1/2" x 1 1/2" x 1 1/2".
- POWER REQUIREMENTS—10 mA quiescent and 150 mA peak from 9V. battery or power supply.

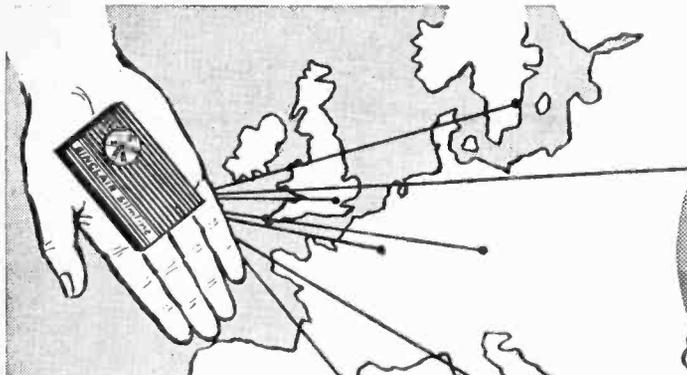ALL EQUIPMENT UNCONDITIONALLY GUARANTEED
SINCLAIR radionics LTD
69 HISTON ROAD, CAMBRIDGE



EUROPE IN THE PALM OF YOUR HAND with the wonderful *Sinclair Slimline* MICRO-RADIO RECEIVER

- ★ NEW improved solid dielectric tuning capacitor
- ★ FULL coverage of medium waveband
- ★ USES Micro-Alloy Transistors throughout (MATs)
- ★ TRUE high-fidelity performance with quite incredible volume and quality of reproduction
- ★ EXTREMELY SENSITIVE—pulls in literally dozens of continental stations right across the band
- ★ IDEAL for use in car or train where the tremendous volume is really valuable
- ★ COMPLETELY self contained; uses internal ferrite rod aerial and a PP5 battery
- ★ ELEGANT royal blue case with gold trim and calibrated dial

TOTAL COST

49/6

WITH FEATHERWEIGHT QUALITY EARPIECE

Size 2 1/2 x 1 1/4 x 3/8 in.

Comprises brand new sub-miniature components, printed circuit board, genuine MAT transistors, case, earpiece and well illustrated easily followed instructions.

FULL SERVICE FACILITIES ALWAYS AVAILABLE

THOUSANDS ALREADY IN USE

... and thanks to all the hundreds of enthusiasts who have written to us about the Slimline.

Here are still more typical examples of what constructors write

"The case is superbly designed ... I have built several other kits and none have been truly successful, but yours is a winner." A.E.C., Leicester.

"I completed assembly of your Sinclair Slimline and I'm really delighted with the quality of reproduction. It's the best small transistor set I have ever heard." J.D.G., Coventry.

"The performance in a car was remarkable!" F.G.P., Bedford.

"Was honestly amazed at the performance, especially the tone." F.B.T.H., London, S.W.11.

BUILD IT IN A COUPLE OF HOURS !

Success is assured before you begin to build, even if you are new to receiver construction, and the finished result is a delight to experienced builder and beginner alike.

★ The originals of these and countless other unsolicited testimonials may be seen at our offices at any time during business hours.

POST TO-DAY

To SINCLAIR RADIONICS LTD., 69 HISTON RD., CAMBRIDGE

PLEASE RUSH.....SLIMLINE(S)

FOR WHICH I ENCLOSE £.....:.....s.....d.

NAME.....

ADDRESS.....

Block letters please



SEND FOR OUR 1963/4 COMPONENTS CATALOGUE

48 pages of valves and accessories. Send 1/- in stamps for your copy. Trade catalogue also available, for which please attach your business letter heading.

CHASSIS

Aluminium Undrilled with Reinforced Corner, available in the following sizes:

6in. x 4in. x 2 1/2in.	4/6 each
8in. x 6in. x 2 1/2in.	6/3 each
10in. x 7in. x 2 1/2in.	7/3 each
10in. x 7in. x 2 1/2in.	5/9 each
12in. x 5in. x 2 1/2in.	6/9 each
12in. x 8in. x 2 1/2in.	8/6 each
14in. x 3in. x 2 1/2in.	6/- each
14in. x 9in. x 2 1/2in.	12/- each
16in. x 6in. x 2 1/2in.	9/3 each
16in. x 10in. x 2 1/2in.	14/- each

All are four-sided—ideal for radio receivers, amplifiers, power packs, etc.

GRAMOPHONE UNITS

BSR TU12 unit, with Mono TC8H cartridge, £3.19.6.
 BSR GU7 unit, with TC8M or TC8H cartridge, Mono, £4.15.0.
 BSR GU7 unit, with TC8S cartridge, stereo, £5.5.0.
 Garrard Autoslim, automatic, with GC8 Mono cartridge, £7.15.0.
 Garrard Autoslim, automatic, with EV26 Stereo cartridge, £8.10.0.
 Garrard Autoslim de luxe, with GC8 Mono Cartridge, £11.5.0.
 Garrard Autoslim de luxe, with EV26 Stereo Cartridge, £12.0.0.
 BSR Monarch UA14, with TC8 Mono Cartridge, £6.6.0.
 BSR Monarch UA14 with TC8S Stereo Cartridge, £7.7.0.
 BSR Monarch UA16, with TC8 Mono Cartridge, £6.19.6.
 BSR Monarch UA16, with TC8S Stereo Cartridge, £7.19.6.

METAL RECTIFIERS

Alpha Range of Guaranteed Bridge Rectifiers suitable for Battery Chargers 6 and 12 volt output:

2 amp.	7/-
4 amp.	12/6
6 amp.	15/6

ADAstra 3-3 AMPLIFIER

Specification: Controls—Volume, Treble, Bass with on/off. Valves—EZ80 rectifier, ECL86 amplifier and output. Output power—3 watts at 3.5 ohms impedance. Input sensitivity—200 millivolts. Frequency response—75-20,000 c/s. Hum and noise—70 dB. Feedback—10 dB. For 200-250 volts A.C. 50 c/s. Well finished in blue with a smart panel with gold markings. Soundedly made of good components and performs exceptionally well for the price, £4.19.6.

REPANCO MINIATURE TRANSISTOR COMPONENTS

An entirely new range of Miniature Transistor Transformers, size 3/16in. x 3/16in. x 3/16in., high permeability nickel iron core. Suitable for printed circuits.

TRANSISTORS AND DIODES

Model	Price
Mullard	
AC107	14/6
AD140	25/-
AF102	27/6
AF104	11/-
AF115	10/6
AF116	10/-
AF117	9/6
AF118	20/-
AF124	10/-
AF125	10/6
AF126	10/-
AF127	9/6
OC1EV	35/-
OC19	25/-
OC26	25/-
OC42	9/3
OC44	9/3
OC44M	9/-
OC45	9/-
OC45M	9/-
OC70	6/6
OC71	6/6
OC72	8/6
2-OC72	16/-
OC74	8/-
OC75	8/-
OC78	8/-
OC81	8/-
OC81M	8/-
OC82	10/-
OC83	6/-
OC170	9/6
OC171	10/6

DIODES

BY100	13/-
OA70	3/-
OA79	3/-
OA81	3/-
OA90	3/-
OA91	3/-
OA95	3/6
OQ210	9/6
GEX34	4/-
GEX35	4/-
GEX36	10/-

SETS OF TRANSISTORS

Set 1. Comprising OC44, 2 x OC45, matched pair OC81 ... 32/6 set
 Set 2. Comprising OC81 Driver, matched pair OC81 ... 15/6 set

TT45. DRIVER TRANSFORMER

For double ended push-pull output stage. Ratio 4.5 to 1 + 1. Secondaries bifilar wound, 5/-.

TT46. PUSH-PULL OUTPUT TRANSFORMER

For double ended output matching to a 3 ohm speaker. Ratio 4 + 4 to 1, 5/-.

TT47. DRIVER TRANSFORMER

For single ended output stage matching to a 35 ohm speaker. Secondaries bifilar wound. Ratio 4.5 to 1 + 1, 5/-.

TT49. L.F. TRANSISTOR COUPLING TRANSFORMER

Suitable for interstage coupling in simple L.F. amplifiers. Ratio 4.5 to 1, 5/-.

MINIATURE DOUBLE TUNED I.F. TRANSFORMERS

455 to 475 kc/s. Can size 3/16in. sq. x 1/16in. Ferrite pot and core construction. Suitable for 1st and 2nd I.F.T. giving better selectivity than single tuned I.F.T's. Can be used with normal R.F. transistors. Extra sensitivity when used with diffused alloy 4 element transistors. (Boxed with circuit.) Coil ratios: Total primary to collector tap—2.5 to 1. Collector tap to secondary tap—7.3 to 1, 6/9.

PAXOLIN SHEET

Paxolin sheet 3/16in. thick, 6 x 6in., 1/- each
 Paxolin sheet 1/4in. thick, 12 x 6in., 2/- each
 Paxolin sheet 1/4in. thick, 12 x 12in., 4/- each

EMPTY PLASTIC TAPE SPOOLS

Empty tape spools 3in.	1/6 each
Empty tape spools 4in.	2/- each
Empty tape spools 5in.	2/- each
Empty tape spools 5 1/2in.	2/6 each
Empty tape spools 7in.	3/- each

PERSONAL EARPHONE

A really sensitive dynamic earphone of exceptionally fine quality. Provides clear reproduction of music as well as speech. Fully guaranteed and complete with ear insert, 3 feet cord, sub-miniature plug. Model C.R.5. Crystal Earpiece, high imp. Model MR-4. Magnetic Earpiece, low imp. 6/- each.

VALVES

DK96	7/9	UL41	7/6
DAF6	6/9	UABC80	7/6
DF96	6/9	EY51	8/-
DL96	6/9	PL81	8/6
ECC81	5/-	PL36	9/6
ECC82	5/6	PCL83	9/6
ECC83	6/-	PCF80	9/6
ECC84	7/6	PCL82	9/-
ECC85	7/6	6V6G	4/-
ECH81	7/6	6K7G	2/-
EBC41	7/6	6AM6	3/6
EF41	7/6	EB91	3/-
ECL80	7/6	1R5	5/3
PCF80	7/6	1T4	3/6
PCC84	7/6	1S5	4/6
PL82	7/6	3S4	5/6
PY83	7/6	6K8G	4/9
UABC80	7/6	6L6G	7/6
UAF42	7/6	6Q7G	5/6
UBF80	7/6	6X5G	5/-
UCH42	7/6		

TERMS: Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

ALPHA
 RADIO SUPPLY CO.

103 LEEDS TERRACE
 WINTOUN STREET
 LEEDS 7

CRYSTALS & COMPONENTS LTD

TEL: TEM 1189 Dept. P.W.12 2, 4 EARLHAM STREET, W.C.2.

Near Cambridge Circus. A few minutes' walk from Leicester Square or Tottenham Court Road Underground Stations
 HOURS OF BUSINESS: 9 to 6. Saturdays 9 to 1. OPEN ALL DAY THURSDAY

TYPE 38 TRANS/RECEIVERS

Brand new Operating on 7.4 to 9 Mc/s. Trans/Receivers. Complete with headphones, throatmicrophone, function box and aerial rods. Operate on 150 volts HT & 3 volts LT dry batteries. Complete less batteries and not tested. 42/6 per set plus 6/8 post. Or £4 per pair plus 10/- post and packing.



L.T. TRANSFORMERS

Pri.: 240 volts. Output 6.3 volts 5 amps. 8/6. post 2/6. Pri.: 240 volts. Output 17 volts 1 amp. 9/6. post 2/-.

H.T. TRANSFORMERS

Type (350/120) Tapped 200/250 V. Input 350-0-350 V. 120 mA. 6.3 V. 3i amp. 5 V. at 2 amps. 18/6. P. & P. 3/6. Type 5K Pri. 200/250 V. Output 350/0/350 V. 350 mA. 5 V. 3 amps. Tapped 4 V 2 V. 2 amps. 10 kV. Ins. 20 V. 1 amp. 7.5 V. 1 amp. 5 kV. 5 mA. Price 25/-. Post & Packing 6/-.

SPECIAL H.D. TRANSFORMERS

50 volts 10 amps. transformers. 250 volts input. Brand new and boxed. Conservatively rated. 55/- each. Carriage 7/8.

A GEARED ELECTRIC MOTOR

FOR ONLY 9/6. Post and Packing 2/6. Due to bulk purchase we are able to offer these 24 V. Rotary Convertors at this fantastic price. Easily modified for mains operation (full simple conversion details supplied). Complete with 400 to 1 reduction gearbox.

METERS

0-1 mA Meters, moving coil 3in. diameter surface mounting by Sangamo Weston. 30/- plus 2/- p. & p.
 0-750 Microammeters. Brand new, blank scale. Flush mounting by 3in. diam. Moving coil. 45/6 each plus 2/- P. & P.
 0-50 mA meters. Brand new 2in. diameter flush mounting with square flange. M.C. 12/6 plus P. & P. 1/8.
 0-150 mA Meters. Brand new 2in. dia. flush mounting with square flange. M.C. 12/6. P. & P. 1/8.

CRYSTALS!!!

LARGE RANGE OF 10N, 10N4, FT243, FT241 CRYSTALS ALWAYS IN STOCK

Send stamped and addressed envelope for our free, comprehensive list.

FIELD STRENGTH METERS

100-150 Mc/s. Contains 0-1 mA meter. 150 valve, chrome telescopic aerial, etc. New condition in black crackle case. Operates on 1.5 V. and 90 V. batteries. Dimensions: 7 x 7 x 7in. 45/-. P. & P. 2/8.

SPECIAL OFFER OF 6in. METRO-VIC TEST METERS ALL AT ONE PRICE 25/- FOR CALLERS ONLY

including
 0/20/50 mA, 0/100 mA, 0/15 mA, 0/500 mA, 0/50 mA, 0/300 volts D.C., 0/30 volts D.C., 0/50 volts, 0/100 volts, 0/5 Kv. 0/500 volts, and many others. All in perfect condition (surface mounting).

E.H.T. TRANSFORMERS

E.H.T.1. Input 200/250 volts 50 C/s. Output 2kV. 10 mA 4 V. 1A. 0-2-4V. 1.5A. 3.5 kV. P. & P. 5/-.
 E.H.T.2. Input 200/250 volts 50 C/s. Output 2.5 kV. 10 mA. 6.3V. 3A. 2V. 1.5A. 3.5 kV. D.C. Wkk. 22/6. P. & P. 5/-.
 E.H.T.4. Input 200/250 volts 50 C/s. Output 2,000V. 15 mA. 4 V. 1.5A. 0-2-4V. 2A. 29/6. P. & P. 5/-.

WIRELESS SET NO. 19


Complete with original power supply unit for 12 volts input. Transmitter/Receiver covering 2-8 Mc/s and V.H.F. and 240 Mc/s. 6 valve superhet receiver and 6 valves in Transmitter. Using I.F. of 465 Kc/s. For voice and C.W. In good condition not tested. £4.17.6. Plus £1 packing and carriage. Microphone and headset for this set 17/6 plus 2/6 post and packing. 19 Set Variometers, 17/6 plus 2/6 post and packing. Booklet with circuits and instructions free with set or separately 2/8 post paid.

BARGAIN PACKS

Assorted packets of 100 brand new Resistors including miniature and high stab. 12/6 POST PAID. All useful values. Condensers, 100 assorted, including mica, ceramic, metal tubular, etc. 15/- post free 12 Assorted Potts. All new and useful sizes 12/6, post paid. Components Package containing 3 useful size ports, 3 wafer switches, 50 assorted resistors and condensers including electrolytic and ceramics. AS NEW 15/- plus 2/- P. & P.

B.C. 221 FREQUENCY METERS

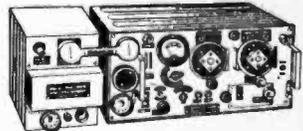Every one tested and working in perfect order. Exterior slightly soiled. From £12.10.0. Packing and carriage 17/6.



Control box for 19 set. 10/- plus 2/- post and packing.

VIBRATORS

6V. 4 pin. 3/8 plus 1/6 P. & P.
 6V. 7 pin. 3/8 plus 1/6 P. & P.
 12V. 7 pin. 4/6 plus 1/6 P. & P.

DECCA X.M.5 L.P. Pick-up Heads

Brand New 8/6. P. & P. 1/-.

TF.144G STANDARD SIGNAL GENERATOR

85 Kc/s to 25 Mc/s. Fully serviced and in perfect condition. £38 post paid.

VIBRATOR POWER SUPPLY UNIT

6 volts D.C. input, 230 volts 100 mA A.C. output and 6 V. L.T. out. Fully smoothed, with OZ4 rectifier valve. Brand new in steel case with pilot light, on/off switch and Silydlok fuse on front panel. Measures 8 1/2 x 6 x 5 1/2in. 39/6 plus 6/6 post and packing.

VARIABLE AIR-SPACED CONDENSERS

150 pFd with 1in. spindle, 4/8 each.
 75% 73 pFd with 1in. spindle, 4/8 each.
 100 pFd with 1in. spindle, 2/6 each.
 50 pFd pre-set, 2/- each.
 50 pFd pre-set, 1/6 each.
 4 Gang H.R.O. Variable 390 pFd. 12/6 each.

TYPE 68 TRANS/RECEIVER

3 to 5.2 Mc/s. Portable station with range up to 10 miles under good conditions. In very good condition, complete with valves hand mike and aerial rods. 70/- plus 8/6 carriage and packing. Require 150V. H.T. 3V. L.T. and 9V. G.B.

MICA CAPACITOR

In cast metal and ceramic .0002 Mfd 6000V. working, 2/6 plus 1/6 P. & P. each.

TERMS OF BUSINESS

CASH WITH ORDER. Handling charge of 1/6 on all orders under 20/- where P.P. is not otherwise stated. Postage charges indicated apply to U.K. only. C.O.D. orders min. £1.

WOBBULATOR FREQUENCY MULTIPLIER

Band 1. Channels 1-13. with 50 micro/ammeter and 0-80 dB attenuator. 29. P. & P. 10/-.

TEST SET 193A

For testing quartz crystals of 1in. and 4in. pin spacing and BTG based crystals, 240V and 30V A.C. input including 0-100 micro-amps, 3 1/2in. scale meter, indicator light and variable control. 19in. rack mounting but completely enclosed. AS NEW. £4.15.0 carr. paid.

ON VIEW IN OUR SHOP FOR CALLERS ONLY. VERY LARGE RANGE OF TEST GEAR including

Signal generators. Decade resistance boxes. Pen recording Voltmeters and thermometers. Electronic Tuning Forks, etc.

SILICON RECTIFIERS

Westinghouse 1,000 P.I.V. 500 mA. 9/- each; 800 P.I.V. 500 mA. 7/6 each. 400 P.I.V. 200 mA. 3/6 each.

TECHNICAL TRAINING in radio television and electronics

Whether you plan to have your own business, to become an electronics engineer, to take up a career in industry, or to brush-up your knowledge and study new developments, transistors, etc., an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.

EXAMINATION COURSES FOR:—

C. & G. Radio and TV Servicing Certificate (R.T.E.B.)

C. & G. Radio Amateurs' Exam. (Amateurs' Transmitting Licence) P.M.G. Certificates in Radiotelegraphy

British Institution of Radio Engineers, C. & G. Telecom. Technician's Cert. Gen. Cert. of Education etc.

LEARN AS YOU BUILD

Practical Radio Servicing Course

A basic course in radio electronic and electrical theory backed by thorough practical training. You build radio receivers, signal generators and multimeter.



Post this Coupon TODAY! for FREE book on careers in Radio, and full details of other I.C.S. Courses
Member of the Association of British Correspondence Colleges

INTERNATIONAL CORRESPONDENCE SCHOOLS
(Dept. 171), Intertext House, Parkgate Road, London, S.W.11.

Please send book on _____

Name _____ Age _____
(Block Letters Please)

Address _____


Occupation _____ 10.63

INTERNATIONAL CORRESPONDENCE SCHOOLS

HARVERSON SURPLUS CO. LTD. ▶

For address see opposite page

3-VALVE AUDIO AMPLIFIER. MODEL HA34

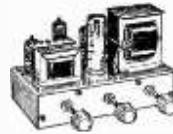

Designed for Hi Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates EOC83, EL84, EZ80 valves, heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feed back line. Peak output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves etc. wired and tested for only **£4.50 P. & P. 4/-**.

TWO VALVE AMPLIFIER similar to above but using ECL82 and EZ80, with tone and volume controls. Output 2 watts. PRICE 75/- P. & P. 4/-

SPECIAL OFFER! MARCONI QUARTZ CRYSTALS TYPES ZHB

Glass encapsulated, 2 wire lead out. Size 1 1/2 in. high x 1/2 in. dia. Following frequencies (Kc/s) only available:

- 13521, 13583, 13646.
- 13708, 13771, 13833.
- 13896, 13958, 14021.
- 14083, 14146, 14206.
- 14271, 14333, 14396.
- 14459.

6/- each. P. & P. 1/- per crystal, 3 or more Post Free.

CALLERS SPECIAL

Through purchase of Electronics Manufacturing Company we have a large selection of extremely high grade

OUTPUT AND MAINS TRANSFORMERS

to suit all modern types of Hi Fi Amplifiers. Also a few quality

HI-FI EQUIPMENT CABINETS

suited for housing Hi Fi Equipment.

All available at Bargain prices

BRAND NEW CAR-RADIO AERIAL BARGAINS!

BY WELL KNOWN MAKER

Following types available for wing mounting; simple one hole fixing, all heavily chromed, telescopic and complete with coax plug and lead, **TYPE H51.** 3 section, open 43 1/2 in. closed 17 in., (List 32/6), OUR PRICE 22/-.

TYPE H52. 4 section, open 44 1/2 in., closed 2 in., length below wing 12 in., adjustable angle 0-26° (List 47/6), OUR PRICE 40/-.

TYPE H53. 5 section, open 41 in., closed 1 1/2 in., length below wing 9 in., adjustable angle 0-26°. Features a tamper-proof locking device, aerial cannot be extended without using special key provided. (List 57/6), OUR PRICE 50/-.

All aerials plus 2/6 P. & P.


Limited number available

TELEFUNKEN HI-FI STEREO AMPLIFIER



Model 882 with BALANCE CONTROL 110/250 v. A.C. input. 5 watt undistorted output (10 watts nominal). Size 12 x 9 x 2 in. Weight 9 lb. Complete with spec. and instructions. STILL ONLY £5.19.6 Carr. 7/-.

FEW ONLY!

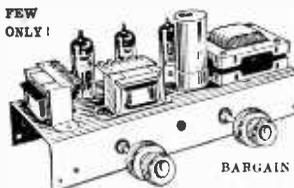

STEREO AMPLIFIER

Incorporating 2 ECL82's and 1 EZ80, heavy duty double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.

BARGAIN PRICE **89/6** P. & P. 5/-

SPECIAL PURCHASE!
TURRET TUNERS
 by famous maker.
 Brand new and unused.
 Complete with PC084 and PCF80 valves, 34-38 Mc/s I.F. Circuits for Channels 1 to 3 and 8 and 9. Circuit diagram supplied.
ONLY 25/- each. P. & P. 2/6.

F.M. TUNER HEAD



A permeability tuned tuner head by a famous maker, supplied without valve (EC085) and drum and spindle, 13/6, plus 1/9 P. & P. Valve 8/6 extra. Drum and spindle 3/8 extra.

GORLER F.M. TUNER HEADS
 10.7 Mc/s I.F.
 15/-, plus 1/9 P. & P. (EC085 valve, 8/6 extra.)

E.M.I. 4-speed Player and P.U.
FURTHER HUGE PURCHASE enables us to offer these **67/6** P. & P. 4/6.



Heavy 8 1/2 in. metal turntable. Low flutter performance 200/250V shaded motor with tap at 45 V for amplifier valve filament if required. Turnover 1.2/78 head.

RECORD PLAYER AMPLIFIER
 2 valve (E250, EC199). A.C. mains. 10 watts output, ready built, tested and complete with valves and output transformer. Size 7 1/2 in. w. x 2 1/2 in. d. x 5 1/2 in. h. 55/- P. & P. 3/- Suitable speakers: 6 in. 15/- P. & P. 1/6. 10 in. 25/- P. & P. 1/6.

4-SPEED PLAYER UNIT BARGAINS SINGLE PLAYERS
 TU12. £3.10.0. Carr. 8/6.
AUTO CHANGERS
 R.S.R. UA11. £6.2.6.
 Latest B.S.R. UA16. £7.2.6.
 Latest Garrard 'Auto-Slim' £8.17.0. Carr. 5/- on each.

LOOK OPPOSITE FOR MORE BARGAINS

HARVERSON'S F.M. TUNER Mk.1

● P.M. tuning head by a famous maker.
 ● Guaranteed non-drift.
 ● Permeability tuning.
 ● Frequency coverage 88-100 Mc/s. ● OA81 balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3 in. glass). ● Self powered, using a good quality mains transformer and valve rectifier.
 ● Valves used EC085, two EF80s, and E280 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 5 1/2 in. ● All parts sold separately. Set of parts if purchased at one time £5.10.6, plus 8/6 P.P. and insa. Circuit diagram and instructional 1/6 post free. Mark II version as above but complete with magic eye, front panel and brackets, £6.12.6. P. & P. 9/6.
 Mark III version as Mark I but with output stage (ECL82) and tone control. £7.7.0. P. & P. 9/6.
 Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I, 25/-, P. & P. 2/6. To fit Mark II, 17/6. P. & P. 2/6.

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 valve/half transistor superhet. ● Printed circuit panel (size 8 1/2 x 2 1/2 in.) ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite rod aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions.
 All parts sold separately. Set of parts if purchased at one time.

ONLY £4.5.0 P. & P. 2/6

35 OHM SPEAKERS
 Suitable for use with above.
 2 in. Goodmans. Ideal replacement for most pocket portables 8/6. 2 1/2 in. 10/6. 3 1/2 in. 12/6. 5 in. 17/6. 7 x 4 in. 21/-.
 E. & P. 1/6 per speaker.

Portable CABINET
 Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker, 25/-, P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET
 3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (med., long and aerial coupling). 28/6 complete, post 1/-.
 6 transistor printed circuit, board to match, 8/6, post 9d. Circuit diagram 1/6 extra.

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. This amplifier (which is used in a 30 gn. record player) employs EC085, EL84, E280 valves. Base, treble and volume controls. Complete with output transformer matched for 3 ohm speaker.
PRICE 69/6 P. & P. 3/6
DITTO. Mounted on board with output transformer and 6 in. speaker.
Complete at 89/6, P. & P. 4/6.


TRANSISTORS
 GET 15 (Matched Pairs) 15/-

OC71	5/-	PA A101	6/6
OC72	5/-	XA103	6/6
OC76	6/-	V1510p	12/6

Set of Mullard 6 transistors OC44, 2—OC45, OC81D matched pair OC81, 25/-, All Post Free

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1


● Peak output in excess of 14 watts. ● All standard British components. ● Built on printed circuit panel, size 6 x 3 in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (GET114 or 81 Mullard OC81D and matched pair of OC81 o/p). ● 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Completely easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately.

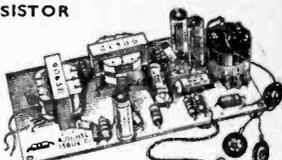

SPECIAL PRICE 45/-
P. & P. 2/6

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram also records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls and separate bass and treble controls are provided giving good lift and out. Valve line-up 2 EL84s, EC085, EF86 and E280 rectifier. Simple instruction booklet 1/6. (Free with parts).
All parts sold separately. ONLY £6.19.4 P. & P. 6/6

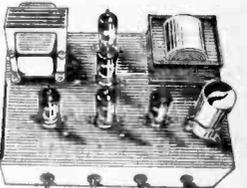

BRAND NEW 3 OHM LOUDSPEAKERS


2 1/2 in. 12/6; 5 in. 12/6; 6 1/2 in. 15/-; 8 in. 21/-, 10 in. 25/-; 12 in. 27/6.
 E.M.I. 2 1/2 in. tweeter 10/6
 5 in. x 3 in. by famous maker 10/6
 E.M.I. 1 1/2 in. x 8 1/2 in. high flux 32/6
 Rola Celestion approx. 9 in. x 6 in. middle register speaker also 15 ohm 12 inch. 30/-
 P. & P. up to 6 in. 1/6; over 6 in. 2/6 per speaker.

AMPLIFIER CARRYING CASES BRAND NEW.

Strongly made wooden construction, tough vyndie covered, complete with carrying handle. Overall size 13 1/2 in. wide x 8 in. deep x 8 in. high with sloping front panel. Weight only 4 1/2 lbs. Ideal for our 10/14 watt amplifier and many others.
BARGAIN PRICE 28/6
 P. & P. 4/-.

AMPLIFIER ON PRINTED CIRCUIT BOARD

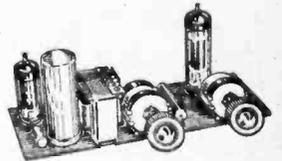Two valve. UY85, UL84 O.P. trans., use with 80 volt tap off motor, 39/6.
 P.P. 2/6 on above. Dropper res. for filaments if required. 2/6.



B.S.R. AUTO UNITS
 180 v. Suitable for use with above. (Slightly noisy) £4.4.0.
LARGE CABINET Suitable for above two items. Complete with 3 ohm speaker. £8.9.6. Carr. 6/-.
Superior CABINET Similar to above to take 8 x 5 in. speaker, with motor board, will accommodate BSR UA14 or UA16. £8.9.6. Carr. 6/6. Speaker 15/- extra. P. & P. 1/6 extra.

SPECIAL BARGAIN OFFERS!

MAINS TRANSFORMERS. Tapped Primary, 4 wave or Bridge Rectifier. Secondary 250 v. at 75 mA 6.3 volts at 2 amps. 10/6 each. P. & P. 3/-.
TWO GANG .0005 TUNING CONDENSER. Geared precision reduction drive. Size 2 1/2 x 2 1/2 in. Brand new and unused. 3/6 each. P. & P. 1/-.
WOUND TRANSFORMER. Impregnated and fully shrouded. Size 4 1/2 x 3 1/2 x 2 1/2 in. Weight 8 lbs. Tapped primary 205, 225, 245V. Electrostatic screen. Output 360-0-360 v. at 130 mA D.C. plus 1050 v. half wave at 3 mA D.C. 6.8 v. at 3.5 amps, centre tapped 6 v. at 2 1/2 amps and 6.3 v. at 6.5 amps P.H.C. 6.3 v. 1.25 amp. P. & P. 5/-.
CARBON MIKE INHERITS. Brand new, 2 1/2 in. dia. 3/6. P. & P. 9d.
ELECTROSTATIC H.F. TWEETERS. Type L.S.H. 15 Size 3 x 3 in., 2/6 each, plus 9d. P. & P.
MIDGET 2 GANG CONDENSERS. Capacity 185 and 100 pF. Polystyrene case with built-in trimmer. Size 1 x 1 1/2 x 1 1/2 in. Not used but removed from H.F. Boards. Two for 9/-, plus 1/- P. & P.
ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity 18/6. P. & P. 1/6.
TSL CRYSTAL STICK MIKE. Listed at 45/-. Our price 18/6. P. & P. 1/6.
TRANSISTOR DRIVER and O/P TRANSFORMERS. (Tapped 5 ohm and 15 ohm output) plus 4 suitable Transistors giving approx. 1 watt output 30/-. P. & P. 2/-.
3 PUSH-BUTTON TRANSISTOR SWITCH. D.P.—D.T. Each Switch 5/8 and 1/- P. & P.
ACOS GP66/1 T/O MONO CRYSTAL CARTRIDGE. Complete with carbide stylus and mounting bracket. Limited number only at 12/6. P. & P. 1/-.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19. CHERRYWOOD 3985/6

Open all day Saturday Early closing Wed., 1 p.m.

A few minutes from South Wimbledon Tube Station. (Please write clearly)
 PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEA ORDERS CHARGED EXTRA. (S.A.E. ALL ENQUIRIES)

TAPE DECKS
COLLARO STUDIO DECK
 £10.10.0 plus 5/6 carr. and ins.
B.S.R. MONARDECK
 (Slightly noisy) 3/6 in. per sec., simple control, uses 5 1/2 in. spools. £8.15.0 plus 5/6 carr. and ins. (Tapes extra on both).

SPEAKER & CABINET FABRICS
 Oatmeal fabric for speaker or cabinet or Red resin for cabinet 5 1/2 in. wide, 12/6 per yard length. (Minimum order). P. & P. 1/6.

Stern's

MULLARD DESIGNS

COMPLETE KITS OF PARTS

MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifiers requiring input up to 250mV. Incorporates 5 input Channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 160 c/s. low pass filter 5-9 Kc/s. Totally enclosed in case size 11 1/2" x 4 1/2" x 4".



KIT OF PARTS £10.0.0 ASSEMBLED & TESTED £13.13.0
(Carr. & Ins. 5/-).

MULLARD "5-10" MAIN AMPLIFIER



For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained. SPECIFIED COMPONENTS AND MULLARD VALVES including PARMEKO MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer. **COMPLETE KIT (PARMEKO Output Trans.) ASSEMBLED AND TESTED £10.0.0**

ABOVE Incorporating PARTRIDGE OUTPUT TRANS. £1.6.0 extra.

THE MULLARD 510/RC AMPLIFIER

The popular complete "5-10" incorporating Passive Control Unit providing up to 10 watts high quality reproduction with input of 600 mV. Specified components and new MULLARD VALVES. Includes PARMEKO MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE Output Transformers. Surplus Power available for Tuner.




COMPLETE KIT £12.0.0 ASSEMBLED AND TESTED £16.0.0
(Carr. & Ins. 7/6).

With PARTRIDGE OUTPUT TRANS. £1.6.0 ex.

THE MULLARD 33/RC

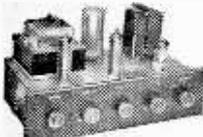A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN.



KIT OF PARTS £8.8.0 ASSEMBLED AND TESTED £11.10.0

Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. Switched inputs for 78 and ECL85 Valve, separate BASS and TREBLE controls and produces up to 3 watts undistorted output. (Carr. & Ins. 3/6).

THE "MONO-GRAM"

A small Amplifier of genuine high quality performance. Incorporates MULLARD controls and produces up to 3 watts undistorted output. (Carr. & Ins. 3/6). **Kit of Parts £4.10.0 Assembled and Tested £6.0.0**



Perfectly suited for Portable Installations for which purpose we offer PORTABLE CASE (£3.10.0, the AMPLIFIER (Kit) and 8" x 5" SPEAKER (£1.0.0). All for **£9.0.0**

Alternatively with ASSEMBLED AMPLIFIER. **£10.0.0** (Carr. & Ins. 5/-). The Case quoted above will accommodate some 4-speed Single Record Units. A larger model is available for extra 10/-. With this equipment a COMPLETE PORTABLE RECORD PLAYER can be built for **£14.0.0**



MULLARD FOUR CHANNEL MIXING UNIT

Self powered Cathode follower output, incorporates two inputs for CRYSTAL MICROPHONES, one for CRYSTAL PICK-UPS and a fourth for Radio or Tape. **KIT OF PARTS £8.8.0 ASSEMBLED AND TESTED £11.10.0** (Carr. & Ins. 5/-). Alternative Model I/L provides for one input matched for moving coil or ribbon mike £11.7.0 extra.



ARMSTRONG

RADIOGRAM CHASSIS

We have the full range in stock. Prices range from £20.10.0. Full details are readily available.



Send S.A.E. for fully descriptive technical leaflets, or call at our showrooms and hear the equipment on demonstration.

MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard AMPLIFIERS but also perfectly suitable for other makes with input up to 250 mV. ★ Equalisation for the latest R.I.A.A. characteristics.



★ Input for Crystal Pick-ups and variable reluctance magnet types. ★ Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier. ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE Controls. **KIT OF PARTS £6.6.0 ASSEMBLED AND TESTED £9.10.0** (Carr. & Ins. 5/-).

PRICE REDUCTIONS

- (a) THE KIT OF PARTS to build both the "5-10" Amplifier and the 2-Valve Pre-Amplifier.... **£15.15.0** (Carr. & Ins. 3/6).
- (a) Assembled and Tested **£21.10.0**
- (b) THE KIT OF PARTS to build both the "5-10" Amplifier and the 3-Valve Pre-Amplifier.... **£19.10.0** (Carr. & Ins. 10/-).
- (b) Assembled and Tested **£25.10.0**
- With PARTRIDGE OUTPUT TRANSFORMER **£1.6.0 extra.**

HIGH FIDELITY LOUDSPEAKERS

WE STOCK THE COMPLETE RANGE BY GOODMAN'S, WHARFEDALE and W.B. STENTORIAN A few recommended examples

8 INCH TYPES	
GOODMANS "AXIETTE"	£5.5.7
W.B. HF 816	£5.19.8
WHARFEDALE "SUPER 8/RS/DD"	£6.14.2
10 INCH TYPES	
GOODMANS "AXIOM 10"	£6.5.11
W.B. MODEL HF 1016	£7.0.0
WHARFEDALE "GOLDEN 10/RS/DD"	£7.17.5
12 INCH TYPES	
GOODMANS "AXIOM 201" 15 watts	£10.7.0
GOODMANS "AXIOM 301" 20 watts	£14.10.0
W.B. MODEL HF 1214 15 watts	£10.5.8
WHARFEDALE "W12/RS"	£10.15.0
WHARFEDALE "Super 12/RS/DD"	£17.10.0
Carr. & Ins. on above 5/6 each.	

We are pleased to announce that all Stern's products are now available from

CLYNE RADIO LTD.

12 SUFFOLK HOUSE
GEORGE STREET, CROYDON

Telephone: MUN 3250

RECORD PLAYERS

THE COLLARO "JUNIOR" 4-speed single player with separate crystal pick-up	£3.10.0
THE NEW GARRARD "AUTOSLIM" 4-speed autochanger with crystal pick-up	£6.10.0
GARRARD "AUTOSLIM DE LUXE" 4-speed autochanger, incorporates transcription pick-up arm	£11.8.0
THE COLLARO "C60" 4-speed autochanger unit with Studio "O" pick-up	£6.19.6
B.S.R. Model UA14, 4-speed mixer autochanger with crystal pick-up	£5.19.6
The new GARRARD Model JHF High Quality Single Record Player fitted with the latest T.P.A. 12 pick-up arm and G.C.S. crystal Cartridge	£16.17.6
GARRARD Model S.R.P. 10 single record player fitted with high output crystal pick-up	£5.9.1
PHILIPS Model AG1016. A 4-speed player can be operated both manually and automatically. Suitable for Mono or Stereo operation .. Carr. & Ins. on each above 5/6 extra.	£12.12.0

Mk. 11 "Fidelity" FM TUNING UNIT

An attractively presented Unit incorporating MULLARD PERMEABILITY TUNING HEART and corresponding Mullard valve line-up. Very suitable to operate with our Mullard Amplifiers. **KIT OF PARTS £10.10.0 ASSEMBLED AND TESTED £14.5.0** Carr. & Ins. 5/-.

IF YOU ARE PLANNING TO INSTALL "HI-FI" and UNCERTAIN OF THE TYPE OF EQUIPMENT TO USE—OUR WIDELY EXPERIENCED TECHNICAL STAFF WILL WITH PLEASURE PUT FORWARD RECOMMENDATIONS—STATE TYPE OF INSTALLATION CONTEMPLATED AND APPROX. PRICE LEVEL. CREDIT SALE TERMS are available on all Equipment over £10.0.0. FULLY DESCRIPTIVE LEAFLETS are ready available—please advise items of interest and enclose S.A.E.

SPECIALISTS IN SOUND EQUIPMENT FOR OVER 25 YEARS

Stern's



MODEL CR3/S TAPE RECORDER

MODEL CR3/S incorporates the HF/TR3 Mk. II Tape Amplifier (described below) and the Collaro "Studio" Twin Track 3-speed Deck operating at 1 1/2 in., 3 in., and 7 1/2 in. speeds. Complete with microphone and 1,200 ft. tape.

KIT OF PARTS **£33.8.0**
ASSEMBLED AND TESTED **£43.0.0**

(Carr. & Ins. 15/- extra).

MULLARD "10+10" STEREO AMPLIFIER

A high fidelity design providing up to 10 watts (per channel). Superb reproduction frequency response flat to within 3db from 3 c/s to 60 Kc/s at 50 mV Total Harmonic Distortion at 10 watts 0.1%.

(a) THE ASSEMBLED MAIN AMPLIFIER (AS ILLUSTRATED) **£24.0.0**

(b) KIT OF PARTS **£20.0.0** (Carr. & Ins. 7/6).

Built to the highest technical standards and presented strictly to MULLARD'S specification. Two specially designed GILSON ULTRA-LINEAR OUTPUT TRANSFORMERS with 20% taps are used.

We can also supply the assembled MAIN AMPLIFIER only for operation with our DUAL CHANNEL PRE-AMPLIFIER; this provides a more versatile installation and is essential if a low output pick-up is to be used. When ordering specify loudspeaker impedance.

(a) THE ASSEMBLED MAIN AMPLIFIER AND ASSEMBLED DUAL CHANNEL PRE-AMP **£34.0.0**

(b) KIT OF PARTS for both Units **£27.0.0** (Carr. & Ins. 10/6).



STEREO TAPE PRE-AMPLIFIER

MODEL STP-1. For use with current TRUVOX, BRENNEL, or COLLARO "STUDIO" 1 and 1/2 track Stereo Decks. Incorporates Ferroxcube Oscillator, 4 speed Equalisation Signal Level Meter and separate Gain Controls. Includes separate Power Unit.

KIT OF PARTS **£22.0.0** (Carr. & Ins. 8/6). ASSEMBLED **£28.0.0**



TAPE PRE-AMPLIFIER MULLARD Type "C"

Suitable for most 1 track, Mono Tape Decks. Incorporates Ferroxcube Push Pull Oscillator, Treble Inductor and 3-speed Equalisation. Includes separate Power Unit.

KIT OF PARTS **£14.0.0** ASSEMBLED **£19.10.0** (Carr. & Ins. 7/6).



MULLARD TAPE AMPLIFIER

Based on Mullard's Type "A" design and suitable for most 1 track Mono Tape Decks. Incorporates Ferroxcube Treble Inductor, Gilson Output Transformer, and 3-speed Equalisation. Includes separate Power Unit.

KIT OF PARTS **£13.13.0** (Carr. & Ins. 7/6). ASSEMBLED **£19.0.0**



STERN'S "ADD-A-DECK"

A self contained Unit consisting of Garrard Deck and matched Preamplifier on one chassis. Provides full tape recording facilities and replays through Pick Up Sockets of Standard Radio receiver or Amplifier.

PRICE includes complete Tape Magazine. **£18.18.0** (Carr. & Ins. 10/-).



COMBINED PRICE OFFERS !!!

Includes small charge for special testing and PRECISE MATCHING OF THE ASSEMBLED PRE-AMPLIFIER (or Amplifier) to TAPE DECK

STP-1 (Kit) and "STUDIO" Deck	£39.0.0	Assembled	£46.0.0
STP-1 (Kit) and Brenell Deck	£66.0.0	Assembled	£75.0.0
STP-1 (Kit) and Truvox Deck	£51.0.0	Assembled	£59.0.0
TYPE "C" (Kit) and "STUDIO" Deck	£26.10.0	Assembled	£33.0.0
TYPE "C" (Kit) and BRENNEL Deck	£43.0.0	Assembled	£50.0.0
TYPE "C" Assembled and Wearite Deck	£70.0.0	Inc. Head Lift Trans.	
HF/TR3 (Kit) and "STUDIO" Deck	£28.0.0	Assembled	£33.0.0
HF/TR3 (Kit) and BRENNEL Deck	£43.0.0	Assembled	£50.0.0
HF/TR3 Assembled and Wearite Deck	£70.0.0	Inc. Head Lift Trans.	

MULLARD DUAL-CHANNEL PRE-AMPLIFIER

A four Valve design for both STEREO-PHONIC and MONOPHONIC operation. Operates equally well with any make of Amplifier requiring an input of up to 250 mV.

KIT OF PARTS **£12.10.0**



ASSEMBLED AND TESTED **£15.0.0** (Carr. & Ins. 5/-).

THE "TWIN THREE" STEREO AMPLIFIER

ASSEMBLED AND TESTED

£9.0.0 (Carriage and Insurance 5/- extra)



Based on a recent design by MULLARD LTD., is ideally suited for use in Portable RECORD PLAYERS for which purpose we offer a specially designed Case: incorporates MULLARD ECL 86 Valves, separate BASS and TREBLE CONTROLS and produces up to 3 watts per channel. Frequency response is 40 c/s to 35 Kc/s. size is only 1 1/2 in. x 3 in. x 5 in. To construct a STEREO PORTABLE RECORD PLAYER we offer: ASSEMBLED AMPLIFIER with two ROLA 8 in x 5 in. **£16.10.0** Carr. & LOUDSPEAKERS and PORTABLE CASE for **£16.10.0** Ins. 10/-

THE "TUDOR" STEREO AMPLIFIER

PRICE **£15.0.0** (Packing & Carr. 7/6)



A self-contained Shelf-mounting Amplifier designed to provide high quality stereophonic and monophonic reproduction. Each channel provides a rated output of 6 watts and for monophonic operation approx. 12 watts is produced. Separate BASS and TREBLE CONTROLS. The Cabinet is finished in Black Crackle. Size 14 x 8 x 4 in. Send for full specification.


PLESSEY 15in. P.M. LOUDSPEAKER

Ex B.B.C.

A high quality 15in. loudspeaker, handling 20 watts of audio. Suitable for use in public address systems where considerable power is handled, or as a bass reproducer in dual or triple loudspeaker systems where full use can be made of the low fundamental resonance and smooth response.

Impedance	15 Ohms at 400 c/s.
Dia. of pole piece	2 inches
Power ratings	20 watts
Flux density	12,000 lines
Total flux	185,000 Maxwells
Resonance	25 C.P.S.
Frequency range	20 C.P.C. to 5 Kc/s.
Nett weight	25 1/2 oz.

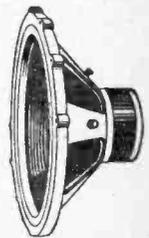PRICE **12 gns.** Carr. & Ins. 10/6 extra.



Our Technical dept. will be happy to advise on the choice of matching PICK-UPS, Microphones, Loudspeakers.

Send for current price list of all leading recording tapes and accessories

WHEN ORDERING OR WRITING FOR LEAFLETS PLEASE STATE DEPT. P.W.

POSTAL ENQUIRIES and MAIL ORDERS TO

STERN RADIO LTD.

6-12, TUDOR PLACE, TOTTENHAM COURT RD. LONDON W1. TEL. MUSEUM 6128/9

DEMONSTRATION and SHOWROOMS AT...

STERN RADIO LTD.

109, FLEET ST, LONDON, EC4

TEL. FLEET ST, 5812/3

OPEN...9 a.m. to 6 p.m. SAT. close 1 p.m.


PREMIER RADIO

23, TOTTENHAM COURT RD.

LONDON, W1. TEL. MUSEUM 6128/9

OPEN...9 a.m. to 6 p.m. THURS. close 1 p.m.

ARMSTRONG AF208AM/FM RADIOGRAM CHASSIS

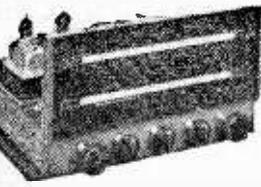

STEREO 12 Mk. 2 #40/5/-
8 watts push-pull output from each channel. 16 watts total; V.H.F. with automatic frequency control medium and long bands; A hi-fi system on one compact chassis. **229/18/-**
Junior version of Stereo 12: 5 watts per channel. 10 watts total; V.H.F. and medium bands; inputs for tape, pick-ups and future stereo radio.
JUBILEE Mk. 2 #28/5/-
Mono; 8 watts push-pull output; V.H.F. and automatic frequency control, medium and long bands; Separate tone controls: Pick-up and tape inputs.
AF208 (ILLUSTRATED) #21/4/-
An AM/FM mono chassis of 5 watts output covering V.H.F. and medium bands. An inexpensive version of the Jubilee Mk. 2.
All carriage free. Write for free literature.

New Boxed VALVES 90-day Guarantee

OZ4	6/-	6K7G	5/-	EB91	4/-	PCL82	10/-
1R5	6/-	6K83	5/-	EB41	5/-	PCL124	10/-
1R5	6/-	6L6G	5/-	EB81	4/-	PL81	10/-
1T4	3/-	6N7M	5/-	EBF80	9/-	PL83	8/-
2X2	2/-	6Q7G	6/-	EBCH43	9/-	PY33	15/-
3B4	7/-	6R87	5/-	EBH91	9/-	PY80	8/-
5Y4	6/-	6X4G	5/-	ECL80	9/-	PY81	8/-
3Q4	4/-	6X4	5/-	ECL82	10/-	PY83	7/-
5U4	6/-	6X5	5/-	EP85	6/-	PQ25	7/-
5Y3	6/-	12AT7	7/-	EP89	8/-	SP41	3/-
5Z4	8/-	12AU7	6/-	EL32	5/-	SP61	3/-
6AC7	4/-	12AX7	7/-	EL84	7/-	U29	2/-
6AM6	4/-	12BH7	7/-	EY81	9/-	UBC41	8/-
6AT6	6/-	12K7	5/-	EV96	9/-	UBC81	9/-
6BA6	7/-	12K8	4/-	EZ40	7/-	UBF89	7/-
6BE6	5/-	12Q7	5/-	EZ80	7/-	UCL61	9/-
6BW6	6/-	25Z5G	6/-	EZ81	8/-	UCL82	10/-
6C4	5/-	35L6	6/-	HABC810	10/-	UCL83	12/-
6D6	5/-	35Z4	5/-	HVR2A	5/-	UF89	9/-
6G6	4/-	35A	2/-	KT33C	8/-	UL41	9/-
6H6	3/-	DAF98	8/-	KT76	8/-	UY41	7/-
6J6	5/-	DP96	8/-	MU14	7/-	UY85	7/-
6J6	5/-	DK96	8/-	PC884	8/-	UY9	7/-
6J7G	6/-	DL96	8/-	PCF80	8/-	VR150	7/-
6K6	5/-	EABC80	8/-	PCF82	8/-	WB1	6/-

NEW FAMOUS ELECTROLYTICS MAKES TUBULAR TUBULAR CAN TYPES

1/350V	2/-	50/350V	5/6	8/600V	9/-
2/350V	2/3	100/25V	3/7	16/600V	12/-
4/450V	2/3	250/25V	3/7	16/450V	5/-
8/450V	2/3	500/12V	3/7	32/350V	4/-
16/450V	2/3	1000/12V	3/7	50/450V	6/8
32/450V	3/9	5,000/6V	5/7	32+32/350V	5/-
25/25V	1/8	8+8/450V	3/6	32+32/450V	6/-
25/50V	2/-	8+16/450V	3/9	32+32+32/350V	7/-
50/25V	2/-	16+16/450V	4/8	50+50/350V	11/8
50/50V	2/-	32+32/350V	4/6	100+200/275V	12/8

TELESCOPIC CHROME AERIALS. 13in. extending to 43in., 8/6 ea. Coax Adapter Plug, 1/8 extra.
TRIPLEXERS Bands I, II, III ... 12/8
COAX PLUG 1/- LEAD SOCKET ... 2/-
PANEL SOCKETS 1/- OUTLET BOXES 4/-
BALANCED TWIN FEEDER var. 6d. 50 to 300 ohms
DITTO SCREENED per var. 1/6. 80 ohms only
Wirewound Ext. Speaker Control, 10 Ω 3/-, 25 Ω 6/6,
WIRE-WOUND POTS, 3 WATT. Pre-set Min. TV Types. All values to 10 ohms to 25 k. 3/- ea.
20 K. 50 K. 1/4". Carbon 30 K. to 2 meg. 3/6.
WIRE-WOUND 4 WATTS POTS. Long spindle. Value, 50 ohms to 50 K. 6/6; 100 K. 7/6.
PHILIPS TRIMMERS. 0-10 p.f., 3-30 p.f., 1/-.
TRIMMERS. Ceramic, 30, 50, 70 p.f., 9d.; 100 p.f., 150 p.f., 1/2; 250 p.f., 1/6; 500 p.f., 1/30 p.f., 1/9.
TV etc. TRIMMER, 1000 p.f. with knobs. 2/-.
RESISTORS. Preferred values. 10 ohms to 10 meg., 1/1 w., 4d.; 1/1 w., 4d.; 1/1 w., 6d.; 1/1 w., 8d.; 2 w., 1/-.
High Stability, 1/1 w., 1%, 2/-.
Preferred values 10 Ω to 10 meg. Ditto 5% 10 Ω to 22 meg. 1/1
1 watt } 1/3
10 watt }
10 ohms-10,000 ohms }
12.5K to 47K 10 w. ... 3/-

Volume Controls 80 ohm COAX Cable Semi-air spaced 1in. Stranded core 6d. yd. 40 yds. 1/7 60 yds. 2/0 Fringe Quality Air spaced 1/- yd.

MAINS TRANSFORMERS 200/250 v. A.C.

Postage 2/- each transformer.
STANDARD. 250-0-250, 80 mA, 6.3 v. 3.5 a. Tapped 4 v. a. Rectifier, 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. 22/6. Ditto, 350-0-350 29/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a. 10/6
MIDGET, 220 v. 45 mA, 6.3 v. 2 a. ... 15/8
SMALL, 220-0-220, 50 mA, 6.3 v. 2a. ... 17/8
STD. 230-0-230, 65 mA, 6.3 v. 3.5 a. ... 17/8
HEATER TRANS. 6.3 v. 1 1/2 amp. ... 7/8
Ditto, tapped 1.4, 2, 3, 4, 5, 6.3 v. ... 8/8
Ditto, sec. 6.3 v. 4 amp. ... 10/6
GENERAL PURPOSE LOW VOLTAGE, 2 amp. 3, 4, 5, 6, 9, 9 1/2, 12, 15, 24, 30 v. ... 22/6
AUTO TRANSFORMER, 150 w. ... 22/6
0, 115, 200, 230, 250 v. 500 w. ... 32/6
MULLARD "510" Mains Transformer ... 38/8
PARMEKO MAINS TRANSFORMER. Made for special contract, the ratings can safely be doubled. Guaranteed 2 years. Primary 0-110-230-250 v. H.T. 300-0-300 v. 50 mA. L.T. 6.3 v. 1.8 amp. Size 4 x 3 1/2 x 3in. ... 17/6

INTERVALVE TRANSFORMERS. 3.1 or 5.1, 9/0-0. P. TRANSFORMERS. Heavy Duty 50 mA 4/6. Multiratio, 7/6. Multiratio heavy duty push-pull 10 w. 15/6. Miniature, 384, etc., 5/9.
10 w. O.P. matching trans. 3, 7, 15 Ω, 12/6.
P. CHOKE 15/1011, 60/65 mA, 5/-; 1014, 85 mA, 10/6; 10 H., 150 mA 14/-
TINNED COPPER WIRE 16 to 22 swg. 1lb. 3/-.
ENAMEL COPPER WIRE 16-22; 2/9; 24-30, 3/6; 32-40, 4/8; D.C.C. 28. 34. 36 swg. 2oz. 3/6.

I.F. TRANSFORMERS 7/8 pair 465 K/s Slug Tuning Miniature Can. 2 x 1 x 1 in. High Q and good bandwidth. Data sheets. Standard size Weyrad, 10/6 pair.

FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 6 or 12 v. 1 1/2 amp., 8/9; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v. 1 1/2 amps., 15/6; 2 amps., 17/6; 4 amps., 22/6. (Circuit included).
4 AMP CAR BATTERY CHARGER with amp. meter Leads, Fuse Case, etc., for 6 v. or 12 v., 69/9.
AMMETER 0 to 5 amp., 6/6.

BOOKS list S.A.E.
Boys' Book of Crystal Sets. ... 2/6
"W.W." Radio Valve Data ... 6/-
High Fidelity Speaker Enclosure 5/-
Valve and Tube Equivalents ... 5/6
TV Field Pictures ... 8/8
Mullard Amplifier Manual ... 8/6
Radio Valve Guide, Books 1, 2, 3, 4 or 5 ... 5/- each
Transistor Superhet Receivers ... 7/6
Practical Radio Transformer, 4 Transistors. ... 3/6
Master Colour Code Chart ... 1/6
Transistor Controlled Models ... 7/6
Principles of Colour TV ... 18/-
International Radio Stations List

4 TRANSISTOR PUSH-PULL AUDIO AMPLIFIER


Size 3 x 1 1/2 x 1.
A ready built miniature push-pull amplifier with Driver and output transformers, 4 transistors. Ideal for use with record players, intercoms, BARRY ALARMS, etc. Complete with instructions and circuit.
Price, 47/6 9v. Batt. 2/3 2in. Speaker 15/-.

BAKER SELHURST LOUSPEAKERS

12in. Baker 15w. Stalwart 3 or 15 ohms, 45-13,000 c.p.s. ... 90/-
12in. Stereo, 12w., 35-16,000 c.p.s. ... 82/6
12in. Standard H.D. 20w. 40-14,500 c.p.s. ... 28.0
12in. De Luxe 15w. 25-17,000 c.p.s. ... 29.10
12in. Bass 25w. 20-18,000 c.p.s. ... 212.12.0
15in. Auditorium, 35w., Bass, 20 c.p.s. to 12 kc/s. Ideal Bass Guitar. £18.
Details and Enclosures, plans, S.A.E.
LOUSPEAKERS P.M. 3 OHM. 2 1/2, 3, 4in., 5in. Rola, 7in. x 4in. Rola, 15/6; 6 1/2in. Rola, 18/6; 8in. Plesey 17/6; 10 x 6in., 22/6; 10in. Rola, 30/-; 12in. R.A. 30/-; 13 1/2 x 5in. Double Cone E.M.I., 30/-
STENTORIAN HF1012. 10in. 3 to 15ohms, 10w. 87/6; 8in. HF812 72/-; Tweeter T359 30/-.



1963 RADIOGRAM CHASSIS

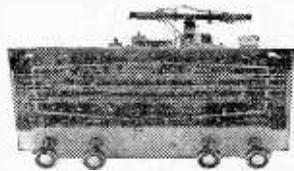

THREE WAVEBANDS FIVE VALVES
S.W. 16 m.-50 m. LATEST MULLARD M.W. 200 m.-350 m. ECH81, EP89, EB81, L.W. 800 m.-2,400 m. EL84, EZ80
A.C. 200/250 v. 4-way varacite. 12-month guarantee.
A.C. 200/250 v. 4-way Switch; Short-Medium, Long/Gram. Ferrite Aerial A.V.C. and Negative feedback; 3 ohm output, 5 watts. Glass dial, horizontal wording, size 13in. x 4in. Aligned and calibrated, isolated Chassis, size 13 1/2in. x 9in. high x 9 1/2in. deep.
£8.19.6 Carr. & Ins. 4/6.

C.R.T. BOOSTER TRANSFORMERS for heater cathode short circuit, or tubes with falling emission. Full instructions supplied, mains input. Type A optional 25% and 50% boost 2v. or 4v. or 6.3v. or 10.8v. or 12.6v. State voltage required. PRICE 10/6.

TWIN GANG TUNING CONDENSERS. 365 pF. miniature 1in. x 1 1/2in. x 1 1/2in., 10/-; 300pF standard with trimmers, 9/-; midget, 7/6; with trimmers, 9/-; 300pF evo motion tuning, standard or midget, 9/-.
SMALL 3 gang 500 pF, 17/-. **SINGLE 365 pF, 7/6.**
SINGLE 10 pF, 25 pF, 50 pF, 75 pF, 100 pF, 160 pF, 5/8. Solid dielectric 100, 300, 500 pF, 3/6.
CONDENSERS. New stock, 0.001 mfd., 7 k. 9/6, P.C.C., 5/6; Dito, 20 kV, 9/6; 0.1 mfd., 7 kV, 9/6. Tubular 500 v. 0.001 to 0.05 mfd., 9d.; 0.1-1 pF, 0.25, 1/8; 0.5/350 v., 1/8; 0.1/350 v., 9d.; 0.1/2,000 v., 0.1/1,000 v., 1/8; 0.1 mfd., 2,000 volts, 3/6.
CERAMIC CONDS. 500 v. 0.3 pF to 0.01 mfd., 9d.
SILVER MICA CONDENSERS. 10 pF to 500 pF, 9d.; 500 pF to 3,000 pF, 1/- (close tolerance +1 pF); 32 pF to 47 pF, 1/-; Ditto 1% to 50 pF to 815 pF, 1/-; 1,000 pF to 5,000 pF, 1/8.

465 kc/s SIGNAL GENERATOR Price 15/-, New B.F.O. Unit, ZA 30038 ready made with valve IS5. PICKET SIZE 2 1/2 x 4 1/2 in. One resistor to change, full instructions supplied. Battery 3/6 extra. 69V14V. Details S.A.E.

WAVECHANGE SWITCHES

3 p. 4-way 2 wafers long spindle ... 8/6
2 p. 2-way, or 2 p. 6-way long spindle ... 3/6
4 p. 2-way or 4 p. 3-way long spindle ... 3/6
2 p. 4-way or 1 p. 12-way long spindle ... 8/6
Wavechange "MAKITS" wafers available: 1 p. 12 waf., 2 p. 6 waf., 3 p. 4 waf., 4 p. 3 waf., 6 p. 2 waf. 1 waf. switch, 8/6
2 waf. switch, 12/6; 3 waf. switch, 16/-; additional wafers up to 12, 3/6 each extra; Toggle Switches, s.p.d., 2/-; d.p., 3/6. d.p.d.t., 4/-; Min. Slide d.p.d.t., 3/6.

CRYSTAL MIKE INERTS, 6/6 High output. Size 1 1/2in. dia. x 1in.
ACOS MIKES 14. Insert 1 1/2in. dia. x 1in. 8/6
ACOS 39-1 DE LUXE STICK MIKE 35-TSL QUALITY STICK MIKE... 25/-

Valveholders, EA50, 6d. B12A, CRT. 1/3. Grid, an. An. 5 and 7 pin. 1. MOULDED Mazda and Int. oct. 6d.; 6/6. B8A, B8C, B9A, 9d. B7G with can. 1/6. B9A with can. 1/9. Ceramic EF50, B7G, B9A, Int. oct. 1/7. B7G, B9A cans. 1/- each. Valve plugs B7G, B9A, 2/3.

HIGH GAIN TV PRE-AMPLIFIERS BAND I B.B.C.
Tunable channels 1 to 5. Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PCC84 valves if preferred.) Coils only 9/6.
BAND III I.T.A.—Same prices. Tunable channels 8 to 13. Gain 17dB. Circuit and coils only 9/6.


THE ORIGINAL

RADIO COMPONENT

Our written guarantee with every purchase
NEW COMPONENT LIST 1/-

Bus 133 or 68 pass door.
S.R. Station Selhurst.

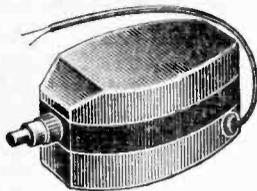THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETIZER



200/250 v. A.C. **35/-** Leaflet S.A.E.

AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE

Double Play 7in. reel, 2,400ft. 42/-	Spare Plastic Reels
5in. reel, 1,300ft. 25/-	
Long Play 7in. reel, 1,800ft. 35/-	3in. 1/6
5in. reel, 1,200ft. 23/6	4in. 2/-
5in. reel, 900ft. 18/6	5in. 2/-
Standard 7in. reel, 1,200ft. 25/-	6in. 2/-
5in. reel, 800ft. 16/6	7in. 2/6
7in. Metal Reels 1/6	
"EASISPLICE" Tape Splicer 5/-	

CRYSTAL SET BOOKLET, 1/-
CRYSTAL DIODE G.E.C. 2/-, GEX34, 4/-, OA91, 3/-
HIGH RESISTANCE PHONES, 4,000 ohms, 15/-
MOVING COIL PHONES, 100 ohms, 10/-
SWITCH CLEANER, Fluid squirt sprout, 4/6 tin.

"6+1" TRANSISTOR RADIO MEDIUM AND LONG WAVE KIT

First class components to make a 6 transistor 2 waveband superhet chassis. Ideal for portable or table radio. All parts including BVA transistors, ferrite aerial, with car aerial coil printed circuit, 84in. x 2 1/2in., but EXCLUDING Speaker and cabinet.
Speakers, 35 ohms, 7 x 4in. 21/- £4.5.0
 5in., 17/6, 3 1/2in., 15/6.

BULGIN PLUGS AND SOCKETS. Non-reversible P74, 2-pin, 4/3; P75, 3-pin, 4/6; P194, 6-pin, 8/6.

"DOMINA" plugs 2/6; sockets, 3/6.
JACKS. English open circuit, 2/6. Closed circuit, 4/3. Grounding type, 3-pin, 1/3. Grounding lead jack, 3/6.

JACK PLUGS. English, 3/-; Screwed, 4/-; Grundig, 3-pin, 3/6; Phone Plugs, 1/-; Sockets, 6d.
ALADDIN FORMERS and cores, 4in., 8d.; 5in., 10d.
FORMERS 5937 or 8 cans TV1 or 2, 4in. sq. x 2 1/2in., or 4in. sq. x 1 1/2in., 2/- with cores.
SLOW MOTION DRIVES, 6/1, 4/6.

SOLON IRON, 250V or 300V, 24/-
ANTEX SUB-MIN. IRON, 15w., 200 or 240v., 29/6
BENCH STAND for above, 12/6. Spares in Stock 1/16in. Paxolin Panels, 10 x 8in., 2/-.

Miniature Contact Cooled Rectifiers, 250V 50mA, 7/6; 250V 60mA, 8/6; 250V 85mA, 9/6; Selenium Rect., 300V 85mA, 5/-; TV, etc. Silicon Sub. Min. Rectifier, 250V 450mA, 10/-; K3/25, 600V, 5mA, 5/-; RMS, RMS, 14A10, 14A115/10/- each; FC31, 20V-Colls Weaire "P" Type, 3/- each.

Osmor Midget "Q" type, ad. dust core, from 4/- each. All ranges. List S.A.E.
Teletron D.W.R., L. and Med. W.F.R.F. with reaction, 4/-; Med. wave D.R., 3/6.
Ferrite Aerials, M., 8/8; M. and L., 12/6
Osmor Ferrite Rod Aerials, L. and M. for transistor circuits, 10/- each.
Ferrite Rods, 8 x 1in., 6 x 1in., 3/-
H.F. Chokes, 2/6; Osmor, OC1, 6/9.
T.R.F. Coils, A/HF, 7/-; Pair, HAX, 3/-
Repenco DRR2, 4/6. DRX1, 4/6.
Radio Screwdriver, 5in., 6d. Test Prods., 2/9. Neon Trimming Tool, 1/9. Neon Mains Tester, Screwdriver, 5/-.
Multicore Solder, 4d. vd., Dispenser 2/6.

Aluminum Chassis, 18 s.w.g. Plain undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/9; 11 x 7in., 6/9; 13 x 8in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6.
Aluminum Panels, 18 s.w.g., 12 x 12in., 4/6; 14 x 8in., 4/-; 12 x 6in., 3/-; 10 x 7in., 2/3; 8 x 6in., 2/-.

JASON FM TUNER COIL, SET 29/-. H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer, heater choke. Circuit book using four 6AM6, 2/6.
Complete Jason FMTI Kit. Jason chassis with calibrated dial, components and 4 valves, £6.5.0.
Model FMTI with new shelf cabinet, 5 valves, components and powerpack, £10.

MAINS DROPPERS. Midget adjustable sliders 0.5A, 1,000 ohms, 5/-; 0.2A, 1,200 ohms, 5/-; 0.15A, 1,500 ohms, 5/-; 0.1A, 2,000 ohms, 5/-.
MIKE TRANSFORMERS, 50-1, 3/9. P.V.C. Covered Wire, single or stranded, 2d. vd. Sleeving, 1 or 2 mm., 2d.; 4 mm., 3d.; 6 mm., 5d. vd.
SPEAKER-FRET, Gold, Maroon or Green Chold, 17 x 2 1/2in., 5/-; 25 x 3 1/2in., 10/-. Tygan, various colours 62in. wide from 10/- ft.; 26in. wide from 5/- ft. Samples S.A.E. Expanded Metal, Gold, 12 x 12in., 6/- Panel mounting fuse holders 2/-. Fuses 60mA -5A, 5d.

RADIO AND TELEVISION SPARES
 All leading makes, volume controls, etc., line output transformers, etc.
B. V. A. valves (current and obsolete types). Send S.A.E. for quotation.


WEYRAD

COILS AND TRANSFORMERS FOR 2-WAVE TRANSISTOR CIRCUITS WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL.
 Long and Medium Wave Aerial—RA2W On 5in. rod, 200K tuning, with car aerial coupling coil, 12/6
 Osc. Coil P50/1AC, 176pF tuning 5/4
 1st and 2nd I.F. Trans.—P50/2CC, 470Kc/s 11/16in. dia. by 1in. 5/7 each
 3rd I.F. Trans.—P50/3CC. 6/-
 Spare Cores 6d. each
 Driver Transformer—LFD1, 9/6
 Wavechange Slide Switch d.p.d.t. 3/6
 Printed Circuit—PCA1. Size 2 1/2 x 8 1/2in.
 Ready drilled, and printed 9/6
 Volume Control, 5K-2P 4/6
 35 ohm Speakers, 3 1/2in., 15/6; 5in., 17/6; 7 x 4in., 21/-
 Tuning Gang with trimmers 10/6
 6 Mullard Transistors and diode, 42/6
 Constructive Booklet 2/-
 3 ohm O.P. Trans. O.P.T.1 10/6

NEW MULLARD TRANSISTORS
 OC71 6/-, OC72 7/6, OC81D 7/6, OC81 7/6, OC48/9, OC45 8/6, OC71 10/6, AF117 8/6.
 Sub Miniature Condensers, 0.8 mF, 30V, 1/3, 1/2, 4, 5, 8, 16, 25, 30, 50, 100 mF, 15c. 10/2 ea. Transistor Holders 1/3.

B.B.C. Pocket 2 Transistor, Plus Diode M.W. and L.W. Radio Kit, 29/6.
 Minute earpiece, 7/6. Batt. 2/3.
 Circuit details, etc., S.A.E.

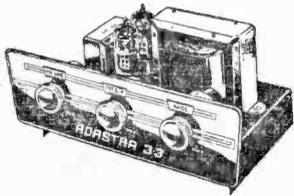ADASTRA 3-J AMPLIFIER 3 WATTS HIGH FIDELITY AT LOW COST



READY BUILT, WIRED & TESTED A.C. only, 200-250 V. Valves EC15B and FZ80, 3 ohms quality output. Mullard tone circuits. Controls: bass boost, treble and volume. Separate engraved front panel with de luxe finish. Quality mains transformer, stove enamelled chassis, size 6in. x 5in. x 3in. Barkain Price £4.19.8. Details S.A.E.
 "Performs agreeably well!" (The Gramophone)

BUILD YOUR OWN RECORD PLAYER

AND SAVE POUNDS!!



4 Speed Autochange or Single Player units supplied with Brand New 2-tone Portable 4 cabinets 17 x 15 x 8 1/2in. de luxe Strong carrying handle, gilt finish clips and hinges. As used by Famous Make for 30gn. models. Ready cut-out motor board 14 x 13in. Front baffle with 7 x 4in. high flux loudspeaker and 3 watt 2 valve U185, UCL82 2-stage amplifier ready built on metal chassis 12 x 3 x 2 1/2in. Quality 3 ohm output transformer, how hum level circuit, Volume and Tone controls, 3-core safety mains lead. All items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to join; 12 month written guarantee. Available separately or package deals as below.

AUTOCHANGER KITS COMPLETE (as above)
 B.S.R. Monarch ... £11.10. P.P. 5/8
 Collaro ... £11.15.0 P.P. 5/8
 Garrard ... £12.5.0 P.P. 6/6

SINGLE PLAYER KITS Complete (as above)
 Garrard auto stop/start ... £11.5.0 P.P. 5/6
 E.M.I. auto stop/start ... £11.5.0 P.P. 6/6

OR SEPARATELY
 Cabinet with cut out board £3.2.6 P.P. 3/6
 Amplifier with 7x4in. speaker £3.17.8 P.P. 2/6

AUTOCHANGERS
 B.S.R. UA14 ... £6.5.0 P.P. 4/6
 Garrard Autoslim ... £6.17.8 P.P. 4/6

SINGLE PLAYERS
 E.M.I. auto stop/start ... £5.10.0 P.P. 4/8
 Garrard SRP10 ... £5.10.0 P.P. 4/6
 E.M.I. (separate pick-up) ... £2.7.8 P.P. 3/6

TRANSCRIPTION UNITS Stereo/Mono
 Garrard 4HE ... £19.10.0 P.P. 6/-
 Philips AG1016 ... £12.5.0 P.P. 5/-
 Garrard AT8 ... £10.10.0 P.P. 6/-

BARGAIN
 B.S.R. Autochange UA12 Stereo/Mono ... £7.10.0 P.P. 4/9

Replacement sapphire styli available from 5/3
 Replacement Atas from 15/- Stereo from 31/6.

GABY MULTIMETER

Moving-coil Model M.1. 54/-
 Measures D.C. or A.C. 6 v., 30 v., 120 v., 600 v., 1200 v. D.C. 30 mA, 300 mA, Ohms 0-100K. Leaflet S.A.E.

ARDENTE Transistor Transformers

Type D3035, 7.3 CT; Push-Pull to 3 ohms for OC72, etc., 1 x 1 x 1in. 9/6
 Type D3034, 1.75 : 1 CT. Push-Pull Driver for OC72, etc., 1 x 1 x 1in. 9/6
 Type D3058, 11.5 : 1 Output to 3 ohms for OC72, etc., 1 x 2 x 1in. 9/6
 Type D167, 18.2 : 1 Output to 3 ohms for OC72, etc., 1 x 1 x 1in. 12/-
 Type D239, 4.5 : 1 Driver Transformer, 10/-
 Type D240, 8.5 : 1 Driver Transformer, 10/-

ARDENTE TRANSISTOR CONTROLS

5K or 1M G. switched, dia. 0.9in., 5/3
 Type VC1780, 5K with switch, dia. 0.7in., 10/6
 Deaf aid earpiece xtal or magnetic, 7/6
 Sub-min Jacks 1/9. Plugs 1/9.

COMPONENT SHOP SPECIALISTS

337 WHITEHORSE ROAD WEST CROYDON

Telephone: **THO 1645**
 (Export welcome. Send remittance, and extra postage, no C.O.D.)

P.P. charge 1/- C.O.D. 2/- extra.

FREE THIS BOOK WILL INTEREST YOU!

LEARNING the PRACTICAL WAY

Radiostructor
EQUIPMENT-COURSES

A NEW-PRACTICAL WAY of UNDERSTANDING

Radio - Television - Electronics

Including: Transistors; VHF/FM, Hi-Fi equipment; Computers; Servo-mechs; Test instruments; Photo-Electrics; Nucleonics, etc.

FOR ...Your Career...Your Own Business...An absorbing Hobby

Radiostructor—an organisation specialising in electronic training systems offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis.

You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact—you really have fun whilst learning! Post the coupon below, now, for full details.—

RADIOSTRUCTOR
LEADS THE WORLD
IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G82)
READING, BERKS.

Please send brochure, without obligation, to:—

★ Name _____

Address _____

10/63

★ **BLOCK CAPITALS PLEASE**
(We do not employ representatives)

Practical Wireless

Vol. XXXIX No. 680 OCTOBER, 1963

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes Ltd., Tower House,
Southampton Street, W.C.2.

© George Newnes Ltd., 1963

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

To any part of the world £1.9.0

Contents

	Page
Editorial	493
Round the World of Wireless ...	494
A Signal Generator	496
A Novel A.F. Amplifier	500
The Photophone	501
On Your Wavelength	507
Personal Transistor Two	508
The Euphon	512
A Versatile Double-trace Oscilloscope	516
Quality MW Tuner	520
An Electric Nim Machine	524
Printed Circuit Boards	530
A Variable Mains Transformer ...	533
Trade News	538
Test Gear Techniques	541
Club News	546
Ohm's Law Calculator	549
Letters to the Editor	553
Book Review	554

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

BE PREPARED!

At this time of year, as autumn approaches and the evenings draw in, most readers will be spending less time in outdoor pursuits and more on indoor activities. And in particular, thoughts of the impending constructional "season" will occupy a good many minds.

For whereas the majority of enthusiasts (quite rightly) enjoy as much of the outdoor life as our capricious climate allows during the summer months, the winter sees a peak in constructional activity that restores the average.

After a reduction of building projects for a month or two, most amateurs look forward keenly to this resurgence of activity which begins to gain impetus as the autumn leaves fall. Many readers, of course, maintain a certain level of practical activity all through the year, but nevertheless there is something about the autumn and winter that presents an irresistible lure even to those who temporarily forsake practical work in the summer.

Perhaps it is the cosy atmosphere of the workshop, den or "shack", with the smell of flux on the soldering iron and the low hum of power packs. Perhaps it is because, shut off from the obtrusive world with the curtains drawn, one can get to work without external distractions and concentrate fully on the work in hand. Or maybe it is because the true enthusiast, though seemingly inert during the summer, has been quietly planning new ideas for equipment and now feels the time is ripe to put them to the test.

Whatever it is, one thing is certain: during the next few months much solder is going to flow, many holes are going to be drilled and many thousands of components are going to be wired into hundreds of different circuits. With, we hope, a large percentage of successes!

But despite the fact that this general pattern follows regularly, we wonder how many are *really* prepared for the approaching high level of activity. The facilities available to the radio amateur vary enormously from, literally, the kitchen table to the separate permanent workshop—with a wide assortment in between.

Yet whatever the enthusiast's personal circumstances, he would do well to ensure that he is fully prepared to embark on an extended period of constructional work. For instance, is the wiring in the workshop adequate and is it really safe? Have those important extra points been installed? Are all tools in good shape? Are there any gaps in the tool kit? Is the spares box in reasonable order? Are the boxes of nuts, bolts, small components, etc., sorted and conveniently housed? In other words—are you ready for working at maximum efficiency and ease?

If somewhere along the line you get a negative answer, now is the time to put things right. *Before* the season really gets under way—when you will *never* find the time!

Our next issue dated November will be published on October 4th



of WIRELESS

NEWS AT HOME AND ABROAD

RADIO EXHIBITION IN AMSTERDAM

NINETEEN manufacturers will have exhibits on the official British stand at the International Exhibition of Radio, Television and Electronic Equipment (FIRATO) to be held in Amsterdam, Netherlands, from September 13th to 22nd.

The stand, which will cover 2,600sq.ft, has been organised by the Board of Trade and the Audio Manufacturers' Group. A special demonstration room on the stand will enable visitors to judge the performance of British made tape recorders, record players, amplifiers, loudspeakers and radios, under the best acoustic conditions.

STEREOPHONIC TRANSMISSIONS

THE number of experimental stereophonic transmissions per week from the BBC's Wrotham Third Programme transmitter, has been increased recently from one to three. Test transmissions can now be received on Tuesdays, Wednesdays and Thursdays on 91.3Mc/s.

A tone test transmission between 10.30a.m. and 11a.m. will be followed by a programme test transmission from 11.15a.m. to 11.45a.m. A tuning signal consisting of two tones of different pitch is transmitted for four minutes before the test transmissions.

U.S. Order for Blind Persons' Aids

AN order for a number of electronic aids for blind persons, which were described in these pages a few months ago and which rely on the difference of frequency between an ultrasonic beam of energy and its reflection from nearby objects to enable the blind user to "hear" obstacles ahead, has been received by the manufacturers from the Bureau of Rehabilitation Services of the Department of Education for the State of Kentucky, U.S.A.

Ultra Electronics Limited, who produced the first of the aids for the preliminary evaluation tests, have also received an order for 50 units from St. Dunstan's.

H.F. Equipment for Ministry of Aviation

THE Ministry of Aviation has recently ordered a number of Marconi type D11 and D13 high-frequency mobile radio stations. The contract is valued at approximately £1,500,000.


The type D11 transmitter/receiver equipment is a mobile field communication unit providing the latest h.f. facilities, including s.s.b./i.s.b. telephony and f.s.k. telegraphy, with incorporated teleprinter. The output power of the transmitter is rated at 300-350W over the frequency range 2 — 21.999Mc/s. The receiver is a high stability independent side-band and telegraph equipment, crystal controlled and operating on the double superheterodyne principle.

The type D13 equipment operates over the same frequency range but with a transmitter power output rating of 1kW. It also differs from the D11 in that it employs two receivers (for dual diversity operation) instead of one.

REGULATORS FOR BBC

THE BBC's v.h.f. transmitting and radio link stations as well as television stations, require very stable voltage supplies, and recently at the Wimbledon works of Foster Transformers (a member of the Metal Industries Group) six new voltage regulators for various BBC stations have been undergoing extensive tests prior to delivery.

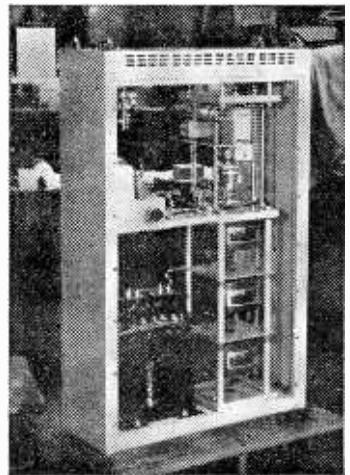Each of the regulators has an output of 17kVA which is necessarily maintained stable for the transmitter and associated equipment it will be serving when installed.



One of the voltage regulators made by Foster Transformers for the BBC.

IMPROVED SOUND FOR ST. PAUL'S

AFTER extensive tests made by engineers from Standard Telephones and Cables Limited, the sound system of St. Paul's Cathedral, London, has undergone considerable alteration, designed to improve audibility to every part of the congregation.

The Cathedral's architecture and size have posed special problems for the sound engineers involved on the operation, and in

particular there is a problem of the time lapse of speech from the altar and pulpit areas, and along the length of the Nave. (It was found that sound took three-tenths of a second to travel from the altar to the far end of the Nave.)

As it was decided to incorporate the Cathedral's existing system of loudspeakers in the new improvements, it was obvious

that a delay mechanism would be necessary to co-ordinate sound arriving direct from the source and the sound delivered over the loudspeakers; which, in the normal course of events, would arrive almost immediately. Failure to compensate for this phenomenon would result in garbled speech reaching the distant parts of the congregation.

The method used by STC to give the necessary delay employs a magnetically loaded neoprene belt, stretched around a metal drum. In operation the drum is revolved at 80 revolutions per minute. Several magnetic heads are distributed at specific points around the drum and held in contact with it as it revolves. One of two of these heads, records speech on to the belt from either the altar or pulpit microphone. As the drum revolves, the recorded speech is carried to replay heads successively spaced further around the drum from the recording head; and from these the speech is carried to loudspeakers situated at various distances from the microphone. The time taken for the signal to travel round the drum from record to replay heads provides the necessary delay.

Finally as the recorded speech moves past the last replay head, an erase head removes the signal before once again the recording heads are reached at the end of one complete revolution of the drum.



An STC engineer positions an 8 ft. column loudspeaker in St. Paul's Cathedral during recent acoustic tests.

SERVICING EXAMINATION

IT was announced recently that out of the 853 candidates who entered the final written examination for the Radio and Television Servicing Certificate of the City and Guilds of London Institute, 456 passed and thus qualified for the practical test to be held later this year.

Chairmen for B.V.A. and VASCA

TWO associations of valve manufacturers have recently elected their chairman for the forthcoming year. The British Radio Valve Manufacturers' Association (B.V.A.) has elected Mr. F. V. Green of Brimar Limited, and the Electronic Valve and Semiconductors Manufacturers' Association (VASCA) has elected Mr. A. J. Young of the English Electric Valve Company Limited.

Modernisation for East African Telephone Link

TEN years ago the Marconi Company installed a multichannel link between Nairobi, Mombasa, Tanga and Dar-es-Salaam in East Africa. Now the East African Posts and Telecommunication and Administration has placed a contract with Marconi's to modernise the complete system which will result in improved performance and increased capacity for the telephone channels.

After modernisation there will be two radio paths over the whole link, carrying a total of 96 telephone channels, and automatic change-over facilities will ensure that priority traffic is not interrupted by failure of either radio path.

Despite the increased capacity of the links, the original terminal and repeater stations will be used, some of which link distances of up to 97 miles.

A SIGNAL GENERATOR

**transistorised . . . a.f. and modulated
r.f. outputs . . . battery operated . . .**

BY F. G. RAYER

THIS signal generator uses two transistors, and will provide either an audio frequency output or a modulated radio frequency output. The a.f. output can be used to check audio amplifiers, or the a.f. stages of a receiver. The r.f. output is tunable from about 1.6Mc/s to 170kc/s (approximately 190 to 1.800m) and can be used to test or align intermediate frequency amplifiers, or medium and long wavebands of a receiver. Harmonics of 200kc/s are audible to 10mc/s, while harmonics of 1Mc/s are audible to 30Mc/s, with a sensitive receiver. This allows frequency spotting through the short wave ranges of a receiver.

The generator operates from a 4.5V dry battery supply, and may be used for checking transistor sets, or mains or battery operated valve receivers.

The circuit is shown in Fig. 1. Tr1 is a radio frequency transistor, such as is commonly employed as a self-oscillating mixer in superhet receivers. Tr2 is an audio type; a yellow-green spot audio transistor was used by the author, but any small transistor in working order should be satisfactory.

T1 is a transistor coupling or driver transformer, with a ratio of about 1:2 or 1:1. The transformer

fitted was intended for push-pull, so one secondary lead is unused. If Tr 2 does not oscillate, connections to the primary of T1 should be reversed. With the switch S1 in position 1, the audio signal is taken to the output control potentiometer VR1, which allows volume to be kept down as required.

Tr1 is the r.f. oscillator. A two-gang 400pF or similar value tuning capacitor is used to obtain adequate coverage with only two bands.

With the switch S1 in position 2, the generator tunes from about 1.6Mc/s to 500kc/s (190 to 600m approximately). When the switch is in position 3, the coverage is approximately 500 to 170kc/s (600 to 1.800m approximately) and this includes most of the long wave band, in addition to 370kc/s and adjacent intermediate frequencies.

C5 provides coupling from the a.f. oscillator, which acts as modulator, so that the note can be heard on a receiver tuned to the same frequency as the generator.

Small transistor type components can be used throughout, except for C6, which must be a mica or other high voltage capacitor, in order to provide effective isolation from mains equipment.

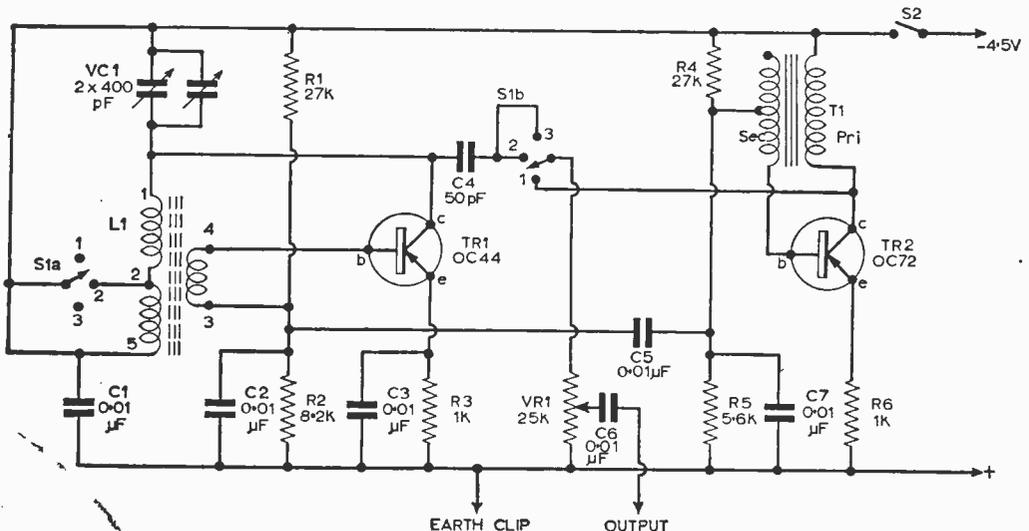


Fig. 1: The complete circuit of the generator.

Tuning Coil

This was wound as in Fig. 2, silk covered wire of 34s.w.g. being used throughout. The m.w. section consists of 50 turns wound side by side, between points 1 and 2, a layer of paper being placed over the rod. A space of about 1/5in. is left, and seven turns are wound side by side (leads 3 and 4). A narrow space (about 1/20in.) is left, and 100 turns are wound in a compact pile, for the l.w. section. The end of the m.w. winding is joined to the beginning of the l.w. winding (lead 2). The end of the l.w. winding is lead 5. Dabs of cement are used to hold windings and the ends secure, and all turns must be in the same direction.


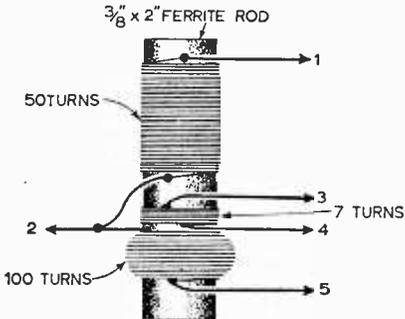


Fig. 2: Winding details of the tuning coil, L1.

In general, other coils should be satisfactory. However, some experiment may be needed. If coverage is too high in frequency (low in wavelength) additional turns are required; but if frequency coverage is too low, turns need removing. Air cored coils were found to work, but need many more turns. Some ready-made dual-wave coils could be expected to be satisfactory, though coverage might need modifying slightly, either by changing the core positions, or by altering the number of turns. With most coils, turns will need

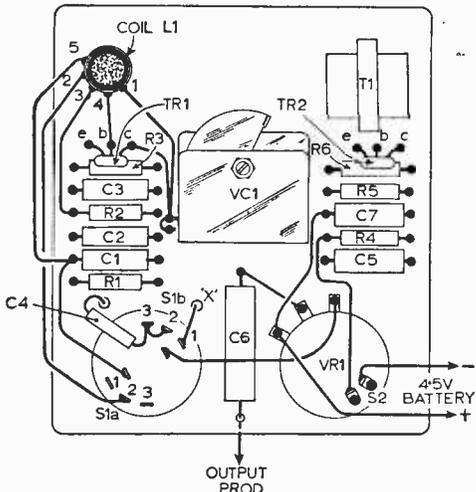

removing, to reach about 500kc/s on the l.w. band, with VC1 fully open.

Construction

A paxolin panel about 4in. x 4 1/2in. is used, drilled as in Fig. 4. The ferrite rod (L1) is a push fit in a 3/8in. diameter hole, being held with cement. A 1/16in. drill will do well for all the small holes, with 3/8in. hole for the switch and potentiometer and a 1/2in. hole to clear the gang capacitor.

The components are mounted as in Fig. 3. Emitter, base and collector leads of Tr1 and Tr2 are inserted as shown and there is no need to cut these wires short. The transformer T1 is held by its leads.

Three short 4B.A. bolts hold the gang capacitor. These must not penetrate sufficiently to short-circuit or damage the capacitor. The circuit requires a three-way, two-pole switch and, if a surplus switch with more contacts is fitted, unwanted tags are ignored.

Fig. 4 shows wiring on the front of the panel between resistors and other parts. Any thin, insulated wire is satisfactory or thin tinned copper bare wire can be employed with 1mm sleeving.

The audio oscillator stage can be tested alone when wired. To do this connect phones from C6 to battery positive. If no tone is heard reverse the primary leads to T1 as mentioned.

Two short pieces of thin flex are provided for battery connections and there was found to be no advantage in using more than 4.5V. Consumption is between about 2mA and 6mA according to the actual transistors, so very small cells will do well. To avoid trouble from bad contact leads may be soldered to the cells. Three dry cells in series will provide 4.5V and the zinc case is negative.

Output Lead

A flexible lead from the positive line terminates in a clip which can be attached to the chassis or other earthed circuit of a receiver.

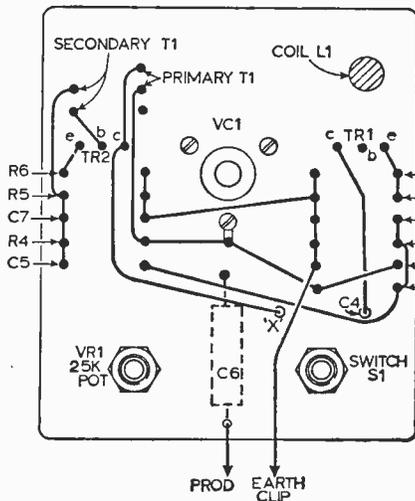


Fig. 3 (above) and Fig. 4 (right): Component layout and wiring diagrams.

The output lead from C6 is fitted with an insulated prod so that the signal can be injected into various parts of a circuit.

There is no chance of shocks when testing a battery operated transistor receiver. With battery operated valve sets the h.t. may be sufficient to cause a shock. In the case of mains receivers the usual care must be taken. The danger is particularly great with a set of the a.c./d.c. type or one drawing h.t. directly from the mains.

The Case

The case is made of thin wood approximately 4½ in. x 4½ in. x 2½ in. deep internally. The panel is thin paxolin 4½ in. x 5½ in. if the case is of thin, thick wood. Nuts on the switch and potentiometer secure the generator and panel together and scales are marked on the paxolin or on thin card placed over the paxolin. For tuning a fairly large knob is required and is fitted with a celluloid cursor marked with a line to permit reading against the scales.

To check the generator the a.f. output may be applied to a pair of phones or to an amplifier or receiver. To test for modulated r.f. output place the prod or lead near the aerial of a receiver. The audio tone should be heard when the receiver and generator are tuned to the same frequency.

Harmonics

The generator note will also be heard when the receiver is tuned to a multiple of the generator frequency. For example, if the generator is tuned to 200kc/s its note will be heard at 200, 400, 600, 800, 1,000, 1,200kc/s and so on. This fact is very useful both to calibrate the generator tuning scales and to furnish a signal for a short-wave receiver.

The correct tuning point will most easily be found when coupling between generator and receiver is low, and output small, so that the received signal is not too strong.

Calibration

If a calibrated generator is available, set this to various frequencies, tune in the signal on a receiver, then tune the transistor generator to the same frequency and mark its scale.

If no calibrated generator is to hand, calibration can first be at 200kc/s points. Find this fundamental point from the BBC Light Programme transmitter. Tune the generator to the same frequency and mark its long-wave scale. Then tune the receiver to a harmonic as mentioned. Leave the receiver tuning untouched and tune the generator until its fundamental is heard on the receiver. This can then be marked on the generator scale. Repeat the whole procedure until the scales are calibrated to 1.6Mc/s (1,600kc/s). Other calibration marks can be obtained by selecting other harmonics. For example, the third harmonic of the Light Programme (long waves) is 600kc/s. The generator may then be tuned to 300kc/s (600kc/s is the second harmonic of 300kc/s) to obtain the 300kc/s point between 200 and 400kc/s. Proceeding in this way, sufficient calibration points can be secured.

Note that the tone is not heard if the generator is tuned to a multiple of the receiver frequency but only when the receiver frequency is a multiple of

COMPONENTS LIST

Resistors:

R1	27kΩ	R4	27kΩ
R2	8.2kΩ	R5	5.6kΩ
R3	1kΩ	R6	1kΩ
VR1	25kΩ potentiometer with s.p. switch (S2)		

Capacitors:

C1	0.01μF paper
C2	0.01μF paper
C3	0.01μF paper
C4	50pF ceramic
C5	0.01μF paper
C6	0.01μF mica, or paper 500V
C7	0.01μF paper
VC1	400+400pF 2-gang variable

Inductors:

L1	H.F. coil (see text)
T1	Transistor coupling or driver transformer

Switches:

S1	2-pole, 3-way miniature rotary
S2	s.p.s.t. (see VR1)

Transistors:

Tr1	OC44 or similar r.f. or mixer type
Tr2	OC72 or similar a.f. type

Miscellaneous:

Two small pointer knobs. One 1½ in. diameter knob. Paxolin, wire, sleeving, clip and prod, etc. Ferrite rod for L2 (2in. x ¾ in.).

the generator frequency.

The signal generator may be used to test or align a receiver in the normal way. The following brief details will help indicate how this work is carried out.

Checking Audio Circuits

If a receiver or audio amplifier does not operate, a quick check of the audio stages can be made by utilising the a.f. output of the signal generator. An insulated test lead with prod is used to apply the a.f. output to various circuit points in turn, working backwards from the loudspeaker. When the point at which a fault arises is passed, reproduction will deteriorate or cease.

As an example the first test will show if the loudspeaker is working. The next test will indicate if the output transformer is in order and connected. The output valve or transistors are then brought into the portion of the circuit under test by injecting the signal at the control grid or base. The coupling capacitor or driver transformer can then be checked by removing the prod to the input side of this component. Earlier a.f. stages are then taken in one by one.

This is a very rapid means of localising a fault. If such tests are carried out on a receiver or amplifier in good order this will show what to expect. When the a.f. signal is applied directly to a loudspeaker or output transformer and loudspeaker, volume is low. An earth return lead from generator to receiver chassis will be necessary when little or no amplification is available. To test a loudspeaker, output and earth leads must be taken to the speech coil. As one or more stages of amplification are introduced, by moving the output lead to grid or base, volume from the loudspeaker should increase considerably. The earth lead from generator to receiver is then often unnecessary.

If a fault is present in audio stages these tests will show where it arises. If the whole audio section of a receiver works satisfactorily this shows the defect is in earlier stages.

I.F. Testing, Alignment

If the receiver is already aligned, stage-by-stage tests of the intermediate frequency amplifier can be made in the same way as described for audio stages. However, the generator is tuned to provide a modulated radio frequency output corresponding to the receiver intermediate frequency. This is done by tuning the generator for best output from the receiver.

The signal may be injected at the final IFT primary. If the audio section has tested satisfactorily and there is no output from the receiver, then the IFT or detector or wiring here must be suspected. If output is satisfactory the prod is moved back to take in the last i.f. valve or transistor, then the preceding IFT and so on. The whole i.f. amplifier may thus be quickly checked.

The strength of the signal injected into the receiver is adjusted as required in a similar manner to that already explained. When a stage or two of i.f. amplification has been introduced into the part of the circuit being tested, loose coupling between prod and receiver circuit will generally be sufficient. That is, the prod point only need be placed near the receiver lead or against the insulation of the lead.

Should the receiver be newly built, and not aligned, the generator should be tuned to the wanted frequency (often 470kc/s). This signal is injected at the last IFT and the IFT core is adjusted for best output from the receiver. The previous IFT is then taken in and adjusted, followed by any earlier IFTs present.

As capacity from the generator prod will slightly influence alignment, all the IFTs are given a final check to see if any slight readjustment is wanted. This is done with the generator coupled to the input (grid or base) of the mixer or frequency changer.


When i.f. or earlier stages are being tested the receiver volume control should be at maximum, but volume should be kept quite low by reducing the strength of the injected signal as described. This is to avoid the automatic volume control circuit of the receiver making accurate adjustment difficult.

If some form of output meter is preferred to adjustment by ear this is easily arranged. A 25mA, 50mA or other d.c. meter may be added in one battery lead of transistor sets having push-pull output. Alignment is then to secure maximum meter reading. An a.c. voltmeter with 0.5 μ F or other blocking capacitor in one lead can be used as an audio output meter. A d.c. meter can be used to measure the anode current of an i.f. stage

to which a.v.c. is applied, adjustments being to obtain minimum current. The meter should be at the h.t. side of the IFT primary with a bypass capacitor to chassis. Alternatively a high-resistance voltmeter may be used to measure the a.v.c. line voltage. Adjustments are directed towards securing an increased negative voltage with valve sets. With transistor receivers the a.v.c. line is positive.

Mixer, R.F. Stages

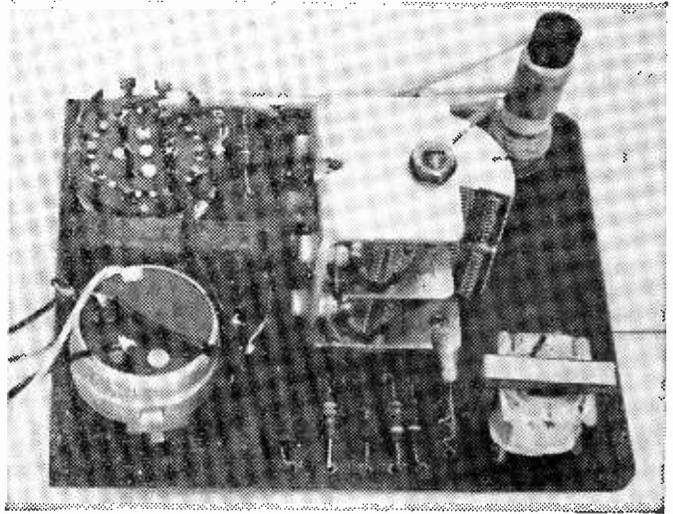Tests in r.f. stages are as described, the generator being tuned to the same frequency as



The instrument completely wired up, ready for installing in its case.

the receiver. To trim such stages adjust the generator to a high frequency (low wavelength). To make adjustments to coil or aerial inductance tune the generator to a low frequency (high wavelength). It is usual to deal with the m.w. band first, followed by long waves.

Sufficient input should be obtained by placing the generator prod or lead near the receiver aerial socket or frame aerial or ferrite rod. If trimming is initially badly out a fairly strong signal (closer coupling) may be used, followed by more accurate trimming on a weaker input (looser coupling).

To secure agreement with a printed dial, trimming and inductance adjustments are made as described for various frequencies after checking that the dial or pointer is properly fitted to the tuning capacitor. If a dial is to read accurately throughout, the tuning capacitors, trimmers, coils or aerial and padders must all be of the specified values intended for use together.

With mains operated equipment, remember to take the usual care to avoid shocks. Receivers of the a.c./d.c. type or sets drawing h.t. directly from the mains may have dangerous mains voltages present on the chassis, etc., if fed from a reversible two-pin plug or adaptor or from a wrongly wired three-pin plug. ■

A Novel A.F. Amplifier

BY E. A. PARKER

FIG. 1 is the circuit diagram of an amplifier which has been used for some time past in conjunction with a simple regenerative transistor receiver to provide loudspeaker output for a fairly large living-room. In fact the output was sufficient at times to make the provision of a volume control essential. The amplifier was found to be capable of driving loudspeakers of diameters of from 3in. to 8in. with equal efficiency and has been incorporated into a small portable t.r.f. receiver using a 3in. speaker.

Directly-coupled Output Stage

The main design considerations were that the amplifier should be easy to construct, economical to run and should require as few components as possible—this saved space and money. It was

was the circuit of Fig. 1, which seems to provide a large current gain in addition to providing an output well in excess of 100mW.

Alternative Transistors

The transistors used were XB102s (or XB112s) for Tr1 and Tr2 and an XC101 (or XC111) for Tr3, the output transistor.

Although Ediswan transistors were used the Mullard OC71 and OC72 (Tr3) are equally suitable. The amplifier also works well with surplus transistors (red spots for Tr1 and Tr2 and green/yellow spots for Tr3) but if these are used the directly-coupled pair should be selected so as to have low leakage currents.

The layout of the amplifier was not found to be critical and in view of this no constructional details are given, but Fig. 2 indicates the orientations of the connecting leads of the transistors. One point to note is that the emitter bias of the output pair tends to be slightly more critical than does that of a conventional single-ended output stage, but the value of 100Ω for the resistor R5 in the emitter leads as shown in Fig. 1 will be found to be satisfactory in most cases. Depending on the individual transistors used, the optimum value of this resistor should be found to be within the range 50-500Ω.

The interstage transformer T1 may be replaced by an R-C coupling circuit if economy demands this; the collector load

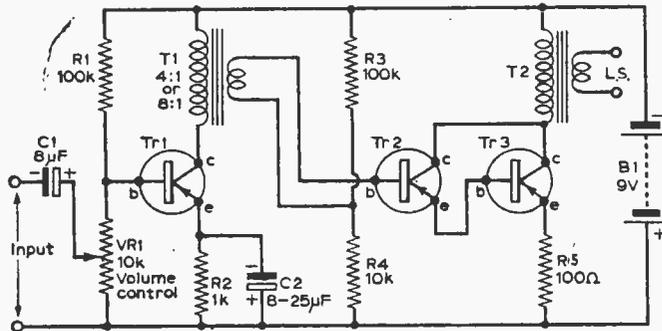


Fig. 1: The circuit of the amplifier.

decided, therefore, that two of the transistors should be d.c. coupled. Now audio amplifiers capable of driving a loudspeaker are as often as not of the push-pull variety, requiring expensive push-pull driver and output transformers and matched transistors. So an attempt was made to construct a directly-coupled output stage.

As stated above, the final product of experiment

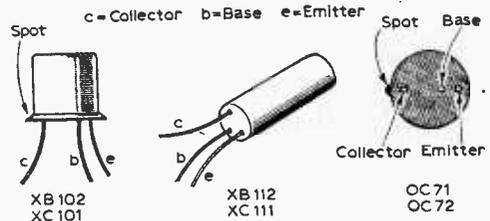


Fig. 2: Lead identification of types of transistors that can be used in this circuit.

COMPONENTS LIST

Resistors:

- R1 100kΩ
- R2 1kΩ
- R3 100kΩ
- R4 10kΩ
- R5 100Ω (see text)
- All 10%, 1/4W carbon.
- VR1 10kΩ potentiometer

Capacitors:

- C1 8μF electrolytic 12V
- C2 8-25μF electrolytic 12V

Transformers:

- T1 Interstage transformer; 4 : 1 or 8 : 1
- T2 Output transformer (see text)

Transistors:

- Tr1, 2 XB102, XB112, OC71 or red spot
- Tr3 XC101, XC111, OC72 or green/yellow spot

should then be of the order of 4.7kΩ and the coupling capacitor should have a value of 8μF with a minimum of 12V d.c. working voltage. A slight loss in stage gain will result with this arrangement.

Output Transformer

The output transformer T2 should be chosen so as to reflect a collector load of about 4.8kΩ to Tr2 and Tr3. If this load be designated by Rc and the

—continued on page 504

The PHOTOPHONE

By M. L. Michaelis

Experiments with
light waves - a new
interest for the amateur
electronics enthusiast.

CONTINUED FROM PAGE 427 OF THE SEPTEMBER
ISSUE

CONTINUING the discussion from last month on radiation, it may be said that the intensity of an electromagnetic radiation is given by the electric or magnetic field intensities on the wave picture and by the *average* number of photons arriving in a given time on the "photon" picture. It is necessary to stipulate "average" rate of arrival of photons in the second case because the actual sequence of arrival of photons, in common with all particle radiations, is quite random, subject to purely statistical fluctuations over short periods. This phenomenon has already been discussed in detail in connection with the digital Geiger counter apparatus published in this journal in the February, 1962, and following issues. The methods of interpreting quantitative results when forced to use the particle way of looking at things, rather than the wave method, at the very high frequencies represented by atomic radiations have also been described in the named articles.

Visible light represents just about the reasonable borderline case where it is about equally convenient to treat it statistically as a random sequence of particles, called photons, or to treat it as a continuous wave electromagnetic radiation. Indeed some optical devices are most conveniently treated on a basis of photons, whereas others are more conveniently explained on a wave basis, it always being necessary to remember that the two treatments amount to the same thing, and thus the practical engineer designing equipment operating at visible light frequencies will use the method of approach offering the greater simplicity in a given case.

A final point should bear this out. We are normally accustomed to thinking of light as a wave radiation, which is indeed more often than not the most useful line of approach. However, the photophone unit described in this article is an excellent example of the manifestation of the "photon" particle properties of light if we look more closely.

The detailed action is best represented by a "photon-for-electron" picture. Each photon particle of the incident light *actively* reaching the cathode of the photocell ejects one electron contributing to the resulting anode current. Were the rate of arrival of photons absolutely steady, then the stream of electrons produced in the photocell would be quite steady for an unmodulated steady beam of incident light. An audio amplifier connected to P2 would register no a.c. signal. Upon trying this in practice, however, we find that this condition is only approximately true. If the gain of the audio amplifier is very high, or at least reasonably high (e.g. both stages of an ECC83, followed by an EL84 output stage), a *powerful hiss* will be heard as soon as a steady beam of light is shone into the photophone. This shows that there are random statistical fluctuations taking place in the rate of arrival of the photons, leaving only a constant long-term average. Exactly the same hiss is heard if a Geiger counter is subjected to strong atomic radiation, giving a high average counting rate. The true average frequency of arrival of atomic particles, which may in that case, be in the region of 10kc/s, is not heard primarily, but rather the band of frequencies represented by the random variation, leading to a raucous hiss.

The same effect is found, yet again, in the thermionic emission of electrons from a valve cathode. The average rate of emission of electrons, representing the total saturation cathode current of which the valve is capable, nevertheless contains the short-period random statistical fluctuations characteristic of all particle emissions and radiations in Nature. These statistical fluctuations of cathode emission give rise to the same characteristic hiss, responsible for the major portion of "valve noise" in sensitive input stages of amplifiers.

The same statistical laws apply for the absorption of particle radiation as for its emission, thus if several grids and anodes are receiving each a certain average portion of the total cathode current the exact momentary partition of current among the electrodes is subject to further random statistical fluctuation, giving further hiss. Thus, as will doubtless be familiar to many readers, multi-electrode valves are more "noisy" than triodes.

Use of Valve Voltmeter

With the valve voltmeter circuit of Fig. 4 it is seen that, when using the universal probe shown, connected to P5, d.c. ranges of 5, 50 and 500V f.s.d. are available.

The upper range is not useful for the Photophone, being intended for general usage of the valve voltmeter, but the lower two ranges are so intended. For this purpose P5 of the valve voltmeter is connected directly with P1 of the Photophone without any probe. The probe

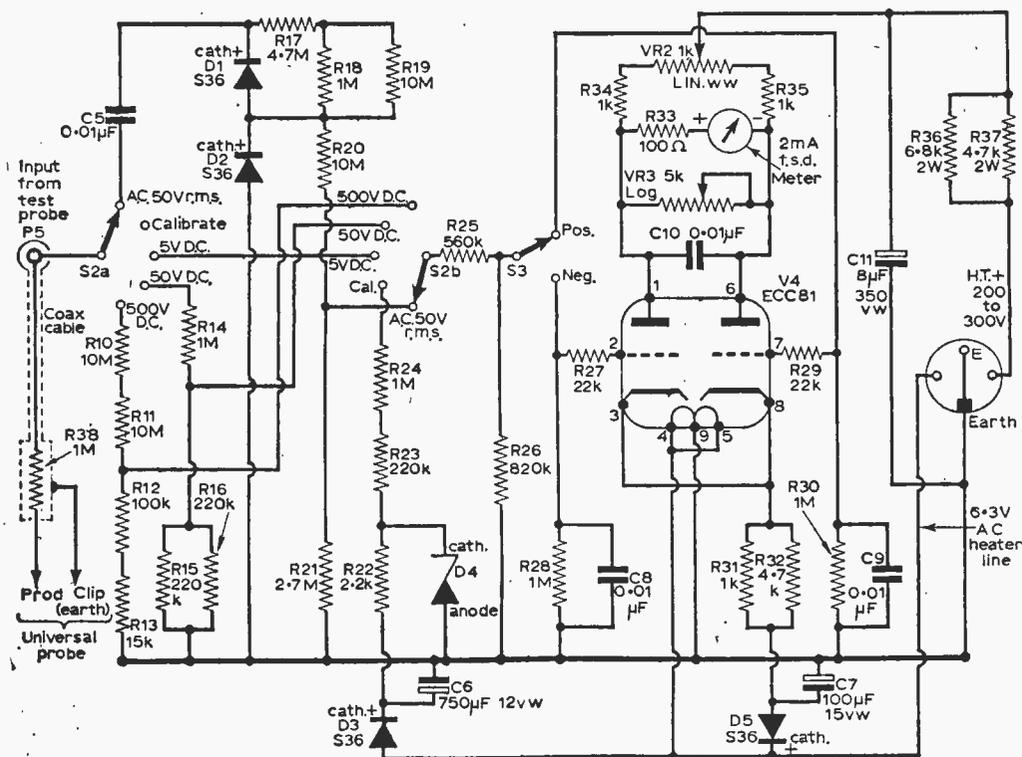


Fig. 4: A high quality valve-voltmeter circuit for use with the Photophone.

resistor R38 is missing under such circumstances so that the effective sensitivity is doubled, f.s.d. being obtained for 2.5 and 25V input respectively.

As the voltage calibrations on the meter for correspondence to readings with the universal probe are 5V or 50V f.s.d., and we have seen that an output of 0.5V per foot-candle is to be expected, the valve voltmeter readings on the existing voltage scales give foot-candles directly.

If, upon more accurate comparisons, corrections are found necessary to bring the voltage calibrations of the meter in Fig. 4 and the foot-candle values into true correspondence, various measures can be adopted. Within limits the values of R5 and/or R6 in the Photophone may be adjusted if only small corrections are required either way. If larger reductions are found to be needed, then suitable resistors may be included in series in the cable connecting P1 and P5.

Larger increases of sensitivity are best obtained by fitting a switch to select different values for R25 and R26 in the valve voltmeter when switching to "photometer" setting on this switch. Much greater overall sensitivity is easily obtainable by using a more sensitive meter. This can be fitted with a universal shunt for switching back to the 2mA f.s.d. sensitivity for normal use in the design of Fig. 4 or for multiplying the sensitivities of the incorporated voltage scales.

The Valve Voltmeter

It is not proposed to go too deeply into the principles of the circuit but merely to give sufficient information to enable the reasonably experienced reader to build the valve voltmeter.

The design is based on a simpler version which was published in the December, 1961, issue of PRACTICAL WIRELESS. This earlier design suffered to some degree in the matter of obtaining linearity up to full-scale deflection.

However, some further experiments have in the meantime been undertaken on this circuit, Fig. 4 showing the result. For the price of some appreciable increases in complexity, it was ultimately found possible to get good linearity to full-scale deflection for both positive and negative inputs, polarity-switching being undertaken by changing over between the two grids of V4 by means of S3.

The same 2mA meter was able to be retained and in fact virtually the same layout and design as published in December, 1961. Thus the same disposition of tagstrips was maintained and those readers who have already built the simpler instrument could very easily and quickly convert to the new comprehensive form.

Those building the unit new from scratch will find that the layout is not critical except for the need to mount the grid stoppers R27 and R29 very

close to the grids concerned and to connect nothing else directly to the grids. These grid stoppers were not required in the simpler circuit because this operated at much lower standing anode current, where parasitic oscillations were far less likely than in the present circuit.

In all other respects meticulous insulation, to avoid errors due to leakage in the high-impedance circuits, is far more important than any particular layout which may be chosen to suit individual requirements and available materials.

Methods of Cathode Bias

To get the present circuit to operate on negative inputs as well as positive ones, the operating point of the valve had to be shifted to higher current, at the same time retaining the relatively high cathode load to give proper coupling between the two sections. The only way of achieving this was to bias the cathodes down to a negative voltage, which was conveniently obtained at sufficient current capabilities by means of D5 and C7 from the heater line.

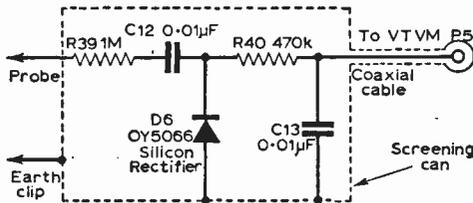


Fig. 5: An a.c. probe usable throughout audio, long wave, medium wave and short wave ranges, and able to tolerate all voltages present in normal receiver and amplifier circuitry. (See also table below).

Trimming the Valve Voltmeter

The combination R31, R32, as in the earlier circuit, remain the crucial components for proper operation. Too low a value gives insufficient deflection sensitivity on the meter, too high a value severe non-linearity in the form of cramping near full scale. This might, however, be considered useful in the interests of opening up low readings and those readers taking this point of view could use an appropriately calibrated non-linear scale attached to the meter.

To reduce the actual current swing required in the valve for f.s.d. meter deflection, it is useful to ascertain that as little current as possible is normally shunted through VR3. For this purpose R25 and R26 are simultaneously adjusted in such

COMPONENTS LIST FOR VALVE VOLTMETER

Resistors:

R10 10MΩ	R26 820kΩ
R11 10MΩ	R27 22kΩ
R12 100kΩ	R28 1MΩ
R13 15kΩ	R29 22kΩ
R14 1MΩ	R30 1MΩ
R15 220kΩ	R31 1kΩ
R16 220kΩ	R32 4.7kΩ
R17 4.7MΩ	R33 100Ω
R18 1MΩ	R34 1kΩ
R19 10MΩ	R35 1kΩ
R20 10MΩ	R36 6.8kΩ 2W
R21 2.7MΩ	R37 4.7kΩ 2W
R22 2.2kΩ	R38 1MΩ
R23 220kΩ	R39 1MΩ
R24 1MΩ	R40 470kΩ
R25 560kΩ	

All carbon 1W ±20% unless otherwise stated

Capacitors:

C5 0.01μF paper 500V
C6 750μF electrolytic 12V
C7 100μF electrolytic 15V
C8 0.01μF paper 500V
C9 0.01μF paper 500V
C10 0.01μF paper 500V
C11 8μF electrolytic 350V
C12 0.01μF paper 500V
C13 0.01μF paper 500V

Miscellaneous:

V4 ECC81 (noval holder)
D1-3 Diode Type S36. Inverse resistance 10MΩ or better. Inverse voltage rating 350.
& D5 Capacity approx. 10pF or less. Forward current 20mA or more.
D4 5V Zener-diode
D6 Silicon mains rectifier Type OY5066. Inverse voltage rating 700. Current rating unimportant. Selected specimen for performance up to 20Mc/s in Fig. 5.
S2 2-pole 5-way ceramic rotary switch; high insulation
S3 Single-pole double-throw toggle switch
VR2 1kΩ lin. carbon or wire-wound
VR3 5kΩ log. carbon
Meter 2mA f.s.d. moving-coil
P5 Coaxial socket
P6 4-pole socket (as on Grundig tape recorders)
Chassis, casing, wire, solder, bolts, etc.

Full scale deflection at 50c/s mains frequency input, using this probe in P5 of the prototype valve voltmeter (Fig. 4) represents:—

VTVM switched to: Sensitivities:

50V r.m.s. a.c. range	Do not use here
5V d.c. range	15V r.m.s.
50V d.c. range	150V r.m.s.
500V d.c. range	500V r.m.s.

Notes: (1) The sensitivities given hold true up to about 100kc/s and down by factor six at 20Mc/s in the prototype. (2) On the 500V d.c. range do not exceed 250V r.m.s. input.

This, incidentally, is a most useful general method of biasing a cathode negative wherever this may be required in a circuit to enable the cathode-load resistor to be increased without choking back anode current. The converse of biasing a cathode more positive still than the voltage given anyway by virtue of anode current through the cathode load, is available by means of taking an additional high resistor from the cathode to h.t. positive, a measure capable of driving the valve even beyond cut-off in the resting state. This is, of course, never possible with a cathode load alone, for a cut-off valve takes no anode current and thus cannot produce bias across a cathode load, and thus could not be cut off, which contradiction proves the impossibility.

a manner that the dividing ratio is altered, but the sum of R25 and R26 in parallel with 1M Ω remains equal to 1M Ω —in order that the input voltage dividers to the left of S2b remain correct.

This adjustment of R25 and R26 is undertaken on the "calibrate" setting, with VR3 disconnected, until the meter only still reads *very slightly* high, final correction then being continuously available on VR3 when this is reconnected. This adjustment of R25 and R26 has already been carefully undertaken in arriving at the component values specified and these should be found satisfactory.

If trouble is experienced, readers should first check for low emission in V4 by substitution and also check that R25 and R26 are of the values specified.

Further New Features

While modifying the original simple valve voltmeter circuit to a form ideal for use with the Photophone, other changes were made to improve its general usefulness, again at some additional expense and complication.

The two grid circuits have been fully symmetrised and kept to normal impedance levels of around 1M Ω . This avoids trouble from zero point drifts due to electron impact grid current otherwise present in high-impedance grid circuits and also makes the zero point fall at virtually the same setting of VR2 on *all* ranges.

Furthermore the zero point now falls very close to the middle position of VR2 under all conditions and requires only very infrequent adjustment after an initial five to ten minutes' warming up. These advantages have been obtained at the price of one disadvantage over the original, namely a reduction of overall impedance presented as load across the voltage source being measured. However, a reasonable compromise has been struck.

The disposition of smoothing capacitors has been changed to give a quicker response and quicker return to zero and a high resistance has been removed to the probe head to prevent a.c. damping stopping, for example, oscillators functioning when d.c. potentials at electrodes are to be measured.

Furthermore the whole aggregate around D1 and D2 has been incorporated to give a 50V r.m.s. f.s.d. range for a.c., usable at mains frequency only, without changing probes. The combination R17 to R19 should be adjusted until this scale reads correctly; it may be possible to select a single 5.6M Ω resistor in place of these three. The new circuit uses a pair of diodes, D1 and D2, for achieving high inverse voltage rating, preventing damage even if the a.c. signal is superimposed on a d.c. voltage of some hundreds of volts, which is blocked at C5.

It is thus possible to measure the gain of amplifier stages with this instrument, using a 50c/s sine-wave signal and comparing levels at grid and anode, without any need to be concerned with d.c. potentials which may or may not be present. Finally the work on this valve voltmeter was completed with the design of a special a.c. probe, for use at other frequencies, operating into the d.c. ranges. This rectifies at the probe head in the usual way so that high-frequency signals do not have to pass down the coaxial cable and get lost in the capacity thereof.

Experiment revealed the interesting fact that, although D6 is a silicon rectifier intended for mains power rectification, usable performance was possible at frequencies up to 20Mc/s. The high inverse voltage rating of the silicon diode is a great advantage, so that this probe cannot be damaged by any normal h.t. voltages found in receivers and amplifiers. Otherwise it is of the conventional form already mentioned in the other publications.

Conclusion

It is hoped that this article has been successful in introducing the possibilities of optical frequencies for radio experiments as well as explaining some of the significances and aspects of various types of radiation in the light of modern science in a form which is surely of a more practical usefulness for the understanding of one's equipment than mere philosophical theory for which it might at first sight be mistaken. ■

Novel A.F. Amplifier

—continued from page 500

Loudspeaker impedance by RL, then use a transformer of turns ratio $n = \frac{\text{number of primary turns}}{\text{number of secondary turns}}$ where $n^2 = \frac{R_c}{R_L}$

The following table gives the value of n for three popular loudspeaker impedances. (Here, R_c 4.7k Ω .)

Loudspeaker impedance (RL Ω)	Output transformer turns ratio (n:1)
3	40:1
8	25:1
35	10:1

The transformer used by the writer was abstracted from a defunct battery operated valve portable receiver—its physical size was small enough.

Additional Pre-amplifying Stages

Clearly the number of transistors preceding the output pair may be varied according to the number available and the final output required; three such transistors would overload the power output transistor Tr3 on loud passages of music if the amplifier is used with an average local station t.r.f. receiver. Only one was required in the writer's home town (Orpington, Kent) to provide ample listening volume on the Light Programme (247m) and the Home Service (330m) from a one-transistor regenerative receiver with a 5in. loudspeaker connected to the amplifier outputs.

The amplifier is powered by a PP7 (9V) battery which has a life of more than 70 hours when the amplifier is run at full volume. ■

RADIO-AMATEUR GEAR
EDUCATIONAL KITS



TEST INSTRUMENTS
HI-FI EQUIPMENT

*With the clearly-written instruction manuals,
anyone can build any of these models—
Have the world's best equipment—and save money*



AMATEUR BANDS RECEIVER. Model RA-1. Covers all Amateur Bands from 160 to 10m. Special features incl. half lattice crystal filter, 8 valves, signal strength "S" meter, tuned R.F. amplifier stage £39.6.6

HI-FI F.M. TUNER. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s. I.F. output (£2.15.0 inc. P.T.). I.F. Amp. (FMA-4U) complete with cabinet and valves, (£12.6.0). Total ... £15.1.0



5W HI-FI MONO AMPLIFIER. Model MA-5. A low-priced amplifier based on the S-33. Printed circuit construction makes it easy to build £10.19.6
STEREO CONTROL UNIT. USC-1. Luxury model with inputs to suit any pick-up or tuner £19.10.0
MONO CONTROL UNIT. Model UMC-1. Ideal for use with MA-12 or similar amplifier. Send for specification £8.12.6
HI-FI EQUIPMENT CABINETS. Large range, in kit form or assembled and finished, available to meet various needs. Details on request from £6.19.6 to £29.8.0

6W DE LUXE AMPLIFIER. Model S-33H. An inexpensive Stereo-Mono amplifier, with high sensitivity. Suitable for Decca Deram cartridge £15.17.6
6 TRANSISTOR PORTABLE. Model UXR-1. Prealigned I.F. transformers. Printed circuit, 7 x 4in. high flux speaker. Real hide case. Very easy to build £12.11.0
SHORTWAVE TRANSISTOR PORTABLE. Model RSW-1 Two short bands, trawler and medium wave £19.17.6 (Inc. P.T.).
HI-FI A.M./F.M. TUNER. Covers F.M. 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 inc. P.T.) and I.F. Amp. (£20.13.0). Printed circuit board. Total ... £25.6.6



"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-U. Fully Transistorised. Excellent portable or general purpose receiver for amateur or short wave listening. See full spec. leaflet. £39.17.6

NEW!
"OXFORD" LUXURY TRANSISTOR PORTABLE. Model UXR-2. The ideal domestic, car, or personal portable receiver. 10 Semi-conductors. Send for full details. £14.18.0 (inc. P.T.).



Assembled models also available; prices on request — Deferred terms available over £10. Free delivery U.K.

SEND FOR FREE BRITISH HEATHKIT CATALOGUE—OVER 50 MODELS TO CHOOSE FROM

AVAILABLE SHORTLY

GIUITAR/PA AMPLIFIER. Model PAI. 50 W. rms. 100 W. pk output. For vocal and instrument groups, public address etc. 4 inputs, 2 loudspeakers. Send for full details ... £54.15.0



S-33

6 W STEREO AMPLIFIER. Model S-33. 3 w/chl. Inputs for radio-tape-gram. Stereo/Mono ganged controls. Sensitivity 200 mV. £13.7.6


HI-FI 18 W STEREO AMPLIFIER. Model S-99. Ganged controls. Stereo/Mono gram, radio and tape recorder inputs. P/B selection. £27.19.6

PORTABLE SERVICE OSCILLOSCOPE. Model OS-1. Compact portable scope, ideal for servicing and general work. Printed crct. Case 7 1/2 x 4 1/2 x 12 1/2 in. long. Wt. only 10 1/2 lb. £19.19.0
5in. OSCILLOSCOPE. Model O-12U. Wide band amplifiers essential for TV servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges £35.10.0
VALVE VOLTMETER. Model V7A. Measures up to 1,500 volts (D.C. and R.M.S.) and 4,000 pk. to pk. Res. 0.1Ω-1,000MΩ £13.18.6

HI-FI SPEAKER SYSTEM. Model SSU-1. Two speakers in ducted port bass reflex cabinet. Bookcase model £10.17.6 Legs 14/6 extra.

MULTIMETER. Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. A.C. and D.C. 150μG-15A D.C. 0.2Ω to 20MΩ 4 1/2 in. 50μA meter £12.10.0

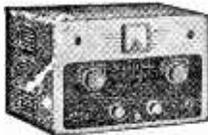R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s on harmonics. Up to 100 mV output all bands £12.15.6




DX-40U

250 AMERICAN HEATHKIT MODELS
Full details of direct Mail Order Scheme and catalogue can be obtained from us for 1/- post paid. (FREE to Service Departments).

AMATEUR TRANSMITTER. Model DX-40U. Self-contained. 80-10 m. Power input 75 w. CW., 60 w. peak C.C. phone. Output 40 w. to aerial. Provision for V.F.O. £33.19.0

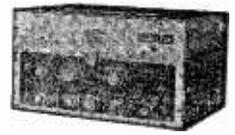AMATEUR TRANSMITTER. Model DX-100U. Covers all amateur bands, 160-10 m. 150 w. D.C. input, self contained with power supply. Modulator, V.F.O. £74.19.0



DX-100U

DAYSTROM LTD.

Dept. P.W.10, GLOUCESTER, ENGLAND.

A member of the Daystrom Group, manufacturers of the
WORLD'S LARGEST-SELLING ELECTRONIC KITS

Send me **FREE BRITISH CATALOGUE** (Yes/No)

Full details of model(s).....

NAME

ADDRESS


PW10

INEXPENSIVE BASIS OF A COMPLETE HI-FI SYSTEM

OR TOP QUALITY RADIOGRAM


Armstrong

STEREO 55 TUNER AMPLIFIER CHASSIS

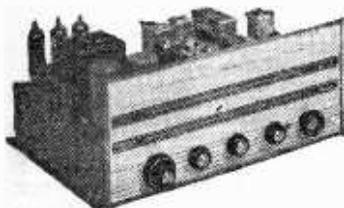

One compact chassis combines AM and FM tuners, Stereo Control Unit and two High Fidelity Amplifiers. For mono reproduction the two amplifiers are used together so that up to 10 watts output is available. Provision for tape recording and play back is made with a choice of inputs for crystal or ceramic pick-ups including the Decca Deram. The facilities are also available for use with a tape deck and its associated pre-amplifier.

PRICE £29.18.0

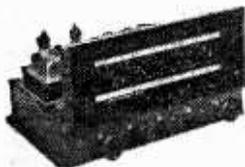

AF 208 AM/FM CHASSIS

A high quality tuner amplifier chassis which can be used for the conversion of an existing radiogram or as the basis for building a new radiogram or reproducing system. A system which can include tape recording and play back as well as the normal AM and FM radio and record reproduction.

PRICE £21.4.0

Write for descriptive literature to

ARMSTRONG (Dept. POC.)

Walters Road, London, N.7. Tel: NORTH 3213

WHARFEDALE SUPER 8/RS/DD

"Strikes the right note"

SAYS DONALD ALDOUS




In a review of the Wharfedale Super 8/RS/DD in "Audio & Record Review", Donald Aldous reported as follows:—

The latest Wharfedale Super 8/RS/DD speaker strikes the right note the moment it is removed from its box. It is beautifully made and finished and looks right.

The unit was tested in a corner enclosure approximately 1½ cu.ft. with the interior heavily lined with carpet felt and a vent of 1½ in. wide across the front at the bottom. The bass radiated with this enclosure was smooth and at an ideal level to give balance with the extended top response.

The music signals and tone bursts confirmed that the speaker is free from any obvious discoloration.

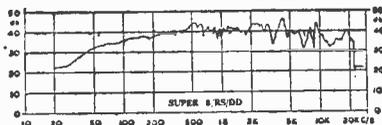Summary—We agree entirely with the view of Gilbert Briggs expressed to us as "his humble opinion", that the Super 8/RS/DD unit is easily the best 8 in. model Wharfedale has ever produced. A stereo pair in small enclosures gives sound quality that will come as a revelation to any listeners wedded to massive enclosures. This can easily be matched to 2-5 ohms with the WMT1.



Impedance 10/15 ohms.
 CERAMIC MAGNET Flux density 14,500 oersteds.
 Total flux: 60,000 maxwells.


PRICE 134/2 incl. P.T.



**WHARFEDALE
 WIRELESS
 WORKS LTD**

IDLE BRADFORD YORKSHIRE

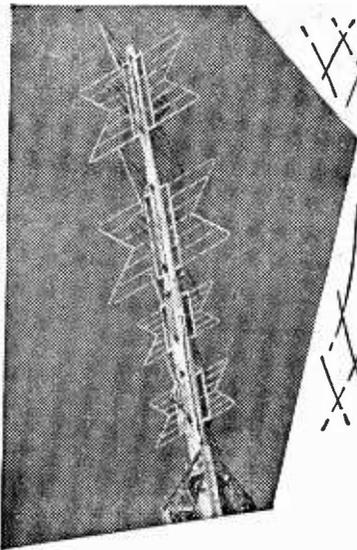Telephone: Idle 1235/6 Telegrams: 'Wharfed' Idle, Bradford



On Your Wavelength

By THERMION

While thorough-going wiring-up methods are justified with equipment required for military or similar purposes, they are not warranted (or indeed desirable) with more commonplace equipment. But, let me emphasise, guard against going to the other extreme of merely bringing the two surfaces into contact and relying on a generous blob of solder to do the rest. True, I admit, that this procedure can be quite effective with some miniature components where mechanical strain is negligible. Even so, I consider it advisable to make a self-supporting connection wherever this is at all possible. This is certainly no hard task, and the following suggested methods will usually suffice.

Push the lead through the hole in the tag and, if it is a loose fit, bend the protruding portion just sufficiently to provide a locking effect, then cut off the surplus wire fairly close to the tag. With larger components it is sometimes necessary to make a full right-angled bend and to squeeze the end of the wire against the flat surface of the tag. Where the lead is not passed through a hole in the anchoring device, it should be hooked around the edge of the tag or terminal.

A Tape Teaser

One of the interesting uses to which magnetic tape recording is now being applied is the training of foreign language students in correct pronunciation. Recording systems known as "Language Laboratories" allow a number of students to perform oral exercises simultaneously without causing interference.

The usual method of operation is like this: each student sits in a booth equipped with a special tape recorder and, via headphones, listens to speech pre-recorded by the tutor. This recording is divided into a number of fairly short passages, and each is followed by a pause of similar duration. At the end of each passage the student repeats this phrase or sentence into his microphone endeavouring to copy faithfully the pronunciation of the original.

Whenever he wishes, the student can rewind his recorder and set it to playback. He then hears once again the tutor's voice followed immediately by his own efforts at imitation. For further practice he resets to record and proceeds as before, his earlier efforts being erased in the process, as is normal.

The little problem I now leave you with is this: how is it contrived that the tutor's recording remains preserved throughout and cannot be erased by the student no matter how often he re-records his own voice in the gaps provided?

IT is unfortunately true that some amateur constructors (and not only "beginners" at that) fail to take sufficient pains with their soldering operations. Bad workmanship really does not pay, since much time and effort are often spent afterwards in tracking down obscure faults that have their origin in inadequately made connections. Even when satisfactory performance is obtained initially, there is always the danger of leads becoming disconnected later due to the shock or vibration sustained under normal working conditions. This applies particularly to miniature receivers and to other electronic equipment of a portable nature.

One of the cardinal rules of soldering is that a sound mechanical joint should be made before the solder is applied. (It is, of course, essential that the mating surfaces are perfectly clean and free from grease and such like.)

Joints, Various

Now, what constitutes a sound mechanical joint? Certainly it is not necessary to go to the lengths illustrated by some ex-government radio and electronic equipment. Most of my readers will have handled surplus equipment of one sort or another, and many of you will have had experience in stripping down various specimens for the sake of the components contained therein. I recall the tussles that occurred when trying to detach resistors and capacitors from groupboards—the difficulty arose because the manufacturers' wiremen, dutifully following the Ministry's directions, had tightly wrapped each component lead two or three times (if not more) round the tag prior to soldering. The problem was always whether to arm oneself with soldering iron and long-nosed pliers and attempt to acquire the desired component complete with its leads, or whether to take the simpler course and to seize the diagonal cutters and amputate!

PERSONAL TRANSISTOR TWO

A Simple Medium
Wave Set Suitable
for the Beginner

BY A. SYDENHAM

ONLY a comparatively small cash outlay is involved in the construction of the receiver to be described and little or no test equipment is required to bring it into use.

Quite often a newly constructed superhet fails to provide any kind of signal when first switched on due to severe misalignment, but this is not likely to occur here as only a single tuned circuit is used. This set can, if necessary, be built quite easily on the kitchen table and no risk of lethal mains shocks is likely since transistors are used, two being employed since this is about the minimum number capable of providing a decent signal in a pair of headphones.

The prototype has also been tested with a loudspeaker by substituting the primary of a ratio 8:1 transistor output transformer in place of the headphones and connecting a 3Ω loudspeaker unit to the secondary winding. If the surroundings are quiet, as in a bedroom, for example, programmes can be heard quite well.

The receiver is powered by a single 4.5V dry battery and the current consumption is so low (less than 1mA) that replacement is likely but rarely.

The frequency coverage is 600-1460kc/s (500-205m), this covering practically the whole of the medium waveband. If long-wave reception is required this can be incorporated but has not been attempted in the prototype.

In common with all simple t.r.f. circuits arranged to work at their most sensitive point the receiver is likely to prove slightly temperamental at the first try-out and slight adjustments to certain of the components might be occasioned. This point has been taken care of in the layout, however, which if followed accurately will allow changes to be made very easily. The range of component tolerances and the pro-

duction spreads in the transistors, etc., cause discrepancies that cannot be disposed of cheaply.

The Circuit

In Fig. 1 it may be seen that the first transistor Tr1 is operated as a regenerative demodulator feeding a stage of audio amplification built around Tr2, high impedance headphones being inserted in the collector circuit of this transistor to enable the user to hear the selected programme.

The circuitry around Tr1 might be more easily understood by referring to Fig. 2, where a typical

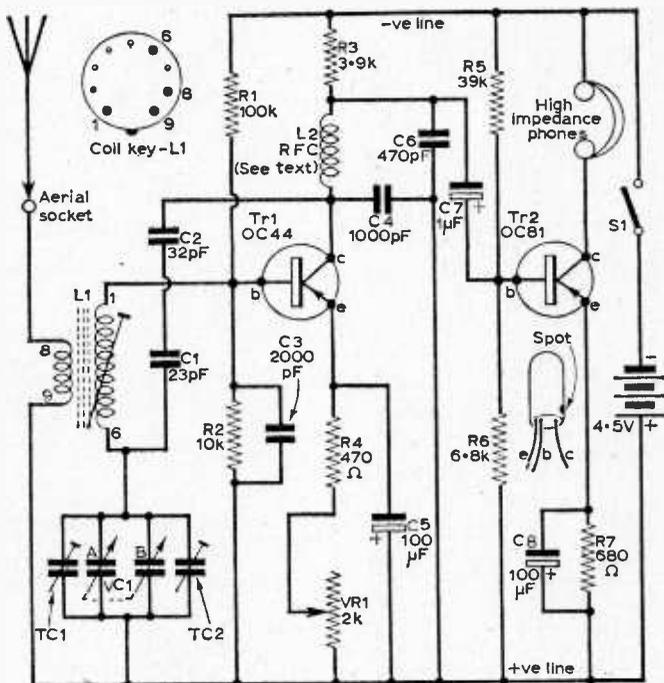


Fig. 1: The circuit.

valve oscillator circuit is shown. Here the external tuning of the coil L is effected by capacitors Cx and Cy. Sometimes no resistor is included in the cathode circuit, bias for the valve being derived entirely from grid current. This circuit is widely used, the triode usually being part of a frequency changer valve when Cx is often made one section of a twin-gang tuning capacitor with Cy operating as a "padding" capacitance.

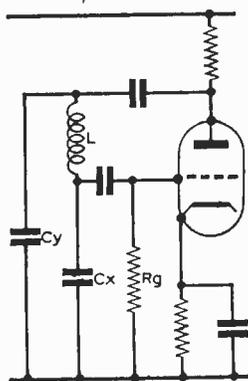


Fig. 2: A typical valve oscillator circuit.

Looking now at the circuitry around Tr1 (Fig. 1) the similarity will immediately be apparent and it will be appreciated that the transistor will oscillate if operating conditions are suitable.

By controlling the emitter current by means of a variable resistor bypassed by a capacitor, detection can occur if the transistor is not allowed to oscillate but instead is brought close to the point of the occurrence.

A suitable impedance match into the base of Tr1 can be effected by employing a capacitive potentiometer across the coil and using one section of it for tuning. Capacitors VC1 and C3 perform

this function and are in effect identifiable with Cx and Cy respectively in Fig. 2.

Since these capacitors are connected across the coil in series the total value of capacitance available will always be less than that of the smaller of the two. This reduced capacitance effect will make itself most apparent at the low-frequency end of the band, i.e. where the vanes of C1 are most fully engaged, and if a suitable coil is not used for L1, only a section of the band will be receivable. Fortunately suitable coils are available from the Denco miniature range.

A miniature Jackson "00" twin gang with sections paralleled (208+176pF) form a total value of 384pF, ignoring the trimmers, but this is reduced to about 330pF by C3 and is then suitable for use with the coil specified. When another coil designed to work with a 500pF tuning capacitor was tried in the circuit maximum low frequency coverage was reduced to 750kc/s.

Note that two capacitors—C1 and C2—are fitted between Tr1 collector and L1; this is not a safety

COMPONENTS LIST

Resistors:

- R1 100kΩ
- R2 10kΩ
- R3 3.9kΩ
- R4 470Ω
- R5 39kΩ
- R6 6.8kΩ
- R7 680Ω

VR1 2kΩ wire-wound potentiometer

Capacitors:

- C1 23pF mica
- C2 32pF mica
- C3 2,000pF ceramic
- C4 1,000pF mica
- C5 100μF electrolytic 6V
- C6 470pF mica
- C7 1μF electrolytic 6V
- C8 100μF electrolytic 6V
- VC1 208pF } twin-gang variable (Jackson '00')
- 176pF }
- TC1 } trimmers—with VC1
- TC2 }

Switch:

- S1 Toggle switch, on/off

Inductors:

- L1 M.W. coil (Denco Yellow dual purpose, range 2)
- L2 R.F. choke (see text)

Transistors:

- Tr1 OC44
- Tr2 OC81

Miscellaneous:

- Miniature 18-way tag board 4½in. x 1¼in. (Radio-spares). Battery 4.5V (Ever Ready 1289). High impedance headphones. Panel material, hard-board, Aerial and phone sockets. Control knobs.

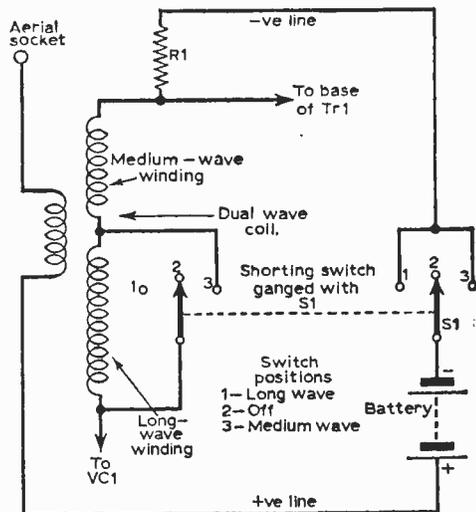


Fig. 3: The modified circuitry necessary to provide long wave coverage.

measure but an aid to obtaining good results on completion, since these items control the amount of positive feedback to a great extent.

The efficiency of the receiver largely depends upon the characteristics of Tr1 and this should be a good specimen; the use of a surplus type is not recommended.

The small r.f. choke of 3.000μH inductance (L2) fitted in the collector circuit of Tr1, consists of the main winding of a dust-cored long-wave coil, the primary winding being removed and the coil former sawn off to the length of the core.

As mentioned earlier, inclusion of long wave-band facilities can be provided either by fitting a separate coil from the Denco range (Range No. 1) or by using a miniature dual-waveband coil as shown in Fig. 3. The additional switching required can be incorporated with S1 by using a rotary switch. A two-pole, three-way switch used as shown will allow the central position to be "off"

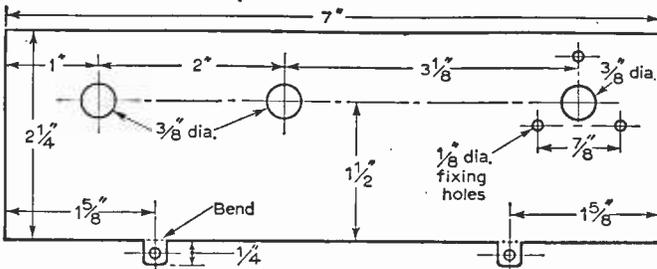


Fig. 4: Dimensions of the control support panel.

with "medium" and "long" situated on either side. This makes accidentally leaving the receiver switched on less likely than in other arrangements. No extra panel control will be needed if this idea is followed.

Constructional Notes

The receiver is built around a miniature 18-way tag board to which is affixed a simple metal panel that carries the three controls. This assembly is finally located on a main hardboard panel to which simple sections are finally fitted to form a cabinet. A short throw-out type aerial is required and this, together with the headphones, is plugged into sockets provided on one side. The completed receiver is 7 1/2 in. wide and 5 in. high and the front slopes backwards slightly, for the sides taper from 3 in. at the base to 2 1/2 in. at the top.

Preliminary work consists of constructing the metal control support panel from 16s.w.g. aluminium or tinfoil and details of this are given in Fig. 4. Prior to bolting this panel to the tag-board, one of the small holes running down the centre of the board must be enlarged with a circular file to 1/4 in. diameter—as indicated in Fig. 6—to accept the coil mounting stem. The coil is locked in position by means of a polystyrene nut provided and this should only be twisted thumb tight, if pliers are used the stem will fracture.

Wiring Up

The remaining construction consists of mounting and wiring the various components to agree with the above and below plans shown in Figs. 5 and 6 respectively, leaving the transistors to one side until a good check has been made.

When satisfied that no mistakes have been made the lead-out wires of the transistors may be sleeved and then passed through existing holes from above the board. These may then be soldered to the tags shown, using a heat shunt. The actual transistor shells should

remain on top of the paxolin board as shown in the photographs and diagrams.

Black and red insulation should be used for the battery negative and positive leads respectively and it is not difficult to fashion a pair of sliding clips from thin tinfoil to act as connectors soldered to the ends of the leads.

Testing

High impedance headphones should be connected before switching on and these should not be removed whilst the set is working or Tr2 collector circuit will be broken. With VR1 set to approximately half travel and a short aerial connected the set may be switched on and C1 swung through its full range of rotation. If oscillations are heard all is well, but VR1 should be adjusted very quickly to just remove them, when little difficulty should be experienced in receiving transmissions. The quality should be crisp and will be surprisingly clear and alive. It will now be discovered that VR1 can be used as a volume control and should normally operate very smoothly indeed. Smoothness of operation will best be obtained from use of a wirewound component in

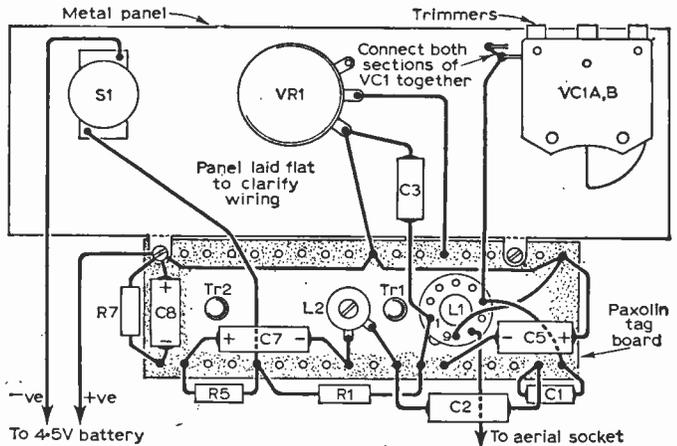


Fig. 5: Showing connections between the tag board and control panel. The tagboard has been drawn in the same plane as the panel for clarity.

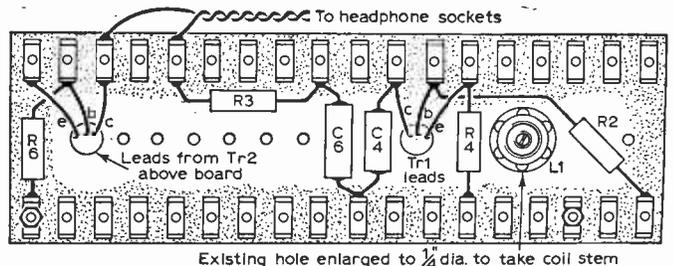


Fig. 6: The reverse side of the tag board.

the VR1 position, but care should be taken not to advance the control excessively or the programme material will be supplanted by undesirable oscillation.

Final Adjustments

The next step lies in adjusting the waveband coverage. If no signal generator is available transmitters must be used and the various regional transmitters can most easily be recognised at such times as separate news bulletins are being radiated. After dark Radio Luxembourg might be heard when the vanes of VC1 are almost fully disengaged. The coverage can be varied within limits by adjusting the core of L1 by means of the brass stem fitted and also by changing the trimmer positions.

Faults

If the receiver fails to oscillate at any setting of VR1 or VC1, either C1 or C2—but not both together—may be temporarily short-circuited to increase feedback. Resistor R1 might need changing also if an indifferent transistor is in use and the value may be reduced to about 56kΩ. Noise may result in the form of a rushing sound if R1 is excessively reduced in value and 39kΩ is about the limit.


If on the other hand it is not possible to eliminate oscillations at any setting of VC1 or VR1, remove C2 and replace it with one of smaller value—say 10pF—and try again. Emitter resistor R4 can also be increased to, say, 680Ω or even 820Ω,

this further limiting Tr1 current. The receiver should, of course, be switched off to make alterations.

Cabinet

Since negligible weight is involved it is possible to construct a simple cabinet from hardboard using a frame of 3/8 in. quadrant beading mitred at the corners to improve the frontal appearance. The dimensions of the case used for the prototype are shown in Fig. 7 the whole being held together with impact adhesive and small reinforcement strips.

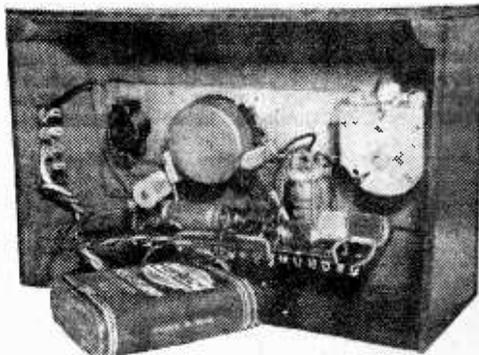With the aerial and phone sockets mounted on



A rear view of the receiver nearing completion.

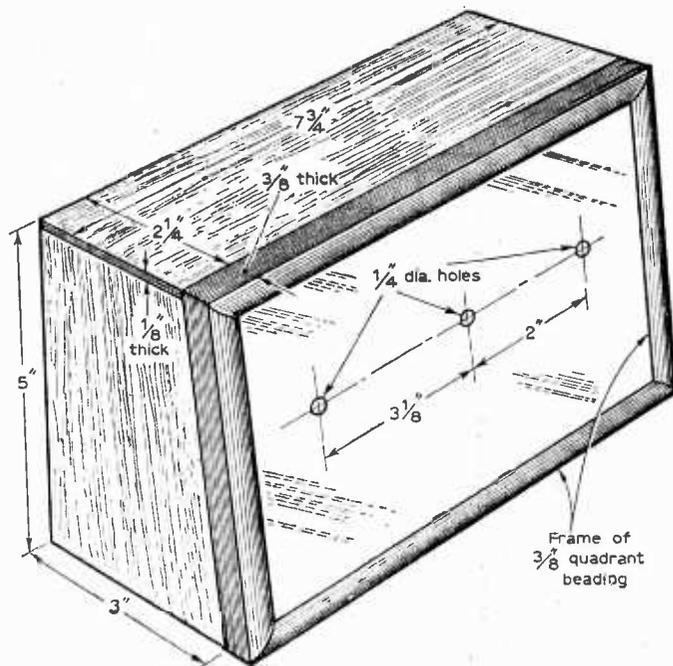


Fig. 7: The construction of a simple cabinet for the receiver.

one side, ample space exists for the battery which can if necessary lie flat on the cabinet base plate beneath the tag-board or stand at the rear. On completion the case may be lacquered or otherwise finished to suit individual tastes.

Conclus'on

Although this simple little set can provide a great deal of constructional and listening enjoyment, it obviously has its limitations and cannot be expected to compare with the high sensitivity and selectivity of the superhet form, for, of course, it is not in the same price class.

The receiver can be used as a simple tuner to feed an existing audio amplifier by connecting a 4.7kΩ resistor in place of the phones and taking the audio from between Tr2 collector (via a 0.1μF capacitor) and the positive line.

No such connection must be made under any circumstances to d.c. apparatus or to so called a.c. equipment that derives its h.t. direct from the mains supply or danger to life will result.

The EUPHON

A frequency selective unit for feeding two loudspeakers

By I. Kampel

THE unit about to be described is a simple and inexpensive means of obtaining a special effect in audio reproduction. With the addition of the two loudspeakers required, the total cost of the author's model was about two guineas only, and this included the cost of making the walnut cabinet.

Two loudspeakers are set up as for stereo, but instead of two channels, one loudspeaker handles the lower frequencies, while the other handles the higher frequencies. With the aid of the balance control an effect similar to stereo is achieved as the

arrangement having the same effect as a single paper capacitor, though not the same value as used in the conventional divider network. The two coils are the most expensive items (7s. 6d. each) and are of 3Ω to match the output transformer. The potentiometer of 25Ω simply acts as a balance control between the two loudspeakers to obtain bass or treble emphasis, or a perfect balance as required.

Cabinet construction

The whole unit may be built into a cabinet 7½ in. x 4¼ in. x 2¼ in. A small square of ¼ in. five-ply will be good enough for the first stages of construction. Fig. 2 shows an end elevation. The cross shaded triangle in Fig. 4 is a small length of ¼ in. quadrant. The two end pieces of Fig. 2 fit on to the sides of the 6¼ in. x 4¼ in. baseboard. However, the top, which is made to slide out, rests on the top of these two edges and hence is ¼ in. greater in

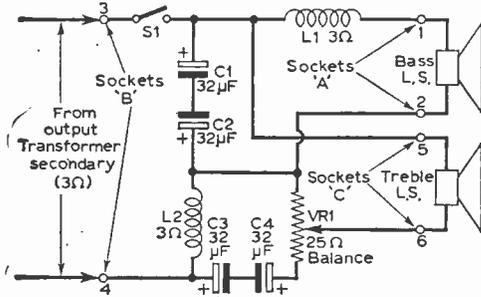


Fig. 1: The simple circuit of the Euphon.

higher pitched instruments come through on the tweeter and the bass instruments on the woofer.

The idea is based on the familiar divider network, used in modern audio equipment, but the original crossover circuit is not suitable when the speakers are separated as there will not be enough volume in the tweeter to give the required effect. The conventional divider network uses paper capacitors and extra components, whereas the Euphon uses ordinary electrolytics.

Fig. 1 shows the circuit. On the actual model there are single-type wander-plug sockets at the back of the cabinet, to plug in the bass and treble loudspeakers, and also sockets for the radio input. Numbers 1 to 6 indicate these sockets.

The circuit incorporates four identical electrolytic capacitors coupled in pairs, can to can, this

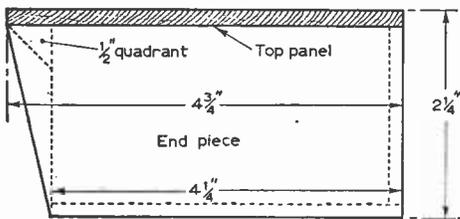


Fig. 2: An end view of the cabinet.

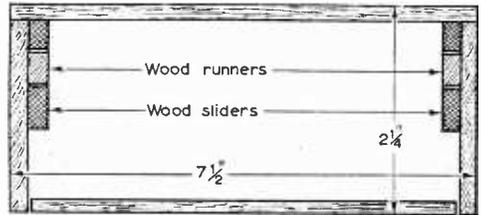


Fig. 3: This front elevation shows the wooden runners fitted to the sides.

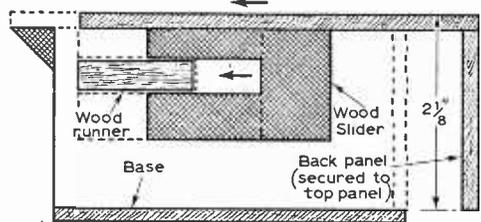


Fig. 4: How the top is slid into place along the runners and tops of the sides.


length. Fig. 3 shows this, the shaded portions being the ends.

Fig. 4 shows the method of sliding the top into place, the back being permanently joined. Crossed shading indicates the extra shaped pieces of ply fitted to the top panel to run next to the walls (also indicated by crossed shading in Fig. 3). The piece of oblong ply cut from the wood slider is fixed on to the inner wall of the cabinet to form the runner (see Fig. 4). Panel pins and glue will hold this construction firmly; however, the front panel should not be affixed yet, but be made to slide out freely.

HOME CONSTRUCTORS LOOK!

AT THESE OUTSTANDING ADDITIONS TO THE

WIRECOMP RANGE !!

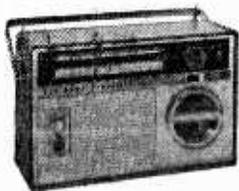

THE SKYROVER

7 TRANSISTOR PORTABLE RECEIVER

THE SKYROVER

De Luxe 7 TRANSISTOR PORTABLE



GENERAL SPECIFICATION FOR BOTH MODELS

7 transistor and 2 diode superhet—4 waveband portable receiver, covering the full Medium Waveband (180-576 M) and Short Waveband (31-84 M) and in addition 4 separate switched Band Spread Ranges on 13M, 16M, 19M, and 25M/bands—with manual Band Spread Tuning for accurate Station selection. I.F. frequency 470 Kc/s. Output 500 MW. 5in. Ceramic Magnet P.M. Speaker. Telescopic and Internal Ferrite Rod Aerial. All Mullard Transistors and Diodes. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our detailed and easy to follow instructions. Operates on four 1.5V torch batts. (U2 or equivalent).

THE SKYROVER Individual Details—controls: Waveband Selector, Volume Control with on/off switch, Tuning Control with easy to read Dial Scale. In attractive plastic cabinet, size: 10 x 6½ x 3½in., with metal trim and carrying handle.

MAY BE BUILT FOR **£10.19.6**

FOR All Parts Sold Separately.


THE SKYROVER De Luxe. Tone Control Circuit is incorporated with separate Tone Control in addition to Volume and Tuning Controls and Waveband Selector. In sturdy wood cabinet, size: 11½ x 6½ x 3½in., covered in washable material with plastic trim and carrying handle. Also Car Aerial socket.

MAY BE BUILT FOR **£12.19.6**

FOR All Parts Sold Separately.

Circuit diagram and data for each set 2/6 extra, free if all parts bought. Four U2 batteries 2/8 extra. Four Leak-Proof Batteries 3/4 extra. Add ½ P. & P. on each set.

THE 'REALISTIC 7'

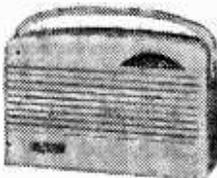

A fully transistorised Portable Receiver made to the highest professional standards—is now available to the home constructor. Comprises 7 Mullard Trans. OC44, 2 OC46's, OC71, OC81D, and 2 OC81's plus OA70 Crystal Diode. Delivers 360 milliwatt output to 4in. high flux speaker—I.F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. All components mounted on single printed circuit board, size 5½ x 5½in. Attractive two-tone plastic cabinet with carrying handle—size 7 x 10 x 3½in. with easy to read dial and socket for car aerial, choice of Red/Grey, Blue/Grey or all Grey. Complete with full instructions. All parts sold separately.

WIRECOMP'S **£5.19.6** Battery 3/8 extra.

PRICE ONLY P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought).

THE COROVER '6'




This superhet receiver uses the very latest circuitry, 6 transistors and two diodes and is fully tunable over both medium and long wavebands. First stage uses three Mullard AF.117 alloy diffused transistors with OA79 and OA91 diodes, output—OC81D and two OC81's in push-pull. I.F. frequency 470 Kc/s. Large internal ferrite rod aerial gives excellent reception over all ranges. 3 inch high flux speaker has a maximum output of 330mW. Operates on four 1.5 v. pen torch batteries. All components are mounted on a single printed circuit board. Attractive plastic case with carrying handle—fitted sockets for personal earpieces, tape recorder and car aerial. Size 6½ x 4 x 1½in.

MAY BE BUILT FOR **£5.7.6** All parts sold separately.

P. & P. 4/- extra. (Data and instructions 2/6, free if all parts bought.)

AND THE 'REALISTIC 7' De-Luxe

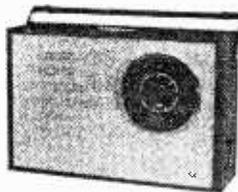

A "De Luxe" version of the well known "Realistic 7" is now available, with the same specification as the standard model PLUS a restyled superior wood cabinet covered in attractive washable material, with chrome trim and carrying handle, AND ALSO a full vision circular tuning dial (externally mounted) to further improve this wonderful set.

Only **£1.0.0** extra

P. & P. etc. as Standard Model

THE 'SPRITE'



A unique Wirecomp offer. The Sprite is a Six transistor superhet Miniature Pocket Radio of Commercial Quality—offered to you in three main pre-assembled units—which together with simple wiring—enable you to build it in only one hour! Fully tunable over Long and Medium wavebands. Uses printed circuit and High sensitivity internal ferrite rod aerial. I.F. frequency 470 Kc/s. Transistors: 3 Philco 2067's, 2 Mullard OC81M, OC81DM and OA90 diode. 3 inch speaker. Works on single PP3 battery. Supplied with the complete R.F. and I.F. stages. Driver and Output stages, ready built and mounted on the printed circuit; for final assembly you only have to fit the wave-change switch, tuning condenser and drive volume control, earphone socket and aerial rod. In very attractive plastic case, size 4 x 2½ x 1½in.

COMPLETE AS ABOVE **79/6** All parts sold separately. Real Calf Leather Case, wrist strap and Personal Earphone with case and battery 12/6 extra. P. & P. 3/6 extra. (Data and instructions 2/6, free if all parts bought.)

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON, W9.

TEL: CUNNINGHAM 9530

Hours of business: 9 a.m. to 6 p.m. Open all day Saturday, Opposite Paddington General Hospital. Buses 18B and 36 pass the door.

SPECIAL WIRECOMP OFFERS TO THE READERS OF "PRACTICAL WIRELESS"

SPEAKERS 6 x 4in. 30 8/8. 5in. Round 30 8/8.
R. R. U.A. 14 Autochangers. £19.6
COLLARO Studio Tape Decks £10.12.6
POST FREE



DUOMOLDS AND SUPAMOLDS

CAPACITORS FOR HIGHER TEMPERATURES

These outstanding T.C.C. Capacitors are a vast improvement on the previous wax-coated type, being encapsulated in a tough moulded plastic material. They will not soften or leak in the higher temperature ranges of 85°C. This new coating affords a good protection against the ingress of moisture and enables the insulation resistance to remain at a high level for long periods under adverse conditions.


DUOMOLD (a mixed paper and plastic dielectric) with voltage ranges up to 750 v. D.C. at 85°C or 1,000 v. D.C. at 70°C and having an insulation resistance at 20°C—after one minute—of 10,000 megohms or 5,000 ohm farad whichever is the less.

SUPAMOLD (a paper dielectric) with voltage ranges up to 600 v. D.C. at 85°C or 750 v. D.C. at 70°C, and having an insulation resistance at 20°C—after one minute—of 10,000 megohms or 2,000 ohm farad, whichever is the less.

Power factor for both Duomolds and Supamolds is less than .01 at 1 Kc/s at 20°C.

For ease of identification Duomolds are bright yellow and Supamolds bright green.

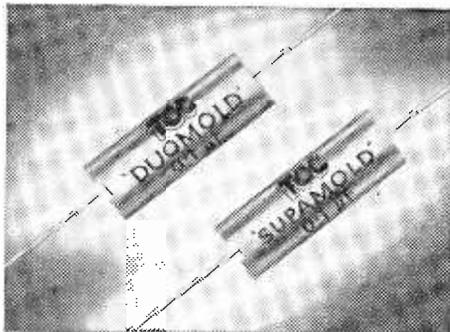For full details of these new T.C.C. Capacitors send for Bulletins No. 89R and 90R.



THE TELEGRAPH CONDENSER CO. LTD.

(Head Office and Works) North Acton, London, W.3. Telephone ACOrn 0061

(Also at) Chessington, Surrey • Bathgate, Scotland

OVER 400,000 PARTS SOLD

COMMON  CORE

basic electricity

630 pp.

IN FIVE PARTS

900 Illns.

AND

basic electronics

675 pp.

IN SIX PARTS

1,000 Illns.

COUPON - SEND NOW!

OR ASK YOUR BOOKSELLER

To THE TECHNICAL PRESS LTD.
112 Westbourne Grove, London, W.2.

Please send me your FREE prospectus describing
the COMMON-CORE SERIES.

NAME _____

ADDRESS _____

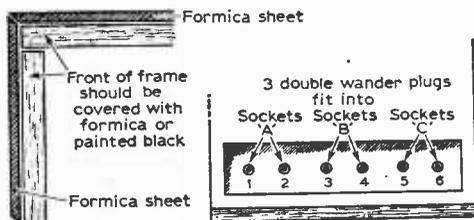


Fig. 5 (left): Showing the use of Formica to provide a suitable finish to the cabinet.

Fig. 6 (right): The three double wander-plug holders at the back of the cabinet.

To make a professional job of the cabinet Formica panels can be cut to cover the whole of the cabinet, excepting the base. Most "do-it-yourself" shops have a selection of cheap offcuts, and the author found in this way an offcut which had the appearance of expensively polished walnut. This costs only 1s.

Fit the Formica panels to the plywood case, seeing that the Formica sides are a little over $\frac{1}{4}$ in. above the ply sides, so that these meet the Formica panel on the sliding lid. All edges of Formica should be bevelled (Fig. 5), so that they fit snugly together. Take care not to stick the lid in when fixing these. Also see that a length of Formica is fitted over the quadrant to be at top of front panel.

The frame round the front panel may be painted black or surrounded with Formica. The

COMPONENT LIST

L1, L2	Divider network coils, 3Ω (Denco)
C1-C4	$32\mu\text{F}$, 450V
S1	Toggle switch
Sockets A-C	Double type mounted on small paxolin strip
VRI	25Ω potentiometer

latter may be a little tricky however as allowance has to be made for the sliding lid. Fig. 6 shows the back of the cabinet and the three double wander-plug holders, which can be obtained on a small strip of Paxolin.

Components should be arranged in the cabinet after the potentiometer and toggle switch have been mounted on the front panel, and the front panel secured. As it is advisable to mount the coils at right angles, a small strip of ply will hold one coil in place leaving space for sliders to pass, whilst the other may be mounted straight on the reverse side of the front panel.

As the input and output sockets are mounted on the back which comes out with the lid, the wires going to these should be left a little (not too much) long to allow for this.

The Euphon in use

A certain amount of care is necessary in the choice of loudspeakers. The h.f. loudspeaker should be small ($2\frac{1}{2}$ in.—6in.) and the l.f. one larger (8in.—12in.), both being matched at 3Ω . The author uses a 3in. and a 7in. with excellent results.

However, the most important point to stress is that it is *absolutely essential to have a good bass cabinet*. If the l.f. loudspeaker does not have this, results will most certainly be disappointing. Only a small cabinet is necessary for the tweeter, which may, of course, be fixed in a cabinet to match the woofer.

Set up the loudspeakers as for stereo, and sit between them adjusting balance. This system is mainly for music and has no application on speech only. Loudspeakers should be 6ft to 12ft apart, and connections should be reversed on one loudspeaker until, by judgment, the best arrangement is found.

It should be noted that when used to simply improve the response of an old radio, it might have very little effect. It will only reproduce the frequency ranges supplied to it, and if the receiver cuts off below 10kc/s, or before it reaches the higher notes, nothing will be gained by the use of this unit.

Beginning in the next issue of **PRACTICAL TELEVISION**

A new series of articles describing the construction
of a complete

CLOSED CIRCUIT TELEVISION SYSTEM

including an inexpensive

VIDICON TUBE TV CAMERA

Make sure to get your copy of the October issue
on sale September 19th - 2/-

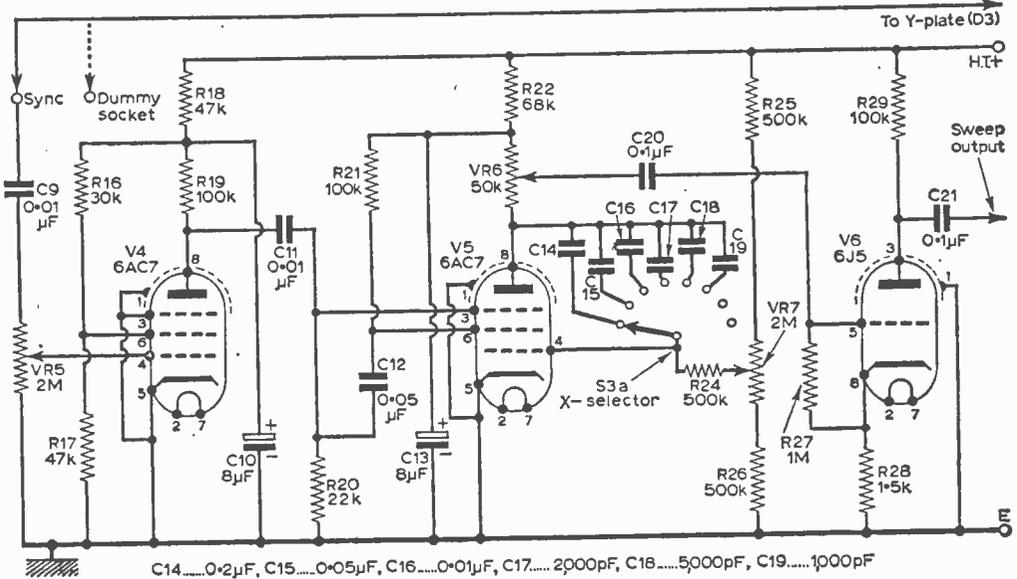


Fig. 10: Timebase generator, timebase and sync amplifiers.

sweep generator, S3 also decides whether the X plates will be fed from the timebase or from some external source via the "X" terminals on the panel.

For this reason, the switch has two wafers, the wiring to the second of these being given in Fig. 11. (If it is intended to build amplifiers into the oscilloscope, S3 will need *three* wafers; the wiring to the third is shown in Fig. 13.

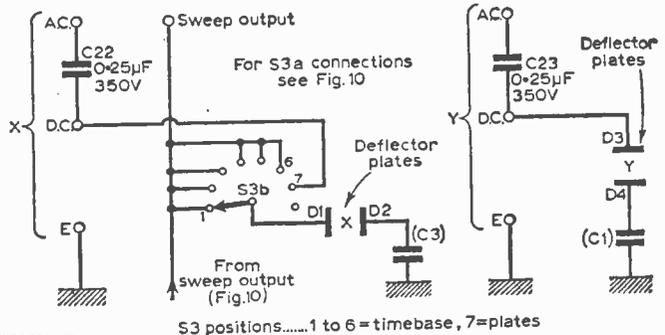


Fig. 11: Selector switching (without amplifier).


Fine control of the sweep frequency is made possible by potentiometer VR7. Most people will find it easier to set up a waveform with this control if the slider moves *positive* as the control knob is turned *clockwise*.

Power Supplies

A power pack is necessary to supply the timebase valves and a suitable circuit is suggested in Fig. 9. This power unit includes a circuit for providing a 50V peak-to-peak output for the calibration terminal.

Deflector Polarity

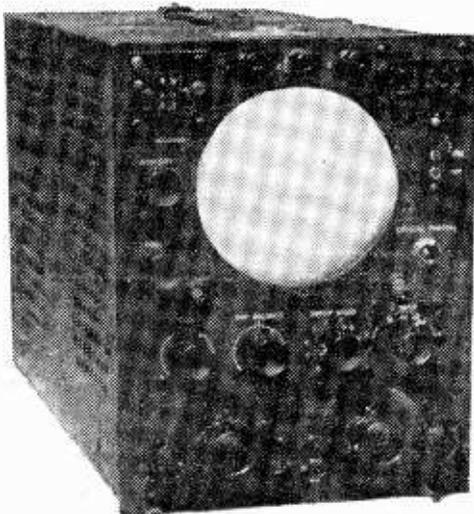In the timebase generator, the working part of the sawtooth waveform is negative-going with



Left—The author's finished model.

COMPONENTS LIST FOR INSTRUMENT TYPE 2 (timebase version Figs. 9, 10 and 11)

Resistors:

R13 470k Ω	R22 68k Ω
R14 33k Ω	R23 —
R15 100k Ω 1W	R24 500k Ω
R16 30k Ω	R25 500k Ω
R17 47k Ω	R26 500k Ω
R18 47k Ω	R27 1M Ω
R19 100k Ω	R28 1.5k Ω
R20 22k Ω	R29 100k Ω
R21 100k Ω	

All 10%, $\frac{1}{2}$ W carbon except where otherwise stated.

Variable Resistors:

VR5 2M Ω carbon potentiometer
VR6 50k Ω carbon potentiometer
VR7 2M Ω carbon potentiometer

Capacitors:

C7 8 μ F electrolytic 350V
C8 32 μ F electrolytic 350V
C9 0.01 μ F paper
C10 8 μ F electrolytic 350V
C11 0.01 μ F paper
C12 0.05 μ F paper
C13 8 μ F electrolytic 350V
C14 0.2 μ F paper
C15 0.05 μ F paper
C16 0.01 μ F paper
C17 2,000pF ceramic or mica
C18 5,000pF ceramic or mica
C19 1,000pF ceramic or mica
C20 0.1 μ F paper
C21 0.1 μ F paper
C22 0.25 μ F paper 350V
C23 0.25 μ F paper 350V

Transformer:

T2 Mains (h.t.) transformer. Tapped primary.
Secondaries: 250-0-250V 30mA; 5V 2A;
6.3V 3A

Inductor:

L1 Smoothing choke 5H, 30mA

Switches:

S3 2-pole 7-way wafer type rotary or 3-pole
8-way if Instruments Type 3 or 4 are to be
built

Valves:

V3 5Y3	V5 6AC7
V4 6AC7	V6 6J5

respect to time. The waveform is then inverted by the amplifier before being fed to the plates.

In order to provide a timebase crossing the screen from left to right, a positive signal at the "X" terminal should deflect the spot to the right, i.e. precisely as described for the simple oscilloscope.

Sweep Generator Output

As will be seen from Fig. 11, the output of the timebase amplifier goes to a panel terminal. If a wobbulator is to be used with the oscilloscope, the sweep-frequency drive will be obtained from this terminal and not from "X a.c." which leads nowhere when the timebase is working.

INSTRUMENT TYPE 3

By adding a.c. amplifiers and associated switching, the development of the progressive oscilloscope can be taken a stage further. The details which follow, discuss the progression from Instrument type 2 to Instrument type 3.

Amplifiers

"A1" and "A2" are wideband a.c. amplifiers, identical to each other, each consisting of a triode voltage amplifier and a cathode follower. The circuit is given in Fig. 12. As double triodes are used in the circuit, two valves only are necessary.

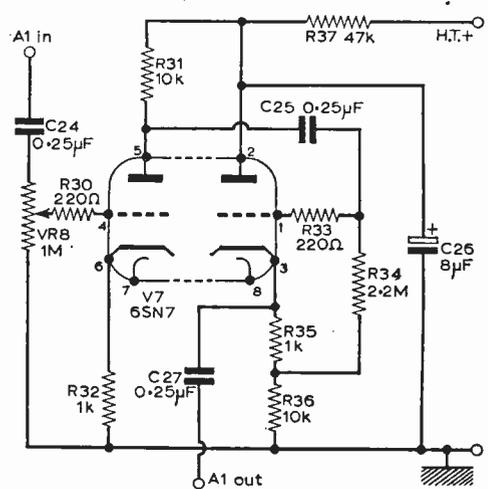


Fig. 12: The circuit of the A1 amplifier—the A2 amplifier is identical.

COMPONENTS LIST FOR INSTRUMENT TYPE 3 (a.c. amplifier version Figs. 12 and 13)

Resistors:

R30 220 Ω	R35 1k Ω
R31 10k Ω 1W	R36 10k Ω 1W
R32 1k Ω	R37 47k Ω 1W
R33 220 Ω	R38 470k Ω 1%
R34 2.2M Ω	R39 2M Ω 1%
VR8 1M Ω potentiometer	

All $\frac{1}{2}$ W, 10% except where stated.

Capacitors:

C24 0.25 μ F	C27 0.25 μ F
C25 0.25 μ F	C28 20pF

C26 8 μ F electrolytic

All 350V d.c.

TCl 3-30pF trimmer

Valve:


V7 6SN7

Switches:

S3 3-pole 8-way wafer type rotary
S4 3-pole 4-way if Instrument type 3 only is
to be built. 4-pole 5-way if Instrument
Type 4 is to be built

The only controls are the two gain potentiometers.

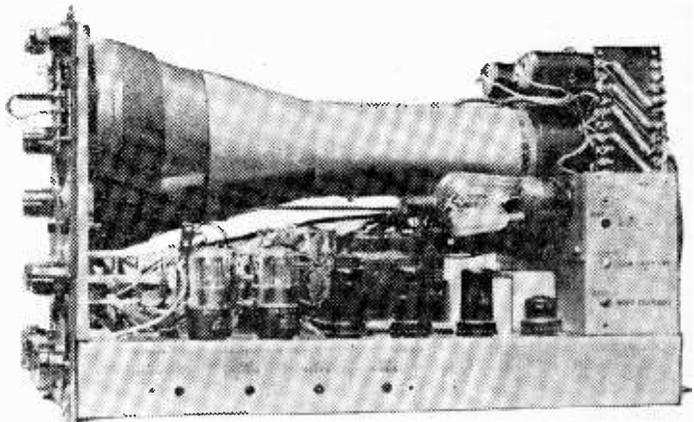The amplifiers should not be used at low levels of gain if high-frequency components are present in the signal, as the valve input capacitance will act with the potentiometer as a frequency-selective filter, distorting the waveform before it appears on the screen.



The oscilloscope in an advanced stage of construction.

Switching Scheme

Fig. 13 shows the switching scheme for use with these amplifiers. Both the switches are of the rotary (wafer) type.

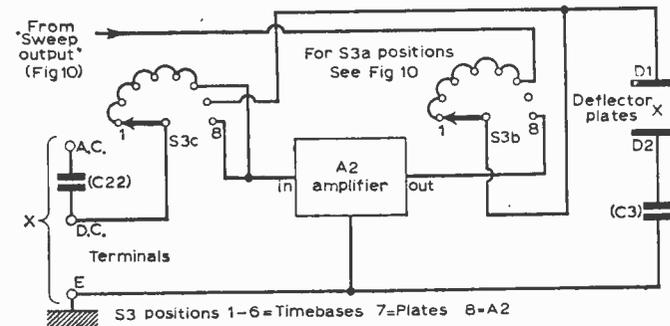


Fig. 13: Selector switching (with amplifiers): a (left); "X" (sweep) selector: b (below); "Y" selector.


The first pole of the X-selector switch "S3" is used in the timebase generator to select the band-setting capacitors. The first six positions are concerned with the timebase and the seventh connects the input terminal directly to the deflector plate; only in the eighth position does the "A2" amplifier come into play on the X plates.

The input signal should be fed to the "X a.c." or "X d.c." terminals regardless of whether the selector switch is at "Plates" or "A2"; this saves a lot of trouble in swopping-about wires.

The "Y Selector" switch "S4" offers a choice of four ways in which a signal can reach the plates from the Y terminals: attenuated, direct, amplified by one amplifier or amplified by both amplifiers in cascade.

The Attenuator

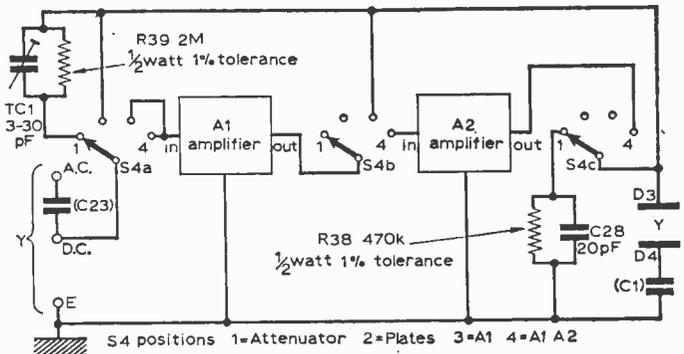For good high-frequency performance, the trimmer capacitor shunting the upper arm of the attenuator should be set to balance out stray circuit capacitances. A square wave applied to the Y terminals will soon show up any faults in the frequency characteristic of this circuit.



If it is proposed later to build the trace-splitter circuit, this can be used for the purpose.

Rotary Switches

The information given in Table 3 (Sept. issue) requires amending as follows: Instruments 3 and 4: S3 should be 3-pole 8-way. Instrument 4: S4 should be 4-pole 5-way.

**SERIES TO BE CONTINUED
NEXT MONTH**

QUALITY MW TUNER

W. GROOME

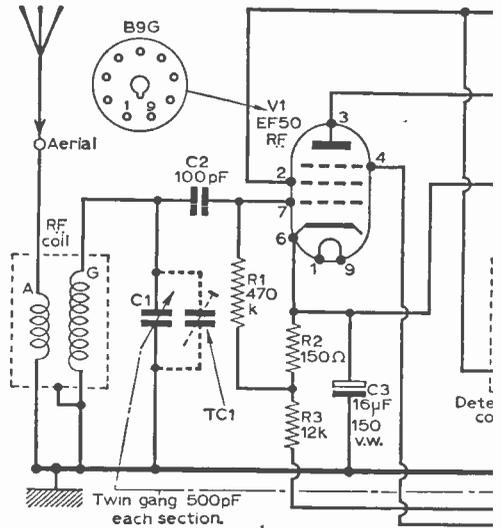


Fig. 1: Two-valve t.r.f.

WHILE a v.h.f. tuner in most areas will provide the finest local radio input for high fidelity equipment, the quality of some medium-wave broadcasts justifies the addition of a small a.m. unit. Leaving local transmissions to the existing tuner, the new unit can be designed for a balance between sensitivity and fidelity to make the best of those Continental stations that reach the aerial relatively unblemished.


Superhet selectivity is undesirable because of bandwidth considerations; on the other hand the usual fidelity t.r.f. designs are too insensitive for any distant signals. The unit to be described, however, has a high sensitivity for a two-valve circuit and brings in the worthwhile transmissions with satisfactory quality.


The Circuit

The circuit, Fig. 1, is based on principles developed by BBC engineers to enable automatic gain control to be applied to high-slope pentodes capable of much greater gain than the variable- μ types generally used for a.g.c. The advantage of this high gain is that the use of a second r.f. stage—a notoriously unstable arrangement—is avoided.

A.G.C. by grid injection is not practicable with high-slope pentodes but it is possible to control the mutual conductance—and hence the gain—by applying sufficient negative bias to the suppressor. This inhibits the arrival of electrons at the anode and compels many (*all* at full cut-off) to alight upon the screen, where they are unable to influence the external circuit. As a rather high control potential is required, some d.c. amplification is necessary and this, fortunately, can be provided by the detector.

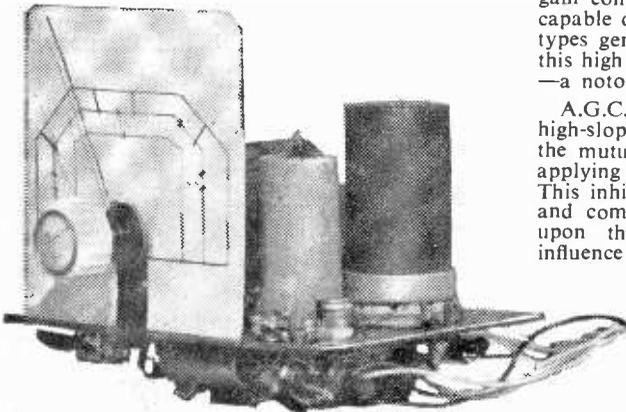At this stage, as audio quality is one of the



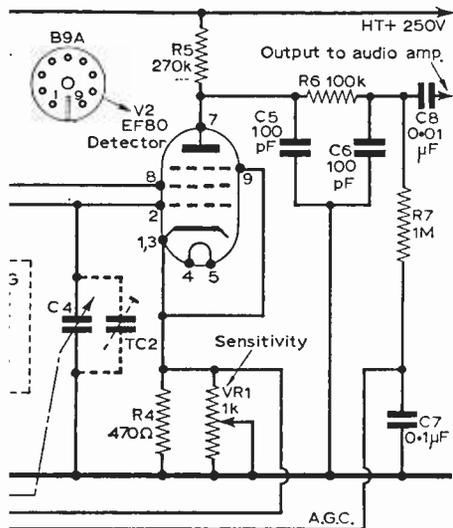

with amplified a.g.c.

objects, the question of detector distortion must be put into correct perspective. So far as background silence and audio bandwidth are concerned v.h.f. is supreme, but the harmonic distortion of the usual discriminator, at about 3%, is rather higher than that of some a.m. detectors. (I know of only one somewhat rare, though simple, f.m. discriminator that can maintain a truly distortionless performance.)

The figure is horrifying but complaints are few even among high fidelity enthusiasts and we can bear this in mind when balancing the interests of sensitivity and quality.

The distortionless a.m. detectors have less than unity gain and require some r.f. amplification even for local station reception. Additional r.f. amplification to improve the sensitivity is almost certain to bring distortion and instability to cancel all the advantages of such a detector. Better results are likely with a detector that can itself contribute enough gain to work well with the stable single r.f. stage.

Although an anode-bend detector may distort on occasional heavy modulation, its performance on average signal is good. With a high-slope pentode a gain of over 100 is possible and the stage is particularly suitable as a source of amplified a.g.c. potential. To avoid loss of d.c. gain through negative feedback in the cathode resistor R4 it must be kept small (a bypass capacitor would not prevent this feedback from reducing the gain of the d.c. component of the signal).

Nevertheless the resistor must still yield the correct bias and this is achieved by making it carry additional current to increase the voltage drop, the current being that of V1, which has the earthy end of its cathode network common with that of V2.

For a similar reason the screen of V2 derives a stable potential from the cathode of V1, which is raised rather high above earth to suit the a.g.c. conditions. The d.c. control potential from the anode of V2 is filtered by the network C5, R6, C6

to eliminate the r.f. content and passed via the a.f. filter C7, R7 to the suppressor of the r.f. valve.

It is, of course, a positive potential varying with the signal strength but must be negative with respect to the cathode of V1. It is for this reason that the 12kΩ resistor R3 is included to raise the cathode. The normal potential difference for grid bias is picked off by returning the grid resistor R1 to the junction of R2, R3. The grid capacitor C2 is essential to block the d.c. path to earth through the tuning coil.

Choice of Valves

Choice of r.f. valve is governed by its suppressor grid base, for this must be short enough to lie within the range of available control voltage. My admittedly brief experiments seemed to indicate that the EF50 recommended by the originators of this a.g.c. system is more suitable than some newer types, but there is scope for the interested amateur to take the investigation further. As the veteran EF50 is readily obtainable as a surplus item at less than half a crown it is included in the present unit.

Although this valve seems large by today's standards, and other components used were by no means the smallest made, the tuner was built on a "bread board" measuring 6in. x 3½in. without crowding. The detector is an EF80 but type EF50 can be used for this stage, too.

Ordinary aerial and r.f. coils are suitable for a circuit such as this, in which knife-edge selectivity is undesirable, and it is not necessary to limit the constructor to one specific make. They should be canned because of the high gain of the circuit. The base connections of coils may not be the same as indicated in the point-to-point wiring diagram (Fig. 2) but this will necessitate only slight variation of the wiring layout.

The potentiometer in the detector cathode circuit is included to enable the a.g.c. operating conditions to be adjusted. Once set it can be forgotten, but experimenters who wish to exploit the full gain of the unit could mount this component on the front for use as a sensitivity control.

It is usual to power a small unit—such as this from an outlet in the main amplifier, and therefore no supply arrangements are included here. It is unlikely that the tuner will be granted the efficient aerial so often recommended for a good signal-to-noise ratio and it must be admitted that a really large one would bring selectivity troubles with the simple tuned circuits employed. In the Midlands the customary bit of wire—about 2yd dangling behind the tuner—brings in several Continental transmissions at good strength and quality.

Conventional chassis construction could be adopted but a "bread board" layout can be made compact, reliable and requires no metalwork.



Using available components rather than the smallest possible, the prototype was assembled on a piece of unmetallised laminated plastic 6in. x 3½in. x ¼in. thick.

The wiring was arranged as shown in the point-to-point diagram, Fig. 2. The potentiometer VR1 is under the panel and occupies more depth than is generally needed for bread board wiring, but this depth permits C3, C7 and C8 to be housed below to avoid increasing panel area.

The two-gang capacitor, canned coils, standard valveholders, aerial socket and audio output socket are all mounted on top and solder tags are fitted under their fixing screws to enable earth continuity wires to link them. Small trimmers should be fitted if there are none already present in the tuning capacitor.

Wiring-up

Begin wiring by soldering bare wire from tag to tag on the top side to form the earth links, remembering to include the frame of the tuning gang and the coil cans, which are not earthed automatically as in the case of metal chassis construction. Drill small holes at convenient points to enable short earth connections to be passed through to the underside and soldered to the appropriate tags on the valveholders, coils and potentiometer as shown in the diagram.

Next connect the heater wiring, which has been omitted from the diagram for clarity. As this will be taken from the main amplifier it will probably

be a centre-tapped supply requiring an insulated twisted pair. For an unbalanced supply (one side earthed) run a single insulated wire to one heater tag on each valveholder and earth the other tag. No socket is fitted for power supply connections: instead the heater, h.t. and earth wires are led out as flexible leads ending at a plug to suit the outlet on the main amplifier.

Most of the circuit wiring is in 20 s.w.g. bare tinned copper wire "stitched" to the panel by passing it through small holes. Anchorage, where needed, is provided by passing wire twice through close pairs of holes and bonding solid by soldering.

At first glance the diagram may seem to show breaks in the coil-to-grid connections, but use is made of the tags provided on both sides of the fixed vanes in most tuning gangs so that the path to the grids is continuous across the vanes. Insulated wire is shown at points where the diagram might suggest contact in unwanted places but in practice these could be air-spaced and bare wire used.

The prototype has an epicyclic tuning drive, this being simple and reliable and free from the troubles so likely to occur with cord and pulley arrangements. As the interest is in only those transmissions that are received well it was decided that a ready-made dial printed with all stations from here to Tokyo would be of little benefit. The home-made one used instead has a limited number of stations marked to indicate three standards of reception quality.

Although it was intended to add the station

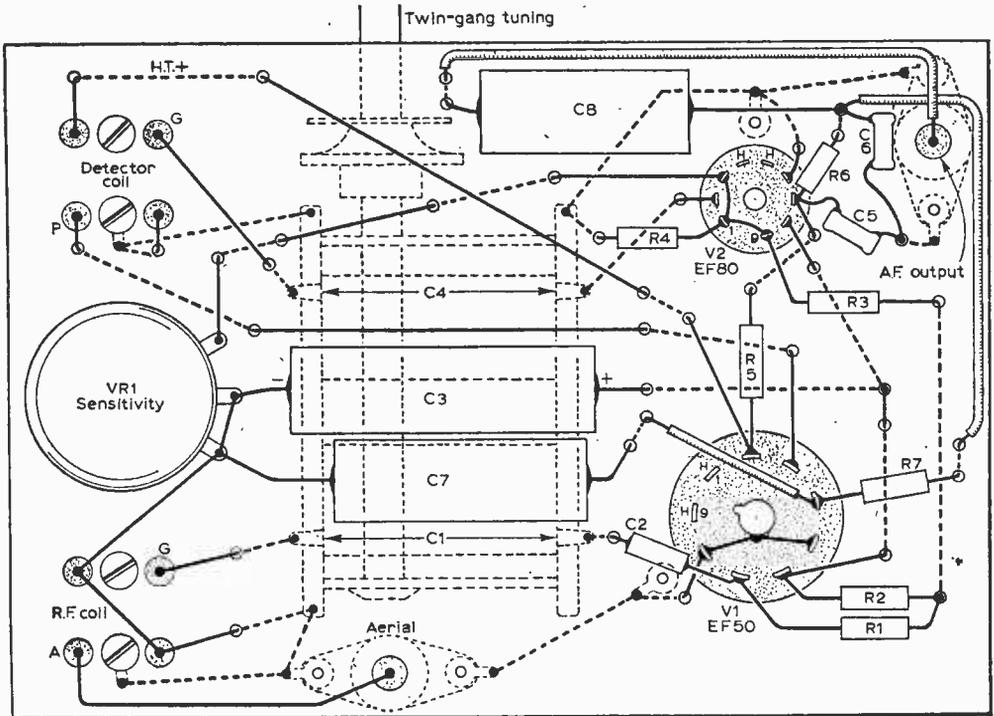


Fig. 2: Underside view of the "bread-board" wiring.

COMPONENT LIST

Resistors:

R1	470kΩ ¼W	R5	270kΩ ½W
R2	150Ω ¼W	R6	100kΩ ½W
R3	12kΩ ¼W	R7	1MΩ ¼W
R4	470Ω ¼W	VRI	1kΩ pot.

Capacitors:

C1, C4	2-gang 500 pF
C2, C5, C6	100pF
C3	16μF electrolytic 150V
C7	0.1μF

Valves:

V1	EF50	V2	EF80
----	------	----	------

names the users so quickly memorised the transmissions associated with the simple dash marks that even that refinement has been omitted! The usual dial lighting arrangements can be included if required.

Alignment of the tuned circuits follows the usual procedure for a t.r.f. tuner and can be done "by ear". The split-vane type of gang permits a useful correction for tracking error that might be evident at the ends of the band, but if overdone there is a risk of contact between fixed and moving vanes. In the conditions that have to be accepted

as normal for the medium-wave band nowadays, only a few of the receivable transmissions are acceptable as entertainment for the music lover.

When these have been logged the split vanes can be used to favour them. The potentiometer has "dead" and "live" positions at each end of the track. Set it at the live end and then adjust it until a weak signal just begins to fall in strength. A.G.C. will then be operative.

If you are more interested in quality than in logging the maximum number of stations it is worthwhile to reduce the sensitivity still further with this control to the point where the best signals are still comfortably received. This avoids overloading the detector and also keeps the unit free of the slight positive feedback that can degrade quality at the highest sensitivity levels even though still clear of oscillation.

The quality obtainable is about the best that is likely from distant medium-wave stations but the unit cannot restore audio frequencies missing from the transmission nor adjust for the over-modulation that is evident in some broadcasts. Whistles can sometimes be handled by the filters and tone-control circuits of the high-fidelity equipment. However, it is generally possible to log a number of stations that can provide an agreeable standard of entertainment. ■

**TUNE-IN
TO THE
WORLD!**




FREE *INSIDE NEXT MONTH'S*
**PRACTICAL
WIRELESS**

DOUBLE-SIDED
BLUEPRINT
with instructions to build
**BEGINNERS SHORT
WAVE RECEIVER**
plus **COMPLETE GUIDE
TO WORLD-WIDE
SHORT WAVE RECEPTION**

ORDER YOUR COPY TODAY

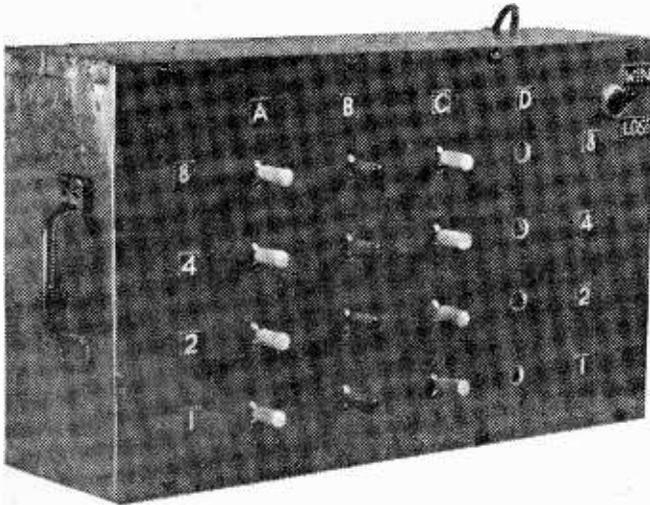An unbeatable machine based on the game of Nim



AN ELECTRIC NIM MACHINE

By J. R. Stewart

NIM is a game for two players. Starting with a number of matches, counters or other objects arranged in piles or rows, each player alternately draws as many matches as he chooses from one row only. Two variations of the game are possible; in one, the player who picks the last match wins the game, in the other, he loses. There is no limit to the number of counters in any one row, nor to the number of rows with which to begin the game, although recent TV programmes have made popular the game of "last match loser" with four piles containing 7, 5, 3 and 1 matches.

The Theory of Nim

The theory of this game has been completely worked out, and an elementary knowledge of it helps to understand the construction of the machine. To begin with, the operation of "last match wins" variation will be explained.

Briefly, any number can be written as the sum of some of the powers of 2, together with the number 1, i.e. using the numbers in the sequence 1, 2, 4, 8, 16, etc. For example, $9 = 8 + 1$; $30 = 16 + 8 + 4 + 2$. In representing any number by such a sum, none of the sequence numbers occurs more than once. This can be checked by noting that the sum of all the sequence numbers up to any point is always 1 less than the next number in the sequence; for example, $1 + 2 + 4 = 7$, and the next sequence number is 8.

Calling the individuals Player and Opponent, it can be shown that in playing Nim, if the Player produces what we call a safe combination, the Opponent's move always upsets this arrangement, allowing the player to reset a safe combination when he draws in his turn. By safe combination we mean a set of numbers (the numbers of counters in each row) which will lead to a win for the Player. The secret of the game lies in

knowing the safe combinations, and how to produce them. For "last match wins" variation, the safe combinations are found as follows:

- (1) Represent the number of counters in each row as the sum of the sequence number: given above;
- (2) Count the number of 1s, 2s, 4s, 8s, etc. which appear in the arrangement;
- (3) A safe combination is one in which the numbers of each of the 1s, 2s, etc. is EVEN and the Player who sets up such a combination will win.

Take the familiar example of 7, 5, 3 and 1.

$$\begin{array}{r} 7 = 4 + 2 + 1 \\ 5 = 4 + 1 \\ 3 = 2 + 1 \\ 1 = 1 \end{array}$$

Reading vertically we see that the numbers of 1s, 2s, etc. are all even, hence this is a safe combination for the Player who set it up. When the Opponent draws, because he draws from one pile only, he must make some of the numbers of 1s, 2s, etc. odd, since he can remove only one 1, 2 or 4. This makes the combination unsafe, and the Player has then only to even things up again to keep a winning line. Suppose the Opponent removes all the 7 counters from the first row. This then leaves

$$\begin{array}{r} 5 = 4 + 1 \\ 3 = 2 + 1 \\ 1 = 1 \end{array}$$

All the 1s, 2s and 4s are now odd. To even this arrangement, the 4 must go, so that the Player must draw from the 5 row. The other rows are even in 1s and odd in 2s. Thus if he leaves only 2 counters in the 5 row, the combination will be safe, i.e.

$$\begin{array}{r} 2 = 2 \\ 3 = 2 + 1 \\ 1 = 1 \end{array}$$

When the machine plays, the procedure is that it is "told" the numbers of counters in all but one of the rows. These numbers are given to it in the form of the sequence numbers 1, 2, 4, 8, etc. It then counts the numbers of 1s, 2s, etc. or rather it selects the cases in which these numbers are odd. This selection is then the number of counters which the machine decides to *leave* in the last row. Again, an example will make things simpler. Suppose three rows contain 9, 7 and 4 counters.

$$\begin{array}{r} 9 = 8 \quad + 1 \\ 7 = \quad 4 + 2 + 1 \\ 4 = \quad \quad 4 \end{array}$$

This is odd in 8s and 2s, so that the machine will elect to have $8 + 2 = 10$ in the fourth row, making its own safe combination. If the opponent draws 5 from the 10 row, this leaves—

$$\begin{array}{r} 9 = 8 \quad + 1 \\ 7 = \quad 4 + 2 + 1 \\ 4 = \quad \quad 4 \\ 5 = \quad \quad 4 \quad + 1 \end{array}$$

If the machine is again told the first three numbers, it will again select 10 for the last row, which is now impossible, since 10 cannot be left

that the machine refuses to play.

Thus when playing with 7, 5, 3 and 1, which we have seen is a safe combination, if we tell the machine 7, 5 and 3, it will reply 1; if we tell it 5, 3 and 1, it will reply 7 and so on. To sum up, the machine is unbeatable if it is allowed at the start of the game to select the number in one row, having been told the numbers in the others.

If the opponent sets out the numbers in all the rows at the start, the machine will beat him if he sets an unsafe combination. If he sets a safe combination, the machine will refuse to draw from any pile; this could be called a drawn game.

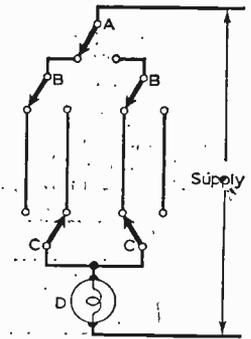


Fig. 2: The basic switching circuit.

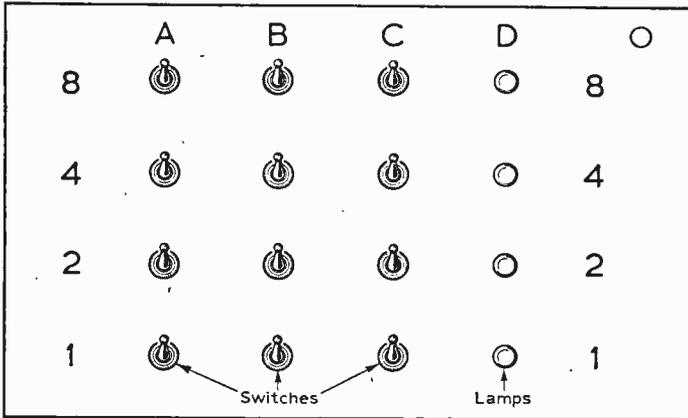


Fig. 1: The layout of the front panel.

if there are only 5 in the row. Looking at the last three, the combination is odd in 4s and 2s. Thus if the machine is told the numbers 7, 4 and 5, it will select $4 + 2 = 6$ for the other row, i.e. it draws 3 from the 9 row, again making its own safe combination. The machine does not always draw from the row having the largest number of counters; if the rows contain 9, 8, 7 and 4 it will reduce this to 9, 8, 5 and 4.

With a four-row machine, there are four possible ways of selecting any three rows, i.e. there are four possible sets of numbers which can be told to the machine. One of these will always give a workable answer—workable in the sense that the number selected by the machine will be less than the number already in the remaining row. This applies provided that the combination is unsafe. If the combination is already safe, no matter what selection of three from four is made, the machine will always reply with the number already in the remaining row; in this sense we can say

Construction

Using four rows the machine requires to be told the numbers in three rows. This is done by throwing various switches. The reply which the machine makes is read off on small lamp bulbs. The 1s, 2s, etc. of the sequence numbers are completely independent, and depending on the number of switches one uses, the machine can be made to cope with any given number in a row.

Calling the rows A, B, C and D, and designing for up to 15 in a row, we need (Fig. 1) 12 switches, and four lamps. The number of counters in rows A, B and C, are told to the

machine by throwing the appropriate switches in each column; the lamps which light up in row D tell us how many counters to leave in that row. Remembering that a safe combination has an even number of 1s, 2s, etc. and that the 1s, 2s, etc. are independent of each other we get the following set of rules which the switching circuit must give:

- Reading horizontally along any row,
- (1) None of the switches A, B or C, thrown must keep the lamp off;
 - (2) Any one of the switches A, B or C, thrown must bring the lamp on;
 - (3) Any two of the switches A, B or C, thrown must keep the lamp off;
 - (4) All three switches A, B and C, thrown must bring the lamp on.

In this way we always have an even number of (lamp + switches) in the ON position.

A switching circuit which will perform these operations is shown in Fig. 2. As drawn, all the switches are in the OFF position, and the arrowed

contact moves across to the "free" contact when the switch is thrown. Each switch and lamp has been marked to correspond with the row in which it is situated. If the connections are traced out, it will be seen that conditions 2 and 4 bring the lamp on, while conditions 1 and 3 provide no conducting path for the supply. From Fig. 2, the switches in row A require a single change-over contact; those in B and C a double change-over contact.

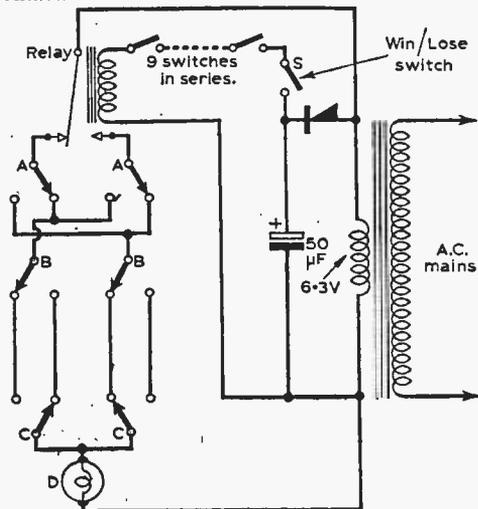


Fig. 3: The circuit of the bottom row of switches and power supply.

Toggle switches having a double change-over can be purchased; because the writer required a machine which would play both variations, and as "last match loses" needs an extra contact on nearly every switch, Post Office type key switches were used in the unit to be described. These have the added advantage that the handle, being longer than the toggle dolly, is more easily read to determine a given number.

Once again it should be emphasised that there are no connections between the horizontal rows of switches except that of a common supply line. A 3V dry battery can be used, together with 2.5V bulbs. One side of all the bulbs in D will be connected together to one side of the battery, while the other battery terminal, through an ON/OFF switch if desired, goes to the movable contact point of all the A switches.

Last Match Loses

The above is the simplest version of an unbeatable Nim player, playing last match wins. For those who want to play last match loses, or both variations, the circuit becomes more complicated. In playing last match loses the theory of the game is only slightly different. The same combinations as in last match wins are safe, until the game reaches the stage of only 1 or 0 in all the piles. Then an odd number of 1s is safe, while an even number is unsafe. A little reflection will show this to be true; if there are three singles matches left, the opponent who picks the first of these must also pick the last, thus losing the game.

We therefore require a circuit which is the same as in Fig. 2 for the top three rows, i.e. 8s,

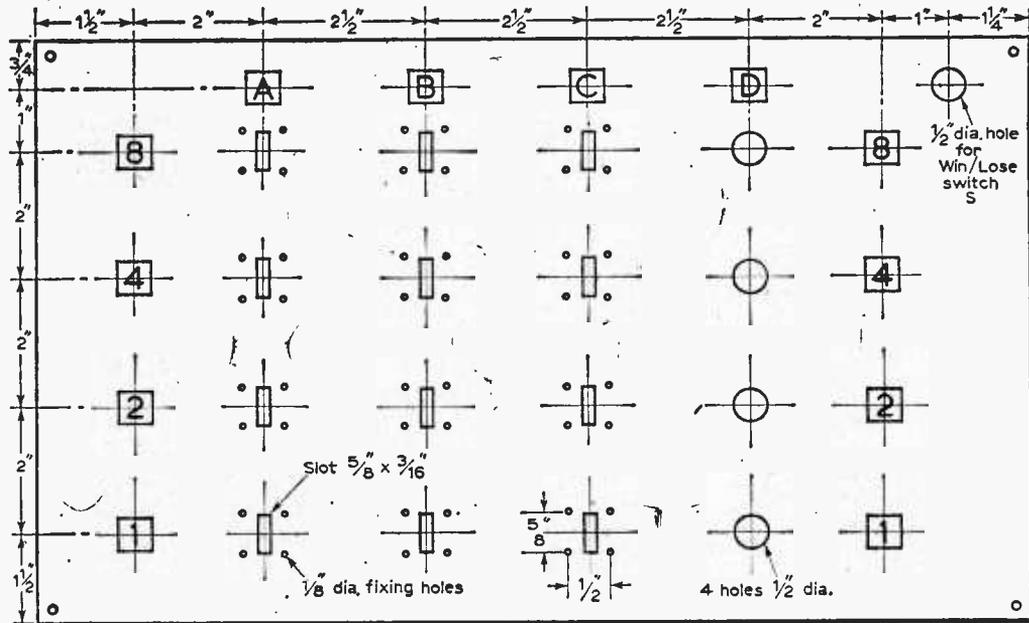


Fig. 4: Details of the front panel. The four holes for the keys are drilled in tin plate only, not in the cover.

RADIO CLEARANCE LIMITED

27 TOTTENHAM COURT ROAD, LONDON W.1

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE

TRADE ENQUIRIES INVITED

Telephone: MUSEUM 9188

EST. 35 YRS.

AGAIN CRASHING THE SOUND BARRIER!

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

SCHEDULE OF LOUDSPEAKERS AVAILABLE

Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price
2	7000	80	8/-	4	7000	3	8/6	5	6000	3	8/-	5	6000	25	10/6
2 1/2	7000	35	8/6	4	9500	5	9/6	5	6000	5	8/-	5	9500	25	11/6
2 1/2	7000	50	8/6	4	6000	25	10/6	5	7000	3	8/6	5	9500	35	11/6
3 1/2	8500 (E.M.L.)	3	8/6	4	7000	25	11/8	5	7000	5	8/6	5	10000	25	12/-
3 1/2	7000	35	8/6	4	6000	35	10/8	5	8500	3	9/6	6 1/2	7000	3	11/-
3 1/2	9500	50	10/6	4	7000	35	11/-	5	8500	5	9/6	6 1/2	7000	5	11/-
4	5000	3	7/6	4	9500	35	11/6	5	9500	3	10/6	6 1/2	8500	3	11/6
4	6000	3	8/-	4 tweeter	7000	5	8/-	5	9500	5	10/6	8	7000	3	12/-
5	6000	3	8/-					5	10000	3	11/6				

Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price
5 x 3	6000	3	7/6	6 x 4	8500	3	9/6	7 x 4	9500	50	11/6	8 x 2 1/2	9500	5	10/-
5 x 3	7000	3	8/-	6 x 4	9500	3	10/-	7 x 4	10000	15	12/6	8 x 2 1/2	10000	5	10/6
5 x 3	9000	3	8/6	6 x 4	9500	5	10/-	7 x 4	9500	3*	13/6	8 x 3	6000	3	8/6
5 x 3	9000	4	8/6	7 x 4	9500	3	10/8	8 x 2 1/2	6000	3	8/6	8 x 5	6000	3	9/6
5 x 3	9000	5	8/6	7 x 4	7000	3	10/-	8 x 2 1/2	7000	3	9/-	8 x 5	7000	3	9/6
5 x 3	6000	25	9/6	7 x 4	7000	5	10/-	8 x 2 1/2	7000	5	9/-	8 x 5	8500	3	9/6
5 x 3	7000	25	10/-	7 x 4	8500	3	10/6	8 x 2 1/2	6000	6	8/6	8 x 5	9500	3	10/-
5 x 3	9000	25	11/-	7 x 4	9500	3	11/-	8 x 2 1/2	6000	9/4	7/6	8 x 5	9500	3	10/-
5 x 3	9000	35	11/-	7 x 4	9500	4	11/-	8 x 2 1/2	8500	5	9/6	8 x 5	9500	15	13/6
6 x 4	6000	3	8/6	7 x 4	9500	5	11/-	8 x 2 1/2	9500	3	10/-				
6 x 4	7000	3	8/6	7 x 4	9500	30	11/6	8 x 2 1/2	9500	4	10/-				

* With matching transformer.

ALLOW 2/- each Speaker for postage and packing, and please specify the exact requirements—the nearest available will be sent.

OVER 50,000 SOLD & STILL THE DEMAND CONTINUES FOR OUR 'HEAVENLY TWINS'

Ask for a demonstration in the shop.

"CAPRI"

Sensitive!
Super-selective!
Superb Speaker!
New Price NOW ONLY **79/6**



(2/- p. & pkg.)
Pocket Super-hot MW and Droitwich LW
Size 4 1/2 x 2 3/4 x 1 1/4 in.
Constructional data 1/9 Post Free.

The best and easiest transistor build-yourself sets available.

Send S.A.E. for FREE PARTS LIST

6 First Grade MULLARD Transistors, Diode(s) and all components BRAND NEW and GUARANTEED

Choice of a dozen stations in daylight . . .

"CONTESSA Mk. III" "QUEEN OF THEM ALL"

ONLY **£9.19.6**

(3/6 p. & pkg.)
PORTABLE CAR RADIO
2 WAVEBAND SUPER-HET



Construction manual 2/10 Post Free.


Inclusive price for all associated components, case, battery and instruction Book complete in every detail.
ANY PARTS SOLD SEPARATELY ON THE BUILD-AS-YOU-BUY SCHEME

CONTESSA III £9.19.6 (plus 3/6)
CAPRI (Battery 2/6 extra) **79/6** (plus 2/-)

SELECTED GUARANTEED BARGAINS—BRAND NEW

Beautifully geared AM/FM 2 Gang Condensers, 4/6; AM/FM IFT's 465kc/s and 10.7 Mc/s, 4/6 pair; Magnavox Crystal Tape Recorder Mikes, 12/6; Double-tuned Transistor IFT's Q120, 470 kc/s, 5/6 pr.; 3 matched IFT's and oscillator coil for Mullard transistor circuits, 10/6 the set; Plessey-Brayhead turret tuners 34/38 Mc/s, valved 8/6 each; 3 watt Stereo Amplifiers, complete, ready to switch on 79/6; Sentercoil rectifiers R3/2D-D3-2-Y, 2/6 each. DIODES—OA79, OA81, OA90, CG46H, ORP60, GD10 2/- each. TRANSISTORS: Set of 6 (RF and LF) including 1 watt matched pair, heat sink and diode, 13/6 the set; OC44 (or equiv.), 6/9, OC45 4/6, OC81 5/6; matched pair 12/-, PXC 101A 4/6, matched pair 9/6, PXA 101 3/9, AF 115 4/6. SB 305 2/-, Submin. Germanium diode 1/3 Please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogues—our stocks move too quickly! Kindly make provision for additional postage and packing charges to avoid delay.

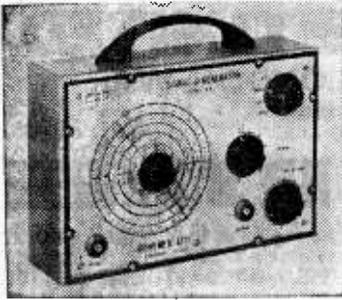TERMS: CASH WITH ORDER or C.O.D. ON ORDERS OVER 10/-.



Wide-range Transistorised
SIGNAL GENERATOR—Model 27
Range 150 Kc/s to 350 Mc/s.

- ★ Accuracy better than 2%
- ★ Directly calibrated
- ★ Battery operated
- ★ Compact and light

£7.18.6

with lead test and battery.
Post and Packing 3/6 extra.



Trade and Export Enquiries Invited

NOMBREX INSTRUMENTATION

Wide-range Transistorised
AUDIO GENERATOR—Model 63
Range 10—100,000 c/s.

- ★ Laboratory Standard Specification
- ★ Sine and Square Wave
- ★ Direct Frequency Calibration
- ★ Accuracy and Low Distortion
- ★ Calibrated Output Voltage
- ★ Battery Operated and Compact

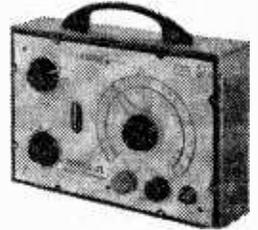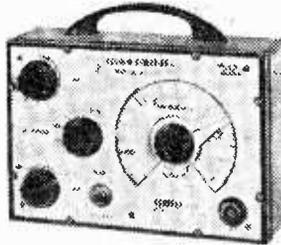£15.0.0 complete with
test lead
Battery 2/3. Post and Packing 3/6.



Wide-range Transistorised
C.R. BRIDGE—Model 62
6 Ranges: 1Ω to 100MΩ
1pF to 100μF

- ★ Visual null indicator
- ★ Power Factor check
- ★ Electrolytic leakage test
- ★ Battery operated

£7.2.3

including battery.
Post and Packing 3/6 extra.

S.A.E. for full technical leaflets

NOMBREX LTD. Instruments
Division 63

ESTUARY HOUSE, CAMPERDOWN TERRACE,
EXMOUTH, DEVON. Phone: 3515.

It's so easy to build TAPE EQUIPMENT with a MARTIN RECORDAKIT ...such honest value!

With a Martin Recordakit you can either build a complete tape recorder (in which case you can have it with deck and portable type case if desired) or assemble a pre-amp to connect the deck to existing amplifier system. There are Recordakits for two or four track Collaro, Magnavox and B.S.R. decks. When finished, you will enjoy performance and quality of wonderfully high standards more usually associated with far costlier equipment.

- Printed circuit board sections supplied complete tested and with valves in position.
- All kits complete down to last screw and measured length of wire.
- Leads attached in position at one end.
- Full assembling and operating instructions.



**THE KIT
YOU BUY WITH
SUCCESS BUILT IN**

- AMPLIFIERS FOR COMPLETE INSTRUMENTS
- PRE-AMPS TO ADD TO HI-FI
- 2 TRACK AND 4 TRACK

AMPLIFIER ASSEMBLIES

- 8311V—2 Tr. for Collaro 3 sp. deck with valves, transformers, knobs, ecc. **11 gns.**
- 8311-4-V as above, but for 4-track deck. **12 gns.**
- Kit 'D' with 8311-4-V amp., case, and 9" x 5" speaker. **34 gns.**
- Kit 'A' with 8312-4-M amp. B.S.R. deck, case and spkr. **24 gns.**

PRE-AMP ASSEMBLIES

- 8312-BP for B.S.R. 2 Tr. **8 gns.**
- 8312-4-BP for B.S.R. 4 Tr. **9 gns.**
- 8312-CP for Collaro 2 Tr. **8 gns.**
- 8312-4-CP for Collaro 4 Tr. **9 gns.**

Pre-amps with deck and polished wood cabinet from **17 gns.**

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD, MIDDLESEX
Phone: ISLEWORTH 1161/5885

MARTIN ELECTRONICS LTD., 154/155 High St., Brentford, Middlesex.
Full details of Martin Recordakits, please.

NAME

ADDRESS

(Block letters) PW10

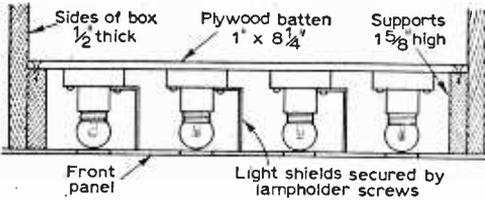


Fig. 5: Details for mounting the lamps.

4s and 2s, and which will reverse the lamp operation in the bottom row of 1s if, and only if, all the switches in the 8s, 4s and 2s, are in the OFF position. Fig. 3 shows the circuit for the bottom row of switches, and the power supply. A change-over contact on a relay is used to reverse the operation of the bottom row, the relay being controlled by the position of the keys in the 8s, 1s and 2s. When the relay is off, as drawn, Fig. 3 gives the same conditions as Fig. 2. When the relay closes, the right-hand contact of switch A comes into operation, and we then get

- (1) None of A, B or C, brown, lamp lights;
- (2) Any one of A, B or C, brown, lamp off;
- (3) Any two of A, B or C, brown, lamp lights;
- (4) All three of A, B and C, brown, lamp off.

[These are the safe combinations for last match loses when reduced to only one match in a row.

The relay is controlled by switch 1 and by nine contacts in series, one on each of the 8s, 4s and 2s switches. These contacts are closed when the switches are off; when any one of these switches

is thrown, the relay is kept off. Switch S is brought out to the front panel; if it is open the relay remains off and the machine plays last match wins, if closed the machine will play last match loses.

Convenience and price dictated the design of the power supply; batteries were discarded because of the trouble of replacement, and also because a rather higher voltage is usually needed for a relay than for the lamp bulbs. A search through the catalogues brought up a 6V operating relay with a change-over contact, and it was then decided to use a valve filament transformer together with 6V dynamo bulbs, each taking 0.3A. If it is felt that these may be overrun on 6.3V, and there is a tendency sometimes to be over-generous with filament voltages, particularly as the transformer is not working at full load—a 6.3V, 2A rating transformer is used—a length of

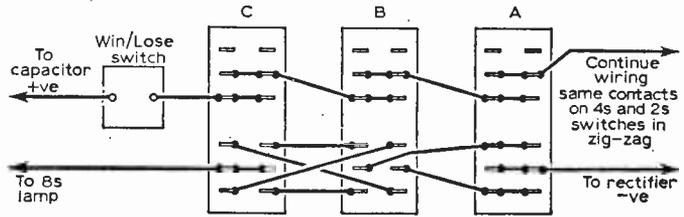


Fig. 7: The wiring of keys in 8s, 4s and 2s rows. The upper half of each key carries the relay control switch; the lower half controls the lamp in the D pile.

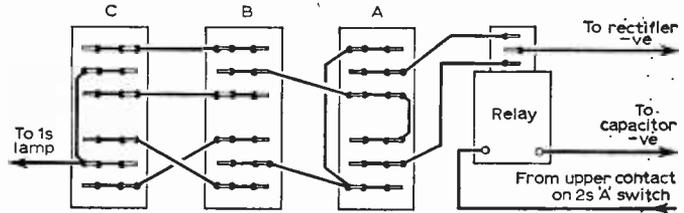


Fig. 8: Wiring the keys in 1s row.

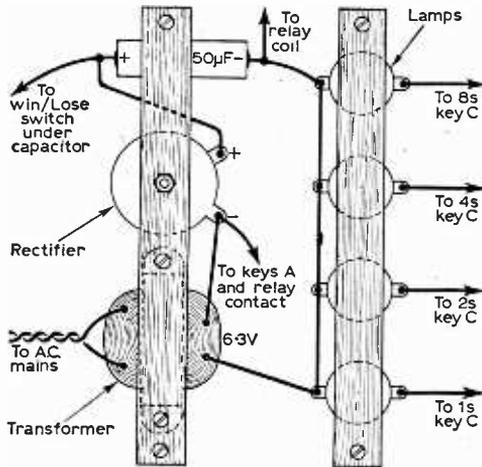


Fig. 6: Mounting and wiring of power supply and lamps.

resistance wire can be incorporated in each lamp lead. The direct supply to the relay is obtained from a battery charger type half-wave rectifier, rating 6V, 1A charging a 50µF, 12V electrolytic. This gives an off load voltage of 8V, dropping to just under 6V when the relay comes in. No mains switch has been used, the unit being on when it has been plugged in. This is permissible since it is unlikely that it will be left plugged in when not in use.

Housing the Instrument

The writer already had a wooden box with hinged lid, measuring 15 1/2 in. x 9 1/2 in. x 4 in. deep, and this was used to house the unit. Any other similar size will serve, the only critical dimension being the 4 in. depth, as the keyswitches require this amount. Lid and base were removed, and a front panel 15 1/2 in. x 9 in. of tin plate was cut and drilled as shown.

Two small wooden supports, 1 in. x 1 1/2 in. x 1/2 in. were glued one on each side of the box opposite

—continued on page 537

THE HOME
PRODUCTION OF

Printed Circuit Boards

DESCRIBED BY
H. W. RUTT

PRODUCING printed circuit boards in a home workshop is not as difficult as it may sound. This type of circuitry is very convenient for miniature units, and it practically eliminates wiring errors.

The first step, naturally enough, is to design the layout of the conductors on the circuit board. Until some practice is gained in designing these boards it will be found rather difficult. The only tips one can give are not to have the conductors spaced by less than $\frac{1}{16}$ in., and not to have the conductors narrower than $\frac{1}{16}$ in. It should also be remembered that the circuit will have to be painted out by hand, and so should not be impossibly complicated.

Drawing the Circuit

When the design has been finalized it should be drawn out on a piece of tough paper of the correct size. The copper-clad laminated plastic board is then cut to size, using a fine-bladed hacksaw, and cutting with the copper layer uppermost. When the board has been cut, its edges should be smoothed down with a fine-toothed file to remove the rough edge of the foil. The design is now transferred to the coppered side of the board by means of carbon paper.

The areas where the copper must remain are now painted with a black, cellulose paint, of the type sold by garages, and this is allowed plenty of time to dry. It is wise to check the painted areas for tiny holes in the paint caused by air bubbles, and to check the layout of the conductors against the design.

Etching Process

The next step in producing the board is to etch away the exposed copper. The etching bath consists of a solution of ferric chloride with 1% by volume of dilute hydrochloric acid added. A 10% solution of ferric chloride may sometimes be

obtained from the chemist without waiting. However this 10% solution gives a rather slow etch and if one is prepared to wait a few days the chemist will usually be able to obtain, or make up the correct etching solution, which is a 30% solution of ferric chloride in water, with 1% of dilute hydrochloric acid (i.e. 30 gr of ferric chloride made up to 100cc with distilled water and 1cc of dilute hydrochloric acid). This solution will not burn skin (though it should be quickly washed off however, it stains terribly, and old clothes should be worn when using it).

The board, with the design painted on it, is placed in a shallow tray of the type used by photographers, and just covered with the etching solution, which may be warmed to about 40°C; it must *not*, however, be hot. The tray is now gently rocked until all the exposed copper has dissolved. When this has happened the board should be well washed, and then allowed to dry.

When the board is dry the paint used to protect the conductors has to be removed. The best substance for this job is trichloroethylene, which may be ordered from the chemist. It costs about 6s. for a $\frac{1}{2}$ litre jar. *If one does use this substance, care should be taken not to inhale much of its vapour as it has harmful effects.* It is possible that other substances such as turps or petrol could be used to soften the paint, but if something like this is tried it should be checked (on an old piece of board) that it does not damage the bakelite backing, and cause the copper to peel off.

Whatever substance is used, the board should be allowed to soak in it until the protective paint is soft, and then it should be gently brushed off.

Drilling the Board

The final operation in preparing the board is to drill it. Each point where a hole is needed is marked, but not centre punched; centre punching can easily cause the backing to crack. A No. 5 slow spiral drill is used to make the holes for wires which have to be soldered to the copper. The board *must* be drilled from the coppered side, to prevent the copper peeling off the board, and slow spiral drill is essential for this operation.

The board itself is now finished, but several points should be observed when wiring it. Firstly, all connections to the board should be made quickly, or the heat may cause the copper conductor to peel off the bakelite backing. Secondly, one should be very careful to solder in multiple contact parts (such as IFT's) the right way round the first time—they can be very difficult indeed to remove if you do not get it correct. Thirdly, resistors, capacitors, etc., should be right up against the bakelite backing, for if they are not any pressure on the component will tend to peel the copper off the board. When the board is completely wired up and tested the soldered side of the board may be varnished to protect it from corrosion, but this tends to make servicing rather more difficult.

Any constructors wishing to make their own printed circuit boards should have little difficulty obtaining the chemicals or the copper-clad laminate board, and it is hoped that this article will help to bring printed circuits out of the "oh, that much too difficult" class of construction. ■


TOP QUALITY—LOW COST  **AMATEUR RADIO EQUIPMENT**

CR 66 COMMUNICATIONS RECEIVER

THE FINEST KIT EVER OFFERED



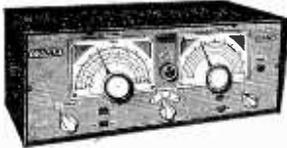Frequency Range 540 Kc/s to 30 Mc/s in four Band-switched ranges.



Electrical Bandsread. Coil Unit wired ready and I.F. Transformers factory aligned, no test equipment required. Temperature compensated trimmer. Regenerative I.F. stage for maximum gain and B.F.O. Panel aerial trimmer, separate speaker switch, 3 watts output for external 2-3 ohm speaker. Separate cathode follower for tape recording etc. Valve line-up—ECH81, EBF89, ECC81, EL84, EZ80, EM84. (Optional extra). For 200-250 volt A.C. Cabinet size 16 x 6½ x 8½in.

Complete Kit with 17-page Instruction Manual Carriage 6/- **£18.50**

Tuning indicator parts with EM84 17/6. H.P. Terms available on request.

★ **P.R. 30 R.F. PRESELECTOR** ★



Frequency range 1.5-30 Mc/s.




Substantially improves the performance of any superhet receiver.

G4HZ writes . . . I am delighted with it, it improves my Eddystone 640 in all respects. The difference with the Preselector is fantastic, a weak signal on 15 metres about S2 changed to S8. On the L.F. Bands, unwanted noise and mush is cut out. G3RIA writes . . . The results in conjunction with my Eddystone 888 are amazing. Signals are twice as strong with much higher signal/noise ratio. A first class product well worth the money. The P.R.30 uses EF 183 Frame Grid R.F. Amplifier and provides up to 20 dB gain. Features include vernier tuning, gain control, selector switch for either dipole or end fed antenna. External power supplies (obtainable from Rx). Smart styling in grey and black. Complete, ready for use, with all plugs, cables.

£4.17.6 Carr. 3/-.

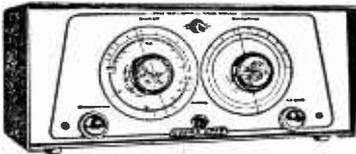THE NEW CR 45 ★ **NEW STYLING TOP PERFORMANCE**



- ★ Tunes 10-2000 metres (5 Coils).
- ★ Separate electrical bandsread.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel Silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb styling. World-wide reception. Total building cost, with 2 Coils, 25-75 and 60-175 metres. Instruction Manual 11 pages, less Cabinet

£6.19.6 carr. 3/6.

CR 45 Cabinet Silver Grey, 12 x 5½ x 7in. sliding door for easy coil changing **27/6**

Extra coils, all ranges **4/9** each.

ALL PARTS AVAILABLE SEPARATELY

★ **THE MINI-CLIPPER**



- ★ Tunes 10-2000 metres (5 coils).
- ★ Miniature 1 valve, all band receiver.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Air spaced ball bearing condensers.
- ★ Provision to add two-transistor amplifier.
- ★ Battery lasts months.

36/6



Can be built in an evening, will receive Amateur and Broadcast stations from all parts of the world. Total building cost with one coil 25-75 metres, Instruction Manual 4 pages, 36/6, carr. 2/6. Extra coils, all ranges, 4/9 each. Electrical bandsread available. All parts available separately.

★ **THE SUPER CLIPPER** ★

- ★ Tunes 10-2000 metres (5 coils).
- ★ Large precision dial, dual slow motion drives.
- ★ Bandsread on all Bands.
- ★ High gain valve/transistor hybrid circuit.
- ★ 2 Mullard transistor amplifiers, pre-assembled and tested.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Batteries last months.

88/6



Easy to assemble, this top performance All Band Receiver brings a new world of listening pleasure to your finger-tips at low cost. Total building cost with 2 Coils, 20-60 and 55-190 metres, Instruction Manual 7 pages, 88/6, carr. 2/6. Extra Coils, all ranges, 4/9 each. Front Panel, Silver Grey, 10 x 7½in. 6/9.

Please note **NEW** address. We have now acquired new modern premises, combining all depts., offices and laboratories. New equipment under development will be announced in due course. CODAR Equipment is famous for Top Quality, Peak Performance and Easy-to-Follow Instructions—no guesswork. 6d. in stamps brings illustrated leaflets.

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX

G3IRE


Canadian Distributors: JAYCO ELECTRONICS, TWEED, ONT.

G3IPA

THE LINEAR L1/10

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 9 x 7 x 5ins. In addition two high impedance input sockets are provided for microphone and gram., etc. With selector switch and vol. control, five B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81, H.T. and L.T. power supply point is included for a radio tuner.

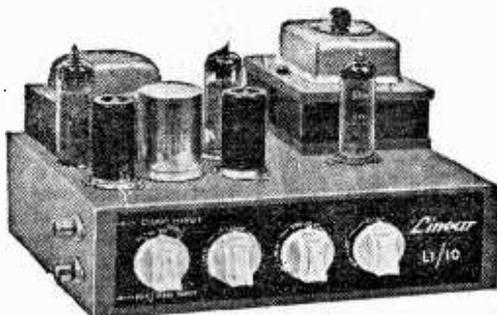

FREQUENCY RESPONSE

1 d.b., 30-20,000 c.p.s.

MAXIMUM POWER OUTPUT

in excess of 14 watts.

SENSITIVITY

L.P. 220 m.v. for 10 watts. 78 r.p.m. 220 m.v. for 10 watts. Radio/Microphone 40 m.v. for 10 watts.

TREBLE LIFT CONTROL

+ 10 d.b. to -22 d.b. at 12,000 c.p.s.

BASS CONTROL

+ 14 d.b. to -10 d.b. at 50 c.p.s.

HUM LEVEL

Referred to maximum output and including integral pre-amp.—70 d.b.

NEGATIVE FEEDBACK

21 d.b. in main loop.

HARMONIC DISTORTION Less than 0.1% measured at 8 watts at 1000 c.p.s. Weight 10 lbs. Power consumption 90 watts. For 200-230-250 v. 50 c.p.s. A.C. mains. Outputs for 3 and 15 ohm speakers. Chassis finish stoved Gold hammer.

HIGHEST QUALITY Retail Price

MAXIMUM RELIABILITY **13**

AT A PRICE YOU CAN AFFORD **GNS.**

Send S.A.E. for descriptive literature

Also Available—THE L.45.A compact High Quality 4.5 watt amplifier. Size approx. 7.5-5 1/2 in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner etc. B.V.A. valves used are ECC83 EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5.19.6.

THE L745 TAPE DECK AMPLIFIER. A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loudspeaker and practically any make of deck.

Negative feedback equalisation adjustment by multi-position switch for 1 1/2, 3 1/2 and 7 1/2 in. per second. Retail price 12 gns.

DIATONIC 10-14 WATT. High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

CONCHORD 30 WATT. Hi-Fi amplifier with two separately controlled inputs. Retail 16 gns.

L50 50 WATT AMPLIFIER. Size approximately 14 x 10 x 8 in. Sensitivity 25 mV. Output for 3 and 15 Ω speakers. Retail price 22 gns.

L5/5 STEREO AMPLIFIER 5 x 5 watt 12 gns.

TRADE ENQUIRIES to

LINEAR PRODUCTS LTD.

ELECTRON WORKS, ARMLEY, LEEDS

H.A.C. SHORT-WAVE EQUIPMENT AND SHORT-WAVE KITS

Famous for over 25 years for... S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVERS KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-valve Kit, Model "C". Price 85/-. Two-valve Kit, Model "E". Price 50/-. New Addition: Model "K". Super sensitive "All Dry" Receiver. Special inc. price. Complete Kit, 77/-.
All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS

(Dept. TH), 44 Old Bond Street, London W.1

Please send me FREE and without obligation your 1963 literature.

NAME.....

ADDRESS.....

NEW VALVES!

Guaranteed Set Te. ted 24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF9L, DF9L, DK91, DL92, DL94, SET of 4, 16/9.

DAF96, DF96, DK96, DL96, SET of 4, 24/-

OA2	4/6	DL33	7/3	PCF80	5/6
1D3	6/9	L36	6/6	PCF32	6/6
1R5	4/9	DL92	4/9	PCL82	7/6
1S5	3/9	DL94	5/6	PCL83	8/6
1T4	2/9	DL96	6/-	PCL84	4/9
3S4	4/9	EB91	2/-	PL34	8/6
3V4	4/6	EB41	7/-	PL81	7/3
5U4G	4/3	EBP80	7/-	PL82	5/6
5Y3GT	4/3	EBL21	9/-	PL83	5/3
5Z4G	7/-	ECC40	7/6	PL81	6/6
6KT7	1/6	ECC81	3/9	PY31	6/6
6K9G	3/9	ECC82	4/6	PY32	8/9
6QT6	4/6	ECC83	4/6	PY90	5/6
6V6G	3/9	ECC84	6/-	PY81	5/6
6X5GT	5/6	ECC85	7/-	PY82	5/3
12K7GT	3/11	ECP80	6/3	PY83	6/3
12K9GT	9/6	ECP82	7/6	U25	8/9
12K9GT	3/11	ECH42	7/9	U26	7/9
12SN7GT	5/6	ECL80	6/-	UABC90	5/6
1487	14/-	EF41	6/9	UAF42	7/6
35L8GT	7/6	EP80	4/-	UBC41	9/6
35Z4GT	4/9	EP85	4/9	UBP80	7/6
8A2	6/6	EP88	6/3	UCC85	6/6
AC/TP	19/6	EP89	4/3	UCH42	7/3
CL33	3/6	EP91	2/9	UCB81	7/3
DAC32	8/3	EL41	7/6	UCL82	3/6
DAF91	3/9	EL84	5/6	UCL83	9/6
DAF96	6/-	EY75	6/-	UF41	6/9
DF33	8/6	EY86	6/-	UF89	6/3
DF91	2/9	EZ40	5/9	UJ41	7/6
DF96	6/-	EZ80	4/6	UL84	6/3
DH77	4/6	EZ61	4/3	UJ8	12/6
DK32	8/9	KTW81	5/-	UY21	9/-
DK91	4/9	MU11	5/-	UY41	5/-
DK92	6/9	PCC84	5/9	UY85	4/3
DK98	6/6	PCC89	7/6		

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra Any C.O.D. Parcel 4/3 extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD, STOKE NEWINGTON, LONDON, N.16



The PUNCH you need!

HOLE PUNCHES

Instant Type	6/10 ea.
3/4" diameter	
Screw-up Type	
1/2" diameter	8/6 "
3/8" diameter	9/- "
1/4" diameter	10/2 "
3/16" diameter	10/8 "
1/8" diameter	11/8 "
3/16" diameter Int. Octal	13/4 "
1/4" diameter	16/2 "
3/8" diameter	18/10 "
1/2" diameter	21/8 "
3/4" diameter	24/4 "
2 1/2" diameter	33/2 "

Complete Set £8.15.0.

No extra charge for postage and packing in the U.K.

Oliver & Randall Ltd

Dept. 7
7 KELSEY PARK ROAD,
BECKENHAM, KENT
Tel.: Beckenham 8262

A Variable Mains Transformer

BY T. PALMER

WHEN it is required to apply a fraction of the mains voltage to a given load, it is possible to use a resistive potential divider, but often the resistors will be bulky, and there may be problems of heat dissipation. If the supply is a.c., a variable voltage mains transformer is frequently more convenient; also, in addition to providing a ratio less than unity, the transformer can step up the voltage, which is beyond the scope of the resistive potential divider.

Commercial Equipment

Variable mains transformers are commercially available, and are known by various trade names. They work on the principle of an auto-transformer: a manual control determines the position of a tapping on a toroidal winding. It enables adjustments to be made in such small increments that the transformers are described as being infinitely variable. They can also be described as rather expensive.

The device discussed in this article uses a comparatively cheap battery-charging transformer; and it is not infinitely variable. The increments of voltage are however small enough for most purposes. A suitable transformer is the Douglas MT3. It has a 30V secondary, tapped at

12, 15, 20 and 24V. A fraction of the secondary voltage is added to, or subtracted from, the mains voltage. This gives a range of 60V. However the primary has tapplings for 240, 220 and 200V. These enable us to use auto-transformer action and to obtain a wider range. When the tapplings on the primary and on the secondary are fully used, the output can be varied from 155 to 308V, with the mains voltage at 225V.

The wiring is such that, if necessary, the secondary can be quickly disconnected from the primary; it is then available for supplying voltages less than 30V. A voltmeter is incorporated in the instrument, with a switch which provides a reading of the incoming mains, the outgoing mains, or the low voltage secondary.

In Fig. 1, P1 and P2 represent voltage-adjusting panels of the type frequently associated with mains transformers. S1 and S2 are single-pole, 3-way switches. They are not ganged.

Principle of Operation

Let us first assume that the incoming mains voltage is 220V, and that the studs in the voltage-adjusting panels, P1 and P2, are both set to 220V. If switches S1 and S2 are both set to position A, the outgoing mains voltage is the same as the incoming. For simplicity, only one tapping is shown on the secondary. If S1 is set to A and S2 to B, the voltage AB may be added to the primary voltage. Then, if S1 is set to B, and S2 to A, the voltage AB is subtracted from the incoming mains

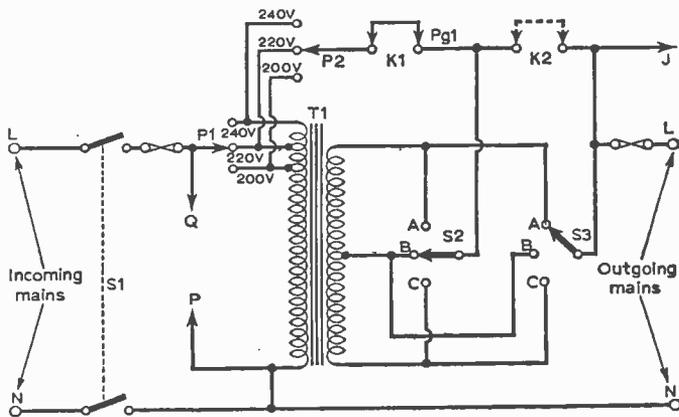


Fig. 1: The circuit of the transformer.

voltage. Thus, adjusting the secondary switches S1 and S2 gives a range from 220+30V to 220-30V, i.e. from 250 to 190V.

Suppose we want a voltage higher than 250V. We shall continue to assume that the incoming mains voltage remains at 220V.

We screw the stud in P1 in the 200V position and that in P2 in the 240V position. The full secondary voltage is now more than 30V, and it can be added, by suitable operation of S1 and S2, to a voltage which is now greater than 220V, because of the auto-transformer action in the primary. It is on

this basis that the outgoing mains voltage can be stepped up to a value of the order of 300V.

If we want a voltage which is less than 190V, we screw the studs in P1 in the 240V position, and that in P2 in the 200V position. S1 and S2 are adjusted so that the secondary voltage subtracts from the primary voltage.

In the model made by the writer, sufficient variation was obtained for his purpose by adjusting switches S1 and S2 on the front of the instrument. The voltage-adjusting panels P1 and P2 were mounted at the back. If greater variation is frequently required, it may be more convenient to have P1 and P2 in the form of two single-pole, 3-way switches on the front.

The secondary voltage, as selected by switches S1 and S2, is taken to a 2-pin, 2A socket, K2. A 2-pin, 5A plug Pg1, with the pins connected by a short length of wire, connects the primary to the secondary. It fits into the socket K1. The 5A plug has a small paxolin panel associated with it so that when the plug is inserted in K1, the 2-pin, 2A, socket K2 is masked by the panel. It is thus impossible to insert a plug into the socket for the secondary, when the secondary is connected to the mains.

The Voltmeter

The writer used a meter scaled from 0 to 300, which had a full scale deflection of 5mA. A 5mA rectifier was used with it. The voltmeter had two ranges: 0-30V, for measuring the secondary voltage; and 0-300V for the incoming and outgoing mains voltage. The series resistors to be used with the meter depend on the full-scale deflection of the meter, and on the range. The following will show the method of calculating their values. The example relates to a 5mA meter used on the 300V range.

When a current with a mean value of 5mA flows through the meter giving full scale deflection, the maximum current in each half cycle is $5 \times \pi/2$ mA.

If the r.m.s. value of the voltage is 300V, the maximum voltage in each half cycle is $300 \times \sqrt{2}$. Thus the resistance in the circuit must be

$$\frac{300\sqrt{2}}{5/1,000 \times \pi/2} = \frac{300,000}{5} \times \frac{1}{1.11} = 54,000\Omega.$$

For the 30V range the resistance of the circuit must be 5,400Ω. The resistance of the meter itself (and the rectifier) is negligible in comparison with these values. The voltmeter circuit is shown in Fig. 2.

The terminals at the top of the instrument are provided so that the 30V range of the voltmeter can be used to measure external voltages. Alternatively, the external voltage can be applied by inserting a plug into a socket situated between two of the terminals. (This socket is not the socket K2, which is masked by the paxolin panel.) The voltmeter range switch, S4 in Fig. 2, is next to the meter. Switches S1 and S2 have pointer-type knobs. Of the remaining two

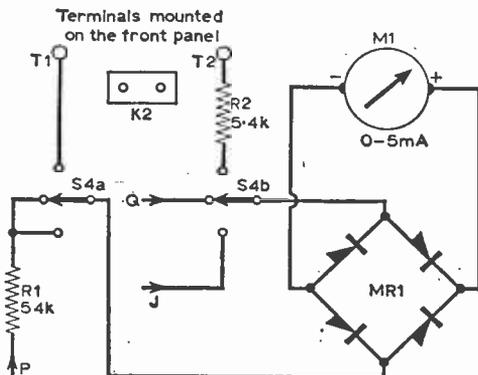



Fig. 21 The voltmeter circuit.

switches, one is the on/off switch S3; the other is not used in the final form of the instrument. The model is larger than is necessary for the facilities mentioned in this article; it includes a 12V, 2A rectifier, and a 3-pin, 2A socket, for the rectified voltage.

To measure the secondary voltage selected by switches S1 and S2, the socket K2 must be connected to two of the terminals at the top of the instrument.

Resistance and Capacitance Measurement

The provision of a link Pg1 to connect the primary to the secondary enables the instrument to be used for measuring resistance and capacitance. With the link Pg1 in position, the outgoing mains voltage is adjusted to the same value as the incoming mains voltage, V_1 . The resistor or capacitor to be tested is then connected in place of Pg1. The voltage V_2 , read when the voltmeter switch is thrown to the position for the outgoing mains, is then observed to be less than V_1 . The ratio V_1/V_2

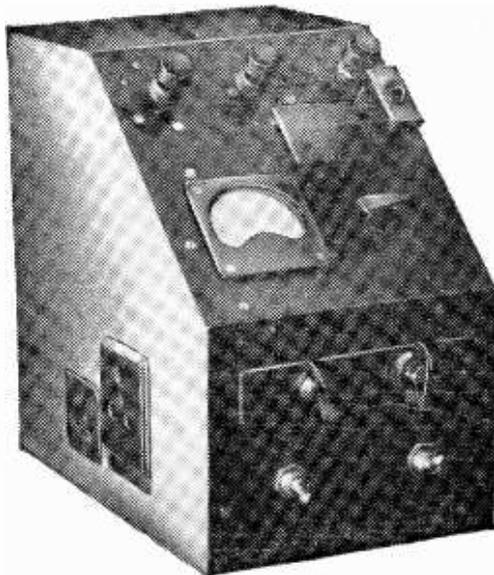

A view of the author's unit.

RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt. * Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer, GEC912 Plus. Fully detailed list on any of these sent upon request. Instruction Manual; All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5. GEC912 4/6. All post free.

● TRANSISTORISE YOUR CRYSTAL SET

We have two new designs for Transistor amplifiers which can be used to greatly improve the signal from any crystal set. RLD4 Kit, one stage 10/6; RLD5 Kit, two stage 17/6, both post free. The kits are easy to build and very detailed instructions are supplied. Leaflet available.

● CLOSE TOLERANCE CONDENSERS

Radio spares first grade Silver Mica. Tolerance—up to 39pf. ± 1pf. 47pf. up to 1%. 4.7, 10, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 100, 120, 150, 180, 200, 220, 250, 270, 300pf. All 9d. each. 330, 390, 470, 500, 556, 680, 800pf. A.1 1/4 each. 1000, 1500, 1800, 2200, 2700, 3600, 4700, 5000pf. All 1/8 each. Postage extra.

● MINIATURE WIRE WOUND RESISTORS

5 watt, 5% tol. Size 1 x 1/4 in. 15, 25, 30, 39, 50, 68, 75, 100, 125, 150, 180, 200, 220, 250, 270, 300, 350, 400, 470, 680, 750, 820 ohms. 1k, 1.2k, 1.5k, 1.8k, 2.2k, 2.7k, 3k, 3.3k, 3.9k, 4.7k, 5.6k, 6.8k, 8.2k. All 1/6d. each. Postage extra on all above.

● NEW MULLARD CONDENSERS

Mullard Miniature Foil and Polyester condensers as used in the latest TV and Transistor sets. Miniature Foil, 30 volt working for Transistor sets. .01mfd, 71d.; .022mfd, 9d.; .047mfd, 9d.; .1mfd, 11d. Polyester Tubular Capacitors. Moulded outer case designed to withstand accidental contact with the soldering iron. Tolerance 10%. 15v. range: .01mfd, .022mfd, .047mfd, all 9d. each. .1mfd, 12d.; .22mfd, 13d.; .47mfd, 14d.; 1mfd, 21d. 400v. range: .01mfd, .022mfd, .047mfd, .1mfd, .022mfd, all 9d. each. .047mfd, 1/2, .1mfd, 1/3, .22mfd, 1/6, 47mfd, 2/5. Postage extra.

● MINIATURE ELECTROLYTIC CONDENSERS

Latest miniature types by Mullard and Radio spares. RADIO SPARES. All 15 volt, 2mfd, 4mfd, 5mfd, 8mfd, 10mfd, 16mfd, 32mfd, 50mfd, 100mfd, all 2/3 each. Postage extra. MULLARD. 2mfd, 10v, 1/8; 4mfd, 4v, 1/8; 10mfd, 10v, 1/8; 16mfd, 10v, 1/8; 25mfd, 4v, 1/8; 25mfd, 25v, 1/8; 32mfd, 2.5v, 1/8; 32mfd, 40v, 1/8.

● "SYNCHROTAPE" RECORDING TAPE

Low priced British tape, all reels fitted with leaders. Standard Play: 800ft. (5") 13/8; 850ft. (5 1/2") 17/-; 1,200ft. (7") 21/-; Long Play: 900ft. (5 1/2") 17/-; 1,200ft. (5 1/2") 20/-; 1,800ft. (7") 30/-. All Post Free.

● TAPE RECORDING EQUIPMENT

TAPE DECKS	Hire Purchase	
ALL CARRIAGE FREE	Cash Price	Deposit Mthly/Pmts.
COLLARO STUDIO, Latest Model, Two track, Bracmatic Heads	£10.19.6	£2. 3.6 12 of 16/4
Four Track, Marriot Heads	£17.17.0	£3.12.0 12 of 26/2

MARTIN TAPE AMPLIFIER KITS	Hire Purchase		
Tape Amplifiers	Cash Price	Deposit Mthly/Pmts.	
For Collaro 8311-V 2-Track	£11.11.0	8311-4-V 4-Track	£12.12.0
Tape Pre-Amplifiers			
For Collaro 8312-CP 2-Track	£8.8.0	8312-4-CP 4-Track	£9.9.0
Drop through assembly for mounting 8312 Pre-Amp under Collaro Deck, £11.1.6.			
Casing Cases with speaker. For Collaro Deck and 8311 Amplifier	£5.5.0.		

H.P. TERMS available on decks, amp. and cases. Ask for quote. MULLARD TAPE PRE-AMPLIFIER KIT We stock complete kits and all separate components for the Mullard Tape Pre-Amp kit. Fully detailed list available.

● LOUDSPEAKERS

GOODMANS: Axiotea 8in., £5.5.7; Axiom 10in., £6.5.11; 12in., Axiom 201, £10.7.0; 12in., Axiom 301, £14.10.0; 12in., Audiom 51 Bass, £9.14.0; 12in., Audiom 41 Bass, £13.14.0; Trebas Tweeter, £6.4.0; X05000 Crossover unit, £1.19.0. WHITELEY: HF106 10in., £7.0.0; HF1012 10in., £4.7.6; HF516 8in., £6.0.0; T816 8in., £5.13.6; T10 Tweeter, £4.8.3; T359 Tweeter, £1.10.6; CX3000 Crossover unit, £1.11.6; CX1500 Crossover unit, £2.0.0. H.P. Terms available on all speakers.

● STEREO COMPONENTS

Morganite warged potentiometers as specified for the Mullard circuits. * Log/Anti-Log, 500k, 1 meg, 2 meg. * Log/Log, 50k, 250k, 1 meg, 2 meg. * Lin/Lin 250k, 500k, 1 meg, 2 meg. All 10/6 each. Postage extra.

● TRANSISTORS

MULLARD. Current production types, not rejects. All in makers' boxes. Postage 3d. on each. AF114, 11/-; AF115, 10/6; AF116, 10/-; AF117, 9/8; OC44, 2/3; OC45, 9/-; OC70 and OC71, 8/6; OC72, 8/6; OC72 Matched Pairs, 16/-; OC78, 8/-; OC81, 8/-; OC110, 9/6; OC171, 10/6. Any other Mullard type obtained promptly. Ask for quotation.

● JASON F.M. TUNERS

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows:

FMT1, 28.12.6; FMT2 (less power),	£7.15.0.
FMT2 (with power), 29.12.6; FMT3 (less power),	£9.9.6.
FMT3 (with power), 21.7.6; Mercury 2,	£10.14.6.
JTV75,	£14.12.6.

Hire Purchase Terms available. Ask for list. P.W. STRAND, MAYFAIR & SAVOY UNITS We stock parts for the P.W. Strand Amplifier, Mayfair Pre-Amplifier and Savoy FM Tuner. Detailed price lists are available.

● LATEST TEST METERS

	Cash Price	Deposit	Mthly/Pmts.	Hire Purchase	
AVO Model 8 Mark II ..	£24. 0.0	£4.16.0	12 of	£1.15.2	
AVO Model 7 Mark II ..	£21. 0.0	£4. 4.0	12 of	£1.10.10	
AVO Multimeter Mark 4 ..	£9.10.0	£1.18.0	12 of	1/4/4	
T.M.K. TP3 ..	£5.19.6	£1. 3.6	3 of	£1.2.0	
T.M.K. TP35 ..	£5.19.6	£1.15.6	3 of	£1.1.4	
T.M.K. Model 500 ..	£8.19.6	£1.15.6	12 of	13/8	
TAYLOR MODEL 127A ..	£10.10.0	£2. 2.0	12 of	15/8	
CARY A10 ..	(Post 1/6)	£4.7.6	£1. 7.6	3 of	£1.6.6
CARY B-20 ..	(Post 1/6)	£4. 8.0	£2. 0.0	3 of	£1.3.4
CARY M-1 ..	(Post 1/6)	£2.14.0			

Full details of any of the above supplied free on request. The AVO models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

● OUTPUT TRANSFORMERS

GILSON: W0666A, W0666B, 50/6, post 2/6. W0710, 55/6, post 2/6. W0892, 62/3, post 2/6. W0767, 27/-, post 1/6. W01766A, 67/6, post 2/6. W01932, 84/-, post 3/-. PARMER: P3667, 75/-, post 2/6. P4131, 75/-, post 2/6. PARMER: P2622, P2623, P2642, 45/-; P2643, 47/6. All plus post 2/6; P2641, 29/6, post 2/-; P2628, 17/-, post 2/-; P2632, 41/-, post 2/6. ELSTONE: OT/ML, 49/6, post 2/8; OT/3, 27/6, post 2/6.

● MAINS TRANSFORMERS

GILSON: W0741A, 63/-, post 4/-; W0839, 48/6, post 2/6; W01326, 58/6, post 3/6; W01288, 58/-, post 3/6; W01566, 80/-, post 4/6; W01841, Choke, 38/-, post 2/-. PARMER: P2631, 35/-, post 2/6; P2630, 54/6, post 3/6; P2644, 76/6, post 4/-; P2590, 41/-, post 3/6; P2631, 56/6, post 3/6. ELSTONE: MT/BU, 49/6, post 3/6; MT/3M, 58/6, post 3/-; MT/610, 46/8, post 3/6.

● GRAMOPHONE EQUIPMENT

ALL LATEST MODELS	Hire Purchase	
ALL POST FREE	Cash Price	Deposit Mthly/Pmts.

RECORD CHANGERS				
GARRARD AUTOSLIM (Mono PU)	£7. 2.6	£1. 8.6	12 of	11/8
GARRARD AUTOSLIM De-luxe AT6 (Mono PU)	£11. 9.0	£2. 6.0	12 of	16/11
GARRARD AUTOSLIM De-luxe AT6 (S/M PU)	£12. 5.4	£2. 9.4	12 of	18/-
B.S.R. UA14 (TC8 Mono PU)	£6.19.6	£1. 7.6	12 of	11/-
B.S.R. UA14 Monarch (TC8 Stereo/LP/78)	£7.19.6	£1.11.6	12 of	12/4
B.S.R. UA16 (TC8 Mono PU)	£7.19.6	£1.11.6	12 of	12/4
B.S.R. UA16 (TC8 Stereo/LP/78)	£8.19.6	£1.15.6	12 of	13/8
SINGLE RECORD PLAYERS				
B.S.R. TU12 (TC8 Mono PU)	£3.17.6	£1. 4.6	3 of	£1.1.0
B.S.R. GU7 (TC8 Mono PU)	£4.18.8	£1. 8.8	3 of	£1.6.8
GARRARD SRP10 (Mono PU)	£5. 9.11	£1.12.11	3 of	£1.9.0
TRANSCRIPTION UNITS				
GARRARD 4HF (GC8 PU)	£16.12.6	£3. 6.6	12 of	£1.4.5
PHILIPS AG1016 (S/M PU)	£12.12.0	£2.12.0	12 of	18/6

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

* TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £25, minimum of 4/2. Over £25 and under £10, 2/8. Over £10, no charge. Postage extra on CASH orders; under £5 except where stated. Postage extra on overseas orders irrespective of price.

WATTS RADIO

(MAIL ORDER) LTD.

54 CHURCH ST., WEYBRIDGE, SURREY

Telephone: Weybridge 47556

Please note: Postal business only from this address

Callers welcome by appointment

* HIRE PURCHASE TERMS

Available on any item. Repayments over 3, 6 or 12 months as below. Three months: Deposit 6/- in the £. Service charge 5%. minimum charge 10/-. Six months: Deposit 5/- in the £. Service charge 7%, minimum charge 15/-. Twelve months: Deposit 4/- in the £. Service charge 10%, minimum charge 20/-.

ANOTHER TAPE RECORDER BARGAIN

*Mfrs. end of production
Surplus Offer*



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A modern Circuit for quality recording from Mike, Gram or Radio, using latest B.S.R. Twin Track Monardeck Type TD2. Valve line up EF86, ECL82, EM84, EZ80 and Silicon Diode.

- 2 tone Cabinet and 8" x 5" Speaker, Size 14" x 10 1/2" x 7 1/2" **£3.10.0** +5/- Carr.
- Wired Amplifier complete with 4 Valves, front Panel, Knobs **£5.12.6** +3/6 Carr.
- B.S.R. Monardeck Type T.D.2 **£7.7.0** +4/6 Carr.
- Accessories—Mike, Tape, Spare Reel, Scr. Lead, Plugs, etc. **£1.0.0** +2/- Carr.
- COMPLETE KIT** comprising items above **15 gns.** +10/- Carr.

Leaflet, circuits, instructions, 2/- post free

NEW BRITISH RECORDING TAPE

Famous Manufacturer. Bulk purchase, genuine recommended Tape Bargain. Unconditional Guarantee. Fitted Leader & Stop Folds (except 3in.).

Standard (PVC base)	Long Play (PVC base)	D'ble Play (Mylar base)
3in. 150ft. 3/9	225ft. 4/9	300ft. 6/6
5in. 600ft. 11/8	900ft. 15/-	1200ft. 25/-
5 1/2in. 1200ft. 14/8	1200ft. 17/8	1800ft. 32/8
7in. 1200ft. 17/8	1800ft. 22/8	2400ft. 42/8

Post and Packing—3in. Reels 6d. Each additional Reel, 3d.
4in. to 7in. Reels 1/-, Each additional Reel, 6d.

EMPTY TAPE REELS (Plastic): 3in. 1/3, 5 1/2in. 2/-, 7in. 2/3.
PLASTIC REEL CONTAINERS (Cassettes): 5in. 1/9, 5 1/2in. 2/3.

Condensers—Silver Mica. All values 2pF to 1,000pF. 6d. each. Ditto, Ceramics. 9d. Tub. 450V T.C.C. etc. 0.001 mfd to 0.01 and 0.1/350V. 9d. 0.02-0.1/500V. 1/-, 0.25 Hmths 1/6. O.5 T.C.C. 1/9 etc. etc. Close Tol. 8/Micas—10% 5pF-500pF. 8d. 600-6,000pF. 1/-, 1% 2pF-100pF. 9d. 100pF-500pF 11d. 575pF. 5,000pF. 1/6. **Resistors**—Full Range 10 ohms-10 meg. ohms 20% 1/2 and 1W. 8d., 1W. 5d. (Midget type modern rating) 1W. 6d., 2W. 9d., 10% 1W., 1W., 4d. Hi-Stab. 5% 1/2, 1W. 6d. (100 ohms-1 meg). Other values 9d. 1% 1W. 1/6.

TUB-ELECTROLYTICS-CAN
25/25v. 50/12v. 1/9; 8+8/450v. 4/6. 50/50v. 100/25v. 2/-; 32+32/275v. 4/6 8/450v. 4/350v. 2/3; 50/50/350v. 6/6 16+16/450v. 5/8; 60/250/275v. 12/8 32+32/450v. 6/6; 100+200/275v. 12/8
Transistor Midget types—all values 1 mfd to 50 mfd 1/9 ea., 100 mfd. 2/- Ditto 150 v. wkr. .01 to .04 mfd. 9d. .05 to 1 mfd. 1/- .25 mfd. 1/3, etc.
Enamelled Copper Wire—1lb. reels 14g-20g 2/6; 22g-25g. 3/-; 30g-34g. 3/8; 36g-38g 4/3; 38g-40g. 4/6, etc.

JASON FM TUNER UNITS. Designer-approved kits of parts. FMT1, 5 gns. 4 valves, 20/- FMT2, £2. 3 valves, 37/6. JTV MERCURY 10 gns. JTV2 £13.19.6, 4 valves, 32/8. New JASON FM HANDBOOK, 2/6. 48 hr. Alignment Service. 7/6. P. & P. 2/6.

Volume Controls—5K-2 Meg. ohms. 3in. Spindles. Morganite Midget Type 1 1/2in. diam. Guar. 1 year. LOG or LIN ratios less Sw. 3/- DP. Sw. 4/6. Twin Stereo less Sw. 6/6. DP. Sw. 9/-.
TYGAN FRET (contem. pattern), 12 x 12in. 2/-, 12 x 15in. 3/-, 12 x 24in. 4/-, 18 x 24in. 6/- etc.

BARGAIN CORNER
Brand New. Manufacturers Surplus First Grade.
1 OC44 and 2 OC45, 15/8. 1 OC81D and 2 OC81. 15/6. All above plus OAS1, 32/8 post free.
1/2 Meg. Volume Controls. DP. Sw. 1 1/2in. flatted Spindle Famous Manufacturers. 4 for 10/- post free.

RECORD PLAYER CABINETS

Cabinet Price **59/6** Carr. & Ins. 5/-.
Attractive, contemporary two tone. Size 15 1/2 x 14 1/2 x 8 1/2in., fitted all accessories.
2-VALVE 2-WATT AMPLIFIER.
Twin stage ECL82 with vol. and neg. feedback Tone control. A.C. 200/250 v. with knobs, etc., ready wired to fit above cabinet Inc. 6 1/2in. speaker, etc. £3.19.6. Carr. 2/6.



Complete Kit including BSR UA14 Unit as illus. New reduced Bargain Price **£11.10.0**. Carr. 7/6.

Terms C.W.O. or C.O.D. Post and Packing up to 1/2 lb. 7d., 1lb. 1/1. 3lb. 1/6, 5lb. 2/-, 10lb. 2/9. Hours: 9 a.m. to 6 p.m., 1 p.m. Weds.



RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK ROAD, THORNTON HEATH SURREY. Est. 1946. Telephone: THO 2188

ADAMIN-
by **LITESOLD**



These new ADAMIN micro soldering instruments supplement the well-known LITESOLD models for special applications and still further extend our very comprehensive range of specialised soldering equipment.
Bit sizes now 1/2in. to 1 1/2in.

A POPULAR ADAMIN MAINS MODEL

The C10L (shown on bench stand) is probably the smallest mains voltage model in the world. Bit dia. 3/32in., length 7in., weight 1oz. (less flex). Heats in 30 secs.

Brochure No. S10 sent free on request.

Sole proprietors and manufacturers:
LIGHT SOLDERING DEVELOPMENTS LTD
28 Sydenham Road, Croydon, Surrey
Phone: CROYdon 8589 Grams: Litesold Croydon

NEW, REVISED EDITION OF A STANDARD TEXT BOOK

Wireless Servicing Manual
W. T. COCKING, M.I.E.E.

WIRELESS SERVICING MANUAL has become the standard guide to repair, maintenance and adjustment of radio receivers. Brought fully up to date for this tenth edition, it includes a chapter on transistors and transistor sets. In practice transistor sets present similar problems to valve sets, and the policy has been to emphasise differences. Other chapters cover every aspect of radio receiver servicing, and an appendix provides much useful data. The author is well known as former editor of *Electronic Technology* and present editor of *Industria Electronics*.

288 pp., 8 3/4" x 5 1/2". 25s. net, by post 26s.

Published for "Wireless World" by **LILFEE BOOKS LTD**

DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

and the value of the voltmeter resistor R_1 , enable the value of the resistor or capacitor under test to be calculated.

If R_x is the value of the resistor which replaces $Pg1$ it can be shown that

$$R_x = R_1 \left(\frac{V_1}{V_2} - 1 \right) = R_1 \left(\frac{V_1 - V_2}{V_2} \right) \dots (1)$$

If X_c is the reactance of the capacitor which replaces $Pg1$, it can be shown that

$$X_c^2 = R_1^2 \left[\left(\frac{V_1}{V_2} \right)^2 - 1 \right] \dots (2)$$

If the frequency is 50c/s, we have

$$C = \frac{10^6}{314 R_1 (V_1^2 - V_2^2)^{1/2}} \mu F \dots (3)$$

These expressions assume that when resistance is being measured, the component under test has no reactance, and when capacitance is being measured, the component has no resistance.

Alternatively, with the mains voltage at a value which is usual for a given site, various resistors of known value can be connected in place of the link $Pg1$. The corresponding values of V_2 are noted. A graph can be drawn relating R_x and V_2 . When an unknown resistor is connected, V_2 is noted, and the corresponding value of R_x is read from the graph.

A similar graph can be constructed for capacitance.

Constant Output Voltage

The action of the variable transformer has been described in terms of deriving a variable voltage from a constant mains voltage. It may be worthwhile mentioning that it can also be used to give a constant output voltage when the input voltage varies. The equipment was originally devised for this purpose. Soon after it was completed, the local supply company improved the stability of its mains voltage.

AN ELECTRIC NIM MACHINE

—continued from page 529

the line of lamp holes, to support a wooden plywood battens $8\frac{1}{2}$ in. x 1in. on which were screwed the four M.E.S. lampholders. This brings the bulbs flush with the front panel holes. One of each of the lampholder fixing screws was used to anchor a 1in. wide strip of tin plate which also extends to the front panel; this serves to shield the hole from the light of the bulbs adjacent to it. A similar batten of $\frac{1}{2}$ in. thick wood, screwed to two supports $3\frac{1}{2}$ in. x 1in. x $\frac{1}{2}$ in. supports the transformer, rectifier and condenser. The relay is screwed direct to the side of the box, counter-sinking the fixing bolts from the outside.

All wiring is done from the rear with the front panel screwed into position, the relay being mounted with its contacts forward, so that the soldered ends of these contacts are readily

COMPONENTS LIST

Resistors:

R_1 54k Ω R_2 5.4k Ω

Transformer:

T1 Douglas MT3 with primary tapped at 240, 220 and 200V, and secondary tapped at 12, 15, 20, 24 and 30V.

Switches:

S1 Double-pole, on-off
S2, S3 Single-pole, 6-way rotary
S4 Double-pole, 3-way rotary

Meter:

M1 Moving coil with full scale deflection of 5mA, preferably scaled 0-300

Rectifier:

MRI Bridge type, full wave, 5mA

Sundries:

3-pin, 5A socket for outgoing mains.
K1 2-pin, 5A socket
K2 2-pin, 2A socket
P1, P2 Voltage-adjusting panels
Pg1 2-pin, 5A plug with pins connected together

In fact, if any readers are troubled with a fluctuating mains voltage, it may be worth their while to make up a unit of this kind. When they have finished it, they are pretty sure to find that their supply has been improved. If however, the supply company reacts slowly, when the unit has been completed, and if some readers actually need to use the unit, they may like to know that operation is very simple: you switch on, turn the voltmeter switch to the position for the outgoing mains, and adjust S1 and S2 until you have the desired voltage. You then switch on the load.

Incidentally, with a secondary tapped at 12, 15, 20, 24 and 30V, the following increments are available: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V.

These values can be obtained without using the voltage-adjusting panels. If these panels are used, fractions and multiples of these values are available. ■

accessible. The wiring diagrams assume that the keyswitches have a central OFF position and a down ON position, i.e., all the key contacts shown are above the centre line of the keys.

The keys drawn have four change-over contacts, arranged in two side-by-side banks. When off, the lower two of each trio of contacts are connected, and when switched on, the centre contact is lifted to connect with the top one. In the 1s keys, only two change-overs are needed on each switch, so that side-by-side contacts can be wired together, rather than leave one set unused. This serves as a precaution against a dirty contact on one set. On the 8s, 4s and 2s keys, another contact is needed to control the relay, and these connections have been drawn on the upper trio of contacts, again wiring the two side-by-side in parallel.


The unit was completed by cutting a cover of polished sheet (Formica was used by the writer, but paxolin will do equally well) to the same dimensions as the front panel, with lamp holes and slots only for the key handles. ■

T rade N ews

Mains/Battery Receiver

FROM Ekco Radio and Television Ltd. comes a new transistor receiver, designed to operate either from the mains or from its own internal battery. The receiver has been named "Varsity" (model number MBT425) and it sells for 19 guineas.

The eight-transistor circuit covers medium and long waves and incorporates a transformerless output stage. The makers of the "Varsity" are Ekco Radio and Television Ltd., Southend-on-Sea, Essex.

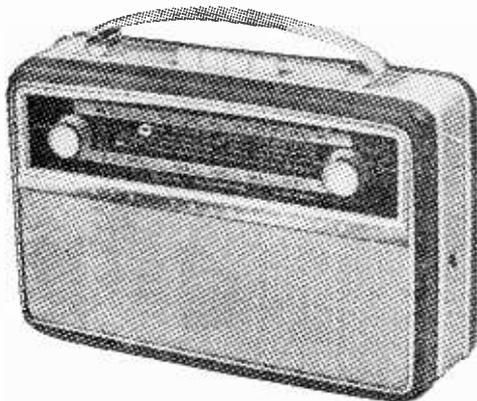


This 8-transistor portable is made by Ekco Radio and Television Ltd.

Dual-function Receiver

THE second transistor receiver made by the Ever Ready Co. (Great Britain) Ltd. to have the dual function of portable and car radio has just been announced. Called the "Sky Tourer", it has been designed to fit into a special container which is permanently installed in the vehicle and which, with the receiver inserted, automatically connects it to the car's power supply, external aerial and separate 6in. x 4in. loudspeaker.

When removed from the container the "Sky Tourer" operates as a normal transistor portable, using its own internal battery, aerial and speaker.

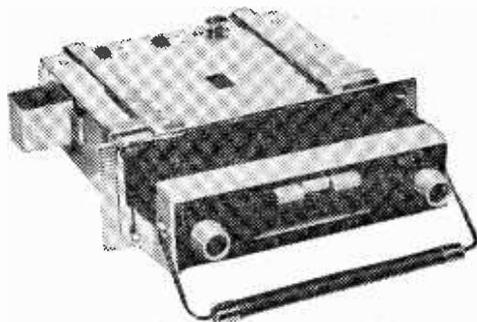The set tunes over the long and medium wave bands and the six-transistor circuit provides 540mW output when used as a portable and 1W when used in the car. The price of this new receiver complete is £22 1s. and it is manufactured by the Ever Ready Co. (Great Britain) Ltd., Hercules Place, Holloway, London, N7.



The "Sky Tourer" is a new dual-purpose receiver from Ever Ready.

Portable Radiogram

ONE of the most interesting pieces of radio merchandise to be handled recently by Denham and Morley Ltd. (U.K. distributors of imported electrical equipment) is a portable record player/transistor receiver called the "Swing-Along".

The receiver section covers both medium and long waves and the record player will take 45r.p.m. records. The circuit employs six transistors and provides a maximum output of 750mW.

The "Swing-Along" weighs only 6lb and is finished in cream and red. The agents for this German-made "radiogram" are Denham and Morley Ltd., Denmore House, 173-175 Cleveland Street, London, W1.



Denham and Morley Ltd. are the U.K. distributors for this German-made record player/receiver.

**LASKY'S
RADIO**

**THE FINEST RANGE OF
TRANSISTOR RECEIVERS**

we consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.



LASKY'S FIRST AGAIN!
Now offer to the Home Constructor - full short wave coverage
The SKYROVER
and the **SKYROVER DE LUXE**

The SKYROVER

Controls: Waveband Selector, Volume Control with on/off Switch, Tuning Control. In plastic cabinet, size 10 x 6 1/2 x 3 1/2 in. with metal trim and carrying handle.

Can be built for
£10.19.6

Post & Pkg. 5/- extra.

Data for each receiver: 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries, 2/8 extra. Four Leak-Proof batteries, 3/4 extra. All Components Available Separately.

GENERAL SPECIFICATION:

7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 torch batteries. The SKYROVER and SKYROVER DE LUXE covers the full Medium Waveband and Short Waveband 31-94 Mc. and also 4 separate switched band-spread ranges. 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions.
SPECIFICATION:
Superhet, 470 Kc/s. All Mullard Transistors and Diode.
Uses 4-U2 batteries. 5in. Ceramic Magnet P.M. Speaker.
Easy to read Dial Scale. Band Spread Tuning.
500 MW Output. Telescopic Aerial & Ferrite Rod Aerial.
WAVEBAND COVERAGE: 180-576Mc; 31-94M and Band Spread on 13, 16, 19 and 25 metre Bands.

The SKYROVER de luxe

Tone Control Circuit is incorporated, with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet, size 11 1/2 x 6 1/2 x 3 1/2 in. covered with a washable material, with plastic trim and carrying handle. Also car aerial socket fitted.

Can be **£12.19.6** P. & P. built for 5/- extra

"SPRITE"

Can be built for
79/6
P. & P. 3/6 extra.



★ Six-Transistor Superhet Miniature Personal Pocket Radio. ★ Long and Medium wavebands. ★ Ferrite Rod aerial. ★ I.F. Frequency 470 Kc/s. ★ 3in. Speaker. ★ Printed circuit 2 1/2 x 2 1/2 in. ★ Slow Motion Drive. ★ In Plastic Case. Size 4 x 2 1/2 x 1 1/2 in. In order to ensure perfect results, the SPRITE is supplied to you with R.F. and I.F. stages. Driver and Output stages ready built with all components mounted on the printed circuit. The SPRITE pre-assembled, plus cabinet, speaker and all components for final construction. at the inclusive price of **79/6** P. & P. 3/6 extra. Data and instructions separately 2/6. Refunded if parcel is purchased. Real calf leather case wrist strap, personal earphone and case for earphone and battery 12/6 the lot extra. Make no mistake this is a SUPERHET receiver of genuine commercial quality. It is not a regenerative circuit.

"COROVER"

'SIX'


★ A 6-transistor plus 2-diode superhet. ★ I.F. 470 Kc/s. ★ Covers the full, medium and long wavebands. ★ Sockets for personal earpiece or tape recorder and car radio aerial. Uses MULLARD Transistors, Diode and large internal ferrite rod aerial. ★ Uses four 1.5 v. pen torch batteries. ★ All components on a single printed circuit. Simple stage by stage instructions. ★ Cabinet size 6 1/2 x 4 x 1 1/2 in. With carrying handle. ★ All coils and I.F.'s ready wound.



ALL COMPONENTS AVAILABLE SEPARATELY. Data and instructions separately 2/6. Refunded if you purchase the parcel.
£5.7.6 P. & P. 4/- extra. Batteries 1/4.

"REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high impedance speaker. ★ All components mounted on a single printed circuit board, size 6 1/2 x 5 1/2 in. in one complete assembly. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. in Red/Grey, Blue/Grey or all Grey. ★ Easy to read Dial. ★ External socket for car aerial. ★ I.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery. ★ Full comprehensive data supplied with each receiver. ★ All coils and I.F.'s etc. fully wound ready for immediate assembly.

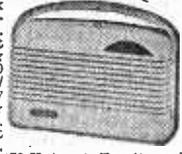

An Outstanding Receiver. LASKY'S PRICE for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction **£5.19.6** P. & P. 4/6.

PP9 Batt. 3/6. Data and instructions separately 2/6. Refunded if you purchase the parcel.

PRIVILEGE PARCELS

A "Privilege Parcel" allows you to purchase the Audio System of your choice at a worth while cash saving. Some examples are listed below, but we shall be pleased to quote our "Privilege Parcel" Prices for any selection of equipment of your own choice. Send us details of your requirements.

Collaro Studio Tape Deck, i-track model **£10.10.0**
Lasky's Tape Amplifier **£8.19.6**
7 x 4in. spkr. **£3.15.0**
15.6

REALISTIC Seven DE LUXE

By popular request a De Luxe version of the well-proven Realistic "Seven" now available. With the same electrical specification as standard model—PLUS A SUPERIOR WOOD CABINET IN CONTEMPORARY STYLING, covered in attractive washable material, with super-chrome trim and carrying handle. Also a full vision circular dial, externally mounted to further enhance the pleasant styling. ALL FOR ONLY **£1** EXTRA. P. & P. as for Std. model.

Tudor Stereo Amp-lifier £15. 0.0	Tudor Stereo Amp-lifier £15. 0.0
Connoisseur Craftsman, 2-speed transcription player. £18. 6.6	Braun PC4L Stereo Transcription Unit £12. 9.6
Decca FFSS Stereo Pick-up £18.18.0	2 x Sharon Loud-spkr systems £19.19.0
Total £50. 4.6	Total £47. 8.6

Collaro Studio Tape Deck, i-track model £10.10.0	Collaro Studio Tape Deck, i-track model £13.19.6
Lasky's Tape Amplifier £8.19.6	Martin Tape Amplifier, i-track model £12.12.0
7 x 4in. spkr. £3.15.0	Portable Case with Speaker £5. 5.0
Total £24. 0.0	Total £31.16.6

"Privilege Parcel" Price: **£47.16.9.**

"Privilege Parcel" Price: **£22.10.0**

"Privilege Parcel" Price: **£20.0.0.**


Carriage and Packing on all the above parcels, 10/6 extra.

207 EDGWARE ROAD, LONDON, W.2. | 33 TOTTENHAM COURT ROAD, W.1. | 152/3 FLEET STREET, LONDON, E.C.4.
Near Praed St. PADDINGTON 3271/2 Nearest Stn., Goodge St. MUSEUM 2605 Telephone: Fleet Street 2833.
BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W., Edgware Rd. Open all day Thursday. Early closing Sat.

WEYRAD

6-TRANSISTOR 2-WAVE SUPERHET RECEIVER MODIFICATIONS NOW AVAILABLE FOR 500 mW OUTPUT


- ROD AERIAL—RA2W**
6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208pF tuning capacity. Complete with Car Aerial Coil 12/6
- OSCILLATOR COIL—P50/1AC**
M.W. covered with 176pF tuning capacity, L.W. by extra padder 5/4
- I.F. TRANSFORMERS**
1st and 2nd Stage—P50/2CC 5/7
(2 required)
- 3rd Stage—P50/3CC 6/-
- DRIVER TRANSFORMER—LFDT4** 9/6
- OUTPUT TRANSFORMER—OPT1** 10/6
- PRINTED CIRCUIT—PCA1** 9/6

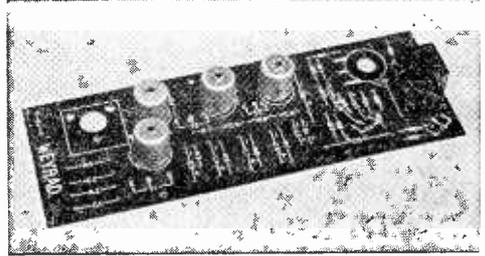

In response to many requests we have redesigned the output stages to give 500mW and to enable a standard 3 ohm Speaker to be used. Full details of the simple changes are given on a separate leaflet available on receipt of stamp.

- CONSTRUCTOR'S BOOKLET WITH FULL DETAILS** 2/-
- TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 3-TRANSISTOR, 500 mW OUTPUT, FULLY ASSEMBLED WITH VOLUME CONTROL** 63/6

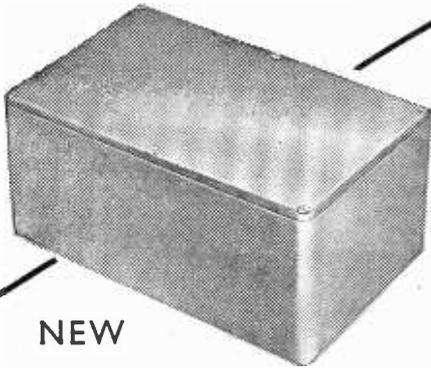WEYMOUTH RADIO MANUFACTURING CO., LTD.
REGENT FACTORY, SCHOOL STREET,
WEYMOUTH, DORSET



NEW
EDDYSTONE
DIECAST
INSTRUMENT BOX

An addition to the three existing Diecast Boxes is the Cat. No. 903, illustrated above. This has dimensions of approximately 7 1/2 in. x 4 1/2 in. x 3 in. deep—the increased depth is a notable feature. The box is cast in aluminium, thus saving considerable weight and, as with the others, is complete with a close-fitting flanged lid. Natural finish. Data sheet on request.

- No. 896. 4 1/2 in. x 2 1/2 in. x 1 in.
- No. 850. 4 7/8 in. x 3 1/2 in. x 2 in.
- No. 945. 7 1/2 in. x 4 1/2 in. x 2 in.

Write the Manufacturers:

STRATTON & CO. LTD.
BIRMINGHAM 31



EXPRESS ELECTRONICS
32 SOUTH END CROYDON SURREY
TEL. GRO 9186

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	4/9	6BE6	7/-	12A07	6/9	DH77	5/-	EF99	9/-	PL82	7/-
1C2	7/6	6B16	5/9	12AX7	6/9	DH142	8/6	EF91	4/-	PY33	10/-
1C3	6/6	6B16	5/9	12BE6	8/6	DH150	10/-	EF92	5/6	PY81	6/9
1F1	6/6	6BR7	8/9	12BH7	10/6	DK91	4/9	EL41	9/6	PY82	7/6
1F3	2/9	6BW6	6/6	12CKGTT11	-	DK96	6/6	EL84	7/-	PY83	7/6
1FD1	6/6	6BW7	7/-	12Q7G	7/6	DL92	5/6	EM85	10/-	R19	8/6
1FD9	4/-	6D2	4/-	12SN7	6/-	DL94	8/-	EY51	7/6	86A1	9/6
1P1	6/6	6F12	4/-	18A3	9/-	DL96	6/6	EY81	10/-	U32	7/6
1P10	5/6	6H6GT	2/-	19A45	9/6	EB91	4/-	EZ40	5/6	U76	7/6
1P11	6/-	6J7GT	7/6	25A6G	7/6	EB41	7/6	EZ80	6/-	U78	5/-
1R5	4/8	6K7G	6/6	25L6GT	7/6	EBF80	8/6	EZ81	8/9	U142	8/6
1R5	4/-	6K9G	6/-	30C1	7/6	ECC81	4/-	HVR2	9/6	U3C41	8/6
1T4	2/9	6Q7G	5/6	30L1	7/6	ECC82	6/9	KT33C	6/-	UCH42	9/6
1U5	5/6	6SL7GT	6/-	35L6GT	7/6	ECC83	6/9	N17	5/6	UF41	8/6
3A4	5/6	68N7GT	7/6	35W4	8/6	ECC84	6/6	N18	5/6	U141	8/6
3B4	5/6	6V6G	7/6	35Z4GT	8/-	ECC85	7/6	N19	6/-	U441	7/6
6V4	6/-	6X1	5/-	37G3	7/6	ECC80	6/6	N709	7/-	W17	3/-
5Y3GT	5/-	6X5Q	5/9	80	6/-	ECC82	7/6	PCC84	7/6	W76	4/6
6Z4G	7/6	787	9/6	DAF91	4/-	ECH42	9/-	PCF90	7/6	W142	8/6
6AK6	5/6	8D3	4/-	DAF96	6/6	ECH81	10/-	PCF82	6/6	X17	4/9
6AL5	4/-	9D7	9/6	DC090	12/6	ECL80	8/6	PCL82	6/9	X142	8/-
6AM6	4/-	12AD6	11/6	DF91	8/-	ECL82	7/6	PCL84	9/-	X150	9/-
6AT6	5/-	12AH3	10/-	DF96	6/6	EF41	9/-	PL81	9/6	Z77	4/-
6BA6	5/-	12AT7	4/-	DH76	7/6	EF80	8/-	PL82	7/-	ZD17	4/-

ASK FOR RESISTOR AND CAPACITOR COLOUR CODE FREE WITH EVERY PURCHASE

High Stability Resistors 1/2W 5% 50Ω to 1M, 9d. Midget Ceramics 500 v., 9d. Coax. Super Quality 1/2in. 9d. yd. Plus 9d. Sockets 9d. Silicon H.T. Rects. 250 v. 300 mA 1/2in. x 1/2in. 8/6. Contact Cooled 250 v. 50 mA 8/6. 85 mA 8/6. NEW TRANSISTORS BY MULLARD. OC19, OC29, OC56, 25/-; OC44, OC45, 8/-; OC70, 6/-; OC71 5/-; OC72, 6/-; OC72 Matched pair, 12/-; OC74, OC75, OC78, 7/6; OC81, 8/-; OC81 Matched pair, 12/-; OC170, OC171, 7/6.

VALVES MATCHED IN PAIRS

EL34 27/6, EL84 15/-, N709 15/-, 6V6G 15/-, 6BW6 14/- per pair. Push Pull O.P. Transformer for above 3 1/2 14/6, P. & P. 1/6. 12in. P.M. Speakers 3/ 24/6. Baker's "Seibsturz" 12in. 15Ω 15W Stalwart 80/-, 12in. Stereo Model 88.15.0.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94.....	16/6	ECH42, EF41, EBC41,
DK96, DF96, DAF96, DL96.....	28/-	EL41, EZ40.....
1C3, 1F1, 1FD1, 1P1.....	28/-	UCH42, EF41, EBC41,
1R5, 1T4, 1R5, 3B4 or 3V4.....	16/6	UL41, UY41.....

Postage and packing 6d. Over 21 post free. C.O.D. 4/.

TEST GEAR techniques

PART 8 THE OSCILLOSCOPE CONTINUED

H. W. Hellyer

THE facility of "Trace Expansion" was mentioned in the preceding article (Part 7) of this series. While we pay a lot of attention, quite properly, to the sensitivity and bandwidth of the Y amplifier, and consider the provision of the X amplifier as a simple means of trace expansion, it is as well to remember that for several useful applications the X amplifier comes into play.

Typical of this test technique is the display of Lissajous figures, and wobblator waveforms.

When two sinusoidal a.c. waveforms are applied to the X and Y inputs of the oscilloscope simultaneously, the pattern displayed will depend

Typical Lissajous figures, with the Y frequency twice the X frequency (a), half the X frequency (b) and a ratio of 3:2 (c) are shown in Fig. 11.

If the mains frequency is used as a "yard-rule" to the X input, via a suitable attenuator for matching the two signals to be compared, and the frequency under test, say, the 300c/s output from an audio oscillator, a trace of six whole loops should be displayed when the two frequencies are in step, ratio 6:1, as shown in Fig. 11(d). As can be seen from the display, when the number of loops touching an imaginary horizontal line is divided by the number of loops touching an imaginary vertical line, we have the ratio of Y:X.

Involved Waveforms

Interpretation of these figures is simple when the waveforms are exactly sinusoidal and the ratio a whole number, as in the cases stated above. Considerable experience is required to determine how many loops are displayed, let alone touching the imaginary axes, when the waveforms are distorted, the phase angle varying, and the ratio an odd figure. Take for example the drawings of actual oscillograms in Fig. 12. Drawings are used here as the difficulty of photographing the more erratic of these figures makes the outline indistinct, and for the purpose of our argument clarity is essential.

As we shall see in a moment (Phase Measurement), when the waveform X is equal to Y in frequency and the phase angle is 90°, and voltages equal, a circle is displayed. If the phase angle changes, the circle becomes an ellipse, inclined according to the phase angle.

Fig. 12 (b) and (c) shows the ellipse with sinusoidal inputs and again with a distorted waveform, such as given by the clipping of the X waveform shown in (d). Note that the first ellipse can be considered as one loop touching the horizontal and one the vertical line and thus $f_y = f_x$. But the severely distorted display also resolves to $f_y = f_x$, if a close look is given to the actual loop formation.

Going a little further, consider Fig 12(e) where the Y waveform is three times that of the X waveform (frequency). The phase angle has distorted the trace, but there are still three contact points on the horizontal line and one on the vertical, as indicated.

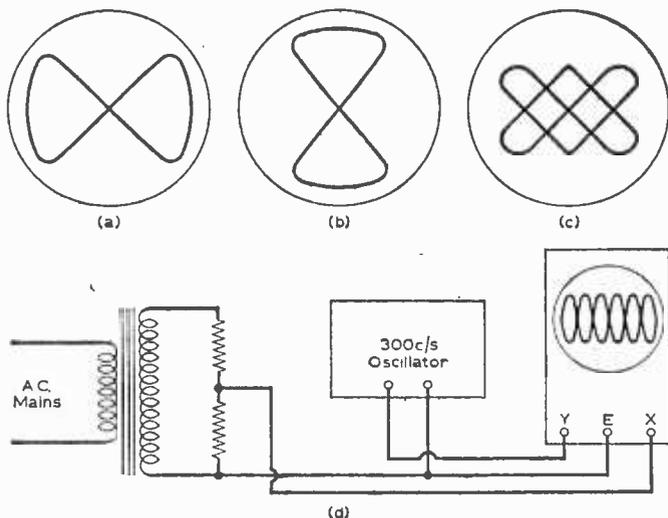


Fig. 11: Typical Lissajous figures: (a) $f_y = 2f_x$; (b) $f_y = \frac{1}{2}f_x$; (c) $f_y = \frac{3}{2}f_x$; (d) $f_y = 6f_x$; using 50c/s mains.

on a number of factors. Principal among these are: relative amplitudes, frequencies and phase of the two waveforms. If the input to the X timebase is a known frequency, and that to the Y amplifier a variable frequency, then the display will form a number of loops, according to the ratio between them. For normal work, ratios of about 10:1 are the maximum practical, and there must be a definite, stable relationship for a still trace.

If the waveforms are not exact multiples of each other the patterns of loops will rotate on the screen. This may be very pretty but does not help us much, although it is possible to note the speed of rotation of the individual loops and calculate the frequency difference.

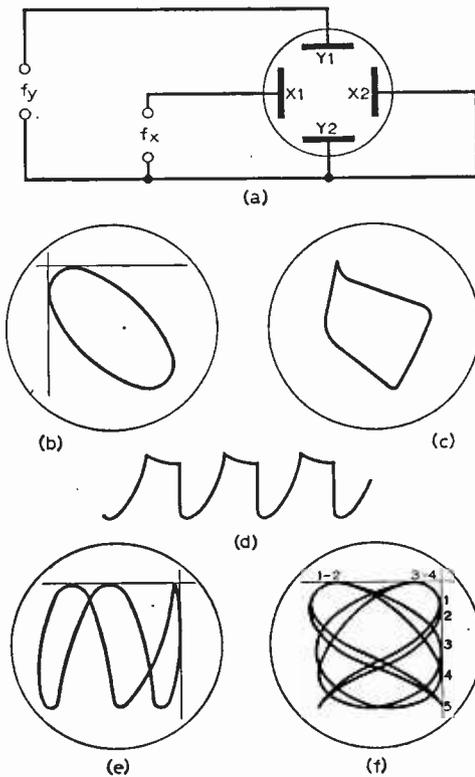


Fig. 12: Frequency comparison: (a) shows the basic connections; (b) ellipse formed when $f_y = f_x$ — phase angle 90° ; (c) distorted trace of (b) when input is non-sinusoidal; (d) X-waveform producing (c); (e) $f_y = 3f_x$, waveform distorted; and (f) $f_y : f_x = 4 : 5$; note superimposed loops.

Even more complicated is Fig. 12(f), which indicates a ratio of $f_y : f_x = 4 : 5$, and where the superimposition of the loops can only be sorted out by careful tracing.

The point of the X amplifier can now be seen. If it is required to interpret a complicated display, and, moreover, one that may be moving all the while, it is desirable that the trace be expanded or contracted to readable limits.

The Circular Timebase

It is evident, from some of the traces of Fig. 12, that a large ratio of the two frequencies being compared would make interpretation extremely difficult. A method of comparing frequencies with a wide difference is to apply a circular timebase. This consists of a phase-splitting network, as in Fig. 13(a), producing a phase difference of 90° between points A and B.

To obtain this, R must equal the reactance of C, and so the frequency of the X signal must be

known. If the mains frequency is used, and C, for example is $0.1\mu F$, then $XC = \frac{10^6}{2\pi fC} \Omega$ which is $\frac{10^7}{314} = 32,000\Omega$, which must be the exact value of R.

The test frequency is applied between the deflector plate system and the final anode, thereby effectively varying the deflection sensitivity, so the circular timebase is modified into a succession of ripples. Each inward and outward excursion of the spot represents one multiple of f_x , so that the trace shown in Fig. 13(b), having six such ripples, denotes an f_z of $6 \times 50 = 300c/s$. If a double trace is obtained the frequency ratio is $n/2$, where n is the number of loops. Thus, Fig. 13(c) has nine loops and a double trace and the ratio is therefore $9/2$, or 225c/s, where a 50c/s f_x is used. Where a triple trace is obtained, the ratio, is $n/3$, and so on.

Other methods of applying networks to produce an elliptical trace for easier counting of the loops, and of modulating the tube differently to produce a dotted trace, are employed for frequency comparison.

Phase Measurement

Of more practical use to the amateur and serviceman is the hook-up used to measure phase shift. This can be applied to an audio or r.f. amplifier, an LC filter or similar network, and proves handy in checking phase shift of an amplifier, particularly of negative feedback loops. Obviously, some care is needed, both in the methods of connection and in the observance of frequency limits, as the oscilloscope amplifiers themselves can introduce some phase shift.


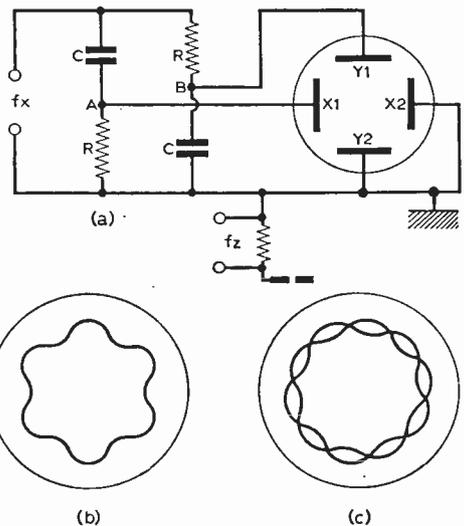
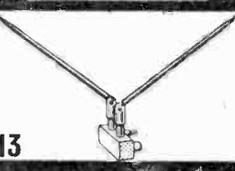
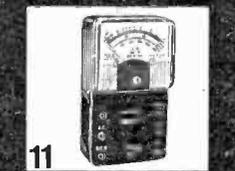
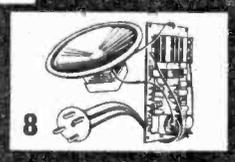
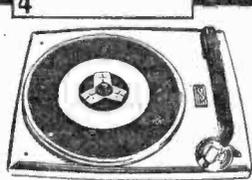


Fig. 13: Phase-splitting network for circular timebase; (b) $f_z = 6f_x$; (c) $f_z = 9/2f_x$ — double trace.

Just a few of our BARGAINS

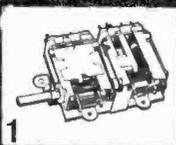

**RADIO & T.V.
COMPONENTS
[ACTON]
LIMITED**

- 1. A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION.** Size 2 1/2 x 2 1/2 in. approx. By famous manufacturer. A.M. -I.F. 470Kc/s. F.M.-I.F. 10.7Mc/s. A.M. coverage from 1.620 Kc/s-525Kc/s. F.M. coverage 108Mc/s-88Mc/s. Circuit diagram 2/6, FREE with Tuner. 25/-, plus 1/- P. & P.
- 2. TRANSISTORISED POCKET RADIO** with printed circuit, mini-circuit, high gain ferrox slab aerial. No aerial or earth required. To build yourself for completely personal listening. 4 1/2 x 3 1/2 x 1 1/2 in. Luxembourg in favourable areas Only 21/-. P. & P. 2/6. All parts available separately.
- 3. A.C./D.C. POCKET MULTI-METER KIT.** 2 1/2 in. moving coil meter scale, calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50 0-100, 0-250, 0-500. Milliamperes 0-10, 0-1000 Ohms ranges 0-10,000, 0-100,000, 19/8. P. & P. 2/-. Wiring diagram 1/- free with parts.
- 4. SIGNAL GENERATORS:** Cash £7.5.0, or 30/- deposit and 6 monthly payments of 21/8. P. & P. 6/6. Coverage 100 kc/s to 100 Mc/s on fundamental and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6 1/2 x 5 1/2 in. Three miniature valves and Metal Rectifier. A.C. mains 200/250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.
- 5. SIGNAL GENERATORS,** Cash £5.5.0. P. & P. 6/6. Coverage 120 kc/s to 84 Mc/s. Case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 1 1/2 in. 2 valves and rectifier. A.C. mains 230-250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy ± 2 per cent.
- 6. STAAR 45, 9 v. BATTERY RECORD PLAYER** complete with pick-up and deck. A completely portable player. Head protected by plastic dome with a brush which cleans the stylus as it rises into playing position. 45 r.p.m. Auto on-off switch governed motor, attractive two-tone grey finish, £2.9.6. P. & P. 2/-.
- 7. CARRYING CASE for STAAR 45 or COMPLETE KIT** beautifully styled in two tone with record compartment. Specially designed to take player and amplifier. Just screw in and connect up. All parts available separately. Case only 22/8. P. & P. 6/-. Complete kit, £5.10.0. P. & P. 5/-.
- 8. TRANSISTORISED AMPLIFIER,** suitable STAAR 45. Output 1 watt. Size 4 1/2 x 2 1/2 in. Printed circuit, tone/volume controls plus 4 transistors. Push-pull output complete with 3 in. moving coil speaker. Built and tested, 49/8. P. & P. 2/-.
- 9. CHANNEL TUNER I.F.** 16-19 Mc/s. Continuously tunable from 174-218 Mc/s. Valves required—PCF89 and PC234 (in series). Covers BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker 10/-. P. & P. 3/-.
- 10. B.S.R. MONARCH UA14 WITH FUL-FI HEAD.** 4-speed, plays 10 records, 12 in., 10 in. or 7 in. at 16, 33, 45 or 78 r.p.m. Internals 7 in., 10 in. and 12 in. records of the same speed. Has manual play position; colour brown. Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 in., below baseboard 2 1/2 in. Fitted with Ful-Fi turnover crystal head, £5.19.8. P. & P. 6/6.
- 11. POCKET MULTI-METER.** Size 3 1/2 x 2 1/2 x 1 1/2 in. Meter size 2 1/2 x 1 1/2 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100K Ω Complete with test prods, battery and full instructions, 38/-. Plus 1/4 P. & P.
- 12. 8-watt PUSH-PULL 4 VALVE AMPLIFIER plus METAL RECTIFIER.** A.C. mains 200-250 v. Case 10 1/2 x 6 1/2 x 2 1/2 in. 5 valves. For use with all makes and types of pick-up and tone. Negative feedback. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. 2 dB down to 20 kc/s. Output 8 watts at 5 per cent total distortion. Noise level 40 dB down at 100 Hz. Output transformer tapped for 3 and 15 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, £3.19.6. P. & P. 6/-. Crystals mike to suit 15/-. P. & P. 2/-. Sin. P.M. Speaker to suit, 12/8. P. & P. 2/-.
- 13. 'INDOOR AERIAL' or TV/BBC/FM.** Complete with standard co-axial plug. Heavy chrome extending dipoles—7 ft. fully extended. Flugs straight into T.V. or VHF Tuner. Fully directional, 10/6. P. & P. 1/6.
- 14. NO MORE FLAT BATTERIES.** Charge your own battery overnight with this wonderful little charger. Output 6 and 12 volts, 2 amps. Input 200-250 v. A.C. mains. Mains fuse incorporated. Attractive silver hammer finished case, 6 x 3 x 3 in. Complete with leads and battery clips only 21/-. P. & P. 3/6.

**21b HIGH STREET
ACTON, LONDON, W.3.**

ALL ENQUIRIES S.A.E.
GOODS NOT DISPATCHED OUTSIDE U.K.


New Reduced Price!!
"MERCURY-6" CABINET



We can now offer this fine Timber Cabinet (Grey Leatherette) with gilt grill and fittings for the **LOW PRICE OF 35/-** P.P. 2/6.
 Previously 48/-. (14 x 7 x 4in.).
 Takes 7 x 4in. Speaker.

"NOMAD"

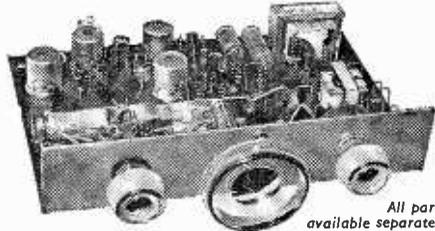SEVEN TRANSISTOR TWO WAVEBAND BRAND NEW DESIGN FOR CAR RADIO AND GENERAL PURPOSE GIVING ONE WATT OUTPUT WHEN CONNECTED TO ANY STANDARD 3 ohm SPEAKER




All parts available separately
 Size: 7 x 5 x 1 1/2 in. Building Plans 2/6 (Free with kit).
 This versatile unit has been designed to fit into a variety of cases and all components, down to control knobs and battery clips, are supplied together with clear illustrated plans. It gives a superb performance with dozens of stations including Luxembourg when connected to a 9 volt battery and speaker.

ONLY **£6.19.6** COMPLETE P.P. 2/-.

ALIGNMENT SERVICE

FOR PW-6. | MERCURY-6. | NOMAD
 FOR WHICH WE STOCK ALL COMPONENTS AND BUILDING PLANS. Send S.A.E. For Lists.

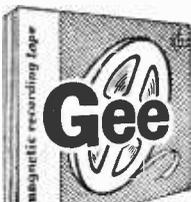NORCOL LTD. 147 LONDON ROAD, YORKTOWN, ELECTRONIC COMPONENTS CAMBERLEY, SURREY Phone: CAMBERLEY 3743



LOWEST EVER PRICES

5in. Std.	600ft.	...	8/6
7in. Std.	1,200ft.	...	12/6
5in. L.P.	900ft.	...	10/-
5 1/2 in. L.P.	1,200ft.	...	12/6
7in. L.P.	1,800ft.	...	15/-
4in. D.P.	600ft.	...	9/-
5in. D.P.	1,200ft.	...	15/-
5 1/2 in. D.P.	1,800ft.	...	22/6
7in. D.P.	2,400ft.	...	25/-

SPECIAL!! "LAFAYETTE"
 7in. Std. 1,200ft., 12/6
 7in. L.P. 1,800ft., 15/-
 7in. D.P. 2,400ft., 25/-

EXCLUSIVE TO GEE'S! AMERICAN "SHAMROCK"
 Professional quality.
 7in. L.P. 1,800ft., 15/6

SPARE SPOOLS. 4in., 5in., 5 1/2 in., 2/- each; 7in. 2/6; 8 1/2 in. 5/-.

AMERICAN "CBS" TAPE

5in. Std.	600ft. (CIP-6)	...	13/-
5 1/2 in. Std.	900ft. (CIP-9)	...	16/-
7in. Std.	1,200ft. (CIP-12)	...	21/-
5in. L.P.	900ft. (LP-9)	...	16/-
5 1/2 in. L.P.	1,200ft. (LP-12)	...	19/6
7in. L.P.	1,800ft. (LP-18)	...	28/6
5in. D.P.	1,200ft. (CMXP-12)	...	32/-
5 1/2 in. D.P.	1,800ft. (CMXP-18)	...	37/-
7in. D.P.	2,400ft. (CMXP-24)	...	47/-

P. & P. 2/- per order (over £3 post free). Other types available. S.A.E. for Bumper Tape and Accessories list.

Obtainable only from:— *Special discounts for quantities.*
GEE BROS. (RADIO) LTD., Dept. P.W.10
 15 LITTLE NEWPORT ST., LONDON W.C.2
 (Adjoining Leicester Sq. Tube) GER 6794/1453

ERSIN MULTICORE SOLDERS

for a first class joint every time

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

THE NEW HANDY DISPENSER

Easy to find in the tool box—simple to use. The solder is in a continuous coil which can be used direct from the handy free-standing dispenser—in fact, it is virtually a third hand for those tricky soldering jobs. Containing 15 feet 5-core 18 s.w.g. Ersin Multicore Savbit alloy. 2/6



HOME CONSTRUCTORS 2/6 PACK

The Home Constructors Pack contains 32 ft. of 22 s.w.g. 60/40 alloys, which is especially suitable for printed circuitsoldering.



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruding hex. 3/6 each



MULTICORE SOLDERS LTD

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)

CMMS.11*

In the set-up shown in Fig. 14(a), the signal applied to the amplifier input is also fed to the Y input of the scope, while the signal from the output of the amplifier goes to the X input, with a correct load resistor R to maintain matching, and a variable resistor X Def. for

The procedure is to apply sufficient signal to drive the amplifier fully, but not to overload it, adjusting the Y amplifier gain of the scope to give about two-thirds deflection. If the Y input is now disconnected and the deflection potentiometer adjusted (timebase switched off), a similar horizontal deflection can be obtained. (If the oscilloscope has the internal X amplifier we discussed formerly, so much the better; the potentiometer can be dispensed with).

When the Y input is reconnected, an ellipse will be displayed, its size, shape and angle depending on the phase shift between input and output of the amplifier. A sample of the ellipses that are displayed for various principal angles are shown in Fig. 14(b). Note that in each case the shift controls are adjusted so that the ellipse sits centrally about the crossover line on the graticule.

Now, if a measurement is taken from the point where the upper limit of deflection is projected across to the vertical axis, to the horizontal axis, calling this B; then another measurement from the point where the ellipse cuts the vertical axis, calling it A, we can calculate the phase angle from the formula $\sin \theta = A/B$.

It will be noted that only when the phase angle is zero (or 360°, which is the same thing in this case), or 180°, is there a straight, diagonal line. And when the phase angle is 90° the trace displayed is a circle.

In practice, this also depends on matching the amplitudes of the signals, and will often require that the sensitivities of the oscilloscope amplifiers have to be known. Again, this is where the X amplifier becomes useful. Note also that a variation in the supply voltage can make a difference, and a flattening of the trace in opposite quadrants, as opposed to the formation of an ellipse, indicates the presence of harmonics in the base supply.

Use of a Graticule

Where an oscilloscope does not have a transparent graticule, it is essential that some form of visual indication of trace length is available. A graticule is easily made from a piece of transparent plastic, and one simple method of noting measurements is to mark the plastic where required with a soft chinagraph pencil, whose mark can easily be erased.

The foregoing is sufficient also to demonstrate the way a response curve is traced out. For further notes on alignment, the reader is referred to the companion articles to this series, entitled

“TV Alignment,” which appeared in the May and June issues of *Practical Television*, and to Part 5 of this series.

The latter article, dealing with f.m. signal generators, with illustrations of some typical response curves, appeared in the July issue of PRACTICAL WIRELESS. Alignment of an a.m. receiver can be carried out in much the same way as described previously, with the difference that input settings and oscilloscope connections will be different. The Y input of the scope is connected to the detector load, via a screened lead. A convenient point for connection is often the top of the volume control.

Wobbulator Deviation Frequency

The deviation of the wobbulator must be slightly more than the passband characteristics of the tuned circuits of the receiver. Too small a deviation will restrict the response curve, too great a deviation will make the displayed curve too narrow for effective observation.

The deviation frequency is derived from the X sawtooth waveform, the wobbulator connected to the aerial and earth sockets of the set (or to the

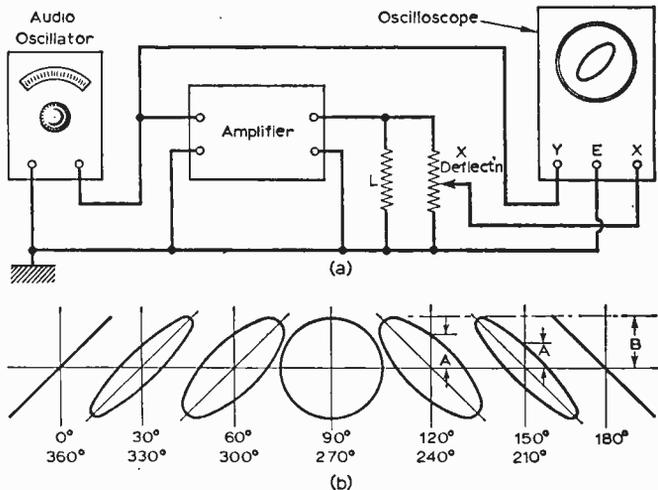


Fig. 14: Phase shift measurement: (a) typical hook-up; (b) phase-difference oscillograms.

output from the frequency changer if only the i.f. amplifiers are to be checked). The wobbulator is set to the central frequency either the nominal i.f. or the selected radio frequency, and the deviation about 20c/s, adjusted at the wobbulator. The X timebase is set for an adequate display, and the marker signal, if available, applied from a fixed r.f. oscillator—which can be a signal generator with the modulation switched off.

As previously described, many wobbulators have an inbuilt marker generator, often crystal-controlled. But even if this is absent, and the

—continued on page 550

CLUB

AMATEUR RADIO MOBILE SOCIETY

Hon. Sec.: G3FPK, 79 Murchison Road, London, E.10.

The extensive programme of events which made up the Torbay A.R.S. mobile rally, held on August 11th, was arranged by A.R.M.S. member G3NBR.

The June/July issue of "Mobile News",—the A.R.M.S. journal—sets a new "high" in standards of amateur radio society publications by employing, for the first time, three colour printing for its front and rear covers.

COVENTRY AMATEUR RADIO SOCIETY

Hon. Sec.: A. J. Wilkes, G3PQQ, 141 Overlade Crescent, Coundon, Coventry, Warwickshire.

Of late, members of this Society have been anticipating a move to new headquarters, affording better accommodation and facilities, car parking space, etc.

August 12th was mobile night on the air, and on 26th August, G5PP gave a talk entitled "Mobile Operation".

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

The programme for August began with a surplus sale held on the 7th. This was followed on the 14th by a meeting devoted to preparations for the Society's mobile rally which was held four days later at Rykneld School.

The last event to be held in August was a direction finding practice run on the 28th.

Another sale was held on September 4th, the first meeting of the month.

FLINTSHIRE RADIO SOCIETY

Hon. Sec.: A. Antley, Fairholme, Fairfield Avenue, Rhyl, Flintshire.

At the meeting on August 26th, L. W. Barnes (GW3PCZT) gave a lecture on "Single Sideband", which followed the usual slow morse practice and talk on "Simple Hints and Kinks".

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

Members of this Society manned another two demonstration stations during August; one on the 10th at the Halifax Agricultural Show and the other on the 17th at the Forest Cottage Community Centre Gala. August 14th was ragchew night and on the 28th, a number of members brought along their photographic slides to provide the evening's entertainment.

RADIO CLUB OF SCOTLAND

Hon. Sec.: A. Barnes, GM3LTB, 7 Southpark Terrace, Glasgow, W.2.

The constitution and financial affairs of this relatively young society are still rather involved, owing to the decision to operate the Glasgow section as a separate group within the RCS, and not as the "mother" body as had been the situation previously.

The Club's journal—"GM Magazine"—has undergone a change in cover design with the latest issue.

READING AMATEUR RADIO CLUB

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven", 9 Holybrook Road, Reading, Berkshire.

This Club reports increasing attendance figures for meetings. On August 25th another mobile picnic meeting was held at the Childs Beale Trust when members and their families enjoyed an informal afternoon outing.

At the last meeting for August, Dud Charman (G6CJ) gave a lecture and demonstration of aeriels.

RODING BOYS SOCIETY: RADIO SECTION

Hon. Sec.: R. T. Marchant, 154 Essex Road, Leyton, London, E.10.

The Society's annual field day was held successfully during August with the single transmitter operating on 160m.

SCARBOROUGH AMATEUR RADIO SOCIETY

Hon. Sec.: P. B. Briscombe, G8KU, "Roesacre", Irton, Scarborough, Yorkshire.

Local short wave enthusiasts and visitors to Scarborough are invited to the meetings of this club which are held at 8 p.m. every Thursday at Chapman's Yard, Waterhouse Lane, North Street, Scarborough. At the meeting for August 8th, "v.h.f. working" was under discussion.

An R.A.E. paper formed the topic for the meeting on August 15th and a week later "Servicing" was discussed.

STOCKPORT RADIO SOCIETY

Hon. Sec.: E. G. Houldsworth, G6NM, 52 Worsley Crescent, Stockport, Cheshire.

Any potential members are invited to go along to meetings of this Society, which are held on alternate Wednesdays at 8 p.m. All meetings are at the Blossoms Hotel, Buxton Road, Stockport; the next being on September 11th.

STOKE-ON-TRENT AMATEUR RADIO SOCIETY

K. H. Parkes, G3EHM, 28 Grove Road, Heron Cross, Stoke-on-Trent, Staffordshire.

Recent events have included a talk on aeriels and a demonstration of a transistorised electric organ.

Decoration and renovation work is at present in progress at the club premises.

STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: R. A. G. MacIntosh, 50 Field Lane, Oldswinford, Stourbridge, Worcestershire.

As it was not possible for the Society to meet at the usual rendezvous during August, members assembled at a local hotel where a meeting was held.

WESSEX AMATEUR RADIO GROUP

Hon. Sec.: G. K. Fowle, 138 Surrey Road, Branksome, Poole, Dorset.

The only meeting for August was held on the 12th, when members heard a talk given by R. Weston.

G. J. Fowle's lecture of September 2nd was entitled "Building Mains and Battery Operated Communication Receivers".

WEST KENT AMATEUR RADIO SOCIETY

R. Trevitt, 28 Delves Avenue, Tunbridge Wells, Kent.

On August 25th members and their families were able to enjoy a picnic, arranged by the Society and held in the beautiful grounds of Sheffield Park.

R.S.G.B. Contests for September. V.H.F. National Field Day (September 7th to 8th); D.F. National Final (September 15th) and Low Power Field Day (September 22nd).

COURSES OF INSTRUCTION

Below are listed a number of technical institutes which will be running radio and television courses this autumn. All courses begin in September (except where stated) and further details can be obtained from the institute itself or from the address given.

Allan Glens School, Montrose Street, Glasgow: radio theory, morse, G.P.O. regulations, aeriels, etc., and a general radio course. Bradford Technical College: inquiries—Mr. D. M. Pratt, 30 Lyndale Road, Eldwick, Bingley, Yorkshire: R.A.E. and morse courses.

Brentford Evening Institute: inquiries—Evening Institute Department, Education Offices, Town Hall, Chiswick, London, W.4: radio amateurs' course, morse, radio and TV servicing.

Carshalton College for Further Education: inquiries—The Registrar, Carshalton College for Further Education, Nightingale Road, Carshalton, Surrey: if enough interest is shown radio theory and morse classes will be held.

Central Evening Institute, Lea Mason Centre, Bell Barn Road, Birmingham: R.A.E. courses.

Hendon College of Technology, The Burroughs, Hendon, London, N.W.4: short courses on digital computers, transistor circuit design (beginning October), microwaves, global communications (beginning October) and high fidelity sound reproduction (beginning October), also a design course for electronic engineers (beginning October).

Holloway L.C.C. Evening Institutes: inquiries—A. W. H. Wannell, 145 Uxendon Hill, Wembley Park, Middlesex: R.A.E. and morse classes.


North End Evening Institute, Portsmouth: inquiries—The Secretary, Eastney Modern Boys' School, Reginald Road, Southsea, Hampshire: R.A.E. course.

Northwood Evening Institute, Potter Street, Northwood Hills, Middlesex: radio amateur examination, morse and practical courses.

Wembley Evening Institute, Copland School, High Road, Wembley, Middlesex: R.A.E. and morse classes.

Wesley Evening Institute: inquiries—"Jeanville", Brighton Road, Adlestons, Weybridge, Surrey: radio and television course.

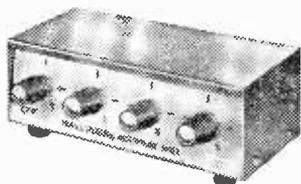MM44-CHANNEL TRANSISTORISED MICROPHONE MIXER



Add musical highlights and additional sound effects to your recordings. The MM-4 permits mixing of four signals such as microphone, records, tuner etc. into a single output. Inputs and output take standard plugs. Fully transistorised and self contained in handsome case.

PRICE ONLY 59/6

HAWAIIAN PORTABLE RECORD PLAYER Model HN707

Uses a unique pick-up unit, turntable and special speaker to give amazing volume and reproduction without the use of valves or transistors. Battery operated, plays up to 12in. records at 33 $\frac{1}{3}$ or 45 r.p.m. Separate fine speed and volume controls. 45 r.p.m. adaptor and stereo-capsule. Durable plastic cabinet, fully waterproof with carrying handle and record storage compartment. Size 9in. dia. x 3 $\frac{1}{2}$ in. deep. Weight 2 lb., 9 ozs.



PRICE £7.70

8" DOUBLE CONE HI-FI SPEAKER Model 8A7

Frequency range 50-16,000 c/s. Lowest resonance 90 + 15 c/s. Sensitivity 98dB. Programme source input 8 watts. Voice coil impedance 16 ohms. Net weight 970 grammes. BRAND NEW AND GUARANTEED.

PRICE 79/6

CT.10 HORN TWEETER

For true high fidelity reproduction of the upper, middle and top frequency ranges in multi-unit speaker installations. Pressure unit type utilizing a spun aluminium diaphragm. Output 10 watts. Frequency response 1500-1800 c.p.s. Impedance 16 ohm. Finished in matt black, flanged and drilled for baffle mounting.



PRICE 29/6

SIGNAL INJECTION PROBE ITI.1.



Push button operation. Ideal for making rapid checks on radios, TV. Amps tuners, etc. PRICE 42/6

PORTABLE RADIO PHONE



Consisting of trans-receiver covering 7.4-9 Mc/s. Range up to 8 miles, depending upon obstructions and elevation. On test the receiver astounded us for we heard 65 short wave stations (one as far away as Russia). Complete with 5 valves, headphones, microphone, junction box and 6ft. telescopic aerial. Operates from standard 120 v. and 2 x dry batteries.

ONLY 65/- EACH
TWO FOR £8
(Batteries 20/- per set extra.)

SA.80 INTEGRATED STEREO AMPLIFIER



(11ms.). 4 x 4 watt. The perfect choice for a low cost Hi-Fi stereo system. Dual pick-up and tuner inputs. Tone control. Independent volume controls. 15 ohm speaker output. Supplied complete for only

£9.10.0

A MINIATURE TAPE RECORDER IN KIT FORM ONLY

£4.19.6



Exclusively offered complete with all accessories. No extras to buy. Consisting of three transistor amplifier, record-play, volume control, miniature speaker.

forward-stop-rewind switch, reel of tape and spare reel, motor, attractive coloured case, Mic. and earphone sockets, pick-up coil mike, earphone and carrying handle supplied. Standard battery operated. Simple to put together in less than one hour. Brand new and guaranteed.

PORTABLE MAINS SOLDERING IRON SP.1

30 watts. Features removable handle that covers tip and barrel. Complete with lead and plug. ONLY 14/6



RELDA EXCLUSIVE!!!

100,000 O.P.V. MULTI-TESTER

MODEL EP.100K. A handy size high sensitivity multi-tester with a shock-proof meter of 9.5µA. Incorporates three germanium diodes and simplified meter scale for easy reading.
RANGES: D.C. Volts: 0.5V, 2.5V, 10V, 50V, 500V, 1000V. (35,000 ohm/V), A.C. Volts: 2.5V, 10V, 50V, 250V, 1000V, (12,500 ohm/V). D.C. Amps: 10µA, 250µA, 2.5mA, 25mA, 250mA. Ohms: 0-20K ohm, 0-200K ohm, 0-2M ohm, 0-20M ohm. Centre-160 ohm, 1.6K ohm, 16K ohm, 160K ohm. L.I.: 18µA, 180µA, 1.8mA, 18mA. L.V. 3V.

Decibels: minus 20db—plus 62db. Size: 5 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in.

ORIGINALLY £14.14.0.

OUR PRICE £6.19.6 COMPLETE

"KEW" PANEL METERS

"S" Meter. 35/-; DC Microammeters, 5 mA, 27/6; 300 v., 27/6; 0-500µA, 30/6; 0-500µA, 32/6; DC Milliammeter, 0-1mA, 27/6. Available in Clear Plastic or Black Bakelite. Will fit 1 $\frac{1}{2}$ in. dia. cut out. State choice when ordering. All models individually boxed and fully guaranteed.



EDGEWISE PANEL METERS

Size 3 $\frac{1}{2}$ in. w. x 1 $\frac{1}{2}$ in. h. x 3 $\frac{1}{2}$ in. d. 0-200 µA, 69/6; 0-1 µA, 59/6. All boxed and fully guaranteed.



R.101 TUNING AND BATTERY INDICATOR

This ultra-miniature tuning and battery indicator is easily mounted into portable radios or tape recorders for indicating tuning centre and residual capacity of batteries. Galvanometer movement assures complete accuracy. Insulation resistance between case and terminals: 20 Megohms/500V. Sensitivity: 400 µA. Solder terminals are provided at rear. Plastic case cover. Complete with example circuit for use. Size: 1 x 1 $\frac{1}{2}$ in.

PRICE 24/6


3-WAY SLIM CRYSTAL MICROPHONE



MODEL 100C. May be hand-held, floor stand or desk stand mounted or suspended by lavaliere cord. Response 60-10,000 cps. Built in on/off switch. Output level—52dB. Omni-directional head. Clips on or off standard

stand adaptor permitting tilting for multi-angle use. Satin chrome finish. Supplied complete with table stand, cable and lavaliere cord. PRICE 48/-

AUTOMATIC SOLDERING IRON SF.1.

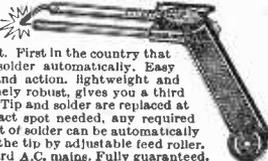

30 watt. First in the country that feeds solder automatically. Easy one hand action. Lightweight and extremely robust, gives you a third hand. Tip and solder are replaced at the exact spot needed, any required amount of solder can be automatically fed to the tip by adjustable feed roller. Standard A.C. mains. Fully guaranteed.

ONLY 52/6

INEXPENSIVE HI-FI RADIO JACK GT.50.

Full medium wave coverage. Ideal for all tape recorders, amplifiers etc. No batteries required—just plug in. You will be amazed at the reception this pushes into your equipment. ONLY 29/-.

LEAD ACID ACCUMULATORS (Unspillable).



2 volts 16 A.H. Brand new. Size 4in. x 7in. x 2in. Six for 20/- (min). (2/6 each for callers)

MAIL ORDERS TO (DEPT. P), 32a COPTIC STREET, LONDON W.C.1.



CALLERS WELCOME AT 87 TOTTENHAM COURT ROAD, LONDON, W.1. MUS 9606

"THE CONSTRUCTOR'S PARADISE"
BEAR HUDSON LTD.
 63, GOLDHAWK ROAD, SHEPHERD'S BUSH, LONDON, W.12
 (Next to Goldhawk Road, Metropolitan Str.) Phone SHE 2581/4794
 Open all day Saturday

COMPONENTS - HI-FI - BOOKS - SERVICE

24-HOUR MAIL ORDER SERVICE with all goods guaranteed.
 ★ FREE POSTAGE on orders over 20/-; add 1/- postage if under.
 ★ HI-FI INSTANT COMPARISON ARRANGEMENTS.
 ★ COMPREHENSIVE TECHNICAL SERVICE for Customers.
 ★ BULK PURCHASING DEPT. and own manufacturing facilities mean **LOWEST PRICES.**

**EXCITING NEW BOOKS
 FOR THE TRANSISTOR USER**

- 184 Tested Transistor Circuits using 2/6 Modules. *Post free.*
 185 Tested Shortwave Receiver Circuits using Micro-Alloy Transistors (MATs) *Post free.* 5/-
 186 Tested Superhet Shortwave and Communication Receiver Circuits using Micro-Alloy Transistors (MATs). *Post free.* 5/-

WE STOCK ALL BERNARD'S RADIO BOOKS for Constructors. Over 70 titles. 3rd ed. for full catalogue. We Stock the Parts You Need for the Circuits too!

R.F. TRANSFORMERS FOR TRANSISTORS CIRCUITS

- 1st and 2nd Stage 455 Kc/s A.M. double tuned I.F. (Ref. 86). 180Q. 13/-
 455 Kc/s A.M. double tuned for final stage I.F. amplifier (Ref. 87) 140Q. 12/-
 Double tuned 10.7 Mc/s. I.F. for 1st and 2nd stage F.M. super gain (Ref. 88). 12/-
 Double tuned F.M. ratio detector stage 10.7 Mc/s final stage, super gain (Ref. 89). 12/-

PREFABRICATED TRANSISTOR UNITS BY GÖRLER etc.

We stock all famous Görler prefabricated de-luxe transistorised units for constructors seeking the very finest standards. 24 page book of circuits, 2/6 post free.


HI-FI AUDIO AMPLIFIERS

150 mW	22/8	1 1/2 Watt	97/8
4 Watt	52/8	2 Watt	102/8
1 Watt	92/8	2 1/2 Watt	107/8

**TRUE HI-FI FROM CRYSTAL P.U.s.
 TSL**

CONSTANT VELOCITY EQUALISER

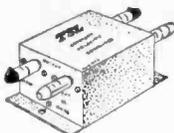This remarkable new TSL development copies quality almost as good as the finest professional magnetic pick-ups to be obtained from crystal or ceramic types. With its even cheap record players become first-class instruments. With good equipment results are astonishing. Ideal for B.S.R., Collaro, Garrard and Aoco. With plugs for mono or stereo. 3 years' guaranteed. Ready for use.



30/-
 POST FREE

M.A.T. MICRO-ALLOY GOLD-PLATED TRANSISTORS

Phenomenal Performance

A revolutionary advance in transistor technique and performance. Will operate up to 150 Mc/s with current gains of better than 250. With a single "MAT" stage gains as high as 1,000 times are possible. Absolute minimal voltage and current collector requirements; ultra low-noise, gold-plated leads. FULL DATA SHEETS FREE. Also "22 Tested Circuits using MATs" covering S.W., Hi-Fi, Personal and TV applications (size 10 1/2 x 7 1/2 in.) 5/- post free.

MAT 100	7/9
MAT 120	7/9
MAT 101	8/6
MAT 121	8/6

ADT.140 New wonder transistor with cut off at 500 Mc/s. 15/-

HI-FI by JASON, LEAK, LORENZ, QUAD, RADFORD, TSL, WHARFEDALE, W.B., etc.

10% HI-STAB RESISTORS

1/2 and 1/4 W. 10Ω to 10 meg, 6d. each. 5/- per doz. State values required. Specially recommended for transistors.

THE FANTASTIC

SINCLAIR 'SLIMLINE'

VEST-POCKET RECEIVER



- ★ MAT TRANSISTORS
- ★ AMAZING RANGE AND QUALITY
- ★ LESS THAN 3 x 1 1/2 x 1 in.
- ★ SUPER SENSITIVE


All parts (except bat.) come to Transistor brings in countless stations (med. wave) with truly superb quality and sensitivity. Absolutely self-contained with printed circuit board and all parts for easy building. With instructions. special ear-piece.

EVERYTHING FOR THE TRANSISTOR USER

Britain's largest and most varied stocks—S.A.E. with your enquiries, please.

JACKSON 
 the big name in **PRECISION** components

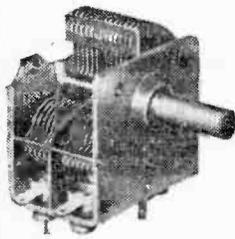Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components.



"00" Twin Condenser

Designed for use in miniature transistor receivers. The front (aerial) section is 208 pF to provide coverage for medium waves, and the rear section is 176 pF, which may be padded to match the oscillator—very robust yet lightweight. Front area 1 1/2 in. x 1 1/2 in. x 1 1/2 in. deep.


JACKSON BROS. (LONDON) LTD.

(Dept. P.W.) KINGSWAY-WADDON,
 CROYDON, SURREY
 Phone: Croydon 2754-5. Grams: Walfico, Souphone, London

**HOUSING
 HI-FI?**

This is one of a wide range of furniture for every hi-fi purpose—speakers, equipment, tapes and records. Soundly designed, superbly finished, sensibly priced. Send for illustrated catalogue and name of local stockist.

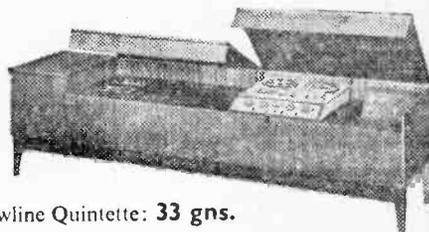One of the Record Housing range of 25 models



Lowline Quintette: 33 gns.

RECORD HOUSING

(Dept. P.W.10), Brook Road, London N22.
 Telephone: BOWes Park 7487/8

The Practical Wireless

OHM'S LAW CALCULATOR

*A time-saving aid for every
enthusiast*

By F. P. Rozee

THE relationship between voltage, current, resistance and power is of the utmost importance; a full understanding of the terms and the ability to manipulate them rapidly is the first essential of radio engineering. The relationship is known as Ohm's Law and the importance of this law to the engineer cannot be overstated.

As arithmetical operations are somewhat tedious and mental calculations are unreliable, a mechanical means of computing, with an accuracy better than the tolerance of practical components, becomes necessary.

The Ohm's Law Calculator presented with this month's issue of PRACTICAL WIRELESS has been designed by the author for readers of this publication. It will be found to be a valuable addition to the workshop and a useful companion to the Parallel Resistor Calculator presented with the April 1963 issue of PRACTICAL WIRELESS.

Ohm's Law, using the terms E, I and R, only holds good for d.c. circuits, but it can be used at low frequencies where the load is almost purely resistive.

A mains dropper resistor, although wire-wound and thus to some extent inductive, would, at 50c/s, behave more or less as if d.c. were being applied. Computations using the calculator may be made at mains frequency for any resistive loads such as fires, heaters, etc.

A word about filament lamps and valve heaters; these will have a very low resistance when cold, only at their working temperature will the resistance agree with the working voltage and current.

The range of voltage, resistance and current encountered in radio and television engineering is far greater than in most other branches of electrical work. Depending on the type of equipment, voltage may range from a few microvolts to several kilovolts, current from a few microamps to several

amps and resistance from an ohm or so to several megohms. It is necessary to cater for all of these possibilities and for this reason a range extension chart has been printed on the calculator.

The Two Scales

An inspection of the calculator shows that it consists of two scales. Scale "A" being the inner or slide and scale "B" the outer. Scale "A" is used for current only and is marked on a logarithmic scale from 1mA to 1,000mA, this being the current range that is most likely to be encountered.

Scale "B" is used for resistance, voltage and power ratings. It is marked 1—1,000, and for voltages would be regarded as 1 to 1,000V. For resistance, using the left-hand pointer on scale "A", the fixed scale covers from 1 to 1,000k Ω , while with the right-hand pointer, the range is from 1 to 1,000 Ω .

For power rating, using the left-hand pointer, scale "B" covers from 1 to 1,000mW, and with the right-hand pointer from 1 to 1,000W. The whole of this latter range is not likely to be required, the largest resistor that would be used is probably a 60W component, where 200V are dropped in a 300mA heater chain. Power dissipations below 100mW are rarely of interest as a $\frac{1}{10}$ W is the smallest component normally available.

To Find Voltage or Current

Where the unknown value is that of either voltage or current, set the known resistance against the appropriate pointer. The unknown voltage is then revealed directly above the known current, or the unknown current directly below the known voltage.

Examples

Known values, 200 Ω and 10mA. Set ohms pointer to 200, read 2V above 10mA.

Known values, 8k Ω and 5mA. Set kilohms pointer to 8, read 40V above 5mA.

If it is found that with the appropriate pointer on the value of resistance, either the known voltage is not above some part of scale "A" or that the known current is not below some part of scale "B", it will be necessary to use the other pointer and refer to the range extension chart.

Examples

Known values, 50k Ω and 100mA. Set the kilohms pointer to 50, it will be seen that 100mA is not below any part of scale "B". Set the ohms pointer to 50. We now know that the ohms pointer must indicate in kilohms, the chart (under the column headed "ohms pointer") shows that this could be in association with either microamps and volts, or milliamps and kilovolts. As we have 100mA, it must be then, that the figure 5 revealed above the 100 is kilovolts. Therefore 50k Ω , 100mA = 5kV.

Known values, 2.5M Ω and 200 μ A. The chart

shows that in association with microamp, megamp could either be set against the ohms pointer and the answer be in kilovolts, or megohm could be set against the kilohms pointer and the answer be in volts. As the first does not allow 200 to appear against scale "B", the second is used. Set kilohms pointer to 2.5 and 500 is revealed above 200. Therefore $2.5M\Omega$, $200\mu A=500V$.

To Find Resistance

Where the unknown value is that of resistance, set the known current in scale "A" directly below the known voltage in scale "B" and read the resistance from whichever of the pointers is on scale "B". If this is the right-hand pointer the answer is in ohms and if the left-hand pointer, in kilohms.

Examples:

Known values, 8mA and 4V. Set 8 on scale "A" against 4 on scale "B" and read 500Ω from the ohms pointer.

Known values, 3mA and 120V. Set 3 on scale "A" against 120 on scale "B" and read $40k\Omega$.

Should either or both of the known values not fall in the ranges 1—1,000mA or 1—1,000V, refer to the range extension chart, this is quite easy to follow.

According to the top line of the chart, if scale "A" is used for microamps and scale "B" for microvolts, the resistance reading is in ohms and will be indicated by the kilohms pointer, and so on down the chart to amps and volts where the resistance in ohms is indicated by the kilohms pointer.

Should the ohms pointer be on the scale when microamps and microvolts are associated, or milliamps and millivolts, or amps and volts, the indication would be in thousandths of an ohm. When microamps and kilovolts are associated, the

kilohms pointer would indicate from $1.000M\Omega$ up, about equal to an open circuit.

To Find Power Rating

It is necessary to know both the voltage and the current in order to find the power dissipated in either watts or milliwatts (to accommodate the formulæ $P=E^2/R$ and $P=I^2R$ would require an extra sliding scale and make the calculator unduly complicated):

Should either voltage or current be the unknown value, finding this using the method described earlier, will take but a moment. The known voltage is set against the left-hand pointer and the power in milliwatts read directly above the known current. If the current is not below some part of scale "B" the power is in excess of 1W and it is necessary to set the right-hand pointer to the voltage, when the power in watts is read directly above the known current.

The extension chart includes a multiplying or dividing factor on certain ranges. Where no factor is shown the power dissipation is negligible.

Resistor Voltage Ratings

The reader is reminded that resistors have a maximum voltage rating. This is not troublesome on the lower resistance values. With a $100k\Omega$ component $1.6mA=160V$ which is approximately $\frac{1}{4}W$, so 160V is the maximum that would be applied if the power rating were observed. However with a $5M\Omega$ component, the full $\frac{1}{4}W$ rating is met by 1.1kV at $210\mu A$, and 1.1kV is well above the voltage rating for a $\frac{1}{4}W$ carbon resistor.

The following figures will serve as a rough guide to the maximum voltages for carbon composition resistors: $\frac{1}{4}W-250V$, $\frac{1}{2}W-400V$, $\frac{1}{2}W-600V$, $1W-800V$, $2W-1.2kV$.

Manufacturer's data should be consulted where possible as the construction, composition and certain techniques in production are among the factors that impose these limits. ■

TEST GEAR TECHNIQUES

—continued from page 545

provision of a connecting terminal for a marker is lacking, the marker signal can be loosely coupled to the wobulator signal input lead.

Miscellaneous Points

There are one or two small points to be noted when using an oscilloscope for alignment. Inversion of the trace, vertically, while presenting no real problem, can be confusing. Simply reverse the Y input leads to invert the image. Horizontal reversal is rather more difficult to detect, and requires a frequency shift of the wobulator input, to determine whether a rise or fall produces the correct lateral shift. Used in conjunction with the marker, this method soon becomes familiar to the operator.

As a final reminder—the response curve displayed is linear, with reference to amplitude—and due allowance must be made when comparing with a published curve, which may be drawn to a logarithmic (decibel) scale. ■

THE PRACTICAL WAY . . .

. . . to make sure of your regular copy of PRACTICAL WIRELESS is to place an order with your newsagent. Do it now! The order form below is included for your convenience. Simply complete it and hand it to your newsagent next time you call.

ORDER FORM

To _____
(Name of newsagent).

Please send/reserve PRACTICAL WIRELESS (2/-) every month, commencing with the next issue.

NAME _____

ADDRESS _____

DETACH AND HAND TO YOUR NEWSAGENT

Brand new individually checked and guaranteed VALVES

AC/HL 4/6	E80P 2/6	EF95 5/-
AC/P4 6/-	E1148 25/-	EF183 9/-
AC6/PEN 5/-	E1232 9/-	EF184 9/-
AR 5/-	E1266 50/-	EL32 3/9
AR3 3/-	E1415 30/-	EL34 12/-
AR4 3/6	E1824 12/6	EL35 5/-
AR12 2/6	E2134 16/-	EL41 8/-
AR21 7/6	E450 1/6	EL42 8/-
AR24 3/6	E476 7/6	EL50 9/-
AR34 4/6	EABC80 6/8	EL94 6/8
ARTF1 6/6	EAC91 3/6	EL95 9/-
ATP4 2/3	EAF42 8/-	EL91 4/6
ATP7 5/8	EB34 1/6	EL95 6/6
AU7 50/-	EB91 3/6	EM80 7/6
B84 10/-	EB93 5/-	EM84 8/6
B854 47/6	EB90 5/6	EM92 20/6
BT19 25/-	EBF90 7/8	EY1 8/-
BT35 25/-	EBF89 7/8	EY86 7/-
BT43 15/-	EC85 12/6	EY91 8/-
RT9B 20/-	EC92 20/6	EZ40 6/6
RT83 35/-	EC90 20/-	EZ41 6/6
CV34 2/-	EC91 3/-	EZ80 6/-
CIC 6/-	ECU1 4/6	EZ81 6/-
CL33 9/-	ECU2 4/6	EZ87 5/-
CV284 12/6	ECU3 7/6	F137/1K 1/-
CV4014 5/-	ECU4 7/6	F137 19/-
CV4025 10/-	ECU5 8/-	F142 19/-
CV4046 40/-	ECU6 9/-	G50/2G 5/-
CV731 6/-	ECU7 9/-	GZ32 9/-
D1 1/8	ECU8 9/-	H63 7/-
D41 3/3	ECU9 10/-	HV800 100/-
D77 4/3	EL182 11/-	HK54 22/6
DA30 12/6	EL236 3/8	HL23 6/-
DAF70 7/6	EL280 6/6	HL23DD 6/-
DAF96 7/6	EL282 6/6	K7561 4/6
DD41 4/6	EL283 10/-	KL24 22/6
DE75 8/6	EL284 11/-	HL2K 2/6
DET20 2/-	EL285 11/-	HL23 6/-
DP31 3/6	EL286 11/-	Q1202 3/6
DP92 3/6	EL287 11/-	Q1203 3/6
DP96 7/6	EL288 11/-	Q1204 3/6
DK92 7/6	EL289 11/-	Q1205 3/6
DK96 7/8	EL290 11/-	Q1206 3/6
DL18 5/6	EL291 11/-	Q1207 3/6
DL93 3/6	EL292 11/-	Q1208 3/6
DL94 3/6	EL293 11/-	Q1209 3/6
DL96 7/6	EL294 11/-	Q1210 3/6
DL97 15/-	EL295 11/-	Q1211 3/6

M8100 9/-	T41 6/8	1LH4 4/-
M8142 12/-	TP22 5/6	1N43 4/-
M8190 5/-	TP25 15/-	1N70 4/-
MH4 3/8	TT1 3/8	1R4 5/6
ML4 6/-	TT15 30/-	1R5 6/6
MS/PEN 6/6	TTR31 60/-	1S4 5/-
N78 12/-	TZ20 16/-	1S5 5/6
NGT2 10/-	TZ05-20 4/-	1T4 3/6
OC3 6/8	U19/14 8/-	2A3 5/-
OD3 7/6	U17 5/-	2A5 6/-
OD5 6/6	U18 6/8	2A6 6/-
OZ4 4/-	U25 10/-	2C26 3/6
P2 10/-	U26 11/-	2C26A 3/6
PC84 6/6	U27 8/-	2C34 2/6
PC85 7/6	U28 9/-	2C38 42/6
PC89 10/8	U801 20/-	2C46 50/-
PCF80 7/6	YABC80 7/-	2C51 12/-
PCF82 6/6	YABC41 7/-	2D21 5/-
PCF83 8/-	YBF80 8/-	2D21W 8/6
PCF89 9/-	YBF69 7/6	2D22 3/6
PL84 7/6	YBCH42 7/8	3A4 3/6
PLC86 10/6	YBCH81 5/-	3A/167M 5/-
PEN25 4/6	UCL82 11/-	3B7 5/-
PEN46 4/6	UCL83 11/-	3B7 5/-
PEN220A 2/6	UCL84 11/-	3B7 5/-
PL36 3/6	UY1 6/-	3E29 50/-
PL81 8/-	UY85 6/-	3E29 50/-
PL82 6/8	V1507 18/-	3E34 6/-
PL83 6/8	V1524 18/-	5A173G 5/-
PL84 6/6	V2023 13/6	5A174G 5/-
PM24A 5/-	VMP44G 12/-	5B/257M 5/-
PT15 10/-	VP23 3/-	5R4G 9/-
PZ5H 7/6	VP133 10/-	5T4 4/6
PX14 10/-	VR 105/30 5/8	5V4G 8/6
PX25 9/6	VR150/30 5/8	5X30 8/6
PX32 9/6	VT4C 20/-	5Y34T 8/-
PY80 8/6	VX39 6/-	6A 9/-
PY81 6/6	VY82 10/-	6A4 9/-
PY82 6/6	VY83 10/-	6A5 9/-
PY83 6/6	VY84 10/-	6A6 9/-
PY84 6/6	VY85 10/-	6A7 9/-
PY85 6/6	VY86 10/-	6A8 9/-
PY86 6/6	VY87 10/-	6A9 9/-
PY87 6/6	VY88 10/-	6A10 9/-
PY88 6/6	VY89 10/-	6A11 9/-
PY89 6/6	VY90 10/-	6A12 9/-
PY90 6/6	VY91 10/-	6A13 9/-
PY91 6/6	VY92 10/-	6A14 9/-
PY92 6/6	VY93 10/-	6A15 9/-
PY93 6/6	VY94 10/-	6A16 9/-
PY94 6/6	VY95 10/-	6A17 9/-
PY95 6/6	VY96 10/-	6A18 9/-
PY96 6/6	VY97 10/-	6A19 9/-
PY97 6/6	VY98 10/-	6A20 9/-
PY98 6/6	VY99 10/-	6A21 9/-
PY99 6/6	VY100 10/-	6A22 9/-
PY100 6/6	VY101 10/-	6A23 9/-

6V6G 4/-	35L6GT 8/-	5704 9/6
6B17 5/-	35T 17/6	5726 9/6
6B8G 2/6	35Z3 8/-	6058 7/-
6BA6 6/6	35Z4GT 6/-	6084 7/6
6B8E 5/6	6X5G 5/6	635G 5/6
6BR7 12/-	6X6GT 6/6	637 4/6
6B16 9/-	6Y6G 6/-	6073 7/-
6C4 2/6	6-30L2 10/-	6120 4/6
6C5G 4/6	6Z4 7/6	6516 3/6
6C6G 5/6	6Z5 8/6	6193 18/-
6C8G 5/6	7B7 7/6	6475 6/-
6CH6 5/6	7C5 7/6	813A 25/-
6D6 3/6	7C6 7/6	9001 3/6
6E5 3/6	7C7 5/6	9002 4/6
6F7 7/6	7H7 7/3	9003 6/6
6G1 7/6	7B7 7/6	9004 2/6
6F8G 3/6	7D5 7/6	9006 2/6
6E6 3/6	7E4 4/6	
6F7 5/6	8D2 2/6	
6F8G 5/6	9E3 3/6	
6F12 4/6	11E3 17/6	
6F13 6/6	12A6 2/6	
6F24 4/6	12AH7 5/-	
6F23 3/6	12A8 11/-	
6G6G 2/6	12AT7 4/6	
6G1 6/6	12A8 6/6	
6H6M 1/6	12B17 9/-	
6J4 9/6	12AX7 5/6	
6JAWA 10/6	12A7 10/6	
6J5 3/6	12BH7 7/6	
6J6 3/6	12C 3/6	
6J6G 6/6	12E1 1/6	
6J7G 5/6	12H6 2/6	
6K6GT 6/6	12J5GT 2/6	
6K1 6/6	12K7GT 4/6	
6K7G 4/6	12L5M 7/6	
6K84 5/6	12Q7GT 4/6	
6K8GT 8/3	12R7 4/6	
6K8M 8/6	12RH7 3/6	
6L8G 6/6	12S1 3/6	
6L9 9/6	12S2 3/6	
6L9GT 6/6	12S3 3/6	
6L9 9/6	12S4 3/6	
6L9 9/6	12S5 3/6	
6L9 9/6	12S6 3/6	
6L9 9/6	12S7 3/6	
6L9 9/6	12S8 3/6	
6L9 9/6	12S9 3/6	
6L9 9/6	12S10 3/6	
6L9 9/6	12S11 3/6	
6L9 9/6	12S12 3/6	
6L9 9/6	12S13 3/6	
6L9 9/6	12S14 3/6	
6L9 9/6	12S15 3/6	
6L9 9/6	12S16 3/6	
6L9 9/6	12S17 3/6	
6L9 9/6	12S18 3/6	
6L9 9/6	12S19 3/6	
6L9 9/6	12S20 3/6	
6L9 9/6	12S21 3/6	
6L9 9/6	12S22 3/6	
6L9 9/6	12S23 3/6	
6L9 9/6	12S24 3/6	
6L9 9/6	12S25 3/6	
6L9 9/6	12S26 3/6	
6L9 9/6	12S27 3/6	
6L9 9/6	12S28 3/6	
6L9 9/6	12S29 3/6	
6L9 9/6	12S30 3/6	
6L9 9/6	12S31 3/6	
6L9 9/6	12S32 3/6	
6L9 9/6	12S33 3/6	
6L9 9/6	12S34 3/6	
6L9 9/6	12S35 3/6	
6L9 9/6	12S36 3/6	
6L9 9/6	12S37 3/6	
6L9 9/6	12S38 3/6	
6L9 9/6	12S39 3/6	
6L9 9/6	12S40 3/6	
6L9 9/6	12S41 3/6	
6L9 9/6	12S42 3/6	
6L9 9/6	12S43 3/6	
6L9 9/6	12S44 3/6	
6L9 9/6	12S45 3/6	
6L9 9/6	12S46 3/6	
6L9 9/6	12S47 3/6	
6L9 9/6	12S48 3/6	
6L9 9/6	12S49 3/6	
6L9 9/6	12S50 3/6	

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. orders below £1 P. & P. 1/-; over £1, 2/-; over £3, P. & P. free C.O.D. 2/6 extra. Overseas Postage extra at cost.

MARCONI COMMUNICATION RECEIVERS. CR.150. Frequency coverage 2-60 Mc/s in 5 bands. Two I.F.s. 1st 1,600 kc/s, 2nd 463 kc/s. Image signal protecting over 40 dB up to 30 Mc/s and 20-40dB for 30-60 Mc/s. Self checking calibration (built in calibrator). Stabilisation of supply and temperature compensation. Electrical and mechanical bandspread. Metering and visual tuning indicator. Bandpass from 100c/s to 10Kc in 5 stages. Acoustic filter associated with 100c/s. Bandpass position for CW reception. Facilities for diversity reception. In as new guaranteed condition with original mains power supply unit £70 or without power supply unit £60. Carriage 30/-.

P.C. RADIO's mains power supply unit for above, 90/-.

CR.150/2. Frequency coverage 1.5-22 Mc/s in 4 bands, all other features as in CR. 150. Price £35. Carriage 30/-.

P.C. RADIO's mains power supply unit for above, 90/-.

CR.150/3. Same as CR.150 with additional separate antenna trimmer on front panel, crystal controlled 1st oscillator for fixed frequency reception, muting switch (during transmission), wide bandpass extended to 13 kc/s. In as new guaranteed condition with original mains power supply unit £75 or without power supply unit £65. Carriage 30/-.

P.C. RADIO's mains power supply unit for above, 90/-.

H.R.O. Senior. Table Model. In excellent, fully checked, and tested condition (without coils and power pack),

£15.10.0. As above but rack mounted model, £14.10.0.

Individual frequency coils for above £1 each set or set of 4 £8. Either model, carriage £1.10.0.

Original mains power pack for H.R.O. 110/220 v. A.C. Brand new in original packing, 45/-, P. & P. 4/-.

"CONNECT AND FORGET—CANNOT OVERCHARGE"—"ESSTRON" MARK I AUTOMATIC BATTERY CHARGER. Initial charging rate 6-7 amps. The charging rate automatically adjusts itself to the charge in the battery. Automatic current and voltage control. Patented application of magnetic amplification to battery charging. Indicator lights show battery fully charged, receiving charge, incorrectly connected or faulty cells. Mains voltage 200/250 v. Built for 6 or 12 v. batteries. Measurements 7 x 5 x 3 1/2 in. Weight 8 1/2 lb. Price £7.19.6. P. & P. 3/6.

CHR. HIGH RESISTANCE HEADPHONES. New 14/-, P. & P. 1/6.

CONNECTORS FOR T.C.S. RECEIVER, TRANSMITTER AND REMOTE CONTROL, with original plugs on both ends. New £1.17.6 each. P. & P. 2/6.

P. C. RADIO LTD
170 GOLDHAWK ROAD, W.12
Shepherd's Bush 4946

R.209 RECEPTION SET. A 10-valve high-grade Superhet Receiver with facilities for receiving R/T (A.M. or F.M.) and C.W. frequency 1 Mc/s-20 Mc/s. Hermetically sealed. Built on miniature valves and incorporating its own vibrator power supply unit driven by a 6 v. battery (2 point connector included). The set provides for reception from rod, open-wire or dipole aerial with built-in loudspeaker or phone output. Dimensions: Length 12in., width 8in., depth 9in. Weight 23 lb. In as new, tested and guaranteed condition, £23.10.0, including special headphone and supply leads. Carr. £1.

CARBON INSET MICROPHONE. G.P.O. type 2/6. P. & P. 1/6.

PANEL METERS


0-500mA 2 1/2 in. round D.C. ...	30/-
0-25mA 2 1/2 in. round D.C. ...	12/-
0-30mA 2 1/2 in. round D.C. ...	12/-
0-100mA 2 in. square D.C. ...	9/-
0-100mA 2 1/2 in. round D.C. ...	10/-
0-150mA 2 1/2 in. round D.C. ...	10/-
0-200mA 2 1/2 in. round D.C. ...	10/-
0-250mA 2 1/2 in. round D.C. ...	10/-
0-300mA 2 1/2 in. round D.C. ...	10/-
0-500mA 2 1/2 in. round D.C. ...	10/-
150-0-1500mA 3 1/2 in. round ...	29/-
0-4amps Thermo 2 1/2 in. round ...	8/-
0-6amps Thermo 2 1/2 in. round ...	8/-
0-20amps Thermo 2 1/2 in. round ...	8/-
0-15 v. 2 1/2 in. round A.C. ...	17/6
0-20 v. 2 1/2 in. round A.C. ...	17/6
0-500 v. (Shunt) 2 1/2 in. round D.C. ...	20/-
0-600 v. 2 1/2 in. round D.C. ...	15/-
0-5KV electrostatic 3 1/2 in. round ...	85/-

Postage 2/- extra.

SENSATIONAL NEW 1963 DESIGNS — BY CONCORD

LOW PRICES ★★ PICTORIAL STEP-BY-STEP PLANS ★★★ EASY AS A.B.C.

THE NEW "COSTA BRAVA"

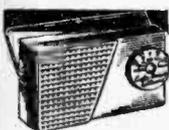

42/6

No earth or aerial required. All-transistor Radio.

Revolutionary **INTERNAL FERRITE AERIAL** and moving coil speaker makes this sensational pocket-size radio the best money-saving bargain of all time. Powerful, superb tone and clarity, ensures perfect reception for all your favourite programmes. Completely portable only 6 1/2 x 3 1/2 in. Two-tone case. Anyone can assemble with our simple **PRINTED CIRCUIT PLAN**. Send 42/6, plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. (All parts available separately). **FREE HIGH SENSITIVITY RIDE-AWAY EAR-PIECE GIVEN WITH EACH SET.**

FREE HIGH SENSITIVITY RIDE-AWAY EAR-PIECE GIVEN WITH EACH SET



THE MINUTE TRANSISTOR RADIO MIAMI ONLY 32/6

Unbelievably small—Outrageously cheap. You will be amazed at the fine quality of tone emitted by this tiny radio. Only a fantastic entertainment for months on a 1 1/2 battery. Simple assembly plan with each set. **ONLY 32/6. YES 32/6!** Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.




BIG PROFITS FOR YOU IF YOU BUY NOW!

Made to retail at 7 gns. you can now buy this famous Twin-gong Alarm for only 37/6—but only if you act now—stocks are strictly limited. Easily installed and operated. Switches on or off at any time. Fantastic **FINAL** reduction to clear (minimum order of 3). Car. Free. Free literature. **37/6** assure sent. with each alarm.

THE NEW 4-STAGE "MINUETTE"

32/6

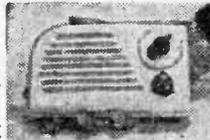

Build this newly-designed "MINUETTE" 4-STAGE transistor set in very strong ready drilled **ULTRA-MODERN CASE**.

size only 6 1/2 x 3 1/2 in. Uses three transistors and diode and **SELF-CONTAINED LOUDSPEAKER**. Very sensitive. Ideal for office, bedroom, holidays, etc. Months and months of listening off 1 1/2 battery. Can be built for **ONLY 32/6**, including **PROPER CASE**, miniature speaker, etc. **SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS** etc., plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

and volume of this great little radio. Only a fantastic entertainment for months on a 1 1/2 battery. Simple assembly plan with each set. **ONLY 32/6. YES 32/6!** Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.

SELL SAFETY TO THE MOTORIST

Bulk purchase of bankrupt stock ensures this fabulous money-making offer, **AUTOMATIC CIGARETTE LIGHTER** Instantly provides ready lit cigarette without the driver taking his eyes from the road. Heavily chromium plated case holds 10. Easily and simply fitted to any car dashboard. Works off 6 or 12 volts. Retail Price 44/8. Special Clearance offer only sold in minimum lots of 6. **12/6** each. Carriage free.

FABULOUS ST. TROPEZ Mk.6

Pocket Radio

ONLY 18/6



NO MORE TO PAY This fantastic offer will amaze you—the compact **ST. TROPEZ** measuring 4 1/2 x 3 1/2 in. receives perfectly in bedroom, office or garden—over all medium waves including Luxembourg. Under 1/2 per hour running cost. ANYONE can assemble it using our simple A.B.C. plan (P. & P. 2/6 extra). C.O.D. extra. Parts can be bought separately. Demonstrations daily. Satisfaction guaranteed.

CONCORD ELECTRONICS (Dept. 14/18)

210, Church Road, Hove, Sussex

SPEAKERS

by **GOODMANS, ELAC, FLESSEY**, etc.

4in. square	12/-	1/6
5in. round	12/-	1/6
7 x 4in. elliptical	13/8	1/6
7 x 5in.	18/6	2/-
10 x 6in.	23/6	2/-

GRAM-TAPE DECK MOTORS!

Special offer of famous manufacturers' motors.

10/6 each. P. & P. 2/- **TAPE HEAD ASSEMBLIES** Dramatic, as fitted to Colloredo studio deck; (Erase & Record/Playback heads, complete on mounting plate).

39/8 each. P. & P. 1/6 **TRANSISTORISED MIXERS** Limited number of 3-channel mixers (Hi-Impedance).

69/8 each. P. & P. 2/- **TUNING CONDENSERS** 500 pF Plus FM Twin gang (rear drive).

10/6 each. P. & P. 2/- **BATTERY CHARGERS** by "LINEAR"

1 1/2 amp. 49/9 ea. **3 amp.** 75/- ea. P. & P. 4/-

CAR AERIALS! High quality 3-section 42in. extended, complete with fittings.

19/6 each. P. & P. 1/6 **METAL RECTIFIERS** 300V. 300 mA. Few only 9/6 each.

PYE co-ax. Miniature Plugs and sockets. **5/6 per pair.** P. & P. 1/- pair

OUR FAMOUS READIPACKS

- No. 1 100 resistors 1w to 5w 10ohm to 50 meg.
 - No. 2 25 condensers 1pf to 10000pf 5% to 20%.
 - No. 3 20 condensers 1000pf to .01mf
 - No. 4 12 condensers .01mf to .1mf
 - No. 5 32 Hi-stab resistors 1, 2 and 5% 100hm-25meg.
 - No. 6 10 w/w Resistors 60hm-82K ohm
 - No. 7 4 Carbon controls volume, tone, etc.
- All at 8/6 each. **POST FREE**

SWITCHES FOR MULLARD CIRCUITS

to specification and "Mullard approved"

TR2	2V Pre-Amp.	12/9
TR3	3V Pre-Amp.	12/9
TR4	3V Pre-Amp. Lo/Pass Filt.	10/9
TR5	3V Pre-Amp. Hi/Pass Filt.	9/4
TR6	3V Tape Amp. Rec/Play	18/6
TR7	3V Tape Amp. Eaz	7/4
TR8	Tape Pre-Amp. Rec/Play	18/6
TR9	Tape Pre-Amp. Eaz	7/4
TR10	Stereo Pre-Amp. Selector	18/6
TR11	Stereo Pre-Amp. Ch/E	9/6
TR12	Stereo Pre-Amp. Stereo Mono	9/6

P. & P. 1/- per switch.

TELE-RADIO (1943) LTD

189 EDGWARE ROAD, LONDON W.2
PADDINGTON 4455

AMATEUR RADIO CHAS. H. YOUNG LTD.

AERIAL EQUIPMENT

TWIN FEEDER. 300 ohm twin ribbon feeder, similar K25, 6d. per yd. d. K35B Telecon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

COPPER WIRE, 14 G., H/D 140ft. 17/-; 70ft. 8/6. P. & P. 2/6. Other lengths pro rata.

RIBBED GLASS, 3in. aerial insulators, 1/9 each. Shell ins 2in. 9d. each. P. & P. 2/- Up to 12.

CERAMIC FEEDER SPREADERS, 6in. type F.S. 10d. each. P. & P. 2/-.

CERAMIC "T" PIECES, Type A.T. for centre of dipoles, 1/6 each. P. & P. 1/-.

2 METRE BEAM 5 ELEMENT W.S. YAGI. Complete in box with 1-2 1/2in. mast head bracket. **PRICE 49/-.** P. & P. 3/6.

SUPER AERIAL CABLE. 75 ohms, 300 watts, very low loss, 1/8 per yard. P. & P. 2/- 50 ohm, 300 watt coax, very low loss, 1/9 yd. P. & P. 2/-.

ABSORPTION WAVEMETERS. 3.00 to 35.00 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham bands, marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack, 22/6 post free.

VARIABLE CONDENSERS. All brass with ceramic end plates and ballrace bearings. 50 pF. 5/9. 100 pF. 6/6. 160 pF. 7/6. 240 pF. 8/6. and 300 pF. 9/6. All fitted with rear extension for ganging. P. & P. 1/- Also Flexible Couplers, 1/- each.

8.1-8 MFD. 1,200 v. D.C. Wkg. Capacitors, 12/6 each.

METERS. 3 1/2in. with 2 1/2in. scale, 0-10 mA, 15/-, 0-100 mA, 15/-, P. & P. 1/6.

THERMO, 2 1/2in. square, 0-1 amp, 7/6 each. P. & P. 1/6.

170-172 CORPORATION ST.
BIRMINGHAM 4

Telephone: CEN 1635



LETTERS TO THE EDITOR

EGG CRATE LINING

SIR,—Recently I was loaned a copy of July 1951 P.W. by a friend. In this issue is an article describing how to make use of papier mâché egg crates as a lining for loudspeaker cabinets of the bass reflex or infinite baffle type.

Having a loudspeaker enclosure which suffered badly from cabinet resonance, I tried this idea and found that the quality of absorption and irregular surface of the egg crate lining allowed 10W of audio power to be fed into the loudspeaker, without the troublesome "booming" which had occurred previously. I should like to take this opportunity to thank Mr Simmons who wrote this most useful article.—R. W. MOTH (Tettenhall, Staffordshire).

LANGUAGE BARRIER

SIR,—I absolutely agree with Mr. Dhenau when he says in his letter (PRACTICAL WIRELESS, July) that Esperanto "would be an untold boon" to wireless communication.

I should like to add that I too know from personal experience that it is much easier to understand and be understood by a foreigner using Esperanto than broken English. Quite apart from the obvious fact that it is a neutral language, one cannot fall into errors and ambiguities of speech. It is impossible to detect the nationality of a reasonably fluent Esperantist, and this surely helps to break down the barriers of language.—Miss E. STOREY (Hexham, Northumberland).

NOVICE LICENCES

SIR,—For some months now I have followed carefully all the correspondence published in P.W. with regard to the licensing of individuals to operate transmitters, and I am convinced that the issue involved is far wider than the question of whether or not "novice licences" should be introduced.

As a member of a free and democratic society, I believe that every citizen of the U.K. should be able to look upon the use of the ether as his right as an individual and not as the privilege of the initiated few. To refuse anyone permission to use such a convenient method of communication in this day and age is not only narrow-minded but also dictatorial.

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents

Of course there must always be limitations on power, frequency, etc., but such things are easily enforced and whereas only limited rights prove acceptable, the complete rejection of these rights is criminal.

No one would deny that, in view of the good name of amateur radio, established over the years, and in consideration of the pioneer work of early hams in "opening up" new bands, the privilege of working certain frequencies should remain exclusively theirs. However, that is no excuse for forbidding the man-in-the-street the use of part of the spectrum and, if we are to be logical about this, we cannot expect every individual to sit and pass a highly technical examination beforehand.—R. L. J. STEVENSON (Carlisle, Cumberland).

Sir,—I would be grateful if any reader could sell or loan me . . .

. . . a manual or any information on the G73 wavemeter.—F. MURDON, 13 Bridge Street, Risca, Newport, Monmouthshire.

. . . the manual of the Bendix RA-1B receiver.—M. J. LANG, 4 Lynton Road, Burnham-on-Sea, Somerset.

. . . the September 1961 issue of P.W.—R. D. SAXTON, 165 Gloucester Road, Patchway, Bristol.

. . . the handbook for the oscilloscope No. 11 (A.A. Predictor Mk. 1).—J. E. GRIFFIN, 113 Gladys Avenue, North End, Portsmouth, Hampshire.

. . . data or circuit diagram of the R.1392D receiver.—W. SMITH, 6 Salisbury Crescent, Blandford Forum, Dorset.

CORRESPONDENT WANTED

SIR,—As a regular reader of PRACTICAL WIRELESS and an enthusiast of amateur radio and television, I would like a correspondent in England of about my own age (16 years). I will answer all letters received.—RON SWALLOW, JNR., 1 Chauvel Street, North Ryde, Sydney, N.S.W., Australia.

BOOK REVIEW

RADIO AND LINE TRANSMISSION: VOLUME 2

By G. L. Danielson, M.Sc.(Tech.), B.Sc., A.M.I.E.E., and R. S. Walker, Grad.I.E.E., Grad.Brit.I.R.E.; published by Iliffe Books Limited.

295 pages, 224 diagrams, 5½in. x 8½in. Price 22s. 6d.

THE whole of the syllabus of the City and Guilds of London Technicians' Certificate examination in Radio and Line Transmission B is covered by this volume.

Communications students preparing for this third year examination will find that the authors have catered for their requirements using the same well-defined style as in their first volume of this series. As readers of volume 1 will know, both authors are particularly qualified to write on this subject; Mr. Danielson is the Head and Mr. Walker a Lecturer of the Telecommunications Department of the Norwood Technical College.

The range of subjects dealt with is substantially the same as volume 1, but the treatment is deeper; where general introductory statements often sufficed in the earlier book, fuller explanations and mathematical proofs are now given. The text still continues to be mainly of a descriptive nature, and the standard of mathematics required is no higher than ordinary level G.C.E.

For those not familiar with the syllabus of Radio and Line Transmission B it should perhaps be explained that it embraces both general principles and practical aspects of components employed in communications equipment.

CORRIGENDA

An Electric Timer

Referring to Fig. 1 (page 131 June issue), the batteries should be transposed: B1 (3V) feeds the buzzer (Z1) and lamp (LPI); B2 (22.5V) supplies the main circuit.

This article was written by D. Gibson and we apologise for misprinting the author's name.

Making Tin Plate Chassis

In Fig. 1 (page 73 May issue) tinplate of 16 or 28s.w.g. was specified in error for 26 or 28s.w.g. Bearing in mind the simple tools employed, the technique described in this article is applicable only to the thinner gauges of tinplate.

Double Conversion Communications Receiver

(1) Referring to Fig. 2a (pages 50, 51 May 1963 issue), L6 should be redesignated "L6A" and the following item should be added to the components list (page 141 June 1963 issue):

L6A 2nd oscillator coil (Repanco R03).

On page 142 (last line but one) the reference to "second oscillator coil L5" should be amended to read "L6A".

(2) The correct type for V13 is VR150/30 (Brimar) or QS150/40 (G.E.C.).

Kenilworth Public Address Amplifier

In the components list (page 320 August 1963 issue) the resistors are described as 5W types; this was a misprint for ½W.

JUST TO PUT YOU IN THE PICTURE

TO a steadily increasing band of practical enthusiasts TV no longer signifies passive viewing of BBC or ITV programmes, but a branch of communications offering opportunities for experimental and creative work, just as sound radio has provided for many years past.

Television DX hunting, or the reception of distant TV stations, can be a fascinating hobby where one's knowledge of v.h.f. and u.h.f. propagation conditions, operating skill, location and—of course—a certain amount of luck! all contribute to the bag of stations received. A standard TV receiver can be modified for DX hunting without much difficulty—and there is at the moment a plentiful supply of secondhand receivers on the market at rock bottom prices. A commentary on DX TV now appears regularly in our companion journal *Practical Television*. This interesting feature lets you know what the other fellow has received and gives guidance on seasonal conditions, and transmitting frequencies and times of operation of the quarry.

Why not build your own TV camera? Starting in this month's *Practical Television* is a series of articles describing the construction of a closed-circuit TV camera suitable for use with any domestic TV receiver. This camera opens up all kinds of possibilities for home entertainment, as well as more serious applications in picture production. No prior knowledge of camera circuit technique is needed—everything essential is fully explained in these articles.

Of course if you are a little more ambitious there is no reason why you should not build and operate your own TV station. Amateur TV transmissions are permitted on 70cm and on shorter wavelengths by licensed operators—and there is still an element of pioneering in the establishment of contact and the exchange of pictures with fellow hams on these ultra high frequencies. The background to TV ham activities will be discussed in the November issue of *Practical Television* and subsequent articles in this new series devoted to Amateur Television Transmission will provide full constructional details for a 70cm converter, a complete receiver, a transmitter and a camera unit; aerials and ancillary equipment for the TV ham's station will also be described.

So if you are looking for some further interest in the realm of electronics and communications to help occupy the long Winter evenings that loom ahead, may we suggest that you get into focus and start scanning the pages of *Practical Television* right away!

Despite our opening paragraph *Practical Television* is not oblivious of the millions of broadcast viewers. In fact many of its pages are devoted regularly to the servicing and maintenance of domestic TV receivers. Commencing shortly will be a series describing an all-transistor dual-standard TV receiver for the home constructor. ■

UNIVERSAL AVOMETERS



Guaranteed perfect working order. Supplied complete with leads, batteries and instructions. Model "D" 34 range £8.19.6 Model "M" 50 range £11.0.0 Registered Post 5/- extra.

R.C.A. HEADSETS

Low impedance, comfortable headband. Suitable for AR88, CR100, etc. Brand New, 15/6. P. & P. 1/6.

MICROAMMETERS

0-500 microamps. 2 1/2 in. circular flush panel mounting. Dials engraved 0-15, 0-300 volts. BRAND NEW. BOXED. 15/- P. & P. 1/6. **230/250 VOLT A.C. MOTORS** 4 1/2 x 3 in. dia. 90 watts, 5,000 r.p.m. 1 in. spindle. Brand New, 22/6 each. P. & P. 2/-.

FIELD STRENGTH METERS

Frequency coverage 1 to 250 Mc/s. Fitted with 200 micro-amp meter. Supplied with telescopic aerial, ear-piece and instructions. 99/8 post paid.

FIELD TELEPHONES TYPE "F" Suitable for many applications. Generator bell ringing, 2 line connection. With batteries and wooden carrying case, fully tested. £4.19.6 per pair. Carr. 5/-.

HEAVY DUTY AUTO TRANSFORMERS

0-115-230 volt step up or step down Brand New. boxed. Ex U.S.A. 3,000 watt. £7.10.0, carr. 10/- 7,500 watt. £15, carr. £1.

MINIFLUX TAPE HEADS Set of three record, playback, erase. Only 29/6 set. P. & P. 9d.

PANEL METERS

100uA	2 1/2" F.M. D.C.	42/6
100uA	3 1/2" F.M. D.C.	62/6
1 mA	2 1/2" F.M. D.C.	25/-
30 mA	2 1/2" F.M. D.C.	12/6
30/0/30 mA	2 1/2" F.M. D.C.	9/6
350 mA	2 1/2" F.M. D.C.	10/6
15 amp.	3 1/2" F.M. D.C.	39/6
5/0/5 amp.	3 1/2" F.M. D.C.	25/-
300 v.	2 1/2" Proj. A.C.	19/6
300 v.	2 1/2" F.M. A.C.	25/-
500 v.	2 1/2" F.M. D.C.	35/-
120 v.	3 1/2" F.M. D.C.	35/6

Postage extra.

SILICON RECTIFIERS

400V. p.i.v. 4.7 amp	7/8
200V. p.i.v. 6 amp	5/6
800V. p.i.v. 500 mA	5/6
400V. p.i.v. 500 mA	3/8
70V p.i.v. 1 amp.	3/8

OA 202 miniature silicon rectifiers 1/- each.
Discount for quantities
Please add postage.

R.C.A. AR.88 D. RECEIVERS

New release, limited number available. Frequency coverage 550 Kc/s to 32 Mc/s on 6 bands. Operation 110/230 volts A.C. Offered in excellent used condition, fully checked and guaranteed perfect order. £45 each. Carr. £2.



P.C.R.2 COMMUNICATION RECEIVERS

Excellent performance for modest outlay. Frequency coverage on three bands 800-2,000 metres, 190-550 metres, 6-22 Mc/s. Output for phone or speaker. Supplied in perfect condition £5.19.6 each. Carr. 10/-. The receiver can be supplied with an internal power supply to operate on 200/250 volt A.C. at 39/8 extra or plug in external power supplies are 35/- extra. Full circuit supplied.

AVO WIDE RANGE SIGNAL GENERATORS

Frequency coverage 50 Kc/s to 80 Mc/s in six turret operated ranges. For use on standard A.C. mains. Packed in original transit cases with accessories. Supplied in as new condition, fully checked before despatch. £15. Carriage 10/-.

NATIONAL H.R.O. RECEIVERS

SENIOR MODEL. Supplied complete with full set of 9 coils covering 50 Kc/s to 30 Mc/s. Each receiver thoroughly checked and available as follows—
TABLE MODEL. As new condition £25. TABLE MODEL. Good used condition £19.19.0
RACK MODEL. As new condition £22.10.0
RACK MODEL. Good used condition £18.18.0

NB—Rack model is identical to table model with extended front panel to fit a 15in. rack. Carriage £1 extra.
200/250 volt A.C. power supplies for all above receivers, also sold separately. 59/6, Carr. 5/-.

HALLICRAFTER S-36 V.H.F. RECEIVERS

F.M./A.M. 27-143 Mc/s. 110 volt A.C. (transformer supplied for 230 v. A.C.) Improved version of S-27. Tested before despatch. Brand new boxed with instruction manual. £40 each Carr. £2

LAFAYETTE BRAND TAPES

First grade quality, brand new guaranteed. Discounts for bulk purchases.
5in. 800ft. std. .. 8/6
5in. 900ft. L.P. .. 10/-
5in. 900ft. L.P. .. 10/-
5in. 1200ft. 'Super Mylar' 12/6
7in. 1200ft. std. .. 15/-
7in. 1800ft. L.P. .. 15/-
7in. 1800ft. L.P. .. 15/-
7in. 2400ft. 'Super Mylar' 20/-
7in. 2400ft. D.P. .. 25/-
Post 2/- Over £3 post paid.

MULTIMETERS BRAND NEW—FULLY GUARANTEED LOWEST EVER PRICES

Supplied with Leads, Batteries and Instructions.
1,000 Ω/VOLT 0/15/150/1,000 v. A.C. and D.C. 20,000 Ω/VOLT 0/10/50/250/500/1,000 v. A.C. and D.C.
0/150 mA D.C. 0/50uA/0/10/25/500 mA. D.C.
0/100 K Ω etc. 0/50K/500K/5 meg. etc. 97/6. P. & P. 2/6.
30,000 Ω/VOLT 0/1/10/50/250/500/1,000 v. D.C. 0/10/50/250/500 v. A.C. 0/50uA/0/10/250 mA. D.C. 0/10K/1 meg./10 meg., etc. £5.10.0. P.P. 2/6.
30,000 Ω/VOLT 0/1/1/2/10/25/100/250/500/1,000 v. D.C. and A.C. 0/50uA/5/50/500 mA/0/12/ amp. D.C. 0/60K/6 meg./60 meg., etc. £8.17.8. Post paid.
50,000 Ω/VOLT 0/10/50/250/500, 000 v. D.C. and A.C. 0/25uA/2.5/25/250mA D.C. 0/10K/100K/1 meg./10 meg., etc. £7.10.0. P.P. 2/6.
100,000 Ω/VOLT 5/2.5/10/50/250/500/1,000 v. D.C. 2.5/10/50/500 mA. A.C. 10/25uA/2.5/25/250 mA/10 amp. D.C. 20K/200K/2 meg./20 meg. ohm, etc. £6.18.6. Post paid.

Hours of Business: 3 LISLE STREET, 9 a.m.—6 p.m. Half Day Saturday
34 LISLE STREET, 9 a.m.—6 p.m. Half Day Thursday

MARCONI CR100/8 RECEIVERS BRAND NEW

Packed in original transit cases and complete with handbook/manual. 60 Kc/s to 30 Mc/s. 200/250 volt A.C. operation. Tested before despatch.

£35 Carriage £2.

A few CR.100 receivers available in good used condition. £21 Carr. £2.

COLLARO/MAGNAVOX STUDIO TAPE DECKS

Latest 1963 model. Fitted with latest bradmatic heads and interlock button. Brand new, guaranteed, with instructions and fittings. £10.10.0 Carr. 5/-.

MINE DETECTOR NO. 4A

Will detect all types of metals. Fully portable. Complete with instructions, 39/8 each. Carr. 10/- Battery 8/6 extra.

OSCILLOSCOPES

All guaranteed perfect working order.
COSSOR 1035 £45
SOLARTRON D.300 £20
SOLARTRON CT.316 £75
SOLARTRON CD.518 £75
SOLARTRON C.D.568 £75
E.M.L. W.M.5 £100
E.M.L. W.M.8 £110
Carriage extra.

L.T. METAL RECTIFIERS

All full wave, bridge connected. Brand new.
12/18v.1.5A. 3/9 24/36v. 6A. 27/8
12/18v.2.5A. 6/3 24/36v. 15A. 45/-
12/18v. 4A. 9/4 36/48v. 2A. 19/8
12/18v. 6A. 12/3 36/48v. 4A. 29/8
12/18v. 10A. 22/6 36/48v. 6A. 32/6
12/18v. 15A. 37/6 48/60v. 2A. 21/-
24/36v. 1A. 7/3 48/60v. 10A. 52/6
24/36v. 2A. 13/6
Please add postage.

L.T. TRANSFORMERS

All primaries tapped 200/250 volts
1 Battery Charging, 3.5, 9 or 17 volt, 1 amp., 9/9. Ditto 2 amp., 14/3. Ditto 4 amp., 1/6. 9 or 17 volt, 6 amp. 26/-.
2 Model Type 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 volt, 2 amp. 18/6. Ditto 4 amp., 30/-. Ditto 5 amp., 37/6. Add Postage.


MINIATURE MODEL ACCUMULATORS

Lead Acid, BRAND NEW, 7/6. 1.5 A.H., 4 x 1 1/2 x 1 1/2 in. Hb. 5/6. P.P. 1/3. 12v. 0.75 A.H., 4 x 3 x 1 1/2 in. 21b., 15/6. P.P. 1/6.

MINIATURE PANEL METERS

For 1 1/2 in. dia. panel hole.
0-50uA 39/6 0-1 mA 27/6
0-500uA 32/6 0-5 mA 27/6
0-300 v. D.C. 27/6
"S" meter 35/-

TWIN MOTOR BARGAIN

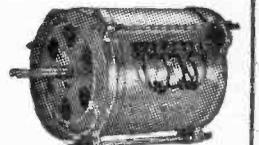

200/250 volt A.C. Twin concentric spindles operated independently. Either motor reversible. 1440 r.p.m. Brand New, Boxed. Only 12/6 each. P. & P. 2/6.

CW SMITH & CO (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

RECEIVERS & COMPONENTS

TRANSISTORS now half-price. Unmarked but tested packets of 16; unmarked untested packets of 40; duds suitable as diodes packets of 80. All packets 10/- each, postage 1/-. Four packets post free. C.W.O. K. R. WHISTON (Dept. PWT), New Mills, Stockport.

SPEAKER REPAIRS. Cones/Fields fitted. Clock coils wound. L. S. REPAIRS, Pluckley Ashford, Kent.

NEW VALVES! GUARANTEED!

EBP80	7/6	EY51	6/6	PL81	7/9
EBP89	7/6	EY86	6/6	PY33	10/9
ECC81	4/3	EZ40	8/-	PY81	8/-
ECC82	4/9	EZ80	5/6	PY82	5/6
ECC83	6/3	PC84	6/3	U25	9/9
ECL80	5/9	PC89	8/-	UCC85	6/9
ECL82	7/9	PCF80	6/3	UCH2	8/3
EF89	4/5	PCF89	6/9	UCH81	7/8
EF85	5/-	PCL83	9/-	UY85	5/9
EF86	6/9	PLC84	5/9	BW86	7/6
EL84	6/-	PL36	9/3	6X4	4/3

Postage 6d. per valve extra. S.A.E. for full lists and discounts.

LEWIS ELECTRONICS

16 GLENWOOD GARDENS, GANTS HILL, ILFORD, ESSEX. Telephone: Crescent 5685.

DIRECT TV REPLACEMENTS LTD., largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. S.A.E. for quotes. Day and Night Telephone GIPSY Hill 6166. 126 Hamilton Road, West Norwood, SE27.

EX-GOVERNMENT AMPLIFIERS. 1,155 Receiver, many Valves, Microphones, 500V Megger, etc. Phone: ONE 6105 after 7 p.m.

Glasgow Electronic Services

21 OLD DUMBARTON ROAD, GLASGOW, G3 Telephone: WEST 2642

SINGAL LAMP HOLDERS: Adjustable bracket type, panel mounting, takes M85 Bulbs. For panels up to 1 1/2in. thick. Red, Green, Amber or Clear, 1/10. **PANEL ENCLOSED HOLDERS:** Totally enclosed, front or rear access to bulb. M85 bulbs. Red, Green, Amber, Blue or Clear. For panels up to 2 1/2in. thick. Chrome metal parts. 5/4. **MINIATURE PANEL ENCLOSED HOLDERS:** As above but smaller, takes LES bulbs. 3/6. **PANEL NEON INDICATORS:** Self-contained resistor for direct mains operation. Mounted body. Red only, push fitting, 4/-; **MINIATURE NEONS:** Wire ended long life neon suitable direct wiring into equipment with appropriate series resistor. (270K for Mains), 2/-. **PILOT BULBS:** Lilliput type. 6.5V 1W or 12V 1/4 75W. 1/7. Standard Round M85 types, first grade bulbs, as follows at 8d. ea.—2.5V 2A, 3.5V 1.5A, 3.5V 3A, 4.5V 3A, 5V 1.5A, 6V 1.5A, 6V 1.15A, 6.5V 1.5A, 6.5V 3A, 6.5V 4.5A, 8V 1.5A, 8V 3A, 12V 1A, 12V 2.2W. Also available 20V 1A and 24V 2W at 17/-; **FUSE HOLDERS:** Panel mounting, for 1 1/4in. Fuses. Moulded body, 4/-; Miniature type, for 1/4in. Fuses, also 4/-; **MULTICORE CABLE:** Standard types: 71,0076 conductors covered by .02in. P.V.C. Whole tinned copper braided and P.V.C. sheathed overall. Cores individually coloured. 4-way 2/-, 8-way 2/7, 12-way 3/6, 20-way 4/6, all per yard. Miniature type 71,004 conductors covered .01in. P.V.C., otherwise similar to above; 4-way 1/10, 6-way 2/3, 12-way 3/-, all per yard. **MICRO SWITCHES:** Small reliable switches. SPDT contacts, rated 5A 250V A.C. Button type, 8/-; Lever type, 6/9, 80 OHM CO-AX CABLE: 1/6 per yard post paid.

Send for our latest list—6d. post paid.

Terms of Business: Cash with Order; C.O.D. 3/- extra. Postage extra, unless otherwise stated, under £3 total value.

RATES: 7/3 per line or part thereof, average five words to line, minimum 2 lines. Box No. 11 extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.


RECEIVERS & COMPONENTS

(continued)

A1 POST-FREE BARGAINS. Guaranteed Secondhand set Tested Valves: EF80, EB91, 10F1 9d. each, 3 for 1/6; L63 2/-; ECL80 2/6, 3 for 6/-; PZ30, PY81, EL38, PL33 3/6; PL83, PL82, PY80, PY82, PCF80 4/-; KT 36, N37, B36, PY31, U281, U282, 20P1, 27SU 4/6; EB41, EBC41, ECC81, ECC82, EL42, PL21, U31, UB41, UF41, UF42, UL41, UL44, UL46, UY41, 6C13, 10C2, 6L20, 20L1 5/-; 30P4, 53KU, EL33, PL36, U07 7/-; Thousands of Valves in stock, including obsolete types. Ex-Service, reclaimed and all new E.V.A. types and makes. **A1 RADIO COMPONENTS.** 14 The Borough, Canterbury, Kent.

EXCEPTIONAL VALUE: Picture Tubes, brand new. Mazda 19in., CME1901, Mullard 19in., AW47-80/91, £6/10/-; Mullard 23in., AW59/91, £8/10/-; carriage (insured) paid, 12 months guarantee. Note: All brand new. We also supply most other sizes completely regunned at £4/17/6, guaranteed 12 months. TOMLINS, 156 Lewisham Way, New Cross, SE14. TID 3857.

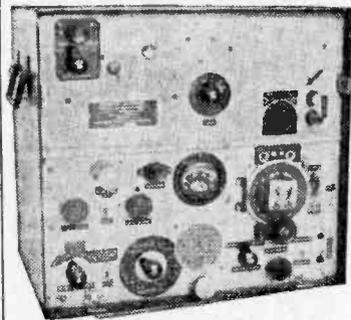MARCONI CANADIAN RECEIVER No. 52 (Brand New)



AMATEUR SHIPPING BROADCAST Magnificent Hi Valv Receiver. 3 wave band 1.75-16Mc/s. (19-170 metres), with 3 valve Xtal calibrator, speaker and phone outputs, complete for 230/240 AC mains or 12V DC. Fully tested before dispatch. **BRAND NEW 212 19in. Carr. £1.** W.S. No. 19 Mk. 3 T.R.C. 2-8Mc/s. with economy power pack 12/24V DC. Excellent condition, 80/-, carr. 25/-; Set only 55/-, carr. 19/-, all parts available. **COMMAND RECEIVERS.** BC454-B (3-6Mc/s.), BC455-B (6-9.1Mc/s.) each at 90/-, post 5/-; **BRAND NEW.** **ROTARY TRANSFORMERS.** 12V DC input, 300V, 120mA output, note size only 4 1/2 in., 15/-, post 2/6. **MOVING COIL H/phones, BRAND NEW.** Chamois padded with lead and jack plus. 15/6, post 2/-; **SET OF VALVES** for 52 receiver, 13 in all with vibrator, 12/6, post 2/8. Ditto for No. 19 set including 807, 92/6, post 2/6. **HRO POWER PACKS.** 115/250V AC. 25/-, NEW 35/-, post 5/-; Many other bargains. List 6d. Stamp inquiries.

A. J. THOMPSON
"TELLING LODGE"
CODICOTE, HITCHIN, HERTS.
Phone: Codicote 242.

RECEIVERS & COMPONENTS

(continued)

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.** Dept. PW7/9, 126 Hamilton Road, West Norwood. SE27. GIPSY Hill 6166.

RECEIVERS

MARCONI B28/CR100. Good working order and condition. £18.10.0, carriage 1/.

R1132, 100 to 120 Mc/s. 10 valve superhet, ideal for "Satelite" reception on 108 Mc/s. Good, clean condition, £4.10.0, carr. 12/6.

CANADIAN MARCONI 52. Tested and working, £5.10.0, carriage 1/.

Power Unit ZEI1, for above, £2, carr. 10/-; **VHF Superhet.** Ex-Police, approx. 80 to 90 Mc/s, built-in power unit and 6in. speaker. £3 ONLY, carriage paid. No circuit available.

G.W.M. RADIO LIMITED

40/42 PORTLAND ROAD WORTHING, SUSSEX.


"TELECOMM" v.h.f.-a.m. Monitor Receivers, fully transistorised. Type TVR, weight 3lbs. Two models 80/90Mc/s also 80/100Mc/s. Brand new, £30. **RADIO COMMUNICATIONS COMPANY,** Crewkerne, Somerset.

RESTORERS. brand new assorted values wattages, 3/6 50, 5/6 100, 50/- 1,000. Post paid. **BROAD (RADIO ENGINEER),** The Haven, Stodmarsh Road, Canterbury, Kent.

DATA TRANSISTOR POCKET KITS

NO SOLDERING OR DRILLING, COMPLETELY SELF CONTAINED

NO AERIAL REQUIRED - MEDIUM & LONG WAVE - ASSEMBLY TOOL PROVIDED - CAN BE BUILT BY ANYONE

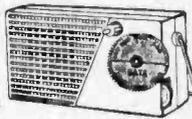

DATA 55
5 SEMI-CONDUCTORS
3 STAGES
MOVING COIL SPEAKER
50/- P.P. 2/9 extra.
Battery 2/3 extra.

DATA 427. 4 TRANSISTORS, 2 DIODES, 7 STAGES, MOVING COIL SPEAKER
65/- P.P. 2/9 extra.
Battery 2/3 extra.


All Parts Supplied Separately

"DATROLA" transistor ELECTRONIC ORGAN 2 octave. Complete and ready to play, with instructions and music. size 1 1/4 x 3 1/4.

£5.19.6 post free.

DATA ELECTRONICS LTD.
6 HILLSIDE GDNS., EDGWARE, Middlesex

FOR SALE
(continued)

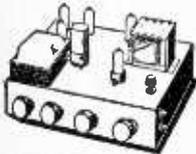**GUITAR AMPLIFIERS
WITH TREMOLO**


Hi Fi 15 watts. Valves ECC83, ECC83, ECF82, EL84, EL84, E281. Four jack inputs. Six controls: two volume, bass, treble, tremolo speed, depth. Remote plug, 3 and 15 ohm outputs. Real value. Kit £8, ready built £11. Similar 30 watt. Valves ECC83, ECC83, ECF82, EL84, EL84, E281. Kit £11, ready built £14. Similar twin input less tremolo 15 watt (illus.). Kit £6.10.0, ready built £9. 30 watt, Kit £9.10.0, ready built £12.

Add carr. 7/6 any amplifier.
Send for free leaflet.

STROUD AUDIO
Bath Road, Stroud, Glos.

250 "12-DRAWER UNITS" New, ex-works. £4/15/-, carriage paid (mainland). Each drawer 5 1/2 in. wide, 3 in. high, 10 1/2 in. long. Stove enamelled green, heavy gauge perfect steel. 12 dividers free. Catalogue free. (Dept. Z4), N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs.

240W ELECTRIC POWER ANYWHERE
ANYTIME from 12V CAR BATTERY
AMERICAN DYNAMOTOR UNIT
Input 12v, output 200/250w at 150 to 220 volts.
Perfect for TELEVISION, POWER TOOLS and all
national AC/DC ELECTRICAL EQUIPMENT, gives
wonderful results. Price ONLY £8 + car. carriage.
Send stamped envelope for full illustrated details
to SCIENTIFIC PRODUCTS, CLEVELY, Lancs.

**FANTASTIC
SUMMER OFFER!**

**ELECTRIC
SOLDERING IRON**

Lightweight but robust, firm Pistol Grip handle. 240 v. A.C. Solid copper bit. Complete with 4ft. twin flex lead and 2-pin plug. Indispensable for every home handyman. A boon to model makers and a necessity for every wireless enthusiast. Offered to you at this new amazing price.

ONLY
9/6
P. & P. U.

C. H. SERVICE, Dept. P.W.
Lusted Hall Lane, Tatsfield, Kent.

WANTED
**WANTED
VALVES ONLY**

Must be new and boxed
Payment by return.

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WANTED
(continued)

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. R.H.S., Beverly House, Manville Terrace, Bradford 7.

WANTED: TEST GEAR, Meters, Valves, Components, Communication Sets, Amplifiers. Letters only. HUG-GETT'S LTD., 2-4 Pawson's Road, West Croydon, Surrey.

WANTED: NEW VALVES and Transistors, any quantity. S. N. WILLETS, 43 Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

NEW VALVES WANTED

Any type, any quantity

CASH PAID

R.S.T. Valve Mail Order Co.,
211A Streatham Road
Mitcham, Surrey
Telephone: MITCHAM 6202

MISCELLANEOUS

KITS BUILT, repairs, alignment. S.A.E. Leaflet for details. KINDER, 6 Hooker Road, Heartsease, Norwich, Norfolk.

YOUR KIT—Amplifier, Radio, etc., professionally assembled, wired, tested. Moderate charges. Prompt attention. Write to M. JOHNSON, Ivy Cottage, Astwood Bk., Redditch.

READY BUILT KITS: Mercury 6 and Contessa £14; Sprite, Pandora 6 gns.; Capri £6/10/-; Good Companions 9 gns. and £10/5/-; "P.W.6" 8 gns.; Scala 7 gns.; Milan £8; guaranteed. Two PP3 type batteries 3/11. List 3d. Quick, post free delivery. M. L. COLTON, 21 Maplewood Dr., B'pool.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 2) Maude Street, Darlington, Durham. Send 2hd. stamp.

AERIALS
**MARCONI COIL AERIAL TUNING
SYSTEM**

Last few of these popular aerial matching units, containing 140ft drum of copper aerial wire and insulators feeding into a tunable matching unit, enabling your TX or RX to work to its best efficiency, originally used for the 52 TX-RX. LAST FEW NOW ONLY 27/6 carr, 5/- 19 SET PARTS, all brand new. J. T. SUPPLY receiver power supply kit, 200-50 mains to 275V d.c. and 12V LT, choke smoothed, lead and connector to set, 45/-, p.p. 5/-. **CONNECTORS** 12-12 pin (long) 8/6, short lead 6/-, 12 pin plug and flex 5/-, 6-6 pin (long) 5/-, 6 pin and flex 3/6, post long 1/6, others 9d. **CONTROL BOX** 6/-. Mk 2 improved date double type 8/6, p.p. 1/6. Mic and Phone headset, 17/6, p.p. 1/6.

J. T. SUPPLY,
Dept. N, 150 MEADOW LANE, LEEDS.

SOUND RECORDINGS

A UNIQUE BUY! Recording Tape, 50p brand, 5 1/2 in., 1,200ft, 19/6; 7 in., 2,400ft D.P. 25/- P. and p. 1/6 per spool. Bargains in all sizes. S.A.E. for list. E. C. KINGSLEY AND CO., 132 Tottenham Court Road, London W1. EUSTON 6500.

SERVICE SHEETS

SERVICE SHEETS, Radio and Television, 3/6, post paid. VEST AND EMERY, 17 Hallgarth Street, Durham.

SERVICE SHEETS, also Current and Obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London, W12. Phone: SHE 8441.

SERVICE SHEETS: Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries, TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS, Radio and TV, 4/- each. List 2/-. All orders dispatched on day received. Also Manuals for sale and hire. List 1/-. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

WHY TOLERATE DELAY when we can supply your Radio or TV Service Sheet by return of post at 4/- each, plus postage. List 2/-. S.A.E. with inquiries, please. Mail orders only to S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

TRADE SERVICE SHEETS offered by retired engineer. If I haven't got it you won't get it. All 4/- each by return. Please include large S.A.E. Mail orders only. ETZIGONI, 50 Merrion Avenue, Stanmore, Middx.

FAULT-FINDING FILES showing common faults that each receiver is prone to and other useful servicing information 2/- each. Mail orders only. S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

S.E.S. Service Sheets for all TV, Radio, including Transistors, Tape Recorders, Echo Units, Amplifiers, Record Players and Autochangers etc. also various domestic appliances. List 1/- S.A.E. Mail order only. SUN ELECTRICAL SERVICES, 38 St. Georges Road, Hastings.

SERVICE SHEETS for all makes of Radio and TV, 1925-1963. Prices from 1/- with free fault-finding guide. S.A.E. enquiries. Catalogue of 6,000 models 1/6. 125 Radio/TV sheets covering many popular models 21/-. Valves, modern and obsolete. Radio/TV books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

METAL WORK

METALWORK. All types cabinets, chassis, racks, etc. to your specifications. PHILPOTT'S METALWORKS LTD., Chapman St., Loughborough.

Cases, Chassis, Frames, etc., anything in metal. Send your drawing for quotation. 'One-offs' with pleasure.

Stove enamelled any professional finish. Steel Shelving, Drawer Units, etc.

Moss Watson

40 MOUNT PLEASANT STREET
OLDHAM, LANCs. MAIN 9400

SITUATIONS VACANT

PUBLIC SCHOOL MAN under 25 required as Trainee for Electronic and or Mechanical Engineering design and development work on machines to make fibreglass products. Starting salary £936. Write giving details of education, interests and experience to **PIBRELITE INDUSTRIES**, Trafford Hall, Chester.

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. **B.I.E.T.** (Dept. 242A), 29 Wright's Lane, London, W8.

TV AND RADIO, A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc., on "No pass—no fee" terms. Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook—free. **B.I.E.T.** (Dept. 242G), 29 Wright's Lane, London, W8.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, G.C.E., etc., brings high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams, and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook—free. **B.I.E.T.** (Dept. 242B), 29 Wright's Lane, London, W8.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES IN MINUTES from that great book "The Principles of TV Receiver Servicing". 10/6 all book houses and radio wholesalers. If not in stock from Secretary, **I.P.R.E.**, 32 Kidmore Road, Caversham, Reading, Berks.

COURSES

CITY AND COUNTY OF BRISTOL EDUCATION COMMITTEE

BRISTOL TECHNICAL COLLEGE

Principal: E. Poole, B.Sc. (Eng.), M.I.Mech.E. N.I.Prod.E.

SCHOOL OF

MARINE RADIO AND RADAR

Senior Lecturer: F. E. Barltrop (ex. A.S.T. Hamble)

MARINE RADIO OFFICERS

A full-time course for prospective Radio Officers in the Merchant Navy, leading to the 2nd and 1st Class P.M.G. Certificates, and the M.O.T. Radar Maintenance Certificate, is provided, and entry may be made in January, May and September of each year.

Fees: Under 18 Years of age: £2 per College year. Over 18 years of age: information from Registrar.

A six-week Course of Pre-Sea Training is also held, and entry is normally on completion of the Radar Course.

For further particulars apply:

Registrar, Bristol Technical College, Ashle Down, Bristol 7. Please quote ref.: PW.

EDUCATIONAL

BECOME "TECHNICALLY QUALIFIED" in your spare time. Guaranteed Diploma and Exam. Home-study Courses in Radio "TV Servicing and Maintenance", R.T.E.B., City and Guilds, etc. Highly informative 120-page Guide — **FREE!** **CHAMBERS COLLEGE** (Dept. 363), 148 Holborn, London EC1.

EDUCATIONAL

(continued)

Radio Television & Electronics

Learn at home with the world's largest home study organisation, **Brit.I.R.E.**; **City & Guilds**; **P.M.G.'s** certs., etc. Also Practical Courses with equipment.

All books supplied.

Write for **FREE** prospectus stating subjects to

I.C.S.

(Dept. 541), Intertext House, Parkgate Road, London, S.W.11

THE Incorporated Practitioners in Radio and Electronics (I.P.R.E.) Ltd. Membership Conditions booklet 1/- Sample copy of **I.P.R.E. Official Journal** 2/- post free. Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

DON'T FUMBLE with Formulae. Master Mathematics quickly and easily the Understandable Way.

1st lesson and details **FREE**

The Dryden School of **UNDERSTANDABLE MATHEMATICS**

11F10 Dryden Chambers, Oxford St., London, W.1.

Name _____
Address _____

RADIO OFFICERS see the world. Immediate sea-going appointments. Our many recent successes provide additional trainee vacancies during 1963. Day and boarding students. Grants and Scholarships available. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

f's MADE

By repairing Radio and TV Sets as a job or as a spare time business. Our practical course will show you the way. No previous experience is required.

SEND FOR FREE BOOK TODAY!

RADIOSTRUCTOR
Dept. G77 READING, BERKS

HAVE YOU EVER SEEN T.V. TROUBLES?

That is "Pin-Point T.V. Troubles in 10 minutes" we mean! Thousands of *Practical Television* readers already own and use "T.V. Troubles" every day. Designed for use by amateur or expert, this amazingly practical manual shows you how to find the trouble in any T.V. circuit FAST!

A simple cross-index tells you where you'll find cause of trouble, handy check charts then help you accurately locate the EXACT trouble spot! You will eliminate hours of aggravation, cut out waste time, because this new Coyne system will help you get right down to the heart of the trouble in minutes.

Over 700 trouble spots are covered in the 340 cross-index pages. Included are 50 time saving check charts as well as 280 diagrams and photos together with explanations of circuits and designs.

YOU CAN USE THIS BOOK RIGHT ON THE JOB—NO NEED TO MEMORIZE!

This Pin-Point Book was designed especially for on-the-job trouble shooting. You simply turn to the indexed section, locate the circuit description and check-charts, and in minutes you have the trouble spot located and ready for repair.

NO COMPLICATED THEORY OR MATHEMATICS. Just practical circuit description, service methods and trouble shooting techniques to help you make faster t.v. repairs.

EVEN AN EXPERT CAN SAVE TIME BY USING "T.V. TROUBLES"

Here is a way to reduce "thinking time". All the logical reasons for each problem are stated in black and white—you use your skill to take it from there!

Don't miss out any longer. Time wasted now locating t.v. faults could be saved by quick reference to this lightning fast t.v. problem answer book. Send for your trial copy now, then when you decide to keep it (as we are sure you will), pay only 5/- per week until completed.

The price? Only 38/6 plus postage.

FREE ELECTRONIC DATA HANDBOOK WITH EVERY ORDER IRONCLAD GUARANTEE

This book must be able to earn you more than its cost within two weeks or your money refunded!

FREE TRIAL OFFER!

TERMS ONLY 5/- PER WEEK!

To **SIM-TECH TECHNICAL BOOKS** Dept. WTTI

West End, Southampton, Hants.

Please send "T.V. Troubles" for a full seven days' free trial. If not delighted I may return the manual, post paid, without further obligation on my part. Otherwise I will pay cash or 5/- weekly until paid. (No extra for interest if paid regularly.)

Tick here if enclosing full price (we pay postage). Same 7-day money back guarantee. Postage charges 1/8 extra. Overseas customers please send full amount (including Ireland).

Name

Address

City..... County.....

FANTASTIC BARGAINS IN BRAND NEW GUARANTEED ELECTROLYTICS

BY FAMOUS BRITISH MAKERS

Every constructor must have first-class electrolytic capacitors to work with. A terrific bulk-purchase by Bear Hudson buyers enables us to offer these by Plessey, T.C.C., Hunts, C.C.L., etc., etc., at less than half price. Two years' guarantee. From 1 mFd to 6000 mFd, 1 to 1000 volts D.C. working. Typical value—8+8 mFd, 500V. D.C., list 12/-, our price 4/6.

Send for list. Orders over 20/- post free. Under, add 6d. for each 5/- for postage.

SPECIAL CONSTRUCTORS PARCEL - £10 VALUE FOR 35/-

In assorted useful values.

Another bargain bombshell from BEAR HUDSON, LTD.

63 GOLDHAWK RD, SHEPHERD'S BUSH, London, W.12
Next to Goldhawk Rd. Stn. Metro. ● Open all day Sat.
Phone: SHE 2581 and 4794

COMMUNICATION RECEIVERS
CR100/SMOD. Covers 60 kc/s-30 Mc/s in 6 bands. 11 valves 2 R.F. and 3 I.F. stages. Crystal gate. B.F.O. etc. Ready for 200/250 volt a.c. mains. 21 watts output for 3Ω speaker. BRAND NEW, in original packing. £35, carr. £2 S.A.E. for illustrated details.
HRO SENIOR RECEIVERS. Complete with 9 coils. £17.10.0. S.A.E. for full details.
PC1-3 RECEIVERS. 3-wave bands, medium wave and 2 short wave, from 120-13 metres. Good condition, tested 8 mos. Carr. 10/- . A.C. mains internal power supply £2 extra.
SILICON RECTIFIERS. Type 1EA2 (1 x 1in.) will handle 250 volts at up to 500 mA. Replaces any TV metal rectifier. 7/6.

MOVING COIL PHONES. Finest quality Canadian with Chamois ear muffs and leather-covered headband. With lead. BRAND NEW 22/6, post 1/6

AVO WIDE RANGE SIGNAL GENERATORS. Six turret operated ranges covering 50 Kc/s to 80 Mc/s. For use on standard A.C. mains. Packed in original transit cases with accessories. Post-war type in new condition. £15. Carriage 10/- . REAL BARGAIN.

RECEPTION SETS R220/R230. Consists of TWO identical receivers in one cabinet. EACH receiver is complete with 14 modern miniature valves (3 x 6AK5, EF91, 3 x EF92, 2 x EB91, 2 x 12AT7, Q570/20, EL91 and 5U4G) its OWN stabilised A.C. mains power supply and speaker. Intended for reception of one fixed frequency between 60-100 Mc/s according to crystal used but ideal for modification to 72 Mc/s or 144 Mc/s. Price complete £7.10.0 (Carr. £1) or individual receivers (less cabinet) £3.19.8 (Carr. 7/6). Circuit supplied.

AR-88 SPARE VALVES. Complete set of BRAND NEW individually boxed original valves (14). 50/- . P. & P. 2/6.

RCA AR-88 SPEAKERS. 3Ω 8in. P.M. speaker in heavy gauge black crackled steel cabinet 11 x 10 x 6in., with rubber feet. A SUPER QUALITY unit. BRAND NEW, for ONLY 65/- . P.&P. 5/-.

AR-88 VIBRATOR PACKS. For 6 v. operation. Complete with vibrator and OZ4 rectifier. BRAND NEW in original cartons, 17/6. P. & P. 5/-.

MULTIMETER SPECIAL MODEL CT-500. 20,000Ω/V. DC volts: 0 to 2.5-10-50-250-500-5,000 (20KΩ/V). AC volts: 0 to 10-50-250-500-1,000 (10KΩ/V). DC Current: 0 to 50μA, 5 mA, 50 mA, 500 mA. RESISTANCE: 0 to 12KΩ, 120Ω, 1.2KΩ, 12MΩ. Mid scale 100, 600, 6K, 60K ohms. Decibels -20 to +22. In neat moulded case 5 1/2 x 3 1/2 x 1 1/2 in., with leather carrying handle, complete with batteries, leads and instructions. BRAND NEW. Fully guaranteed. 95/- . P. & P. 2/6.

CHARLES BRITAIN (RADIO) LTD.
11 UPPER SAINT MARTINS LANE, LONDON, W.C.2
TEMPle Bar 0545
Shop Hours 9-6 p.m. (9-1 p.m. Thursday).
Open all day Saturday.

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 .. Set of 4 for 17/-
DAF96, DF96, DK96, DL96 4 for 25/6

1A7GT 9/-	6U4GT 9/9	185BT 19/6	ECC85 7/3	MU14 5/6	U52 4/3
1D5 7/6	6V6G 3/11	AC7/TH1 19/8	ECC89 7/1	MX40 13/6	U78 7/1
1HSGT 8/6	6V8GT 6/6	AZ1 7/6	ECC82 7/9	N18 7/1	U191 11/-
1NSGT 8/6	6A4 4/1	B38 5/1	ECH35 6/6	N37 10/-	U281 9/6
1R5 5/-	6X5GT 6/9	CB11 12/-	ECH42 8/3	PC95 9/-	U282 14/6
1S5 4/4	6J30L2 8/6	CL33 9/6	ECH81 6/9	PC97 8/6	U291 9/-
1T4 3/9	7B7 8/-	CY1 12/8	ECL80 6/3	PC94 8/6	U301 12/6
3A5 5/9	7C5 7/9	CY31 5/9	ECL82 7/9	PCC85 7/6	U801 5/1
3A4 5/9	7C6 7/8	DAC32 8/6	ECL86 9/-	PCC89 8/-	UAB80 5/9
3S4 5/9	7H7 5/9	DAF91 4/-	EF2A 6/-	PCF80 5/9	UAF42 8/-
3V4 5/9	7S7 9/-	DAF96 6/6	EF39 3/9	PCF82 6/9	UBC41 6/11
5U4G 4/6	7Y4 8/-	DFC90 6/9	EF49 11/-	PCF86 8/-	UBP80 7/9
5V4G 3/1	10C1 9/6	DF33 8/9	EF41 7/3	PCL82 7/3	UBF89 7/3
6Y3GT 5/1	10C2 13/-	DF91 3/-	EF42 5/9	PCL83 9/-	UBL21 13/6
524G 8/9	10LD11 10/9	DF96 6/6	EF80 4/3	PCL84 5/-	UC92 7/6
6AL5 2/1	12A76 4/9	DH76 4/3	EF85 5/9	PCL85 8/6	UC84 9/9
6AM6 3/3	12A77 4/3	DH77 4/9	EF86 6/9	PEN43 11/6	UCF90 7/6
6AC5 6/9	12A78 4/3	DK32 9/-	EF89 4/6	PEN36C 8/-	UCH42 10/3
6AT6 4/9	12AX7 4/8	DK91 5/-	EF91 3/3	PL38 8/9	UCH81 7/6
6BA6 5/3	12K7GT 4/3	DK92 6/9	EF92 2/6	PL81 7/6	UCL82 8/9
6BE6 5/3	12K8GT 8/9	DK96 7/-	EF194 8/6	PL82 5/6	UCL83 7/8
6BG6 13/6	12K9GT 4/3	DL33 7/3	EL33 7/6	PL83 5/6	UCF83 10/3
6BH6 6/9	12Z3 8/6	DL35 6/9	EL41 7/9	PL84 6/9	UF41 7/3
6B76 5/6	14S7 14/6	DL92 5/-	EL42 8/6	PX4 9/-	UF89 6/3
6CD6G 28/6	19BG6G 13/6	DL94 5/9	EL84 5/6	PX25 8/6	UL41 7/9
6F1 9/6	20L1 15/-	DL96 6/6	EM34 7/3	PX32 9/-	UL44 10/6
6F13 9/6	20P4 14/9	EABC30 7/3	EM39 6/9	PY33 9/6	UL46 9/6
6F14 9/6	20P5 14/9	EAF42 8/-	EM81 7/9	PY80 5/9	UL84 6/3
6F23 9/6	25L6GT 6/-	EB91 2/-	EM84 8/3	PY81 5/9	UR1C 7/3
6K7G 1/6	25U4GT 10/6	EBC33 5/-	EM85 8/3	PY82 5/9	UU7 8/6
6K7GT 4/3	27S1 17/6	EBC41 7/3	EM87 9/6	PY83 6/8	UY21 11/-
6K8G 4/3	30FL1 10/-	EBF30 7/3	EV31 6/-	R16 4/1	UY41 5/6
6K9GT 7/6	30L15 10/3	EBF89 6/9	EY86 6/-	TH2C 12/6	UY85 4/9
6L6G 6/6	30PL1 10/-	EBL21 9/3	EZ40 6/-	TH233 18/-	VP4B 9/6
6LD20 5/6	30PL13 10/6	ECC40 7/8	EZ41 7/8	U22 8/-	VP41 5/-
6P25 8/6	35A5 14/8	ECC81 4/3	EZ80 4/6	U24 13/-	W76 4/4
6Q7G 4/9	35L6GT 7/9	ECC82 4/9	EZ81 4/6	U25 9/-	W77 2/6
6Q7GT 7/9	35Z4GT 4/11	ECC83 7/-	KT32 5/6	U26 8/-	W79 14/-
6SL7GT 5/9	50L6GT 7/-	ECC84 6/3	KT61 7/6	U50 4/6	Z77 3/3

READERS RADIO
24 COLBERG PLACE, STAMFORD HILL
LONDON N.16 STA. 4587

LEARN ELECTRONICS BY BUILDING

by J. Schroeder.

EASY-TO-BUILD PROJECTS
Chassis for experiments no-tube no-battery receiver. 2 and 4 transistor amplifiers. 2-tube broadcast and shortwave receiver. All-transistor short-wave receiver. 3 transistor pocket radio. Simple stereo amplifier. Antennas and lightning arresters. 1 long-wave and short-wave coils.
Postage 1/-.

WIRELESS SERVICING MANUAL by W. T. Cocking. New 10th Ed. 25/- . Postage 1/3.
PIN-POINT TRANSISTOR TROUBLES IN 12 MINUTES, by L. E. Garner Jr. 47/6. Postage 1/3.
ELEMENTARY ECONOMUNICATORS EXAMINATION GUIDE, by W. T. Perkins. 17/6. Postage 9d.
RADIO VALVE DATA, 7th Ed. Compiled by "WW". 6/- . Postage 10d
THE AMATEUR RADIO HANDBOOK, an R.S.G.B. Pub. 34/- . Postage 2/- .
UNDERSTANDING AMATEUR RADIO, by A.R.R.L. 18/- . Postage 1/3.

NEW 1963 CATALOGUE 1/-.
THE MODERN BOOK CO.
BRITAIN'S LARGEST STOCKIST of British and American Technical Books
19-21 PRAED STREET
LONDON, W.2
Phone: PADdington 4185
Open 6 days 9-6 p.m.

Post 6d. per valve extra.
Any Parcel Insured Against Damage in Transit. 6d. extra.
Any C.O.D. Parcel 4/3 extra.

D. & B. TELEVISION

(WIMBLEDON) LIMITED. PHONE: CHE 3955

131 & 131a, KINGSTON ROAD,
SOUTH WIMBLEDON, LONDON, S.W.19.

"COMPARE OUR PRICES WITH ANY OTHERS"

For the FINEST SERVICE in the COUNTRY. We are open from 9 a.m. to 6 p.m.—1 p.m. on WEDNESDAYS. For any information or problems you have, call or phone, we are always pleased to help.

LINE OUTPUT TRANSFORMERS AND SCAN COIL SPECIALISTS

ALL TYPES IN STOCK. See Previous Lists or send S.A.E. Enquiries.

FERGUSON 992—994—996—998 L.O.P.T.s. BRAND NEW 27/6 each. P.P. 3/-.
FYE SCAN COILS and L.O.P.T.s. V4, VI4, V7, VI7. Used part in perfect working order 25/- each. P.P. 3/6.

90° SCAN COILS BRAND NEW, 12/6 per pair. P.P. 3/-.

110° SCAN COILS, 15/- per pair. P.P. 3/-.

MISCELLANEOUS SURPLUS L.O.P.T.s. NEW £1.0.0 each. P.P. 3/-.

FIREBALL TURRET TUNERS. 38 Mc/s. Ex. Equipment. Perfect, 25/- each. P.P. 3/-.

CYLDON AND BRAY HEAD TURRET TUNERS, 38 Mc/s. 10/- each. P.P. 3/-.

SURPLUS AND SECONDS C.R. TUBES 12in. 25/-, 14in. 45/-, 17in. 65/-. All Guaranteed. Carriage 25/- extra.

MAINS DROPPERS, modern flat type, 1/8 each. P.P. 6d.

SURPLUS MAINS DROPPERS. ROUND, 100 ohms, 420 ohms, 110 ohms. Tapped 200 V., 234 V., 250 V. (Brand New) 1/8 each. P.P. 3d.

EDGE TYPE PRE-SET POTS. 500 K., 1 meg., 100 K., 250 K., 2 meg., 5d. each. Unused. P.P. 3d.

38 Mc/s. NEW CHANNEL COILS, 1/8 pair, most channels.

VALVES CHEAPEST IN THE COUNTRY, SEND FOR LISTS, S.A.E. PLEASE

GLASS RADIO DIALS. Long and Medium Wave. 1/8 each. P.P. 9d.

RADIO DIALS, V.H.F. PERSPEX Volume Tone Tuning, suitable for car radios (new), 1/- each. P.P. 6d.

RADIO DIALS. Long and Medium Wave. Approx. 2 1/2 in. diameter. Printed Black/Red on Gold. 6d. each. P.P. 3d.

PERSPEX DIALS. Direct Drive Type. Black/Red on Gold. 1/8 each. P.P. 3d.

OO-AXIAL SOCKETS ON PANEL. NEW. 6d. each. P.P. 3d.

M.E.S. NEW DIAL LAMP HOLDERS. 3d. each.

E.H.T. LEADS, complete with Cavity Clip, 6d. each. P.P. 3d.

SLOW MOTION INDICATOR SPRINGS. 1/- each. P.P. 3d.

TAG STRIPS (17). 6d. each.

WE CAN ALSO SUPPLY ALL TYPES OF NEW AND USED L.O.P.T.s. SCAN COILS AND T.V. SPARES FOR ALL MAKES AND MODELS. SEND S.A.E. FOR YOUR REQUIREMENTS FOR RETURN POST QUOTATION.

TRANSISTOR RADIO CABINETS. Two/Tone. Very attractive. 2 sizes, 5 1/2 x 3 1/2 x 1 1/2 in. or 5 1/2 x 3 1/2 x 1 1/2 in., will take 2 1/2 x 3 in. Speakers. ONLY 6/8 each. P.P. 2/-.

RADIO CABINETS. Finished in Grey covering, 13 x 7 1/2 x 6 in. Very smart, 10/- each. P.P. 4/-.

REPLACEMENT RECORD PLAYER MOTORS. Tapped. 200V., 230V., 250V., 12/6 each. P.P. 3/-.

SERVICE SHEETS

Although we are new in this field, we can now supply almost any service sheet from stock. And if not we will get it for you. Radio and T.V. 4/- each. P.P. 3d.

THESE AND MANY MORE BARGAINS ALWAYS AVAILABLE.

CALLERS ALWAYS WELCOME.

WE ARE PLEASED TO ASSIST WITH ALL YOUR PROBLEMS!

NOTHING IS TOO MUCH. IF WE HAVE NOT GOT WHAT YOU WANT, WE'LL DO OUR BEST TO GET IT.

TERMS: S.A.E., ALL ENQUIRIES C.W.O. C.O.D. 5/- EXTRA.

POSTAGE ON VALVES 6d. EACH.

SATISFACTION ASSURED.

RETURN POST SERVICE (SUBJECT TO STOCK),

AN AEI PRODUCT



6 ft. flexible lead
with cordgrip

Will give a lifetime
of service

Heats up from cold
in 2 1/2 mins

25 watt model
for radio work

Heat concentrated
in bit

Anatomy of a Superior Soldering Iron

The Solon range of electric soldering irons includes 15 and 25 watt models for radio, TV and electronic equipment; 65 watt models for household and workshop use. Larger models up to 240 watt also available.

Select a

SOLON

TRADE MARK

Used in industry for over 30 years
Obtainable from your usual radio or electrical supplier

ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses.
 12 volt 36 watt AC/DC SHC 6/6. P. & P. 1/-.
 12 volt 60 watt AC/DC SHC 8/6. P. & P. 1/-.
 Transformer to suit the above: Input 200-240 A.C. Output 12 Volt A.C. 36 watt, 16/8. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 60 watt, 22/6. P. & P. 3/6.

Set of 4 colours **FLUORESCENT Paint**. Red, Orange, Green and Blue in 1 oz. tins. Ideal for use with the above Ultra Violet Bulbs. 9/6. P. & P. 1/8.

BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P.

NSP2 CV2296 STROBOTRON FLASH-TUBE made by Ferranti, brand new, I.O. base. Price 15/-. P. & P. 1/-.

MAGNETIC TONES 10 IMPULSES PER SECOND

Very latest **High Speed type** ex P.O. guaranteed perfect, type No. 100B, coil 2,300 ohms, for 48 volt D.C. operation (will work on 36 volt), overall size 4 1/2" x 1 1/2". Also available, type 101A which can be used as an interesting accessory with our Strobe unit. Either type price 15/-. P. & P. 1/6.



VARIABLE VOLTAGE TRANSFORMER

Input 230 v. A.C. Output 0-250 v. at 2.5 amp. Fully shielded. New. £5.19.6. inc. carriage. Also available from stock, 5, 8, 10 and 20 amp. Write for details.



4,000 Ohm Headphones, brand new (imported), 12/6 each pair. P. & P. 1/6.

SIEMENS H.S. RELAY. Very latest type, sealed. H96E. 1,700 ohms plus 1,700 ohms, single C/O contacts. Price 16/6 each, plus 1/- P. & P.

6 VOLT 40 A.H. ACCUMULATOR, in metal case with leather carrying handle. New. Price 27/6, carriage 8/-.

500 MICROAMP SUB-MINIATURE M/C METER, 1 1/4" diameter, flush mounting, single hole fixing. Sealed 0-1 mA. Supplied with resistor for use as IMA if required. 29/6 plus 1/- P. & P.

230 VOLT A.C. GEARED MOTORS
 Type B16G 80 r.p.m., 26 lb. inch. £1-19.6. P. & P. 2/-. Type D16G 5 r.p.m., 1.7 lb. inch. £2-9.6. P. & P. 2/6. Type D16G, 13 r.p.m., 1.45 lb. inch. £2-12.6. P. & P. 2/6.

LIGHT SENSITIVE SWITCH

Kit of parts including ORP .12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. Additional ORP.12, 8/6 each plus 1/- P. & P. (Resret not supplied separately.)

AVO METER MODEL 7. Individually tested on all ranges and guaranteed. Inclusive of Test leads, £11.0.0. P. & P. 5/-.

MINIATURE LEAD ACID ACCUMULATORS (Brand New). 2V, 1.5 A.H. Size 4 x 1 1/4 x 1 1/4. Wt. approx. 1 lb. 16/6 for 3. P. & P. 1/6. 12V, 0.75 A.H. Size 4 x 3 x 1 1/4. Wt. approx. 2 lb. (can be used as double 6V). 15/6 each. P. & P. 1/6.

TRANSISTORS

OC30	10/-	OC75	7/-	Get 114	5/-
OC41	7/-	OC78	6/-	Get 573	12/6
OC45	5/-	OC77	9/-	Get 573	25/-
OC45	9/-	OC139	12/-	M/Pair	
M/Pair		OC170	9/8	1N135A	4/-
OC71	5/-	OC71	10/8	2N458	20/-
OC72	7/-	OC200	10/8	2S005	30/-
OC72	14/-	OC201	21/-	2S013	100/-
M/Pair		Get 104	6/-	SB455	7/8
OC73	6/-	Get 105	10/-	TK20B	4/-

SERVICE TRADING CO.

All Mail Orders also callers.

47-49 High Street, Kingston on Thames
 Tel: KINGSTON 9450

Personal callers only

9 Little Newington Street, London W.C.2
 (off Leicester Square)
 Tel: GERrard 0578.

RADIO BOOKS
BASIC ELECTRICITY
ELECTRONICS

TESTED SHORT WAVE RECEIVER
 CIRCUITS USING M.A.T.S. 5/6
 TESTED SHORT WAVE SUPERHET
 RECEIVER CIRCUITS USING MICRO-
 ALLOY TRANSISTORS. 6/6
 22 TESTED Circuits using

Micro Alloy Transistors 5/6
 AT A GLANCE Valve and T.V. Tube equivalents 4/-

BRITISH Transistor Directory 9/-
 OSCILLOSCOPE Book 5/6
 USING an Oscilloscope 7/-

OSCILLOSCOPE Equipment 5/6
 MULLARD Transistor Radios 5/6
 MULLARD Ref. Transistor Circuits. 13/6

EXTRA Equipment Tape Recorder 6/6
 COIL Design and Construction 5/6
 TRANSISTOR Audio Amplifiers 6/8

TRANSISTOR Circuits for Radio Control Models 8/-
 BOY'S Book of Crystal Sets 3/-
 SERVICING Transistor Receivers 8/-

ELECTRONIC Novelties 5/6
 ELECTRONIC Gadgets 5/6
 RADIO Valve Data "Wireless World" 7/-

REGINN'S Guide to Radio 8/6
 MODERN Transistor Circuits for Beginners 8/-

TRANSISTOR Test Equipment 4/-
 TRANSISTOR Circuits for the Constructor (Bradley) Nos. 1, 2, 3 and 44/- each

All books include postage. List S.A.E.

SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY KENT. Tel. HURstway 1818

PADGETTS RADIO STORES

OLD TOWN HALL,
 KNOWLER HILL,
 LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

ARMY SET TYPE 19 MK. 3. Complete with one 6K8 valve, four 6K7, one 6B8G and one 6V6. The Receiver side of the set is complete in every way including the 500 micro-amp. meter. The valves and a few parts in the "B" set have been removed.

The set is very clean inside but the outer case is soiled. We are offering a first class receiver at the special price of 32/-. carr. 10/-, two for 60/-, carr. 15/- . Set less Valves 12/-, carr. 7/-.

Valves Removed from TV Sets. Tested on Mullard Valve Tester, and are 100% as new. Three months unconditional guarantee. POST FREE.

ECL80	2/-	10C2	5/-	PY80	5/-
ECC82	5/-	10F1	1/-	PY81	4/-
EY51	2/6	10P13	5/-	PZ30	5/-
EBF90	4/6	10P14	5/-	PZ30	4/6
EB91	9/4.	20D1	3/-	PCF30	4/6
EP91	9/4.	20P1	5/-	PCC84	4/6
GSN7	2/9	20L1	5/-	EAC91	1/6
6F1	1/-	185BT	8/6	PL83	5/-
6F13	2/-	U2B1	5/-	PL33	4/4
6F14	5/-	U2B2	5/-	13K3	4/4
6F15	5/-	U229	5/-	N37	5/-
6LD20	5/-	KT36	5/-	GJ5	3/-
PCL82	6/-	PL81	5/-	U801	6/6
		PL82	5/-	U12	4/-

EP80 1/6 or 10/- per doz. Grade 2 EF80 for test purposes. 4/- doz.

New Valves Ex. Units. POST FREE.

ARP12 1/6, 6/ for 5/6, box of 50 20/-, 174 9/-, AR30 2/-, ART22 2/-, APTV 2/-, APP37 2/-, 6K7 2/-, 6K8 4/-, 5U4 3/-, 6SN7 3/-, 6V6 3/-, 6V6GT 4/6, VR150/30 2/6, 6C4 2/-, EL91 1/9, EP91 1/9, EF50 1/-, 6/- doz., 6F6 2/6, 5Z4 5/6, 6X5 4/8.

P.M. Speakers. Removed from TV Sets. All perfect condition. Rola and Plessey, 8 x 4in., 5/-; Goodman and 8 and 7 x 4in., 6/-; Rola and R. and A. 6in. round, 3/6; 6in. Shid. round, 5/-; 8in. round, 6/- . Post on any speaker, 2/-.

TV Tubes Picture Tested. Reclaimed from TV Sets. 12in. 17/-, 14in. 30/- . Carr. 7/6. 12 months unconditional guarantee. **TYPE 46 SET** complete with valves, less coils, crystals, and send-receive switch, but otherwise complete in new condition. 8/8. Grade two 4/8. Post 3/9.

Mixed Mains Droppers. Removed from TV chassis. 10/- per doz. Post free.

New Boxed 12 Volt Vibrator Power Pack with spare vibrator and leads. 13/6. Carr 6/-.


Tube unit complete with meter and VCR138 tube and valves 38/6. Carriage 10/-.

Lewis have the Cabinet for you

We can supply any cabinet to your own specification

This is only one example of—
THE LARGEST RANGE OF CABINETS IN THE COUNTRY

Equipment is also our speciality.

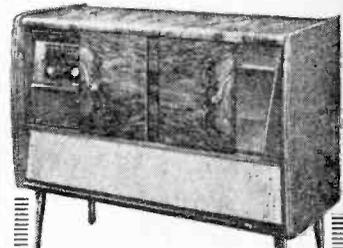

The Grosvenor
 Price 18 gns.



The Lowboy
 Price 24 gns.

LEWIS radio

100(P103) Chase Side, Southgate, London, N.14. Pal 3733/9666

Send today for the two new Lewis Catalogues

Designed to assist your choice of cabinet and equipment.

THE New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. THE unique 64 page equipment catalogue.

Please send your two new catalogues enclosed in P.O. for 3/6 which will be credited against any purchase I make.

Name _____
 Address _____

BLOCK CAPITALS PLEASE

of this famous Catalogue
NOW READY!

NEW EDITION



- **200** PAGES plus a page of useful formulae.
- Over **800** illustrations.
- Over **5000** components clearly listed and priced.

OBTAINABLE ONLY FROM HOME RADIO LTD.

187 London Road, Mitcham, Surrey

ONLY 2'6 PLUS 1/- POST AND PACKING

This is the 4th Edition and 8th Re-printing of our Catalogue. In addition to enlarging it we have re-arranged many sections for easier reference. Customers who purchased earlier editions will need no encouragement to obtain this one. To new customers we would point out that of 5,000 items listed all but 14 are actually in stock, and that this unique catalogue is backed by a Mail Order service second to none!

POST COUPON TODAY

Enclose P.O. 316

NAME _____
ADDRESS _____

14 INCH
£7.10.0

12 months' Full written Guarantee. Part Exchange allowance Legs 39/6 per set. Shown working all channels in Show. Personal collection advised. Ins. and Carr. 14in. 20/- 17in., 30/-



17 INCH
£11.10.0

How do we sell at this low price? Sets are ex Rental. Already well maintained. We regun tubes ourselves. Valves and Parts are manufacturers surpluses. All sets have a written guarantee covering tube, valves and all components. Only Duke's can offer this.

TV TUBES Regunned
21in. 99/6 17in. 79/6
15, 14 and 12in.—59/6
Guaranteed One Year
Ins. and Carr. 10/-
Add 10/- refundable on OLD TUBE. 110° Tubes in Stock. Tested Service Tubes

15/- 121, 31/74, 36/24, 141, 14KP4 and others. Carr. Miniature Transistor set type. Tape Cabinets 20/-

To fit B.S.R. and Collaro Studio Decks. Carriage 5/-. Vol. Control s/w with side knob. Miniature Transistor set type. 2/- each. 12 for 20/-. Post for one, 6d.: 12 for 1/6.

VALVES 9d. each. 40—£1 Thousands of Valves available P.P. on 1—4 6d., 12 1/6. **LATEST LIST** (stamps only).

TELEPHONE HANDSETS 15/6 pair. G.P.O. standard pattern. House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.

SPEAKERS 7/9 each 6in., 8in., 7in. x 4in. Money back guaranteed. Other sizes, few only. Ex. mfd. salvage. P.P. 2/3.


EXTENSION SPEAKERS 19/9 2-tone covered cabinet, 6in. PM speakers, switch and flex. Ideal for kitchen, sick-room, etc. P.P. 3/3.

Stamp for **DUKE & CO. (LONDON) LTD.** Phone
FREE 621/3 Romford Road, Manor Park, E.12 ILFORD
LIST Liverpool St.—Manor Pk.—10 mins. 6001/2/3

SPECIAL OFFER!
OBTAINABLE ONLY FROM R. & T.V. THE

Elegant Seven

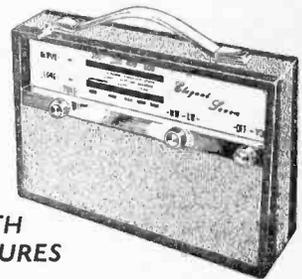COMBINED PORTABLE AND CAR RADIO
THE RADIO WITH THE STAR FEATURES




★ 7-transistor superhet. Output 350 mW. ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½in. ★ Horizontal tuning scale, size 1½ x 2½in. In silver with black lettering. ★ All stations clearly marked. ★ Ferrite-rod internal aerial. ★ 1F 470 Kc/s. ★ Operated from PP9 battery. ★ Full comprehensive instructions and point-to-point wiring diagram. ★ Printed circuit board, back-printed with all component values. ★ Fully tunable over medium and long waveband. ★ Car aerial socket. ★ Full after sale service.

ONLY £5.9.6 PARTS LIST AND CIRCUIT DIAGRAM 2/6. FREE with parts. PLUS 5/6 POSTAGE & PACKING

Goods not despatched outside U.K.
All enquiries S.A.E. Terms C.W.O.
RADIO & T.V. COMPONENTS LTD.
21c HIGH STREET, ACTON, LONDON, W.3.

TEST METERS

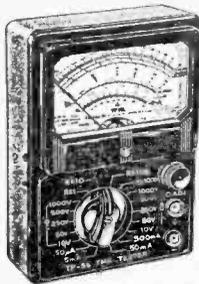

20,000 OHMS PER VOLT MODEL TP-5S (Illustrated). Reads voltages up to 1,000 V.C. at 20,000 ohms per volt and A.C. at 10,000 ohms p.v.; D.C. current to 500 mA; Resistance to 10 Mega. Capacitance to 0.1 μF; Decibels from -20 to +36. Size 3 1/2 x 5 1/2 x 1 1/2 in. £5.19.6.

2000 OHMS PER VOLT MODEL TP-10. Reads A.C. and D.C. volts up to 1,000; D.C. current to 500 mA; Resistance to 1 Mega; Capacitance to 1 μF; Decibels from -20 to +36; Output jack for Audio measurements. Size 3 1/2 x 5 x 1 1/2 in. £3.19.6.

30,000 OHMS PER VOLT MODEL 500. Reads voltages up to 1,000 D.C. at 30,000 ohms per volt, and A.C. at 15,000 ohms p.v.; D.C. current to 12 amps; Resistance to 10 Mega; Decibels from -20 to +56. Sizes 3 1/2 x 5 1/2 x 2 1/2 in. £3.19.6.

LAVOIE UHF WAVEMETER MODEL 105. Coverage 375/725 Mc/s. Complete with correct Calibration Chart. First-class condition. Battery operated and portable. Size 11 x 8 x 7 1/2 in. ONLY £3.19.6 (Carriage 7/6).

HRO SENIOR TABLE MODEL RECEIVER. Complete with 9 coils set covering 50 Kc/s to 30 Mc/s. Used, very good condition, aerial tested. A few late Model 5T with I.O. valves, £22.10.0 (carriage 30/0).

DOUBLE BEAM OSCILLOSCOPE TUBES. Another purchase of Type CV 1596, equivalent to Cossor 09D as used in Oscilloscopes by Cossor (339 series) and Hartley & Erskine (13 series). Listed £12. Brand new in maker's crates, 25/- (carr. 5/-).

CRYSTAL DESK MIKE with screened lead and built-in stand. ONLY 15/- (Post 1/6).

COSSOR TYPE 1035 DOUBLE BEAM OSCILLOSCOPES. A few only of these modern scopes, overhauled and in perfect order ONLY £35. Further details on request.


AMERICAN DESK TELEPHONE. Complete with handset. Non-ideal type, but has internal bell. Ideal for extension or inter-com. BRAND NEW. ONLY 30/-. (Post 4/-).

ACOS 89/1 STICK MIKE with screened lead and table stand. ONLY 32/6. (Post 1/6).

PCR COMMUNICATION RECEIVERS

Manufactured by Pye and Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of 1P using 6 British I.O. type valves. Large 180 degrees Illuminated and Calibrated Dial. Flywheel switching with locking device. Aerial trimmer. Tone and volume controls. Band switch from panel jacks for speaker or phones. In black metal case, size 17" L x 8 1/2" H x 10" D. Model PCR2 covers 6-22 Mc/s, 200-550 metres, and 850-2,000 metres, £5.19.6. Model PCR3. As PCR2 but has 2 Short Wave Bands, 2.0-7.0 Mc/s and 7.0-23.0 Mc/s and Medium Wave Band 190-550 metres, ONLY £3.8.0. Every receiver aerial tested before despatch. Add 10/6 carr. Both types used, but excellent condition. Designed to operate from bulky external power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200/250 v. A.C. at extra cost of £2. S.A.E. for illustrated leaflet.


P.W. "CELESTE 7" RECEIVER

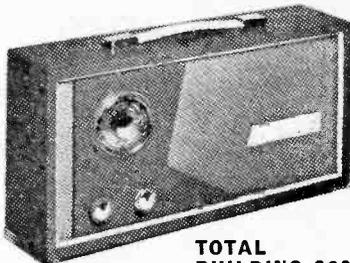

Build this latest P.W. seven transistor portable, as described in June and July issues. Medium and Long waves, with output of 1 watt (from large 7 x 4 in. loud-speaker. Internal high gain aerial with car aerial socket. All components sold separately—parts list S.A.E.

TOTAL BUILDING COST £9.19.6

"POCKET 4" TRANSISTOR RECEIVER

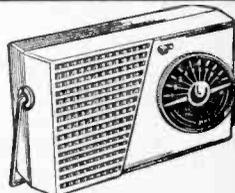

Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components and case for only 42/6 (P. & F. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.

"Practical Wireless" 6 transistor Personal Receiver. 2 band printed circuit, etc. Building cost £7.19.6. "Pocket 4" Transistor Personal. Ideal for beginner. Building cost 42/6. All components sold separately, price lists for either of above S.A.E. **MINIATURE MOTORS.** Ideal for models. Operates on 3-6 volts D.C. Size 1 1/2 x 1 x 1 1/2 in. plus 1/4 in. spindle. BRAND NEW, 5/- or 6 for 25/-. **20/- CONSTRUCTOR'S PARCEL.** Assorted colours wiring wire, solder, resistors, condensers, volume controls, tag panel. ALL NEW (Post 2/6). **RESISTORS.** 100 assorted values our choice. NEW 10/-. **CONDENSERS.** 100 assorted mica and silvermica. NEW 12/6.

HARRIS ELECTRONICS (LONDON) LTD.

138 GRAY'S INN ROAD, LONDON, W.C.1 Telephone TErminus 7937 Please include carriage costs on ALL items. Open until 1 p.m. Saturdays. We are 2 mins from High Holborn (Chancery Lane Sta) and 5 mins bus from King's Cross

TRANSISTORS FROM 1/3

GREEN SPOT A.F. 3 volt. ONLY 1/3. YELLOW SPOT A.F. 6 volt 1/6. RED SPOTS. Now ONLY 1/9 each. WHITE SPOTS. ONLY 2/6 each.

MICRO-ALLOY TRANSISTORS MAT100 7/9, MAT101 8/6, MAT120 7/9, MAT121 8/6. 22 Tested Circuits using Micro-Alloy Transistors 5/-.

MULLARD TRANSISTORS

OC70 6/6, OC71 6/6, OC72 8/-. Matched Pr. 16/-, OC81 8/-. Matched Pr. 16/-. OC78 8/-. OC44 9/3, OC45 9/-. OC170 9/6, OC171 10/6, AF102 27/6, AF114 11/-. AF115 10/6, AF116 10/-. AF117 9/6, AF124 11/-, AF125 10/6, AF126 10/-. AF127 9/6. **DIODES** OA70, OA79, OA81, OA90, OA91 all 3/- each. BY100 13/-.

SURPLUS DIODES CG3E 1/6. Miniature Type 3 for 2/-, 7/- doz. **TRANSISTOR HOLDERS** 3 or 5 pin 1/-.

REPANCO COMPONENTS

TRANSISTOR TRANSFORMERS TT49 Interstage, TT45 Driver, TT46 Output, TT47 Driver. All 5/- each. TT2 Ferrite Rod Aerial 12/6. DRX1 Crystal Set Coil M. & L. 3/-. DR2 Dual Range Coils 4/6. CH1 Miniature R.F. Chokes 2/6. **THE HIKER.** 4 Transistor Portable. Step-by-Step Instructions 1/6.

ALL SENT POST FREE IN U.K. by

PETHERICK'S RADIO SUPPLIES

22 High Street, Bideford, N. Devon. Tel.: Bideford 1217 S.A.E. with ALL enquiries please.

2 METRES 4

The thrills of VHF Amateur Radio can now be yours for as low as 39/6, complete kit, by post 2/6 extra. Tunable range 70-150 Mc/s. Write today for interesting literature, s.a.e. please. If a newcomer to Short Wave Radio, ask for free copy of world-famous "Globe-King" Short Wave Kits and other receivers. Stamp for post please, not s.a.e.

JOHNSONS (Radio) St. Martins Gate, Worcester

BBC · ITV · F.M. AERIALS



R.B.C. (BAND 1). Telescope loft, 21/-. External S/D 30/-. **L.T.V. (BAND 3).** 3 Element loft array, 25/-, 5 Element, 35/-. Wall mounting, 35/-. 5 Element, 45/-.

COMBINED R.B.C./L.T.V. Loft 1+3, 41/3; 1+5, 48/9. Wall mounting 1+3, 56/3; 1+5, 63/9. Chimney 1+3, 63/9; 1+5, 71/3.

F.M. (BAND 2). Loft S/D, 12/6; "H", 30/-. 3 Element, 52/6. External units available. Coax. cable 8ft. yd. Coax. plugs 1/3. C.W.O. or C.O.D. P.P. 3/-. Send 6d. stamps for illustrated lists. Band IV 625 line Aerials also available.

K.V.A. ELECTRONICS (Dept. P.W.) 3B, Godstone Road, Kenley, Surrey.

JAG ELECTRONICS & CABINET MAKERS LTD.

No. 9 WORKSHOPS GRAYES PLACE, SLOUGH, BUCKS.

Valves and Line OPT. Surplus or Ex-equipment

EB91	2/-	PCL82	4/6	6F1	3/-
EBP80	4/6	PCL83	5/-	6F12	2/-
EBP89	5/-	PL84	6/6	6P13	5/-
ECH35	6/-	PL33	7/-	6F14	5/-
ECC81	3/6	PL36	7/-	6F15	6/-
ECC82	3/6	PL35	6/6	6L1	7/-
ECC83	4/6	PL81	6/6	6L18	6/-
ECC80	4/6	PL82	4/6	6P25	5/-
ECC82	5/-	PL83	5/-	6P28	8/-
ECC81	5/-	PL84	6/6	10F1	3/-
ECL80	4/-	PL82	7/6	10P13	6/6
ECL82	6/-	PL83	7/6	10P14	6/3
EF80	2/-	PL80	3/6	20D1	4/-
EF85	4/6	PL81	3/6	20F2	6/-
EF91	1/6	PL82	3/6	20L1	8/-
EL33	5/-	PL83	6/-	20P1	7/-
EL84	4/6	PL80	7/-	20P3	7/6
EY51	3/-	U24	6/-	20P4	12/-
EY86	4/6	U25	6/-	20P5	7/6
EZ80	4/-	U26	6/-	30P4	7/6
EZ81	4/6	U191	6/-	6L1	10/-
GZ32	5/-	U301	9/-	10C2	10/-
KT33C	4/-	U801	14/-	10C1	10/-
KT36	7/-	UBC41	5/-	ECH42	8/-
PCB84	4/6	UCB4	7/6	UF42	2/6
PCP80	4/6	UCF80	7/6	UAF42	5/-


Many other Types. TERMS: S.A.E. all enquiries C.W.O. Postage on valves 6d. each. Send for list. CABINETS. Many types available including speaker, gram, tape recorder, and radio. TRADE ENQUIRIES INVITED.

RES/CAP. BRIDGE 39/6


Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading. **READY CALIBRATED** Stamp for details of this and other kits.

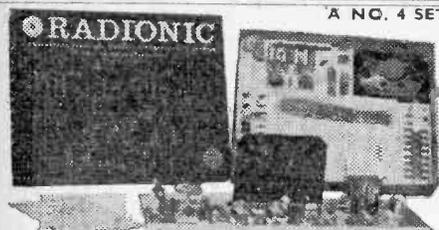Please write to: **RADIO MAIL (Dept. Pq)** Raleigh Mews, Raleigh Street, Nottingham



A NO. 4 SET

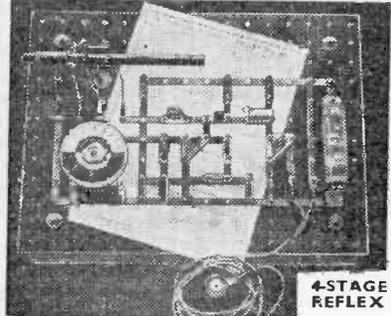

4-STAGE REFLEX



6-TRANSISTOR SUPERHET

RADIONIC CONSTRUCTIONAL AND EXPERIMENTAL SYSTEM

(SELECTED BY THE COUNCIL OF INDUSTRIAL DESIGN FOR DISPLAY IN THE DESIGN CENTRE, LONDON)

The Radio and Electronic construction system you have been waiting for. With top quality components mounted on colour-coded plastic bases, perforated transparent panel, perforated brass connecting strip and screw connection for positive contact you can quickly build any circuit and check it at a glance. Peak performances achieved. Already used by many schools and technical colleges for instructional purposes.

NO SOLDERING—NO SPECIAL SKILL—NO MAINS—FULLY ENGINEERED—COLOUR-CODED MOUNTINGS—FIRST CLASS COMPONENTS—MULLARD TRANSISTORS—PROGRESSIVE — FLEXIBLE — EXPERIMENTAL — INSTRUMENTAL—IDEAL RESEARCH FACILITY—RADIONIC NEWS LETTER.

Set No. 1. £5.18.6.
14 Circuit Sheets.
Diode Detector and two Amplifier stages;
Transistor Detector and Amplifier; Multi-vibrator.
Regenerative Receivers;
Earphone operation.

Set No. 2. £6.19.6.
20 Circuit Sheets.
Circuits of Set No. 1 plus capacity reaction, T.R.F. and Reflex Receivers;
Earphone operation.

Set No. 3. £10.19.6.
22 Circuit Sheets.
High quality Push-Pull Amplifier and 11,000 lines 7x4 inch 3 Ω loudspeaker convert circuits 1-20 to loudspeaker operation.
Amplifier can be operated from microphone or gramophone pick-up.

Set No. 4. £14.19.6.
26 Circuit Sheets.
Builds high quality six transistor superheterodyne receivers, as well as circuits of sets 1-3.

Postage and Packing extra on each of the above.
Sets or Separate Components available from authorised Retailers or direct from Radionic Products Limited.
TRADE ENQUIRIES ARE INVITED.
Full Details and price lists from:

RADIONIC PRODUCTS LIMITED
ADASTRAL HOUSE, NUTFIELD, Nr. REDHILL, SURREY
Telephone: Redhill (RL6) 5050 Telex: 21433

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
“NO PASS — NO FEE”

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

BRITISH INSTITUTE OF ENGINEERING¹
TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.
A.M.I.C.E.
A.M.I. Prod. E.
A.M.I.M.I.
A.I.O.B.
A.F.R. Ac. S.
& Sc.
A.M. Brit. I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V. Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.C. Certificate Practical Radio

Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW

Please send me your FREE 156-page “ENGINEERING OPPORTUNITIES”
 (Write if you prefer not to cut page)


NAME _____

ADDRESS _____

SUBJECT OR EXAM THAT INTERESTS ME _____ **SE/21**

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

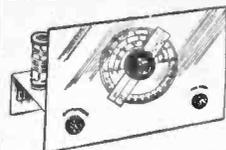LISTEN TO THE WORLD on TELSTAR our I-VALVE



SHORT WAVE RADIO
Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. **Total Building Costs 35/- P. & P. 2/-.**

R.C.S. TRANSISTORISED TAPE TUNER

Wonderful reproduction of all your favourite programmes. Covers full medium wave band. Special circuit incorporating ferrite rod aerial and tuning condenser gives **COMPLETE STATION SEPARATION**. Attractive case size 3 1/2 x 2 1/2 x 1 1/2 in. deep. **NO EXTERNAL AERIAL OR EARTH REQUIRED**. Chassis and components colour coded for easy construction. All parts supplied with step by step instructions.



ONLY 25/- P. & P.
(VT3 battery 2/6 extra).

THE R.C.S. PERSONAL SET

For Private Listening

An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 2 1/2 x 3 1/2 x 1 1/2 in. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. **Total Building Costs (including earpiece) 30/- P. & P.**



R.C.S. CRYSTAL RECEIVER

Covering medium wave band. Ideal for the beginner! All components in- **8/6 P. & P.** cluding case. **1/6.**
(Suitable headphones 9/6). Easily converted to 1-transistor or 2-stage transistor receiver.



All parts available separately. Send S.A.E. for free layout plans and parts lists of any of the above sets.

R.C.S. PRODUCTS (RADIO) LTD.

11 OLIVER ROAD, LONDON, E.17

(Mail Order Only)

OSMOR

PRICE LISTS & INFORMATION ON Various Designs in

Practical | Radio | Wireless | R.S.G.B.
Wireless | Constructor | World | Bulletin

SEND 6d. POSTAGE FOR



CIRCUITS

OSMOR LTD

418 BRIGHTON ROAD
S. CROYDON SURREY
Telephone CRO 5148

90 DAY GUARANTEE ABSOLUTELY BRAND NEW VALVES ALWAYS IN STOCK

DAF91	5/3	EL84	7/3	U801	22/6
DAF96	7/9	EY51	8/3	UABC80	8/3
DF91	5/3	EY86	8/3	UCH81	8/6
DF96	7/9	EZ40	8/6	UC183	12/3
DK91	6/9	DZ90	5/9	UF99	7/3
DK92	8/9	PC94	8/-	UL41	8/-
DK96	7/9	PCF80	8/6	UL84	7/9
DL92	6/9	PCL82	8/6	U08	17/-
DL94	7/-	PCL83	10/6	174	5/3
DL96	7/9	PCL85	10/6	1R5	6/9
ECC81	5/9	PL81	10/3	3S4	6/9
ECC82	7/3	PL83	7/9	3V4	7/-
ECC83	7/3	PY33	12/-	5Y3GT	7/9
ECC84	7/3	PY81	7/-	6V6G	5/9
ECC85	7/3	PY82	8/6	20L1	18/6
ECH81	7/3	PY800	9/6	20P4	20/-
ECL80	7/6	U25	11/3	30FL1	9/9
EF80	5/-	U38	9/6	30PL1	10/6
EF86	8/9	U191	11/9	30PL13	10/3
EL41	8/-	U301	17/-	8S1B1	19/6

IF VALVE NOT LISTED SEND S.A.E.
AMPLIFIERS

Individually made in our own workshop. From 500 m/w output to 75 watts output. These amplifiers can also be made to your own specification if required. Mono or Stereo. Please send S.A.E. for all enquiries. **Condensers - Resistors - Diodes Potentiometers - Speakers - Metal Rectifiers - All Types of Radio and TV Spares - L.O.P.T.S - F.O.P.T.S - Line and Frame Blocking Caps. TX.** We specialise in second-hand spares Technical Advice Always Available by Phone TERMS: C.W.O. plus 6d. postage per valve. C.O.D. S.A.E. for all enquiries.

We offer Green Shield stamps

Satisfaction Assured - Return Post Service WITWORTH T.V. SERVICE

32a, All Saints Road, London, W.11
Tel. PARK 9972 Open all day Mon-Sat inc

MULTIMETERS

Fully Guaranteed, brand new, boxed with test leads, batteries, instructions.
LOWEST PRICES IN THE COUNTRY
1,000 o.p.v. 0-15-150-1,000 v. D.C. and A.C. 0-150mA. D.C. Resistance 0-100K.. 35/-, Post 1/6.
10,000 o.p.v. 0-5-25-100-500-1,000 v. D.C. and A.C. 0-100µA and 0-250mA. D.C. Resistance 0-30K. 0-3M.. 72/6. Post 1/6.
30,000 o.p.v. 0-0.25-1-10-50-250-500-1,000 v. D.C. 0-10-50-250-500 v. A.C. 0-50µA. 0-10-250 mA. D.C. Resistance 0-10K. 0-1M, 0-10M.. 99/6. Post 2/-.
50,000 o.p.v. 0-10-50-250-500-1,000 v. D.C. and A.C. 0-25µA. 0-2.5-25-250mA. D.C. Resistance 0-10K. 0-100K. 0-1M. 0-10M. Capacity. Inductance. dB ranges. 27.2.6. Post 2/6.
Illustrated leaflet on request.
18,000 o.p.v. 25 range Multimeter kit, with Weston 0-50µA meter now reduced to 65/- post paid. Circuit etc.. free, for stamp.

**PLANET INSTRUMENT CO.,
25, DOMINION AVENUE, LEEDS 7**

THE AMATEUR RADIO HANDBOOK

by R.S.G.B., 3rd edition. 34/-, postage 2/6.
Wireless Servicing Manual, new edition, by Cocking. 25/-, postage 1/-.
How to Listen to the World, new edition, by Johansen. 14/6, postage 1/-.
Radio and Lite Transmission, by Danielsson. Vol. 1. 21/-, Vol. 2. 22/6, postage 1/-.
Beginners Guide to Television, new edition. 8/6, postage 9d.
More about Loudspeakers, by Briggs. 3/6, postage 1/-.
Multiband Transistor Radios, circuitry and Servicing. 5/-, postage 6d.
Guide to Amateur Radio, new edition, by R.S.G.B. 3/6, postage 6d.
Special offer of Micro Alloy Transistors, etc. Send for List.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2
(adjoining Lisle Street)

FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio/T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER
150,000 SUCCESSES**

CHAMBERS COLLEGE
(Incorp. National Inst. of Engineering)
(Dept. 461), 148 HOLBORN
LONDON, E.C.1

★ GUARANTEED VALVES ★

by return of post
THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY

All valves are new and unused unless otherwise advised.

POST 1 Valve 6d., 2-11, 1/-
FREE for 12 or more valves.

3 MONTHS GUARANTEE in writing with every valve.

FREE TRANSIT INSURANCE Satisfaction or Money back Guarantee on Goods if returned within 14 days.

024	4/8 6K7	5/9 20D1	8/9 DL82	9/- E240	6/8 U18	7/6
1A7GT	9/8 6K7G	2/- 20P2	9/8 DL82	5/- E241	6/8 U22	6/9
105GT	7/8 6K7GT	4/6 30P1	16/- DL94	6/8 E280	5/8 U24	12/6
1D5	9/- 6K8G	5/- 30P1	5/8 DL86	6/8 E281	5/8 U25	10/6
1D8	9/8 6K8GT	8/8 30P3	12/6 EA50	1/3 FW4500	7/- U28	8/8
1E5GT	8/8 6K8S	8/8 20P4	17/- EA0C80	6/8 G1C	12/6 U31	7/6
1L4	3/- 6L1	9/8 20P5	16/- EA0F1	4/- G282	7/6 U33	14/-
1L4S	4/3 6L6	7/6 21A6G	8/- EA0F2	8/8 G284	11/6 U35	12/6
1N5	4/8 6L6G	6/8 21A6GT	7/9 ER32	1/3 HK82	9/8 U37	28/-
1N5GT	9/8 6L18	7/9 25Y5G	8/- EB41	5/- HL41DD	8/8 U50	4/9
1R5	5/8 6L19	12/6 25Z4G	7/- EB91	3/8 HN309	19/- U52	4/9
1U3	5/8 6L20	7/9 25Z5	8/- EBC33	4/9 HV82	9/- U78	5/6
184	7/8 6N7	7/8 25Z6G	8/- EBC41	7/9 K782	6/8 U78	4/6
184S	9/8 6P1	17/6 25Z7	7/9 EB01	7/8 K782	4/- U77	12/6
1T4	3/- 6P25	8/6 30C1	6/9 EBF80	7/8 K786	14/- U191	11/6
1XD1	5/8 6P28	9/8 30C15	11/6 EBF85	8/8 K744	6/- U281	9/6
2A4	4/- 6G7G	5/6 30P5	8/- EBF29	7/9 K755	17/6 U282	15/-
2A5	8/8 6G7GT	8/- 30FL1	9/6 EBL12	9/8 K761	3/8 U301	12/6
2D6	4/- 6G8	9/- 30L1	8/8 EBL11	9/8 K761	3/8 U301	12/6
3Q4	7/- 6S4T	5/9 30L15	9/8 EC52	4/9 K768	13/6 U329	9/6
3S4	5/- 6SCT	4/9 30P4	9/8 EC81	4/8 K776	8/- U339	11/6
3V4	6/8 6S8G	4/9 30P19	7/8 EC82	8/8 K788	19/- U404	3/6
3Y4GT	9/8 6S8T	3/8 30P19	18/6 ECC81	7/8 K787	5/8 U404	3/6
3Y4	8/- 6S7	5/- 30P11	9/8 EC82	7/8 K782	4/- U407	12/6
3Y4G	9/8 6K7	5/- 30P13	9/8 EC83	4/8 K768	5/8 U438	7/6
3Y4G	7/8 6S8LGT	5/9 35C5	8/6 EC84	9/- K7263	11/- U412	7/6
3Y8G	9/8 6S7GT	4/8 35L8GT	8/- EC85	5/8 L63	3/8 UBC41	7/6
3Y8GT	5/8 6S8T	5/8 35W4	8/- ECC40	9/8 ML152	6/- UBC01	7/6
3Y8G	5/8 6S8GT	3/8 35AGT	3/8 EC86	4/8 ML14	4/8 UBC01	7/6
3Z4	9/- 6U4GT	9/8 35Z6GT	7/- EC82	4/9 N37	10/6 UBP90	7/6
3Z4G	7/- 6V6G	4/8 41	6/8 EC88	6/- N78	13/- UB121	12/6
3Z4GT	9/8 6V6GT	6/- 42	6/8 EC84	7/8 N108	13/- UC92	12/6
4/30L3	9/- 6X4	4/6 50B5	7/9 EC85	7/8 N156	8/- UCC94	8/6
4/30L5	9/8 6X6G	5/8 50C3	8/8 EC88	6/8 P41	12/- UC99	7/6
6A7	9/- 6X5GT	5/8 50L6GT	7/8 ECF80	8/8 P61	2/8 UCF90	13/6
6A8G	7/8 7B8	9/- 53K9	9/8 ECF82	8/8 PAB00	9/- UCH21	9/6
6A8GT	17/8 7B7	7/9 61B1	17/8 ECH21	11/8 PC86	11/8 UCH42	7/6
6A7	3/- 7C7	7/8 61BPT	11/- ECH35	9/8 PC87	9/8 UCH81	7/6
6A9S	2/8 7C6	7/8 62B7	13/6 ECH42	8/8 PC854	5/8 UCL85	7/6
6A7	6/8 7E7	7/8 7E5	5/6 ECH31	7/- PC85	7/8 UCL83	12/6
6A6S	5/- 7G7	15/- 7E3	5/- ECH38	8/8 PC88	11/8 UF41	7/6
6A1L	3/8 7E7	8/9 80	5/6 ECH80	9/8 PC89	8/8 UF42	5/6
6A6S	8/8 7E4	9/8 80E	9/8 ECH8	9/- PC159	13/6 UF80	7/6
6A9S	6/- 7Z4	5/- 185B7	19/8 ECL83	10/8 PCF80	6/8 UFB5	9/6
6A7E	5/- 8D3	3/- 185B7A	19/8 ECL86	10/8 PCF82	7/- UFB6	14/6
6A9S	7/- 10C1	11/8 807(A)	5/- EFB2	7/- PCF84	12/- UFB9	7/6
6A9V	5/8 10C2	14/8 807E	4/9 EFB8	3/8 PCF88	11/- UL41	7/6
8E7	8/8 10F1	4/8 913	4/9 EFB7A	7/- PCL82	7/8 UL41	14/6
8E8G	3/- 10F9	10/8 932	14/- EFB9	4/8 PCL83	9/- UL48	9/9
8E8A	5/8 10F18	10/- 866A	12/6 EFB40	11/- PCL84	7/3 UL84	7/6
8E8E	5/8 10D1L1	14/8 964	3/8 EFB1	8/- PCL85	10/- UM80	9/6
8E8G	5/8 10F13	5/8 965	2/3 EFB2	8/8 PCL86	10/8 URIC	7/6
8E8E	5/- 10P14	5/8 986	2/- EFB-BR1	19/8 PCL85	5/8 UY5	8/6
8E8E	5/8 10P16	7/- 1925	5/8 EFB(A)	2/6 PEN45	8/8 UY8	9/6
8E8T	8/8 12A8	2/3 5763	7/8 EFB4	3/8 PEN46	4/8 UY8	13/6
8E8S	9/8 12A8S	9/- 9001	8/8 EFB0	4/8 PL82	9/8 UY11	11/6
8E8E	6/8 12A7	9/8 9002	4/9 EFB5	6/- PL86	9/8 UY21	9/6
8E8W	9/- 12A7T	5/8 9003	6/8 EFB8	7/8 PL86	17/6 UY41	6/6
8C4	2/8 12A0E	9/- ATP4	2/6 EFB9	6/8 PL81	3/8 UY85	8/6
8C5	5/8 12A0T	6/- AZ31	7/8 EFB1	3/- PL82	6/8 VP49	9/6
8C6	3/8 12A0E	6/8 AZ41	7/- EFB2	3/- PL83	9/8 VP22	2/6
8C9	11/- 12A07	6/8 B36	8/8 EFB3	9/8 PL84	7/6 VP41	5/6
8C6D	17/8 12B4S	8/8 B37	8/- EFB4	9/8 PL820	5/8 VR105	6/6
8C6E	6/8 12B8E	6/8 CCH35	13/6 EK32	7/6 PM84	9/8 VR105	6/6
8D2	3/8 12B8T	8/8 C33	9/- EL32	3/8 PX4	12/8 W78	4/6
8D3	9/8 12C8	5/8 C131	7/8 EL33	7/- PX25	9/- W81	7/3
8D6	3/- 12F13	17/8 D77	3/8 EL34	11/8 PX31	5/- X81M	11/6
8F1	4/8 12H6	10/8 D30	11/8 EL35	10/8 PX32	10/8 Y85	8/6
8F6	7/8 12J6GT	3/8 DAC92	9/8 EL36	12/8 PY33	11/- X85	11/6
8F6G	4/8 12J7GT	8/- DAP91	4/8 EL41	8/- PY80	6/8 X86	7/9
8F13	4/8 12K7GT	8/8 DAF96	7/3 EL42	7/9 PY81	6/8 X76M	11/6
8F14	9/8 12K8	8/8 DAF95	8/8 EL43	8/8 PY82	5/8 X78	21/6
8F15	6/- 12K9GT	9/8 DFP91	3/- EL48	6/8 PY83	6/8 X79	21/6
8F19	6/- 12X5GT	4/8 DFB96	7/3 EL55	9/8 PY88	9/- X81E	8/6
8F32	4/8 12S4T	7/- DFB97	7/8 EL91	3/8 PY800	8/- Y83	6/6
8F33	4/- 12B0T	4/8 DFB93	5/8 EL95	8/8 PZ30	9/8 Z83	4/8
8F36	11/8 12B7	6/8 DFB76	4/8 EL94	8/8 RL34	9/8 Z88	8/6
8J5	4/- 12B77	5/8 DKB32	9/8 EM80	7/8 RL18	11/-	
8J5G	3/- 12B7K	4/8 5DK91	5/8 EM81	8/8 SP41	2/3	
8J5GT	4/8 12S7GT	6/8 DK92	7/- EM84	8/8 SP61	2/3	
8J6	3/8 12S4T	3/8 DK96	7/8 EM85	8/8 SU25	16/-	
8J7	6/8 12S7	5/8 DL33	7/8 EM81	15/- SU215	2/3	
8J7G	4/8 143T	14/8 DL35	7/8 EY51	7/8 T41	8/6	
8J7GT	7/8 19A4S	7/8 DL58	8/- EY88	7/8 TDD4	8/6	
8K6GT	6/- 19B8G	14/- DL75	8/- EY88	8/8 U14	7/6	

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/-, etc. (C.O.D. 2/- extra). ALL ITEMS LESS 5% AND POST FREE IN DOZENS. Send 6d. for list of 1,000 items.

Tubes

Carr. & Ins. 12/6.

MOST MULLARD, MAZDA, COSSOR, EMITRON, EMISCOPE, BRIMAR, FERRANTI TYPES, PROCESSED IN OUR OWN FACTORY

HIGHEST QUALITY—
COMPARE OUR PRICES
GUARANTEED NEW TYPES

6 Mon hrs	12 Months	MW 31/74	
12in.	£2. 0.0	£3. 0.0	£3.15.0
14in.	£2.10.0	£3.10.0	£4.15.0
15-17in.	£3. 5.0	£4. 5.0	CRM 172
21in.	£3.15.0	£5.15.0	MW 36/84
			£4.15.0
			£6.0.0
			CRM 172
			MW 48/64
			£6.0.0

SPECIAL TEMPORARY OFFER
Due to huge Bulk Special Purchase we are offering MW 31-74 Tubes at the unrepeatable price of 29/- MW 36/24 ditto. 39/- P.P. 12/6. The above are guaranteed for 6 months.

P.M. SPEAKERS, 3Ω Top Makes.
6in. 7/6
8in. 8/6
7 x 4in. 8/6

VALUE!
4 watt AMPLIFIERS
excellent amplifier with high gain preamp stage, 10F3 driving 10P14 output stage, complete with 8in. speaker. In attractive 3-tone case. Tube control, negative feedback. Ready for immediate use, individually tested. Amazing volume and clarity, ideal for guitars, record players, p.a. In small health, baby alarms etc. Easily worth 25. Our price whilst stocks last. Carr. Packing, etc. 7/6. **45/-**

100 RESISTORS 6/6
Excellent. Sizes 1-3 watt.

100 CONDENSERS 10/-
Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER 25.

12 POTS. Popular values. 5K to 2 Meg. Unused wired, pre-set, 500k sp., switched, etc. 4/6
CONDENSERS. 20 Mixed. Electrolytic. Many popular sizes. List Value 25. Our Price 10/-

SILICON RECTS.
250V 600ma standard TV replacement. Top quality 8/6 (3 for 24/-)

3 VALVE AMPLIFIERS
Kit of new parts, consisting chassis, mains and output transformers, valves (F61, 6X6G, 6X5G) and all components. With full instructions for making high gain amplifier with separate base and treble controls, negative feedback, etc. Truly unusual value at **29/-**

CO-AX, low loss, 6d. yd., 25 yds., 11/6, 50 yds., 22/-, 100 yds., 42/6, Co-ax Plug, 1/3. Wall outlet boxes 3/6.

NEW SHOP BRIGHTON

OPENING IN LARGE PREMISES
11-12 North Rd., BRIGHTON

With Widest Stocks, Keenest Prices. TV's, Radios, Valves, Transistors, Hi-Fi Equipment, Loudspeakers, Autochangers, Cables, Components, etc.

AM/FM RADIOS

Fantastic offer. 7 valves plus 2 diodes. Contemporary Cabinet. Top quality and finish. A.F.C. P.V.C. Absolutely complete. Guaranteed 3 months. **£11**

TRANSISTORS

Guaranteed Top Quality Huge reductions. Red Spot standard H.F. type now only 1/6; White Spot R.F. 2/-, Mullard Matched Output Kits (OC81D and 2-OC81's), 12/8. Receiver Kits (OC44 OC45(2), OC81D, OC81E), 24/-

PORTABLE RECORD PLAYERS. Take all sizes Records, all speeds, amplifier, auto-changer Garrard new 'Blue-line' Grand. In two-tone Case. **13 gns.** All absolutely new.

PORTABLE RADIOGRAMS. As above with 5 valve superhet radio. Med. and Long wave. Fantastic value. 17 gns.

100+ TYPES NOT LISTED E.A.E. ENQs.


ENQUIRIES WELCOMED
Quantity Prices or Quotes for items not listed, particularly rare valves

TECHNICAL TRADING CO.

RETAIL SHOP 350-352 FRATTON ROAD, PORTSMOUTH DEVONIAN COURT, MAIL ORDER ONLY PARK CRESCENT PLACE, BRIGHTON 7, SUSSEX

FROM STOCK We can supply a complete range of Valves, Crystals, Transistors, Diodes, Miniature and Standard Components.
 The largest range of Components and Equipment in the Country.
 Latest 68 page Illustrated Catalogue 2/- post free. Includes new HI-FI Section. Price Reductions.

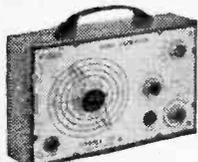NEW MODEL TRANSISTOR PORTABLE SIGNAL GENERATOR



PRICE **£7.18.6**

With battery and test probe. P.P. 2/-.

A 1st class Signal Generator covering 149 Kc/s to

350 Mc/s in 8 ranges. Radio broadcasts and I.F., Amateur, VHF, Shipping, TV, etc. R.F., I.F., A.F., modulated R.F. outputs. Easy to read and use with full details. Within 2% accuracy. Size 6 1/2 x 4 1/2 x 2 1/2 in.
12 MONTHS' GUARANTEE
 Leaflet on Request.

SUBSTITUTION BOXES

- Capacitor Box. Provides 9 standard values from 0.001 to 0.22 mfd at 600 volt working, 29/6.
 - Resistor Box. Provides 24 standard values at 1 watt. 15 ohms to 10 meg., 37/6.
- Each box fully calibrated with insulated leads. Invaluable for service and design.

● **TRANSISTORISED CAPACITANCE/RESISTANCE BRIDGE.** 1 Ohm to 100 Meg. 1 pF to 100 mid. (Appearance as Above Generator).
 Leaflet on Request.

PRICE **£7.2.3**, P.P. 2/-.

1 Track Record/Playback Tape Heads. 2 KΩ impedance, 15/-.

SILICON RECTIFIERS 500mA


100 PIV	3/-	1000 PIV	... 10/-
200 PIV	3/6	100 PIV 1 amp	... 4/6
300 PIV	4/6	200 PIV 6 amp	... 12/6
400 PIV	5/-		

Complete list free on request

100 Kc/s QUARTZ CRYSTALS

2 Pin: OCTAL or RCA...	15/- ea.
500 Kc/s 2 Pin 15/-
455 Kc/s (AR88) 12/6
5000 Kc/s 2 Pin 10/-
10 Mc/s 2 Pin 15/-

Complete list free on request

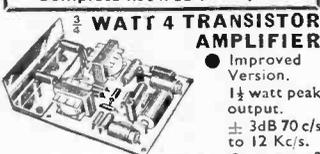

3 WATT 4 TRANSISTOR AMPLIFIER

- Improved Version.
- 1 1/2 watt peak output.
- ± 3dB 70 c/s to 12 Kc/s.
- Output to 3 ohm speaker
- 9 volt operated.

Details on request.

Built and Tested 59/6 OR Kit of Parts 52/6
 P.P. 1/6 P.P. 1/6

FIELD STRENGTH METER
 Five channels cover 1 Mc/s to 200 Mc/s. Fitted 200 microamp meter for CW or R.F. Indication and Earphone for A.F. monitoring. Designed for checking all types of transmitters. Size 4 x 2 1/2 x 2 1/2 in. Complete. Ready to Use, with instructions and telescopic aerial, 69/6. Post Free.

TRANSISTOR BABY ALARM
 As previously advertised. **£5.10.0**

TELEPHONE AMPLIFIER
 Speaker output from G.P.O. phone **£5.10.0**

RADIO CONTROL
 Special Offer of Miniature 3rd Overtone 27-25 Mc/s Crystals.
 Usually Twice the Price **15/-** Only

TYPE 38, TRANSMITTER RECEIVER
 Complete with 5 valves. In new condition. These sets are sold without guarantee but are serviceable. **22/6** P.P. 7.4 to 9 Mc/s. 2/6
 Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Aerial Rod 2/6.

DEAC RECHARGEABLE BATTERIES

- (a) 18 volt 100mA/H 4 x lin. diameter. Brand new sleeved, 30/-.
- (b) As above but 150mA/H, 35/-.
- (c) 3.9 volt 450mA/H, 12/6.

All types easily split into any multiple of 1.2 volt. Brand new.

Crystal High Impedance Contact Microphone for Guitars, 12/6. P.P. 9d

RUN YOUR RADIO OR AMPLIFIER FROM MAINS BATTERY ELIMINATORS AND CHARGERS

1. For PP3 or equivalent 9 volt Pocket Radio Battery, 18/- P.P. 1/-.
2. For PP4, PP7, PPS, PP10, 9 volt Portable Radio and Equipment Supplies up to 300 mA. 49/6, P.P. 2/-.
3. De Luxe version of No. 1 also charges PP3 type batteries. 24/- P.P. 1/-.
4. Rechargeable PP3 battery. Runs as long as 100 batteries. Complete with charger unit, 25/- P.P. 1/-.

LIGHTWEIGHT HEADPHONES

- 2,000 OHMS 12/6
- 4,000 OHMS 14/6

HIGH EFFICIENCY

METER BARGAINS

50 Microamp 2in. square MC ... 35/-
 0/100 Microamp 2in. Flush Round ... 32/6
 1 mA 2 1/2in. Flush Round ... 30/-
 2 1/2in. Moving Coil double range Voltmeter centre zero. 30-0-30 and 3-0-3 volts. Ideal for transistor tester or voltage measurements, 12/6. Post Free.

0/500μA 2in. ... 15/-
 0/500μA 2 1/2in. flush-mounting. D.C. 20/-
 2 1/2-0-2 1/2mA, 2 1/2in. flush D.C. ... 12/6
 0/15 volt M.I. 2 1/2in. F.R. A.C. ... 8/6

Miniature Panel Meters

*0/50μA (D.C.) 39/6 *0/5mA (D.C.) 27/6
 *0/500μA (D.C.) 32/6 *0/300V (D.C.) 37/6
 *0/1 mA (D.C.) 27/6 *Vu Meter 42/6
 *"S" Meter 35/- All Brand New Boxed.
 * Available Clear Plastic Front or Black Moulded. State which.

D.C. to A.C. CONVERTER. Converts 12 volts D.C. i.e. Car Battery, up to 230 volts A.C. 15 watts. Uses 2 power transistors in special circuit. Kit 62/6. P.P. 1/6. A REPANCO Design.

Henry's Radio Ltd
 PADddington 1008/9
 303 EDGWARE RD., LONDON W.2
 Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

TRANSISTOR TAPE RECORDER

The best obtainable

WELL KNOWN "MINY" TWO TRACK RECORDER. Features 4-Transistor push-pull amplifier, 2 motors, single switch operation, pause, speed, wind/rewind, record/playback. Can be used horizontally, vertically, carried or table top. Take it anywhere.
 Reduced from 12 gns. NOW **£8.19.6** P. & P. 2/6.
 Fully guaranteed—complete with microphone, tape, batteries and fully detailed booklet.

MULTI-METERS



THL33. 2000Ω/V. (Illustrated) 0/10/50/250/500/1,000 volts A.C. and D.C. 0/500μA/10/250 mA. D.C. 0/10k/100k/1 meg. etc., etc. Size 5 x 3 1/2 x 1 1/2 in. 75/- P.P. 1/6.	EP30K. 30,000Ω/V. 0/1 1/2/10/50/250/500/1,000 volts A.C. and D.C. 0/50μA/10 mA./250 mA. D.C. 0/10k/1 meg./10 meg. etc. Size 4 1/2 x 3 3/8 x 1 1/2 in. £6.19.6 P.P. 1/6.
ITI-2. 20,000Ω/V 0/5/25/250/500/2,500 volts A.C./D.C. 0/50μA 0/2 1/2/250 mA. D.C. 0/6k/6 meg. etc. Size 4 1/2 x 3 1/2 x 1 1/2 in. 5 gns. P.P. 1/6.	EP50K. 50,000Ω/V. 0/10/50/250/500/1,000 volts A.C. and D.C. 0/25μA./2 1/2/250 mA. D.C. 0/10k/100k/1 meg./10 meg. etc. Size 6 1/2 x 4 1/2 x 2 1/2 in. £9.19.6 P.P. 2/-.
PT34. 1000Ω/V. 0/10/50/250/500/1,000 volts A.C./D.C. 0/1/100/500 mA. D.C. 0/100k etc. Size 3 1/2 x 2 1/2 x 1 1/2 in. 45/- P.P. 1/6.	500. 30,000Ω/V. 0/1 1/2/1 1/2/10/25/100/250/500/1,000 volts A.C. and D.C. 0/50μA/5/50/500 mA. 0/12 amps short test etc. 0/60μ/6 meg./60 meg. etc. Size 6 1/2 x 4 1/2 x 2 1/2 in. £8.19.6 P.P. 2/-.
TPSS. 20,000Ω/V. 0/10/50/250/500/1,000 volts A.C./D.C. 0/50μA 0/5/50/500 mA. D.C. 0/10k/100k/1 meg./10 meg. etc. Size 5 1/2 x 3 1/2 x 1 1/2 in. £5.19.6 P.P. 1/6.	TRANSISTORS A SPECIALITY Let us quote.
EP10K. 10,000Ω/V. 0/5/25/100/500/1,000 volts A.C. and D.C. 0/100μA/250 mA. D.C. 0/30μ/3 meg., etc. Size 3 1/2 x 4 1/2 x 1 in. 89/6 P.P. 1/6.	

All meters supplied complete with batteries test leads and instructions. See latest catalogue for full details. Fully guaranteed.

Practical Wireless

BLUEPRINT SERVICE

ALL of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-SIDED BLUEPRINTS

Each blueprint in this series contains details of two separate instruments or items of equipment.

The Strand Amplifier	}	*	5/-
The PW Signal Generator			
The Savoy VHF Tuner	}	*	5/-
The Mayfair Pre-amplifier			
The Berkeley Loudspeaker Enclosure	}	*	5/-
The Luxembourg Tuner			
The PW Troubadour	}		7/6
The PW Everest Tuner			
The PW Britannic Two	}	*	6/-
The PW Mercury Six			
The PW Regency	}	*	5/-
The PW International Short Wave Two			

RECEIVERS

The Tutor *	3/-
The Citizen *	5/-
Junior Crystal Set	PW94 2/-
Dual-wave Crystal Diode	PW95 2/6
Modern One-valver	PW96 2/6
All-dry Three	PW97 3/6
Modern Two-valver	PW98 3/6
A.C. Band-pass Three	PW99 4/-
A.C. Coronet-4	PW100 4/-
A.C./D.C. Coronet	PW101 4/-
The PW Pocket Superhet	5/-

MISCELLANEOUS

The PW 3-speed Autogram	8/-
The PW Monophonic Electric Organ ...	8/-
The PW Roadfarer *	5/-
The PT Band III TV converter	1/6
The Mini-amp *	5/-
The PT Olympic *	7/6
The PT Multimeter *	5/-

SOME EARLIER DESIGNS

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Experimenter's Short Wave	PW30a	2/6
Midget Short Wave Two	PW38a	2/6
Simple S.W. One-valver	PW88	2/6
Pyramid One-valver	PW93	2/6
BBC Special One-valver	AW387	2/6
A One-valver for America	AW429	2/6
Short-Wave World Beater	AW436	3/6
Standard Four Valve S.W.	WM383	3/6
Enthusiast's Power Amplifier	WM387	3/6
Standard Four Valve	WM391	3/6
Listener's 5-Watt Amplifier	WM392	3/6

QUERY COUPON

This coupon is available until 4th October, 1963, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, OCTOBER, 1963.

COMPONENTS EQUIPMENT HI-FI

SEE OUR NEW 68 PAGE 10 x 7 in. FULLY DETAILED AND ILLUSTRATED CATALOGUE. TRANSISTORS, COMPONENTS, VALVES AND CRYSTALS.

2/-

POST FREE



TOTAL COST OF ALL PARTS

£9.19.6

P.P. 3/6.

All parts sold separately.

Guaranteed the Best Obtainable.

- Attractive Appearance—Reliable Design—Quality Performance

UNBEATABLE FOR QUALITY AND VALUE

Fully Detailed and Illustrated Leaflet on request.

★ 6 Mullard Transistors and 2 Diodes.

"THE CONTESSA"

★ COMBINED PORTABLE AND CAR RADIO ★

AMAZING SENSITIVITY AND SELECTIVITY ON MEDIUM AND LONG WAVEBANDS

★ The easiest Superhet Radio to build on the market. Features clearly-marked printed circuit and packaged components with full illustrated building instructions. Full tuning of medium and long wave bands with unbeatable sensitivity and selectivity. Excellent tone and volume with over 600mW push-pull output.

★ Clearly marked horizontal station dial with slow motion tuning. Two colour Blue or Beige cabinets with Gold handles, grilles and fittings. Size 10½ x 7½ x 3½ in., includes car aerial socket, recording sockets.

"CAPRI" POCKET RADIO SUPERHET 6-TRANSISTOR



Size only 4½ x 2½ x 1½ in. **REALLY POCKET SIZE!**

The most compact 6-transistor and diode radio with speaker available to the home constructor. Features the latest in miniature components and circuitry. Supplied with Mullard transistors and two-tone moulded cabinets in red-white or blue-white with gold fittings. All components are supplied in packets and clearly identified. A printed circuit is used with fully illustrated building instructions. Push-pull output coupled with a sensitive and selective circuit make the "CAPRI" hard to beat. Fitted Earphone/Record Socket. Full tuning on medium waves with long wave Light. All parts sold separately.

TOTAL COST OF ALL PARTS **79/6** P.P. 2/- (Battery 2/6 extra. Earphone 6/6 extra.) Illustrated leaflet on request.

● Slip it into your Pocket ●

10 WATT TRANSISTOR HI-FI AMPLIFIER

Replace that Valve Amplifier with this High Fidelity Amplifier. Call for demonstration—any time.



- 40 C/S TO 20 KC/S ± 1db
- LESS THAN 0.3% TOTAL DISTORTION
- 100mV INPUT FOR 10 WATTS OUTPUT
- MAINS OR BATTERY

Ideal for all Mono and Stereo Hi-Fi systems.

Supplied complete with booklet showing preamplifiers, mixers, stereo, public address, etc. Can be used with any commercially available valve or transistor preamps, tuners, etc. Can be used with batteries—any voltage 4½ to 24 volts.

Complete Booklet Free on Request.

PERFORMANCE EQUIVALENT TO VALVE AMPLIFIERS OF FOUR TIMES THE PRICE AND MANY TIMES THE SIZE

FULL FUNCTION HI-FI TRANSISTOR PREAMPLIFIER



- 6 position input selector—Treble—Volume—Bass—Filter controls.
 - 9 to 40 volts mains or battery. Without change in performance.
 - + 12 db boost at 50 c/s and 15 kc/s. — 15 db cut at 50 c/s and 15 kc/s.
- A new two transistor printed circuit preamplifier designed for use with the 10 watt transistor Hi-Fi amplifier or any valve or transistor amplifier. Built and ready to use. Panel size 9 x 2½ inches.

Complete with circuit and details **99/6** P.P. 2/- or kit 92/6. P.P. 2/-.

Built ready to use **£5.19.6**

P.P. 2/- OR KIT **£5.15.6** P.P. 2/- (Mains Unit 69/6 extra)

7-TRANSISTOR RECORD/PLAYER/RADIOGRAM AMPLIFIER



- 4 watt peak.
- Full Treble and Bass boost and cut.
- 40 c/s to 20 kc/s ± 3db.
- Inputs for Pick-ups, Radio Tuners, Microphones, mixers, etc.

Built and Ready to Use **£5.19.6**

P.P. 2/- (Complete with full descriptive Booklet)

- 15 ohm Speaker (8" x 5" 22/6 extra).
 - 12 to 18 watts mains or battery.
 - Size only 6" x 2½" x 2".
- Ideal for mains or battery, portable or domestic record players, grams, etc. (Mains Unit 80/- extra.) Call for demonstration.

● Booklet Free on Request ●

"MINIRANGER"
3-Transistor Plus 2 Diodes. Smallest radio to build yourself. Printed circuit; full tuning. **ONLY 3 x 2 x 1½ in.** Over 20 stations. Diagrams Free. **TOTAL 49/6** P.P. 1/6.

Both Models as Previously Advertised. ● All Parts Sold Separately. ALSO IN STOCK. Sinclair Slimline, 49/6. P.P. 1/6. PW-6 Superhet, £7.19.6. P.P. 2/-.

"QUINTET" POCKET RADIO
Diagrams Free. Size 5½ x 3 x 1½ in. 5-Transistor, plus Diode MW/LW to build. **79/6** P.P. 2/-



● Booklets Free on Request.

STEREO AMPLIFIERS—BRAND NEW

(a) 2 watts each channel	79/6
(b) SA80 4+4 watts, full controls and inputs	£9.10.0
(c) SA150 7+7 " " "	£16.10.0
(d) SA300 15+15 " " "	£32.10.0

Items b, c and d, complete in cabinets with multi-range controls and inputs. Leaflets on request—Speakers—Microphones—Amplifiers.

4-WAVEBAND COMMUNICATIONS RECEIVER. MODEL RX60.

● 550 kc/s to 30 Mc/s.—BFO—AVC—Noise Limiter—Bandspread—"S" Meter—Telescopic Aerial. Full World Wide Coverage.

PRICE **£33**

P.P. 7/6. With Full Instructions.

BRAND NEW IN CARTONS.

← PLEASE TURN PAGE

P.W. CELESTE ... £9.19.6
P.W. SPINETTE ... £10.19.6

HI-FI SPEAKERS

12in. 15 ohms, 12,000 Gauss	35/-
13½ x 8½ in., 3 ohm	32/6
8in., 15/16 ohm (BA7)	78/6
12in. 15/16 ohm (CR30AE)	10gns

BRAND NEW—GUARANTEED

Henry's Radio Ltd.

303 EDGWARE ROAD, LONDON, W.2
PADddington 1008/9
Open Monday to Sat. 9-6. Thurs. 1 o'clock.

We can supply from stock most of the components and items specified on circuits published in this and other magazines and radio books. Let us quote for your circuit.