

PRACTICAL WIRELESS

NOVEMBER 1964


2¹/₂

**FREE
INSIDE!**

BLUEPRINT

TO BUILD THIS
LOW COST

**CAR
RADIO**

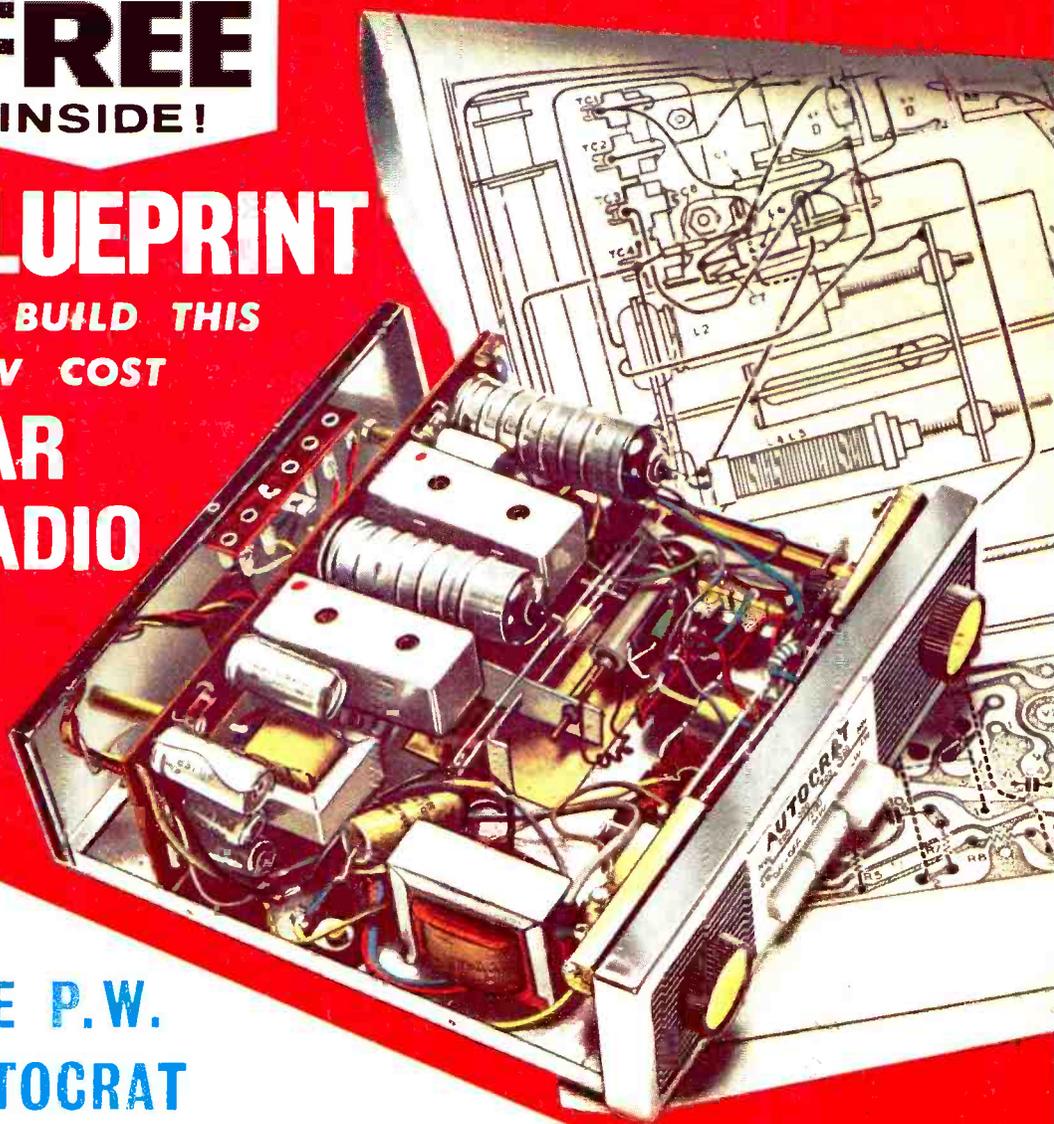


**THE P.W.
AUTOCRAT
CAR RADIO**

ADCOLA

PRODUCTS LIMITED
(Regd Trade Mark)

SOLDERING EQUIPMENT

FOR
THE
RADIO
CONSTRUCTOR

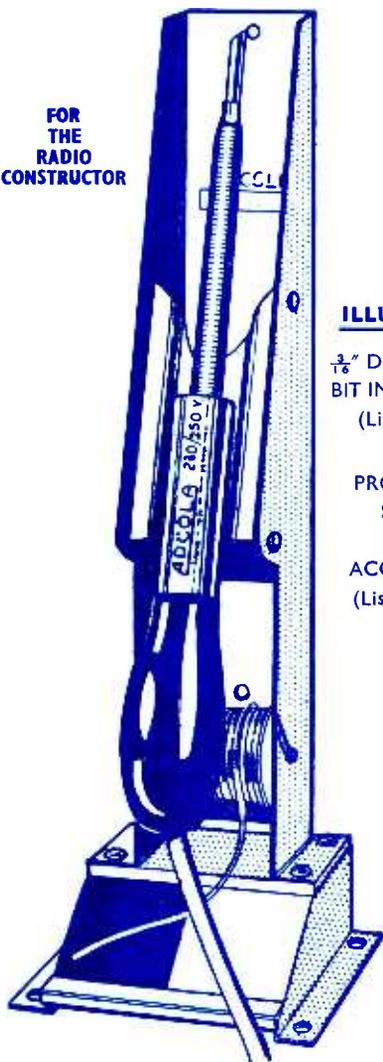

ILLUSTRATED

$\frac{3}{16}$ " DETACHABLE
BIT INSTRUMENT
(List No. 64)

IN
PROTECTIVE
SHIELD
WITH
ACCESSORIES
(List No. 700)

FOR CATALOGUES APPLY DIRECT
ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4

Telephones:
MACaulay 3101
4272

Telegrams: "SOLJOINT" LONDON SW 4

'SUPER SIX' TRANSISTOR RADIO KIT

NOW ONLY £4.17.6

(post 5/-)

Owing to a fortunate bulk component contract the price of this model is now reduced to £4.17.6. Purchasers who have already paid the previous higher price will have the difference refunded on application.



- All new parts.
- 6 transistors and diode.
- 350mW output.
- Superhet circuit, Ferrite rod aerial.
- Weymouth Radio printed circuit board.
- Component positions and references printed on back of board.
- Nicely styled wooden cabinet, 11 x 7½ x 3½ in.
- Vinyl covered in various colours.
- 6 x 4 in. speaker giving good bass and treble response.
- Full instruction booklet 2/-, Free with kit.
- I.F. frequency 470 kc/s.
- Lining up service if required.
- All parts supplied separately. Write for list. S.A.E. please.
- Set can be supplied fully built for £6.17.6 tax paid and carriage paid.
- 9v. battery required. VT9 or P.P.9 (3/9 with kit).

TRANSISTORS

Packet of 3 coded RF transistors (equivalent of OC44/5) 7/6 post paid. Trade supplied.
Set of 6 transistors and diode with circuit diagram. Neatly packed in foam-lined box; useful for presentation 15/- post paid.

ELECTRONICS (Camberley) Ltd.,
15, Victoria Avenue, Camberley, Surrey.
(Closed Saturday)

TO DESIGNERS & CHIEF ENGINEERS

OSMOR

Specialises in winding miniature coils and transformers of interest to bulk manufacturers in the industrial field. Manufacturers using up to 50 s.w.g. will find our service economical and reliable.

ENQUIRIES APPRECIATED
LARGE CAPACITY AVAILABLE!

Please Telephone **CROYDON 5148** for
Swift Action.

OSMOR
Radio Products Ltd
540 PURLEY WAY, CROYDON,
SURREY
(Parking facilities)

Tubes

Carr. & Ins. 12/6

HIGHEST QUALITY - COMPARE OUR PRICES		NEW TYPES
GUARANTEED 6 Months	12 Months	MW 31/74 £3.15.0
MAZDA COSSOR	12in. £2.0.0	MW 36/24 £4.15.0
EMI-CORON	14in. £2.10.0	CRM 172 MW 43/84
FERRANTI TYPES	15-17in. £3.5.0	£6.0.0
OUR OWN FACTORY	21in. £3.15.0	

MOST MULLARD. MAZDA COSSOR. EMI-CORON. FERRANTI TYPES. PROCESSED IN OUR OWN FACTORY

★ GUARANTEED VALVES ★

by return of post
THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY

All valves are new and unused unless otherwise advised

POST	3 MONTHS GUARANTEE	FREE TRANSIT INSURANCE
1 Valve 6d., 2-11, 1/- FREE for 12 or more valves.	in writing with every valve	Satisfaction or Money Back Guarantee on Goods if returned within 14 days.

SATISFACTION GUARANTEED

EKO L.O.P.T. Unused replacements for Perspex cased 1954/7 models, complete with E.H.T. rect. unrepairable. **39/-**

CO-AX. low loss, 6d. yds. 25 yards, 11/6, 50 yds., 22/-, 100 yds. 42/6 Co-ax Plugs, 1/3. Wall outlet boxes 3/6

SPECIAL C.R.T. OFFER
Due to huge Bulk Special Purchase we are offering MW 31/74 Tubes at the unrepeatable price of 29/-. MW 36/24 ditto, 39/-. P.P. 12/6. The above are guaranteed for 6 months.

LOUDSPEAKERS 3 Ω Top Makes
6in. **7/6** 8in. **8/6**
7 x 4in. **8/6**

CONNECTING WIRE
P.V.C. Bright colours. Five 25ft. coils only. **4/-**

3 VALVE AMPLIFIERS
Kit of new parts, consisting chassis minus and output transformers, valves (6W6, 6X4, 6X5) and all components. With full instructions for making high gain amplifier with separate bass and treble controls, negative feedback, etc. Truly unusual value at **29/-**

MAINS TRANSFORMERS
Excellent Quality guaranteed. Upright mounting 250-0-250 V 60 mA, 6.3 V 3 A (80mA 12/6) Hitto semi-enclosed 9/6 **9/6**

13 CHANNEL T.V.s
Table Models. Famous Makes. Absolutely Complete. These sets are unequalled in value due to huge purchases direct from sources. They are untested and not guaranteed to be in working order. Carr. etc. 15/-
12in. **£2.19.0** 14in. **£4.19.0**

LEAK AMPLIFIER SNIPS
Due to a fortunate purchase we are able to make the following unrepeatable offers. All amplifiers have fine matching Output Transformers (Transformers to match these Amplifiers to 15Ω Speakers can be supplied at 22/6 each).
TL/25 WATT (new)..... 21s
Note—These Leak Amplifiers all have the added facility of volume and tone controls so that they can be used without a pre-amp. If very high gain is not required.

★ **BULK BARGAINS** ★
19 POTS. Popular values, 4 5K to 2 Meg. Unused, mixed, per set, long sp., switch, etc. **-4/6**
CONDENSERS. 25 Mixed. Electrolytic. Many popular sizes. List Value £5. Our price **10/-**

100 RESISTORS 6/6
Excellent. Sizes 1/3 watt.

100 CONDENSERS 9/6
Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER £5.

25 TAG STRIPS 4/-
2, 4, 6, 8 way etc. Unused.

100 HI STABS 9/6
1% to 5% 100 Ω to 5M Ω.

TRANSISTORS

GUARANTEED TOP QUALITY
High reduction. Red Spot Standard I.F.T. type now only 1/6
3 Transistors:
White Spot R.F. 2/-
Mullard Matched Output Kits OC81D and 2-OC81. R.F. Kits OC34, OC45 (2) AF 114 8/- OC44 5/6 AF115 7/6 OC45 5/6 AF116 7/- OC46 5/6 AF117 7/- OC47 5/6 AF127 9/6 OC48 6/- OC28 12/6 OC82 6/- OC38 14/- OC170 8/6 OC171 8/6

GERMANIUM DIODES
General Purpose miniature detector. A.V.C., etc. 8d.
Gold bonded highest quality. Individually tested. 9/6 doz. **1/-**

SILICON RECTIFIERS
Guaranteed performance. Top Make. Tested 250V working. 100mA 3/9 250mA 7/6 (13 for 9/6) (13 for 19/6)

VALVE HOLDERS. 676. 6d. ea., with Screen 8d. ea., B9A 6d. ea., with Screen 8d. ea. Int. Octal 6d., Mazda Octal 4d. BXA 6d. (these 15% in dozens).

TURRET TUNERS
Most makes, your choice if available, with valve 18/-, less valves 10/- S.A.E. enquiries.

COSSOR D.B. SCOPE TUBES. Type 001 Split Beam. Ideal for building your own quality oscilloscope whilst stocks last. **55/-**

LINE TRANS.
Huge quantity, most makes S.A.E. enquiries. **29/-**

RECTIFIERS. 250 V., 80 mA. 5/- R.M2, 6/9; R.M3, 7/6; R.M4, 19/6; R.M5, 19/6; 1A48G, 17/-; 1A49T, 19/6; 1A410, 19/6; 1BR3-116-11 7/9; 1RCA-1-148, 8/-; 1RCA125-2-1, 14/-; 1HRA1-2-22, 17/-; 1HRA1-2-3, 20/-
ELECTRIC MOTORS. A.C./D.C. 3-8 volts. Totally enclosed standard mounting, powerful V pulley, spare brushes, 2in. x 2in. **7/6**

AM/FM RADIOS
Fantastic offer. 7 valves plus 2 diodes. Contemporary Cabinet. Top quality and finish. A.F.C. A.V.C. Absolutely complete. Guaranteed 3 months. **11** gms.

ENQUIRIES WELCOMED
Quantity Prices or Quotes for items not listed, particularly rare values. TELEPHONE C.O.D. ORDERS DISPATCHED THE SAME DAY

024	4/8 6K7G	9/- 20P3	12/6 DM71	5/9 E281	6/- U22	6/9
1A7GT	8/9 6K7GT	4/9 20P4	17/6 EA50	1/3 FW4500	7/- U24	12/6
105GT	7/- 6K8G	5/- 20P5	15/- EA6C80	6/9 GT1C	12/6 U25	10/6
1D5	7/- 6K8SGT	11/- 25A6G	8/- EA6C91	4/- G23Z	7/6 U28	8/6
1D6	9/9 6K8S	9/8 25L6GT	7/9 EA6F42	8/3 G234	11/6 U31	7/6
1H6GT	9/- 6L2	9/8 25Y6G	6/- EB34	1/3 HK90	9/6 U33	14/-
1L4	3/- 6L6	7/6 25Z4G	7/- EB31	5/- HCL39	5/6 U35	12/6
1LD5	4/3 6L18	7/9 25Z5	8/- EB31	3/- HN309	19/- U37	26/-
1LN5	4/6 6L19	11/6 25Z6G	8/- EB38	4/9 HVR2	9/- U50	4/9
1N5GT	8/9 6L20	7/9 27S0	17/6 EB41	7/9 K73Z	6/9 U52	4/9
1R5	5/9 6N7	7/6 30C1	6/9 EB41	7/9 K733C	4/- U76	5/6
1S5	5/9 6P1	9/8 30C15	11/6 EB480	7/6 K736	13/6 U301	12/6
1S4	7/6 6P25	8/6 30F5	7/6 EB487	9/6 K744	6/- U37	12/6
1S5	4/6 6P23	9/9 30FL1	9/6 EB488	7/9 K755	17/6 U191	11/6
1T4	3/- 6Q6G	6/6 30L1	6/6 EB421	10/9 K761	11/- U381	9/6
2D21	5/6 6Q7GT	8/9 30L15	9/9 EC52	4/9 K768	4/6 U232	12/-
3Y4	6/6 6R74	9/- 30P4	6/6 EC52	8/6 K768	13/6 U301	12/6
3A5	8/9 6SA7	5/9 30P12	7/6 EC92	8/6 K776	8/6 U309	6/6
3D6	4/9 6S6GT	4/9 30P19	13/6 EC93	7/6 K758	10/6 U329	9/6
3Q4	7/- 6S7G	4/9 30P11	9/6 EC93Z	4/- K7W61	5/9 U303	11/6
3S4	5/- 6S7H	3/- 30P13	9/6 EC93Z	4/9 K7W62	5/9 U439	10/6
3Y4	6/6 6S7G	5/6 35C1	6/- EC93Z	11/6 K785	9/6 U381	7/6
5R4Y	9/6 6SK7	5/- 35L6GT	8/- EC93Z	9/- K7W63	5/9 U404	9/6
5T4	8/- 6SL7G	5/9 35W4	6/- EC940	9/6 L6	3/- UABC80	7/6
5U4G	5/6 6SN7GT	4/9 35Z4GT	5/6 EC931	5/6 L15Z	7/6 UAF42	7/9
5V4G	7/6 6S8GT	5/6 35Z6GT	7/- EC932	6/- M14	7/6 U41	7/-
6Y4	6/9 6S8GT	6/9 35C1	6/9 EC933	8/6 N78	10/6 UB41	7/6
5Y3GT	5/6 6U4GT	9/6 42	6/9 EC933	8/6 N108	17/- UB49	7/6
5Y4G	9/6 6V6G	4/6 50B5	7/9 EC934	11/6 N148	7/6 UB121	12/-
5Z4G	7/6 6X4	4/9 50L6GT	7/6 EC934	8/6 P61	2/9 UC92	7/9
6Z6GT	9/6 6X6	9/6 58K0	6/9 EC934	10/9 PABC80	8/- UC94	9/6
6J30L2	9/6 6X6GT	6/- 61E1T	17/6 EC931	8/6 PC86	11/6 UC98	10/6
6A6	3/9 7B6	10/6 61SPT	11/6 EC932	8/6 PC86	8/6 UC98	10/6
6A7	9/- 7B7	7/6 62BT	13/6 EC932	8/6 PC94	8/6 UC98	10/6
6B6G	7/9 7C5	7/9 75	5/- EC931	7/6 PC94	8/6 UC98	10/6
6ASGT	12/6 7C6	7/9 80	5/- EC931	8/6 PC94	8/6 UC98	10/6
6AC7	3/- 7H7	7/9 80	5/6 EC933	8/6 PC95	7/9 UC94	7/3
6A65	2/9 7S7	15/- 38	6/9 EC930	8/6 PC98	11/6 UC91	7/6
6A67	6/9 7Y4	6/- 185BT	19/6 EC932	8/6 PC99	9/6 UC91	12/-
6A65	3/6 8D5	4/- 185BTA	8/6 EC933	10/6 PC98	9/6 UC91	12/-
6AL5	3/3 8D	3/8 80	6/9 EC934	12/6 PC98	9/6 UC91	8/6
6AM6	3/- 10C1	11/6 813	4/9 EC936	10/3 PC98Z	7/- UF42	5/6
6A05	6/- 10C2	14/6 83Z	14/- PF22	7/- PCF84	12/- UF80	3/6
6A70	5/- 10P1	4/9 866A	12/6 EF36	3/3 PCF88	11/6 UF81	3/6
6B2B	3/6 10A6	6/9 868	8/6 EF37A	8/6 PC98	7/3 UF81	3/6
6AV6	5/9 10F18	10/- 855	2/9 EF39	7/6 PC983	11/6 UF81	3/6
6B7	8/6 10D11	14/6 956	2/- EF40	11/- PCL84	7/3 UL44	14/-
6B8G	3/- 10P13	8/6 1625	5/- EF41	3/- PCL85	10/6 UL44	9/6
6B4E	5/6 10P14	9/6 5763	7/6 EF42	8/9 PCL86	10/6 UM80	3/6
6B2B	5/6 10P13	7/6 5783	3/6 EF50-BR1	9/6 PC925	3/9 UR19	3/6
6B6G	15/- 12A6	9/6 9002	4/6 EF50A	2/6 EF80	11/6 UR19	3/6
6B6H	6/6 12A8S	11/- 9003	5/9 EF54	3/1 PEN48	5/6 UR19	3/6
6B6J	5/9 12A76	9/6 ATP4	2/6 EF59	4/6 PL33	9/6 UDS	13/6
6B7K	8/6 12A7T	5/6 AZ31	7/6 EF85	6/- PL36	9/6 UY11	11/6
6B7S	9/6 12A16	8/- AZ41	7/6 EF88	7/6 PL33	13/6 UY11	11/6
6B7W	7/9 12A17	6/- B36	6/9 EF89	6/6 PL81	3/3 UY41	6/-
6B7W	5/- 12A16	6/9 C1C	8/- EF91	1/- PL82	8/6 UY85	6/-
6C4	2/3 12A17	6/6 CBL31	13/6 EF92	3/- PL83	6/6 VP48	9/6
6C5	5/6 12B4A	7/- CCH35	13/6 EF183	9/6 PL84	7/- VP23	2/6
6C6	3/6 12B6	6/9 C91	9/6 EF184	9/6 PL820	8/9 VP41	5/6
6C9	11/- 12B7H	8/9 CY31	7/6 EK32	7/6 PM84	8/- VR105	5/6
6C0D6G	19/6 12C8	5/6 D77	3/3 EK32	3/9 P21	12/6 VCL50	9/6
6C0H6	6/6 12E1	17/6 DA30	11/6 EL33	11/- P25	9/- W76	4/6
6D2	3/3 12H16	1/6 DAC32	8/6 EL34	11/6 PY31	8/- W81	7/6
6D3	4/9 12H27	3/3 DAF91	6/6 EL35	6/- PY32	10/- X61M	11/6
6D6	3/- 12J7GT	8/- DAF98	7/6 EL38	12/6 PY33	10/6 X66	8/6
6F1	4/9 12K7GT	4/9 DFP33	8/6 EL41	8/6 PY31	6/6 X66	8/6
6F6	7/6 12K8	8/9 DFP31	3/3 EL42	6/6 PY81	7/9 X66	7/9
6F6G	4/6 12K8GT	11/6 DFP96	7/6 EL81	8/9 PY82	5/9 X76M	21/6
6F13	6/6 12L27	10/6 DFP7	7/6 EL84	6/6 PY83	6/9 X78	11/6
6F14	9/6 12S47	7/- DHE3	5/6 EL85	9/9 PY88	8/9 X79	21/6
6F15	9/6 12S67	4/6 DHT78	4/6 EL95	6/- PY80	7/9 Y63	6/-
6F19	6/- 12S7H	3/6 DK32	9/6 EL95	6/- PY81	7/9 Y63	6/-
6G3G	4/9 12S77	5/6 DK91	5/6 EM34	8/9 P230	9/6 Z63	4/6
6F33	3/- 12S77	7/6 DLS2	7/- EM34	8/9 P230	9/6 Z63	4/6
6H6	1/6 12S7GT	6/9 DK96	7/6 EM80	7/6 P19	9/6 Z66	8/6
6J5	4/3 12S97	8/6 DL33	7/6 EM81	8/9 RL18	11/-	
6J5G	3/- 13D3	6/6 DL35	7/6 EM85	9/6 SP41	2/3	
6K3G	6/6 13E6	9/6 DLS2	8/9 EN31	16/- SP31	2/-	
6J6	3/6 19A45	7/6 DL62	6/- EY51	7/6 SU25	10/-	
6J7	8/6 19B6G	14/- DL83	9/- EY58	7/6 SU250	4/6	
6J7G	4/9 20D1	8/9 DL92	5/- EY88	9/6 T41	6/9	
8J7GT	7/6 20P2	6/9 DL94	6/6 FZ40	7/- TDD4	8/6	
8J8SGT	6/6 20P3	10/6 DPL2	7/6 FZ41	7/6 TDD4	8/6	
6K7	5/9 20P1	9/6 DM70	3/6 EZ80	5/9 U18	7/6	

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/-, etc. (C.O.D. 2 - extra). ALL ITEMS LESS 5% AND POST FREE IN DOZENS.

SHOPS RETAIL ONLY

350-352 Fratton Road, Portsmouth (Tel: 22034)

72 East Street, Southampton (Tel: 25851)

ALL MAIL ORDER, RETAIL SHOP AND HI-FI ROOM

11-12 NORTH ROAD, BRIGHTON, TEL: 67999

TECHNICAL TRADING CO.

**SHORTWAVE RECEIVERS
'AMATEUR' EQUIPMENT**

**INSTRUMENTS FOR TEST,
SERVICE AND WORKSHOP**

World-Famous kit-sets anyone can build.

**Quality you can see, quality you can compare...
by appearance, by performance... by any standard**

DEFERRED TERMS ON ORDERS UK OVER £10.

ALL MODELS ALSO AVAILABLE ASSEMBLED

TEST INSTRUMENTS


10-12U

Sin. OSCILLOSCOPE Model 10-12U. Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing. F.M. alignment, etc. T/B covers 10 c/s -500 kc/s in 5 ranges.

£41.10.0 Assembled **£32.12.6 Kit**

PORTABLE 'SCOPE Model OS-1. A compact portable oscilloscope, ideal for servicing and general work. Printed circuit board. Case: 7½ x 4½ x 12½ in. long. Wt. only 10½ lbs. **£29.8.0 Assembled £21.18.0 Kit**

ELECTRONIC SWITCH. Model S-3U. Converts a single beam oscilloscope into double beam operation at low cost.

£18.10.0 Assembled **£12.18.0 Kit**



VALVE VOLTMETER. Model V-7A. The world's best selling VTVM. Measures up to 1,500 volts (d.c. and r.m.s.) and 4,000 pk. to pk. Res. 0.1Ω 1,000 MΩ. Centre zero dB scale, d.c. input resistance 11MΩ. 4½ in. meter. Complete with test prods, leads and standardising battery. **£19.18.6 Assembled £13.18.6 Kit**

De-luxe 6" VALVE VOLTMETER, Model ZM-13 V-TA Similar spec. to Model V-7A but with improved accuracy, larger meter, unique cymbal mount

£26.18.0 Assembled **£18.18.0 Kit**

RF PROBE. 309-CU extends range to 100 Mc/s. Indication to 300 Mc/s.

£1.13.6 Kit

HV PROBE, HV-336 measures up to 30,000V d.c.

£2.19.6 Kit

RF SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands.

£19.18.0 Assembled **£13.8.0 Kit**


MULTIMETER Model MM-1U. Ranges: 0.15 v. to 1,500 v. a.c. and d.c.; 150µA to 15A d.c.; 0.2Ω to 20MΩ. 4½ in. 50µA meter.

£18.11.6 Assembled **£12.18.0 Kit**

TELEVISION ALIGNMENT
GENERATOR, Model HFW-1.

Accurate alignment of TV receivers achieved in minimum time at low cost. Covers 3.5 to 220 Mc/s on fundamentals. A must for the service man.

ONLY £30.15.0 Kit
£44.10.0 Assembled

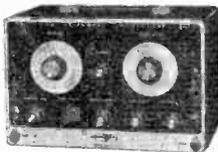

HFW-1

A wide range of other test instruments available including: R/C Bridge C-3U £10.10.0. AF V/Voltmeter AV-3U £16.10.0. Wattmeter AW-1U, £17.5.0. (Capacitance meter) CM-1U £15.15.0. Power supplies. Decade boxes etc. Many other instruments available under American Mail order scheme. Why not send for full details?

DAYSTROM LTD.

Dept. P.W.-11, GLOUCESTER, ENGLAND

TRANSISTOR RECEIVERS
**"OXFORD" LUXURY TRANSISTOR
DUAL WAVEBAND RECEIVER.**

The ideal domestic, or personal portable receiver. 10 Semi-conductors. Solid leather case. Send for full details.

Incl. P.T. **£14.18.0 Kit**



UXR-1

6 TRANSISTOR PORTABLE. Model UXR-1. Prealigned I.F. transformers. Printed circuit, 7 in. x 4 in. high flux speaker. Real hide case. Very easy to build.

Incl. P.T. **£12.11.0 Kit**

7 TRANSISTOR PORTABLE. Model RSW-1. Two short, trawler and medium wave bands.

Incl. P.T. **£19.17.6 Kit**

"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. Excellent portable or general purpose receiver for "amateur" or short wave listening. See full spec. leaflets.

Assembled £45.17.6 **£37.17.6 Kit**



GC-1U

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS OR PRICES.

"AMATEUR" EQUIPMENT
AMATEUR BANDS RECEIVER

Model RA-1. Covers all amateur bands from 160-10 m. Half lattice crystal filter. 8 valve, "S" meter, tuned R.F. amplifier stage.

£39.6.6 Kit

Assembled **£52.10.0**



RA-1

AMATEUR TRANSMITTER. Model DX-100U. Covers all amateur bands 160-10M. 150 w. d.c. input, self contained with power supply. Modulator, VFO

Assembled **£104.15.0 £79.10.0 Kit**



DX-40U

AMATEUR TRANSMITTER

Model DX-40U. Covers 80-10 m. Power inputs 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Prov. for V.F.O.

£33.19.0 Kit

Assembled **£45.8.0**

**COMMUNICATIONS TYPE
RECEIVER RG-1.**

A high performance low cost receiver for the discriminating listener. Freq.: cov. 600 kc/s-1.5 Mc/s and 1.7 Mc/s to 32 Mc/s. Send for details.

£53.0.0 Assembled **£39.16.0 Kit**



Other kits in the amateur range include: SSB Adaptor SB-10U, £39.5.0. Variable freq. Oscillator VF-1U, £10.17.6. Balun Coil Unit, B-1U, £4.15.6. Grid-Dip Meter GD-1U, £10.19.6. Q Multiplier QPM-1, £8.10.0. Wide range of models under American Mail Order Scheme.

THE WORLD'S BEST SELLING KIT-SETS




HIGHEST QUALITY AT LOWER COST

More and more people are buying and specifying Heathkit models because:

- ★ **Easy-to-Follow instructions** ... The step-by-step instruction manuals tell you what to do and how to do it. Large size pictorial diagrams show you how.
- ★ **A satisfying Hobby** ... assemble any Heathkit model, switch on and find that it performs exactly like an expensive, factory-built set. You will be proud of your model, your friends will admire it, and you built it successfully yourself.
- ★ **You save money** ... and get better performance at lowest possible cost.

HI-FI AMPLIFIERS

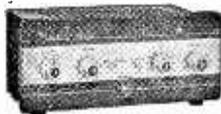

6W STEREO AMPLIFIER. Model S-33. 3 w/ch. Inputs for radio, tape and gram. Stereo/Mono, ganged controls. Sensitivity 200mV. **£18.18.0 Assembled £13.7.6 Kit**

18W STEREO AMPLIFIER. Model S-99. Ganged controls. Stereo/Mono gram, radio and tape recorder inputs. P/B selection. **£37.19.6 Assembled £27.19.6 Kit**



6W DE-LUXE STEREO AMPLIFIER. Model S-33H. An inexpensive stereo/mono amplifier with high sensitivity. Suitable for use with Decca Deram cartridge. **£21.7.6 Assembled £15.17.6 Kit**


5W HI-FI MONO AMPLIFIER. Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build. **£15.10.0 Assembled £10.19.6 Kit**

TAPE RECORD/REPLAY AMPLIFIER KITS. Will operate with most tape decks. Send for details. **TA-1M (Mono), £19.18.0 Kit TA-1S (Stereo), £25.10.0 Kit**

HI-FI MONO POWER AMPLIFIER. Model MA-12. Ideal for use with Models USC-1 and UMC-1, 0.1% THD at 10 W. Wide freq. range. **£15.18.0 Assembled £11.18.6 Kit**

HI-FI TUNERS

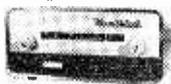Model FM-4U. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s I.F. (£2.15.0 inc. P.T.). I.F. Amp. (FMA-4U) complete, with cabinet and valves (£13.3.0).



Total **£15.18.0 Kit**

FM-4U

AM/FM TUNER. Covers FM 88-108 Mc/s, A.M. 16-50, 200-550 900-2,000 m. Tuning heart (£4.13.6 inc. P.T.), and I.F. Amp (£21.16.6) Total **£26.10.0 Kit**
Send for leaflets.

SPEAKER SYSTEMS

SSU-1 MODEL



A practical solution to the problem of a moderately priced speaker suitable for Stereo/Mono amplifiers, where the equipment has to be compact. Two speakers, balance control, ducted port reflex cabinet.

Horizontal or vertical (without legs) **£10.17.6 Kit**
Inc. P.T.
Horizontal or vertical (with matching legs) **£11.12.0 Kit**
Inc. P.T.

COTSWOLD STANDARD MODEL
Acoustically designed enclosure "in the white" 26 x 23 x 15 1/2 in. 12in. bass speaker, elliptical middle speaker, 2in. pressure unit. Covers 30-20,000 c/s. Complete kit with all controls.



MFS SYSTEM

A minimum floor space model for the smaller room: 26in. high x 16 1/2 in. x 14in. deep. Similar performance to standard model.

Price either model **£23.4.0 Kit**

EQUIPMENT CABINETS



A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request.

Prices from **£7.7.0 to £37.16.0**

Many other models covering a wide range of equipment for **HOME, OFFICE or WORKSHOP**
SEND FOR FREE BRITISH CATALOGUE
American Catalogue sent for 1/- post paid.

PUBLIC ADDRESS AMPLIFIER, PA-1. 50 w. output, two heavy duty speakers, variable Tremolo. Ideal for use with guitars, etc. **£74.0.0 Assembled £54.15.0 Kit**
Legs optional extra 17/6. Set of 4.



50 W POWER AMPLIFIER, MA-50. Ideal for PA work, electronic organs etc. **£27.18.0 Assembled £19.18.0 Kit**

DAYSTROM LTD.

Dept. P.W.-11, GLOUCESTER, ENGLAND

A subsidiary of Western Instruments Group, manufacturers of the **WORLD'S LARGEST-SELLING ELECTRONIC KITS**

SPEAKERS FOR YOUR OWN ENCLOSURE

- 12" Heavy-duty Bass (Fane 122/12) **£7.7.0.**
- 2" Tweeter (Fane 301) **£3.1.6.**
- (both as used in the Cotswold systems)
- 12" Goodman's General Purpose G81A **£5.10.6.**
- 8" Goodman's General Purpose G8 **£1.8.6.**
- Two Speakers + Cross-over System, SCM-1.
- (As used in model SSU-1) with details for enclosure **£4.12.0.**

MONEY BACK GUARANTEE

Daystrom Ltd. unconditionally guarantee that each Heathkit product assembled in accordance with our easy-to-understand instruction manual must meet our published specifications for performance or the purchase price will be cheerfully refunded.








Please send me **FREE BRITISH CATALOGUE (Yes/No)**

Full details of model(s).....


NAME

ADDRESS

Just a few of our BARGAINS

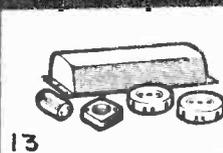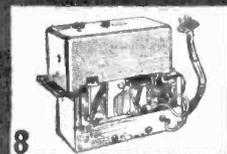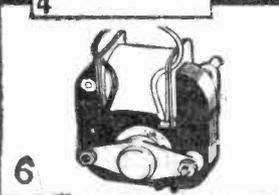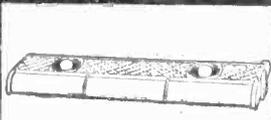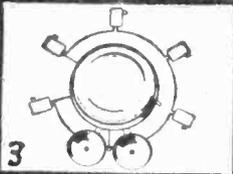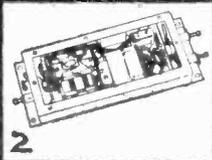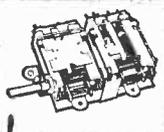

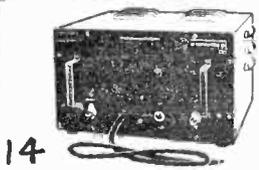FREE OFFER
ELECTRIC
SOLDERING IRON
with the
POCKET
MULTI-METER
See item No. 7
for further details



- 1. CYLINDON A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION.** Size 2 1/2 x 2 1/2 in. approx. By famous manufacturer. A.M. 1 F. 470 Kc/s. F.M. 1-1 F. 10.7 Mc/s. A.M. coverage from 1620 Kc/s-525 Kc/s. F.M. coverage 108 Mc/s-88 Mc/s. Circuit diagrams 2/6. FREE with Tuner, 1st, 2nd, 3rd A.M. I.F.'s, 1st, 2nd, 3rd and 4th F.M. I.F.'s V.H.F. Osc. choke. A.M. I.F. trap, A.P. 114 and A.P. 115. All the above at the R.P. end of an A.M./F.M. receiver car radio, etc. The above six items £2,10.0.
- 2. TRANSISTOR INVERTOR.** 50 v. D.C. Input. Output 240 v. A.C. 40 watts incorporating transformers, choke, condensers and 2 Get578. In solid 16 gauge aluminium case size 15 x 6 x 2 1/2 in., by famous manufacturer, 19/6, plus 6/- P. & P.
- 3. RINGO BURGLAR ALARM SYSTEM.** A.C. mains, 200/240 volt. Fire salvage slightly tarnished. List price 7 gns. Our price, complete with double gong bell five micro switches and full instructions. 49/6. P. & P. 4/-.
- 4. SIGNAL GENERATORS.** Cash £7.5.0. P. & P. 6/6. Coverage 100 Kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6 1/2 x 5 1/2 in. Three miniature valves and Metal Rectifier. A.C. mains 200/250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 multivolts, C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.
- 5. FLUORESCENT LIGHT FITTING.** Twin 40 watt 200/250 v. less tubes 59/6. P. & P. 6/-.
- 6. A.C. MAINS MOTOR.** Can be used for a variety of purposes, silent running, satisfactory in every way. 230/250 v. A.C., 9/8. P. & P. 2/-.
- 7. POCKET MULTI-METER.** Size 3 1/2 x 2 1/2 x 1 1/2 in. Meter size 2 1/2 x 1 1/2 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts. 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100K Ω. Complete with test probe, battery and full instructions. 35/-. P. & P. 9/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.
- 8. CHANNEL TUNER I.F.** 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PC180 and PC084 (in series). Cover BBC and ITA rings. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/-. P. & P. 3/-.
- 9. THE MOTORIST'S REV. COUNTER.** Kit of parts comprising 270 degree 3in. moving coil movement. Manufacturer's price plus the movement would be at least £7. Complete with full instructions and circuit diagram. Scale calibrated up to 8,000 r.p.m. Can be used with any 4 or 6 cylinder car. 49/6, plus 3/6 P. & P.
- 10. B.S.R. MONARCH UA14 WITH FULL FI HEAD.** 4-speed, plays 10 records, 12in., 10in. or 7 1/2 in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position: colour brown. Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 1/2 in., below baseboard 2 1/2 in. Fitted with Full FI turnover crystal head, 25.19.8. P. & P. 6/6.
- 11. 50 MICRO-AMP METER** movement by world famous manufacturer. Size 3 x 2 1/2 in., 25/- plus 1/6 P. & P.
- 12. 8-watt PUSH-PULL 5 VALVE AMPLIFIER plus METAL RECTIFIER.** A.C. mains 200-250v. Size 10 1/2 x 6 1/2 x 2 1/2 in. 5 valves. For use with all makes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. 2 dB down to 20 kc/s. Output 8 watts at 5 percent total distortion. Note level 40 dB down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with 8Ω or L.P. records, musical instruments such as guitars, etc. Suitable for small halls. 23.19.6. P. & P. 7/-. Crystal mike to suit, 15/- P. & P. 2/- 8in. F.M. Speaker to suit, 12/6. P. & P. 2/-.
- 13. FLUORESCENT LIGHT KIT.** 40 watt fluorescent lighting kit comprising Siemens choke. 2 16-pin holders starter holder and starter, 11/6. P. & P. 3/-. Twin 20 choke instant start, complete with 4 bi-pin 200/250 v. holders, 11/6. P. & P. 4/-. Twin 40 choke instant start with 4 bi-pin 200/250 v. holders, 17/6. P. & P. 4/-. P. & P. 4/-.
- 14. FIXED FREQUENCY SIGNAL GENERATOR.** (Crystal control in metal) case, size 10 x 6 x 6 in. Incorporating two FC13 valves, mains transformer, metal rectifier, choke, indicator, lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new. 39/6, plus 6/- P. & P. A.C. mains 200-250 volts.
- 15. SILICON RECTIFIERS.** 250 v. P.I.V. 750 mA. Six for 7/6 post paid.

RADIO & T.V. COMPONENTS (ACTON) LTD.

21b High Street, Acton, London, W.3.

All enquiries S.A.E. Goods not despatched outside U.K.

Shop Hours 9 a.m.—6 p.m. Early closing Wednesday.

SPECIAL OFFER! FROM R. & T. V. LTD.

Elegant Seven

COMBINED PORTABLE & CAR RADIO

The Radio with the STAR features
4½ in. SPEAKER


- ★ 7-transistor superhet. Output 350mW.
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12¼ x 8½ x 3½ in.
- ★ Horizontal tuning scale, size 11¼ x 2⅝ in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. 470 Kc/s.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket.
- ★ Full after-sale service.

ONLY
£4.19.6

Plus 5/6 P. & P. Parts list & circuit diagram 2/6. FREE with parts.

SPECIAL OFFER—POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer etc. A.C. mains 200-250v. Output 9v, 100mA, 7/6.

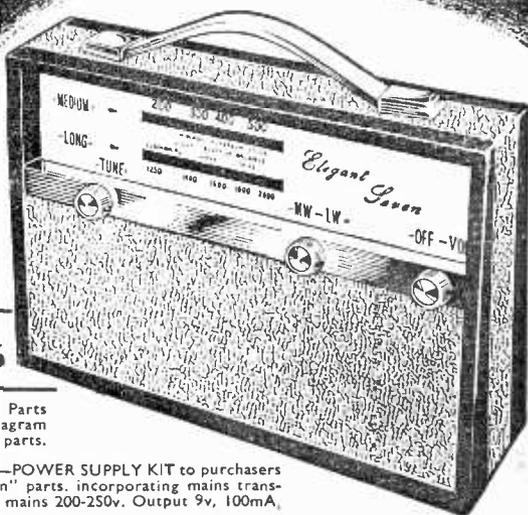Goods not despatched outside U.K. All enquiries S.A.E. Terms C.W.O.



RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3

Open 9 a.m.—6 p.m. including Sats. Early closing Wed.

BARGAINS FROM BROADWAY ELECTRONICS

12in. ALTHAM SPEAKER with built-in tweeter. 3 ohm or 15 ohm 7,000 Gauss Magnet. Only 29/6, postage 3/6.
L.S.H.75 ELECTROSTATIC TWEETER—2/6 with diagram.
BAYDON CABINET (17 x 15 x 8in.) designed to take a 12in. Heavy Duty Speaker. 50/-, postage 7/6.

ATTRACTIVE TWO-TONED CABINET. 11 x 6 x 5½ in., room for small amplifier, fitted with ex T.V. 5in. speaker. Only 19/6, post. 2/6. The Famous B.M. 3XTAL MICROPHONE with neck lanyard, 32/6 table stand for above, 9/6 extra. Xtal Insert. 7/3.

GUITAR PICK-UP, complete with clip and screened lead, 15/-, 3-WAY PUSH-BUTTON UNITS. Each button operates a 4-pole, 2-way switch, 4/6.

BARGAINS IN TRANSISTORS. Mullard RF Packs, OC44, two C45, 12/6; AF Packs, OC8D, 12/6; OC44, 3/6; OC45, 3/6; OC71, 2/6; OC72, 3/6; OA81 diode, 2/3; AF115, 6/6; AF117, 6/6; ORP12 Light Cell, 7/6; OC29, 12/6; OC35, 12/6.

TRANSISTOR ELECTROLYTICS. 1, 2, 4, 5, 8, 10, 16, 32, 50 100mF d—all at 15 volts. 1/3 each.

MEMICHAEL TELESCOPIC TV AERIAL. 23in. extends to 45in. Fitted with co-ax plug will suit any set. Only 7/6.

CARTRIDGES. Acos 67-1G Low Output, 67-2G Medium Output GP59-5 High Output, Garrard GC2 or GC3, all with mounting brackets, 15/-. Ronette Stereo with mounting bracket, 25/-.

EARPIECES with cord and 3.5 mm. plug. 8 ohm magnetic, 3/6; 250 ohm, 4/6; 180 ohm magnetic with clip, 6/6; Xtal, 4/6; 3.5 mm. plugs with nice long shank, complete with jack, 3/6; 3.5 mm. plugs with nice long shank, complete with jack, screened 4/6.

TOGGLE SWITCHES. Single pole with on-off plate, 2/6.

NEON PANEL LIGHTS. 240c A.C. Arcoelectric, 2/6.

TERMS: C.W.O. OR C.O.D.

BROADWAY ELECTRONICS


92 MITCHAM ROAD, TOOTING, S.W.17

Phone: BALham 3984

(four minutes from Tooting Broadway Underground Station)

EX-RENTAL T.V. SETS

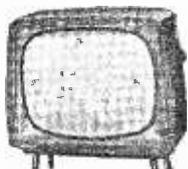Coloured FREE LIST. Demonstrations daily from our large selection



17in. £11.10.0
14in. £7.10.0

12 months written guarantee.

Channels for all areas.

Carr. 14in. 20/-
17in. 30/-
Personal Collection Advised

REGUNNED TUBES

21 in. 99/6
17 in. 79/6
15,14 59/6
12 in.



Guaranteed one year Carr. 10/6. Add 10/- refundable on OLD TUBE (110° Tubes in stock).

EX-MAINTENANCE TESTED TUBES

17in. — 35/-. 14in. — 15/-. Carriage 5/- Satisfaction Guaranteed.

AERIALS. BBC/ITA combined loft and room aerials—From 25/-
BBC2,UHF and colour aerials—From 37.6
SEND FOR FREE LIST.

VALVES 9d. each. 1,000's available. Send for list.

CONDENSERS. 100—10/-. New. Assorted electrolytic and pfs. P. & P. 2/6.
V/CONTROLS. 20—10/-. A selection of types and sizes. P. & P. 2/6.

SPEAKERS, 7/9. 6in., 8in., 7 x 4in., and 8 x 3in. Ex. mtd. Salvage. P. & P. 2/3.


NEONS. 25 box 2/-. (S.B.C.D.P. fittings). Mains tester and visual reminders. P. & P. 1/-.
Telephone Handset 15/6 pair

G.P.O. pattern House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.

Phone ILFord 6001/2/3 DUKE & CO. (LONDON) LTD. Stamp For Free List
621/3 Romford Road, Manor Park, E.12
Liverpool St.—Manor PK.—0 mins.



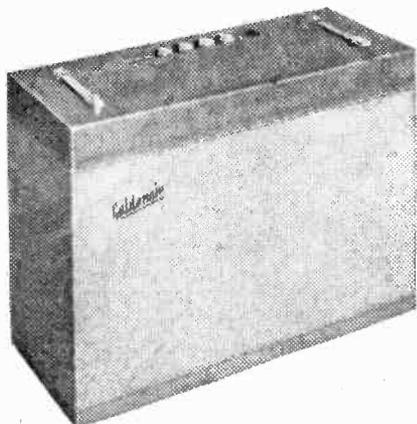The **Coldenair** GROUP-MASTER 30 WATT GUITAR AMPLIFIER



A VERSATILE UNIT FOR INSTRUMENTALISTS AND VOCAL GROUPS

being suitable for clubs and public address

- Ideal for bass, lead or rhythm guitar, and all other musical instruments.
- ★ The two 12 inch 25 watt heavy duty loudspeakers are specially designed for this type of amplifier, and give outstanding reproduction.
- ★ Robust attractive two-tone finished cabinet of compact size, 28" x 20" x 10 1/2" fitted with carrying handles.
- ★ For standard AC mains 50 c/s operation.
- ★ Four inputs provided can be used simultaneously with instrument pickups or mikes.
- ★ Separate Bass and Treble controls are incorporated.
- ★ A polished black control panel is fitted to the amplifier with distinctively marked control indications set in gold relief.

Go **Coldenair**

TWICE THE QUALITY AT HALF THE PRICE

Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade. Send S.A.E. for leaflet.



or deposit of £4.12.0 and twelve monthly payments of £3.12.5.
Carriage and insurance 17/6 to be sent with deposit.

The **Coldenair** "THIRTY" HI-FI AMPLIFIER

A high quality 30 watt amplifier developed for use in large halls and clubs etc. Ideal for bass, lead or rhythm guitars, schools, dance halls, theatres and public address. Suitable for any type of mike or pickup.

Valve line-up: two 6F86; one ECC83; one GZ34; two EL34.

Four separate inputs are provided with two volume controls. Bass and Treble controls are incorporated. Amplifier operates on standard 50 c/s mains. 3 ohm and 15 ohm speakers may be used.

Perforated cover with carrying handles can be provided if required, price


21/-

Go **Coldenair**

**TWICE THE QUALITY
HALF THE PRICE**

Send for leaflet of suitable loudspeakers that we can supply.

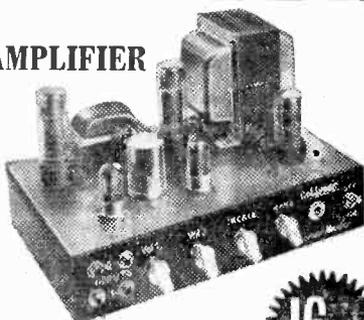
Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade.
Send S.A.E. for illustrated leaflet.



or deposit of £1.16.0 and twelve monthly payments of £1.9.2.
Carriage 15/- to be sent with deposit.

NORTHCO BATTERY CHARGER

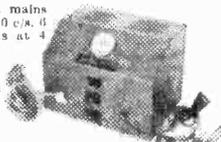For all A.C. mains 200/250 v., 50 c/s. 6 and 12 volts at 4 amps. Fitted ammeter. Robust louvered steel case. Ready for use complete with leads and battery clips. 12 months guarantee.



Price 69/11. P. & P. 4/6.

MANUFACTURER'S SURPLUS 5 WATT AMPLIFIER

Suitable for guitars, record decks and microphone. Cabinet size approx. 13 x 18 x 7 1/2 in. The cabinet is well made and attractively finished. Volume, bass and treble controls incorporated. Price £9.19.6. P. & P. 10/-. Only a few left.

CRYSTAL SET

A wonderful educational kit for all children. Provides hours of amusement while following the easy step by step instructions. It is powered entirely by wireless waves, eliminating the expense of batteries. No soldering required. Receives all main stations. Price 25/-, P. & P. 2/6.



SONA STREAMLINE MICROPHONE



Omni-directional response 100-10,000 c/s. Output level 92 dB. Built in on/off switch. Provision for conversion to hand-held, cord suspended or stand mike. Attractive satin chrome finish.

Microphone 37/6 P. & P. 1/9.
Desk Stand 10/- P. & P. 1/9.
Floor Stands Available.

BATTERY CHARGE ADJUSTERS

● Charge Rate Adjuster. ● Government manufacture. ● Easily fitted to charging circuit. 3/6 each: 2 for 6/6. P. & P. 2/6.

HANDY POWER PACK

Housed in compact metal case. 200/250 v. A.C. mains. Output 250 v. 60 mA fully smoothed, 6.3 at 2 amps. Can be used for powering almost any pre-amp, or radio tuner. Price 39/6. P. & P. 2/6.



TRANSMITTER RECEIVER NO. 46

Compactly built to be carried by one man. This has a range of up to 10 miles and being crystal controlled tuning is avoided and operation is as accurate as a telephone. Frequency 400-1 Mc/s. Complete station comprising receiver, transmitter, rod aerial, one pair of headphones and microphones in canvas carrying bag. Crystal power pack available for authorised use only. 35/- per set.



Price per station.
£4.10.0 P. & P. 10/- each.
Two stations for **£9.10.0** Post free.

R.A.F. SHORT WAVE RECEIVER

35 to 40 Mc/s. Power supplies 12 volts and 250 volts D.C., in excellent condition with exceptionally fine slow-motion tuning and clean component layout. Price **£219.6.** P. & P. 6/-.

LIGHTWEIGHT GRAMPHONE PICK-UP ARM

Complete with Acous hi-fi turnover cartridge. Price **27/6.** P. & P. 1/-.

DOUBLE THROAT MIKES

Double throat mikes. Can be adapted for use with musical instruments. 5/11. P. & P. 9d.

No. 19 SET INSTRUCTION HANDBOOK 3/6 each P. & P. 6d.

1155 INSTRUCTION HANDBOOK 3/6 each P. & P. 6d.

H.R.O. INSTRUCTION HANDBOOK 3/6 each P. & P. 6d.

IMPEDANCE MATCHING UNIT

An impedance matching device enabling both high and low resistance phones to be used from any given piece of equipment. Incorporates a matching transformer enclosed in a metal case with pasolux terminal board. Four standard jack sockets enabling four pairs of phones to be used simultaneously—two LR and two LR. Price 19/11. P. & P. 2/6.

19/11

HIGH IMPEDANCE HEADPHONES

Lightweight. Suitable for all applications. 11/- per pair. P. & P. 1/6. 2 pairs for 22/6, post free.

SONA STREAMLINE BM3 MICROPHONE CRYSTAL INSERTS
Price 7/6. P. & P. 9d.

NEW WALK ROUND STORE OPEN IN LAMBERT'S ARCADE, LOWER BRIGGATE, LEEDS 1. NEXT TO HALFORDS CYCLE SHOP. OPEN ALL DAY SATURDAY. 4 HOUR DESPATCH SERVICE. ALL MAIL ORDERS TO OUR BRIGGATE HOUSE ADDRESS.

Postage rates apply to U.K. only

TERMS:
CASH WITH ORDER.
5/- EXTRA ON C.O.D.
ORDERS
No C.O.D. under 30/-.



SONA ELECTRONIC CO. LTD. (Dept. PW11), BRIGGATE HSE, 13 ALBION PL., LEEDS



Mains Powered No. 19 Short Wave Receiver



This mains powered short wave receiver has a built in mains power pack and requires only headphones for immediate operation.

£5.19.6 P. & P. 10/-.

Suitable headphone 15/-, P. & P. 2/6. During an evenings' testing on this excellent receiver, we obtained clear reception from scores of stations, many of them thousands of miles distant, including ship stations, Government transmitters, maritime broadcasts and also the short wave radio Luxembourg broadcasts.

MICRO ALLOY TRANSISTORS

Mat 100	7/9
Mat 101	8/8
Mat 120	7/9
Mat 121	8/8

Above MAT's postage paid.
Ferrite Slab Aerials suitable for transistor sets 3/-, P. & P. 9d.

RESISTOR COLOUR CODE INDICATOR

Enables you to determine value of resistor at a glance. A must for the constructor. Price 1/6. P. & P. 3d.

HI-FI GT50 RADIO JACK

MAKE A RADIO RECEIVER OUT OF YOUR AMPLIFIER. Full medium wave coverage. Ideal for all tape recorders, amplifiers, etc. No batteries required—just plug in. 29/-.




FOUR IMPORTANT BOOKS

Tested superhet circuits for short wave and communication receivers using MAT's. Price 6/-. At a Glance radio valve and TV tube equivalents. Price 3/6. Transistor circuits for radio control models. Price 7/6. Tested short wave receiver circuits using MAT's. Price 5/-. Special offer to P.W. readers, all four books for **£11.0.** Post free.

TEST SET TYPE 46

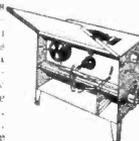Will radiate a continuous note. Range 1.250 Mc/s. 20,000 Mc/s. 12—24 Mc/s. 5 switched bands, contains VR21 valve and has a precision slow motion tuning unit enclosed in grey metal case, rod aerial base on side. Good condition. Power requirement 2 v., 90—120 v. Battery space provided. Due to large purchase reduced to only **2 gns.** P. & P. 6/6



RF FIELD INDICATORS

Designed for checking the radiation from a transmitting antenna. The sensitivity can be controlled by adjustment of the panel control, the antenna length, or by increasing the distance from the radiator. Frequency range 1 to 250 Mc/s. 200mA D.C. Complete with instruction book. Post free.



67/6

STABILISED POWER SUPPLY UNIT

Valuable unit comprising mains transformer, neon stabiliser etc., 50 c/s mains input 110 v. or 80 v. Stabilised output 130 v. D.C. and 6.3 v. A.C. Should make ideal battery eliminator. Price 29/6. P. & P. 5/-.



MINIATURE WIRE-WOUND 6 OHM POTENTIOMETERS

With standard spindle. 2/5 each. P. & P. 6d. 2 for 4/6. Post free.

LEAD ACID ACCUMULATORS (Unspillable)

2 volts at 16 A.H. Brand new. Size 4 x 7 x 2 1/2 in. 4/11 each. 3 for 12/6. P. & P. 3/- per cell.



SENSITIVE MULTIMETER



20,000 ohm per volt. 1% resistance used throughout. Single control system for all ranges. Compact and lightweight. Highly accurate. **£5.10.0** P. & P. 3/-.

MAINS TRANSFORMER

TYPE 1. 250/250 v. 50 c/s primaries filament type. Secondary 6.3 v. at 2 amps. 6/11. P. & P. 2/-.
TYPE 2. 250/250 v. 50 c/s primaries. Secondary tapped as follows: 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v. all at 4 amps. 39/6. P. & P. 3/6.
TYPE 3. 250/250 v. 50 c/s primaries. Secondary tapped as follows: 5 v., 11 v., 17 v., at 4 amps. 35/-, P. & P. 3/6.
TYPE 4. 450-0-450. 250 mA. 6.3 v. at 4 amps. 5 v. at 3 amps. fully shrouded upright mounting. 55/-, P. & P. 5/-.

VALVE SALE

All valves 2/6 each. P. & P. 9d. 2 for 4/6. P. & P. 6d. 6K76, 6E0, 6H6, 6F92, 6K80, 6B34, 1L4.

TRADE SUPPLIED
ORDERS FROM
ABROAD WELCOMED

Telephone: 34703

LASKY'S RADIO

Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.

THE SKYROVER & SKYROVER De Luxe

★ LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THESE WELL-KNOWN SETS



The SKYROVER

Controls: Waveband Selector, Volume Control with on/off switch, Tuning Control in plastic cabinet, size 10 x 8 1/2 x 3 1/2 in. with metal trim and carrying handle.
Can now be built for **£8.19.6** P. & P. 5/-.
H.P. Terms: 20/- deposit and 11 months, at 18/6.

A simple additional circuit provides coverage of the 1100/1550 M. band (including 1500 M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data **Only 10/- extra** Post Free.
This conversion is suitable for both models that have already been constructed.

GENERAL SPECIFICATION:


7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operates from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94 M., and also 4 separate switched band-spread ranges, 13M., 16M., 19M and 25M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.

SPECIFICATION:

Superhet 470 Kc/s. All Mullard Transistors and Diode. Uses 4-U2 batteries. 5in. Ceramic Magnet P.M. Speaker Easy to read Dial Scale, Band Spread Tuning, 500 MW Output, Telescopic Aerial & Ferrite Rod Aerial. **WAVEBAND COVERAGE:** 180-576M; 31-94M and Band Spread on 13, 16, 19 and 25 metre Bands.

The SKYROVER DE LUXE

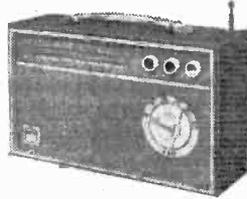Tone Control Circuit is incorporated, with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet size 11 1/2 x 9 1/2 x 3 1/2 in. covered with a washable material with plastic trim and carrying handle. Also car aerial socket fitted.
Can now be built for **£10.19.6** P. & P. 5/-.



H.P. Terms: 25/- deposit and 11 months, at 20/-. Data for each receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All Components Available Separately.

The "Sixteen" Multirange METER KIT

This outstanding meter was featured by *Practical Wireless* in the Jan. '64 issue. Lasky's are now able to offer the complete kit of parts as specified by the designer.

RANGE SPECIFICATION: D.C. volts: 0-2.5-25-50-250-500 at 20,000 Ω/V. A.C. volts: 0-25-50-250-500 at 1,000 Ω/V. D.C. current: 0-50 μA, 0-2.5-50-250 mA. Resistance: 0-2,000 Ω, 0-200k Ω, 0-20M Ω. Basic movement: 40 μA i.s.d. moving coil. With universal slant full scale deflection current is 50 μA. Size/finish: Black plastic case, 3 1/2 x 5 1/2 x 1 1/2 in. Controls: 12 position range switch; separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment pot, meter; meter zero. External connections: Two 4mm. sockets for test lead plugs. Power requirements: One 15V. and one 1.5V. batteries. Complete with all parts and full construction details.

Data and circuit available separately 2/6 refunded if all parts bought. Pair of Batteries, 2/5 extra.

LASKY'S PRICE £5.19.6

P. & P. 5/-

H.P. Terms: 21/- deposit and 5 months at 21/-.

TWO NEW SUPER MINIATURE POCKET RADIOS



THE SINCLAIR MICRO-6

A marvel of modern miniaturisation—truly amazing performance. Without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data. **Can be built for only 59/6** Mercury cell 1/11 extra (2 required). All parts sold separately.


THE SINCLAIR SIBLIME

The new 2-transistor pocket radio size only 2 1/2 in. x 1 1/2 in. Easy to assemble. **CAN BE BUILT FOR 49/6**

Self-contained pocket radio Size only 1 1/2 x 1 1/2 x 1 1/2 in.

E.M.I. 4-SPEED RECORD PLAYER


New, unused and individually boxed fitted with lightweight pick-up with ACOS G.P. 73/2 stereo cartridge. Cabinet space required 13 1/2 x 12 1/2 x 4 1/2 in. A 9in. metal turntable is fitted. For use on 200/250 volt A.C. Mains, with Auto-stop. The stereo cartridge will play all types of Mono Records, 78's, L.P.'s etc., but if desired a G.P. 67 LP/78 Mono cartridge will be supplied in lieu of the G.P. 73 at no difference in cost.

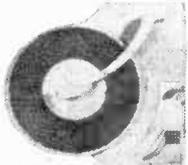

LASKY'S PRICE 79/6 P. & P. 9/6 extra.

The "REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker
★ All components mounted on a single printed circuit board. ★ Full medium and long wave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in., Blue/Grey or all Grey. ★ Easy to read dial.
★ External socket for car aerial.
★ I.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery.
★ Full comprehensive data supplied with each receiver. — All coils and I.F.'s etc. fully wound ready for immediate assembly.

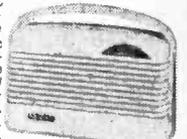

An Outstanding Receiver. **LASKY'S PRICE** for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data. Can be built for **£5.19.6** P. & P. 4/6

PP9 Batt. 3/9. Data and instructions separately 2/6. Refunded if you purchase the parcel.

REALISTIC Seven DE LUXE

With the same specification as standard model—PLUS a superior wood cabinet in contemporary styling. ALSO a full vision circular dial. **FOR ONLY £1 EXTRA** P. & P. as std. model

RECORD PLAYERS

45 r.p.m. 8 volt Batt. operated. Complete with pick-up fitted crystal cartridge. Size only 7 1/2 in. x 6 in. Fitted auto. stop and start. New and perfect.



45 r.p.m. Model **49/6** P. & P. 2/6
2 speed model for 33 and 45 **69/6 P. & P. 4/6**
45 r.p.m. (as illustrated) **8/6** 2/6

DEAC RECHARGEABLE NICKEL CADMIUM CELLS

Rating 1.22 v. 3.5 AH at 10 hour rate. 1001 uses for model makers, miniature equipment, portable radios, transistor radios, TV's, tape recs, trans receivers, photo flash etc. Hermetically sealed. Size 3 1/2 x 1 1/2 x 1 1/2 in. Listed at 35/- each. **LASKY'S PRICE 15/-** Post Free. Bank of 9 7/8/6.



TRANSISTORISED TELEPHONE AMPLIFIER

Powerfully amplifies the incoming call. The pick-up is suction fixed to phone. Battery-operated at negligible cost. Fitted with on/off switch and vol. control. Size: 4 1/2 x 3 x 1 1/2 in. Complete with PP3 battery. **LASKY'S PRICE 69/6** P. & P. 2/6.

GUITAR PICK-UPS

CGM5 Crystal-finger imp. Size only 1 1/2 x 1 1/2 in. Clips to tuner board—no screws. Complete with cable. **LASKY'S PRICE 15/11.** P. & P. 1/-
CGM35. Fully adjustable pick-up position carrier. Simply fixed. Separate tone and volume control. Heavy chrome finish. Pick-up size 3 x 1 1/2 in., control size 2 1/2 x 1 1/2 in. Complete with long lead and jack plug. **LASKY'S PRICE 59/6** P. & P. 1/6

LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

Service in Great Britain to both & HI-FI ENTHUSIASTS

TAPE RECORDERS · RECORD PLAYERS · AMPLIFIERS ETC. COMPLETE MONO/STEREO SYSTEMS TO YOUR SPEC.



TRANSISTORISED MICROPHONE MIXER

The Harrow will mix 4 high impedance channels: mikes, tape rec's, tuners, grams, etc. 9 v. battery operated. Neatly styled, size only 6 x 2 1/2 x 2 1/2 in. Standard jack sockets. Complete with PP3 batt., full circuit diagram and operating instructions.

Model TM4 Mono 59/6 P. & P. 2/6

Model SM5 Stereo 72/6 P. & P. 2/6

SPEAKERS SPECIAL OFFER 12in. FANE

HEAVY DUTY DUAL CONE HI-FI SPEAKER

Type 122/17A—listed at 12 gns. Power handling 25 watts—15 ohms imp. Flux density 17,000 gauss. Special Anisotropic magnet. Limited stock.



LASKY'S PRICE £6.19.6 P. & P. 5/-

TYPE 8CX1 8in. HI-FI SPEAKER—(IMPORTED) Power handling 10 watts—15 ohms impedance. LASKY'S PRICE 6 Gns. P. & P. 5/-

THE HARROW CV1 VARIABLE CROSSOVER

Gives variable volume control of Woofer and Tweeter. Strong metal construction. Size 4 1/2 x 1 1/2 in. Screw lag connections. LASKY'S PRICE 22/6 P. & P. 1/6

NOW IN STOCK THE NEW STUDIO RANGE OF CELESTION HI-FI SPEAKERS

"HARROW" POWER PACK

Battery eliminator—converts your battery portable to A.C. mains. Replaces 6 v., 4 1/2 v. or 9 v. batteries. State voltage required when ordering. Size only 3 x 2 x 2 1/2 in. LASKY'S PRICE 29/6 P. & P. 1/6


LAFAYETTE TAPE

Famous American Brand—Fully Guaranteed

5in. Double play, 1,200ft., Mylar base	15	0
5in. Long play, 900ft., Acetate base	8	0
5in. Standard play, 900ft., P.V.C. base	8	0
7in. Long play, 1,200ft., Mylar base	15	0
5 1/2in. Double play, 1,900ft., Mylar base	22	6
5 1/2in. Long play, 1,200ft., Acetate base	12	8
5 1/2in. Standard play, 850ft., P.V.C. base	11	6
7in. Standard play, 1,200ft., Mylar base	12	6
7in. Long play, 1,900ft., Mylar base	19	6
7in. Double play, 2,400ft., Mylar base	25	0
7in. Long play, 1,800ft., Acetate base	15	0
3in. Message tape, 150ft.	3	6
3in. Message tape, 225ft.	4	11
3in. Message tape, 500ft.	7	6
3in. Triple play, 450ft., Mylar base	12	6
4in. Triple play, 900ft., Mylar base	22	6
5in. Triple play, 1,800ft., Mylar base	42	6
5 1/2in. Triple play, 2,400ft., Mylar base	55	0
7in. Triple play, 3,600ft., Mylar base	75	0


P. & P. 1/- extra per reel; 4 reels and over Post Free

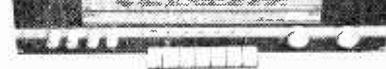THE NEW "KUBA" CONTINENTAL AM/FM STEREO RADIOGRAM CHASSIS



Long, medium and short waveband coverage plus VHF/FM. Piano key wave-changer. Separate five-wheel tuning on AM and FM. Bass, treble and balance controls. Magic-eye tuning indicator. Ferrite rod aerial. The very latest printed circuitry. Provision for multiplex adaptor. 5 valves—line up: ECC85, ECH81, ECC83, ELL80, EAF801. Full vision tuning scale size 2 1/2 x 6 in. Overall dimensions: 21 x 6 1/2 x 8 in. Made to the very highest standards.

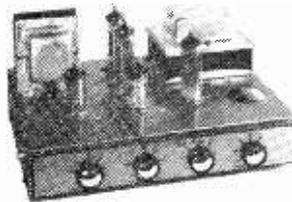LASKY'S PRICE 29 1/2 GNS. Carriage & Insurance 12/6 extra.



THE BH-14 HI-FI MONO 14 WATT AMPLIFIER KIT

High quality 14 watt power amplifier with bass and treble controls and separate volume controls on each input. Inputs: 1—5 m/v; 2—40 m/v. Output impedance 3 or 15 ohms. 5 valves—line up: 2 x EL84, 1 x 6X8, ECC83 and E251. Frequency response 15—20 Kc/s. Ideal for the discerning hi-fi enthusiast or for guitar amplifier. Gold hammer finish with distinctive Perspex front panel. Complete kit of parts with detailed construction data. LASKY'S 9 GNS. P. & P. Instruction book PRICE 7/6, avail. sep. 1/6. AVAILABLE READY BUILT AND TESTED. LASKY'S PRICE 11 GNS. P. & P. 7/6.



AUTOCHANGER SCOOP!!!

LASKY'S CAN NOW OFFER B.S.R. AUTOCHANGERS AT LOWEST EVER PRICES

All brand new and fully guaranteed—competes with cartridge and stylus.

UA14 4 speed, mains	£3.19.6
UA16 4 speed, mains	£4.19.6
UA14 4 speed, 9 v. battery operated	£5.19.6
UA20 4 speed, mains	£5.19.6

Add 5/- carriage and packing on each.

IT'S FABULOUS!! THE TRANSISTOGRAM

A portable battery operated fully transistorised Record Player for the music of your choice - any time and place! Made by famous British manufacturer, fully guaranteed. Size only 6 1/2 x 12 x 10 1/2 in., weight 10 lbs. Operates on 6 U2 torch batteries. 4 speeds—16 2/3, 33 1/3, 45 and 78 r.p.m. Goldring 83 gram record player unit with lightweight pick-up fitted with CM-90 turnover ceramic cartridge. Output 500 mw to 5in. ceramic magnet loudspeaker, fitted into lid for maximum sound distribution. Cabinet constructed of wood, covered in two tone (pale blue-grey) leathercloth. Fitted carrying handle and strong lid catches. High quality amplifier with tone and volume controls gives excellent reproduction at all speeds. Plays 7, 10 and 12in. records. Today's value 12 Gns.



LASKY'S PRICE £6.19.6

Carriage & Insurance 7/6. New, boxed and guaranteed—ex. batts.

CRYSTAL PICK-UP CARTRIDGES LOWEST EVER PRICES!

All complete with Styli L.P. and Standard (and Stereo where shown) fully guaranteed. Standard Fitting will fit most P.U. Arms and Heads. Postage 1/- each extra.

STEREO	MONO
Acostereo 73/1, 2 sapphires	Garrard Magnetic T.O.M.2
Acostereo 73/2, Diamond LP/Stereo and sapphire std.	Acos GP.5/3
Ronette Stereo O.V. Turnover, 2 sapphires	Acos GP.65/3
Ronette Stereo type 105 and 106, 2 sapphires	Acos GP.65/1
Ronette Stereo type 105 and 106 Diamond LP/Stereo and sapphire Std.	Acos GP.57/1

AND EVEN LOWER PRICES!

Mono C.T.1	4	11	Sonotone #7, stereo, 2 sapphires	19	11
Collaro Type 1, stereo, 2 sapphires	15	0	Sonotone 2TA, mono, 2 sapphires	15	0
Collar S.C.1, Diamond LP Stereo	17	6	Postage 1/- each extra.		

207 EDGWARE ROAD, LONDON, W.2.

33 TOTTENHAM COURT ROAD, W.1.

152/3 FLEET STREET, LONDON, E.C.4.

Near Praed St. PADDINGTON 3271/2

Nearest Stn., Goudge St. MUSEUM 2605

Telephone: Fleet Street 2833

BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W., Edgware Rd.

Open all day Thursday. Early closing Sat

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop your talents and help you to success.

STUDY IS EASY with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. **MODERATE FEES INCLUDE ALL BOOKS.**

Take the right course now . . .

ADVERTISING & ART

Copywriting
Layout & Typography
Commercial Illustrating
Oil & Water Colour

BUILDING & CIVIL ENG'NG

Architecture, Bricklaying
Building Construction
Builders' Draughtsman
Builders' Quantities
Interior Decoration
Quantity Surveying
Heating & Ventilation
Carpentry & Joinery

COMMERCE

Book-keeping
Accountancy & Costing
Business Training
Office Training
Purchasing, Storekeeping
Secretaryship

SHORTHAND & TYPING

Computer Programming
Small Business Owners

DRAUGHTSMANSHIP

Architectural, Mechanical
Drawing Office Practice

ELECTRONICS

Electronic Technicians
Industrial Electronics

FARMING

Arable & Livestock
Pig & Poultry Keeping
Rabbits & Chickens

GENERAL EDUCATION

G.C.E. subjects at Ordinary & Advanced Level
Good English
Foreign Languages

INTENSIVE COACHING for all principal examinations

—G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management, Radio, Architecture and Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

Start today the I.C.S. way!

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 172)
Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....


Address.....

Occupation

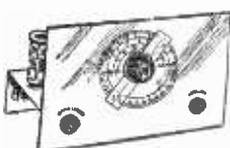11.64

INTERNATIONAL CORRESPONDENCE SCHOOLS

LISTEN TO THE WORLD on TELSTAR our I-VALVE SHORT WAVE RADIO



Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 16-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. **Total Building Costs 35/-** P. & P. 2/-.

All parts available separately

READY TO USE POCKET RADIO



P. & P. 2/- **9/11**
Covers Medium waveband. No batteries needed. Complete with earpiece

R.C.S. PERSONAL SET

Designed for personal listening without disturbing others. Supplied complete with battery and earpiece—no extras to buy! Sensitive one transistor diode circuit gives quality reproduction over medium wave band. Protective case with large tuning dial. Ideal for use as tape tuner. Size only 3 1/2 x 2 1/2 x 1 1/2 in. **27/6** P. & P. 2/-.



BATTERY ELIMINATORS

The ideal economical and safe way of running any TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. requiring voltages shown. Types Available: 9 v.; 6 v.; 4 1/2 v. (single output). Size 3 1/2 x 3 1/2 in. PRICE 39/6 each. P. & P. 2/9. 9 v. + 9 v.; 6 v. + 6 v. or 4 1/2 v. + 4 1/2 v. (Two separate outputs). Size 3 1/2 x 3 1/2 in. PRICE 42/6 each. P. & P. 2/9. (Please state output required.) All the above units are completely isolated from mains by double wound transformer ensuring 100% safety

FOR THE CONSTRUCTOR

Easy to build CRYSTAL RECEIVER, 8/8. P. & P. 2/-.
Easy to build PERSONAL SET with earpiece, 27/6. P. & P. 2/-.
Easy to build 3-TRANSISTOR SET with speaker, 37/6. P. & P. 2/-.

All parts available separately

R.C.S. PRODUCTS (RADIOS) LTD.

11 Oliver Rd., London, E.17. (Mail Order only)
Export Trade Enquiries Invited

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1A5, 1T4, 3Z5, 3V4, DAF91, DF91, DK91, DL92, DL94: Set of 4 for 15/-, DAF96, DF96, DK96, DL96: 4 for 23/6.

1A7GT	7/6	6X6GT	6/6	1F91	2/6	EF42	4/0	PCF82	6/0	U282	11/9
1B3	6/6	7H7	2/6	1F96	6/6	EF80	4/3	PCF84	5/6	U291	9/6
1HG6T	8/3	7C5	7/6	DH75	3/6	EF85	5/6	PCF86 1A4	1/60	U301	15/6
1N6GT	9/6	7C6	7/6	DH77	3/6	EF86	6/3	PCLE2	6/6	U4020	5/9
1R5	4/0	7H7	5/9	DH81	12/6	EF89	4/3	PCLE3	9/6	UAB30	5/9
1A5	2/6	7M7	8/6	DK32	2/6	EF91	2/9	PCLE4	7/6	UAF42	8/6
1T4	2/6	7Y4	5/6	DK91	4/9	EF92	2/6	PCLE5	8/6	UHC41	6/3
3A5	6/0	12AT6	4/3	DK92	6/9	EL35	7/6	PCN4110	1/60	URK1	7/3
3Q4	4/10	12AT7	2/6	DK96	6/6	EL35	11/6	PCN4120	1/60	URK60	6/6
3B4	4/9	12A16	5/6	DL35	7/3	EL1	7/3	PEN44	6/6	URF89	6/6
3V4	5/6	12A17	4/9	DL35	6/9	EL4	4/9	PENB4 170	1/60	UCB2	5/6
6X4G	4/6	12A27	4/9	DL92	4/9	EM34	7/11	PEN383	9/6	UCC84	8/6
6Y3GT	5/6	12K7GT	4/3	DL96	5/6	EM30	5/6	PL36	8/6	UCG85	8/6
5Z40	7/6	12K9GT	3/9	DL96	6/6	EM41	7/9	PL81	7/6	UCF80	8/6
6AL5	2/6	12K9GT	4/3	EACR30	5/3	EM34	6/3	PL82	5/6	UCR42	7/6
6AQ5	6/6	19B6GG	6/6	EAF42	2/6	EM87	7/6	PL83	5/6	UCH81	6/6
6AT6	3/6	20P1	12/6	EB41	4/6	EY51	6/6	PL84	5/6	UCI82	7/6
6AA6	6/6	20P5	14/6	EB41	2/6	EY86	5/6	PL84	8/6	UCI83	8/6
6BE6	5/3	20P6	14/6	EB33	5/6	EZ40	6/6	PL85	7/9	UCF41	7/6
6B06G	12/6	25L6GT	4/9	EB41	7/3	EZ41	7/6	PL82	6/6	UCI82	8/6
6BH6	5/6	25L7GT	4/9	EBF80	6/6	EZ80	4/6	PL83	9/6	UF98	6/6
6B16	5/6	30P1	8/6	EBF89	6/6	EZ81	4/6	PL80	5/3	UL41	7/6
6B9G	4/6	30P1L3	9/6	ECC40	7/6	EW4500B83	PL81	5/6	UL44	15/6	
6F13	4/6	30P1L3	9/6	ECC81	3/9	KT32	5/6	PL82	5/6	UL46	8/6
6F14	9/6	30P1L4 12/3	ECC82	4/0	KT61	7/6	PL83	5/6	UL64	6/6	
6J5G	3/6	35A5	14/6	ECC85	7/6	KT63	8/9	PL88	7/6	UC7	7/6
6K7G	1/6	35L6GT	6/3	ECC84	6/3	KT66	12/3	R17	16/6	UW8	10/6
6K7GT	4/6	35Z4GT	4/11	EVC85	6/3	KTW61	4/9	TD4	7/9	UY21	7/6
6K9G	4/9	32K13	13/6	EVC80	5/3	MU14	5/6	TH2C	9/6	UY41	4/9
6K9GT	7/9	53K10	8/6	EVC82	5/3	MUS/PENB	PL233	5/6	UY85	5/6	
6P28	9/6	ACV/P212B	ECF86	10/9			12/6	U32	4/9	VP48	12/6
6Q7G	4/9	B36	4/6	ECH35	6/6	N15	4/10	U25	8/6	VP41	4/9
6Q7GT	7/6	CL33	9/6	ECH42	8/3	PC95	6/9	U26	8/6	W76	3/6
6R7G	9/6	CV1	12/6	EH81	6/6	PC97	7/6	U37	8/6	W77	2/6
6S7GT	5/6	DAC92	8/3	ECL90	6/3	PC84	5/6	U30	5/6	W79	10/6
6SNTG	3/9	DAF96	6/6	ECL92	7/6	PC85	5/6	U52	4/9	X31M	19/6
6V8G	3/9	DAF96	6/6	ECL96	8/6	PC88	9/9	U78	3/9	X109	17/6
6V8GT	6/6	DCS80	6/9	EF39	3/9	PCU89	8/6	U191	8/6	Y63	4/9
6X4	3/9	DF33	8/6	EF41	6/6	PCF86	8/6	U281	7/6	Z66	7/6

READERS RADIO

24 COLBER PLACE, STAMFORD HILL, LONDON N.16
STA. 4587

Post 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra.

STERN-GLYNE

Electronics Centres throughout Great Britain



THE "AIR KING"

Our highly successful six-transistor luxury portable with the "SLIM LINE" look. To build yourself, with printed circuit chassis for reliability and simplicity in construction. May be used as Car Radio with full MEDIUM wave and LONG wave coverage.

Look at these features:
★ 500 milliwatt output to high flux 7 x 3in. high fidelity loudspeaker

★ Six selected MULLARD TRANSISTORS in latest supersensitive circuit, plus germanium diode. ★ Compact size only 3 1/2 x 3 1/2

x 6in. high. ★ Attractive three-tone cabinet, black, dark grey and silver grey with gilt control knobs and all gilt fittings.

★ Coax. socket for car aerial. ★ Brand new guaranteed components. ★ Push-pull output. ★ Automatic volume control.

★ Long-life battery. ★ Super-sensitive internal Ferrite rod aerial. Special inclusive price for **£7.19.6** (Plus P. & P. 4/-).

Alignment service available. Full assembly details and individually priced parts lists, all of which are available separately price 1/6 post free.

NOW AVAILABLE!! MAINS UNIT

To replace PP1 4 1/2 x 4 1/2 volt battery as used in our "AIR-KING" Receiver described above. Size 2 1/2 in. x 2 1/2 in. (fits into battery compartment). A.C. mains 200/250 v. operation. Complete with mains lead. Also suitable for any other receiver using same type battery. PRICE 29/6. P. & P. 2/-.

TRANSISTORISED SOUND MIXER



Mixing 4 channels from high impedance source, giving professional results, inputs for high impedance Microphone, Tuner, Gram and/or Tape Recorder. Compact and beautifully styled, size 6" x 2 1/2" x 2 1/2". Standard Jack socket inputs.

PRICE 59/6 P.&P. including PP3 battery circuit. 2/6 diagram and instructions.

Stereo version available. 72/6. P. & P. 2/6.

POCKETCORDER TRANSTORISED REC ORDER


Why be bothered with a notepad? Take Pocketcorder with you on those business trips, the mighty Midget is ideal. Simple to operate, a unique 4-way push-button Switch for record/playback, etc., and remote control switch built into microphone ensures complete ease of handling. Fully adjustable speed through the life of Batteries and the volume and tone from the 2" internal speaker is outstanding. All accessories included such as Leather Case, Accessory Case, Crystal Earpiece, Tape, Batteries and Microphone, no other extras required. Up to 34 mins. recording time, operates on 1.5 volt PP3 and 2-1/2 volt U12 Pen Batteries. Size 5 1/2 x 4 x 2 in. Weight 12 Gns. P. & P. 4/-.



Spare 2" empty spools. 1/-; Spare 2" 200ft. L.P. Tape. 5/-.

"STARFLITE" TRANSMITTER

Designed to meet the needs of most amateurs the Starflite has single-knob band-switching, front panel switch to select any of five crystal positions with provision for an external VFO. Controlled carrier modulator permits almost 100% of the CW input to be used on AM peaks. Grid-block keying provides chirp-free operation. A full wave silicon diode power supply effects extremely low output ripple for

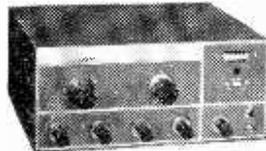


cleaner CW transmission, electron-coupled Pierce Oscillator, capacitance bridge neutralisation of the final and a three-stage lowpass filter. An illuminated edgewise D'Arsonval panel meter. Pi-network output provides the correct impedance match between the plate circuit and any 50-72 ohm co-axial feeder. Easy to follow point-to-point instructions supplied with each set of components. When constructed the Unit is housed in a heavy gauge steel Cabinet finished in grey crackle.

SPECIFICATIONS: Power input—20 watts peak; Operation: C.W., AM Phone—crystal or VFO Control; Band coverage: 80-10 metres; Coupling: Pi-network; Valve Line-up: 6146, 2) 6C1.6, 12AX7, 6DE7, Low Pass Filter. Size 13 1/2 in. wide x 12 in. deep (inc. knobs) x 6 1/2 in. high (inc. rubber feet). Weight 28lb. Power requirements, 200/240 v. 50/60 c.p.s. 225 watts.

MAY BE BUILT FOR 35 Gns. Carriage & Insurance 15/-

THE 'HIGHWAYMAN'

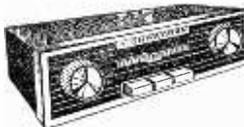

OUR QUALITY CAR RADIO TO BUILD YOURSELF AT A NEW LOW PRICE

Look at these features:

★ Attractivestyling. ★ Push pull output. ★ Three latest type, 7 x 4in. high flux D.M. speaker and baffle. ★ Medium and LONG Waves. ★ Push button for fingertip control. ★ Extremely low battery consumption (less than 1-amp). ★ Easy to fit any make car (Positive earth only). ★ 12-volt operation. ★ Compact size, measures only 7 x 7 x 2in. deep. ★ Easy assembly, supplied with dial and drive already mounted.

Mullard transistors plus valves types EBF83 and ECH83. ★ No Buzz, high output and sensitivity. ★ Printed circuit (latest type). ★ Coax. socket for car aerial. ★ Brand new guaranteed components. ★ Push-pull output. ★ Automatic volume control. ★ Long-life battery. ★ Super-sensitive internal Ferrite rod aerial. Special inclusive price for **£7.19.6** (Plus P. & P. 4/-).

Special inclusive price of ONLY **£7.19.6** Plus 5/- P. & P. All parts available separately. Individually priced parts list and comprehensive instruction booklet 2/6 post free. (Deducted from cost if complete parcel purchased later.) Optional extras, 3 section chromium plated weatherproof telescopic aerials type 1 17/44, 19/6; type 2, 27/43, 29/6, both plus P. & P. 2/6 if purchased separately.

P.W. AUTOCRAT CAR RADIO

ALL REQUIRED COMPONENTS AS SHOWN ON BLUEPRINT AVAILABLE FROM STOCK AT ALL BRANCHES

Component price list available on request.

SPECIAL OFFER!

GARRARD MAGAZINE TAPE DECK

Suitable for use on 200/250 v. A.C. mains.
2-Track **£5.19.6** 4-Track **£6.19.6** P. & P. 5/- each.

Magazine complete with 600ft. D.P. Tape, 32/- extra.

RECORD PLAYERS

GARRARD Model SRP10. Single Record Player fitted with high output crystal pick-up, **£5.9.1.**
THE NEW GARRARD "AUTOSLIM" 4-speed Autochanger with crystal pick-up, **£6.10.0.**
GARRARD "AUTOSLIM DE LUXE" 4-speed Autochanger, incorporates transcription Pick-up Arm, **£11.2.0.**
B.S.R. Model UA14, a 4-speed Mixer Auto-changer with crystal pick-up, **£5.19.6.**
The new GARRARD Model 4HF high Quality Single Record Player fitted with the latest T.P.A. 12 pick-up arm and G.C.S. crystal Cartridge, **£16.17.6.**
PHILIPS Model AG1016. A 4-speed Player which can be operated both manually and automatically. Suitable for Mono or Stereo operation. **£12.12.0.** Carriage and insurance on each above 5/- extra.

AGOS MONAURAL STETHOSCOPE HEADSETS

Suitable for Tape Recorders, or monitoring tape recorders, 100 ohm impedance magnetic. Complete with lead. **12/6** P. & P. (Originally 21/-). **OUR PRICE 1/6.**

CHASSIS BARGAIN



A 6 valve Superhet Radiogram Chassis of outstanding quality covering MW 200/550 Metres, LW 1200-3000 Metres. VHF 87-100 Mc/s.

Incorporating Internal Ferrite Rod Aerial and the famous Gortler Tuning Heart for VHF

Pick-up input suitable for most modern Record Players. Power output 4 watts, valve line up E280, EABC80, EF86, ECH71, EL84, ECC85, Volume On/Off and Tone Control, attractive black Tuning Dial size 1 1/2 x 1 1/2 in. with gold lettering and contrasting cream and gold knobs. A.C. 200/250 v. Size 15 x 7 1/2 x 6 1/2 in.

PRICE 16 Gns. P. & P. 5/-
Or £3.9.6 deposit (plus P. & P.) and 9 monthly payments of 3/8.

SEE FOLLOWING PAGES FOR ADDRESSES AND OTHER ITEMS

STERN-CLYNE

Electronics Centres throughout Great Britain

MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard AMPLIFIERS but also perfectly suitable for other makes with input up to 250 mV.

★ Equalisation for the latest R.I.A.A. characteristics. ★ Inputs for Crystal Pickups and variable reluctance magnetic types. ★ Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier. ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE Controls.

KIT OF PARTS **£6.60** ASSEMBLED **£9.10.0** (Carr. & Ins. 5/-)
Instruction book and detailed price list (free with kits) available separately at 2/- Post Free.



MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifiers requiring input up to 250mV. Incorporates 5 input Channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 160 c/s. Low pass filter 5-9 Kc/s. Totally enclosed in case.

KIT OF PARTS **£10.00** ASSEMBLED AND TESTED **£13.13.0** (Carr. & Ins. 5/-)
Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.



MULLARD "5-10" MAIN AMPLIFIER



For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained SPECIFIED COMPONENTS and MULLARD VALVES including PARTRIDGE MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer.

COMPLETE KIT (Parmeko Output Trans.) **£10.00**

ASSEMBLED AND TESTED **£13.13.0**
 ABOVE incorporating PARTRIDGE OUTPUT TRANS. £1.6.0. extra.
Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.

COMBINED PRICE REDUCTION

MULLARD 5-10 Main amplifier and 2 valve Pre-Amp. Kit **£15.15.0**. C. & I. 8/6. Built and tested. **£21.10.0**. C. & I. 8/6.
 MULLARD 5-10 Main Amplifier and 3 valve Pre-Amp. Kit **£19.10.0**. C. & I. 8/6. Built and tested. **£25.10.0**. C. & I. 8/6. With Partridge Transformer **£1.6.0** extra.


THE MULLARD 5-10RC AMPLIFIER

The popular complete "5-10" incorporating Passive Control Unit providing up to 10 watts high quality reproduction with input of 600mV. Specified components and new MULLARD VALVES. Includes PARTRIDGE MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE Output Transformers. Surplus power available for Tuner.

COMPLETE KIT **£12.00**
 ASSEMBLED AND TESTED **£16.00** (Carr. & Ins. 7/6).
Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.



With PARTRIDGE OUT-PUT TRANS. £1.6.0 ex.

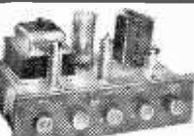

THE MULLARD 3-3RC A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN.

KIT OF PARTS **£8.8.0**
 ASSEMBLED AND TESTED **£11.10.0** (Carr. & Ins. 8/6).
 Complete to the MULLARD specification including PARTRIDGE OUTPUT TRANSFORMER. Switched inputs for 78 and

L.F. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. Please state L.S. impedance.
Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.

TAPE PRE-AMPLIFIER MULLARD Type "C"

Suitable for most 1/2 track, Mono Tape Decks. Incorporates Ferroxcube Push-Pull Oscillator. Treble Inductor and 3-sp. Equalisation. Includes separate Power Unit.

KIT OF PARTS **£14.0.0** (Carr. & Ins. 7/6). ASSEMBLED **£19.10.0**
Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.



THE "MONO-GRAM"

A small Amplifier of genuine high quality performance. Incorporates MULLARD ECL86 Valve, separate BASS and TREBLE controls. PARTRIDGE output Transformer producing up to 3 watts undistorted output.



KIT OF PARTS **£4.10.0** (Carr. & Ins. 3/6). ASSEMBLED **£6.0.0**
Instruction book and detailed price list (free with kit) available separately at 2/6 Post Free.

Perfectly suited for Portable Installations for which purposes we offer PORTABLE CASE (£3.10.0), the AMPLIFIER (Kit £4.10.0) and 8" x 5" SPEAKER (£1.0.0). All for **£9.0.0**

Alternatively with ASSEMBLED AMPLIFIER (Carr. & Ins. 5/-) **£10.0.0**

The Case quoted above will accommodate some 4-speed Single Record Units. A larger model is available for extra 10/- with this equipment a COMPLETE PORTABLE RECORD PLAYER can be built for **£14.0.0**



MODEL CR3/S TAPE RECORDER

MODEL CR3/S incorporates the HF/TR3 Mk. II Tape Amplifier (described below) and the Collaro "Studio" Twin-Track 3-speed Deck operating at 1 1/2 in., 3 1/2 in. and 7 1/2 in. speeds. Complete with microphones and 1200ft. tape.

KIT OF PARTS **£33.0.0**
 ASSEMBLED AND TESTED **£43.0.0** (Carr. & Ins. 15/- extra).



STEREO TAPE PRE-AMPLIFIER

MODEL STP-1. For use with current TRUVOX BRENELL or COLLARO "STUDIO" 1 and 1/2 track Stereo Decks. Incorporates Ferroxcube Oscillator, 4-speed Equalisation Signal Lever Meter and separate Gain Control. Includes separate Power Unit. KIT OF PARTS (Carr. & Ins. 8/6) ASSEMBLED **£28.0.0**



Instruction book and detailed price list (free with kit) available separately at 5/- Post Free.

MULLARD TAPE AMPLIFIER

MODEL HF/TR3/MK. II Based on Mullard's Type "A" design and suitable for most 1/2 track Mono Tape Decks. Incorporates Ferroxcube Treble Inductor, Gilson Output Transformer, and 3-speed Equalisation.

Includes separate Power Unit, using PARTRIDGE Mains Transformer. KIT OF PARTS **£13.13.0** (Carr. & Ins. 7/6). ASSEMBLED **£19.0.0**
Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.



COMBINATION TAPE UNITS

All our Tape Units can be supplied specially matched to any Tape Deck such as Collaro, Brenell Mk.5 Series II, also the Wearite. Specimen prices as below.

	Kit	Assembled
STP-1 Pre-amp with Collaro Studio Tape Deck.....	£36. 0.0	£42. 0.0
Assembled with track switch fitted, £44.2.0		
STP-1 with Brenell Mk. 5 Series II with Track Switch fitted	£68. 4.0	
STP-1 with Brenell Mk. 5 Series II, 1/2 Track Deck....		£74.15.0
Type "M" Pre-amp with Collaro Studio Tape Deck....	£24.10.0	£30. 0.0
Assembled with deck wired and matched, £32.2.0		
Type "C" Pre-amp with Brenell Mk. 5 Series II Deck	£46.11.0	£53. 1.0
Assembled with deck wired and matched, £55.3.0		
HF/TR3 with Collaro Studio Tape Deck	£24. 3.0	£29.10.0
Assembled with deck wired and matched, £31.12.0		
HF/TR3 with Brenell Mk. 5 Series II Deck	£46. 4.0	£61.11.0
Assembled with deck wired and matched, £55.12.0		
Carr. & Ins. 15/- on above units, Send S.A.E. for comprehensive price list.		

SEE PRECEDING PAGE FOR OTHER STERN-CLYNE PRODUCTS

SEND FOR CURRENT PRICE LIST OF ALL LEADING RECORDING TAPES AND ACCESSORIES

STERN-CLYNE

Electronics Centres throughout Great Britain

THE TUDOR STEREO HI-FI SYSTEM



Comprising a Self Powered AM/FM Tuner, Stereo Pre-amplifier, 12 watt per channel Stereo Power Amplifier. The Tuner and Pre-amplifier are housed in matching black crackle finish metal cabinets for shelf mounting, with silver metal dials and matching knobs. Specifications: Tuner:

Outstanding quality providing full VHF/FM long and medium waveband coverage. Frequency range FM 87.5-108.5 Mc/s. AM/MW 522-1630 Kc/s. LW 145-270 Kc/s. 100 mV output mains supply 105/240 A.C. Valve line-up: ECC83, ECH81, EBF89, EB91, EM84, ECC83. Multiplex outlet provided. Pre-amplifier—Designed for use with Tudor Stereo Power Amplifier with inputs for most types of Pickups, direct play from Tape-Heads and ample sensitivity for either Crystal or Moving Coil Microphone. Distortion 0.1% tape outputs 100 mV from 90 K ohm source inputs—Microphone 5 mV. Tape 5.3 mV. R.I.A.A. 4.3 mV flat 250 mV. Tuner 100 mV. Valve line-up: 2—EF86. 4—ECC83. Power Amplifier—12 watts per channel, sensitivity 1 volt r.m.s. for 12 watts output, frequency response ±0.5dB 20—20Kc/s. Speaker impedance 4, 8, or 16 ohms, surplus power available for Tape Pre-Amp. mains supply 105/240 V. A.C. Valve line-up: 2—ECC83, 4—EL84, 1—GZ34.

AM/FM TUNER AVAILABLE AT 24 GNS. P. & P. 7/6.

STEREO PRE-AMPLIFIER AND POWER AMPLIFIER TOGETHER AT 24 GNS. P. & P. 10/-.

DUE TO PRODUCTION STREAMLINING WE ARE PLEASED TO ANNOUNCE REDUCTIONS IN PRICE!

★ J.L.10 POWER AMPLIFIER



Incorporates the latest triode-pentode ECL86 valves in push-pull. PARTRIDGE ultra linear output transformer. PARTRIDGE mains transformer and smoothing choke. 10 watts power output, surplus power available for tuner. Output impedance 3—7.5—15 ohms.

KIT OF PARTS **£10.00** C. & I. 7/6
 READY BUILT **£13.13.0**

★ DOUBLE FEATURE PRE-AMPLIFIER




Inputs for microphone, crystal or magnetic pickups, tuner unit, and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck. Push-button switching for 3 tape speeds equalised. Tape erase Bias Oscillator circuit incorporating ferrox-cube transformer. Function switch, separate base, treble and volume controls, level control and latest EM87 magic eye level indicator. The pre-amplifier is totally enclosed in a silver hammer finish steel case, and an attractive perspex front panel completes the presentation.

KIT OF PARTS **£13.13.0** READY BUILT **£19.19.0** C. & I. 5/7
 PRICES: If both above units are purchased together:
 KIT OF PARTS **£23.13.0** READY BUILT **£32.0.0** C. & I. 10/-

SEND STAMP FOR COPY OF OUR INTERESTING LITTLE BOOKLET "What is High Fidelity!"

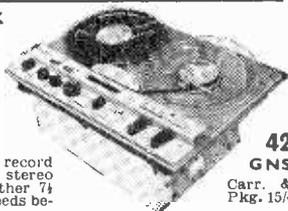STEREO TAPE-DECK WITH BUILT-IN PRE-AMPLIFIER




A professional addition to your Hi-Fi Stereo System consisting of two basic units, the Tape Deck and Pre-amplifier, which employs 4 Transistors and 4 Valves. The Unit with record and playback: 1 track stereo or 1 track mono at either 7 1/2 i.p.s. or 3 1/2 i.p.s. both speeds being fully equalised. Features: Track System: 1 track 2 channels stereo or monaural record and playback. Independent single channel recording on either channel while playback on other channel. Head Type: 1 track 2 channel inline stereo and associated erase heads. Low loss laminated pole pieces. Level indicators: 2 Meters, 1 per channel. Digital Counter: 3 digit tape position indicator. Automatic Stop: When tape runs out or breaks. Inputs: Microphone 1mV (50k ohms impedance) Gram/Tuner 50mV (high impedance). Output: (cathode follower). Monitor Sockets: 2 x 5 K. ohms impedance. Audio Output: 500mV. Oscillator: Push-pull 80 Kc/s. S/N Ratio: -45dB or better at 7 1/2 in. tape speed Separation: 45dB or more between stereo channels. Frequency Response: 40 to 15,000 cycles per sec. at 7 1/2 i.p.s., 40 to 9,000 cycles per sec. at 3 1/2 i.p.s. Single Motor: 4 pole heavy duty induction type. Power Supply: 240 v. A.C. 50 cycles. Size 6 1/2 x 10 x 15 in. Tape size: Up to 7 in. Line up: 4—2SB173 Transistors, 2-12AT7, 1-1AU7, 1-12BH7 Valves.

42 GNS
 Carr. & Pkg. 15/-

OUTSTANDING PRICE REDUCTIONS

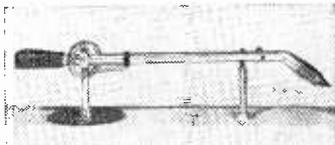THE B. & O. ST/M PICKUP COMPLETE WITH SP 11 STEREO DYNE MAGNETIC CARTRIDGE



A Transcription Pickup of outstanding quality employing a specially designed counter balanced and unique weight adjustment. Specifications: Length 10 1/2 in. from tip of Cartridge. Height 2 1/2 in. Stereo/Mono Cartridge. Frequency Response: +2.5dB from 30 c.p.s. to 15 Kc/s. Output Voltage: 7mV per channel at 5 cm/sec. at 1000 c.p.s. Separation: 20dB minimum. DC Resistance: 1250 ohms. Inductance: 200mHs. Recommended Tracking Force: 2 to 4 grams. Compliance: 5 x 10⁻⁶ cm/dyne in all directions. Stylus: Diamond, radius of curvature: 7th. Recommended Load: 47000 ohms.

PRICE **9 1/2 Gns.** Plus 3/6 P. & P.

NEWS FLASH!!

YET ANOTHER NEW ELECTRONICS CENTRE OPENING SHORTLY AT 125, THE MOOR, SHEFFIELD

WEST END:	18 Tottenham Court Road, W.1.	MUSEum 5929/0095	Half-day Sat
(Premier Radio)	23 Tottenham Court Road, W.1.	MUSEum 3451/2	Half-day Thurs
(Premier Radio)	309 Edgeware Road, W.2.	PADDington 6963	Half-day Thurs
CITY:	109 Fleet Street, E.C.4.	FLEet St. 5812/3	Half-day Sat
NORTH LONDON:	162 Holloway Road, N.7.	NORTH 7941	Half-day Thurs
SOUTH LONDON:	9 Camberwell Church Street, S.E.5.	RODney 2875	Half-day Thurs
CROYDON:	12 Suffolk House, George Street.	MUNICIPal 3250	Half-day Wed
BRISTOL:	26 Merchant Street, Bristol 1.	Bristol 20261	Half-day Wed
LIVERPOOL:	52 Lord Street, Liverpool.	Royal 7450	Open 6 days a week
MANCHESTER:	20/22 Withy Grove, Manchester 4.	BLACKfriars 5379	

Mail Orders and enquiries to Dept. P.W. 3/5 Eden Grove, Holloway, London, N.7

BENLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT LANE, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK. ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM FAULTY EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE

OA2	4/8	6BW6	6/9	6X5	4/6	20P5	12/3	ACHL08/8-	EAB05	5/8	E137	12/3	KTE21	5/8	4Q450/158/6	U50	4/6	AF125	10/6		
OB2	4/8	6C47	3/6	6Y4	5/6	20Y9	7/6	AC/PEP	EAC31	4/6	E138	7/3	LM134	7/6	4Q450/158/6	U50	4/6	AF126	10/6		
OZAGT	4/8	6BX6	3/6	6Z4	5/6	25L6	4/9	(5) 17/6	EAF42	7/6	EL12	7/6	LN152	6/1	R16	29/1	U72	4/6	AF127	9/6	
LA3	2/6	6C4	2/3	7A7	12/6	25UG17/6	12/6	AC/PEP	EBA34	1/1	EL81	8/3	LN309	7/9	R17	17/6	U78	3/9	BY123	11/6	
LA5	5/1	6C5	4/1	7B6	12/6	25Y5	7/2	(7) 17/1	EB41	4/8	EL83	6/9	LN319	8/9	R18	9/6	U84	10/6	GD3	5/6	
1A7GT	7/9	6C8	3/1	7B7	7/7	25Y9	7/2	AC/NO	EB91	2/3	EL84	4/8	LZ139	5/8	R19	6/10	U191	19/6	G194	5/6	
1C1	4/1	6C8	3/1	7C5	7/3	25Z4	6/6	AC/SG/VM	E183	20/6	EL85	7/6	LZ239	5/8	R22	9/1	U197	17/6	G195	10/1	
1C2	6/9	6C9	10/9	7C6	6/9	25Z7	7/3	AC/NO	EB03	8/6	EL86	7/3	LZ2	9/6	R27	9/6	U191	9/6	GET102	8/6	
1C3	6/3	6C10	7/6	7D3	15/1	25ZGT	8/1	ACTH1	EB41	6/8	EL91	2/6	ME41	13/1	54/1	U251	9/1	GET103	7/1		
1C5	5/1	6A12	6/1	7D5	15/1	27STU	23/3	AC/TPP	EBC51	5/9	EL95	5/6	ME91	12/6	RK34	7/6	U281	8/9	GET104	10/1	
1C6	10/6	6A17	12/6	7D6	14/6	28D7	6/9	AC/CPV	EBC30	3/9	EL360	27/1	M114	3/6	S120	22/6	U282	12/3	GET106	17/6	
1D3	4/6	6A18	15/1	7E18	15/1	30C1	5/6	AC/PT	EB91	5/6	EL98	18/4	M134	7/6	SP15	18/6	U301	11/3	GET112	12/1	
1D6	9/6	6A16	5/6	7H7	5/9	30C15	3/1	TP4	EBF80	5/6	EL82	8/6	M15D12/6	7/6	SP18C	12/6	U329	9/2	GET113	6/9	
1F1	5/9	6C0V4	2/4	7R7	12/6	30C18	10/6	AZ1	5/9	EBF89	7/3	EL120	20/5	M16	5/9	SP41	2/1	U339	9/6	GET114	6/6
1F2	2/3	6D14	1/6	7R7	14/6	30F5	5/9	AZ21	6/6	EBF89	7/3	EM4	17/9	M84B	20/5	SP42	12/6	U343	9/6	GET172	10/1
1F5	2/3	6D3	9/6	7Y4	5/1	30F15	9/3	AZ41	6/6	EB121	10/6	EM34	11/6	M8P4	12/1	SP61	2/1	U344	6/1	GET173	9/3
1FD1	5/9	6E18	2/6	8K5	10/6	30L1	6/6	B31	6/6	EB32	12/6	EM35	12/1	M15	14/6	SP23	27/2	U347	6/6	GET174	6/6
1FD9	3/6	6E5	9/6	9BWB	9/6	30L15	9/3	B319	5/6	EB525	12/6	EM71	13/6	MX40	8/9	SP61	5/6	U4020	6/6	GEX35	3/1
1G6	6/1	6F1	9/6	9D2	3/1	30P4	12/3	BL63	10/6	EC54	6/1	EM80	6/3	N3	23/3	T41	9/1	VMP4G	11/9	GEX36	10/1
1H9GT	7/9	6F3	5/3	9U7	7/6	30P12	7/6	C1	12/6	EC70	4/9	EM81	7/1	N78	26/3	TD2	12/6	VMS4B	12/6	GEX45	2/6
1L4	2/3	6F6G	3/9	10C1	8/9	30P16	9/1	C1C	12/6	EC80	2/3	EM84	6/9	N108	26/2	TD14	7/6	VP1	3/6	GEX64	11/6
1L8	12/19	6F6G	3/9	10A12	12/6	30P17	12/6	C1G	12/6	EC85	12/6	EM85	4/6	N134	7/6	VP2	12/6	VPB	9/6	GEX65	10/1
1L85	4/1	6F8	5/1	10I1	7/1	30P11	8/6	CK506	9/6	EC92	6/6	FM-7	7/6	P11	3/6	TH1C	10/6	VP4	1/6	MAT100	7/6
1L85	4/6	6F11	17/9	10D2	11/8	30P11.3	9/6	CL4	19/6	EC31	7/3	EX31	10/1	P16	2/6	TH3C	10/6	VP4A	1/6	MAT101	3/6
1N3GT	8/6	6F12	3/1	10P1	10/1	30P11.1	12/6	CL33	11/6	EC32	4/1	EX31	5/9	PARC80	6/9	TH233	6/9	VP4B	20/5	MAT120	7/6
1P1	5/9	6F13	4/9	10P9	9/9	35A5	13/6	CV6	2/6	EC34	21/7	EX31	5/6	PC66	10/3	TP22	5/1	VP13C	7/1	MAT121	6/6
1P10	4/6	6F14	2/6	10P12	12/6	30P16G	12/6	CV7	17/6	EC35	17/6	EX31	5/6	PC66	10/3	TP22	5/1	VP13C	7/1	MAT121	6/6
1P11	5/3	6F15	6/9	10D1.3	6/3	35W4	4/9	CV85	14/6	EC34	7/1	EX83	9/3	PC95	11/8	TP23	10/3	VP14	5/1	OA10	6/6
1R5	4/1	6F16	6/9	10D11.1	9/6	35Z3	14/6	CV271	12/6	EC31	3/6	EX84	9/6	PC97	7/3	TP27	11/8	VP133	9/9	OA70	3/1
184	5/1	6F17	12/6	10P13	8/3	35Z4G	4/6	CV1	16/4	EC02	4/6	EX86	5/6	PC08	5/6	CAB08	5/1	VR75	2/1	OA73	3/1
185	3/6	6F18	13/6	10P14	11/6	35Z5G	5/9	CV1C	6/6	EC03	4/6	EX88	9/6	PC085	6/9	CAB42	7/1	VR105	5/6	OA74	3/1
186	2/6	6F19	12/6	10P15	11/6	35Z6G	5/9	CV1D	6/6	EC04	4/6	EX89	9/6	PC085	6/9	CAB42	7/1	VR105	5/6	OA74	3/1
1T4	2/3	6F23	6/3	11D5	17/6	40U8A	6/6	D1	1/3	EC05	5/9	EX25	4/6	PC09	7/9	UF61	6/3	VT61A	7/1	OA85	3/1
1U4	5/6	6F24	9/6	11E1	15/1	41R18	15/1	D12	15/6	EC08	8/9	EX20	6/3	PC189	10/6	UF63	6/3	VT501	3/1	OA86	4/1
1U5	5/3	6F26	5/1	11E3	17/1	42	5/1	D12	10/6	EC19	11/6	EX21	6/1	PC08	5/6	UF80	5/9	VU111	5/1	OA90	3/1
2A7	12/6	6F32	3/1	12A6	2/3	45	10/1	D63	5/1	EC04	16/4	EX20	3/6	PC082	6/3	UF89	6/9	VU111	5/1	OA91	3/1
2B7	3/9	6F33	1/6	12A6	18/6	45Z6	12/6	D63	5/1	EC04	16/4	EX20	3/6	PC082	6/3	UF89	6/9	VU111	5/1	OA91	3/1
2D130	7/1	6G6	2/6	12A6	6/6	50A5	21/10	DAC32	7/9	EC90	8/1	EX20	3/6	PC082	6/3	UF89	6/9	VU111	5/1	OA91	3/1
2D21	5/6	6H6	1/6	12A06	9/6	50B5	6/6	DAP91	3/6	EC92	6/3	EX4	9/6	PCF05	10/6	UF85A	8/9	W21	5/1	OA211	13/8
2P	23/3	6J5G	3/1	12A06	6/1	50C5	8/6	DAP96	5/9	ECF86	11/6	FC13	14/6	PCF82	6/3	UCF85	5/6	W42	20/5	OC16W	35/1
2X2	3/9	6J5GT	4/3	12A07	5/1	50P06G	10/6	DC090	6/9	ECF04	24/1	FC13	17/1	PCF83	7/9	UCF86	8/9	W16M	24/6	OC22	23/1
3A4	3/9	6K7	4/6	12A08	10/6	50P07	12/6	DD1	12/6	EC15	23/6	FC14	17/1	PCF84	7/9	UCF87	8/9	W16M	24/6	OC22	23/1
3A5	6/9	6J6GT	4/6	12A76	4/6	52K0	14/6	DD41	10/6	EC21	9/1	FC15	17/1	PCF85	7/9	UCF88	8/9	W16M	24/6	OC22	23/1
3R7	5/1	6J7GT	7/1	12A77	3/6	53K0	14/6	DD4	7/1	EC23	22/8	GT1C	8/9	PCF86	8/9	UCF81	8/9	W77	2/6	OC28	25/1
3D6	3/9	6J8	12/6	12A06	5/9	52U2	12/6	DDT25	7/6	EC25	6/3	GT1C	5/9	PCF86	8/9	UCF81	8/9	W77	2/6	OC28	25/1
3Q4	5/3	6K6GT	5/6	12A07	4/6	77	5/1	DE33	3/6	EC24	12/6	GT20	7/6	PCF87	8/9	UCF82	7/9	W77	2/6	OC28	25/1
3Q4	7/1	6Q6GT	7/1	12A08	10/6	78	4/9	DE34	15/1	EC25	6/3	GT20	7/6	PCF87	8/9	UCF82	7/9	W77	2/6	OC28	25/1
3Q4	4/6	6K7GT	4/6	12A07	4/6	80	5/3	DE72	3/6	EC28	6/6	GT23	17/6	PCF88	8/9	UCF83	7/9	W77	2/6	OC28	25/1
3V4	5/3	6K8GT	3/3	12A07	9/9	83	22/6	DE91	2/3	EC28A	9/6	GT24	10/1	PCF89	8/9	UCF84	7/9	W77	2/6	OC28	25/1
4D1	3/9	6K8GT	7/9	12A06	5/9	83V	8/1	DE96	5/9	EC28	6/1	GT27	14/6	PCN45	7/1	UF80	6/3	X14	7/9	OC41	8/1
5R4GY	8/6	6K25	2/4	12B08	4/9	85A2	6/6	DE97	10/1	EC28E	6/3	H30	5/1	PCF45D1	10/6	UF86	8/9	X14	7/9	OC41	8/1
6T4	7/1	6L1	10/1	12B07	7/6	85B2	12/6	DE98	15/1	EC29	6/3	H30	5/1	PCF45D1	10/6	UF86	8/9	X14	7/9	OC41	8/1
5U4G	4/6	6L6G	6/6	12E1	16/9	90AV	6/7	DH63	4/1	EC28	9/6	IAB0C0	9/3	PCN46	4/3	UF41	6/9	X61	6/3	OC44M1P11	1/6
5V4G	7/6	6L6M	9/1	12H6GT	1/6	90CG	42/1	DH76	3/6	EC28	10/6	I12	7/6	PCN38	3/10/3	UF44	23/3	X63	4/9	OC45	8/1
5Y3GT	4/6	6L7GT	4/6	12J3GT	2/6	90CV	42/1	DH77	3/6	EC28	10/6	I12C	4/6	PCN43D1	10/6	UF46	8/9	X64	4/9	OC45M10	1/6
5Y4	9/6	6L17	12/6	12K7GT	7/3	90E1	16/1	DH11	23/3	EC28	10/6	I12C	4/6	PCN43D1	10/6	UF46	8/9	X64	4/9	OC45M10	1/6
5Z3	7/1	6L18	10/1	12K3	10/1	90E12	16/6	DH12	25/9	EC28	10/6	I12D	7/6	PCN44	7/1	UF47	10/6	X65	5/3	OC46	8/1
5Z4	7/1	6L19	9/6	12K7GT	3/6	150C2	4/6	DH107	16/1	EP22	6/6	H141	3/9	PCN44	7/1	UF47	10/6	X65	5/3	OC46	8/1
6/3012	8/3	6L1D3	6/6	12K6GT	9/6	181	13/1	DK32	7/9	EP36	3/3	HL41D10/8	6/6	PC211	10/6	UM80	8/3	X78	20/6	OC71	3/6
6A90	5/9	6L1D13	7/6	12Q2GT	3/6	185BT	34/11	DK40	15/6	EP37A	8/1	HL42D10/8	6/6	PEN/DD	CR1C	6/6	X79	27/1	OC72	8/1	
6A37	4/1	6L1D20	5/6	12S47	6/9	2158G	6/6	DK91	4/1	EP39	3/9	HL133D1	6/1	4020	17/6	UC7	7/1	X80	29/1	OC73	9/1
6A37	2/6	6A37	4/1	12S47	6/9	220	12/6	DK92	6/1	EP40	7/1	HL133D1	6/1	4020	17/6	UC7	7/1	X80	29/1	OC73	9/1
6A05	2/6	6P1	9/3	12S47	3/1	301	20/1	DK96	6/3	EP41	8/9	HN309	25/1	PL36	8/1	UC7	7/1	X101	10/6		

SURBITON PARK RADIO LTD.

ALL ORDERS DESPATCHED SAME DAY WE PAY POSTAGE AND INSURANCE
MONEY REFUND GUARANTEE

LEADING STOCKISTS OF MARTIN RECORDAKITS AND AUDIOKITS

MARTIN RECORDAKITS

HALF TRACK
TAPE AMPLIFIER FOR STUDIO DECK with ready wired printed circuit, control and input panels, mains and output transformers, knobs, plans, screws, etc. EF86, ECC83, EZ80, EM85 and 2 EL84. 3 watts output. Magic eye, Radio and Mic. Inputs. Ex. speaker socket. Tone and Monitor controls. Can be used as an amplifier £11.10
COLLAR STUDIO DECK. Very latest model, 3 speeds, 3 motors and 7-inch spools £10.10
CASE for above with 8 x 5 in. speaker, two-tone grey £3.50
COMPLETE KIT with tape and microphone £29.10

QUARTER TRACK

TAPE AMPLIFIER FOR STUDIO DECK as above £12.00
CASE as above with speaker, two-tone grey £5.50
COLLAR STUDIO DECK fitted Marriot "X" Merica heats £13.10
COMPLETE KIT with tape and microphone £39.10

TAPE PRE-AMPLIFIERS

HALF TRACK for STUDIO deck, 400 mV out. £8.80
QUARTER TRACK as above £9.80

TAPE HEADS

BRAMATIC Half track Record/Replay and Erase on plate £1.10

Dep.	&	Mthly. pmts. of
47/-	3	25/6
44/-	8	24/6
120/-	12	44/-
52/-	8	27/6
58/-	12	20/6
130/-	12	49/10
34/-	6	25/8
39/-	6	28/4

MARTIN AUDIOKITS

The new MARTIN all-transistor TEN WATT AMPLIFIER kits represent excellent value for money. Each unit is complete, requiring only to be connected to the next. We show only the popular units here. Others are available. Lead on request.

UNIT 1. FIVE INPUT SELECTOR. Size 31 x 3in. Nag. P.U., Crystal P.U. Radio, Mic. Tape head. 9-15 Volts. Must be used with Unit 4. £2.70
UNIT 4. PRE-AMPLIFIER AND CONTROL. Size 31 x 2 1/2 in. Volume on/off, Bass and Treble controls. 9-15 Volts. Must be used with Unit 1. £3.25
UNIT 7. MAIN AMPLIFIER. 10 watts. 6-transistor Transformerless Push-pull output. Mounted on Heat sink. 15 ohms output. 40 Volts supply. £6.10
UNIT 8. POWER SUPPLY. Gives 9 and 40 Volts. Heavy duty transformer, rectifier and smoothing. £2.15
CONTROL PANEL for Units 1 and 4. 10.8
ALL FOUR ABOVE UNITS WITH PANEL. 15 ohms output. £15.80
UNIT 5. MAIN AMPLIFIER. As Unit 7 but 3 ohms output. 24 Volt supply. £4.10
UNIT 6. POWER SUPPLY. As Unit 8, use with Unit 5. £2.10
ALL FOUR UNITS 1, 4, 5 & 6 WITH PANEL. 3 ohms output. £14.50
STEREO VERSIONS NOW AVAILABLE. LEAFLET UPON REQUEST.

Dep.	&	Mthly. pmts. of
62/-	12	22/6
67/-	12	20/10

NEW ARMSTRONG TUNERS AND AMPLIFIERS

224 F.M. Tuner	£22.10	30/-	12	33/-
225 A.M./F.M. Tuner	£28.10	115/-	12	42/9
227 M Mono AM/FM Tuner/Amp.	£36.10	147/-	12	53/10
127 S Integrated Stereo Amp.	£37.10	150/-	12	55/-
227 S Stereo AM/FM Tuner/Amp.	£52.10	213/-	12	77/4
228 S Stereo AM/FM Tuner/Amp.	£61.00	260/-	12	86/-
222	£27.10	110/-	12	40/4

SHELF MOUNTING TEAK CASE £3.10. EXTRA ALL MODELS. Descriptive Leaflet on request.

MONO AMPLIFIERS

LINEAR L45/4 3 valve, 3 watt.	£6.80			
DULCI GA6 Integrated, 5 watts, ECL86 valve	£13.25	52/6	12	19/3
TRIPLETONE HI-FI MAJOR 10 watts output, 2 EL84	£15.18.9	64/8	12	23/3
LEAK TL12 10 watt MAIN AMPLIFIER	£20.00	80/-	12	28/4
LEAK WARELOPE Mono Pre-amplifier	£18.10.0	83/-	12	23/1
DULCI DPA15 16 watt with 2 valve Pre-amp.	£28.50	105/-	12	38/6

STEREO AMPLIFIERS

DULCI GA606 Integrated 5 watts per channel	£18.10.0	76/-	12	27/8
ROGERS CADET Mk. II with P.A. 4 ECL86 valves	£26.10.0	107/-	12	39/2
LEAK TRANSCOR STEREO 30 P.A. and Main amp.	£49.10.0	198/-	12	72/7
LEAK STEREO 30 P.A. and main amplifier, complete	£55.80	229/-	12	80/8

HI FI LOUSPEAKERS

GOODMANS AXIETTE 8 inch.	£5.57			
GOODMANS AXIOM 10 inch.	£6.51			
GOODMANS 5K/20/XL Tweeter and crossover.	£7.70			
GOODMANS X05000, £2.0.11. X0050, £5.10.11				
W.B. HF1012 10in. unit, 3.75, 7.5 & 15 ohms.	£4.12.0			
WHARFEDALE SUPER 3 Tweeter.	£5.18.8			
WHARFEDALE SUPER 5 Tweeter.	£5.19.7			
WHARFEDALE SUPER 8 RS/DD	£6.14.2	44/-	8	24/3
WHARFEDALE SUPER 10 RS/DD Full range	£10.18.0	43/6	8	24/3
GOODMANS 210 12in. unit, Full range, 15 watt	£10.17.8	46/-	8	25/6
WHARFEDALE RS/12/DD 12in. unit, Full range	£11.10.0	61/-	12	22/4
GOODMANS 301 12in. unit, Full range, 20 watt	£16.4.8			

LEAFLETS BY WHARFEDALE AND GOODMANS AVAILABLE ON REQUEST.

SURBITON PARK RADIO LTD.

Phone: KIN 5549

48, SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

- Orders for Cash, C.O.D. or Terms.
- Hours 9 a.m.-6 p.m. (1 p.m. Wed.)
- Open Lunch Time and all day Sat.

F.M. TUNERS

TRIPLETONE F.M. TUNER, Less power	£13.10.0	55/-	12	20/6
TRIPLETONE F.M. TUNER, With power	£19.14.0	63/-	12	25/1
JASON JTV2 F.M. and T.V. sound. Switched, self-powered	£22.5.0	89/-	12	32/7

GRAMOPHONE UNITS

B.S.R. UA14 with TCS Mono cartridge	£20.10.8	28/-	6	29/-
GARRARD SR210, Single player, Mono cart.	£5.9.11	33/-	6	24/-
GARRARD AUTOSLIM, 4 speed changer, Mono	£7.17.0	47/-	8	25/8
GARRARD AT6 AUTOSLIM DE LUXE, Mono	£11.9.0	68/-	12	24/11
GARRARD 4HF Transcription Unit, Mono	£17.0.0	79/-	12	28/11
GARRARD LAB. "A" Transcription changer	£19.14.5	88/-	12	32/3
GARRARD 801 STROBE Transcription unit	£22.0.0	50/6	12	18/6
PHILIPS AG1019, Stereo cartridge, will change 7in. records with adaptor, 10/- extra	£12.12.0	69/-	12	24/11
GOLDRING GL58 with arm but less cartridge	£17.1.9	111/4	12	40/1
GOLDRING GL70 with arm but less cartridge	£27.9.8	76/6	12	27/8
GOLDRING "88" Transcription, less arm	£12.15.8			

GUITAR SPEAKERS

FANE L 12in. Heavy duty unit, 20 watt.	£5.5.8			
GOODMANS AUDIOM 51 12in. 15 watt BASS	£9.2.1	36/8	6	27/8
WHARFEDALE W18/EG 12in. 15 watt LEAD	£10.10.9	42/-	8	23/6
WHARFEDALE W15/EG 12in. 15 watt BASS	£17.10.3	70/-	12	25/8
GOODMANS AUDIOM 51 12in. 50 watt BASS	£25.15.3	119/-	12	43/7
GOODMANS AUDIOM 61 12in. 20 watt LEAD or BASS	£14.7.3	57/8	12	21/1

WRITE FOR GOODMANS LEAFLET "LOUD-SPEAKERS FOR ELECTRIC GUITARS".

GUITAR AMPLIFIERS

LINEAR DIATONIC 12 watt, 2 inputs	£13.2.8	52/6	12	19/3
LINEAR CONCORD 30 watt with COVER	£19.4.6	77/-	12	26/2
LEAK TL25 with Pre-amp, 25 watt	£42.5.0	169/-	12	61/11
LEAK TL50 with Pre-amp, 50 watt	£51.5.0	208/-	12	73/2

MICROPHONES AND FLOOR STANDS

RESLO RBH/7 Ribbon	£11.7.8	44/8	8	24/9
RESLO RBH/7S Ribbon with on/off switch	£13.10.0	54/-	12	19/9
RESLO Heavy Duty Floor Stand	£7.0.0			
TEISCO DM304 Dual Impedance with switch	£4.10.0			
PIEZO BM3 Crystal with switch	£2.10.0			
JAP. FLOOR STAND	£8.3.0			

EASILY REACHED BY FREQUENT TRAINS FROM WATERLOO TO SURBITON



CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil Panel.

meters. available ex-stock S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MR. 32P 2 1/2 x 2 1/2 in. square fronts

50µA	32/6	1A.	DC	22/6
100µA	29/6	5A.	DC	22/6
200µA	27/6	3V.	DC	22/6
500µA	25/-	10V.	DC	22/6
100-0-50µA	29/6	20V.	DC	22/6
100-0-100µA	27/6	50V.	DC	22/6
500-0-500µA	22/6	100V.	DC	22/6
1-0-1mA	22/6	150V.	DC	22/6
5mA	22/6	500V.	DC	22/6
1mA	22/6	300V.	DC	22/6
10mA	22/6	750V.	DC	22/6
50mA	22/6	15V.	AC	22/6
100mA	22/6	50V.	AC	22/6
150mA	22/6	150V.	AC	22/6
200mA	22/6	500V.	AC	22/6
300mA	22/6	500V.	AC	22/6
500mA	22/6	'S' Mr. 1mA		
750mA	22/6			29/6.

Type MR. 52P. 2 1/2" sq. front.

50µA	57/6	1mA	32/6	
100µA	47/6	20V.	DC	22/6
500µA	37/6	100mA	32/6	
50-0-50µA	57/6	1A.	DC	32/6
100-0-100µA	47/6	300V.	DC	32/6
300V.	AC	32/6		

Type MR. 65P. 3 1/2 x 3 1/2 in. fronts

50µA	59/6	1mA	35/-	
100µA	49/6	10mA	35/-	
500µA	39/6	100mA	35/-	
50-0-50µA	59/6	1A.	DC	35/-
100-0-100µA	49/6	300V.	DC	35/-
VU Meter	59/6	300V.	AC	35/-

Type MR. 85P. 4" x 4" sq. fronts

50µA	69/6	1mA	45/-	
100µA	59/6	10mA	45/-	
200µA	55/-	50mA	45/-	
500µA	45/-	100mA	45/-	
50-0-50µA	69/6	lamp DC	45/-	
100-0-100µA	59/6	5 amp DC	45/-	
500-0-500µA	49/6	300V.	AC	45/-
1-0-1mA	45/-	300V.	DC	45/-

*Post extra



BAKELITE PANEL METERS

First grade quality. 3 1/2 in. square fronts.

25µA	65/-	100mA	29/6	
50µA	42/6	1A.	DC	29/6
100µA	39/6	5A.	DC	29/6
500µA	35/-	'1A.	AC	29/6
50-0-50µA	45/6	5A.	AC	29/6
100-0-100µA	39/6	10A.	AC	29/6
50mV	39/6	30A.	AC	29/6
100mV	39/6	50A.	AC	29/6
1mA	29/6	300V.	DC	29/6
5mA	29/6	'300V.	AC	29/6
10mA	29/6	'300V.	AC	35/-
50mA	29/6	VU Mtr	49/6	

*Moving iron. All others moving coil.

ILLUMINATED 'S' METERS

Cal. in 'S' units. 1mA Basic. 1 1/2 in. sq. front. 29/6 P. & P. 1/-

2 1/2 in. sq. front. 39/6 P. & P. 1/-

MORE METER BARGAINS

100µA gin.	Flush sq.	92/6
100µA 2in.	Flush rd.	42/6
500µA 2in.	Flush rd.	22/6
1mA 2in.	Flush rd.	22/6
300-0-30mA 2in.	Flush rd.	37/6
350mA R.F. 2in.	Plug in	8/6
300V. AC 2in.	Flush rd.	25/-
500V. AC 2in.	Flush rd.	25/-

1mA Meter Rectifiers 8/6

Please add postage.



SEMI AUTOMATIC BUG KEY

Super speed key. 7 speed adjustments. 10 WPM to as high as desired weight scale for reproducible settings. Precision toolled anti-rust nickel plated brass and stainless steel operating parts. Size 6" x 3 x 2 1/2 in. Brand new. £4.10.0. P. & P. 1/6.



LAFAYETTE "PRECON" AMATEUR PRESELECTOR CONVERTER

*Crystal Controlled *For 30-40-15-10 Metre Bands *As a converter—converts your receiver to dual conversion *Improves selectivity *Widens bandspread *High signal to noise ratio *Improved image rejection *Modern styling

SPECIFICATIONS. 80, 40 Metres preselector only. 20, 15 and 10 metres preselector and converter. GAIN: Preselector, 36dB at 80 metres; converter, 22dB at 20 metres. OUTPUT FREQUENCY: 3.5-3.85 Mc on 20M. Band, 3.5-3.85 Mc on 15M band, 3.5-5.2 Mc on 10M band. VALVES: 2-5BA6, 1-6BL3. CONTROLS: Aerial trimmer, function, bandwidth, gain. 70 stages of R.F. Amplification and stability excellent. 3 crystals are included for 20, 15 and 10M Bands. SIZE: 10" x 6" x 8". Operation 220/240V A.C. 19 Wms. Carr. 7/6 S.A.E. for full details.

CODAR AMATEUR EQUIPMENT

PR.30 R.F. PRESELEC-TOR 1.5-30Mc/s £41.76

model, 200/250V A.C. £7. 2.0


R.Q.10 X MULTIPLIER £6.15.0

R.Q.10X Self powered model, 200/250V A.C. £8.8 0.

A.T. NEW 12 WATT 160/80 metre TRANS-MITTER £16.10.0

Matching P.S.U. for A.T.5 200/250V A.C. £8. 0.0

S.A.E. for full details.

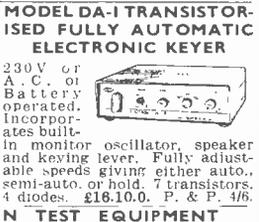

MODEL DA-1 TRANSISTORISED FULLY AUTOMATIC ELECTRONIC KEYS


230 V. or A.C. or Battery operated. Incorporates built-in monitor oscillator, speaker and keying lever. Fully adjustable speeds giving either auto, semi-auto, or hold. 7 transistors. 4 diodes. £16.10.0. P. & P. 1/6.



LAFAYETTE PRECISION TEST EQUIPMENT

Modern range of precision test equipment for the service man. Supplied brand new and guaranteed with manual. For operation on 220/240 volts A.C.

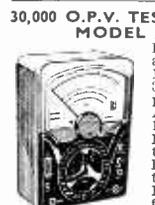TE-20 Signal Generator. 120Kcs/2500 Mc/s on 6 Bands. Directly calibrated. Variable R.F. Attenuator. Variable audio output. £12. Carr. 5/-.
TE-46 Capacity Resistance Analyser. Ranges 2pF-2.000mF; 2 ohms-200 Meg. Includes check impedance, turns ratio. Insulation. £15. Carr. 5/- S.A.E. for full details.



30,000 O.P.V. TEST METER MODEL 500

Reads voltages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 o.p.v.; D.C. current to 12 amps. Resistance to 60 Megs; D.C. resistance from -20 to +500 Megs.

+56. Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3 1/2 x 6 1/2 x 2 1/2 in. Price £8.17.6.



TS. 76 20,000 O.P.V. PUSH BUTTON MULTI-TESTER

Large clear plastic scale. Simple operation, DC and AC volts up to 1,000V. Resistance up to 10 megohms. Current up to 250 mA. Decibels -20 to +36db. Size 6 x 4 1/2 x 2 1/2 in. Complete with leads, batteries and instructions. £5.19.6. P. & P. 2/-.

ERSKINE TYPE 13 DOUBLE-BEAM OSCILLOSCOPE

Time base 2c/s-750Kc/s. Calibrators at 100Kcs and 1Mc/s. Separate Y1 and Y2 amplifiers and miniature valves. Time base 1 in. A.C. Supplied in perfect working order. £27.10.0. Carr. 20/-.

TRIPLETT SIGNAL GENERATOR 1632

10 RANGES: 100Kcs-120Mc/s on fundamentals. Six valves, stabilised H.T. Fully attenuated OUTPUT. 100 µamp carrier level meter. 1Mc/s xtal check. Operation 115V. A.C. Supplied in perfect working order. £12. Carr. 10/6 (230/115V). Transformer 12/6

OSCILLOSCOPE OS-57 USM-38

Brand new high quality American oscilloscopes incorporating 3in. tube, printed circuit and miniature valves. Time base 1, 10, 100 1K and 10Kµs/in. Calibration markers 1, 10 and 100µs. Calibrated Y input valves. X expansion, sweep stability. Operation 115V. A.C. Supplied brand new, fully tested with test leads, probe and circuit diagram. £29.10.0 each. Carr. 10/- 230/115V. Transformer 18/6 extra.

MINE DETECTOR No. 4A


Fully detect all types of metals. Fully portable. Complete with instructions. 99/6 each. Carr. 10/-. Battery 8/6 extra.

MINIFLEX 1 TRACK TAPE HEADS

Set of three, record, playback, erase. Only 29/6 set. P. & P. 9d.

12 VOLT A.C. TIME SWITCH

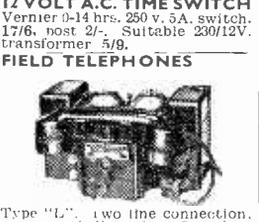Vernier 0-14 hrs. 250 v. d.A. switch. 17/6. post 2/- Suitable 230/12V. transformer 5/9.




FIELD TELEPHONES

Type "L". Two line connection. generator bell ringing. Complete telephone intercom. Supplied in excellent condition, fully tested and complete with batteries. Only 69/6 per pair. Carr. 5/-. Type "F". As above but moulded bakelite case (as illustrated). Supplied complete with wooden trunk case for field use. £4.19.6 per pair. Carr. 5/-.

TELEPHONES TYPE H

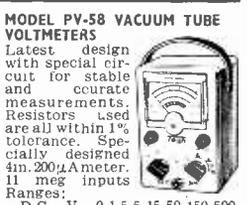Sound powered. generator bell ringing 2 line connection. Fully tested. £4.19.6 pair. Carr. 5/-.



MODEL PV-58 VACUUM TUBE VOLTMETERS

Latest design with special circuit for stable and accurate measurements. Resistors used are all within 1% tolerance. Specially designed 4in. 200µA meter. 11 meg inputs

Ranges:

-D.C.	V.	0-1.5-5-15-50-150-500-1500V.
+D.C.	V.	0-1.5-5-15-50-150-500-1500V.
A.C.	V.	0-1.5-5-15-50-150-500-1500V. RMS.
		0-1.4-4-14-40-140-400-1400-4000 P.

Resistance: 2 ohm to 1,000 ohm. Imp. —10dB to +65dB. Operation 220/240 volt A.C. Size 7 x 4 1/2 x 4in. Supplied brand new and guaranteed complete with probe and instructions. £13.19.6. P. & P. 3/6.

CHASSIS PUNCH SET

Set of 10 circular size hole cutters 1/2", 1", 1 1/2". Supplied complete with punches, dies, T drive handle, tapered reamer, fitted leather case and instructions 49/6. P. & P. 2/-.

PLUGS AND SOCKETS

Painton 15-pin in-line printed circuit connectors. 7/6 pair. Large quantities available. Ditto 32-pin. 12/6 pair. Unifers. 4-pin, 2/6 pr; 8-pin 3/6 pr; 12-pin, 4/- pr; 18-pin, 4/6 pr. Painton Miniature Jones. 4-pin 3/6 pr; 6-pin, 4/- pr; 8-pin 4/6 pr; 18-pin, 7/6 pr; 24-pin, 10/6 pr; 33 pin, 12/6 pr. Post extra.

L.T. METAL RECTIFIERS

FULL wave bridge connected.

12/18V 1A	3/9	23/36V 1A	7/3
12/18V 2A	6/3	24/36V 2A	13/6
12/18V 4A	9/6	24/36V 15A	45/-
12/18V 6A	12/3		
12/18V 10A	22/6		Post extra.

L.T. TRANSFORMERS

For chargers, models etc. All primaries tapped 200/250V.

- (1) 3.5, 9 or 17V, 1 amp. 9/9;
- (2) Cito 2A., 14/3; (3) ditto 4A., 16/6; (4) ditto 6A., 20/-; (5) 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30V, 2 amp. 18/6; (6) ditto 4A., 30/-; (7) ditto 5A., 37/6; (8) 50V, 1 amp. 13/6; (9) 50V, 1 amp., 15/6. Post extra.

AUTO TRANSFORMERS

Step up or step down. Tapped 0/15/200/230/250V. 20W., 9/-; 60W. 12/6; 75. 15/6; 150W. 18/6; 200W. 27/6; 300W. 42/6; 500W. 67/6; 1,000W. 90/-; 1,500W. 126.19.6; 3,000W. £7.10.0; 7,500W. £15. (only tapped 0/110/230V.) Post extra.

PETTIMAX 9 VOLT BATTERY ELIMINATOR

220/240V. A.C. Same size as PP3. 15/6. P. & P. 1/3.

SUBSTITUTION BOXES

Resistance—24 ranges ... 27/8
 Capacitance—9 ranges ... 19/6
 Post 1/6 extra.



LAFAYETTE HI-FI STEREO HEADPHONES

Air Cushioned headband, soft foam rubber ear pads, freq. response 25-15,000 cycles, high sensitivity, impedance 8 ohms per phone. Supplied complete with all cable, wires, overload junction box and 3-connector plug. 80/6. P. & P. 2/6.

G. W. SMITH & CO. (RADIO) LTD.
 3 & 34 LISLE STREET, LONDON, W.C.2.
 SEE OPPOSITE PAGE

TM-59 'er 'S' METER



Signal strength meter using VTVM principles. Calibrated in S units. Sensitivity and zero adjustments. For any superhet receiver with AVC. Requires 150/200V, and 6 or 12V. Complete with valve and full instructions. 82/6. P.P. 2/6.

MAINS ISOLATION TRANS.
230V. to 230V. 50W. 1/6/6. P.P. 3/-; 100W. 29/6. P.P. 3/6; 1,000W. 25. Carr. 10/-.

MINIATURE LEAD ACID ACCUMULATORS
Brand new. 2V. 1.5A. 4 x 1 1/4 in. 5/6. P.P. 1/3. 12V. 0/75A. 4 x 3 x 1 1/4 in. 15/6. P.P. 1/6.

MARCONI TF14G/4 STANDARD SIGNAL GENERATORS

First release of this late mark. 85Kcs to 2Mc/s +1%. Output variable from 1µV to 1 volt. Internal sine wave modulation 400cs up to 75% depth. Operation 200/250 volt A.C. Offered in really excellent condition. Like new, fully tested and guaranteed. 225. Carr. 30/-.

HEAVY DUTY POWER SUPPLIES
Input 200/250 volt A.C. Three H.T. outputs 2 x 400V. 175mA and 350V. 225mA. All fully smoothed. 2 x 6.3V. 5 amp. 6.3V. 4 amp. 2V. 0.5 amp. Supplied in perfect condition. 25-10.0. Carr. 20/-.

PRECISION PORTABLE VOLTMETERS
Polished wood case. 8in. scale with knife edge pointer. A.C. and D.C. volts. 0-180 volts. 0-160-200 volts. 25-19.6. P.P. 3/6.

TWIN MOTOR BARGAIN
200/250V. A.C. Twin concentric spindles. Either motor reversible. 14000 r.p.m. Brand new. 12/6. P.P. 2/6.

VARIAC TRANSFORMER
24 amp. Pri. 230V. Sec. 185/250V. £12-10.0. Carr. 10/-.

MAINS MOTORS 220/240V
30 watts. 5,000 r.p.m. 4 x 3 1/4 in. spindle. 82/6. P.P. 2/-.

GEARED SLIDER RHEOSTAT
1.2 ohms 12 amp. 15/6. P.P. 3/6.

R.C.A. HEADSETS
Low Imp. Fitted with std. Jack Plug. 15/6. P.P. 1/6.

DESK TELEPHONES
Std. type with handset and bell. No dial. Unused. 25/-, P.P. 3/6.

ROTARY TRANSFORMERS
12V. D.C. input. Output 310/360V. D.C. 30mA. New boxed. 10/-, P.P. 2/-.

COLLAPO MAGNAVOX STUDIO TAPE TRANSCRIBER
Brand new. 3 speeds, 1"1", 3"1", 7"1". P.S. 3 motors, digital counter. Complete with instructions. 2 Track. £10.10.0; 4 Track. £13.10.0. Carr. Paid.

HEADSET & BOOM MICROPHONE
American type. Low impedance. padded. 49/6. P.P. 2/6.

BEST BUY!
Send 1/- P.O. for full catalogue and lists. Open 9 a.m. to 6 p.m. Every day. Monday to Saturday. Trade supplied.



A SUPERB RECEIVER FOR ONLY £27.10.0 Carr. 10/-.

NEW LAFAYETTE COMMUNICATIONS RECEIVER

MODEL HA. 63
Plus Selenium Rectifier
7 VALVES Covering 550 kc/s-31 Mc/s.
4 BANDS

● Illuminated "S" Meter ● 1.5 Microvolt Sensitivity ● Electrical bandspread ● Aerial trimmer ● Noise limiter ● B.F.O. ● R.F. stage ● Big slide rule dial ● Output or headphones or 4/8Ω speaker ● Modern steel cabinet size 13in. x 7 1/2in. x 10in. ● Operation 220/240 volt A.C. S.A.E. for Full Details.
Supplied Brand New and guaranteed with instruction manual. Matching Speaker in Cabinet..... 55/-

FULL RANGE of Other LAFAYETTE RECEIVERS in Stock

MODEL HE-40 4 Bands, 550Kcs to 30Mc/s. **£19.10.0** Carr. 10/-
MODEL HE-30 9 Valves: 4 Bands, 550Kcs to 30 Mc/s. **£35. 0.0** Carr. 10/-
MODEL HE-80 15 Valves 5 Bands, 550Kcs-30Mc/s and 142-148Mc/s. **£52.10.0** Carr. 10/-

Each receiver supplied brand new and fully guaranteed complete with manual. All models for operation on 220/240 Volt A.C. S.A.E. for illustrated leaflet. Generous part exchange allowances.

TE-20A R.F. SIGNAL GENERATOR



A precision signal generator of extremely high accuracy and quality. Six ranges from 120Kcs to 130Mc/s on fundamentals with calibrated harmonics from 130-300 Mc/s. 400 cps. INT. MOD. OR EXT. MOD. OUTPUTS MOD. RF. UNMOD. RF. or 400 c/s audio. R.F. output in excess of 100 mV. Large clear 5 inch dial. Handsome metal case with handle. Size 7 1/2 x 10 x 4 1/4 in. Complete with leads. Operation 220/240 volts A.C. Supplied brand new and guaranteed. £12-19.6. Carr. 5/-.

MAINS RECORD PLAYERS & AUTOCHANGERS HALL GUARANTEED WITH ARM AND CARTRIDGE

GARRARD SRP-10 PLAYER..... £4.17.6
GARRARD AUTOSLIM CHANGER..... 66. 9.6
GARRARD ATS CHANGER MONO..... 210. 9.6
GARRARD ATS CHANGER STEREO..... 210.18.6
GARRARD 4 H/F MONO..... 214.10.6
GARRARD 4 H/F STEREO..... 215.15.0
GARRARD TYPE A CHANGER..... 217.15.0
GARRARD 301 STROBO. NO ARM..... 219.10.0
B.S.R. GUT SINGLE PLAYER..... 24. 7.6
B.S.R. UA16 CHANGER..... 26.12.6
B.S.R. UA15 NEW SLIMLINE CHANGER..... 26.18.6
POSTAGE EXTRA

MULTI-METERS
Brand New—Fully Guaranteed. Lowest ever prices. Supplied with leads, batteries and instructions.



MODEL NH-400
10,000 o.p.v.
0/3/3/30/120/300/600/1,200V. D.C.
0/12/60/120/300/1,200V. AC
0/120 n A/30/300mA D.C
0/2K/200K/2 Meg Ω
100pF--2mFd
79/6. P.P. 2/6.

MODEL 250C
2,000 o.p.v.
0/10/50/500/2,500V. D.C
0/10/50/500/2,500V. AC
0/2 Meg Ω
0/350mA
—20 to +36dB
49/6. P.P. 2/6.

MODEL PT-34
1,000 o.p.v.
0/10/30/250/1000V. AC
and D.C.
0/1/100/500mA D.C.
0/100K Ω—0.2mFd
39/6. P.P. 1/6.

MODEL TE-12
20,000 o.p.v.
0/1/6/6/30/120/600/1,200/3,000/6,000V. D.C.
0/6/30/120/600/1,200V. AC
0/60µA/6/60/600mA
6/6K/60K/6 Meg/60 Meg Ω
5pF--2mFd
25-19.6. P.P. 2/6.

TWO-WAY RADIOS

New improved "LAFAYETTE" Models.

Type 1. 3 transistor. Range up to 1 mile. £8.17.6 per pair.
Type 2. 9 transistor. Range up to 5 miles. £21 per pair.
Postage extra. S.A.E. for full details.



LAFAYETTE BRAND RECORDING TAPE

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.

3in. 200ft. L.P. mylar 4/-
3 1/2in. 600ft. T.P. mylar 10/6
5in. 600ft. std. plastic 8/6
5in. 900ft. L.P. acetate 10/-
5in. 1200ft. L.P. mylar 15/6
5 1/2in. 1200ft. L.P. acetate 12/6
5 1/2in. 1800ft. D.P. mylar 22/6
7in. 1200ft. std. mylar 12/6
7in. 1800ft. L.P. acetate 15/6
7 1/2in. 1800ft. L.P. mylar 25/-
7in. 2400ft. D.P. mylar 25/-
Postage 2/- Over £3 post paid.

BRAND NEW R.C.A. AR88D RECEIVERS

Unboxed 25/-; Boxed with spare valves, copper aerial, headset, and manual, 285. Carr. 30/-.

VARIABLE VOLTAGE TRANSFORMERS

Pri. 230V. Sec. 0-260V. 1 amp. £2-10.0; 2 amp. £5-17.6; 5 amp. £9. 9 amp. £14.10.0; 10 amp. £18-10.0; 15 amp. £18-15.0; 20 amp. £32-10.0. All fully shrouded.

CHAMOIS PADDED MOVING COIL HEADPHONES

Canadian noise excluding type. Complete with M/C microphone. New, boxed, 25/-, P. & P. 2/6.

Brand New Double Beam CRT's

Cosor 89D 59/6. P.P. 4/6.
Dumont K1651P1. 59/6. P.P. 4/6.

SILICON RECTIFIERS
400 P.I.V. (SCR) 4.7 amp 7/6
200 P.I.V. 6 amp 5/6
1,000 P.I.V. 650mA 7/6
800 P.I.V. 500mA 5/6
200 P.I.V. 200mA 3/6
400 P.I.V. 90mA 3/6
150 P.I.V. 165mA 1/6
70 P.I.V. 1 amp 3/6
95 P.I.V. 3 amp 5/6
Post extra.

MINIATURE HIGH SPEED COUNTERS

4 Digit available, 6V, 24V, or 60V. ALL 7/6 ea. P. & P. 9d

NEW LOW IMPEDANCE HEADSET

Latest Ministry Type. Rubber moulded. Fitted with Std. Jack Plug. Brand New, boxed. 17/6. P. & P. 1/6.

4-CHANNEL TRANSISTORISED MICROPHONE MIXER

Add musical high-lights and additional s o u n d effects to your recordings. The MN-4 permits mixing of four signals such as microphone, records, tuner, etc. into single output. Input and output take standard plugs. Fully transistorised and self contained in handsome case. PRICE 55/-, P. & P. 2/6.




G.A. SMITH & CO (RADIO) LIMITED
Phone GERRARD 8204/9153
Cables SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

Lewis have the Cabinet for you

We can supply any cabinet to your own specification

This is only one example of—
THE LARGEST RANGE OF CABINETS IN THE COUNTRY

Equipment is also our speciality.

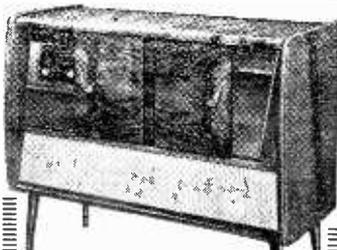

The Grosvenor
Price 18 gns.



The Lowboy
Price 27 gns.



100 (P114) Chase Side, Southgate
London, N.14. Tel 3733/9666

FREE CATALOGUE

Send today for the new
Lewis Catalogue

Designed to assist your choice of cabinet.

Sent absolutely free. The new Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Choose from 49 different Models.

Please send your new free 24 page colour cabinet catalogue.

Name _____
Address _____

BLOCK CAPITALS PLEASE

A BEGINNER'S GUIDE TO RADIO

This new 6th edition has been fully revised and the lesson on Transistors considerably amplified.
8/6 Postage 6d.

THE RADIO AMATEUR'S HANDBOOK, 1964 by A.R.R.L. 36/-, Postage 2/-.

HI-FI YEAR BOOK, 1964. 10/6, Postage 1/-.

101 WAYS TO USE YOUR VOM (Testmeter) and VTVM (Valve Voltmeter), by R. G. Middleton. 16/-, Postage 1/-.

RADIO & TELEVISION TEST INSTRUMENTS, by G. J. King. 25/-, Postage 1/-.

RADIO, TELEVISION AND ELECTRICAL REPAIRS, by R. C. Norris. 50/-, Postage 2/-.

TELECOMMUNICATIONS PRINCIPLES (IN M.K.S. UNITS), by R. N. Renton. 45/-, Postage 2/-.

GUIDE TO BROADCASTING STATIONS, compiled by "WW". 5/-, Postage 6d.

INTER.G.E.C. S.C.R. MANUAL, 3rd ed. 16/6, Postage 1/3.

COMPLETE CATALOGUE 1/-
THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books
**19-21 PRAED STREET
LONDON, W.2**

Phone: PADDINGTON 4185
Open 6 days 9-6 p.m.

FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad.Brit. I.R.E. Guide also gives details of range of diploma courses in Radio-T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of


SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER
150,000 SUCCESSSES**

CHAMBERS COLLEGE

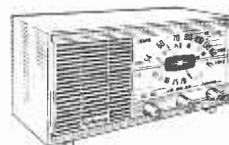(Incorp. National Inst. of Engineering)
(Dept. 461), 148 HOLBORN
LONDON, E.C.1



**BRAND
NEW
A.C. MAINS
5 VALVE
SUPERHET
RADIO
RECEIVER**

Housed in beautifully styled cabinet offering terrific performance and very high quality reproduction. Built-in ferrite rod aerial for reception of all your favourite programmes. Fully guaranteed MODEL 55. Covers Medium, Long and Short Waves, size 8 1/2 in. w. x 3 1/2 in. d. x 4 1/2 in. h. **PRICE ONLY £7.17.6 P. & P. 3/6.**

SPECIAL OFFER

HIGH GRADE 2-STAGE GERM AMPLIFIERS
Made by very well-known manufacturer
Using a double-wound mains transformer (fully isolated chassis) with tapped primary, full wave contact cooled rectifier, and Millard PL.1.2 triode-pentode valves. 3 watt output, separate tone and volume controls. Overall size 6 1/2 in. wide x 3 in. deep x 4 1/2 in. high. Each amplifier Brand New and tested and supplied complete with valve, 3 ohm output transformer and knobs.
PRICE 49/6 P. & P. 4/-.

(Ideal as an add-on self contained Audio unit for our MK1 or MK2 FM Tuner).

BRAND NEW 3 OHM LOUDSPEAKERS

2 1/2 in. 12/6; 3 in. 12/6; 4 in. 15/-; 5 in. 21/-; 10 in. 25/-; 12 in. 27/6; (12 in. 15 ohm. 30/-); 10 in. x 6 in. 28/-
Latest type E.M.1. 1 1/2" x 8 in. with high flux ceramic magnet, 11,000 gauss. Aluminium centre cone. 10 watts, 50 ohm to 10 K ohm. 42/-; P. & P. up to 6 in. 1/6; over 6 in. 2/6 per speaker.

SPECIAL OFFER !!

BRAND NEW HEAVY DUTY 12in. SPEAKERS
Response 45 cycles/Kc/s. 1 1/2 in. voice coil. Available in 3 or 15 ohm. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. **LIMITED NUMBER ONLY. UNREPEATABLE AT 89/6. P. & P. 5/-.**

SPEAKER AND CABINET FABRIC
Outboard or Red and Gold Vinyl for speaker and cabinet covering, also Red Rexine for cabinet covering only. All 5 1/2 in. wide and usually sold at 35/- yard.

OUR PRICE 13/6 per yard length.

Plus P. & P. 1/9 (Minimum order 1 yard), send S.A.E. for samples.

BARGAIN OFFER CORNER

ROLA CELESTION. Approx. 9 in. x 6 in. x 6 in. Middle register speaker. 10/6. P. & P. 2/6.

MAINS TRANSFORMER

Drop thru type. Tapped primary 110v., 200v., 220v., 240v., 320-0-320v., at 80mA and 6.3v. at 3 amps. Generous core. Stack size 3 1/2 x 2 1/4 x 1 1/2 in. Weight 4 lbs. **ONLY 15/-.** P. & P. 3/6.
ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity. 18/6. P. & P. 1/6.
TSL CRYSTAL STICK MIKE. Listed at 45/-. Our price 15/6. P. & P. 1/6.

T.C.C. SUPPRESSOR CONDENSERS. 250v. A.C. .005 + .005 x .1. In tubular can 1 1/2 in. long x 3/4 in. dia. 2 for 3/6. Post free.

TRANSISTOR DRIVER 0.5W O/P TRANSFORMERS. (Tapped 3 ohms and 15 ohms output), plus 4 suitable Transistors giving approx. 1 watt. output. 30/6. P. & P. 2/-.

CONDENSERS. 5,000 mF/d. 19 v. wkg. Size 3 x 1/2 in. dia. 2 for each. P. & P. 6/6.

T.V. or AMPLIFIER EDGE CONTROL PANELS
Two 500k Log. pots; one 500k Log; one D/P mains switch. Brand New 3/6 per panel. P. & P. 1/-.

3-PUSH BUTTON SWITCH UNIT. 4 single pole changeover in each push-button. 3 x 1 1/2 x 1/2 in. Absolute Bargain at 4/6 each. P. & P. 1/- each.

MATCHED PAIR OF 21 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 in. Output trans. tapped 3 ohms and 15 ohm output. 10/- pair, plus 2/- P. & P. Worth double.

MARCONI QUARTZ CRYSTALS TYPES ZHS
Glass encapsulated, 2 wire lead out. Size 1 1/2 in. high x 3/4 in. dia. Following frequencies (Kcs) only available.

13583, 13646, 13708, 13771, 13833, 13896
13958, 14021, 14085, 14146, 14208, 14271
14333, 14396, 14459.

6/- each. P. & P. 1/- per crystal. 3 or more. Post Free.

Harverson Surplus Co. Ltd.

3-VALVE AUDIO AMPLIFIER MODEL HA34



Designed for Hi-Fi reproduction of records A.C. mains operation. Really built on plated heavy gauge metal chassis, size 7 1/2" x 4 in. d. x 3 1/2" h. Incorporates EC783, EL84, EZ80 valves, heavy duty double-wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, P. & P. etc., wired and tested for only

£4.5.0 P. & P. 5/-


TAPE DECKS

COLLARO STUDIO DECK. £10.10.0 plus 5/6 carr. and ins.
B.R. MONARDECK. Single speed. 3 1/2 in. per sec. simple control uses 5 1/2 in. spools. £8.15.0 plus 5/6 carr. and ins. (Tapes extra on both.)

STEREO AMPLIFIERS

Incorporating 2 EC182s and 1 EZ80, heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.

FEW ONLY

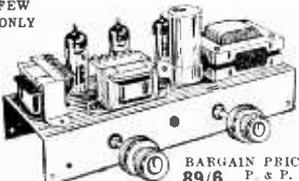

BARGAIN PRICE 89/6 P. & P. 5/-

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 8 1/2 x 3 1/2 in.). ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite rod aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time.

ONLY £4.5.0 P. & P. 2/6.

35 OHM SPEAKERS

Suitable for use with above. 2 in. Goodmans. Ideal replacement for most pocket portables, 8/6, 9/11n, 12/6; 5 in. 17/8; 7 x 4 in. 21/-.

Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker. 25/- P. & P. 2/-.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (incl. long and aerial coupling). 3/6 complete, post 1/6. 6 transistor printed circuit board to match 8/6. Post 9d. Circuit diagram 1/6 extra.

SPECIAL

TRANSISTOR BARGAINS

ALL BRAND NEW

GET 15 (Matched Pair) 15/-

OC71 5/-; OC76 6/-; AF117 7/8; Set of Mullard 6 transistors, OC44, 2—OC45, OC81D matched pair. OC81, 25/-

EDISWAN MAZDA

PXA101 6/8; XA103 6/8. R.F.1 Pack: 1—PXA102 Mixer; 2—PXA101 I.F. Amp.; (Equip. 06/44 and 06/45) 10/6 R.F.2 Pack: 2—PXA101 I.F.—PXA102 Oscillator 12/6 I.F.—PXA102 Mixer 12/6 I.F.—PXA101 Driver. Matched pair PXE171, mounted complete with heat sinks (Equip. OC81D and 06/41) 12/6 ALL TRANSISTORS POST FREE.

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. Size 7 1/2" w. x 2 1/2" d. x 8 1/2" h. This amplifier (which is used in a 29 in. record player) employs EC783 EL84, EZ80 valves. Bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Ready built and tested

PRICE 69/6 P. & P. 3/6

ALSO AVAILABLE. Mounted on board with output transformer and 8 in speaker, ready to fit into cabinet below. **PRICE 89/6.** P. & P. 4/6.

QUALITY PORTABLE RECORD PLAYER CABINET

1 in. motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or single Record Player Unit. Size 18 x 14 x 8 1/2 in.

PRICE £3.9.6 Carr. 5/-.

EMISSY PORTABLE RECORD PLAYER CABINET.

Will accommodate amplifier, up to 7 x 4 in. speaker and B.S.R. or GARRARD auto-changer or single player unit. Attractive rexine performance finish. Overall size 17 x 15 x 8 1/2 in. Supplied with 1 in. motor board. **PRICE 69/6.** Carr. 5/-.

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Makers' Original Packing

SINGLE PLAYERS
B.S.R. TU12 £3.10.0 Carr. 3/6
B.S.R. GU7 with unit mounted pick-up arm £4.18.8 Carr. 4/-

AUTO CHANGERS

B.S.R. UA14 £5.19.6
Latest B.S.R. UA16 £5.19.6
Garrard Auto-Matic £10.10.0
LATEST GARRARD AUTO-SLIM. With heavy duty, 4-pole motor. FEW ONLY £7.7.0. (Standard Auto-Slim £6.10.0.) Carr. 5/- on each.

NEW CARTRIDGE BARGAINS

B.S.R. TC85. High output compatible Stereo Cartridge. Brand new. Complete with Stereo LP/78 sapphire stylus and universal mounting bracket. Original price 47/11. OUR PRICE 22/6. P. & P. 1/-.

RONETTE STEREO 105 CARTRIDGE. Stereo/LP/78. Complete with two sapphires. Original list price 67/8. OUR PRICE 24/- P. & P. 1/-.
COLLARO HI-FI STEREO T/O CARTRIDGE. Type "C". Complete with universal bracket and stylus for Stereo, L.P. and 78. Original list price 59/8. OUR PRICE 25/- P. & P. 1/-.

E.M.I. 4-speed Player and P.U.

FURTHER HUGE PURCHASE enables us to offer these at

67/6 P. & P. 4/6.
Heavy 8 1/2 in. metal turntable. Low flutter performance. 200/250 rev. shaded motor with tap at 45v. for amplifier valve filament if required. Turnover LP/78 head.



THE NEW HARVERSON KIT FOR THE HOME CONSTRUCTOR

A really excellent all purpose A.C. mains 200/240v. **AMPLIFIER KIT TYPE HSL 'FOUR' 3 VALVE, 4 WATT USING EC883, EL84, EZ80 VALVES**



Special features include:

- Heavy duty double-wound mains-transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● All the kit fits into a chassis size only 7 1/2 in. x 4 in. deep. Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder etc (No extras to buy)

79/6 P. & P. 5/-

Comprehensive circuit diagram, practical layout and parts list 2/6. (Free with kit).

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram, allow records and announcements to follow each other. Fully shielded section wound output transformer to match 8-15 ohm speaker and independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EC83, EF86 and EZ80 together. Simple instruction booklet 1/6. (Free with parts).



All parts sold separately. **ONLY £6.19.6** P. & P. 6/6
Also available ready built and tested complete with standard input jack sockets. **£8.15.0.** P. & P. 6/6.
Carrying case for above 28/6 P. & P. 4/-

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI

● Peak output in excess of 12 watts. ● All standard British components. ● Built on printed circuit plate size 6 x 3 in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 8 ohm and 16 ohm speakers. ● Transistors (GET 114) or 81 Mullard OC81D and matched pair of OC81A p.p. 9 volt operation. ● Everything supplied, wire-battery clips, solder, etc. ● Comprehensive, easy to follow instructions and circuit diagram 1/6 (Free with kit). All parts sold separately.

SPECIAL PRICE 45/6 P. & P. 2/6
Also ready built and tested, 58/8. P. & P. 2/6.
A pair of TAI's are ideal for stereo



HARVERSON'S F.M. TUNER MK. I

● F.M. tuning head by famous maker. ● Guaranteed non-drift. ● Permeability tuning.

Frequency coverage 88.1-100 Mc/s. ● OA81F balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold (4 x 3 in. base). ● Self powered, using a good quality mains transformer and valve rectifier. ● Valves used EC85, two EF80s and EZ80 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 3 1/2 in. ● All parts sold separately.

Mark III Version as Mark I but with output stage (EC182) and tone control. £7.7.0. P. & P. 8/6. Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I, 25/- P. & P. 2/6. To fit Mark II, 17/8. P. & P. 2/6.



SPECIAL PURCHASE TURRET TUNERS

By famous maker. Brand new and unused. Complete with PV84 and PCF80 valves, 3A-35 Mc/s. I.F. Biscuits for Channels 1 to 5 and 8 to 9. Circuit diagram supplied. **ONLY 25/-** each. P. & P. 2/6.

BRAND NEW CYLON F.M. TUNER HEAD

Permeability tuned. 88.100 Mc/s. Printed circuit. A completely screened unit ready for direct mounting in chassis. 10.7 Mc/s. I.F. O/P. Supplied complete with EC85 valve and full circuit diagram. Aerial input circuit suitable for either 75 ohm unbalanced or 500 ohm balanced. Size only 5 1/2 in. x 2 1/2 in. x 1 1/2 in. h. (2 1/2 in. high with valve). Limited number only at 27/6. P. & P. 1/4.
Also available 19.7 Mc/s. I.F. trans. and disc. trans 11/6 pair. P. & P. 1/6.

GORLER F.M. TUNER HEAD

88-100 Mc/s. 10.7 Mc/s. I.F. 15/-, plus 1/9 P. & P. (EC85 valve, 8/8 extra)

SEE LEFT HAND PAGE FOR MORE ITEMS

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985

Open all day Saturday Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station (Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.
SEND STAMPED ADDRESS ENVELOPE WITH ALL ENQUIRIES

TRANSISTORS					
AC115	4/-	OA79	3/-	OC75	5/8
AC155	4/-	OA81	2/-	OC76	8/6
AC156	5/8	OA85	3/-	OC78	8/-
AC154	5/8	OA86	4/-	OC79	8/-
AC113	5/8	OA90	3/-	OC91	5/8
AC157	7/-	OA91	3/-	OC92	10/-
AD140	25/-	OA95	3/6	OC83	4/-
AF102	27/6	OC16W	35/-	OC84	8/-
AF114	11/-	OC19	25/-	OC139	8/-
AF115	10/8	OC26	25/-	OC140	19/-
AF116	5/-	OC35	12/-	OC141	31/-
AF117	9/6	OC36	21/6	OC169	10/-
AF118	20/-	OC41	8/-	OC170	8/6
AF124	11/-	OC42	8/-	OC171	8/-
AF125	10/8	OC43	12/6	OC200	10/6
AF126	10/-	OC44	5/-	OC201	29/-
AF127	9/6	OC45	5/-	OC202	24/6
BY100	7/8	OC70	6/6	OC203	13/-
BY114	8/-	OC71	4/3	OC204	19/-
GET113	6/9	OC72	5/6	OC312	31/-
GET114	6/8	2XCOT2		MAT100	7/9
GET115	9/6	matched		MAT101	8/6
GET116	17/-	pair	16/-	MAT120	7/9
OA70	3/-	OC73	16/-	MAT121	8/6
OA73	3/-	OC74	8/-	ADT140	15/-

SETS OF TRANSISTORS
 Set No. 1: comprising OC84, 2 x OC45, OC81, matched pair OC81, 20/-
 Set No. 2: comprising OC81, matched pair OC81, 10/-

CATALOGUE
 Our latest 1964/65 Catalogue is now available. Copies have been sent to many of our regular customers. If you have not received your copy please drop us a card. Please send 1/- in stamps.

Trade catalogue now available. Please apply on business letter-heading.

TERMS: Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d. Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

ALPHA

RADIO SUPPLY CO.
 103 LEEDS TERRACE
 WINTOUN STREET
 LEEDS 7



MICROPHONES

MIC 39/1	32/6
MIC 40	19/6
MIC 45	19/6
Foster DFI Dynamic 500 ohms	39/6
Foster DFI Dynamic 50K ohms	39/6
DX 62 Dynamic	69/6
DX 29	49/6
CM21 Planet	12/6
DM15 Dynamic	49/6
MC70 Crystal	69/6
100C Crystal	39/6
DM16HL Dual Imp.	147/-

MULTI-RANGE TESTMETERS

Eagle TK20A	£2.96
Eagle EP10K	£4.96
Eagle EP20K	£4.19.6
Eagle EP30K	£6.19.6
Leather Case for above	19/6.
Eagle EP50K	£9.19.6
Leather Case for above	20/6.
Caby M1	£2.14.0
Caby A10	£4.17.8
Caby B40	£6.2.6
Altium 200H	£5.5.0
Taylor 127A	£10.10.0
Leather Case for above	£2.5.0.

RECORD PLAYER AND TAPE DECK UNITS

BSR Monarch UA14, £6.6.0.
 Stereo Version, £6.17.6.
 BSR Monarch UA15, £6.19.6.
 Stereo Version, £7.15.0.
 BSR Monarch TU12, £3.10.0.
 Battery version of above, £3.17.6.
 BSR Monarch GUT, £3.17.6.
 Battery version of above, £4.4.0.
 BSR Monarch TP2 Tape deck, 2 track, £8.8.0.
 4 track version of above, £9.9.0.
 Garrard Autoslim, £6.19.6.
 BSR Monarch TD10 Tapedeck, 2 track, £9.9.0.
 4 track version of above, £10.10.0.
 Garrard Autoslim De Luxe Model AT6, £11.5.0.

GOODMAN HIGH FIDELITY LOUDSPEAKERS

8" Axiette 8, 6 watts, £5.5.7; 10" Axiom 10, 10 watts, £6.5.11;
 12" Axiom 2201, 15 watts, £10.17.4; 12" Axiom 301, 20 watts, £15.4.6;
 9" Axiom 80, 6 watts, £20.6.3; 12" Triaxiom 1220c, 20 watts, £18.10.0.

DM1 Dynamic	105/-
GCM5 Guitar	12/6
BM3	45/-

All the above are listed and illustrated in our current catalogue along with many stands etc.


MAINS TRANSFORMERS

Primaries 200/230/250V

250-0-203v 80mA 0-4-6.3v 4A 0-4-5v 2A	21/9
300-0-300v 80mA 0-6.3v 4A 0-6.3v 1A	22/6
350-0-350v 80mA 0-4-6.3v 4A 0-4-5v 2A	21/9
250-0-250v 100mA 0-6.3v 4A 0-5v 2A	27/6
350-0-350v 100mA 0-6.3v 4A 0-5v 2A	27/6
350-0-350v 200mA 0-6.3v 4A 0-5v 3A	55/-

TRANSISTOR AMPLIFIER T65 KE

15WT—Two mixing and separately controlled inputs. Description: P/Pull Class B.P.A. set with inputs for microphone and gram. Operated from 12v. battery. Output 15 watts Peak into 15 ohm load. Fully mixing inputs. Pre-amplifier stage being of such sensitivity that practically any make or type of microphone may be used. Specification: Mic Sensitivity 2 m.v. (600 ohm). Gram sensitivity 200 m.v. (100K). for full output. Frequency response ±3 dB 60 c.p.s. to 7 Kc/s. Harmonic distortion 1% at 10 watts. Current Consumption: Quiescence 270 mA. Average Speech Music 1.3/1.5 Amps. Size: 9" x 5" x 6 1/2". Weight 6 1/2 lbs. Special Features: Sensible size permits generous heat sink which is 10 swg. aluminium and occupies whole of roof area. Accret is upon reliability, even to extent of hand-made wire-wound resistors. Useful output even when worked from car battery down to 10v.. £16.10.0.

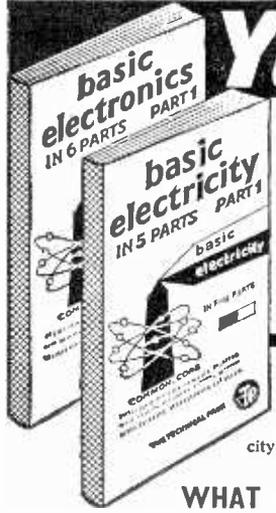

YOURS FREE FOR 7 DAYS

The New 'Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate, cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

"After reading section on Filter Circuits once, I understood more about them than in a whole year from the obscurities of other manuals." L.G. West Wickham. "I must say they are the best books on the subject as they explain in simple language what other books make hard going of." C.B. Hartlepool. "They have a wonderful system of imparting the subject to the beginner." H.C.L. Leicester. "What a contrast to the many text books I have attempted to struggle through." J.G. Rugby. A TECH- PRESS PUBLICATION

To Selray Book Co.

60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY BASIC ELECTRONICS

Signature _____ (If under 21, signature of parent or guardian)

Name _____

BLOCK LETTERS BELOW

FULL POSTAL

Address _____

POST NOW FOR THIS OFFER!!

R.C.S.

BRADFORD, BRISTOL, BIRMINGHAM, DERBY, DARLINGTON, EDINBURGH, GLASGOW, HULL, LEICESTER, LEEDS, LIVERPOOL, LONDON, MANCHESTER, MIDDLESBROUGH, SHEFFIELD

PAGE 614 FOR ADDRESSES

BASS-MAJOR 30 WATT GUITAR AMPLIFIER

A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

Eminently suitable for bass, lead or rhythm guitar and all other musical instruments

- * Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- * Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- * Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vmair.
- * For 200-250 v. to 50 c.p.s. A.C. mains operation.
- * Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- * Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- * LEVEL frequency response throughout the audible range.
- * SUPERIOR TO UNITS AT TWICE THE COST.

39½ Gns.

Send S.A.E. for leaflet OR DEPOSIT £4.3.0 and 12 monthly payments of £3.8.11. Carr. 17/6.

R.S.C. G5 GUITAR AMPLIFIER

5-watt high quality output. Incorporating high flux 12in. 10 watt 12,000 line loudspeaker. Sensitivity 50 m.v. High impedance jack input. Handsome strongly made cabinet (size 14 x 14 x 7in. approx.) finished in complementary shades of Rexine/Tygan. 200-250 A.C. mains. OR DEPOSIT £2/3 and 9 monthly payments of £2/3. Carr. 7/6

LINEAR TREMOLOPREAMP. UNIT Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruption), Depth (for heavy or light effect) Volume and Switch. Three sockets are for two inputs and Foot Switch. **4 Gns. ONLY**

R.S.C. SENIOR 15 WATT LEAD OR RHYTHM GUITAR AMPLIFIER

High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Cabinet is well made and finished as Junior Model. Size approx. 18 x 18 x 8in.

Only **19 Gns.** Carr. 10/-

Send S.A.E. for leaflet. OR DEPOSIT 99/11 and twelve monthly payments of 33/4


R.S.C. B20 BASS GUITAR AMPLIFIER

A highly efficient unit incorporating a massive 6in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vmair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains.

Send S.A.E. for leaflet. **29½ Gns.** OR Deposit £3.2.0 and 12 monthly payments of 51/8. Carr. 17/6.

HE-40 De-Luxe 4 COMMUNICATION RECEIVERS

50/60 c.p.s. A.C. mains operation. Frequencies covered 550 Kc/s to 30 Mc/s continuous. Incorporates 5in. speaker. Slide rule tuning dial, 5v. meter. Internal ferrite aerial for medium wave. Telescopic whip aerial 59in. 10 section for short waves. Fitted sockets for optional outdoor aerial. Headphone, external speaker socket. Other features are electrical bandspread tuning, 0-100 logging scale. Noise limiter, A.V.C., B.F.O., stand by switch. Size approx. 14 x 9 x 5in. Handsome grey crackle finished metal cabinet with chromium fittings. Brand new with full instructions manual. Usual guarantee. **TERMS:** Deposit £3.15.0, and nine monthly payments of 52/6. Cash price cleared only **£24.15.0** Carr. in 3 months

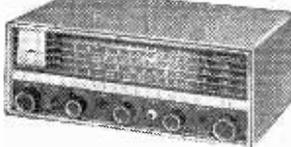

HE-30 4 Band

Continuous coverage 550 Kc/s to 30 Mc/s. Illuminated slide rule dial. Edgewise 'S' meter 0-100 logging scale. Built in 'Q' multiplier aerial trimmer electrical bandspread, noise limiter, controls are: Function switch, audio gain, selectivity, frequency (B.F.O.), band selector, audio gain, trimmer, A.V.C./M.V.C. Switch, ANL switch, main tuning, bandspread tuning. Output for H/Phones or standard speaker. Provides 15 watts output. Size 15 x 10 x 7in. For 220/240v. 50/60 c.p.s. A.C. mains. A highly efficient receiver representing exceptional value at only **40 Gns.** Post Free.

TERMS: Deposit £5.4.0, and nine monthly payments of 91/2. Cash price if settled in 3 months.

SELENIUM RECTIFIERS

F.W. BRIDGE	24 v. 2 amp.	.. 14/9
6/12 v. 1a.	3/11 24 v. 20 amp.	89/9
6/12 v. 2a.	6/11 H.T. TYPES H.W.	
6/12 v. 3a.	9/9 150 v. 40 mA	.. 3/9
6/12 v. 4a.	12/3 250 v. 50 mA	.. 3/11
6/12 v. 6a.	15/3 250 v. 60 mA	.. 4/11
6/12 v. 10a.	19/9 250 v. 100 mA	.. 5/11
6/12 v. 15a.	35/9 250 v. 250 mA	.. 11/9

CONTACT COOLED. 250 v. 75 mA. F.W. (Bridge). 10/11. 250 v. 50 mA. F.W. (Bridge). 8/11. H.W. 250 v. 60 mA. 5/11.

HI-FI 10-WATT AMPLIFIERS

Brand New Complete Units. **£7.19.6** Carr. 5/6
Manufacturer's discontinued Model. Push-Pull output. Latest high efficiency valves. Dual separately controlled inputs for "Mike" and gram. Separate Bass and Treble Controls. High Sensitivity. Output for 3 or 15 ohm speaker. Guaranteed tested and in perfect working order.

LARGE REXINE COVERED SPEAKER CABINETS. Full range for 12", 15" and 18" Speakers. Cash or H.P. **from 11 Gns.** Send S.A.E. for leaflet.

HEAVY DUTY LOUDSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS

Type BGL. Suitable for Bass Guitar. Speaker Unit 15in., High Flux, 15 ohms. 30 watts. Cabinet size approx. 24 x 21 x 13in. Only 19½ Gns. OR Deposit 43/- and 12 monthly payments of 34/- Type BG3/2. Suitable Bass and Lead Guitar. Two 12in. high flux 15 ohm 25 watt speakers, one with aluminium speech coil and dual cone to provide smooth frequency response from 25 to 10,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of grey Vmair and Rexine. Rating 50 watts. Only 29 Gns. OR Deposit £3.7.6 and 12 monthly payments of 50/-.

FANE EXTRA HEAVY DUTY LOUDSPEAKER 15in. TYPE 153. 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm voice coil. Only 18 Gns., OR Deposit 37/6 and 12 monthly payments of 31/6.


FANE EXTRA HEAVY 1/SPEAKER 13in. 18in., 15 ohms. 60 watts. 3in. diam. Speech Coil. Total Flux 375,000 lines. High sensitivity. ONLY 24 Gns., OR Deposit 51/- and 12 monthly payments of 42/9. Send S.A.E. for leaflet on 153 and 183.

TRANSRECEIVERS. Two-way Transmitter Receivers. 9 transistor S/H circuit. Crystal controlled range up to 6 mcs according to conditions. Size of each unit 6½ x 3 x 1¼in. Complete with batteries, Telescopic aerials and leather cases. Brand new guaranteed **£25.0.0** Per Pair.

COMPLETE POWER PACK KIT, 19/11 Consisting of Mains Trans., Metal Rectifier, Double electrolytic, smoothing choke chassis and circuit. For 200-250 v. A.C. mains. Output 250 v. 60 mA. 6.3 v. 2 a.

R.S.C. POWER PACK, 39/9. Louvred metal case only 8 x 5 x 1¼in. Stove enamelled. For 200-250 v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA. fully smoothed at 6.3 v. 2 a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

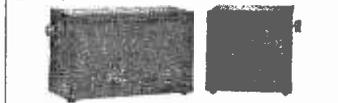R.S.C. BATTERY ALARM or INTER-COMM. KIT. Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully intercomm. Controllable at both units. An intercomm. of this class would normally cost £20-£30. Only 89/6, carr. 5/- or assembled ready for use 6 Gns.



TRANSISTOR SALE. Mullard OC71 3/9, OC45 4/6, OC44 4/11, OC72 4/9, OC81 4/11, OC171 5/6, Edisval XA101 3/6, XB102 3/9, XA112 3/9, XB113 3/9, XB104 3/9, XC101A 3/9. Postage 6d. for up to 3 Transistors, EX. GOVT. SMOOTHING CHOKES. 200 mA. 3-5 H. 50 ohms. Parmeko 8/9. 150 mA. 10 H. 50 ohms. 9/9. 120 mA. 12 H. 100 ohms. 8/9. 60 mA. 50 H. 1,000 ohms 6/9. 100 mA. 10 H. 100 ohms 6/9. 60 mA. 5-10 H. 250 ohms 2/11.

EX GOVT SELENIUM RECTIFIERS 12v 15 AMP 19/9 (BRIDGE) F.W. ONLY

R.S.C. (Manchester) Ltd.

MAIL ORDERS TO:

54 WELLINGTON STREET, LEEDS 1

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied.

S.A.E. with all enquiries, please. Personal shoppers welcomed at any of the branches below. Open all day Saturday.

BRADFORD 54 Morley Street, Nr. Alhambra Theatre (Half-day Wednesday)

BRISTOL 14 Lower Castle Street Open 5th October

BIRMINGHAM 6 Gt. Western Arcade, opp. Snow Hill Station (No half day)

DERBY 26 Osaston Rd., The Spot (Half-day Wednesday)

DARLINGTON 13 Post House Wynd (Half-day Wednesday)

EDINBURGH 133 Leith Street (Half-day Wed.)

GLASGOW 326 Argyle Street (Half-day Tuesday)

HULL 51 Savile Street (Half-day Thursday)

LEICESTER 32 High Street (Half-day Thursday)

LEEDS 5-7 County (Mecca) Arcade (No half-day closing)

LIVERPOOL 73 Dale Street (No half-day closing)

LONDON 238 Edgware Road (Half-day Thursday)

MANCHESTER 8-10 Brown St. (Market Street) (No half-day)

MIDDLESBROUGH 106 Newport Rd. (Half-day Wednesday)

SHEFFIELD 13 Exchange Street, Castle Market Bldgs (Half-day Thursday)


Ex. Gov. 2 v. Accumulators. 16 A.H. Size 7 x 4 x 2ins. Brand new. 4/9 each. Three for 12/6, carr. 5/-.

Jason FMTI V.H.F./F.M. Radio Tuner design. Total cost of parts including valves, Tuning dial, Escutcheon, etc., £6.19.6.

LINEAR L45 MINIATURE 45 WATT QUALITY AMPLIFIER. Suitable for any record playing unit and most microphones. Negative feedback 12dB. Separate Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves E280, ECC83, EL84. Size only 7 x 5 x 5 1/2 in. high. Guaranteed 12 months. Price 6 gns. Send S.A.E. for leaflet. Terms: Deposit 2/4/9 and 5 monthly payments of 2/4/9.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

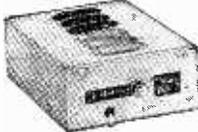R.S.C. BATTERY TO MAINS TYPE BML. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 and 90 v. This includes low consumption types. Complete kit with diagrams, 39/9, or ready to use, 46/6.



kit of parts with diagrams and instructions, 49/9, or ready for use, 59/6.

R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp, Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response ± 3 dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUT-DOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

11Gns.

Carr. 10/-.

TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9. Suitable microphones and speakers available at competitive prices

FANE HEAVY DUTY HI-FI SPEAKERS

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 122/10 20watt, 5gns. 122/10A 20watt, 6 gns. 122/12 20watt, 7 gns. 122/12A 20watt, 8 gns. 122/12 22watt, 9 gns. 122/12A 22watt, 10 gns. 122/12 25watt, £11.17.6 122/12A 25watt, £12.17.6
15in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 152/12 20watt, 12 gns. 152/12A 20watt, 13gns. 152/12 27watt, 14gns. 152/12A 27watt, 15gns. 152/13 27watt, 16gns. 152/13A 27watt, 17gns. "A" indicates dual cone type. 300-250 c.p.s. Send S.A.E. for leaflets. Terms available.

R.S.C. 4/5 WATT A5 HIGH-GAIN AMPLIFIER

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest High-fidelity pick-up heads, in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long playing equalisation. Hum level is negligible being 71 dB down. 45 dB of Negative Feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s, and includes fully punched chassis (with baseplate) and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0 or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 4 monthly payments of 22/6 for assembled unit.

THE SKYPOUR T.R.F. RECEIVER. A design for a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage with low distortion detector. Valve line-up 6KT, SP61, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-Point wiring diagrams, instructions and parts list 1/9, maximum building cost £4.19.6, inc. attractive walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

TWEETERS, R.A. 3 ohm 25/9; 15 ohm 25/9

R.A. 12in. DUAL CONE 3 ohm 8 watt Speakers. Ideal for Stereo. Only 30/0 ea.

TYPE BM2. Size 8 x 5 1/2 x 2 1/2 in.

Supplies 120 v. 90 v. and 60 v. 40 mA and 2 v. 0.4 a. to 1 amp. fully smoothed. Theoretically completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. 84 U.M.A. FOR ALL BATTERY R.F. RECEIVERS normally using 2 v. accumulators. Complete kit of parts with diagrams and instructions, 49/9, or ready for use, 59/6.

12in. 10 WATT HIGH QUALITY LOUSPEAKER.

In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6. Carr. 5/-.

Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6. For larger types see page 613.

R.S.C. CORNER CONSOLE CABINETS

Polished walnut veneer finish. Pleasing design.

JUNIOR MODEL. Size 20 x 11 x 8in. for 8 x 5in. or 10 x 6in. speakers. £2.9.9.

STANDARD MODEL. Size 27 x 18 x 12in. for 8 or 10in. speakers. £4.11.9.

SENIOR MODEL. Size 30 x 20 x 15in. for 12in. Speaker. Suitable Speaker systems below. Only 7 gns.

AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; crossover unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprising realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/-.

R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL. Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished Walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensures superb reproduction for only £3.19.6.

STANDARD MODEL. As above but for 12in. speakers. Size 20 x 15 x 13in. For vertical or horizontal use, £5.19.6. Set of legs with brass ferrules, 19/6.

P.M. SPEAKERS. 10in. W.B. "Stentorian"

3 or 15 ohms type HF1012 10 watts, hi-fidelity type. Recommended for use with our All 11 Amplifier, £4.12.6. 12in. R.A. 3 ohms 10 watts (12,000 lines), 59/6.

ARMSTRONG, DULCI, LINEAR, ROGERS, LEAK and JASON EQUIPMENT, GOODMAN'S, W.B. and FANE SPEAKERS, GARRARD and GOLDRING T/ABLES CASH or H.P.

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, W/Ch. and Vol. Only 250 v. 15 mA H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. A.T. Basic Meter sensitivity 150 microamps A.C. and D.C. ranges £4.11.6. R.40. Sensitivity up to 10,000 ohms per volt A.C. and D.C. £5.2.6. 30,000 ohms per volt, with overload buzzer, £8.19.6.

MULTI-METER, CABY MII. Sensitivity 2,000 ohms per volt. A.C. and D.C. 54/-.

A.T. Basic Meter sensitivity 150 microamps A.C. and D.C. ranges £4.11.6. R.40. Sensitivity up to 10,000 ohms per volt A.C. and D.C. £5.2.6. 30,000 ohms per volt, with overload buzzer, £8.19.6.

AUDIOTRINE HI-FI TAPE RECORDER KIT 25¹ GNS.

REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR
 Incorporating the latest Collaro Studio Tape Transcriptor. The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds, High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet tastefully covered in two contrasting shades of Rexine and Vinyl, size 14 1/2 x 8 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets.
TERMS. Deposit £2-13-9 and 12 monthly payments of 44/-. Cash price if settled in 3 months.



ONLY 3 PAIRS OF SOLDERED JOINTS PLUS MAINS

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT 'BUILT-IN' TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mlke" and gram., as in A10 High sensitivity. Includes 5 valves, ECC83, ECC83-EL84, EL84, E281. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut".** Frequency response - 3 dB 30-30,000 c/s. Six negative feedback loops. Hum level 60 dB. **ONLY 23 millivolts INPUT required for FULL OUTPUT.** Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for **STANDARD or LONG PLAYING RECORDS.** For **MUSICAL INSTRUMENTS** such as **STRING BASS, LEAD or RHYTHM GUITARS, etc.**



OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5 A. For supply of a **RADIO FEDER UNIT.** Size approx. 12 x 9 x 7 1/2 in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohms speaker. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. **Only 8 Gns.** Carr. 10/-. (Or factory built 51/- extra.)
 If required louvered metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9 and 9 monthly payments of 24/9.** Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

LINEAR TAPE PRE-AMPLIFIER, Type LP/1, Switched Negative feedback Equalisation. Positions for Record 14in., 3 1/2in., 7in. and Playback. FM84 Recording Level Indicator. Designed primarily as the link between a Collaro Tape Transcriptor and a high fidelity amplifier, but suitable for almost any Tape Deck. **Only 9 gns. S.A.E. for leaflet.**

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation for "lift" and "cut". Provision is made for use as straight (monoaural) 10-watt amplifier. Valve line-up ECC83, ECC83-EL84, EL84, E281. Outputs for 2-3 ohm speakers. **Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. 8 Gns.** Full constructional details and price list 2/6. Carr. 10/- ready to use for 59/6 extra.

Kit can be supplied assembled and ready to use for 59/6 extra.


R.S.C. GRAM. AMPLIFIER KIT. 3 watts output. Negative feedback. Controls Vol. Tone and Switch. Mains covered in two contrasting shades of Rexine and Vinyl. **200-250 v. A.C. Fully isolated chassis.** Circuit, etc., supplied. **Only 39/9. Carr. 3/9.**
III-FI CRYSTAL PICK-UP HEADS. (Cartridges) Aco's Standard replacement for Garrard, B.S.R. and Collaro. 16/9. Aco's Stereo-Monaural 29/9. Ronette Stereo-Monaural 39/9. B.S.R. Stereo 39/9.
BRADMATIC RECORDING HEADS. High Impedance Record/Playback 22/-. Low Impedance Erase, 12/6.
MARRIOTT RECORDING HEADS. High Impedance. Record/Playback. Low Impedance. Erase, 25/- pair
PICK-UP ARMS. Complete and with latest Aco's/hi-f Turnover Cartridge 29/11 **CRYSTAL MICROPHONES.** Hand type NP110 14/9. R.T.C. 19/9. Aco's Mic 40 25/9. Aco's Mic 45 25/9. Stick type Aco's 39-1 39/9. BM3 with neck band and heavy table stand 59/9. Lapel type 29/9.
COLLARO JUNIOR. 4-speed Single Player Unit and Crystal Pick-up with hi-f Turnover head. **Only 25-18-6.**
B.S.R. UA14 4-sp'd AUTO-CHANGERS with hi-f turnover head, 24-19-6. Carr. 4/6.
GARRARD AUTO-SLIM 4-SPEED AUTO-CHANGER with high fidelity pick-up. Latest model. For 200-250 v. A.C. mains, 27-17-6. Carr. 4/6.
GARRARD ATC AUTO-SLIM DELUXE 4-SPEED AUTO-CHANGERS. Turnover GC8 head. For 200-250 v. A.C. mains, £11-9-0.
GL3A MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2/3 ohm speaker. For 200-250 v. A.C. mains, Size 1 1/2 x 2 1/2 in. Controls: Vol. and Tone with Switch. **Only 59/6.**

SENSATIONAL STEREO OFFER

A complete set of parts for the construction of a **4 Gns.** quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 19/9 extra with above only.

HEAVY DUTY CHARGER KIT 6/12 v. 6 amps., variable output. Consisting of Mains Transformer 0-250-250 v. P.W. (Bridge) Selenium Rectifier. Ammeter. Variable Charge Rate Selector Panels. Plugs. Fuses. Fuseholder and circuit. **59/9. Carr. 4/6.**

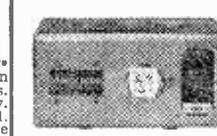R.S.C. BATTERY CHARGING EQUIPMENT Guaranteed 12 months



All for A.C. Mains 200-250v. 50c s.
ASSEMBLED 6/12 v. 2 amps. Fitted Ammeter and selector plug for 8 v. or 12 v. Louvered metal case. Attractive selector plug for 6 v. or 12 v. Fused, ready for use with mains and output leads. **39/9 Carr. 3/9.** 6/12v. 1 amp. 27/9 Less meter.

charging. Louvered steel case with stoved grey hammer finish. Fused and ready for use with mains and output leads and battery clips. Carr. 4/6. **59/9**
 Terms: Deposit 12/- and 5 monthly payments of 12/-.

BATTERY CHARGER KITS Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses. Fuse-holders. Grommets, panels, Heavy Duty Clips, circuit. Carr. 3/6 extra.
 6v. or 12v. 1 amp. 22/9
 As above with Ammeter 29/9
 6v. or 12 v. 2 amps. 25/9
 6v. or 12 v. 2 amps. Inclusive of Ammeter. 35/9
 6v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 52/9

CHARGER AMMETERS 0-1.5 a. 0-4 a. 0-7 a. 8/9 each.

R.S.C. MAINS TRANSFORMERS (GUARANTEED)

200-230-250 v. 50 c/s. Screened	
TOP SHROUDED DROP THROUGH	
250-0-250v. 70mA. 6.3v. 2a. 0.5-6.3v. 2a	17/9
350-0-350v. 80mA. 6.3v. 2a. 0.5-6.3v. 2a	19/9
250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a	21/9
250-0-250v. 100mA. 6.3v. 3.5a. C.T. 5v.	19/9
300-0-300v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a	27/9
Mullard 510 Amplifier	33/9
300-0-300v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a	27/9
350-0-350v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a	27/9
350-0-350v. 150mA. 6.3v. 4a. 0.5-6.3v. 3a	35/9
a. for Mullard Amplifier	35/9
350-0-350v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a	28/9
350-0-350v. 150mA. 6.3v. 4a. 0.5-6.3v. 3a	37/9
FULLY SHROUDED UPRIGHT	
250-0-250v. 60mA. 6.3v. 2a. 0.5-6.3v. 2a	17/11
250-0-250v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a	28/9
300-0-300v. 100mA. 6.3v. 4a. 5v. 3a	28/9
300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v.	35/9
FULLY SHROUDED	
250-0-250v. 60mA. 6.3v. 2a. 0.5-6.3v. 2a	17/11
250-0-250v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a	28/9
300-0-300v. 100mA. 6.3v. 4a. 5v. 3a	28/9
300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v.	35/9
a. for Mullard Amplifier	35/9
350-0-350v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a	28/9
350-0-350v. 150mA. 6.3v. 4a. 0.5-6.3v. 3a	37/9

CHARGER KIT, 12 v. 14 AMP or 24 v. 7 AMP
 Consisting of mains trans. 200-250-250 v. F.W. (Bridge) Selenium Rectifier. Ammeter. Fuses. Variable Resistor. Heavy Steel Stove enamelled case and Circuit. **Only 29-19-6. Carr. 15/-.** Please state if 12 v. or 24 v. kit required.

SMOOTHING CHOKES
 150mA. 7-10 H. 250 ohms ... 11/9
 100mA. 10 H. 300 ohms ... 8/9
 50mA. 10 H. 300 ohms ... 5/9
 60mA. 10 H. 400 ohms ... 4/11

CHARGER TRANSFORMERS
 All with 200-250v. 50 c/s Primaries:
 0-9-15v. 1a. 12/9; 0-9-15v. 2a. 14/9; 0-9-15v. 3a. 16/9; 0-9-15v. 5a. 19/9; 0-9-15v. 6a. 23/9; 0-9-15v. 8a. 28/9.

AKT-O (Step up/Step down) TRANS.
 0-110/120/230/250v. 50-80 watts. 13/9; 250 watts. 39/9; 150 watts. 27/9.

MICROPHONE TRANSFORMERS
 120:1 high grade. clamped. 8/9.

INTRODUCING THE R.S.C. STEREO/20 HIGH FIDELITY AMPLIFIER PROVIDING 10/14 WATTS ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL


Facilities include:

- * Three-position tone compensation switch.
- * Stereo/Mono switch so that peak monaural output of 28 watts can be obtained.
- * Separate Bass 'lift' and 'cut' and 'treble' 'lift' and 'cut' controls.
- * Neon panel indicator.

SUITABLE for 'MIKE', GRAM, RADIO OR TAPE.

INTENDED FOR THE HOME or STUDIO BUT EQUALLY SUITABLE FOR LARGE HALLS or CLUBS.

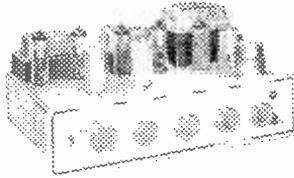For operation on standard 200-250v. A.C. mains.




Complete set of parts with point to point wiring diagrams and instructions, or Factory assembled, tested and supplied with our usual 12 months' guarantee for 16 gns. Or DEPOSIT 37/9 and nine monthly payments of 37/9. Protective wooden cabinet covered in pleasing shade of leathercloth and fitted carrying handles and plastic feet 59/9 extra or DEPOSIT 6/9 and nine monthly payments of 6/9.

12GNS. Carr. 10/-

Based on a current Mullard design and employing valves ECC83, ECC83, ECL86, ECL86, ECL86, ECL86, ECL86, EZ81. Output transformers are high quality sectionally wound to required specification. Output matchings for 3 and 15 ohm speakers on each channel. FREQUENCY RESPONSE + 2dB. 30-20,000 c.p.s. Hum level 65dB down. SENSITIVITY: 15 millivolts maximum. Send S.A.E. for illustrated leaflet.

THE AUDIOTRINE 3D/1

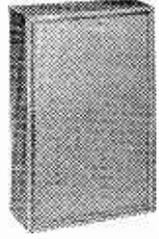

A complete three diaphragm high fidelity loudspeaker unit designed to occupy a minimum of space. Depth is only approx. 3in. Height 24in. Width 15in. This has been made possible by the latest developments in loudspeaker design. The 12in. cast chassis Bass unit has a resonant frequency which is extraordinarily low. It has a second diaphragm which extends the frequency range to 17,000 c.p.s. A further speaker operates only on the middle frequencies and ensures a smooth response from 40-17,000 c.p.s. Rating 20 watts. Imp. 15 ohms. Cabinet finish is either polished walnut veneer or leathercloth to match stereo/20 cabinet. Highly recommended for any Stereo or Mono amplifier. **11GNS.** Or Deposit 25/9 and nine monthly payments of 25/9.

R.S.C. COLUMN SPEAKERS

Cabinets polished walnut finish. Ideal units for vocalists and public address systems.


Type C58 20 watts for 15 ohms and 100v. line. Fitted five 3in. high flux P.M. Speakers and matching transformers. Size approx. 42 x 10 x 5in. **15GNS.** Carr. 10/-

Or Deposit 34/9 and nine monthly payments of 34/9.

Type C37 as above model but 10 watts rating and incorporating five elliptical speakers with an overall size of approx. 26 x 9 x 4in. **11gns.** Carr. 7/6

or DEPOSIT 25/9 and nine monthly payments of 25/9.

TRANSISTORISED MICROPHONE MIXER

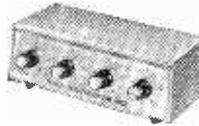

Enables mixing of up to 4 instruments, i.e. mic, tape, gram, tunes, etc., into single output. Compact and completely self-contained uses standard outputs take **59/6**

9v. battery. Inputs and standard plugs. PRICE

R.S.C. BRADFORD, BRISTOL, BIRMINGHAM, DERBY, DARLINGTON, EDINBURGH, GLASGOW, HULL, LEICESTER, LEEDS, LIVERPOOL, LONDON, MANCHESTER, MIDDLESBROUGH, SHEFFIELD

PAGE 614 FOR ADDRESSES

HOME RADIO CATALOGUE

New Edition! New Policy!

With the arrival of the 10th Edition of the famous Home Radio Catalogue we announce a fresh policy. The new price of 5/- will just cover the cost of the paper and printing, but on the first page of the catalogue you will find 5 coupons, each worth 1/- if used as directed. Briefly the system will operate thus: for each complete £1 of your order you enclose one of the coupons and deduct 1/- from the money you send. **There is no time limit** so if you purchase £5 worth of components from us—even though spread over several years—your catalogue will have cost you nothing!

We need only add that our new Catalogue is bigger and better than ever . . . so fill in the Coupon, enclose 6/- [5/- plus 1/- postage], and pop it in a letter box right away!

PLEASE WRITE YOUR NAME & ADDRESS IN BLOCK CAPITALS

NAME _____

ADDRESS _____

HOME RADIO LTD., DEPT. P.W., 187 LONDON RD., MITCHAM, SURREY

Why NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

BACKED BY OUR SUPER AFTER SALES SERVICE


ROAMER SEVEN Mk III

5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification ★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 9 stages—7 transistors and 2 diodes
Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned heavy duty 5in. speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Real leather look case with felt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses 1287 battery available anywhere).

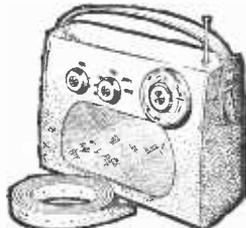Total cost of parts now only **£5.19.6** P. & P. 5/6
Parts Price List and easy build plans 3/-




"... amazed at volume and performance... has really come up to my expectations."
S. G. Stockton-on-Tees.

● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push-pull output.

MELODY SIX

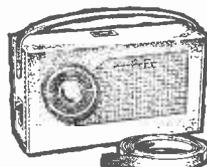

Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2in. approx. with felt speaker grille and supplied with hand and shoulder straps.
Parts Price List and Total cost of all **£3.9.6** P. & P. 3/-
easy build plans 2/- parts now only


TRANSONA FIVE

"Home, Light, A.F.N.; Lux. all at good volume"
G.P. Durham

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser volume control, new type fine tone super dynamic 2 1/2in. speaker etc. Attractive case—Size 6 1/2 x 4 1/2 x 1 1/2in. battery available anywhere.

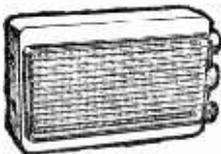Parts Price List and easy build plans 2/-



with red speaker grille. (Uses 1289 battery available anywhere).
Total cost of all parts now only **42/6** P. & P. 3/6

TRANSONA SIX

● 8 stage—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull transformers for ample power. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2in. (Uses PP4 battery available anywhere).

Total cost of all parts now only **59/6** P. & P. 3/6
Parts Price List and easy build plans 2/-



POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2in. moving coil speaker, built into attractive black case with red speaker grille. Size 4 1/2 x 1 1/2 x 3 1/2in. (Uses 1289 battery available anywhere).
Parts Price List and easy build plans 1/6.

Total cost of all parts now only **42/6** P. & P. 3/-



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful

reception. Special circuit incorporating 2 RF Stages, push-pull output. 3in speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2in. (Uses 9v battery, available anywhere).
Total cost of all parts now only **£3.19.6** P. & P. 3/6
Parts Price List and easy build plans 2/-



ROAMER SIX NEW!!


NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND!!

● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long waves. Trawler band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with felt fittings. Size 7 1/2 x 5 1/2 x 1 1/2in. Carrying strap 2/- extra.

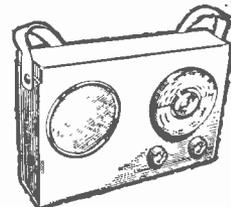★ Extra band for easier tuning of LUX, etc.
Parts Price List and easy build plans 2/- Total cost of all parts now only **£3.19.6** P. & P. 3/6



All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at prices stated. Overseas post 10/-.

RADIO EXCHANGE CO.
61, HIGH STREET, BEDFORD. Phone: 2367

Callers side entrance
Barratts Shoe Shop
Open 9—5 p.m.
Sats. 10—12.30 p.m.

THE TRIPLETONE HI-FI MAJOR

PRICE ONLY **£15.18.9** COMPLETE
Guaranteed 12 Months



A 12 watt quality amplifier incorporating negative feedback, with a pre-amp for mic. and provision for mic./gram mixing. Frequency response ± 1 dB 15-20,000 c/s. Distortion only 0.15%, with noise and hum -50 dB. Separate Bass, Middle and Treble lift controls. Valve line-up: 6X7, 12AX7, 6L6, EL84 and EZ81. Push-pull output with matching to 3 or 15 Ω . Fully isolated power supply from 200/250 v. A.C. input, with take-off for tuner etc. Size 12 x 6 x 6 in. high.

De Luxe Case: 14in. x 9in. x 7in., 30/- extra.

NEW R.C.S. VALVES 90-day guarantee

1R5	6/-	6Q7G	6/-	6BC41	8/-	6PCL84	5/-
18S	6/-	6D87	5/-	6BC8	5/-	6PL81	10/-
1T4	3/-	6V6G	5/-	6BF50	5/-	6PL83	8/-
384	7/-	6X4	5/-	6ECH42	9/-	6PY80	7/-
3V4	7/-	6X5	6/-	6ECH81	9/-	6PY81	8/-
5U4	6/-	12AT7	6/-	6ECL80	9/-	6PY82	7/-
6	6/-	12AC7	6/-	6ECL82	10/-	6PY83	8/-
5Y3	6/-	12AX7	7/-	6EF183	7/-	6SP1	3/-
5Z4	9/-	12K7	5/-	6EF184	7/-	6U2	2/-
6A36E	4/-	12K3	14/-	6EF86	10/-	6UC41	8/-
6A7E	6/-	12K7	6/-	6EF81	8/-	6UC81	8/-
6BA6	5/-	12X7	7/-	6F99	5/-	6UF89	5/-
6BE6	5/-	30L6	9/-	6EL84	7/-	6UC81	8/-
6H6	3/-	30Z4	5/-	6EY86	9/-	6UCL82	10/-
6T6	5/-	6A4	2/-	6EZ80	5/-	6EF89	5/-
6J6	5/-	6AF96	8/-	6E240	7/-	6EL41	9/-
6J7G	6/-	6C7G	8/-	6EY81	7/-	6U14	5/-
6K6	5/-	6DL96	8/-	6EY85	7/-	6U85	7/-
6K7G	6/-	6L96	8/-	6C97	7/-	6U9	7/-
6K8G	5/-	6AEC80	6/-	6PC84	5/-	6VR160	7/-
6N7M	5/-	6B91	4/-	6PC80	5/-	6W81	6/-

I.F. TRANSFORMERS 7/6 pair
465 K/c Slog Tuning Miniature Can. 2 x 1 1/2 in.
High Q and good bandwidth. Data Sheets.

NEW ELECTROLYTICS

TUBULAR	TUBULAR	CAN TYPES
1/350V 2/-	50/350V 5/6	18/600V 9/-
2/350 2/3	100/250 2/6	16/450V 5/6
4/450V 2/3	250/25V 3/-	16/800V 12/-
8/450V 2/3	500/12V 3/6	16+16/3500V 7/6
16/450V 3/-	1,000/12V 3/-	50/450V 6/-
32/450V 3/6	5,000/6V 5/-	32+32/3500V 5/-
55/25V 1/8	8+8/450V 3/6	32+32/3500V 5/-
26/50V 2/-	8+16/430V 3/6	50+50/3500V 7/6
50/25V 2/-	16+16/450V 4/6	64+120/3500V 11/6
60/50V 2/-	32+32/3500V 4/6	100+200/275V 3/6

TELESCOPIC CHROME AERIALS. 12 to 38in., 6/6.
TRIPLETERS Bands I, II, III, 12/6. COAX PLUGS, 1/-.
LEAD SOCKETS, 2/-. PANEL SOCKETS, 1/-.
OUTLET BOXES (surface or flush), 4/- ea.
BALANCED TWIN FEEDER Yd. 6d. 50 or 300 ohms.
TWIN SCREENED per yd. 1/-. 80 ohms only.
Wirewound Ext. Speaker Control, 10 Ω 3/-, 25 Ω 8/6.
WIRE-WOUND POTS. 3 WATT. Pre-set Min. T.T. Types. All values to 10 ohms to 25 Ω , 3/- ea. 30 K., 4/- (Carbon 30 K to 2 Meg., 3/-).
WIRE-WOUND 4 WATTS Pots. Long spindle. Value, 50 ohms to 50 K., 8/6; 100 K., 7/6.
PHILIPS TRIMMERS, 0-10 p.f., 3-30 p.f., 1/-.
TRIMMERS, Ceramic, 30, 60, 70 p.f., 9/6; 100 p.f., 150 p.f., 1/8; 250 p.f., 1/6; 500 p.f., 750 p.f., 1/6. P.T. etc. TRIMMER, 1000 p.f., with knob, 2/-.
RESISTORS. Preferred values, 10 ohms to 10 meg. $\frac{1}{2}$ W. 4 W., 1 W., 4d.; 1 1/2 W., 8d.; 2 W., 1/-.
High Stability. 4 W., 1 1/2 W., 2 W., Preferred values 10 Ω to 10 meg. Ditto 5% 10 Ω to 22 meg. 2d.
BRIMISTORS CZ1, 3/6; CZ2, 2/6; CZ3, 1/6.
5 watt } WIRE-WOUND RESISTORS { 1/3
10 watt } 10 ohms-10,000 ohms { 2/-
15 watt } 10 ohms-10,000 ohms { 2/-
12.5 K to 25 K 10 W. 3/-
Toggle Switches, s.p., 2/-; d.p., 3/6.
d.p.d.t. 4/-; Min. Slide d.p.d.t. 1/6.

Volume Controls 80 ohm COAX
Linear or Log Tracks Rem-aid spaced 1/2 in.
Long spindles. Midget 40 yds. 17/8
5 K ohms to 2 Meg. 60 yds. 25/- 6d.yd.
L.S., 3/- D.P., 4/6
Ideal 625 lines
Low loss 625
100ft. 500 Mef. 1/3 yd.

MAINS TRANSFORMER 200/250 v. A.C.

Postage 2/- each transformer
STANDARD, 250-0-250 80mA. 6.3 v. 3.5 a. tapped 4 v. 4 a. Recliter 6.3 v. 1 a., 5 v. 2 a. or 4 v. 2 a., 25/6, ditto 350-0-350 29/6
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 10/8
MIDGET, 220 v. 45 mA. 6.3 v. 2 a. 15/6
SMALL, 250-0-250, 45 mA. 6.3 v. 2 a. 17/6
STD. 250-0-250, 65 mA. 6.3 v. 3.5 a. 17/6
HEATER TRANS., 6.3 v. 1 1/2 a. 7/8
Ditto, tapped 1.4, 2, 3, 4, 5, 6.3 v. 1/8
Ditto, sec. 6.3 v. 4 amp. 8/6
GENERAL PURPOSE LOW VOLTAGE, 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/6
AUTO TRANSFORMERS, 150 w. 2/8
0, 115, 200, 230, 250 v. 500 w. 1/- 32/6
MULLARD '510' Mains Transformer 33/6
MAINS POWER PACKS. Ready built with Transformers, Rectifiers, Condensers, providing H.T. and L.T. outputs.
200 v. 20 mA. D.C. 6.3 v. 1 a. A.C. 25/8
220 v. 50 mA. D.C. 6.3 v. 2 a. 35/6
220 v. 80 mA. D.C. 6.3 v. 3.5 a. tapped 4 v. 45/6
and 3 v. 1 a. tapped 5 v., 4 v., 2 a.

INTERVALVE TRANSFORMERS. 3:1 or 5:1, 9:1, O.P. TRANSFORMERS. Heavy Duty, 6/8. Multi-ratio, 7/8. Multiratio heavy duty push-pull, 10 v. 15/8. Battery, 4/6. sub. min. DL86, 3/4, etc., 5/8. 10 v. O.P. matching type, 3, 7, 15, 12, 12/8. L.F. CHOKES. 15/101, 60/65 mA. 5/-; 10H. 85 mA. 10/8; 10H. 150 mA. 14/-.

C.R.T. BOOSTER TRANSFORMERS for heater cathode short circuit or tubes with falling emission. Full instructions supplied, mains input. Type A optional 25% and 50% boost 2v. or 4v. or 6.3v. or 10.8v. or 12.5v. State Voltage required. PRICE 10/6.

TINNED COPPER WIRE 16 to 22 swg., 1lb., 3/6
ENAMEL COPPER WIRE 16-22, 2/8; 24-30, 3/6; 30-40, 4/6; D.C.C. 28, 34, 36 swg., 2oz., 3/8
FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 6 or 12 v., 1 1/2 amp., 8/9; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 14 amps., 15/8; 2 amp., 17/8; 4 amp., 22/8. Circuit included.
4 AMP CAR BATTERY CHARGER with ammeter, Leads, Fuse case, etc., for 6 v. or 12 v. 59/8.


BOOKS list S.A.E.

Boys' Book of Crystals, S.A.E. 2/6
"W.W." Radio Valve Data 7/6
High Fidelity Speaker Enclosure 5/- Valve and TV Tube Equivalents . . . 9/6
TV Fault Finding 5/-
Mullard Amplifier Manual 8/6
Radio Valve Guide, Books 1, 2, 3, 4 or 5 5/- each
Practical Radio Inside Out 3/6
Master Colour Code Chart 1/6
"Transformer Controlled Models" 7/6
International Radio Stations . . . 2/6

4 TRANSISTOR PUSH-PULL

Size 3 x 1 1/2 x 1/2 in. AUDIO AMPLIFIER
A ready built miniature push-pull amplifier with Driver and output transformers, 4 transistors. Ideal for use with record players, intercoms, BABY ALARMS, etc. Complete with full Price 47/6 instructions and circuit. 9v. Batt. 23.2V. INCH SPEAKER 15/6

1964 RADIOGRAM PHISSIS

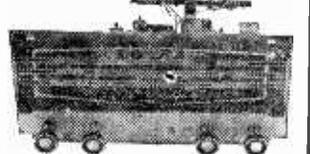

THREE WAVEBANDS FIVE VALVES
S.W. 16 in - 50 m. LATEST MULLARD, etc. M.W. 200 m - 650 m. EC181, EF89, EB81, L.W. 800 m - 2,000 m. EL34, EZ20
A.C. 200/250 12-month guarantee
Ferrite Aerial A.C.V. 3 ohm output, 3 watta. Tape Sockets, Glass dial, horizontal winding size 13in. x 7in. Aligned and calibrated, isolated Chassis size 13 1/2 in. x 7 in. high x 5 1/2 in. deep. £9.15.6 Carr. & Ins. 4/6.

Post 1/- (unless otherwise stated)
C.O.D. 2/- extra. Full list 2/-.

RADIO COMPONENT
Some clients' letters posted 25/26th August are missing, please write.

BAKERS 'Selhurst' LOUDSPEAKERS



THE CONNOISSEUR'S CHOICE

BAKERS' 8in. JUNIOR SPECIAL. 8w. 17,000 lines. 5 kns. Foam Suspension 40-20,000 c.p.s.

BAKERS 12in. STALWART HEAVY DUTY 15w. 5 kns. 3 or 15 ohm voice coils. Unlimited Applications. Response 45 to 13,000 cps. Magnet 12,000 lines. Quality unbeatable.

BAKERS 12in. STANDARD HEAVY DUTY 20w. 7 kns. More powerful magnet 14,000 lines special suspension, 40-14,500 cps. Recommended wherever a high standard of reproduction is desired.

BAKERS 12in. BASS HEAVY DUTY 25w. 12 Fns. New 1964 high power model. Aluminium coil former with magnetic damping 25-15,000 cps. Ideal for all electric guitars.

BAKERS 16in. AUDITORIUM MODEL 35w. 18 kns. Improved magnet alomax with heavy plated assembly. weight 8lbs., 17,000 lines. 90-12,000 cps. Solid heat proofed Parolin Coil Former. Ideal for all Electric Guitars.

LOUDSPEAKERS P.M. 3 OHM.

2 1/2, 3, 4, 5in. 7 x 4in., 15/6; 8in. Kola, 16/6; 8in. Selhurst, 17/6; 9 x 6in., 8 x 6in., 21/-; 10 x 6in., 22/6; 10in. Kola 30/-; 12in. R.A., 30/-; EM1, Double Cone Ceramic magnet 10 v. 13 x 3in., 45/-; Horn Tweeter, 29/6. STENTORIAN HF1012, 10in., 3 to 15 ohms 10 v., 92/-; 8in. HF1012, 7 1/2" - Transducer (X:2000, 33/-). EXTENSION SPEAKER CABINET. 6in., 15/6; 6 1/2in., 18/6; 8in., 19/6; 10in., 29/6; 12in., 60/-.
TWIN GANG TUNING CONDENSERS. 365 pF. 1in. x 1 1/2 in. x 1 1/2 in., 10/-; 500 pF Standard with trimmers 8/-; 7/6; 7/6 with trimmers, 9/- 500 pF slow motion tuning standard, 9/-, Transistor gang 208+176 pF with trimmers, 10/6. SMALL 3 gang 500 pF, 17/-, SINGLE 365 pF, 7/6. SINGLE 10 pF, 25 pF, 50 pF, 75 pF, 100 pF, 150 pF, 5/6. Solid dielectric 100, 500, 500 pF, 3/6.
CONDENSERS. 0.001 mid, 7 kv. T.C.C., 5/8; 20 kv. 9/8; 0.1 mfd. 1 kv. 9/8; Tubular 500 v. 0.001 to 0.05 mfd. 9d.; 0.1, 1/-; 0.25, 1/8; 0.5/350V, 1/8; 0.1/350V, 9/8; 0.01/2,000v., 0.1/1,000v., 1/8; 0.1mfd., 2,000 volts, 3/6.
CERAMIC COND. 500 v. 1 pF to 0.01 mfd. 9d. SILVER MICA CONDENSERS. 10% 5 pF to 500 pF 4d.; 600 pF to 3,000 pF, 1/-, Close tolerance (-1 pF) 2.2 pF to 47 pF, 1/1-. Ditto 1% to 50 pF to 815 pF, 1/-, 1,000 pF to 5,000 pF, 1/8.

FERGUSON QUALITY AMPLIFIER 4 watts.

41 x 5 x 4 in. Mullard Valves. Mains Transf., 200 v. Volume and tone control. Sensitivity 250 mv. Response 25 to 20,000 cps. Price 49/8 ea. or 2 units matched for Stereo, 89/6.

WAVECHANGE SWITCHES

8 P. 4-way 2 water long spindle 6/8
2 P. 2-way or 2 P. 3-way long spindle . . . 3/8
4 P. 2-way or 4 P. 3-way long spindle . . . 3/8
3 P. 4-way or 1 P. 12-way long spindle . . . 3/8
Wavechange "MAKITS". Wafers available: 1 p. 12 way, 2 p. 6 way, 3 p. 4 way, 4 p. 2 way, 5 p. 2 way, 1 waffer switch, 3/8; 2 waffer switch, 12/8; 3 waffer switch, 16/- additional wafers up to 12, 3/6 each extra. Valveholders. EA50, 6d. B12A, CRT, 1/3. ENGL. and Amer. 4, 5 and 7 pin, 1/-.
MULLEND MZodia and int. oct., 6/1; 8/7G, BEA, 88C, BA9, 9d. Ceramic EF80, B7C, 58A, int. oct., 1/-; B7G, B9A cans 1/- each. Valve plugs B7G, BA9, int. oct., 2/3.

HIGH GAIN TV PRE-AMPLIFIERS

B.B.C. Channel 1 to 5. Gain 18dB, ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PC94A valve if preferred). Coils only 9/6.
BAND 11 I.T.A. - Same prices.
Tunable channels to 13. Gain 17dB. Circuit and coils only, 9/6. Chassis 4/9.

THE ORIGINAL
OPEN ALL DAY
(Wed. 1 p.m.)

THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 200/250 v. A.C.



35/-

Leaflet S.A.E.

PLASTIC RECORDING TAPE

Double Play	7in. reel, 2,400ft. 42/-	Spare Plastic Reels
	5in. reel, 1,200ft. 25/-	
Long Play	7in. reel, 1,800ft. 22/6	3in. 1/6
	5in. reel, 1,200ft. 17/6	4in. 2/-
	5in. reel, 900ft. 15/6	5in. 2/5
Standard	7in. reel, 1,200ft. 17/6	7in. 2/6
	5in. reel, 600ft. 11/6	5in. 2/6

"FANISPLICE" Tape Splicer 5/-
Leader tape 4/6; Splicing tape 3/-

CRYSTAL SET BOOKLET 1/-
CRYSTAL DIODE G.E.C. 2/-, GEX34 3/-, OA81 3/-,
HIGH RES. PIPNES, 4,000 ohms, 12/6, 2,000 ohms,
12/6. MOVING COIL PHONES, 100 ohms, 10/-,
SWITCH CLEANER. Fluid squirt opert, 4/6 tin.

"6+1" TRANSISTOR RADIO

First class components to make a 6 transistor 2 waveband superhet chassis. Ideal for portable or table radio. All parts including BVA transistors, ferrite aerial, with car aerial coil, printed circuit, 8 1/2 in. x 2 1/2 in., but EXCLUDING Speaker and cabinet.
Speakers, 3ohms, 6 x 4in., 2 1/2-5in., 17/8; 3 1/2 in., 15/6.

£4.50

BULGIN PLUGS AND SOCKETS. Non-reversible P7, 2-pin, 4/3; P7, 2-pin, 4/3; P19, 6-pin, 6/6. JACKS. English open circuits, 2/6. Closed circuit, 4/8. Grundig type, 3-pin, 1/3. Grundig lead jack, 3/6. JACK PLUGS. English, 3/4; Screened, 4/-; Grundig 3-pin, 3/8; Phone Plugs, 1/-; Sockets, 6d. ALADDIN FORMERS and cores, 4in., 8d.; 1/2 in., 10d. 0.3in. Former, 59/7 or 3 cans 47/1 or 2 1/2 in. sq. x 2 1/2 in., or 1/2 in. sq. x 1 1/2 in. 2/- with cores. SLOW MOTION DRIVERS. 6:1, 4/3; 36:1, 10/6. BOLON IRON, 25W, 200V or 230V, 24/-. POKKET SIZE, 2 1/2 x 4 1/2 in. One resistor to change. Full instructions supplied. Battery 8/6 extra. Details Free.

465 kc/s. SIGNAL GENERATORS. Price 10/6, ready made with valve ISS. POKKET SIZE, 2 1/2 x 4 1/2 in. One resistor to change. Full instructions supplied. Battery 8/6 extra. Details Free.

Coils Weirite "P" Type, 4/- each. Osamor Midget "Q" type, ad. dust core, from 4/- each. All ranges. List S.A.E. Kepanco DRIS L. and Med. T.R.F. with reaction, 4/6. Med. wave D.R. 3/- Ferrite Aerials, M., 8/9; M. and L., 12/6. Osamor Ferrite Rod Aerials, L. and M. for transistor circuits, 10/- each. Ferrite Rod, 2 x 1 1/2 in., 6 x 1/2 in., 6 x 1/2 in., 3/- H.F. Chokes, 2/8. Osamor QCI, 6/9. T.R.F. Coils, A/HF, 7/- pair; HAX, 3/6. Screwdriver, 5/9. 6d. Test Prods. 2/9 ea. Neoside Trimming Tool, 1/9. Non-Mains Tester, screwdriver, 5/-. Multicore Solder, 4d. yd. Dispenser, 2/6.

Blank Aluminium Chassis, 18 s.w.g. 4 sides, riveted corners, lattice fixing holes, 2 1/2 in. sides, 7 x 4 in., 6 x 7 1/2 in., 5/9; 1 1/2 x 7 in., 6/9; 1 3/8 x 9 in., 8/6; 1 1/2 x 11 in., 10/6; 1 1/2 x 14 in., 12/6. Aluminium Panels, 18 s.w.g., 12 x 12 in., 4/6; 14 x 9 in., 4/-; 12 x 8 in., 3/-; 10 x 7 in., 2/6; 8 x 6 in., 2/-; 6 x 4 in., 1/6.

MARTIN TAPE PRE-AMPLIFIERS (PLAY-BACK THROUGH YOUR OWN AMPLIFIER)
For Collaro 2 Track Decks 8 gus. COMPLETE RECORDING & PLAY-BACK AMPLIFIERS
For 2 Track Collaro £11.11.0
TAPE DECKS
Collaro Studio 2 Track £10.15.0
BS1 T12 2 Track Tape Deck £7.5.0
Collaro Record/Erase Heads, 1 track 35/- pair

MAINS DROPPERS. Midget adjustable slide 0.5A, 1,000 ohms, 6/-; 0.2A, 1,200 ohms, 6/-; 0.15A, 1,500 ohms, 6/-; 0.1A, 2,000 ohms, 6/-.
LINE CORD. 3-way 100 ohms ft., 1/- ft.
MIKE TRANSFORMERS. 50-1, 3/6.
P.V.C. Covered Wire, single or stranded, 2d. yd. Sleeving, 1 or 2 mm., 2d.; 4 mm., 3d.; 6 mm., 5d. yd.

B.T.H. TAPE MOTORS. 115 v. A.C., 28 w. 12/6 ea. or pair for 230 v., (in series), 12/6.

SPEAKER-PRET. Gold Maroon or Green Cloth 17 x 25in., 5/-; 25 x 35in., 10/-; Tygan, various colours 52in. wide from 10/- ft.; 26in. wide from 5/- ft. Samples 1/-. Expanded Metal, Gold, 12 x 12in., 6/-. Panel mounting fuse holder, 2/-. Fuses 1 1/2 in., 60mA, 5A, 6d. Insulated side cutters, 3/6. Rib Strippers, 3/6

RADIO AND TELEVISION SPARES

All leading makes, volume controls, etc., line output transformers, etc.
B. V. A. valves (current and obsolete types). Send S.A.E. for quotation.

WEYRAD P50

COILS AND TRANSFORMERS FOR 2-WAVE TRANSISTOR SUPERHET
Long and Medium aerial—RA2W 8in. rod 208 pF tuning, with car aerial coil 12/6
Osc. Coil P50/LAC 178 pF tuning 5/4
1st and 2nd I.F. P50/2CC 470 kc/s 5/7 each
3rd I.F. P50/3CC 6/-, Spare Cores, 6d.
Driver Transformer—LFD74 9/6
Wavechange Slide Switch d.p.d.t. 3/6
Printed Circuit—PCAL, Size 2 1/2 x 8 1/2 in. Ready drilled and printed 9/6
Volume Control, 5K-DP 4/6
35 ohm Speakers, 3 1/2 in., 15/6; 5 in., 17/6; 6 x 4 in., 21/-
J.B. Tuning Gang with trimmers 10/6
Constructor's Booklet 2/-
3 ohm P.P. Trans. O.P.T.1 10/6

NEW MULLARD TRANSISTORS
OC71 6/-, OC72 7/6, OC81D 7/6, OC81 7/6, OC74 8/-, OC45 8/-, OC171 10/6, AF117 9/6.
Sub Miniature Condensers, 0.1 mFd, 10V, 1/3.1, 2, 4, 5, 6, 16, 25, 30, 50, 100 mFd, 15 volt, 2/6 ea. Transistor Holders, 1/6.


SINCLAIR "SLIMLINE" RADIO
Med. wave kit, 2 transistors, 2 diodes, earphone, ferrite aerial, Cabinet 3 x 11 x 11 in., 49/6. No aerial required.

Transistor 4 Channel Mixer with 4 separate input-output controls 59/6.

"THE POWER MITE" 45/- 200/250V.

PM9 Mains Unit 9 volt for Transistor Radios. Same size as P.P.9 Miniature PP3 model. 19/6

ADASTRA 3-3 AMPLIFIER 3 WATTS

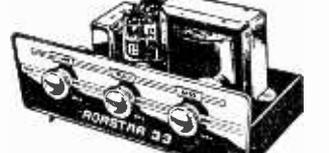

A.C. 200-250V. Valves ECL86 and EZ80. 3 ohms output. Controls: bass, treble and volume. Separate front panel with de luxe finish, aerial, mains transformer. Enamelled chassis 6 in. x 5 in. x 3 in. Price £4.19.6. Details S.A.E.
"Performs agreeably well" (The Gramophone)

BUILD YOUR OWN RECORD PLAYER FROM £9.19.6

AND SAVE POUNDS!!



4 Speed Autochanger or Single Player units with Brand New 2-tone de Luxe Cabinets 17 x 15 x 8 in. Strong handle, gilt finish clips and knobs. Used by Famous Make for 20 kns. models. Ready cut out motor board 14 x 13 in. Front baffle with 7 x 4 in. high flux loudspeaker and 3 watt 2 valve U385, UCL2 amplifier built on metal chassis 12 x 3 x 2 1/2 in. Quality 3 ohm output transformer, low hum level circuit. Volume and Tone controls. 3-core safety mains lead. All items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to join! 12-month written guarantee. Available separately or package deals as below.

AUTOCHANGE KITS COMPLETE (as above)

E.S.R. Monarch	£11.10.0 P.P. 5/6
Garrard Autolium	£12.18.0 P.P. 5/6
SINGLE PLAYER KITS COMPLETE (as above)	
E.M.I. Junior	£9.19.6 P.P. 5/6
Garrard SP10	£11.5.0 P.P. 5/6

OR SEPARATELY

Cabinet with board 14 x 13 in. cut out to your choice £3.9.6 P.P. 3/6
Amplifier with 7 x 4 in. speaker £3.17.6 P.P. 2/6
AUTOCHANGERS

E.S.R. UA14	£5.19.6 P.P. 4/6
Garrard UA15 Slimline	£6.17.6 P.P. 4/6
Garrard Autolium	£6.17.6 P.P. 4/6

SINGLE PLAYERS

Garrard SP10	£5.5.0 P.P. 4/6
E.M.I. auto stop/start	£5.5.0 P.P. 4/6
E.M.I. Junior	£3.7.6 P.P. 3/6

TRANSCRIPTION UNITS

Garrard 4EF	£15.15.0 P.P. 5/-
Philips AG1016	£12.5.0 P.P. 5/-
Garrard AT6	£10.10.0 P.P. 5/-

BARGAIN XTAL PICK-UP ARM
Complete with ACOS LP-78 Turnover Head, 20/-

Replacement sapphire stylus 5/-, diamond 15/-
Mono ACOS Xials 15/-; Stereo Ronette 30/-

BARGAIN SINGLE PLAYER KIT 200/250 v. A.C.
(less cabinet) **£5.15.0**
Post 5/-

With 2-stage Amplifier; 3 watt; 2 valve, UCL85, U385. High-fux 5in. speaker; 4-speed E.M.I. Turntable, 16, 33, 45, 78 r.p.m.; Crystal Pick-up for LP/ST, Records, 7in. 10in., 12in.; Cut out Mounting Boards 12 1/2 x 9 1/2 in.

ARDENTE TRANSISTOR TRANSFORMERS

DB035, 7.5 CT.1 Push-pull to 3 ohms output	11/-
DB034 1.5:1, C.T. Push-pull Driver	11/-
DB058, 11.6:1 Output to 3 ohms, etc.	11/-
DB89, 4.6:1 Driver, 1in. x 1in. x 1in.	11/-
D240, 8.5:1 Driver, 1in. x 1in. x 1in.	11/6

ARDENTE TRANSISTOR VOLUME CONTROLS

VC145, 5K with switch disc, 3in.	5/8
SUB-MIN. EARPIECE Xial or magnet	7/6
SUB-MIN. JACK AND PLUG 2.5 or 3.6 mm. 3/6 pair	

MINIATURE PANEL METERS
Size 1 1/2 in. sq. Precision jewelled bearings. 2% accuracy, silvered dials, black numerals and fine pointers, zero adjustment screw on front of meter.

1 mA .. 27/6	50 uA .. 39/6
5 mA .. 27/6	500 uA .. 32/6
300V .. 27/6	"SI" Meter 35/-

MOVING COIL MULTIMETER TK 20a
0-1000 v. A.C./D.C., ohms 0-100k, etc., 49/6
0-150 mA pocket size with 2in. scale

CRYSTAL MIKE INSERTS, 6/8
High output, Size 1 1/2 in. dia. x 1 in. 8/6
ACOS MIC. insert, 1 1/2 in. dia. x 1 in. 8/6

ACOS 39-1 DELUXE STICK MIKE 35/-
BEST QUALITY STICK MIKE .. 25/-
TELEPHONE TAPE MIKE .. 10/6
GUITAR CONTACT MIKE .. 15/6
MOVING COIL MIKE, high or low impedance, 80/- FLOOR STAND, 57/-
TANNOY Carbon Hand Mike .. 7/8

COMPONENT SHOP 337 WHITEHORSE ROAD WEST CROYDON
Telephone: THO 1665
Export welcome. Send remittance, and extra postage, no C.O.D.

SPECIALISTS

Buses 133 or 68 pass door. S.B.R. Station, Selhurst

ELECTRONICS

**LEARN - THE
PRACTICAL
WAY . . .**

your career . . .
hobby . . .
own business . . . ?

The demands for good Electronic Engineers is increasing almost daily throughout the world. Electronics is now the most rapidly expanding of all industries with its applications reaching into almost every sphere of human activity. If you are looking for a new career with new opportunities, then now is the time to choose—Electronics. If you are already employed in this field—then now is the moment to seek high qualifications to secure the top jobs which are waiting to be filled. Most of all, the great potential of electronic development means unlimited scope for the future and will ensure a secure occupation for you—unlikely to be affected by possible future recessions in other industries.

The British National Radio School has had 25 years' experience of HOME STUDY coaching for students wishing to master the fascinating subjects of Electronics—whether the object be career or as a hobby or new interest. The School is entirely independent and specialises ONLY in the teaching of electronic subjects. It employs only fully qualified staff to conduct and supervise each individual course taken by a student and it is this close and personal contact between Tutor and Student which we believe makes possible the successful completion of a course of study.


A special feature of our system is that all courses start right from the beginning and no previous knowledge or experience is necessary or expected. Training is carried out in easy step-by-step stages using the most modern methods of tuition. The great advantage of the home study method is that it provides a complete self-contained course giving everything needed for the subject concerned and enabling work to be done in the comfort of one's own home and over any period of time desired.

EXAMINATION COURSES

- CITY & GUILDS TELECOM. TECHNICIANS CERT.
- CITY & GUILDS FULL TECHNOLOGICAL CERT.
- A.M.Brit.I.R.E. EXAMINATION.
- RADIO AMATEURS LICENCE EXAMINATION.
- P.M.G. CERTIFICATES FOR RADIO OPERATORS.
- R.T.E.B. SERVICING CERTIFICATES.

OTHER COURSES

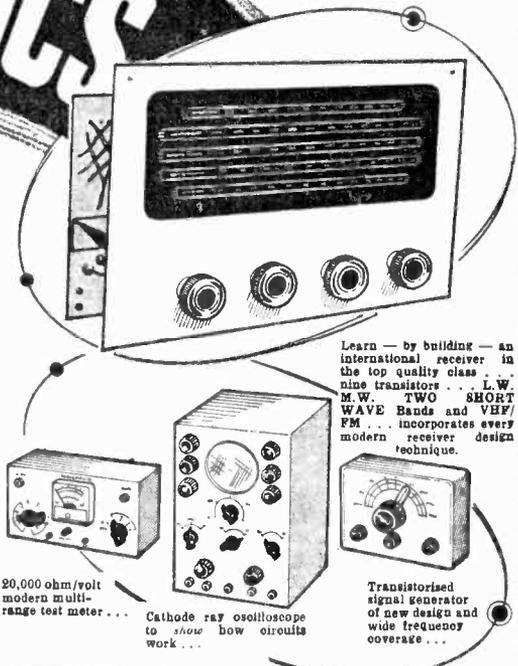- MATHEMATICS
- TELEVISION
- TRANSISTORS
- SERVO-MECHANISMS
- COMPUTERS
- RADAR & NAVIGATIONAL AIDS



Learn — by building — an international receiver in the top quality class . . . nine transistors . . . L.W. WAVE Bands and VHF/FM . . . incorporates every modern receiver design technique.

20,000 ohm/volt modern multi-range test meter . . .

Cathode ray oscilloscope to show how circuits work . . .

Transistorised signal generator of new design and wide frequency coverage . . .



Complete picture way library of theory books and practical manuals
NO MATHEMATICS!

BUILD AND EXPERIMENT WITH ALL THE ABOVE—AS—YOU—LEARN . . .

This is a new complete experimental course comprising a mixture of theory and practical work using a very full range of electronic components and apparatus. Starting right from the beginning—or at a later stage if needed—the course enables the student to build up all the basic electronic circuits—amplifier; oscillator; rectifier; detector; etc.—and finally to the design, construction, testing and servicing of a latest design fully transistorised receiver using nine transistors and covering long and medium wave and TWO SHORT WAVEBANDS plus VHF/FM reception. It is of real luxury quality throughout—operates from a 9v. battery and can be used anywhere in the world. Every present-day technique in circuitry is covered and the course also includes multi-range test meter; signal generator and oscilloscope. By the end of the course the student will be able to deal with any type of servicing work with confidence and will also have a very useful workshop of equipment. Nearly 100 interesting and absorbing EXPERIMENTS are carried out during this comprehensive course enabling anyone to gain full mastery of electronics.

FREE

POST NOW

TO: BRITISH NATIONAL RADIO SCHOOL, RADIO HOUSE, READING, BERKS

Please send me your free Brochure, giving details of your Courses, without any obligation, to:—

NAME.....

ADDRESS.....

I am interested in.....

} Block Caps Please

courses above PW 11/64

(We do not employ representatives)

British National Radio School

Practical Wireless

Vol. XL No. 693 NOVEMBER, 1964

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes Ltd., Tower House
Southampton Street, W.C.2

© George Newnes Ltd., 1964

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London.

SUBSCRIPTION RATES

including postage for one year
To any part of the world £1.9.0

Contents

Editorial	621
Round the World of Wireless	622
The Autocrat	624
Preparing for the R.A.E. ...	627
A Midget Antenna	629
Twin Triode Two	632
TV & Radio Show	636
A T.R.F. Transistor Portable	643
On the Short Waves	646
Dual Calibration Standard ...	648
The "Ten-Five"	652
Understanding Semiconductors	662
Practically Wireless	669
The "Spectreuphon"	670
Electronic Timer	678
Club News	686
Letters to the Editor	688

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Times have Changed!

THE problem of pirates has been with us since radio began. In this context we are not talking of floating pop-music stations but of illegal amateurs operating in (or out of) the amateur bands.

In pre-war days, a prospective radio amateur had first to obtain from the GPO an "Artificial Aerial" licence which permitted him to build and experiment with equipment to be used only under dummy load conditions.

Log books and records of experiments, together with an inspection of the actual equipment, formed the basis for assessing the ability of the applicant to put his station on the air and receive his full licence.

Occasionally an impatient AA licence holder would succumb to temptation and put some r.f. out. Even so, a pirate of this nature had at least built his own equipment, had a working knowledge of amateur radio practice and was in most cases a qualified amateur operator anticipating the issue of his full "ticket".

Today's pirates are largely in a different category. Most seem to operate war surplus units or imported American and Japanese walkie-talkies. Most have little or no knowledge of ham radio procedure, have only a rudimentary knowledge of how the equipment works, and often do not even operate in the authorised bands.

Perhaps the root cause of this new situation is that nowadays *anyone* can buy, without question, transmitting equipment from a radio dealer. Advocates of "freedom" see nothing wrong in this; they urge that *anyone* who wants to go on the air should be allowed to do so. They think it an impertinence that an enthusiast should have to pass a simple technical test when all he wants to do is to operate a transmitter for his own amusement.

Such theories are shortsighted and irresponsible. All right, we'll abolish the radio examination—and with it examinations for doctors, opticians, dentists, lawyers! We'd like to see a "free air" fan having his molars drilled by an unqualified dentist.


The allusion, of course, is undoubtedly shaky—but it serves to illustrate a principle. For there is much more to it than just switching on a transmitter and exchanging small talk with a pal. Amateur frequency allocations are extremely small and vastly overcrowded and these conditions demand efficient equipment and intelligent operating.

Amateur radio cannot be regarded purely as a personal hobby, for thousands of other people are involved. Other amateurs, of course. The general public (how would a modern pirate deal with TVI problems?). And those anarchists who feel they do not even have to consider authorised amateur bands can involve any of the other services legally using the restricted airways. Uncontrolled freedom can only lead to chaos and confusion.

There are many angles to examine, but perhaps the most important is that often put forward as the platform of the "free-air" devotees. *Times have changed!* Indeed they have—and next month we will see just how.

In the meantime, we hope prospective pirates will turn to page 627 this issue...

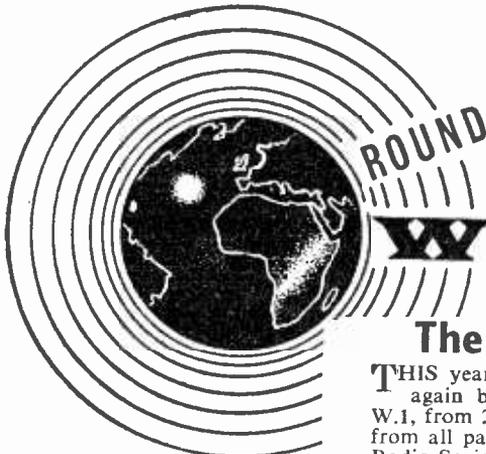Our next issue dated December will be published on November 6th



**NEWS AT HOME
AND ABROAD**

ROUND THE WORLD of WIRELESS

The 1964 R.S.G.B. Exhibition

THIS year's International Radio Communications Exhibition will again be held at the Seymour Hall, Seymour Place, London, W.1, from 28th to 31st of October, and once again radio enthusiasts from all parts of the country will visit this, the annual show of the Radio Society of Great Britain.

Manufacturers — British, American and Japanese—will be displaying the very latest in

receivers and transmitters for the amateur, including a transistorised all-band communications receiver. Kit and aerial manufacturers, technical publishers, etc., will all be exhibiting as will the Royal Navy, Royal Air Force, Army and General Post Office with their newest communications equipment.

The 1964 Radio Show



Here is a view of this year's Radio Show at Earls Court, London. Attendance this year was down on the last Show, held in 1962. A Report on the show appears on page 636.

The 1964 Silver Plaques for the most outstanding home built piece of equipment and manufacturers' new equipment, head the list of awards which will be presented during the show.

The R.S.G.B. will this year operate a new home-constructed transmitter on 435Mc/s, 144Mc/s and 3.5Mc/s. A demonstration of r.t.t.y. will also be on the air on 3.5Mc/s, 80m and 145Mc/s, 2m.

The official opening will be performed at noon on 28th October, by E. D. Whitehead, M.B.E., Director of Electrical Inspection at the Ministry of Aviation, and the Exhibition will be open daily from 10 a.m. to 9 p.m., admission 3s.

MICROWAVE TELEPHONE NETWORK FOR PORTUGAL

A HIGH capacity microwave relay network for Portugal that can handle as many as 960 telephone conversations simultaneously, is to be supplied to the government of Portugal by the Raytheon Company of America.

The 140 mile network will consist of seven stations and will span northern Portugal with terminals for the main line at Porto

and Nogueira. At Nogueira, the system will interconnect with a scatter communications system linking Portugal to France and the European Telecommunication network. Three other cities — Penafiel, Vila Real and Braganca—will be linked into the network via feeder spurs.

The main line will consist of Raytheon's RM-1C microwave

relays, as will the Vila Real spur, because of its heavy traffic pattern. The two other spurs will feature 600 channel microwave relays built by Raytheon's Italian affiliate, Selenia S.p.A.

To provide maintenance centres with a complete picture of the system's operating condition, the network will incorporate automatic fault-reporting systems.

NEW INSTRUMENT CHECKS EQUIPMENT FOR SPACE

AN instrument which will perform fault-revealing checks on the electronic equipment of future space vehicles launched by the National Aeronautical and Space Administration of the U.S.A., is being developed by the Raytheon Company of Massachusetts.

The equipment consists of a fast scanning infra-red microscope that can forecast possible failure of electronic space devices without long, complex tests.

The microscope, which has been termed a Performance Analyzer, will sense minute amounts of infra-red radiation and from this will indicate the reliability and probable life expectancy of an integrated circuit or semiconductor device. Potential electrical failure can be pin-pointed by this equipment, not only in conventional parts but in the micro-circuits and thin-film assemblies which are featuring more and more in space vehicle electronics. So tiny are some of these integrated circuits, that they fre-

quently contain faults which cannot be detected by conventional testing methods.

In operation the analyser relies on the fact that virtually all built-in causes of failure result in abnormal thermal behaviour when electrically activated. The

infra-red detector measures the heat dissipated when a component or circuit is operating. Comparing this with a standard, an engineer can determine performance and discover the presence of hidden defects that could cause later failures.

Eire Telephone Expansion

TO expand the trunk telephone network in Eire, orders worth £145,000 have been placed with AEI Telecommunications Transmission Department for terminal equipment capable of handling 300 separate conversations, for transmission over small diameter coaxial cables.

Four new links are to be established: from Dublin to An Uaimh and Ceanannus Mor (24 high quality speech circuits), Limerick to Tipperary (96 circuits), Cork to Youghal and Cork to Bandon (both with 60 circuits).

In using conventional small diameter coaxial cable, AEI will be taking advantage of the low cost compared with conventional telephone cable networks of similar capacity, and better speech quality, since the incorporation of transistorised repeaters has overcome the problem of housing which the considerably larger counter-part valve equipment presented before.

With transistors however, the size of amplifiers that AEI will use, along with their power consumption, has been considerably reduced and large numbers of repeaters will take their power from current fed along the cable.

Radar Developments on Show at Farnborough

TWO new Marconi developments in radar were shown publicly at the recent Farnborough air show. One was a new high power, long range meteorological radar system which can track and pin-point storms and rain producing clouds within an area of 125,000 miles, with extreme accuracy and reliability.

Named RAINBOW, the system has been designed to provide


an inexpensive equipment suitable for use at airports, where it can provide first hand meteorological information to the air traffic control centre.

RAINBOW's 70kW p.e.p. high power transmitter and receiver are both housed in a 12ft. high conical shaped aluminium tower on top of which is mounted a 6ft. diameter parabolic dish aerial

The other Marconi innovation seen on their Farnborough stand,

was the production model of a new radar display which can be viewed in bright daylight.

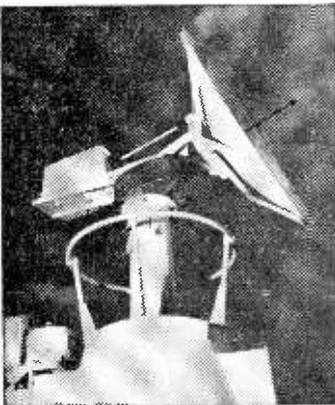A considerable step forward is claimed for this new development, which is based on the use of a direct view storage tube. The tube, which produces a very bright radar picture using a high efficiency short persistence phosphor, contains a storage element to introduce persistence to the picture.



On the left is the transmitter and receiver and dish aerial of Marconi's new RAINBOW meteorological radar system. The equipment in the photograph shown on the right is Marconi's daylight radar display in use at London Airport.

PRESENTED FREE
WITH
"PRACTICAL WIRELESS"
NOVEMBER 1964

Practical Wireless

"AUTOCRAT" CAR RADIO

PRICE
5/-

PUBLISHED BY GEO. NEWNES LTD., TOWER HOUSE, SOUTHAMPTON STREET, LONDON W.C.2.

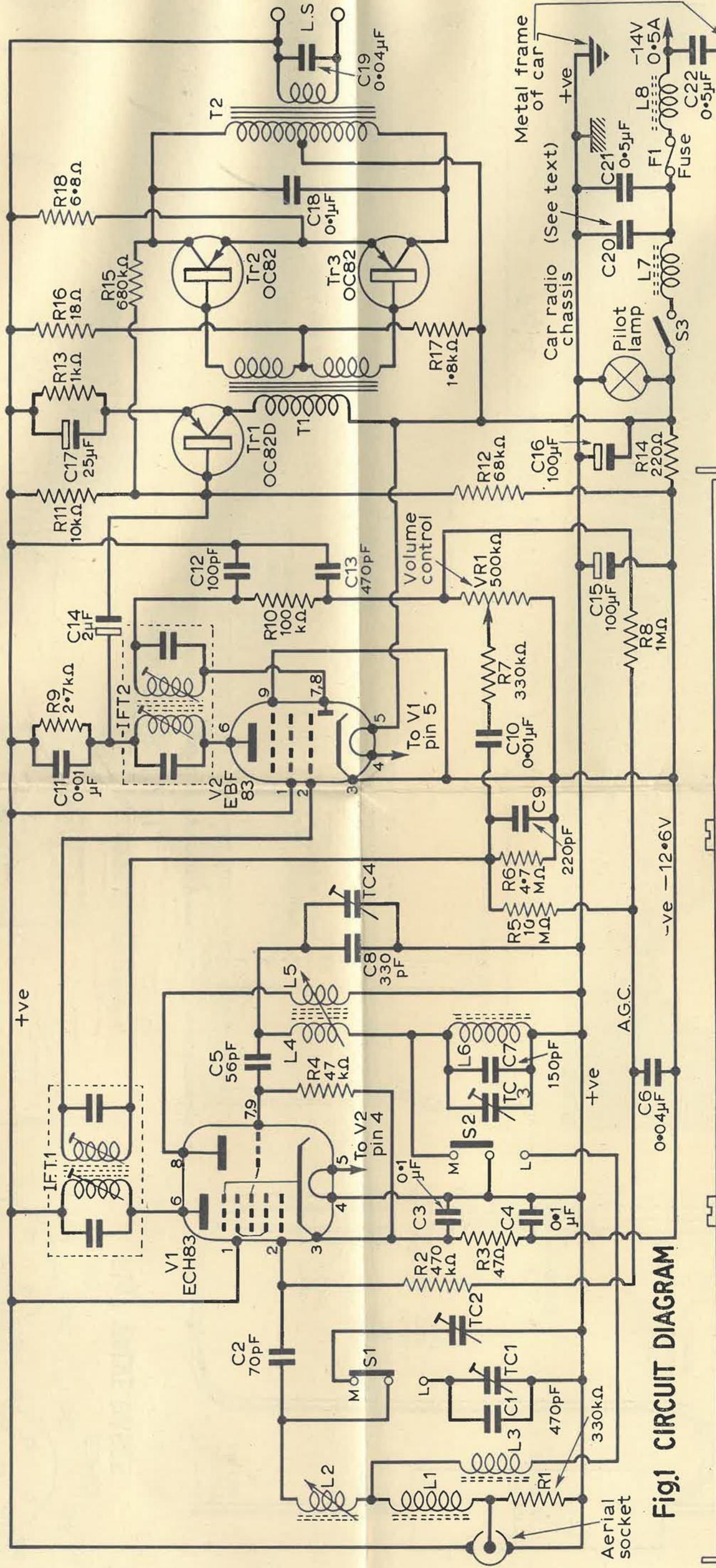


Fig.1 CIRCUIT DIAGRAM

COMPONENTS LIST

Resistors:

- R1 330kΩ
 - R2 470kΩ
 - R3 47Ω 10%
 - R4 47kΩ 10%
 - R5 10MΩ
 - R6 4.7MΩ
 - R7 330kΩ
 - R8 1MΩ
 - R9 2.7kΩ 10%
 - R10 100kΩ
 - R11 10kΩ 10%
 - R12 68kΩ 10%
 - R13 1kΩ 10%
 - R14 220Ω 10%
 - R15 680kΩ
 - R16 18Ω 5%
 - R17 1.8kΩ 5%
 - R18 6.8Ω 10% 1W
- All ± 20% and ¼W carbon, unless otherwise stated.
 VR 500kΩ log. potentiometer

Capacitors:

- C1 470pF silver mica or Polycap 5%
- C2 70pF ceramic or silver mica
- C3 0.1μF Polycap
- C4 0.1μF Polycap
- C5 56pF ceramic or silver mica
- C6 0.04μF Polycap
- C7 150pF Polycap or silver mica 2.5%
- C8 330pF Polycap or silver mica 2.5%
- C9 220pF ceramic or silver mica
- C10 0.01μF ceramic
- C11 0.01μF ceramic
- C12 100pF ceramic or silver mica
- C13 470pF ceramic or silver mica
- C14 2μF elec. 15V
- C15 100μF elec. 15V
- C16 100μF elec. 15V
- C17 25μF elec. 6V
- C18 0.1μF Polycap
- C19 0.04μF Polycap
- C20 Spark plate, see text
- C21 0.5μF paper
- C22 * 0.5μF paper

Variable Capacitors:

- TC1-4 4-way trimmer bank

Inductors:

- IFT1, 2 I.F. transformers
- L1 25μH r.f. choke
- L2, 4, 5 M.W. aerial and oscillator coils, part of permeability tuner unit mounted on chassis.
- L3 L.W. aerial loading coil (yellow)
- L6 L.W. oscillator loading coil (green)
- L7 25μH r.f. choke
- L8* 25μH r.f. choke
- T1 Push-pull driver transformer
- T2 Push-pull output transformer

Valves and Transistors:

- V1 ECH83
- V2 6BF83
- Tr1 OC82D
- Tr2, 3 OC82 matched pair

Miscellaneous:

- S1, S2, S3 Push-button switch unit
- LPI 12V 2.2W bulb MES
- F1 2A fuse
- Bulbholder. Elliptical loud-speaker. Printed circuit board. Tuning dial. Two 1½in. x 4BA spacers. One two-pin plug and socket. One 3-way tag strip. One grommet. One 6-way tag strip. Speaker baffle. Two control knobs. Two B9A printed circuit valveholders. Two valve screening cans B9A. Two screening can earthing clips. Fuseholder. Three transistor heat sinks.

Main Metalwork and drive components, etc.:

- Main chassis fitted with dial-drive assembly, aerial socket and permeability tuner unit (L2, L4, L5).
- Rear panel
- Metal cover
- Chrome escutcheon

* The filter/suppressor components, C22/L8, are supplied as a complete, assembled unit

● Sterne-Clyne, Ltd.

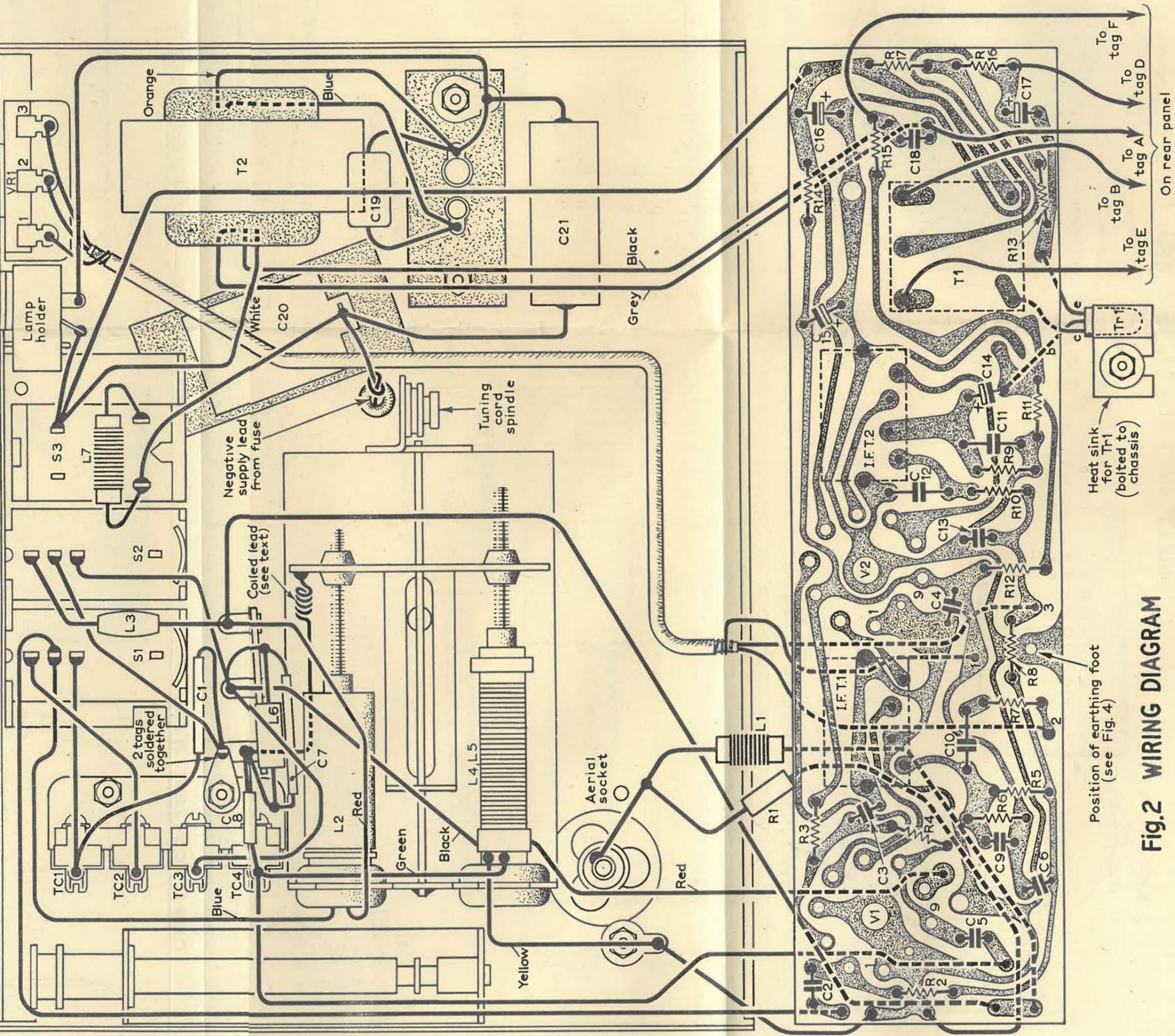


Fig.2 WIRING DIAGRAM

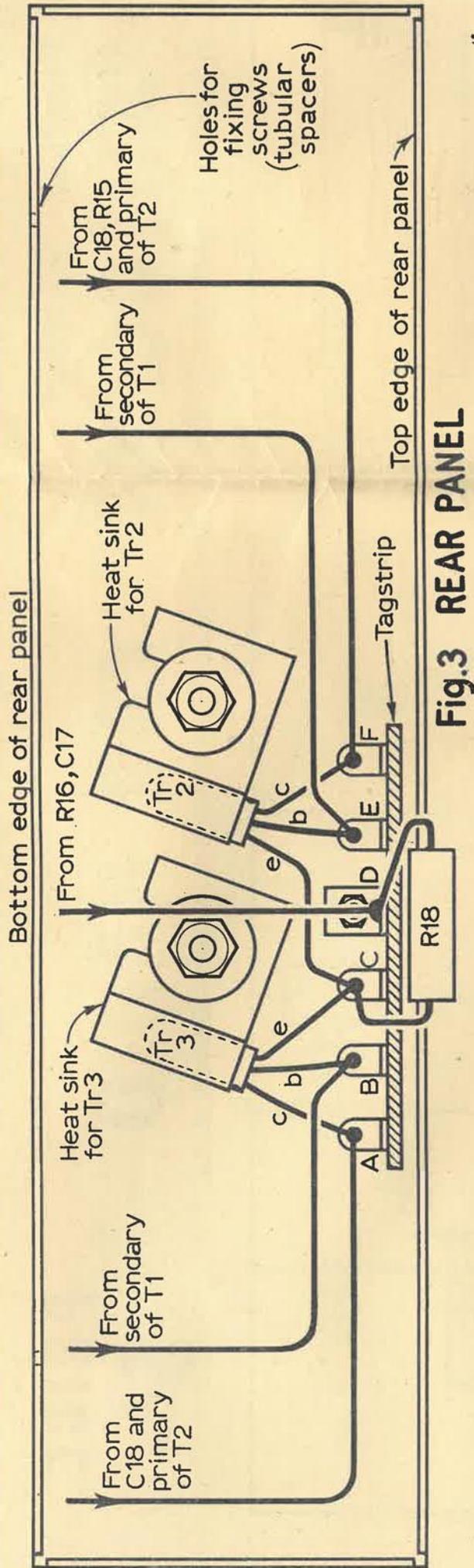


Fig. 3 REAR PANEL

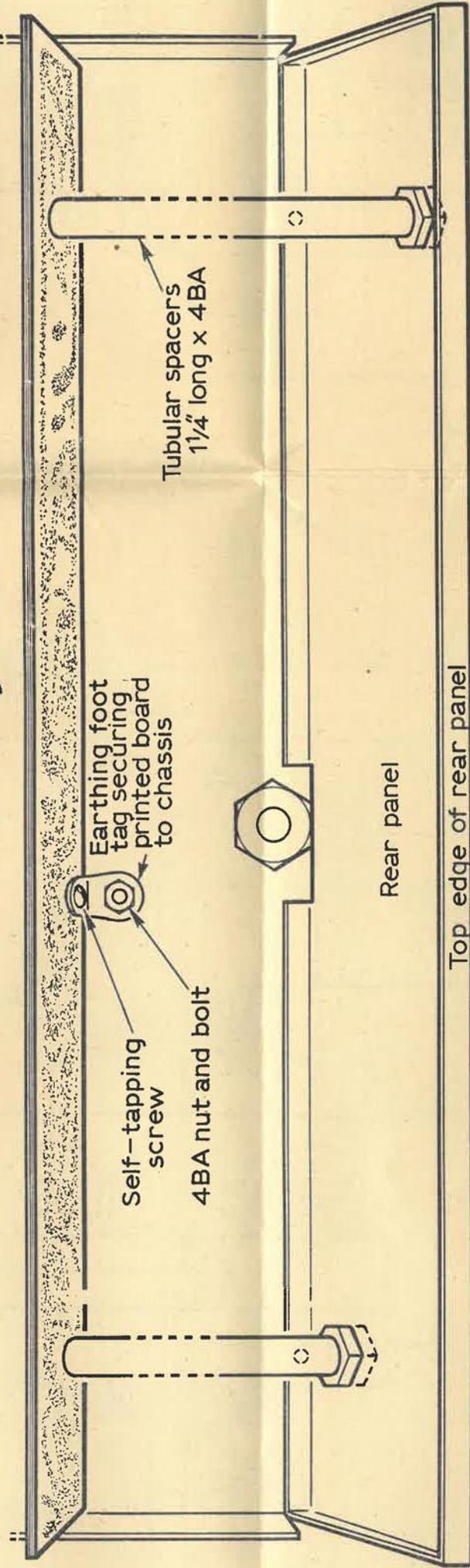


Fig. 4 SECURING PRINTED CIRCUIT BOARD

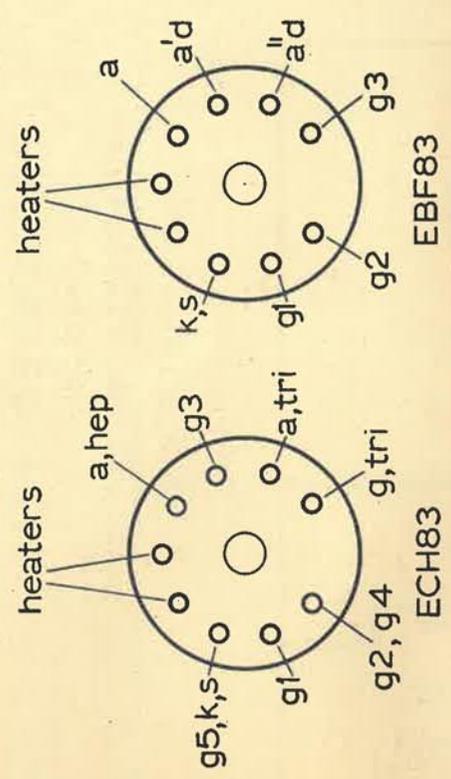


Fig. 7 VALVE BASES

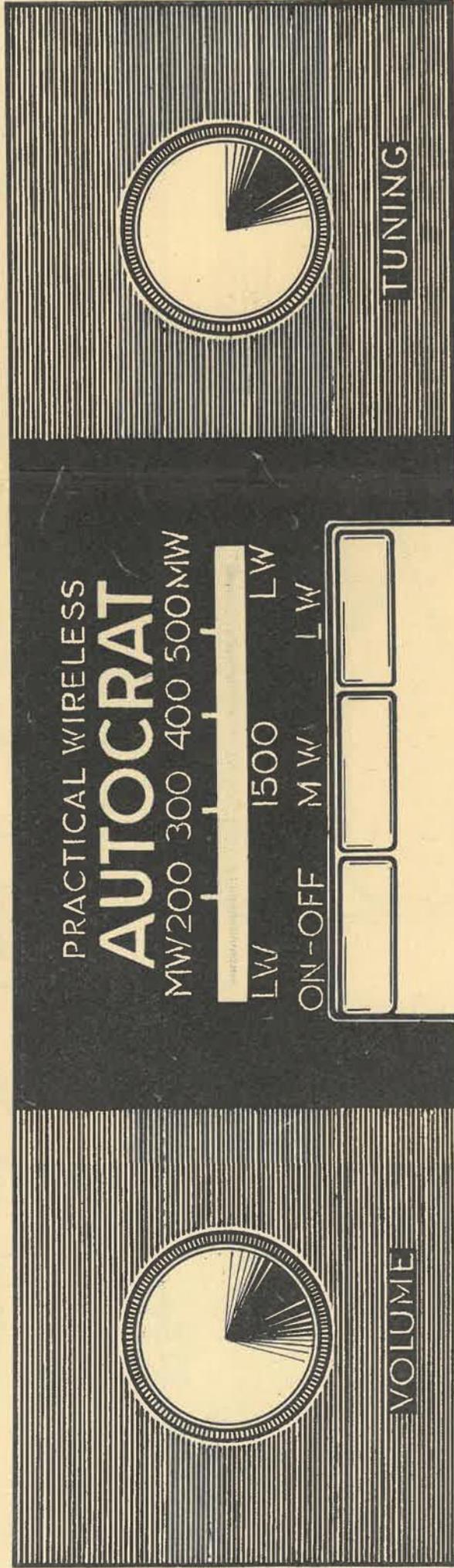
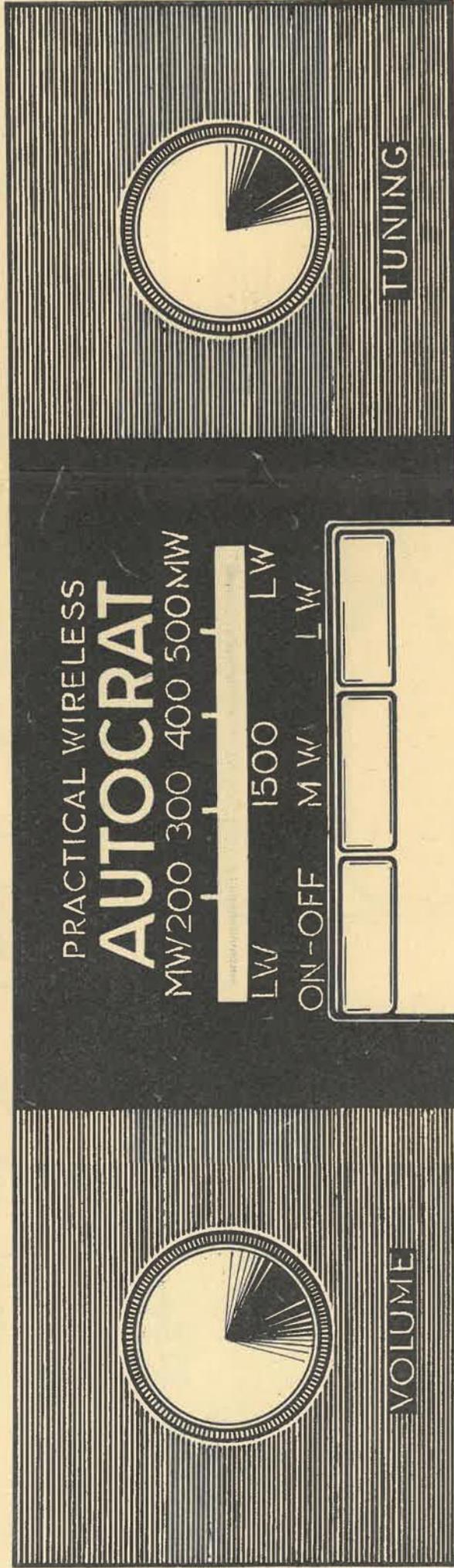
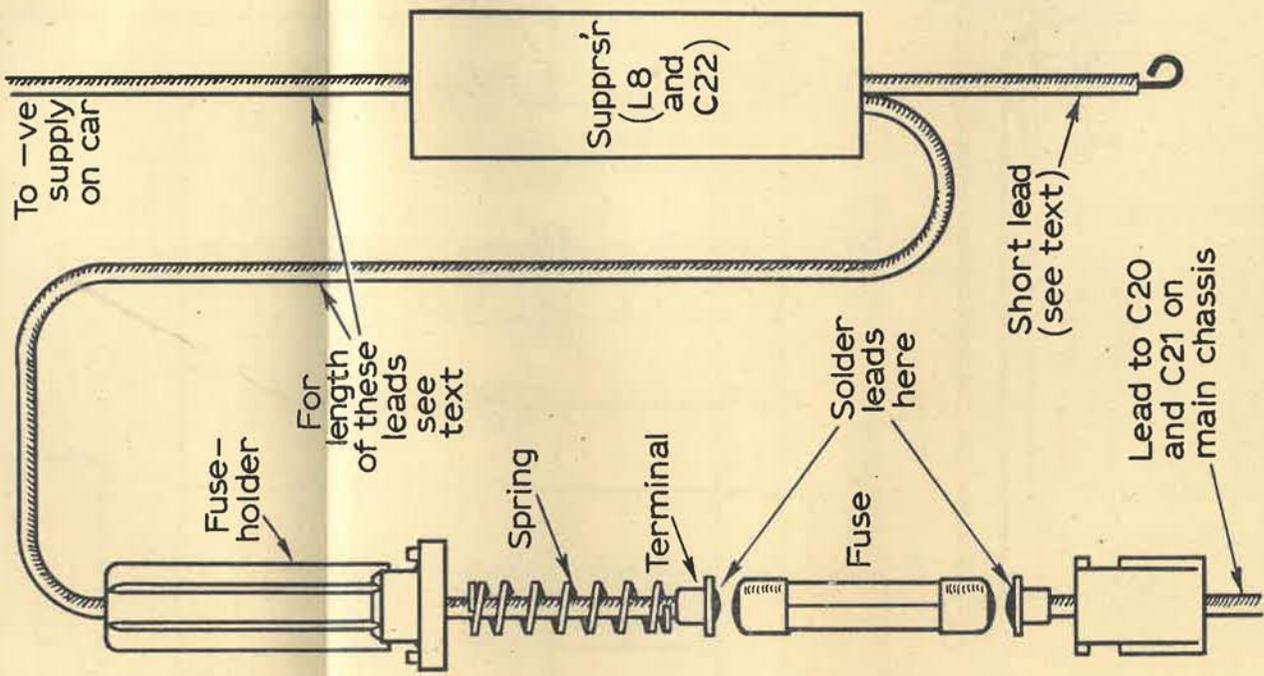


Fig. 4 SECURING PRINTED CIRCUIT BOARD

Fig. 5 FRONT VIEW

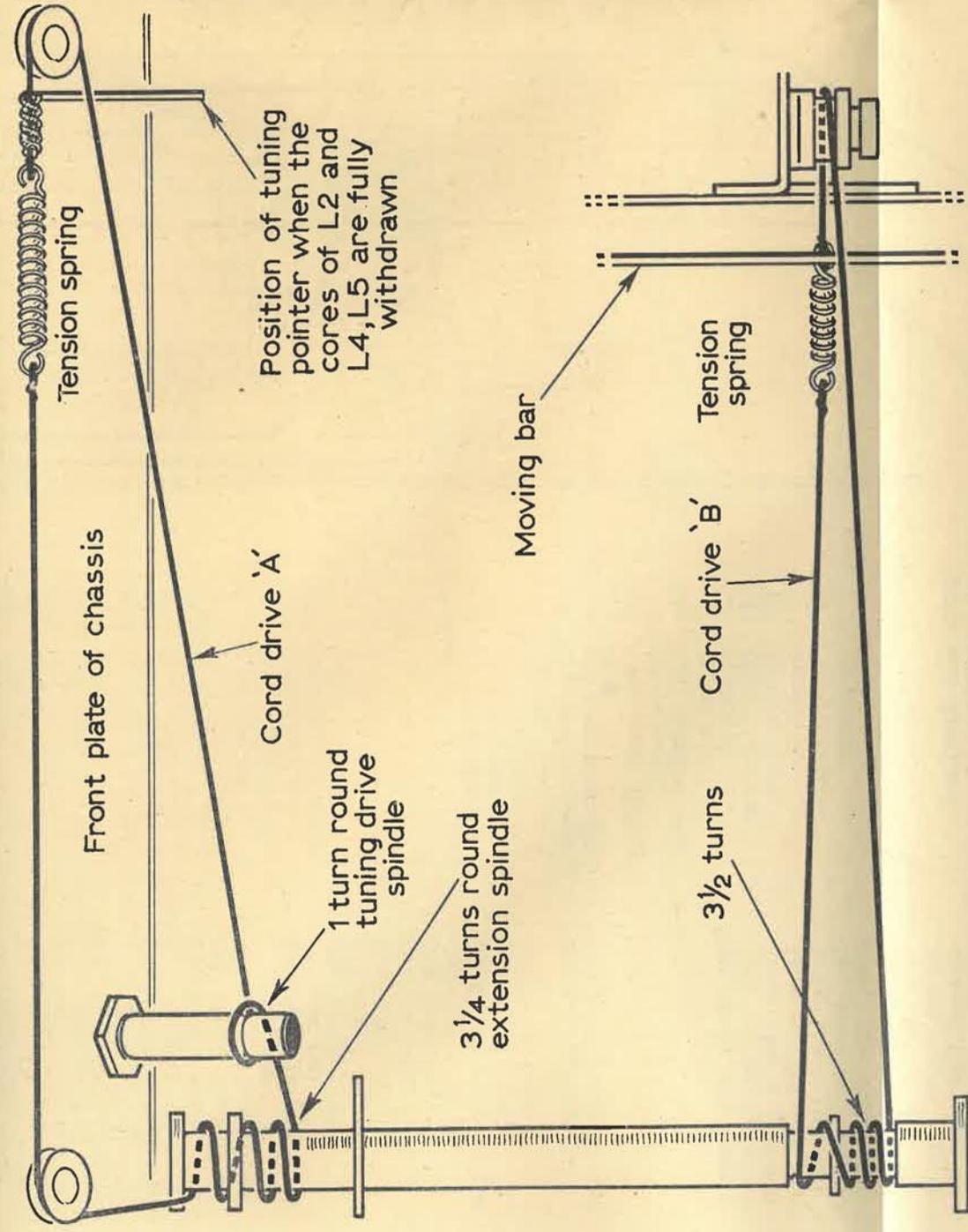


Fig. 8 SUPPRESSOR AND FUSE-HOLDER ASSEMBLY

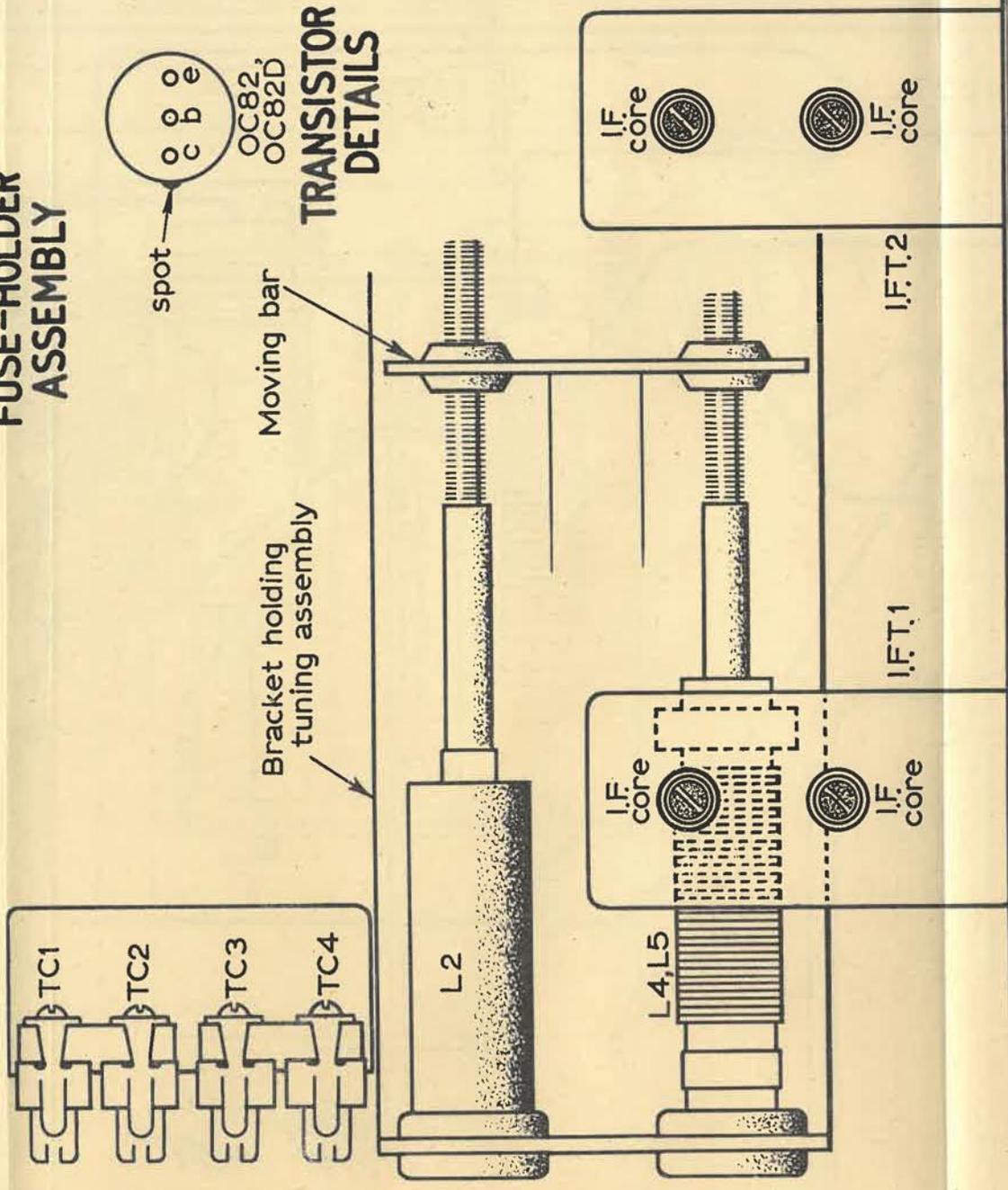


Fig. 9 ALIGNMENT DIAGRAM

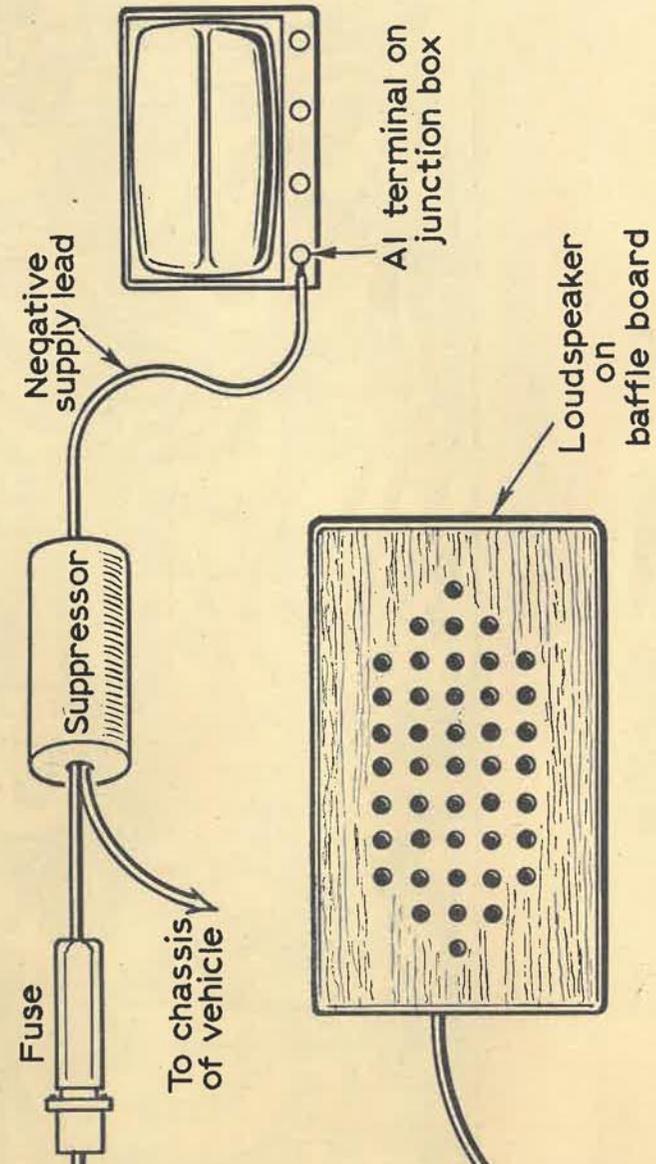


Fig. 6 CORD DRIVE DETAILS


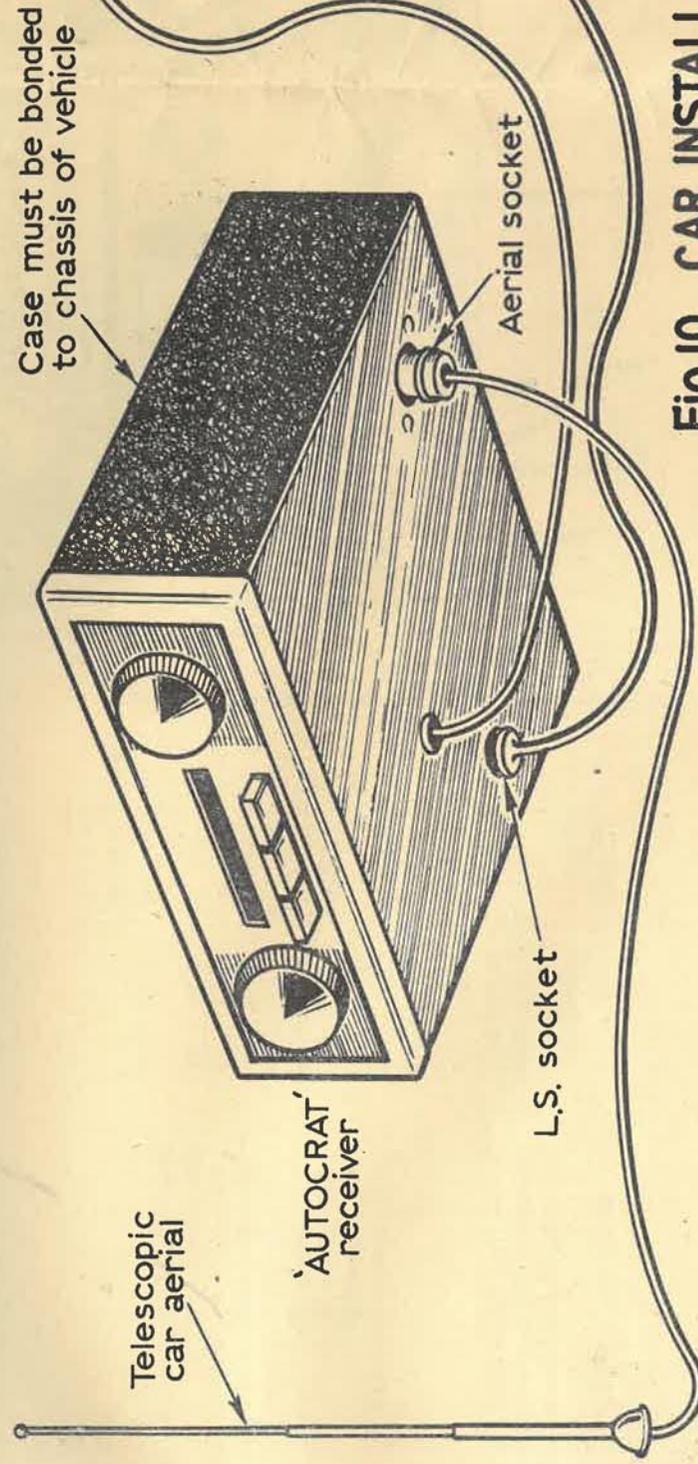


Fig. 10 CAR INSTALLATION CONNECTIONS

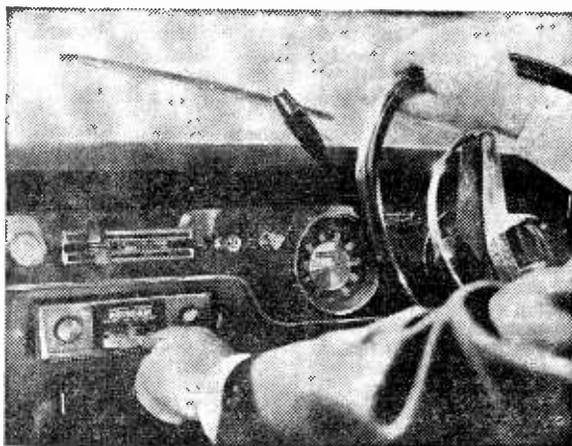The subject of this month's free Blueprint is a two-band, hybrid car radio employing printed-circuit construction.



The PRACTICAL WIRELESS AUTOCRAT

THE parts to build this inexpensive car radio, including the drilled chassis and metalwork, are readily available* and if all the components are ordered at one time, they will be supplied to PRACTICAL WIRELESS readers for under £10, this being a considerable saving on the total cost of the individual components.

The "Autocrat" car radio utilises a printed circuit board, thus ensuring simplicity and reliability in construction and making it an ideal project for the home constructor. Two valves plus three transistors are used in the superhet circuit which includes a push pull transistor output stage, giving an audio output of approximately 1.5W. Selectivity and sensitivity are quite good, despite the fact that no r.f. stage is employed.

The receiver covers the whole of the medium waveband from 180-550 metres. The tuning is also adjustable on the long waves, although coverage is restricted to reception of the BBC Light programme transmitted on 1500 metres. This has simplified the design of the receiver and also the final alignment.

As the receiver is designed for a 12V positive earth system only, i.e. the + terminal of the battery is connected to the metal frame of the motor vehicle, the metal chassis and case of the radio will be connected automatically to the positive supply when it has been correctly installed in the car. *Any reversal of polarity for however brief a period may permanently damage the transistors.*

The car radio is unsuitable for cars where the negative, i.e. the - terminal of the battery, is connected to the vehicle chassis (e.g. many Continental models).

*Messrs. Sterne-Clyne Ltd., 3-5 Eden Grove, Holloway, London N.7, and branches. An accessory kit comprising brackets, screws, etc., for fitting the car radio is also available.

The dial drive assembly and permeability tuning unit is supplied already assembled and fitted to the chassis, which considerably simplifies the mechanical work involved in the construction of the radio. Located just behind this tuning unit is the aerial socket. This, plus the spark plate (C20) are also supplied already fitted in their correct positions on the main chassis (see Fig. 2 on the Blueprint).

The dimensions of the radio are such that it will fit the majority of standard "cut-outs" in cars. In instances where this does not apply, the car radio may be conveniently installed below the dashboard, or any other convenient position. Metal bushes, tapped for 2BA bolts are provided on the sides of the metal cover to facilitate the fitting of brackets, etc.

When the receiver has been completed and all wiring and connections checked, it will be necessary to carry out alignment of the aerial, oscillator and i.f. tuned circuits with a signal generator before the car radio will function correctly.

Messrs. Stern-Clyne Ltd., offer an alignment service to those constructors who have purchased all parts from them and are unable to obtain the use of suitable alignment equipment. A charge is made for this service, details of which may be obtained on application.

The i.f. transformers in this receiver contain adjustable iron-dust cores. These are extremely fragile and on no account should they be adjusted with a metal type of electrician's, or so called "grub" screwdriver. The correct type of trimming tool must be used and readers are referred to the article on page 524 of the October 1964 issue of PRACTICAL WIRELESS. The free trimmer and alignment tools supplied in that issue are ideal for the purpose. Alternatively a plastic knitting needle or even a matchstick with the end suitably shaped to fit the slot in the dust cores exactly should be used.

ASSEMBLY

To commence assembly, fit the various components to the printed circuit board, with careful reference to Fig. 2.

All components are fitted on the paxolin side of the printed circuit board and solder applied to the copper side.

To simplify the assembly, it is recommended that some order is followed, and therefore commence by soldering all the resistors in position. If they are of the printed circuit variety, the ends will be already trimmed and formed to the correct length. If not, they will have to be trimmed accordingly. Before the capacitors are fitted, it is advisable to fit the twin screened lead that runs from the printed circuit board. This should be approximately 10in. in length and again with reference to Fig. 2, is soldered to points 1—2—3. The earth braid that goes to point 1 should be fitted with insulating sleeving to avoid contact between the braid and other points of the circuit.

All the capacitors may now be fitted to the printed circuit board, noting particularly the polarity working of the electrolytic capacitors. C14, C13, C16 and C17. The + and - markings on these components must coincide with those shown in Fig. 2.

The two B9A valveholders and i.f.t.1 and i.f.t.2 should now be fitted. The i.f. transformers are identical and may be fitted in either position, and as their pins are offset they can only be fitted in one way. Do not forget to solder the can earthing clips to the printed circuit. Small clips are also supplied for earthing the valveholder screening can, and are fitted between pins 1 and 9 and soldered. They should be fitted in such a manner that they tend to bend away from the valveholder.

The driver transformer T1 and the two 4BA x 1½in. bolts plus spacers are next fitted. A 4BA solder tag is bent to form a foot, and is bolted and then soldered in position where shown in Figs. 2 and 4.

Tr1, a Mullard OC82D transistor, is next fitted with sleeving on its three leads and soldered in position. The leads should not be cut, and particular note should be made of the lead connections, e—b—c.

Mains Chassis Assembly

The following components should be fitted in the order given. The push button selector switch, taking 6BA x ¼in. bolts, is fitted to the cut-out at the front of the chassis, and the volume control VR1 fitted alongside. Next T2, the output transformer is fitted, along with the bank of four trimmers TC1—TC4. An earthing solder tag may also be fitted under one of the nuts holding this component, but if considered possible, this solder tag can be dispensed with, provided the earthing foot of the three-way tag strip can be persuaded to fit instead. Whichever method proves easiest should be utilised. The loudspeaker socket should be mounted using 6BA x ¼in. bolts, plus an earthing tag where shown. Also fix an earthing tag to one side of the aerial socket. A polythene grommet is fitted to the large hole adjacent to C20, through which the negative supply lead will eventually pass. Join the blue and orange leads to the loudspeaker socket, fit C19 in position and earth one

side of the socket.

Take L1, the r.f. choke, and solder this, together with R1, to the aerial socket. R.F. chokes L1, L7 and L8 are all identical and are therefore easily identified.

Rear Panel

Fit the 6-way tag strip to the inside of the rear panel as shown in Fig. 3 using 4EA x ¼in. bolts, also Tr2/Tr3 the two OC82 push-pull output transistors—remembering to fit heat sinks. Do not cut the transistor leads, and cut sleeving to fit over each lead, as for Tr1. Solder R18 in position and fit a 6in. length of insulated wiring to tags A—B—D—E and F.

Final Assembly

Join the free ends of the five leads that emerge from the rear panel to the printed circuit board. Refer to Figs 2 and 3 for this.

With reference to Fig. 4, bolt the rear panel assembly to the printed circuit board using the 4BA x 1½in. bolts and spacers previously fitted.

Carefully bolt the lower edge of the rear panel to the rear of the main chassis using two small self-tapping screws, and then finally secure the printed circuit earthing foot in position. The heat sink may now be fitted to Tr1 and then bolted to the main chassis. The remainder of the wiring and mounting of the balance of the components shown in Fig. 2 may now be completed.

The coiled lead shown between the moving metal bar on the tuning unit and the tag strip is simply a short length of stranded lead which has been wound onto the shaft of a small diameter screwdriver to form a coil. This is then simply soldered in position where shown.

When fitting the lampholder and pilot lamp, make sure that the metal surround to the lamp is not shorting to the metal chassis.

L3 coil is supplied fitted with a yellow sleeve and L6 with a green sleeve.

If the blue lead from L2 coil is short, it should be extended as necessary.

Fig. 8 shows the assembly of the suppressor filter unit and fuseholder.

The loudspeaker is fitted to the baffle using suitable 4BA bolts and washers. It is possible that the holes in the loudspeaker frame will not coincide with those in the baffle. Simply punch extra holes if necessary, using a sharp pointed object or even a small screwdriver. A suitable length of twin lead should also be fitted to the two loudspeaker tags, plus a two-pin plug at the other end.

Insert the two valves into their respective sockets V1 ECH83 or equivalent 6DS8, V2 EBF83 or equivalent 6DR8, and fit the metal screening cans to both valves. Finally the dial and the push-on control knobs are fitted. Now re-check all wiring very carefully.

Alignment

This requires the use of a signal generator for optimum results and for those constructors who either own such an instrument, or who have access to one, the following details are given. It will be necessary to obtain a suitable 12V d.c. supply, the

battery + is connected to the car radio chassis and the battery— to the —ve supply lead.

Connect the loudspeaker and switch on the radio. The dial lamp should immediately come on. Press the medium wave push button and adjust pointer to 550m on the dial.

Set the signal generator to the i.f. frequency of 470kc/s and feed a modulated signal to aerial socket. Adjust the cores in i.f.t.1 and then i.f.t.2 for maximum audio output. Adjust the volume control to a suitable level, and adjust the output from the signal generator to a minimum.

Set signal generator to 550kc/s and adjust the core of L4/L5 for maximum signal and then L2 core. By using a pair of thin nose pliers, draw the brass threaded rod attached to the dust core either in or out of the coil former. The cores have a slot at the grommet end, and the end of the brass thread has been flattened to facilitate adjustment with suitable trimming tools, but some difficulty may be experienced if this method is used due to limited working space. Re-adjust the signal generator to 1.5Mc/s, and tune the pointer to 200m and adjust TC4 trimmer for maximum signal, followed by TC2. Depress the L.W. button and re-adjust the signal generator to 200kc/s. Set the pointer to 1500m and adjust first TC3 and then TC1 for maximum output. Disconnect the signal generator and connect a suitable aerial (preferably a car aerial) to the aerial socket and check the performance.

The aerial circuit trimmers TC2—medium wave—and TC1—long wave—may be then re-peaked for optimum sensitivity. This final operation may, however, be carried out in the car.

The cover and chrome escutcheon is held in position using small self-tapping screws.

Installation

If the radio will fit the cut-out in the dashboard of your motor vehicle installation will be relatively easy. Alternatively, it may be held under the dashboard by use of suitable home-made strips. As mentioned earlier, the "bushes" fitted to the sides of the radio's metal cover are tapped for 2BA bolts, and this should not be any longer than $\frac{1}{4}$ in.

Any paint around the bushes and on the car chassis where the brackets are to be bolted, must be scraped away, i.e. the car radio metal case must make good electrical (and mechanical) contact with the metal frame of the motor car. The loud-speaker may also be fitted in any convenient position.

The negative supply lead from the car radio is normally taken to the A1 terminal on the junction box. Reference to the "owner's handbook" should indicate its location. The "short lead" shown coming from the suppression unit in Fig. 8 must be securely connected to the nearest earthing point on the car chassis.

Interference Suppression

Now, although the "Autocrat" is fitted with a


filter unit in the negative (—) supply lead to reduce the effects of electrical interference, it is also of prime importance that the ignition system, dynamo, sparking plugs, windscreen wiper electric motor, flasher indicators etc., are also fitted with suppression devices.

The ignition system, if insufficiently suppressed will cause a continuous clicking or popping sound in the receiver, and the dynamo will cause a whine which will increase in level when the engine is accelerated.

The majority of modern cars are already fitted with adequate suppression devices but brief details are included herewith for those vehicles that still require suppression. The types of devices that are utilised for suppression of electrical interference are capacitors, resistors and chokes of various sizes. Some vehicles may have a resistance type suppressor fitted to the distributor, but if not it should be fitted in the high voltage lead that runs between the spark coil and distributor rotor. This must be fitted as close to the distributor as possible. The nominal resistance of these devices is 5—10k Ω .

Resistance type suppressors should also be fitted to each lead that runs from the distributor head to the spark plugs. Simple cut lead or clip-on type suppressors may be purchased from a radio dealer or garage. Once again, these units must be fitted as close to the sparking plugs as possible.

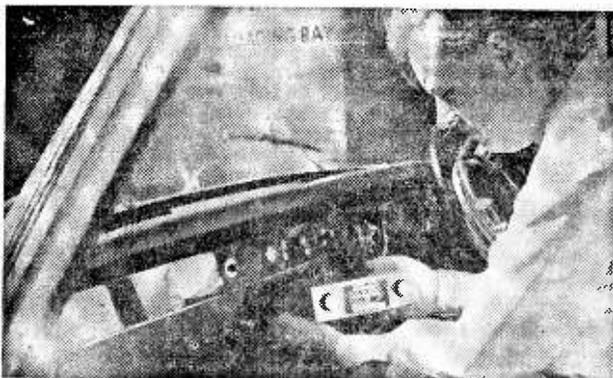Suppressor capacitors for the dynamo are normally contained in a metal can, which has a metal bracket for mounting plus a flying lead. The



A P.W. "Autocrat" car radio takes its place in the fascia of a modern family saloon.

bracket is securely fitted under the nearest convenient earthing nut on the case of the dynamo, and the loose lead is then taken to the dynamo live output terminal. The value of capacitor is normally 0.5 or 1 μ F.

It may also be necessary to fit a suppressor capacitor to the ignition coil and once again this may be of the same type as fitted to the dynamo. Bolt the fixing bracket to the nearest earthing point and take the loose lead to the SW terminal on the ignition coil.

For further information on the fitting of these and other devices, approach a local supplier or garage who will normally give assistance. ■

PREPARING FOR THE R.A.E.

BRIAN ROBINSON.

I: BASIC THEORY, RESISTANCE, OHM'S LAW

IT is the wish of the writer to include in a series of only twelve articles, sufficient theory work to enable the reader to sit the City and Guilds of London Institute "Radio Amateurs' Examination" in November 1965. I have tried to explain the more difficult theory in simple language and have included diagrams and sketches wherever they are likely to help the reader. As all the theoretical material cannot be included in detail the reader is urged to study suitable text books—and a list of suitable books is given at the end of this first article.

At the end of each article will be a series of questions which have been designed to help the reader; these will be generally of the "calculation" type, and answers will be given at the end of the following article. If the work is undertaken diligently, a "pass" in the examination would not be too great a reward!

1.1 The Electric Current

All materials are composed of *Atoms*. A simple atom, such as that of Hydrogen, consists of a central core or *Nucleus*, which carries a positive charge, and a particle called an *Electron*, which carries a negative charge. The electron spins round the nucleus in much the same way as the earth orbits round the sun. (See Fig. 1.)

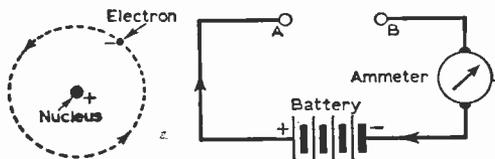


Fig. 1 (left): The Hydrogen atom.

Fig. 2 (right): A simple test set-up for conductors and insulators.

The Hydrogen atom is the simplest of all the atoms and if we were to draw a diagram of say a Copper atom, it would have no less than 29 electrons orbiting round it. If an electron can be made to leave its orbit and join the orbit of the electron next to it, an *Electric Current* will flow. If we make a current flow through a material such as a length of copper wire, we must supply a "force" to make the electrons of the copper atoms move along. This force is generally supplied as a result of a *Chemical Reaction in a Cell or Battery*. (The "force" can also be supplied by heating and magnetic effects but these will not be dealt with here.) Therefore, for our purposes we can consider that an **electric current is in fact a flow of electrons.**

1.2 Conductors and Insulators

Materials which will give up electrons easily to form an electric current are said to be *Conductors*. Those materials which will not easily allow an electron flow to take place are called *Insulators*. In Fig. 2 we can connect various substances between A and B to determine which are conductors and which are insulators. If no current shows on the ammeter the material is an insulator, if a current shows on the meter the material is a conductor; the higher the current the better the conductor. Conductors have a *Low Resistance* to the passage of an electric current and insulators have a *High Resistance*.

1.3 Electrical Units

The *Coulomb* is a basic electrical unit, and is represented by "Q". The coulomb indicates the rate at which an electric current flows and therefore it has a time component. The unit used to measure the current flowing (average) in a circuit is the *Ampere* or *Amp.*, which is denoted by "I", and this is given in the expression $I = \frac{Q}{T}$ where Q is in coulombs and T is in seconds.

We can also see that 1 coulomb of electricity passes when a current of 1 amp. flows for 1 second, or from the above expression:

$$Q = I \times T$$

If a current flows through a conductor, it can be increased by increasing the *Potential Difference* across the ends of the conductor, i.e. a greater *Electrical Pressure* has to be used to "push" the current round the circuit. Potential difference or electrical pressure is measured in *Volts*. Therefore to increase the current flowing through a conductor, the voltage across its ends must be increased.

All materials do not allow a current to flow through them with equal ease (see 1.2) and they can be said to possess different amounts of *Resistance* to the flow of an electric current. The unit which is used to measure this resistance is the *Ohm*.

1.4 Ohm's Law

The scientist Ohm discovered a relationship between voltage (E), current (I) and resistance (R). The circuit shown in Fig. 3 can be used to demonstrate (N.B. *not* prove) the results he obtained.

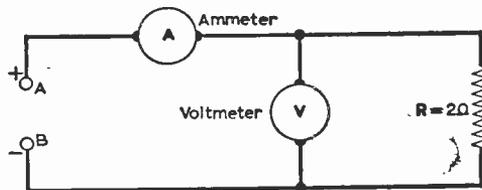


Fig. 3: Arrangement for demonstrating Ohm's Law.

A resistance of say 2 ohms is connected to batteries of various voltages, the battery being connected to AB. An ammeter measures the current flowing through the resistance and a voltmeter measures the voltage appearing across the resistance. Values of I and E are recorded, and also values of $\frac{E}{I}$

each set of readings. The results are tabulated as shown in Fig. 4.

<i>E</i>	<i>I</i>	$\frac{E}{I}$
2 V	1 A	2
4 V	2 A	2
6 V	3 A	2
8 V	4 A	2

Fig. 4: Typical values to indicate Ohm's Law.

It can be seen that $\frac{E}{I}$ gives a constant result of 2, but we also know that the value of the resistance *R* was 2 ohms, so it appears that $R = \frac{E}{I}$ and thus if *E* and *I* are known *R* can be calculated. The equation can also be written as $I = \frac{E}{R}$ or $E = I \times R$.

Thus if any two of voltage, current and resistance are known, the third can be found. Ohm's Law can be stated as follows: "the current flowing in a circuit is directly proportional to the applied Voltage and inversely proportional to the Resistance". When Ohm's Law is applied the voltage must always be in volts (not kilovolts, millivolts, etc.), the current must always be in amperes (not milliamperes, etc.), and the resistance must always be in ohms (not megohms, kilohms, etc.).

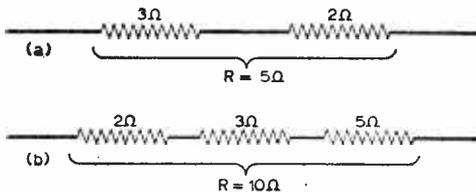


Fig. 5: Examples of resistances in series.

1.5 Resistance in Series

If two resistances are connected in Series as shown in Fig. 5a, the total resistance, *R* is equal to $R_1 + R_2$ in this case $R = 3 + 2 = 5$ ohms.

In Fig. 5b three resistances are connected in series and the total resistance, *R*, is $2 + 3 + 5 = 10$ ohms. (N.B.—Ohms are generally represented by the Greek letter Omega, Ω.) Therefore for any number of resistances connected in series the total resistance is $R = R_1 + R_2 + R_3 + R_4 + \dots$

1.6 Resistance in Parallel

If two resistances are connected in parallel, as shown in Fig. 6a, the total resistance, *R*, can be found by using the expression

$$R = \frac{R_1 \times R_2}{R_1 + R_2}$$

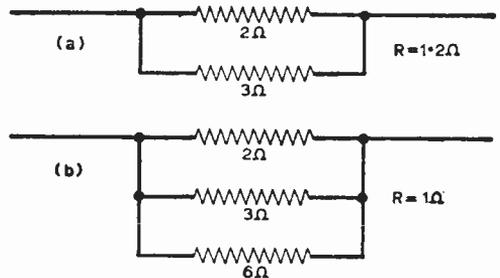


Fig. 6: Examples of resistances in parallel.

Thus in Fig. 6a, $R = \frac{2 \times 3}{2 + 3} = 1.2 \Omega$.

If three or more resistances are connected in parallel, the formula used to determine *R* is

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

or $R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$

Thus in Fig. 6b $R = \frac{1}{\frac{1}{2} + \frac{1}{3} + \frac{1}{6}} = 1 \Omega$.

For resistances connected in parallel, the total

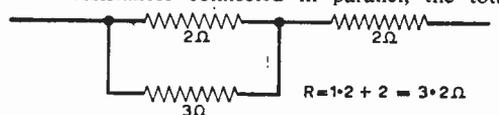


Fig. 7: Examples of resistances in series/parallel connection.

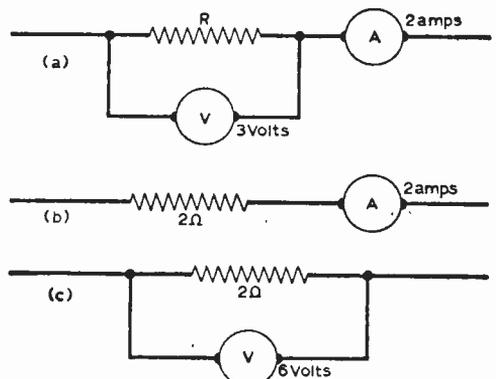


Fig. 8: Arrangements to find the power dissipated by a resistance.

effective resistance, *R*, is always less than that of the lowest value resistance in the circuit.

1.7 Resistances in Series/Parallel Arrangements

The resistance of a series/parallel arrangement such as that shown in Fig. 7 can easily be found by finding the resistance of the parallel connected resistances and

—continued on page 631

a midget ANTENNA for the DX bands

by D. GIBSON G3JDG

THE miniature antenna, like the perfect v.f.o. will always rate high in the dreams of any amateur or shortwave listener. From time to time various ingenious approaches have been made to clip off the precious inches and yet still preserve the effectiveness of the antenna. Discussion with other amateurs tends to indicate the opinion that if element lengths are reduced then something must invariably suffer.

Either the radiation resistance drops to a ridiculously low value or the bandwidth is microscopic. Often such a system is difficult to load or exhibits a very high standing wave ratio.

The handbooks and theoretical text books do not appear very eager to praise the undersize antenna either and usually give diagrams and discussions on systems of the "correct length". They take a piece of wire say half a wavelength long and suspend it by some miraculous means so that it is held in mid-air with no supports at either end. (To introduce any supports might interfere with the polar diagram so they conveniently dispense with them!)

This wire is then situated some half wavelength high completely in the clear and over a wonderfully efficient earth—probably an empty 50 acre field on top of a hill.

All the time the amateur is reading this he is thinking about his back garden some 30 feet long at best, the telephone wires nearby, a metal shed in a neighbours garden etc., and wondering how to make the best of it all.

The writer is one of such creatures and the main interest centres on the 20 metre band 14,000—14,350kc/s. The dipole length for this band is some 34ft. long but in order to "give it a chance" it needs to be 34ft. high as well. This implies at least one 35ft. mast and possibly two, or some form of extension pole attached to the side of the house—see Fig. 1.

Those who frequent the 20 metre amateur band will know that these days a dipole will not always prove a particularly suitable aerial. Not that it is inefficient, nor to imply that there are amateurs who cannot work DX with a dipole on twenty. However if one does use this simple system today then it will have to compete with shiny new 3-element beams (often commercially made and pre-adjusted) 4-element beams and cubical quads etc., not to mention the hundreds of watts p.e.p. of side-band that is often pumped into them.

On the other hand there are many who would be thankful if they could erect even a dipole but who are unable to do so on account of available space or neighbours who object to various objects waving above the skyline. It is for just such a need that this article is intended.

It was reasoned that although the text books and more learned brethren may be quite correct in their scepticism of pruning element lengths it was a very real fact that mobile stations with their short loaded whips were busy working half the world. This, be it noted, with element lengths that were not so much pruned as massacred!!

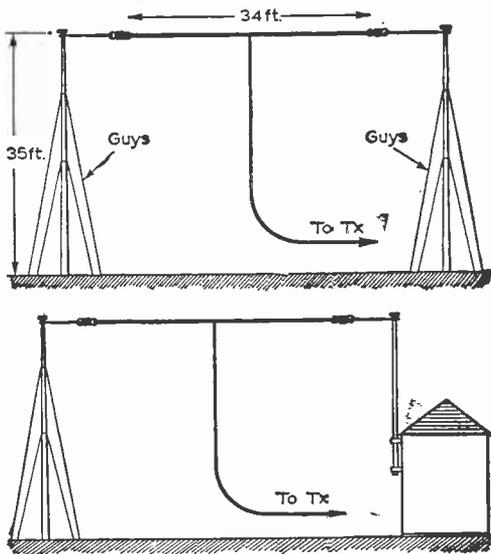


Fig. 1: Two variations on the aerial apparently necessary for efficient reception on 20m.

It was decided to pursue this line of thought and see how far it could be developed.

Basic Design

The maximum length was set at 8ft. and since this was to be a vertical would require no space at all other than the diameter of the element itself. (Owners of 2in. square gardens please note). Accord-

dingly an antenna was rigged up as per Fig. 2.

The 8ft. element was made as follows: a 9ft bamboo pole about 1—1½in. diameter was covered with an 8ft. x 6in. length of baking foil. The pole was merely rolled in the foil rather like rolling a cigarette, and this was held in place by small pieces of p.v.c. tape.

The whole assembly was then once again rolled in a long piece of polythene sheeting to protect it from the weather, the polythene being held in position by attaching a spiral of p.v.c. tape.

TABLE 1.

Band Mc/s	Coil Dimensions
7	19 turns Tap 3 turns from earth.
14	8 turns Tap 2 turns from earth
21	6 turns Tap 1½ turns from earth

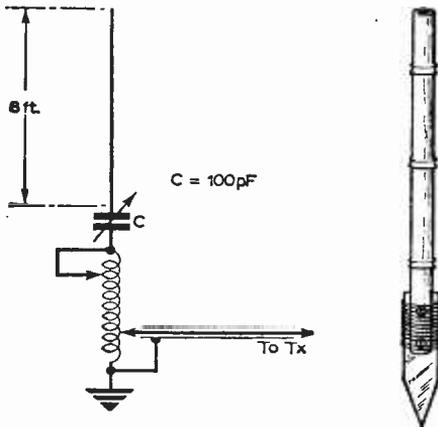


Fig. 2 (left): The theoretical set-up for the basic antenna. Fig. 3 (right): The element may be attached to a shaped piece of wood for simple erection in any convenient plot of ground.

The result is an element which is weather-proof, lighter than the same diameter aluminium tubing, cheaper and will "give" in the wind. It may, if required, be fixed to an 18in. length of 1½in. x 1in. wood and stuck in the ground wherever is convenient (Fig. 3).

Note also, that it will require no unsightly guy wires either. The capacitor in Fig. 2 is 100pF, and the coil consists of some 26 turns of 16s.w.g. tinned copper wire on a 2in. ceramic former spaced the diameter of the wire.

It was found, much to the writer's joy, that by shorting out some of the turns, i.e. varying the inductance and also the tapping point of the co-ax, that the element could be tuned up and loaded with a low s.w.r. on 7, 14, and 21Mc/s. (See Table 1.)

A tentative call on 14,040kc/s brought a 599 report from OE5XXL in Austria and this was with the antenna propped up against the wall of the house. Note that a dipole on this band would be 34ft. long and 34ft. high. By contrast, the present

antenna was 8ft. long and about 3in. (three inches) off the ground.

Adding the 2nd Element

Fired with enthusiasm the next obvious line of experiment appeared to be the addition of another element to make it a sort of 2-element miniature vertical beam and another element exactly the same as the first was manufactured. This was spaced some 7ft. from the driven element and the coil was wound on the lower end of the actual bamboo pole itself. (Not the best of low loss coil formers).

This coil consisted of 12 turns of 16s.w.g. tinned copper wire and the capacitor was a 140pF. The grid dip oscillator indicated that this combination could be resonated from 13—15Mc/s. Thus it could be tuned as a director or reflector.

Setting Up

Method of setting up was first to tune the driven element to 14.050kc/s since c.w. was the prime interest. This was done with the aid of a transistorised g.d.o. Then, the parasitic element was tuned as a director. In the event of no g.d.o. being available, the parasitic can be roughly tuned by ear, and tuning the capacitor C2 Fig. 4 with an insulated screwdriver, signals can be peaked or attenuated some two S-points. After this, all that remains is to adjust the tapping point of the co-ax for minimum s.w.r.

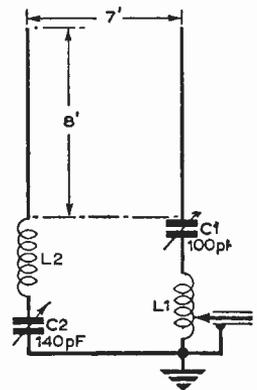


Fig. 4: The arrangement used in the setting-up procedure.

As with all aerials of this type a good earth will make a difference to performance. The earth used for the experiments with the prototype consisted of two 6ft. lengths of ½in. diameter copper pipe driven 5½ft. into the ground 6ft. apart and bonded together by a length of 7/029 wire.

This is far from being an ideal earth and better results might be possible with an improved earthing system. Note that there is a heavy gauge wire from the parasitic to the driven element and the whole system is earthed at this one point (Fig. 4).

Results

Results so far seem encouraging, but a longer period of trial is needed before any definite con-

clusions can be reached. A CQ call brought 599 from UAIKAG in Leningrad and with the beam in the same position a 569 was received from I1SC1 in Italy indicating a 3S-point difference. The s.w.r. appeared reasonable from 14.010—14.070kc/s.

In the first few days of operating, some 13 countries have been worked with the worst report of 579 when the beam was peaked and DJ5DR reported 5 and 8 on 'phone. Note this was on 14.200kc/s whereas the system was lined up and adjusted to work on 14.050kc/s. This antenna system will not compete with say a quad, but where space is at a premium it will enable a respectable signal to be radiated.

The above results were obtained with the beam propped up against the side of the house wall not 4in. off the ground, most unfavourable conditions.

Further Suggestions

There is ample room for further experiment, the spacing of the elements for instance. The spacing of 7ft. used proved successful, but may not be optimum, and increasing it to 10ft. proved detrimental to performance.

A further line of thought would be the addition of another element to make a 3-element beam (director, driven element, and reflector). Or perhaps the third element could be arranged as per Fig. 5. The two parasitics arranged to tune as reflector or director with a small relay. In this way, the beam would be rotated electrically.

Capacitor A would be tuned as a director in each case then the relay could be energised and capacitor B adjusted to tune the element as a reflector.

For those who like their information compact,

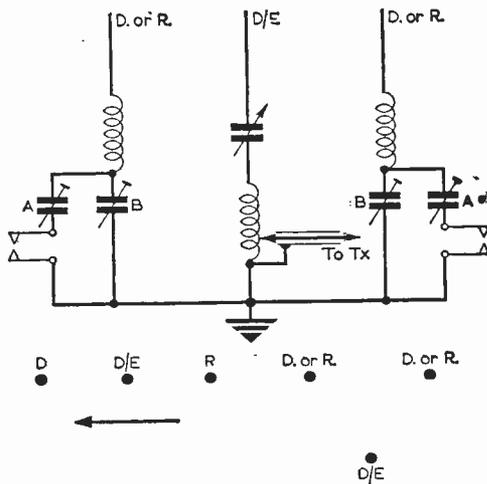


Fig. 5: Providing a third element.

the details of the driven element are shown in Table 1. These figures will vary depending on proximity to earthed objects, efficiency of the earthing system etc., but will provide a useful starting point and guide, after which the system can be adjusted for peak performance under actual local conditions.

The author would be very interested to hear from readers experimenting with aerials along the lines suggested in this article.

Preparing for the R.A.E.

—continued from page 628

then adding to this the value of the series resistance.

Thus, in Fig. 7 the value of the parallel resistances is

$$R = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{2 \times 3}{2 + 3} = 1.2 \Omega.$$

Add to this the value of the series resistance to obtain the total resistance. Therefore total resistance 1.2+2=3.2 Ω.

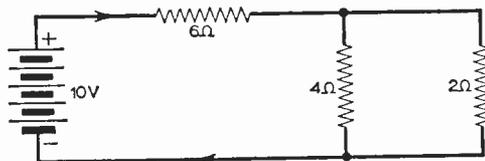


Fig. 9: Circuit for Question 1.

1.8 Power

Power is the rate of doing work and its unit, in electrical work, is the *Watt*, which is denoted by W.

$$W = I \times E$$

or by substitution from Ohm's Law,

$$W = I^2 \times R$$

$$\text{or } W = \frac{E^2}{R}$$

Three ways of finding the number of watts dissipated as heat in a resistance are shown in Fig. 9.

In Fig. 8(a) $W = I \times E = 2 \times 3 = 6$ watts.

In Fig. 8(b) $W = I^2 \times R = 4 \times 2 = 8$ watts

In Fig. 8(c) $W = \frac{E^2}{R} = \frac{36}{2} = 18$ watts.

Question 1

The answer to the following questions will be given at the end of next month's article.

In the circuit diagram given in Fig. 9, calculate:

1. The total current drawn from the battery.
2. The voltage appearing across the 6 Ω resistance.
3. The power dissipated by the parallel connected resistances of 2 Ω and 4 Ω.
4. The power dissipated in the entire circuit.
5. The current flowing through the 4 Ω resistance.

Recommended Literature

- (a) "The Amateur Radio Handbook"—Radio Society of Great Britain.
- (b) "A Guide to Amateur Radio"—Radio Society of Great Britain.
- (c) "The A.R.R.L. Handbook"—The American Radio Relay League.
- (d) "Physics and Radio"—M. Nelkon.
- (e) "Foundations of Wireless"—M. G. Scoggie.

Part 2 Next Month

Twin Triode Two TWO-VALVE PUSH-PULL AMPLIFIER

BY A. C. RODEN

THIS amplifier was designed to obtain reasonable volume and quality for a small outlay. It uses two twin triodes in a simple circuit, only consumes 25mA h.t. and has adequate gain for a crystal p.u. The first stage is half a 12AX7 in a conventional amplifier circuit and the output is fed to the other half of the valve which is wired as a

"concertina" phase splitter. The outputs from this are fed to the two halves of a 12BH7 twin triode arranged in push-pull.

Components

The majority of components are not critical but the phase splitter is rather important. R7 and R5

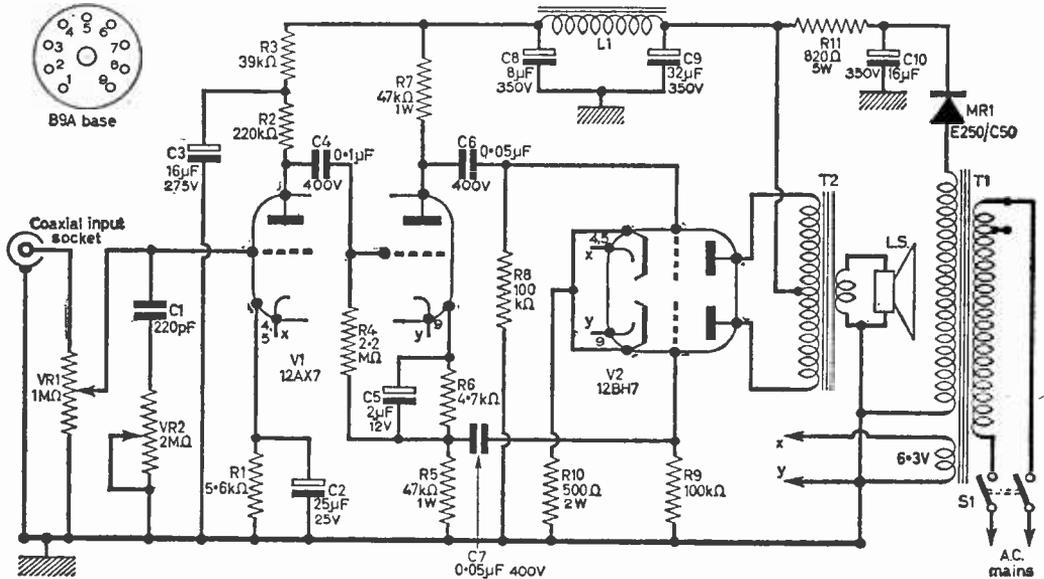


Fig. 1: The simple two-valve circuit.

COMPONENTS LIST

Resistors:

R1	5.6kΩ	R7	47kΩ 5% 1W
R2	220kΩ	R8	100kΩ
R3	39kΩ	R9	100kΩ
R4	2.2MΩ	R10	500Ω 2W
R5	47kΩ 5% 1W	R11	820Ω 5W w.w.
R6	4.7kΩ 5%		

All $\pm 10\%$ $\frac{1}{2}$ W carbon unless otherwise stated.

VR1 1MΩ potentiometer with d.p. switch, S1

VR2 2MΩ potentiometer

Valves:

V1	12AX7	V2	12BH7
----	-------	----	-------

Transformers:

T1	Mains transformer. Secondaries: 250V 50mA; 6.3V 2A
T2	Output transformer. Primaries: 8000Ω anode-anode centre-tapped. Secondary: 3 or 15Ω

Capacitors:


C1	220pF paper or mica
C2	25μF 25V electrolytic
C3	16μF 275V electrolytic
C4	0.1μF 400V paper
C5	2μF 12V electrolytic
C6	0.05μF 400V paper
C7	0.05μF 400V paper
C8	8μF 350V electrolytic
C9	32μF 350V electrolytic
C10	16μF 350V electrolytic

Miscellaneous:

L1	20H 20mA smoothing choke
MR1	E250/C50 250V 50mA half-wave metal rectifier
S1	Double-pole on/off switch (on VR1)

Aluminium chassis. Two B9A valveholders. Tag strip. Coaxial socket, grommets, nuts, wire, etc.

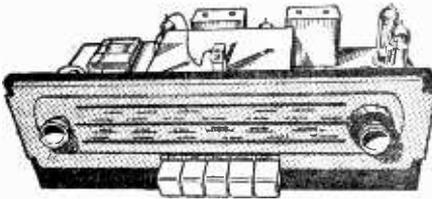BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/2 x 4 in. in 2 colours, predominantly gold. 200-250v. A.C. only. Pick-up, Ext. Speaker, Ac. E. and Dipole Sockets. Five Push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.; 200-550 M.; 88-98 Mc/s. Valves EZ80 rect.; EC81, EF89, EABC80, EL84, ECC85. 10 x 5 in. ELLIPTICAL SPEAKER 26/- to purchasers of this chassis. **TERMS:** (Chassis) £3.10.0 down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F. 12/6. Feeder 6d. per yard. **ALTERNATIVE DESIGN.** L.W. 1000-1900 M.; S.W. (9-15 Mc/s); M.W. 190-475 M.; V.H.F. 87-100 Mc/s. Gram position. Otherwise similar to above chassis. Price £15.15.0 (carr. paid). **TERMS:** £3.10.0 down and 6 monthly payments of £2.4.0. Circuit diagram 2/6



PUSH-PULL O.P. AMPLIFIER £5.5.0 (6/- Carr.)

Brand new 200-240 A.C. mains Base, treble and vol. controls. With valves EZ80, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 5 1/2 x 3 1/2 in. With op. trans. for 2-ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel"


LAFAYETTE BRAND TAPE

FULLY GUARANTEED AT RECORD LOW PRICES

NYLAE BASE		P.V.C. BASE	
5in. Double play, 1,200 ft.	15/-	5in. Standard play, 600ft.	3/6
5 1/2 in. Double play, 1,800ft.	22/6	5 1/2 in. Standard play, 850ft.	11/6
7in. Stand play, 1,200ft.	12/6	ACETATE BASE	
7in. Long play, 1,800ft.	19/6	5in. Stand. play, 600ft.	8/-
7in. Double play, 2,400ft.	25/-	5in. Long play, 900ft.	10/-
		5 1/2 in. Long play, 1,200ft.	12/6
		7in. Long play, 1,800ft.	15/-
TRIPLE PLAY		MESSAGE TAPES	
5in. 450ft.	12/6	3in. Stand. 150ft.	3/6
4in. 900ft.	22/6	3in. L.F., 225ft.	4/11
6in. 1,800ft.	42/6	3in. D.P., 300ft.	5/6
5 1/2 in. 2,400ft.	55/-	3in. Triple, 600ft.	14/-
7in. 3,600ft. (Unboxed)	75/-		

P. & P. 1/- extra per reel; 4 reels and over Post Free

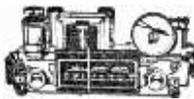SELF-POWERED VHF TUNER CHASSIS Covering 88-95 Mc/s. Mullard permeability tuner. Dims. 8 x 6 x 6 in. high. Valves ECC85 and 2-EF89's plus 2 diodes with EZ80 rectifier. Mains transformer. Fully wired and tested **ONLY £9.17.6** (carr. paid). Room dipole 12/6. Feeder 6d. per yard.



6-TRANSISTOR PORTABLE — Fully Built

The "SCALA" for only £7.10.6 carr. paid. 8 1/2 x 2 x 6 1/2 in. high. Choice of colours. Rexine. M.W. and L.W. Ferrite aerial Battery 2/9 extra. Printed circuit. Nicely styled. A professional job 3 1/2 in. speaker. Fully tunable M.W. and L.W. Superhet circuit.



BATTERY ELIMINATOR

For 4 Low Consumption Valves (68 range) 90r. 15 mA and 1.4v. 125mA 42/6 (4/- post). 200-250v. A.C. Also for 250mA 1.4 v. and 90r. 15mA at same price. Two separate units to replace existing batteries. 4 x 2 1/2 x 2 1/2 in. and 3 x 2 1/2 x 1 1/2 in.

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Delivery by return. Terms available on items over £5. Send 6d (stamps will do) for 20 page illustrated catalogue. C.O.D. 2/- extra.


ALL ITEMS GUARANTEED 12 MONTHS. VALVES 3 MONTHS. Regret overseas orders cannot be executed.

GLADSTONE RADIO

NOTE NEW ADDRESS:— (CLOSED)
66 ELMS ROAD, ALDERSHOT, Hants. MON. 11.00
 (2 mins. from Station and Busco). Aldershot 22240

"REALISTIC" 'SEVEN'

7 Transistor Superhet. 350 Milliwatt output. 4-inch speaker. All components mounted on a single printed circuit board size 3 1/2 x 5 1/2 in. in one complete assembly. Plastic cabinet, with carrying handle, size 7 x 10 x 3 1/2 in. External Socket for car aerial. Ferrite rod aerial. Price for the complete parcel including Transistors, Cabinet, Speaker, etc. and full Construction Data: **£5.19.6** P. & P. 4/6.

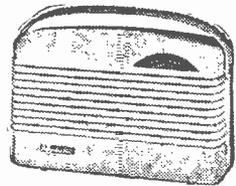

PP9 Battery 3/9. Data and instructions separately 2/6. Refunded if you purchase the parcel. Any parts supplied separately.



4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE

PRINTED CIRCUIT. 4in. x 2 1/2 in. 1 1/2 in. over transformers. Output for 8-ohm speaker. Suitable for microphone, record player, guitar and inductor. 9 volt battery required. Frequency range 100 cps to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Two types. 200 mw. 29/6; 1 watt. 41/- P. & P. 2/6.

SINGLE RECORD PLAYER USING EMI DECK AND PICK UP

4 speed, 200/240 v A.C. Valves, rectifier and ECL82. Cab. size 12 x 11 1/2 x 5 1/2 in. at trac. coloured imitation leather finish. Takes 7" & 10" records. £7.19.6 carr. paid.



ALTERNATIVE TYPE OF SINGLE RECORD PLAYER available, using BSE GUY motor and pick up on one plate. Valves UX85 and UCL82. Cab. size 13 1/2 x 13 x 5 1/2 in., red or blue rexine. Takes 7 in, 10 in. & 12 in. records. Price £8.9.6, carr. paid.

PROTECT AGAINST FIRE. AUTOMATIC FIRE ALARM

Sounds siren when air temperature reaches 125°F. Measures 8 x 2 1/2 x 1 1/2 in. Only £7/6 (Post 2/-). Or in Kit Form with calibrated Bi-metal contacts 27/6. (Post 2/-).

2 1/2 WATT AMPLIFIER

Our price **ONLY 66/-** (post 5/-); a few hundred only; valves **EF89** and **EL82** with metal rectifier: 6 x 4 x 1 1/2 in. high (5in. over **EL82**). Mains trans. and o.p. with vol. and tone controls; on-off; no-ex. input.

GRAMOPHONE AMPLIFIERS AND PLAYERS

1 1/2 watt type. With 6in. x 4in. speaker. Baffle 18 1/2 x 7 1/2 in. 200-240v. A.C. ECL82 and Rectifier. Tone and Volume On/Off switch. Two knobs. Ready to play, 49/6, post 5/-.
 4 watt type. Valves UX85, UF80 and UL84. 200-240v. A.C. Covered, baffle 15 1/2 x 7 1/2 in. (6in. speaker), 3 front controls: bass, treble, on-off/vol. 60/-, post 5/- Double wound mains transformer. Cabinet to fit either type with plain motor board £3 carr. pd. Complete record player in beautifully styled cabinet, fully built (NOT A KIT) £10.17.6, with UA14 4-speed autochanger, or with Garrard Antecolium 4-speed autochanger, £11.5.0.
 Single player in Cab., 13 1/2 x 13 x 5 1/2 in. B.S.B. Monarch 4-speed deck, £8.12.6

QUALITY PUSH-PULL OUTPUT AMPLIFIER

Chassis 10 x 7 1/2 x 7 1/2 in. high over trans. Used, guaranteed and in excellent order. New valves EZ40, ECC83 and 2 x EL41. 8 watta. Mains trans. tapped 200-250 volts. Op. Trans for 3, 8 or 15 ohms. Choke smoothing On/Off/vol. and tone controls. For Tuners, Record Players, etc. **£8.15.0** P. & P. 6/-. We can modify for Guitar input for 15/- extra.

TAPE RECORDER AMPLIFIER

Fully built. Front panel 12 1/2 x 3in. Chassis size 10 1/2 x 5 x 4in. Valves **EF89**, **ECC83** and **2EL84**. Controls (1) MIC. Vol. (2) Tuner/P.U. Vol. (3) Play back or monitor. (4) Tone. 2 jack sockets for Tuner/P.U. and MIC with superimpose. Separate power pack containing transformer and rectifier. For Colliaro studio deck only. Price **£8.14.0** (6/- P. & P.).

4-SPEED AUTOCHANGERS

BSR-UA14	22.10.0
GARRARD AUTOBLIM	25.10.0
STEREO	21.10.0
AUTOBLIM DE LUXE AT9	21.10.0
STEREO	21.10.0

Carr. 5/- each


13 x 8 in. LOUDSPEAKER 49/6 (post 2/6)

Three ohm. Ceramic magnet of latest type. BRAND NEW.

HEATER TRANSFORMER

Mains input giving 6.3v. 2 amp. Size 2 1/2 x 2 x 1 1/2 in. (2 1/2 in. over windings). 5/8 ea. Less 10% for 12, or 20% for 50. P. & P. 2/- for 1 to 6, post free more than six.

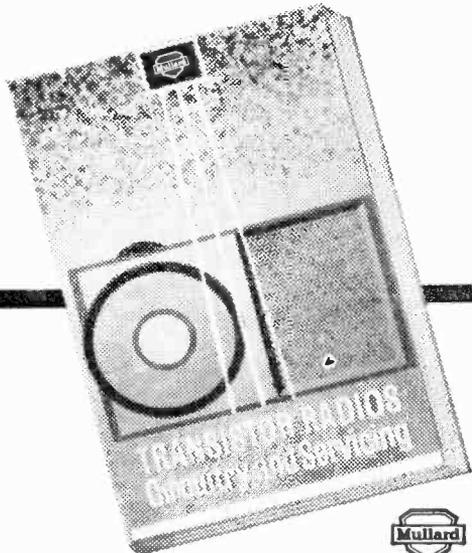A SIMPLE EXPLANATION OF TRANSISTOR RADIOS FOR THE APPRENTICE ENGINEER



Starting with a description of the basic properties of semi-conductors, the action of a transistor is explained in detail and without recourse to complex mathematics. The circuits used in transistor radios are described, and the techniques for servicing these sets are considered.

CONTENTS INCLUDE:

Semiconductor materials; Transistor action; Transistor circuits; Servicing, etc. In all, seven chapters with the emphasis always on practical considerations.

U.K. PRICE 5/-

Published by Mullard Ltd. Get your copy from your radio dealer or send remittance with direct order (Postage and packing 6d. extra).

MULLARD LIMITED - DEPT. B. - MULLARD HOUSE · TORRINGTON PLACE · LONDON WC1

MVM1021

"THE CONSTRUCTOR'S PARADISE"

BEAR HUDSON LTD.

63 GOLDHAWK RD, SHEPHERD'S BUSH, LONDON, W.12 Phone: SHE 2581
 Also at 11 JERDAN PLACE, FULHAM LONDON, S.W.6. Phone: FUL 3405



BEST OF ALL

B.H. "HI-FI 14" with integrated tone controls and mix facilities

A real break-through in hi-fi value! This superb amplifier designed by Dr. W. J. May incorporates valuable features including two high gain inputs, each with its own volume control to permit mixing! Multiple neg. feed-back loops can be varied. Robust design using quality components means dependability at all times. Frequency response—25-25,000 c/s ±2dB. Separate bass and treble cut and lift controls. Output 3 or 15 ohms. With punched chassis, elegant escutcheon plate, valves and instructions.

FANTASTIC VALUE AT THE PRICE!

Complete kit of parts as described **£9.9.0** Built and tested
 Fitting metal cover with handle 32/6. **£11.11.0**

TSL TRI-CHANNEL MIXER

Newly designed, with improved circuitry and fully transistorised. 3 separate input channels permit correct matching of high or low impedance inputs. Output suitable for every type of recorder or hi-fi amplifier system. Battery contained in rose-copper finished case. Noiseless in use. No distortion. A "must" for every serious listener. Superb value. **57/6**
 Leaflet available.

ALL SINCLAIR DESIGNS, MICRO-6, SLIM-LINE, X-10, ETC. IN STOCK.

"HIGH LIGHT" MAGNIFIER

Wide field, good magnification. With protective wallet cover for keeping in pocket. Useful for micro assembly work. Good value at **4/11**

VAST STOCKS OF COMPONENTS, BATTERIES, ETC. ALWAYS AVAILABLE

A SUPERB FM TUNER

Extra sensitive circuit for fringe and difficult areas. Variable tuner, should be used with nothing but the finest hi-f equipment. Has range power and stability. Full AFC, etc. For building or available complete. Leaflet available. **£14.2.1** Ready built and tested **£15.14.6 + 52/- P.T.**

TSL "AUDIO HEART"

A VERSATILE HI-FI TRANSISTOR AMP.
 Uses 2 x 811 transistors with 2 x OCS; in push-pull to give full watt output at 3-5 ohms. Input sensitivity 5 to 10mV for 1 w. out. Operating voltage—8V. 2" x 2.2" x 1.2". Response 60-15,000 c/s. ±3 dB This superb amplifier is characterised by exceptional stability, providing full output at up to 112 dB. Available ready built or for building yourself. Guaranteed. With transistors, transformer, etc., etc., and instructions. **BUILT IT FOR 52/6**
 Ready built and tested **59/6**

COMPONENTS - HI-FI - BOOKS - SERVICE
 24-HOUR MAIL ORDER SERVICE with all goods guaranteed.
 ● FREE POSTAGE on orders over 20/-; add 1/- postage if under.
 ● LOWEST PRICES FROM BULK PURCHASING AND MANUFACTURING.


BERNARDS BOOKS FOR TRANSISTOR CONSTRUCTORS

- 183** How to receive foreign TV programmes on your TV set using simple mods. **5/-** Post free
 - 184** Tested Transistor Circuits using Modules. **2/6** Post free
 - 185** Tested Shortwave Receiver Circuit using MATs. **5/-** Post free
 - 186** Tested Superhet Shortwave and Communication Receiver Circuits using MATs. **6/-** Post free
- Send for full catalogue of **Bernards Radio Books**. We stock the Parts You Need for the Circuits too!

"KEY-LITE"

A 'Must' for Motorists
MAKES IT EASY. A novel key-ring with modern style light attached (solid plastic case) for lighting up keyhole of car, doors, etc. Gives good light. Complete with battery (about 12 months' use). **10/6**

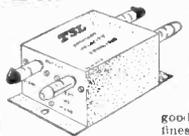MAKE YOUR CRYSTAL P.U. REAL HI-FI WITH THE TSL CONSTANT VELOCITY EQUALISER



This remarkable new TSL development enables quality almost as good as the finest professional magnetic pick-ups to be obtained from crystal or ceramic types. With it, even cheap record players become first-class instruments. With good equipment results are astonishing. Ideal for R.S.R., Collaro, Garrard and Acos. With plug for mono or stereo. 3 years' guarantee. Ready for use. Thousands sold. **30/-** POST FREE

TRANSISTOR OPPORTUNITIES

OC.71—special offer. 3/9; OC.45. 5/6; OC.44. 6/-; OC.169. 8/-; MAT 100 or 120. 7/9; MAT 101 or 121. 8/6; ADT.140 with 500 mc/s cut-off. 15/-.

Orders by post to BEAR HUDSON LTD., Dept. PW6, 63 Goldhawk Rd., London, W.12

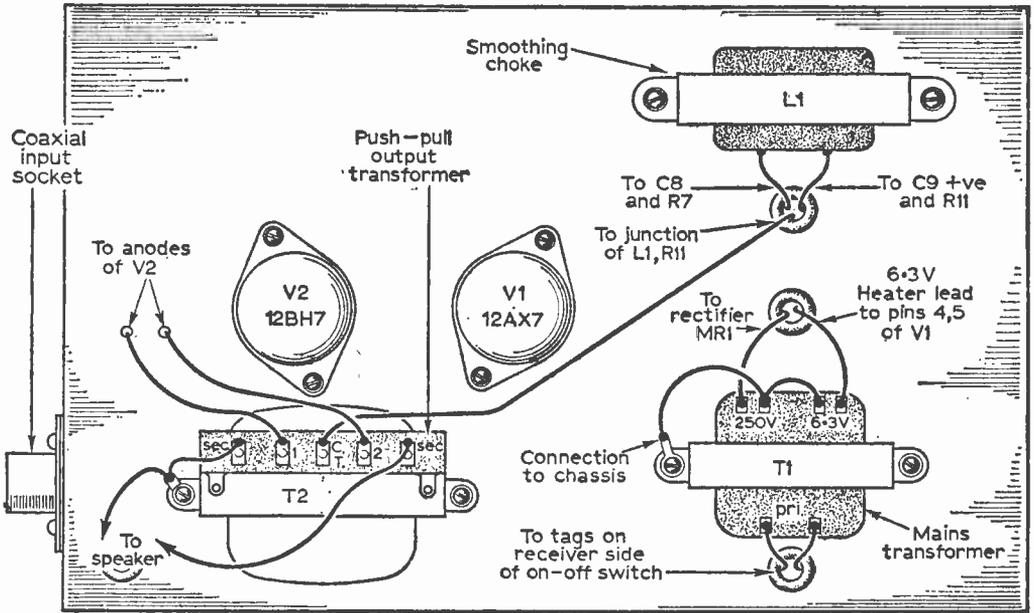


Fig. 2: The above-chassis layout of the amplifier

also R8 and R9 must be as accurately matched as possible or the output will be unbalanced, with distortion.

undecoupled and thus introduces some negative feedback.

The cathode bias resistor in the output stage is

—continued on page 647

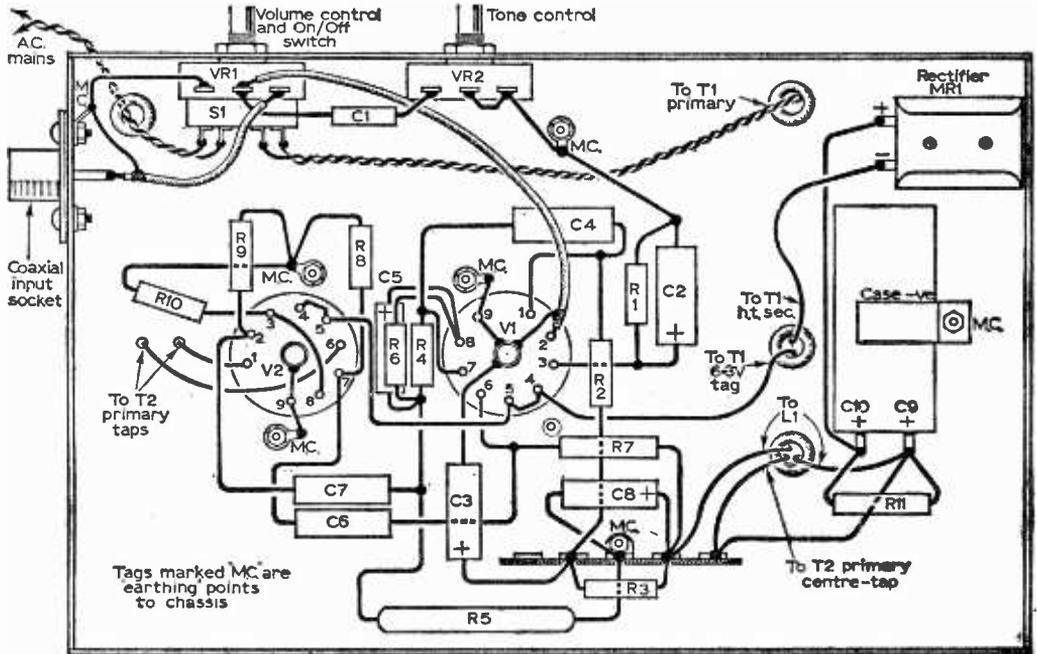


Fig. 3: The underchassis wiring diagram.



Practical Wireless Report

★ A summary of new models seen at Earls Court and the trade exhibitions around London, and notes on design trends and features.

★ The tables list new models only and do not necessarily represent the complete range of the makers concerned.

★ For details of all the new TV sets, refer to the November issue of *Practical Television*.

Earls Court, August 24-September 5, 1964

Transistor Portable Radios

TENDENCY of most manufacturers has been to concentrate on improved quality rather than a reduction in size. Several makers now market portables that are more applicable to a static site—fit to grace any sideboard—yet light and completely self-contained. Facilities available have been greatly extended.

There is no lack of tiny sets but most of these were to be found in the "splinter shows" of imported goods scattered around London. Lightest was a medium wave only matchbox sized receiver with an eight-transistor circuit, weighing only 4oz.

Most comprehensive was probably the *Perdio Marco Polo* with six short wave bands, long, medium and v.h.f. bands—the latter covering the international range—three aerials, two tuning controls, tuning meter, a.g.c., a.f.c., b.f.o., wide-range separate tone controls and a host of specialist facilities.

In general, more concentration was on band coverage with short waves (in readiness for the Olympics, some makers stated), v.h.f., Luxembourg bandspreading and even Radio Caroline marked on the dials of at least two of the models we inspected. New types of transistor have made for tighter tuning and consequently a better look to most dials and pointers.

Tape sockets and car radio aerial cut-out sockets are now accepted inbuilt features with most responsible manufacturers. Several makers featured the portable that doubles as car radio with the addition of a simple bracket and connector.

Micro-miniaturisation has entered the domestic radio field and was a feature of some *Stella* portables. Larger, flatter and more powerful loudspeakers have improved quality all round.

Of the "special" gimmicks one was the **STC** mains-operated charger and rechargeable battery which **K-B** were adding to their *Carioca* and **Regentone** to their *Regenteener* model at no extra charge for the show period. Value is put at 30s. Then there was the **G.E.C.** camera portable at 19gns., advertised as the first camera that receives Luxembourg—which could equally well be the first receiver taking colour pictures!

Camera-like, too, were some of the Japanese imports, while the German models and a few of the American range tended to be more severely functional and at least three of these claimed to be the best in the world.

Of these, the receiver which is probably of most interest to *Practical Wireless* readers is the **Braun** T1000, a 13-waveband portable with all the features and specifications of a communications receiver. Imported by Argelane Ltd. at £195.

Space limitation precludes a coverage of the many imported innovations. For example, **Sharp Sales and Service** had over 20 new models in their personal portable range from Japan. Practically every variation in price and facility could be seen in the foreign shows, one small pocket set even having provision for multiplex stereo! British manufacturers tended to be more conservative.

On our rounds of the splinter shows we several times overheard strong criticism by dealers, public and Press of the imports that could not be backed by adequate service information. One salesman dared to tell us that the model we queried was so cheap that it "was hardly worth repairing"; another stated that all repairs could be handled by the importing agents. *Readers should be warned—check on after-sales service facilities before buying.*

TRANSISTOR PORTABLE RADIOS

Model	Wavebands	Price	Notes
ACE Promenade	L.M.	10½ gns.	Carrying case and earplug £1 5s. extra.
ALBA 939 Olympic	L.M.S.	18 gns.	High "Q" ferrite aerial plus telescopic. 6 x 4 in. speaker Two-speed tuning for Lux. bandspread.
ACME Ajax Express TR330	L.M.S.	£14	Leather case, earpiece. Car ae. socket. Fine tuner.
BUSH TR112	L.M.	21 gns.	Car ae. socket. Tone control. 6 x 4 in. speaker. 7-transistor.
BANG & OLUFSEN Beolit 611	L.M.S.FM	£33 12s.	Ext. ae.: ext. L.S., Gram and T/Rec. sockets. 9 x 5 in. speaker. M/C meter (tuning or battery condition). Ferrite rod and whip aerials.
Biolit Teena	L.M.FM	18 gns.	1-4W output. 7 x 5 in. speaker. Sockets as 611.
COSSOR CR1341T	L.M.FM	24½ gns.	Push-button. 4in. speaker. Telescopic ae. 9 transistor.
CR7243T	L.M.S.FM	38 gns.	AFC. Light-flash battery state indicator. 4 in. speaker. 10 transistor.
DENHAM & MORLEY			
Sonocolor Clipper	L.M.S.	19½ gns.	Push-button. Tuning/Battery meter. 6 x 4 in. speaker.
Sonocolor Rhythm	M.L.FM	24 gns.	9 transistor. Omni-directional aerial. AFC. Tone control. 6 x 4 in. speaker.
Akkord Autotourist	M.L.S.FM	39 gns.	9 transistor. Tone control. Mains unit. Car ae. socket.
DANSETTE Hilton	L.M.	12½ gns.	Sin. L.S. earphone, tape, Ext. L.S. and car ae. sockets.
Sroller	L.M.S.	—	Prototype. Cut-out for car aerial.
Serenade	L. 2xM.	13 gns.	Prototype. Bandspread Lux. 5 in. L.S.
DECCA TP99	L.M.	15 gns.	5 transistor. Car ae., phone and tape sockets. Sin. speaker.
1125 (Intercontinentaf)	L.M.3S.	52 gns.	400mW output. 8 transistors. Bandspread tuning. Telescopic aerial. Phone. Tape. Ext. L/S sockets.
EKCO PT208	L.M.	13½ gns.	Lux. tuning. Personal socket.
PT426/L	L.M.	16 gns.	Lux. tuning. Tape, personal.
PT438	L.M.	9½ gns.	7-transistor. Available Oct.
CR926	L.M.	15 gns.	Car radio, with bracket, speaker baffle, suppressor.
PT424	L.M.FM	22 gns.	Ext. ae. Tape sockets.
EVER READY Sky Queen	L.M.	15 gns.	7-transistor. 4-in. L/S. 500mW Output. Car ae. socket.
EUROPA 25064	L.M.S.FM	37½ gns.	AFC on FM.
25041	L.M.FM	27½ gns.	1-3W output. Car switch.
FERGUSON 3124 "Auto-twin"	L.M.	17 gns.	9 transistor. Car/home set. Permeability tuner, P.B. selection.
3122 "Flight"	L.M.S.	12 gns.	7 transistors. Lux. band-spread. P.B. controls. Telescopic aerial.
3128 "Fieldsman"	L.M.FM	19½ gns.	Recessed controls. Telescopic aerial.
FERRANTI PT1127	L.M.	13½ gns.	Lux. bandspread. Personal skt.
FIDELITY 208	L.M.Lux.	13 gns.	Lux. Bandspread. P.B. switching. 7 transistor. 7 x 4 in. speaker. Car ae., tape, personal sockets.
Fulmar	L.M.	9 gns.	7 transistor. Skts as 208.
Galaxy	L.M.S.	12 gns.	7 transistor. 3 in. L/S. Car ae. socket. Tel. ae.
G.E.C. Transistomatic G822	L.M.	19 gns.	Combined camera. Built-in flash. Cartridge film loading. Lux. tuning.
G.818	L.M.	13½ gns.	Lux. bandspread. Car ae., ext. L/S, personal sockets.
GRUNDIG Transonette 70	M.S.	16 gns.	6 transistors. 800mW output. 5 in. L/S.
HACKER Herald RP30	L.M.	22 gns.	9 transistors. 8 x 5 in. L/S. 1-2W output. Independent tone controls. Car ae. Tape skts.
Herald RP31SW	L.M.S.	26 gns.	11 transistors. Tel. ae.
Sovereign RP18	L.M.S.FM	39 gns.	15 transistors. AFC on FM. 8 x 5 in. speaker. 1-2W o/p. Separate AM and FM tuners.
Mini-Herald RP17A	L.M.	17 gns.	Restyled Herald. 7 transistors. Carrying case £1 5s. extra.
INVICTA 8007	L.M.	14 gns.	Lux. easy tuning. Car ae. skt.
HMV/MARCONIPHONE			
2112	L.M.	12½ gns.	"Junior" model.
2120	L.M.S.	13½ gns.	"Junior" model.
2114	L.M.	15 gns.	
2116	L.M.FM	19½ gns.	
2122	L.M.S.	17 gns.	
KOLSTER-BRANDES KR010	L.M.S.	13 gns.	Lux. bandspread. 8 transistor. Tel ae. Tape, ae. skts.
KR012	L.M.S.	16 gns.	Lux. bandspread. 8 transistors. Slow-SW drive. P.B. control.
WPI1 Carioca	L.M.	10½ gns.	Battery-eliminator and rechargeable battery extra.
LEE PRODUCTS Hitachi TH;600	M only.	9 gns.	6-transistor, camera styling. 2½ in. speaker. Speaker grille tuning ring. Earpiece.
Hitachi WH837	L.M.S.	18 gns.	4 in. speaker. Tel. ae. SW. earpiece.
Hitachi W734	M.S.	26 gns.	Clock radio. Alarm. Auto time switch. Tel. ae. SW. Recording lead and earpiece.
Hitachi KH1002R	L.M.FM	25 gns.	10 transistors. Tel. ae. Recording lead and earpiece.
LOEWE-OPTA Freddy	L.M.FM	34 gns.	9 transistors. "K" version with SW in place of LV.
Auto-Lord	L.M.S.FM	45 gns.	10 transistors. Car bracket. AFC separate tone controls.
Ingelen Golf	L.M.FM	19½ gns.	9 transistor.
Marquis	L.M.S.FM	25 gns.	10 transistors.
Klarad Tourist	L.M.S.FM	27 gns.	10 transistors. Tone control.
720/730	L.M.3S	25 gns.	8 transistor. SW fine tuning.
MASTERADIO D518 "208"	L.M.	13½ gns.	Lux. Bandspread. 7 transistors. 5 in. speaker.
D516	L.M.FM	18½ gns.	Tape, car ae. phone skts.
PAM 5222	L.M.S.FM	24 gns.	9 transistor. 1W p-p output. 7 x 5 in. speaker. Tone control.
PERDIO Marco Polo	L.M.6S.FM	95 gns.	17 transistors. Continuous coverage 1.6Mc/s to 30Mc/s. M/C tuning indicator. Dial light. 6 x 4 in. speaker. Car ae. Sw. Two tone controls. AFC on FM.
PHILIPS 237 Riviera	L.M.	11 gns.	Micro-miniaturised. Camera styled.
336 Majorca	L.M.	16½ gns.	Slow-motion tuning. Tone control. 1W output.
130T Starfinder	L.M.	11 gns.	Micro-miniaturised.
390T Car Portable	L.M.	18½ gns.	Mounting Kit, inc. L/S.
PYE 1357	L.M.	13 gns.	Car ae. socket.
1359 Poppet	L.M.	5 gns.	Pocket portable, incl. strap case and earpiece.
RGD RR214 International	M.2S.FM	29 gns.	10-section Tel. ae. P.B. dial light. Ext. amp. skt.
REVELATION			
W. Wood & Son T20	L.M.FM	28 gns.	10 transistor. Car ae. Sw.
REGENTONE BT23 Regenteener	L.M.	9½ gns.	Battery charger and re-chargeable battery added free for period. Retail value 30s.

—continued overleaf

TV AND RADIO SHOW REPORT

TRANSISTOR PORTABLE RADIOS			
Model	Wavebands	Price	Notes
SOBELL World Ranger Mk. 2	L.M.S.	16½ gns.	Cartridge loading batteries. Top controls. Car ae. Sw.
5316	L.M.FM	18½ gns.	Unbreakable case. Tel. ae.
STELLA ST428T	L.M.	—	Edge-controls. Slow-motion tuning. Tone control.
SANYO BSP25 Cadnica	M.S.	23 gns.	Rechargeable batteries—mains-operated while charging. 8 transistor.
SHARP BXL377	L.M.	10½ gns.	Wrist-strap. Phone output.
FX-L09	L.M.FM	17 gns.	10 transistor. AFC
TELEFUNKEN Bajazzo TS	L.M.S.FM	55 gns.	Doubles as table model. Three separate tuners. 1W output as portable. 2.3W output as car radio. Wood case, choice of colours.
TOSHIBA 8L 688L	L.M.2S	17 gns.	8 transistors. 400mW output, 3½ in. speaker. Fine tuner.
8TL 463R	M.S.	13½ gns.	400mW output. 3½ in. L/S.
ULTRA 6118	L.M.S.	12½ gns.	Restyled version.

Table Radios

Many of the foregoing models can fairly claim a double life as portable and table radio so improved has styling become, especially in the home-built product. Yet there is still a demand for the conventional table radio and a few makers were showing tasteful wooden-cased receivers in addition to the leather, plastics and composition coverings in popular models.

One of the comparatively few sets in this category was a mains-operated set of luxury specifications displayed by **Philips**, while the imported models again swayed toward lavishness with opulent finish, multi-waveband, multiplex stereo decoders, battery or mains operation, multi-speaker systems *et al.*

Impressive, yet by no means prohibitive in price. The consumer is temporarily in the happy position of being wooed from all sides. Now is the time to go shopping, it seems.

Radiograms

Big talking point of the Radio Show was undoubtedly the move to "solid state" by many manufacturers of radiograms. The **Thorn Group** has made a special feature of this design, introducing the first fully integrated receiver-amplifier with transistorised chassis.

There are five transistors and four diodes in the receiver, those in the v.h.f. tuner being silicon planar types. Output stages, due to this innovation, can now be transformerless, frequency range is widened, quality improved and yet an output of

2½W per channel achieved, feeding 8 x 5in. speakers with high-flux ferrite magnets.

A number of other manufacturers included solid state models, some unwrapping their offerings at the very last moment so that dealers visiting the exhibition during the first two (reserved) days may have missed a few of the latest releases. Messrs. **Pye, Defiant, RCA Victor, B. and O.** all had quality radiograms with transistorised circuitry, and the range of models from all makers in the luxury class was wide and impressive.

Much more attention has been paid to the basic construction in design. Teak has taken its place in the forefront, with a solid wood styling made a feature of **Ferranti** models, in the TV and radiogram fields.

The long-awaited decision on stereo broadcasting was not announced as expected at showtime but a number of makers include stereo decoders and multiplex tuners, while others state that their models are easily convertible.

Tone controls are much more elaborate than of late and **RGD** have made a feature of their "low-level-listening" compensation which adds bass boost when the volume is reduced by the flick of a switch. The long, low style has been somewhat modified, but length is still a common feature in an effort to obtain stereo reproduction without the need of an extra loudspeaker.

Pye came out at the last moment with transistorised stereograms in a Robin Day design which even pronounced the speaker positioning in their styling.

—continued on page 640

TABLE RADIOS			
Model	Wavebands	Price	Notes
BUSH VHF/81	L.M.FM	25 gns.	7-valve. Mains. 6 x 4 in. speaker.
BRAUN T1000	13-band	£195	Communications-type. Mains or battery. Portable.
TS45	L.M.FM	—	Transistorised. Can be operated horizontally or hanging. To match L25 speakers. Multiplex fitted.
COSSOR 1102U	L.M.FM	28 gns.	Mains. 2W output. 6 x 4 in. L/S.
DENHAM & MORLEY Trier	M.FM.	14 gns.	Mains.
Violetta	L.M.S.FM.	21 gns.	Mains.
Symphonia	L.M.S.FM	25½ gns.	Mains.
DALTRADE Unitra Rumba	L.M.S.FM	25½ gns.	6-valve, mains.
FERRANTI 1103	L.M.FM	26 gns.	P.B. station selection FM. AC/DC mains.
GRUNDIG Malmo	L.M.S.FM	49 gns.	Press key operation. Lux. selector SW band. 5-valve mains. Light walnut cabinet.
Stockholm	L.M.S.FM	59 gns.	As Malmo, plus stereo decoder. Scandinavian Walnut finish.
LOEWE-OPTA Venus	L.M.S.FM	75 gns.	Hybrid—7 valves, 15 transistors. Two large stereo L/S. Multiplex.
Komet	L.M.S.FM	36 gns.	6-valve mains. Flywheel drive. 3W output, concert L/S.
PYE 11/11	L.M.FM	—	Transistorised. Stereo. Two 7 x 5 in. L/S.

RADIOGRAMS

Model	Wavebands	Stereo/Mono	Price	Notes
ACE Venezia AG636	L.M.S.	S.	69 gns.	Drop doors and lids at each end. BSR deck.
ALBA 8000	L.M.S.	M.	36½ gn.	Boat-shaped sapele cabinet. Garrard deck.
8001/S	L.M.	M.	36 gns.	Garrard Autoslim deck.
8002/S	L.M.S.	M.	39½ gns.	Garrard Autoslim deck. Bass and treble correction.
B. & O. Beomaster 611	L.M.S.	S.	49 gns.	BSR UA16 deck. Balance.
	L.M.S.FM	S.	—	Transistorised. Multiplex. Automatic or Single Transcription player. Record storage cabinet. Meter-type indicator.
COSSOR CR1506A	L.M.	M.	41 gns.	Garrard Autoslim deck. 8 x 5 in. speaker.
CR1508A	L.M.S.FM	S.	89 gns.	Garrard Autoslim deck. Two 10 x 6 in. speakers.
DANSETTE RG65	L.M.	M.	29 gns.	Table-gram.MW bandsread. 8 x 5 in. speaker. BSR UA15. Diamond stylus.
DENHAM & MORLEY Concerto	L.M.S.FM	M.	39 gns.	Eiac changer.
DECCA 575SRG	L.M.FM	S.	77 gns.	Garrard AT5 with Deram pickup. Two 8 x 5 in. speakers in acoustic enclosures. Matt walnut.
700 Mk. II	L.M.S.FM	S.	—	Transistorised.
707	L.M.S.FM	S.	83 gns.	Garrard AT6 deck with Deram cartridge. Two 8 x 5 in. speakers, plus two 3-in. tweeters, with direction control.
800	L.M.S.FM	S.	—	Decca fss pickup.
DR888	L.M.S.FM.TV	S.	—	Combined Gram/TV. 405/625 lines, UHF tuner, Transistorised Gram. Tape Playpack. Deram head fitted. 5W per channel. 10 x 6 plus 4 in. unic per channel.
DEFIANT AF75	L.M.FM	M.	50 gns.	Transistorised. Garrard AT5 deck. Low-boy cabinet.
AF85	L.M.FM	S.	65 gns.	As 75, with extra channel and different styling.
AF87	As 85, with Tola veneer finish.			
DYNATRON Buckingham RG37T	L.M.2S.FM	S.	129 gns.	Available in Scandinavian and Queen Anne styling. Garrard AT6 with Sonotone cartridge. Adaptable M-plex. Tape compartment—4T deck. Both 7½W per channel.
Carlton RG36	As RG37, with period cabinet		175 gns.	Compact. AT6. teak cabinet.
Dorchester RG35	L.M.FM.	S.	94 gns.	—
Hambleden	As RG37, Queen Anne cab.		165 gns.	—
Savoy	As RG37, Chippendale cab.		165 gns.	—
Richmond RG34T	As RG35		99 gns.	Satin Walnut, or oiled teak.
Henley	As RG35, but with 12W push-pull output, styled in teak or walnut		109 gns.	
EKCO SRG431	L.M.S.FM	S.	87 gns.	Garrard deck.
SRG439	L.M.S.FM	S.	69 gns.	7-valve. Tone-compensated V/C.
FERRANTI SRG1120	L.M.S.FM	S.	88 gns.	6-valve. BSR UA15 deck.
SRG1132	L.M.S.FM	S.	69 gns.	Two 8 in. speakers.
SRG1131	L.M.S.FM	S.	58 gns.	BSR UA15 deck. 8W o/p.
FALCON Symphony 66	L.M.S.	S.	39½ gns.	Garrard Autoslim. 6W o/p.
Symphony 77	L.M.S.FM	S.	45 gns.	Controls on scale.
Harmony	L.M.S.FM	S.	51 gns.	7-valve. Press button.
Hi-Life 606	L.M.S.	S.	54 gns.	7-valve, press-button. B.S.R. deck.
Hi-Life 707	L.M.S.FM	S.	60 gns.	6-valve. B.S.R. deck.
F43	L.M.S.	M.	29½ gns.	6-valve. B.S.R. deck.
FERGUSON 3320	L.M.FM	S.	75 gns.	B.S.R. deck.
3324	L.M.	M.	33 gns.	Transistorised. B.S.R. deck. Slide top and drop front.
FIDELITY RG30	L.M.FM	S.	66 gns.	Compact.
G.E.C. G979	L.M.S.FM	S.	69 gns.	B.S.R. Deck. Two 9 x 6 in. speakers.
GRUNDIG KSS40	L.M.S.FM	S.	119 gns.	4-speed changer. Large record storage compartment. AG1025 changer. Two 11 x 7 in. and two 2½ in. speakers.
RG550	L.M.S.FM	S.	155 gns.	AG1025. Tape recorder compartment.
KSS60	L.M.S.FM	S.	185 gns.	Stereo decoder. Reverb Unit.
KSS80	L.M.S.FM	S.	275 gns.	As before. Dual 1009 changer, with variable speed. Space for TM45 tape dec. 10 L/S.
HACKER Serenade RG16	L.M.FM	M.	75 gns.	Consolette. Garrard AT6. 10 x 6 in. and two 5 in. L/S.
KOLSTER-BRANDES KG021	L.M.S.FM	S.	56 gns.	Tone-compensated V/C. B.S.R.
KG022	L.M.S.FM	S.	69 gns.	Garrard Deck. Long-line cab.
VG20	L.M.S.FM	S.	59½ gns.	B.S.R. deck. Two 10 x 6 in. L/S
KG026	L.M.S.FM	S.	129 gns.	Dual deck. "Prima Ballerina."
HMV 2316	L.M.S.FM	S.	145 gns.	6 L/S. 2 gm. pickup with diamond stylus. 5W output per channel. Transistorised.
2312	L.M.S.FM	S.	83 gns.	Two L/S.
LOEWE-OPTA Premiere Stereo	L.M.S.FM	S.	165 gns.	Hybrid circuit. 5 valves 17 transistors. Stereo decoder. Man. Auto switch.
Kora-Stereo	As above.	—	159 gns.	As above.
Oslo-Stereo	L.M.S.FM	S.	85 gns.	FM Decoder. 8 valves, 3 transistors.
Paloma-Luxus	L.M.S.FM	S.	139 gns.	5 valves, 15 transistors.
Clivia Luxus	As above.	—	125 gns.	As above. 4 speakers.
Mallorca	L.M.S.FM	S.	115 gns.	Stereo decoder. 4 speakers.
Zurich	L.M.S.FM	S.	—	Stereo decoder. 2 single-ended outputs, 2W per channel.
MARCONIPHONE 4310	L.M.S.FM	S.	83 gns.	Transistorised.
4304	L.M.FM	S.	53 gns.	Valve-operated. 6W push-pull per channel.
MURPHY A891	L.M.FM	S.	62 gns.	Two 10 in. L/S.
A881	L.M.FM	S.	89 gns.	Four speakers.
A682SR	L.M.FM	S.	—	Garrard Autoslim with Ronette pickup.
MASTERADIO D572	L.M.	M.	36 gns.	Gold-straw grille.
D573	L.M.FM	S.	66 gns.	Paldao cabinet.
McMICHAEL MS207	L.M.FM	S.	66 gns.	Two 8 x 5 in. L/S.
MS208	L.M.FM	S.	—	Paldao cabinet.
INVICTA 8101	L.M.FM	M.	43 gns.	Sliding Tambour door.

—continued overleaf

TV AND RADIO SHOW REPORT

Model	Wavebands	RADIOGRAMS		Price	Notes
		Stereo/Mono	Price		
PAM 5208	L.M.S.FM	S.	89 gns.		Garrard 3000LM, Sonotone cartridge, diamond stylus.
5207	L.M.FM	S.	63 gns.		Garrard Autoslim, Two 8 in. speakers, and tone balance.
PHILIPS 431	L.M.	M.	42 gns.		Less than 20 in. high.
540	L.M.FM	S.	65 gns.		Normal facilities.
541	L.M.FM	S.	79 gns.		Transistorised.
536A	L.M.S.FM	S.	129 gns.		Side and front-facing speakers.
PYE 1207	L.M.S.FM	S.	105 gns.		Transistorised. Robin Day styling.
1203	L.M.S.FM	S.	87 gns.		8 valves. Garrard AT6.
1205	L.M.FM	S.	61 gns.		Small proportions.
REGENTONE SRG25	L.M.S.FM	S.	89 gns.		Cocktail gram. B.S.R. UA16. 9-valve chassis.
RGD 211 De Luxe	L.M.25.FM	S.	115 gns.		Low-listening boost.
STELLA ST320	—	—	—		Narrow styling with drop flap record player.
ST239	—	—	—		Twin elliptical speakers.
SOBELL SG678	L.M.FM	S.	66 gns.		Cocktail cabinet. B.S.R. deck. 6 valves. Two 8 x 5 in. speakers.
SG679	L.M.S.FM	S.	69 gns.		Balfour deck. Drop front and slide top.
ULTRA 6312	L.M.S.FM	S.	77 gns.		Garrard Autoslim deck. 2½W output per channel.
TELEFUNKEN Bayreuth 2584	L.M.S.FM	S.	239 gns.		TW504 changer, 14 valves. Multiplex. Two 13½ x 7 in. woofers, 4 medium-treble speakers. AFC on FM.

Of the imported models, super-de-luxe designs caught the attention at prices in the "millionaire bracket" and with many special features. **Saba Electronics**, the West German firm, returned to the British market with a super-gram priced at 298gns.

Only a little cheaper was the **Bosch New York** with eight speakers, 15 valves, Garrard Lab. A deck, built-in stereo decoder, a.m./f.m. coverage and 7W output.

Grundig, mounting their own opulent show at the Hilton Hotel, showed a 365gns. stereogram with inbuilt TV (23in.) and space for a tape recorder deck.

Not to be outdone, **Philips** featured their TV/gram, the *Combinado*, incorporating a five-waveband stereogram and 23in. TV chassis and using the AG1025 deck with push-button controls and diamond stylus.

In contrast the sister-firm, **Cossor**, had a four-band stereogram, the CR1508A, only 13in. from front to back with the playing deck mounted on a drop-flap, while **Stella** showed their "flat-dweller's model" which is only 9in. deep at the top.

We were interested in a new British record deck by **Balfour Electronics** fitted in the **Sobell SG679**. Well known in the export field, this auto-changer makes its first appearance on the **G.E.C.** stand.

In the lower price range an attractive range of new designs under the **Falcon** brand was shown by John Street, and the **STC Group** had representative models under the **Ace**, **Regentone** and **RGD** names.

Alba brought out new show releases, one of them, as stated above, at the very last moment. In addition many of the established models were shown by **Bush**, **Pam**, **Decca** and, as ever, **Dynatron**. One of the latter had the rare 4T tape deck incorporated, but no news is yet given of this deck being used in a separate tape recorder.

Services

Of particular interest to *Practical Wireless* readers—concentration at Earls Court on radio and electronics as a career. On Stand 18 a cinema had been arranged, showing a specially produced film to tell youngsters of the opportunities in

graphic emphasis. Special staff were constantly on hand to explain apprenticeship schemes and training.

B.R.E.M.A., looking ahead, are sponsoring the training of engineers with a deeper basic grounding in the trade. Developments are outstripping general information and special training is a must for the future.

The larger firms are well aware of this and back the approach wholeheartedly. Making some contribution toward this, **Philips** were holding a novel competition for youngsters on Stand 61, where their toy kits were used to test lads (and lasses) in speed and dexterity of simple circuit wiring.

Service aids were also a feature of the **A.E.S.** stand, where the very fine tool kits shared a place of honour with two new ideas, the plastic "fakir's bed" to act as a simple jig for small printed circuits and the aspirated soldering iron which sucks solder from a joint as the bit melts it. Constructors with experience of printed circuit techniques will realise the value of this device.

Constructors, too, were welcomed on the **Heathkit** stand, where much of their latest equipment was shown and a staff was always ready with advice.

Dealers and their engineers were well served with advice and demonstrations within the closely guarded confines of the dealer-only stands. Indeed there was said by one cynic to be more of interest here than publicly on show! **Brimar**, **Mullard**, **R.T.S.**, **A.E.S.** and others had some intriguing exhibits.

On the **Cossor**, **Stella** and **Philips** stands, for example, we were shown some very attractive tape recorder designs not yet for general release, their showing being restricted by the ban on goods not of British manufacture, a ban which many critics consider has killed the Radio Show.

Dead, they may think it, but this year's showing was evidence that the British radio industry is far from lying down.

Details of all the new Record Players and Tape Recorders will be published in the December issue.

INCREASE YOUR KNOWLEDGE



CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING,
INDUSTRIAL TELEVISION, RADIO AND
TELEVISION SERVICING, ELECTRONICS,
COMPUTERS AND PROGRAMMING,
ELECTRONIC TECHNICIANS, SERVICE MECH-
ANISMS, TELEMETRY, COLOUR TV
INSTRUMENTATION, AND PRINCIPLES OF
AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. Telecommunication Techns' Cert.
C. & G. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificates. Radio Amateurs' Exam.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver and Transistor Portable, Signal Generator and High Quality Multimeter. At the end of the course you have invaluable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Courses open a new world to the keen amateur.

RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialised knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examinations and ICS technical course in radio, television and electronics. PLUS details of over 150 specialised subjects.

**YOUR
CAREER
IN**

ELECTRONIC ENGINEERING
RADIO AND TELEVISION
ENGINEERING
ELECTRICAL ENGINEERING

INTERNATIONAL CORRESPONDENCE SCHOOLS - LONDON


PLEASE SEND FREE BOOK ON _____

NAME _____

ADDRESS _____

OCCUPATION _____ AGE _____

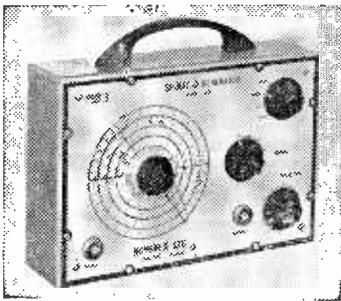INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEX HOUSE, PARKGATE RD, London SW11



Wide-range Transistorised
SIGNAL GENERATOR—Model 27

Range 150 Kc/s to 350 Mc/s

- ★ Accuracy better than 2%
- ★ Directly calibrated
- ★ Battery operated
- ★ Compact and light

£9.12.3

with test lead and battery.
Post and Packing 3/6 extra.

H.P. 48/- deposit and 27/- monthly.

Trade and Export Enquiries Invited

NOMBREX INSTRUMENTATION

Wide range Transistorised AUDIO GENERATOR—Model 63

Range 10—100,000 c/s

- ★ Laboratory Standard Specifications
- ★ Sine and Square Wave
- ★ Direct Frequency Calibration
- ★ Accuracy and Low Distortion
- ★ Calibrated Output Voltage
- ★ Battery Operated and Compact

£16.15.0 complete with test lead

Battery 2/3. Post and Packing 3/6.
H.P. 4 gns. deposit and 41/- monthly.



Wide-range Transistorised C.R. BRIDGE—Model 62

6 Ranges: 1Ω to 100M
1pF to 100μF


- ★ Visual null indicator
- ★ Power factor check
- ★ Electrolytic leakage test
- ★ Battery operated

£8.7.3

including battery.

Post and Packing 3/6 extra.

H.P. 40/- deposit and 24/- monthly.

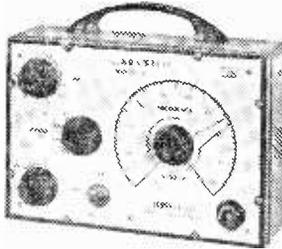

S.A.E. for full technical leaflets

NOMBREX LTD. Instruments Division

ESTUARY HOUSE, CAMPERDOWN TERRACE
EXMOUTH, DEVON. Phone: 3515



The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60/40 in 22 s.w.g. for printed circuits, transistors, etc.

SAVBIT ALLOY
saves wear on soldering iron bits

SAVBIT SIZE 1 CARTON

Contains approximately 37 feet of 18 s.w.g. SAVBIT. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.



5/- each

THE HANDY DISPENSER

Easy to find in the tool box—simple to use. Virtually a third hand for tricky soldering jobs. 14 feet 5-core 18 s.w.g. ERSIN MULTICORE SAVBIT alloy in a continuous coil used direct from free-standing dispenser. **2/6 each**



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex. **3/6 each**



LK ELECTRONICS OFFER 2,000 TV RECEIVERS ALL FAMOUS MAKES SLIMLINES AND STANDARDS

17" - 19" - 21" - 23"

These Sets are Warehouse soiled. Very Clean and all working.

Orders in Strict Rotation

17"

£10.0.0 each

19"-21" £12-10-0 23" £15-0-0

Carriage 2/-

Personal Callers Welcome

LK ELECTRONICS

17, GILLINGHAM ROW
LONDON, S.W.1.

Vic 5091

MULTICORE WORKS - HEMEL HEMPSTEAD - HERTS. (BOXMOOR 3636)

CHMS 24

WITH a t.r.f. receiver of the type described here there is only one tuned circuit. This simplicity is the great advantage of the t.r.f. circuit over the superhet, as there are no aerial, oscillator, and intermediate frequency circuits to trim or align. There is also some simplification in wiring, compared with a superhet.

The circuit for this receiver is shown in Fig. 1 and it will be seen that VC1, with the associated ferrite rod windings, forms the only tuned circuit. No reflexing is employed, Tr1 being the first r.f. amplifier, Tr2 the second r.f. amplifier, and D1 the diode detector. A conventional audio amplifier follows, with Tr3 as first a.f. stage, Tr4 as driver, and Tr5 and Tr6 in the push-pull output stage. Current drain is approximately 10mA with no signal or at very low volume, rising from 20—40mA on peaks, at good volume. A non-miniature 7.5V battery is used, and has a very long life.

The circuit was primarily intended for local station reception, but a fair selection of stations could be received quite well, including some of the more powerful continental transmitters. A telescopic aerial rod is provided, for use when necessary, but it is suggested this item is omitted until the receiver has been tested. To increase sensitivity, fixed regeneration may easily be added, including Tr1 and Tr2, but this is best omitted until it has been found that the receiver performs well without it.


Construction

The receiver is built on an insulated panel approximately 8½ in. x 6 in., but the actual size is not very important. The panel has an aperture to suit the loudspeaker, as in Fig. 2. A further panel

by F. G. Rayer

A T.R.F. Transistor Portable

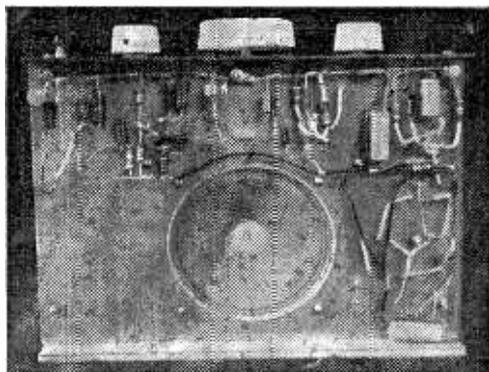A SIX - TRANSISTOR
MEDIUM AND LONG -
WAVEBAND RECEIVER



Above: A view of the front of the finished receiver. A rear view is shown at the top of the page.

8½ in. x 3 in. is secured with angle brackets, and drilled for volume control, tuning capacitor, and wavechange switch, as in Fig. 3. To accommodate components, the 8½ in. x 6 in. panel is set back about ½ in. from the edge of the 8½ in. x 3 in. panel.

A length of 20s.w.g. tinned copper wire is run between tags, as in Fig. 2, to form the positive line, and capacitors and resistors are soldered to this, as indicated in this diagram.

Transistor leads are left nearly full length, and pass through small holes, as in Figs. 2 and 3. If maximum possible volume is required, Tr5 and Tr6 should be held in cooling clips. Good volume can be maintained without these clips, however.

Two mounts for the ferrite rod are cut as in Fig. 3. The aerial connections are numbered in Figs. 1, 2 and 3. Tag 1 on the aerial is the beginning of the m.w. winding. Tag 2 is the junction of the m.w. and l.w. sections, while tag 3 is the end of the l.w. winding. A single base coupling winding is employed, tag 4 going to Tr1 base, and tag 5 to the junction of R1 and R2.

The driver transformer T1 has primary wired to Tr4 collector and negative line. The secondary centre-tap goes to R17 and R18, and remaining secondary leads to Tr5 and Tr6 base wires. The output transformer T2 has centre-tap wired to negative on C12, and remaining primary leads to collectors of Tr5 and Tr6, as in Fig. 2.

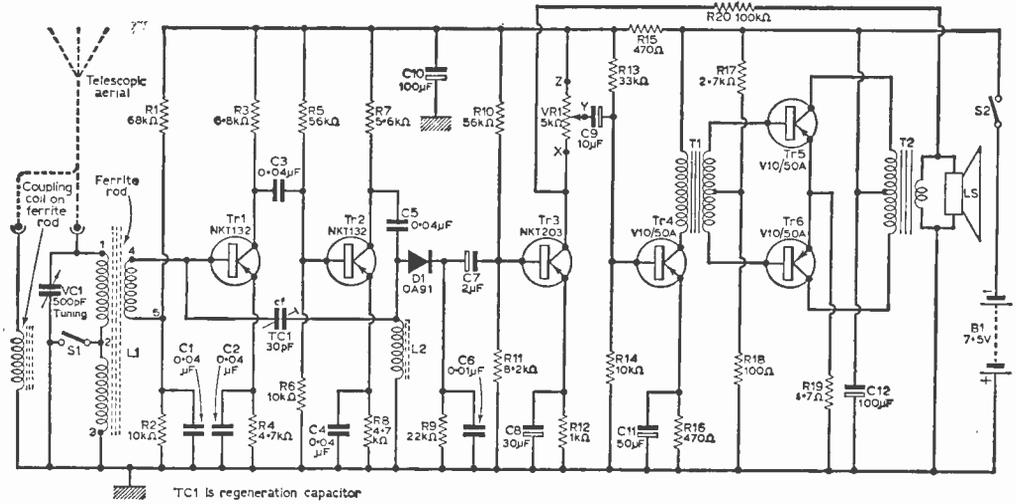


Fig. 1: The dual-wave t.r.f. receiver circuit.

The receiver should first be tested with R20 disconnected. The loudspeaker is then wired to positive line and R20, as in Fig. 3. If there is a

reduction in volume, these connections are correct. But if howling begins, the leads from R20 and positive line to the loudspeaker should be reversed.

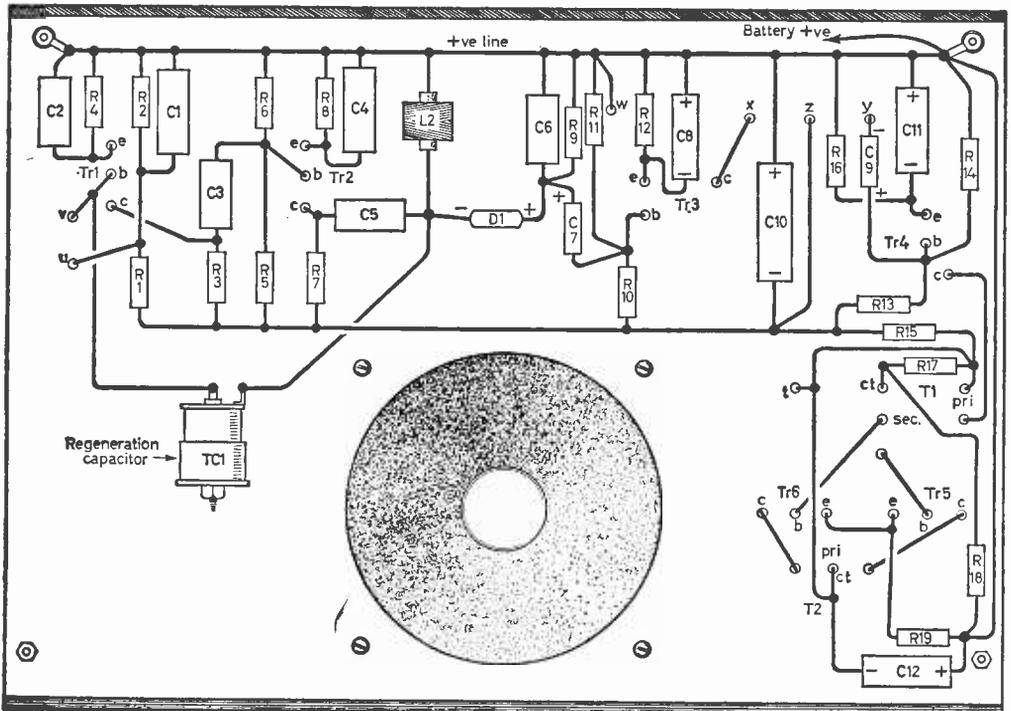


Fig. 2: Component layout and wiring on the front of the panel.

COMPONENTS LIST

Resistors:

R1	68k Ω	R11	8.2k Ω
R2	10k Ω	R12	1k Ω
R3	6.8k Ω	R13	33k Ω
R4	4.7k Ω	R14	10k Ω
R5	56k Ω	R15	470 Ω
R6	10k Ω	R16	470 Ω
R7	5.6k Ω	R17	2.7k Ω
R8	4.7k Ω	R18	100 Ω
R9	22k Ω	R19	4.7 Ω
R10	56k Ω	R20	100k Ω

All 10%, $\frac{1}{4}$ W carbonVR1 5k Ω potentiometer with s.p. switch (S2)

Inductors:

- L1 Dual wave ferrite rod with coupling winding
L2 R.F. choke 10-20mH

Transformers:

- T1 Push-pull driver transformer
T2 Push-pull output transformer

Capacitors:

C1	0.04 μ F paper	C7	2 μ F electrolytic
C2	0.04 μ F paper	C8	30 μ F electrolytic
C3	0.04 μ F paper	C9	10 μ F electrolytic
C4	0.04 μ F paper	C10	100 μ F electrolytic
C5	0.04 μ F paper	C11	50 μ F electrolytic
C6	0.01 μ F paper	C12	100 μ F electrolytic
TC1	see text		
VC1	300pF air spaced variable (any value 250 to 350pF will suit)		

Transistors:

Tr1	NKT132	Tr4	V10/50A
Tr2	NKT132	Tr5	V10/50A
Tr3	NKT203	Tr6	V10/50A

} matched pair

Miscellaneous:

- D1 OA91. S 1s.p.s.t. rotary switch Loudspeaker 3 $\frac{1}{2}$ in. dia. 2-3 Ω . 7.5V battery. Telescopic aerial. Two lin. knobs. One 2in. knob. Paxolin sheet: 8 $\frac{1}{2}$ in. x 6in.; 8 $\frac{1}{2}$ in. x 3in. Plywood $\frac{1}{8}$ in. x 2 $\frac{1}{2}$ in. Angle brackets, bolts, etc.

Aerial

If the telescopic aerial is required, it is mounted with long 6B.A. bolts fitted with extra nuts, so that it can be extended vertically. The simplest method of connecting the aerial is to take a lead from it to tag 1 on the rod aerial, as in Fig. 1. This was found

to be satisfactory. It does mean, however, that hand capacity effects, due to proximity with the aerial, slightly upset tuning. This may be overcome, if wished, by fitting an aerial coupling winding on the centre of the ferrite rod. This

—continued on page 666

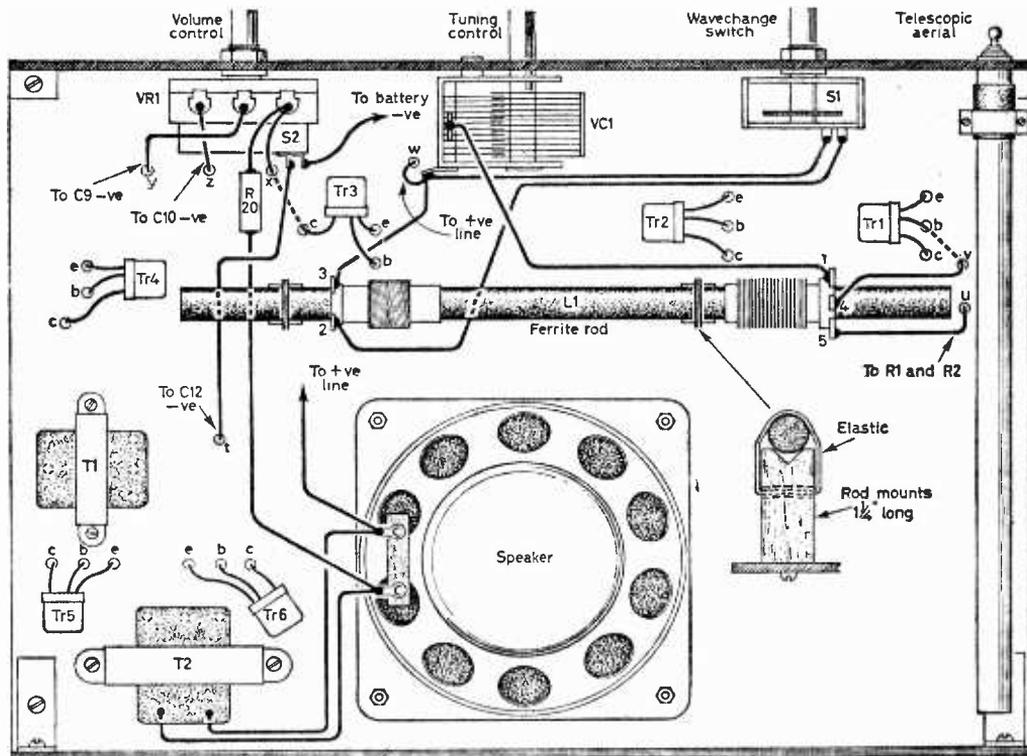


Fig. 3: The rear of the panel on which side most of the larger components and the transistors are mounted.

on the Short Waves

MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

The Broadcast Bands—by John Guttridge

MOST stations are prepared to give something in return for a good reception report. This normally takes the form of a verification or QSL card, although some stations send a letter instead. Stations not issuing verification cards or letters are not usually interested in receiving reception reports.

TYPICAL QSL CARDS

QSL cards normally take the form of a design or perhaps photograph on one side with verification details on the reverse. Several of the short wave clubs issue certificates to members who can produce various sets and combinations of cards.

Often these clubs insist that the cards bear certain details before they will accept them for certificates. For example, the International Short Wave Club says that a card is not a proper verification unless it contains the date, time and frequency involved.

From time to time stations issue special cards to mark special occasions—the opening of a new transmitter or studio perhaps. These are worth obtaining as only a limited number are issued.

Several stations, especially Latin American ones, also send colourful pennants to listeners submitting reception reports. Regular reporters are occasionally even more favoured by stations, gifts of items such as gramophone records being made sometimes.

Here are details of the verifications given by a few stations. *Radio Voice of the Gospel* in Ethiopia sends a card with a simple design and the station's name and address on one side. On the reverse there is space for time and frequency details **only**, although the date is normally written in. Also on the reverse of the card there is a mass of technical information about the station.

On the front of the card produced by the Canadian Broadcasting Corporation's *International Service* there is an outline map of Canada which shows transmitter and studio location pictorially. The back of the card is printed in English and French with space for frequency, time and date. A separate card is issued for correct reports on Northern Service transmissions.

Radio Havana, Cuba, uses a colour picture postcard printed on the reverse in English and French. Frequency and date are the only details given. A pennant is also sometimes sent by this station.

One of the most disappointing cards is that

produced by *Radio Pakistan*. This has remained unchanged for several years and carries a simple design but no verification details.

One of the most colourful verifications comes from *Radio Clube de Goiania* in Brazil which sends several picture postcards, a letter of verification and a pennant.

HAPPY BIRTHDAY!

Just celebrating its first birthday is the Sudbury World Communications Club. The club publishes a monthly called "*Contact*" and has a subscription of 10s. One service offered to members by this club is the free supply of report cards. Anyone interested in joining should contact the club secretary, Mr. D. J. Wilson, at 23 Newman's Road, Sudbury, Suffolk.

RADIO CANADA CLUB

A different kind of short wave club is that run by *Radio Canada*. To qualify for membership you must send five separate reports of any Radio Canada short wave transmission to the Radio Canada Short Wave Club, C.B.C. International Service, P.O. Box 6000, Montreal, Canada. These must be numbered from one to five consecutively at the top.

To remain a member you must send in at least one reception report every two weeks. Members receive a membership certificate, pennant, stickpin and Radio Canada short wave programme schedule.

DX NEWS

D. Greer, of Billingham, County Durham, reports good reception of *Cairo Radio* in English between 2132—2227 on 9,495/11,915. He says the station verifies reception reports with a QSL card and a programme schedule. The station's address is U.A.R. Broadcasting and TV, Maspero, Cairo, Egypt.

Still in the Middle East, news comes from *Kol Israel*, Jerusalem, Israel, that its English transmission now includes a Hebrew language lesson. It is aired on Sundays at 2015 on 9,009.

Transmitting to the Middle East between 1100 and 1400 G.M.T. is the *Osterreichischer Rundfunk*, Wien IV, Argentinierstrasse 30a, Austria. This transmission is on 17,750. Other frequencies which can be heard in Europe are 6,155/245/9,770/11,785.

According to *Radio New York Worldwide* the

Trans-World Radio station at Bonaire in the Netherlands Antilles is now testing on short wave. Frequencies reported are 9,715/11,855/15,435.

In common with a number of other short wave stations Radio New York Worldwide itself made

several frequency changes on September 6. Transmissions to Europe is from 1200—1815 on 17,760/15,440, 1815—1830 on 15,440 and 1830—2145 on 11,875. The beam to Africa is from 1200—1930 on 17,760 and 1940—2145 on 15,290.

The Amateur Bands—by David Gibson G3JDG

IT is indeed strange that DX can be heard and worked on 14Mc/s, and that there is a great deal of activity on 144Mc/s, yet 28Mc/s in the middle appears to be far more "allergic" to the sun's activity than the bands on either side of it.

However SWLs and amateurs are urged to check 10 metres as it is already beginning to stir, and reports of EDX and DX are getting more frequent every week; even W's have been heard! One Sunday morning brought DL7QB5 & 6, YO5NR 558 and SP8AOV 589. (Numbers signify the R.S.T. reports).

For the vigilant ones a good DX'er to listen for is 5N2JKO. Heard but not worked—VQ2AP, HZ2AMS, 5B4CZ, 5N2JKO. Also of interest is the beacon station GB3LER and 29.00Mc/s, situated at Lerwick in the Shetland Isles. A date for your diary is Dec 5th to 6th which is the R.S.G.B. 21/28Mc/s phone contest.

"TWENTY"

The 14Mc/s band at the moment is fading out from about 0100 on, although some good DX comes in during the day and evening. Notably loud signals (5+7 to 5+9) were OA4KY, KZ5KY, YSIO, Ti2IO, Hi8WSR, KG4AM, CN8GB, HK4EB, VP7NS, HP1MN, WE1FY and YV5A1P. KG4AM, incidentally, is the American base at Guantanamo in Cuba. All the above on 'phone SSB or AM.

Should you hear the calls K3UIG/K7UGA, it will mean you're listening to Senator Barry Goldwater—yes he is active on the band, very much so!

ON 7Mc/s

The other band explored this month was 7Mc/s and as usual lived up to its reputation of being both lively and noisy. Using the P.W. 7Mc/s transceiver (P.W. June, '64) the following stations were

worked on a 60ft. end fed wire:—YUIAV, LZZKSK, UA3CD, YUIAR, YO2ADG, UB5VNU, YUIAST and OH5VF/Ø. Maximum input—5W and the receiver an O-V-1. The latter station, OH5VF/Ø, is situated on Aaland Island, (Look it up in an Atlas!)

Expeditions are often organised to various islands and are well worth searching for. At the moment Christmas Island is in the capable hands of VK9DR, and Lord Howe island is another favourite spot.

RALLIES GALORE

Dates to listen on for your "sked" diary.—Sept. 13th there will be three mobile rallies. Listen on 160 metres and 2 metres for the talk-in stations. R.S.G.B. Mobile Rally, Woburn Abbey, Beds. Reading A.R.C. Rally, near Pangbourne, Berks. International Mobile Rally, Holland.

The 1964 VK/ZL Oceana contest, Oct. 3—4th 'phone section, Oct. 10th—11th c.w. section. If you haven't heard or worked Australia or New Zealand try these dates in October.

Just a reminder too that R.A.E. evening classes will be starting shortly and now is the time to check up and enroll.—See Club News page, last month.

THE G3JDG GEAR

Finally, in order that readers can assess results, the following is the equipment used for this column. TX—120W a.m./c.w. RX—single conversion s'het r.f., f., i.f., det/b.f.t., o./p. Antennas—160/80/40/20/10—60ft. end fed wire, maximum 12ft. high; 20 metres Dipole; 10 metres cubical quad 12ft. high.

Anything of interest on the amateur bands will be welcome plus gen on the gear, transmitting or receiving.

Twin Triode Two

—continued from page 635

The rectifier MR1 is a modern contact cooled type, the E250/C50 rated at 250V 50mA.

Layout and Wiring

Layout is again not critical but to minimise hum the following points should be noted. Heater leads should be put in first, twisted and kept close to the chassis. The leads before the grid of the first 12AX7 should be screened and the screened braiding earthed at one end only. Hum in the prototype was almost inaudible with normal volume settings.

The layout is given in Fig. 2 but can be altered fairly freely to fit other chassis.

Power Requirements

The power supplies are quite conventional and little needs to be said about it. Initial smoothing is done by C10 R11 and thereafter the h.t. is split and smoothed further by L1, C8 and C9. Both valves have centre tapped heaters and for 6.3V operation have pins 4 and 5 strapped together for one lead and pin 9 taken to the other lead.

The performance is hard to assess without instruments but with such vigorous music as the 1812 Overture the system is an improvement on a commercial record player in the £16 class. Volume is ample to overload an eight inch speaker rated at four watts.

A DUAL CALIBRATION STANDARD

WITH home-built receivers and signal generators the lack of accurate dial markings is often a nuisance and limitation. The unit described here enables receivers or signal generators to be calibrated at 100kc/s points from 100kc/s (3000 metres) to 30Mc/s (10 metres). The original frequency from which calibration is made is taken from the long wave Light Programme transmitter on 200kc/s (1,500 metres) and a high degree of accuracy can be achieved.

The 1Mc/s signal gives calibration marks at 1Mc/s, 2Mc/s, 3Mc/s, 4Mc/s and so on up to 30Mc/s and is particularly useful for short wave equipment. The 100kc/s or 0.1Mc/s signal provides calibration marks at 100kc/s, 200kc/s, 300kc/s, 400kc/s, etc., which allow medium wave equipment to be calibrated and also fill up at 0.1Mc/s intervals between the 1Mc/s marks over the short wave bands.

Equipment of this kind often employs 100kc/s and 1Mc/s crystals. These have high stability but are expensive. In the unit shown here tuned coils are employed instead of crystals. Provided the unit is always set to harmonic resonance with the 200kc/s Light Programme, before use, a high degree of accuracy is obtained—better, in fact, than that expected from ordinary ready-made receivers or signal generators. The method of use is described later.

CIRCUIT: POWER SUPPLIES

The circuit is shown in Fig. 1 and uses a 6C4 triode. This needs 6.3V 0.15A for heater and about 10mA at 200V to 300V for h.t. As the unit is employed with a receiver it is intended that these supplies be drawn from the receiver power pack.

The three power supply leads are fitted with small clips. The h.t. negative and 6.3V return is clipped to the receiver chassis. To obtain 6.3V the 6.3V clip is attached to a heater circuit tag. The h.t. positive lead is taken to any convenient h.t. positive point, such as the smoothing choke.

The receiver must have 6.3V valves so that 6.3V may be drawn. It should also be of the usual a.c.

type with all power supplies obtained from a mains transformer. The unit must not be attached to an a.c./d.c. receiver or to a set deriving h.t. directly from the mains.

A two-way switch is fitted so that 100kc/s or 1Mc/s signals may be obtained at will. The 150pF and 100pF variable capacitor trimmers have to be set initially by referring to the 200kc/s Light Programme but are then left untouched.

COILS

The dual-frequency coil is shown in Fig. 2 and is wound on a 3in. piece of $\frac{3}{8}$ in. diameter ferrite rod, using 34s.w.g. silk-covered wire throughout.

The 1Mc/s coil has 80 turns, tapping B being 20 turns from end C. A layer of glued paper is wound


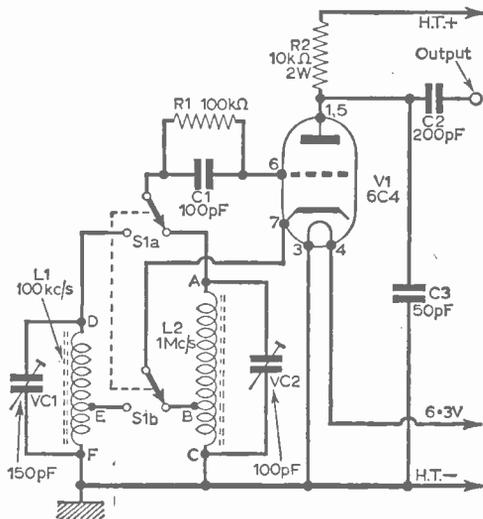


Fig. 1: The simple, single-valve circuit.

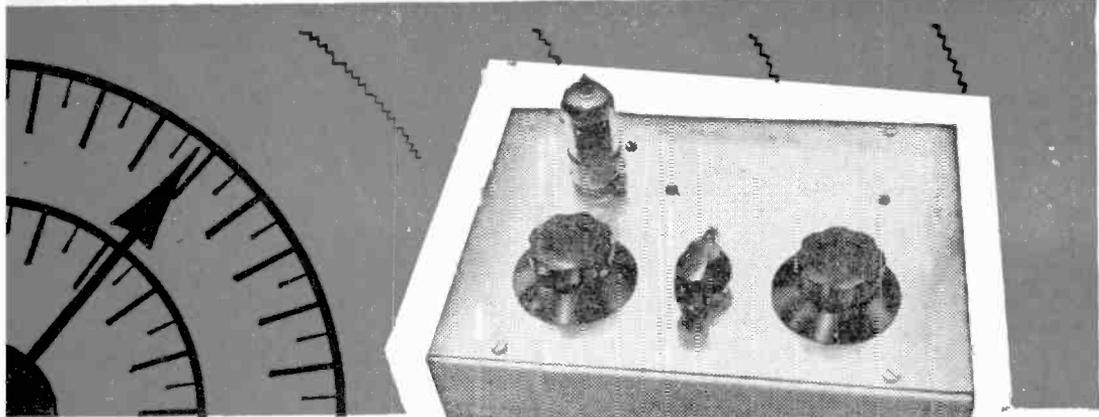

R. F. GRAHAM


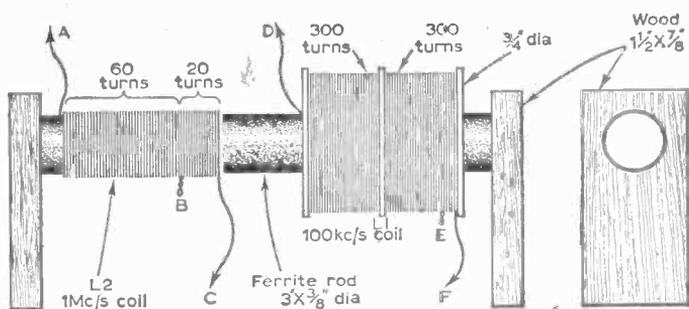


Fig. 2: Coil winding details for L1 and L2.

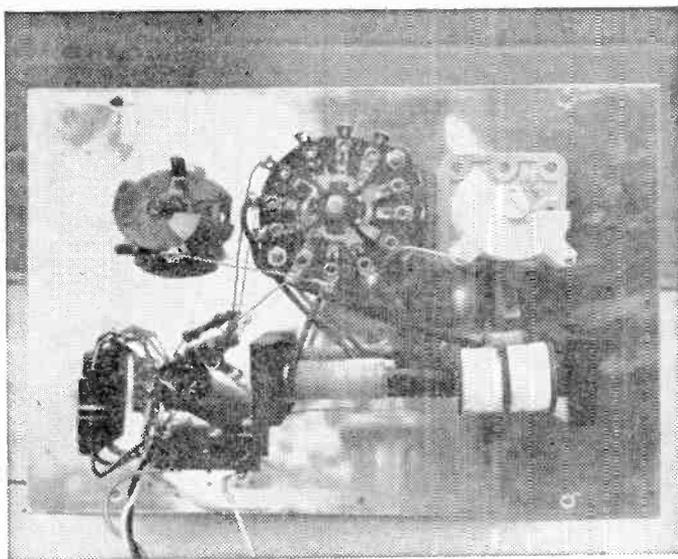

A rear view of the finished instrument.

round the rod first. The turns are wound closely side by side. The ends are secured with adhesive tape, and touches of cement.

For the 100kc/s coil, three $\frac{1}{8}$ in. thick paxolin washers $\frac{1}{4}$ in. in diameter are cut. They are a tight fit on the rod, and cemented in place with winding spaces $\frac{1}{8}$ in. wide between them, the wire passes through a small hole near the rod, end D. The first space is filled by winding 300 turns. The wire is then taken over into the second space, and 250 turns are wound, and loop E is made. A further 50 turns are then wound on, and the coil terminated at F. The windings should be fairly tight, and reasonably even, and each is covered with adhesive tape.

Two small pieces of wood have $\frac{1}{8}$ in. holes, to take the ends of the rod. Screws passed through the aluminium panel hold the wooden pieces in position.

CONSTRUCTION

The unit is built and wired on a 5 in. x 7 in. aluminium panel, all parts and connections being shown in Fig. 3. The panel is afterwards screwed to a 5 in. x 7 in. aluminium box (see component list) so that the whole is completely rigid.

A 4-sided chassis, 5 in. x 7 in. and 3 in. deep, could be used, but wiring will be less easy. The actual layout is not important, and a rigid box, case or cabinet to hand may be used.

A tag strip anchors h.t. positive

setting of the unit will give marks at 3.5Mc/s, 3.6Mc/s, 3.7Mc/s and 3.8Mc/s. With the 7Mc/s band, the 1Mc/s signal will give a mark for 7Mc/s. and the 100kc/s will give 7.1Mc/s. In the same way, 14Mc/s and other bands may be accurately found and marked on the receiver.

For best accuracy, the receiver and unit are switched on for twenty minutes or so before calibration, and the unit is always re-adjusted to zero beat with the long wave Light Programme, or MSF, before using it to calibrate a receiver or generator. The accuracy is then easily higher than

the aerial socket, removing the usual aerial. This should be checked before beginning calibration.

GENERATOR CALIBRATION

To calibrate a signal generator, the generator and unit are both coupled to the aerial circuit of the receiver. The receiver is only used to listen for heterodynes between the generator signal, and marker harmonic, so exact calibration of the receiver is not necessary.

The generator and receiver are tuned to 1Mc/s points and the generator is adjusted to zero beat with the unit harmonic. The 1Mc/s points may thus be marked on the generator scale. The 0.1Mc/s (100kc/s) divisions are then filled up with the aid of the 100kc/s signal.

FREQUENCY WAVELENGTH

If it is wished to obtain wavelength markings, this can be done by noting that wavelength in metres =

$$\frac{300,000}{\text{kc/s}}$$

For example, 1200kc/s is 250m, and 1500kc/s is


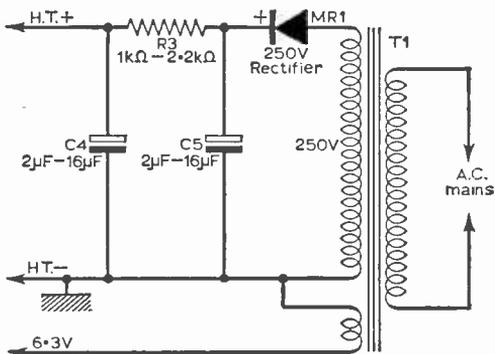


Fig. 4: The circuit of a suitable power supply.

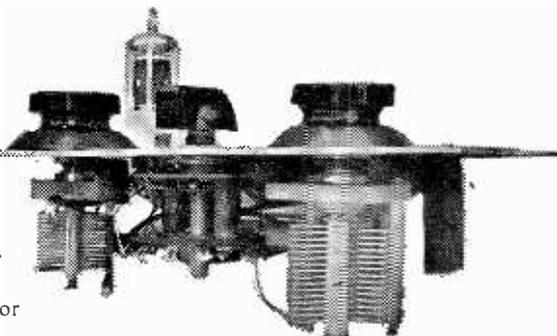

An edge-on view showing the construction of the unit.

the accuracy with which the average receiver or generator tuning scale can be read.

RECEIVER ADJUSTMENT

T.R.F. receivers may be readily calibrated, because if the reaction control is just sufficiently advanced, the harmonics can be tuned in as whistles.

Superhet receivers having tuning meters or beat frequency oscillators are also easily calibrated, because the signals can be observed on the meter, and heard with the b.f.o. on.

With the popular domestic type superhet, a tuning meter can be improvised by connecting a meter between the intermediate transformer and h.t. line, with a 0.01μF Capacitor from i.f.t. to chassis. A meter range of 10mA or so is normally suitable, and the receiver must have the usual a.v.c. circuit. Or oscillation may be induced by twisting an insulated wire round the intermediate frequency amplifier grid and anode circuits, adjusting this until oscillation is heard. (This is a crude form of b.f.o.)

Some adjustment of coupling between the unit and receiver may also be necessary. With low multiples, the signal is strong, and the output lead may be placed near the receiver. But with high multiples, it may be necessary to take the lead to

200m. A megacycle is 1000kc/s. So 10Mc/s is 30m, 12Mc/s is 25m, 15Mc/s is 20m, and so on. In general, kc/s and Mc/s markings are preferred on equipment.

Fig. 4 shows the circuit of a suitable power pack, so that the unit may be employed with battery or transistor receivers or signal generators, or without drawing power from a mains operated receiver. ■

DON'T FORGET YOUR

PTV

PRACTICAL TELEVISION

every month, 2s.

that the dial mechanism is suitably spaced from the front panel which is fitted fairly well on, in the construction. This front panel is also allowed to extend $\frac{1}{2}$ in. deeper than the front runner and thereby brings the various controls to a more convenient operating height whilst also improving the appearance due to the sloping front effect obtained.

A diagram giving the top layout of the receiver is shown in Fig. 3 and it is doubtful if this can be much improved upon. The 1.6Mc/s wavetrapp and first converter lie along one side of the 3-gang unit, coils being placed as close as possible without the moving vanes being fouled. A curved aluminium screen is erected between the aerial and interstage coils to prevent unwanted coupling. The signals proceed around the rear of the ganged unit (the 1.6Mc/s amplifier) to the second converter and main 470kc/s i.f. strip which lies along the other side of the 3-gang, the metal casing of which assists in screening.

Panel connections are required for the b.f.o. and audio stages so these are placed conveniently at one corner. This leaves a 3 x 3 1/2 in. area free at the rear corner and here it is convenient to accommodate the powering section, battery or mains unit.

Above deck the neat appearance is due to the fact that practically all the wiring is accommodated below.

Mounting the Main Components

The first constructional step is to prepare the board which requires some cutting to accommodate the 3-gang capacitor and dial mechanism. A diagram giving basic essentials is shown in Fig. 4 which should be used only as a guide, checking as the work proceeds by tentatively placing the items in position. The narrow slot shown across the board allows the moving vanes to disengage fully and is best left uncut until the other work has been done. Once the ganged unit is bolted home rigidity is regained.

Six sub-miniature i.f. transformers have to be mounted and eight holes have to be drilled for each, seven of which may be made with a $\frac{1}{8}$ in. drill, the central one—used to apply a trimming

tool to the core—requires to be larger. This hole also requires small “keys” which may be clearly seen on the underside (see inset diagram, Fig. 2b). A “sure fire” way of obtaining exact drilling points for these items is to press a piece of thin card against the pin and lug ends. The resultant “impression” is then pricked with a needle and the piece of card used as a template. I.F. transformer orientation may be seen at Fig. 5 whilst the mounting line may be seen at Fig. 4.

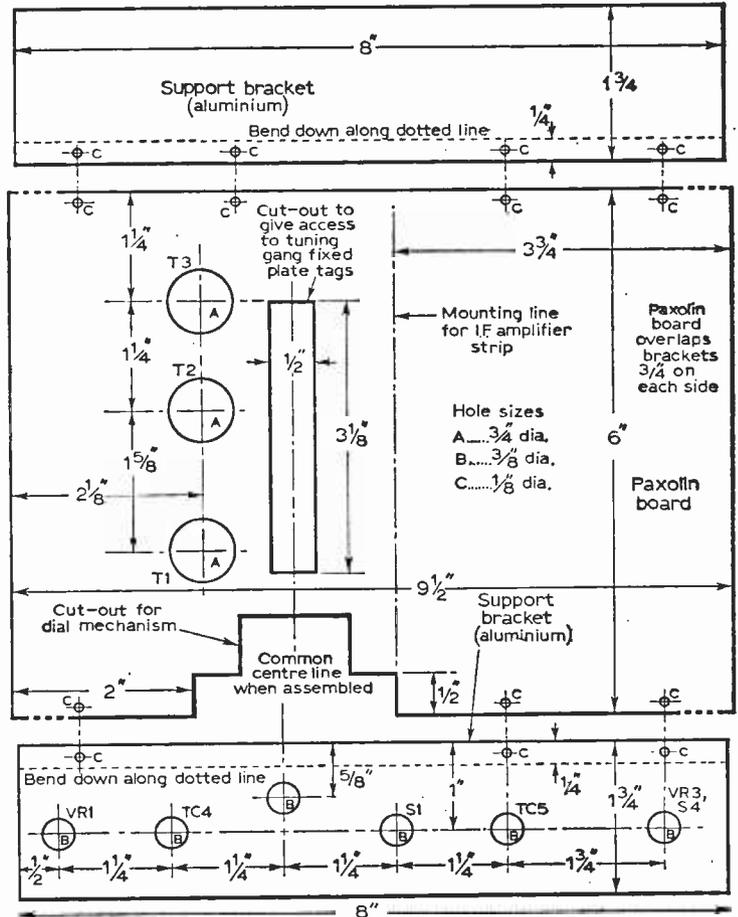


Fig. 4: Dimensions of the paxolin board and its aluminium supports.

When these transformers are correctly located the locking lugs are bent over on the underside and a round blob of solder applied to each lug whilst maintaining pressure from above. Great care is necessary to ensure that solder does not run down the core stems and a small piece of p.v.c. sleeving inserted in each will prove beneficial.

The novel valveholders used for the plug-in

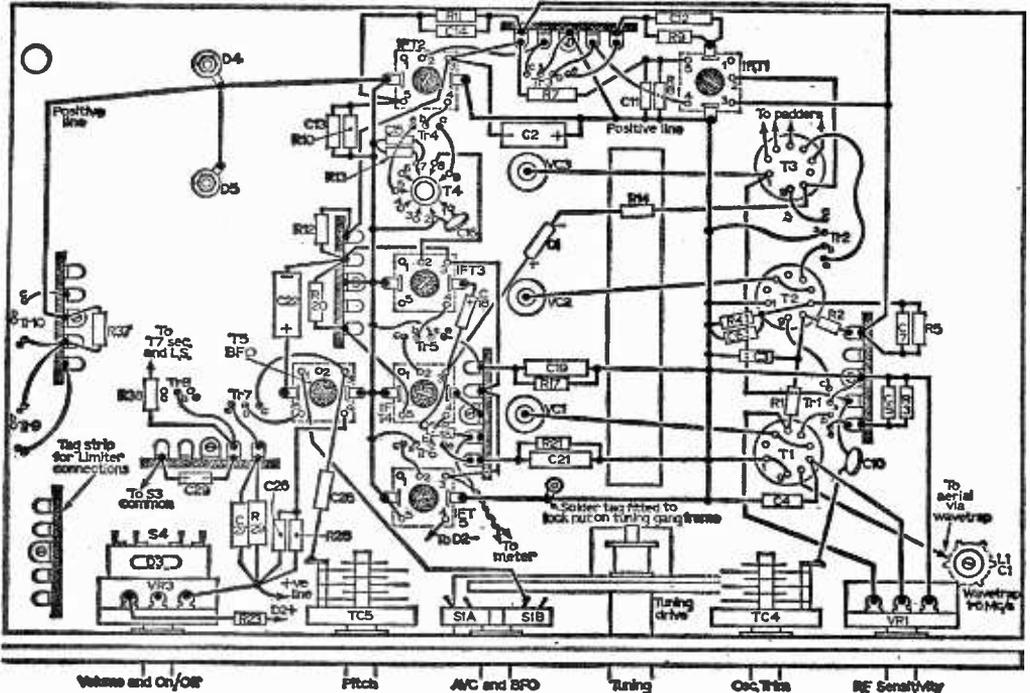


Fig. 5: An underside view showing most of the wiring. Note positive bar and orientation of i.f.t.'s.

coils must be of low-loss construction and may be mounted as shown.

Locating the 1-6Mc/s Wavetrap and T4

These coils must be screened but the methods used differ. To mount the coil L1 drill a 0B.A. hole to accept the threaded section of coil stem.

rene nut provided. Pass a 6B.A. bolt through one of the 1/4 in. holes and fit a solder tag and nut on the underside—this tag “earths” the can when screwed into the lid later. The two remaining holes are required for coil leads.

To fit T4 press its pins against a piece of card to obtain a template, then, using this, drill nine 1/16 in. or smaller holes to accept the pins, orientating the coil as shown in Fig. 5. Place the coil in position, then splay out the pins on the underside to lock it firm. Next take the freed coil container and saw it off carefully just above the threaded portion so that it is 1 1/4 in. long. Drill a 0B.A. hole centrally in the bottom to accept the threaded coil stem and place in position. Before locating the polystyrene nut add a metal washer and a twist of wire for soldering to. Apply the lock nut and tighten. Solder a lead through to the positive bar as convenient to “earth” the can.

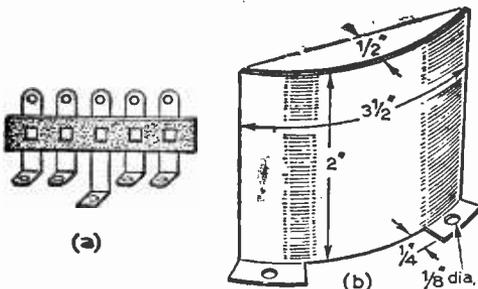


Fig. 6(a): The type of tag strip used in the construction of the “Ten-Five”; (b): details of the coil screen.

Next take the coil container lid and drill a similar hole centrally plus three further 1/4 in. holes, spaced at 120°, fairly close to the rim. Also drill holes in the paxolin board to agree, then mount the coil from above through the lid and secure both thumb tight on the underside, using the polysty-

Wiring Notes

Full point-to-point wiring plans are not given, for it is thought that readers capable of constructing a receiver of this complexity will not be handicapped; it is doubtful, too, if all the wiring could be accommodated on a single plan. All wiring needs to be both short and direct, particularly in the tuned converter section. It is important, too, to use modern, physically small resistors and capacitors, etc., to ensure efficiency and ease of construction. The locations of most of the components may be seen in Figs. 3 and 5.

ANOTHER TAPE RECORDER BARGAIN

Mfrs.' end of production Surplus Offer



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A modern Circuit for quality recording from Mike Gram or Radio, using latest B.S.R. Twin Track Monardeck Type TD2. Valve line up—EF86, EL82, EL84, EZ80 and Selenium Diode. Send for detailed list—3d. stamp.

Complete Kit comprising items below. **BARGAIN PRICE 15 Gns.** + 10/- Carr.

- 12-tone Cabinet and 8in. x 5in. Speaker. Size 4in. x 10in. x 7in. £3.10.0 + 5/- Carr.
- Wired Amplifier complete with 4 Valves, front Panel, Knobs, etc. £5.12.3 + 3/6 Carr.
- B.S.R. Monardeck Type TD2 £7.7.0 + 4/6 Carr.
- Accessories: Mike, Tape, empty Reel, screened Lead and Plugs, Instructions, etc. £1.0.0 + 2/- Carr.

NEW BRITISH RECORDING TAPE

Famous Manufacturer. Bulk purchase, genuine recommended Tape Bargain Unconditional Guarantee. Fitted Lever & Stop Foms (except 3in.).

Standard (PVC base)	Long Play (PVC base)	Double Play (Melar base)
3in. 150ft. 3/9	225ft. 4/9	300ft. 1/3
5in. 600ft. 11/3	900ft. 15/-	1200ft. 35/-
5 1/2in. 850ft. 14/6	1200ft. 17/6	1500ft. 32/3
7in. 1200ft. 17/6	1800ft. 22/6	2400ft. 42/6

Post and Packing—3in. Reels, 6d. Each additional Reel, 3d.
4in. to 7in. Reels, 1/- Each additional Reel, 6d.

EMPTY TAPE REELS (Plastic): 3in. 1/3, 4in. 2/-, 5in. 2/-, 5 1/2in. 2/-, 7in. 2/3.
PLASTIC REEL CONTAINERS (Cassettes): 3in. 1/3, 5in. 1/9, 5 1/2in. 2/-, 7in. 2/3.

Condensers—Silver Mica. All values 2pF to 1,000pF, 6d. each. Ditto, Ceramic 9d. Tuh. 450V T.C.C. etc. etc. 0.001 mFD to 0.01 and 0.1/350V. 9d. 0.02-0.1/500V, 1/- 0.25 Values 1/6 (C.S.T.C.C. 1/9, etc. etc. Close. Tol. 5/Micas—10% 5pF, 500pF 8d. 600-5,000pF, 1/- 2pF-1,000pF, 9d. 100pF-500pF, 1d. 575pF 5,000pF. 1/6 Resistors—Full Range 10 ohms-10 meg. ohms 20p. 1 and 1/4. 3d. 1/4. 5d. (Midget Type modern ratings) 1W, 6d. 2W, 9d. Hi-Stab. 5% 1W, 1/4. 6d. (100 ohms-1 meg). Other values 9d. 1% 1/4. 1/6, etc. etc.

JASON FM TUNER UNITS
Designer-approved kits of parts. FMT1, 5 gns. 4 valves, 20/-; FMT2, £7. 6 valves, 35/-; JTV MERCURY 10 cms. JTV2 £13.19. 6 valves, 28/6. NEW JASON FM HANDBOOK, 2/6. 48 hr. Alignment Services, 7/6. P. & P. 2/6.

TRIMMERS, Ceramic (Compression Type)—30pF, 50pF, 70pF, 9d.; 100pF/150pF 1/3; 250pF, 1/6; 500pF, 1/9.

PHILIPS. Bee Hive Type (conc. air spaced)—2-8pF, 1/-; 3-30pF, 1/-.

KNOBS—Modern Continental Types Brown or Ivory with Gold Ring; 1" dia., 9d. each; 1 1/2" dia., each; Brown or Ivory with Gold Centre, 1" dia., 10d. each; 1 1/2" dia., each. LARGE SELECTION AVAILABLE.

METAL RECTIFIERS. STC Types—RM1, 4/9; RM2, 5/6; RM3, 7/6; RM4, 16/-; RM5, 21/-; RM41, 17/6.

TUB-ELECTROLYTICS-CAN
25/25v. 50/12v. 1/9; 8+8/450v. 4/6; 50/50v. 100/125v. 2/-; 32+32/275v. 4/6 8/450v. 4/350v. 2/3; 50/50/350v. 6/8 16+16/450v. 5/8; 80/250/275v. 12/9 32+32/450v. 8/6; 100+200/275v. 12/6

Volume Controls—5K-2 Meg. ohms, 3in. Spindles. Morgante Midnet. Type 1 1/2in. diam. Guar. 1 year. LOG or L.I.N. ratios less 8w. 3/-; 10P. Sw. 4/6. Twin-Steer less 8w. 6/6. DF. Sw. 7/-, Specials to order.

SPECIAL BARGAIN

1/2 Meg. VOL. Controls DP. Sw. 1/2 flatted spindle. Fomula Rsr. 4 for 10/-, post free.

RECORD PLAYER CABINETS 59/6

Carr. & Ins. 5/- Contemporary style, rexine covered cabinet in two-tone maroon and cream. Size 15 1/2" x 14 1/2" x 4 1/2", fitted with all accessories including battle board and Vynair treat. Space available for all modern amplifiers and auto-changers etc. Uncut record player mounting board 14 1/2" x 12 1/2" supplied.

2-VALVE 2 WATT AMPLIFIER, E/280 and Twin stage ECL82 with vol. and neg. feedback tone control. A.C. 200/250V with knobs, etc. ready wired to fit above cabinet. £2.17.6. P. & P. 1/6. 7" x 4" speaker and trans. 22/-, P. & P. 2/6.

COMPLETE R/PLAYER KIT. As ill. inc. BSR UA14 Unit. New Bargain Price Now Only £11.10.0. 7/6 carr. Double wound mains Tr. no live chassis



BONDAOUND Speaker Cabinet Acoustic Wadding (lin. thick approx.) 12in. wide, any length cut, 1/6 ft. 4/- sq. **TINNED COPPER WIRE**, 16-22g. 2lb/100. **ERSIN MULTICOE SOLDER**, 60/40 4d. per yard. Cartons 2/6 etc.

TYGAN FRET (Contem. pat.). 12 x 12in. 2/-; 12 x 18in. 3/-; 12 x 24in. 4/-, etc.

EXPANDED ANODISED METAL. Attractive gilt finish. 3in. x 1/2in. diamond mesh 4/6 spft. Multiples of 6in. cut. Max. size 4ft. x 3ft., 47/6 plus carr.

ENAMELLED COPPER WIRE— 1lb. reels 14g-20g. 2/60 22g-28g. 3/-; 20g-34g. 3/9; 30g-38g. 4/3; 39g-40g. 4/6, etc.



MULLARD "3.3" HI-FI AMPLIFIER 3 VALVES 3 WATT



Hi-Fi quality at reasonable cost. Bass Boost and treble controls, quality sectional output transformer, 40 cms-2. ke/s + 1 d. 100 mv for 2V. less than 1% distortion. Bronze scotchcon panel. Complete Kit only £8.19.6 Carr. 5/-. Wired and tested 8 gns.

MULLARD "45-10" AMPLIFIER. 5 valves 10W 3 and 1.5 ohms output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer. Basic amplifier kit price £9.19.6 Carr. and Ins. 7/6. Ready built £11.19.6.

CONTROL PANEL KIT. Bass, Treble and Volume controls with 4-position selector switch and Dim. A. 4in. acousticon panel. £2.5/6. Carr. 2/6.

AMPLIFIER KIT AND CONTROL PANEL KIT £11.19.6. Ditto, ready wired, £14.10.0.

2-VALVE PRE-AMP. UNIT. Based on Mullard's famous 2-valve (2xEP86) circuit with full equalisation, with volume, bass, treble and 5-position selector switch. Size 9 1/2" x 4" x 2 1/2" Complete Kit £5.19.6 plus carr. 3/6

6 VALVE AM-FM TUNER UNIT
Med. and V.H.F. 150 Mc-30 Mc. 6-100 m.c.s. valves and metal rectifier. Self contained power unit. At 200-250v. operation. Magic eye indicator, 3 push-button control panel. Med., V.H.F., low and high output with gain control. Perspex front panel 12in. x 4in. with 7in. illuminated dial. Overall size 11 1/2in. x 4in. x 3 1/2in. A recommended facility unit for use with Mullard 3-3 or 5-10 Amplifiers. Available only at present as built-up units, signed and tested ready for use. Bargain price £12.10.0. Carr. 5/-. Available shortly in Kit Form at approximately 10 gns.

DE-LUXE RECORD PLAYER KIT



Incorporating 4 St. Garrard Auto-Slim unit and Mullard latest 3 w. amplifier (ECL 86 and EZ 80), vol., bass and treble controls, with 8" x 7" in. one way speaker. Contemporary styled 2-tone cabinet, matching grey and off-white with matching blue relet. Size 17 1/2" x 16 1/2" x 5". **COMPLETE KIT £13.19.6** Carr. and Ins. 10s. Cat. & Const. details 2/6 (free with kit). **FRONT SECTION**, which houses amplifier and speaker, is detachable from cabinet. Price as separate unit for stereo £13.17.6. Carr. 5/-.

TRANSISTOR COMPONENTS

- Midget 1.1's—465 Kcs 9/16in. diam. 5/8
- Conc. Coil M. & L.W. 5/6
- Milicec Driver Trans. 3.5i. 8/9
- Midget Output Trans. Push-Pull—3 ohms 6/9
- Elect. Condensers—Midget Type 1 mid-50 mid. ea. 1/8, 100 mid. 2/-, 12/-.
- Condensers 150 v. working: .01 mid., .02 mid., .03 mid., .04 mid., .05 mid., .1 mid., 1/2-25 mid., 1/3; 5 mid., 1/6, etc.
- Midget Tuning Condensers, J.B. "00" 25-25 pF and 176 pF. 8/8, ditto with trimmers, 9/8. J.B. 220 pF and 108pF conc. slow motor. 100 pF single 7/8. Sub. min. 1in. Dilemma 100 pF, 300pF, 500pF, 7/- each.
- FERRITE AERIALS, M. & L.W.** car aerial coil 9/3. Midget coil control with edge control knob, 5 K/ohms, with switch 4/9; Ditto less switch 3/9. Speakers: P.M.: 2in. Plessey 7/6 ohms 15/6. 2 1/2in. Continental 8 ohms, 14/6. 7 x 4in. Plessey 35 ohms 22/6.
- Ear Pick Phones—Min Continental type 3ft. lead, jack plug and socket. High Imp. 8/-, Low Imp., 7/6.
- Brand New, Mfrs. 1st grade, 1 OC44 & 2 OC45, 15/6. 1 OC81D & 2 OC1, 15/6. All above and OA41, 32/6. Post Free.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up EOC85, ECH81, EF89, EABC80, EL84, EM81, EZ80. Three Waveband and Switched Gram positions. Med. 200-530 m. Long 1,000-2,000 m. V.H.F./I.M. 88-95 Mcs. Phips Continental Tuning Insert with permanent tuning on FM and combined AM/FM HF transformers. 150 Kcs and 10.7 Mc/s. Direct core tuning, all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2" x 6 1/2in. Height 7 1/2in. Edge illuminated glass dial 11 x 8 1/2in. Vertical pointer. Horizontal station names. Grid on brown background. A.C. 200/250v. operation. Magic-eye tuning. Oct. Diagram now available. Aligned and tested ready for use £13.10.0 Carr. & Ins. 7/6



Complete with 4 Knobs—walnut or ivory to choice. Indoor FM aerial 3/6 ext. 3 ohm P.M. Speaker only required. Recommended Quality Speakers 10in-Elac H19, 30/-; 15i x 5in. E.M.L. "Fidelity", 35/-; 12in. B.A. with cone-Tweter, 42/6. Carr. 2/6.

We manufacture all types Radio Mains Trans., Chokas, Quality O/P Trans., etc. Enquiries invited for Specials, Prototypes for small production runs. Quotations by return. Send for detailed bargain lists, 3d. stamp
RADIO COMPONENT SPECIALISTS
70 Bristolock Rd., Thornton Heath, Surrey. Hours: 9 a.m-6 p.m., 1 p.m. Wed. THU 21st. Terms C.O.D. Post and Packing up to 4 lb. 9d.; 1 lb, 1/3; 3 lb, 2/6; 5 lb, 2/6; 8 lb, 3/6.

WEYRAD

TRANSISTOR COILS

The P50 series remain the most popular and widely used components for Medium and Long-wave Transistor Superhets:—

P50/1AC Oscillator Coil for 176 pF tuning	5/4 ea.
P50/2CC 1st & 2nd I.F. Transformers	5/7 ea.
P50/3CC 3rd I.F. Transformers	6/- ea.
All mounted in individual cans $\frac{1}{4}$ in. diam. x $\frac{3}{4}$ in. high.				
RA2W Ferrite Rod Aerial 208 pF Tuning	12/6 ea.
LFDT4 Driver Transformers	9/6 ea.
OPTIA Output Transformers	10/6 ea.
PCAI Printed Circuit Panel	9/6 ea.
Constructor's Booklet	2/- ea.

VALVE RECEIVER COILS

Our Individual "H" type iron-cored coils are without equal for the construction of a wide range of receivers. For the simplest T.R.F. sets covering one or more wave-bands the Aerial and H.F. Transformer coils are ideal. The standard superhet circuit using the ever-popular triode-hexode frequency change layout would employ the Aerial and Oscillator coils and the coverage can be selected from 7 different bands ranging from 12.5 to 2,000 metres. For a really high-performance receiver an R.F. stage can be added by using the Aerial, H.F. Transformer and Oscillator Coils and a circuit is provided illustrating such a layout.

H Coils 3/9 each.

WEYMOUTH RADIO MANUFACTURING CO. LTD.

REGENT FACTORY, SCHOOL STREET,

WEYMOUTH, DORSET

pitman

AN ELECTRONIC ORGAN FOR THE HOME CONSTRUCTOR

Alan Douglas, Sen. Mem. I.E.E.E.

A very popular "how to make it" book. Shows exactly what is involved in work and materials (a list of sources of supply is included) in constructing an inexpensive instrument for use in the home. For this new edition, an alternative arrangement of continuous tuning has been added to a revised and up-to-date text.

Second edition 20s. net.

from all booksellers

Pitman Parker St. London WC2

HOUSING HI-FI?

This is one of a wide range of cabinets for every hi-fi purpose—speakers, equipment, tapes and records. Specially designed, superbly finished, sensibly priced. Send for illustrated catalogue and name of local stockist.

Fanfare Record
Cabinet. Walnut or
Mahogany
£9.19.0.
Teak
£10.19.0.



RECORD HOUSING

(Dept. P.W.11), Brook Road, London N22

Telephone: BOWes Park 7487/8

Extensive use is made of small tag strips (Lektrokit, part No. 2231), see Fig. 6(a), seven of these being required on the underside of the board and two above. Use is also made of a thick, plain, tinned copper wire which forms a rough square below deck and is the positive bar. A screen is also required, as mentioned earlier, between aerial and interstage coils and this is shown in Fig. 6(b).

The Front Panel

Essential details regarding the panel may be seen in Fig. 7. It is secured to the "chassis" by means of additional $\frac{1}{4}$ in. nuts placed over the various control shafts. The top may be held by locking it to the dial (holes are provided) and with brackets if required. Items fitted direct on the

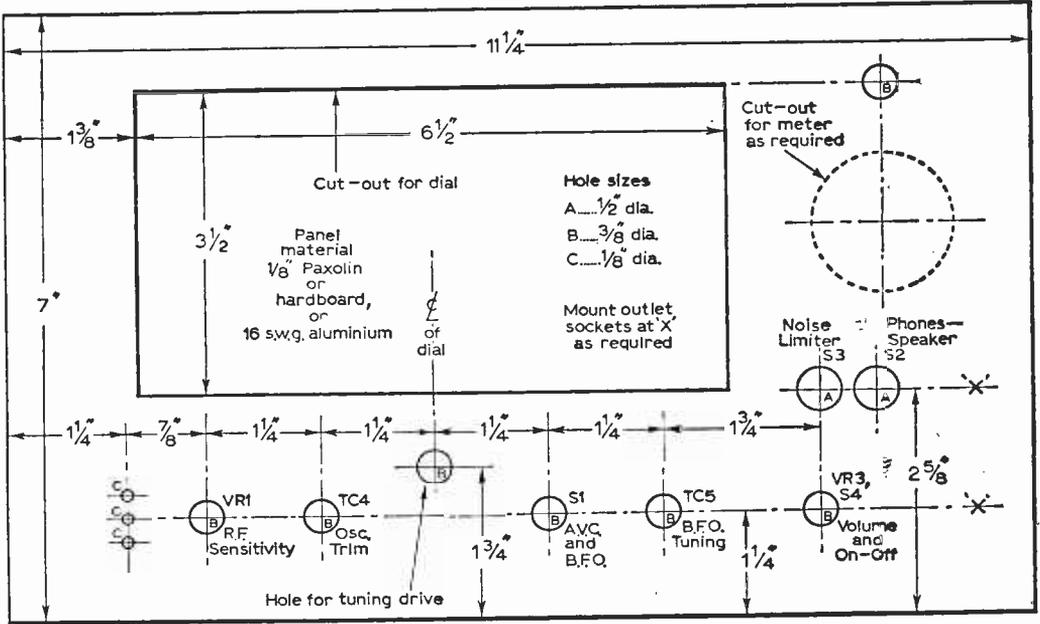


Fig. 7: Front panel control layout and dimensions.

A photograph showing the layout of the prototype receiver is shown on page 661.

Fitting the Transistors

The ten transistors are best mounted by letting their shells stand upright above the top of the board, $\frac{1}{16}$ in. holes being drilled close together through which each sleeved lead-out wire is passed. This gives a firm anchorage. Four such holes are needed for transistors 1, 2, 3, 5 and 6 and three for the others. The locations and correct orientation may be seen by referring to the diagrams. A pair of tweezers (the type used by printers' compositors is ideal) will be found extremely useful in this connection. Transistors 9 and 10 must be fitted with copper clips and the white spots designating the collectors should be carefully checked before sliding the clips fully home.

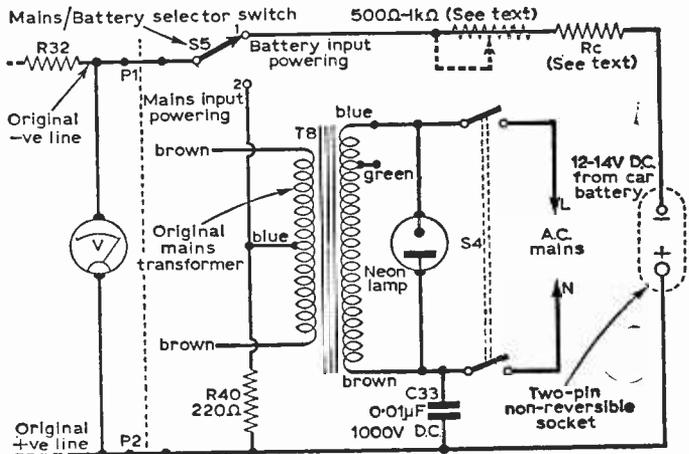


Fig. 8: Modifications for mains/battery operation. See page 661.

panel are: the aerial socket, S2, S3, VR2, the signal/tuning meter and the two outlet sockets. Later the finished unit may be placed in a small cabinet which may be either of metal or of wood, etc., lined with aluminium foil. This cabinet will require a lift-up top so that coil changing can be effected.

Testing the Receiver

After making certain all connections are correct, particularly in the power supply section, whether this be battery or mains, a milliammeter set to read 0—50mA should be inserted in series with the negative supply. Phones and speaker should be connected and VR2 set to "min". The "on/off" switch is then closed, whereupon a reading should be obtained approximating to 12mA if the function switch is set to "LS". Should the reading be much higher, say 30mA, switch off immediately and investigate. If all is well rotate S1A to bring in the b.f.o. and adjust VR2 for a full-scale tuning meter deflection, after which the a.v.c. may be switched in, i.e. b.f.o. "out". A few spot voltage checks may next be made, referring to Figs. 2a, b and c as necessary, allowing for slight discrepancies caused by resistor tolerances, transistor variations, etc. At this stage connection of an aerial is unlikely to produce any signals since alignment will be well out. If "howling" results reverse the connections to T7 secondary.

Circuit Alignment

The constructor who has got this far will be able to align the receiver. Some results might be obtained without a signal generator but these are likely to be very poor ones; even a generator only covering up to about 2Mc/s is better than none at all.

I.F. Stages

Initially the first converter is made inoperative, say, by short-circuiting a winding of T3, then with the noise limiter "out" and a.v.c. "in" a low value 470kc/s modulated signal is applied via a 0.01µF capacitor between the positive bar and pin 5, i.f.t.2, and should be heard via the loudspeaker if the volume control is well advanced. Only the smallest perceptible reading on the signal/tuning meter is required and it might also be necessary to short-circuit pins 1 and 2, T4. An alternative form of indicating device consists of a meter inserted in the line from -9V and the output transformer centre tap and adjusted to read 0—50mA or as appropriate.

The cores of i.f.t.5, 4, 3 are then carefully adjusted for maximum deflection on the indicator used, using a suitable non-ferrous trimming tool. As the circuits come into line, generator output is attenuated so as

not to cause the a.v.c. system undue disturbance and the cores retrimmed for maximum reading.

With the generator set to 1.6Mc/s the short-circuit to T4 is removed and its core adjusted to resolve the signal; should two settings be possible choose the one giving largest output. Lock T4 coil stem firmly with a 6B.A. bolt and transfer generator to pin 7, T2. Peak i.f.t.2 and i.f.t.1, using the cores.

R.F. Alignment

This is carried out on the basis of core adjustment first at the low frequency end of the band, followed by trimmer adjustment at the high frequency end. In this case commence with the highest range to be used, i.e. range 5 (Table 1) and with TC4 set so that with its pointer upright the vanes are about 25% enmeshed.

1. Connect the generator via a standard dummy aerial (or 400Ω resistor) to the aerial socket and inject a 10.5Mc/s signal with the vanes of the tuning gang fully enmeshed and the converter stage *operative*.

2. Adjust the core of the oscillator coil (T3) to resolve the signal (see note re "second channel" later).

3. Set generator to 31.5Mc/s and fully disengage vanes of the tuning gang (VC1/2/3). Set oscillator trimmer for maximum output. Repeat these operations.

4. Set generator to low frequency tracking point (Table II). Tune it in, using VC1/2/3 gang, then adjust the yellow and blue cores for maximum output (see note on "pulling" later).

5. Adjust generator to the high frequency tracking point and tune it in, using VC1/2/3 gang capacitor. Adjust interstage and aerial trimmers for maximum output.

Second Channel

Two responses can usually be found on short-wave ranges and the one requiring minimum core or trimmer in circuit is the correct one. To check move generator pointer on completion above and below its setting (3Mc/s), when a second response will be noted. This should be higher in frequency than the one used for the initial adjustment.

Pulling

Detuning of the oscillator can occur when aligning the signal circuits (pulling) but may be overcome by slightly rocking the tuning gang capacitor when making adjustments.

TABLE II
Tracking Points

Range	L.F. Band end	L.F. Tracking point	H.F. Band end	H.F. Tracking point
1	175 kc/s	192 kc/s	525 kc/s	472 kc/s
2	515 kc/s	566 kc/s	1545 kc/s	1390 kc/s
3	1.67 Mc/s	1.83 Mc/s	5.3 Mc/s	4.5 Mc/s
4	5.0 Mc/s	5.5 Mc/s	15.0 Mc/s	13.5 Mc/s
5	10.5 Mc/s	11.5 Mc/s	31.5 Mc/s	28.5 Mc/s

Note.—Uses of Ranges 1 and 2 is not envisaged here but is included for completeness.

FOR PEAK PERFORMANCE AT LOW COST —

PICK CODAR AMATEUR RADIO EQUIPMENT



Advanced design and craftsmanship plus an unequalled reputation proved by the many hundreds of testimonials received from CODAR users is your guarantee of complete satisfaction. Only the best is good enough for CODAR—Mullard, Brimar, Jackson, Denco, Electroniques, Thorn, A.E.L. are just some of the famous names built into CODAR equipment. CODAR-KITS are supplied with clear pictorial diagrams and easy to follow instructions—no technical knowledge or special tools are required for complete success. Build your Short Wave Station with CODAR-KITS and enjoy peak performance and world wide reception previously possible only from much more expensive equipment.

For illustrated leaflets giving fullest details send 6d. in stamps.

CODAR R.F. PRE-SELECTOR. Will considerably improve the performance of any superhet receiver. "Results are amazing." "Well worth the money." **MODEL P.R.30.** Uses EF183 Frame Grid tuned R.F. Amplifier and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12 M/A H.T. 6.3 volts 3 amp L.T. Size 8 1/2 in. x 5 in. x 4 in. Ready built, complete with cables, plugs and instructions. £4.17.6. Carr. 3/- **MODEL P.R. 30X.** Self powered version for 200-250 V. A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £7.2.0. Carr. 3/-.

CODAR "Q" MULTIPLIER, MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW or SSB. Both PEAK and NULL functions tuneable over receiver I.F. passband. B.F.O. facility included. Size 8 1/2 in. x 5 in. x 4 in. Power requirements 180-250V. H.T. at 5 M/A 6.3V. 3 amp L.T. Ready built complete with cables, plugs and instructions. £6.15.0. Carr. 3/- **MODEL R.Q. 10X.** Self powered version for 200-250V A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £8.8.0. Carr. 3/-.

CODAR A.T.5. 12 WATT 2 B BAND TRANSMITTER. The newest, most compact transmitter for fixed or mobile use on 160/80 metres. "The tiny TX with the BIG voice." Size only 8 1/2 in. x 5 in. x 4 in. (Base area is less than two thirds of this page). High stability new type calibrated V.F.O. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR-QOIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate/screen modulator. AM/CW switch and Panel key jack. Plug changeover for 6 or 12 V. heater supply. Ready built £16.10.0. Carr. 4/- **A.T.5 POWER SUPPLY UNITS.** For 250V. or 230V. A.C. with Stand by/Net/Transmit and aerial changeover switching, stabilised V.F.O. supply, neon standby/transmit indicator. £8.0.0. Carr. 5/- Type 12/MS 12V. Transistor power supply unit available shortly. (H.P. Terms available)

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT WAVE RECEIVER. ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4 page instruction manual. PRICE 39/6. Carr. 2/6. Extra Coils 4/9 each. Instruction Manual only, 2/- (credited on order). Electrical Bandsread available. Provision to add 2 transistor amplifier.

CODAR-KIT CR45 MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandsread. ★ 3 slow motion vernier drives. ★ Low loss polyethylene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line up: ECC81, EL84, EZ80. **CODAR-KIT CR45** complete with valves, 3 coils (10-23, 25-75, 60-176 metres) and 11 page instruction manual (LESS Cabinet). £7.5.0. Carr. 4/6 **CR.45 CABINET.** £12. x 5 in. x 7 in. with sliding door for easy coil changing. 29/6. Extra coils 4/9 each. Instruction manual only 4/- (credited on order). (Can now be supplied ready built—price on request.) (H.P. terms available.)

CODAR-KIT CR 66 COMMUNICATION RECEIVER. The finest superhet kit ever offered. ★ Covers 540 Kc/s—30 Mc/s in 4 bands. ★ Separate electrical bandsread. ★ Factory aligned Coil unit and I.F. Transformers. ★ Regenerative I.F. stage for maximum gain and B.F.O. for C.W. reception. ★ Power output 3 watts for 2/3 ohm speaker. ★ Panel controls: Aerial Trimmer, A.V.C., Standby, Bandswitch, A.F. Gain, I.F. Gain, B.F.O., etc. ★ Valve line up: ECH81, EBF89, ECC81, EL84, EZ80, EM84. ★ Size 16 in. x 6 1/2 in. x 8 in. **CODAR-KIT CR 66.** Complete with 17 page instruction manual. £19.2.6 (Ready-built £21.12.6) **CR 66 "S"** Meter Model Kit £21.2.6 (Ready-built £25.15.0). Carr. 6/- extra on all models. (H.P. terms available.) Instruction Manual only, 7/6 (credited on order).

We are exhibiting on stand 20A, at the
R.S.G.B. RADIOCOMMUNICATIONS EXHIBITION

CODAR RADIO COMPANY

GMRE G3HGQ

BANK HOUSE, SOUTHWICK SQUARE,
Southwick, Sussex. Tel. 3149

Canada: Codar Radio of Canada, Tweed, Ontario.

IMPROVED

Modern styling in light grey with legible black engraving.

Constructed to withstand adverse climatic conditions.

Ever ready case, including leads, prods and clips.

Improved internal assemblies.

Re-styled scale plate for easy rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy using an individual calibrated scale plate d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.

STANDARDS OF

ACCURACY AND RELIABILITY

The Mk. 4 MULTIMINOR is an entirely new version of this famous Avo instrument and supersedes all previous models. It is styled on modern lines, with new high standards of accuracy, improved internal assemblies, and incorporating panclimatic properties.

The instrument is supplied in an attractive black carrying case, which also houses a pair of leads with interchangeable prods and clips, and an instruction booklet. It is packed in an attractive display carton. Robust real leather cases are available, if required, in two sizes, one to take the instrument with leads, clips and prods, and the other to house these and also a high voltage multiplier and a d.c. shunt.



Mk 4

MULTIMINOR

D.C. Current: 100µA f.s.d. — A f.s.d. in 5 ranges
 A.C. Voltage: 10V f.s.d. — 1,000 f.s.d. in 5 ranges
 D.C. Voltage: 2.5V f.s.d. — 1,000 f.s.d. in 6 ranges
 D.C. Millivolt range: 0 — 100mV f.s.d.

Resistance: 0.2 MΩ in 2 ranges using 1.5V cell.
 Sensitivity: 10,000Ω/V on d.c. Voltage ranges.
 1,000Ω/V on a.c. Voltage ranges.

For full details of this great new pocket-size instrument, write for descriptive leaflet.

AVO LTD AVOCET HOUSE. 92-96 VAUXHALL BRIDGE ROAD - LONDON, S.W.1 - VICTORIA 3404 (12 lines)



MP17

THE PEMBRIDGE COLLEGE OF ELECTRONICS PROVIDES TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 5th January, 1965.

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:
The Pembridge College of Electronics (Dept. P11)
 34a Hereford Road, London, W.2.

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____


CHPP

I.F. Wavetrap and B.F.O.

There is a small break in the coverage between ranges 2 and 3 to assist stability due to use of a 1.6Mc/s i.f. and a signal of this frequency applied should not be heard. The wavetrap is adjusted, however, using a large signal, by means of L1 core for minimum response.

To adjust the b.f.o. rotate S1 to "b.f.o. in" and with an unmodulated signal set the core of i.f.t.5 to obtain the required beat note in conjunction with TCS.

With the receiver completed it only remains necessary to house it suitably along the lines mentioned earlier and to mark up the scale as required, for which purpose a crystal marker is undoubtedly most useful. The "20" and "40" metre bands should appear at a little more than mid-scale with "80" at about "1" on the appropriate ranges and as indicated by the bandset pointer. Reception on the highest frequency bands will greatly depend on conditions, on the kind of aerial used and so on, whilst appreciating that receiver sensitivity falls off in this region. A lot of DX listening is done on "20", however, and here excellent results are assured.

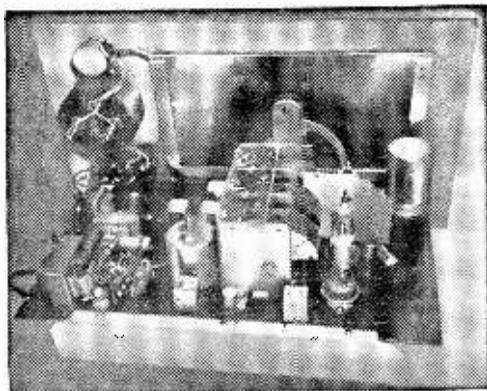

A rear view of the finished receiver.

Further notes and portable operation

Functionally it is not easy to improve the "A.C. Ten-Five" to any great extent—at least, not with components generally available to constructors—and the only modifications so far, found worth while have merely added to the versatility of the receiver. One useful addition—when the mains-powered system is adopted—is to fit a coloured warning lens and lamp to the front panel.

This has been done to the prototype and a Bulgin D841/250V neon signal lamp will easily fit into the corner occupied by the "S" meter. The leads from the signal lamp should be soldered across the primary winding of the mains transformer and it should here be noted that low voltage dial lamps should on no account be used in conjunction with the secondary winding of T8.

One of the most appealing features of the receiver however is its low current and voltage requirements and it is thought not unlikely that some users would like to utilise it in their cars by

powering it from the battery thereof.

Going "portable" can be great fun and with the aid of a car it is, of course, quite easy to find a pleasant and favourable reception area far from surrounding buildings and high above sea level. An effective aerial can easily be transported (a 2 dipole for 14Mc/s is only 34ft. long) and may be very simply erected whereupon searching for DX can be a pleasant and healthy pastime!

To enable the "A.C. Ten-Five" to run from a 12V car battery it is necessary to add, basically, a function selector switch, a resistor and a simple non-reversible 2-pin socket. These items may be fitted to the rear chassis flange—on the side occupied by the mains transformer—with the switch positions legended on to the back of the cabinet. At the home station the switch will be set to "Mains" but when moved to a distant field location it will be moved to "Battery". It will also then function as an On/Off Switch. A pair of small hooks screwed into the cabinet back outside and at each end will be found useful around which to wind the flexible power supply lead when not in use.

The modification to the original receiver wiring merely entails breaking the negative feed supply line from the mains transformer and reconnecting it via the added switch. The scheme is illustrated in Fig. 8 where S5 is the "Mains/Battery" switch. The location of the added neon warning lamp is also indicated.

The additional resistor is R_c and the inclusion is a necessary one since a potential of 14V might be available from a healthy battery—as would probably be the case at the time of year when outdoor working is most likely. The value of R_c depends largely on whether headphones are likely to be in use or a speaker and the value chosen might be 800Ω for the former mode and 80Ω for the latter. Ideally R_c should be made a fixed value item of say 1000Ω or thereabouts and wired in series with a 500Ω—1kΩ variable resistor so that adjustments may be made. It would then be beneficial to fit a monitoring voltmeter or, alternatively, to include test point terminals to which an external meter may be connected. These changes are indicated by the broken lines in Fig. 8. In any case the voltage across points P1 and P2 should be monitored, 10V being the maximum permissible d.c. voltage.

It is advisable when making voltage checks to disconnect the aerial from the receiver and to set the volume control to minimum. In passing it may be noted that should the function selector switch be accidentally left at "Battery" on returning to the home station no harm will be done even if the mains supply is connected. The receiver will not function of course but R40 (already fitted) will adequately load the mains transformer secondary.

A non-reversible 2-pin plug and socket arrangement will also be needed at the car end of the battery feed lines and care must be taken to ensure polarities are correct. Modern cars employ a positive "earth" and sometimes the courtesy lamp provides a convenient take-off point. Mobile listening is not envisaged here since this would raise the problem of suppression. The receiver should not be used close to a station transmitter,


—continued on page 666

PART 2—JUNCTION TRANSISTORS AND TRANSISTOR PARAMETERS

Understanding SEMICONDUCTORS

BY LESLIE MOORE

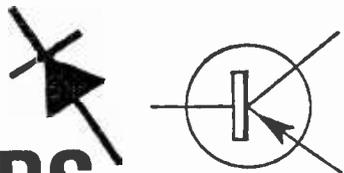CONTINUED FROM PAGE 529 OF THE OCTOBER ISSUE



THE junction transistor makes use of p.n. junctions in a manner which relies on the physical dimensions of the crystalline materials used.

The rectifier circuit, in the last article, functions because of one basic fact which is shown diagrammatically in Fig. 11a.

When the p type material is made positive with respect to the n type, current flows through the junction. It can be said that electrons pass from the n type to p type material or holes pass from p type to n.

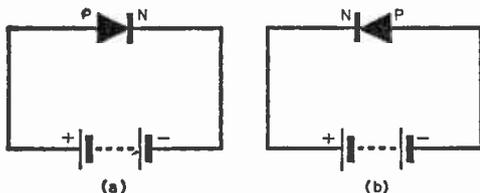


Fig. 11(a): Here, current flows, but at (b) only leakage current flows.

The two circuits, a and b, in Fig. 11 joined as in Fig. 12 would produce the same current flow through each diode as before.

Joining the two pieces of n type material together gives exactly the same effect as the circuit in Fig. 12.

We have now a three terminal device consisting of a piece of p type material on each side of a piece of n type, which in operation, gives the effect of two semiconductor diodes "back to back".

By making the n type material extremely thin the p type materials will have an increased electrostatic effect upon each other.

Because of the decreased thickness of the n type, the hole flow in the equivalent circuit of Fig. 12 is shown in Fig. 13.

In Fig. 12 holes passing from the p type material to the n type were conducted back to the source of supply, B1.

If the bias were to be reversed as in Fig. 11b, ideally no current flows. Apparently when a reverse bias is applied to a diode junction an extremely small amount of current does flow. This is in the order of "micro amperes" or millionths of an amp. The amount of "leakage current" flowing depends on the materials from which the junction diode is made. The most common materials in use are germanium and silicon; a germanium junction produces more leakage current than the silicon.

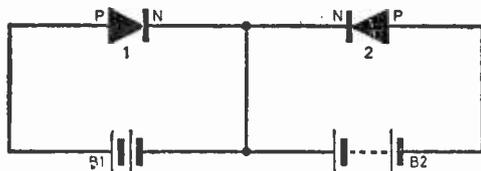


Fig. 12: Joining the two circuits of Fig. 11 produces the same current flow through each transistor, i.e. flows through diode 1 and only leakage current through diode 2.

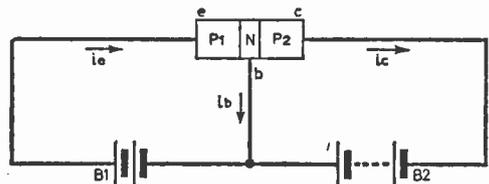


Fig. 13: When the n-type material is made extremely thin, current flows through both junctions.

In Fig. 13 holes passing from the p type to n type are split up. The negative potential of the second piece of p type material provides an attraction greater than that of B1; although a potential barrier exists at the second junction the holes are attracted through and conducted to B2. A small number of holes are attracted by B1.

The names of the semiconductor component parts of the transistor are of great importance. With reference to Fig. 13.

- P₁ is known as the emitter, denoted by e;
- P₂ is known as the collector, denoted by c;
- N is known as the base, denoted by b.

The sum of the currents in the base and collector is equal to the current flowing in the emitter.

Fig. 13 shows the common base connection of a transistor.

Obviously it would be impractical to draw small boxes as in Fig. 13 to represent transistors in

- all these and hundreds more

Mon.—Sat. 9 a.m.—5.45 p.m.
Wednesday 1 p.m.
Lunch 1.30—2.30

Special 24 Hour Express Mail Order Service

AC5/PEN 19/6	ECC84 6/6	EY51 7/6	P2 10/1	SP61 3/6	UL85 7/6	6A8G 8/6	6L19 15/1	12Q7GT 6/1
AC2/PEN 19/6	ECC85 7/6	EY81 8/6	PABC80 13/1	T41 15/1	UM80 10/6	6A8GT 13/6	6N7GT 9/6	12SA7 8/6
DD 29/6	ECC88 12/6	EY83 12/6	PCC84 7/1	TDD4 12/6	URIC 15/6	6AC7 6/1	6P25 10/6	12S17 8/6
AC/TP 19/6	ECC91 3/1	EY86 7/1	PCC85 9/6	TDD13C 17/6	U6 17/6	6AK5 5/1	6P28 12/6	12S17 8/6
AC/VPI-5-7 15/1	ECH3 21/6	EZ40 7/1	PCC88 12/6	TH41 20/1	U8 15/1	6AL5 4/1	6Q7 9/6	12S17 8/6
AZ1 15/1	ECH21 21/1	EZ41 7/1	PCC89 8/6	TY86F 12/6	U9 7/6	6AM5 5/1	6Q7G 6/1	12S17 8/6
AZ31 13/6	ECH35 12/6	EZ80 5/6	PCF80 7/6	U10 9/1	UY21 12/6	6AM6 4/1	6Q7GT 8/6	12S17 8/6
B36 9/1	ECH42 9/6	EZ81 5/6	PCF82 7/6	U11 9/1	UY41 7/6	6A05 6/6	6SA7 7/1	14H7 21/1
CIC 10/1	ECH81 7/1	EZ90 4/6	PCF84 12/6	U12 9/1	UY85 6/1	6A06 6/1	6SC7 8/6	14R7 21/1
CCH35 20/1	ECH83 8/6	E1148 2/1	PCF86 12/6	U14 9/1	VP4 15/1	6BBG 2/6	6SF5 10/1	19A05 8/1
CL33 12/6	ECL80 6/6	FC2 15/1	PCL82 7/6	U22 8/1	VP4B 15/1	6BA6 6/1	6SH7 6/1	20D1 10/1
CY1 15/1	ECL81 10/1	FC2A 17/6	PCL83 9/1	U24 21/1	VR15 30/7	6BE6 6/1	6S17 6/6	20D2 21/1
CY31 12/6	ECL82 9/6	FW4 500 9/1	PCL84 7/1	U25 11/1	VR150 30/7	6BG6G 15/1	6SK7 5/6	20F2 17/6
D77 4/1	ECL83 10/6	FW4 800 9/1	PCL85 12/6	U31 9/1	VR150 30/7	6B16 7/1	6SL7GT 5/6	20L1 22/6
DAC32 9/6	ECL86 9/6	GZ30 10/6	PEN44 19/6	U35 17/6	W61 11/1	6B07A 12/6	6SN7GT 5/1	20P1 15/1
DAF91 5/1	EF6 21/1	GZ32 10/6	PEN42 22/6	U37 17/6	W7 5/1	6BR7 10/6	6SQ7 8/6	20P3 24/1
DAF96 6/6	EF9 21/1	GZ33 19/3	PEN4VA 17/6	U47 11/1	W77 4/1	6B87 12/6	64UGT 10/1	20P4 20/1
DCC90 12/6	EF22 14/1	GZ34 13/6	PEN36C 20/1	U50 7/1	W81 6/1	6BV6 9/1	6USG 7/6	20P5 20/1
DF33 9/6	EF37 8/1	GZ37 19/3	PEN45DD 20/1	U52 4/1	WB1M 6/1	6BV7 9/1	6V6G 4/1	25A6 8/1
DF91 3/6	EF37A 8/1	HABC80 10/1	PEN45 10/1	U76 6/6	X41 22/6	6C4 3/6	6V6GT 8/1	25L6 8/1
DF92 7/1	EF39 4/1	HL41 8/1	PEN45DD 20/1	U78 4/6	X61M 12/6	6C5GT 8/1	6X4 4/6	25Y5 8/1
DF96 6/6	EF40 15/1	HL41DD 8/6	PEN46 5/1	U145 10/6	X65 12/6	6C6 6/6	6X5G 5/1	25Y5G 8/1
DH63 6/1	EF41 8/1	HL92 8/6	PEN46 5/1	U191 13/6	X76 12/6	6C9 12/6	6X5GT 8/6	25Z4 7/6
DH77 7/1	EF42 10/1	HL133DD 9/6	PEN46DD 20/1	U251 15/1	X76M 12/6	6CD6G 25/1	6Y30L2 12/6	25Z5 8/6
DK32 11/1	EF50A 3/6	HN309 25/1	PENDD4020 20/1	U281 15/1	X78 26/1	6CH6 10/1	7B0 12/6	25Z6 8/6
DK91 5/6	EF50E 3/1	IW4:350 10/1	PL33 15/1	U329 15/1	X79 40/1	6CW4 16/1	7B7 8/6	27SU 19/6
DK96 7/6	EF80 5/1	IW4:350 10/1	PL36 12/6	U339 13/6	Y61 10/1	6D2 4/1	7C5 8/1	30C1 9/1
DL33 8/6	EF85 5/1	KT33C 8/1	PL38 17/6	U403 10/1	Y63 10/1	6D6 5/6	7C6 8/6	30C15 12/6
DL35 10/1	EF86 7/1	KT36 17/6	PL81 8/1	U404 10/1	Z66 10/1	6E5 10/6	7D5 15/1	30F5 10/6
DL91 7/1	EF89 8/1	KT61 12/6	PL82 7/6	U801 19/6	Z77 4/1	6F1 10/6	7D8 15/1	30FL1 12/6
DL92 5/1	EF91 4/1	KT66 17/6	PL83 7/6	UABC80 5/6	1A7 11/1	6F6 5/9	7F7 6/1	30L15 8/6
DL93 7/1	EF92 4/1	KT76 10/1	PL84 8/1	UAF42 8/6	1C5 10/6	6F12 4/1	7F7 17/6	30P4 18/1
DL94 7/1	EF95 5/1	KT81 8/6	PL820 8/1	UBC41 7/6	1D5 10/6	6FL3 10/1	7Y4 6/6	30P12 10/1
DL96 6/6	EF98 10/1	KTW61 8/1	PM24M 13/6	UBC81 10/1	1D6 10/6	6FL15 12/6	8D3 4/1	30P16 9/6
EA50 2/1	EF183 8/1	LN512 6/6	PX4 15/1	UBF80 7/6	1H4 5/6	6F19 12/6	9BW6 12/6	30P19 17/6
EABCC80 5/6	EF184 8/1	LN309 9/1	PX25 25/1	UBF89 7/1	1H5 9/6	6F23 10/6	10C1 12/6	30PL1 15/6
EAC91 4/6	EFK32 8/6	LZ319 12/6	PY31 10/1	UBC85 7/1	1I4 5/6	6F25 16/6	10C2 17/6	30PL13 12/6
EAF42 9/6	EL3 21/6	MKT4 17/6	PY32 15/6	UC884 11/6	1I5 5/6	6F26 13/6	10F1 10/1	30PL14 12/6
EB34 2/6	EL32 4/6	MS4B 17/6	PY33 10/6	UC85 7/1	1I5 5/6	6F33 5/6	10F9 12/6	35A5 15/6
EB41 6/1	EL33 12/6	MVS/PEN 17/6	PY80 7/6	UCF80 12/6	1I7 3/6	6H6 2/1	10P1 19/1	35L6GT 8/6
EB91 4/1	EL34 14/1	MVS/PENB 17/6	PY81 6/6	UCH21 20/1	1I8 5/9	6H6 2/1	10P1 19/1	35W4 6/6
EBC3 21/1	EL35 10/1	MU14 9/1	PY82 5/6	UCH42 8/6	1I8 5/9	6H6 2/1	11D5 23/6	35Z4 6/6
EBC33 5/6	EL37 17/6	MX40 15/1	PY83 8/1	UCH81 7/1	2P 22/6	6I7 7/6	12A6 6/6	35Z5 8/6
EBC41 8/6	EL38 17/6	N18 8/1	PY88 10/1	UCH82 7/1	3A4 5/1	6I7G 5/1	12AH8 11/1	41STH 22/6
EBC81 10/1	EL41 9/6	N37 14/1	PY800 10/1	UCL82 9/1	3A5 10/6	6I7GT 7/6	12AT6 7/6	42 12/6
EBF80 7/6	EL42 9/6	N78 22/6	PZ30 15/1	UCL83 11/6	3Q4 8/1	6K7 7/6	12A77 5/1	50C5 10/1
EBF83 8/1	EL81 12/6	N108 26/1	R2 10/1	UF41 7/6	3Q5 5/6	6K7G 7/6	12A06 17/6	50CD6G 30/1
EBF89 7/6	EL84 6/1	N308 18/1	R16 17/6	UF42 7/6	3S4 5/6	6K7GT 7/6	12A07 5/1	50L6 8/6
EBL1 21/1	EL85 10/1	N339 30/1	R19 16/6	UF80 7/1	3V4 7/1	6K8 9/6	12A07 5/1	75 8/6
EBL21 21/1	EL90 8/6	N369 10/6	R20 16/6	UF85 7/6	3V4 7/1	6K8 9/6	12BA6 7/6	78 7/6
ECC35 8/1	EL91 4/1	OD3 5/1	R21 10/1	UF86 12/6	3V4 7/1	6K8GT 9/1	12B26 7/6	80 7/6
ECC40 15/1	EL95 10/6	OZ4 5/1	R21 10/1	UF86 12/6	5V4G 7/6	6K8GT 9/1	12B26 7/6	80A 7/6
ECC43 8/1	EM80 8/6	Q54 5/1	R21 10/1	UF86 12/6	5V4G 7/6	6K8GT 9/1	12B26 7/6	80B 7/6
ECC81 4/1	EM81 8/6	Q54 5/1	R21 10/1	UF86 12/6	5V4G 7/6	6K8GT 9/1	12B26 7/6	85A2 12/6
ECC82 5/1	EM84 8/1	Q54 5/1	R21 10/1	UL41 8/1	5Y3G 4/6	6L1 10/1	12JGT 8/6	185B7 30/1
ECC83 5/1	EM85 10/1	Q54 5/1	R21 10/1	UL44 20/1	5Y3GT 5/6	6L1 10/1	12K7GT 5/1	807A 9/6
				UL84 6/1	5Z4GT 8/6	6L7 10/1	12K8GT 10/1	807B 9/1

COMPLETE VALVE LIST FREE WITH ORDER

METAL RECTIFIERS

RM1 7/6	14A86 23/1	16RD 2-2-8-1 12/1	(FC142)
RM2 8/1	14A97 26/1	16RE 2-1-8-1 10/1	(FC150)
RM3 10/1	14A100 28/1	18RA 1-1-8-1 5/1	(FC118)
RM4 17/6	14RA 1-2-3-2 21/1	18RA 1-1-16-1 7/1	(FC116)
RM5 19/6	14RA 1-2-8-3 25/1	18RD 2-2-8-1 16/1	(FC124)

BRAND NEW TRANSISTORS			
OC35 10/1	OC72 8/1	OC81D	5/1
OC42 6/1	OC74 8/1	OC81M/pr	12/6
OC44 5/1	OC75 8/1	OC82	6/1
OC45 5/1	OC77 8/1	OC82D	6/1
OC71 5/1	OC81 5/1	OC170	6/1

SILICON RECTIFIERS
400 volts 350 mA 7/6 each


TERMS OF BUSINESS C.W.O. or C.O.D.
4/2 PACKING CHARGE ON ALL C.O.D. ORDERS.
POSTAGE 6d. per VALVE

SETS OF VALVES			
IR5, 155, 1T4, 354, 3V4	Set of 4, 17/1		
DAF91, DF91, DK91, DL91, DL92, DL94	Set of 4, 17/1		
DAF96, DF96, DK96, DL96	Set of 4, 25/1		

R.S.T. VALVE MAIL ORDER CO.

211a STREATHAM ROAD MITCHAM SURREY

Tel: MITCHAM 6202
Open Daily to Callers

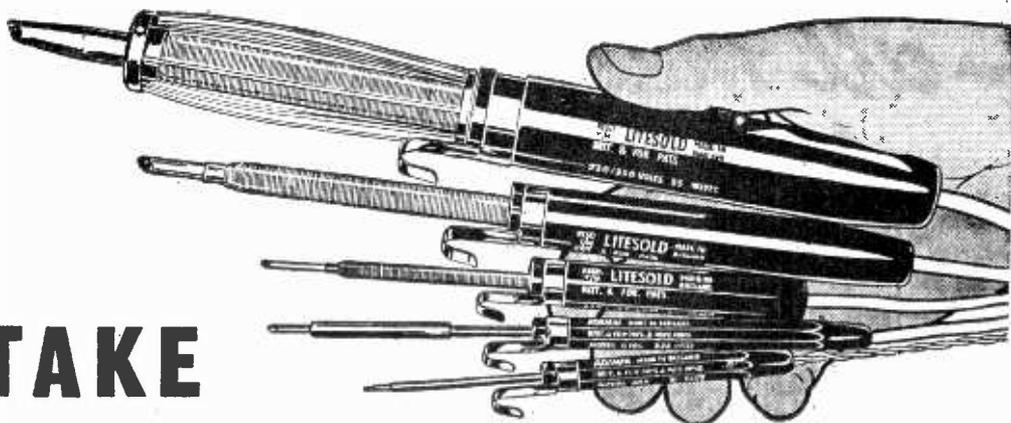

TAKE FIVE!

There are 30 other models, too. There ARE several other makes of soldering instruments. Big ones. Small ones. Good ones. We've seen them. We don't make the biggest ones. Or the most expensive ones. Or the most elaborate ones. We DO make the smallest ones. And the widest range. We make the best. Always have. May we send you details?

Brochure P.W.10 post free on request

LIGHT SOLDERING DEVELOPMENTS LTD., 28, Sydenham Road, Croydon, Surrey.

Telephone: CROYdon 8589

It's so easy to build TAPE EQUIPMENT with a MARTIN RECORDAKIT

With a Martin Recordakit you can either build a complete tape recorder (in which case you can have it with deck and portable type case if desired) or assemble a pre-amp to connect the deck to existing amplifier system. There are Recordakits for two or four track decks. Complete with instructions. When finished, you will enjoy performance and quality of wonderfully high standards more usually associated with far costlier equipment. With transistorised Audiokits you can build Hi-Fi to your personal requirements for mono or stereo reproduction

- Printed circuit board sections supplied complete tested and with valves in position on Recordakits.
- Kits well packed in fitted cartons and complete down to last screw and measured length of wire.
- Full assembling and operating instructions.



THE KITS YOU BUY WITH SUCCESS BUILT IN

MARTIN AUDIOKITS

A brilliant new technique enabling you to combine, interchange and add stereo by means of cleverly designed transistorised units to produce equipment just as you want. The range of kits so far includes:

- 5-STAGE SELECTOR SWITCH WITH MATCHING INPUTS.
- PRE-AMP & TONE CONTROL UNIT.
- 8 WAY MIXER WITH NEW MATCHING SYSTEM
- AMPLIFIERS
- POWER PACKS

AMP. & PRE-AMP. KITS

8311-V—2 Tr. for Collaro 3 sp. deck with valves, transformers, knobs, etc.
8311-4-V as above, for 4 Tr.
8312-CP for Collaro 2 Tr.
8312-4 CP for Collaro 4 Tr.

11 gns.
12 gns.
8 gns.
9 gns.

COMPLETE KITS

Kit 'C' with 8311-V amp, case, 9" x 5" speaker and Collaro Deck.
Kit 'D' with 8311-4-V amp, case, Collaro Deck and 9" x 5" speaker.

28½ gns.
34 gns.

- AMPLIFIERS FOR COMPLETE INSTRUMENTS
- PRE-AMPS TO ADD TO HI-FI
- 2 TRACK AND 4 TRACK
- PRE-BUILT AND TESTED BEFORE PACKING

MARTIN ELECTRONICS LTD., 154-155 High Street
Brentford Middlesex.

Full details of Martin Recordakits

Full details of Martin Audiokits

NAME _____

ADDRESS _____

(Block letters)

PW11

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD, M'SEX

Phone: ISLeworth 1161/2

circuit diagrams, Standard symbols for transistors have been devised, two of which are shown in Fig. 14.

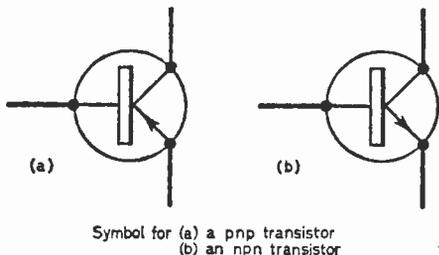


Fig. 14: Circuit symbols for (a) a p-n-p transistor and (b) an n-p-n transistor.

An increase in the base-emitter voltage would give a larger resistance to the effect of the collector-emitter voltage to the hole conduction through the base-collector junction.

A decrease in the base-emitter voltage would give less resistance to hole conduction, hence the collector current would increase.


If the base were made too positive with respect to the emitter, so that the collector potential would not have any effect whatsoever on holes present in the emitter, no collector current would flow. Under this condition the transistor is said to be "cut-off".

Reversing the base-emitter bias would have the effect of "saturating" the transistor, i.e., maximum collector current will flow for the collector-emitter voltage applied.

Under normal use then, the base must be kept slightly positive with respect to the emitter.

There are several parameters in a transistor circuit that are of great importance. They include: base current I_b

Fig. 16: A circuit for obtaining static output characteristics.

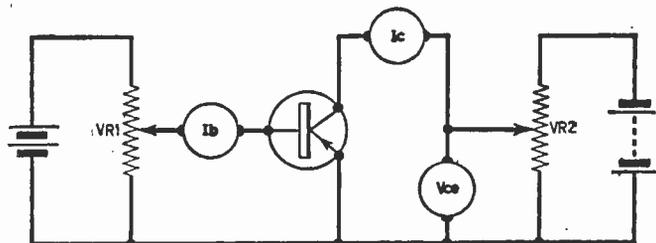

The type of transistor that has been dealt with is the p-n-p transistor. It would have been as easy to deal with the n-p-n type which operates with the opposite potential to the p-n-p.

Transistors are most commonly used in the "grounded emitter" connection where the emitter is common to both input and output.

Before transistor circuitry is discussed relationships between transistor parameters must be understood.

TRANSISTOR PARAMETERS

Fig. 15 shows a p-n-p transistor in the common emitter connection.

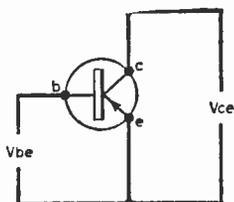


Fig. 15: A p-n-p transistor in common emitter connection.

When the base of the transistor is made positive with respect to the emitter, the emitter-base junction would act as a diode under reverse bias. By making the collector negative with respect to the emitter, holes are attracted through the base providing the collector-emitter voltage is large enough to overcome the effect of the base voltage.

base-emitter voltage V_{be}
 collector current I_c
 collector-emitter voltage V_{ce}

The static output characteristics are found by using a constant value of base current and plotting values of I_c against V_{ce} on a graph. Several curves

—continued overleaf

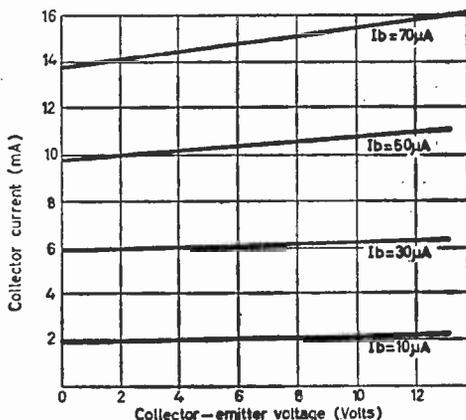


Fig. 17: Typical static output characteristics.

A T.R.F. TRANSISTOR PORTABLE

—continued from page 645

winding is connected from the aerial to the receiver positive line.

When the rod aerial is not in use, the receiver should be turned because of the directional properties of the ferrite aerial. If the rod aerial is extended, this directional effect is much reduced.

Regeneration

As this is so easily added, the extra sensitivity obtained may be felt worthwhile. To obtain regeneration, a very small capacity is added between the negative end of D1 and base of Tr1, at tag 4. Two lengths of 26s.w.g. insulated wire, twisted together, were found to provide a suitable capacitor. A 30pF air spaced beehive trimmer was also found satisfactory.

To adjust regeneration, the capacity is slowly increased until the receiver just fails to go into oscillation. With correct adjustment, sensitivity is quite high.

The actual positions of the windings on the ferrite rod are not very important, except that these will influence waveband coverage, and the tuning positions at which stations are found.

Cabinet

The receiver lends itself well to construction to suit an existing cabinet. A case can, however, be made with $\frac{1}{2}$ in. thick wood for sides and bottom, with 3-ply or $\frac{1}{4}$ in. hardboard for front and back. The front should have an aperture, covered with silk, and the whole cabinet can be finished with self-adhesive material of the required colour. A strap type handle is fitted, and the receiver is inserted as a single unit from the top.

A shelf to carry the battery is held by two brackets, as in Fig. 3. This item can be of 3-ply or hardboard, and it is slightly less than 8 $\frac{1}{2}$ in. x 3in. It also allows the receiver to stand upright, when removed from its case. ■

UNDERSTANDING SEMICONDUCTORS

—continued from previous page

are usually plotted for several different values of base current.

Fig. 16 shows a circuit used for obtaining the output characteristics.

Base current is kept at a constant value by use of VR1. VR2 controls the actual value of collector-emitter voltage.

The "curves" produced from this are seen in Fig. 17.

Abbreviations μ A and mA mean microamp and milliamp.

The slope of the lines plotted increases with base current, therefore the output resistance decreases as the base current increases.

Base current governs the output resistance which, for the majority of transistors, may be anywhere within the region of 5,000 Ω to 50,000 Ω .

Input static characteristics are obtained by

plotting values of V_{be} against I_b for several values of V_{ce} .

A typical curve for the input characteristics is shown in Fig. 18.

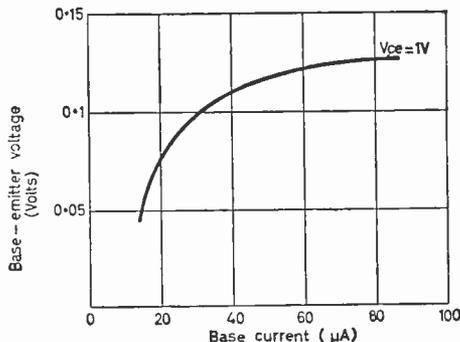


Fig. 18: Typical static input characteristics.

The use of these curves and other relevant information provided by transistor manufacturers is of great importance in the design of transistor circuitry.

Part 3 follows next month

THE "TEN-FIVE"

—continued from page 661

whether fixed or mobile, either since no transistor protection circuitry is incorporated.

On Taking Off

Nothing is more exasperating than to arrive at a distant site and on unpacking find an essential lead is missing! To prevent this from happening an inventory should be drawn up and checked prior to setting out both on the outward and return journeys. Some of the items required at a portable location extra to the receiver are: (1) The battery/car power supply lead. (2) Phones and/or speaker. (3) The coil set. (4) A high resistance d.c. voltmeter with leads! (5) Insulating tape. (6) A suitable aerial already fitted with receiver lead-in and plug plus sectional masts with guys. (7) Screwdriver. (8) Sidecutters. (9) Sharp pocket knife. (10) Mallet.

Other useful items might be: A map, watch, compass, a.t.u., notebook and pencil, etc.

And finally, if an even smaller tuning rate to that catered for is required, fit a Jackson epicyclic reduction unit to the bandspread dial pointer spindle. This is the lower of the two shafts. The already 48:1 bandspread ratio will then be still further beneficially reduced, a facility soon found extremely useful when exploring the highest frequency ranges. And all ranges are tuneable, of course, with a much quieter background when the receiver is transported to an area well clear of fluorescent lighting and other man-made electrical interference! ■

DO IT YOURSELF

Build a Record Player and Save Pounds The Cheapest Way The L.K. Way

●**SCOOP!** Transistor Tape Recorder. The best obtainable by very famous manufacturer. Brand new, boxed, guaranteed. Reduced from 12 gns. **OUR price £7.10.0 P.P. 3/6.** Complete with microphone, tape, batteries and operational booklet. Features push-pull amplifier, two motors, single switch operation, pause, speed, wind, rewind, record, play back. Can be used in any position, indoor or outdoor.

Famous Autochanger or Single Player Units supplied with brand new, two-tone, de-luxe portable cabinets, 17 x 15 x 8½ in. Strong carrying handle, gilt finish clips and hinges are used by famous make for 22 gn. model. Ready cut out motor board, 14 x 13 in. Front baffle 7 x 4 in. High flux loudspeaker and 3 watt amplifier. Amplifier ready built on metal chassis with output transformer, volume and tone controls. All items fit together perfectly. Assembly in 30 minutes. Only 5 wires to join. 12 months' written guarantee. Available separately or package deals as below.

Our NEW MKII Superb Kits are now being dispatched.

L. K. PRICES FOR COMPLETE KITS:

Autochanger Kits as above	
8 B.S.R. U.A. 14, T.C. 8 Mono	£10.17.6 P.P. 7/6
B.S.R. U.A. 25, T.C. 8, Mono	£10.17.6 P.P. 5/6
Garrard Autolism, Mono	£11.7.6 P.P. 7/6
Single Player Kits as above	
Garrard S.R.P. 10, Mono	£10.12.6 P.P. 5/6
E.M.I. Autostop, Mono	£10.17.6 P.P. 5/6
Individual Prices for those who wish to purchase separately.	
Record Player Cabinet with Cut-out Board	£2.15.0 P.P. 3/6
Amplifier with 7 x 4 in. speaker	£3.10.0 P.P. 2/6

Autochangers

B.S.R. U.A. 14, T.C. 8 Mono	£5.7.6 P.P. 5/6
B.S.R. U.A. 25, T.C. 8, Mono	£5.7.6 P.P. 5/6
Garrard Autolism, Mono	£6.0.0 P.P. 4/6

Single Players

E.M.I. Autostop, Mono	£5.7.6 P.P. 4/6
Garrard S.R.P. 10, Mono	£5.5.0 P.P. 4/6
E.M.I. Separate Pick-up	£3.0.0 P.P. 3/6

Transcription Units—Stereo Head—Mono

Garrard 4 H.F. Stereo	£14.10.0 P.P. 5/-
Phillips A.G. 10/16, Stereo	£12.0.0 P.P. 5/-
Garrard A.T.6, Stereo	£9.19.6 P.P. 5/-
Garrard 301	£16.10.0 P.P. 5/-

●**SCOOP!** B.S.R. U.A. 25 Autochangers. T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note **OUR price £5.7.6 P.P. 5/-.** The very, very latest model.

●**SCOOP!** Now released Garrard A.J.5 Semi-transcrip-tor Auto—The Finest Charger of them all—Our Price **£8.10.0 only** with Stereo Head.

●**SCOOP!** B.S.R. U.A. 14 Autochangers. T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note **OUR price £5.7.6 P.P. 5/-.** Latest model

●**SCOOP!** Garrard Autolism. Mono P.U. Brand new and boxed. Wired for stereo. Latest model. Note **OUR price £6.0.0 only P.P. 5/-.**

●**SCOOP!** Diodes—over 1,000,000 in stock—ideal substitute O.A.B.I. vision detector. Note **OUR price £1.0.0 per 500 P.P. 2/-.** (In 500 lots only).

●**SCOOP!** 3-watt Gramophone Amplifier. Complete with 5in. Speaker, 49/6. P.P. 5/-.

The amplifier is complete, on a fabric-covered baffle board. Output transformer included. Tone and volume controls and on/off switch. Ready to switch on and play. Terrific volume. Size 12½ in. x 6 in. x 3½ in. back to front. For 200-250 v. A.C. Output 3 watts.

●**IF NOT ADVERTISED IT IS STILL IN STOCK**

●**MAIL ORDER ONLY TO THIS ADDRESS PLEASE**

●**MAGNIFICENT SCOOP!** Continental push-button 3-wave band Stereo Chassis—plus the latest Garrard A.J.5 Semi-auto Transcrip-tor—plus two W.B. Hi-Fi speakers. **27 Guineas only**, the package deal. Regret no H.P. P.P. 12/6.

●**SCOOP!** A Brittamer Stereo Amplifier by this world famous amplifier designer. 5 watts per channel. Assembled, tested, guaranteed. Even leads and plugs supplied. Maker's package unopened.

OUR price £7.10.0. List price £15.15.0. P.P. 5/6. Please send for our Amplifier and Hi-Fi lists they are FREE. Our prices the most competitive in the trade.

●**SCOOP!** Microphones. Complete Lead Coax. Plug, Brand New. Our Price 5/- only. P.P. 1/6.

TRANSISTOR SECTION

●**SCOOP!** A first-class 2 wave-band 6 transistor superhet chassis by world famous manufacturer. Fully built, aligned, tested, guaranteed. Full coverage long and medium waves. Note **OUR price £4.4.0 only.** Suitable speaker 10/6. A few cabinets can be supplied at 22/6 each. **OUR price** for the package deal **£5.5.0 only P.P. 2/6.**

●**SCOOP!** As above, 8 transistor. **OUR price £5.4.0 only.** Suitable speaker 10/6. Cabinet (very attractive two-tone), 22/6. **OUR price** for the package deal **£6.10.0 only P.P. 2/6.**

●**SCOOP!** A Limited Number Only. Tape Decks by B.S.R. Latest model A.C./200/240 v. Brand new and boxed **OUR price £6.10.0 only P.P. 4/6.**

●**SCOOP!** Tape Recorder Amplifiers. Suitable for B.S.R. or Collaro Decks. Price: **£6.10.0 for B.S.R. Deck; £6.12.0 for Collaro Deck P.P. 6/-.** Mk.III. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel 13 x 1½ in. Overall height 5½ in. Front to back measurement 5½ in. The amplifier is supplied complete with the switch wafer fully wired for B.S.R. deck. For Collaro deck, a completely wired separate switch with spindle is supplied Magic Eye DM70.

●**SCOOP!** 1964 Radiogram Chassis. Stereo 3-wave bands, long, medium, short. 5 watts per channel. 6 valves, Latest Mullard. A.C. 200/250 v. Ferrite aerial. Glass dial. horizontal wording. Size 13 in. x 4 in. Aligned and calibrated. Concentric controls. Isolated chassis. Size 13½ in. x 9 in. high x 5 in. deep. Product of famous national manufacturer. Brand new and boxed. Maker's guarantee.

OUR price £13.10.0. List price £19.8.0. P.P. 5/6. Our Chassis List quotes prices—the keenest in the Trade. We are Main Agents for the complete range of Brittamer Chassis and Amplifiers. "Brittamer"—makers of Radiogram Chassis to the Top Names in Radio.

●**SCOOP!** Limited number only. Miniature Superhet 4 valve Portable Radios. Ferrite rod aerial. Hide leather case. Complete with valves, speaker and circuit. To clear **OUR price 50/- only.** Cannot be repeated. Speakers ex Equipment. 5in. 5/-, 7in. x 4in. 6/-, 6in. 6/6, 8in. 7/- P.P. 1/6 each.


S.A.E. enquiries please. Our Complete Lists 1/- only—credited against your order.

●**THE CHEAPEST, THE BEST, THE QUICKEST SERVICE.**

L.K. ELECTRONICS (Victoria) LTD.

17 GILLINGHAM ROW, WILTON ROAD, LONDON, S.W.1.

LISTEN ♦ LEARN ♦ PLAY

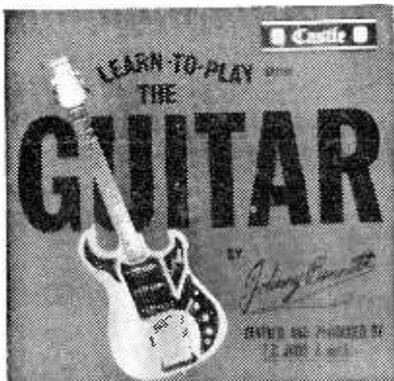

A FABULOUS 10 INCH L.P. RECORD WITH SIX COMPLETE GUITAR LESSONS FROM TUNING TO MODERN BEAT RHYTHMS!

YOU PLAY WITH THE RECORD—Learn tuning, chords, plectrum technique, modern beat and blues rhythms.

NO MUSICAL KNOWLEDGE. Just pick up your guitar and LEARN TO PLAY READY FOR ANY GROUP.

ELECTRIC GUITAR techniques used throughout record with BURNS guitars, including multi-track guitar recordings you can practise with too.

RECORD COMES COMPLETE WITH FULLY ILLUSTRATED TUNING, CHORDS AND PRACTICE CHARTS

RECORD No. LPG-1. PRICE 25s. (UK only) inc. p. tax, special packing and postage, from:

F. C. JUDD (Sound Recording) Ltd.

174/6, MAYBANK ROAD, SOUTH WOODFORD, LONDON, E.18.

(BUC 9315)

MAIL ORDER ONLY—CASH WITH ORDERS

NEW NEW

not just 1 but 2 NEW TUNER-AMPLIFIERS

model 127 Stereo £37.10.0 model 127M £26.10.0




Armstrong

Optional case (both models)
TEAK & VINYL HIDE £3. 10. 0
For full details, technical specification and list
of over 300 stockists, post coupon or write

Name _____

Address _____

PW.11.64 _____

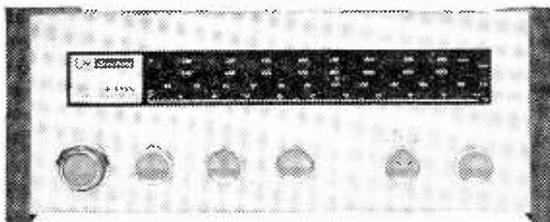

ARMSTRONG AUDIO LTD. WALTERS ROAD. LONDON N7

Wright + Connor

A COMMENTARY BY HENRY

PRACTICALLY WIRELESS

No. 3 Help!

"MY set won't go. What's wrong?" came the *cri-de-cœur*. Although there must be a strong temptation to answer "Kick it!" it says much for the panel of experts who advise our Editor that the reader in trouble is more likely to be gently quizzed on symptoms and guided as to tests.

The quiz may be quite explicit. When did the set fail? Did it succumb slowly or cut out like a snuffed candle? Any smell of burning? Anything lighting up? Any preliminary symptoms, strange noises, sparks, flashes, etc.?

The guidance is even more precise: exact tests are indicated to eliminate stages. Correct voltage readings—and, sometimes more important, voltage readings that may be expected when things are *not* correct—may occupy a page of notes.

And all for free!

Readers who have had occasion to solicit the Query Service will be able to bear this statement out. Some will probably bridle at the cheeky picture drawn below. They are the gentlemen who offer complete case histories of their receivers or who tell, in all the gory details, of the tests that proved ineffective. They would bridle even more at the suggestion that half their tests were not needed

and some of their conclusions could even have obscured the fault.

I am reminded of the reader who ripped his precious tape recorder to bits. The fault was a gradual one: first, recording was obviously weak and possibly noisy, although playback seemed normal. Then, as recording deteriorated, playback, too, began to fail. This must be a deep and serious fault, he thought, flourishing his screwdriver. By the time he had reached an irrevocable stage of dismantling he was forced to call for aid.

The expert at this point is rather reluctant to suggest the fault may only be a minor one. He uses the utmost tact when he says: "*Did you clean the recording head?*"

And, sure enough, that was the origin. A simple thou'-thick layer of oxide! But by the time our reader had reassembled and discovered where the surplus parts should have fitted he had a couple of real faults. His pile of correspondence is still growing.

Other correspondents omit the essential details: model and make of the receiver. Still more are impossibly vague about the fault. "*The set bursts into oscillation*", says one. "*There's a horrible noise*", says another, and "*The picture went all funny*", complains a third.

There are precise instructions about sending in queries. Each must be accompanied by the relevant coupon and a stamped, addressed envelope. Only one subject must occupy each query. But the Editor is too tactful to demand that the description both of the set and the symptoms should be sufficiently detailed to give his advisory panel half a chance at diagnosis.

There need never be any shame at having to appeal to our omniscient Editor. It isn't that he has a bottomless well of



His "in" tray overflows daily.

electronic knowledge beside his desk. But he does have a telephone—several in fact. And he does know who to ask when somebody cries in despair for that esoteric item of information which has eluded all the local dealers.

His answer may not come by return of post. Like the fan mail of a pop star his "in" tray overflows daily. He has been known to shy like a hedged pony at the sight of a Christmas postman. But, unlike the aforesaid fan mail, every query that reaches the office is dealt with, the stupid and the studious alike receiving the best attention.

When all else fails, and the combined efforts of Editor and panel cannot ferret out the vital fact, there is one last-ditch expedient. The desperate reader can insert his own advertisement or appeal to other readers through the correspondence columns. Obviously the former will be quicker; four bob a line is not much to pay when the family is clamouring for music and pictures. The vast readership of *Practical Wireless* and *Practical Television* makes it pretty certain that some Good Samaritan will come forward with the answer to the problem.

Which reminds me—anybody got a circuit of the Super 5-Star X-Band Special to spare?



Strange noises, sparks, flashes, etc?

The "Spectreuphon"

SOME IDEAS FOR EXPERIMENTS WITH CHROMASONIC DISPLAYS

BY I. J. KAMPEL

CONTINUED FROM PAGE 539 OF THE OCTOBER ISSUE

FIG. 8 indicates the circuit for the stereo Spectreuphon unit. The block diagram of Fig. 1b (page 536, October) indicates what is to be done. Basically there are two units as described last month, one for each channel. The left-hand channel controls the lights on the left of the visual unit, and the right-hand channel the lights on the right. Here, instead of six bulbs on each channel (treble, mid and bass), four are used, as there are six channels. In the second unit, Sk5, though controlling different bulbs, is as Sk1; Sk6 in a similar manner, as Sk2; Sk7 as Sk3. The fourth socket does not exist as it is directly coupled to Sk4, the common negative. The volume control potentiometers on the two units are ganged. The figure indicates crossover networks on each channel, to improve audio. If these exist at the speaker cabinets or are not required, simply connect the single speaker of each channel directly across the appropriate 50Ω pot.

To save space, the complete circuit has not been given, as the circuit is identical to sections on Fig. 2.

Visual Units

There are many ways in which the lights might be displayed. The author, however, favours the method to be described first.

A length of aluminium is bent to make a long reflector, and fitted into a rectangular tracking, which may be metal or wood (see Fig. 9a). Holes

of suitable size and spacings are then drilled in the reflector, and bulbs screwed in, and soldered in place if they are at all loose. The reflector itself will then form the common negative contact, with the various positive leads going to the point contact of the bulbs. The end elevation is shown in the figure, and the width should be about 3in.

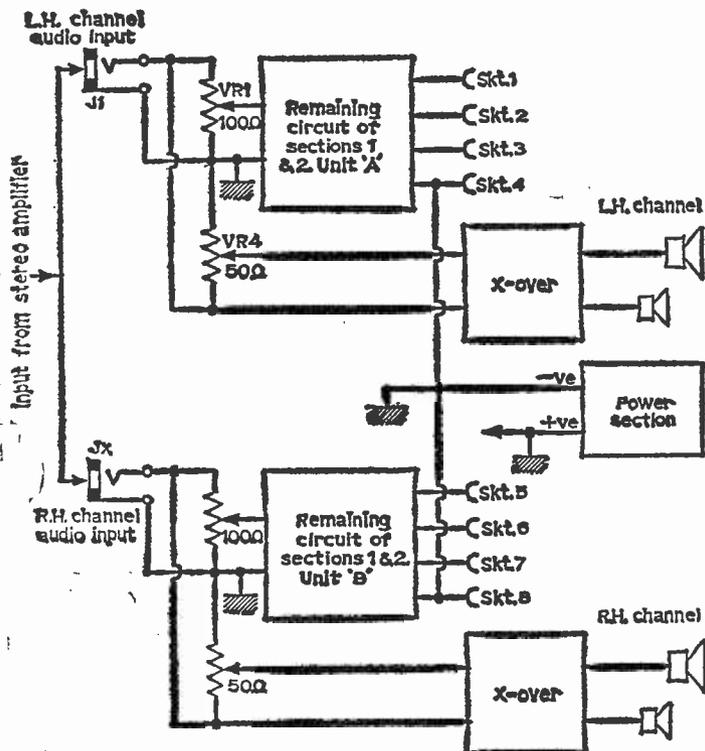


Fig. 8: The stereo Spectreuphon unit.

RETURN-OF-SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt ● Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

● MARTIN AUDIO KITS

High quality Transistor Amplifying Equipment. Following units now available. Input Selector Unit £2.7.6; Pre-Amplifier with Volume Control £1.7.6; Mixer Unit £3.19.6; Pre-Amplifier with Tone Control £3.2.6; 10 watt Main Amplifier £5.12.6; Power Supply Unit £2.12.6. Fully detailed literature available. H.P. Terms on any combination of units—ask for quotation.

● SPECIAL LOUDSPEAKER BARGAINS

E.M.L. 13 x 1/2 in. Elliptical, 10 watts, 3 ohms. 30/6. P. & P. 2/6. RICHARD ALLAN 12 in. 5 watts, 3 ohms. 27/6. P. & P. 2/6.

● STEREO COMPONENTS

Morganite Ranged potentiometers as specified for the Mullard circuits. ★ Log/Anti-Log, 500k, 1 meg., 2 meg. ★ Log/Log, 50k, 20k, 1 meg., 2 meg. ★ Lin/Lin 250k, 500k, 1 meg., 2 meg. All 10/6 each. Postage extra.

● GRAMOPHONE EQUIPMENT

ALL LATEST MODELS ALL POST FRBE	Cash Price	Deposit	Hire Pmtly	Purchase Pmts.
RECORD CHANGERS				
GARRARD AUTOSLIM (Mono PU fixed head)	£6.17.6	£1.12.6	6 of	£1
GARRARD AUPUSLIM Deluxe AT6 (Mono PU)	£11. 9.0	£2. 6.0	12 of	16/11
GARRARD AUPUSLIM AT6 (Stereo/Mono PU)	£12. 5.4	£2. 8.4	12 of	18/-
GARRARD AUTOSLIM (Mono PU plug in head)	£7.19.6	£1.10.6	6 of	£1.4.0
GARRARD A.T.5. (Mono PU plug in head)	£10. 8.2	£2. 4.2	12 of	15/4
B.S.R. UA14 (TCB Mono PU)	£6.15.0	£1.10.0	6 of	£1
B.S.R. UA14 Monarch (TCBS Stereo/LP/78)	£7.15.0	£1.18.0	6 of	£1.2.0
B.S.R. UA15 (TCB Mono PU)	£7.15.0	£1.18.0	6 of	£1.2.0
B.S.R. UA15 (TCBS Stereo/LP/78)	£9.15.0	£2. 6.0	6 of	£1.4.0
SINGLE RECORD PLAYERS				
B.S.R. TU12 (TCB Mono PU)	£3.17.6	£1. 4.6	3 of	£1.1.0
B.S.R. GU7 (TCB Mono PU)	£4.18.6	£1. 8.8	3 of	£1.6.8
GARRARD SRT10 (Mono PU)	£5.9.11	£1.12.11	3 of	£1.9.0

TRANSCRIPTION UNITS
GARRARD 4HF (GC8 PU) £16.12.6 £3. 6.6 12 of £1.4.5
PHILIPS AGH6 (SM PU) £12.12.0 £2.10.0 12 of 18/6
Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

● JASON F.M. TUNERS

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows:

FMT1, £6.12.6; FMT2 (less power), £7.15.0.
FMT2 (with power), £9.12.6; FMT3 (less power), £9.9.5.
FMT3 (with power), £11.7.6; Mercury 3, £10.14.6.
JTV/£14.12.6.

Hire Purchase Terms available. Ask for list.

● OUTPUT TRANSFORMERS

GIL. 50N: W0696A, W0696B, 60/8, post 2/6. W0892, 75/-, post 2/9. W0767, 32/6, post 1/6. W01796, 66/-, post 2/6. W1796A, 65/-, post 2/6. W01932, 92/6, post 3/-.
PARMIFK: P2367, 75/-, post 2/9. P4131, 75/-, post 2/9.
PARMFKO: P2625, 40/6; P2612, 47/3; P2611, 49/9. All plus post 2/9.
P2641, 30/6, post 2/-; A2521, 16/9, post 2/-; P2632, 43/-, post 2/6.

● MAINS TRANSFORMERS

GIL. 50N: W0741A, 75/-, post 4/-; W0839, 58/6, post 2/9; W01328, 39/6, post 3/9; W0132, 69/6, post 3/6; W01566, 96/-, post 4/6; W01341, 43/-, post 2/-.
PARMFKO: P2331, 37/-, post 2/9; P2330, 57/3, post 3/3; P2344, 80/-, post 4/-; P2330, 43/-, post 3/-; P2331, 59/6, post 3/3.

● PHILIPS ELECTRONIC ENGINEER KITS

The Philips EEK. A wonderful new kit for the beginner. Eight different circuits can be built including two radio receivers, a gramophone amplifier and Morse practice set. High quality components only are supplied including Mullard Transistors. No soldering required—all components can be used again and again. Price £4.19.6, post free.
The Philips A20 Accessory Kit. This is for use with the EEK Kit and it makes possible the construction of a further twelve circuits including an Electronic Organ and Inter-comm set. Important. The A20 Kit cannot be used by itself and is only suitable for use in conjunction with the EEK. Price £3.9.6, post free.
An illustrated leaflet is available free. Please send ad. stamp for postage.

★ TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £5 minimum of 4/2. Over £5 and under £10, 2/8. Over £10, no charge. Postage extra on CASH order under £5 except where stated. Postage extra on overseas orders irrespective of price.

● SPECIAL OFFER PICK UP CARTRIDGES

IONETTE 103 Stereo/Mono Cartridge, List 59/4. OUR PRICE 23/6. U.S.S.: TC8 M Mono, 19/6; GARRARD GC8 and GC2 Mono 15/-. All complete with fixing bracket and stylus. All Post Free.

● ILLUSTRATED LIST

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Amplifier. Fully detailed list on any of these sent upon request.

Instruction Manual: All Mullard Audio Circuits in "Circuits or Audio Amplifiers", 9/5. Post free.

● LATEST TEST METERS

	Cash Price	Deposit	Hire Pmtly	Purchase Pmts.
AVO Model 8 Mark III	£24. 0.0	£4.16.0	12 of	£1.15.2
AVO Model 7 Mark II	£21. 0.0	£3. 0.0	12 of	£1.10.10
AVO Multimeter Mark 4	£9.10.0	£1.15.0	12 of	14/4
T.M.K. TP10	£3.10.6	£1. 3.6	3 of	£1.2.0
T.M.K. TP58	£5.19.6	£1.15.6	3 of	£1.11.4
T.M.K. Model 500	£3.12.6	£1.15.6	12 of	19/8
TAYLOR MODEL 47A	£10. 0.0	£3. 2.0	12 of	15/8

Full details of any of the above supplied free on request. The AVO Models 7 and 8 are both latest models, from current production—not to be confused with Government Surplus.

● TAPE RECORDING EQUIPMENT

TAPE DECKS	Cash Price	Deposit	Hire Pmtly	Purchase Pmts.
ALL CARRIAGE FREE COLLARO STUDIO, latest model, two track, Bradmatic heads	£10.18.6	£2. 3.6	12 of	18/4
Four track, Marriott heads	£17.17.0	£3.12.0	12 of	26/2

MARTIN TAPE AMPLIFIER KITS
Tape Amplifiers
For Collaro 8311-V 2-Track £11.11.0. 8311-4 V 4-Track £12.12.0.
For Collaro 8319-CP 2-Track £8.8.0. 8319-CP 4-Track £9.9.0.
Drop through assembly for mounting 8319 Pre-Amp under Collaro Deck, £1.11.6.
Carrying Cases with speaker. For Collaro Deck and 8311 Amplifier, £5.0.
H.P. TERMS available on decks, amp. and cases. Ask for quote.

MULLARD TAPE PRE-AMPLIFIER KIT
We stock complete kits and all separate components for the Mullard Tape Pre-Amplifier. Fully detailed list available.

● "SYNCHROTAPE" RECORDING TAPE

Low priced British tape, all reels fitted with loaders.
Standard Play: 600ft. (5") 13/6; 350ft. (5 1/2") 17/-; 1,200ft. (7") 21/-.
Long Play: 900ft. (5") 17/-; 1,200ft. (5 1/2") 20/-; 1,800ft. (7") 30/-.
All Post Free.

● HI-FI LOUDSPEAKERS

GOODMANS: Axiotee 8 in., £5.5.7; Axiom 13 in., £6.5.11; 12 in. Axiom 30, £10.17.4; 12 in. Axiom 301, £15.4.8; 12 in. Audiom 51 Bass, £9.8.8; 12 in. Audiom 61 Bass, £14.7.8; Trelex Twister, £6.10.2; X05000 Crossover unit, £2.0.11.
WHITELEY: HF1016 10 in., £7.7.0; HF1012 10 in., £2.12.0; HF816 8 in., £6.6.0; TM16 8 in., £5.10.6; T10 Tweeter, £4.12.0; T359 Tweeter, £1.12.3; CX3000 Crossover unit, £1.1.3; CX1500 Crossover unit, £2.2.0. H.P. Terms available on all speakers.

● NEW MULLARD CONDENSERS

Mullard Miniature Foil and Polyester condensers as used in the latest hi-fi and transistor sets.
Miniature Foil: .001 ufd. working for Transistor sets, .01 mfd. 74d.; .022 mfd. 9d.; .047 mfd. 9d.; .1 mfd. 11d.
Polyester Tubular Capacitors: Moulded outer case designed to withstand accidental contact with the soldering iron. Tolerance 10%. 1.5v. range: .01 mfd., .022 mfd., .047 mfd. all 9d. each. .1 mfd. 1/2; .22 mfd. 1/3; .47 mfd. 1/6; .1 mfd. 3/4.
400v. range: .001 mfd., .022 mfd., .047 mfd., .1 mfd., .22 mfd. all 9d. each. .047 mfd. 1/2; .1 mfd. 1/3; .22 mfd. 1/6; .47 mfd. 2/5. Postage extra.

● MINIATURE ELECTROLYTIC CONDENSERS

Latest miniature types by Mullard and Radio Spares.
RADIO SPARES: All 15 volt, 2 mfd, 4 mfd, 5 mfd, 8 mfd, 10 mfd, 10 mfd, 22 mfd, 40 mfd, 100 mfd, all 2/3 each. Postage extra.
MULLARD: 4.7 mfd. 10v. 1/9; 10 mfd. 10v. 1/8; 10 mfd. 15v. 1/8; 10 mfd. 10v. 1/8; 25 mfd. 10v. 1/3; 25 mfd. 25v. 1/3; 32 mfd. 25v. 1/8; 32 mfd. 40v. 1/8; 100 mfd. 10v. 1/4

★ HIRE PURCHASE TERMS

Available on any item. Repayments over 3, 6 or 12 months as below. Three months: Deposit 6/- in the £. Service charge 5%. Minimum charge 10/-. Six months: Deposit 5/- in the £. Service charge 7%. Minimum charge 15/-. Twelve months: Deposit 4/- in the £. Service charge 10%. Minimum charge 20/-.

WATTS RADIO

(MAIL ORDER) LTD.

54 CHURCH ST., WEYBRIDGE, SURREY

Telephone: Weybridge 47556

Please note: Postal business only from this address
Callers welcome by appointment

NOW ANYONE CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO, TV, AND ELECTRONICS

Anyone can afford these amazing courses—anyone can understand this practical training—No complicated mathematics to hold you back—No old fashioned, obscure explanations to frustrate you!

The lessons are **CRYSTAL CLEAR, PRACTICAL, EASY TO MASTER AND USE**—Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert. Compare favourably with some courses costing very much more! By creating a mass market through large volume sales and eliminating individual letter writing we are able to pass on these savings directly to you!

Each course is printed on extra large quarto size sheets and bound into one manual to simplify handling and distribution.

Please select the course most suitable for your requirements from the following:

No. 1. RADIO COURSE. Fundamental facts—Electrons—Conductors and Insulators—Radio Batteries—Circuits—Magnetism—Ohm's Law—Resistor Colour Code—Chart—What resistor to use—Electro-Magnetism—Electromagnetic Induction—Self Induction—Radio Frequency Inductances—Capacity Coupling—I.P. Transformers—Radio Coils—Radio Capacitors—The Farad—Dielectric—Capacitor Colour Code—Alternating Current Theory & Filters—Reactance and Resistance—Charts to calculate Capacity Frequency and Inductance—Handy Radio Formulae—Practical Aspects of Radio Servicing—Radio Valves—Transistor Theory—N Type Germanium—P Type Germanium—Diode Action—Transistor Action—D.C. Stabilization—Transistor Bias Adjustment—R.F. Amplification—Superheterodyne Principles—A.V.C. Power Supplies—Meters—Multitesters and Valve Testers—Point to Point Servicing—Signal Generators and Signal Tracers—Using an Oscilloscope for Servicing—Alignment—Amplifiers and P.A. Equipment—High Fidelity—Advantages of Inverse Feedback—Speaker—Frequency Modulation—How to Obtain Radio Jobs. Price for the complete course. **ONLY 38/-**. Plus postage 1/6.

No. 2. ELECTRONICS COURSE. Includes most of the above lessons plus L.C. and R. Combined Circuits—Resonance Phenomenon—Behaviour at Resonance—How Meters Work—Making a Voltmeter—Ohm meter Connections—Valves—Electron Behaviour—Triode—Characteristic Curves—Power Supplies—Audio Amplifiers—Microspeakers—Frequency Coupling—Obtaining Grid Bias—Push Pull and Parallel—Phase Inverter Circuit—Radio Frequency Voltage Amplifiers—I.F. and Multiband Coils—Detection—Receiver Circuits—Results of Frequency Mixing—A.V.C.—Electronic Oscillators—Quartz Crystals—Radio Transmitter Circuits—Modulation and Tuning—Lines, Antennas and Radiation—Test Equipment—Using Meters—Electronic Test Equipment—Thyratron—Photo-Cell Equipment—Radio Compass—H.F. Heating—Electronic Shaping Circuits—Electron Microscope—Electric Strain Gauges—Inter-Communicators—Radio Servicing Techniques—Servicing Printed Circuits. Price for the complete course. **ONLY 39/6**. Plus postage 1/6.

Graduates of the Electronics Course can qualify for a certificate—details sent with each order.

No. 3. TELEVISION COURSE. Effect of Mis-adjusted controls—Pictures of various faults—Service adjustments—Circuit Faults indicated by a Poor Pattern—Finding Bad Valves by observing Picture Faults—Separate Channel I.F. System—Intercarrier I.F. System—Negative Picture—Interference—Antenna Principles and Practices—U.H.F. Transmission Lines—Facts About the T.V. Signal to Help you in Service Work—Synchronizing Separators—T.V. Interference Aids—All about Cathode Ray Tubes—Explanation of T.V. Circuits—Video Detector—Video Amplifier—D.C. Restorer Circuit—Automatic Gain Control Circuits—Oscillators—Deflection Coils—Automatic Frequency Control Circuits—Analysis of Stagger—Tuned I.F. Receiver—Analysis of Three Inter-Carrier Type Receivers—The Vertical Deflection Circuit—The Horizontal Deflection Circuit—Waveforms—Schematics of various sections of a T.V.—U.H.F. Converters and Tuners—T.V. Test Equipment and Alignment—Analysis of Various Problems. Price for the complete course. **ONLY 38/-**. Plus postage 1/6.

UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION You must be convinced that this is the best value you have ever seen in Electronic, Radio or T.V. Training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a full seven days.

IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE 70-PAGE, BOOK Tick on the coupon one book for each course ordered with full cash. **RADIO SERVICING FAULT FINDING BOOK. TELEVISION FAULT BOOK. OSCILLOSCOPE BOOK.**

These free books are authoritative, and loaded with information. Would cost at least 5/- each if bought separately—by sending cash you reduce book-keeping and other costs, which savings we pass back to you!

FREE TRIAL OFFER

Pay only 5/- per week if you wish. Clip coupon right now for this special offer To: Sim-Tech Book Company, Dept. CW6, Gater's Mill, West End, Southampton, Hants.

Please send the following courses for a full seven days' trial.

No. 1. RADIO COURSE. 37/6, incl. postage. No. 2. ELECTRONICS COURSE. 41/-, incl. postage.

No. 3. TELEVISION COURSE. 37/6, incl. postage.

(Free trial customers tick only one please).

If not delighted, I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price OR 5/- weekly until purchase price plus 2/6 service charge has been paid.

Tick here if enclosing full purchase price.

Please send me FREE, RADIO FAULT FINDING BOOK.

FREE, T.V. FAULT FINDING BOOK. FREE, OSCILLOSCOPE BOOK.

Amount enclosed £

I understand that you will refund this money in full if I am not 100% satisfied. Overseas customers please send full amount (including Ireland).

NAME

ADDRESS

City

County



65 or 25 GIVE A SOLON FOR CHRISTMAS



Do-it-yourselfers of all ages will welcome a Solon Electric Soldering Iron. The 25-watt model above, or 65-watt below, are ideal for radio work or household jobs.



Obtainable from your usual electrical or radio dealer from 24/8.

SOLON

Electric Soldering Irons

13/64

Amazing value!

Now add tape to your Hi-Fi outfit with the Gramdeck

TRANSISTOR PRE-AMPLIFIER

at a fraction of the normal cost



- ★ Patented printed circuit. Three transistors. Over 600 hours working with internal P199 battery. Compact metal casing (6 x 4 x 3 1/2 ins.). Simulation oak front panel.
- ★ Radio and low/medium impedance microphone inputs. Rotary function-selector switch, standard co-axial sockets. Fitted screened leads to amplifier and radio.
- ★ 60-10,000 cycles/sec. \pm 3 db. Signal to noise better than 50 db, below peak recording level. Maximum total distortion at peak level 2%, output 1 volt RMS.

COMPLETE £4.12.0
with battery (Post Free)

superb 'Lustraphone'

MOVING COIL MICROPHONE



- ★ World-famous make, nearly half list price. Omni-directional, moving coil. dual impedance—low or medium. 9 foot lead and co-axial plug.
- ★ Response substantially flat between 70 and 12,000 cycles/sec. Superb quality. Limited stocks. Send cash or P.O. to:

39/-

(Post Free)

Andrew Merryfield Ltd., Dept. PA821

29-31 Wright's Lane, Kensington, London W.8

to 4in. This tracking is then affixed to a wall of light colour—preferably white—by means of screws in the wall, fitting into key-hole slots on the tracking. Adjust bulb position for best focus. A multi-way cable then leads off to the *Spectreuphon*.

A length, or several short lengths of frosted glass, is placed on a lip at the bottom of the tracking. This glass should be the sort which either has 'ribs' on it, or the type which is covered with hills and indentations, helping to scatter the light. This glass far improves the effect of the lights, causing angular shades and pin-points of shades, rather than a general area of colour. The unit may be anything from 3ft. to 6ft. long, though 6ft. is a little long for the 18 bulb, mono version.

This system, throws down the wall—or screen below if a coloured wall—the various changing

The fluctuating, dancing colours then slowly revolve around the room, darting across all the walls, changing, subtly mixing colours of the rainbow, responding to the mood of the music!

Fig. 9c is another similar omnidirectional unit. Here, the device is mounted on the ceiling. Coloured lights on a dome-like surface, shine through a revolving, irregular, translucent plastic material. A hoop holds this firm if necessary, on the diameter, and the spindle passes through the centre of the lights dome, to the motor beneath. It should be remembered that a very slow motor is required. Lampshades, of indented plastic material, might be used for this purpose of deflecting the lights.

Again, another method that might be employed, is to mount the lights in a circle, and have a system of slowly revolving mirrors behind.

Fig. 9a (below): The stationary wall-mounted display unit.


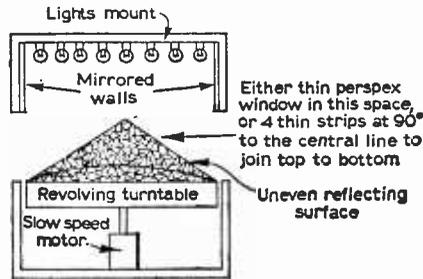
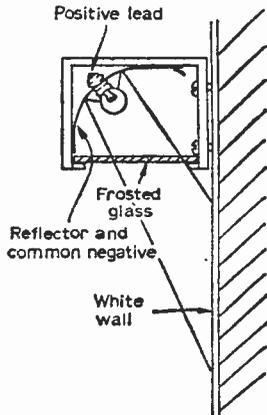


Fig. 9b (above): A lights display using a revolving reflecting surface.

Fig. 9c (right): Another revolving device which is suspended from the ceiling.

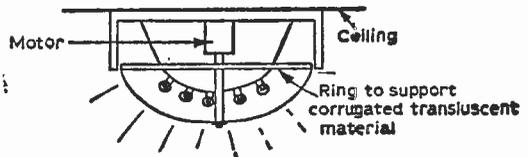

colours, so using part of a whole wall as a focal point.

Another method of presentation is to use the bulbs as projection lamps, and project the lights on the wall. Except where the colours cross, however, only plain patches of light will be obtained. A suitable lens system would be required for this method of course. To create a more interesting effect, if the bulbs shine on to a moving, irregular reflective surface, some very interesting results may be obtained.

Fig. 9b is an interesting method of display. Here the coloured lights shine onto a cone, the side of which is covered with irregular pieces of mirror glass. This cone, mounted on a turntable, is revolved slowly by an electric motor. The device is either hung, or placed at least four feet up from the floor—this will vary according to the angle of the cone—in the centre of the room. This will produce remarkable effects, though best suited for mono, as no difference would be noticed if it were stereo.

For an interesting, compact unit, if a little less dramatic, bulbs mounted behind a translucent screen of ground glass or perspex, can be quite effective (see Fig. 10). Perspex may be suitably ground, on one side, using 180 grade abrasive powder. Bulbs may have individual sockets, or be busbarred.

If a very thin piece of copper or phosphor-bronze is taken, bulbs may be soldered on to this as indicated in Fig. 11. Here, firstly a blob of solder is made on the sheet in the place the bulb is required. The underside of the sheet is then heated by means of a soldering iron, directly beneath the solder. This is best done with the aid of a firm metal plate, with a hole in it large enough to take the soldering iron bit. The bulb may then be pressed on to the sheet until it melts on, the iron removed as soon as it does this.


This sheet is then bolted on to a firm base-plate, and holes drilled through to take the side-contact (positive) wires, a hole beside each bulb. This is then placed behind the screen, with crinkled tin-

foil placed behind to help scatter the light. The base-plate is of course the common negative.

There are many different methods of display, however, for the stereo version, a system in which there is a definite left and right is more suitable, so getting the benefit of colour shift and positional emphasis. However, a six-colour omnidirectional method could be very effective.

Positioning of Finished Unit

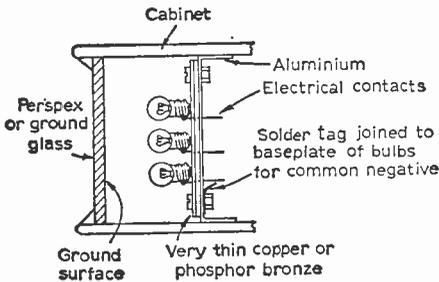The shaded areas on Fig. 12, indicate the areas effectively covered by each of the two speakers. Therefore, only the area which is covered by both (double-shaded) is effectively covered by both




the ideal listening position. Speakers should also be at the same level.

It is a pity that so many stereophonic units to-day, for the sake of compactness (and perhaps economy), house the whole unit in one cabinet, with the speakers sometimes less than 3ft. apart. This may seem very handy to those with no experience of stereophonic sound, but this means, that on a unit with speakers placed 3ft. apart, the ideal listening position is about 2½ft. away from the unit, on the central line between the speakers!

On the diagram, position 'a' is the ideal position for stereo listening, with positions 'b' next rated.

Fig. 10 (left): A compact arrangement using a perspex screen.

Fig. 11 (below): The technique of soldering the bulbs to sheet copper or phosphor bronze.

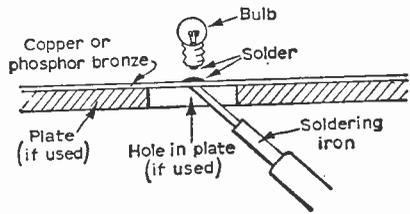

speakers. For this reason, listeners to stereophonic sound should be within this area. The distance between the two loudspeakers should not be less than 6ft., and in most rooms, not more than 12ft. If an imaginary equilateral triangle is drawn, with its two base corners the cones of the two loudspeakers, the third corner of this triangle indicates

Next comes any other position in the shaded area, preferably on the central line 'c'.

This positioning applies equally well for two-speaker mono systems as for stereo systems.

Unless an omnidirectional method of light display is used (such as the revolving reflector), this should be placed centrally between the two loudspeakers—this is most important in stereophonic systems to get the benefit of colour shift.

By the term "colour shift", it is meant that there will be a shift of colour from one side of the 'screen' to the other if there is a matching directional audio shift. This only occurs of course, when stereo-amplifier is used in conjunction with stereo-Spectrephon.

Choice of Speakers

Care should be taken in the choice of speakers. Table 2 should be taken as a rough guide rather than a ruling. Those systems marked * or D.N.C. should stick to 3 or 25Ω impedances, as these systems require divider network coils. These coils, if not home-made, are sometimes diffi-

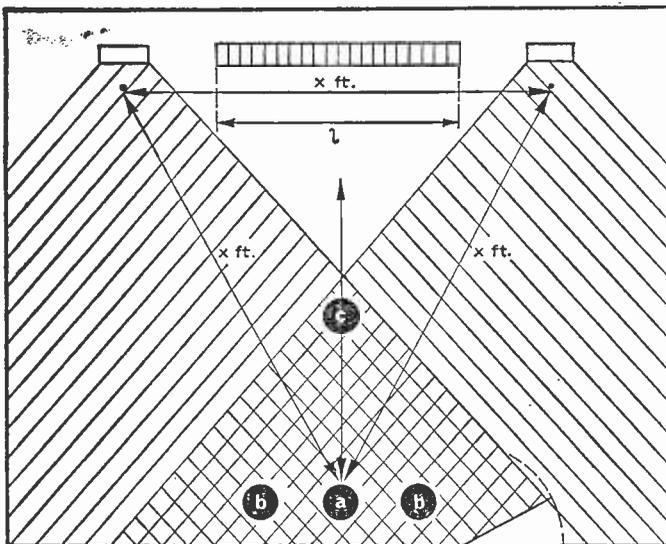


Fig. 12: The double-shaded section of this illustration indicates the optimum reception area for listeners to stereo reproduction.

Brand new individually checked and guaranteed VALVES

Table listing various vacuum tube valves with their types, manufacturers, and prices. Includes categories like AC/HL, AR, ARP, ARP2, ARP24, ARP34, ARP37, ATP, ATP7, B1, BL3, BR, BS, BR84, B2134, BT19, BT35, BT45, BT83, CB, CB33, CB37, CB77, CV102, CV103, CV4014, CV4015, CV4023, CV4046, CV31, D1, D41, D411, D413, D460, DAP96, DD41, DFT3, DFT20, DFT23, DFT3, DFT91, DFT92, DFT96, DK92, DK96, DL92, DL93, DL94, DL96, DL97, DL98.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves All U.K. orders below £1 P. & P. 1/-; over £1, 2/-; over £5, P. & P. free C.O.D. 2/6 extra. Overseas Postage extra at cost.

MARCONI COMMUNICATION RECEIVERS. CR.150. Frequency coverage 2-60 Mc/s in 5 bands. Two I.F.s. 1st 1,600 kc/s, 2nd 463 kc/s. Image signal protecting over 40 db up to 30 Mc/s and 20-40 db from 30-60 Mc/s. Self-checking calibration (built in calibrator). Stabilisation of supply and temperature compensation. Electrical and mechanical bandwidth. Metering and visual tuning indicator. Bandpass from 100 c/s to 10 kc/s in 5 stages. Acoustic filter associated with 100 c/s. Bandpass position for CW reception. Facilities for diversity reception. Excellent checked condition. £49. Mains P.S.U. by P.C. Radio. £4.10.0. Carriage 30/-.

CR.150/2. Frequency coverage 1.5-22 Mc/s in 4 bands all other features as in CR.150. Price £35. Carriage 30/-.

P.C. RADIO'S mains P.S.U. for above, 90/-. R.209 RECEPTION SET. A 10-valve high-grade superhet. Receiver with facilities for receiving R/T (A.M. or F.M.) and CW frequency 1 Mc/s-20 Mc/s. Hermetically sealed. Built on miniature valves and incorporating its own vibrator power-supply unit driven by a 6 v. battery (2) point connector included. The set provides for reception from rod, open-wire or dipole aerial with built-in loudspeaker, or phone output. Dimensions: Length 12in., width 8in., depth 9in. Weight 23lb. as new, tested and guaranteed condition. £23.10.0, including special head-phone and supply leads. Carr. £1. VARIOMETER FOR No. 19 SET, 17/6 each. P. & P. 3/-. TELEPHONE HANDSET. Standard G.P.O. type, new, 12/-. P & P 2/-.

CARBON INSET MICROPHONE. G.P.O. type, 2/6. P. & P. 1/6. WELL PROVEN RELIABLE COMMUNICATION RECEIVER P.C.R.2 (Made by Pye). 120 kc/s-350 kc/s. 525 kc/s-1600 kc/s, 6 Mc/s-22 Mc/s. Overall sensitivity 1-2 uV. S/Noise ratio 10 db at 6 uV. Circuit incorporates an RF stage, two I.F. stages, tone control, A.V.C. antenna trimmer, 6V6 output. Set in fully working condition together with headphones and speaker plug. £7.12.6. Carriage 15/-. Ditto but with built in power supply for 210/250 v. A.C. £9.19.6. Carriage 15/-.

SIGNAL GENERATOR MARCONI TF 995A-2. Arranged 1.5-220 mc/s in 5 bands. Output voltage variable in db steps from 1 uV to 100 mV. Carrier may be unmodulated, frequency modulated, amplitude modulated, or simultaneously frequency and amplitude modulated. Frequency deviation is variable from 25-600 kc/s for FM and modulation (internal or external) up to 50 x for A.M. Crystal calibrator for checking frequencies incorporated. Directly calibrated incremental frequency control. Fully checked and guaranteed. Price £88.15.0. Carriage in U.K. 30/-.


CONNECTORS FOR TCS RECEIVER, TRANSMITTER AND REMOTE CONTROL, with original plugs on both ends. New £1.17.6 each. P. & P. 2/6. EVERSHED MEGGER CIRCUIT TESTER. 2 ranges 0 to 1000Ω, 100Ω to 200,000Ω. With test leads, leather carrying case. Tested £4.19.6. P. & P. 3/6. 32/44ft. AERIALS each consisting of ten 3ft., 7in. dia. tubular screw-in sections, 14ft. (7 section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer etc. Absolutely brand new and complete, ready to erect, in canvas bag. £2.19.6. P. & P. 10/6. AR88D RECEIVERS. Fully reconditioned. £55; rebuilt models, £85; brand new, £95. Carriage paid U.K. CHR HIGH RESISTANCE HEAD- PHONES. New, 16/-. P. & P. 1/6.

PANEL METERS (found) table listing meter types and prices: 0-50 microamps 2 1/2 D.C.** 40/-, 0-100 microamps 2 D.C.** 35/-, 0-200 microamps 2 D.C.** 30/-, 0-500 microamps 2 D.C. 21/-, 0-500 microamps 2 1/2 D.C. 30/-, 0-1 mA 2 D.C. 21/6, 0-1 mA 3 D.C.** 35/-, 0-1 mA 3 D.C. 45/-, 0-5 mA 3 D.C. 29/-, 150-0-1,500 mA 3 D.C. 17/6, 0-15 v. 2 D.C. 28/-, 0-150 v. 2 D.C. 24/-, 0-500 v. (shunt) 2 D.C. 20/-, 0-10 kv 2 1/2 D.C. 63/-, **Weston's, as usually used in H.R.O. as "S" meter. **Projection type.

P.C. RADIO LTD 170 GOLDHAWK ROAD, W.12 Shepherd's Bush 9496 Open 9-5.30 p.m. Thursday 9-1 p.m.

THE WORD **MAXI-Q** IS THE REGISTERED
 TRADE MARK
 OF DENCO (CLACTON) LIMITED
 IT IS ALSO A GUARANTEE OF
 WORKMANSHIP AND
 TECHNICAL PERFORMANCE

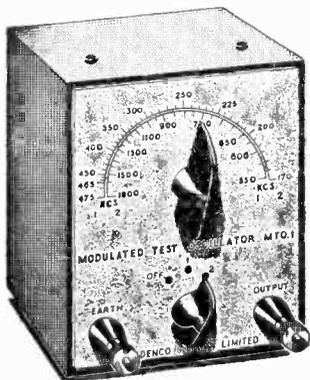OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 1s. 6d. FOR OUR GENERAL CATALOGUE AND TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST SEND 1s. 6d. IN STAMPS.



MODULATED TEST OSCILLATOR MTO.1

- ★ Provides modulated signal suitable I.F. alignment, also trimming and tracking R.F. circuits.
- ★ Frequency is continuously variable from 170-475 kc/s and 550-1,600 kc/s.
- ★ Suitable for the alignment of transistor receivers.
- ★ Operates from a single 9-volt grid-bias battery (not supplied) which is housed within the unit.
- ★ The case is manufactured from steel and is finished in silver hammer. The front panel is gloss black bearing white lettering. Dimensions are $5\frac{1}{16}$ in. x $4\frac{1}{16}$ in. x 3 in.
- ★ Supplied with full operating instructions.

PRICE £3/17/6

PLEASE SEND S.A.E. WITH ALL ENQUIRIES

DENCO (CLACTON) LTD.

(DEPT. P.W.)


357/9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Goldencore

A SUPERBLY DESIGNED HIGHLY SENSITIVE
 QUALITY AMPLIFIER INCORPORATING A PRE-
 AMPLIFIER AND TONE-CONTROL STAGES.

THIRTY AMPLIFIER

16 GNS.

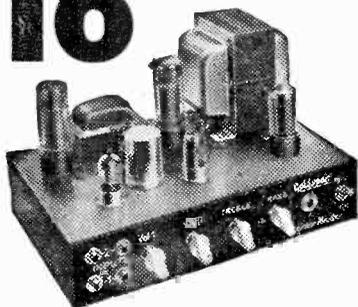

Full guarantee for 12 months. Excellent trade terms.

Trade and Export Enquiries to:

EON PRODUCTS LIMITED

EON WORKS 164 TOWN STREET RODLEY YORKSHIRE Tel. 34703

SPECIFICATION

SIZE: Approx. 12 in. x 9 in. x 9 in. Well ventilated metal cover available price 21/-.

A polished black control panel is fitted to the amplifier with distinctively marked control indications set in gold relief.

TEST FIGURES

FREQUENCY RESPONSE: ± 2 db. 25-20,000 c/cs. Bass Control. ± 12 db at 50 c.p.s.

NEGATIVE FEEDBACK: is employed with 20 db feedback in the main loop.

HUM AND NOISE LEVEL: 70 db down.

TREBLE CONTROL: Plus 12 db to minus 6 db at 12,000 c.p.s.

SENSITIVITY: 12 millivolts for full output. Thus being suitable for any type of mike or pick-up.

POWER OUTPUT: 30 watt.

POWER CONSUMPTION: 150 watts.

MAINS SUPPLIES: AC 200/230/250 50 c/s. A reserved power supply is provided for radio feeder or tremolo unit if required.

OUTPUT MATCHINGS FOR 3 and 15 ohm Speakers.
MULLARD VALVES: One GZ34, one ECC83, two EF86, two EL34.

cult to obtain, certainly more so to match any other impedance. With other systems, the impedance has little effect.

It is important to have good cabinets for 6in. and larger diameter speakers, to get full resonance benefit. With the two-speaker mono *Euphon* circuit, the importance of this can not be too greatly stressed. This unit will not give the required effect with an inadequate bass cabinet for the I.F. speaker.

Extra care in the choice of the h.f. speaker for this system is also required, especially if a speaker in-hand, is to be utilised. It must be remembered that when a small diameter speaker is normally quite capable of good reproduction, even at high volume, it may appear 'tinny' when fed selected h.f. signals, if they are too high for it to cope with. Then there is no bass to smooth things out, and save that speaker-cone consequent fretting. Only a small cabinet for the h.f. speaker is required in the *Euphon* system (Section 2/ Fig. 2).

Except in the case where the original single speaker on the existing mono source is being used, all speakers on this feeder unit, should be cut-out. Consequently, if there is no plug or switch on the speaker of the audio source, a switch should be fitted to cut it out.

If the divider network (Fig. 7) is to be used, it is best to actually mount this in its speaker cabinet, as otherwise a three-core cable is required. The coils should be mounted away from any metalwork, and function best if placed at right-angles to each other. This should also be remembered in the two speaker, two cabinet, mono *Spectrephon*, as Fig. 2.

A fact so often overlooked, is that for good reproduction, when great care is taken elsewhere, *screened cable should be used between speaker and source.*

Choice of Colours

Red, blue and yellow, the primary colours, would seem the most suitable for the three channels of this unit. With a stereo unit it is up to the individual to decide whether he uses six distinct colours, or three on each side. For colour shift, the latter would seem more suitable. The red and blue mix very well together, producing many different shades, but some are of the opinion that the yellow introduces too much light, and that orange is a little less severe. Experiment is the only way. Bulbs can be coloured quite successfully with dry-ink pads. A solvent known as carbon tetrachloride will remove this ink when it has dried, if required. Many other solvents will also clean the bulbs.

The switch S3 allows any of the colours to be on any of the ranges, with any other colour on any other range—in other words—all combinations of colours to ranges. A six-way six-pole switch may be used in the stereo version, or any other switching device to give other combinations.

Whether the colours are arranged in banks, in systematic patterns, or at random, is purely a matter of personal taste. The author prefers a systematic pattern.

TABLE 2

D.N.C.	System	No. of Speaker cabinets	No. of speakers	Diameter	
					Tweeter
•	Mono	1	1	6"-12"	
	Mono (x-over)	1	2	6"-12"	1½"-2"
	<i>Euphon</i>	2	2	8"-12"	2½"-5"
	Stereo	2	2	7"-12"	
	Stereo	2	4	7"-12"	1½"-3"
				(x2)	


Control Panel (Mono)

Two toggle switches—sound and light—are required. Also, four or five potentiometers, according to whether the *Euphon* circuit is used or not, and then there is the six-way rotary switch, for colour combinations, graded 1 to 6. A table might then be constructed for colours and ranges on the six positions. The audio circuit will function if the lights circuit is not even connected to the mains. There is therefore no need to disconnect when lights are not in use, to use the audio alone.

Control Panel (Stereo)

Two toggle switches—sound and light—are again required. Six potentiometers for sensitivity controls, one ganged potentiometer for volume control, and the rotary switch, have to be catered for. Again, audio is independent of mains.

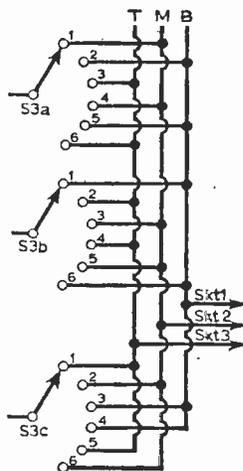In the mono "Spectrephon" circuit (Fig. 2) given in last month's issue, the switching of S3 a, b and c (Section 3) was unfortunately drawn incorrectly. A revised diagram of that part of the circuit is shown below.



We have been advised that the term "Chromasonic" (as used in the heading of this article) is, in fact a registered trade name and company and that any commercial equipment manufactured under that name has no connection with the present article.

In recent years, however, the word "chromasonics" has come into general use as descriptive of this type of electronic equipment.

wide-range ELECTRONIC TIMER

BY J. McCARTHY

THIS timer is designed to be cheap, and is extremely accurate. As it stands, it performs a timing function from about half a second to ten minutes. At the end of a run, one of two operations may occur, i.e. (a) a light, which was originally off, is pulsed on for about one second or (b) a light, which was originally off, is switched on for an infinite period till it is switched off manually.

Very few components are required and the timer can be built for less than 15s.. The original components were obtained from an Automat T3 timer for less than 2s. 6d, on the surplus market.

The basic circuit, in Fig. 1, is that of the ubiquitous cathode-follower bootstrap whose principle will now be explained: Initially, the current through the valve is small, giving a voltage almost equal to the cut off voltage of the valve (grid base) across r_k . A low d.c. voltage exists across C when it is discharged, the remainder being dropped across R. When V_c has risen by a volt, the grid potential rises by 1V and also the voltage across r_k rises by 1V. This means that the difference of voltage between V_c and V_{rk} is equal throughout the timing period which means C charges linearly. Also since V_c increases by the grid-base in one time constant and since the grid-base is roughly 15–25V for the valves used and the relay requires, say, a basic voltage of 30 to energise, between 2 and 1 1/5 of the length of the time constant RC is "passed through" before the valve operates sufficiently for the relay to energise. If a resistor of equal resistance to the relay coil is connected in series with it, the relay's operating voltage is effectively doubled, and since the capacitor's charging curve is approximately linear, the length of the timing period is also doubled.

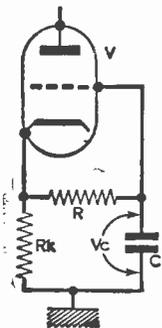


Fig. 2 shows: (a) the charging curve of a simple RC circuit, (b) the idealised curve of a cathode-follower bootstrap, (c) the actual curve and (d) the effect of doubling the relay's operating voltage. The slight curve in (d) is due to the combined effects of the curvature of the Ia-Vg curve of the valve, and leakages in C.

Fig. 1: The basic cathode-follower bootstrap circuit. (NO—normally open contacts; NC—normally closed.)

The simplest functional circuit is shown in Fig. 3, and operates as follows: when C1 has charged sufficiently for V1 to conduct, the relay falls-in, the contact RL1.NO short-circuits and discharges the capacitor C1, also the relay coil is disconnected by RL1.NC from the circuit. However, due to time constant RL1.C2 it remains in for a few seconds. This enables C1 to be completely discharged at the end of every timing period. This

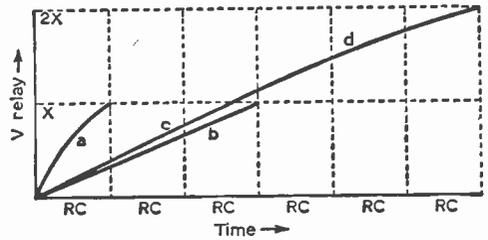


Fig. 2: Here relay voltage is plotted against time; a, b, c, d —see text.

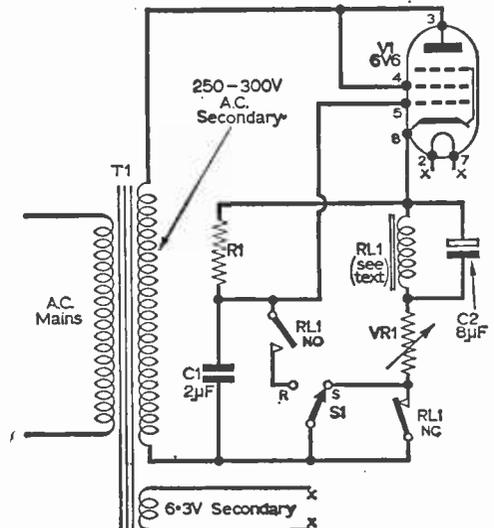


Fig. 3: A practical timer circuit.

TRADE ENQUIRIES
INVITED

RADIO CLEARANCE LTD.


Telephone: MUSEum 9188
EST. 35 YRS.

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE
27 TOTTENHAM COURT ROAD, LONDON W.1

“THE MINIGRAM” — LIMITED QUANTITY ONLY

Don't miss a chance like this!

Transistorised Record Player

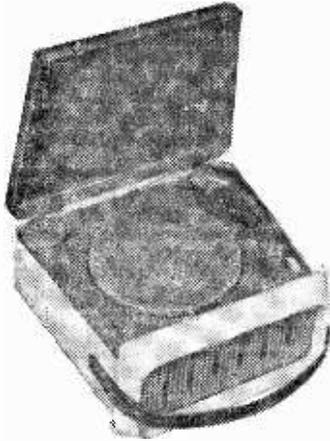

FEATURES

- ★ Ready-built amplifier with four first-grade Mullard transistors.
- ★ Plays 45 R.P.M. pop records.
- ★ Built-in automatic stop.
- ★ Lightweight and Portable.
- ★ Instruction leaflet supplied.
- ★ Crystal pick-up with expendable Stylus, GP50 Type.
- ★ Operates from a 9V battery (3/9 ext)
- ★ Available in two colours—cream/red or cream/blue.

- ★ A real “FAMILY FAVOURITE”.
- ★ Ideal for Teenagers.
- ★ For use ANYWHERE.
- ★ Hours of amusement for the younger members of the family.
- ★ Assemble one of these amazing Players in less than 30 minutes, supplied in 3 complete units with only 10 connections to make. Approximate dimensions 9x8x4in.

- A** Motor and pick-up deck.....(2/6 P. & P.) **39/6**
- B** Ready-built 4-transistor amplifier, complete with volume control and L'speaker (2/- P. & P.) **35/-**
- C** Portable two-tone case with handle, and expand metal fret.....(2/- P. & P.) **5/-**

ONLY 79/6
the complete Pckgs. (plus 5/- P. & P.) or any unit sold separately.

Loudspeaker Bargains Still Available

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER of the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

SCHEDULE OF LOUDSPEAKERS AVAILABLE

Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price
2	7000	80	8/-	3 1/2	9500	3	10/6	4	10000	3	11/6	6	9500	3	10/8
2 1/2	7000	35	8/6	3 1/2	9500	3	10/6	4	10000	15	12/-	6	9500	5	10/8
2 1/2	7000	60	8/6	3 1/2	7000	35	8/8	5	0000	3	8/-	6	9500	10	12/8
2 1/2	7000	80	8/-	3 1/2	9500	50	10/6	5	8000	5	8/-	6	8500	25	10/6
3	8500	3	10/-	4	7000	25	11/6	5	7900	3	8/6	6	9500	35	11/6
3	6000	5	8/6	4	6000	35	10/6	5	7000	5	8/8	6 1/2	9500	3	11/-
3	7000	5	9/-	4	7000	35	11/-	5	7500	3	9/-	6 1/2	9500	3	11/-
3	7000	35	9/-	4	9500	35	11/6	5	8500	3	9/6				

Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price
5 x 3	9500	3	9/-	7 x 3 1/2	9500	3	10/8	8 x 2 1/2	7000	5	9/-
6 x 4	6000	3	8/6	7 x 4	9500	3	11/-	8 x 2 1/2	8500	5	9/6
6 x 4	7000	3	9/-	7 x 4	10000	3	12/6	8 x 2 1/2	9500	3	10/-
6 x 4	8500	3	9/6	7 x 4	10000	15	13/6	8 x 2 1/2	9500	4	10/-
6 x 4	9500	3	10/-	7 x 4	9500	30	12/6	8 x 2 1/2	9500	5	10/-
6 x 4	9500	35	12/-	7 x 4	9500	35	12/6	8 x 2 1/2	8500	3	11/-
7 x 3 1/2	7000	3	9/6	8 x 2 1/2	6000	3	8/6	8 x 5	10000	3	13/-

ALLOW 2/- each Speaker for postage and packing, and please specify the exact requirements—the nearest available will be sent.

BOTH SETS STILL AVAILABLE HERE!

Ask for a demonstration in the shop.

“CAPRI”

Sensitivel
Super-selective!
Superb



Speaker!
NOW ONLY
79/6

(2/- P. & Pkg.)
Pocket Super-net MW and Freq-twitch LW
Size 4 1/2 x 2 1/2 x 1 1/2 in.
Constructional data 1/9 Post free.

The best and easiest transistor built-yourself sets available. Send S.A.E.

for FREE PARTS LIST
6 First Grade MULLARD Transistors
Diodes and all components
BRAND NEW and GUARANTEED

Choice of a dozen stations in daylight...


THE “CONTESSA” “QUEEN OF THEM ALL”

To clear existing stock

ONLY **£7.19.6**

(3/6 P. & Pkg.)

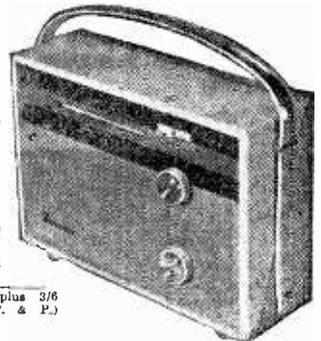PORTABLE and CAR RADIO
2 WAVEBAND SUPERHIT
Construction manual 2/10 Post Free.



Inclusive price for all associated components, case, battery and Instruction Book complete in every detail.
ANY PARTS SOLD SEPARATELY ON THE BUILD-AS-YOU-BUY SCHEME

CONTESSA Battery 3/6 extra. **£7.19.6** (plus 3/6 P. & P.)
CAPRI Battery 2/6 extra. **79/6** (plus 2/- P. & P.)

SELECTED BARGAINS

Beautifully geared AM/FM 2 Gang Condensers, 4/6; AM/FM IFT'S 465 kc/s and 10.7 Mc/s. 4/6 pair; Magmarox Crystal Tape Recorder Mikes. 12/6 set; 3 watt Stereo Amplifiers, complete, ready to switch on, 79/6; Sentercel rectifiers R3J2-D3/21Y1 2/8 each. DIODES—OA70, OA79, OA90, CG46H, GD10, 2/- each. TRANSISTORS—OC45, 1/6; PXA101, 3/9; AF115, 4/6. Sub min. Germanium diode 1/3, M1 diode, 6d, each. Silicon diodes, 200 p.i.v., 200 mA 1/- each, 500 p.i.v., 350 mA, 2/6 each.
Please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogues—our stocks move too quickly! Kindly make provision for additional postage and packing charges to avoid delay. Terms: Cash; With Order or C.O.D. on Orders over 10/-

UNUSUAL SINGLE SPEAKER SYSTEM

A CONCRETE COLUMN

An inexpensive column speaker constructed from a concrete pipe and fitted with a good 8in. or 10in. unit has attracted much interest and admiration because of its clean open sound. Complete kits of wooden fixtures are available including absorbent wadding and diffusing cone.



Price **£3.15.0** for 8" model. Recommended 8" unit—Super 8/RS/DD **£6.14.2** including purchase tax.

Price **£4.18.0** for 10" model. Recommended 10" units—Super 10/RS/DD **£10.18.8**; Golden 10/RS/DD **£7.17.5**; 10" Bronze/RS/DD **£4.12.9** *Prices include purchase tax.

Suitable concrete pipes can be purchased from builders' merchants at about 12/6 and 17/6.

Descriptive leaflet free on request from:



WHARFEDALE WIRELESS WORKS LTD.
IDLE BRADFORD YORKSHIRE
Grams: Wharfedel Bradford
Phone: Idle 1235/6

New TO NORTH LONDON A CONSTRUCTORS PARADISE THOUSANDS OF COMPONENTS IN STOCK!

Including: Valves, Transistors, Resistances, Condensers, Plugs, Sockets, Ferrite Rods, Dropper Sections, Knobs, Transformers, L.O.P.T., F.O.P.T., S.O.P.T., Mains, Stylii, Loudspeakers, Tapes and Spools, Indoor Aerials, Headphones, Earpieces, Record Decks and Many Others!!

YOU NAME IT - WE HAVE IT!!

SPECIAL OPENING OFFER ★ £5!

17" Second-Hand T.V.'s from £5!

SEE THEM WORKING BEFORE YOU BUY!

DOZENS OF NO-GOERS FROM 5/- (Full of useful spares) **Ideal for Beginners!**

JOHN TRAPP SERVICE SHOP
at 52 COLERIDGE ROAD, THE BROADWAY,
CROUCH END, N.8.

TELEPHONE; MOUNTview 1183

TRIPLETT 1632 SIGNAL GENERATOR. Handsome well designed instrument, ex U.S.A. Forces. 100Kc/s to 120 Mc/s on fundamentals. 10 directly calibrated ranges. 6 valves, buffer amplifier, well screened ladder, attenuator, variable carrier level (100µA monitor meter), stabilised H.P. Int. mod., Ext. mod., 1 Mc/s crystal mixing facilities for crystal check and for use as heterodyne wavemeter. In first-class condition, tested, with circuit attenuator, etc. In special portable case, operates from 115V A.C. 50 c/s (suitable auto transformer for 240V. A.C. operation. 17/6 extra). PRICE ONLY **£12.** Carr. 10/-.

SILICON RECTIFIERS. Type BY100 (4in. x 4in.) will handle 250 volts at up to 50 mA. Replaces any TV metal rectifier. BRAND NEW—not seconds, 7/6.

AR-88 VIBRATOR PACKS. For 6V operation. Complete with vibrator and OZ4 rectifier. NEW in original cartons, 17/6. P. & P. 2/6.

AR-88 SPARE VALVES. Complete Set of BRAND NEW individually boxed original valves (1-4). 50/- Plus 2/6 P. & P.

MOVING COIL PHONES. Finest quality Canadian with Chamols ear muffs and leather covered headband. With lead and jack plug. Noise excluding, supremely comfortable BRAND NEW..... 22/6, post 1/6.

MAGNETIC COUNTERS (ex-G.P.O.). 4 figures to 9,999. Coils 500 Ω for 24 V. operation. Tested. (No reset), 5/- each. P. & P. 1/6. SPECIAL OFFER! 10 for 30/-, P. & P. 6/-.

MICRO-AMMETER. 0-500µA. Made by R.C.A., Weston Westinghouse, and other famous American manufacturers. Circular 2 1/2in. flush panel mounting. Dials are engraved 0-15 0-300 volts. As used in the American version of the "19 SET". TESTED AND GUARANTEED 15/-.
0-1ma 2 1/2in. circular flush panel mounting. Resistance 75 Ω. 25/-.
0-300V. A.C. (moving from 2 1/2in. circular flush panel mounting. 22/6. Post and packing 1/- per meter.

HEAVY DUTY TRANSFORMER. Input 220 to 250 volts A.C. mains (tapped every 5 volts). Output 50V. at 15 amps. A really rugged job. Very conservatively rated. Size 7 1/2 x 5 1/2 x 7 1/2in. Weight **28 lbs.** Only **£5.19.6.** Carr. 7/6.

CHARLES BRITAIN RADIO LTD.

11 UPPER SAINT MARTINS LANE, LONDON W.C.2

TEMPle Bar 0545

Shop hours 9-6 p.m. (9-1 p.m. Thursday). Open all day Saturday

sequence only occurs with the function-switch at "R" (repeat). If the switch is at S (single), the relay "jams" with the external circuit on permanently. The circuit is "unjammed" by moving the switch to "R". The relay in the prototype was a 6.5kΩ relay marked JL.288567. This had the following contacts: 1 pair NO light duty, 1 pair NO heavy duty, 1 pair NC light duty. A Siemen's high speed relay with a resistance of only 500Ω was found to operate, although this introduces problems in that it only has a one-pole two-way light-duty set of contacts. This means that the function-switch becomes a 2p 2W type which may be purchased for about 2s. in toggle form, also the external contacts must be home-made, unless the timer is only to be used as a metronome. A suitable circuit for one of these relays is given in Fig. 4.

The method of finding the values of R1 and VR1 for Fig. 3 will now be given: Temporarily connect a 2kΩ resistor at "R" and connect a variable resistor with a value between 10kΩ and 20kΩ in the position of VR. Set VR1 to minimum. In this position, the timer should operate at about two times a second, increase VR1 slowly until the timing interval becomes unstable, then reduce VR1 till stability is again evident. Measure the value of VR1 with a 6.5kΩ relay, this was found to be 6kΩ. Resistors should be placed in parallel with VR1 till the maximum value of VR1 is similar to the measured value.

The required value of the shunt resistance is found by the following formula:

$$\frac{1}{R_t} - \frac{1}{V_r} = \frac{1}{R_p}$$

where R_t is the measured value. V_r is the variable resistor's maximum value and R_p is the value of the shunt resistor. This variable-resistor is now the timing-line control.

The resistor R1 depends on the length of the timing-period required, table 1 gives a list of resistors for R1 compared with time. The first three resistors give substantially the same time interval since most of the time is taken up by the time-constant $r1.a.c2$. If inversion of the heavy duty pair is affected, by converting to NC, this

Fig. 4: A suitable circuit employing a 500Ω Siemen's high speed relay.

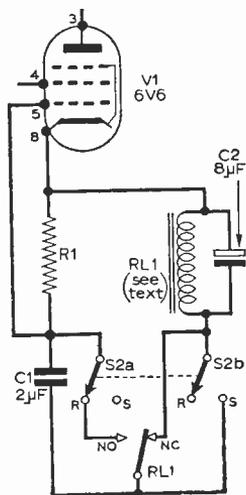


Table 1: Values of R1 in Fig. 3 for different timing periods.

R1	Minimum timing period—seconds	Maximum timing period—seconds
2kΩ	1/4	5/12
4kΩ	2/7	5/12
8kΩ	2/7	5/12
100kΩ	1	4
235kΩ	2	8
470kΩ	5	14
940kΩ	9	26
2MΩ	20	62

may be used as an enlarger timer giving times from 1 second to 7 minutes in five overlapping ranges.

The timing period may be increased far above this by increasing the values of resistor or capacitor (do not use electrolytics however and use only best quality paper capacitors). New electrolytics, however, may be used if great accuracy is not required but remember that they can vary +100% by -50%.

Should the relay be unable to fall-in, due to low emission of the valve, a small rectifier of about 20mA rating (which may be purchased surplus for a few shillings) may be connected in series with a 25kΩ preset potentiometer and placed between the anode and cathode of the valve. Set the preset to maximum, the timer function-switch to position "R", and make R1 between 100kΩ and 500kΩ. Decrease the value of the 25kΩ preset potentiometer until the timer starts to operate cleanly, reliably, after the same time interval (±10%).

The timer can be run off either a.c. or d.c. for h.t. although for reliable operation with relay resistances in excess of 4.5kΩ, at least 300V d.c./r.m.s./a.c. is required. A suitable rectifier circuit is given in Fig. 5. The poor smoothing is deliberate in that as the valve current increases the relay vibrates slightly (with the 8μF capacitor disconnec-

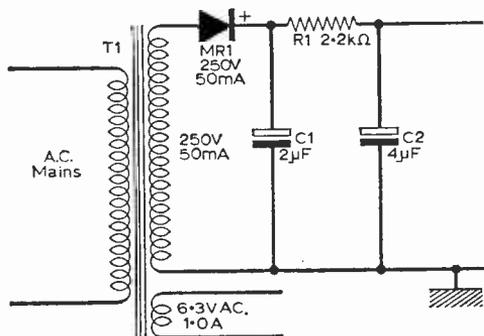


Fig. 5: A power pack for the timer.

ter, this is actually audible), the vibration serving to "unstuck" any contacts which may have been slightly welded together by sparking. If a d.c. supply is used, the low current rectifier and preset resistor necessary in cases of low-emission valves may be replaced by the preset resistor alone. With an a.c. supply, a transformer supplying 300V upwards is required.

In the actual circuit a 6V6 was used although any output tetrode or pentode would be satisfactory, although ventilation must be good if octal valves are used as they can get extremely hot. If a valve of the ECL class is used, the triode section may be paralleled with the pentode if the symptoms of low emission are shown—as an alternative to the rectifier and preset resistor combination.

Construction

The timer was built in a case of $8\frac{1}{2}$ in. by 6in. by $3\frac{1}{4}$ in. deep which is about the minimum size in which an octal valved timer may be placed, although a considerable decrease in size will be expected if a miniature valve is used.

Due to the shallowness of the box, slight difficulty is experienced in mounting the valve, this problem is most simply solved as follows: a valveholder with a metal rim is used, one end is bent upwards at right-angles and the holder bolted to the chassis by the end. The fixing of the relays varies with the type. Large relays are fixed by brackets, the approximate dimensions of which are shown in Fig. 6(a).

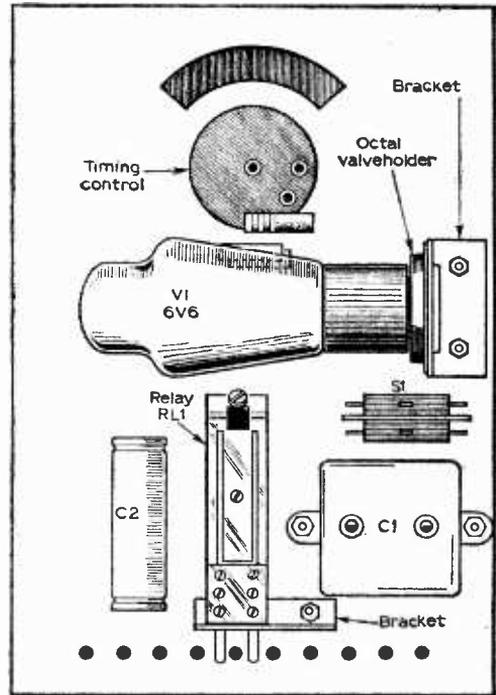


Fig. 7: A suitable layout of components for the timer.

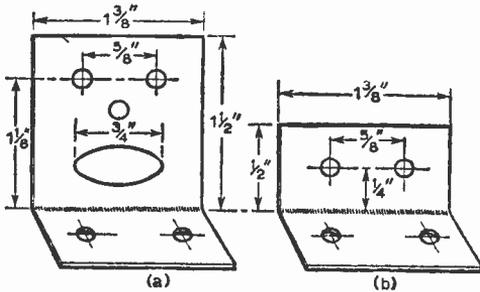


Fig. 6 (a): A bracket for mounting large relays; (b): dimensions of a bracket for a Siemens relay.

Siemens' high speed relays are fixed by brackets as in 6(b). The layout diagram is shown in Fig. 7 showing fixed positions of both octal and miniature valves. The layout is not in the least critical but excellent insulation of wires and valveholders is essential, tag strips should not be used and all connections should be floating. In the prototype, the leads going out—that is the heater, the h.t., the charging resistor R1, and the leads to the external circuit, went through holes in the lid of the box, to which all the parts are affixed, to a Belling-Lee plastic screw-connector on the lid.

As was earlier stated, the wires to which the charging resistor are connected are brought out externally and not switched from resistor to resistor. This method gives greater flexibility of

control of the timing period although there is no objection to switched control.

Finally, a note on the more unorthodox uses of this timer. If the insulation of a capacitor is considered faulty, it could be connected in place of R1 and the time measured between the insertion of the capacitor and the operation of the relay. If the interval is greater than half an hour, the insulation is at least $200M\Omega$ and may be considered safe as a coupling capacitor. It must be remembered that the charging surge of the capacitor may be sufficient to operate the timer once or possibly twice in quick succession if its value is greater than $0.01\mu F$. The actual testing proceeds immediately after this occurs.

Extension of Range I

If it is necessary to increase the range of a timer to several hours, as may be used for experimental purposes, it becomes expensive to supply paper capacitors of several hundred microfarads and a different approach to circuit design is required. In the circuit shown in Fig. 8 two timers are used in cascade. The first timer is set to "repeat" and gives pulses of say, 1 second duration, at say, 2 minute intervals. If a second timer set to, say 20 seconds is fed with these pulses, the second timer will operate at 20×2 minutes or 40 minutes. Similarly, a period of many hours may be recorded by means of this technique. Although an extra valve is required, the overall cost of an extra valve,

SOUTH SUPPLIES

(ELECTRICAL LTD.)


Post orders to 85, Old Kent Road, London, S.E.1

95, OLD KENT RD. S.E.1
72, BOROUGH HIGH ST. S.E.1.
90, HIGH ST., EDGWARE, ILFORD.
17, WOODFORD AVE. ILFORD.

BER 5810
HOP 2125
EDG 6751
GRE 4815

EECO 4-Ch. Transistorised MICROPHONE MIXER

49/6
Post paid

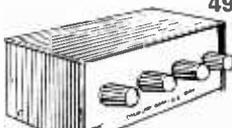

Give all your recordings that professional touch. The Eco mixer allows you to mix 4 signals such as—Mic-tape, records and tuner into a single output. Wonderful for groups, amateurs recorders, etc. Guaranteed to give hours of pleasure.


FAMOUS MAKES AMPS & PRE-AMPS

at Vastly Reduced Prices
3/4 watts, £4.15.0. 4/5 watts, £5.7.6.
5/5 Stereo, £11.5.0. 10 watts with separate Pre-amp, £14.3.6. 30 watt, £15.2.6. 50 watt, £20.14.3. Tremolo Unit, £3.15.6. Tape Pre-amp, £8.10.0.

MINIATURE PUSH-PULL AUDIO AMPLIFIER

4 Transistor
Output 200 mW. Low and high gain inputs to operate 3/6 speaker. Wonderful value **31/6** 2/-

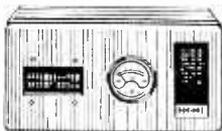Complete with operating instructions.
A GENUINE 4 AMP BATTERY CHARGER for Only 45/-, P. & P. 4/6.



Made in England to our own specification and fully guaranteed. High-Low-Med. change rate. 6V. or 12V. Selector Plug. 200/250V. Mains Selector Plug. 4 amp Cartridge Fuse protection, complete with mains lead charging lead and crocodile clips.

MAXWELL BATTERY CHARGER
For four P12 transistor radio, works direct from the mains **15/6** P. & P. Our Price..... 9d.

HIGH IMPEDANCE HEADSETS
2000 Ω or 4000 Ω Light-**13/6** P. & P. weight cream earpieces. 2/6

VANTONE MAINS RADIOS
5 valve superhet with built in Ferrite tuning bar.



£3.15.0 plus 3/9 P. & P. Fully Guaranteed.

all stations on Med/wave loud and clear inc. Luxembourg. Ideal for bedrooms kitchens or as a second mains radio.

INTERCOM BABY/ALARM



Fully transistorised. Size 4 x 2 1/2 x 1 1/2. Complete with 60ft. of twin flex. P.P.3 batt. Push to call on sub station. Push to talk on master and volume control. Our Price **55/6** P. & P. 2/6



TECH. MODEL PV-58 VACUUM TUBE VOLTMETER

Finest design for stable and accurate measurement. 1% tolerance on all resistors. Large design 4in. 200A meter for accurate readings 11 meg. ohm input.

Ranges:
— D.C.V. 0.1-5-15-50-150-500-1300V.
+ D.C.V. 0.1-5-15-50-150-500-1300V.
+ A.C.V. 0.1-5-15-50-150-500-1500V. RMS.
0.1-4-4-14-40-140-1400-4000 P.P.

Resistance: 2 ohms to 1000 megohm.
Decibels: —10dB to +65dB
Operation: 20/240V A.C. Size 7 x 4 1/2 x 4in.

Each tester is supplied brand new and fully guaranteed complete with probe and operating instructions.

The finest value in tester available at only Complete **£12.19.6** P. & P. 3/6 ex.



EECO MODEL S.E.100 TRANSISTORISED VARIABLE D.C. POWER SUPPLY

Meter Ranges: Volt 0-20 V.D.C. Current 0-20mA 0-200mA
Voltage Range: 0-20 Volts Continuously variable

Maximum Current Cap. 0-10V 200mA Intermittent. 0-20V 150mA continuous.
Impedance Source: Current position, 3.3 ohms. Voltage position 0.2 ohms.
Power Input: 220/240 V. Size 6 x 3 1/2 x 2 1/2 in.
Fuse: 0.5 amp slow blow in D.C. circuit.

The extremely wide variable voltage range, low A.C. ripple and source impedance of the S.E.100 makes it a most satisfactory power supply to operate transistor radios, hearing aids, pre-amplifiers, instruments and other electronic devices under repair. The S.E.100 can be used in television and radio servicing, as an A.C.V. or voltage source as a D.C. filament supply, operate relays, recharge small batteries and light electro plating as in dentistry. **£6.10.0** P. & P. 4/6. Fully guaranteed and complete with test lead, croc. clips and operating instructions.




EECO Model UD801 UNIDIRECTIONAL DYNAMIC MICROPHONE

dual impedance (600 Ω , 50 k Ω)
Frequency Characteristics: 100 Ω , 14,000 c/s. 15dB.
Sensitivity: —75dB \pm 3dB at 600 Ω —55dB \pm 3dB at 50K Ω 0dB over 15dB at 160°.

Directionality unidirectional 60° 2.000 c/s over 15dB at 160°. This is a new and high class dynamic uni-directional microphone, very high in sensitivity and excellent in frequency characteristics, maintains high stability even against poor ambient conditions. **£9.10.0** P. & P. Complete with 12in twin screened mic cable. Fully Guaranteed. 3/6



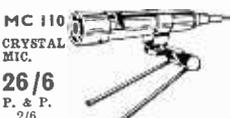
EECO Model MS4 FLOOR STAND
Height fully opened 55ins. Fully closed 32 ins. Three sections fully telescopic. 1/2 or 1in. mic adaptor. Price **39/6** ea. P. & P. Heavy cast iron base. Wonderful value.



MC 110 CRYSTAL MIC.
26/6 P. & P. 2/6 with on/off switch and holder. Satin chrome finish.



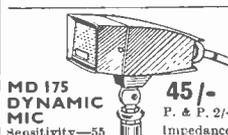DM 260 DYNAMIC MIC
Sub-miniature type, complete with stand. **52/6** P. & P. 2/-.



MD 175 DYNAMIC MIC
Sensitivity—55 dB at 1000 non-directional, latest American design. **45/-** P. & P. 2/- Impedance 50K Ω .

ACOS 45
Die cast, hand shaped body. Special offer 15/6 plus P. & P. 2/6


MULTI METER BARGAIN. Model TK20A
1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts 0/15 0/150, 0/1000V. D.C. Current 0/150mA. Resistance 0/100k. Size 3 1/2 x 2 1/2 x 1 1/2 in. Meter size 2 1/2 x 1 1/2 in. Complete with test leads and **31/6** Plus 1/6 battery. Wonderful value at..... P. & P.

RONETTE BINOFLEUD B.F.40 STEREO CARTRIDGE
Freq. Res. 30-12,000 c/s. Sensitivity 180m V/cm/sec. Load 10 Ω 100 μ Complete with Sapphire Stylus. OUR PRICE 12/6 each. P. & P. 1/-.

RONETTE STEREO O.V.S. TURNOVER CARTRIDGE
with 2 Sapphire Stylus. OUR PRICE 19/6 each. P. & P. 1/-.

EECO Model S.E.37B

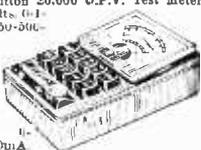Push Button 20,000 O.P.V. Test Meter
D.C. Volts 0-1
10.50-250-500-1000



A. C. V. 0-10-50-250-500-10000
D. C. V. 0-10-50-250-500-10000
Current 0-50A, 10mA, 50mA
Resistance 0-5K Ω -500K Ω -5M Ω
Inductance 50H-5000H. Capacitance 150pF-0.02 μ F. 11B. —20 μ + 221B 20 μ 3611B. The simplest and most efficient meter on the market at £22's below its true **£5.15.0** P. & P. 2/6

EECO Model S.E.550

100,000 O.P.V. PROFESSIONAL TEST METER



Highest accuracy:
3% on D.C.V. —amps —ohms.
4% on A.C.V. D.C. Volts:
0-0.5-2.5-10-50-250 at 100,000 O.P.V.
0-500-1000 at 25,000 O.P.V.
A.C. Volts:
0-2.5-10-50-250-1000 at 12,500 O.P.V.

D.C. Amps: 0-10mA at 500mV. 0-250 μ A-2.5mA-250mA-10 at 150mA.
Resistance: 0.20-2m-200K-20k 160k-16k-160 Ω Cent. Scale.
Decibels: —20 to 62 (0dB = 0.775V). **£7.19.0** P. & P. 3/-

HOMER

4 Transistor Tape Recorder
Power output 180mW
Freq response 500-40,000 C.F.s. Recording D.C. bias track W o a n d Flutter less than 2% Signal to noise ratio 25db (1,900c/s). Built in 2 1/2 in. p.m. speaker. Battery life approx 10 hours. Remote control switch on microphone active. Many more uses to this tape recorder. It also has a built in amplifier socket or tele-phone amplification. Many other uses. It comes complete with personal earpiece, 3in. Tape, Spare spool, Batteries. All this for **ONLY £21.5.0**, plus 5/9 P. & P. (Fully guaranteed).



SUN ACE

4 transistor new push button Super deluxe tape recorder circuit 4 transistors. Recording D.C. bias track built in 2 1/2 in. P.M. speaker. Recording time 17 mins. approx. on 300ft. tape. Batteries 1 U2 — 1 P.P.3. Complete with crystal microphone, personal ear phone, 200ft. tape and reel spare coil carrying strap and batteries. Wonderful value. At only **£4.15.0**, plus 4/9 P. & P. Fully guaranteed.



THE 'REALISTIC' 7

Transistorised Portable Receiver made to the highest professional standard. Comprises 7 Mullard Trans. plus Crystal Diode, 350 milliwatt output to 4in. speaker—L.F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. Two-tone plastic cabinet with handle—size 7 x 10 x 3 1/2 in. fitted socket for car aerial. Complete with full instructions.



MAY BE BUILT FOR £5.19.6 All parts sold separately Battery 3/9 extra.
P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)
 Also De Luxe Model with superior PVC covered wood cabinet and full view tuning dial.

ONLY £1 EXTRA All parts sold separately. Battery 3/9 extra. P. & P. 4/6.

T.V. POWER PACK

Takes a PY32 or 33. Contains: Filament transformer and smoothing choke, mains dropping resistor, Brimistor, smoothing capacitor 100-200-16-16mfd, 275V/w, 350V spec. Also 16-16 mfd, 275 V/w and sundry capacitors, resistors, etc. On metal chassis, size 6 x 4 1/2 in. x overall height 5 1/2 in. No circuit available. WIRECOMP'S 12/6 (valve) **23/6** valve **3/6** P. & P. PRICE

SUPER AMERICAN TAPE

LAFAYETTE BRAND, FULLY GUARANTEED

MYLAR BASE	ACETATE BASE
5in. Double play, 1,200ft. 15/-	5in. Long play, 900ft. 10/-
5in. Long play, 1,200ft. 15/-	5in. Long play, 1,200ft. 12/6
5in. Double play, 1,300ft. 22/6	7in. Long play, 1,800ft. 15/-
7in. Stand. play, 1,200ft. 12/6	
7in. Long play, 1,800ft. 19/6	
7in. Double play, 2,400ft. 25/-	
3in. Triple play, 450ft. 12/6	
4in. Triple play, 900ft. 22/6	
5in. Triple play, 1,800ft. 42/6	
5in. Triple play, 2,400ft. 55/-	
7in. Triple play, 3,600ft. 75/-	

P. & P. 1/- extra per reel. 4 reels and over Post Free.

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON W9

TEL: CUNNINGHAM 9530
 Hours of business: 9 a.m. to 6 p.m. Open all day Saturday.
 Opposite Paddington General Hospital.
 Buses 158 and 38 pass the door.

NEW SUPER MINIATURE POCKET RADIOS



THE SINCLAIR MICRO-6. Self-contained pocket radio. Size only 1 1/8 x 1 3/10 x 1/2 in. A marvel of modern miniaturisation—truly amazing performance. Without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data.

Can be built for only Mercury cell 1/11 extra (2 required). **59/6**

THE SINCLAIR SLIMLINE. The new 2-transistor pocket radio size only 2 1/2 in. x 1 1/2 in. x 1 1/8 in. Micro alloy transistorised and printed circuit. All components available separately. Easy to assemble. Can be built for..... **49/6**

IT'S FABULOUS!! THE TRANSISTORGRAM



A portable battery operated fully transistorised Record Player—for the music of your choice—any time any place! Made by famous British manufacturer, fully guaranteed. Size only 6 1/2 x 12 x 10 1/2 in., weight 10lbs. Operates on 6 U2 torch batteries, 4 speeds—194, 33 1/3, 45 and 78 r.p.m. Holding System record player unit with light weight pick-up fitted with CM-80 turn over ceramic cartridge. Output 500 mw to 5 in. ceramic magnet loudspeaker fitted into lid for maximum sound distribution. Cabinet constructed of wood, covered in two-tone (pale blue/gray) leather cloth. Fitted carrying handle and strong lid catches. High quality amplifier with tone and vol. controls gives excellent reproduction at all speeds. Plays 7, 10 and 12in. records.
 Today's Value **£6.19.6** Carr. & Ins. 7/6.
 WIRECOMP'S **£6.19.6** New boxed and guaranteed—exc. bats. PRICE

Transistor TELEPHONE AMPLIFIER

A must for business or pleasure. This neat little transistorised amplifier powerfully amplifies the incoming call and at last leaves you with both hands free while continuing your conversation normally. The pick-up is suction fixed to phone. Battery-operated at negligible cost. Fitted off switch for private conversation. Size 4 1/2 x 3 x 1 1/2 in. Complete with battery. WIRECOMP'S PRICE **69/6** P. & P. 2/6.

EXPRESS ELECTRONICS

32 SOUTH END CROYDON SURREY
 TEL. CRO 9186

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

101	5/6 6B4A	5/-	12K8G11/L	DL3	6/-	EL84	7/-	PY81	6/9		
102	7/6 6B5E	7/-	12Q7GT	7/8	DL86	6/8	8M85	10/-	PY82	7/6	
103	7/6 6BR7	8/9	12RN7	4/8	EB91	4/-	EY51	7/6	PY83	7/6	
1P1	7/6 6BW7	7/-	16A5	9/-	EB41	7/6	EY81	10/-	R19	5/6	
1ES	2/-	RD2	4/-	19A45	9/8	EBP80	5/6	EY86	6/9	85A1	9/6
1F11	7/6	8P12	4/-	15L9GT	5/-	ECN1	4/-	EZ40	5/6	TP15	27/6
1F09	6/6	6HG7	2/-	30M1	7/8	ECN2	6/9	EZ80	6/-	U32	7/6
1P1	7/6	6K7G	5/6	30L1	7/6	ECN3	6/9	EZ81	6/9	U78	5/6
1P10	5/6	6K8G	6/9	35L1GT	7/6	ECN4	6/9	EV82	9/6	U142	7/6
1P11	8/-	6Q7G	5/6	5763	7/6	ECN5	7/6	N17	5/6	U8C41	8/6
1R5	5/9	6SL7GT	6/-	50	6/-	EPF80	6/8	N18	5/6	U8C42	9/6
1R5	5/6	68N7GT	7/6	DAF91	5/6	EPF82	7/6	N19	6/-	U8F41	8/6
1T4	2/-	8V6G	7/6	DAF96	7/6	ECH42	9/-	N709	7/6	U4L1	8/6
1U5	5/6	6X4	5/-	DF91	2/-	ECH81	10/-	PC84	7/6	U41	7/6
3Q4	5/6	6X8G	5/9	DF96	7/6	ECL80	8/6	PC80	7/6	W17	2/-
3B4	5/6	8D3	4/-	DH76	7/6	ECL82	7/6	PC82	7/6	W67	4/6
3V4	6/-	9D7	9/6	EH77	5/-	EP41	9/-	PC82	6/9	W149	8/6
5Z4G	6/6	12AD6	7/6	DH142	8/6	EP90	8/-	PL84	5/9	X17	9/6
6AK6	5/6	12AT7	4/-	DH150	10/-	EP86	9/-	PL81	11/6	X142	9/-
6AL5	4/-	12AU7	6/9	DK91	5/6	EP91	4/-	PL82	7/-	X150	9/6
6A86	4/-	12AX7	6/9	EP86	7/6	EP82	5/6	PL83	7/-	Z77	4/-
6AT6	6/-	12BE6	4/6	DL92	5/6	EL41	9/6	PY83	12/6	ZD17	5/6

ASK FOR RESISTOR AND CAPACITOR CODE FREE WITH EVERY PURCHASE

Latest model Radiogram Chassis, L.M.S.G. ext. L5 and Tape sockets, complete with 10 or 12in. Speaker, £11.19.6.
 High Stability Resistors 1/2 W 5%, 50Ω to 1M, 9d. Midget Ceramics 500 v., 9d. Coax. Super Quality 1/2 in., 6d. yd. Flux 9d. Sockets 9d. Silicon H.T. Resist. 250 v., 300 mA 1/2 in. x 1/2 in. 8/6. Contact Cooled 250 v., 50 mA, 6/6. 85 mA, 8/6.
 NEW TRANSISTORS BY MULLARD. OC19, OC29, OC66, 25/-; OC4, OC45, 5/-; OC70, 8/-; OC71, OC72, 9/-; OC73 matched pair, 12/-; OC74, OC75, OC78, 7/6; OC81, 6/-; OC81 Matched pair, 12/-; OC170, OC171, 7/6.

VALVES MATCHED IN PAIRS


EL34, 27/6. EL84, 15/-, N709, 15/-, 6V6G, 15/-. Push-Pull O.P. Transformer, 21/-, 12in. 3Ω (or 15Ω) Speaker, 30/-, P. & P. 1/2in. P.M. Speakers 3Ω, 24/6. Baker's 'Selhurst' 12in. 15Ω 15W Stalwart, £55.0. 15in. Auditorium 15 Ω 50w, 18 gns.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94.....	17/6	EH42, EF41, EB41, DL96.....	29/6
6K8, 6K7, 6Q7, 8V6, 5Z4 or 6X8G.....	19/6	EH42, EF41, EB41, 1R5, 1T4, 1R5, 3B4 or 3V4.....	17/6

Postages and packing 6d. Over £1 post free C.O.D. 4/-

GUITAR AMPLIFIERS WITH TREMOLO

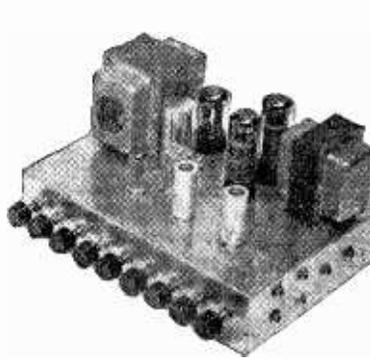

Five jack socket inputs, four with separate volume controls, and one input 'straight through'. All inputs are of very high sensitivity, only 10 millivolts input is required for full output, making it suitable for all types of guitars and microphones. Separate Bass and Treble

controls, giving a wide range of lift and cut. Separate master gain control. Tremolo speed and depth controls. Jack socket for remote tremolo switching. Outputs for 3 and 15 ohms speakers. Valves used in the 30 watt and 50 watt amplifier ECC83, ECC83, EL34, EL34, GZ94. In the 15 watt amplifier ECC83, ECC83, EL84, EL84, EZ81. An extra valve ECC83 is used in the tremolo circuit. The chassis is complete with baseplate and is solidly made of 18 gauge steel, finished silver Grey hammer. Size 12 x 8 x 6 1/2 inches high.

50 watt with tremolo	£21.10.0
50 watt less tremolo	£20.10.0
30 watt with tremolo	£15.10.0
30 watt less tremolo	£14.10.0
15 watt with tremolo	£12.10.0
15 watt less tremolo	£11.10.0

Add carriage 10/- any amplifier. Send for free descriptive leaflet.

STROUD AUDIO

FAGANHILL LANE, STROUD, GLOS. Stroud 387

2 μ F block-paper capacitor and relay is far less than one 300 μ F or thereabout, paper capacitor.

With reference to Fig. 8, the operation of the circuit is as follows: The circuit on the left of the dotted line is normal and gives pulses of duration fixed by C1 at intervals determined by VR1 and VR2. With each pulse, the contacts RL1 NO2 close and C3 gains a little charge each time until V2 conducts sufficiently for RL2 to operate.

The calibration of the unit is as follows: Calibrate VR1 and VR2 as normal, then adjust VR3 to minimum, at this point, RL2 should operate on the first click of RL1. Then increase the value of VR3 slightly till RL2 works on the second click of RL1 and mark with a symbol, such as 2X. Continue around the dial until calibration is complete.

The circuit to the left of the dotted line in Fig. 8 is in every way identical to Fig. 3 with the exception of VR1 replacing R1. VR2 is calculated by experiment as is VR1 in Fig. 3.

VR3 is decided by the factor of multiplication of this section of the circuit and by the duration. The RL1 NO2 contacts are closed. With a typical conduction period lasting two seconds due to C2 and a maximum multiplication of ten, the circuit requires a maximum time constant of 20 seconds. If a 2 μ F capacitor is used, a maximum resistance of approximately 2M Ω is required. To double the multiplication factor, twice the value of resistance or twice the value of capacitance is required. With the timing factor remaining con-

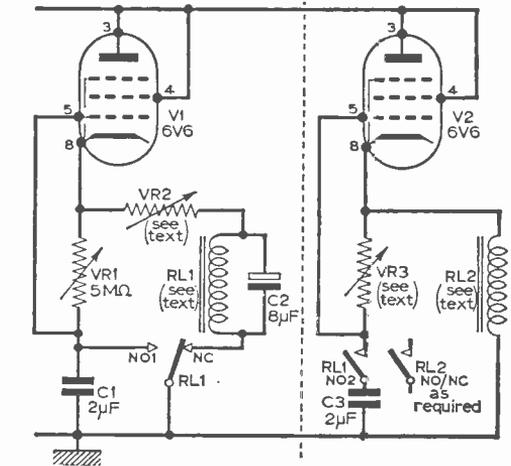


Fig. 8: Using two timer circuits in cascade to provide long timing periods.

stant, the resistance may be multiplied by the factor by which the capacitance is divided and vice versa. This means that the product RC remains constant where the timing period remains constant.


The coil resistance of RL1 and RL2 may be anything greater than about 500 Ω , but the higher the better, the same limitation regarding contacts applying as before.

FREE DOUBLE SIDED BLUEPRINT

to build this BEGINNERS' SHORT-WAVE SUPERHET

- ★ Plug-in coils
- ★ Separate power unit
- ★ 5-valve circuit
- ★ 1.6 Mc/s intermediate frequency
- ★ Panel aerial trimmer

and a simple ALIGNMENT OSCILLATOR

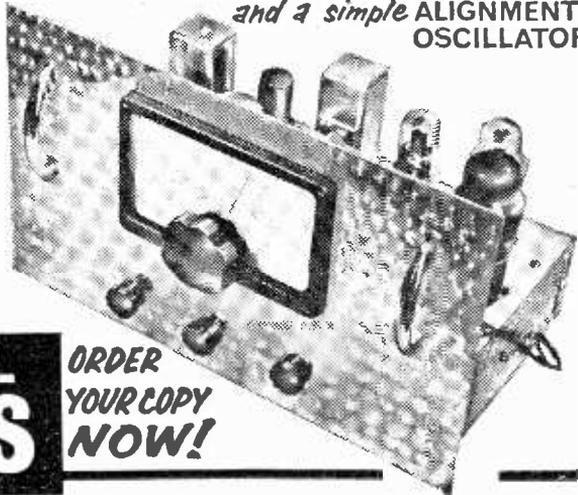


Also—details of an oscillator to align this and other receivers.

INSIDE NEXT MONTHS

PRACTICAL WIRELESS

ORDER YOUR COPY NOW!

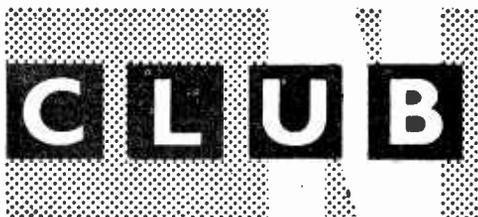

ACTON, BRENTFORD AND CHISWICK RADIO CLUB
 Hon. Sec.: W. G. Dyer, G3GEH, 188 Gunnersbury Avenue,
 London, W.3.

At the next meeting of this society, members will take part in a discussion on subjects of their own choosing. This meeting will be on 18th October.

BADEN-POWELL HOUSE SCOUT AMATEUR RADIO GROUP

Hon. Sec.: A. Watts, G3FXC, 8 Thornycroft Court, Kew Road, Richmond, Surrey.

A new scout amateur radio club has recently been formed at the headquarters of the British scouting movement, Baden-Powell House, London.

The group intends to take part in many ham activities and the permanent club station, G3TGS, will be used for demonstrations to encourage scouts to provoke an interest in amateur radio and to encourage contacts between scouts who are licensed operators.

Meetings are held on the third Thursday of each month and begin at 7.15 p.m. Recently members have been kept busy preparing GB3BPH for "Jamboree-on-the-Air" to be held on the weekend of 17th and 18th October.

BRADFORD RADIO SOCIETY

Hon. Sec.: E. G. Barker, G3OTO, 63 Woodcot Avenue, Baildon, Nr. Shipley, Yorkshire.

Members of this club attended the first meeting of the new session at Cambridge House, Bradford, on 15th September.

CHESTER AND DISTRICT AMATEUR RADIO SOCIETY
 Hon. Sec.: P. J. Holland, Field House, 19 Kingsley Road, Gt. Boughton, Chester, Cheshire.

Apart from the sale of surplus equipment held on the 8th, all of this Society's meetings for September were devoted to lectures. Altogether members attended three lectures on the 15th, 21st and 29th September. The lecture on the 15th was given by Mr. Gilbert of the G.P.O. and that on the 21st by Mr. B. Poole (G3JAZ) whose subject was "Modifications to the HRO".

GUILDFORD AND DISTRICT RADIO SOCIETY

Hon. Sec.: D. H. Mead, G3OXI, 41 Egley Road, Woking, Surrey

"Amateur Mottos" was the title of the talk given to members at the meeting on 1st September, when the speaker was Mr. S. W. Smith of the G.P.O.'s Radio Interference Branch.

Later in the month on the Guildford Model Engineering Society's Open Days, members operated the club station, GDRS, for demonstrations to visitors.

HARLOW AND DISTRICT RADIO SOCIETY

Hon. Sec.: G. O'Donald, Harlow Road, Roydon, Harlow, Essex.

The Harlow and District Radio Society Mobile Rally was held recently at a village near to Harlow. From 10 a.m. on Sunday, 27th September, mobile visitors were talked-in on 160m by G3ERN to enjoy a full and interesting day of events.

MELTON MOWBRAY AMATEUR RADIO SOCIETY

Hon. Sec.: D. W. Lilley, G3DFD, 23 Melton Road, Asfordby Hill, Melton Mowbray, Leicestershire.

Members of this Society met during September to attend the Annual General Meeting, held on the 24th.

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogdon, Halifax, Yorkshire.

To encourage enrolment for the R.A.E. course being held at the Percival Whitley College of Further Education, members of this Society manned a demonstration station there from 7th to 10th September.

Later in the month, on the 16th, members heard an interesting talk given by Mr. G. E. Craven on "Cathode Ray Oscilloscope". At the last meeting of the month members enjoyed a ragchew.

At a meeting on 21st October, members of local clubs will be invited to hear a tape recorded lecture made by that famous American amateur Mr. Stewart S. Perry (W1BB). "DXing on 160m" will be the title of Mr. Perry's recording and anyone interested in attending is invited to contact the Secretary to make suitable arrangements for seating.

READING AMATEUR RADIO CLUB

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven", 9 Holybrook Road, Reading, Berkshire.

The most recent of the "mobile picnics" to be held by this Club, was on 20th September, when members and their families welcomed visitors from other societies to the venue on the banks of the River

Thames at the Childe Beale Trust Pavilion, Lower Basildon, Berkshire.

The next meeting at the clubroom was on the 26th, when Messrs. Green and Davies demonstrated some of their equipment designed for the amateur.

RODING BOYS' SOCIETY

R. Marchant, 154 Essex Road, London, E.10.

Although membership of the amateur radio group of this Society is now large enough for the limited space available at their headquarters, visitors to the meetings will always be welcomed and sufficient interest from local enthusiasts would prompt a search for better facilities.

SLADE RADIO SOCIETY

Hon. Sec.: D. T. Wilson, 177 Dower Road, Four Oaks, Sutton Coldfield, Warwickshire.

On 4th September, members of Slade faced a team from Wolverhampton A.R.S. in a friendly quiz.

Later in the month Slade Radio Society held what they called a "Television Spectacular", when members, their families and visitors saw a live entertainment staged in the club's headquarters in Erdington, Birmingham. The show included a panel game, a guitar group and a brass band and was held on 18th September. Part of the audience saw the performances in a "studio" and the remainder viewed the whole show on television receivers in a separate room. Television cameras in the studio televised the show and relayed the pictures by closed-circuit television to the second audience.

October began for members of Slade with an exhibition of their equipment on the 2nd. There were two prizes to be won in competitions for the best made equipment, the Enterprise Trophy and the Craftsman's Cup.

SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pride, 100 Raikes Lane, Birstall, Leeds.

The meeting for 17th September was devoted to a junk sale.

The next meeting was on 1st October when members heard a lecture on "Transistors" given by Mr. M. Taylor.

WESSEX AMATEUR RADIO GROUP

Hon. Sec.: P. Cutler, G3MXF, 43 Langside Avenue, Wallisdown, Poole, Dorset.

This Group reports a current membership of over 50 of whom 31 are licensed amateurs.

The club's new Heathkit transmitter is on the air at every meeting under the callsign, G3FVU.

A GIFT ON THE RIGHT WAVELENGTH

You'll be sending your Christmas message loud and clear if you give friends who are fellow radio enthusiasts a Year's Subscription to PRACTICAL WIRELESS. It's a gift you know they'll appreciate... and every new issue will remind them afresh of your good wishes.

Simply send your friends' names and addresses, together with your own and remittance* to cover each subscription to The Subscription Manager (G.1), PRACTICAL WIRELESS, Tower House; Southampton Street, London, W.C.2. We will despatch first copies to arrive in time for Christmas, and send an attractive Christmas Greetings Card in your name to announce each gift.

* RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES): U.K. AND OVERSEAS £1 9s. 0d. U.S.A. \$4.25.


To make sure of your own copy why not place a regular order with your newsagent.

★ ★ **MANY BARGAINS** ★ ★
DUE TO MOVING TO LARGER PREMISES

MAKE 5 DIFFERENT TRANSISTOR RADIOS FOR

35/-

NO EXPERIENCE NECESSARY.

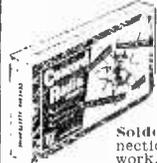


Soldering. Only 8 connections for first radio to work. Just look, you get Giant 4 colour box. 1ft. 2in. x 10in. x 2 1/2in. containing Radio Book, A.B.C. Plans, Cabinet, Carrying Case, Loudspeaker (alone 17/6) Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, screws, etc. **YES—EVERYTHING!** Loud, clear English and 1 Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS:** G.A.L.O.R.E. Mr. R. O'D. of London writes:— "I received your components and I must say that I am very satisfied with them. I have it already set up!" **COMPLETE HOME RADIO COURSE,** originally 85, **SEND ONLY 35/- plus 2/6 post etc. (C.O.D. 3/- ex.)**

NEW RADIO

ANYONE CAN BUILD IN 2-3 HOURS

19/6

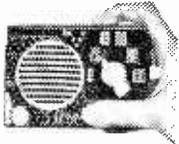

EVEN THE OLDER CHILDREN BUILD THEM!... no soldering—only 16 connections! then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/2in. Many Testimonials: M.H. of Bradford writes:— "I have just completed one of your sets successfully, it is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim-wit can follow them..." **Direct from Manufacturers to You. SEND 19/6 plus 1/6 post etc. (C.O.D. 2/6 ex.). PARTS AVAILABLE SEPARATELY.**

AMAZING CIGARETTE

RADIO!

ONLY 18/6



Yes, a perfectly ordinary packet of cigarettes—but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! **Still holds 10 Cigarettes**—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. **No soldering.** No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file, Mr. D.B. of Huddersfield writes:— "I have fitted the parts in and it is working wonderfully..." **ALL PARTS** including Semi-Conductors, A.B.C. Plans, etc. **ONLY 18/6 plus 1/6 post, etc. (C.O.D. 2/6 ex.). (Parts available separately).**

READ WHAT SATISFIED CUSTOMERS SAY

R.C. of HARRINGAY writes
Received with thanks Skyrama
... Very pleased. Working well.

L.S. of LONDON W.8 writes
... given it a good try out
and I am very pleased with the results.

D.R. of GLASGOW writes
... it is a lovely little thing
and as clear as a bell.

J.W. of BRIGHTON writes
... I have recommended your
radio to many of my friends.


B.M. of HARROGATE writes
... I would like to thank
you ... It is a real bargain.

S.B. of SOMERSET writes
... delighted with this radio
... glad if you could send
one more.

T.F. of STEVENAGE writes
I would just like to say how
pleased my son is with this
radio.

W.H. of MIDDLESEX writes
Thank you for my dear
little radio, it is a real
treasure to me.

MINIATURE SPY CAMERA

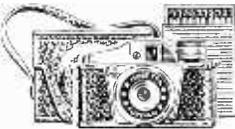

ONLY 19/6 NO MORE TO PAY


World shattering Purchase by our FOREIGN AGENTS makes this exclusive yours for **ONLY 19/6**. This exciting little 2 speed camera is not a toy but a precision-made photographic instrument in chromed steel and leather with minute milli-Magnifying Lens—each 14mm. film takes 10 pictures—size 1 1/2 x 1 1/2 x 2in—**Only 19/6, P. & P. 1/6 ex**
FREE Leather Carry-case. Six Rolls of Film.

TRANSISTOR POCKET RADIOS



ONLY 28/6
No More To Pay

BULK PURCHASE ENABLES US TO MAKE THIS FANTASTIC OFFER—AND WITH MONEY BACK GUARANTEED!
The "SAN REMO"
... so tuned that it brings the voices of star entertainers and vocalists dramatically to life—in your home, office, etc. Only 4 1/2 x 2 1/2 x 1 1/2in. Fits easily into your pocket or handbag. Works for months off 1.2 battery. Should last a lifetime, any one can assemble it in an hour or two with our easy plan. Miniature speaker, carrying case—everything only 28/6, 2/6 P. & P. C.O.D. 2/6 extra. (Parts can be bought separately.) Limited period—so rush your order before it's too late. DEMONSTRATIONS DAILY.

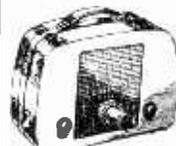

THE MINUTE TRANSISTOR RADIO MIAMI ONLY 17/6

Unbelievably small—outrageously cheap. You will be amazed at the fine quality of tone and volume of this great little radio. **Only a fantastic 3 1/2 x 2 1/2 x 1 1/2in.** the MIAMI will bring you great entertainment for months on an 8L battery. Simple assembly plan with each set. **ONLY 17/6, YES 17/6. Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.**

AMAZING NEW INVENTION AUTOMATIC CAR LIGHTER ONLY 10/-



We have been lucky enough to purchase 1,000 only of the fully automatic Car Cigarette Dispenser/Lighters because of a frustrated export shipment. Originally made to sell at about 45/-! Robust and ingeniously designed in heavy chromium. Holds packet of cigarettes (any make and size) you reach out with one hand, press a button and a lighted cigarette is in your hand! Can be fitted by anyone in 2-3 minutes. For 6 or 12 volts full connecting details—only one wire to connect! Each one in own coloured box, brand new and untouched. **Only 10/-, add 2/- P. & P. (C.O.D. 2/6 extra).**

READY TO PLAY

TRANSISTOR RADIO FULLY TRANSISTORISED SKYROMA Mk. 7. This latest 1964 model is cheered by experts for its fantastically low price. Built in two-tone case, size 4 1/2 x 2 1/2 x 1 1/2in. Receives M.W. stations loud and clear. Every radio is fully tested before despatch. Price ready built 25/-, P. & P. 1/6 extra. Free earpiece with set.



FOR ONLY 25/-
No more to pay

Fabulous ST. TROPEZ MK. 6

The Sensational Pocket Radio



This fantastic offer will amaze you—the lastingly compact ST. TROPEZ, measuring 4 1/2 x 3 x 1 1/2in, receives perfectly in bedroom, office or garden—over all medium waves including Luxembourg. Under 1 1/2 per hour running cost. **ANYONE** can assemble it in one or two hours using our simple A.B.C. plan, 25/- P. & P. 2/- extra. (Parts can be bought separately.)

LETTERS TO THE EDITOR

THE ROLE OF BROADCASTING

SIR,—I heartily agree with your editorial on the role of broadcasting (July P.W.). There is undoubtedly a large audience for continuous pop music which must be satisfied. What disturbs me is the fact that, hiding behind a cloak of respectability and desire to serve the public interests while maintaining the highest standards, the BBC spends very large amounts of money on pop artists and programmes of popular music in an attempt to compete with the existing commercial stations. Let there be an end to this hypocrisy! A commercial network using authorised frequencies should be set up to provide programmes of continuous pop music. The BBC should then channel its resources into programmes of a high standard which inform and educate as well as entertain and thus provide a service which does fulfil the true function of broadcasting.—**J. A. D. LOWRIE** (Edinburgh 12).

THE GOOD OLD DAYS

SIR,—I expect the photograph shown on this page will interest some of your readers. It is a copy of a very old print that I made of my set when the BBC first started up. I applied for and obtained an experimental licence. My first sets were crystal with basket coils and I made up several of these and sold them to friends. My photograph shows a straight three, h.f., d., l.f. For h.t. I used lots of 4.5V torch batteries.

I also made a very successful one valve crystal reflex which I turned into a portable set. With accumulator and torch batteries it almost needed a porter to carry it and I was granted a separate licence for it when I took it to Leeds on holiday.

One memorable night I recall is when I sat up to hear the first BBC relay broadcast from America. Those were the days when I was supposed to be experimenting for the elimination of atmospherics!—**F. GRIFFITHS** (Middlesex).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents.

A READER'S THANKS


SIR,—Recently I had a request published in your "Letters to the Editor" page asking for information concerning the No. 19 set.

The response to my request has been tremendous and I would like, through your pages, to express my sincere thanks to those many readers who have helped me.

Although I have answered and am still answering letters received, would those readers who do not receive a letter within the next few weeks please accept this as acknowledgement of their services (some readers will already have received letters) as I have recently been transferred and fear that I may have mislaid some of the letters received.—**T. L. RICHARDS** (South Canterbury, New Zealand).

H.R.O. BANDSPREADING

SIR,—I have been a keen H.R.O. owner for some time now and I know it is a grand receiver for the SWLs as well as the ham. However, I wonder if any reader of P.W. has ever thought of adding a four-gang bandspread capacitor in parallel with the main tuning gang. I came across the idea when I purchased a few extra bandspread coils for my set. On trying two of these coils I found the bandspread set screws in all but one of them were

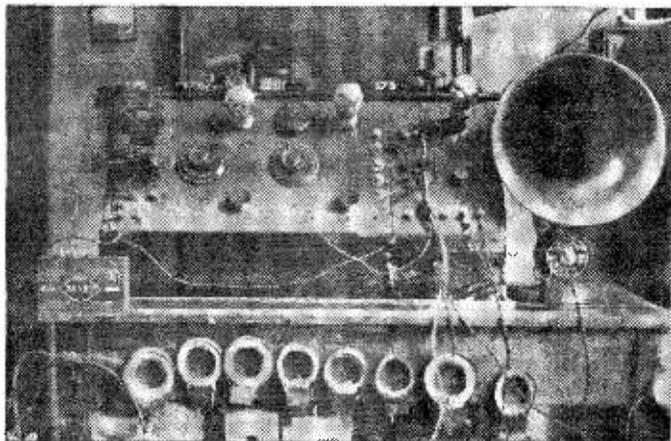

The majesty of a bygone age: this magnificent receiver was built by F. Griffiths in the earliest days of the BBC.

RADIO SOCIETY OF GREAT BRITAIN



International
RADIO

COMMUNICATIONS EXHIBITION

SEYMOUR HALL, SEYMOUR PLACE
MARBLE ARCH, W.1

**OCTOBER 28th to 31st (Wednesday
to Saturday)** 10 a.m. to 9 p.m.

FIFTH ANNIVERSARY FLEET AIR ARM DISPLAY OF
AIRCRAFT CARRIER RADIO CONTROL ROOM
POST OFFICE ENGINEERING, ROYAL AIR FORCE, ARMY
DISPLAY & DEMONSTRATIONS

COMPETITIONS OF HOME CONSTRUCTION EQUIPMENT

LATEST RECEIVING & TRANSMITTING SETS

NEW TV & V.H.F. AERIALS and MASTS

EDUCATIONAL & BOOKSHOPS DISPLAY. MOBILE EQUIPMENT

**Win £140 Hammarlund HQ 170A
Latest Communication Receiver**

(EXCHANGE THIS ADVERTISEMENT FOR ENTRY FORM AT DOOR)

ADMISSION **3/-**

loose, the threads being stripped completely. Putting the coils back in the H.R.O. resulted in a lot of crackling in the speaker and I found that the loose screws were the cause, hence my thought of trying an alternative method of bandspreading.

I think the value of the H.R.O. tuning capacitor is 225pF. The problem is what value of bandspread capacitance would be needed to obtain the desired results?

Perhaps one of your readers has already made this modification to his H.R.O. receiver and would be good enough to let us SWLs have a bit of gen. on same as I am sure that many readers of *Practical Wireless* who have an H.R.O. would welcome this information with open arms.—A. TAYLOR (Blackburn, Lancashire).

PRE-WAR FIELD DAYS

SIR.—It was indeed delightful to read P. O. Hubbart's letter in the August issue of P.W. about pre-war field days.

I believe that the field day in 1938 was my first and that I went out to Shirley Hills with G3FP. I was an active SWL in those days and a keen radio enthusiast, Ron Haddow, used to pick me up in his Aerial four-square sidecar and we would go to the Thornton Heath Short Wave Society meetings.

I have not heard from Croydon hams for many years, although I have had the pleasure of contacts with G5BZ and G61X since coming to South Africa.

I believe that G4AA was lost in a Beaufighter in the early days of the war and that Alvar Liddell became a budding baritone and made several records.

I am not active but still hold a call sign—ZS11Q—and I was formerly ZS5YF and G3BYF. I do dabble with radio occasionally and I really would welcome a line or two from some of the old-timers, and the SRCC meeting place at South Croydon would certainly be in for a visit should I ever manage a trip to Britain.—P. J. W. SAWYER (98 Woodley Road, Plumstead, C.P., South Africa).

CORRESPONDENTS WANTED

SIR.—I am about to build the G.P. Communications Receiver described in the January, 1963, issue of P.W. and would like to correspond with any reader who has already built this receiver.—H. BINFIELD (4 Elm Road, N. Colerne, Chippenham, Wiltshire).

SIR.—I would very much like to hear from other readers who have an interest in DX-ing and radio construction and are about 17 years of age.—DESMOND WALSH (Ballylynch, Carrick-on-Suir, County Tipperary, Ireland).

SIR.—I would like to correspond with someone of my own age (14) and in any country. I am very interested in transistor circuitry.—RONNIE SNG (327-H Potong Pasir, Singapore 13, Malaysia).

SIR.—I would be delighted to correspond with any other P.W. reader of about my own age (15) on anything concerning radio. My main interest is SWL.—PHILIP REILLY (62 Grantham Street, Kensington, Liverpool 6).

SIR.—I am interested in electrical and radio service technology and would like to correspond with radio service men from any country.—V. A. SUNDARAMURTHY, B.Sc. (13 Veeraperumal Koil Street, Mylapore, Madras 4, S. India).

SIR.—I started radio when I was seven. I am now 11 years old and would like to correspond with any radio constructors of my own age.—TIMOTHY PEARSON (37 Sunningdale, Round Green, Luton, Bedfordshire).

SIR.—I am interested in radio and amateur radio and would like to correspond with enthusiasts of any country. I am 15 years old.—KEITH BIRSE (20 Murphy Street, Invercargill, New Zealand).

SIR.—I would like to correspond with other P.W. readers who are about my own age (16). I am a keen SWL and I am studying for the RAE.—WILLIAM MORROW (Hill Street, Ballina, County Mayo, Ireland).

SIR.—I am 16 years old and have recently purchased a CR100 receiver. I would very much like to correspond with anyone who owns one of these receivers.—R. CORR (53 Cecil Avenue, Enfield, Middlesex).

REQUESTS FOR INFORMATION ARE INSERTED IN THIS COLUMN ON THE UNDERSTANDING THAT READERS USING THE SERVICE UNDERTAKE TO REPLY TO ALL OFFERS RECEIVED AND TO RETURN ALL DATA NOT REQUIRED. BECAUSE OF THE LARGE NUMBER OF REQUESTS RECEIVED, ILLEGIBLE WRITING WILL AUTOMATICALLY DISQUALIFY LETTERS FROM PUBLICATION. FOR THE SAME REASON, WE CAN NO LONGER GIVE SPACE FOR REQUESTS FOR PAST ISSUES OF PRACTICAL WIRELESS.

Sir—I would be grateful if any reader could sell or loan me . . .

. . . information on different faults peculiar to the B.2 Type 3 Mk. 2 receiver.—T. PRICE, The Rose Gardens, Wallingford, Berkshire.

. . . a good course of home study for the R.T.E.B.—R. D. DAVIS, 48 Kings Road, Sutton Coldfield, Warwickshire.
. . . the circuit diagram and/or operating manual for the 88 Walkie Talkie and information on the power supply and i.f. amplifier unit No. 1 ZA 21531.—J. W. PURKIN, 13 Walnut Grove, Redcar, Yorkshire.

. . . data on receivers R3118, 62B, A109, R220.—A. MCROBERTS, 12 Banner Road, Glasgow, W.3.

. . . coil pack connections in table receiver Jonell NY02204 and any information on a GEC radio, serial No. 304631 and a valve marked "E BVA 142".—G. A. WOODS, 456 Longmoor Lane, Fazakerley, Liverpool 9.

. . . the wiring diagram with data and instructions on how to convert a Pye Domestic Radio Receiver Battery Type Vibrator, Model PE39B, SR No. 128507 (6V accumulator) to a mains supply of 230V a.c.—E. P. ADJOKATCHER, Accra Line District Office, G.P.O., Accra, Ghana.

. . . the service sheet for English Electric TV model No. 16C14.—I. L. PELLAR, 13 Severn Avenue, Tutshill, Chepstow, Monmouthshire.

. . . circuit details for a 'scope built around a CV1526 (701D) tube.—M. J. WOOD, 21 Homelands Road, Sale, Cheshire.

. . . a service sheet or the valve line-up of the Scott Sixteen.—C. ORPIN, 29 Belmont Road, Whitstable, Kent.

. . . information on the U.S. Air Force Pulse Generator TD58/GPN.—F. B. NORMAN, 33 Burlington Road, Sherwood, Nottingham.

. . . circuits for Receiver Model 3/11, Power Supply Type 3 Mk. 2 a.c. 90V to 260V. 6V Transmitter tuning 3-8Mc/s. Receiver tunes 3-15.5Mc/s.—L. O. TULLY, 120 Victoria Street, Fairfield S3, Brisbane, Queensland, Australia.

. . . circuit and data concerning the PCR-3 Communications Receiver.—G. HUSSEY, 66B Trinity Street, Fareham, Hampshire.

. . . details of the cord drive for Ekco type U.199A.—P. DORRINGTON, 383 Spen Lane, Leeds 16, Yorkshire.

. . . a copy of the circuit diagram of the R1155 communications receiver.—A. J. MULLEY, 59 Cootie Lane, Lostock Hall, Preston, Lancashire.

DON'T MISS THESE BARGAINS

Transistor ferrite rod aerial with medium and long wave coils with circuit. 7/6.

Oscillator Coil and set of 3 L.F. transformers for transistor set with circuit. 12/6.

Midget 2in. P.M. Loudspeaker 3 ohm 12/6, 50 ohm 13/6.

Midget 208 pF +176 pF two-gang Tuning Condenser with trimmers for transistor set 17/6 9/-.

Push-Pull Transformer. Sub-miniature 8/6. 0005 mfd. Single Tuning Condenser. Solid dielectric 1in. spindle for transistor of Crystal set, with spindle tapped 6 BA. 2/6. Zener diodes for voltage control and stabilisation. Complete with circuit diagram 3/6 each.

Pre-Amplifier. Made to Mullard design to suit the 10 watt amplifier map to specification. New Unit. Simply needs valves. Type EF86. 27/6 each.

46 Sets (Receiver/Transmitter pack set). Unused sets complete except for crystals. Packed with parts and easily rebuildable into other gear. 19/6 each. Post 3/-.

Battery Charger Kit. Comprises 5 amp. transformer, 5 amp. rectifier, metal case and meter to charge 6 or 12 volt batteries up to 3 amps. With variable charge rate. 39/6 each. Post and insurance, 3/6.

Mains Transformer. 250-0-250 at 80 mA. 6.3 volts. 5a. (normal mains input). 12/6 each. Carriage 2/6.

Output Transformer. Standard pentode matching type. 4/6 each. 4/- per doz. Slide Switch. Sub-miniature but dplit. 2/- each. 18/- per doz.

T.C.C. or Dubilier Tubular Condensers.
 .5mf 500 v. 10/- doz.
 .25 mf 500 v. 7/6 doz.
 .25 mf 350 v. 6/- doz.
 .05 mf 500 v. 5/- doz.
 .01 mf 500 v. 4/- doz.
 .0001 mf 1,000 v. 5/- doz.
 .001 mf 1,000 v. 6/- doz.
 .002 mf 1,000 v. 7/6 doz.
 .005 mf 1,000 v. 7/- doz.
 .02 mf 750 v. 8/6 doz.
 .01 mf 1,000 v. 10/- doz.

Battery Charger Rectifier—selenium 12-15 v. 5 amp. 9/6.

Metal Chassis—punched for Mullard 510 Amplifier, complete with inner screening sections and stove enamelled. 12/6 set.

Twin Twisted Lighting Flex—equivalent 12/6, rubber insulated cotton covered 12/6 per 100 yard coil.

Movink Coil Meters.
 0-500 microamp. 2in. flush . . . 17/6
 250-0-250 microamp. 2 1/2in. surface . . . 27/6
 750 microamp. 2 1/2in. surface . . . 17/6
 0-20 milliamp. 2 1/2in. flush . . . 17/6
 0-200 milliamp. 2 1/2in. flush . . . 15/-
 0-200 milliamp. 2 1/2in. flush . . . 15/-

Filament Transformer, 6.3 v. 1 1/2 amps. 6/6.

Neon Lamp—midget wire ended. Ideal mains tester, etc. 2/-. Ex. Govt. 1/6.

Phillips Trimmers—0.30pF. 1/- ea. 9/- doz. Heavy Duty Test Prods—red and black with plug-in lead attachments, 6/6.

Low Resistance Head Phones. Ideal crystal sets, etc. 7/6, plus 2/6.

Cold Cathode Valve CV413. Voltage regulator or trigger switch—unused but ex-equipment. 2/- each.

TaF Panels. Ideal for constructors, experimental circuits, etc. 3 of each of 12 different types 5/-.
 Snydok Panel Mounting Fuses with carrier. 5 amp. 2/- each. 15 amp. 2/6 each.

Metal Rectifier. 25 v. 60-80 milliamps ideal for mains set or instrument or to replace that expensive valve. 4/6.

Piano Key Type Switches. 3 key type 3/-, 4 key type 3/9, 5 key type 4/6, post and packing 1/- regardless of number ordered.

500 MW Amplifier. Uses 3 Transistors, 2 of which are in Class B push pull for battery economy. Ideal little unit for baby alarm, record player, intercom, etc., etc. 19/6. Speaker 12/6 extra.


Electrolytic Condenser—Bargain. sub-miniature type 50 mfd. 6v. made by T.C.C. 7/6 per dozen (minimum quantity supplied).

Transistor Set Cases. Finished in two tone with handle and back. Size 10 1/2 x 7 1/2 x 3 1/2—each plus 2/6 carriage and insurance.

MAINS POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v—9 to 12 volts for up to 500ma (Class B working). Takes the place of any of the following batteries. PP1-PP4-P6-PP7-PP8 and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor 6600 and 500 mfd condensers, zener diode and instructions. Ideal size at only 14/6 plus 2/6 post.

OUR BARGAIN OF THE YEAR

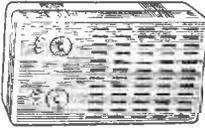

approximately 4 1/2 x 2 1/2 x 1 1/2in. Supplied complete with carrying case.

A Complete kit of parts to build transistor 2 wave superhet receiver at only 39/6.

"CORONET" Mk. IV
 It fully covers the medium waveband and that part of the long waveband to bring in R.B.C. Light. The circuit includes a highly efficient slab aerial and 2 1/2 in. P.M. speaker, overall size approximately 4 1/2 x 2 1/2 x 1 1/2in. Supplied complete with carrying case.


Infra Red Heater

Make up one of these latest type heaters, ideal for bathroom kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—uses silica enclosed element designed for the correct infra red wavelength (3 microns). Price for 750 watt element and metal casing as illustrated 19/6 plus 2/6 post and insurance.



MOTOR BARGAIN

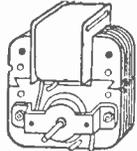
silent running mains motor by very famous maker. Ideal for gramophone, tape recorder, fan, etc., etc. 200-250 volts. A.C. shaded plun start. Size approximately 2 1/2 x 2 1/2 x 1 1/2in. 2,750 r.p.m. Spindle diameter 3/32in. Spindle length 2in. Brand new guaranteed. Price 12/6, plus 1/- post.



THIS MONTH'S SNIP

GOOD COMPANION Mark III

The 6 transistor set with the 8 transistor performance. Incorporating all the latest requirements. Anyone who can solder can make it. Many thousands already in use all over the country. Full coverage of Long and Medium wavebands. Fine looking cabinet, size 4 1/2 x 8 x 3 in. (4 1/2 P.P. output approx. 750 mW. Excellent reception of difficult stations like 20s. Variable feed back gives excellent tone. Complete kit every thing for ONLY £4.19.6 Post and ins. 5/-

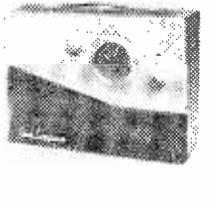

YAXLEY SWITCHES

POLES	2 way	3 way	4 way	6 way	8 way	10 way	11 way	12 way	15 way
1	2/8	2/10	3/11	3/6	4/-	4/6	4/6	4/8	
2	3/33	3/8	4/11	4/11	6/-	7/-	7/-	7/6	
3	3/11	4/6	5/22	6/9	8/-	9/6	9/6	10/3	
4	4/6	7/4	6/22	7/10	10/-	12/-	12/-	13/6	
6	3/9	7/-	8/23	10/9	13/-	17/-	17/-	18/6	
8	8/-	8/8	10/4	13/8	18/-	22/-	22/-	25/-	
10	10/-	10/6	12/5	16/9	22/6	27/-	27/-	30/-	
12	12/-	12/6	14/6	19/8	27/6	32/-	32/-	36/-	
14	14/-	14/6	17/-	22/6					
16	16/-	16/6	19/6	25/6					

Last opportunity to build this Pocket Radio

Constructor's parcel comprises: matched two-tone cabinet as illustrated, tuning coil, two gang tuning condenser, printed circuit. Costing value 37/6—ordered while supplies last at only 19/6 plus 2/6 post. Suitable for your own circuit or to build original circuit. All parts available at highly competitive prices. Do not miss this tremendous bargain.



Speaker Bargain

12in. High-fidelity loudspeaker. High flux permanent magnet type with standard 3 ohm speech coil. With handle up to 10 watts. Brand new, by famous maker. Price 27/6 plus 3/6 post and insurance.



Waterproof heater wire

16 yds. length, 70 watts, self regulating temperature control. 10/-, post free.

Fluorescent Light Kits

For pelmet lighting, etc. Kit consists of: Super silent choke; 2 chrome clips to hold tube; 2 bi-pin holders for tube and starter with a starter holder. Kit A for 80 watt tube at 27/6. Kit B for 40 watt tube at 19/6. Kit C for 2 x 2 ft. 50 w lamp 25/- . Kit D for 1 x 2 ft. 20 w lamp 17/6 Post and Insurance 2/6 per kit.

Building a 'Scope



3in. oscilloscope tube. American made type No. 3EP7. 6.3 v. 0.6 amp. heater electrostatic deflection brand new and guaranteed with circuit diagram of scope. 15/- each. Plus 2/6 post and insurance.

Adjustable Thermostat



Suitable for controlling furnace, oven, immersion heater etc. Can also be used as a flammest or fire alarm. Made by Sunvic, approximately 1 1/2in. long and adjustable over a range 0 to 550F. The contacts are rated at 15 amps. 230 volts. Listed at £3 or £4 each, these are offered at only 8/6, plus 2/6 postage and insurance.

Ice-Stat

This is a small thermostat which cuts on and off at around freezing point. Has many uses, one of which could be as ice warning device to be fitted under your motor car. Price 7/6, post 1/-.

Refrigerator Thermostat

Standard type with adjustment for all normal refrigerator temperatures. 7/6, plus 1/- post.

Simmerstat Heater Regulator
 Suitable to control elements, heater, soldering irons and boiling rings up to 2,500 watt. Complete adjustable, normal price 55/- each, special snip; price 12/6, plus 1/6 postage and insurance.

Suppressor Condenser

Stop your drill or other appliances interfering with your or your neighbour's radio or television. Simple instructions given. 1/6 each. 12/- dozen.

Timer Kit
 Special offer of all components except metal box to make mains operated interval timer for photography etc., 12/6 plus 2/6 post.

Flood Lamp Control

Dim and full switch for controlling photo flood lamps; gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances. With circuit 2/6 plus 9d. postage.



Where postage is not definitely stated add 2/- all orders under £3.

ELECTRONICS (CROYDON) LTD

266, LONDON ROAD, WEST CROYDON, SURREY
 Post orders to: 43 Silverdale Road, Eastbourne, Sussex

Amplifier by

***Be first to own the
only amplifier of its kind
in the world!***

FACTS YOU SHOULD KNOW

ABOUT THE X-10

Number of transistors—11

Overall size—6 x 3 x $\frac{3}{4}$ in.

Input Sensitivity—1 mV

Total harmonic distortion
—Less than 0.1%

Output power—10 watts

Frequency response—
5-20,000 c/s \pm 0.5dB

Speaker impedance—15 Ω

Damping factor—Greater
than 100

Quiescent consumption—
75mA

Supply voltage—12 to 15
volts.

Fully guaranteed

FANTASTIC PERFORMANCE STANDARDS

The SINCLAIR-X10 combined 10 watt amplifier and pre-amplifier (Pats. applied for) is so advanced in design that it outdates every type of amplifier ever made available to constructors, hi-fi enthusiasts, experimenters and industrial users.

The unique eleven transistor circuit specially developed for this amplifier solves once and for all problems inherent in conventional transistor amplifier design so that users of the Sinclair X-10 system enjoy far better reproduction, true 10 watt output for less current consumption (the amplifier will run for about 3 months from two 41- Ever Ready 996 bat-

teries) and great savings in space AND COST. Furthermore, the Sinclair X-10 is so designed that with the aid of the manual included with each amplifier built or in parts) the purchaser can select the tone control and input matching system appropriate to his requirements. This is truly the amplifier of tomorrow—and it can be yours today!


NEW design
principles
performance

SINCLAIR X-10

COMBINED 10 WATT AMPLIFIER AND PRE-AMP

Breakthrough

SINCLAIR

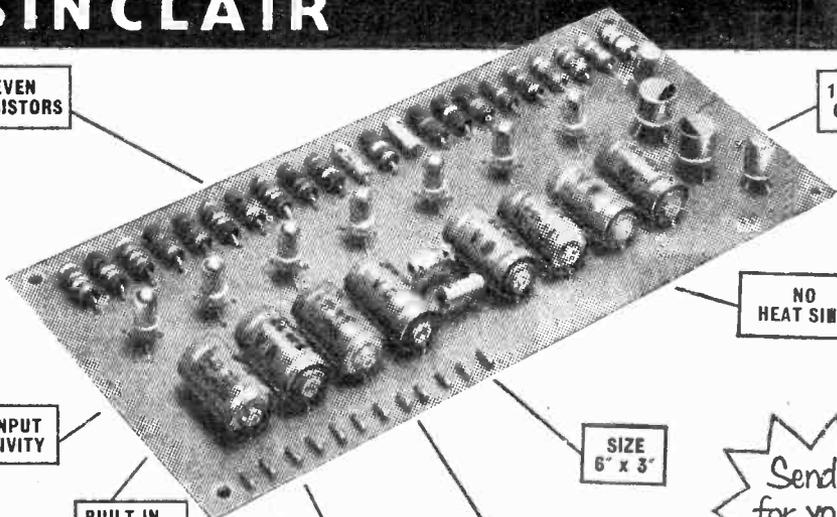

ELEVEN TRANSISTORS

10 WATT OUTPUT

NO HEAT SINK

1mV INPUT SENSITIVITY


SIZE 6" x 3"

BUILT-IN PRE-AMPLIFIER

WILL RUN FROM TWO 4/- BATTERIES

FOR 12 VOLT OPERATION

Send for yours today

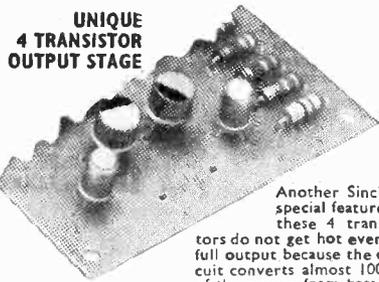

UNIQUE 4 TRANSISTOR OUTPUT STAGE

Another Sinclair special feature—these 4 transistors do not get hot even at full output because the circuit converts almost 100% of the power from battery

or mains unit into audio power for the loudspeaker.

PWM is the answer!

The SINCLAIR X-10 is the only amplifier in the world which gives you the benefits of this unique system. The use of Pulse Width Modulation (P.W.M.) ensures much better transient response—it is instantly noticeable the moment you hear it—no falling off in the higher audio frequencies, no intermodulation distortion and a response curve so flat you could

draw it with a ruler! Eleven transistors, four of which are used in a new type of output stage and P.W.M. plus many other circuit refinements result in an amplifier which is compact, rugged, stable and does not require a heat sink—and it costs so little. Used in pairs the X-10 brings new depths to stereo listening and there are no channel matching problems.

Price, inclusive of all parts and Instruction Manual for building X-10

£5-19-6

THE SINCLAIR X-10 MANUAL

Supplied with every Sinclair X-10 (whether purchased built or in parts for home construction) the X-10 Manual explains how the amplifier functions and how to add the correct tone and volume control system to suit your requirements exactly. A variety of systems is shown, none of which will add more than a few shillings to the original cost of your Sinclair X-10 amplifier, and because it is so simple to modify this part of the assembly, further matching is very easy should you change your type of pick-up or other input.

READY BUILT AND TESTED including Instruction Manual

£6-19-6

Mains Power Supply Unit (A.C. 200/240V) will power one or two amplifiers

£2-14-0

Order form and further Sinclair designs on next pages


SINCLAIR RADIONICS LTD, COMBERTON, CAMBRIDGE Telephone Comberton 682

Build the smallest

SINCLAIR MICRO-6

6-STAGE RECEIVER

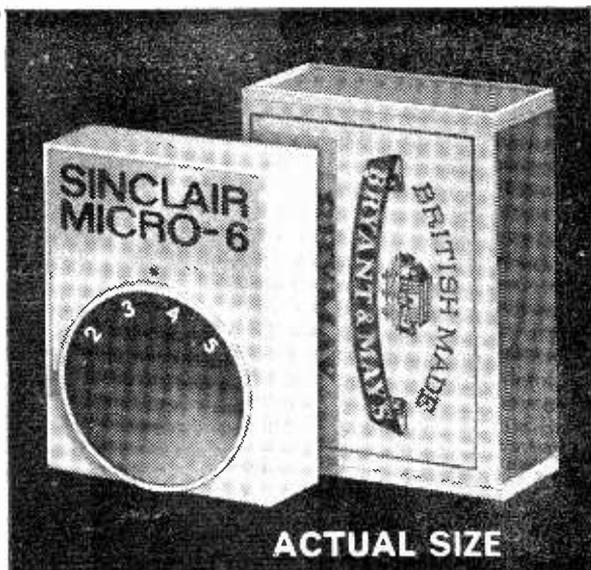*Over 8,000
have been built
and are in use
throughout the
world*



ACTUAL SIZE

The Micro-6 continues unchallenged as the smallest and most efficient set of its kind in the world. It uses only three Micro-Alloy Transistors (MATs) in a unique double reflex circuit to achieve performance normally obtained with twice the number of transistors used. Vernier-type tuning ensures easy reception of distant stations. The output feeds into the featherweight ear piece (or the TR 750 power amplifier for powerful loudspeaker reproduction) tuning is over the medium waveband with bandspread at the high frequency

end for easy reception of Luxembourg. A.G.C. eliminates fading. It is important to realise that the Micro-Alloy-Transistors which the Micro-6 uses not only give extremely high gains and low noise levels, but they consume only a fraction of a mA from the two batteries used to power the set, each cell being smaller than an aspirin tablet! Battery working life is over 70 hours! The Micro-6 cannot be too highly recommended, both as an intriguing design to build, and a most practical radio to use.

MEASURES ONLY
1 1/5 x 1 3/16 x 1/2 in.

**WEIGHS LESS THAN
1 OZ. WITH INTERNAL
AERIAL AND
BATTERIES**

**TUNES OVER M.W.
WITH BANDSPREAD
FOR LUXEMBOURG**

**PLAYS IN CARS,
TRAINS, BUSES
MODERN BUILDINGS
ETC.**

You can build it in a single evening

The Micro-6 uses components never before made available to the public, yet it is simplicity itself to build when you follow the meticulously detailed instructions. All parts including lightweight earpiece and 8-page instructions manual come to


59/6

"Transista" strap for wearing your Micro-6 on the wrist. Smart black nylon.

7/6

MALLORY MERCURY CELL
—Type ZM312 (2 required)
Pack of 6 10/6 each

1/11

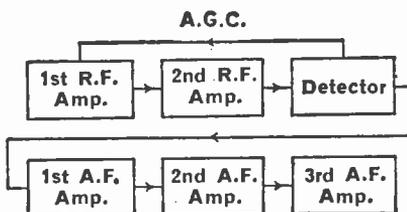

MORE ENTHUSIASTIC COMMENTS FROM CONSTRUCTORS

"Never really believed such results were possible. With longer nights, stations pour in all round the dial. A marvellous design."

G.L.S., Leicester.

"I am very impressed with the design and performance of your little Micro-6. Until I built mine, I never dreamed how useful the set could be."

R.B.W., Reigate.

"It turned out easier than we expected and is going very well indeed. Please send me one more and TR750 for using with the Micro-6 we are keeping at home."

F.T.F., Leeds.

SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE

Telephone: COMBERTON 682



Radio Set in the World!

SINCLAIR TR750 POWER AMPLIFIER

WITH BUILT-IN VOLUME CONTROL AND ON-OFF SWITCH



SIZE!
2" X 2"

DESIGNED TO BE USED WITH
THE MICRO-6 OR SLIMLINE

Makes a car-radio, also a powerful
record player, intercom, etc.

Measuring only 2 x 2 in. and having its own built-in volume control and on-off switch, the TR 750 has a full 750 milliwatts of undistorted output power for 10mV into 10 K ohms. Frequency response is from 30 to 20,000 c/s within ± 1 dB. The output of this amplifier enables it to be used as a powerful car, domestic or portable radio used with the Micro-6 or Slimline receivers, and a plug for connecting the TR 750 to either of these sets is supplied with it. The TR 750 will also make a useful hi-fi record reproducer singly or paired for stereo. There are many other uses for the TR 750 which is available for building yourself or ready built and tested.

Parts for building with instructions come to

39/6

Ready built and Tested

45/-

What our Guarantee means to you

When you deal with Sinclair Radionics Ltd., every effort is made to ensure your complete satisfaction in all your transactions with us. All goods are guaranteed, and if for any reason you should not be delighted, your money will be refunded in full immediately, without question. This is how confident we are you will be thrilled with your purchases from us.

FULL SERVICE FACILITIES ALWAYS AVAILABLE TO SINCLAIR CUSTOMERS

The extra-easy-to-build SINCLAIR SLIMLINE 4 STAGE POCKET RECEIVER

Because the Slimline is a little larger than the Micro-6, it is the ideal constructional transistor set for newcomers. Nevertheless, it is completely self-contained and has built in ferrite rod aerial and uses a standard PP6 battery. Yet it only measures $2\frac{1}{2} \times 1\frac{1}{2} \times 1\frac{1}{2}$ in. The Slimline tunes over the medium waveband and its great power and quality ensure choice of many stations at home and abroad. This is a smart looking set backed by all the advantages of being a Sinclair design. All parts including royal blue and gold case, earpiece and instructions come to



49/6

SINCLAIR MICRO-INJECTOR

An invaluable aid in tracing faults

Using 2 Sinclair MATs, the Micro Injector generate and injects a signal into any part of equipment at any frequency from 1 kc/s to 30 Mc/s to locate faults rapidly in radio or audio equipment. Measures only 1.8in. x 1.8in. x 0.5in. excluding probe, it is the smallest and most efficient of all signal injectors—and it is inexpensive tool. With full instructions. Takes standard 6D battery which will last about 6 months.



All parts and instructions come to **27/6**

Ready Built **32/6**

TO SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE

Please send items detailed below

£ s. d.

Phone: COMBERTON 682

NAME

ADDRESS

TOTAL £

BLOCK LETTERS

P.W.11

For which I enclose cash/cheque/money order.

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV 1925-1964. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogues of 6,000 models. 1/6. Valves, modern and obsolete. Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio and Television. 3/6 post paid. VEST AND EMERY, 17 Hollisarth St., Durham.

SERVICE SHEETS: Radio, TV. 5,000 models. List 1/-. S.A.E. inquiries. TELRAY, 11 Maudland Bank, Preston.

S.E.S. SERVICE SHEETS for all TV Radio and Tape Recorders, etc. List 1/6 plus S.A.E. SUN ELECTRICAL SERVICES, 38 St. George's Road, Hastings, Sussex.

SERVICE SHEETS, also current and obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London. W12. Phone: SHE 8441.

SERVICE SHEETS

4/- ea., plus postage

We have the largest display of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc., in the country, and can supply by return of post.

To obtain the Service Sheet you require, please complete the attached coupon:

From:

Name:

Address:

To: **S.P. DISTRIBUTORS**
44 Old Bond St., London, W.1
Please supply Service Sheets for the following:

Make:

Model No.:..... Radio/TV

Make:

Model No.:..... Radio/TV

Make:

Model No.:..... Radio/TV

I also require list of Service Sheets at 1/6.

I also require list of Manuals at 1/-.

(please delete items not applicable)

I enclose remittance of.....

MAIL ORDERS ONLY

RECEIVERS & COMPONENTS

TRANSISTORS now half price. unmarked but tested packets of 16; unmarked, untested packets of 40; duds suitable as diodes packets of 80. All packets 10/- each, postage 1/-. Four packets post free C.W.O. K. R. WHISTON (Dept. PWT), New Mills, Stockport.

RATES: 7/3 per line or part thereof average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS

(continued)

TRANSISTORS! Give-away price. NKT124 5 Power Type, 6 for 10/-, 25017 4W, up to 60Mc/s, 5/- each. Post free. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

RESISTORS! You can't resist this! 1W, 1W 2W Polythene wrapped on cards of 10. Mixed values and wattages £2/10/- per 1,000. G. F. MILWARD, 17 Peel Close, Drayton Bassett Staffs.


SPEAKER REPAIRS, cones fitted. Satisfaction guaranteed. L. S. REPAIRS, Pluckley, Ashford, Kent.

A.1. POST FREE BARGAINS. Guaranteed reclaimed valves. Send for full list to Dept. MO/W., A1. Radio Components, 14 The Borough, Canterbury, Kent.

NEW VALVE TESTERS £12. Molineux, Lowfield Heath, Sussex.


VHF COMMUNICATION RECEIVER 1392

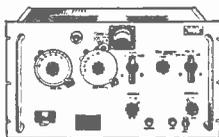15 valve Superhet. Covering 95-155 Mc/s (2-3 meters) Police, Aircraft and Amateur Broadcasts. Power required 240-250 volts at 80mA, 6.3v at 4amps Size 19 x 10 x 10in. £6.15.0. Carr. 15/-



"4 VALVE 4 WATT AMPLIFIER

"C" Core transformers. A.C. Mains 110/230 volts 600 ohms or high Impedance input. Output 600 ohms. Controls: On/Off switch. Gain control. Indicator light Valve inspection panel. 19 x 7 x 7in. Brand New in makers cartons. £4.5.0. Carr. 12/6. **TRANSMITTER.** 1.75-16 Mc/s 3 waveband tuneable, 4rd modulation using 813. Used complete with all valves, circuit £7.10.0. Carriage 10/-. **MOVING COIL HEADPHONES.** BRAND NEW. Chamois padded, complete with jack plug 15/6. Post 2/-. **ROTARY TRANSFORMERS.** 12V D.C. input, 300V D.C., 120mA output, note size only 4 x 2in. 15/-. Post 2/6. **R.C.A. AR8RD RECEIVERS.** Brand New. 27.5. Carriage 30/-. **POWER UNIT.** Type ZE12. Designed for Canadian No. 52 receiver. 52/6. Carr. 5/-. All No. 19 set parts available. **B44 MK. III.** Dipole and rod aerials 30/- per set, P. & P. 5/- Microphone with connecting plug 15/6. P. & P. 2/- Battery input and phone plug 5/- each, P. & P. 1/6. Many other bargains. S.A.E. all enquiries

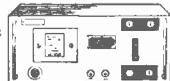

A. J. THOMPSON
"EILING LODGE"
CODICOTE, HITCHIN, HERTS
Phone: CODICOTE 242

RECEIVERS & COMPONENTS

(continued)

DIRECT TV REPLACEMENTS LTD. largest stockists of TV Components in the UK. Line Output Transformers, Frame Output Transformers, Deflector Coils for many makes. Official sole suppliers for many set makers. Same day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. For quotes. Day and Night Telephone GIPSY Hill 6166. 126 Hamilton Road, West Norwood, S.E.27.

TUBES—FAMOUS MAKES!

MW43/69, AW43/80, MW36/24, AW43/88 etc. Fully screened, aluminised, 100% new (except glass). Mostly £4.15s. (12/6 cge.). **LISTS.** One Year's Guarantee Card. **STOP PRESS!**—BY100/PY800 57/- doz. U.26 (equivalent) 8/6 each!
P. BEARMAN, 43 Leicester Road
New Barnet, Herts. Tel.: BAR 1934.

SILICON TRANSISTORS p-n-p, max. ratings 20V, 50mA, 33mW, 2A leakage. Minimum beta of 10 at 5mA, 1/6 each. Detector diodes 6d. "By return" service. **LONGLAND'S 34** Hounslow Road, Hanworth, Middx.

R & R RADIO & T V SERVICE

Dept. P.W.
MARKET STREET, BACUP, LANCs.
Telephone 4663

SALVAGE VALVES Tested before dispatch

6F13	4/6	10P14	5/6	PL82	3/6	20P4	6/6
6L18	4/6	20F5	6/6	U801	7/6	30P16	5/6
EF80	1/6	30P4	7/6	10F1	1/6	PC284	4/6
ECU82	3/6	6F15	5/6	20F2	5/6	PY183	5/6
8CL80	3/6	EB91	1/6	30FL1	5/6	PY81	3/6
30F5	5/6	EF85	5/6	PY32	6/6	U301	6/6
PL18	6/6	630L2	4/6	6U4GT	5/6	10P13	5/6
W180	4/6	20F5	6/6	6F1	2/6	20D1	2/6
PLX1	5/6	30FL1	4/6	ECU81	3/6	30P12	5/6
PZ30	5/6	PL16	6/6	Y86	4/6	PY82	5/6
U329	5/6	PL82	5/6				

Speakers, Er-TV, 5in. round, 6 x 4in. 3/6; 8in. round, 6/-; post 2/-.

Line Output Transformers available. State set model No.

Turret Tuners, 3/-, post 2/-.

Scan Coils etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.** Dept. PW/79, 126 Hamilton Road, West Norwood, S.E.27. GIPSY Hill 6166.



Receivers, Marconi CR100. 60 kc/s to 30 Mc/s. Crystal filter, B.F.O., two r.f. stages, etc. Good condition and working order. £18.10.0, carriage 1/-.

Silicon Rectifiers, 1 amp., 70 p.i.v. Only 6d. each, post 3d. any number. American Morse Keys with lead and jack. 4/6, post 1/-. Power Units 220v. A.C. for R1132, P104, or R1392. £2.5.0. Carriage 10/-.

Headphones, low impedance complete with lead and jack, new, 6/6, post 2/- (Carriage charges apply to England and Wales only).



RECEIVERS & COMPONENTS

(continued)

ARMATURE REWINDS — Hoover Junior Exchange Service. Mod. 375/119/1224. 32/6 inc. post. Fields 15/-.

Send for list. **JERVIS & TONGE LTD.**, Ringwood Road, Brimington, Chesterfield, Derbys. Tel.: Chest 75267.

FOR SALE

HAMMER FINISH PAINT. The modern finish for electronics. Can be brushed or sprayed. Blue or silver. 2 1/2oz tins 3/6, 1/2 pint 7/6, 1 pint 15/-. Post 6d. on any order. Trade supplied. **FINNIGAN SPECIALITY PAINTS** (p.w.), Mickley Square, Stocksfield, Northumberland.

MORSE MADE EASY!

The famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum!

One student, aged 20, took only 13 DAYS and another, aged 71, took 6 WEEKS to obtain a G.P.O. pass certificate. If you wish to read Morse easily and naturally, please enclose two 3d stamps for full explanatory booklet.

To **GREENS, THE MORSE CENTRE, 45 G33 LANE, PURLEY, SURREY.**

CONDENSER BARGAIN! Miniature paper condensers, 1in. x 1in. Ideal for transistor sets. .001, .001, .002, .005, .02, .04uf. Your choice 7/8. per 100 or £3 per 1,000. **G. F. MILWARD, 17 Peel Close Drayton Bassett, Staffs.**

ALBATROSS ENGINEERING CO.

INSTRUMENT DIVISION

78/80 High Street, Gosberton, Spalding, Lincs.

Tel. Gosberton 458

- ★ Transistorised A.C. Millivoltmeter
- ★ 4 Ranges. 10 mV-100 volts.
- ★ Input Impedance 3 Megohms.
- ★ Response 10 c/s-50 Kc/s.
- ★ PRICE £5.8.10. Less Case.
- ★ Transistorised Generator
- ★ Frequency 1 Kc/s.
- ★ Output 200 millivolts variable at 5K ohms
- ★ PRICE £1.10.8. Less Case.
- ★ Transistorised Model Control Receiver
- ★ Frequency 27mc/s (variable).
- ★ 2 transistors.
- ★ Supply 6 volts.
- ★ Size 2 1/2 x 1 1/2 in.
- ★ PRICE £1.19.6
- ★ Transistor Test Set
- ★ Measures by Meter
- ★ Gain.
- ★ Leakage Current.
- ★ Input resistance.
- ★ Short Circuit.
- ★ PRICE £5.19.6. Less Case
- ★ Transistorised Mixer Unit
- ★ 4 Separate channels.
- ★ 4 Independent controls.
- ★ 1 Master control.
- ★ 10 dB Gain.
- ★ 9v. Supply.
- ★ PRICE £5.19.6 in Case.

FOR SALE

(continued)

240-watt ELECTRIC POWER ANYWHERE

ANYTIME! from 12-watt CAR BATTERY

with **THE AMERICAN DYNAMOTOR UNIT**

Input 12v. output 200-250v at 150 to 220 watts. Perfect for TELEVISION. POWER TOOLS and all universal AC/DC ELECTRICAL EQUIPMENT, gives wonderful results. Price ONLY £8. - incl. carriage

Send stamped envelope for full illustrated details

SCIENTIFIC PRODUCTS, CLEVELAND, OHIO

TESTED TRANSISTORS

All new. few equivalent. OA202

1/- each, Red or White Spots.

2/- each, XA101, XA102, XB103, OA90, OC430, XA112, XA111.

3/- each, OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16.

4/- each, AF114, AF115, AF117, OC170, OC171, SX658, XU611.

5/- each, OC72, OC139, OC140, OC204, ORP60, BY100, GET8.

10/- each, OC35, OC26, OC28, GET57, 2SO13. All new, few equivalent.

ZENER DIODES 4.7 v. to 33 volt 1/4 watt, 3/6 each. 1.5 watt, 5/- each, 7 watt, 6/- each.

Send 3d. stamp for Full Price List, and Free Equivalent Chart.

B. W. CURSONS

78 BROAD STREET CANTERBURY, KENT

ELECTRIC SOLDERING-IRON



FANTASTIC BARGAIN OFFER

Lightweight Pistol Grip handle 40 watt, 240/250v. A.C. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handyman. A boon to model makers and a necessity for every wireless enthusiast. Offered to you at this new amazing price.

ONLY 9/6

C. H. SERVICE, (Dept. P.W.3) Lusted Hall Lane, Tatsfield, Kent

SUPER BREAKDOWN UNIT

Remote Control Unit Type F. New in sealed cartons, containing P.O. Relay 2,000 ohms Resistance, 100 volt Plessey Hand Generator, Telephone Ringing Bell A.C. 8 amp Morse Key on base, 2 D.P. D.T. Key Switches, Double Phone Jack, moulded 5 position 6 pole Yaxley Switch, induction Coil tapped 1-17-33 ohms, 7 Brass Screw Terminals on panels, plus Resistors, Condensers, Pointer Knobs. All in a handy metal box with hinged lid and side fasteners. Also web carry strap. Size 10 1/2 in. x 7 in., 2 1/2 in., post free. Or items may be purchased separately. Relay 5/-, Hand Generator 7/6, Bell 5/-, Morse Key 4/6, Key Switches 5/- pair, Double Phone Jack 2/6, Yaxley Switch 2/-, Ind. Coil 2/-, Terminals 7 for 2/-, all post free.

Also available Key Switches. 4 pole 2 throw 3/6 each or 3 position D.P. plus D.P. centre off 5/- or rotary switch 6 pole 3 way 3/-.

Bank of 4 Pye Sockets with plugs and leads 5/- set. Ever Ready Batteries, 90 volts plus 4 1/2 volts 4/6 each.

Plessey 2-4-12-25 way plugs and sockets all 5/- pair.

Jones Plugs and Sockets 4-12-18-24-32 way all 5/- pair.

Special Lightweight 7in. x 4in., 3 ohm P.M. Speaker, 6/-.

Metal Frames, suitable for stock, Job Cards, Bins, Crates, 2 1/2 in. x 5 in. 12/6 per 100—£4 per 1,000.

19in. RACK FITTING CABINET. 3 1/2" high by 21" deep with telescopic drawer slides. Louvred sides, back and top. Brand new Swedish make, £4.4.0 only, plus B.R.S. delivery.

ECR Tube with Screen and Base with ECR 35 data. 25/-.

5U7 Tube with Screen and Base, with data. 30/-.

20ft. Steel Telescopic Mast, 70/-.

COLLARO AUTO CHANGE

speed Gramophone Decks Tested and guaranteed Post free 50/- each Brown or Cream

Copper Laminate Board, single or double sided, 5/- per square foot panels, either type 3ft. by 4ft., 33/-.

High Stab Resistors. 5%. 6d.; 2%. 9d.; 1% 1/-.

Every six packed in 7-compartment linen finish component box. Unmarked.

Speakers, 3 ohm P.M. 5in. 5/-, 6in. C/-, 7 x 4in. 7/-, 8in. 8/-, 10in. 12/6.

U.K. ONLY

E. R. NICHOLLS

Mail Order and Retail Shop 46 LOWFIELD ROAD off SLAW HEATH, STOCKPORT, CHESHIRE

FOR SALE

(continued)

5-TON FACTORY CLEARANCE. Radio, TV Electrical Components, in mixed parcels. Example: 28lb. mixed parcel £1, pp 5/-. Speakers, grilles, valves, bases, i.f.s. covers condensers etc. Hundred other items. S.A.E. List and Postal Orders to P. NEWTON, 16 Shalcross Crescent, Hatfield, Herts.

WANTED

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

WE BUY new valves for cash, large or small quantities, old types or the latest. Send details, quotations by return. **WALTONS WIRELESS STORES**, 15, Church Street, Wolverhampton.

WANTED VALVES ONLY

Must be new and boxed
Payment by return.

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WE BUY new Valves and transistors, Amplifiers, Short-wave Receivers and Components, etc. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

NEW VALVES WANTED

Any type, or quantity

CASH PAID

R.S.T. Valve Mail Order Co.

211A Streatham Road
Mitcham, Surrey

Telephone: MITCHAM-6202

SOUND RECORDINGS

A UNIQUE BUY! Recording tape top brand, 7in. 2,400 ft. D.P. 25/-; 5in. 1,200 ft. 19/6d., P. & P. 1/6d. per spool. Bargains in all sizes. S.A.E. for list. We repair, buy and sell recorders. **E. C. Kingsley & Co. Ltd.** 132 Tottenham Court Road, London.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES IN MINUTES from the great book, The Principles of TV Receiver Servicing. 10/6 all book houses and radio wholesalers. If not in stock from Dept. B Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. **WILLEN** (Dept. 40), 61a Broadway, London. E.15.

MISCELLANEOUS

ALUMINIUM

Sheet for Radio Chassis and general use. Cut to size. Also Brass, Copper, steel, etc. in Sheets, Tubes, Rods, Foils, Sections, etc. Write for **FREE ILLUSTRATED PRICE LIST**. Callers welcome.

SENMOR METALS, Dept. R/6
35 St. Johns Road, Isleworth, Middx.
ISL: 0312

CONVERT ANY TV SET into an oscilloscope. Instructions and diagrams 12/6. **REDMOND**, 26 St John's Road, Hove, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write **NOW** for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2hd. stamp.

COIL, METAL WORK, ETC.

METAL RADIO CASES CHASSIS ETC.

Precision Wound Supersensitive Coils—JDR1 Dual-range Ferrite Rod Aerial, 8 x 3/8in. with circuits, 10/-; JDR2 Matched Pair Dual-Range Coils with reaction and circuits, 7/6; JDRX1 Miniature Dual-Range Coil with reaction and circuits, 3/6; Printed Circuit Kit comprising 6 x 3in. printed circuit (of 3 transistor Reflex Radio), Ferrite Rod, All Coils with plans, 18/6, suitable Cabinet, 7/6; Radio or Instrument Case, crackle finished, 8 x 5 x 4in. with handles and front panel, 18/6. Add 1/- P. & P., over 10/- add 2/-.

Production Undertaken of Coils, Chassis, Metal Cases, lowest prices consistent with quality. **TRADE ENQUIRIES INVITED.**

JETRONIC ENGINEERING CO. (Dept. PW 1), 9 Western Road, Hove (Catalogue of Coil Range, Metal Work, etc. 1/-)

EDUCATIONAL

THE INCORPORATED PRACTITIONERS in Radio and Electronics (I.P.R.E. Ltd.). Membership Condition booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/- post free. Dept. B Secretary, 32 Kidmore Road, Caversham, Reading Berks.

EDUCATIONAL

(continued)

RADIO OFFICERS see the world. Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1964/65. Day and Boarding Students. Grants and scholarships available. Stamp for Prospectus. **WIRELESS COLLEGE** Colwyn Bay.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

DON'T FUMBLE

with Formulae. Master Mathematics quickly and easily the Understandable Way.



The Dryden School of **UNDERSTANDABLE MATHEMATICS**
11 J. Dryden Chambers, Oxford
St., London W.1.

Name.....
Address.....
.....
.....

BECOME "TECHNICALLY QUALIFIED" in your spare time. Guaranteed Diploma and Exam Home-study Courses in Radio, TV Servicing and Maintenance. R.T.E.B., City and Guilds, etc. Highly informative 130 page Guide—FREE. **CHAMBERS COLLEGE** (Dept. 363), 148, Holborn, London, E.C.1.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs), R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor. Write for **FREE prospectus** and find out how **ICS** can help you in your career.

ICS DEPT. 541, PARKGATE ROAD LONDON, S.W.11.

EDUCATIONAL

CITY AND COUNTY OF BRISTOL EDUCATION COMMITTEE

BRISTOL TECHNICAL COLLEGE

Principal: E. Poole, B.Sc. (Eng.), M.I.Mech.E., M.I.Prod.E.

CAREERS IN RADIO AND RADAR

Marine Radio Officers

2-year full-time course for young men aged 16 upwards, leading to 1st and 2nd class P.M.G. Certificates and M.O.T. Radar Maintenance Certificate.

Conversion Course (2nd class to 1st class). R.T. Courses (for Full or Restricted Licence).

Training given on the latest types of Marine and Aircraft Equipment in newly equipped Laboratories at

THE SCHOOL OF RADIO AND RADAR

Senior Lecturer: F. E. Bartrop

For details write to

The Registrar, Bristol Technical College, Ashley Down, Bristol 7

Aircraft Radio Maintenance Engineers

2-year full-time course for A.R.M.E. Licences, categories A & B.

Courses for Radar Rating in association with the above.

BUSINESS OPPORTUNITIES

IF YOU are a Self-employed TV Service Engineer wishing to increase your profits by a least 25% and receive free technical information send S.A.E. for details to Box No. 55.

METAL WORK

CABINETS • CASES CHASSIS

Anything in metal. "One-offs" a pleasure. Send your drawing for quote. Stove enamelled in any professional finish

MOSS, WATSON

40 Mount Pleasant Street, Oldham, Lancs. MAIN 9400

METAL WORK. All types cabinets, chassis racks, etc. to your specifications. PHILPOTTS METAL WORKS LTD., Chapman St., Loughborough.

SITUATIONS VACANT

(continued)

I.E.R.E. CITY AND GUILDS and R.T.E.B. exams. Specialised I.C.S. home-study course will ensure success. For details of wide range of exam and diploma courses in Radio TV and Electronics, also new practical courses with kits, write to I.C.S. (Dept. 542), Parkgate Road, London, S.W.11.

A.M.I.Mech.E., A.M.I.E.R.E., City & Guilds, G.C.E., etc. brings high pay and security. "No pass—no fee" terms. Over 95% success. For details of Exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook — FREE. B.I.E.T. (Dept. 242B), London, W.8.

RADIO AND TV Exam. and Courses by Britain's finest Home-Study School. Coaching for Brk.I.R.E. City and Guilds, Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from BRITISH NATIONAL RADIO SCHOOL Russell Street, Reading.

RADIO TECHNICIAN

A number of suitably qualified candidates will be required for training, leading to permanent and pensionable employment. (Normally at Cheltenham but with opportunities for service abroad or appointment to other U.K. stations.)

Applicants must be 19 or over and be familiar with the use of Test Gear and have had Radio/Electronic workshop experience. They must offer at least "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19 £722, at 25 £929 (highest pay on entry) rising by four increments to £1,067.

Prospects of promotion to grades in salary range £997—£1,634.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days.

Normal Civil Service sick leave regulations apply.

Apply:

RECRUITMENT OFFICER (RT 37)

Government Communication

Headquarters, Oakley, Priors Road, Cheltenham.

SITUATIONS VACANT

(continued)

TV and Radio—A.M.I.E.R.E., City & Guilds, R.T.E.B. Cert., etc. on 'No pass—no fee' terms, over 95% successes. For details of exams and home training courses (including practical apparatus in all branches of radio, TV and electronics) write for 148-page Handbook—free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London, W.8.

NEW VALVES!

Guaranteed Set Tested 24-HOUR SERVICE

1R5, 1R5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET OF 4, 14/-, DAF96, DF96, DK96, DL96, SET OF 4, 22/-

OA2	3/9	DL35	6/3	PCL83	7/9
1D5	4/9	DL92	4/3	PCL84	7/-
1R5	4/3	DL94	5/3	PL36	7/9
1R5	3/3	DL96	5/3	PL81	6/3
1T4	2/3	EB31	1/11	PL82	5/-
3S4	4/3	EB41	6/3	PL83	5/-
3V4	5/-	EBF80	5/3	PL84	5/-
6Y3GT	5/-	ECC40	6/9	PY32	8/6
6Z4G	6/9	ECC81	3/-	PY33	8/6
6KTG	1/3	ECC82	4/-	PY80	4/9
6K8G	3/9	ECC83	4/6	PY81	5/-
6QTG	4/3	ECC84	5/6	PY82	4/11
6GTG	6/9	ECC85	6/-	PY83	5/6
6V6G	3/6	ECP80	5/9	U26	8/-
6X3GT	6/3	ECP82	5/9	U26	7/9
12K7GT	8/6	ECH42	7/3	U191	8/3
12K8GT	8/6	ECH81	5/3	U801	15/-
12Q7GT	3/3	ECL80	5/9	UABC80	5/-
25L9G	4/9	ECL82	6/3	UAF42	6/9
30FL1	7/9	EP41	5/9	UBC41	6/-
36L6GT	4/3	EP8	3/9	UBF80	5/6
35Z4GT	4/6	EP85	4/6	UCC84	7/11
85A2	5/9	EP88	5/9	UCC85	6/-
CL33	8/6	EP89	4/3	UCF80	8/3
DAC32	7/9	EL41	7/-	UCH42	6/9
DAF91	3/3	EL84	4/6	UCH81	5/9
DAF96	5/6	EY31	5/6	UCL82	7/3
DF33	7/6	EY86	5/-	UOL83	7/9
DF91	2/9	EZ40	5/-	UF41	6/3
DF96	5/6	EZ80	3/9	UF89	5/9
DH7	3/9	EL1	3/9	UL41	6/9
DK82	7/6	PCC84	3/3	UL84	6/9
DK91	4/3	PCC89	8/6	UR10	5/-
DK92	6/9	PCF80	6/9	UY21	7/3
DK96	6/-	PCF82	6/-	UY41	3/11
DL33	6/9	PCL82	6/3	UY85	4/9

Postage 6d. per valve extra. Any Parcel insured against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra.

GERALD BERNARD

83 OSBALDESTON ROAD, STOKE NEWINGTON, LONDON, N16

Get your copy NOW...

"PRACTICAL WIRELESS" RADIO AND TELEVISION REFERENCE DATA

Contains full details of colour codes; everyday formulae, for calculating the values of biasing components, potential dividers resonance, gain, etc.; aerial dimensions; a quick frequency-wavelength conversion table; stations and frequencies; common symbols and abbreviations; notes on amateur radio and a list of call-sign prefixes; communication receiver I.F.s; wire and cable data; battery equivalents; valve, transistors and picture tube pin connections, bases, ratings and equivalents. Illustrated. 10s. 6d. FROM ALL BOOKSELLERS ... or, in case of difficulty 11s. 6d. by post from GEORGE NEWNES LTD., Tower House, Southampton Street, London, W.C.2.

RADIO BOOKS

TELEVISION & RADAR ENCYC.

Published Price 30/- Book Bargain 9/6 INDUSTRIAL TELEVISION

Published Price 15/- Book Bargain 4/6

- STEREO FOR BEGINNERS 8/6
- HIFI FOR BEGINNERS 8/6
- SOUND & CINE FOR BEGINNERS 8/6
- AUDIO & ACOUSTICS by Briggs 11/6
- MORE about Loudspeakers by Briggs 8/6
- CABINET Handbook by Briggs 8/6
- AT A GLANCE Valve and TV Tube equivalents 4/-
- OSCILLOSCOPE Book 5/6
- USING an Oscilloscope 7/-
- OSCILLOSCOPE Equipment 5/6
- MULLARD Circs. for Audio Amp. 7/6
- MULLARD Ref. Transistor Circs. 13/6
- EXTRA Equipment Tape Recorder 6/6
- TRANSISTOR Circuits for Radio Control of Models 8/-
- SERVICING Transistor Receivers 8/6
- ELECTRONIC Novelties 5/6
- ELECTRONIC Gadgets 5/6
- RADIO Valve Data "Wireless World" 5/6
- TRANSISTOR's Guide to Radio, 2nd Edition 9/6
- MODERN Transistor Circuits for Beginners 8/-
- ABC of Translators 5/6
- ABC of Ultra shorts 5/6
- ABC of Magnetism 5/6
- ABC of Missile Guidance 5/6

All books include postage. List S.A.E.

SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY KENT. Tel. HU7stway 1818

2 METRES 4

The thrills of VHF Amateur Radio can now be yours for as low as 42/6 complete kit (by post, carriage and packing, 2/6 extra). Tuning range 70-150 Mc/s. Stamped addressed envelope for free copy of literature and full details. Newcomers to Short-Wave Radio ask for details of the famous "Globe-King" kits and receivers. Home and Overseas Sales.

JOHNSONS (Radio)

St. Martins Gate, Worcester

Football Pool Computer

Novel low-cost circuit for forecasting Analogue Computer. Multiplication and division by electrical analogue. Simple demonstration of computer principles. Both above circuits for 3/6 post free.

Naughts and Crosses Machine. Full circuit and instructions for our fabulous design 3/6. Cannot be beaten!

Multimeter Kit, 18,000 o.p.v. 26 range kit with Weston 502A meter, only 65/-. (2.5A range 4/- extra). Stamp for details.

Multimeters, TK20A, 1000 o.p.v., 33/-, post 1/6; EP10K 10,000 o.p.v., 69/8, post 1/6; EP30K, 30,000 o.p.v., 95/8, post 2/-; EP50K, 50,000 o.p.v., 130/-, post 2/6. Illustrated leaflet on request.

Audio — I.F. — R.F. Oscillator. Simple square wave circuit giving output at audio and radio frequencies up to 1.5 Mc/s. For rapid "dead" set testing, morse practice etc. Variable amplitude. Basic kit of transistors, condensers, resistors, tag strips, pot, switch, knob. Price 10/-, post 1/-, with circuit and instructions.

Precision Wirewound Resistors 1W, 1 ohm to 5K 1% 3/-; to 20K 4/3; 1% add 3d. Your value wound to order.

High Stab Resistors. 1W 1% 2/-. Full standard range 10 ohms to 10M plus many special multimeter values.

PLANET INSTRUMENT CO.

25 DOMINION AVENUE, LEEDS 7

SEMI-AUTOMATIC "BUG" SUPER SPEED MORSE KEY



7 adjustments, precision tool- ed, speed adjustable, 10 w.p.m. to as high as desired. Weight 2 1/2 lb. Price £4.12.6. post paid.

LIGHT SENSITIVE SWITCH

Kit of parts, including ORP, 12 Cadmium Sulphide Photo cell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP 1/2 including circuit, 10/6 each, plus 1/- P. & P.

TRANSISTORS

OC41	7/-	OC84*	10/-	GET573	12/6
OC45*	5/-	OC139	12/-	2G110	17/6
OC71	5/-	OC140	19/-	2N458	20/-
OC72*	7/-	OC171	10/6	5B345	7/6
OC73	6/-	OC200	10/6	AC107	14/6
OC75	7/-	OC201	21/-	AF114	13/-
OC78	9/-	OC203	14/-	AF115	10/6
OC77	9/-	GET104	6/-	AF116	10/-
OC81*	8/-	GET105	10/-	AF117	9/6

* Available in matched pairs.

SIEMENS SEALED HIGH SPEED RELAYS

H96A.	2.2 ohm + 2.2 ohm, new	12/6
H96B.	50 ohm + 50 ohm, new	12/6
H96C.	145 ohm + 145 ohm, new	12/6
H96D.	500 ohm + 500 ohm, new	12/6
H96E.	1700 ohm + 1700 ohm, ex-equip.	16/6

SERVICE TRADING CO

PADGETTS RADIO STORES

OLD TOWN HALL, KNOWLER HILL, LIVERSEDGE, YORKS. Telephone: Cleckheaton 2868

Single Pulse 230 V. 1400 r.p.m. 1/2 h.p. motor with pulley, 26/-. Less pulley, 24/-. Fully guaranteed ex-washing machine. Carr. 6/6.

One Sixth H.P. Motor 15/-. Post 6/9. New Indicator Unit, C.R.T. 100. Complete with two tubes, type VCRX393 and VCRX298 plus 21 small valves. Relays removed, 57/- or less valves 32/-. Carr. 10/-. Sorry no details on the unit.

New Boxed Test Set, 100 only. Type 350. Complete with meter and case. No details. 37/6. Post 6/9.

New Condenser Parcel. Mixed. Send 6/-. Post paid.

New 12in. Speaker with built in tweeter. 15 or 3 ohms. 28/6. Post paid.

P.M. Speakers, all 3 ohm, ex-TV Sets. 6in. round, 6 x 4in. and 5in., 3/-. Post 2/-. 6 for 20/-. Post paid. 8in. round, 6/-. Post 2/-. 7 x 4in. 5/-. Post 2/-.

VALVE LIST

EL91	1/6	20L1	5/-	PL38	8/-
ECC80	2/-	20P3	4/-	PY80	3/6
ECC82	3/-	20P4	8/6	PL32	3/6
EF51	2/6	K708	4/-	PL33	3/6
EBF80	4/6	U801	8/6	PL33	3/6
EB91	9d.	U281	5/-	PY81	3/6
EL38	5/-	U232	5/-	PY82	3/6
EF91	9d.	U323	5/-	PCF80	4/-
6P1	1/6	K736	5/-	PCC84	4/6
5F14	5/-	K708	4/-	VR150/30	4/6
6F15	5/-	6V6GT	4/-	1T4	1/9
6LD20	5/-	6B8	1/6	12AT7	3/6
10C2	5/-	6K25	5/-	6CH6	1/6
10P1	1/-	6P25	3/6	6X4	3/6
10P13	5/-	6T4	5/-	R18	3/6
10P14	5/-	PY33	8/-	ARP12	3/6
20D1	2/-	PL81	4/-	807	5/-

EF50 1/-, doz. 6/-; 6K7 1/3, doz. 10/-; 6V6 1/9, doz. 18/-; 6K8 1/9, doz. 18/-; Send S.A.E. for rare valve enquiry.

Breaking up Mark III Type 19 Sets. Meter, 500 micro-amp., 5/-, Post 1/9. Jack Socket 1/-. Post 6d. Doz. 10/-. Post paid. Jack 1/6. Post 6d. Toggle Switch Metal 6d. Post 6d. Doz 10/-. Post paid. Relay Type 300 1/9. Post 1/9. Doz. 20/-. Post paid. Any other spare send 2/- plus post to cover.

TV Sets, 13 channels. Untested but complete. 14in. 30/-, 17in. 50/-, Carr. 10/-. Well packed but sent at owner's risk.

Reclaimed Tubes. Six months guarantee. 14in. Mullard and Mazda 17/6, Carr. 7/6. 7in. 30/-. Carr. 7/6.

BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.

The Ideal Instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P. NSP2 CV2296 STROBOTRON FLASH-TUBE made by Ferranti, brand new, I.O. base. Price 15/-. P. & P. 1/-.



VARIABLE VOLTAGE £4.10.0

TRANSFORMER Post Paid Input 230 v. A.C. Output 0-230 v. at 1 amp., fully shrouded, new. Also available 2.5, 5, 8, 10, 12 and 20 amp. Write for details.



Insulated Terminals available in black, red, white, yellow, blue. New 15/- per doz. P. & P. 1/-.

D.C. AMMETERS

0-15 amp. D.C. M-Coil 2 1/2 in. round	12/6
0-5 amp. D.C. M.L. 2 1/2 in. round	11/6
0-500 Microamp. sub-min. 1 1/2 in. dia.	21/6

Scaled 0-1 milliamp. Postage extra.

All Mail Orders. Also Callers at: 47-49 High St., Kingston-on-Thames Telephone: KINGston 9450

ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses. 12 volt 36 watt AC/DC SBC 6/6. P. & P. 1/-, 12 volt 36 watt AC/DC SBC 8/6. P. & P. 1/-, Transformer to suit the above: Input 200-240 A.C. Output 12 Volt A.C. 36 watt, 10/6. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 60 watt, 22/6. P. & P. 3/6. Set of four colours FLUORESCENT Paint. Orange, Yellow, Green and Red, in foz. tins. Ideal for use with the above Ultra Violet Bulbs. 9/6. P. & P. 1/6.

VAN DE GRAAFF ELECTRO-STATIC GENERATOR

Fluted with Motor drive for 230 v. A.C. giving a potential of approx. 50,000 volts. Supplied absolutely complete, including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price £28.6.0. plus 4/- P. & P.

A.C. VOLTMETERS

0-15 v. A.C.M.I. 2 1/2 in. F.L.	12/6
0-200 v. A.C. Rect. M-Coil 3 1/2 in. Type W23	45/6
0-300 v. A.C. M.L. 2 1/2 in. F.L.	22/6
0-300 v. A.C. Rect. M-Coil 2 1/2 in.	29/6
0-300 v. A.C. Rect. M-Coil 3 1/2 in. Type W23	55/6

A.C. AMMETERS

0-1, 0-5, 0-10, 0-15, 0-20 amp. F.R. 2 1/2 in. dia. All at 21/- each.

Personal Callers only: 9 Little Newport St., London, W.C.2. Tel. Ger 0576 (off Leicester Square)

A.R.R.L. AMATEURS RADIO HANDBOOK 1964

New Edition 36/-. Postage 2/6.

HI-FI Year Book 1964, 10/6, postage 1/-. Beginners' Guide to Radio, new edition, 8/6, postage 9d. Radio Circuits Handbook by Rufus Turner, 18/-. postage 1/-. Radio Amateurs Examination Manual by R.S.G.B., 5/-, postage 6d. British Transistor Directory by Bradley, 8/6, postage 6d. Guide to Broadcasting Stations by W.W. new edition, 5/-, postage 6d. Transistor Amplifiers for Audio Frequencies by Roddam, 45/-, postage 2/-. Teach Yourself Radio Servicing by Butterworth, 10/6, postage 1/-.

UNIVERSAL BOOK CO.

12 Little Newport Street London, W.C.2 (adjoining Lisle Street)

KITS

Top Band Receiver (also medium wave BC) £10.0.0

Top band transmitter (8 watts) £14.0.0

NOMAD car radio (1 watt output) £6.19.6

Also transistors [AF from 3/6; RF from 6/-] components. S.A.E. list.

Transistor power supplies from 35/-

ENQUIRIES WELCOME ABOUT ALL TYPES OF KITS, Write in to:

NORCOL LTD.

147 London Road, Yorktown Camberley, Surrey Tel: Camberley 3743

RES/CAP. BRIDGE 39/6

p. & p. 2/6 Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading READY CALIBRATED Stamp for details of this and other kits.

RADIO MAIL (Dept. F)

Raleigh Mews, Raleigh Street Nottingham

FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS



H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc. IMPROVED 1964 RANGE 1-Valve model "CX", complete kit, Price 34/6 Customers say: 'Definitely the best one-valve N.W. kit available at any price.' This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and, of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model 'k' price 77/-

Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to—

"H.A.C." SHORT-WAVE PRODUCTS (Dept. T.H.), 44 Old Bond St., London W.1

CRYSTALS & COMPONENTS LTD



TEL: TEM 1189 Dept. P.W.18 2, 4 EARLHAM STREET W.C.2.

Near Cambridge Circus. A few minutes' walk from Leicester Square or Tottenham Court Road Underground Stations
 HOURS OF BUSINESS: 9 to 6. Saturdays 9 to 1. OPEN ALL DAY THURSDAY

CRYSTALS!!! CRYSTALS!!! CRYSTALS!!!

WE ARE NOW UNDER NEW MANAGEMENT AND WISH TO ASSURE READERS THAT THEIR ORDERS AND ENQUIRIES WILL BE DEALT WITH PROMPTLY AND RELIABLY

We have a large and varied range of 10X, 10X1, FT241 and FT243 types and will be pleased to send you our current list on request (S.A.E. preferred). Below are just a few of the many useful 10X crystal frequencies in stock.

5840	5842	5865	5870	5875	5880	6000	6010	6015	6020
6021	6040	6050	6070	6076	7730	7840	7850	8001.43	8007.69
8021	8036	8090	8091	8092	8103	8104	8110	8790	—

most of stock frequencies including the above are offered at 5/- each. A special discount of 20% (4/- in the £) on all orders for crystals in these ranges amounting to 25/- and over. Allow 6d. per xtal, P. & P.

Also in stock at 10/- each: 2 Mc/s, 3 Mc/s, 4 Mc/s, 5 Mc/s. 15/- each, 1 M/c, 500 kc/s.

Sockets for all above types 1/3 each, universal (1/2 in. or 3/16 in.) 2/-.

Miniature twin crystals in glass envelope wire ended, 5/- each.

10xac1 19887 5 and 19937 5 kc/s
 10xac4 20187 5 and 20237 5 kc/s

10xac2 19987 5 and 20037 5 kc/s
 10xac5 20287 5 and 20237 5 kc/s
 10cac10 (single) 31 5 kc/s

10xac3 20087 5 and 20137 5 kc/s
 10xac6 20837 5 and 20437 5 kc/s

HIGH SPEED IMPULSE COUNTERS

By DAVIS, WYNN and ANDREWS

4in. dial and pointer registers up to 100 and 4-digit counter, both manually re-settable. The drive to the counter is by an inverse escapement so that there is no loading of the pointer mechanism when digits are changed, and adjustable pawls are unnecessary.

Coil resistance 100 ohms for nominal 50 volt operation, but the device works reliably from 20 volts at rates up to 10 impulses/sec. In circuit with a thyratron or neon-tren counting rates up to 100 impulses/sec are possible provided pulse width is restricted to keep mean current to 100 mA.


Highly suitable as readout element for Geiger counters and similar devices where the pointer movement would give a clear impression of change in rate of count.

Brand new in individually sealed boxes..... **£4.7.6** p. & p. 2/6.



WIRELESS TRANS-RECEIVER

TYPE 19

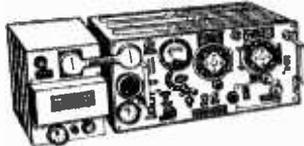

with power pack for 12V. input covers 2-8Mc/s and 240 Mc/s. V.H.F.I.F. used 465 kc/s. C.W. or speech. Untested, in good condition, fully valued.

£4.17.6 plus £1 p. & p.
 Combined Mike-headset 17/6, p. & p. 2/6.
 Aerial variometer 17/6, plus 2/6 p. & p.
 6-pin Power Connector 5/- each, P. & P. 1/-.

Control box 10/- plus 2/- p. & p. 12-way connector lead 12/6 plus 2/- p. & p.

SELENIUM F.W. BRIDGE RECTIFIERS

BRAND NEW WITH MAKER'S GUARANTEE

Plate size 7 1/2 x 7 1/2 x 7 1/2 in.

	£	s	d	curr		18V max. input	
12 V.D.C. 12 amps	1 19 6	3/6	D.C. out 1 amp	.. 3/6 plus 1/-
12 .. 26	1 19 6	3/6	" .. 2 1/2 8/6 plus 1/6
12 .. 36	3 19 6	7/6	" .. 4 12/6 plus 1/6
12 .. 54	5 17 6	7/6	" .. 8 19/6 plus 2/-
24 .. 18	3 19 6	7/6	New and guaranteed transformers suitable for use in conjunction with above, tapped at following voltages: 3.4.5.6.8.9.10.12 15.18.20.24.30.	
24 .. 30	5 19 6	7/6	2 amps	£ 5 6 p. & p. 3/6
24 .. 54	11 15 0	7/8	4 ..	1 19 6 .. 4/-
36 .. 18	5 17 6	7/8	5 ..	2 5 0 .. 4/6
36 .. 36	11 15 0	7/8	10 ..	4 15 0 .. 8/-

Plate size 4 1/2 x 4 1/2 in.

12 V.D.C. 8 amps	1 9 6	2/8
24 .. 8	1 19 6	3/6
36 .. 8	2 19 6	3/6

FOSTER VARIABLE Voltage TRANSFORMER

Input 120-250V. output 0-250 at 3 amps or 280 at 2 amps. Brand new in cylindrical pot size 6 1/2 in. high plus 1 in. control knob, diam. 6 1/2 in., weight 11 lb.

Few Only **£7.5.0** p. & p. 4/-.

DUBILIER "PULSPAK" CAPACITORS

Latest type, 1,000 mFd, 250 V.D.C. size 4 1/2 in., 2 1/2 in. diam.

12/6 p. & p. 1/-.

FIELD STRENGTH METERS

100-150 Mc/s incorporates 0-1 mA meter 1.8.5. telescopic aerial battery operation 50 and 1.5 V. in black crackle case. 7 x 7 x 7 1/2 in.

35/- p. & p. 2/9.

SILICON RECTIFIERS

800 P.I.V. 550 mA out 7/6 each, 1000 P.I.V.

9/- each. P. & P. 1/- each.

L.T. TRANSFORMERS

Pri. 240V. Output 3.3V 5a 8/6, P. & P. 2/6

LOUDSPEAKER

8 in. 8/6, P. & P. 2/6. 5 in. x 3 1/2 in. 15/6, P. & P. 2/6.

T.S.R.3 RECEIVER

Frequency range 36-85 meters. Complete with all valves £2.10.0. Carr. 3/-.

A.P.N.I. RADIO

ALTIMETER

Transmitter unit includes 2 x 855 acorn valves and transducer. As used in Wireless World wobulator. 6/6, P. & P. 2/6.

AERIAL WIRE

100 yards plastic covered on drum. 10/6. P. & P. 2/-.

FOOT SWITCH

With 1 yard of cable and two pinned plug. 5/-, P. & P. 1/6.

FOR CALLERS ONLY

Large and varied quantity of odd types of valves, many brand new, all at 1/- each. Many other items

TEST METERS



30,000 OHMS PER VOLT MODEL 500. Reads voltages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 o.p.v.; D.C. current to 12 mps. Resistance to 60 Megs.; Decibels from -20 to +35; Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3 5/16 x 6 5/16 x 2 1/2 in. **£8.19.6.**

2,000 OHMS PER VOLT MODEL TP-10. Reads A.C. voltages up to 1,000 D.C. at 2,000 ohms per volt and A.C. at 1,000 o.p.v.; Resistance to 1 Meg.; Capacitance to 1 µF; Decibels from -20 to +35; Output jack for Audio measurements. Size: 3 1/2 x 5 x 1 1/2 in. **£3.19.6.**

20,000 OHMS PER VOLT MODEL TP-55. Reads voltages up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 o.p.v.; D.C. current to 500 µA; Resistance to 10 Megs.; Capacitance to 0.01 µF; Decibels from -20 to +25. Size: 3 1/2 x 3 1/2 x 1 1/2 in. **£5.19.6.**

DOUBLE BEAM OSCILLOSCOPE TUBES
Another purchaser of Type CV 1596 equivalent to Cosor 99D as used in Oscilloscopes by Cosor (339 series) and Hartley & Erskine (13 series) Listed £12.
Brand new in Maker's **25/-**

HIGH FREQUENCY A.C. VOLTMETER. A First Grade Moving Iron Instrument with 5in. Mirror Scale, reading up to 150v. A.C. at 400 and 1,200-2,400 cycles. In substantial Oak case with removable lid overall size 8 1/2 x 8 1/2 x 5 1/2 in. Made for the Air Ministry by Everet Edgecumbe and in perfect order. Brand New and Unused. **ONLY 25/-**. Can also be supplied for 50 cycles, use either 0-150 or 0-300 volts.

TRANSISTORISED INSULATION TESTER. One handed operation, no cranking of generator, 3 testing Voltages 100, 250 and 500, to measure up to 500 Megohms. Complete with leather carrying case and test leads. **ONLY £17.10.0.** Illustr. details on request.

SUPER CRYSTAL STICK MIKE, complete with heavy desk stand neck cord, and screened lead. **ONLY 49/6** (post 2/6).

SPRAGUE CONDENSERS. Metal cased, wire end, New 0.1 mFd. 1,000 volt and 0.1 mFd. 500 volt, 7/6 per dozen. Special quotes for quantities.

RESISTORS. 100 assorted values, our choice. **New 7/6.**

PANEL METERS

25 microamps 1 1/2 in. Proj. circular 58/6. 50 microamps 1 1/2 in. Proj. circular 58/6. 100 microamps 1 1/2 in. Proj. circular 59/6. 250 microamps 1 1/2 in. Proj. circular 7/6. 500 volts A.C. 2 1/2 in. Flush circular 25/-.



MOVING COIL STICK MIKE, complete with heavy desk stand, and screened lead. **ONLY 59/6** (post 2/6).

ACOS 39/1 STICK MIKE with screened lead and talite stand **ONLY 35/6** (post 1/6).

CRYSTAL DESK MIKE with screened lead and built-in stand. **ONLY 15/-** (post 1/6)

15 OHMS P.M. SPEAKERS. Special Heavy Duty 12in. **£5.5.0.**

Wharfedale W12EG 12in. for Lead Guitars, **£10.10.0.** Wharfedale W15EG 15 in. for Bass Guitars, **£17.10.0.** 12in. wedge type speaker cabinet, **£2.17.8.** (Please add 5/- carr. all items.)

CONDENSERS. 100 assorted mica and silver mica. **NEW 10/-.**

VARIABLE VOLTAGE TRANSFORMERS. Fully shrouded. Input 230 v. A.C. 50/60 cycles. Output 0-20V. v. 2.5 amps. type 25.17.5. 5 amps. type 29 10.17.5. type 216.10.0. Brand new import, fully guaranteed. Immediate delivery and service. Illustrate details on request.

20/- CONSTRUCTOR'S PARCEL. Assorted colours wiring wire, solder, resistors, condensers volume controls, tag panel. **ALL NEW** (post 2/6).

LINEAR AMPLIFIERS. LG34, 4 watts, size 8 1/2 x 4 1/2 x 2 1/2 in. high, **£5.5.0.** L454 5 watts, size 7 x 7 x 5 in. high, **£5.19.6.** Protective cover, 12/9. L555 5 watts stereo-phonics, size 10 1/2 x 8 x 6 in. **£12.12.0.** Cover with carrying handles. 19/6. L110 10 watts Hi-Fi Ultra Linear size 9 x 7 x 5 in. high, **£13.13.0.** Cover with carrying handles. 19/6. "Conchord" 30 watts Hi-Fi Ultra Linear size 12 1/2 x 9 x 7 1/2 in. high, **£16.16.0.** Cover with carrying handles. 25/-, 150-50 watts Hi-Fi Ultra Linear, size 14 x 10 x 8 in. high, **£23.2.0.** Cover with carrying handles, 32/6. All amplifiers for normal A.C. mains, and ex stock. Details on request.

"Tripletone" Convertible Amplifier, size 10 x 3 x 4 1/2 in. high, 4 watts output matched for 2-3 ohms, OR 2 amplifiers can be coupled together for STEREO **£6.18.6** each.

"Tripletone" F.M. Tuner, size 11 x 6 x 3 in. high. Coverage 96-104 Mc/s, **£13.19.8** unpowered), or 215.14.6 (self powered). Details on request.

HETERODYNE FREQUENCY METERS TYPE LM14. Frequency range 125-20,000 kcs/s in 2 band. This is the United States Navy Model of the well known RC221 Frequency Meter, but has many additional features which increase accuracy and in addition it is fitted with an Internal Modulation switch to allow use as a Signal Generator. Size only 8 1/2 x 8 x 8 1/2 in. Full information on request

HARRIS ELECTRONICS (London) LTD.
138 GRAY'S INN ROAD, LONDON, W.C.1

Telephone *TE* Rminus 7937. Please include carriage cost on ALL items
Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross



The PUNCH you need!

HOLE PUNCHES

Instant Type					
3/8" diameter	Toggle switch	6/10 cs.
1/2" diameter	8/6 "
3/4" diameter	B7G	9/- "
1" diameter	B8A, B9A	9/6 "
1 1/4" diameter	10/2 "
1 3/4" diameter	10/8 "
2" diameter	11/8 "
2 1/4" diameter	Int. Octal...	13/4 "
2 3/4" diameter	16/2 "
3" diameter	18/10 "
3 1/2" diameter	B9G	21/8 "
4" diameter	24/4 "
4 1/2" diameter	Meter	33/2 "

Complete Set **£9.3.6.**

No extra charge for postage and packing in the U.K.

Oliver & Randall Ltd

Dept. 7
7 KELSEY PARK ROAD
BECKENHAM, KENT
Tel.: Beckenham 8262

BBC2 (625 LINE) TV AERIALS



EXTERNAL MAST MOUNTING ARRAYS
9 element 45/-; 11 element 55/-;
14 element 62/6

WALL MOUNTING WITH CRANKED ARM. 9 element 60/-; 11 element 67/6; 14 element 75/-.
CHIMNEY ARRAYS WITH LASHINGS. 9 element 72/-; 11 element 80/-; 14 element 87/6.
LOFT ARRAYS. 9 element 61 in. high, with TILTING ARM & 4 ELEMENT GRID REFLECTOR 62/6; 14 element ditto, 70/-; Co-ax. Plugs, 1/3. Low Loss Co-axial Cable, 1/6 yd.

BBC - ITV - F.M. AERIALS



B.B.C. (BAND 2). Telescopic loft 21/-, External S/D 30/-.

I.T.V. (BAND 3). 3 Element loft array 25/-, 5 Element 35/-, Wall mounting, 3 Element 35/-, 5 Element 45/-.

COMBINED B.B.C./I.T.V. Loft 1+3, 41/3; 1+5, 48/9. Wall mounting 1+3, 56/3; 1+5, 63/9. Chimney 1+3, 63/9; 1+5, 71/3.

F.M. (BAND 2). Loft S/D, 12/6. "H", 30/-, 3 Element, 52/6. External units available. Co-ax cable 84. yd. Co-ax. Plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes 12/6. C.W.O. or C.O.D. P.P. 3/-. Send 6d. stamps for illustrated lists.
K.V.A. ELECTRONICS (Dept.P.W.)
3b, Godstone Road, Kenley, Surrey
CRO 2527

Lyons Radio Ltd.

3 Goldhawk Rd LONDON W.12

POWER UNITS. Input 200/250 v. A.C. mains, ex-Air Ministry, 2 types available both housed in metal instrument cases 16 x 8 x 1 1/2 in. deep for rack or bench mounting. Special features include 2 section filter giving high degree of H.T. smoothing paper condensers used throughout, input and output fused, everything conservatively rated and well built.

Type 3. Output approx. 220 v. smoothed D.C. at 80mA, and 6.3 v. A.C. at 4a., fitted with 0/300 v. and 0/150 milliammeter to indicate output volts and current. PRICE **ONLY 47/6.**

Type 24. Output approx. 220 v. smoothed D.C. at 110 mA, and 6.3 v. A.C. at 4a., fitted with 0/300 v. meter and switch to indicate input and output volts. PRICE **ONLY 65/-** or less meter **ONLY 57/6.** Carriage any type 12/6. Plugs to fit input and output terminals 4/-.

RESISTANCE & COPPER WIRES. Eureka, Nickel Chrome, etc. Enamelled, Tinned, Cotton covered etc. Send stamp for list.

HIGH QUALITY 5 WATT AMPLIFIER. For 220/240 v. A.C. mains or 6 v. car battery. Separate gram and mike inputs. Quality output transformer for 3, 8 and 15 ohm speakers. Fully enclosed in metal case 9 x 8 x 6 in. As new and unused, case may be slightly store soiled supplied complete with valves and tested. **REAL SNIP. ONLY 67/6, post 5/-.** (Vibrator, required only for 6 v., 7/6 extra.)

FRONT RESERVE SHORT WAVE RECEIVER. Specially designed kits employing plug-in coils with exceptionally clear wiring diagrams and instructions to enable even the very beginner to construct a short wave radio with every confidence of success. A second and then a third valve can be added, the chassis supplied being punched to take all three stages. Can be operated from dry batteries or from a simply constructed mains power unit. Price 32/6. Cost of all parts to build the 1 valve S/W Radio including one coil 50/100 metres only 35/-, Post 2/-, 1/2 valve conversion stage 7/6, 2/3 valve conversion stage 10/-, Extra Plug-in coils to cover 10/20, 20/40, 100/200, 200/450 metres, 4/- each. Plans supplied separately 1/6.

We supply from stock most of the components and items specified or circuits published in this and other magazines and radio books. Let us quote for your circuit, first grade components at realistic prices.

All Parts in Stock for the following PW Designs.
 PW-6 Superhet.
 PW S.W. Converter.
 PW Beginners SW2.
 PW Transistor Inverter.
 PW Mains Power Pack.
 PW Build and Learn Series.

Send S.A.E. with list of parts required for quotation.

CATALOGUE

86 pages fully detailed and illustrated with hundreds of new items and bargains. PRICE 2/6. Post Paid.

● NEW VALVE, CRYSTAL TRANSISTOR LISTS FREE ●
 ● OUR STOCKS ARE FAR TOO VAST TO ADVERTISE—A CATALOGUE IS, THEREFORE, A MUST ●



MAINS AND BATTERY RECORD AND TAPE DECKS

- ★ All Decks Complete with Cartridges
- ★ BSR UA14 4-speed Auto ... £5 16 6
- ★ BSR UA15 4-speed Auto ... £6 19 6
- ★ Garrard Autolism Auto. ... £6 10 0
- ★ Unpluggable Hd. Versn. Auto ... £6 19 6
- ★ Battery Autolism ... £8 19 6
- ★ Stereo Version Auto. ... £7 19 6
- ★ SRP10 4-speed Single Player ... £5 0 0
- ★ SRP10 Battery Version ... £5 19 6
- ★ BSR GU7 4-speed Single Player ... £5 0 0
- ★ Garrard AT6 with Stereo Cartridge Autochanger ... £10 19 6
- ★ AT6 Mono ... £10 10 0
- ★ Collaro 2-track Studio Deck £10 10 0
- ★ Collaro Stereo 4-track Deck £13 19 6
- ★ BSR TD2 2-track Deck ... £7 19 6
- ★ P. & P. 3/6 any type above.
- ★ 9 volt Starr, 45 r.p.m. 39/6
- ★ 45 or 33 r.p.m. Starr 9V. 89/6
- ★ 45 r.p.m. Garrard, 6V. 35/-
- ★ 4-speed B.S.R. 9V. 5 gns
- ★ Garrard 9V. 2-speed, 2-track Tape Deck with cassette ... £11 15 0
- ★ P. & P. 2/6 any of above.

NEW LOW PRICES



MULTI-METERS
 Multi-range test meters featuring easy to read scales and provided with full operating instructions, lead and batteries. Suitable for amateurs, designers, repair shops, all domestic uses. Full details and specification in our catalogue.

- PT34 1 Kohm/volt £1 19 6
- M1 2 " " £2 9 6
- THL33 2 " " (illus.) £3 15 0
- ★ EP10K 10 " " 79/6
- ★ ITI-2 20 " " 82/6
- ★ TP55 20 " " £5 19 6
- ★ EP30K 30 " " £5 10 0
- ★ 500 30 " " £8 19 6
- ★ EP50K 50 " " £8 10 0
- ★ EP100K 100 " " £9 19 6

★ Leather Cases available.

RECORD/REPLAY/ERASE TAPE HEADS



Marriot Type R/RP/3 1/2 track record/replay head and Mullard type TS erase head with mounting post. Bargain offer 15/- pair. P.P. 9d.

- TRANSISTOR POCKET RADIOS**
 Ready to use, complete with Battery. Leather Case. Earphone. P.P. 2/- any type. Fully Guaranteed.
- 6-Transistor De Luxe ... 69/6
 - 7-Transistor Zephyr ... 79/6
 - 6-Transistor MW/LW ... £5.19.6

TRANSISTOR PORTABLE TRANSCIEVERS

9-transistor Portable Transreceivers. Supplied complete with leather cases, batteries, aerials, etc. in presentation case. Range up to 5 miles in favourable conditions. Sizes 6 1/2 x 3 x 1 1/2 inches. Superhet crystal controlled on transmit and receive. Price £21 Per Pair. P.P. 3/6.

TRANSISTOR TRANSCIEVER

3-transistor crystal controlled version of above. Range up to 1/2 mile. Price £8.19.6 Per Pair. P.P. 2/6.

A SELECTION FROM OUR STOCKS—NEW PRICES

- See Catalogue for full details.
- Sinclair Micro-6 (to build) 59/6
 - Sinclair TR 750 amp. (to build) ... 39/6
 - Sinclair Micro Injector (to build) ... 27/6
 - PP3 9 volt Battery Eliminator 18/6
 - Tap Jack Tuner 29/6
 - 10-Watt Horn Tweeter 27/6
 - 20-Watt Super Tweeter 69/6
 - Two-channel Mixer 15/-
 - 1 to 200 Mc/s. F/str. Meter 59/6
 - 1/2-Watt 4-transistor 9 v. 3 ohm ... 49/6
 - 5-hole Chassis Punch Kit 49/6
 - Headphones 2K ohm 12/6; 4K ohm Stereo Headphones 8+8 ohm. 3 gns.
 - Stereo Stethoscope Headset 8+8 ohm 25/-
 - Resistor Substitution Box 32/6
 - Crystal Mono Stethoscope Headset 10/6
 - Magnetic Mono Stethoscope Headset 12/6
 - Transistor Signal Injector 35/-
 - Fully Disappearing Car Aerial ... 35/-
 - Test Lead Kit with Pouch 8/6
 - Capacitor Substitution Box 22/6
 - De Luxe Stereo Headsets with junction box £6
 - 4-channel transistor mixer 49/6
 - ★ 3-Transistor MW Superhet tuner 67/6
 - ★ 4-Transistor Superhet MW/SW Tuner £7.9.6
 - Transistor Telephone Amplifier 59/6

FM VHF TUNING HEART

Printed circuit construction. RF stage and osc. mixer stage, fully tunable 85 to 105 Mc/s. Completely screened. Requires UCC85 (8/6). Brand new in maker's cartons 15/-. P.P. 1/-.

MULLARD POT CORES

LA1 12/6	LA5 17/6	LA45 15/-
LA2 15/-	LA6 22/6	LA2503 15/-
LA3 19/6	LA9 17/6	LA2504 15/-
LA4 12/6	LA10 17/6	LA2505 17/6

- 30 watt Soldering Iron 14/6. P.P. 1/-.
- Tape Demagnetiser 29/6
- 2K ohm lin. diam. mag. mic. 15/-
- Antex 15 watt min. soldering Iron 29/6
- Earphones Mag. or Crystal 5/-
- Telephone Recording attachment... 9/6
- Crystal Guitar contact mic. 12/6
- ★ 7-Transistor Record Player or tuner amplifier with treble/bass and vol. controls. £5.19.6.
- ★ 4-Transistor 1/2 watt amplifiers. Kit, 39/6. P.P. 1/6. Built 49/6. P.P. 1/6.

RECORDING TAPE

Sin. 600ft., 12/6; Sin. 900ft., 15/-; 7in. 1,200ft., 18/6; 7in. 1,800ft., 25/-; 7in. 2,400ft., 27/6. Excellent quality.

★ SCOTCH BOY TAPE. 3 1/2 in., 300ft. L.P. complete with spare spool. 5/6 P.P. 9d.

BUILD A QUALITY TAPE RECORDER




- ★ 6 Valve Printed Circuit designs. 2-track or 4-track units. 11 gns. 2-track, 12 gns. 4-track.
- ★ Collaro Studio Decks. 2-track 10 gns. P.P. 3/6. 4-track £14. P.P. 3/6.
- ★ Portable cabinets with Speakers. 5 gns. P.P. 3/6.

Complete Systems

2-track £26, P.P. 8/6. 4-track £30, P.P. 8/6.
 ● Complete in Every Detail ●
 Leaflet on request also on amplifiers to use decks with existing hi-fi equipment.

NOMBREX TEST EQUIPMENT

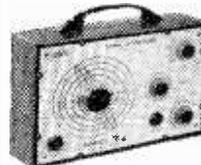

All transistor portable units supplied with full instructions.

Leaflets on Request.

- ★ 150 Kc/s to 350 Mc/s generator. RF Mod., AF. 8 ranges. Leads, batteries, instructions, £9.10.0.
 - ★ Resistance/Capacitance Bridge. £8.5.0.
 - ★ Transistorised Power Supply. £6.10.0.
 - ★ Audio Generator, £16.15.0.
 - ★ Inductance Bridge, £18.
- Fully Guaranteed.

CRYSTAL MICROPHONES

(See Catalogue for Full Range)

- Acos 39-1 Stick Microphone 32/6
- Acos 60-1 Stick Microphone 19/6
- Acos 40 Deck Microphone... 15/6
- Acos 45 Hand Microphone 19/6
- Lapel/Hand Microphone... 12/6
- 100C Stick with Stand..... 32/6
- BM3 Stick with Stand..... 49/6
- Lapel/Hand Magnetic..... 8/6

MINIGRAM PORTABLE TRANSISTOR RECORD PLAYER KIT, as previously advertised.

79/6 P.P. 3/6 (Battery 3/9).

QUARTZ CRYSTALS

100 kc/s 15/-; 500 kc/s 15/-; 455 kc/s 12/6; 456 kc/s 15/-; 27,255 Mc/s 15/-; Twin Crystal, 1 Mc/s, and 100 kc/s 22/6. Over 800 frequencies in stock.

Henry's Radio Ltd.

PADdington 1008/9
 303 EDGWARE RD., LONDON W.2
 Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

PRACTICAL WIRELESS

blueprints

MOST of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-SIDED BLUEPRINTS

The Strand Amplifier	*	5/-
The PW Signal Generator
The Savoy VHF Tuner	*	5/-
The Mayfair Pre-amplifier
The Berkeley Loudspeaker Enclosure	*	5/-
The Luxembourg Tuner
The PW Troubadour	7/6
The PW Everest Tuner
The PW Britannic Two	*	6/-
The PW Mercury Six
The PW Regency	*	5/-
The PW International Short Wave Two
Beginner's Short Wave Two	*	5/-
S.W. Listener's Guide
Beginner's 10-watt Transmitter	*	5/-
Transmitting and Aerial Data
P.W. "Sixteen" Multirange Meter	*	5/-
Test Meter Applications Chart
The Celeste 7-transistor Portable Radio	*	5/-
The Spinette Record Player
The P.W. 35-watt Guitar Amplifier	*	5/-
Transistor Radio Mains Unit	*	5/-
7 Mc.s Transceiver

RECEIVERS

The Tutor *	3/-
The Citizen *	5/-
Dual-Wave Crystal Diode	FW95	2/6
Modern One-valver	PW96	2/6
All-dry Three	FW97	3/6
Modern Two-valver	PW98	3/6
A.C. Band-pass Three	PW99	4/-
A.C. Coronet-4	PW100	4/-
A.C./D.C. Coronet	PW101	4/-
The PW Pocket Superhet	5/-

MISCELLANEOUS

The PW 3-speed Autogram	8/-
The PW Monophonic Electric Organ	8/-
The PT Band III TV converter	1/6
The Mini-amp *	5/-
The PT Olympic *	7/6
The PT Multimeter *	5/-

PLEASE NOTE that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

QUERY SERVICE

The P.W. Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) Be clear and concise.

(f) **We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

QUERY COUPON

This coupon is available until 7th November, 1964 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, NOVEMBER, 1964.

WE ARE THE SPECIALISTS *Transistor Equipment & Components*

86 PAGE CATALOGUE
PRICE 2/6. Post Paid.

TRANSISTOR HIGH FIDELITY EQUIPMENT FOR MAINS OR BATTERY OPERATION 10 OR 20 WATTS MONO OR 20 WATTS STEREO


● MONO FULL FUNCTION PREAMPLIFIER/ CONTROL UNIT

PRICE **£5.10.0** P.P. 2/-.

★ Fully detailed. Dark brown and gold front panel plate 8/6.

(Kit price 99/6 P.P. 2/-)

For use with transistor power amplifiers as below or valve amplifiers—hum free—high sensitivity—8 inputs between 1.5 mV. and 300 mV., with full equalisation. For all pick-ups—microphones, tuners—tape replay. Separate treble and bass with cut and boost—4 position low pass filter. Volume, 40 c/s. and 20 kc/s., etc. Output 250 mV. Overall size 9 x 2½ x 2in. Battery operated (2½ mA.) or from power supply. Signal to noise ratio 70 dB at 10 watts with power amplifier. Can feed two amplifiers for 20 watts. Supplied built or as a kit to build.

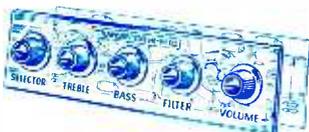

● INTEGRATED STEREO PREAMPLIFIER



Two channel version of above with addition of balance and mono/stereo controls. Overall size 9 x 3½ x 1½in. deep. Designed to feed two 10 watt power amplifiers as below. Supplied built and ready to use.

PRICE **£10.19.6** P.P. 3/6

★ Dark brown and gold front panel plate 12/6.

● MULTI-INPUT PREAMPLIFIER

For use with the transistor power amplifier. A simplified version of the full function preamp. 8 inputs from 1.5 mV. to 300 mV. Input selector, tone and volume controls. Size 5 x 2½ x 2in. Can feed one or two power amplifiers for 10 or 20 watts or the new 1½ and 4 watt amplifiers. Ideal for public address.

PRICE **65/-** P.P. 1/6.



★ Dark brown and gold front panel plate, 6/6.

● 10 WATT POWER AMPLIFIERS

★ 15 ohm 10 watt
40 volt supply.
£5.19.6 P.P. 2/6
(Kit price **£5.10.0**
P.P. 2/6)

★ 3 ohm 10 watt
24 volt supply.
£5.10.0 P.P. 2/6
(Kit price 99/6
P.P. 2/6.)



Direct coupled transformerless design. Sensitivity 100 mV. from 10 K ohm source for 10 watts output. Response -1 dB. 40 c/s. to 20 c/s. 0.25% total distortion at 10 watts. Push-pull class B output. 60 dB feedback. Two versions available for 3.4 ohm and 15/16 ohm output. Battery or mains supply operation. For use with mono or stereo preamplifiers as above. Supplied built and ready to use or as kits to build.


● MAINS POWER PACKS

PS245. For single amplifier, 24 volt 59/6
PS402. For single amplifier, 40 volt 59/6
PS24. For two amplifiers, 24 volt 69/6
PS40. For two amplifiers, 40 volt 69/6

DETAILS WITH
CIRCUITS OF
ABOVE UNITS
ON REQUEST

● VHF FM TRANSISTOR TUNER ●

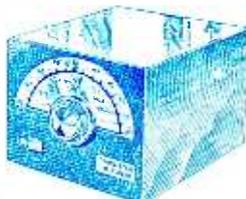- 5-Transistor.
- High Sensitivity.
- 4 Diodes.
- Full coverage 87 to 105 Mc/s.
- AFC and AVC.
- Up to 1 volt output.



Printed circuit design of high sensitivity and quality. Output for valve or transistor amplifiers. Size 3½ x 2½ x 4in. Simplified building instructions. All parts sold separately.

TOTAL COST **£7.19.6** P.P. 2/6.

(Gold sprayed cabinet assembly 20/- extra.)

Detailed Circuit Book on Request.



“CONVAIR”

PUSH-BUTTON
MW/LW
PORTABLE/
CAR RADIO

Total Cost of
ALL Parts
£7.19.6

P.P. 3/6

- New printed circuit 6-Transistor superhet design. Over 700mW push-pull output.
- Push-button selection of MW and LW with full tuning on both wavebands.
- A new design with amazing performance at a realistic price.
- New attractively designed portable cabinet with horizontal tuning and all stations marked. Colours Red or Blue with White.

Batteries 6/- extra.

Size 10 x 7 x 3½in.

ALL PARTS SOLD SEPARATELY

Leaflet on Request.

★ The easiest to build—the best performance—realistic price.

TWO NEW MINIATURE TRANSISTOR AMPLIFIERS

★ 1½ watts and 4 watts

6-Transistor and rectifier printed circuit designs. Overall size only 2½ x 2 x 1½in. Battery operated with push-pull output for 3 to 5 ohm speakers. Input 6 mV to 1½K ohm. Response 30 c/s. to 12½ c/s.

- 1½ watt version for 9 to 12 supplies. 150 mA average maximum current.


★ Built **65/-** P.P. 1/6

★ Kit **57/6** P.P. 1/6

- 4 watt version for 12 to 18 volt supply. 200 mA average maximum current. Ideal as a public address amplifier.

★ Built **79/6** P.P. 1/6

★ Kit **69/6** P.P. 1/6

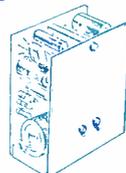

Either type ideal for microphones pickups, intercoms, radio amplifiers, etc. Can be used with any of our Hi-Fi preamps. For mono or stereo. ● Leaflet with circuits on request.

HENRY'S RADIO LTD. PADdington 1008 9.

303 EDGWARE ROAD, LONDON W.2.
(Open Monday to Saturday all day 9 a.m. to 6 p.m. Half-day Thursday 1 p.m.)

● Trade and Export enquiries invited ●

PLEASE TURN TO INSIDE PAGE

● ANYTHING TO DO WITH TRANSISTORS CONTACT US WITHOUT DELAY ●