

PRACTICAL WIRELESS


APRIL 1966

2¹

★The PW Reflex-2

A 2-transistor, 4-stage
Pocket Receiver
Simple step-by-step
assembly instructions

★SPECIAL FEATURE ARTICLE

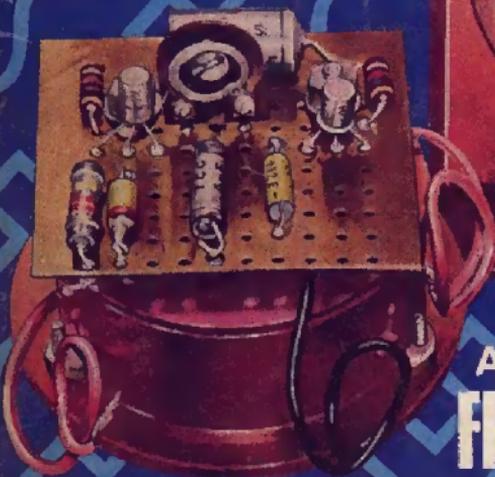

A DIRECT READING
FREQUENCY METER
AND REV. COUNTER

ADCOLA

REGISTERED TRADE MARK
Patent Invention

SOLDERING INSTRUMENTS AND EQUIPMENT



**DESIGNED FOR
THE AMATEUR'S
RADIO STATION**

ILLUSTRATED

List No. 70 $\frac{1}{2}$ " BIT

IN

**PROTECTIVE
SHIELD**

List No. 68

for catalogue apply direct to:—
Sales and Service Dept.

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD, LONDON, S.W.4**

Telephones
MACaulay 4272 & 3101

Telegrams
SOLJOINT LONDON SW4

JACKSON

the big name in PRECISION components

MINIATURE TUNING CAPACITORS TYPE "00"

The Jackson 'O' range contains six basic types of different air-dielectric tuning capacitors with a wide variation of capacities available in each type. In addition, there are optional extras such as concentric-spindle slow-motion drives, built-in trimmers and plastic covers. The maximum capacitance per section ranges from 12, 18 or 24 pF for FM types to 420 pF for AM types.



- ★ Type OO subminiature twin capacitor at 12/6
- ★ Type OFM two-gang for FM at 11/-
- ★ Type OPC for printed circuit mounting at 14/-
- ★ Type OG2 with internal reduction gearing at 16/-

MADE IN ENGLAND

Write for literature

JACKSON BROS. (LONDON) LTD.

(Dept. P.W.) KINGSWAY-WADDON, CROYDON,
SURREY

Phone: Croydon 2754-5 Grams: Walfico, Souphone,
London

NOMBREX INSTRUMENTATION

TRANSISTORISED AUDIO GENERATOR Model 63 £17.1.9

- ★ Laboratory Specification 10 C/s to 100 Kc/s.
- ★ Direct Calibration. ★ Sine and square output



Also available:

- ★ INDUCTANCE BRIDGE 66 ... £18.6.9
- ★ POWER SUPPLY UNIT 61 ... £6.14.6
- ★ C.R. BRIDGE 62 ... £9.6.9
- ★ R.F. SIGNAL GENERATOR 27 ... £10.16.9

All prices include Battery, Post and Packing.

Prompt delivery

S.A.E. for Technical
Leaflets

Trade and Export
enquiries invited


NOMBREX LTD.

Phone: 3515

Estuary House, Camperdown Ter., Exmouth, Devon

R.S.C. STEREO 20 HIGH FIDELITY AMPLIFIER

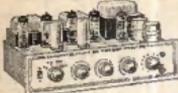PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL



- ★ Four-position tone compensation and Loudness Selector switch.
- ★ Will amplify direct from Tape Deck or Hi-Fi source.
- ★ Stereo/Mono switch.
- ★ Separate Bass "Lift" and "Cut" and Treble "Lift" and "Cut" controls.
- ★ Neon Panel Indicator.
- ★ Handsome Perspex Frontplate.

SUITABLE FOR "MIRK", GRAM, RADIO or TAPE. Employing valves ECC83, ECC85, ECC85, ECC85, ECC85, ECL84, E231. Send S.A.E. for leaflet. FREQUENCY RESPONSE $\pm 3dB$. 30-20,000 c.p.s. HUM LEVEL 46dB down.

SENSITIVITY 23 millivolts, maximum. HARMONIC DISTORTION (each channel) 0.3%. Output transformers are high-quality sectionally wound for specified specification. Output matching for 8 and 16 Ohm speakers. Price £17/8 channel. Complete set of parts with point-to-point wiring diagrams and instructions, or factory assembled, tested and supplied with our usual 12 months' guarantee for

13 Gns.

18 Carr. 12/6 or DEPOSIT 6/7 and 9 monthly GNS. payments 3/10 (Total £20.15.6).

R.S.C. A15 20 WATT R.M.S.

HIGH FIDELITY TRANSISTOR AMPLIFIER

With integral pre-amp tone control stages



Output for 8, 16 and 15 ohm speakers. Kit of parts consisting of Printed Circuit and all components for same including 9 Mullard or Newmarket latest type semi-conductors. Includes neat full wiring instructions or with printed circuit fully wired and tested £2 extra. Post 5/-

£6.19.9

Frequency Response $\pm 1dB$ 20-20,000 c.p.s. Harmonic Distortion 0.1% measured at 1000 c.p.s. Hum and Noise $\pm 80dB$. Sensitivity 20V. Bass Control $\pm 6dB$ to $-12dB$ at 40 cps. Treble Control $\pm 4dB$ to $-12dB$ at 10 Kcs. Suitable Power Pack Kit 3/9/6, Or ready built 5/9/6

AUDIOTRINE HI-FI TAPE RECORDER KIT

REALISED AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR. ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS. Incorporating the latest Magnavox Tape Deck. High Quality Tape Amplifier with equalisation for each of 3 speeds. 3 1/2" Flux P.M. Spinning empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet of latest styling and finished dark grey leathercloth with silver handles. A specially designed 14 x 17 x 9 1/2 in. high and circuit. Total cost if purchased individually approx. £35. Performance equal to units in the £50-£80 class. S.A.E. for leaflets. TERMS: Deposit 4/8, and 12 monthly payments of 4/2/- (Total 28 Gns.). 4 Track Model 3 Gns. extra.



25 1/2 Gns.


INTEREST CHARGES REFUNDED

ON H.P. ACCOUNTS SETTLED IN 6 MONTHS

LINEAR TAPE PRE-AMPLIFIER. Type LP.1. Switched Equalization. Positions for Recording at 14 in., 10 in., 7 1/2 in. per sec. and Playback E.M.S. Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier suitable almost any Hi-Fi Tape Deck. S.A.E. for leaflet. **9 1/2 Gns.**

R.S.C. A10 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER

A highly sensitive Push-Pull high output unit with self-contained Pre-amp./Tone Control Stages. Performance figures compare equally with most expensive amplifiers available. Hum level $\pm 70dB$. Frequency response $\pm 3dB$ 30-20,000 c.p.s. A specially designed sectionally wound ultra linear output transformer is used with 80V output valves. All first grade components. Valves EF86, EF87, ECC83, 6BT, 6Z3. Separate Bass and Treble Controls. Minimum input required for full output 12 millivolts so that any kind of Microphone or Pick-up is suitable. The unit is designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions. Complete kit of parts with point-to-point wiring diagrams and instructions. **12 Gns.** Carr. Supplied factory built with EL84 output valves. 10/-

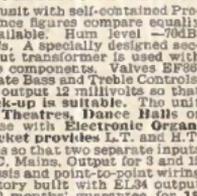

G.S. If required perforated cover with carrying handles can be supplied for £1. TERMS: Deposit 4/8 and 9 monthly payments of 3/3 (Total £17.3.6).

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP

Two input sockets with associated controls allow mixing of "mike" and gram. etc. High sensitivity. Valves ECC83, ECC83, EL84, EL84, E231. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers, etc. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response $\pm 3dB$ 30-20,000 c.p.s. Six negative feedback loops. Hum level $\pm 60dB$. SENSITIVITY 23 millivolts. Suitable for Crystal or Ceramic P.U.'s all types "mikes". Comparable with the very best designs. For Musical Instruments such as String Bass, Electronic Guitars, etc. Output Socket provides 30V, 50V, and 80V. L.S. for supply of a Radio Tuner. Size approx. 12 x 10 x 7 1/2 in. For A.C. mains 200-250V, 50 c.p.s. Output for 3 and 15 ohm speakers. Kit complete to last unit. Chassis fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns.** (Or factory built 5/1/8 extra).



Metal covers with 2 carrying handles can be supplied for £1. TERMS ON ASSEMBLED UNITS: Deposit 3/3/8 and 9 monthly payments of 3/4 (Total £12.16.0). Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, etc.

R.S.C. STEREO TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a stereo amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable all crystal or ceramic stereo heads. Ganged Bass and Treble Control give equal variation of "lift" and "cut". Provision is made for use as sprinter (mono) and 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E231. Outputs for 3-ohm speakers. Point-to-point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. **8 Gns.**



Or supplied factory assembled with 12 months' guarantee for £11.7.6. Carr. 10/-

TERMS: Deposit 2 Gns. and 9 monthly payments of 2/4 (Total 21.15.6).

R.S.C. 4/5 WATT AS HIGH GAIN AMPLIFIER

A highly-sensitive 4-valve quality amplifier for the home small club, etc. Suitable for all crystal or ceramic P.U. head units. Practically all "mikes". Separate Bass and Treble controls giving "lift" and "cut". Hum level 71dB down. Negative Feedback 15dB. H.T. of 300V. 55mA and wiring diagrams supplied. L.S. for supply of a Radio Tuner or Tape Deck Pre-amp. For A.C. mains 200-250V. Speaker output 5 ohms. Kit is complete in every detail with fully illustrated Handsome finished chassis, point-to-point wiring diagrams and instructions. Exceptional value **£4.15.0** or assembled ready for use 2/5/- extra, plus 3/6 carr. deposit 2/2/6 and 5 monthly payments of 2/8 (Total £2.15.6), for assembled unit.

CORNER CONSOLE CABINETS

Strongly made. Beautiful polished walnut veneered finish. Pleasing design. JUNIOR MODEL. For up to 2 in. speaker. Approx. 20 x 11 4/9 x 3 in. Carr. 5/6. STANDARD MODEL. To take up to 10 in. speaker. Size 37 x 18 x 10 in. **5 Gns.** Carr. 7/6. SENIOR MODEL. To take up to 12 in. speaker and with Tweeter cabinet. Size approx. 30 x 30 x 15 in. (Recommended for use with Audiotrine speaker system.) Carr. 8/6. Terms available.



12 in. HIGH QUALITY LOUSPEAKERS

In walnut veneered cabinet. 10 WATT MODEL. Class A, 12,000 lines, speech cut 3 or 15 ohms. **£4.19.6** Carr. 5/6. Terms: Deposit 1/5/- and 9 monthly payments of 10/10 (Total £5.12.6).



30 WATT MODEL. 15 ohms. Size 15 x 15 x 10 in. Terms: Deposit 2/6/- and 9 monthly payments of 17/- (Total £8.17.6). Carr. 8/6. 80 WATT MODEL. 15 ohms. Carr. 10/- or Deposit 3/5/- and 9 monthly payments of 22/- (Total £11.15.0). Any of above in extra heavy rexine covered Cabinets, 21 extra.

R.S.C. JUNIOR BASS REFLEX CABINET. Designed to take 15 ohm high quality speaker. Acoustically lined and ported. Polished Walnut veneer finish. Size 18 x 12 x 10 in. Strongly made. Handsome appearance. Superb reproduction. Carriage 5/-. **£4.7.6**

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12 in. 12,000 lines 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 x 7 1/2 in. size. Carr. **£4.19.9** Or Senior 20 watt, £6.19.6 Carr. 7/6. Or Deposit 2/1/- and 8 monthly payments of 1/5/- (Total £7.16.0).



TWEETERS

Fane 3 ohm or 15 ohm 25/9.

R.S.C. BABY ALARM or INTERCOM KIT. All parts with diagrams etc. In two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250V, 50 c.p.s. Fully isolated. Controllable at both units. A unit of this class would normally cost £20-£30. Only 5/9/6, carr. 5/-. Ready for use. 6 Gns.

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT

For lead, rhythm, bass guitar and all other musical instruments
For vocalists, gram, radio, tape and general public address



* UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a FANE 12in. 30 watt unit with extended frequency response. 4 Jack Inputs and two Volume Controls for simultaneous use of up to 4 pick-ups or "mikes".

* Cabinets covered in two-tone Rexine/Vynair with gold trimmings.

* Separate Bass and Treble Controls giving 'lift' and 'cut'. Send S.A.E. for leaflet. Or call at one of our branches and compare with units at three times the cost.

49 GNS. Or deposit of £7.18.0 and 12 monthly payments of Carr. 25/- 81/6 (Total 54 5/6s.).

R.S.C. B20 MULTI-PURPOSE AMP. especially suitable for Bass Guitar

With Massive 15in. high flux loudspeaker. Rating 25 watts. Individual bass and treble controls. Two jack inputs separately controlled. Heavy cabinet attractively finished in Rexine/Vynair. Size approx. 8 1/2 x 11 x 4 1/2 in. Send S.A.E. for leaflet. Carr. 17/6 Or deposit 24.14.6 and 12 monthly payments of 49/- (Total 59.14.6).



R.S.C. G15 IS WATT AMPLIFIER for Lead or Rhythm Guitar, Mike, Gram or Radio

High-fidelity output. Separate bass and treble controls. Twin separately controlled inputs. Heavy Duty 12in. 50 watt speaker. Cabinet covered in attractive Rexine/Vynair. Size approx. 18in. x 10in. x 4 1/2 in. Carr. 12/6. Or Deposit 8 gns. and 12 monthly payments of 32/6 (Total 22.15.6).

JASON FM/L VHF/FM Radio Tuner design. All parts inc. valves. £6.19.6

TANNOY RE-ENTRANT LOUD-SPEAKERS. For outdoor or 27/6 (Carr. 5 gns. 3 watts) 4/6

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 250-250-250 v. 50 c/s. Screened. MIDGET Clamped Type 24 x 24 x 2 1/2 in. 60ma. 6.3v. 2a. 14/9

250-250V. 60ma. 6.3v. 2a. 14/9

250-250V. 60ma. 6.3v. 2a. 14/9

250-250V. 100ma. 6.3v. 2a. 17/9

TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 standard jack inputs, i.e. mic, tape, gram, tuner, etc., into single output. Compact and completely self-contained, uses standard 9v. battery. **49/9**

FILAMENT TRANSFORMERS

200-250V. 50/0 primaries 6.3v. 1.5a. 6/6; 6.3v. 2a. 7/6; 12v. 1a. 7/12; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. 17/6

200-250V. 50/0 primaries 6.3v. 1.5a. 6/6; 6.3v. 2a. 7/6; 12v. 1a. 7/12; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. 17/6

200-250V. 50/0 primaries 6.3v. 1.5a. 6/6; 6.3v. 2a. 7/6; 12v. 1a. 7/12; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. 17/6

200-250V. 50/0 primaries 6.3v. 1.5a. 6/6; 6.3v. 2a. 7/6; 12v. 1a. 7/12; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. 17/6

INTEREST CHARGES

REFUNDED ON R.P.

ACCOUNTS SETTLED IN

6 MONTHS



(MANCHESTER) LTD.

Addresses Page 1010

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100v. line for 30/- extra.

Type C38, 15-30 watts. Fitted

5in. high flux speakers. Overall

size 5 1/2 x 4 1/2 x 4 1/2 in.

12 1/2 Gns. Carr. Or deposit

3 monthly payments of 27/9

(Total 51.4.9).

Type C42, 40 watts. Fitted

40 12in. 12,000 line 10 watt

speakers. Overall size 5 1/2 x 4 1/2

5in. approx. 19 Gns.

Carr. 15/-

Or deposit 3 gns. and 3 monthly

payments of 43/6 (Total 51.6s.).

30 WATT HI-FI AMPLIFIER

For ELECTRONIC ORGAN, GUITAR, VOCAL or INSTRUMENTAL GROUPS



A Four Input two volume control hi-fi unit with separate Bass and Treble 'cut' and 'boost' controls. Attractive 30 watt valve. Strong Rexine covered cabinet. Attractive Black/Gold fascia plates. For 200-

250V. A.C. mains. Output for 3 or 15 ohm

speakers. Send S.A.E. for leaflet.

Carr. 12/6 Or Deposit 3 gns. and 3 monthly

payments of 37/- (Total

17 Gns. £19.13.0).

18in. 60 WATT EXTRA HEAVY DUTY LOUDSPEAKERS

Famous Carr. 15/-

each. Normal price over 17 Gns.

22S. Very limited number

to clear fully guaranteed. Terms available.

LINEAR TREMOLO PRE-AMP UNIT

BENTLEY AGOUST CORPORATION LTD.

Suppliers to H.M. Government. 38 CALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK. ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' SPECIFICATIONS. ALL PARTS ARE GUARANTEED. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT OR FROM MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS 'NEW AND TESTED' BUT HAVE A SHORT AND UNRELIABLE LIFE.

0A2	8/0	3BX6	4/8	7B2	9/8	3Z5Z	7/8	AC/FPN 4/9	8AF4Z	7/9	EL84	4/6	L2319	6/8	ROL340A	U901	11/-	GD14	10/-	
0A2	8/0	3BX6	4/8	7B2	9/8	3Z5Z	7/8	AC/FPN 4/9	8AF4Z	7/9	EL84	4/6	L2319	6/8	ROL340A	U901	11/-	GD14	10/-	
0C24GT	4/8	3C0	2/5	7C3	6/8	28D1	8/9	(b) 1/78	EB4	1/-	EL83	7/6	LK329	6/8	8K34	65/-	U839	9/-	GT103 7/-	
1A3	2/6	8C8	3/-	7C7	5/-	39C1	6/8	AC/FPN	EB91	2/8	EL91	2/8	MHL4D12B	6/8	S135	22/6	U839	9/-	GT104 10/-	
1A4	1/6	3C	2/-	7D3	1/5	39C15	10/-	(b) 1/77	EB93	3/6	EL92	6/8	MHL4D12B	6/8	S135	22/6	U839	9/-	GT104 10/-	
1A5	5/-	6C9	10/10	7D6	14/6	39C17	11/8	AC/8G 28/6	EB93	3/6	EL90	8/7-	M84D	6/8	SP13C	18/6	U91	15/-	GT113 6/8	
1A7GT	7/6	8C10	8/-	7F7	7/-	39C18	9/3	AC/8G1V	ED04	6/8	EL90	15/4	M84D	12/-	SP41	2/-	U4929	8/6	GT114 6/8	
1C1	4/-	8C13	5/8	7F7	5/9	39F3	7/3	AC/8G1V	EL95	2/6	EL95	22/6	P12214	6/8	SP42	18/6	VMF43	12/0	GT117 7/-	
1C2	6/6	8C16	18/-	7F7	15/6	39F11	8/2	AC/8G1V	EL95	2/6	EL95	22/6	P12214	6/8	SP42	18/6	VMF43	12/0	GT117 7/-	
1C3	6/6	8C17	9/6	7X	5/-	39F11A	11/8	AC/TP 18/-	EB91	5/8	EM85	12/-	N8	10/8	SV25	27/2	YP2	8/6	GT174 8/8	
1C5	5/-	8C18	8/6	7Y4	5/-	39L1	8/6	AC/VP1 18/-	EBF90	5/9	EM7	12/8	N78	22/6	TA1	9/-	VP28	9/6	GT183 8/6	
1C6	10/6	8C19	24/-	8D2	2/4	39L15	10/6	AC/VP2 12/6	EB95	7/6	EM8	6/8	N108	20/2	TBD2	12/6	VM4	14/8	GT184 8/6	
1D6	9/6	8D3	9/6	9D2	3/-	39L17	11/6	ATP4	EMF99	9/9	EMM1	7/-	N39	25/2	TD4	7/6	VP4	14/6	GT186 10/-	
1ED1	4/6	8D6	3/-	9D7	7/6	39P13	7/8	AZ1	EM84	4/6	EN3	10/6	PC8	9/6	TR4	10/-	VP4	14/6	GT186 10/-	
1ED2	9/6	8D7	9/6	9D7	7/6	39P15	8/6	AZ1	EM84	4/6	EN3	10/6	PC8	9/6	TR4	10/-	VP4	14/6	GT186 10/-	
1G6	6/6	8F1	9/6	10K2	12/-	39P16	9/6	B38	4/9	EC22	9/8	EN1	5/6	PC8	9/6	TR4	10/-	VP4	14/6	GT186 10/-
1HE2GT	7/6	8F6	3/6	10D1	7/-	39P17	9/6	8B49	10/8	EC70	4/9	EN1	5/6	PC8	9/6	TR4	10/-	VP4	14/6	GT186 10/-
1H4	2/8	8F8	9/6	10D2	11/8	39P18	10/8	8T18	5/8	ECF90	7/8	ET51	6/8	PC8	9/6	TR4	10/-	VP4	14/6	GT186 10/-
1L4A	17/6	8F7G	8/-	10F1	10/-	39P14A	11/8	8L43	10/8	EM1	4/6	ET4	7/2	PC97	6/8	TP25	5/-	VR103	5/6	GT184 6/8
1L4B	16/10	8F8	5/-	10F3	9/6	39P15	9/6	C	10/8	EC92	6/8	EV48	9/3	PC84	8/6	TP2690	7/6	VR190	4/8	GT184 6/8
1LD6	4/6	8F12	3/6	10P18	9/9	39P18	12/6	CK006	6/6	ECU31	7/8	EV54	9/3	PC86	9/6	TY98	11/8	VR184	7/8	GT184 6/8
1LNGT	8/6	8F13	9/6	10P19	9/9	39S48	8/9	CV1	10/8	EC45	9/6	EV54	9/3	PC86	9/6	TY98	11/8	VR184	7/8	GT184 6/8
1N1	6/6	8F14	25/-	10D1D	9/6	39S49	8/9	CV8	11/8	EC53	9/1	EV57	8/7	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1P1	6/6	8F15	6/6	10P13	12/-	39S47	4/6	CV8	2/6	EC54	21/7	EV57	8/7	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1P10	4/6	8F16	6/6	10P14	11/6	39Z42	10/2	CV21	10/6	EC55	4/8	EV51	8/7	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1P11	4/6	8F17	12/6	11D5	2/6	39Z43	4/6	CV21	10/6	EC55	4/8	EV51	8/7	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1R4	4/6	8F18	18/6	11D6	17/6	39Z44	4/6	CV28	18/6	EC58	3/1	EV3	8/9	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1R4	4/6	8F18	18/6	11D6	17/6	39Z44	4/6	CV28	18/6	EC58	3/1	EV3	8/9	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1R4	4/6	8F18	18/6	11D6	17/6	39Z44	4/6	CV28	18/6	EC58	3/1	EV3	8/9	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1R4	4/6	8F18	18/6	11D6	17/6	39Z44	4/6	CV28	18/6	EC58	3/1	EV3	8/9	PC88	11/6	UB43	7/6	VU11	6/6	GT184 6/8
1R4	4/6	8F18	18/6	11D6	17/6	39Z44	4/6	CV28	18/6	EC5										



Heathkit models offer outstanding performance plus highest quality — at lowest cost

Anyone can build a Heathkit model. The easy-to-follow instruction manual issued with each kit-set shows you how. You will be proud of the professional appearance and performance of your finished model.

A KIT FOR EVERY INTEREST . . . FOR HOME, WORKSHOP, SERVICE & TEST DEPT.

TEST INSTRUMENTS



OS-2

3" PORTABLE 'SCOPE. OS-2 With improved performance and modern styling. "Y" bandwidth 2 c/s-3 mc/s. Automatic Lock-in sync. Mumetal C.R.T. shield. P.C. Board. Size 5" x 7" x 12" deep. Weight 9½ lb.
£30.8.0 Assembled **£22.18.0** Kit

5in. OSCILLOSCOPE Model 10-12U. Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing. F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges.
£45.15.0 Assembled **£35.17.6** Kit

DE-LUXE TRANSISTOR TESTER, IM-30U Provides complete d.c. analysis of PNP, NPN transistors and diodes.
£35.10.0 Assembled **£24.18.0** Kit

REGULATED POWER SUPPLY Model IP-20U. Transistorised, 0.5-50 v. D.C. Up to 1.5 amps. Compact: 9½ x 6½ x 11 in.
£47.8.0 Assembled **£35.8.0** Kit

4½" VALVE VOLTMETER, Model V-7A. The world's best selling VTYM. Measures up to 1,500 volts (d.c. and r.m.s.) and 4,000 pk. to pk. Res. 0.1 ± 1,000 Mc/s. Centre zero dB scale, d.c. input resistance 11MΩ. 4½in. meter. Complete with test prods, leads and standardising battery.
£19.18.6 Assembled **£13.18.6** Kit



V-7A

DE-LUXE 6in. VALVE VOLTMETER, Model IM-13U. Similar spec. to model V-7A but with improved accuracy. Larger meter. Unique gimbal mount.
£26.18.0 Assembled **£18.18.0** Kit



IG-82U

SINE WAVE GENERATOR, Model IG-82U. Freq. range 20 c/s-1 Mc/s in 5 bands. Simultaneous sine and square wave outputs.
£36.10.0 Assembled **£24.10.0** Kit

HARMONIC DISTORTION METER, Model IM-12U. Freq. cov.: 20-20,000 c/s.
£34.0.0 Assembled **£24.15.0** Kit

TV ALIGNMENT GENERATOR, Model HFV-1. Covers 3.6 to 220 Mc/s fundamentals.
£47.10.0 Assembled **£37.18.0** Kit

RF SIGNAL GENERATOR, Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands.
£19.18.0 Assembled **£13.8.0** Kit

MULTIMETER, Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. a.c. and d.c.; 150µA to 15A d.c.; 0.2Ω to 20MΩ. 4½in. 50µA meter.
£18.11.6 Assembled **£12.18.0** Kit

A wide range of other test instruments available.


HI-FI DEMONSTRATIONS & EXHIBITION

Concurrent with the Audio Fair.

The Grand Hotel, Southampton Row, London.
11 a.m.-9 p.m. (8 p.m. Sun.) April 14-17 inclusive.

AMATEUR EQUIPMENT

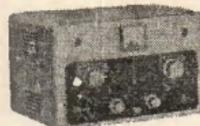AMATEUR TRANSMITTER, Model DX-100U. Covers all amateur bands 160-10M. 150 w. d.c. input, self contained with power supply. Modulator, VFO
Assembled **£104.15.0** **£79.10.0** Kit



DX-40U

AMATEUR BANDS RECEIVER, RA-1 Outstanding performance at low cost. Covers the amateur bands from 160-10 metres. Half lattice filter. Signal strength meter.
£52.10.0 Assembled **£39.6.6** Kit

AMATEUR TRANSMITTER Model DX-40U. Covers 80-10 m. Power inputs 75 w. C.W., 60 w. peak C.E. phone. Output 40 w. to aerial. Prov. for VFO.
£33.19.0 Kit
Assembled **£45.8.0**



Other kits in the amateur range include: SSB Adaptor SB-10U £39.5.0. Variable freq. Oscillator, VF-1U £10.17.6. Balun Coil Units B-1U £4.15.6. Grid-Dip Meter GD-1U £10.19.6. Q Multiplier QPM-1 £8.10.0. Reflected Power Meter HM-1U £8.5.0. Receiver, RG, £39.16.0.

SPEAKER SYSTEMS

BERKELEY Slim-line LOUDSPEAKER SYSTEM

★ Now from Heathkit, a loudspeaker kit with a fully finished walnut cabinet. ★ A 2 speaker system. ★ Modern, slim-line styling. ★ 30 c/s to 17 kc/s. ★ Only 7½" thick. ★ Use it horizontally or vertically. ★ Stand it on the floor or in your bookshelf.
£23.0.0 Assembled **£18.10.0** Kit



Berkeley

COTSWOLD STANDARD MODEL

Acoustically designed enclosure "in the white" 26 x 23 x 15½in., 12in. bass speaker, elliptical middle speaker, 2in. pressure unit. Covers 20-20,000 c/s. Complete kit with all controls.
£25.12.0 Kit



MFS SYSTEM (illustrated)

A minimum floor space model for the smaller room. 26in. high x 16½in. x 14in. deep. Similar performance to standard model.
£25.12.0 Kit

SSU-1 SYSTEM

A practical solution to the problem of a moderately priced speaker suitable for Stereo Mono amplifiers where the equipment has to be compact. Two speakers, balance control, ducted port reflex cabinet.
Incl. P.T. **£11.7.6** Kit
(less legs)



Set of 4 legs (7" or 15") 14.6 extra.

DAYSTROM LTD

Dept. PW4 GLOUCESTER, ENGLAND

MODELS FOR HOME, TEST AND WORKSHOP.
BRITISH HEATHKIT MODELS USE BRITISH COMPONENTS



HI-FI AMPLIFIERS

DE-LUXE ALL TRANSISTOR STEREO AMPLIFIER AA-22U.

A quality British transistor amplifier with high power (20 + 20W) at a reasonable cost, capable of delivering full power at all frequencies in the audio band. Handsome fully finished walnut veneered cabinet available. Professional slim-line styling. Send for full specification. Kit (less cabinet) £39.10.0 Cabinet £25.0. Accessories for panel mounting £1.18.0.



6W DE-LUXE STEREO AMPLIFIER. Model S-33H. An inexpensive stereo amplifier with high sensitivity. Suitable for use with Decca Derram cartridge.

£21.7.6 Assembled **£15.17.6** Kit

TAPE RECORD/REPLAY AMPLIFIER KITS. Will operate with most tape decks. Send for details.

TA-1M (Mono), 19.18.0 Kit. TA-1S (Stereo), £25.10.0 Kit.

STEREO CONTROL UNIT. Model USC-1. Ideal for use with MA-12 amplifiers. Kit £19.10.0. Assembled £26.10.0.



S-33

6W STEREO AMPLIFIER

Model S-33. 3 w/ch. Inputs for radio, tape and gram. Stereo/Mono range controls. Sensitivity 200mV. £18.18.0 Assembled **£13.7.6** Kit

TRANSISTOR MIXER. Model TM-1. A must for the Tape enthusiast. 4 channels, Battery driven.

£16.17.6 Assembled **£11.16.6** Kit

5W HI-FI MONO AMPLIFIER. Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build.

£15.10.0 Assembled **£10.19.6** Kit

HI-FI MONO POWER AMPLIFIER. Model MA-12. Ideal for use with Models USC-1 and UMC-1. 0.1 THD at 10W. Wide frequency range.

£15.18.0 Assembled **£11.18.0** Kit

18W STEREO AMPLIFIER.

Model S-99. Ganged controls.

Stereo/Mono gram, radio and tape

record inputs. PiB selection.

£38.9.6 Assembled **£28.9.6** Kit



S-99

A range of R/players, T/Decks available.
Send for full spec. of any model

Prices quoted are Mail Order and include free delivery in UK.

TRANSISTOR RECEIVERS

"OXFORD" LUXURY TRANSISTOR DUAL WAVEBAND RECEIVER.

The ideal domestic or personal portable receiver. 10 Semi-conductors. Soft leather case. Send for full details.

Incl. P.T. **£14.18.0** Kit



6 TRANSISTOR PORTABLE. Model LXR-1. Presigned I.F. transformers. Printed circuit, 7in. x 4in. high flux speaker. Real hide case. Very easy to build.

Incl. P.T. **£12.11.0** Kit



GC-1U

"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. Excellent portable or general purpose receiver for "amateur" or short wave listening. See full spec. leaflets.

Assembled £45.17.6 **£37.17.6** Kit

PA/GUITAR AMPLIFIERS

Model PA-1 (similar to PA-2 illustration) 50 watt output. Two 12" L.S. Variable tremolo, 4 inputs.

Assembled £74 **£54.15.0** Kit


Legs or castors available (extras). Model PA-2 (illustrated).

Starmaker 33. All transistor 20 watt output, two 12" L.S. Variable tremolo, 4 inputs.

Compact size. Assembled £59.10.0 **£44.19.0** Kit

Legs or castors available (extras). 50 watt Power Amp. MA-50

Assembled £27.18.0 **£19.18.0** Kit

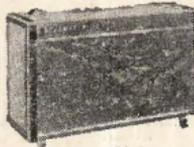

PA-2

HI-FI TUNERS

Model FM-4U. Tuning range 88-108 Mc/s. Tuning unit (FM-T-4U) with 10.7 Mc/s. I.F. (£2.15.0 incl. P.T.). I.F. Amp. (FMA-4U) complete with cabinet and valves (£13.13.0). Total **£16.8.0** Kit

Assembly can be arranged.

AM-FM TUNER. Covers FM 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 incl. P.T.), and I.F. Amp. (£22.11.6). Total **£27.5.0** Kit

Send for leaflets. Assembly can be arranged.



FM-4U



EQUIPMENT CABINETS

A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request.

Prices from **£8.8.0** to **£46.4.0**

SPEAKERS FOR YOUR OWN ENCLOSURE

12" Heavy-duty Bass (Fane 12/12) £7.7.0.

2" Tweeter (Fane 301) £3.1.6.

(both as used in the Cotswold systems).

8" Goodman's General Purpose GB £1.8.6.

Two Speakers + Cross-over, System SCM-1.

(As used in model SSU-1) with details for enclosure £5.5.0.

ELECTRONIC WORKSHOP KIT. Model EW-1. An outstanding experimental kit for children. £7.13.6 incl. P.T.

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS AND PRICES.

American Heath Catalogue, price lists in £ s. d. and details of direct delivery scheme sent for 1/- p. paid.

Welcome to our
LONDON HEATHKIT CENTRE.

We have opened a showroom and retail stores at 233 Tottenham Court Road.

WHEN YOU ARE IN TOWN, WE HOPE
THAT YOU WILL VISIT US THERE

To DAYSTROM LTD. Dept. P.W.-4, GLOUCESTER, ENG.

Please send me FREE BRITISH CATALOGUE (Yes/No) Full details of model(s). Amateur Brochure (Yes/No), American Catalogue 1/- (Yes/No), Instrument Brochure (Yes/No)

NAME _____

ADDRESS _____

LASKY'S RADIO

Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days when the sum paid will be refunded less postage.

THE "SKYROVER" RANGE

GENERAL SPECIFICATION

7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and short Waveband 31-64 M. and also 4 separate switched band-spread ranges, 15M., 16M., 18M. and 23M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.

A simple additional circuit provides coverage of the 1100/1550M. band (including 1500 M. Light programmes). All components and detailed construction data.

Only 10/- extra Post Free
This conversion is suitable for both models that have already been constructed.

Data for Receiver 276 extra. Refunded if you purchase the parcel. Four U2 batteries, 3/4 extra. All components available separately.

NEW—The SKYROVER Mk 111

New supplied with redesigned cabinet, edgewise controls, black and chrome plastic cabinet. Size 10 x 6 1/2 x 3 1/2 in. with carrying handle. Can now be built for H.P. Terms: 27/- dep. and 11 months at 15/6. Total H.P. Price £10-0-5.

NEW—The SKYROVER DE LUXE

Tune Control Circuit is incorporated with separate Control. In a wood cabinet, size 11 1/2 x 6 1/2 x 3 1/2 in., covered with a washable material with plastic trim and carrying handle. Car aerial socket fitted. Can now be built for H.P. Terms: 33/- dep. and 11 mths. at 19/6. Total H.P.P. £12-3-10



The Very Latest MAGNAVOX-COLLARO 363 TAPE DECKS

3 speed model—i.e. 31, 7 1/2 i.p.s., available with either 1 track or 2 track heads. Features include: pause control; digital counter; fast forward and rewind; Bow 4 pole fully screened induction motor; interlocking keys. Size of top plate 13 1/2 x 11 x 5 1/2 in. deep below unit plate. For 200/250V. A.C. mains, 50 c.p.s. operation. New, unused and fully guaranteed.

LASKY'S PRICE with 1 track heads **£10.10.0** Carriage and packing 7/6 extra
LASKY'S PRICE with 2 track heads **£13.9.6**

SPECIAL for OVERSEAS CUSTOMERS—the new Magnavox-Collaro 363 Deck for 110/125V. 50 or 60 c.p.s. mains now available, prices as above. Post to any part of the World, 35/-

SPECIAL PURCHASE! 7 TRANSISTOR RADIO CHASSIS

Superhet chassis, fully built—by famous British manufacturer—on printed circuit. Uses 7 Newmarket transistors giving 500 mV push-pull output—5 L.P. stages; ferrite rod aerial. Covers full, long and medium wavebands—300-3000M and 1200-3000M and switched band spread on 2043 (Luxembourg), 41m, speaker. Steel; volume control on/off switch, tuning dial and position for car aerial socket. Uses any 9V battery. Overall dimensions—7in. x 4 1/2 in. x 2 1/2 in. Absolutely complete except for cabinets.

LASKY'S PRICE 69/6 Post

Recommended battery PP6, 2/6 or PP7, 3/3 extra.

TRANSISTORS new and guaranteed

GET S1, GET S5, GET S8, 3/6; 371A, 374F, 3/6; OC46, OC71, OC81D, 4/6; OC44, OC70, OC75, OC81 (match pair 10/6), 5/6; AF17, OC70, OC200, 8/6; OC28, OC43, OC72, 7/6; OC201, OC204, 15/-; OC200, OC206, 15/6; OC28 24/6.

TRANSISTERS by BRUSH CRYSTAL 60

TO-018 465 kva., 2 kva., 7/6 EACH
TO-01D 470 kva., 2 kva., 7/6 EACH
TO-02B 465 kva., 1 kva., 7/6 EACH
TO-02D 470 kva., 1 kva., 7/6 EACH
TF-01B 465 kva., 2 kva., 7/6 EACH
TF-01D 470 kva., 2 kva., 7/6 EACH

B.S.R. AUTOCHANGERS—BRAND NEW AT LOWEST EVER PRICES

Brand new and fully guaranteed—complete with cartridge and stylus.

UA14 4 speed mains model £4. 9.6
UA16 4 speed mains model £4.12.6
UA18 9v. battery model £5.19.6
UA20 4 speed mains model £5.19.6
Add 5/- carriage and packing on each.

GARRARD AUTOCHANGERS

Auto-Slim Mono £4 19 6
A76 Mono £5 19 6
A76 Stereo £9 9 0
3000M Mono with stereo cartridge £8 9 0
BPS Mono £10 9 6
BPS2 Stereo £10 9 6
A790 less cartridge £10 19 6
A70 less cartridge £12 19 0
A30 less cartridge £9 14 0
A1060 with GCS cartridge £8 9 0
A3060 with GCS cartridge £7 7 0
Postage on all above 6/-

SPECIAL OFFER: GARRARD A75 AUTOCHANGERS

4 speed mains model—brand new and fully guaranteed
LASKY'S PRICE With mono crystal cartridge **£5.19.6** With stereo cartridge **£6.9.6** Post 6/-

LASKY'S FOR D.Y. CONSTRUCTION BARGAINS

The "REALISTIC" Seven

★ 7-Transistor Superhet. ★ 350 milliwatt output into 4in. high imp. speaker.

★ All components mounted on a single printed circuit board. ★ Full modulation and long wave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. Blue Grey or all Grey.

★ Socket for car aerial. ★ Frequency 470 Kcs. ★ Ferrite rod internal aerial. Operates from PP6 or similar battery. ★ Full data supplied.

All coils and I.F.'s etc. fully wound ready for immediate assembly. An outstanding receiver for **£5.19.6**

PP6 Batt. 3/6. Data and instructions separately 2/6. A superior wood cabinet parcel. All parts sold separately.

Can be built for **£5.19.6**

PP6 Batt. 3/6. Data and instructions separately 2/6. A superior wood cabinet parcel. All parts sold separately.

Can be built for **£5.19.6**

PP6 Batt. 3/6. Data and instructions separately 2/6. A superior wood cabinet parcel. All parts sold separately.

Can be built for **£5.19.6**

PP6 Batt. 3/6. Data and instructions separately 2/6. A superior wood cabinet parcel. All parts sold separately.

Can be built for **£5.19.6**

INTERNATIONAL TAPE

Famous American Brand—Fully Guaranteed

3in. Message tape, 100ft.	2 6
3in. Message tape, 250ft.	11 6
3in. Message tape, 500ft.	7 6
3in. Triple play, 800ft., Mylar base	15 0
4in. Triplay, 500ft., Mylar base	17 6
8in. Double play, 1,200ft., Mylar base	16 0
8in. Long play, 900ft., Acetate base	10 0
8in. Standard play, 900ft., PVC base	8 6
8in. Triple play, 1,200ft., Mylar base	25 0
5 1/2in. Double play, 1,800ft., Mylar base	22 6
5 1/2in. Long play, 1,200ft., Acetate base	18 6
5 1/2in. Standard play, 900ft., PVC base	11 6
5 1/2in. Standard play, 1,200ft., Mylar base	15 0
7in. Triple play, 2,400ft., Mylar base	45 0
7in. Standard play, 1,800ft., Acetate base	10 0
7in. Standard play, 1,200ft., Mylar base	15 0
7in. Long play, 1,800ft., Mylar base	18 6
7in. Double play, 2,400ft., Mylar base	26 0
7in. Long play, 1,800ft., Acetate base	15 0
7in. Triple play, 2,400ft., Mylar base	68 0
P. & P. 1 1/2-extra per reel, 4 reels and over Post Free.	

SINCLAIR MINIATURES

We stock the complete range of Sinclair Super-miniature Kits.
THE MICRA-20 pocket radio 59/6
THE 510-FLINE pocket radio 49/6
THE MICRO-FM tuner/receiver 25.19.6
THE X-50 Amplifier £7.19.6
Ready built and tested 25.19.6
THE X-10 Amplifier £5.19.6
Ready built and tested £6.19.6
See our Practical Wireless November '66 advertisement for details.

U.H.F. TUNERS

Only a few available. Complete with PCB and PCB5 valves. We regret no circuit or data is available. Knobs included.

LASKY'S PRICE 59/6

Post 2/6.

GORLER UT 340 FM/VHF TUNING HEART

Permeability tunes—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case, size 3 1/2 x 4 1/2 in. Circuit supplied.

LASKY'S PRICE 15/11

ECC85 valve 9/- extra. Post 2/-

Service in Great Britain to both & HI-FI ENTHUSIASTS

TAPE RECORDERS · RECORD PLAYERS · AMPLIFIERS, ETC. COMPLETE MONO/STEREO SYSTEMS TO YOUR SPEC.




NEW COMMUNICATION RECEIVERS MODEL KT 320 KIT



Designed in sub-assemblies for easy building. Covers range from 540 Kc/s to 30 Mc/s. Ham Band is provided with a scale for direct reading and can also be band spread. 8 valves. Facilitator: A.N.L., A.V.C. and M.V.C. Q-Multiplier also serves as B.F.O. H.F. stage and two I.F. stages ensure high sensitivity and selectivity (all coils and L.P.s are supplied pre-aligned). 2 Aerial Sockets. Stand-by position for use with a transmitter. 8 meter fitted. 200-250V. A.C. mains. Steel cabinet, grey crackle finish. Size 15 x 8 x 10in. Dial 12 x 4in. All parts new and fully guaranteed. Complete with full construction data and operating manual.

LASKY'S PRICE 25 GNS. POST FREE
Also available ready built and tested 25 gns.
H.P. Terms available.

NEW MODEL SR-150

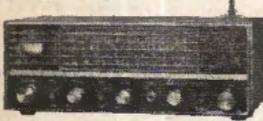

Covers full medium waveband and 1.6-4.4 Mc/s, 4.0-10.0 Mc/s and 11.0-3.0 Mc/s. In separate switched band spread ranges. Two aerials are fitted, an internal loop and external telescopic. Controls include: B.F.O. Sensitivity, C.W., A.N.L., tone switch, receive/stand-by, 8 meter. Easy to read illuminated dial with logging scale. For 200/250 V. A.C. 4 valves plus rectifier. Fitted with internal speaker and socket for phones or external speaker. Complete with full instruction manual. Cabinet size 12½ x 8½ x 6½ in.

LASKY'S PRICE 20 GNS. POST 10/-
H.P. Terms 25 dep. and 11 monthly payments at £11.14.0. Total H.P.P. £28.14.0.

MODEL HE80 12-valve super sensitive communication receiver. Freq. range 540 KHz-30 Mc/s. and 144-146 Mc/s. Dual conversion on 2 metres, with extra R.F. stage. Simple R.F. stage, two I.F. stages on all other bands. B.F.O. and Q-multiplier circuits. Improved A.N.L. and voltage regulated powerpack. "8" meter band spread on monster bands, large illuminated dial with logging scale. All controls fitted. Output for speaker and phones. Valve line-up: 4 x 6AQ5, 2 x 6BA6, 2 x 6BE6, 1 x 6BL6, 6AL5, 6AQ5, 6CA4 and 6AS. Steel case 17 x 7½ x 10in. For 200/250V. A.C. mains. Brand new with full instruction manual. No Kits available.

LASKY'S PRICE 59 GNS. POST FREE
H.P. Terms 25 dep. and 11 monthly payments at £4.18.0. Total H.P.P. £66.17.0.

STILL A FEW AVAILABLE Fully built and guaranteed MODEL BE30—LASKY'S PRICE 33 GNS. MODEL BE40—LASKY'S PRICE 18½ GNS. H.P. Terms available.

207 EDGWARE RD., LONDON, W.2
33 TOTTENHAM CT. RD., LONDON, W.1
Both open all day Saturday. Early closing Thursday.

Mail Orders and correspondence to 3-15 Cavell St., Tower Hamlets, London, E.1.



for multiplex adaptor. 5 valves—line up: ECC85, 6XN50L, ECC85, 6XN50L, ECC85, 6XN50L, ECC85, 6XN50L. Full vision tuning scale, size 21 x 6in. Overall dimensions 23 x 6½ x 8in. Made to the very highest standards.
LASKY'S PRICE 29½ GNS.



TRANSISTOR POCKET RADIOS
IDEAL GIFTS - All supplied complete with personal earpiece, battery and carrying case. Fully guaranteed—ready to use. **POST FREE.**
BOY'S 2 TRANSISTOR In attractive plastic case. Size only 4in. x 3¼in. x 1½in. Fitted 9½in. speaker. Socket for personal earpiece. Uses PP3 battery. Tunable over full medium waveband.
LASKY'S PRICE 35/-

BOY'S 4 TRANSISTOR MODEL
LASKY'S PRICE 45/-


6 TRANSISTOR MODEL
Fully built in plastic case, 4in. x 9½in. x 1½in. with 2½in. speaker. Uses single PP3 type battery. Tunable over full medium waveband.
LASKY'S PRICE 59/6

8 Waveband (Long and Medium) Model. Size 8 x 3½ x 1½in. Cream/black plastic case. Including earpiece and carrying case.
LASKY'S PRICE 89/6

THE "TRANSWAVE" DE LUXE TWO WAVEBAND RADIO
8 Sony transistors give super sensitive reception over the full Med. and Long wavebands. Internal ferrite and detachable chrome telescopic aerials. 2½" diam. speaker. Smart black plastic cabinet with metal trim—size of 8 x 5 x 1½in. Uses 3 pen light batteries. Complete with leather case and shoulder strap, earpiece and batteries. Post 2/6.
LASKY'S PRICE 95/-

2 WONDERFUL SETS FROM THE U.S.S.R.

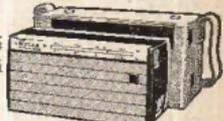THE "SELGA" 7 TRANSISTOR RADIO
High sensitivity circuit gives excellent reception over full Med. waveband and powerful volume. P.M. speaker. Uses PP3 type battery. Black and ivory plastic cabinet, size 7 x 4 x 2in. Socket for external aerial. Complete with solid hide case and shoulder strap, earpiece and battery.
LASKY'S PRICE £5.9.6 Post 2/6



THE "SOKOL" 7 TRANSISTOR TWO BAND RADIO
Super quality receiver covering the full Med. and Long wavebands with exclusive rechargeable battery which can be recharged from any 120/250V. A.C. mains supply. Also operates on PP3 type dry battery. P.M. 8, outer Ivory and black plastic cabinet 8 x 3½ x 1½in. Socket for external aerial. Complete with real leather case, rechargeable battery and charger, dry battery and earpiece.
LASKY'S PRICE £6.9.6 Post 2/6

SPECIAL OFFER — MAKER'S SURPLUS 7 TRANSISTOR PORTABLE RECEIVERS




By famous British maker 7 transistor plus 3 diode superb, 8 waveband portable receiver. Operating from four 1.5 v. torch batteries. Cover the full Medium Waveband and Short Waveband 31-84 Mc. and also a separate switched band spread range, 10M, 10E, 10M and 20M with Band Spread Tuning. All Mutual Transistors and Diode Uses 4-UR batteries, 5in. Ceramic Magnet P.M. Speaker. Easy to read Dial scale, 100 MW Output, Telescopic Aerial & Ferrite Rod Aerials. Very attractively styled plastic cabinet size 10 x 6½ x 3½in. Finished in mid-lava with metal trim and carrying handle.

LASKY'S PRICE £10.19.6 Post 0/-
Four UR batteries 3/4 extra.

Tel: PAD 3271 | 42 TOTTENHAM CT. RD., LONDON, W.1 | Tel: LAN 2573
Tel: MUS 2605 | 152/3 FLEET STREET, LONDON, E.C.4 | Tel: FLE 2833
Both open all day Thursday. Early closing Saturday.

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

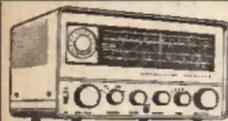


LAFAYETTE HA 43 COMMUNICATION RECEIVER

7 valves + Rectifier. 4 Bands 550 Kc/s - 1 Mc/s. "S" Meter. BFO-ANL-Bandspread Tuning. 200/250v. A.C. Brand New. 24 Gns. carr. paid.

HA.230 DE LUXE GENERAL COVERAGE RECEIVER

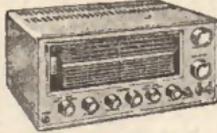Wonderful value. 8 valves + rectifier. Coverage 550 kc/s - 30 Mc/s 1 R.F. and 2 IF stages. "Q" multiplier. B.F.O., A.N.L., "S" meter, electrical bandspread, aerial trimmer, etc. Brand new and guaranteed. £39. S.A.F. for full details. Also available in easy to assemble semi-kit form at 25 gns.




LAFAYETTE HA-55 AIRCRAFT RECEIVER

108-128 Mc/s. High selectivity and sensitivity. Incorporates 2 RF stages including 9CW4 Navigator. 8 tubes for 1 tube performance. Solid state power supply, adjustable squelch control, slide rule dial, built-in 4-in. speaker and front panel phone jack. 220/250v. A.C. Supplied brand new and guaranteed. £18.7.6. Carr. 10/-.



CODAR EQUIPMENT

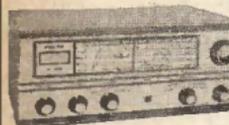Main London Agents
CR.70A. Communication Receiver £19.10.0
P.R.30. Freezerless. £5.10.0
A.S.6 Amateur Transmitter. £16.10.0
Postage extra.



TRANSORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press-to-talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with basic & wall bracket. £8-10.0 pair, P.F. 9/6.

MAGNAVOX 163 Tape Decks
New 3 speed tape deck, supersedes old Coliaro studio deck.
2 track. £10-10.0, 4 track. £13-10.0

GARRARD AUTOCHANGERS

Autoslim £5.5.0
1000 £5.19.0
2000 £5.19.0
3000 £5.19.0
P. & P. 5/- extra.

AMERICAN TAPE

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.

3in. 225ft. L.P.	4/-
3in. 500ft. T.P. mylar	10/-
3in. 1000ft. std. plastic	8/6
3in. 500ft. L.P. acetate	10/-
3in. 1200ft. D.P. mylar	15/-
3in. 1000ft. T.P. mylar	55/-
3in. 1200ft. L.P. acetate	12/6
3in. 1800ft. D.P. mylar	22/6
3in. 1200ft. T.P. mylar	45/-
3in. 1200ft. std. mylar	12/6
3in. 1800ft. L.P. acetate	15/-
3in. 1800ft. T.P. mylar	20/-
3in. 2400ft. D.P. mylar	25/-
3in. 3000ft. T.P. mylar	58/6

Postage 2/- Over 83 post paid.

OPEN 9 a.m. to 6 p.m. EVERY DAY MONDAY-SATURDAY Trade Supplied.

TEST EQUIPMENT

Portable Oscilloscope CT.52

A compact (9 x 8 x 1 1/2 in.) general purpose scope. 17.5 Dc/s-40Kc/s. Bandwidth 1Mc/s. Sensitivity 40 Mc/v. Mullard DG 7/5 2 1/2 in. CRT. For operation on 200/250v. A.C. Supplied complete with metal transit case, straps, test leads, and video head. Brand new and guaranteed. £22.10.0. Carr. 10/-.



OS 8B U OSCILLOSCOPES

High quality Portable American Oscilloscope. 3in. c.r.t. T/B 30c/s-300kc/s X Amp; 600Kc/s V Amp; 0-2 Mc/s. Power requirements 105-120v. A.C. Supplied in "as new" condition, fully tested. £25. Carr. 10/- Suitable 230/115v. Transformer. 15/6.



TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120Kc/s-250Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240 V. A.C. Supplied brand new with instructions. £12-10.0. Carr. 7/6.

Stockists of NOMBEX, SINCLAIR and all Electronic Equipment and Components

ERSKINE TYPE 13 Double Beam OSCILLOSCOPES

Timebase 2 c/s-750 kc/s. Separate Y1 and Y2 amplifiers. Up to 2.5 Mc/s. calib. at 100 kc/s and 1 Mc/s. 100/250 v. A.C. Guaranteed perfect £27.10.0. Carr. 20/-.



LAFAYETTE NUOVISTOR GRID DIP METER

Compact true one hand operation. Frequency range 1.7-180Mc/s. 250v. A.C. operation. Brand new. Supplied complete with all coils and instructions. £12-10.0. carr. 5/-.

LAFAYETTE 46 RESISTANCE CAPACITY ANALYSER

20pF, 2,000 mFD, 2 ohms, 200 Mc/s. Also, checks impedance. Turns ratio. Insulation 200-250v. A.C. Brand New. £15. carr. 7/6.



'9'S METER

50µA	..	29/6
100µA	..	32/6
200µA	..	34/6
500µA	..	37/6
500-500µA	..	39/6
100-0-100µA	..	41/6
500-0-500µA	..	43/6
1mA	..	45/6

CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters available at-stock S.A.F. for illustrated leaflet. Discount for quantity. Available as follows. Type MR3P/1 2 1/2 (3 1/2 in. square fronts.

2mA	..	22/6	3V. DC	..	22/6
5mA	..	22/6	10V. DC	..	22/6
10mA	..	22/6	20V. DC	..	22/6
20mA	..	22/6	50V. DC	..	22/6
50mA	..	22/6	100V. DC	..	22/6
100mA	..	22/6	150V. DC	..	22/6
150mA	..	22/6	300V. DC	..	22/6
300mA	..	22/6	500V. DC	..	22/6
500mA	..	22/6	750V. DC	..	22/6
750mA	..	22/6	150V. AC	..	22/6
1-0-1mA	..	22/6	150V. AC	..	22/6
1-0-1mA	..	22/6	300V. AC	..	22/6
5A. DC	..	22/6	500V. AC	..	22/6
5A. DC	..	22/6	500V. AC	..	22/6
22/6	..	22/6	'S' Meter 1mA	..	22/6

POST EXTRA. Larger sizes available—send for lists.

TWO-WAY RADIOS

Superb quality. Complete with all accessories and fully g'd. 31' transistor £7.18.0 pair. 4 T' resistor 11 gns. pr. 9 T' resistor £22-10.0 pr. 10 T' resistor 28 gns. pr. 20 T' resistor £18.4.0. (See for full details). These cannot be used in U.K.

VOLTAGE STABILIZER TRANSFORMERS

Will stabilize your mains voltage. Ideal for TV receivers and Industrial equipment. Input 80-120 v. and 160-240 v. Constant output 110 v. or 240 v. 2.50 watts. Brand new guaranteed. £10-10.0 Carr. 7/6.

VARIABLE VOLTAGE TRANSFORMERS

Brand New Guaranteed. Fully Shrouded. Input 230v. 50/60 c/s. Output 0-250 v.

1 Amp	£4.10.0
2.5 Amp	£7.12.8
5 Amp	£9. 0.0
8 Amp	£13.10.0
10 Amp	£15.10.0
12 Amp	£19.15.0
20 Amp	£32.10.0

2.5 Amp Portable Metal case with Meter. Fuses, etc. £9.17.6.

SILICON RECTIFIERS

200 P.I.V.	..	200mA	2/6
1,000 P.I.V.	..	500mA	6/6
800 P.I.V.	..	500mA	5/6
800 P.I.V.	..	5 amp	7/6
400 P.I.V.	..	3 amp	7/6
400 P.I.V.	..	500mA	3/6
150 P.I.V.	..	165mA	1/-
70 P.I.V.	..	1 amp	3/6
65 P.I.V.	..	5 amp	5/6

Post extra

MODEL PV-58 VALVE VOLTMETER

11 meg. input. 7 DC volt ranges up to 1,500 v. 7 AC volt ranges 1.5-1,500 v. 4,500 Peak to Peak Resistance 2 ohms 7/6. 1,000 megohm. Decibels -10dB to +50dB. Supplied brand new with instructions, leads and probe. £12.15.6 + P. & P. 9/6.

MODEL 500

300 p.p.m. 0.5/1 12.5/20/50/100/250/500/1,000 v. up to 1,000 v. Resistance up to 10 megohm. Current up to 250mA. Decibels -20 to +36dB. £5.5.0. P. & P. 2/-.

GW. SMITH & CO. (RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

SURBITON PARK RADIO

MARTIN AUDIOKITS & RECORDAKITS

F.M. TUNER UNITS Nos. 15, 16 and 17..... Cash £12.17.8
 Or Dep. 51/6 and 12 m. pymts. of 19/10..... (H.P. Price £12.17.8)
TRANSISTORISED AMPLIFIER with 6 position input selector, pre-amp and controls, 10 watt amplifier and Power Pack
FOUR TRACK AMP., as above..... Cash £14.5.0
 Or Dep. 57/- and 12 m. pymts. 20/10..... (H.P. Price £15.7.0)
 For 10 Ohm Speaker..... Cash £15.8.0
 Or Dep. 63/- and 12 m. pymts. 22/6..... (H.P. Price £16.12.0)
 All above include Front Panels, Knobs and Instructions.
TWO TRACK RECORDAKIT AMP. (Valve) FOR STUDIO DECK, 6 valves, controls, self powered..... Cash £11.11.0
 Or Dep. 47/- and 8 m. pymts. 25/6..... (H.P. Price £12.11.0)
 Or Dep. 39/- and 6 m. pymts. 28/4..... (H.P. Price £12.12.0)
 Or Dep. 52/- and 8 m. pymts. 27/6..... (H.P. Price £13.12.0)
Case for either of above tape amplifiers and Studio deck £5.5.0
TAPE PRE-AMP for Studio Deck, self powered..... Cash £8.8.0
 Or Dep. 34/- and 8 m. pymts. 26/8..... (H.P. Price £9.6.0)
TAPE PRE-AMP as above..... Four Track..... Cash £9.9.0
 Or Dep. 39/- and 6 m. pymts. 28/4..... (H.P. Price £10.9.0)
 All the above amplifiers are for the STUDIO deck which is no longer available. The Martin Recordakits will be modified for the new Magnavox deck in due course. Details will be forwarded to enquirers when to hand.
 We are leading stockists for all Martin Constructional Kits.

AMPLIFIERS-TUNERS Selection

ARMSTRONG 221 10-10 watts Stereo, Mag PU and Filter Cash £23.15.0
 Or Dep. 135/- and 8 m. pymts. 49/6..... (H.P. Price £26.2.0)
ARMSTRONG 222 10-10 watts Stereo Amplifier..... Cash £27.10.0
 Or Dep. 130/- and 12 m. pymts. 40/4..... (H.P. Price £28.14.0)
ARMSTRONG 224 F.M. Tuner Powered..... Cash £22.10.0
 Or Dep. 90/- and 12 m. pymts. 55/-..... (H.P. Price £24.5.0)
ARMSTRONG 225 AM/FM Tuner Powered..... Cash £28.15.0
 Or Dep. 115/- and 12 m. pymts. 52/2..... (H.P. Price £31.1.0)
ARMSTRONG 127 MONO 5W with AM/FM..... Cash £26.10.0
 Or Dep. 104/- and 12 m. pymts. 58/10..... (H.P. Price £26.12.0)

ARMSTRONG 127 STEREO as above Stereo amp..... Cash £27.10.0
 Or Dep. 135/- and 12 m. pymts. 55/-..... (H.P. Price £30.14.0)
ARMSTRONG 227 MONO 10W amp. with AM/FM..... Cash £26.15.0
 Or Dep. 141/- and 12 m. pymts. 58/10..... (H.P. Price £28.13.0)
ARMSTRONG 227 STEREO as above with Stereo Amp..... Cash £52.15.0
 Or Dep. 211/- and 12 m. pymts. 77/4..... (H.P. Price £56.19.0)
ARMSTRONG 226 STEREO as above, but Mag. P.U. Filter..... Cash £51.0.0
 Or Dep. 200/- and 12 m. pymts. 80/-..... (H.P. Price £55.16.0)
Teak Cases for all Armstrong Units..... £3.10.0
ROGERS CADET Mk. 3 10-10 watt Stereo Amp. Mag. P.U. Cash £29.10.0
 Or Dep. 118/- and 12 m. pymts. 43/3..... (H.P. Price £31.17.0)
CASE MODEL ROGER CADET Mk. 3..... £3.0.0 extra
LEAK STEREO 30 TRANSISTOR AMPLIFIER..... Cash £49.10.0
 Or Dep. 198/- and 12 m. pymts. 73/1..... (H.P. Price £53.11.0)

LOUDSPEAKERS Selection

PANE 125/10 Heavy Duty 12in. 20 watt..... Cash £5.17.6
WHARFEDALE SUPER 8/RS/1DD..... Cash £7.4.0
WHARFEDALE SUPER 10/RS/1DD..... Cash £11.13.4
 Or Dep. 47/6 and 8 m. pymts. 26/9..... (H.P. Price £12.13.6)
GOODMANS MAXIM..... Cash £17.10.6
 Or Dep. 70/6 and 12 m. pymts. 25/9..... (H.P. Price £18.13.9)

MOTORS-PICK-UPS Selection

GARRARD 5RP10 Mono..... Cash £5.10.0
GARRARD Model 1000 Mono..... Cash £7.10.0
 Or Dep. 34/- and 8 m. pymts. 29/-..... (H.P. Price £9.10.0)
GARRARD Model 9000 Stereo Lightweight arm..... Cash £11.11.0
 Or Dep. 47/- and 8 m. pymts. 29/4..... (H.P. Price £12.1.0)
GARRARD S.P.35 Less cart.: Single player..... Cash £12.10.0
 Or Dep. 50/- and 8 m. pymts. 27/6..... (H.P. Price £13.10.0)
GARRARD ATW Less cart.: Heavy table..... Cash £13.0.0
 Or Dep. 52/- and 12 m. pymts. 19/-..... (H.P. Price £14.0.0)
GARRARD LAB89 Push button oper. less cart..... Cash £27.10.0
 Or Dep. 130/- and 12 m. pymts. 40/4..... (H.P. Price £28.14.0)
GARRARD 401 Transcription Table. No arm..... Cash £39.10.0
 Or Dep. 130/- and 12 m. pymts. 47/8..... (H.P. Price £35.2.0)
GOLDRING G48 Mono Single Player..... Cash £11.11.0
 Or Dep. 47/- and 8 m. pymts. 25/6..... (H.P. Price £12.11.0)
GOLDRING G168 Less cart.: Pickup lift..... Cash £19.10.0
 Or Dep. 78/6 and 12 m. pymts. 28/1..... (H.P. Price £21.1.0)
GOLDRING G170 Less cart. PU lift. Heavy table..... Cash £28.15.0
 Or Dep. 120/6 and 12 m. pymts. 53/9..... (H.P. Price £32.5.0)
TERMS: C.W.O. or C.O.D. ALL ITEMS CARRIAGE FREE
 Leaflets available upon receipt of 6d. stamp

SURBITON PARK RADIO LTD.

48-50, Surbiton Road, Kingston-on-Thames, Surrey
 Phone KIN. 5549 :: Hours 9 a.m. to 6 p.m. daily (1 p.m. Weds.)



YOURS FREE FOR 7 DAYS

The New Picture-Book way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of excellent value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

EVERY DAY WE RECEIVE LETTERS PRAISING THESE BOOKS, HERE ARE A FEW FROM THIS MONTH'S POSTBAG.
 "... I cannot tell you how delighted I am with them..."
 G.N., B.F.P.O. 84,
 and BASIC ELECTRONICS, and needless to say I am delighted with them, and wish to congratulate you for publishing one of the best ever series dealing with this complex subject..." P.B., Worthing.

POST NOW FOR THIS OFFER!!

To Selray Book Co. 60 Hayes Hill, Hayes Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—3 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.
 Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY BASIC ELECTRONICS

Signature _____ (If under 23, signature of parent or guardian)


NAME _____
 BLOCK LETTERS BELOW
 FULL POSTAL ADDRESS _____

STERN-CLYNE ELECTRONIC CENTRES

HI-FI AND TAPE EQUIPMENT • RADIO • KITS • ELECTRONIC COMPONENTS

Justly famous—superb Hi-Fi designs from the Mullard Applications Research Laboratory, meticulously assembled by Stern and Venton. Buy them as hand-built and tested units, or in Stern-Clyne's famous Homebuilt Kit form. Either way provides performance far unequalled anywhere. If you are working to a budget, kits offer a real saving plus real building satisfaction. Each is absolutely complete and backed by comprehensive, easy-to-follow building instructions.

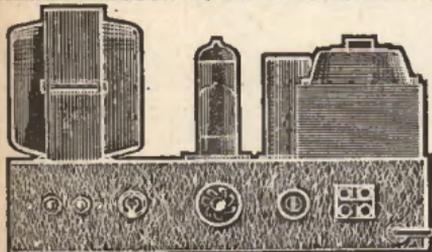* Designs by MULLARD
Interpreted by STERN



FIVE-TEN AMPLIFIER


One of the most famous amplifiers ever made—thousands are in service as the nucleus of high quality installations throughout the world. Check the phenomenal performance, unattainable by any other amplifier obtainable in this price range: Freq. response 0 c/s. to 30 kHz. Sat. 1 db. Distortion 0.1% at full 10 watts output. Noise—68 db. below 10 watts. Input signal 40 mV. for 10 watts. Out. Imp. 8 or 16 ohms. Valves E251, RP96, EC038, 2 x EL84. Size overall: 10 x 7 x 4 1/2 in. high. Incorporates mains outlet for gram and sax. supply of 250 v. at 45 mA. and 4.5 v. at 2 1/2 amps. For pre-amp. tuner, etc. To full Mullard specifications. Assembled and tested £19.10.0 Kit £16. 0/6. **FIVE-TEN AMPLIFIER AND TWO-VALVE PRE-AMP.** Assembled and tested £21.10.0. Kit 18 0/6. **FIVE-TEN AMPLIFIER AND THREE-VALVE PRE-AMPLIFIER.** Assembled and tested £25.10.0. Kit 21.10.0. *Add 5/6 carriage.*

Especially low-priced, but actually a robustly made reliable instrument which can be used anywhere for note taking, idea recording, dictation, etc. Mechanism solidly built on to rigid steel chassis and housed in tough grey plastic case with carrying strap and clear plastic tape-deck cover. Picked up with single multiselector function switch and volume control. Hand microphone has stop/start thumbswitch for remote control of record and playback transcription. Complete with tape and spare spool, teflon and miniature earphone. Size only: 7 1/2 x 7 1/2 x 4 1/2 in. high. **£9.10.0. Carriage 4/6.**

NEW PORTABLE TAPE RECORDER



SUPERB NEW STERN-CLYNE FMI V.H.F. TUNER

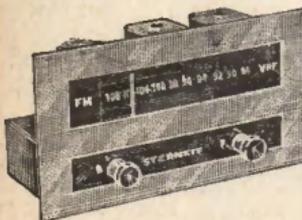


Especially designed for the Amateur builder, a new sensitive tuner unit that provides stable, interference-free reception of BBC FM transmissions. High quality output signal ensures optimum performance from any Hi-Fi audio system; superb styling makes for harmonious integration with existing equipment. Reliable easily aligned circuit employs BF

stage, tuned-anode tuned-grid freq. changer, 2 IP's, noise limiter and delay detector. Valves are 4 x RP91 plus 2 diodes. Input acc. 100mV for each. Dist. less than 1% at full deviation. Power reqd. 200v. at 50mA and 6.5v. at 1.5A. Panel black and silver-grey, size 8 x 5 1/2 in. Chassis: radiumina plated, overall depth 4 1/2 in. **FMI Kit of parts with Instruction Handbook, £7.8.0. Carriage 4/6. FMI Assembled and tested, £10.0.0. Carriage 4/6. Optional Power Pack Type D, Kit of parts, £21.5.0. Carriage 3/6. Power Pack Type D, Assembled and tested, £23.0.0. Carriage 3/6. Handbook only, 8/- post free. Descriptive leaflet on request.**



TWO-VALVE PRE-AMPLIFIER

Specially designed for use with the Mullard series of 3, 10 and 30 watt amplifiers but entirely suitable for all Hi-Fi power units but requiring input of more than 250 mV for full output. Features include inputs for crystal and variable reluctance pick-ups with RIAA equalization, plus radio, sensitive microphone, and tape replay direct or from pre-amp. Controls include 6-position selector, volume and wide range bass and treble boost. Valves 2 x RP96, size 9 1/2 x 4 1/2 x 3 1/2 in. high. Panel 10 1/2 x 9 1/2 in. Requires 300 v. at 3 mA. and 6.3 v. at 0.5 amp. Assembled and tested **£9.10.0. Kit 8.0.0. Add 5/- carriage.**

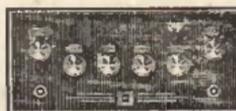

THREE-VALVE PRE-AMPLIFIER

Specially recommended for use with the 3-10 amplifier, but also suitable for use with all Mullard series music amplifiers and any high quality unit requiring an input of up to 250 mV. for full output. Features include: wide range Bass and Treble controls, high and low pass filters, auxiliary input and record output socket, switched inputs for crystal or magnetic pick-ups, radio, tape playback and auxiliary. Power required 250 v. at 6 mA. and 6.3 v. at 1 amp. Valves 2 x RP96 and EC038. Size 11 x 4 1/2 x 4 1/2 in. high. Panel 12 x 4 1/2 in. Assembled and tested **£13.10.0. Kit 11.10.0. Add 5/- carriage.**

TEST 7 Pocket Multimeter 39/6



Carriage 0/-


A really versatile instrument that makes a handy, pocket size tool. Measures AC or DC voltage in three ranges of 10-500-1000 v. Resistance 0-100,000 ohms, and Current 0-100 mA. D.C. Size only: 2 1/2 x 3 1/2 x 1 1/2 in. with ingenious dial design, providing a clear, easily read scale. Complete with battery and test leads.



MAGNAVOX 363 TAPE TRANSPORT

Manufactured to precise limits that permit recording on 1/4 inch tape back to the highest standards set by the Music Industry. Simple reliable design employs a single high-quality motor with heavy flywheel. Features include fast wind on and rapid rewind, pause control, 3-speed selection with interlock, built-in revolution indicator, piano key controls. Speeds 1 1/2, 3 1/2 and 7 1/2 L.P.S. Wow and flutter 0.1% on 7 1/2 L.P.S. Max. speed size 7 1/2. Playing time up to 130 min. per track from 1,200ft. standard tape. Size 13 1/2 x 1 1/2 in. plus 2 1/2 in. below mounting board. With 3 track heads. **£14.0.0. With 3 track heads. £21.0.0. Add 10/- carriage and insurance.**

HF/TR3 TAPE AMPLIFIER

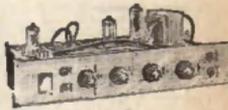

Really the best complete tape amplifier available to the home builder. Supplied already matched for the Magnavox 363 tape deck.

Features include: switched equalization for all speeds (CNR standards at 7 1/2 L.P.S.); Treble boost incorporated during Record. Bass boost during playback, speaker output matched for 4, 7.5, and 16 ohms, additional outputs for extension speaker, phono monitoring on Record and Hi-Fi playback through existing systems, inputs for Mic. Pick-up, and VHF Radio; Valves: RP96, EC038, EL84, 6BM1, 6BM1. Size overall: 11 x 6 x 4 in. (Panel 13 1/2 x 4 in.). Power pack on separate chassis size 7 1/2 x 8 x 4 1/2 in. Amp. & power pack Kit of parts **£18.10.0. Assembled and tested £19. Add 7/6 carriage.**

TAPE PRE-AMP TYPE C



Specially developed by Mullard Laboratories for use with high quality replay systems, and supplied specially matched for use with the Magnavox 363 tape deck. Features include: ferronucleic pole core inductors for treble equalization, push pull oscillator incorporating ferronucleic transformer, adjustable output, for matching to existing high-quality amplifier systems, inputs for Mic. Pick-up, Radio, etc. Valves: 2 x RP96, EC038 and 6BM1. Totally enclosed in case size 11 1/2 x 4 1/2 x 4 1/2 in. (Panel 13 1/2 x 4 1/2 in.) Power supply of 300 v. at 20 mA. and 6.3 v. at 1.5 A. in separate chassis size 6 1/2 x 4 1/2 x 4 1/2 in. high to 2 1/2 in. below mounting board. Pre-amp and power pack Kit of parts **£18. Assembled and tested £19.10.0. Add 7/6 carriage.**

**CLEAR-OUT OFFERS OF WELL-KNOWN HIGH GRADE EQUIPMENT
PRICES SLASHED TO MAKE WAY FOR NEW STOCK RANGES!**

Genuine Bargains! Original prices quoted are exactly those at which we have sold previously.

**FAMOUS MULTI-TESTER
AT TWO-THIRDS USUAL PRICE!**



*Type 2001—90 ranges, 50,000 ohms per volt sensitivity. Size only 2 1/2" x 4 1/2" x 1" deep with ingenious design allowing an extra large, easily read scale. Magnificently damped jewelled meter movement. Fitted with low loss, long life ceramic selector switch, complete with leads and test leads, battery and full instructions.

Ranges: DCV: 0.5-250-500-5000. ACV: 0-10-50-100-500-1000. DC Current: 0-500 uA, 0-5, 0.250mA. Resistance 0-5K-5M. Cap: 10pF-500pF and 0.001 uF-0.1 uF. Output: —30 to +10V.

WAS £5.50 NOW! £3.10.00 SAVE £1.15.00

*Add 2/6 p. & p.

BULK TAPE ERASERS



These are actually manufactured, high quality versions of the powerful demagnetizers used in instrument and aircraft manufacture, and represent the most effective way of restoring recorded or noisy tape to its original unmarked condition. Essential when using high fidelity recorders in conjunction with high-grade tapes: pays for itself over and over in preserving expensive tape performance. Bulk erasers can also be used to demagnetize small parts and tools, and for demonstration purposes, etc. Recommended types available:


Model RT-120
Cleans up to 7in. reels of tape in seconds. For 250/250 v A.C. operation. Size: 4 1/2 x 4 x 9 1/2 in. high. Finished grey crackle.
WAS £5.5.00 NOW 6/16 SAVE £1.17.6

Model 178
Extra powerful professional model. Cleans tape reels in all sizes up to 10 1/2 in. diam. Size: 7 1/2 x 4 1/2 x 9 1/2 in. high. Finished grey crackle.
WAS £7.7.00 NOW £5 SAVE £2.7.00

1/2 p. & p. and Corv.

DIVIDAL CROSSOVER NETWORKS

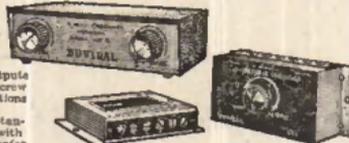Superb construction using selected high-grade components, each hand-soldered finished and constructed in metal cases with integral mounting feet. Inputs and speaker outputs are made to standard screw terminals. Full instructions supplied.



CV-1 Variable Crossover—Standard 3-way unit for use with low to medium power woofer and tweeter arrangement. Variable control permits adjustment of bass and treble output levels. In bronze finished case with black plastic panel size 4 1/2 x 3 1/2 x 1 1/2 in. high.

WAS £12.6 NOW 12/6 SAVE 10/- 3/4 p. & p. and Corv.

CV-2 Crossover Network—Hi-Fi 2-way iron-cored choke and filter system offering high frequency crossover at 2000 or 3500 cycles/sec. Totally enclosed in bronze finished case size 3 1/2 x 3 1/2 x 1 1/2 in. high.


WAS £2.9.6 NOW 25/- SAVE £1.4.6 3/4 p. & p. and Corv.

CV-3 Variable Crossover—Standard 3-way, medium and high power variable level unit offering mid-range crossover at 2000 c/s and tweeter crossover at 3500 c/s. Together with "L" Pad variable level controls for mid-range and tweeter outputs. Matching arrangements also permits use as 2-way crossover, or without level controls when speaker efficiencies are equal. Hand-soldered finished in 9-tone grey metal case size 5 x 3 x 2 1/2 in. high.

WAS £4.10.00 NOW 50/- SAVE £2 3/8 p. & p. and Corv.

WESTWELL CT-2B TWEETER


Adds sparkle and realism to the performance of almost any high quality reproducer. Nominal 1 1/2 diam. moving coil unit is attached to translucent bronze flange with matt black grille for mounting in or outside cabinet; alternatively detachable bracket can be used. Impedance 16 ohms. Rating 16 w max. 5 w nom. Recommended crossover frequency 3000 c/s. Sensitivity 105 dB/W. Size overall: 3 x 3 x 1 1/2 in. deep.

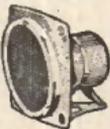

WAS 27/6 NOW 19/6 SAVE 8/- 3/4 p. & p. and Corv.


DIVIDAL SM-5 TRANSISTORISED MONO/STEREO MIXER

Compact, self-contained 8-channel audio mixer providing 4 separate, infinitely variable inputs on mono or stereo inputs for left and right channels on stereo. Superiorly constructed and handsomely styled, and finished in bronze enamelled case size 6 x 3 x 3 in. high. Internal PF3 battery gives approximately 400 hours operation. Input suitable for reel, cassette, record, etc. Max. input 1.5 v, max. output 2.5 v gain 6 dB. Inputs through standard jack plug socket; outputs through phono plugs.

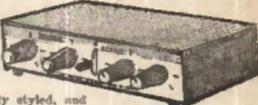

WAS £3.17.6 NOW £2.15.00 SAVE £1.2.6 3/8 p. & p. and Corv.

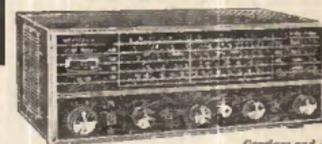VERITONE NEW, ADVANCED COMPACT COMMUNICATIONS RECEIVER



New, highly developed, extremely compact design. Veritone SR-150 has portable radio proportions and a DX performance comparable with many highly expensive, professional receivers. Frequency coverage is continuous from 240 Kc/s to 30 Mc/s in 4 bands, plus bandspread on Ham frequencies of 2.0, 7, 14, and 28 Mc/s. Features include extra large, clearly marked dial, "B" motor, variable "pitch" BFO, noise limiter, built-in headphones and extending rod antenna to receive all but most distant stations. Extras include phone output jack, standby switch, etc. Size only: 12 1/2 x 6 x 5 1/2 in. deep. Valves 12B6E, 12AV5, 12BA6 and 500C plus silicon rect. Invaluable for DX'er's, marine band listeners, etc. Housed in handsomely finished metal case. For 200/250 volts AC or DC. Supplied with 136-page "Wireless World Guide to Broadcasting Stations."

20 Gns.

EXCLUSIVE OFFER OF TOP QUALITY RECORDING TAPE

New American braided tape by world renowned manufacturers and equal in quality to the best obtainable elsewhere. Guaranteed solid free, red oxide coated, with high frequency response and uniform output. Resistant to moisture, heat, cold and abrasion. Available in a wide range of Acetate and Polyester qualities, each distinguished by hard and soft labels wrapped in colour coded cartons showing recording times at 7 1/2, 9 1/2 and 12 1/2 i.p.s. Compare the prices.

Range available:	
Polyester	Acetate
3 1/2 in. 600ft. Double Play 1 1/2	3 in. 600ft. Standard 9/8
1 in. 1,200ft. Standard 1 1/2	3 in. 900ft. Long Play 10/-
5 in. 1,800ft. Double Play 1 1/2	3 1/2 in. 1,200ft. Long Play 12/6
1 in. 1,800ft. Long Play 20/-	3 1/2 inch tapes post and packing
5 1/2 in. 1,800ft. Double Play 22/6	1/- per reel. Four or more reels post free.
1 in. 2,400ft. Double Play 25/6	

STERN-GLYNE ELECTRONIC CENTRES... most exciting shops in Britain!

Member of the Pantyia Group of Companies

MAIL ORDER & ALL ENQUIRIES TO: DEPT. PW, 3-8 EDEN GROVE, HOLLOWAY, LONDON, N.7. Tel. NOBth 8162/6

LONDON: 15 Tottenham Court Road, W.1 23 Tottenham Court Road, W.1 2nd Edgware Road, W.2 109 Finch Street, E.C.4 123 Holloway Road, N.7. 100 Berwell Church Street, S.E.5. 230 Edgware Road, W.2.	MUS 5988/0095 MUS 5988 2461 PAD 5988 2500 FLEET STREET 5811/58 NOBth 7841 RODWAY 2578 PAD 5988 2507	CROYDON: 15 Suffolk House, George St. BRISTOL: 26 Merchant Street, Bristol 1. LIVERPOOL: 96 Lord Street MANCHESTER: 20/22 Wilby Grove, M.4. Sheffield: 125 The Moor NOTTINGHAM: Shelton House, Lincoln St.	MUN 5988 2509 Tel. 50961 Royal 7450 Bickfords 5379/5046 Sheffield 25963 Tel. 46889
--	--	--	--

HIRE PURCHASE? CERTAINLY!

Easy payment terms available on all kits and assembled equipment value £10 or more. Let us have your enquiry.

Circuits • Diagrams • Repair Data

Here's all you need for servicing

OVER

1,450 Models

(1962—1965)



There is no other publication like Newnes **RADIO & TV SERVICING**... the greatest time-saver and money-maker you can own! 3 volumes packed with circuits, data and hints for repairing over 1,450 models (1962-65). TV, radio, tape recorders... all the famous makes are here. Plus big section of latest Radio and TV developments. Examine it, USE it for a week FREE! Don't miss this opportunity—simply post coupon today. Absolutely no obligation to buy!

All these makes

Ace, Aerodyne, Ajax, Alba, Argosy, Baird, Berec, Bush, Cossor, Dansette, Decca, Defiant, Doric, Dynatron, E.A.R., Ekco, Elizabethan, Elpico, E.M.I., Emerson, Eumig, Ever Ready, Ferguson, Ferranti, Fidelity, G.B.C., G.E.C., Grundig, H.M.V., Hitachi, Invicta, K-B, Magnavox, Marconiphone, Master-radio, McMichael, Motorola, Murphy, National, Newmatic, Pam, Perdio, Peto Scott, Philco, Philips, Playmate, Portadynes, Portogram, Pye, Radiomobile, Recording Devices, Rediffusion, Regentone, Retra, Revelation, R.G.D., Roberts' Radio, Sharp, Sinclair, Sobell, Sonolor, Sony, Sound, Standard, Stella, Stereosound, Stuzzi, Teletron, Thorn, Trans Arena, U.K.W., Ultra, Volmar, Waltham-Standard, Zenith.

3 VOLUMES

1,848 PAGES

OVER 2,000 CIRCUITS & DIAGRAMS

Examine it—use it
FREE FOR A WEEK

- TELEVISION • RADIO
- RADIOGRAMS
- TAPE RECORDERS
- RECORD REPRODUCERS

ONE REPAIR JOB CAN REPAY ITS COST

Compiled by a team of research engineers this big 3-volume library gives you, instantly, the vital data and circuits you need. Cuts out guesswork and delays, steps up your earning power.

Nearly 60,000 Sets of previous editions sold! Are you missing extra income? Find out why this big servicing aid is in such demand—send for your Free Trial Set today.

To: George Newnes Ltd.,
15-17 Long Acre,
London, W.C.2

Please send **RADIO & TV SERVICING** (3 volumes) without obligation to buy.

If you accept this application I will post 10/- deposit 8 days after receipt of books, then 20/- monthly for 6 months, paying £8. 10s. in all—or return the books. Cash in 6 days £8. 10s.

43/1775

If under 21 your father must fill up coupon.

Fill Name (BLOCK LETTERS) (Mr., Mrs., Miss)

Address

Occupation

Signature

Tick ✓ where applicable

<input type="checkbox"/> My Property
<input type="checkbox"/> Rented furnished
<input type="checkbox"/> Parents' Home
<input type="checkbox"/> Furnished Accom.
<input type="checkbox"/> Temporary Address

Free Trial applies G.B. For Ireland send cash price (refundable if title returned in 8 days). Overseas send cash price plus 18/- p. & p.

LITESOLD SOLDERING INSTRUMENTS

- SEVEN SIZES, FROM 10 WATTS TO 55 WATTS.
- REPLACEABLE BITS, COPPER & PERMATIP.
- EXCELLENT TEMPERATURE REGULATION.
- COOL, UNBREAKABLE HANDLE.
- RAPID HEATING.
- SIMPLE SERVICING.
- ALL VOLTAGES.
- LOW COST.



LITESOLD instruments are compact and nicely balanced. Bits are spring-collet mounted for firmness and easy removal. Copper bits are standard, in sizes from $\frac{3}{32}$ " to $\frac{1}{2}$ " dia. PERMATIP bits are slightly slower, but eliminate bit face wear. LITESOLD elements are encased in specially pre-oxidised wire for constant temperature regulation from new—less glamour but honest design, also apparent in the simple, unbreakable handle, with the element unit secured by two self-tapping screws (servicing couldn't be easier) and firm, spring-on clip. LITESOLD hollow-spindle construction prevents heat loss into the handle (which DOES stay cool) and improves performance. Useful LITESOLD accessories include HEAT GUARDS for elements, and BENCH STANDS.

Free details of the whole wide range of LITESOLD and ADAMIN soldering equipment in brochure SPI0.

LIGHT SOLDERING DEVELOPMENTS LTD.,

28, Sydenham Road, Croydon, Surrey.

Telephone: CROYdon 8589.

SOUDOGAZ Blowlamp

for the
handyman



Modern, clean
and efficient...

Ready for instant use at the strike of a match, operated by expendable 200 cartridge, gives instantaneous heat at 2198°F. (1200°C.) for approximately 2½ hours. With the three accessories, solderings on lead, bronze, silver, zinc, and aluminium, electrical installations, defrosting pipes, paint stripping, gutter repairs, etc., can be quickly completed.

SOUDOGAZ Blowlamp 45/- (Complete with normal Jet Burner), 200 Cartridge 3/9 extra. Paint Stripper, Fine Jet, Soldering Iron each 9/- extra.



CAMPING GAZ INTERNATIONAL

DIVISION

P.T.C. South Street, Dorking, Surrey

NEW ENLARGED EDITION of the popular GUIDE TO AMATEUR RADIO



An invaluable guide for those new to Amateur Radio. The book, which contains a wealth of interesting and helpful information, is of great assistance in obtaining a transmitting licence.


Several new constructional projects have been added to this Eleventh Edition. The Guide has 88 pages, well illustrated with photographs, circuit diagrams etc.

Price 5/- (by post 5/6) and 80 cents post paid in U.S.A. and Canada.

Further details of other R S G B publications, information about membership of the Society, including a free copy of the monthly R S G B BULLETIN, and the book itself may be obtained from the publishers:

RADIO SOCIETY of GREAT BRITAIN

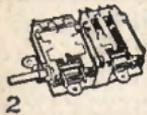
Dept. PW, 28 Little Russell St., London, W.C.1.



2



1

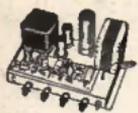

4



3



6



5




7



8



9

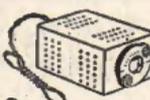

10



11




12



13



14

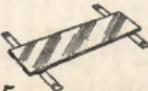

15

- MOTOR** $\frac{1}{2}$ H.P. 1440 revs. £2.10.0. $\frac{1}{2}$ H.P. 1440 revs. £2.19.6. P. & P. 15/- . These have been removed from equipment but are fully guaranteed.
- CYCLON AM FM PERMEABILITY TUNERS FOR ALL TRANSISTOR OPERATION.** Size 2 1/2 x 2 1/2 in. approx. By famous manufacturer. A.M. I.F. 470 Kc/s, P.M.-I.F. 10.7 Mc/s. A.M. coverage from 1620 Kc/s-525 Kc/s. V.H.F. coverage 168 Mc/s-86 Mc/s. Circuit diagrams 1/6. P.P. with Tuner, 1st and 2nd A.M. L.P.s. 1st, 2nd, 3rd and 4th V.M. L.P.s V.H.F. Osc. choke. A.M. I.F. lrasp. All the above are the R.F. end of an A.M./F.M. receiver car radio etc. The above items £2.10.0.
- AMPLIFIER KIT.** 3 to 4 watt Amplifier Kit. Comprising chassis 8 1/2 x 2 1/2 x 1 1/2 in. Double wound mains transformer, output transformer, volume and tune controls, resistors, condensers etc. Valves 8V5, 6X05 and metal rectifier. Circuit 1/6, free with kit, 20/6 plus 4/6 P. & P.
- 8-WATT 6-VALVE PUSH-PULL AMPLIFIER & METAL RECTIFIER.** Size: 9 x 6 x 1 1/2 in. A.C. Mains, 200-250v. 5 valves. For use with 2nd. or L.P. records, musical instruments, all makes of pick-ups and mikes or Output 8 watts at 5 per cent total distortion. Separate bass and treble lift control. Two inputs, with controls for gram, and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested. £4.19.6. P. & P. 8/-.
- MAGNAVOX COLLAR.** Set of three Taps Deck Motors. These are made for 15 but suitable auto transformer is supplied. Three motors 25/6. P. & P. 6/-.
- OSCILLOSCOPE FOR D.C. and A.C. APPLICATIONS.** Push-pull X amplifier. Fly-back suppression; Internal Time-base scan Wave form available for external use; pulse output available for checking TV line O/P Transmitters, etc. Provision for external -1/P and C.R.T. Brightness Modulation. A.C. mains 200-250v. £15.19.6. P. & P. 10/- . **FULL 12 MONTHS' GUARANTEE INCLUDING VALVES and TUBE.**
- FIXED FREQUENCY SIGNAL GENERATOR.** Crystal controls in metal case, size 10 x 5 x 6 in. Incorporating two 6X15 valves, mains transformer, metal rectifier, choke, inductor, lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new. 32/6, plus 7/- P. & P. A.C. mains 200-250 volts. **SILICON RECTIFIERS.** 250v. P.I.V. 750ma. Six for 7/6 post paid.
- POCKET MULTI-METER.** Size 8 1/2 x 2 1/2 x 1 1/2 in. Meter size 2 1/2 x 1 1/2 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1,500. D.C. current 0-150ma. Resistance 0-100K. Complete with test leads, battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron. Value 15/- to every purchaser of the Pocket Multi-Meter.
- CHANNEL TUNER I.F. 16-18 Mc/s.** Continuously tunable from 174-216 Mc/s. Valves required—PC790 and PC054 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxi, etc. Brand new by famous maker, 10/-, P. & P. 3/-.
- POWER SUPPLY KIT** in metal case, size 8 1/2 x 2 1/2 x 2 in. Incorporating mains transformer, rectifier and condensers. 230/200 A.C. mains Output: 9v., 10mA. 16/6 plus 3/- P. & P.
- B.S.R. MONARCH UA16 WITH FULL FT. HEAD.** 4-speed, plays 10 records, 12ins, 10ins, or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play facility; colour brown. Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 1/2 in. below baseboard 2 1/2 in. Fitted with full FT turnover crystal head. £4.19.8. P. & P. 7/6.
- FIRST QUALITY PVC TAPE**

5in. Std. 800ft. .. 9/-	5in. L.P. 800ft. 10/6
7in. Std. 1200ft. .. 11/6	7in. T.P. 600ft. 10/6
7in. L.P. 240ft. .. 4/6	5in. T.P. 1800ft. 20/6
5in. L.P. 1200ft. .. 11/6	5in. T.P. 340ft. 32/6
3in. L.P. 1800ft. .. 18/6	7in. T.P. 800ft. 42/6

 P. & P. on each 1/6. 4 or more Post Free.
- MAYFAIR 5-TRANSISTOR TAPE RECORDER.** Capstan-driven, battery operated, 7 1/2 and 8 1/2 l.p.s. Precision made. Push-button controls. High quality 2 1/2 in. speaker. Push-pull circuit. Output: 400 mw. Frequency response: 50-7,000 Hz. Fast rewind. Up to 1 hour twin track playing time. Automatic crating for re-recording. Dimensions: 8in. x 11in. x 3 1/2 in. Weights only 7lbs. £11.11.0 plus 7/6 P. & P.
- 40W FLUORESCENT LIGHT KIT** incorporating GEC Choke size 8 1/2 x 1 1/2 x 1 1/2 in. 2 bi-pin holders, starter and starter holder, 11/6. P. & P. 4/6. Similar to above: 80W Fluorescent Light Kit incorporating GEC choke size 1 1/2 x 1 1/2 in. 2 bi-pin holders, starter and starter holder, 17/6. P. & P. 5/6.
- GEC FLAT HEATER ELEMENT 500 w.** Can be used for wash boilers, washing machines, etc. Five or six elements can be used in parallel to give 2000/3000 watts. Size 5 1/2 x 1 1/2, copper enclosed. 2/6 each. P. & P. 1/- . 4 or more Post Paid.

RADIO & TV COMPONENTS (ACTON) LTD.


21b High Street, Acton, London, W.3.

All enquiries Stamped Addressed Envelopes

Goods not despatched outside U.K.

Shop hours 9 a.m.—6 p.m. Early closing Wednesday

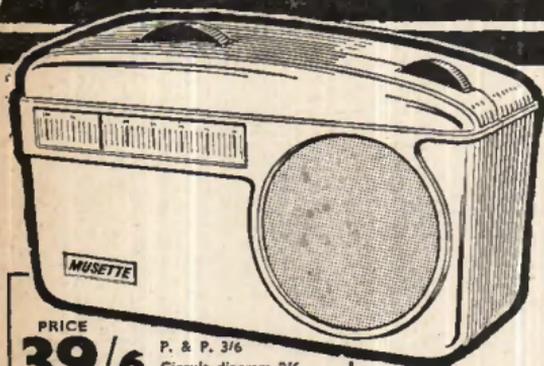MUSETTE 6 TRANSISTOR SUPERHET PORTABLE RADIO



- 2½" Speaker.
- 6 Transistors Superhet Output 200mw.
- Plastic Cabinet in red, size 4½" x 3" x 1½" and gold speaker louvre.
- Horizontal Tuning Scale.
- Ferrite Rod Internal Aerial.
- IF 470 Kc.
- All components, Ferrite Rod and Tuning Assembly mounted on printed board.
- Operated from PP3 Battery.
- Full comprehensive instructions and point-to-point wiring diagram.
- Printed Circuit Board.
- Tunable over medium and long wave band.
- Car aerial and ear piece socket.

PRICE

39/6

P. & P. 3/6

Circuit diagram 2/6
Free with parts.

including carrying strap.

NEW TRANSISTORISED SIGNAL GENERATOR



Size 5½" x 3½" x 1½". For IF and RF alignment and AF output 700 c/s frequency coverage 460 Kc/s to 2 Mc/s in switched frequencies. Ideal for alignment to our **39/6** P.&P. Elegant Seven and Musette. Built and tested.

Elegant Seven Mk II

COMBINED PORTABLE And CAR RADIO

The Radio with the STAR features

- ★ 4in. Speaker.
- ★ 7-transistor superhet. Output 350mW.
- ★ Wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½in.
- ★ Horizontal tuning scale, size 11½ x 2½in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. neutralisation on each stage 460 kc/s.
- ★ D.C. coupled output stage with separate A.C. negative feed back.
- ★ All components: ferrite rod and tuning assembly mounted on printed board.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.

ONLY **£4.4.0**

Plus 6/6 P. & P. Parts list & circuit diagram 2/6, FREE with parts

POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer, etc. A.C. mains 200-250v. Output 9v. 50mA, 7/6 extra.

- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket. Full after-sale service.

All enquiries Stamped Addressed Envelope.

RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3

Open 9 a.m.—6 p.m. including Sats. Early closing Wed.

Goods not despatched outside U.K.

Terms C.W.O.



CODAR QUALITY

ANOTHER CODAR TRIUMPH!

THE NEW 1966 CR.70A COMMUNICATION RECEIVER

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 350 Kc/s-30 Mc/s (540-10 metres) in four ranges; 550 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tune action. Unique aerial input stage exclusive to the CR.70A employing High 'Q' Air-spaced CODAR-404L inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron cored transformers, 470 Kc/s with EF183 frame grid valve for maximum gain and selectivity. 3 valves (including two twin triodes) giving 7 valve lineup. Separate B.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for 'private' listening. 2-3 ohm output for external speaker. Superb styling, metal cabinet in the new Organosol Satin lustre finish. Size 18" x 5 1/2" x 7 1/2". For A.C. 200/250V. Ready built. Not a Kit at the fantastic low price of £19.10.0. Carr. 7/6.

CODAR R.F. PRE-SELECTOR MODEL P.R.38. Considerably improves the performance of any superhet receiver over 1.5-30Mc/s. Uses EF183 Frame Grid Valve, and provides up to 20dB gain plus substantial image rejection, image and signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3 volts 3 amp L.T. Size 8 1/2 x 4 1/2 in. Ready built, complete with cables, plugs and instructions. £5.4.0. Carr. 3/6. **MODEL P.R.39X.** Self powered model for 200-250v. A.C. Also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 3/6.

CODAR 'Q' MULTIPLIER MODEL R.Q.16. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB, BFO. Size 8 1/2 x 4 1/2 in. Power requirements 180-250v. H.T. at 5mA 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions. £6.15.0. Carr. 3/6. **MODEL R.Q.16X.** Self powered version for 200-250v. A.C. and also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £8.8.0. Carriage 3/6.

CODAR A.T.S. 12 WATT 2 BAND TRANSMITTER. The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice". Size only 8 1/2 x 5 x 4 in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL P1-net output. P.A. Plate current meter plus neon indicator. Plate Screen modulator. AM/CW switch and Panel key jack. Plug change over for 6 or 12 volts heater supply. Ready built £16.10.0. Carr. 4/- **A.T.S. POWER SUPPLY UNITS.** For 200/250v. A.C. and 12v. Solid state for Mobile use, complete with all Transmit/Receive changeover switching available.

CODAR-KIT CR.6K MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandspread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2 1/2 ohm speaker. ★ Valve line-up: ECC81, 6X4, 6Z40. Size 12 x 5 1/2 x 7 1/2 in. **CODAR-KIT CR.6K** complete with valves, 3 coils (10-20, 25-75, 80-175 metres) and logging instruction manual. £9.10.0. Carr. 3/6. Extra coils 4/6 each. Instruction manual only 4/- (credited on order). (Can also be supplied ready built—price on request).

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER. ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 30/6. Carr. 3/6. Extra coils 4/6 each. Instruction Manual only 2/- (credited on order). Electrical Bandspread available. Provision to add 2 transistor amplifier.

SEND 6d. IN STAMPS FOR ILLUS. LEAFLETS OF THE CODAR RANGE • H.P. TERMS AVAILABLE • WORLD-WIDE MAIL ORDER SERVICE

CODAR

CODAR RADIO COMPANY
BANK HOUSE, SOUTHWICK SQUARE
SOUTHWICK, SUSSEX. Tel. 3149
G3HRE G3HGQ
Canada: Codar Radio of Canada, Tweed, Ontario.

PRACTICAL WIRELESS

APRIL 1966
VOL 41 NO 710

LAW OF THE JUNGLE

SOME readers take us to task for disapproving of pirate radio stations. A common accusation is that we are "against pop music"; that, teetering on the brink of senility, we cannot appreciate the prodigious talents of the Top Tenners. Such thrusts are wild indeed, for they completely miss the point!

Whether they churn out pop music, symphony concerts, language tuition or talks on advice to the lovelorn is beside the point; they should not be on the air at all.

Aircraft are not allowed to land and take off just where they fancy, flights must be controlled and scheduled—even though some of our critics claim that "the air is free for all to use how they like". Cars are not allowed to be driven at 100 mph in the wrong direction down a one-way street. This complex modern society insists that "liberty" must often be subjected to judicious control. And broadcasting is no exception.

Years of co-ordination and planning have made the jig-saw of the m.w. band fit together reasonably well. Frequencies, sites, power allocations have been arranged to the best mutual advantage. But the pirates burst in with a lofty disdain for law, order and the rights of other people to listen. Consequently protests have come from Sweden, Yugoslavia, Czechoslovakia, etc., concerning reception ruined by pirate stations.

Pirates also evade the Copyright Act, to the financial detriment of authors, composers and musicians. There is no control of programme or advertisement content. There is nothing to stop undesirable elements setting up their own pirate station. Unless . . .

The Government has, by implication, shown that the position of the pirates is indefensible. They are breaking international radio law. They are specifically contravening legislation signed last year by the Council of Europe—which other signatories have already used to shut down their pirates. Then what is the PMG waiting for—could it be a General Election!

Let him no longer tolerate the law of the jungle in broadcasting.

CONTENTS

	<i>Page</i>
News and Comment	1030, 1060
Direct Reading Frequency Meter	1032
Switch-Tuned Superhet—Part 2	1036
On the Short Waves	by John Guttridge and David Gibson, G3JDG 1040
Books Reviewed	1044
E L Key	by P. Murphy 1047
Practically Wireless	by Henry 1052
Versatile Preamplifier and Tone Control	by A. S. Ellis 1053
Reflex 2	by Gordon J. King 1056
No. 19 Set Mods.—Part 2	by S. Simpson 1062
Mic. Preamp	by A. E. J. Simons 1070
Electronic Gate or Trace Doubler	by H. T. Kitchen 1073
Oscillator Circuitry—Part 2	by R. Leyland 1082
Club Spot—Y.M.C.A. Belfast	1089

A New P.W.?

I READ PRACTICAL WIRELESS with great interest and would like to see you enlarge it. I would also like to see a PRACTICAL WIRELESS Annual (similar to the *Practical Motorist Annual*).

One other thing I would like to see is the revision of the *Practical Wireless Circuits* book, as I think this is very out of date—the coils and components being almost impossible to obtain.

I would like to see a licence for Novice Amateurs on 160m using 10W, as I think it would make use of a band which is dead most of the time.

J. Savage.

London,
S.E.11.

★ ★ ★

[PRACTICAL WIRELESS will be "going up in size" from the May, 1966 issue onwards, and *Practical Wireless Circuits* is, at the moment being revised and will contain up-to-date circuits using up-to-date components. It will be on sale in a few months time.]—Editor.

Correspondents' Club?

I HAVE noticed that there are several enthusiasts about my own age (14) who have written to P.W. asking for correspondents. I am sure that we could all get together and have regular correspondence, writing say, each month or fortnight to each in turn. By doing this, we would gain the experience of others and also offer our own experience. Some, like me, no doubt are preparing for the R.A.E. and would certainly benefit from corresponding with other enthusiasts.

Another idea I had was to swap components for stamps or other articles with enthusiasts in India, Ceylon, etc., who find it difficult to obtain electronic components and issues of P.W.

If anyone is interested would they please write to me. I will then write to all the members giving the names and addresses of the other members to start the "Pen Club" off. I would welcome any other ideas on the subject.

S. V. Odgear.

111 The Hollow,
Corsley,
Warminster,
Wiltshire.

NEWS AND..

P.W. AND P.T.V. FILMSHOW



Friday, 4th February, was the date of the P.W. Filmshow. Once again this year, the meeting was well attended by readers from all parts of the country.

In the absence of Mr. Stevens, the Editor, Mr. A. T. Collins, the Managing Editor of the Practical Group took the chair. After his opening speech, Mr. Collins introduced Mr. Ian Nicholson, of Mullard Ltd., the speaker of the evening.

Mr. Nicholson then introduced the first film, entitled "Electromagnetic Waves—Part 2". After this film there was an interval of 25 minutes during which refreshments were served.

During the second half of the programme, Mr. Nicholson gave a talk on Servicing Transistor Receivers. After this, there followed a film entitled "Thin-Film Microcircuits". The evening ended with a question and answer session during which Mr. Nicholson answered questions put to him by members of the audience.

The photograph shows Mr. A. T. Collins (left) and Mr. Ian Nicholson discussing a thin-film microcircuit.

AIRBORNE RADIO AIDS FOR EAST AFRICAN VC-10s
Three Super VC-10 aircraft on order for East African Airways are to be completely equipped with Marconi Sixty Series airborne radio navigation and communication aids, including the Doppler Navigator, which will form the primary en-route navigational system in the aircraft.

Each aircraft will be fitted with dual installations of the AD160 v.h.f. communications system, AD260 v.h.f. navigation system, AD360 automatic direction finder and the aircraft selective calling system, Selcal. Also in each aircraft will be the Marconi Doppler navigator, type AD560.

The AD560 Doppler navigator is currently in operation with BOAC, Qantas Airlines, Ghana Airways and Air New Zealand and will be fitted in new aircraft for Iraqi Airways and Pakistan International Airways in addition to the Anglo/French Concorde supersonic airliner.

.. COMMENT

ARCOLECTRIC RELEASE NEW CATALOGUE

Arcolectric Switches Ltd., Central Avenue, West Molesey, Surrey, announce their 1966 catalogue, No. 136. It describes their current range of switches, neon indicators, and signal lampholders.

Many new products are featured in this catalogue including the "27" and "28" range of lever and semi-rotary switches.

Copies of this catalogue are readily available upon request to Arcolectric Switches Ltd.


HARLOW MOBILE RALLY

The date of the Harlow and District Radio Society's Annual Mobile Rally will be Sunday, 25th September, 1966. Further details available from Hon. Sec., G. O'Donald, G3TLJ, "Great East", Harlow Road, Roydon, Harlow, Essex.

PETO SCOTT AMENDS NAME

Peto Scott Electrical Instruments Ltd. has changed its name to Peto Scott Ltd. It is thought that the former title gave a too restricted view of the wide range of activities now carried out by the company. The field of operation now extends through black and white and colour studio and professional television installations, professional tape recording, video tape recording, sound systems, functional music machines, Eidophor large screen television projection, language laboratories, teaching machines, schools TV equipment and overhead projectors.

SPACE ORDER FOR MARCONI

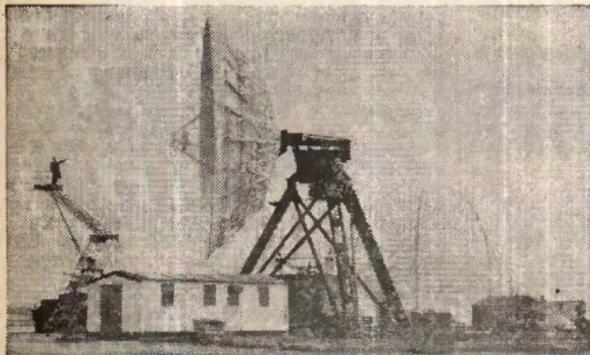

Marconi Co. Ltd., is currently building three space communications stations which are to provide the first British military satellite communications system. These stations are to take part in a joint project with the American military authorities, using a series of near-synchronous satellites launched by America.

This photograph, taken at one of the Marconi Company's experimental sites near Chelmsford, shows the 40ft. diameter dish aerial for the second station. It is seen here, fitted on a temporary mounting for test purposes. The white dome in the background is the 60ft. high inflatable radome into which the aerial will shortly be moved. The radome will provide full weather protection for the aerial, its fully steerable mounting, and for some of the associated equipment.

more News and Comment

The Meaning of Amateur

I HOPE the attitude of Mr. Davidson, G3FG (page 939, March issue) is not typical of the majority of radio enthusiasts.

I fully endorse the remarks of your Birmingham correspondent who G3FG criticises and would suggest that G3FG is being narrow-minded. It is, I think, possible to distinguish two separate hobbies (closely connected, I admit) i.e. set construction and DX (be it ham or broadcast DX). I myself could not really care who or what constructed my set as long as it gives me some DX. I know that some friends of mine will willingly construct a set and "home brew" it but once they get it working and calibrated, give no thought to the matter, take the set to pieces and start on a different circuit.

As to the meaning of "amateur" I hardly think it is relevant to either hobby. The thing that disturbs me most, from what I read of your correspondence, is the unwillingness of some—not many—to accept newcomers, novices not versed in the habit of set construction.

P. Charlton.

Middlesbrough,
Yorkshire.

Single Circuit Panels

I WAS intrigued by W. Groome's approach to the problem of assembling printed circuits without messy chemicals. (P.W. Feb., 1966). I wonder why he assumes that copper cladding has to be used?

I, as an "old timer" faced by this modern chassisless age—have found a simpler approach! I use 22 s.w.g. copper wire! What's more, on top of the board my assemblies look identical. Just as small and just as neat.

The only special tool needed is wire-bending pliers, to put neat loops on the ends of each link. The wires can run point-to-point by judicious use of bits of sleeving (though they needn't).

It's a lot easier to perform mods and de-bug new designs!


When finished, a layer of lacquer holds all in place . . . (Most times, surplus flux does all that is needed).

R. G. Young.

Peacehaven,
Sussex.

on page 1060

A Direct Reading Frequency Meter

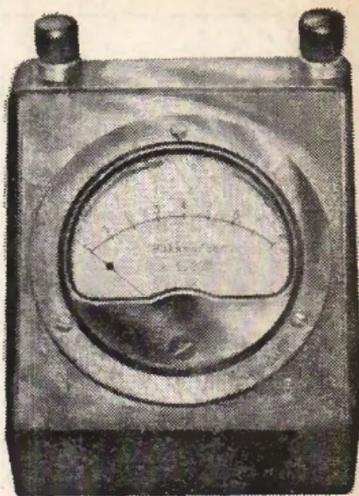

★-Described by K. Royal

THE device about to be described commenced life in the author's laboratory for the measurement of the pulse repetition frequency of an oscilloscope's timebase in terms of a direct reading analogue on a milliammeter. This simply means that the milliammeter is scaled directly in terms of frequency instead of current. The meter circuit thus has to translate frequency to a direct-current value. Moreover, to be of much use it has to do this in a linear manner without progressive compression or expansion of the scale. That is, any change in applied frequency should give a correspondingly linear change in current reading over a specific frequency range.

The device then graduated to a "tachometer" for checking the speed of car engines, and finally, to a meter for indicating the frequency of any audio signal, whether of square, pulse or sine wave.

Frequency Discriminator

The key to the whole thing is a rather special frequency discriminator* whose circuit is given in Fig. 1. This is how it works. When the input signal goes negative, capacitor C1 charges through the signal source resistance, through R1 and through D1. With D1 connected the way round shown on the diagram is, of course, in forward conduction on a negative-going signal, while the emitter junction of the transistor Tr1 is in reverse conduction.

As long as the time constant $C1/R1$ is short (also assuming a low impedance or resistance source), C1 stores an electric charge equal to CV , where C is the value of the capacitor and V is the amplitude of the input signal.

Now, when the input signal changes to positive (or zero), C1 discharges through the emitter/base junction of the transistor and a pulse of current flows in the collector circuit. This happens on each cycle of signal, and since C1 discharge current is equal to $-CV/t$, where t is a time function of the

cycle and is itself equal to $1/f$, where f is the repetition frequency, it follows that the average emitter current is CVf . The average collector current is thus $CV\alpha$, where α is the current gain.

In the common base mode, α is almost equal to unity (actually it is less than unity because the emitter current is equal to the collector current plus the very small base current) so the average collector current can be considered to be CVf . From this, then, it can be seen that the current is proportional both to frequency and the value of C1. The frequency range over which the discriminator will function is thus influenced by the value of C1. Table I relates maximum frequency to value of C1.

In Fig. 1 a milliammeter is included in the collector circuit, and this is scaled to read frequency direct. It is possible to employ a high resistance voltmeter instead of a current meter by putting a resistor in series with the collector and using the voltmeter to indicate the voltage in terms of frequency developed across it. In this case, the voltage as recorded would be equal to $CVfR$, where R is the value of the collector resistor.

Input Limiter

The basic circuit in Fig. 1 is dependent upon the signal source impedance and amplitude, and is thus somewhat unpredictable. For more consistent operation a "buffer" stage should be interposed between the signal source and the discriminator,

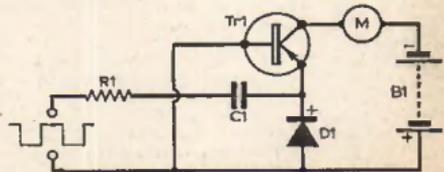


Fig. 1: Circuit of the basic frequency discriminator.

with the buffer acting also as an amplitude limiter.

A practical arrangement in this context is given in the circuit in Fig. 2. Here Tr1 is the buffer/amplitude limiter. It serves virtually as a switching transistor the input signal performing the switching action. This is how it works.

On a negative-going input signal current flows in the emitter/base junction of Tr1 causing a flow of current in the collector resistor R3 and the voltage at the collector to fall. On a positive going input signal, the base is made positive with respect to the emitter and no current flows in the collector resistor and the voltage at the collector rises almost to the supply voltage. During this half-cycle, however, D1 conducts and maintains a constant mark/space ratio. That is, the transistor is switched on and off for equal periods of time.

A square-wave is thus developed at the collector of Tr1, and since the amplitude of this wave is held constant by the transistor bottoming when the input signal swings negative and cutting off when it swings positive, amplitude limiting occurs provided the input signal amplitude is itself sufficient fully to switch the transistor as described. Thus, any increase in signal input amplitude does not influence the amplitude of the square-wave signal at the collector.

The signal, then, is of ideal form to work the frequency discriminator which, in Fig. 2, is Tr2, with C2 as the charging capacitor. A preset resistor is included in series with Tr2 collector and milliammeter to set the current for full-scale deflection at the top frequency it is required to indicate.

Unit Construction

This circuit, in fact, was used by the author both to indicate the pulse repetition frequency of the timebase of an oscilloscope and to determine the turnover speed of a car engine by "counting" the number of pulses produced by the contact breaker of the ignition system, the scale of the milliammeter then translating these direct to revs per minute.

The circuit was built upon a small piece of "Eyelet Board" measuring about $2\frac{1}{2} \times 2\frac{1}{2}$ in. The special "eyelets" (see the Component List) are secured in the holes corresponding to the component lead-out wires. The wires, along with the circuit connecting wires themselves, are then soldered to the eyelets.

A word or two about the eyelet board would not be amiss at this juncture. The board itself is made of a resin-bonded laminate and the eyelets are of tinned brass. The laminate is perforated every 0.2 in. and the holes (which are about $\frac{1}{16}$ in. in diameter) tightly accommodate the eyelets. These are prevented from being pushed right through the holes by a slightly raised flange at one end. This also gives a little clearance for winding round the circuit connecting wire.

The eyelets are fitted to the selected holes by inserting the barrel end to the flange, turning the board over and then gently tapping the protruding barrel end with the tip of a centre punch. One of the automatic press-type punches allows this operation to be handled swiftly and accurately.

Meter Connection

Fig. 3 shows how the board is processed to accommodate all of the components of the circuit. These are wired together underneath the board and connection to the meter terminals is accomplished by the positioning of eyelets close to two holes made in the board to take the terminals of the meter. Each hole thus has one meter connecting eyelet close to it, as shown in Fig. 3. Washers placed on the meter terminals after they have been pushed through the holes in the board thus provide good electrical connection between the adjacent


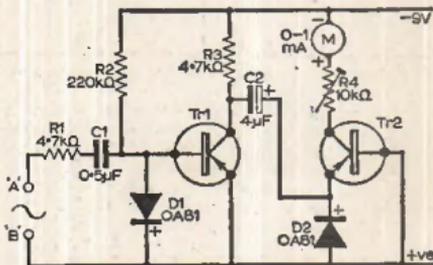


Fig. 2 (above): Circuit of the instrument described in the text.

Fig. 3 (below): Layout of components on the eyelet board.

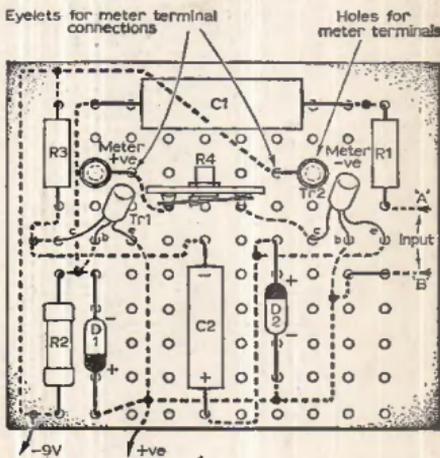

eyelets and the terminals when the terminal nuts are tightly screwed down. In this way, therefore, the module is secured to the meter movement.

The 1mA meter movement employed by the author had its own mounting case and this easily accommodated the meter-mounted module with room to spare for a small PP3 or PP4 battery if required. The author's prototype is externally powered so no on/off switch was fitted. However, a switch would be needed should internal battery powering be adopted, since the limiter takes a small quiescent current of just under 1mA.

The front view of the instrument, with the scale calibrated in pulses per second, is shown in the heading photograph. The two top terminals accept the input signal and supply positive, to which the input signal is relative while a small terminal on the rear of the case picks up supply negative.

TABLE I

Maximum Frequency	Value for C2
100 c/s	1 μ F
1 kc/s	0.1 μ F
10 kc/s	0.01 μ F
100 kc/s	0.001 μ F
1 Mc/s	0.0001 μ F

Table 1: Showing maximum frequency for variations of C2.

As mentioned earlier the instrument was made originally to indicate timebase repetition frequencies of an oscilloscope up to a maximum of 8kc/s. For this application, a value of 0.01 μ F was found suitable for C2 (see Table I). After setting the timebase to 8kc/s as determined by a calibrated audio oscillator, the preset R4 should be adjusted to give a deflection of 8 on the meter. A signal of any frequency below 8kc/s is then read directly from the scale.

As a Rev-counter

For use as a car engine rev-counter, the pulses as developed between the contact breaker (CB) and switch (SW) terminals of the ignition coil are applied to the instrument. The pulses here have a rate proportional to the engine speed. For a four-stroke engine, the frequency is equal to engine


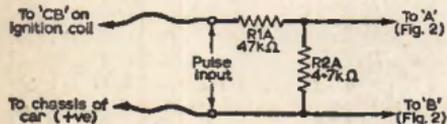



Fig. 4 (above): Circuit of input attenuator required for indicating ignition pulse rate.

Fig. 5 (below): Circuit of zener diode stabilisation.

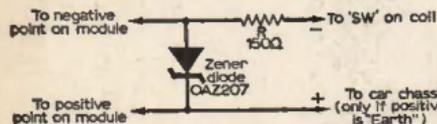

turnover speed in revs per minute $\times n/120$, where n is the number of cylinders. Thus, such an engine running at, say, 3,000 r.p.m. produces a pulse rate of 100 c/s, while a single cylinder, four-stroke motor-cycle engine will produce a pulse rate of only 25c/s at the same turnover speed.

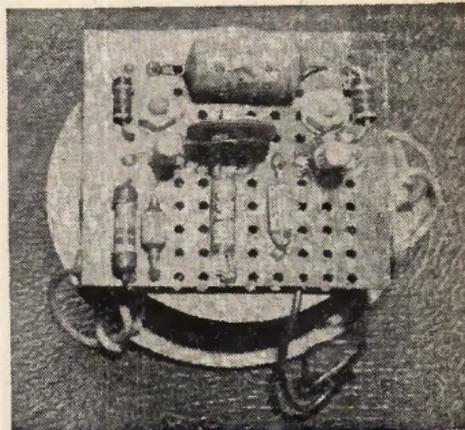A top engine speed of 6,000 or 8,000 r.p.m. is generally conventional depending really on the nature of the engine. Thus, the value for C2 is usually in the order of 1 μ F, but for single cylinder engines a value up to 4 μ F may have to be used. The value in these cases is best determined by experiment for the least ripple effect on the needle at low revs.



Rear view of finished instrument showing completed circuit board.

It is not safe to apply the contact breaker pulses direct to the circuit since their large amplitude could damage the semiconductors. An attenuator after the style of that shown in Fig. 4 circuit should be used at the input. The rev-counter may be powered either by its own, internal battery (as may be required for some motor cycles without battery powering) in which case the "pulse input" point is connected to "CB" on the ignition coil and the supply positive line of the circuit is connected to the metal of the engine or car body, or powering can be from the car battery.

In the latter case, the car supply voltage must be stabilised, as this has a tendency to rise and fall with engine revs and with varying loads on the electrical system.

The best stabilising element for this application is the zener diode. When this kind of diode is biased for reverse conduction it becomes a relatively low resistance at a specific value of reverse voltage, called the "zener voltage". The current then passed by the diode is called the "zener current". Under this condition, the voltage developed across the zener diode remains substantially constant over a range of input voltages. This means, then, that the voltage across the diode is stabilised.

A zener diode stabilising circuit is given in Fig. 5 and "R" in series with the supply and the

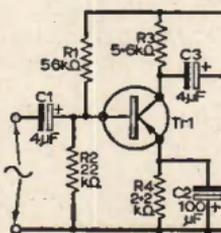


Fig. 6: Circuit of common-emitter amplifier for increasing the sensitivity of the instrument, as described in the text.

COMPONENTS LIST**CIRCUIT FIG. 2**Resistors (all $\frac{1}{2}$ -watt carbon insulated)

- R1 4.7k Ω
 R2 220k Ω
 R3 4.7k Ω
 R4 10k Ω preset (printed-circuit board type)

Capacitors

- C1 0.5 μ F 12v
 C2 (see Table 1)

Semiconductors

- Tr1 and Tr2, OC71
 D1 and D2, OA81

Meter Movement

Moving-coil 0-1 mA

Sundries

Eyelet Board and eyelets (available from Messrs. R. & E. Lamb, 17 Queens Road, Leytonstone, London E.11. Connecting wire, battery (PP4) and battery clips. Instrument case.

CIRCUIT FIG. 5**Resistor**150 Ω 1-watt**Semiconductor**

Zener diode, OAZ207

CIRCUIT FIG. 6Resistors (all $\frac{1}{2}$ -watt carbon, insulated)

- R1 56k Ω
 R2 22k Ω
 R3 5.6k Ω
 R4 2.2k Ω

Capacitors

- C1 and C3 4 μ F, 12v. Electrolytic
 C2 100 μ F, 6V. Electrolytic

Semiconductor

Tr1, OC71


diode sets the zener current. The value is determined by the required load current, the supply voltage and the type of zener diode used. The manner of connecting to the car is revealed in Figs. 4 and 5. This applies only to cars with 12V supplies and positive earths.

The main application of the device, of course, is as a direct reading frequency meter, and the way that it can be used to indicate engine revs may be of academic interest only to some of our readers. Nevertheless, the versatility of the device is revealed.

To provide a frequency indication from low-level signals, an amplifier is required in front of the main circuit of Fig. 2. A suitable amplifier is given in Fig. 6. This is just an ordinary common-emitter circuit, but the lift that it gives to signals is sufficient to allow the device to respond to signals as low as 50-100 mV. When this amplifier is used, R1 and C1 from Fig. 2 circuit should be omitted. ■

* D. E. O'N. Waddington, "A Simple Frequency/Voltage Converter" Marconi Instrumentation, Vol. 10 No. 1.

JUST OUT!

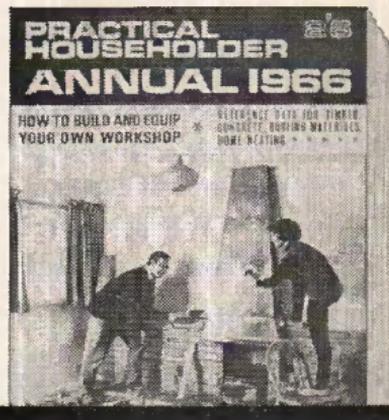


NEW PROJECTS, NEW IDEAS, NEW WAYS TO IMPROVE YOUR HOME

Go for the 1966 PRACTICAL HOUSEHOLDER ANNUAL today. It brings you dozens of ways in which you can give your home an up-to-the-minute new look . . . with detailed instructions and how-to-do-it illustrations that show you how to tackle each job with a sure professional touch. Don't miss it.

SPECIAL SECTIONS ON:**HOME WORKSHOP****SOLVING THE GARAGE PROBLEM****KITCHEN FURNITURE YOU CAN BUILD****GUIDE TO HOME HEATING****GATES AND FENCES FOR HOME AND GARDEN****BUILDING A GLAZED SUNLOUNGE****REFERENCE DATA FOR ROOFING MATERIALS AND CONCRETE****BUILDING AND WOODWORKING****SIMPLIFIED ELECTRIC WIRING****BIG DEMAND - GET YOURS NOW!**

2/6 NEWSAGENTS AND BOOKSTALLS

A
TUNED
SWITCH-
SECTIONS

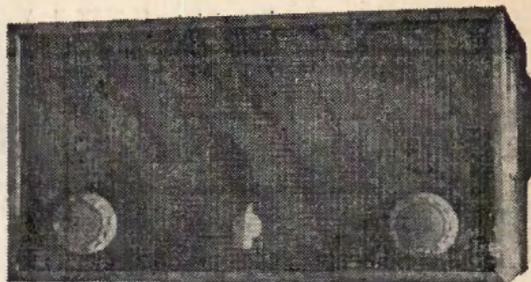

SUPERHET

F. L. THURSTON

PART 2

STAGE 3—AERIAL AND PRE-SELECTOR SECTIONS

A 10 x $\frac{1}{4}$ in. ferrite rod is used in the aerial, which is home wound. While this is recommended, it is not essential, and a ready-made type of aerial may be used if preferred. The winding and mounting details for the home-made type are shown in Fig. 5. Note that the aerial is mounted directly on the speaker.

Secure the external aerial/a.g.c. socket in place at the rear of the chassis, checking that there are no shorts to chassis. Secure L3 in place above chassis.

Secure S2 in place.* It will probably be necessary to make this switch up by modifying an alternative type, and the essential dimensions are given in Fig. 6. Such a conversion is not difficult: a multibank switch, at least as long as that shown, is obtained. The switch must have at least 4-ways. The switch is then dismantled, reduced to the correct length, and re-assembled to conform to Fig. 6. If too many "ways" are available, they can be reduced to the correct number (4) by drilling and tapping a 6BA hole in the switch front to take a short 6BA screw which will act as a stop.

When the switch has been secured in place at the front of the chassis, secure the trimmer capacitors in place, as shown in Fig. 6. The method of mounting the beehive trimmers is shown in Fig. 7, where it can be seen that they are soldered to the drilled-out ends of 2 BA screws, which are then bolted directly to the chassis, using a solder tag in place of a normal washer.

Now wire-up the circuit as shown in Fig. 6. Use screened leads where indicated. Check the wiring and switch on. Test voltages are V1, anode 250V, screen 145V, cathode 1.5V.

*S2 can be made to order by: Specialist Switches Ltd., 79a Duke Road, London, W.4. Price approximately 17/6. Drawings must be supplied with order.

TESTING

Temporarily connect a germanium diode in circuit with one end to the loose end of C10 (audio input) and the other end to the grid of V1. Switch S2 to position 3. The ferrite aerial and diode are now connected as a simple crystal set. If the volume control is turned full up, the Light programme should be heard reasonably well. By adjusting C23 it should be possible to tune the programme in quite sharply, although the Home will probably be heard as well.

Now disconnect the diode from V1 grid and connect it to tag 2 of the 16-way tag strip. The circuit is now connected as a t.r.f. receiver. When S2 is switched to position 3 it will be seen that, by adjusting C23 and C26 together, the Light can be tuned in far more sharply than before, that interference from the Home is greatly reduced, and that the Light now comes in with vastly improved strength. By connecting an external aerial (a few yards of wire into the external aerial socket, the signal strength is increased even more.

The trimmer capacitors should now be aligned, in conjunction with positions of S2, as follows:

- Position 1—(Radio Caroline). Tune C21 and Slug of L3.
- " 2—(Luxembourg). Tune C24.
- " 3—(Light). Tune C23 and C26.
- " 4—(Home). Tune C22 and C27. Fixed padder.

Note that the above tuning sequence must be followed. The stations on positions 1 and 2 may be very weak.

This concludes stage 3.

STAGE 4—OSCILLATOR AND MIXER SECTIONS

Secure L4, the oscillator coil in place below the chassis. This coil is sold as a short-wave oscillator coil, to cover the 90 to 250 metre bands. At the particular frequencies used in this receiver, this coil gives a better L/C ratio, and therefore better frequency stability, than would a normal medium-wave oscillator coil.

with no leads soldered to it). Adjust the lower tuning slug of i.f.t.1 for maximum signal (any position of S2 may be used). Now re-trim upper tuning slug, and finally re-trim lower slug again. The primary of i.f.t.1 is now fully aligned, while the secondary may be considered to be temporarily aligned (it will require re-trimming after the two additional i.f. stages are added in stage 5 of the construction).

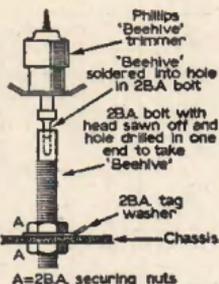


Fig. 7: Method of mounting the beehive trimmers.

EXPERIMENTS WITH THE MIXER/OSCILLATOR SECTION

As constructed, the circuit used for the mixer gives very low noise, while the oscillator is exceptionally drift free and immune from "pulling". By making temporary alterations to the circuits, it is possible to demonstrate quite forcibly the inferiority of some alternative circuits. Space is limited, however, and only two experiments will be given, as follows:

If a small transistor radio with built-in aerial is available, place it near to the oscillator coil (L4) and tune through the medium waveband; a number of whistles will be picked up, demonstrating that the oscillator is working. Tune in to one of these whistles, and then move the transistor set to the r.f. coil, L3; the whistle will still be there, but will be very weak. Finally, move the transistor set to the ferrite aerial; if any whistles are still available they will be very weak indeed.

Now unsolder the 1000pF capacitor, C18, from pin 2 of V2 (mixer cathode) shown as a temporary connection in Fig. 8. Solder a 15pF capacitor between pin 1 of V3 oscillator anode) and pin 1 of V2 (mixer grid). The circuit is now connected as a mixer with the oscillator injected to the grid, quite a common circuit.

If the transistor set is now placed near the r.f. coil, L3, whistles will be heard far more strongly than was formerly the case. Whistles will also be heard at the ferrite aerial. It may be noted that if a superhet is made without a pre-selector stage, using oscillator injection to the mixer grid as is often done the resulting "receiver" will in fact act as a quite effective transmitter!

Another point may be demonstrated with this circuit, by pressing a finger against the

mixer grid pin; a quite considerable reduction in volume will be noticed. This loss of volume can be attributed to loading and de-tuning of oscillator and r.f. stages. If the circuit is now re-wired to conform to Fig. 8 (the "temporary" connections can now be made "permanent") and the same finger test is made to the point of injection (mixer cathode), it will now be found that no reduction in volume takes place. This is because both the oscillator and r.f. stages are isolated from the point of injection, and also because no loading of the actual injection voltage takes place due to the low impedance used.

The mixer gives very low noise and good gain, and an essential part of the design which makes it possible to obtain these results is the voltage divider and decoupling network, R3-R4-C3, which feeds a constant and predetermined voltage to the mixer screen grid; the screen grid voltage must be within 5V of that shown in Fig. 1. An effective way of demonstrating the importance of this voltage is to replace R3 with a variable resistor of about 100 to 250kΩ value, and adjusting the value while monitoring the screen grid voltage; it will be found that as the voltage departs from that specified, the noise increases and the gain decreases. Many conventional mixers are found to have the high noise and low gain that is associated with this test. Once the circuit has been re-wired to conform to Fig. 8, stage 4 of the construction is complete.

STAGE 5—I.F. SECTIONS

Wire up the circuit as shown in Fig. 9. Check wiring. Switch on and check voltages as shown in Fig. 1.

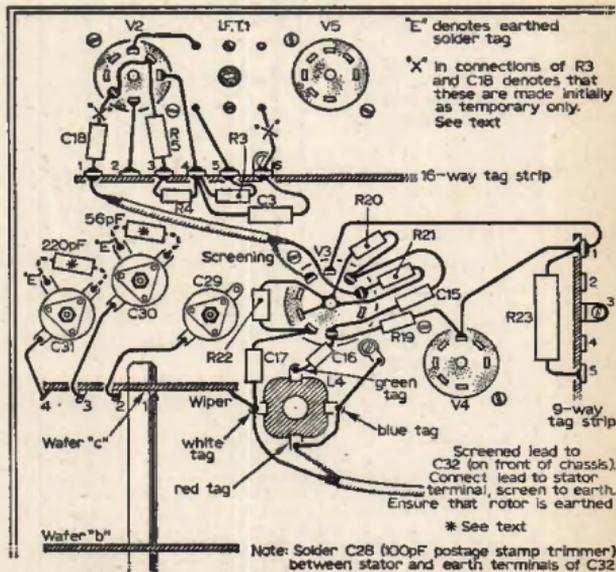


Fig. 8: Wiring and layout for stage 4 of construction.

NOTE. Points marked X in Fig. 9 are temporary connections only.

ALIGNMENT. Disconnect the capacitor used in aligning stage 4 from the secondary of i.f.t.1, and reconnect to the primary of i.f.t.2 (connected to pin 5 of V5). Adjust the primary tuning slug for maximum signal, then re-trim secondary of i.f.t.1 again, and finally re-tune i.f.t.2 primary again. Alignment of i.f.t.1 is now complete.

Move the capacitor to the secondary of i.f.t.2, and repeat the above procedure with the primary and secondary tuning slugs of i.f.t.2. When alignment is satisfactory, move the capacitor to the primary of i.f.t.3, and align the secondary slug of i.f.t.2 and the primary slug of i.f.t.3. To complete the tuning, move the capacitor to the secondary of i.f.t.3 and trim the primary and secondary windings of that i.f.t.

Note that, because of the use of three i.f. stages, the tuning is so sharp that it will probably be necessary to de-tune the i.f.'s slightly if acceptable quality audio is to be received.

Stage 5 of the construction is now complete.

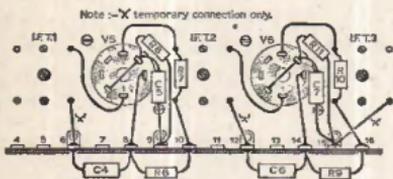


Fig. 9: Wiring and layout for stage 5 of construction

STAGE 6—DETECTOR AND A.G.C.

The permanent detector and filter network can now be connected into the circuit.

Remove the temporary detector circuit used in the two preceding stages (the capacitor and diode). Wire up the circuit as shown in Fig. 10.

The dimensions of the component board shown are approximate only; as an alternative to the board, the components may be soldered to suitable

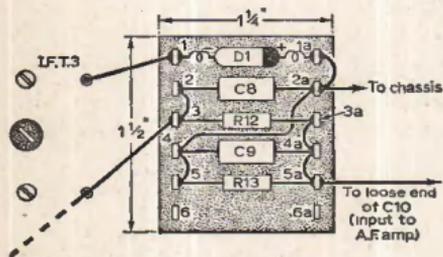


Fig. 10: Wiring and layout of detector/filter.

miniature tag strips. When completed, the circuit is switched on to test that it is working correctly.

If working satisfactorily, wire up the a.g.c. circuit as shown in Fig. 11. Note that the "tem-

porary" connections of Fig. 9 are removed and re-wired as "permanent ones as in Fig. 11. After checking over the wiring, switch on and select a station. The a.g.c. circuit may result in some small loss in volume compared to that obtained earlier; the stations should now, however, be virtually free from "fade".

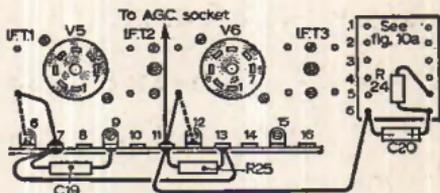


Fig. 11: A.G.C. wiring.

If a voltmeter is available it can be connected to the a.g.c. socket provided at the rear of the chassis. The a.g.c. voltage is negative, and rises in magnitude with the strength of the i.f. signal. Thus, as a signal fades, so the a.g.c. voltage will fall. The voltage will vary between about zero and 5V (measured with a v.t.v.m.), the normal amplitude being about 4V.

The tuning of the r.f. oscillator, and i.f. stages can be perfected if required, by using the a.g.c. point as a tuning monitor.

The construction of the receiver is now complete.

THE CABINET

The prototype receiver was placed in a simple, close fitting cabinet, which was suspended below a cupboard in the kitchen, as shown in the photograph. This cabinet may be a trifle small for really good, cool running of the radio, and the reader may prefer to make a similar cabinet but of larger dimensions. Quarter-inch or heavier ply-wood is used in the construction. The sides and top and base are cut to the required size and nailed and glued together. A fairly rough form of construction can be used, as any mistakes are "camouflaged" when the unit is finally covered with rexine.

Before proceeding further with this "box" section of the cabinet, make up the front panel and check that it fits correctly to the radio. When making the front panel, allow for the thickness of the speaker gauze that will be used to cover it, and the thickness of the Rexine used to cover the "box", when working out the overall dimensions. When the front panel is correctly cut, cover its front and sides with the selected speaker gauze, gluing it in place with "Copydex" adhesive.

Now place the Rexine selected to cover the "box" in position, and after trimming, glue (using Copydex) the Rexine to the front edge and inside only. When the glue has set (about 10 minutes) push the completed front panel in place in the box, peel back the Rexine layed on the box, and secure the front panel in place with a few light nails, hammered in from the outside of the box.

Finally, complete the cabinet by gluing the remaining Rexine in place. ■

on the Short Waves

MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

The Broadcast Bands—by John Guttridge

CONTRIBUTIONS have been lighter than usual this month. Don't forget we want your news. Thanks go to J. McNally, S. Haagensen, S.B.C., A. J. Jenkins, Middlesbrough Boys High School S.W. Club, I. Black and P. A. Church.

Algeria: *Radio Algerie* (21 Boulevard des Martyrs, Algiers) now has English from 2200—2230 on 6,175/890. Same outlets are used for Spanish 2230—2300 and French 0630—0830 and 1700—2200. French is also carried from 1200—1700 (0900—1700 Sundays) or 890/11,835. Report forms are now available from this station which now gives full QSL verification.

Congo: *Radiodiffusion de la Republique Democratique du Congo*, (B.P.3171, Leopoldville) has been heard in French at 1900 on the new frequency of 9,780. Local dialect follows at 1927.

South Africa: *South African Broadcasting Corporation* (P.O. Box 8606, Johannesburg) now carries the Africa service at 0300—0400 on 6,150/7,270, 1000—1600, 15,220/17,805; 1600—1710, 4,975/15,220/17,805, 1710—1845, 4,975/11,900, 15,220; 1845—2000, 4,975/9,525/11,900; 2000—2100, 4,975/7,270/9,525; 2100—2115 7,270/9,525. On Sundays transmissions start at 1100 and 17,805 changes to 11,900 at 1650. One of the stations new 250kW outlets is used on 4,975. At 2000 11,900 carries the programme *Radio Paradys*.

Tunisia: *Radiodiffusion Television Tunisienne* (139 Avenue de Paris, Tunis) is now carrying the home service on the new frequency of 6,305.

Burma: *Burma Broadcasting Service* (Promo Road, Kamayut P.O., Rangoon) can be heard from around 1300 to sign off at 1345 on 4,795.

Japan: *N.H.K.* (Tokyo) can be heard with English around 1300 on 9,525, though there is interference from *Voice of America*, Greenville, in Spanish to Latin America on the same frequency.

Lebanon: *Lebanese Broadcasting Station* (Radio Lebanon, Ministry of Orientation, Information and Tourism, Beirut) has been reported back on 11,770 to Africa from 1830—2030 (English 1830—1900). Reception in England is good.

Papua and New Guinea: *Radio Rabaul* (P.O. Box 71, Rabaul, New Britain) uses 3,385 from 0600—1300. Sends acknowledgement folder. *Radio Kerema* (Gulf District, Papua) on 3,245 from 0720—1100. *Radio Daru* (Western District, Papua) on 3,304 from 0800—1100. *Radio Goroka* (Eastern Highlands, New Guinea) on 2,410 from 0800—1100.

U.S.A. *Voice of America* (US Information Agency, 330 Independence Avenue, S.W. Washington 25, DC) will use the following frequencies to Europe in English from March 6, 3,980 (Munich) 0300—0730, 1400—2345; 5,965 0300—0730, 1630—2200, 5,995 (Greenville) 0300—0730; 6,040 0500—0700; 7,200/7,250 0330—0730; 7,205 1500—1900; 7,210 1900—

2245; 9,540/9,740/15,295 0430—0730; 9,565 1830—2245; 9,760 1700—2245; 11,760 1830—2215; 15,205 (Greenville) 1400—2215; 15,290 1400—2000; 17,780 (Greenville) 1400—1800; 1,196 (Munich) 1600—1830.

Netherlands Antilles *Trans World Radio* (Bonaire) has English at 2100 in the 25m.b. Frequency is believed to be 11,840.

Argentina *Radiodifusora Argentina al Exterior* (RAE), (Sarmiento 151, Buenos Aires) now carries English from 2300—2345 and not 2400 on 11,710. The programme has also been occasionally heard on 11,780 and 9,690. After close down of the International service at 0030, 11,710 is reported to carry the National Service.

Brazil: The following stations are available in the early evening: *Radio Mayrink Veiga* (Rua Mayrink Veija 15, Rio de Janeiro) on 11,770; *Radio Sociedad de Bahia* (Rua Carlos Gomes 57, Sa Ivador, Bahia) on 11,875; *Radio Tupi* (Avenije Venezuela 43, Rio de Janeiro) on the new frequencies of 11,705/9,800; *Radio Bandeirantes* (C.P.372, Sao Paulo) on 11,925; *Radio Brasil Central* (C.P.330, Goiania) on 11,815.

Denmark: *Radio Denmark*, (Radio House, Copenhagen V) may reintroduce the programme "Short-waving to the World" on Saturdays at 1015—1100 on 9,520. On March 6, 15,165 replaces 9,520 for the 1730—1810 transmission.

German Federal Republic, *Deutsche Welle* (Bruedesstrasse 1, Postfach 344, 5 Köln) now uses 9,575/7,175 for the 0300—0340 English transmission.

German Democratic Republic, *Radio Berlin International* (Berlin-Oberschonweide, Nalepastrasse 18-50) uses the additional frequency of 5,300 in their English European transmission at 1730. Other frequencies are 6,080/6,115/7,185/7,300/9,730. There is a new transmission at 1815 on 1,511.

Great Britain, *Manx Radio* (P.O. Box 22, Douglas, Isle of Man) is understood now to have a power of 2kW. After dark uses 1,594.

Hungary: *Radio Budapest* (Brody Sandar—S.U. 5-7 Budapest VIII) has English to Europe on 5,900/7,220/7,305 from 1930—2000 and 2200—2230. The 2200 transmission is also carried on 6,234. English to North America is at 0030—0100, 0130—0230 on 9,833/9,540/7,220/6,234 and 0300—0400, 0430—0500 on 9,833/7,220/6,234/5,900.

Portugal: *Radio Lisbon*, (Rua Sao Marcal, 1-A, Lisbon) reported using 7,285/7,130/6,185/6,025/5,975 for English to Europe at 2015—2100.

Egypt: *Cairo Radio* (UAR Broadcasting and TV, Maspero, Cairo) now carries English to Europe at 2100—2215. Frequencies are 9,475/11,915.

Saudi Arabia: *Saudi Arabia Broadcasting* (Ministry of Information, Airport Road, Jeddah) puts in a strong signal after 2200 on 7,220 but suffers from Budapest on same frequency and a jammer on 7,215.

Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

BACKED BY OUR SUPER AFTER SALES SERVICE

FIRST FOR QUALITY, PERFORMANCE & PRICE!


NEW ROAMER SEVEN Mk IV

Amazing performance and specification. ★ **7 WAVEBAND PORTABLE OR CAR RADIO FULLY TUNABLE ON ALL WAVEBANDS** ● 9 stages—7 transistors and 2 diodes Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 35 metres. Push-pull output for room filling volume from rich toned 7" x 4" speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S waves. Real leather look case with gilt trim and shoulder and hand straps. Size 8 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP7 batteries available anywhere).
★ **EXTRA BAND FOR EASIER TUNING** Total cost of parts now only **£5.19.6** P. & P. 5/6
★ **PIRATE STATIONS etc** Parts Price List and easy build plans 3/- (FREE with kit)

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans available separately at prices stated. Overseas post 10/-.



MELODY SIX

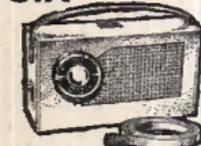


Wonderful reception of B.B.C. Home and Light, 203 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 4 1/2 x 1 1/2 in. approx. with gilt speaker grille and supplied with hand and shoulder straps.
Parts Price List and easy build plans 2/- (FREE with kit)

POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2 in. moving coil speaker, built into attractive black case with red speaker grille. Size 6 1/2 x 4 1/2 x 3/4 in. (Uses 1225 batteries available anywhere).
Parts Price List and easy build plans 1/6 (FREE with kit)
Total cost of all parts now only **42/6** P. & P. 3/-.

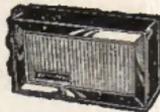

NEW ROAMER SIX

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS ● 6 WAVEBAND !!



★ **EXTRA BAND FOR EASIER TUNING OF LUX, ETC.** Parts Price List and easy build plans 2/- (FREE with kit)
Total cost of all parts now only **£3.19.6** P. & P. 3/6

● 8 stages—6 transistors and 2 diodes
Listen to stations half a world away with this 6 waveband portable. Tuneable on Medium and Long waves. Trawler band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors. 8-inch speaker, handsome case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2 in. Carrying strap 1/6 extra.



NEW TRANSONA FIVE

"Home, Light, A.F.N., Lux. all at good volume." G.F. Durham.

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2 1/2 in. speaker etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in. Parts Price List and easy build plans 2/- (FREE with kit)

with red speaker grille. (Uses 1225 battery available anywhere).
Total cost of all parts now only **42/6** P. & P. 3/6

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 8 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere.) Carrying strap 1/6 extra.

Total cost of all parts now only **59/6** P. & P. 3/6.

Parts Price List and easy build plans 1/6 (FREE with kit)



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2R.F. Stages, push-pull output. 3in. speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses PP7 battery, available anywhere).

Total cost of all parts now only **£3.19.6** P. & P. 3/6

Parts Price List and easy build plans 2/- (FREE with kit)

RADIO EXCHANGE CO

61, HIGH STREET, BEDFORD

Telephone: Bedford 52367

Callers side entrance Barratts Shoe Shop open 9-5 p.m. Sat. 10-12.30 p.m.

THE AUDIO FIDELITY STEREO-33

A High Fidelity All Transistor Stereo Amplifier providing 10 watts R.M.S. on each channel

OUTPUT (per channel)

10 watts R.M.S. into 16 ohm load.
12 watts R.M.S. into 3.75 ohm load.

TOTAL HARMONIC DISTORTION

0.1% at 6 watts R.M.S. into 16 ohm load.
0.8% at 10 watts R.M.S. into 15 ohm load.
1.000 c.p.s. load

DAMPING FACTOR 20

FREQUENCY RESPONSE

+11 dB 20-20,000 c.p.s.

HUM AND NOISE -80dB

CROSS TALK -40dB to -50dB

MAINS INPUT SELECTION

100-110-120-200-210-220-240v.

20/60 c.p.s.

SEMI-CONDUCTORS

(per channel)

AC117, OC44B, OC81Z(2), OA5,

OC12Z, AD168 (2)

BASS CONTROLS

+11 dB to -16 dB at 40 c.p.s.

TREBLE CONTROLS

+15 dB to -15 dB at 10 Kc/s.

EQUALISATION

Gram. to std. R.I.A.A. characteristic.

Tape head to std. C.C.I.R. characteristic.


SIZE 12 1/2" x 4" x 3 1/2"

WEIGHT 12lb.

FILTER (Steep Cut)

7 Kc/s, 11 Kc/s, 15 Kc/s.

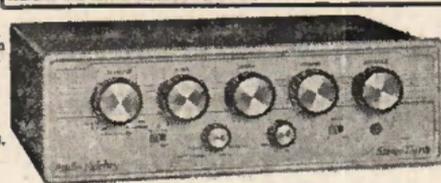Incorporation of the very latest Mullard Transistors has made possible the really outstanding performance figures of this brilliant design. Compare them with other leading makes currently available.
NOTE: Base output is 10 watts R.M.S. (continuous) which should not be confused with I.B.F.M. momentary values.



RETAIL PRICE **39** GNS

THE PRE-AMPLIFIER IS A COMPLETELY NEW DESIGN

IT ELIMINATES THE NECESSITY OF MATCHED INPUTS & COMPLICATED SWITCHING ARRANGEMENTS. IT ALSO PRODUCES CONDITIONS OF MINIMUM NOISE AT HIGHEST SENSITIVITIES.

Please send SAE for leaflet

INPUT SENSITIVITIES

(for 10 watts R.M.S. into 16 ohms)

Pick-up Magnetic

2.5 m.v. 33 1/2 r.p.m.

7 m.v. 78 r.p.m.

Pick-up Crystal/Ceramic 400

m.v.

Microphone 5 m.v.

Tape Head 2 m.v. Aux. (Radio

Tuner, Tape Rec. Ceramic P.U.

etc.) 100 m.v. (Above sensitivities will be doubled when output load is 3-4 ohms.)

INPUT SELECTOR

33 1/2 r.p.m. 78 r.p.m. Aux.

Mic. Tape Head.

INPUT SOCKETS

Magnetic P.U., Crystal/Ceramic

Pick-up Aux. Tape Head

Microphone.

Built to the highest standards employing latest materials and techniques

DESIGNED FOR EASE OF FITTING IN CABINET OR FOR FREE-STANDING USE.

Tested for satisfactory operation in temperatures of up to 50°C. (120°F.)

EXPORT ENQUIRIES INVITED

Designed and developed by the Audio Fidelity Group of Companies.

Manufactured and Distributed by **LINEAR PRODUCTS LTD. ELECTRON WORKS, ARMLEY, LEEDS.**

UNDOUBTEDLY THE FINEST RANGE OF TAPE RECORDER EQUIPMENT ON THE MARKET TODAY

COMPLETE HI-FI TAPE RECORDING SYSTEM FROM 12 VOLTS D.C.

TAPE PRE-AMP SSTR/7

All silicon transistor. Zero hum. High gain and equalised at 70° per sec. to give flat response output. Simple mod. described in accompanying instructions allows equalisation at all speeds. Suitable for all medium impedance heads, Collaro, B.S.R., etc.

29/6

ASSEMBLED

MINICLASSIC PRE-AMP SSPA/49

Tone controlled high gain preamplifier designed specially for application with the SS3/10. All silicon transistor. Zero hum. requires 12 volt + H.T. High Fidelity complete with tone and volume controls. Separate inputs for crystal and radio. ceramic cartridge and radio.

39/-

MINICLASSIC SS3/10

High fidelity 4 watt main amplifier. Ideal for use with SSTR/7 and makes complete tape amplifier. 16 ohm to 30 Kc/s. Requires 12 volt + H.T. and will operate directly from crystal pickup.

8 transistors and two diodes all mounted on precision printed circuit board. Max. music power 4 watts into 8 ohm speaker

69/-



TAPE OSCILLATOR S8013

Complete unit incorporating push pull transistor oscillator giving adequate erase power and recording bias. Ferrite pot core push-pull oscillator, frequency 50-50 Kc. All silicon transistor. Provides high voltage (75 v.) D.C. Rail for operating record amplifier. High efficiency unit requiring 12 v. D.C. at 250 mA. The only unit on the market at such an economical price.

69/-

COMPLETE.

RECORD AMPLIFIER S8H/3

Fully transistorised. High voltage H.T. rail derived from oscillator. Provides substantially constant current record signal. 1 volt input sensitivity. Power consumption 1 mA at 12 volts and 1 mA at 75 volts. Later derived from erase oscillator S8013.

45/-

ASSEMBLED

KEDOCO ELECTRONICS also manufacture and supply ★ Resistors and capacitors ★ TV/FM Booster Bands 1 and 2, 32/1. ★ Miniature Transmitter S87, 159/6. ★ 30 watt 1 amp Power Supply, 69/8. ★ A range of Silicon planar epitaxial transistors. ★ Zener Diodes.

See Practical Electronics for further details or write to use for descriptive leaflets

REMEMBER IF IT'S KEDOCO IT'S O.K.

ORDER FROM: To KEDOCO ELECTRONICS, BEVERSTONE WORKS, TETBURY, GLOS

Please supply

Address

Enclose Cheque/P.O. for Postage 2/6 extra for all orders under £1.

The Amateur Bands—by David Gibson G3JDG

WANTED! James Bond type agents to sniff out the truth. Out of a large mail bag this month most letters were about 20 DX? No, nor about the VK on topband, or the openings on 20 either. They referred to "that man" NS1A but with a new twist. Apparently we now have a NS1B and NS1C too. No, they do not count as separate zones for a countries worked certificate. Briefly the locations of these stations are assured as follows:—On board Radio London; 10 miles south of Herne Bay; in a motor boat with a No. 19 transceiver; on an Irish river (up the proverbial creek perchance). Will the real NS1s please stand up.

I am taken to task about 80 being deserted by George, ZL3QX, who informs that both ZL4IE and ZL3FZ have been consistently working EUs for some months. Two calls for 80 metre sleuths to be on the watch for. The l.f. bands are producing some very good openings at the time of writing. Both phone and c.w. are well represented—go on, live dangerously, listen now on 160, 80, and 40.

Forty and Down

Some very fine logs for 160 shows what's about. **D. Douglas** (Dundee), HRO, 60ft. 1-wire, sends in what might be confused for twenty, but don't be fooled, it is 160, G, GI, GM, GW, GD, DL1FF, DL4SS, EP21W, HK4EB, JA6AK, KV4CI, OE6HS, YV0AA, ZB2A, 9M6BM, R. Iball (Workop), SX28, PR30 pre-selector, 160 raised IS1F, K2DGT, VE2ITU, VE3-AGX, BWY, QU, VO1HN, W1-BB/1, HGT, W2GGL, W8ANO, W9YYG, W0VXO. **Steve Wilson** (Ossett), BC348R, 264ft. 1-wire, 160—DJ2GL, DL7FZ, GI, GM, GW, GD, HB9-CM, TT, IS1FR, OK1-AEF, AKO, OLS-ADO, AFF, OE1FLW/1, OE6HS, PA0DC, PA0PN, VE3BWW, VO1-FB, HN, W1-BB/1, JJU, W8HGW, W0VXO, ZB2AM, 9H1AE. On 40 Steve's best were AP2LK (Pakistan), CN8AW, HK7BCX, VP6BX. On 80 things are lively too, **J. Brown** (Llandaff), 19 Set, dipole, raised the following on phone, CN8AW, CT1-SQ, EE, IT1-AUL, ZGY, MP4BAA (c.w.), many VE's, VP-5GC, 7NP, 9AV, W's including W8-BON, WNL, YN4CU, ZB2AJ, 4X4BO, 7X2AH, 9J2MX. Again, on 40, **Steve Wilson** logged CM2WS, CO1PY, CR7CI (Mozambique), CX2CO (Uruguay), EP2BQ, FG7ND, HK-3AST, 3UZJ, 4ADD, 4ALE, HV1CN (Vatican), JA1OHV, K2-GL, KBT, PCB, K4JC, K0LZU, KG4AN, KP4BBN, LU6FA, PY-1, 2, 3, 5, 6, 7, 8, VP5AR (Turks and Caicos Is.), VP9FT, VP7NW, W3-MGK, CRQ, W4LUV, WB6JJC/M, YV4CJY, ZC4GB, 4X4FA, 5A3TX, 6Y5XG, 9G1FQ, all c.w. **N. Flatman** (Ipswich) R3629, 68ft 1-wire, 80 metres bore first with CN8AW, HP9ABX, K8YWC, UA-1, 3, OX4BK, VE1UW, W-1KVV, 2CPO, 2ZPO, 3HUM, 4WK, 9CJZ, ZB2-AJ, AM, ZL2BE (830 hrs), while on 40 the same set up raised DJ, DL, DM, F, GD, LA, LZ, OZ, T4ZUF (?). From further out—JA2BAY, KG4NV, VK1ATU.

Twenty and Up

More a daytime band but still a hive of activity both phone and c.w. as the following SWL's report. **I. Black** (Gillingham), HE3O, W6BCX Multee antenna, FR7ZC, H11JMF, KZ5LC, MP4BCC, OA4KY, OD5-BV, BZ, EN, PZ1BW, UI8AE, VK-2SG, 3LG, 3VJ, 3ALB, 3ATO, 5RT, 6RU, VP2AA (Antigua), V5FRB, VP6KL, XE3MF, ZB2AJ, ZL2-UW, BG, 4X4AS, 5A1TZ, 7Q7PBD, 7X2MD, 9G1TF, 9J2AB, 9M4TX. **C. Clayton** (Fife), 840c, 60ft. 1-wire, KV4CI, KR6MM (Okinawa), CN8MH, CO2CO, CR6JA, CR7IZ, EA9AQ, LU6FA, OX3LP, UA9KDK, U18ID, UM8KAK, VK3-YS, AXK, VK6WT (Perth), VQ8BJ, W6-EBG, LVF, VS9ARU, ZD7IM, ZD9BE, ZS5UP, ZS6J. From Chepstow one "Colin" complete with 888 and 132ft. 1-wire heard CR7-BV, CZ, KP4NN, KV4CX SV1CX, UA6LP, VK6DR, VS9AWL, ZB4BCA, ZC4LK, ZE6JL, ZS6XP, 4X4IK, 9G1FL, **D. Wraige** (Wirral), AR88-LF and 15-20ft. indoor ant. managed to hear VK3VS, W6AM and W6UED on s.s.b., while **Chris Peel** (Stoke-on-Trent), S750, 90ft. 1-wire around the loft, went fishing for DX. Cream of the catch include CN8FH, CP8AU, CR6AJ, CX4AW, ET3USA, FK8PH, HK7KD, JA2NA, KG6API, KR6CH, KL7BIC, KZ5AW, LU7FAG, OA4KY, PY1FK, PY5AM, TF2WHI, UA9KFS, VE7MS, VE1AED/SU, VK-2ADA, GW, 3ADR, UK, 4SD, 5SM, VP1CY, VP5RB, VU2CK (India), VQ8BFA, W1, 2, 3, 4, 5, 8, 9, Ø, W6-ILT, ABC, AYM, IPA, W7-SEG, QBA, MKI, XW8AX, YA1AW, YA3LCC, YN4CM, YV4IM, ZC4MO, ZL-2UW, 3NO, 4BY, ZS6ALM, 5ASTA, 9Q1FS. While on 15 metres Chris logged CR4BC, CX1WG, EA7GK, ET3USA, HK4XP, JA6QT, H18XM, OA4KY, OX3JV, PY2DXI, VS9AWR, W's, XW8NZ, 4X4UG, 5A4TI, 5A5PJ, 5N2FEL, 5Z4AA, 7Q7BN, 9E1VF, 9G1RM, 9H1R, 9K2AD, 9U51B, 9Q5QR. **F. Simpson** (Hull), RX80, 1-wire, exact length unspecified, reeled in CR7BL, CN8FT, EA8DV, EP3RO, KP4CNC, KW6EJ, KV4CX, MP4TBO, OA8V, VE2AFJ, VK-2NN, 3JA, 4RO, 9PL, VS9AWR, XW8AZ, ZE1AN, ZS1CZ, 4X4SC, 7Q7BN, 9H1S, all on 15 metres. On 20 the same length of wire heard DU1AA, FK8AC, JA1MJ, KA5RC, KR6LU, KW6EJ, KX6DR, PY2BYU, PZ1BW, VK3UQ, VP2AA, VS6AJ, YA1AW, ZL3AB, 9G1LS, 9L1HX. Reports on 28Mc/s are still coming in. **C. Clarke** (Farnham), 12 valve s/het, dipole, G's by the score plus UP2ADZ, ZE2JA, ZS9G, mostly a.m. with a few ssb. **F. Simpson** again heard HB9ED, IICGV, SVIDZ, ZE1AN, ZE2JA, ZE3JU.

Finally a surprise, a genuine log for 144Mc/s, our very first. The honours for the christening go to **David Douglas** (Dundee), who says the following were "got" with an HRO. (With a converter, I hope), G3-BRA 80, HUI 200, MCR 200, HBØLL, 750, SV1AB 1,200, YU1EXY 750. Numbers refer to distance from the transmitting stations in miles.

BOOKS REVIEWED

BASIC ELECTRICITY/ELECTRONICS LABORATORY WORKBOOK. By Training & Retraining Inc. Published by W. Foulsham & Co., Ltd., Slough, Bucks. 224 pages. Size 10½ x 8½in. Price 35s.

THIS is a book whose introduction was printed in England and the balance in the U.S.A. Doubtless in America this is a useful publication but your reviewer doubts its popularity this side of the Atlantic.

It presents a number of projects involving the use of a VTVM and/or oscilloscope. Each chapter is based on a question and answer technique so that the reader is quizzed on knowledge gained as the book proceeds; the answers are given later in the chapter. Projects range from a simple power supply to a superhet receiver but, as one proceeds, various doubts tend to arise.

Constant irritating references to other volumes (by the same publishers perchance) are one source of doubt. Another is the number of odd things which do not seem to tie up. Page 119 assures that we will need a 1,500Ω resistor, yet the relevant circuit on page 122 depicts 1,500kΩ. The availability of a three-gang 365+365+162pF also might prove difficult. Verdict: Go to America to read this one.—*DLG*.

TAPE RECORDING SERVICING MANUAL. By H. W. Hellyer. Published by George Newnes Ltd. 336 pages. Size 9½ x 7½in. Price 33s.

ON first flicking through the pages of this monumental tome the reader is likely to register surprised anticipation; on closer investigation he might well exclaim: "At last!" For while there have been, and still are, books on tape recorders this one reaches a degree of completeness never before achieved. The trouble with most books is that excellent though they may be in themselves, they try to cover too wide a field in the space available. Those interested in the servicing aspects often have to make shift with an odd chapter or two. Here at last is a book devoted exclusively to tape recorder servicing.

The author, H. W. Hellyer, will need no introduction to readers of *PRACTICAL WIRELESS* and *Practical Television*, but it is worth pointing out that in producing his *magnum opus* he was able to draw on his own considerable practical workshop experience of the wayward behaviour of tape equipment.

The introductory chapter covers only 14 of the total 336 pages but condenses in that space a lot of useful information on the basic principles of tape recording. The rest of the book is devoted to an analysis of tape recorders under 62 different trade names! A typical entry details the most important aspects of the machine in question—specification, special features, dismantling, together with notes on special adjustments and servicing with pointers to particular faults peculiar to that model or range of tape recorders. Much of the practical material as mentioned before, is the result of personal experience.

In this way not far short of 300 different tape recorders or decks are dealt with. Circuit diagrams accompany each model or range with mechanical details and component layouts where they serve a useful purpose. In so far as a book of this kind can ever be complete this one is.

Your reviewer has only one criticism and that is the drawings. They are taken from manufacturers' literature and are therefore in almost as many styles as there are circuits, which gives the production a somewhat untidy aspect. However, the meat is there and no doubt the economy involved in not redrawing everything to a standard is reflected in the cost of the book. Still, a pity.

Anyone with any interest at all in tape recording from the servicing angle will miss the buy of the year if he doesn't order this book. For, taking into account the wealth of accumulated data and the potential value of the material, it would be false economy indeed not to add this work to his bookshelf!—*WNS*.

TRANSISTOR RECEIVERS AND AMPLIFIERS. By F. G. Rayer. Published by Focal Press Ltd. 168 pages. Size 8½ x 7½in. Price 30s.

WITH the increasing cheapness and availability of transistors there seems little doubt that the number of enthusiasts using them will also increase. If you are one of these people and you require a not too technical book on the subject of receivers and amplifiers then your problems are solved for 30s. Commencing with an explanation of how these devices work the book continues with chapters on aerials and r.f. amplifiers, mixers, i.f.'s, detectors and a.g.c., Class A, Class B, high-power and hi-fi stages. Bonus chapters include v.h.f. equipment, record players, and test equipment and fault finding. A useful book indeed, steering a practical middle course between high technicalities and boring simplicity.—*DLG*.

MUSICAL INSTRUMENTS AND AUDIO. By G. A. Briggs. Published by Wharfedale Wireless Works Ltd., Idle, Bradford, Yorks. 238 pages. Size 8½ x 5½in. Price 32/6d.


THIS book attempts to bridge the concert-goer and the audiophile both at the same time. The net result is that it falls between two stools, and at 32s. 6d. it is questionable whether it is worth bending down to pick it up. It discusses instruments of all classes, their manufacture, the sounds they emit, wave forms, the formants, harmonics and just about everything. It is degraded by frequent attempts by the author to be funny, and this is further aggravated by the numerous unfunny cartoons and sketches from old issues of *Punch*. There are special chapters written by experts in their field, and had the general style of the book followed the examples set by these writers then the improvement would have been such as to justify a firm recommendation, as it is, however, your reviewer remains unimpressed.—*DLG*.

Don't Miss Next Month's Big-Value Issue!

2 Invaluable **FREE GIFTS**

RESISTOR COLOUR CODE CALCULATOR

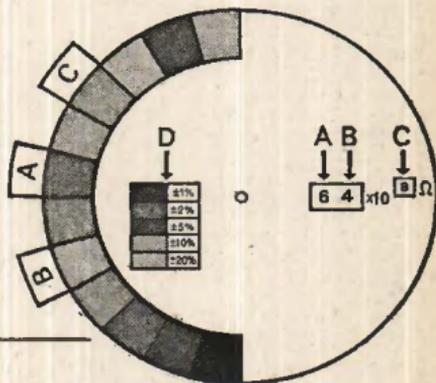A simple-to-use aid for the constructor. Just set the colours and the correct resistance value is shown in the "window". Resistor tolerance is also indicated.




24-PAGE BOOKLET **GUIDE** TO VALVE CIRCUITS

First of 3 month-by-month FREE Booklets covering at-a-glance data on r.f., i.f. and a.f. amplifiers, frequency changers, oscillators and many other aspects of radio and electronic equipment.

Other Outstanding Features:

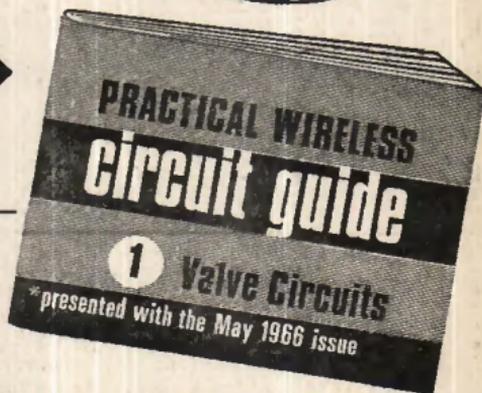1. The 208 Bandsread Receiver.
2. Simplified Cabinet Design.
3. Comprehensive ATU.



PRACTICAL WIRELESS

MAY ISSUE

ON SALE
APRIL 7th **2/6**

ORDER NOW!


SEE FORM ON PAGE 1046

PRACTICAL WIRELESS

MAY
1966
216

FREE INSIDE

- 0 RESISTOR COLOUR CODE CALCULATOR
- 0 24-PAGE BOOKLET GUIDE TO VALVE CIRCUITS

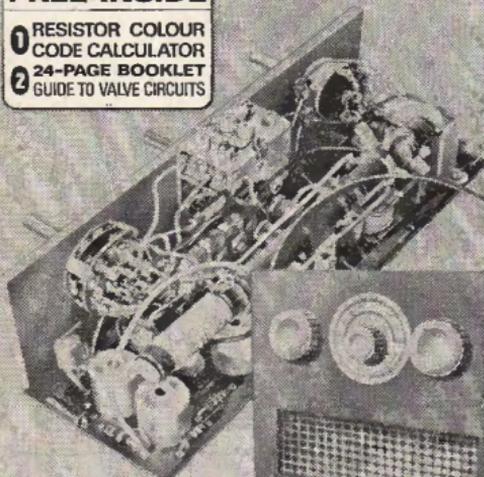

**THE 208
BANDSPREAD PORTABLE**

from
next month
**PRACTICAL
WIRELESS**
will be
published
in a **NEW
LARGE-SIZE
FORMAT**



From next month's issue, on sale April 7, PRACTICAL WIRELESS will appear in an attractive new format, with an increased page-size and heavier quality paper. Many special features plus more FREE insets, have been planned ahead for the new large size issues. See overleaf for details of a FREE Resistor Calculator and a FREE 24-Page Booklet on Valve Circuits inside every copy, next month.

INCREASED DEMAND

*Make sure of
your copy - hand
this form to
your newsagent
today!*

To
(Name of Newsagent)

Please reserve/deliver the May issue of PRACTICAL WIRELESS (216), on sale April 7, and continue until further notice.

NAME

ADDRESS


.....



EL KEY

ELECTRONIC MORSE KEY

P. MURPHY

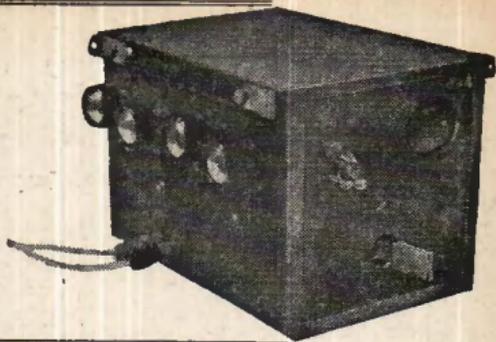

THIS device was built, taking into account the large variety of types of morse one meets with in the communications world. Whether it be slow or fast characteristic or otherwise, e.g. slow dashes—fast dots, or fast dashes—slow dots, short "space" or long "space", and not forgetting of course perfect well balanced morse. The key was thus designed to be as versatile as possible to take into account the above mentioned types of morse, while retaining the advantage of being an automatic device, and works over a range varying from a very very slow pace up to about 40 w.p.m. The key is therefore suitable for both amateur and professional and would be a very useful asset in training establishments. The key is inexpensive to make, suitable for the home constructor to build and has the advantage of being portable. It is economical to run and uses standard transistor batteries.

The newcomer to the electronic key may at first think it is difficult to use, but like everything else a little practice each day for a week or so will soon convince him that it is not as difficult as it first seemed.

Construction

Handle or Paddle:—The construction of the handle can present a small problem, as it must be capable of moving from side to side and returning to its neutral or "central" position automatically when the finger pressure is released from it, also the gap between its central position and the dot or dash stud into which it comes into contact must be very small indeed, approximately between $\frac{1}{8}$ and $\frac{1}{16}$ in., and a general rule which can apply here is that it is better to have too small than too large a gap.

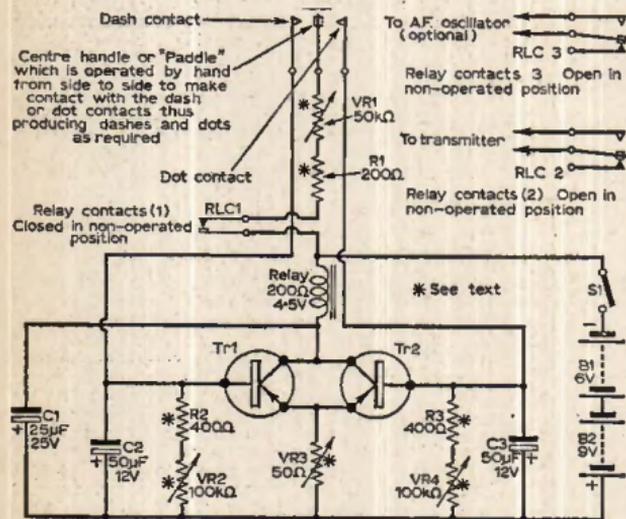


Fig. 1: Circuit diagram of transistorised key.

The paddle described, if constructed properly, can give excellent results and is both simple and easy to construct. However the would-be constructor should pay particular attention to the paddle, a bad handle can spoil the performance considerably, e.g. the letter C is sent thus: — — — a handle which has, for example, a large gap can give an effect which could sound like — — — which produces the letter N twice, an experienced electronic key operator can, of course, overcome things like this, but for the beginner a good paddle is most essential. See Fig. 3.

The paddle consists of a nail file (5in. long), a piece of wood $3\frac{1}{2}$ in. x $1\frac{1}{2}$ in. x $\frac{3}{4}$ in. upon which the nail file is mounted, and an L shaped piece of metal $1\frac{1}{5}$ in. long and $\frac{3}{4}$ in. wide in the horizontal and $1\frac{1}{5}$ in. x $\frac{3}{4}$ in. in the vertical plane (See Fig. 3) which is used to support the nail file on the wooden base. The L shaped piece is secured to the nail file by small nuts and bolts.

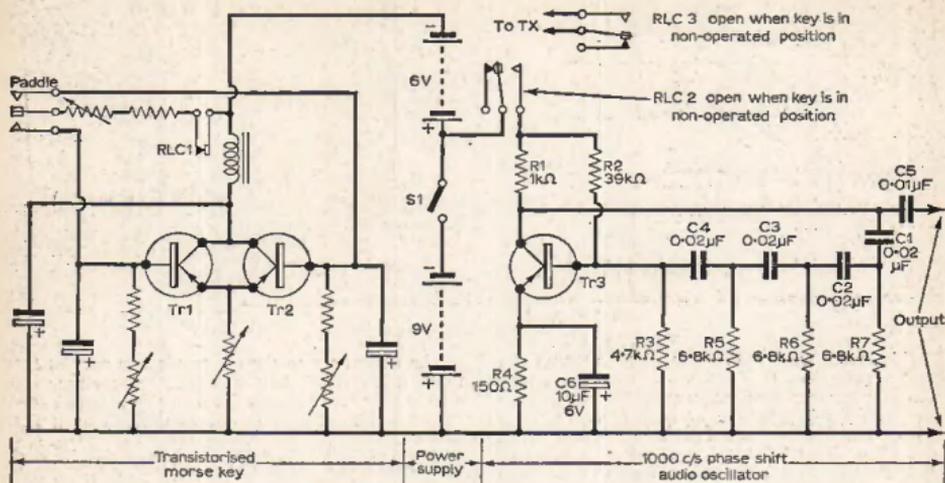


Fig. 2: Diagram of electronic key and phase-shift audio oscillator.

Two flat pieces of formica can be glued to each side of the nail file near its end, which tends to make the paddle easier to operate.

The wooden base can be either glued or screwed to the chassis.

Function of Components in Fig. 1

The components, VR1, R1, C1, make up the time constant (CR) for the space (time interval) between consecutive dots or dashes. Increasing VR1 will therefore increase the space, or vice-versa, the max. space limit chosen was the max. practical limit that would be required although spaces up to unity can be obtained with this type of transistor. They are not required in this case. The min. space depends approximately on the value of C1. In the circuit (Fig. 1) extreme max. and min. values should be obtained, and here as well as the other

variables in the circuit, the constructor may, if he so desires, choose closer limits by using the appropriate value of VR1, which he can quickly determine by experiment. The mark length is slightly affected when varying the space control VR1.

RI Under no circumstances must this 200Ω resistor be omitted or reduced in value as it is a limiting resistor and 200Ω was found to be the min. critical value.

The components, VR2, R2, C2, make up the time constant for the dash side of the circuit. C2 and R2 by themselves provide for the shortest length of dash and by increasing VR2 the length of dash can be increased, here again max. and min. values have been chosen, and it is up to the constructor if he wishes to modify these.

The components, VR4, R3, C3, make up the time constant (CR) for determining the length of dot and as in the case of the dashes extreme max. and min. values were again chosen, R3 and C3 together decide the shortest length of dot and VR4 can be increased to lengthen it.

VR3 varies the overall speed, the ratio of dot to dash and space etc., are fixed by VR1, VR2 and VR4, and VR3 varies the speed of the cycle as a whole, though slight variations do occur in the ratios especially at higher and lower speeds. However this is easily overcome by setting the ratios at approximately the speed one is going to work at and adjusting as necessary. In any case only one control will need adjusting. Increasing VR3 decreases the speed and vice versa.

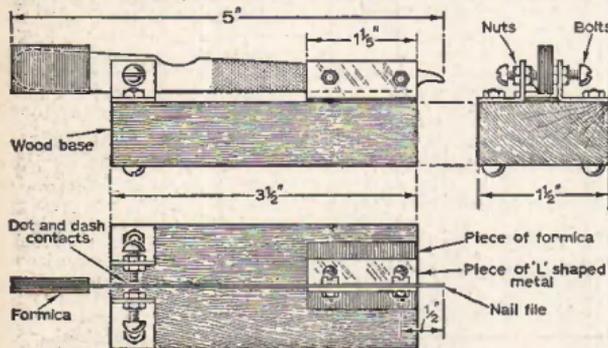


Fig. 3: Complete "paddle" for the key.

THERMOSTATS

Type 'A' 15 amp for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob quickly adjustable from 30°-80°F. 2/8 plus 1/- post. Suitable box for wall mounting. 5/6, P. & P. 1/-.

Type 'B' 15 amp. This is a 17in. long rod type made by the famous Sumvit Co. Spindle adjust this from 80-100°F. Internal screw alters the setting so this could be adjustable over 50° to 1,000°F. Suitable for controlling furnace, oven, kiln, incinerator heater or to make thermostat of sire alarm. 2/8 plus 2/8 post and insurance.

Type 'C' is a small porcelain thermostat as used on electric blankets, etc. 14 amp. setting adjustable by screw through side. 3/6, P. & P. 6d.

Type 'D' call this the Ice-stat as it puts in and out at around freezing point 2/8 extra. Has many uses, one of which would be to keep the hot pipes from freezing if a length of one blanket, 16 yds. 10/- is wound round the pipes. 7/6, P. & P. 1/1.

Type 'E' This is a standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperatures. 7/6 plus 1/- P.

TRANSISTOR BARGAIN

Transistor set case with 4 P.P.S. transistors. Metal case 10" x 8" x 3". 8 P.P.S. transistors made from best plywood and covered Teflon fabric—looks very smart—suitable for receiver—amplifier—extension Speaker etc.—Originally listed at 29/6— but offered this month at only 15/- plus 2/- post and insurance also given free with it is a printed circuit board to suit it and building instructions for the two wave radios—Don't miss this great offer.

TAPE RECORDER BARGAINS

CAPACITAN Driven, 5 Transistors
SP-1000—200/7000 C.P.S.—460 MW output—double track—twin speed (33 and 7 1/2) fast rewinding time—5m. speed gives one hour playing with standard tape weight 7 lb. Size 8 x 1 1/2 x 5 1/2. Complete with batteries, microphone—taps speed and instructing manual. Nothing to go wrong if you use a good tape and keep heads clean. Demonstration gladly given at our Crystal Shop.
 Special 1/11 Price This Month. £11.11.0. Post and Insurance 6/6.

THE 'MINY'

Best of the spot driven machines, remote control on mikes, battery operated.
 26.18.6 plus 5/- post & ins.

TRANSISTOR SET CASE

Very modern cream cabinet, size 8 1/2 x 1 1/2 in. with chrome handle and knob. Price 4/6 plus 2/- postage.

GANGED POTS

Standard type and size with good length of spindle—made by Morganite. List price 1/6—each but if you get quickly you can have them at 12/- doz. for 1/6 each if less than doz. Following rates in stock all 1/6—25K—10K—10K+10K—100K—500K—500K all new and unused. Post 2/0 on lot less than 1/- per doz. 6 doz or more post free.

FINE TUNERS

80 pf with long spindle as illustrated, 1/6 or 12/- doz. Twin 50pf not quite so good as long spindle. 2/6 or 24/- doz.

Where postage is not definitely stated as on an extra line orders over £5 are post free. Below £5 add 2/6.

**See in the Dark
 INFRA-RED BINOCULARS**

These if fed from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red coil. These optical systems can be used as lens for TV camera—light coil etc. (details supplied). The binoculars form part of the army night driving (Tabby) equipment. They are named and believed to be in good working order, but sold without a guarantee. Price £2.17.5 plus 10/- carriage and insurance. Handbook 2/6.



AMPLIFIER BARGAIN—NOT BEATABLE

**750 mW
 TRANSISTOR
 AMPLIFIER**
 4 transistors including two to push-pull input for cerebral or magnetic telephone or push-up—test back loops—sensitivity 5 mV.
 Price 19/6
 Post and insurance 2/6.
 25 often supply 12/6 extra.

STUPENDOUS OFFER £11 for £2

The Princess superb set described below is a very fine little set that has been most carefully designed for high performance. Only recently (under another name of course) this was on offer in many radio shops, at 21s. 10s.6. but we have been fortunate in obtaining the parts at a very low price and now pass this saving on to you. If you act quickly you can purchase this for only 28/6 plus 3/6 post and insurance. Note these features.

- Long and Medium Wave
- Long clear dial with travelling pointer and slow motion drive
- Pull out output approximately 500 m.w.
- A.V.C. and feed back
- Dust cord H. 4/- 1/- transformers.
- High selectivity ferrite aerial
- Six Loctal and guaranteed transistors
- Printed circuit board for fool proof assembly
- Secondary output circuit gives long life from P.P.S. battery
- Permanent magnet moving coil speaker
- Cabinet size 6" x 3" x 1 1/2". Carrying strap

You get over 50 parts (not value over £10). In fact everything you need and easy to follow wiring and aligning instructions. Don't miss this wonderful offer. Make up several while you have the chance. Use them as presents and you'll be loved for ever. Battery 1/8 extra. Data separate 2/6.



INFRA-RED HEATER

Make up one of these latest type heaters. Ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—use allicon enclosed elements designed for the correct infra-red wavelength (8 microns). Price for 750 watt element and metal-casing as illustrated, 21/6 plus 2/6 post and insurance. Full sheet 3/- extra.



THIS MONTH'S SNIP

**Garrard 1000
 Record Changer**
 One of the latest record changers that this famous company make—Automatic selection of records which may be mixed—may also be played manually. Finger tip adjustment of stylus pressure, fitted with mouthhead but pick-up wired for stereo—suitable 300/250—A.C. mains. Cabinet space necessary 14" x 22in. with 4 1/2in. above and 2 1/2in. below. DON'T MISS THIS SPECIAL SNIP only 65.8.0 post and insurance, 6/6.



Bargain for Experimenters and Constructors
 Printed circuit outfit with 16 page booklet of circuits and projects. Use and disk, laminated copper clad board, etching fluid etc. etc. all for 7/6 plus 1/- post.

FLUORESCENT CONTROL KITS

Our 80 watt kit for 8" fluorescent tube is the best money can buy. It contains latest slim line relay to hold away choke made by one of England's largest companies—starts—tube ends—two chrome clips. All wired up ready—fit it in a jiffy with just a few screws—and it's guaranteed for three years—price only 26/- complete plus 2/6 post and ins. or complete as listed but not wired up 22/6 plus 2/6.

Other sizes:
 3" 20 watt wired 22/6 not wired 18/6 + 2/-
 4" 40 watt wired 25/- not wired 22/6 + 2/6
 5" 40 watt wired 18/6 not wired 17/6 + 2/-
 6" 40 watt wired 19/6 not wired 17/6 + 2/-

SEED & PLANT RAISING

Be first this year with heating wire and transformer. Suitable for standard size garden heater. 22/6 plus 2/6 post & ins.



SOUND POWERED TELEPHONES

These require no batteries. In fact they have only to be connected by a pair of wires to a telephone and they can be fitted into existing bell circuits. Results are extremely good and to a vast majority of users are nothing. Handsets only 15/- each. Post, etc. 3/6. Two post free.



Speaker Bargain

12in. High fidelity loudspeaker. High 8" x 1 1/2" x 3" magnet type ratchet wheel for 3 ohm or 16 ohm speech coils. Will handle up to 10 watts. Brand new by famous maker. Price 29/6 + 3/6 post and insurance



Waterproof Heater Wire

16 yds. length 70 watts. all requiring temperature control. 10/- post free.

FOUR-STATION INTER-COM

Will save time and improve efficiency. Ideal in home—office—shop—surgery, etc. Complete outfit comprises Master unit and three subsidiaries, each which can call the master and have full two-way working. No wiring problems as subs fitted with 50W. twin sex and they plug into sockets. Also included is pack of station—batteries and better. Nothing else to buy—£7.16.0 plus 4/6 post and insurance.



ARMCHAIR CONTROL UNIT

Remote Controller for Philips, Gtalia and Cosor T.V. sets etc. but adaptable to most others, and to model control. Comprises 8 rocker switches, two variable resistances and components including Mullard OA81—Krohn—10 way plug—114. 2 way cable etc. etc. etc. List price £3.3.0 yours for only 12/6 plus 2/- post and insurance.



ELECTRONICS (CROYDON) LTD
 Post orders to: Dept. P.W., 4 Springfield Road, Eastbourne, Sussex
 Callers: 266 LONDON ROAD, WEST CROYDON, SURREY
 NEW BRANCH FOR CALLERS: 102 TAMWORTH Rd., CROYDON (op. W. Croydon Stn.)

R.S.T. VALVE MAIL ORDER CO.

All valves
brand new
and boxed

Mon.—Sat. 9 a.m.
5.45 p.m.
No Early Closing
Open Daily to Callers
Tel. MITcham 6202

211a STREATHAM ROAD, MITCHAM, SURREY

OC2	5/8	9B8T	10/6	6L1	8/6	10L11	10/6	50C15	9/6	ATP4	1/8	RB91	3/6	EP08	10/6	N78	15/6	FY8	8/6	UCL88	8/6
OC3	5/8	9B8S	7/6	8L5Q	7/6	10P18	12/6	30C17	12/6	ATP5	7/6	RB03	6/6	EP158	6/6	N106	15/6	PV800	5/8	UF41	7/6
LA7	7/6	9B8T	16/6	8L1E	7/6	12A8H	9/6	30P3	8/6	ATP7	4/6	EB241	6/6	EP184	6/6	NG21	8/6	FY801	6/6	UF68	8/6
LD5	6/6	9BWS	8/6	8Q7G	8/6	12A7T	8/6	30L15	18/6	AU3	8/6	EB030	3/6	EL32	5/6	NG27	8/6	RL	4/6	UL41	6/6
1R6	7/6	9BW7	8/6	9Q7GT	9/6	12A7T	8/6	30L15	18/6	AU5	6/6	EBP80	5/6	EL38	17/6	OZ4	4/6	R19	7/6	UL84	6/6
LLD8	5/6	8C4	1/6	98A7	4/6	12A1V	4/6	30L17	12/6	AZ1	8/6	EBP88	3/6	EL34	9/6	PC88	10/6	RG5/80	8/6	UM80	7/6
1N50T	8/6	8C0G	4/6	98C7	6/6	12A17	5/6	30P18	10/6	AZ31	7/6	EBP89	6/6	EL41	7/6	PC88	9/6	R41	9/6	UC15	13/6
1R5	4/6	8C8	8/6	98C7	4/6	12A1X	4/6	30P19	14/6	CB181	8/6	EBL1	17/6	EL42	7/6	PC87	7/6	8180	10/6	UU7	10/6
1R4	5/6	8C80	8/6	98H7	2/6	12B4E	6/6	30P11	11/6	CK303	5/6	EBL21	10/6	EL54	4/6	PC84	5/6	8P4	9/6	UU9	8/6
1B5	3/6	8C80G	22/6	98J7	3/6	12B8	4/6	30P18	12/6	CL31	18/6	EBL31	27/6	EL80	6/6	PC85	8/6	8P4	1/6	UY21	7/6
1Y4	2/6	8C84	3/6	98K7GT	4/6	12B8T	2/6	30P114	12/6	CM3	18/6	ECU81	3/6	EL85	8/6	PC169	10/6	8P61	1/6	UY41	4/6
5A4	3/6	8CWA	14/6	98L7GT	4/6	12C8GT	7/6	38A5	17/6	DAC32	7/6	ECU82	3/6	EM34	9/6	PCF80	8/6	8U22	19/6	UY85	4/6
3Q4	6/6	8D6	8/6	98N7GT	4/6	12E1	19/6	38L5	5/6	DAF91	3/6	ECU88	4/6	EM60	8/6	PCF82	4/6	8U2180	12/6	VCR8	4/6
8Q5	6/6	8E5	5/6	98Q7	6/6	12J8GT	3/6	38W4	4/6	DAF96	6/6	ECU94	6/6	EM71	7/6	PCP84	8/6	R41	9/6	VCR8175	8/6
8V4	4/6	8F1	9/6	9I44GT	10/6	12J7GT	7/6	38Z3	10/6	DDC80	8/6	ECU88	5/6	EM81	8/6	PCP85	8/6	TD4	7/6	80/	80/
8T4	8/6	8F6G	5/6	9I59G	7/6	12K7GT	5/6	38Z4GT	3/6	DF82	8/6	ECU88	8/6	EM15082/6	PCF81	9/6	TH41	8/6	7/6	VCR817C	80/
8E40	3/6	8F6G	4/6	8V3M	8/6	12K8GT	8/6	38Z5	5/6	DF70	5/6	ECU88	8/6	EY31	8/6	PCF82	9/6	U10	7/6	VMP4G	17/6
8V40	4/6	8F6G	4/6	8V6G	8/6	12Q7GT	3/6	37	5/6	DF91	2/6	ECU82	6/6	EY66	6/6	PCF80/10/6	U14	7/6	80/	VMP4G	17/6
8V40	3/6	8F11	12/6	8V6GT	7/6	128A7	8/6	48	4/6	DF92	8/6	ECU81	10/6	EZ35	4/6	PCF808/12/6	U19	80/	80/	VMP4G	12/6
8Y30T	4/6	8F18	5/6	8X4	3/6	12807	8/6	50B5	8/6	DF95	22/6	ECU83	10/6	EZ40	5/6	PCF805/12/6	U25	18/6	80/	VMP4G	12/6
8Z4GT	8/6	8F14	12/6	8X5Q	4/6	12817	2/6	50C23	6/6	DI77	3/6	ECU82	8/6	EZ80	8/6	PCF808/12/6	U36	10/6	80/	VMP4G	12/6
8Y80L2	10/6	8F88	8/6	8X5GT	7/6	12847	2/6	50CDB98/4/6	DK92	7/6	ECU81	5/6	EZ80	5/6	PC183	8/6	U78	8/6	VT35	20/6	
8A7	15/6	9G6	2/6	7B6	11/6	128K7	2/6	80L6GT	8/6	DK91	5/6	ECU88	6/6	EZ81	8/6	PC184	7/6	U91	11/6	VT91	50/6
8A6G	12/6	8H8	1/6	7B7	7/6	128K7	5/6	75	8/6	DK92	7/6	ECU88	6/6	EZ82	8/6	PC185	8/6	U92	10/6	VT91	50/6
8A6T	3/6	8J8M	8/6	7C8	10/6	128K7	20/6	78	4/6	DK93	6/6	ECU88	6/6	EZ82	8/6	PC186	8/6	U91	12/6	VT91	50/6
8AK5	4/6	8J8G	2/6	7C8	6/6	19AQ6	7/6	80	5/6	DL70	7/6	EAL83	9/6	EZ84	8/6	PEN44	80/	U92	6/6	VY88	25/6
8AL5	3/6	8J8GT	4/6	7D5	8/6	30D1	10/6	86A3	8/6	DL82	4/6	ECU86	8/6	EZ80	22/6	PEN44	20/6	U91	18/6	VY88	25/6
8AMS	2/6	8J8	3/6	7D7	8/6	20P2	11/6	150B8	14/6	DL83	3/6	EP3	17/6	EZ80	8/6	LAC83	8/6	X78	20/6	VY88	25/6
8A8S	2/6	8J8M	8/6	7D7	12/6	20L1	15/6	130C4	12/6	DL84	6/6	EP8	8/6	ET06	20/6	PEN46	2/6	CAF24	7/6	X78	41/6
8AMS	0/6	8J7G	4/6	787	18/6	20P4	14/6	801	5/6	DL85	6/6	EP7A	2/6	ET11	10/6	PL36	9/6	UB41	6/6	XH1-5	41/6
8A8T	22/6	8J7GT	8/6	7Y4	3/6	30P5	12/6	807	7/6	DL86	6/6	EP8	2/6	ET85	25/6	PL33	3/6	UR91	7/6	XPI-5	5/6
8AT5	3/6	8J8GT	5/6	8W8	8/6	28A5	6/6	818	20/6	DM70	5/6	EP41	6/6	ETW61	4/6	PL82	5/6	URF80	6/6	X81-10	5/6
8AT8	0/6	8K7M	5/6	10C1	12/6	32L6GT	8/6	868	10/6	DY88	7/6	EP40	2/6	ET241	8/6	PL83	8/6	URP89	6/6	Y88	7/6
8B6G	2/6	8K70	1/6	10C2	12/6	28Y8	8/6	954	4/6	DY97	7/6	EP80	4/6	ML4	17/6	PL84	9/6	UC88	8/6	ZB4	40/6
8B4S	4/6	8K7GT	4/6	10T1	12/6	32Z4	8/6	1888	5/6	ES8C0	14/6	EP86	4/6	MX40	12/6	PY31	5/6	UC88	8/6	ZB7	12/6
8B8H	7/6	8K8G	8/6	10F3	12/6	28Z5	7/6	402AR	15/6	EA00	8/6	EP86	4/6	MX44	4/6	PY33	8/6	UC82	7/6	ZB7	12/6
8B8H	7/6	8K8GT	3/6	10F18	9/6	33D7	5/6	7183	1/6	EAF43	7/6	EP81	2/6	MX40	12/6	PY31	5/6	UC81	6/6	ZB7	12/6
8B70	7/6	8K8GT	3/6	10F18	9/6	33D7	5/6	7183	1/6	EAF43	7/6	EP82	2/6	MX44	4/6	PY32	8/6	UC82	7/6	ZB7	12/6
8BQ7A	7/6	8K25	20/6	10L4	10/6	30C1	9/6	7472	2/6	EB41	6/6	EP82	2/6	MX44	4/6	PY32	8/6	UC82	7/6	ZB7	12/6

SPECIAL 24 HOUR SERVICE
OBsolete TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
 Postage 6d. per Valve. C.W.O. No C.O.D.
 Send S.A.E. for list

Special 24 Hour
Express Mail
Order Service

SETS OF VALVES
 DAF91, DF91, DK91, DL92, DL94 ... Set of 4, 19/-
 DAF96, DF96, DK96, DL96 ... Set of 4, 25/-
BRAND NEW TRANSISTORS
 OC85 9/6 OC86 8/6 OC82 6/-
 OC44 4/6 OC81 4/- OC82D 10/-
 OC45 3/6 OC81m/r 12/6 OC170 7/6
 OC71 4/6 OC81D 4/- OC200 8/-



RANK WHARFEDALE LIMITED Idle, Bradford, Yorkshire
 Telephone Bradford 612552/3 Telegrams 'Wharfedel' Bradford

POST THIS COUPON TODAY

For fully illustrated 8 page booklet on Wharfedale Speaker Units (Dept. PW.4)

NAME

ADDRESS

TOWN.....COUNTY.....

Transistors

These are GEC S3 type transistors. Type GEC S1 will perform equally well and although others have not been tried in Fig. 1, it is presumed that any p-n-p type transistor which is suitable for a class B output stage e.g. Mullard OC72 would be suitable. GEC types were chosen because they were less expensive at the time. It may be necessary to adjust some of the component values, if other types of transistors are used, because differences in performance was noticed, even with individual transistors of the same type, but these variations were slight.

Layout and General Information

For the right-handed operator it is necessary that all the adjustable controls can be easily turned with the left hand, so that adjustments can be made whilst actually operating, and saves the necessity of having to stop to alter the ratios or speed etc. A left hand operator should have access to the variable controls with his right hand.

The two pairs of wires from the relay contacts RLC2, RLC3 should each preferably be terminated in a plug and socket at the back of the box or chassis to prevent wires going to the tx and osc. (only for separate osc. not built in the key as in Fig. 1) from getting in the way near the paddle. The on/off switch would naturally be convenient in the front, (when Fig. 2 is built only one pair of contacts need be terminated in plug and socket for tx). The max. height of the handle above the bottom of the box or chassis should not exceed 2in., this height also includes the width of the nail file.

When operating the key the correct position of the arm and hand is absolutely essential and it is as follows:— The arm from the elbow down should lie relaxed on the table, with the thumb side of the hand upwards, the handle of the key is then operated with thumb and first finger in a gentle side to side movement. The whole of the hand up to the wrist should follow the movement of the fingers and in this way, an operator can send for hour after hour without getting tired. The writer knows of no other method which can equal that just described for operating the key and getting

the best results from it with the minimum of effort.

When assembling the device; especially when experimenting with it, it was found on several occasions that minute pieces of solder, dust, etc., got between the relay armature and pole face preventing the key from functioning, and it was only after testing everything else that the relay was examined and the fault discovered; however, a thorough clean-up after the unit is placed in the box would avoid this fault altogether, together with careful soldering.

When Fig. 2 is built (i.e. key and oscillator together) a loudspeaker may be built-in or a "split phones" arrangement with a 3-way switch, i.e., e.g. Switch Position

1. One earpiece to Radio Receiver, other earpiece to audio oscillator.
2. Both earpieces to Radio Receiver.
3. Both earpieces to oscillator.

While on the subject of Fig. 2, the current consumption with oscillator and key drawing from the batteries, varies between some 20 to 30mA, negligible current is drawn when not keying; however the on/off switch from the supply should be switched off when the key is not in use.

The photograph shows the key when built; it can however be enclosed in a much smaller space, and must not be too light in weight although the batteries do help to make up weight, also the width should not be less than say 3 to 4in. This helps to stabilise the unit and prevent it from moving when keying. Component tag boards were screwed to the side of the box and the opposite side was used for the variable pots. A suitable lid fits on top and the workings are then completely enclosed.

Although there are many different combinations of capacity and resistance which would give the same results as the key in Fig. 1 the circuit design is a standard, and providing the constructor can comply with the transistor limitations, and provide enough current to operate the relay, a wide range of combinations are open to him. Dots are normally to the right operated by the thumb, dashes are normally to the left operated by the first finger. In Fig. 1 both dots and dashes can be obtained from either side, should an operator require the opposite.

ON THE SHORT WAVES

—continued from page 1043

There are VK's on topband and at least one of our reporters has heard a JA. Anyone else hear these remote parts at this frequency? For those wanting to know when to listen on 20 and 15 the answer is that they are open from 0600-1800 G.M.T. Someone will doubtless hear a piece of fabulous DX at 1081 now that I've said that! Listen on phone only for VQ8AZ and VQ8BZ in Mauritius. ZD8's are planning some DX-peditions in the Caribbean area soon, ZD5M is loose on 21 c.w. (Swaziland), while on 20 c.w. TL8SW is quite a rare bird. ZS2MI reported active from Marion Island, and spies report that an expedition is promised for Rio de Oro soon. Contests for March include 12-13th, ARRL DX Contest (phone); 19-20th, BERU; 26-27th, ARRL DX Contest (c.w.); April 3rd, Low Power (QRP) Contest. All logs welcome, deadline for May issue is March 27th.

PRACTICAL ELECTRONICS

APRIL

4 ELECTRONIC AIDS FOR THE HOME

FREE CAPACITANCE AND
RESISTANCE CALCULATOR

MORE "BONANZA BOARD" PROJECTS
GUITAR SOUND EFFECTS UNIT
AUDIO POWER BOOSTER

On sale MARCH 17—2s. 6d.

PRACTICALLY WIRELESS

THE perennial subject of breakdown has haunted the electronics industry from the "shed-in-the-back-garden" days to this era of chrome and plastic fabricatories, despite the analysis and study of a whole new group of pseudo-scientists, whose main function seems to be to evaluate and correlate and argue at length with each other in the learned journals.

It does not haunt those of us who were raised on the bread-board and makeshift component. Breakdowns were the order of the day. We righteously asserted that one could only learn by one's mistakes. But to a later generation of experimenters and constructors, brought up on ready-made receivers, and elegantly annotated kits, failure is taboo.

It may seem strange that a manufacturer should even admit the possibility of failure when launching a product. Let alone publish his estimate of Mean Time Between Failures, which is what the electronics industry understands by those initials.

The aforesaid pseudo-scientists have great fun working out the MTBF and juggling the figures as dextrously as a radio retailer trying to explain battery working hours to the rather dim purchaser of a portable tape recorder.

It is becoming a modern trend



Trying to explain to a rather dim purchaser.

to admit not only that the equipment can go wrong, but that it will predictably continue in its back-sliding ways. Our postbag shows that many readers are not yet educated into this way of thinking. Any practising service engineer could soon offer a host of demonstrations.

We do not have to look much farther than the cheaper imported transistor radios. Except that a request for repair will show that the MTBF is either zero or infinity depending on whether the harassed salesman is sucker enough to accept the job, or shuns any responsibility.

In the words of the poet: "Radios out of Old Hong Kong, All too frequently go wrong".

And the optimists who imagine that things will improve are due to be disillusioned. Already, rising labour rates, are worrying the Japanese, and have brought the electronics section of Hong Kong's labour force into the "elite" class. With Taiwan emerging as a healthy radio manufacturing centre and the great labour markets of Korea and India as yet untouched it seems likely we shall get more and more of the cheap and nasty cut-price models in the near future.

To digress: a Japanese industrialist told us the interesting story of an argument with a taxi-driver whose radio blared annoyingly in the cab. He took a lot of convincing that Hong Kong was part of the wrong Empire. The sun will never set on shoddy goods—that's for sure! Of course, it is unfair to lay the whole blame abroad. There are too many examples nearer home.

Henry has been taken to task, and is unrepentant, for dwelling on the maker's obsession with profit, to the apparent exclusion of reliability. Apart from the top-quality goods, where competition is for specifications and facilities and where high price seems an added attraction, most development seems to consist of finding



An argument with a taxi driver.

ways of cutting costs.

A nodding acquaintance with the term "serviceability" comes only from the copy-writing lads, who see a hinged chassis or plug in parts and go delirious in print. Original reason for the hinge was probably that it fitted a factory jig or facilitated swifter inspection. The plug and socket connectors are now mass-produced by astute experts who have a formidable range of such products, and can thus supply more cheaply than the set-maker can get his joints laid in and soldered.

There is a notorious television receiver with both these "advantages". Only trouble is that to take full advantage of the hinge it is necessary to partially dismantle the tuner unit and 405/625 system switch, and the first time the serviceman tries it he generally manages to break the edge of the printed board. On later marks, the plug sections have wiring added to the back pins, compounding the felony. The l.o.t. is almost impossible to remove unless the printed board is flexed and the system switch rod bent.

MTBF, in this case, is in inverse proportion to the amount of extra time taken by the service engineer in clearing what may have been originally a simple fault.

Probably one of those plug connectors not making properly. Hong Kong fashion.

FOR
THE BEGINNER

A VERSATILE

PREAMPLIFIER

and

TONE CONTROL

by A. S. Ellis



IN the field of audio, need is often felt for an unspecialised preamplifier capable of being used with a wide variety of equipment for various purposes not necessarily forming a permanent part of any of these pieces of equipment. The particular preamplifier to be described was originally built to give greater sensitivity to a somewhat insensitive "gram" amplifier incorporated in a radio receiver. The preamplifier unit has, however, since then been used with enormous success in a number of other applications.

In the particular "gram" amplifier modified no variable tone controls were present and reproduction of gramophone records tended to be somewhat disappointing at times. Most annoying of all was an almost complete absence of bass. Accordingly the tone control box was constructed

for insertion between the pick-up and the preamplifier. The results, when all modifications had been completed, were astounding. Since then the tone control box, too, has been put to numerous uses, not the least of which has been that of a tone correction device whilst making tape recordings.

No originality whatsoever is claimed for the circuits used; the preamplifier is of fully conven-

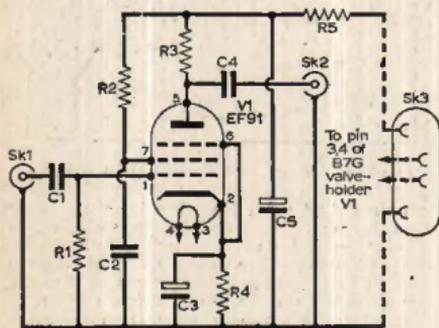


Fig. 1: The circuit diagram of the preamplifier.

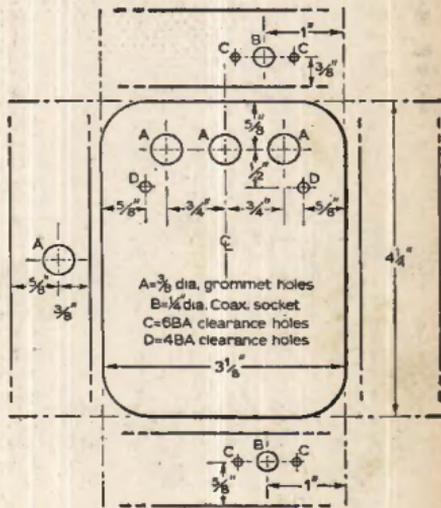


Fig. 2: Preamplifier chassis drilling details (top view).

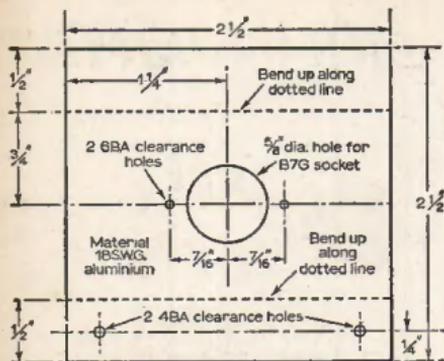


Fig. 2a: Drilling and bending details of valveholder bracket.

tional design, the control circuit is that used in the very popular Mullard two and three valve preamplifiers. However, the form of unit construction is somewhat novel and adds considerably to the versatility of both units.

Externally Powered Preamplifier

The preamplifier circuit is built around the well-known pentode type EF91, which is easily obtainable. In this circuit (Fig. 1) the valve consumes no more than about 1mA h.t. It also requires a heater supply of 6.3V at 0.3A, but both these requirements should easily be met without any overloading of the power-pack of the equipment to which it is attached.

Construction of this unit was carried out in and around a 2oz. tobacco tin of the variety measuring

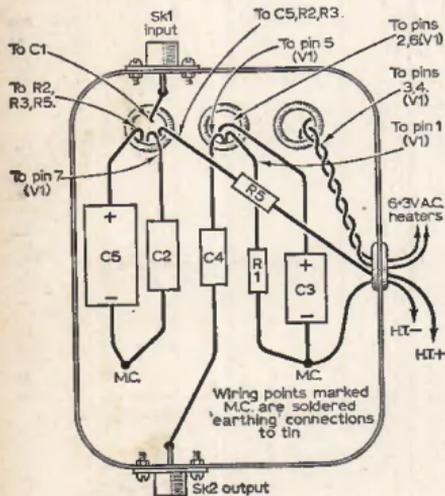


Fig. 3: Preamplifier component layout and wiring.

PRE-AMPLIFIER COMPONENTS LIST (Fig. 1)

Resistors:			
R1	1M Ω	R4	2.7k Ω
R2	1M Ω	R5	15k Ω
R3	220k Ω		
All 10% $\frac{1}{2}$ W carbon.			
Capacitors:			
C1	0.1 μ F	paper	150V.
C2	0.1 μ F	paper	350V.
C3	50 μ F	electrolytic	12V.
C4	0.1 μ F	paper	350V.
C5	16 μ F	electrolytic	350V.

Miscellaneous:

V1, EF91, SK1, SK2 coaxial sockets. PL1 power supply plug to fit socket mounted on receiver or other equipment, type optional. 2oz. tobacco-tin, size approx. 4 x 3 x 1 in.

Small piece aluminium $2\frac{1}{2}$ x $2\frac{1}{2}$ in. One B7G valveholder. Nuts and bolts.

TONE NETWORK COMPONENTS LIST (Fig. 4)

Resistors:			
R1	47k Ω	R3	68k Ω
R2	39k Ω	R4	6.8k Ω
All 10%, $\frac{1}{2}$ w.			
Capacitors:			
C1	560pF	silvered mica	
C2	8200pF	silvered mica	
C3	2200pF	silvered mica	
C4	0.02 μ F	paper	150V.

Potentiometers:

VR1	250k Ω	log.	treble
VR2	250k Ω	log.	bass
VR3	250k Ω	log.	volume

Miscellaneous:

2oz. tobacco tin, approx. 4 x 3 x 1 in., 3 miniature instrument knobs, SK1, SK2 coaxial sockets.

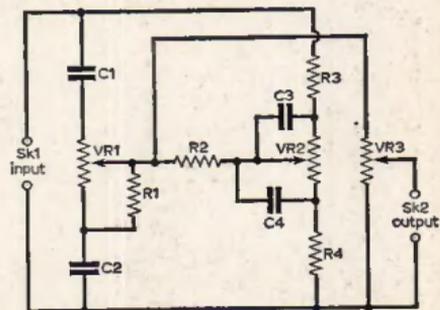


Fig. 4: Circuit diagram of tone control network.

approximately 4 x 3 x 1 in. The lid of the tin was removed, later to become the baseplate of the preamplifier. The tin itself was then turned upside down and used as a chassis. Drilling details are shown in Fig. 2. It was decided not to mount the valve vertically on the tin as it was thought that wiring beneath would become unnecessarily crowded and inconveniently placed. Accordingly a piece of aluminium $2\frac{1}{2}$ x $2\frac{1}{2}$ in. x 18 s.w.g. was

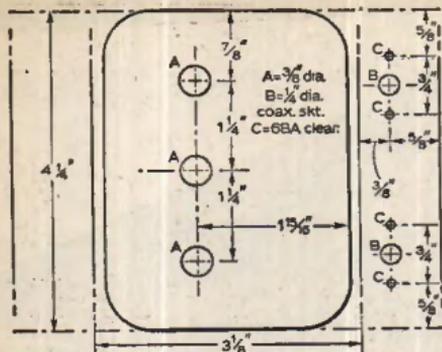


Fig. 5: Tone control chassis drilling details.

cut, drilled and bent as shown in Fig. 2a so that the valve could be mounted horizontally. This support was secured to the main chassis by means of 4BA nuts, bolts and shakeproof washers. Wires to the valveholder were taken from inside the tin via holes A, B and C (see Fig. 2). (Heater wiring was kept well away from the rest of the circuit.) Small components such as R1, R2 and R3 were wired directly to the valveholder but the remainder of the components were mounted inside the tin out of sight (see Fig. 3 underchassis point-to-point wiring diagram). Earthing connections were easily made by soldering directly to the tin chassis. Power supply leads were taken through hole D1, which was fitted with a rubber grommet. The replaced lid forming a baseplate, completed the preamplifier. *Note:* If desired a volume control may be incorporated in the unit by substituting a miniature 1M Ω log. potentiometer for R1. This can be mounted vertically in the tin after drilling a suitable hole and can be fitted with a miniature instrument knob.

Preamplifier Power Supplies

The unit appears to be fairly tolerant of power supplies applied to it, though an h.t. supply voltage of between 200 and 300V d.c. is preferable. In the prototype the power supply leads were terminated in an old Mazda octal valve base which took on the role of a supply plug. A similarly wired

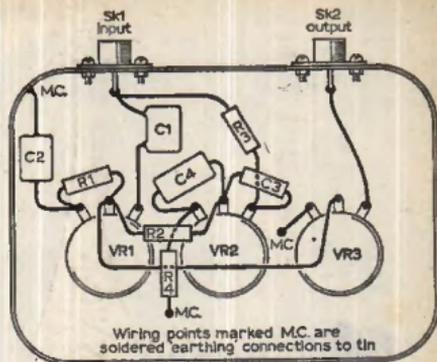


Fig. 6: Tone control wiring and component layout.

matching valveholder was mounted on the main equipment.

Tone Control Box

A very wide range of tone control is available with this circuit (Fig. 4): VR1 provides treble cut and boost; VR2 provides bass cut and boost; VR3 is a volume control. It must, of course, be borne in mind that as with all passive tone control networks there is a considerable insertion loss. However, if the unit is used with the preamplifier already described a fair excess of signal is still available.

As before, a 2oz. tobacco tin was used as a chassis, the lid being temporarily removed to be used as a baseplate later. The drilling details of the tin are given in Fig. 5; holes A, B and C are for the bushes of the vertically mounted potentiometers. (It is recommended that miniature potentiometers be used, otherwise some difficulty may be encountered in fitting all three components into the tin.) There is ample room in the tin for all wiring and components may be supported on the potentiometer and socket connections (see Fig. 6). When complete and with lid replaced the circuit is completely screened; there will therefore be no hum problems.

No difficulty should be experienced in building either of these units even by the newcomer to audio circuitry. ■

PRACTICAL TELEVISION—APRIL

L-C PICOMETER

used with a G.D.O. this instrument enables you to measure small capacitance and inductance values accurately and speedily.

H.T. SHORTS — possible causes and their cures.


FAULTY CHOKES AND TRANSFORMERS — A look at the situations where these are to blame for the trouble.

TV TERMS AND DEFINITIONS

Explaining in simple terms the definitions and phrases peculiar to television.

On sale 24th March 2/-

X
2

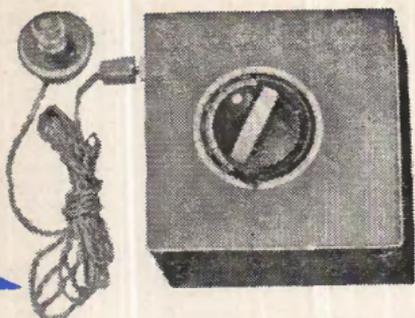

by the reflexed action is well worth while in small receivers.

Now, the audio signal at the junction of R2 L2 is applied to the base of Tr2 through the electrolytic coupling capacitor C4. Tr2 is arranged as a low-level second audio amplifier for working the crystal earpiece. The audio signal is developed across the collector load R5 and is directly coupled to the earpiece via the jack socket, at terminals 1 and 2. Terminal 3 on the jack socket serves as a switch, so that a switch contact in the jack makes when the jack plug is inserted, thereby connecting the battery supply circuit from battery negative to the negative line of the circuit, via jack socket terminals 3 and 1.

Switched Jack

Miniature "switched" jacks are available, but those investigated by the author are arranged so that the switch opens when the earpiece jack is inserted. This action can be reversed, so that the switch closes when the jack plug is inserted, by easing the spring switch contact so that it is above the jack contact (contact 3) which is activated by the plug. Fig. 2 shows at (a) the jack socket in its ordinary state and at (b) the socket with the contact rearranged in the manner described above.

Both transistors run with very small emitter current, and this current is determined by the values of R1 (for Tr1) and R4 (for Tr2). R3 and C3 serve to decouple the two stages and improve the stability margin.

Tr1 is a Mullard AF127, which is a smaller ver-

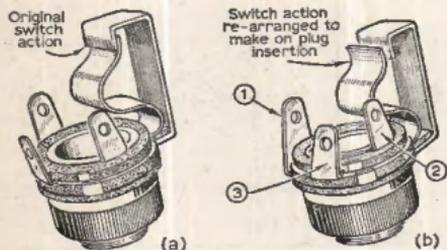


Fig. 2: Modifications for the phone socket.

sion of the AF117. The latter can be used but its larger size takes up most of the room between the tuning gang and the ferrite rod aerial. Tr2 is a medium gain OC71. The diodes D1 and D2 are miniature Mullard OA91's or equivalents. It is important to make sure that they are connected round the right way in the circuit otherwise the sensitivity will be impaired.

The receiver is built on a laminate or bakelite panel of approximately 2½ x 2½ in. Most of the components are secured to the panel and connected in circuit by the use of small eyelets fitted in holes drilled in the panel. In addition to the eyelet holes, the panel carries a ½ in. diameter hole for mounting the tuning gang, two holes for L2 coil former, two holes for the rubber band that fixes around the ferrite rod aerial mounting grommets, two holes for the battery securing rubber band.

Drilling details for the panel are given in Fig. 3, and the holes marked with "Y" are those to accommodate the eyelets, of which there are twenty-four. These holes should be of a size that provides the eyelets with a fairly tight fit, the actual size, however, being determined by the type of eyelet employed. A ready drilled chassis board is available plus twenty-four push-fit eyelets (see components list). A No. 48 drill is used for the former fixing holes of L2, while a ½ in. drill is used for the rubber band holes that are used for securing the ferrite rod grommets and battery.

Fig. 4 shows how the holes in the panel are employed, and this also incorporates a point-to-point wiring diagram. The eyelets, it will be seen, carry the capacitors and resistors on the left-hand side of the panel, also the lead-out wires of Tr1 and Tr2 (the latter in the top left-hand corner) in addition to the two diodes and capacitor C1 (near the ferrite rod aerial). The broken lines on this diagram correspond to point-to-point connections made beneath the panel, while the full-line connections are those made on the top of the panel.

When the holes are drilled in the panel and the eyelets fitted, the next move should be to solder the components to the eyelets, after which the larger components can be more easily fitted. As each component is soldered to the appropriate eyelet the above- or below-panel interconnecting wire or wires should also be soldered. These wire interconnections can either consist of thin, flexible p.v.c. covered stranded wire or about 26 s.w.g. tinned copper wire covered with insulated sleeving. Stranded miniature p.v.c. wire was found to be the best for the job by the author.

The eyelet-connected components on the left-hand side of the panel are mounted vertically, and it is this kind of mounting that enables all the components (of "standard" size) to be accommodated on the board. The idea is to dress one of the lead-out wires from resistor or capacitor back along its length, so that the two ends can then be pushed into the adjacent eyelets. It is a good plan to put a short length of insulated sleeving over the wire running by the side of the component to prevent any possibility of short-circuiting.

A miniature soldering iron will greatly facilitate the various joins and prevent burning the insulated sleeving and components. It is important, though,

continued overleaf

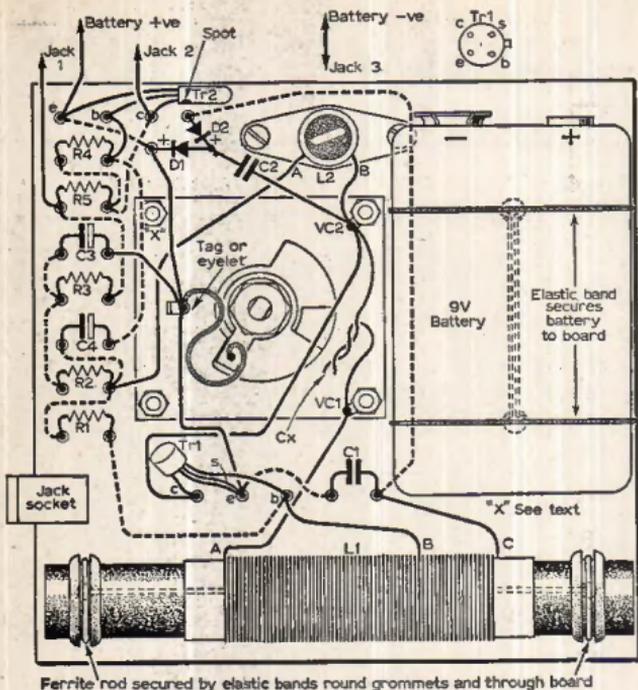


Fig. 4: Component layout and wiring details.

It is best to produce this winding either on a separate former or on the former to be used before it is finally fitted to the panel. The card former can then easily be slid over the former once the latter is in position and screwed down.

The ferrite rod is held clear of the panel by two ¼ in. rubber grommets, one at each end. These are also used for securing the rod a thin rubber band passing round them and through the holes at each side of the panel. A similar rubber band is used to hold the PP3 battery to the panel (see Fig. 3).

Finally, a thin flexible two-conductor lead should be made up for the battery connections, the ends of the conductors terminated in suitable connectors for the PP3 battery and a three-conductor flexible lead should be processed for connecting from the panel at the various

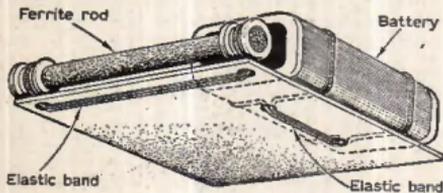


Fig. 5: Method of connecting battery and ferrite rod.

points indicated in Figs. 3 and 4 to the jack socket. Extreme caution should be taken over this latter exercise to ensure that the conductors are terminated to the correct tags or terminals on the jack socket (see Fig. 2). It is also very important, of course, to avoid reversing the battery polarity, for while this may not completely ruin the transistors it could reduce their efficiency and alter their characteristics.

There is sufficient room to accommodate the jack socket between the ferrite rod aerial and R1 (see Fig. 4, for instance), but since the jack socket terminals carry the full negative voltage of the battery, inadvertent contact between one of these terminals and the base end of R1 could immediately destroy Tr1. For this reason, an *insulating sleeve* should be dressed over the terminal end of the jack socket.

Tuning Up

L2 former should be fitted with a dust-iron core and initially this should be adjusted so that it embraces the whole of the winding on the ferrite rod, there should be no difficulty in receiving the local m.w. station. To peak reception on this programme, L2 core should be re-adjusted while slowly turning the tuning gang a little either side of the station for optimum gain.

While it is impossible for a receiver of this kind to track accurately over the whole dial, reasonable tracking is achieved owing mainly to the flat tuning of L2. However, if the set is required to be peaked to a more distant station the station should be tuned as near as possible on the gang and then L2 should be re-adjusted at this new setting for optimum gain.

A degree of feedback occurs in the r.f. stage, especially towards the higher frequency end of the band automatically due to stray capacitance. However increased feedback can be applied simply by flexing a pair of thin, insulated conductors between the two "live" terminals of the tuning gang. This is shown as the "regen coupling" on the circuit (Fig. 1) and the coupling in physical form is clearly shown in Fig. 9. On no account should a d.c. connection exist between the two flexed conductors, for their purpose is simply to provide a small variable capacitance. In the prototype, the five

—continued on page 1081

Modulated Light Telephone

We have experimented with the Modulated Light Telephone Link (February issue) at school and have found results reasonably good although there was a fair amount of background noise and distortion when used outside in daylight.

We discovered that a large lens was better for focusing the light beam onto the photocell than a parabolic reflector. The frequency response at 20ft. went up to nearly 4 kc/s.

I would be interested to know if anybody else tried this and what their results were like.

R. H. Boston.

The Chalet,
Pett Road, Pett,
Hastings,
Sussex.

Copies for Sale

I HAVE the complete copies of PRACTICAL WIRELESS for the years 1959-60-61-62-63-64-65, and if any of your readers are interested I would be willing to dispose of these for a reasonable sum.

All enquiries should be accompanied by a stamped addressed envelope.

W. R. Hebditch.

90 Clarendon Road,
Hove 3,
Sussex.

Who Wants?

OWING to lack of space, I am forced to dispose of an amount of old and new radio chassis and components. Also I have available P.W.'s from January 1961 to March 1965, and a number of various other magazines.

I am willing to give to anyone who cares to call, any of the above items. Sorry, but no letters will be answered.

Nicholas Hansen.

413 Church Road,
Upper Norwood,
London,
S.E.19.

Tapespondent Wanted


I WOULD like to tapespond with anyone of my own age (16) interested in Hi-Fi radio and popular music.

M. K. Beeny.

28 Wheatfields,
St. Ives,
Huntingdon.

NEWS AND.

SINE-SQUARE WAVE GENERATOR

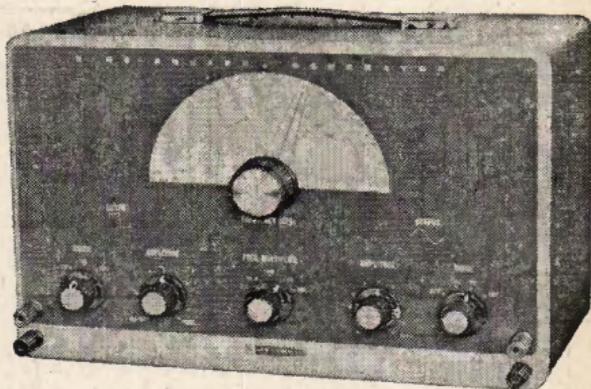

From Heathkit comes the IG-82U sine-square wave generator which has a frequency range of 20c/s to 1Mc/s in 5 bands. Sine and square wave outputs are available separately or simultaneously and there is less than 0.15 μ Sec. rise time on square wave and less than 0.5% distortion on sine wave. Separate output terminals and attenuators permit individual control. In kit form, the price is £24 10s. and assembled and tested £36 10s.

MULLARD MINIBOOKS

"Principles of Electrostatics" is the title of the first in a new series of "minibooks" announced by the Mullard Educational Service.

Based on the successful series of filmstrips and slides produced by the Service, the new books are expected to become popular with both student and teacher.

"Principles of Electrostatics" is a 32-page book measuring 15cm. x 21cm. Its 13 sections each cover a particular aspect of electrostatics. Typical headings are: Insulators and conductors; the electrification theory; the gold leaf electroscope; capacitance and capacitors.

Minibooks are available from The Mullard Educational Service, Mullard Ltd., Mullard House, Torrington Place, London, W.C.1, price 2s. 6d. (including postage), cash with order.

GRUNDIG MANDELLO RESTYLED

Grundig (Great Britain) Ltd. announce that their popular Mandello Stereogram has been restyled to bring it up to date. For those who treasure their discs, the four speed de-luxe record changer incorporates a micro-lift facility. The smart push button radio receives v.h.f., m.w., l.w. and s.w. (band-spread) and can be fitted with a decoder when stereo broadcasts become available.

Two Grundig Superphon ceramic magnet loudspeakers provide 6W of stereo power—3W per channel—and sockets are provided for the connection of extension loudspeakers, stereo decoder, tape recorder and external aerials. The Mandello incorporates a dipole and ferrite aerial, 6 valves, metal rectifier and 2 diodes. Price is 99 guineas including P.T.

.. COMMENT

SILVER MEDAL AWARD FOR MULLARD FILM

The Mullard film, "Thin-film Microcircuits", was awarded a silver medal (1st prize) in its category at the 10th International Festival of Scientific-Teaching Films, organised by the University of Padua in conjunction with the 1965 Venice Film Festival. Over 150 films from 18 countries were entered and of these 52 were selected for showing to the international jury.

Britain did particularly well this year. Seven of the ten films entered were chosen for screening and three gained awards.

"Thin-film Microcircuits" is a 16mm sound and colour film which deals with the manufacture of this new type of electronic component from design stage to the finished product. The film also describes typical applications including space vehicles, miniature computers and industrial electronic equipment.

Another Mullard film, "Electromagnetic Waves—Part 2", won a bronze medal (2nd prize) at Padua last year.

Both of these films were featured at the P.W. and P.T.V. Filmshow on Feb. 4th (see page 1030).

ELECTRONICS GROUP


The St. Cyres Electronics Group are holding a series of meetings in Penarth (Glam.) the first of which was on 14th January, 1966.

By kind permission of Mullard Ltd., this group will be showing a very wide range of technical films which they have issued. As Penarth is only about 5 miles from Cardiff, many readers may be interested in joining the Group and seeing these films.

Further details may be obtained from the organiser, Mr. C. Bogod, "Dickens", 26 Forrest Road, Penarth, Glamorgan.

HAM COMPETITION

An international competition for radio hams is being held in Tenerife. The competition is based on the total number of contacts made during a given period, between operators all over the world and those in Tenerife. Allowance is made for the distances involved. Prizes include a 20-day trip to Tenerife for two people including accommodation in a first-class hotel. Diplomas and Silver Cups will also be awarded.

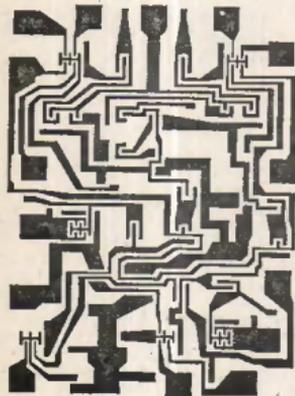

ELECTRIC MODERN ART

Resembling an artistic design of modernistic proportions, this pattern is actually an industrial creation made by electronic engineers at the molecular electronics division of the Westinghouse Corporation in the USA. The pattern is to be reduced thousands of times until it is finally engraved on a piece of silicon of almost microscopic size.

The microminiature will then become an integrated circuit for use in a computer.

Any Ideas Please?

CAN any of your readers suggest a practical design for a simple transistorised audio generator tuning over a range of about 20—200 c.p.s.?

This would be of use in tuning loudspeaker enclosures and would not require a critical waveform output.

F/Lt. G. Halbert.

Officers' Mess,
R.A.F. Lyneham,
Wiltshire.

Frequency Synthesisers

I WAS interested to see in the March issue a description by "Henry" of a piece of apparatus known as a Frequency Synthesiser. He appears, however, to have grasped the wrong end of the wrong stick. As I understand it, and I have used frequency synthesisers, the equipment has nothing to do with diversity reception or multi-channel transmission as Henry would appear to believe.

The frequency synthesiser is a device which combines the stability of a crystal oscillator with the flexibility of a v.f.o. It can give any frequency from 1kc/s to 30Mc/s in 1kc/s steps with an accuracy of ± 2 parts in 10^6 and is normally used by s.w. broadcast stations as the r.f. drive input to a transmitter.

The basis of the synthesiser is a 1kc/s crystal whose harmonics up to 30Mc/s are selected by a triple mixing system to give the required output frequency. It uses about 90 valves and would cost a wealthy ham about £1,500.

J. N. Douglas.

Glasgow, N.W.,
Scotland.

Sell or Loan


Sir, I would be grateful if any reader could sell or loan me...

...ferrite rod aerial for Cosor 524 a.m./f.m. receiver.—T. F. Jones, Flat 2, Block 3, Wychbury Court, Highfields Estate, Halesowen, Birmingham.

...a circuit diagram, and any information (i.e. modern equivalents of valves) etc. of the R1155A and R107 ex Government receivers.—Brian Carling, A4941, 27 Ellis Close, Cottenham, Cambs.

...the circuit diagram of the Sound A20/03858 tape recorder.—N. McFerran, 58 High Street, Newtownards, Co. Down, N. Ireland.

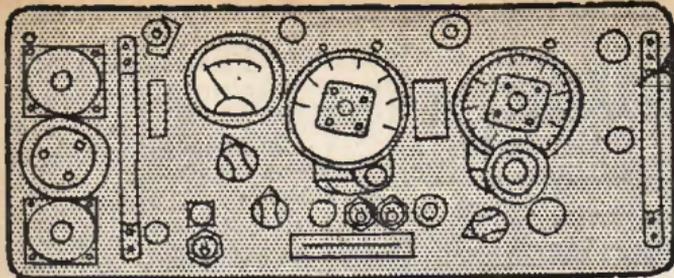...the circuit diagram or service manual for the Air Ministry Oscilloscope type 11 Ref. No. 105/562.—R. E. Fields, 49 Torkington Road, Gatley, Cheshire.



No 19 SET MODS

by S. Simpson

Part 2

Inclusion of output stage

The reader should now have a highly sensitive receiver which, using about 10ft. of aerial, will provide signals all over the 4.5 to 8Mc/s dial. The 2 to 4.5Mc/s band will be relatively quiet at the 2Mc/s end until dusk. One does not always use a headset, however, so the next modification is the provision of loudspeaker output.

- (1) Strip all components and wiring from above and below the v.h.f. end of the chassis, other than the valve sockets and the input plugs. (If desired, the input plugs can eventually be removed and the holes blanked off but, at present, the h.t. and l.t. live leads must be retained for two more checks before the mains power supply is introduced. Take care not to damage the two-gang v.h.f. variable capacitors, to be used later.
- (2) Remove B GAIN and in its place, fit an s.p.s.t. toggle switch (hereafter "LS switch"). Mount the switch horizontally and ensure that ON entails moving the dolly towards the centre of the panel so that it "brings on" the output stage when wanted.
- (3) Check that V8A, pin 8 is earthed. Connect a heater lead from V8A, pin 7 to the ON

contact of the LS switch. Connect the OFF contact of the LS switch to V3A pin 2.

- (4) Make up the circuit for V8A as shown in Fig. 4. The screened, grid-input lead is connected to TS1 tag 4A (already carrying a phone output lead; the lead remains there). The screen is earthed at TS1, tag 3.
- (5) An output transformer was set aside earlier. This should now be fitted adjacent to V8A (Fig. 2). The blue terminal is connected to V8A, pin 3, green to TS1, tag 9, red to one lead of a 10in. length of twin cable, and white to the other lead; white is also earthed.
- (6) Remove the KEY socket; note the required contacts to adapt the KEY socket to serve as a non-self-shortening loudspeaker plug. Connect the twin output lead to these contacts, then refit the socket.
- (7) Fit one of the two 6V6 valves (supplied with W.S.19) to V8A socket. Connect the loudspeaker to the LS plug and insert the plug into the LS (formerly KEY) socket.
- (8) Set up the receiver for phone operation, and when assured signals are being received, set the LS switch to ON. The loudspeaker should operate after the usual warm-up time for V8A. Switch off LS and check the loudspeaker output fades out.

Inclusion of band-spread

The tuning drive on the four-gang capacitor is quite slow, but although satisfactory between 2.5 to about 3.5Mc/s, signals whip through the dial rather swiftly at higher frequencies. A very satisfactory band-spread can be incorporated using existing material, but entails a fair amount of dismantling of the P.A. tuning arrangement.

- (1) Dismantle the P.A. tuning drive as under:—
- (a) Remove the central screw on the FLICK/SET control; remove the knob.
- (b) Remove the four flick pre-set screws from the centre-piece on the P.A. TUNING dial.
- (c) Remove two 4BA screws securing the complete drive and capacitor assembly to the chassis. The assembly should now be loose, but not yet removable.
- (d) Remove one 4BA dome-head screw securing the slow-motion drive assembly to the panel.

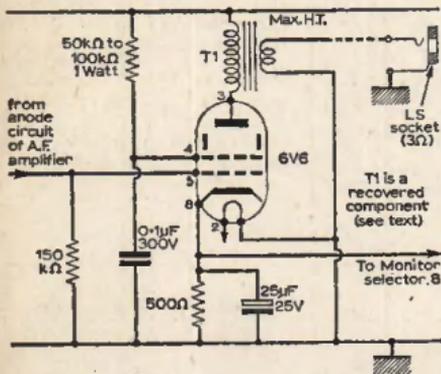


Fig. 4: Output stage, showing monitor point.

EXCLUSIVE TO PRACTICAL WIRELESS READERS

MORE TERRIFIC OFFERS FROM CONCORD!

TRANSISTOR POCKET RADIOS

WITH LOUDSPEAKER



BULK PURCHASE ENABLES US TO MAKE THIS FANTASTIC OFFER

ONLY 28/6

NO MORE TO PAY

etc. Only 4 1/2 x 2 1/4 x 1 1/2 in. Fits easily into your pocket or handbag. Works for months of 12A1 battery. Should last a lifetime. Anyone can assemble it in an hour or two with our easy plan. Miniature speaker — everything only 28/6. 3/6 P. & P. (Parts can be bought separately). Limited supply — rush your order before 3's too late.

IF HAD TO COME EVENTUALLY THE "KEYCRAFTER" PERSONAL COMMUNICATIONS RECEIVER. Highly sensitive. World-wide short-waves reception including news in English and countless other broadcasts from RUSSIA, AMERICA, etc., etc. Take it anywhere — it's featherweight (6in. x 3 1/2in. x 1 1/2in.). Bandspread Tuning. Variable dial. Miniature Valve Circuits. Plug-in Colour Over Red Aerial, etc. 50% of production to be exported. Anyone can assemble it within 2 hours — only a few connections to make — experience unnecessary. Parts Inc. Case, Personal phone. Easy-to-follow plan — 49/6, plus 2/6 Post, etc.

UNIQUE NEW FULLY TRANSISTORISED READY BUILT PORTABLE RADIO



NOW A FRACTION OF THE NORMAL PRICE ONLY 35/-

WHY PAY MORE — All the latest refinements are packed into this new MULTI STATION ALL transistor radio — the internal aerial picks up even remote stations and the powerful built-in speaker gives room filling volume. Individual tuning, first-class reception. Purchase with confidence — packed in original factory cartons. (Personal aerial and battery 4/0). Send 35/- plus 4/6 P. & P.

SAVE YOUR LEGS!



INTERCOM OUTFIT & BABY ALARM

READY BUILT LIMITED QUANTITY SAVE 53-10-6

ONLY 49/6 Robustly made, brand new current models. You get 2 separate, fully transistorised, intercommunicating sets — each can speak or listen to the other — complete with 50ft. connecting wire. Fixed in a flash. Ends baby-crying worries. Ideal for Workshop 12 House, Sickroom, hundreds of uses! Hangs on wall or stands up. Our absurd price 49/6, battery 2/6 extra. Post, etc. 3/6.

MINIATURE SPY CAMERA

Only 12/6 Post 2/6

Offered at a fraction of its Real Worth. Brand new precision made photographic instrument in chrome steel and leather. Two speed shutter, 2 1/2 in. x 3 1/2 in. Easily concealed in Palm-of-hand and takes crystal clear photographs. The rage of America and offered at the absurd price of 12/6, incl. solid leather case — add 6/- for pack of 8 films which give 80 photos. superb craftsmanship in miniature. Send immediately.

CAR CIGARETTE LIGHTER DISPENSER

High Glass Stores sell at 2 gms. — save 22.4d. Top quality chromium. Car cigarette lighter Dispenser. Fixed in a jiffy — Prestige. Butolol delivers 20-cigs! Cigarette into your hand! Takes 10 cigarettes — King size or any size! As fitted to luxury cars. Best foot-proof. 3 1/2 x 4 x 1/2 in. Lifetime tested, ready to use. Refund it not worth 3 gms. 780 only. 18/6 plus 1/6 P. & P. (state 8 or 12v.).

AUTOMATIC POCKET CALCULATOR

Adding and Subtracting up to 999,999 as your finger tips for

ONLY 8/6 plus 1/6 P. & P.

This superb, lightweight calculator is simple to operate yet fantastically accurate. Precision engineered by craftsmen and in a factory tested for reliability. Ideal for use in Offices, Shops, Stores, During Games, etc. Complete with carry case. Slips easily into the jacket pocket or purse. Decimal tables, included for engineers — A terrific bargain that you'll enjoy using.

NEW RADIO NO SOLDERING VOLKSRADIO ANYONE CAN BUILD IN 2-3 HOURS 19/6

EVEN THE OLDER CHILDREN BUILD THEM! ... no soldering — only 16 connections — then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 in. Many Testimonials! M.H. of Bradford, writes: "... I have just completed one of your sets successfully, it is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them..." Direct from Manufacturers to You. Send 19/6 plus 2/6 post, etc.

PARTS AVAILABLE SEPARATELY

MAKE 5 DIFFERENT TRANSISTOR RADIOS



FOR 35/-

NO EXPERIENCE NECESSARY. No soldering. Only 2 connections for first radio to work. Just look, you get Easy ABC Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, 2 Condensers, Resistors, Tuner, Switch, Screws, etc. **YES — EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr R. O'D of Londonderry, writes:—"I received your components and I must say that I am very satisfied with them, I have it already set up!" **"COMPLETE HOME RADIO COURSE,"** originally 86 SEND **ONLY 35/-** plus 3/6 post, etc.

NO SOLDERING AMAZING CIGARETTE RADIO

ONLY 18/6

Yes a perfectly ordinary packet of cigarettes! — but watch your friends' astonishment on hearing it fetch in station after station loud and clear! Still holds 10 cigarettes — yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file. Mr. D. of Huddersfield, writes: "... I have filled the parts in and it is working wonderfully..." **ALL PARTS** including Semi-Conductors, A.B.C. Plans, etc. **ONLY 18/6** plus 2/6 post, etc.

PARTS AVAILABLE SEPARATELY

Read what just a few of our Satisfied customers say

R.C. of Harringay writes Received with thanks Skyrama ... Very pleased. Working well!

B.M. of Harrogate writes ... I would like to thank you ... it was a real bargain.

L.S. of London W.8 writes ... given it a good try out and I am very pleased with the results.

S.B. of Somerset writes ... delighted with this radio ... glad if you could send one more.

T.F. of Stevenage writes ... I would just like to say how pleased my son is with this radio.

MINIY TRANSCIEVER



The latest craze! Push-button operation; crystal circuit. Fully transistor-vised (3-transistor circuit) for perfect reception. Tremendous commercial scope. Complete with strap, battery and 8-section antenna. Uses 9V PP3 battery and operates up to half mile in open country. Measures 8 1/2" x 2 1/2".

9 1/2" x 1 1/2". Frequency 27.125 Mc/s.

ONLY \$6.19.0 Pat. (Post and Insurance 4/8).

More powerful models available.

These sets cannot be operated in U.K.

MINIY PORTABLE TAPE RECORDER Mk. II



Now, a reasonably priced, small portable tape recorder that gives exceptional results.

Precision-engineered throughout. Hand microphones has thumb switch for automatic stop/start/record/playback etc. Ideal sales reports and dictation etc. Tough, unbreakable brown plastic case with deck cover for mobile recordings. Complete with earphone, microphone, tape, two spools, batteries. Size 8 x 7 1/2 x 2 1/2". Usually \$19.9.0


OUR PRICE \$6.15.0.

(Post and Insurance 4/8)

BATTERY/MAINS model. 799-300V. \$7.15.0. (Post and Insurance 4/8).

ELECTRAMA

WINDMILL HILL · HAILSHAM · SUSSEX

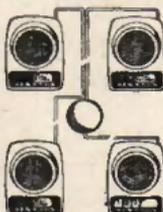

Bargain of the Month Save £7 !!

Benskon 4-way Intercom

Bulk purchase has cut retail price by half! A top quality, fully transistorised system designed for hard office and professional use. Consists of one master unit and three sub-stations with built-in call system. Absolute privacy to each extension. Push-button control. Crystal clear reproduction through 3in. speakers. Suitable desk or wall mounting (size 6 x 4in.). Supplied complete with 50 yards cable, function box, instructions, etc. \$7.10.0 (Post and Insurance 5/1).

CLEARANCE OFFER!

SOLDERING IRONS 250/250V. copper bit and rapid heat element. Ideal printed circuit work 11/8 (Post and Insurance 2/1).

AMPLIFIERS

Two Valve Amplifier for portable gram units. Specification includes volume and tone control with 3-watt undistorted output.

\$6.19.6 (Post and Insurance 3/8).

Linear L 40A. 3-valve amplifier with treble/bass control. Quality reproduction as a realistic performance. \$6.10.0 (Post and Insurance 5/8).

Stereo 3-valve amplifier using 2 UCL82 valves. Mono/stereo control switch with tone control etc. Absolute comp. \$6.12.6 (Post and Insurance 5/8).



WESTROM TELEPHONE AMPLIFIER

You've waited years for this! Just insert PPS battery, plug sensitivity cone to side of phone, and an incoming call is amplified. No need to stop work waiting for numbers to answer! Used with tape recorder (e.g. MINIY, see above), perfect recording of conversation can be made. Ideal field sales reports. ONLY \$9/8 (Post and Insurance 4/1).

TRANSICON 6 RADIO

The very latest 1966 Transicon 6 single waveband with latest PNP circuit. Guaranteed tremendous performance. \$9/8 (Post and Insurance 3/8).

50% SAVING! AUTO RECORD DECKS

Factory-fresh, up-to-the-minute Garrard and B.R.R. decks 200-250V. A.C. Adjustable stylus pressure. Takes mixed record selection. Speeds 78, 45, 33 and 16. Fitted up-and-down, but wired stereo. Limited number only.

GARRARD AUTO-SLIM \$6.19.6.

GARRARD AT6. \$5.15.0.

GARRARD 3,000. \$8.8.0.

B.R.R. UA16. \$4.15.0.

(5/- post and Insurance on each of above)

STEREO CABINETS \$4.10.0 (Post and Insurance 3/1)

Vest Pocket MULTIMETER

Measures A.C./D.C. 0-1000 v., A.C./D.C. 1,000 ohms/V. D.C. current 150 mA. Resistance 100 k ohms. \$9/8 (post and Insurance 2/6)

BATTERY ELIMINATOR

Keeps 6-ft eliminator takes the place of most 9v. batteries. Boorte expanded batteries for re-use. PPS Model 17/6 PPS Model 28/1 (Post and Insurance 3/6).

SPEAKER BARGAINS

Manufactured by famous English company. 10in. high freq. high density, heavy cone model for quality and wide range reproduction. 2 or 15 ohms.

\$9/8 (Post and Insurance 4/1).

15in. specification as above but with built-in Tweeter. 3 or 15 ohms \$9/8 (Post and Insurance 4/6).

RETAIL SHOP

ELECTRAMA, 46 Windmill Hill
RUHSLEP. Tel. 5780

THE
PEMBRIDGE
COLLEGE
OF ELECTRONICS
PROVIDES TRAINING
IN RADIO
AND TELEVISION

FULL-TIME COLLEGE COURSE
IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 19th April, 1966.

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:

The Pembridge College of Electronics (Dept. P11)
34a Hereford Road, London, W.2.

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____

(Note that there is a stout leaf spring holding the slow motion spindle against the edge of the engraved dial.) Remove the drive assembly.

- (e) Loosen the grub-screw in the side of the dial centre-piece; it should now be possible to separate the dial from the flick-stop assembly; this will expose a small tapered pin which passes through the collar of the flick-stop stub-flange and the capacitor shaft. This collar (not the pin) is required for the modification and the pin must therefore be removed. (Note that the pin is fairly soft and easily burred. One way of removing it is to cut away the tapered end with a hacksaw and punch out the remainder.)
- (f) Summing up the results: One should have available the slow motion drive and attaching 4BA dome-head screw, the engraved dial riveted to a metal disc to which the centre-piece is attached by one 4BA dome-head screw, the collar and stub-flange removed from the capacitor shaft. At this stage it is advisable to prepare a new dial to replace the existing engraved plate, which can be removed by withdrawing the 4BA screw from the centre-piece and drilling out the four small rivets securing the plate to the metal disc. In the author's version a circular disc of thin card and of the same diameter as the engraved plate was marked with 30 equidistant divisions around one semicircle and Letraset numerals 1, 5, 10, 15, 20, 25 and 30 attached at the relevant divisions. The centre of the card was removed to almost the diameter of the underside of the centre-piece, then the card disc was secured to the metal disc, using Cowgum. The centre-piece was then refitted to the metal disc to complete the dial assembly.
- (2) Earlier the reader removed the v.h.f. two-gang capacitor mounting plate. This assembly is now used as the bandspreader. Fit the collar to the capacitor shaft and insert the collar through the panel aperture formerly occupied by P.A. TUNING; leave the mounting plate as it stands for the moment.
- (3) Fit the dial to the collar (note the flat on the collar which mates with the dial). Fit the slow-motion drive to loosely mate with the dial.
- (4) By trial assess what shimming is necessary between the bandspreader mounting plate and the receiver chassis to obtain adequate slow-motion drive on the dial. Also check for positioning of the capacitor for all-round smooth drive. Mark the chassis, remove the capacitor assembly, drill and tap the chassis (there is no

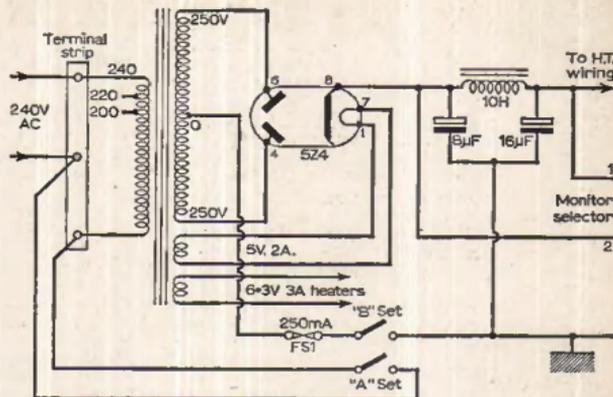


Fig. 5: Power supply circuit, showing monitor points and h.t. control.

access for nuts under the chassis), then fit the complete assembly.

- (5) Set the dial to 30 opposite the right-hand index mark. Fully enmesh the capacitor vanes, then lock the capacitor shaft, using the grub-screw accessible in the stub-flange.
- (6) Strap both sets of fixed vanes and leave approximately 10in. tail on the lead.
- (7) At the four-gang capacitor unsolder and remove the compression trimmer at OSC (marked on top of the capacitor plate). Pass the band-spreader tail through the trimmer hole, assess and cut the length to reach the rear connection, i.e. to the fixed vanes. Withdraw the lead, prepare and heavily tin about $\frac{1}{2}$ in. of the tail, reinsert the lead and solder it to the rear tag.
- (8) Set up and check the receiver to try out the bandspreader. Note that it has little effect around 2-3Mc/s but is extremely useful at higher frequencies, drawing "attention" to dozens of c.w. signals usually unnoticed without band-spreading.

Inclusion of Power Supply

The reader, running through this article as "something to read", may wonder why a mains power supply has been left so late; the reason lies in the weight of the W.S.19, even as found, and the lifting and turning necessary during the preceding changes. If a power supply were added as an early step the work of the succeeding steps would be quite laborious. To add the power supply proceed as follows:

- (1) Obtain a top-of-chassis mains transformer to supply about 250V at 50mA, 6.3V at 3-0A, 5V at 2A, also a smoothing choke giving about 10H at 50mA. A smoothing capacitor assembly providing 8µF and 16µF at 300V working, a 5Z4 rectifier and a three-way tag-board complete the components list.
- (2) The circuit diagram is standard and given in Fig. 5. The locations of the components are shown in Figs. 1 and 2.

- (3) The mains input lead terminates on the three-way tagboard (if possible attached to the choke) which will carry a flat-twin mains lead to the A SET switch.
- (4) Dismantle the two-way switch assembly to gain access to A SET and B SET switches.
- (5) Cut the existing lead on A SET passing into the W.S.19 power input plug cableform. Parallel-connect the freed contact on A SET and its neighbour at that end. Add one wire of the flat-twin mains lead (sub-paragraph 3) to the parallel connection.
- (6) Remove the l.t. connection at the other end of the switch, parallel the two tags at that end and add the remaining wire of the mains lead.
- (7) Ensure that all l.t. leads (less that passing into the W.S.19 power supply cableform) which were associated with the A SET l.t. connection are still in good contact. Fit a short length of sleeving over the common connection and tuck safely away.
- (8) At the B SET switch remove the lead passing into the W.S.19 power supply cableform, cut the lead short at the power input plug. On the B SET remove the lead supplying h.t. to the circuitry and connect it to the tail from the smoothing choke (see Fig. 5). Connect the contact on B SET, just cleared, to chassis. Connect the contact which carried the W.S.19 h.t. lead to the centre tap of the h.t. winding on the mains transformer. The B SET switch now provides means of disconnecting h.t. while the heaters remain active.
- (9) At the remote end of the mains supply cable check for continuity between leads with A SET "on" and open-circuit with A SET "off". Check for open-circuit to chassis with A SET in both positions.
- (10) Connect a voltmeter (to read 300V) between the smoothing choke output and chassis.
- (11) Ensure A SET is switched off and l.s. is also off. Connect the mains supply cable to a power outlet. Switch on A SET and B SET, and note that the valve heaters are alight.

Watch for the developing h.t. in the voltmeter. Switch off A SET.

- (12) Plug in the headset, turn up A GAIN and R.F. GAIN. Connect the aerial and switch on A SET. Check the receiver functions normally, then turn down A GAIN to minimum and check for hum on the h.t. supply. If all is well switch off; if hum is present make the usual checks of capacitors, leaking cathode insulation and so on.
- (13) Fuses. If it is desired to fit fuses a panel fuse to carry h.t. can be installed in the QUENCH aperture and another may be fitted in the rear wall of the chassis to carry mains input. The h.t. fuse should be connected in the earth return from the h.t. winding of the mains transformer (Fig. 5). Suitable fuses would be 250mA (h.t.) and 2A (mains).

Monitoring system

The inclusion of a monitoring system is a fairly simple task but, in a complex receiver, an addition well worth having. The system involves a nine-way single-pole wafer switch instead of the existing five-way double-pole component and uses the existing meter. The monitor system is shown in Fig. 6.

- (1) Remove the panel meter and clamp assembly held by one 4BA screw passing through an eyelet on the clamp.
- (2) Remove the clamp from the meter by loosening an 8BA screw at the top of the clamp.
- (3) Using a 10,000 Ω series resistor check the meter on a 1.5V supply for continuity. If satisfactory proceed to step 4 and then to step 7. If the meter is faulty continue as follows (these instructions are based on the author's findings on a faulty meter and the fault may be common in these meters, now several years old).
- (4) Withdraw three small screws from the side of the meter case, withdraw the meter from the case and ensure the needle is free to move.


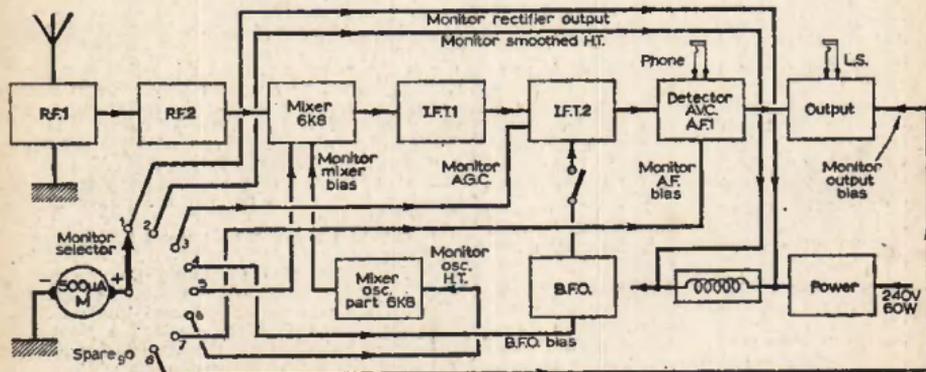


Fig. 6: Monitoring system in modified W.S.19 receiver.

8 tips for practical soldering

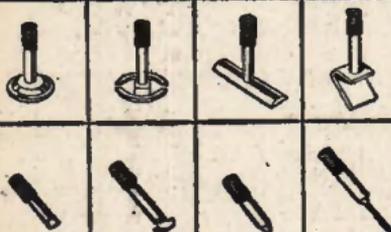

NEW!

The Instant Heat
Soldering Kit complete with
tips, extension barrel, probe and solder.
Complete £3 19 8
Ask for a demonstration from your local
dealer or fill in the coupon below for full
details.

Form 7/66



SG 1225 KIT

Name

Address

.....

BURGESS PRODUCTS CO. LTD.
SAPCOTE, LEICESTER.

Tel: Sapcote 292 Telex: 84549

SLEEP LEARNING EQUIPMENT

(as featured on Page No. 754 January issue)

14 day Swiss movement Time switch—suitable for any tape recorder £4-5-0. P. & P. 5/-

Under Pillow Speaker £1.7-6. P. & P. 2/6

Complete outfit including Tape Recorder, time switch with microphone, underpillow speaker and pre-recorded conditioning tape. £26-10-0. P. & P. 10/-

Send S.A.E. for full details of the sleep learning method—the modern way to learn.

P.W. REFLEX 2 TRANSISTOR RECEIVER



All components available from R.C.S.
8 gang tuners, 5/6; Chassis and speakers, 2/6 or
Chassis with speakers fitted, 3/6; Case, ready
drilled with knob and dial, 4/-; Ferrite rod,
former, wire and grommets, 3/6 or Aerial and
former ready wound, 5/-; B.P. choke, former
slug and wire, 5/-; All diodes and transistors,
14/-; All resistors and condensers, 5/-; Dial and
earpiece and socket, 5/-; P. & P. 1/6.

Mains POWER PACKS

The ideal economical and safe way of running any Transistor Radio, Record Player, Tape Recorder, Amplifier, etc. from A.C. Mains with complete safety.

The MAJOR "Power Plus" for 9v; 6v; 4v; 3v;
Single Output. P. & P. 2/6
For 9v; + 9v; 6v; - 6v;
4v; ± 4v. Two separate
outputs. P. & P. 2/6
Pleasant static outputs required.
All "Power Plus" units are com-
pletely isolated from mains by
double wound transformer ensur-
ing 100% safety.

39/6

42/6

The BIJOU "Power Plus". For the smaller set using PP3 type battery. Supplied complete with special adaptor enabling you to re-activate your existing PP3 type bat-
tery. P. & P. 2/6.

P. & P. 2/6.


R.C.S. PRODUCTS (RADIO) LTD.

11 Oliver Rd., London, E.17. (Mail Order only)

Export Trade Enquiries Invited

GUITAR AMPLIFIERS with TREMOLO

12 months' guarantee (valves 3 months)

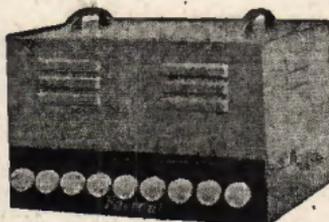

Five jack socket inputs with four separate mixing volume controls. High gain of 16 millivolts makes it suitable for all types of guitars and micro-phones. Separate Bass and Treble controls. Master gain control. Tremolo speed and depth controls. Remote tremolo switch socket. 7.5 and 15 ohm output, 30 and 60 watt valves

BOOKER, BOOKER, EL34, EL34, 6X4. 15 watt valves BOOKER, BOOKER, EL34, EL34. Two extra valves BOOKER used in the tremolo circuit. Tremolo operates on one input only. Black and gold trim panel fitted tremolo type only at present; Chassis finished silver grey hammer. Cover with chrome handles 54/- extra.

PRICES

50 watt with tremolo	£21.17.6	STOP PRESS	150 watt with tremolo	£34.17.6
50 watt less tremolo	£18.10.0		100 watt less tremolo	£24.18.0
20 watt with tremolo	£14.17.6			
20 watt less tremolo	£11.10.0			
15 watt with tremolo	£13.17.6			
15 watt less tremolo	£11.10.0			

Add carriage 16/- any amplifier. Credit terms arranged. Descriptive leaflet free, stamp appreciated. Suitable speakers, Bakers 15" Guitar L.S. 6 ga. Bakers 15" Group 50 L.S. 18 ga. Carriage free.

Cash with order only, request to C.O.D.

"No trade or export"

STROUD AUDIO

CASHEE GREEN ROAD, STROUD, GLOS. STROUD 768.

- (5) Again check for continuity but this time across the movement lead-in connections, i.e. close to the hairspring. If no reading is obtained check, using a lens, for broken connections. If there are no breaks the coil is damaged beyond amateur repair.
- (6) If a reading is obtained when the movement is checked at the lead-in connections look for a minute break at the termination of a small coil on top of a resistor attached to one input terminal. (The break is probably caused by wire, hardened by age and subjected to fairly severe vibration during service life.) Resolder the connection and check the meter from the external terminals.
- (7) Remove the existing dial. Prepare a new dial numbered one to ten and attach it to the existing dial (as was done with the bandspreader dial). Refit the modified dial to the meter.
- (8) Reassemble the meter and put it aside meantime.
- (9) Cut all wiring to the monitor switch. Remove the switch.
- (10) Fit a nine-way single-pole switch in place of the removed monitor switch. (Space is limited, therefore the diameter of the new switch must not exceed 1½ in.)
- (11) Obtain about 15 in. (at least) of nine-way multicore cable, preferably having leads of different colours. Strip the outer sleeve (and screen if any), then prepare ½ in. tinned connections at one end of the cable. Pass the untreated tail of the cable through one of the two eyeletted holes adjacent to the bandspreader capacitor.
- (12) Turn the monitor switch knob fully counter-clockwise and locate contact 1, also the wiper contact. To contact 1 solder one tinned lead of the cable. Follow on with the remainder of the cableform, noting on a monitor schedule the colour of each lead and its relevant contact on the monitor switch.
- (13) When all leads have been attached to the switch contacts solder a 3 in. lead to the switch wiper.
- (14) Refit the meter. Earth the negative terminal. To the positive terminal connect the switch wiper lead.

The selection of monitored points is, perhaps, something for the reader to decide since views on this subject are many. The author suggests the following as being very useful (reasons are given against the less obvious points):

- (1) Main h.t. at rectifier cathode.
- (2) Main h.t. at choke output. If a fault changes the h.t. current demand noticeably this is shown by a change in the known difference between the cathode voltage and the correct value of choke output voltage.
- (3) Automatic volume control (measured by its effect on cathode bias of V1C. This setting provides visual tuning control and indication of signal amplitude but only on R.T.)
- (4) Beat-frequency oscillator cathode bias. (If no b.f.o. note can be obtained this setting provides a quick check on (a) the presence of h.t.

at the valve, (b) whether or not the valve is oscillating. In case (a) there is no bias reading, in case (b) the reading is above normal.)

- (5) Frequency-changer bias. (If the oscillator section of the 6K8 fails the bias reading is slightly, but noticeably, greater than when the oscillator is normal. Two conditions are noted in the monitor schedule: (a) Normal operation at 4.5Mc/s, (b) bias with the oscillator dead.)
- (6) Frequency-changer oscillator h.t.
- (7) First a.f. amplifier cathode bias.
- (8) Output stage cathode bias.
- (9) In the author's receiver this position is used to monitor the +28V supply to a teleprinter used in conjunction with the receiver.

All of the above are shown in Fig. 6. Whichever circuits are chosen the value of resistor to be connected between the monitor point and the cableform lead can be found from the Ohm's Law formula:

$$R = E/I \text{ where } R \text{ is in megohms, } E \text{ in volts, and } I \text{ is a fixed value, } 250 \text{ (this is the half-scale reading of the monitor meter).}$$

For example, supposing one wants to monitor a 10V cathode bias point,

$$R = 10/250 = 0.04M\Omega = 40k\Omega.$$

Since the readings need not necessarily be exactly half-scale any value between (say) 37k Ω and 44k Ω should be satisfactory.

Two points which should have the same resistor value, however, are the rectifier cathode h.t. and the choke output h.t., the reason being that one requires a comparison of meter readings to show the voltage drop across the resistor in the h.t. supply.

When all wiring has been completed in the monitoring system the cableform should be laced with button thread to tidy off. The receiver should then be run up and allowed ten minutes or so for temperature stabilisation, then the various readings taken down on the monitor schedule, which should be attached to the receiver, or filed for reference.

The inclusion of a monitoring system completes the series of modifications carried out by the author. If no snags have been encountered and the original receiver was in reasonable condition to begin with the reader should now possess a receiver whose performance in the 2 to 8Mc/s band is the equal of many very much more expensive receivers. If he has had experience in alignment of receivers he may be able to improve this high performance still further by slight co-ordinated adjustment of the four compression trimmers situated in the area to the rear of the waveband switch. (The fifth trimmer, near the panel, alters beat frequency and should be left alone.) If he has no realignment experience leave these four trimmers to someone with the necessary knowledge to adjust them.

Ensure all superfluous wiring and wire clippings are cleared out of the chassis and that new wiring, components, etc., will be clear of the inner base when fitted. Drill the outer case to pass the mains cable (and provide access to the mains fuse if fitted), then fit the receiver into its outer case to complete the job. ■

A MIC PREAMP

A high-gain unit using
a single transistor

by A. E. J. Simons

PREAMPLIFIER PERFORMANCE 250V H.T.

Voltage gain	320
Current consumption	0.7mA
Output impedance	5k Ω
Input impedance	200 Ω

THIS high-gain preamplifier is suitable for use with a succeeding valve amplifier. The normal 250V h.t. line will supply the requirements of the OC70 Mullard transistor via resistors R4 and R5. Having no hum or microphony and a voltage gain of over 300 the preamplifier is suitable for a low-impedance microphone or pick-up.

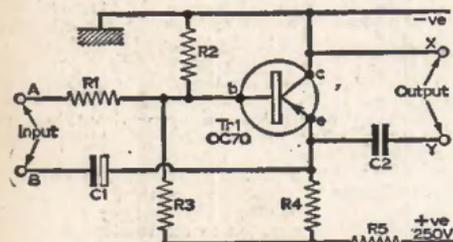


Fig. 1: The single-transistor circuit of the unit.

The writer has used the preamplifier as a second microphone input to an existing valve amplifier with excellent results. The output of the pre-amplifier was connected to the gramophone pick-up sockets; the gramophone volume control thus became the second microphone gain control. Being only 3in. x 1½in. x ¼in. in size, the unit fits easily into a tape recorder, care being taken to keep the transistor away from components which run hot, i.e. valves and smoothing resistors.

COMPONENTS LIST

R1 100 Ω	C1 100 μ F 12V
R2 100k Ω	C2 0.1 μ F 150V
R3 470k Ω	Tr1 Mullard OC70
R4 5-6k Ω	
R5 330k Ω	

All resistors ¼W 5% high-stability.

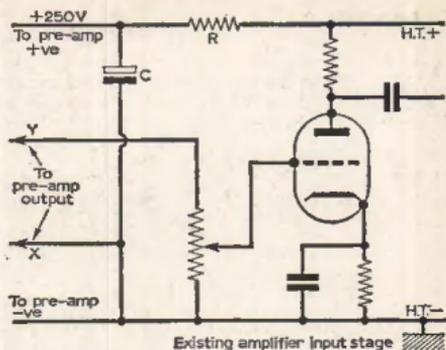


Fig. 2: The arrangement of a valve amplifier input stage for connection of the preamp. R has a value to regulate the amplifier h.t. to 250V for the preamp. C = 8 μ F 350V.

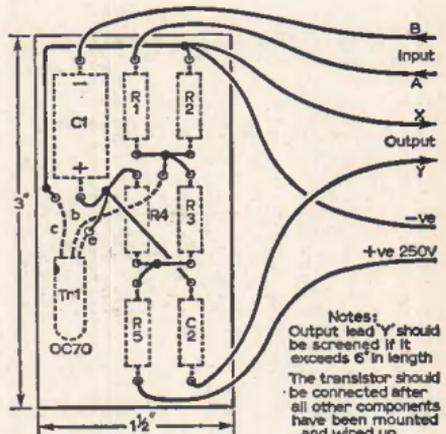


Fig. 3: Construction of the unit is on a piece of paxolin and the above layout was used successfully by the author.

Construction

The preamplifier can be built on a paxolin strip 3in. x 1½in. The strip should be drilled to take the wire ends of the components, which are twisted together behind the strip and soldered—shown by heavy dots in Fig. 3. Input, h.t. and output connections are made with flying leads.

Before connecting to the h.t. supply check the polarity of the preamplifier. Successful operation has been obtained with an h.t. supply of between 150-260V. Should the valve amplifier h.t. be in excess of 260V it can be reduced to a safe level as shown in Fig. 2. This also shows the method of coupling the preamplifier to the valve amplifier.


Exclusive to Practical Wireless Readers

PRIVILEGE PRICE BOOK OFFER

PRACTICAL WIRELESS

Radio and Television Reference Data

COMPILED BY
J. P. HAWKER

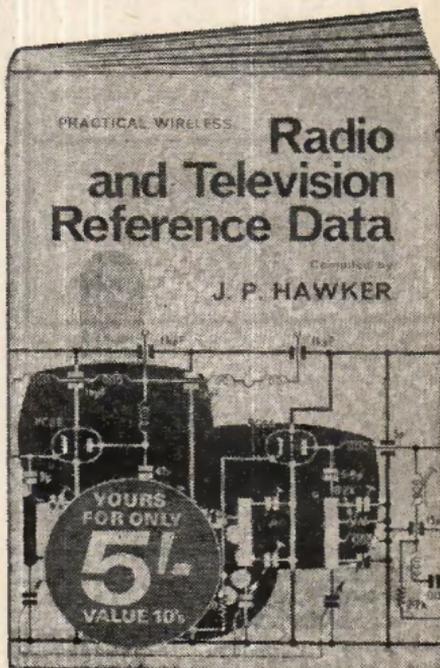

Packed with practical data covering the whole field of radio and television, this invaluable book provides an essential reference source for every amateur constructor and experimenter. Take this unique opportunity now of obtaining this reference book at the privilege price offer of 5/- (value 10/6).

96 PAGES of Factual Tabulated Data, with sections on:

Colour Codes · Formulae · Aerials · Frequency and Wavelength · Broadcasting Allocations · Station Frequencies · Television Standards · Symbols; Abbreviations · Amateur Radio · Useful Constants · Amateur Radio Prefixes · I.F. List for Communications · Receivers · Mathematical Data · Wire and Cable Data · Valve, Picture-Tube, Battery and Transistor Data.

TO ORDER

Please complete the coupon, using block capitals, and enclose remittance for 5/- (Cheques and Postal Orders should be made payable to George Newnes Limited, and crossed.). Name and address must be written on back of cheques. Send your order to: PRACTICAL WIRELESS BOOK OFFER, Carlton House, Great Queen Street, W.C.99. Closing date 30th April, 1966. We regret that this offer is not available to Eire and Overseas.

PW

APRIL 1966

NAME _____

ADDRESS _____

IF UNDELIVERED PLEASE RETURN TO GEORGE NEWNES LTD.,
136 LONG ACRE, LONDON, W.C.2.


**ACT
NOW!
SEND
THIS
FORM
TODAY!**

KITS WITH A FUTURE


The Martin Audiokit assembly you own today can become part of an even better hi-fi system tomorrow. No other system allows you to enlarge your installation stage by stage in the way Audiokits do. They comprise a wide range of very well made prefabricated units in which the connections are standardised throughout. Each is rigorously tested to stated specification before despatch. **NEW KITS FOR ADDING ON ARE IN COURSE OF PREPARATION NOW**—so by starting with Martin today, you insure yourself for still better listening tomorrow.

Choose Martin for quality

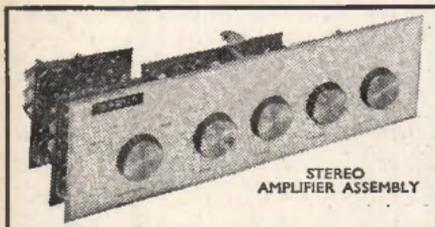- Build for 3 or 15 ohm system
- Start with Mono and add Stereo or start completely with Stereo
- Power packs available
- Professionally styled escutcheon plates
- Assembly is easy by following the well presented instructions.



STEREO
AMPLIFIER ASSEMBLY

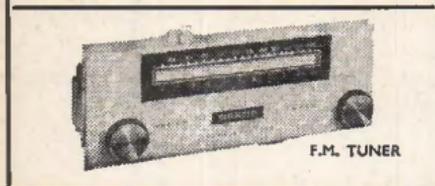

F.M. TUNER

- 5 stage input Selector £2.76
- Pre-amp. and vol. control £1.17.6
- Pre-amp. with tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0

Send for leaflet describing entire range

MARTIN Audiokits

Martin Audiokits and Recordkits are obtainable from good stockists everywhere. In case of difficulty please write direct.

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD, M'SEX

Phone: ISLeworth 1161/2

MARTIN ELECTRONICS LTD. 154-155 High Street
Brentford Middlesex

Full details of Martin Audiokits please

NAME _____

ADDRESS _____

(Block letters)

PW.4

TWO-YEAR GUARANTEED TUBES

14 in. 59/6

17 in. 79/6

21 in. and all
Slimline
Tubes 99/6



100% REGUNNED
Add 10/- or old tube.
110/-30/- or old tube.
Carr. 10/6. 14in. Slim-
line 17 & 19 in. —
overseas postage 30/-.


EX-MAINTENANCE TESTED TUBES

17in.—35/- Most makes and types available. 14in.—15/-
Guaranteed good picture. Carriage 5/- extra.

EX-RENTAL TELEVISIONS

14 in. 17 in.
£7.10.0 £11.10.0

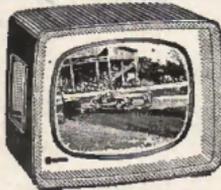12 months' 3 star Guarantee
*Tube-k Valve-k Components
COLOURED FREE LIST
Channels for all areas
Demonstrations daily from Large
Selection.
Personal collection or Insured
Carr. 14in. 20/-; 17in. 30/-.



TWO-YEAR GUARANTEE

On all our slimline TV's send for free list.

Record player
cabinets 49/6.
Largest design
covered cabinet
takes any modern
autodiaper.
Single player
cabinets 19/6.
P. & P. 5/6.

VALVES £1 per 100. Assorted TV and Radio.
Surplus ex-rental dismantled receivers. Post 4/6.
Send for list.
CONDENSERS, 10/- per 100. New Assorted Electro-
lytic and p.p.s. P. & P. 2/6.
RESISTORS, 6/- per 100. New. Mostly High Specs.
Assorted. P. & P. 3/6. Overseas 5/6.
BREAKERS, 7/6. 6in., 8in., 7 x 4in., 8 x 3in. Mk.2nd.
Balvage. P. & P. 2/6. Overseas, 4/-.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12
Liverpool St.—Manor Pk.—10 mins.
Phone: ILFord 600-1-2-3. Stamp for Free List.



For quick, easy faultless soldering

Ersin Multicore 5-core solder is easy to use and economical. It contains 5 cores of non-corrosive flux, cleaning instantly heavily oxidised surfaces. No extra flux is required. Ersin Multicore Savbit Alloy considerably reduces the wear of copper soldering iron bits.



HANDY SOLDER DISPENSER

12 ft. of 18 s.w.g. SAVBIT alloy in a continuous coil, used direct from free-standing dispenser. 2/6 each



LOW TEMPERATURE SOLDER

Size 9 pack contains 24 ft. of 60/40 tin quality 23 s.w.g. 2/6 each
Size 10 pack 212 ft. 15/- each.



SAVBIT SIZE 1 GARTON

Contains approx. 30ft. of 18 s.w.g. SAVBIT alloy. Also available in 14 and 16 s.w.g. 5/- each



BIB WIRE STRIPPER AND CUTTER

Strips insulation, cuts wire cleanly. Adjusts to any size. 4/- each


Available from all Electrical and Hardware shops.

If unobtainable write to:

MULTICORE SOLDERS LTD.

Multicore Works, Hemel Hempstead, Herts. Hemel Hempstead 3696
M.4/3

An ELECTRONIC GATE OR TRACE DOUBLER

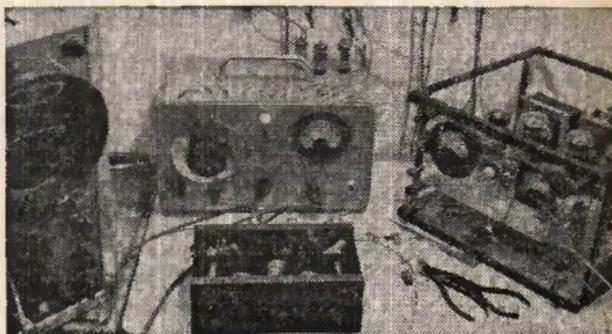

FOR SINGLE BEAM OSCILLOSCOPES

H. T. Kitchen

THE majority of oscilloscopes used by the majority of amateurs have one characteristic in common, the inability of displaying two separate signals as two separate and distinct waveforms on their cathode ray tubes at the same time. They are, in other words, single beam oscilloscopes.

Now it is quite probable that many amateurs will never need, or want to, view two different signals simultaneously, whilst others, like myself, will only need to do so from time to time. Undoubtedly the easiest way of doing so is by using a double beam oscilloscope, though this type of instrument, due to its high cost, can almost certainly be regarded as an unjustifiable luxury in all but a few exceptional cases. We must not, however, overlook the amateur who has either bought or constructed a first-class single beam oscilloscope for, having spent a goodly portion of his hard-earned income upon it, he will not exactly be overjoyed at having to start again.

Fortunately it is not unduly difficult to obtain

double beam operation from a single beam oscilloscope, though not, unhappily, with the same facility as would be obtained from a genuine double beam instrument. This is brought about by the use of a special electronic gate into which the two signals are fed simultaneously. The gate then allows each signal to be passed turnabout to the oscilloscope, suppressing in the meantime the signal that is not being passed, the net result being two separate waveforms corresponding to the two separate signals.

Gate Principles

The principle of the electronic gate is quite simple and is illustrated in Fig. 1. It comprises two amplifiers for the Y1 and Y2 signals and a gate generator which provides two gating signals, these being square waves of identical frequency but out of phase by 180°. These are also fed into the Y1 and Y2 amplifiers and alternately allow them to conduct and then drive them into cut-off.

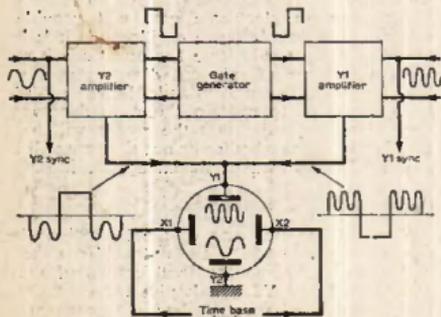


Fig. 1: Diagram showing operation of the electronic gate.

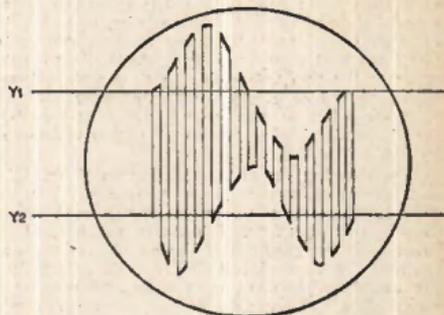


Fig. 2: The effect of a slow gating speed. The Y1-Y2 waveforms are composed of positive and negative peaks of the gating waveform.

Being in anti-phase it follows that when the Y1 amplifier is conducting, the Y2 will be cut off and vice versa, so that the c.r.t. is presented with a sequence of "samples" which, if the gating waveform is of the correct frequency, gives the impression of two separate traces. If the oscilloscope timebase is adjusted to display the gating waveform the Y1 and Y2 signals will be seen to occupy the horizontal portions of the square waves' positive and negative peaks. This effect, which is shown in Fig. 1 and also in Fig. 2, is only shown to explain how the gating waveform provides two separate traces. In actual use the timebase will be used to display the input signals only and the gating waveform will not be visible except under certain circumstances. These will occur when a fairly slow gating speed is used and the input signals will be seen to consist of a series of dots or dashes, depending on actual frequency, which are really the positive and negative peaks of the gating waveform. At high gating speeds it is possible for the intervening spaces to be rendered luminous by the gating waveform and occasionally for the waveform to be faintly discernible. With practice it is possible to ignore both effects and concentrate only on the waveforms to be examined.

With a double beam oscilloscope each trace has its own vertical shift control and so can be positioned just where it is wanted. The two traces can be superimposed, transposed or one removed right off the screen. With an electronic gate, however, the two traces will move as one every time the oscilloscope's vertical shift control is operated. The superimposition and transposition facilities can, however, be retained, though neither trace can be removed off the screen without going to some, and usually unnecessary, trouble anyway. The gating waveform, as already explained, is a square wave which is fed into the two amplifiers out of phase by 180°. If the gains of the two amplifiers are exactly equal the two anti-phase signals will cancel out and in the absence of any Y1 or Y2 signals will show on the oscilloscope as a straight line. Where Y1 and Y2 signals are present they will be superimposed, occupying, as they do, a common baseline. Although this may suffice for some applications it is an unsatisfactory way of doing things, for there is every possibility of the superimposed traces causing misunderstandings and mistakes. It is desirable to either separate the two traces so that they are no longer superimposed or else to make one much brighter than the other or even to make the best of both worlds by combining them and neither objective is particularly difficult to achieve.

It was earlier stated that if the two Y amplifiers had equal gains the gating square wave would cancel out and the oscilloscope would simply display a straight line. It must be understood that since both the gating and the external signals are fed into the Y amplifiers this remark will apply to the gating waveform's gain only and not to the signal gain. If the gain of the two amplifiers to the gating waveform is made unequal the output will be a square wave and it will be possible to separate the two external signals. This is done most easily and conveniently by varying the bias

SPECIFICATION

Power Supply Required:

250V at 20mA
6.3V C.T. at 1.2A

Y Amplifiers:

Freq. Response: 15c/s—50kc/s ± 1 dB
10c/s—200kc/s ± 3 dB

Input Impedance: 1M Ω

Gain: x5

Gate Generator:

Fixed frequencies of 50c/s, 175c/s, 500c/s, 1750c/s, 5000c/s approx.

Gate Output: 85V P-P (anodes of V1)

Gating Transients: 11V P-P (cathodes of V2 V2)

Note 1

All static voltages except multi: V1 measured with VRI at mid position and with S1 at "off" position using 250V and 10V ranges of 20k Ω /V meter.

Note 2

Gain and frequency response of Y1 Y2 amps measured separately with VRI at mid position and gate at "off".

on the gating stages, so causing unequal anode currents to flow in the common anode load resistor, thereby providing the required unequal outputs. It is customary to label the top trace the Y1 and the lower the Y2 trace and to label the input sockets accordingly, thereby making it possible to identify the two signals.

It is also possible to make one trace more or less brilliant than the other by varying the mark space ratio of the gating square wave. The two traces will be equally brilliant when the gating waveform has a mark space ratio of one to one. If the mark space ratio is altered the two traces will differ in brilliance since one waveform, the more brilliant of the two, will be allowed to remain longer on the cathode ray tube than the dimmer trace which will have been allowed the least time. In practice the mark space ratio can be altered by providing the multivibrator with unequal grid leak resistors or by making the cross-coupling capacitors unequal in value. It is not usually possible to alter the mark space ratio to any great extent without adversely affecting the waveform.

Although an electronic gate will provide the services of a double beam oscilloscope it is by no means a perfect substitute for one since it suffers from a number of inherent disadvantages which limit its scope (no pun intended!) and usefulness. It is proposed to explain these disadvantages in some detail in order that the reader will be in a position to judge whether or not the gate will be of any use for his own particular applications.

Limitations

Strangely enough one of the limitations is the oscilloscope into which the output from the gate will be fed. This output will consist of the two external Y1 and Y2 signals plus the gating square wave which has been described, with perhaps some justification, as the carrier wave. Now one of the properties of a square wave is its ability (unwanted

LEARN ELECTRONICS

—AS YOU BUILD

over **40** **CIRCUITS**
EXPERIMENTS
TEST GEAR

including . . .

● CATHODE RAY OSCILLOSCOPE

- | | |
|--------------------------------|--------------------------|
| ● Valve Experiments | ● Square Wave Generator |
| ● Transistor Experiments | ● Morse Code Oscillator |
| ● Electro-magnetic Experiments | ● Simple Transmitter |
| ● Basic Amplifier | ● Electronic Switch |
| ● Basic Oscillator | ● Photo-electric Circuit |
| ● Basic Rectifier | ● Basic Computer Circuit |
| ● Signal Tracer | ● Basic Radio Receiver |
| ● Simple Counter | ● A.C. Experiments |
| ● Time Delay Circuit | ● D.C. Experiments |



The full equipment supplied comprises valves, transistors, photo-tube, modern type chassis board, printed circuit board, full range resistors, capacitors and inductors, transformers, potentiometers, switches, transistors, valves, all hardware, wiring and every detail required for all practical work plus CATHODE RAY OSCILLOSCOPE for demonstrating results of all experiments carried out. All practical work fully described in comprehensive PRACTICAL MANUALS. Tutor service and advice if needed.

This complete practical course will teach you all the basic principles of electronics by carrying out experiments and building operational apparatus. You will learn how to recognise and handle all types of modern components; their symbols and how to read a completed circuit or schematic diagram. The course then shows how all the basic electronic circuits are constructed and used, and HOW THEY ACTUALLY WORK BY USING THE OSCILLOSCOPE PROVIDED. An application is given in all the main fields of electronics, i.e. Radio; control circuits; computers and automation; photoelectrics; counters, etc., and rules and procedure for fault finding and servicing of all types of electronic equipment.

● NO PREVIOUS KNOWLEDGE NEEDED
● SENT IN ATTRACTIVE BOX

● NO MATHS USED OR NEEDED
● COMPLETE ADVICE SERVICE

● REASONABLE FEE—NO EXTRAS REQUIRED
● EVERYTHING REMAINS YOUR OWN PROPERTY

A completely **NEW** up-to-date
home study experimental
course by
**BRITISH NATIONAL
RADIO SCHOOL** —
Britain's Leading Electronic
Training Organisation.

POST NOW FOR FREE BROCHURE

To BRITISH NATIONAL RADIO SCHOOL, READING, BERKSHIRE Please send
free Brochure, without obligation, to

NAME


ADDRESS

Block Capitals Please

OR WRITE IF YOU PREFER NOT TO CUT COUPON

PW 4.66

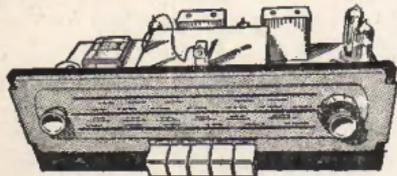BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £15.15.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 144 x 4 1/2 in. in 2 colours, predominantly cream. 900-250V. A.C. only. Pick-up. Ext. Speakers. A.C., B., and Dipole Sockets. Five push-buttons—L.W., M.W., S.W. FM and Gram. Aligned and tested. G.P. Transformer. Tone control. 1600-1800 Mc.; 900-250 Mc.; 85-98 Mcs. 6-17 mfd. E250 rect.; ROHSL, EF89, EAB300, EL84, EOC85, 3-ohm speaker required. 9 x 6 in. ELLIPTICAL SPEAKER BR. 80% to purchasers of this chassis. TERMS: (Chassis) £8.10.0 down and 6 monthly payments of £2.65. Cheap Room Dipole for V.H.F. 12/6. Feeder 6d per yard. Total R.F. price £16.14.0 Circuit diagram 3/6. Carriage to N. Ireland 30/- extra.

NEW 6 PUSH-BUTTON STEREOGRAM CHASSIS M.W.; S.W.1; S.W.2; V.H.F.; Gram; Stereo Grams. Two separate channels for Stereo Grams with balance control. Also operates with two speakers on Radio. Chassis size 15 x 7 x 6 1/2 in. high. Dial cream and red. 15 x 5 in. Valves EOC85, ROHSL, EF89, 3 x ECL86, EL84 and Silicon Rect. Price £17.10.0, carr. paid or £4.0.0 deposit and 6 monthly payments of 60/-, Total R.F. price £18.0.0. Crown moulded enclosures for dial. 7/6 extra.

BATTERY ELIMINATOR

For 4 low consumption valves (96 range) 90v. 15mA and 1.4v. 125 mA, 42/6 (6/- post), 200-250V. A.C. Also for 250v. 15v. and 90v. 15mA at same price. Two units each 2 1/2 x 3 1/2 x 1 1/2 in.

SELF-POWERED VHF TUNER CHASSIS

Covering 80-95 Mc/s. Dims. 8 x 6 x 6 in. high. Valves EOC85, EAB300 and 3-EP89's with metal feedback. Mains transformer. Fully wired and tested ONLY £21.7.8 (carr. paid). Room Dipole 12/6. Feeder 6d. per yard.



100 WATT AMPLIFIER AND SPEAKER SYSTEM FOR COMPLETE GROUP

- * Separate High and Low frequency channels of 50 watts each. Each channel having 4 jack-inputs with 3 volume controls plus bass and treble controls.
- * Amplifier unit contains 12 valves, 6 per channel in four gain stages with pre-amp and push-pull output. 20mV sensitivity, frequency response 30-20,000 c/s. Item level -70dB.
- * Two speaker columns each with 3 x 15in. speakers for High frequency and a bass cabinet housing 4 x 15in. speakers for Low frequency. RA and PA speakers used with total rating 140 watts.
- * Housed in four acoustically designed and styled covered cabinets.

FERMINOMIAL VALUE AT Carr. Free 89 Gns.

* A really Hi-Fi de luxe system with tremolo on HI channel, using all Goodmans speakers is available at 159 Gns. Carr. Free

WE ALSO OFFER FULLY TRANSISTORISED

All units sell contained with 9V battery, Carr. Free.

PRE-AMP—49/6

Variable high gain unit with single jack input, jack output suitable for guitars, microphones, gram, tape, etc.

MIXER-UNIT/PRE-AMP—115/6

Four jack inputs, single jack output using five transistors with four independent volume controls, suitable for many applications. The Ultimate for group microphone mixing.

TREMOLO UNIT—84/6

Two jack inputs, having speed, volume and depth controls with provision for foot-switch operation.

D.A.B. Electronic Consultants
2 Albany Road, Holbury, Southampton.

The SUPER 6 LONG & MEDIUM WAVE TRANSISTOR RADIO



A quality radio available as a kit or ready-built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12.12.0 commercial model.

* All new parts. * 6 transistors and diode. * 950mV output. * Superhet circuit. * Ferrite rod aerial. * Weymouth Radio printed circuit board. * Component positions and references printed on back of board. * Nicely styled wood grain cabinet, 11 x 7 1/2 x 3 1/2 in. * Vinyl covered in various colours. * 8 x 4 in. speaker gives good bass and treble response. * Full instruction booklet, 2/-. Free with kit. * I.F. frequency 470 kc/s. * Lining up service if required. * All parts supplied separately. Write for list, S.A.E. PLUS 6/- POST. COMPLETE KIT ONLY £4.00 OR FULLY BUILT 60.7.6. Fax & Carr. Paid

8 WATT PUSH-PULL O.P. AMPLIFIER £5.5.0 (6/- Carr.)

200-240 A.C. mains. Bass, treble and vol. controls. EF89, EF85 and 2-EL84's. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-3 ohm speaker. Front panel normally screwed to chassis may be removed and used as flying panel. With Cream/Black control panel whole length of front chassis.



GLADSTONE RADIO 66 ELSM ROAD, ALDERSHOT, Hants.

(3 mins. from Gosport and Bournemouth). Aldershot 22040
CLOSED WEDNESDAY AFTERNOON
CATALOGUE 6d.
Regret overseas orders cannot be executed



The PUNCH
you need!

HOLE PUNCHES

Instant Type	diameter	Type	6/10 ea
1/2"	1/2"	Screw-up	Toggle switch	8/6 "
1/2"	1/2"	"	"	8/6 "
1/2"	1/2"	"	B7G	9/- "
1/2"	1/2"	"	B8A, B9A	9/6 "
1/2"	1/2"	"	"	10/8 "
1/2"	1/2"	"	"	10/8 "
1/2"	1/2"	"	"	10/8 "
1/2"	1/2"	"	"	10/8 "
1/2"	1/2"	"	Inc. Octal	13/4 "
1/2"	1/2"	"	"	16/2 "
1/2"	1/2"	"	"	18/10 "
1/2"	1/2"	"	B9G	21/8 "
1/2"	1/2"	"	"	24/4 "
1/2"	1/2"	"	Meter	33/2 "

Complete Set 9.3.6.

No extra charge for postage and packing in the U.K.

Now supplied by

TOMPKINS & LONGMAN LTD.

237 GIPSY ROAD

WEST NORWOOD, S.E.27

Tel. Gipsy Hill 5000

4-STATION INTERCOM



£7/15/0

Solve your communication problems with this new 4-Station Transistor Intercom (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9V battery. On/off switch. Volume control. Complete with 8 connecting wires, each 90ft. and other accessories. P. & P. 4/6.

INTERCOM/BABY ALARM



Usually 50/-

Our Price ONLY

57/6

Modernise business or home with this new two-way Transistor Intercom, consisting of Master and Sub, in strong plastic cabinets, with chromium stands. Designed as a two-way instant communication system—call/talk/listen. Operates on one 9V battery. Complete with 80 ft. wire. Battery 2/6. P. & P. 2/6.

TELEPHONE AMPLIFIER 69/6



Telephone Amplifier with Rotary Calendar and Push-Button. Take down long telephone messages or converse without holding the handset. A status symbol? Yes, but very useful one. On/off switch. Volume Control. Operates on one 9V battery (supplied). P. & P. 3/6. Full money refunded if not satisfied in 7 days. WEST LONDON DIRECT SUPPLIES (PW/1) 6 CHIGHELL PLACE, WEST BALSINGHAM, LONDON W15

in this particular application) to reveal the characteristics of the equipment through which it has been passed. Sagging or sloping tops will denote a phase advance due to a poor low-frequency response, whereas rounded corners will denote a phase lag caused by a poor high-frequency response. In really bad cases the emergent waveform will bear very little resemblance to the ingoing one. It will therefore be evident that for successful operation of the gate the oscilloscope's Y amplifier must pass the gating square wave without distorting it, at least to any excessive extent. If it is unable to do so the output from the gate will have to be fed directly to the cathode ray tube's Y1 plate, in which case some alteration to the deflection circuitry will probably be necessary. Where the oscilloscope's vertical amplifier uses symmetrical or push-pull deflection it will be necessary to earth the Y2 plate (capacitively if there is any z.f. voltage on it) and to feed the gate to the Y1 plate only. Due to the variety of deflection circuits in common use more explicit directions cannot be given, though it can be said that additional amplification before and after the gate will probably be necessary and will be due to the very small gain afforded by the Y1 and Y2 amplifiers plus their inability to deliver the very high peak-to-peak voltages necessary to fill the working area of the c.r.t.. It must be emphasised that these modifications will only be necessary with very simple oscilloscopes with restricted vertical bandwidths and it is quite possible for the gate to work, at least reasonably well, with the majority of amateur oscilloscopes. It is safe to say that if the oscilloscope can reproduce the gating square wave with reasonably vertical sides, square shoulders and reasonably horizontal positive and negative

peaks that it will work well with the gate.

Yet another limitation is the gating speed. In theory it should be half the timebase speed so that each waveform can be traced out in turn. In practice surprisingly good results can be obtained with very widely varying gating/timebase speeds. Some authorities recommend a low gating speed, others a high speed. My own experience is that very slow gating speeds cause the waveform to sparkle in a rather fascinating way which causes eyestrain rather more rapidly, whilst very high gating speeds cause the space between the Y1 and Y2 waveforms to be rendered luminous. Of the two the latter effect is preferable to the slow speed sparkling, but since individual preferences vary and since it is desirable to work at half the timebase speed whenever possible the gating waveform is made variable in frequency.

Bandwidth

The last disadvantage to be covered is that of bandwidth. By the very nature of its operation the bandwidth that can be covered is restricted to the audio and low radio frequencies and is due to the inability of the simple gating circuit used to generate the ideal square wave necessary to bring about satisfactory gating at high frequencies. It will nevertheless satisfactorily handle 200kc/s since waves as shown in the waveform diagrams for which purpose the two inputs were temporarily connected in parallel. The distortion evident was present in the input signal which was derived from a transistorised "Nombrex" signal generator. This shows that in spite of the remarks concerning the recommended gating to timebase speed ratio of 2:1 (or 1:2) acceptable results can be obtained

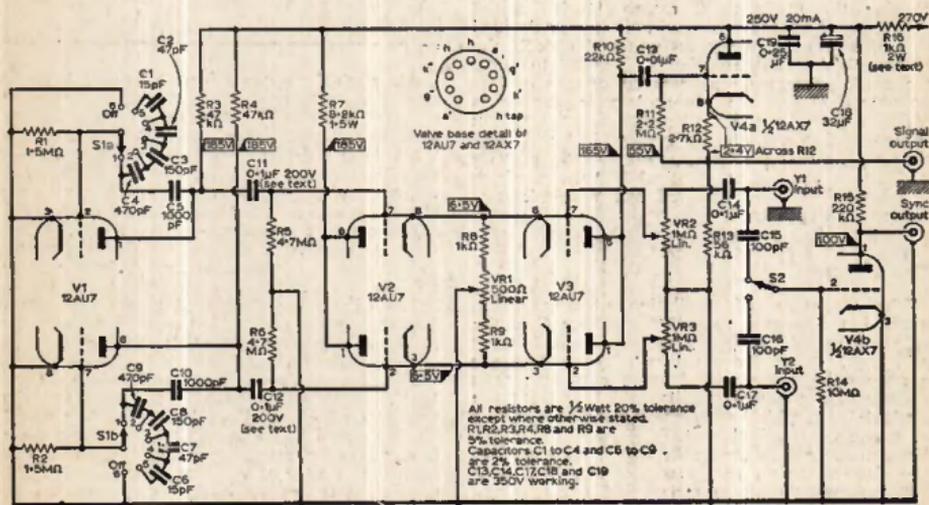


Fig. 3: Complete circuit of the trace doubler.

with widely differing ratios, for the gating speed used in this case was 1,750c/s. Although my own tests ceased at 200kc/s it is not unreasonable to suppose that even higher frequencies could be handled, though the signal gain would be well down when compared to the reference frequency of 1k/c. These remarks apply to sinewaves, the square wave response deteriorating after about 25kc/s, after which considerable rounding off occurs. The waveform diagram shows a square wave with a frequency of 25kc/s as generated Y1 trace and as reproduced at 1W output by a 10W amplifier on the Y2 trace. The rise time of the square wave was 2-0 μ S (the oscilloscope shows this as absolutely square, no rounding off, overshoot or sag) and as the Y1 trace is still reasonably square the performance of the gate as a whole can be considered to be eminently satisfactory—for all but the most exacting requirements anyway.

The complete circuit of Fig. 3 will be seen to be quite simple when split into its individual stages, which will be considered in turn commencing with the gate generator V1. This is connected as a cross-coupled multivibrator, the traditional form of square wave generator. Although the cathode coupled multi is somewhat simpler and cheaper to build the necessity of providing two anti-phase outputs precluded its use in favour of the cross-coupled variety. The variation in the gating speeds is brought about by S1a and S1b, which selects two sets of five close-tolerance (2%) frequency determining capacitors, C1 to C5 and C6 to C10. Two methods of discriminating between the two Y1 and Y2 traces have already been considered. It will be remembered that one method was offsetting the two traces so that they lay one above the other and the other method was making one trace brighter than the other by altering the mark space ratio. During initial development of the gating circuit it was decided that offsetting the two traces was undoubtedly the best method and it was thereby decided to make the mark space ratio as near to one to one as possible. Hence the close-tolerance capacitors which also confer another benefit upon the circuit. In conjunction with close tolerance (5%) grid leaks they ensure that no two positions of S1 provide oscillations at or near identical frequency, which could possibly have occurred had wide-tolerance components been used.

Time Constants

The frequency of oscillation of a multi is approximately equal to $0.77/CR$ where C is the value of one of the coupling capacitors and R the grid leak. Since large values of capacitors are correspondingly larger and more expensive than smaller ones the two grid leaks R1 and R2 are made 1.5M Ω , which means that the largest value of capacitor required is 1,000pF, for $f_0=50c/s$. For convenience in wiring the capacitors are wired in series so that the next capacitor value is 300pF (1,000pF and 470pF in series) and $f_0=1,700c/s$. The frequency therefore changes in five steps of 3-1 and makes it possible to select a gating speed most appropriate to the timebase speed within quite wide limits.

COMPONENTS LIST

Resistors:

All 20% 1W except where stated.	
R1 1.5M Ω 5%	R9 1k Ω 5%
R2 1.5M Ω 5%	R10 22k Ω
R3 47k Ω 5%	R11 2.2M Ω
R4 47k Ω 5%	R12 2.7k Ω
R5 4.7M Ω	R13 55k Ω
R6 4.7M Ω	R14 10M Ω
R7 8.2k Ω 1.5W	R15 220k Ω
R8 1k Ω 5%	R16 1k Ω 2W see text

Potentiometers:

VR1 500 Ω lin.	VR2 1M Ω lin.
VR3 1M Ω lin.	

Capacitors:

2% silver mica except where stated.	
C1 15pF 2%	C6 15pF 2%
C2 47pF 2%	C7 47pF 2%
C3 150pF 2%	C8 150pF 2%
C4 470pF 2%	C9 470pF 2%
C5 1000pF ceramic	C10 1000pF ceramic
C11 0.1 μ F 200V paper. See text.	
C12 0.1 μ F 200V paper. See text	
C13 0.01 μ F 350V paper	
C14 0.1 μ F 350V paper	
C15 100pF ceramic	
C16 100pF ceramic	
C17 0.1 μ F 350V paper	
C18 32 μ F 350V electrolytic	
C19 0.25 μ F 350V paper	

Valves:

V1, V2, V3 12AU7	V4 12AX7
------------------	----------

Valveholders:

4 89A

Switches:

S1 2 pole, 6 way, rotary
S2 1 pole, 2 way, miniature slide

Sockets:

4 co-ax.

Although the outputs from V1 could have been applied directly to the Y1 and Y2 amplifiers' V3, it was considered desirable to incorporate a cathode follower buffer stage V2 between V1 and V3. The gating waveforms are therefore developed across R7, VR1, R8, the cathode loads which are also common to V3, and V3 is therefore allowed to conduct and driven into cut-off, the two halves working in anti-phase. VR1 varies the bias voltages, increasing one as the other is decreased, so bringing about trace separation in the manner already described. The outputs from the two halves of V3 are developed across the common load resistor R9 and are fed via C13 to the cathode follower output stage V4a. It had originally been intended to use direct coupling until the voltage on the anodes of V3 was measured and found to be 165V. This would have necessitated a cathode voltage on V4a of about 170V, which it was felt was liable to put somewhat of a strain on the heater-to-cathode insulation of V4a. The output from the cathode of V4a was connected directly to the output socket without the customary coupling capacitor simply because the oscilloscope contains its own z.f. isolating capacitor and it was felt that two such capacitors in series were quite unnecessary.

EXPRESS ELECTRONICS

32 SOUTH END, CROYDON, SURREY
Telephone: Croydon 9186

FOR THE FOLLOWING BRAND NEW UNITS

AMPLIFIERS AND TUNERS

TRIPLETONE HI-FI MAJOR ...	12 watt ...	£15.18.6
TRIPLETONE CONVERTIBLE ...	5 watt ...	£6.19.6
TRIPLETONE GEMINI STEREO ...	5 watt ...	£15.15.0
TRIPLETONE FM TUNER	£15.14.6
LINEAR ...	3 watt ...	£6. 6.0
LINEAR DIATONIC ...	12 watt ...	£12.12.0
LINEAR CONCHORD ...	30 watt ...	£16.16.0
LEAK TL12 ...	14 watt ...	£18.18.0
LEAK VARILOPE PRE-AMP	£15.15.0
LEAK TL50	£33.12.0
LEAK TROUGH LINE 3 FM TUNER ...	50 watt ...	£31.14.6
QUAD ...	15 watt ...	£22. 1.0
QUAD STEREO/MONO PRE-AMP	£25. 0.0

LOUDSPEAKERS

GOODMANS AXIETTE 8in. ...	6 watt ...	£5. 5.0
GOODMANS AXIOM 10in. ...	10 watt ...	£6. 6.0
GOODMANS AXIOM 20i ...	15 watt ...	£10.15.0

BAKERS 'SELHURST' 3 or 15 ohm

STALWART 12in. ...	15 watt ...	£5. 5.0
BASS GUITAR 12in. 'Group 25' ...	25 watt ...	£5. 5.0
BASS GUITAR 'Group 35' ...	35 watt ...	£8.18.6
BASS GUITAR 'Group 50' ...	50 watt ...	£18.18.0
STANDARD Heavy Duty 12in. ...	20 watt ...	£7. 7.0
BASS Heavy Duty 12in. ...	25 watt ...	£12.12.0
AUDITORIUM 15 ...	35 watt ...	£18.18.0

RECORD PLAYERS

GARRARD MODEL 1000 4-speed MONO	£6.19.6
GARRARD MODEL 2000 MONO	£7.15.0
GARRARD MODEL 3000 STEREO	£10.10.0
GARRARD MODEL 401	£29.10.0
GARRARD MODEL LAB80	£24.10.0
GARRARD AT6 TRANSCRIPTION MONO	£9.17.6
GARRARD MODEL AT60	£11.15.0
GARRARD MODEL AT70	£19.10.0
GARRARD SRP 10	£4.19.6

Delivered free U.K. S.A.E. enquiries.


NEW FROM PITMAN**Telecommunication Principles**

R. N. Renton

One might have thought that a book on principles could have remained unchanged and valid indefinitely, but such has been the pace of developments in telecommunication during the last decade or two that a revised edition of this standard work was thought necessary. The biggest single change is a new chapter dealing with semi-conductor devices (Theory and Application). In addition the book deals with properties of new magnetic and dielectric materials (including square-loop materials and ferrites). The revised City and Guilds Syllabuses are fully covered and recent questions have been added to ensure that this textbook retains its high reputation for easy comprehension and accuracy.

New third edition 50s. net

from all booksellers Pitman Parker St. London

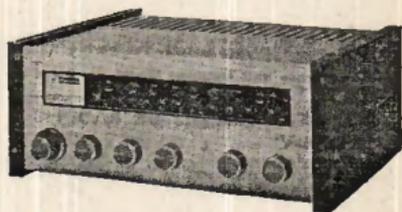HIGH QUALITY**LOWER COST**

Combine an Armstrong Tuner and Amplifier and you have all the advantages of separate units, plus compactness, easier installation, and equivalent performance at a lower price.

Stereo model 127, above, derived from the more expensive 227, has an identical AM-FM tuner section, with an amplifier section designed for those whose power requirements are more modest. It has a more modest price too, as does the mono version model 127M.

Each Armstrong Tuner-Amplifier is ideal as the basis of a high fidelity system for radio and record reproduction, tape recording, and playback, and each unit may be built into your own cabinet or used in our optional case, of teak and vinyl hide, as shown.

For full details and technical specifications of all models plus list of over 300 stockists, post coupon or write mentioning 4PW66.

model 127 STEREO TUNER AMPLIFIER £37.10.0

model 127M MONO TUNER AMPLIFIER £26.10.0

optional case £3.10.0

AUDIO FAIR. ENQUIRY ROOM 539
BOOTH 45 DEMONSTRATION ROOM 537



Armstrong

ARMSTRONG AUDIO LTD-WARLTERS ROAD-N.7
Telephone: NORTH 3213

Name _____

Address _____

4PW66

WIRECOMP ELECTRONICS

TRANSISTOR POCKET RADIOS

Ideal Gifts—all supplied complete with personal earpiece, battery and carrying case. Fully guaranteed. Post Free.

BOY'S 2 TRANSISTOR MODEL (Illustrated)
In attractive plastic case. Size only 4 x 2 1/2 x 1 in.
2in. speaker. Uses PP3 battery. Tunable over full medium
full medium waveband. 39/6

BOY'S 4 TRANSISTOR MODEL 45/-

6 TRANSISTOR MODELS
In plastic case. 4 x 2 1/2 x 1 in. with 2in. speaker.
Uses PP3 type battery. Tunable over full medium
waveband. 59/6

3 Waveband (Long and Medium) Model size 5 x 3 1/2 x 1 in.;
crazoo/black plastic case. 89/6

FAMOUS MAKE TRANSISTOR RADIO THE "STELLA"

7 transistor portable radio. Long, Med. and Short wavebands. Titled tone switch and sockets for personal earphone and external aerial; chrome telescopic aerial. Uses four 1.5 v. torch batteries. Plastic cabinet in beige and red. Size 4 x 7 x 1 1/4 in. Excellent tone. 3in. p.m. speaker. Comp. with shoulder strap and external aerial. Full guarantee. List price 17 Gns.

WIRECOMP'S PRICE **£8.19.6** P. & P. 5/-

WONDERFUL BARGAIN FROM RUSSIA THE "SOKOL"

7 transistor radio covering full Medium and Long wavebands with exclusive rechargeable battery which can be recharged from any 110/250 v. A.C. mains supply. Can also operate on PP3 type dry battery. High quality P.M. speaker. Ivory and black plastic case with metal trim—size 6 x 3 1/2 x 1 1/4 in. Sockets for external aerial and earpiece. Complete with real leather case, dry battery, rechargeable battery and charger, personal earpiece.

WIRECOMP'S PRICE **£6.9.6** P. & P. 2/6

323 EDGWARE RD., LONDON, W.2. ABMssador 7115

All Branches open all day Saturday. Early closing Thursday

WIRECOMP'S SALE! WIRECOMP'S SALE! WIRECOMP'S SALE!

THIS MONTH ONLY AT ALL
OUR BRANCHES

48 Tottenham Court Road, W.1
323 Edgware Road, W.2
378 Harrow Road, W.9

Fantastic Reductions on Thousands of lines—

Transistor Radios — Record Players — Tape Recorders
Radiograms — Amplifiers — Tuners — Components
Chassis — Speakers — Microphones etc. etc.

DON'T MISS IT

INTERNATIONAL BRAND TAPE—Fully Guaranteed

MYLAR BASE	ACETATE BASE	3/6
3in. Triple play, 600ft.	15/-	3in.—120ft.
4in. Triple play, 600ft.	17/6	3in.—225ft. 4/11
5in. Double play, 1,200ft.	18/-	3in.—300ft. 7/6
5in. Triple play, 1,800ft.	35/-	5in. Long play, 900ft.
5in. Double play, 1,800ft.	22/6	5in. Long play, 1,200ft. 12/6
5in. Triple play, 2,400ft.	45/-	7in. Stand. play, 1,800ft. 10/-
7in. Stand. play, 1,800ft.	19/6	7in. Long play, 1,800ft. 15/-
7in. Long play, 1,800ft.	19/6	P.V.C. BASE
7in. Double play, 2,400ft.	25/-	5in. Stand. play, 600ft. 8/6
7in. Triple play, 3,600ft.	58/6	8in. Stand. play, 840ft. 11/6
		P. & P. 1/- extra per reel, 5 reels and over Post Free.

378 HARROW RD., LONDON, W.9. CUNningham 9530

Mail Orders to the above address for prompt service

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explaining the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE.

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £28 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY

(Dept. 344B), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME
LETTERS AFTER
YOUR NAME!

A.E.I. Mech. E.
A.N.I.C.E.
A.E.I. Prod. E.
A.N.I.M.I.
A.I.O.R.
E.S.
A.W.I.E.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics Etc., A.M.I.E.R.E., City & Guilds
Radio Amateur's Exam B.T.E.B. Certificate F.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Microcircuit Engineering
Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training of some with practical equipment. Ask for details

B.I.E.T.
SCHOOL OF
ELECTRONICS



POST COUPON NOW!

- Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)
- NAME
- ADDRESS
- SUBJECT OR EXAM THAT INTERESTS ME..... 344B

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

TRACE DOUBLER

—continued from page 1078

V4b is arranged as the sync amplifying and limiting stage, more as a matter of wiring convenience than electrical necessity. The provision of a suitable sync signal is rather more involved than would be apparent at first. During the gate's early stages trouble was experienced with synchronising the trace using the internal sync position of the oscilloscope. A certain amount of jitter plus a reluctance of the trace to stay synchronised was finally put down to the gating waveform, the frequency stability of which is not

particularly good. The sharp leading edge of its square wave, however, synchronised the oscilloscope's timebase much better than a sine wave input having a much higher frequency stability, with the result that the sync tended to "wander" with the gating waveform. Once this was realised the sync signal was extracted before being gated and was fed into the oscilloscope, switched for external sync, with the result that jitter was absent and the timebase stayed synchronised to the input signal. S2 allows either the Y1 or the Y2 signal to synchronise the timebase.

CONTINUED NEXT MONTH

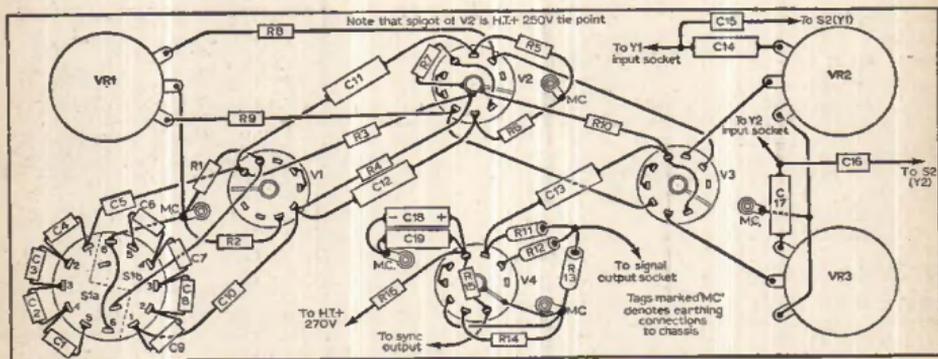


Fig. 4: Chassis wiring. The centre spigot of V2 is used as an h.t.+ point.

Reflex 2

—continued from page 1059

twists on this coupling were sufficient to put the r.f. amplifier in oscillation over the entire band. It was found that just a single twist is sufficient for most purposes, depending upon the nature of Tr1.

Capacitor C1 in the tuned circuit of L1 constitutes a form of padding capacitor, as well as serving as an r.f. bypass. Thus, the tracking can be influenced by varying the value of this component. Unfortunately, there is not available a miniature preset capacitor of sufficiently high value to permit easy adjustment here. The author found that an 0.005 μ F fixed capacitor satisfied the tracking for his reception area, but values above or below this could be tried since C1 is not difficult to change.

It is as well to remember that a simple set of this kind employing a sub-miniature ferrite rod aerial and only two transistors cannot be claimed to have super-sensitivity! Nevertheless, the prototype gave good volume on local stations, while after dark the more powerful European stations were received.

Housing the Receiver

The complete receiver is fitted in a small ready drilled plastic case as shown in the photograph which comes with back, tuning knob and paper

dial. The gang retaining nut being used to lock the assembly to the front panel and a hole in the side of the box to cater for the jack socket which, again, is held secure by its locking nut. The long 6BA bolt on the rear of the tuning gang is used to hold the back of the case in position.

The battery will have many months of useful life provided the carpiece jack plug is removed from the socket when the set is not in use.

PRACTICAL WIRELESS BINDERS

The Practical Wireless Easi-binder is designed to hold normally 12 issues. Please state volume number required otherwise a blank cover will be sent.

A new version of the Easi-binder with a special pocket for storing blueprints and data sheets is now available. The price is 11/6d inclusive of postage.

Order your binder from: Binding Department, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

OSCILLATOR CIRCUITRY

R. Leyland

2—DESIGN OF TRANSISTOR OSCILLATORS

WHEN average transistors are used at low voltages two transistors will probably be necessary as a minimum in a resistance-capacitance oscillator. An advantage of the two amplifying stages as compared with a single transistor is that positive feedback can be obtained directly without resorting to the 180° phase shift of a ladder network. Simpler forms of network can therefore be used which have zero phase shift at the frequency of oscillation.

Wien Network

The most widely used of these is the Wien network (Fig. 3a), which has several less familiar variations, including current duals. The output from these networks reaches a peak equal to one-third of the input at the frequency where the phase shift becomes zero. With the surplus of amplification usually available the oscillator can be stabilised by an appreciable amount of negative feedback applied to reduce the loop gain to unity.

On subtracting the output of a Wien or similar network from its input to give the inverse response, i.e. by taking the new output from the other part of the network, a valley type response is obtained with a minimum equal to two-thirds of the input at the frequency of zero phase shift. In a true null network the minimum output would, of course, fall to zero.

This form of network, e.g. a bridged-T (Fig. 4a), can be utilised in a negative feedback path, but a large amount of positive feedback is required in an auxiliary positive feedback loop to bring about oscillation, so it is quite a difficult type of network to use successfully in the simpler types of oscillator. Since the net feedback will be positive, conditions approximate to those in a Wien bridge oscillator because when the input is a blend of positive and negative feedback it can be influenced by a phase shift in either.

Parallel-T

The true null network is a parallel-T. Although it has a rather different form of phase-shifting characteristic it can be substituted for the bridged-T network and, since the negative feedback now disappears altogether at the frequency of oscillation, considerably less positive feedback is required in the auxiliary loop.

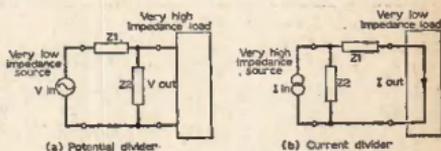


Fig. 2: Single stage networks.

The Parallel-T can likewise be rearranged to give an inverse response, which is a peak at zero phase shift, equal to the input and therefore three times that of the Wien network. Decreasing the impedance of the low-impedance branches will increase the output slightly above the input and it can then be used in an emitter follower type of oscillator where the actual voltage gain of the amplifier is less than unity (Fig. 7).

The disadvantage of the Parallel-T network is that it requires three capacitors and three resistors. The values of these are not all alike and require, for the null circuit, to be in a certain ratio, usually 2:1:1 as in Fig. 4b.

Tuning

In variable frequency oscillators tuning is easily accomplished by means of resistance capacitance networks. With their wide tuning range it is possible to cover from a few cycles per second to

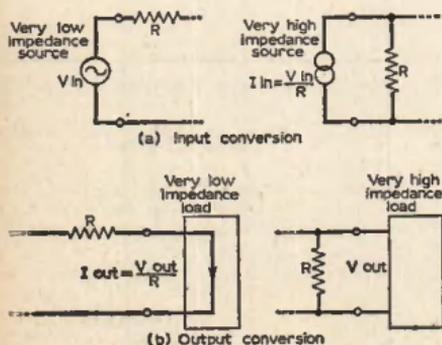


Fig. 1: Alternative arrangements at end of network where there is a resistance.

RETURN-OF-POST

ON CASH OR C.O.D. ORDERS

● GARRARD GRAMOPHONE EQUIPMENT

(Illustrated list sent free)

	Cash Price	Credit Deposit	Monthly Payments	Total Credit
Model 50 (GCS Mono PU)	£5.19.5	£1.19.5	12 of 15/5	£11.4.6
Model 1000 (GCS Mono PU)	£5. 6.6	£1.13.6	12 of 13/5	£9.13.6
Model 3000 (VTABC Stereo Mono PU)	£12.15.0	£2.12.0	12 of 19/5	£14. 0.9
A70 (GCS Mono PU)	£12.18.0	£2.12.0	12 of 19/5	£14. 5.8
A70 (Desram PU)	£22.10.9	£5. 3.6	12 of 39/9	£28.11.8
LA890 (Desram PU)	£21.19.6	£6.19.6	12 of 47/9	£29.5. 2.6

SINGLE RECORD PLAYERS

SP25 (GCS Mono PU)	£12.15.0	£2.12.0	12 of 19/2	£14. 0.0
SP25 (Desram PU)	£16.10.9	£4. 5.6	12 of 24/9	£21. 8.0

IMPORTANT—When ordering tackle with the Decca Desram Ende-U, please state whether Stereo or Mono required.

● GOODMAN LOUDSPEAKERS

(Send for free Illustrated List)

	Cash Price	Credit Deposit	Monthly Payments	Total Credit
Axion 201 12" 5 watts	£11. 5.0	£2. 5.0	12 of 17/4	£13.12. 0
Axion 10, 10" 10 watts	£8.15.4	£1.15.4	8 of 20/2	£9. 7.0
Axlette 8, 8" 6 watts	£5.10.11	£1. 7.11	6 of 17/2	£6.10.11

● MULLARD AMPLIFIER KITS

We stock many of the components for the Mullard 510, 3-3, Two and Three Valve Pre-Amplifier, Tape Pre-Amplifier, Stereo Pre-Amplifier, Seven Valve and Three Valve Stereo Amplifiers all as described in the Mullard Manual for Audio Circuits. We can supply this publication for 9/6 post free. Detailed list sent free on request.

● LATEST TEST METERS

All the latest models from current production. Illustrated list available.

	Cash Price	Credit Deposit	12 monthly Payments	Total Credit
AVO 8, Mk. 3	£25. 5.0	£5. 3.0	£1.17.5	£27.15.0
AVO Multimeter Mk. 4	£9.10.0	£1.15.0	14. 9	£10.15.0
Tripor Model 80E	£24.18.0	£4.18.0	£1.10.0	£27. 2.0
Tripor Model 127A	£10.10.0	£2. 3.0	14. 0	£11.15.0
TNE Model 500	£5.18.6	£1.18.6	14. 0	£10. 4.6

All Cash and C.O.D. orders are dealt with on day of receipt. Credit orders are subject to only the minimum of delay.

WATTSRADIO (Mail Order) LTD

54 CHURCH STREET, WEYBRIDGE, SURREY

Please note: Postal business only from this address.

VALUES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS LRS, 185, IT4, 234, 3V4, DAF91, DP91, DK91, DL92, DL94
Set of 4 for 15/-, DAF96, DP96, DK96, DL96. 4 for 24/-.
1A7GT 7/6 7C5 7/9 AZ81 8/8 EC085 5/8 KT61 8/8 U28 8/8
1B6GT 7/3 7C6 5/9 B56 4/8 ECP89 7/6 MU14 4/- U47 8/8
1N6GT 7/8 7H7 4/9 CL33 5/8 CP29 6/6 1B 5/8 U32 7/9
184 4/9 9Y14 1/8 D1 12/6 ECP86 10/9 CP87 5/9 U04 8/8
184 4/9 9Y9W 6/8 DAC32 7/3 EC135 5/- PC084 5/8 U78 3/8
185 3/9 10C2 1/8 DAF91 8/9 ECH42 5/9 PC029 5/8 U101 9/9
IT4 1/8 10T1 9/8 DAF96 4/- EC181 4/- PC189 8/- U301 10/9
3A3 6/9 10L1D13 7/8 DCC30 6/8 ECL50 8/8 PC960 6/8 U901 15/-
804 6/8 12A7 7/9 DP88 7/8 ECL52 8/8 PC939 8/8 DARC50 5/8
354 4/8 12AD9 1/8 DP81 1/8 ECH42 5/9 PC029 5/8 U101 9/9
3V4 4/8 12AT7 4/8 DP96 1/- EP39 3/8 PC960 5/- U3C41 6/8
5U40 4/8 12AX7 4/8 DH76 3/8 EF41 6/8 PCL82 6/8 U3C81 6/8
5Y3GT 4/11 12K7C1 3/8 DH77 4/- EP60 4/8 PCL83 8/8 U3C90 5/8
5540 (GT) 6/9 12NCT 8/8 D181 12/6 EP96 5/- PCL84 8/8 U3C98 5/8
6/90L2 8/9 12Q07 3/8 DK32 7/8 EF86 6/8 PCL85 8/- U3L81 9/-
6AL5 2/- 19B06 6/8 DK91 4/8 EF89 4/8 PCL86 8/8 UCC94 3/-
6AM9 2/8 20L1 1/8 DP92 5/- EP52 2/8 PEX44 6/8 UCC98 8/8
6AT6 4/8 20P4 1/8 DL38 6/8 EF92 2/8 PEX33 8/8 UCP90 8/8
6A70 4/8 20P4 1/8 DL38 6/8 EF97 7/8 PEX30C15- UCR21 6/8
6A86 4/8 20P9 1/8 DL35 5/- EF183 6/8 PFL200175 UCR42 7/8
6B5 4/8 25A6GT1 1/8 D128 4/8 ELL3 8/8 P185 8/8 UCR81 6/8
6B8E 5/- 25Z40 6/8 D124 5/8 EL38 11/8 P181 6/8 UCR82 7/8
6B96 5/8 30C18 5/- D126 6/8 EL41 7/8 P182 5/8 UCL35 9/8
6B9W 7/8 30E8 8/8 D185 6/8 EL84 4/8 P183 6/- UCF41 6/8
6F12 8/8 30FL1 6/8 D187 6/8 EL90 4/8 P184 8/8 UCF50 9/-
6F14 2/- 30L15 10/8 EABC80 6/- EL95 5/- PL309 14/- UCF89 5/8
6F25 3/- 30L17 12/- EAP42 7/8 EL80 8/8 PL301 7/8 UCL41 7/8
6F30 4/8 30L21 13/8 D181 4/- EM81 7/8 P325 7/8 UCL44 12/8
6K80 4/8 30P12 7/8 E301 2/- EM84 6/8 P332 8/8 UCL46 8/8
6K90T 7/8 30P19 14/8 EBC35 4/- EM87 6/8 P338 8/8 UCL84 9/8
6P29 6/8 30FL1 9/8 EBC41 6/8 EBC41 6/8 P332 8/8 UY31 8/8
6Q70 5/8 30FL13 10/8 EBF60 6/- EY90 6/- P381 8/8 UY41 4/8
6SL7GT 4/8 30FL14 11/- EBF83 7/8 EZ40 6/8 P39 5/- UY85 4/8
5V6G 3/8 35L9GT 3/8 EBF69 8/8 EZ41 6/8 P383 8/8 UY85 11/-
6V6GT 4/8 35W4 4/8 EBC40 6/8 EZ30 4/- UY90 6/8 VPI821 12/8
6X4 2/8 35ZK1 4/8 EBC81 3/8 EZ21 4/8 TH210 9/8 W78 8/8
6X9GT 8/8 35GT 4/8 EBC92 4/8 V400 8/8 TH233 6/8 W77 8/8
786 10/8 35ZK1 4/8 EBC95 7/8 G233 12/8 TV562 3/8 W79 2/8
79 7/8 35ZK1 4/8 EBC94 6/8 G237 8/8 U28 3/8 Z77 8/8

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL, LONDON N.16. STA 4587
& 85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. CRE 7441
Postage on 1 valve 9d. extra. On 2 valves 18p. more postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognised examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- * Institution of Electronics & Radio Engineers (Brit.I.R.E.)
- * C. & G. Telecommunication Techns' Certs.
- * C. & G. Supplementary Studies
- * R.T.E.B. Radio/T.V. Servicing Certificate
- * Radio Amateurs' Examination
- * P.M.G. Certs in Radiotelegraphy
- * General Certificate of Education, etc.

Examination Students Coached until Successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, signal generator and multi-test meter—all under expert tuition. Transistor portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(State Subject or Exam.).....

NAME.....

ADDRESS.....

4.66

INTERNATIONAL CORRESPONDENCE SCHOOLS




MINIATURE METALLIZED POLYESTER CAPACITORS

Ideally suitable for printed wiring panels and transistorised circuits.

Incorporating a new dielectric material and of unique construction, they are of small physical size and meet the requirements of H.5 D.E.F. 5011 Specification. The windings are virtually non-inductive and the wire terminations are soldered direct to the metal-electrodes eliminating contact resistance and ensuring the minimum possible inductance.

Typical 250 volt range

Cap. µF	Dimensions		T.C.C. Type No.
	H.	T.	
0.01	$\frac{11}{16}$ " 9mm	$\frac{3}{16}$ " 5.5mm	PM X1
0.022	$\frac{11}{16}$ " 9mm	$\frac{3}{16}$ " 5.5mm	PM X2
0.047	$\frac{11}{16}$ " 9mm	$\frac{3}{16}$ " 5.5mm	PM X3
0.1	$\frac{11}{16}$ " 9mm	$\frac{3}{16}$ " 7.2mm	PM X4

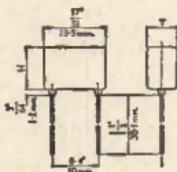

Cap Tolerance $\pm 20\%$

Voltage Ratings:
Ranges available 63, 250,
and 400 volts D.C.

Power Factor:
<0.01 at 1 Kc/s at
+20°C.

Temperature Rating:
Suitable for working at
+85°C. without de-
rating.

Details of the full range
are given in T.C.C. Bulle-
tin 93, available on
request.

Insulation Resistance
10,000 megohms or
2,000 ohm farad which-
ever is less.

Terminations:
22 s.w.g. solder-coated
parallel wires for ver-
tical mounting.

Finish:
Insulated—special non-
cracking heat resisting
thermosetting com-
pound providing good
insulation and good pro-
tection against the in-
gress of moisture.

THE TELEGRAPH CONDENSER CO. LTD.

Electronics Division · NORTH ACTON · LONDON · W.3 · Tel: ACOrn 0061 · Telex: 261383
also at CHESSINGTON, SURREY and BATHGATE, SCOTLAND

Any holes in your knowledge of TRANSISTORS?

Whatever your interest in transistor circuitry, you will find the Mullard "Reference Manual of Transistor Circuits" and "Transistor Radios, Circuitry and Servicing Book", valuable sources of reference.

The former describes more than sixty circuits for both domestic and industrial applications.

The latter is an introduction to the subject and describes the basic properties of semiconductors, their function, elementary circuitry and servicing.

REFERENCE
MANUAL OF
TRANSISTOR
CIRCUITS
U.K. PRICE
12/6

Post extra 1/-

TRANSISTOR
RADIOS
Circuitry and
Servicing
U.K. PRICE
5/-

Post extra, Ed.



Get your copies from your radio dealer, or send remittance with order to:

MULLARD LTD · MULLARD HOUSE · TORRINGTON PLACE · LONDON WC1

THE Radio Constructor

FREE OFFER TO NEW READERS

To Data Publications Ltd. 57 Maida
Vale, London W.9.

Please send me a recent sample copy of
"The Radio Constructor". I enclose 6d.
in stamps for postage.

Name

Address
(Block Capitals)

.....

.....

MONTHLY

2/3

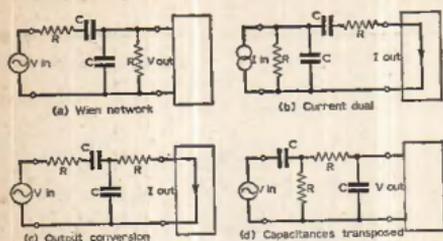


Fig. 3: Variations on the Wien network.

the lower radio frequencies in four ranges of switched capacitances, usually with a 10:1 ratio between adjacent ranges, and ganged potentiometers employed for fine tuning provide scales of about 300°. The potentiometers are normally wire wound to an inverse semi-log characteristic and of adequate resolution to enable a large-scale and sufficient accuracy of setting to be obtained.

Networks of the Wien type require only two capacitors to be switched per range and a dual-ganged potentiometer, by varying both of the network resistances simultaneously, avoids changes in the attenuation of the network, although altering the impedance it presents to the amplifying section. The amplifier normally requires to have a very low output impedance (and high input impedance), assuming a voltage transfer network, to avoid variation of the amplitude with tuning. A thermistor will probably be included to compensate for amplitude variations but it is advisable not to delegate too much of the task to the thermistor.

Amplifier Phase Shift

As far as possible all the frequency dependent phase shift should be concentrated in the R-C network, where it is determined entirely by passive components. The amplifier should be constant in performance and independent of frequency.

At high frequencies internal phase shift in the transistors can be minimised by employing r.f. transistors. At low frequencies amplifier phase shift can be overcome by means of direct coupling. A positive feedback loop nevertheless must normally contain a blocking capacitor to prevent it from exerting an unstabilising effect on the quiescent points of the transistors, but this may be one of the capacitors of the phase-shifting network. A negative feedback loop, on the other hand, has a stabilising effect on the d.c. levels and so may with advantage be direct coupled throughout.

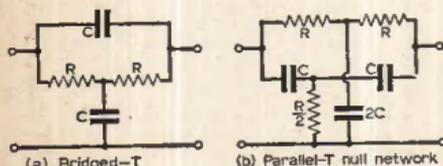


Fig. 4: Networks with valley-type responses.

Impedance Levels

Considering the frequency response as concentrated in the network assumes that the amplifier and network act independently. At both ends of the network, however, variable loading effects, if present, can interfere with the frequency response, making it less predictable and constant. Ideally the network must neither load or be loaded by the amplifier and instead of an impedance match for maximum power transfer the impedance levels of the amplifier and network should be widely different. This is necessary also to avoid distortion due to the non-linear input impedance of a transistor.

There are two ways of minimising the effect of a load variation. One is to make the source impedance much lower than that of the load, in which case the voltage remains nearly constant. The other method is to make the source impedance much higher than the load, in which case the current is nearly constant. When the source impedance is zero it is called a voltage generator and when the source impedance is infinite it is called a current generator. Each is represented by a special symbol in diagrams as in Fig. 1. In practice it is a question of the ratio between source and load impedances and we can speak of a "voltage input" when negligible voltage is developed across the load.

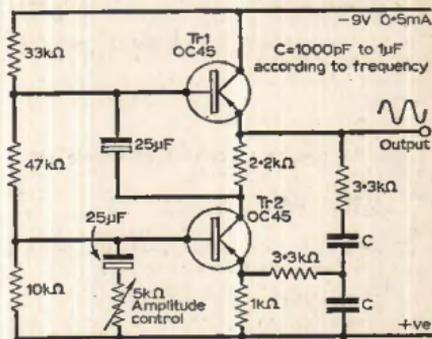


Fig. 5: Oscillator with modified Wien network.

A voltage transfer network, which subjects a voltage to its frequency response, can only be used when an amplifier has a low output impedance and a high input impedance relative to the impedance level of the network. For a current transfer network the reverse conditions apply. High input impedances and low output impedances in the amplifier can be secured by the use of emitter-follower stages. A special arrangement may be necessary for the bias supply to the base of the input emitter-follower, since a d.c. path must be maintained via a resistance to every electrode of a transistor. The high amplifier output impedance that is required for a current transfer network can only be provided easily when one of the resistors of the phase-shifting network serves also as a collector load resistor.

Network Duals

Voltage transfer networks can be regarded as composed of various potential dividers containing resistances and capacitances. Since two impedances in parallel constitute a current divider (Fig. 2b) it is possible to build current transfer networks on close analogy with the voltage transfer networks. To every voltage transfer network there corresponds a current transfer network called its current dual and it can be derived, for all the three-terminal networks we are considering, simply by turning the network round so that the input and output change places. The amplifier impedance levels must also be interchanged.

It is shown in Fig. 1 that a voltage generator in parallel with the resistance is equivalent to a current generator in parallel with the resistance. This is less obvious than the corresponding output conversion based on the current through a resistance being proportional to and in phase with the voltage across it.

It is convenient to be able to alter the feed arrangements of a network in this way but if the change is made only at one end the network maintains its frequency response but now derives an output voltage from an input current, or vice versa, so that the amplifier impedances can be both higher or both lower, as the case may be, than the network impedance.

A similar conversion can be made with capacitances at the ends of the Wien network if the change is made at each end so that the phase shifts cancel. By applying all of the preceding transformations to the Wien network quite a number of other networks with a similar frequency response can be derived. Some of these are shown in Fig. 3.

Networks appear to consist of simple sections but the loading of later sections upon earlier ones makes analysis more complicated. Separation of the sections of some networks is possible by inserting isolating stages between them, but this would be unusual in a transistor oscillator since it would increase the number of transistors.

Oscillator Circuits

It is possible to overrate current duals as oscillator networks and the typical a.f. oscillator uses a Wien network, which is of the voltage

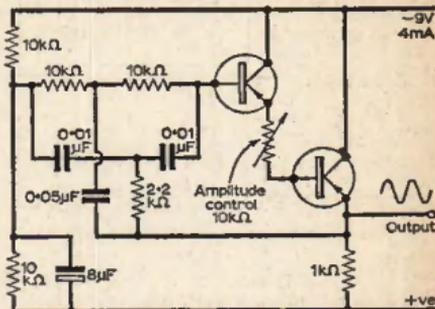


Fig. 7: Parallel-T +ve feedback oscillator.

transfer type. This requires a high input impedance in the amplifying section and with transistors this can be obtained from a compound emitter-follower arrangement involving two transistors. A third transistor will be necessary to secure a low output impedance and the amplifier must provide voltage amplification without phase reversal. The best direct-coupled arrangement combines p-n-p transistors with n-p-n. Increasing the number of transistors in an oscillator allows greater scope in design, enables the performance to be improved and permits variable tuning.

In a two transistor oscillator the possibilities are more limited, especially with direct coupling, and with less orthodox circuits snags are encountered such as the provision of satisfactory forms of amplitude control to prevent limiting.

The oscillator shown in Fig. 5, however, has a good performance and only consumes 0.5mA of current. It contains a Wien network supplied from the low-output impedance of the upper transistor, an emitter-follower, and from the Wien network an output current enters the emitter of the lower transistor, a ground-base stage, whose collector load resistance is increased in value artificially by the bootstrap action of the upper transistor. The current gain of the emitter-follower depends upon a sufficiently low impedance in its output circuit, hence the low resistance values in the network, but the equal capacitors C can be given a range of values to yield various spot frequencies. Amplitude control, gradual in action, is by varying the impedance in the base circuit.

The oscillator of Fig. 6 employs a Parallel-T null network in a negative feedback path. A Bridged-T would not give such a large undistorted output. Positive feedback between the emitters is varied for amplitude control.

An even better oscillator using a Parallel-T is shown in Fig. 7. In this optimum amplifier conditions can be secured with very high input impedance and a low output impedance. The low-impedance arms of the network are made lower in impedance than for a null network in order to step up the output voltage to the base of the first transistor. Amplitude control is by a resistance between the transistors but the low-resistance branch of the network could be varied instead. ■

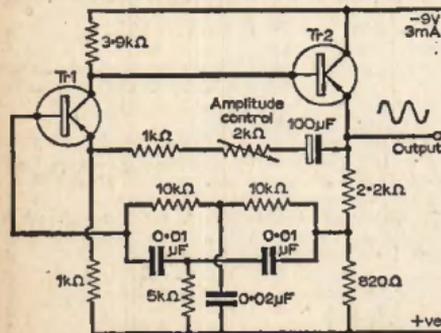


Fig. 6: Parallel-T -ve feedback oscillator.

BROADWAY ELECTRONICS**92 MITCHAM ROAD, TOOTING, S.W.17**Phone: **BALham 3984**

(four minutes from Tooting Broadway Underground Station)

GARRARD 4 SPEED DECKS WITH CARTRIDGE: Auto-changers: AT90, £10.0.0; 3000, £8.8.0; 2000, £7.7.0; 1000, £6.6.0; Autolim 25.5.0; Do Luxe Autolim with plug-in head, £5.15.0; P. & P. 6/- Single Players: SP25, £10.10.0; SRP12, £5.0.0; Garrard Plinth, W.B.1, £3.12.6. P. & P. 4/8 for plinth. Motor boards 6/6 each.

CARTRIDGES: Ronette Stereo 25/-; Acos GP67, 15/-; G.C.2 (Garrard 15/-); AT6 shells 5/-; P. & P. 6d. HGP632 Stereo 20/-.

SPEAKER ENCLOSURES: "TONY" Corner Cabinet 20 x 10 x 7in., takes 10 x 6in. speaker, covered in grey Rexine and Vynair, 45/-; P. & P. 5/-; "BLAKE" Heavy Duty Cabinet with port, 24 x 18 x 9in. Baffle 1in. thick. Covered Rexine and Vynair, £5. P. & P. 10/-; Extra baffle for 8 or 10in. sp. "BLAKE DE LUXE" veneered with wood-grain Formica and standing on smart 6in. legs, £6.5.0. P. & P. 10/-; "HAYDON" 18 x 18 x 7in., fabric covered, suitable 12in. speaker, 45/-; P. & P. 7/6; Crystal Mike 200C replines BMS, 30/-; P. & P. 3/-; Stand for same, 9/6. P. & P. 1/8; Guitar Pick-up with Screened Lead, 12/6. P. & P. 6d. Crystal Lapel Mike, 7/6; Neon Panel Light Arcolitelectric 240v. A.C., 2/6; P. & P. 6d. Tape Spools: 3in., 9d.; 4in., 1/-; 5in., 1/3; 7in., 2/- each.

BARGAINS IN TRANSISTORS. AC127, AF 114, 115, 116, 117, 118, 119, OC169, 170, 171, 172, 5/6 each. OC72, 75, 82, 3/6. OC71, 91M, 3/-; RF Packs—1 OC61, 2 OC65, 9/6. AF Packs—1 OC10, 2 OC1, 8/-; AF Pack—1 GE7118, 2 GE7119, 5/6. OC26, 28, 29, 7/6. ORP12 Light Cell, 7/6. Diodes OA81, 2/8, OA91, 1/8. P. & P. on all these 6d.

EARPIECES with cord and 3.5 mm plug, 8 ohm magnetic 3/-; 250 ohm, 4/-; 180 ohm Magnetic with clip, 8/6; Crystal, 4/-; P. & P. 6d.

SPEAKERS: ELAC Heavy duty Ceramic Magnet, 11,000 lines, 10in. round, 10 x 6, 15 or 3 ohm, 42/6. P. & P. 3/6. 8in. round 15 or 3 ohm, 38/6. P. & P. 3/6. EMI 134 x 6in. 15 or 3 ohm, 42/6. P. & P. 3/6.

Stockists for Earle Products, Goodmans, W.B., Wharfedale, Bakers, Trilphone, Linear, all makes of amplifiers and speakers supplied. Let us quote for your requirements. S.A.E. please. **NO C.O.D.** Trade terms to bona fide dealers.

YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS**, (Technicians' Certificate); the **Grad. Brit. I.R.E. Exam.**; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the **R.T.E.B. Servicing Certificates**; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Fullest details will be gladly sent without any obligation.

To: **British National Radio School, Reading, Berks.**
Please send **FREE BROCHURE** to:

NAME _____ Block
ADDRESS _____ Caps.
Please
4.66

BRITISH NATIONAL RADIO SCHOOL

SERVISCOPE MINOR



Extend the range of your present test instrumentation with this versatile Tequipment oscilloscope. Simplified operation—minimum controls, automatic time base synchronisation—but top quality construction.

2.75in. tube with graticule, contrast filter and rubber light hood. Bandwidth DC-30Kc/s (-3dB); maximum sensitivity 100mV/0.5cm division. Time base continuously variable from 100microsec to 100msec per 0.5cm division. Mains operated, fully portable. Instruction manual supplied.

Descriptive leaflet on request.

Obtainable only direct from the country's largest specialist manufacturer of portable oscilloscopes for science and industry. *Serviscope is a registered trademark*

**TELEQUIPMENT**

Tequipment Ltd., 313 Chace Rd., Southgate, London N.14
Tel: Fox Lane 1166

Please send me, without obligation, the
descriptive leaflet on the Serviscope Minor.

NAME _____
ADDRESS _____

HOME RADIO LTD. 187 LONDON RD., MITCHAM, SURREY 'Phone MIT 3282

ARE YOU LOOKING for the UNUSUAL?


Because it may be standard catalogue stock to us. Here are a few examples

THERMISTORS

Type R.53 £1.10
 Also stocked:
 A.15 ... 12/6 , A.55 ... 12/6
 A.26 ... 12/6 , R.24 ... £1.10
 A.54 ... 12/6 .

HIGH VOLTAGE RECTIFIERS


K3/40 9/-
 Also stocked:
 K.3/15 6/-
 K.3/50 12/4
 K.3/100 £1.03
 K.3/160 £1.56

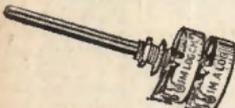S.T.C. FM CRYSTALS £3.15.0**GANGED STEREO POTS**

10K Log + 10KA/Log 10/-
 10K Log + 10K Log D.P.
 switch 12/3

Also stocked:
 (Log or Linear) 10K, 50K,
 100K, 250K, 1M, 2M 10/-

All the above and many thousands of other electronic items, both usual and unusual, may be found in our catalogue, price 7/6, plus 1/6 postage and packing. Each catalogue contains 5 coupons each worth 1/- if used as directed. Post the Coupon on the right with your cheque or P.O. for 9/-.

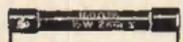RESISTORS

1/6 1/2 watt
 Most values between 22
 Ohms and 10 Meg. 2/-

VALVES

85A1 ... £2.11.6	TT21 ... £2.8.6	VR105/30 18/6
85A2 ... 15/6	EN91 ... £1.6.0	VR150/30 18/6
Z803U ... 18/6	150B2 ... 15/4	6141 ... £2.0.0
150C4 ... 15/9	QVO6/20	5763 ... £1.0.0
OA2 ... 15/-	£2.8.0	OB2 ... 16/-

ALSO MATCHED PAIRS

OAZ222 ... £1.6.0
 OAZ223 ... 17/6
 OAZ224 ... 14/-

TRANSISTORS & DIODES

AF186 £1.7.6	GET103 ... 7/-	OC76 ... 7/-
AC107 ... 14/6	GET106 ... 17/-	OC77 ... 12/-
BZ313 ... 11/6	GET115 ... 9/6	OC83 ... 6/-
ASY28 ... 8/6	GET116 ... 17/-	OC84 ... 8/-
GEX66 ... 15/-		SVC1 ... 28/-

Please write your name and address in block capitals

NAME

ADDRESS

HOME RADIO LTD., DEPT. P W., 187 LONDON ROAD, MITCHAM

RADIO CLEARANCE LTD.27 TOTENHAM COURT ROAD, LONDON W.1. Telephone: MU5EUM 9188
Bulk enquiries invited. The oldest components specialists in the trade. Est. 35 yrs.**LOUDSPEAKER BARGAINS STILL AVAILABLE**

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

Size in inches	Gauss in Hertz	Imped. ohms	Price	Size in inches	Gauss in Hertz	Imped. ohms	Price	Size in inches	Gauss in Hertz	Imped. ohms	Price	
2 7000	80	8/6	3/1	3 7000	3	10/6	4	8000	5	7000	5	8/6
2 7000	80	8/6	3/1	3 7000	35	8/6	3	7000	5	8000	5	8/6
2 7000	50	8/6	3/1	3 9500	30	10/6	5	7000	3	7000	3	8/6
2 7000	80	8/6	3/1	4 6000	35	10/6	5	8000	5	8000	5	8/6
3 8100	3	10/-	4	7000	35	11/-	5	8000	13	12/6	10/6	
3 7000	3	9/-	4	7000	5	8/6	5	8000	30	10/6	10/6	
3 7000	35	9/6	4	4 9000	35	11/6	5	7000	3	11/-	11/-	
3 6000	50	8/6	3/1	5 9000	35	11/6	5					
3 6000	13	10/6	4	9300	13	12/-						
3 7000	3	9/6										
5 x 3 9000	35	12/-	7 x 3 7000	3	9/6	8 x 2 8000	3	5/6				
5 x 3 7000	3	8/-	7 x 3 9500	3	10/6	8 x 3 7000	4	9/-				
3 x 3 9980	3	8/6	7 x 3 8500	5	11/6	8 x 3 9000	3	10/-				
3 x 4 9500	3	9/-	7 x 4 9500	3	12/6	10 x 6 11000	3	22/6				
3 x 4 9500	3	10/-	7 x 4 10000	3	12/6	10 x 6 11000	3	22/6				
3 x 4 9500	35	12/-	7 x 4 12000	3	12/6	10 x 6 13000	30	22/6				

ALLOW 2/6 each speaker for postage and packing and handling charge and please specify the exact requirements—the nearest available will be sent.

SELECTED BARGAINS

Beautifully geared AM/FM 2-range Condensers, 4/6; ANFM IPT'S 465 coils and 10.7 Mc/s 4/6 pair; Magnavox Crystal Tone Recorder Mikes, 12/6; 3 watt Stereo Amplifier complete, ready to switch on, 79/6; Sencorell rectifiers R3ED-D3-2-1-X, 2/6 each. DIODES—0A75, 0A50, CG46H, GD10, 2/- each. TRANSISTORS: OC45 4/6, FX101, 3/6, AP115, 4/6. Sub min. Germanium diode 1/3. M1 diode 8d, each. Silicon diodes, 200 p.t.v., 330mA, 2/6 each, please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogue—our stocks move so quickly! Kindly make provision for additional postage and package charge to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-.

**1966 EDITION
RADIO AMATEUR
HANDBOOK**

40/- by ARRL Postage 2/6

TRANSISTOR POCKET BOOK by

R. G. Hibberd, 25/-, Postage 1/-

ELECTRONIC ORGAN HAND-

BOOK by H. Emerson Anderson,

35/-, Postage 1/-

A LABORATORY MANUAL OF

ELECTRONICS by K. J. Dean 20/-,

Postage 1/-

TRANSISTOR ELECTRONIC

ORGANS FOR THE AMATEUR

BOOK by A. Douglas & S. Astley, 18/-,

Postage 1/-

A BEGINNER'S GUIDE TO

RADIO Pub. Newnes, 8/6, Postage

9d.

SERVICING AGC by H. E. Thomas

28/-, Postage 1/-

A BEGINNER'S GUIDE TO TELE-

VISION Pub. Newnes, 8/6, Postage

9d.

BASIC THEORY & APPLICATION

OF TRANSISTORS by U.S. Dept.

Army, 18/-, Postage 1/-

COMPLETE CATALOGUE 1/-

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS

of British and American Technical Books

19-21 PRAED STREET

LONDON, W.2

Phone: "Aldington 4165
Open 6 days 9-6 p.m.



**G
I
6
Y
M**
No.

CITY OF BELFAST Y.M.C.A. RADIO CLUB

ONE of the international Y.M.C.A.'s most senior organisations, City of Belfast Y.M.C.A. Radio Club (G16YM), is among the oldest radio clubs in the British Isles. The Club was founded in 1922 and received its transmitting licence and call sign in 1927, but there is some evidence of previous activity dating back to shortly after the close of World War I. It may be interesting to note that the Club licence holder, Mr. Robert Barr (G15UR), a "call" well known to the world's c.w. DX fraternity, has been continuously in membership since those early days and is still one of 6YM's most active members.

The lifetime of G16YM spans the history of radio experimentation in the north-east corner of Ireland and thus the City of Belfast Y.M.C.A. Radio Club can rightly be considered as the "cradle" of amateur radio in the most populous region of the six Irish counties comprising Northern Ireland. Certainly the majority of radio men and enthusiasts in the Belfast area, many of whom have made their mark on the "ham" hobby or in the wider radio world outside as Government scientific officers, Post Office, BBC and service technicians and operators, have all been connected with G16YM at one time or another.

In the Y.M.C.A. tradition of "Service, Not Self" the City Club membership takes modest

pride in its record during World War II days and was one of the few clubs which "carried on" in spite of cessation of transmitting activity and the loss of many of its most active members—of all ages—to the Royal and Merchant navies, Army and R.A.F. or engaged in security duties at home. Through its connection with the parent Y.M.C.A.—"Mecca" for thousands of Service men passing through Belfast—the City Club kept "open house" for Service "hams" from all over Ireland, Great Britain, the Commonwealth and the U.S.A. Many of these men held club office while stationed in Northern Ireland and needless to say, the war-time visitors' book is one of the most treasured items in the club archives.

Club accommodation is second to none and comprises a general clubroom on the third floor of the main city Y.M.C.A. building with a transmitting room on the floor above. The clubroom, recently refurbished in contemporary "decor", contains comfortable seating (including settee and easy chairs!) library with technical and current British and U.S. radio publications, listeners' corner complete with junior HRO, Morse practice equipment transcription record player and hi-fi amplifier for the club's audio section.

The well-appointed transmitting room on the floor above contains most of the equipment



As a YMCA organisation G16YM's emphasis has always been on youth. Pictured are some of the Club's SWL members and "junior ops." On the extreme left is G13UKS, Dave Vizard, the area's youngest licensee.



Left: Making checks on the Club's new S.S.B. transmitter are (from left) R. Barr (G1SUR), SWL Evans, F. Robb (G16TK) and Major Ian Kyle, club member and local T.A. "boffin".

Below: Tuning-up the standby T1154 transmitter are (from left) T. J. Moss (G13UFH) Club treasurer, J. Beattie (G13NOH) Club chairman, C. Rourke (G13IV) Club secretary, licence-holder R. Barr (G1SUR) and SWL member.

necessary for efficient operation under present-day conditions (the club recently made DXCC in spite of restricted hours of operation), the gear comprising a KW77 receiver, medium-power c.w. transmitter for 80 40 and 20m, 4m transmitter/receiver and all ancillary equipment. S.S.B. operation is also engaged in using a Sphinx transmitter, until the construction of the Club's own all-band S.S.B. rig is completed.

Main aerial requirements are taken care of by the recent construction and erection of a fine tri-band quad and supporting tower which has been mounted on one of the Y.M.C.A. building's highest points overlooking busy Wellington Place and already a city landmark. This erection also carries the v.h.f. aerial and will eventually be remotely controlled from the transmitting position. The emergency aerial is an all-band trap dipole.

The City of Belfast Club takes a full part in all local, national and international "ham" radio activity, chief among these being National Field Day and the popular Jamboree-on-the-Air, both events being held in conjunction with City Y.M.C.A.'s own Scout troop, which has a splendid QTH on the south side of the city.

Regular meeting nights are held each Wednesday and Saturday evenings from 8 o'clock but activities such as Morse practise and construction take place on other evenings as required and access to the club is available at all times. Any enthusiast—transmitting or SWL—whether "local" or just passing through can be assured of a real Irish Cead Mile Failte in the best "YM" tradition. Club secretary is Mr. Cedric Rourke, G13IVJ, 32 Kirkliston Park, North Road, Belfast 5.




TECHNICAL BOOKS IN NATIONAL LIBRARY WEEK 12th—19th MARCH 1966

The first British National Library Week will take place from 12th to 19th March 1966. The purpose is to interest everyone in making more use of libraries and in building up their own personal libraries. Local committees throughout Great Britain will be organizing book exhibitions, talks, competitions, and other features.

Scientific and technical books will be specially featured by many centres, with displays of students' textbooks, industrial books and 'do-it-yourself' books. Talks by authors of scientific and technical books have been arranged, and some centres are staging exhibitions and discussions.

Further information about National Library Week can be obtained from F. N. Radford Limited, 280-293 High Holborn, London, W.C.1.

TAKE IT WITH YOU EVERYWHERE

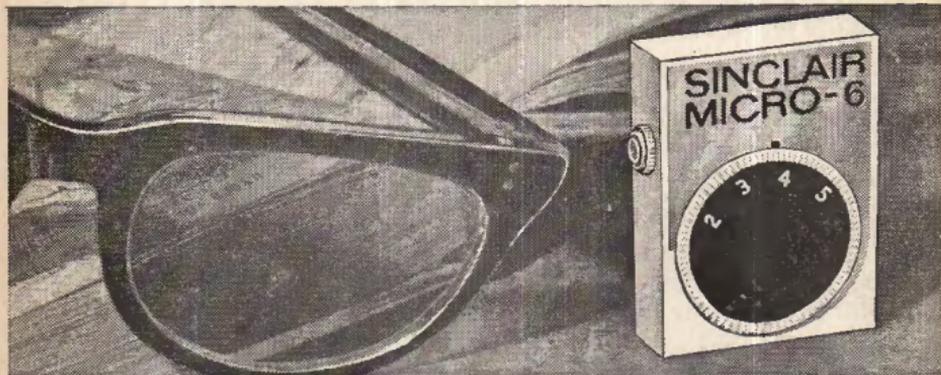

Not only is the **SINCLAIR MICRO-6** the smallest set in the world—it is the most efficient of its kind. This set has already been built by more constructors than any other kit in the history of transistor sets and thousands more are being built each month. It is easy to see why. The power and selectivity of the **MICRO-6** are remarkable by any standards. Its minute size and design are irresistibly attractive and it even has vernier-type tuning for easy station separation. Building is simplicity itself—the instructions make success assured from the moment you unpack the parts for your **MICRO-6**. Everything is guaranteed, and a full time service department is available should you want it so that you cannot possibly go wrong. The **MICRO-6** tunes over the medium waveband with bandspread to bring in Luxembourg like a local station. In fact, this little giant of a set will bring in programmes where larger sets sometimes cannot be heard at all, for it plays virtually everywhere.

Until you have experienced the thrill of owning your own **MICRO-6**, you will never know just how exciting radio can be.

- SIZE $1\frac{4}{5}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$
- WEIGHT (WITH BATTERIES) 1 oz.
- PLAYS ANYWHERE — IN BUS, CAR, TRAIN, Etc.
- BANDSPREAD FOR EASY LUXEMBOURG RECEPTION
- A SINCLAIR GUARANTEED DESIGN

The World's smallest radio



A MOST SATISFYING
SET FOR ANYONE
TO BUILD

Complete kit of parts including white plastic case finished in gold and black, lightweight earpiece, transistors, components and instructions.

MALLORY MERCURY CELL ZM.312 (2 reqd.) each 1/11; pack of 6—10/6

6 STAGE POWER AND SELECTIVITY

In the Sinclair Micro-6 three special Sinclair Micro Alloy Transistors (M.A.T.s) are used in a six stage circuit to provide two stages of R.F. amplification followed by double diode detection and a high gain three stage audio frequency amplifier. Signals are received on the special self-contained ferrite rod aerial. A.G.C. counteracts fading from distant stations. Power comes from two minute pill size batteries which give about 70 hours working life. Plugging in the lightweight earpiece switches the set on.

59/6

SINCLAIR MICRO-6

SPECIAL MONEY SAVING OFFER No. 1 TO P.W. READERS

By buying a Sinclair Z.12 Amplifier (See next 2 pages) with your Micro-6, you can save 9% and have the basis of a powerful car, portable or domestic radio. Bought separately, these items come to £7.9.0. Send now for

PACK 'A' £7.0.0

More money saving offers on next pages

NOW REMOVED TO NEW AND LARGER PREMISES

SINCLAIR RADIONICS LTD., SINCLAIR HOUSE
22 NEWMARKET ROAD, CAMBRIDGE

SINCLAIR

SINCLAIR MICRO FM

7 TRANSISTOR FM SUPERHET TUNER-RECEIVER

A 100%
BRITISH
PRODUCT



Case in black plastic with polished and brushed aluminium front

SIZE $2\frac{1}{2}'' \times 1\frac{1}{2}'' \times \frac{3}{4}''$ (74 x 48 x 19 mm.)

1

- WITH PULSE-COUNTING DETECTOR
- WITH LOW I.F. TO CUT OUT ALIGNING
- WITH 2 OUTPUTS FOR DOUBLE PURPOSE OPERATION

ALL YOU WANT FROM AN FM TUNER AND RECEIVER IN A SINGLE UNIT

For far less outlay and trouble you can enjoy building and using the most advanced F.M. design in the world when you buy the Sinclair Micro FM. This fully-fledged 7 transistor, 2 diode FM superhet has original features that ensure superb audio quality and great sensitivity together with utmost ease of assembly. There are two separate output sockets, an exclusive Sinclair feature which enables you to use your Micro FM as a tuner and as an independent pocket size portable receiver as you wish. This wonderful set is just about as big as a packet of 10 cigarettes and is as outstanding in appearance as in its performance. Many other excellent features are included in the Micro FM to make building an FM set easy for everyone. Best of all, it brings first class performance with a saving of pounds.

★ TECHNICAL DETAILS

Seven transistor, 2 diode FM superhet for use as a tuner and as a self-contained pocket receiver. The R.F. amplifier is followed by a self-oscillating mixer. Low I.F. dispenses with the need for alignment. A 3 stage I.F. amplifier produces a square wave of constant voltage which is fed into the pulse counting discriminator. This is converted into pulses to reproduce the original modulation exactly. After equalisation, the signal is fed to the audio output socket and to the receiver's own audio amplifying stage for using the Micro FM as an independent self-contained receiver. A.P.C. locks on each station tuned in. THE SINCLAIR MICRO FM is self-contained within a neat black plastic case faced by an elegantly designed front panel of brushed and polished aluminium with spun aluminium tuning dial to match.

THE WORD'S FIRST
POCKET-SIZE
COMBINED FM
TUNER —
RECEIVER



Use it as —



- Pulse counting discriminator
- Low I.F. eliminates alignment problems
- Tunes from 88 to 108 Mc/s
- Audio response—10 to 20,000 c/s ± 1 dB
- Signal to Noise ratio—30dB at 30 microvolts
- Operates from standard 9V battery, self-contained

Complete kit inc. telescopic aerial, case, aluminium front panel, dial earpiece, 2nd outlet plug and instructions.

£5.19.6

SPECIAL MONEY-SAVING OFFER

No. 2 TO P.W. READERS

To make it possible for constructors to obtain the best possible standards of reproduction, we are offering the Micro FM together with the Z.12 described opposite for £9.10.0 instead of the usual price of £10.9.0. Send now for

PACK 'B' £9.10.0

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS



NOW REMOVED TO NEW AND LARGER PREMISES
SINCLAIR RADIONICS LTD.
SINCLAIR HOUSE, 22 NEWMARKET ROAD, CAMBRIDGE

SINCLAIR

SINCLAIR Z. 12

COMBINED 12 WATT AMPLIFIER AND PRE-AMP

The ultimate in
**SIZE, POWER
 QUALITY
 AND PRICE**

- **SIZE**—3" x 1½" x 1½" (75 x 44 x 33mm.)
- **12 WATTS R.M.S.** (24w. PEAK)
- **15-50,000c/s ± 1dB**
- **IDEAL FOR 12V. OPERATION**

WITH THE Z.20
 THERE'S POWER
 IN PLENTY FOR
 Mono and stereo
 hi-fi systems

Car for portable
 radion with the
 Micro-6

Quality Radio
 with the Micro
 FM

Electric Guitar

P.A. and Inter-
 com systems

Never has such power and quality been contained within so compact a size as that of the Sinclair Z.12. This eight transistor amplifier includes its own pre-amplifier designed to accept any type of input. The Z.12 incorporates ultra-linear class B output in a circuit using special H.F. transistors to provide exceptional performance standards. This newest Sinclair amplifier may be powered from any supply between 6 and 20 volts D.C.; the output can be fed directly into any load from 1.5 to 15 ohms. Thus the scope of the Z.12 is far greater than that of any other amplifier irrespective of price, making it the most versatile, dependable and compact audio amplifier system ever. The Z.12 is supplied ready built, tested and guaranteed, together with details of tone and volume control circuits by which input sources can be accurately matched to the pre-amp.

Complete kit of
 parts with 8 transistors, instructions and Z.12 manual

89/6

SPECIAL MONEY-SAVING OFFER NO. 3 TO P.W. READERS


You can save still further by buying two Z.12s together at the special price of £8.80 instead of the usual price of £8.19.0. This is a wonderful opportunity to possess a low priced super quality stereo system. The X.1 Power Supply Unit (£2.14.0) will comfortably drive two Z.12s. Send now for

PACK 'C' £8.8.0

THE SINCLAIR GUARANTEE COVERS ALL PURCHASES

Please note our new address
 TO WHICH ALL COMMUNICATIONS SHOULD BE SENT

A 100% British
 product

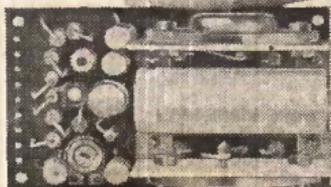

TECHNICAL DETAILS

8 transistor hi-fi amplifier with integrated pre-amp, using special H.F. transistors. Generous negative feedback assures superb quality.

SIZE—3" x 1½" x 1½" (75 x 44 x 33 mm).

WEIGHT—Three ounces.

OUTPUT—12 watts R.M.S. continuous sine wave (24w. peak).

15 watts R.M.S. music power (30w. peak).

FREQ. RESPONSE—15-50,000 c/s ± 1dB.

OUTPUT IMPEDANCE—3 to 15 ohms. Two

3 ohm speakers may be used in parallel.

INPUT—2mV into 2K ohms.

POWER REQUIREMENTS—6-20V d.c.

SIGNAL TO NOISE RATIO—better than 60dB.

QUIESCENT CURRENT CONSTN—15mA.

ONE & VOLUME CONTROLS added to

amplifier as required. A variety of systems for mono

and stereo are given in the manual supplied with

every Z.12.

If you do not wish to cut this page, please

mention PW.4 when writing your order.

ORDER HERE !

To SINCLAIR RADIONICS LTD., SINCLAIR HOUSE,
 22 NEWMARKET ROAD, CAMBRIDGE

Please send goods indicated below

ITEM	QUANTITY
Sinclair Micro-6	£2.19.6
Pack 'A'	£7. 0.0
Sinclair Micro FM	£5.19.6
Pack 'B'	£9.10.0
Sinclair Z.12	£4. 9.6
Pack 'C'	£8. 0.0
Power Pack X.1	£2.14.0

for which I enclose Cash/Cheque/Money Order

value £.....d.

NAME

ADDRESS

BLOCK LETTERS PLEASE

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV, 1925-1966. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models 1/6. Valves, modern and obsolete, Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio and Television, 4/-, post paid. VEST AND EMERY, 47 Hallgatin St., Durham.

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries. TELRAY, 11 Mauldron Bank, Preston.

SERVICE SHEETS (75,000), 4/- each. Orders welcome. Always open. 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service Sheets for all makes and types of Radios and Televisions, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon.

Name: _____

Address: _____

To: **S.P. DISTRIBUTORS**
44 Old Bond St., London, W.1

Please supply Service Sheets for the following:

Make: _____ Model No. _____ Radio/TV

Make: _____ Model No. _____ Radio/TV

Make: _____ Model No. _____ Radio/TV

I require the new 1966 List of Service Sheets at 1/6 each plus postage.

(please delete items not applicable/ I enclose remittance of)

MAIL ORDERS ONLY Apr. PW

SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand A., 2,400ft., 25/-; 58in., 1,200ft., 15/-; P. and P. 1 set 2/-, 2 set 2/3, 3-6 set 3/6. Bargains in all sizes. S.A.E. for list. E. C. KINGSLEY AND CO. LTD., 93 Tottenham Court Road, London, W.1. ESTDn 1850.

TAPE RECORDERS, TAPES, ETC.

TAPES TO DISC—using finest professional equipment—45 rpm—18/-, S.A.E. leaflet. DEROY, 52 West Bank Lane, Lancaster.

RATES: 1/8 per word (minimum 12 words). Box No. 1/8 extra.

Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS

SPEAKER REPAIRS, Cones fitted. Satisfaction guaranteed. L. S. REPAIRS, Pluckley, Ashford, Kent.

R & R RADIO & T V SERVICE

Dept. P.W.
MARKET STREET, BACUP, LANCS.
Telephone 485

SALVAGE VALVES Tested before despatch

6L12	4/6	U399	5/-	PL36	6/-	90P4	6/6
6L18	4/6	10P14	5/-	PL32	5/6	90P18	5/6
6P8	1/6	20P5	6/6	U801	7/6	PC55A	4/-
EC02	2/-	30P	7/-	10P1	1/6	FY31	5/6
EC29	2/6	5F5	5/-	20P2	5/5	V301	6/-
30P3	6/-	EB91	1/6	20P4	6/-	10P15	5/6
PL55	6/-	EP55	6/-	PY32	6/-	20D1	5/-
POP90	4/-	630LE	4/-	6U4GT2	5/-	50F12	5/-
PL81	5/-	20P3	6/-	6F1	2/6	FY83	5/-
F230	5/-	20P14	4/-	BY80	4/-		

Speakers, Ex-TV, 5in. dia. round 6 x 4in., 2/6; 6in. dia. round, 6/-; post 2/-.

Line Output Transformers available. State set model No.

Tuned Tuners, 8/-, post 2/-.

Scan Cds. etc. Quote set model No. with enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

RELAY BARGAINS: Mod plug-in type, 4-pole c/o, 12/-, p.p., incl. base. A. KNOX, 101 Dalkothin Rd., Edinburgh.

Assorted High Stab Resistors, 7/6, 100.

Assorted Syntex P.F. Condensers, 7/6, 100.

Copper Laminate Board, 12" x 12", 6/-, single or double sided.

Paroxlin Sheet, 1/2" x 12" x 12", 3/-.

Thin Paroxlin Sheet, approx. 1/4" x 12" x 12", 6 sheets for 5/-.

White Plastic Sheet, approx. 1/4" x 6" x 24", suitable dials, insulation, case fronts, etc. 4 sheets for 5/-.

Small E.M. Counters, 5 digit, 500 ohm, 6/6.

Buign Extra Sensitive Micro Switch, 5/-.

P.O. Relay 2000 ohm, 1B, 5/-; 1M, 1B 5/-.

Key Switches, 4 pole, 2 throw, 3/6. 3 position DP+DP centre off, 5/-, 3 o/c+5 o/c centre off, 6/-, DP+DP 2 for 5/-.

Flamey Pins and Sockets, 12 way, 3/-; 6 way, 5/-; 12.

8 or 12 way screened cable to match, 8/-; 9 or 12 way, 6/-; Carbon Insert, 1/6.

Power Pack and L.F. Amplifier for 38 Set, 15/-.

Battery Ever-Ready, 90v+7v, 4/6; 12 for 30/-.

Small Component Boxes, 12/6, for 50 sample 6d.

M.J. Metal Screen for 54P7 with fittings 6/6.

250 Ma Power 12" x 4", 5/-, 100.

100 volt Hand Generator, 7/6.

Valves New Boxed, 6V3, 4/6. EP91, 3/-; 6AL5, 3/-.

Rheostat WW Rotary, 15 ohms, 3.6 amp, 12/6.

Details of Instrument Case Assembly. Free send large addressed envelope.

Elac Speakers, 5", 5/-, 7" x 4", 7/-, 8", 8/-.

Terms Cash with Order. Post. 2/- on orders under 20/-.

Test Set Type 219

1/P 230V, 50 c/s this is a Pulse Generator covering 200 c/s to 10 Kc in 2 ranges directly calibrated. The pulse width can be adjusted to 5, 4, 3, 2, 1 or 0.5 Usec, by switch on front panel. O/F pulse can be switched to +20, -10 or -10v, and is variable down to 1 Mill volt. There is also a 20 Usec, sync. O/F pulse. It is also possible to obtain a Square wave 3 to 1 and a linear sawtooth from these units, also it is possible to extend the frequency range. These are supplied in good condition with a case and outer cover, un-tested. Price £41.0.0 plus 12/6 cart.

Time Base Unit 140

These units are sold for breakdown and contain the following: Valve EP91 5, EB91 2 4, EC082 2 4, EC083 2 4, EC081, 60Hz x 4, 11 Pulse W.W. type, 2 Toggle Swt., 8 Coax. Ska., 100 Resistors including a large number of 1, 2 & 5% types, 30 comds, 5 32-way tag boards, etc. Supplied in good clean condition. Price 80/- plus 7/6 post. Coax Cables 1/6 each.

Ind Unit C.R.T. 100

This is a twin tube radar display unit with C.R.T. tubes CV2184 34in., CV2286 34in. and valves EP91 x 2, EB91 x 2, 18 AT 7 5, CV813 x 2, 6CH6, 12AU7, CV1076, 6F3, Meter edge-wise reading type 10 to 2000 v.d.s., 1 Ma. linear scale also 7 relays, 20 Pot. Sln. magnifier etc. Supplied in good condition in transit case. Price £40.17.6 plus 12/6 carriage.

Monitor ANGRD

This comprises a Scope, Bearing Ind. and A.P. monitor. The scope uses C.R.T. type 3BP1 and valves 6AU6 x 2, 6AL5, 12AU7 x 2, 6AQ5 x 2, OA2, 20D1, 12AX7, 6V3 x 2, 6V6 5in. speaker 2000 Bear Ind., 44in. dia. controls power, IRL X & Y shift, sync. gain, X amp, power 1/P is 115v, 50 c/s, 19in. rack unit with outer cover in good condition with circuit. Price £55.0.0 plus 12/6 carriage.

Test set type 5B

This is a battery operated crystal controlled signal generator covering the band 100 to 150 Mc/s with modulation, there is also Meter 1 Ma. 50Hz. Fl. Ed. 3 gang 20 pf tuning cond. var. wvd., 2 sections 4x etc. Complete in case with 4 x 2 1/2in. with front cover. Brand new cond. Price 35/- plus 10/- carriage.

Rx Unit Type 3582

This is a 6 stage 7 Mc/s I.F. strip with Det. & V.I.F. Op. a high cycle P.U. is fitted with 6U4 & 6X5 valves, this can be removed to leave space room to fit other P.U. These units are a modern version of the 1355 Rx and the I.F. 24/27 tuning units will plug into the front of these units. Supplied in good condition with circ. Price 35/- plus 10/- carriage.

Blower Motors

1/P 115v, 50 c/s 22 watt, 3000 r.p.m., casted 2 1/2 x 1 1/2in., inlet 1 1/2in., dia. overall length 5 1/2in. Black crackle finish. Brand new and boxed. Price 25/- plus 3/- post. 330/115v. Auto Trs. 9/6 post paid.

Meters 500 U.A.

Scaled 0 to 5, Marconi single hole strip type. 24 0-8-D, 90 ohm int. res. Price 15/- plus 1/6 post.

Selenium Rectifiers

H.W. type 1/P 300V, O/P 100 Ma with mounting brackets. American manufacture. Brand new Price 2/6 ea. plus 1/- post or 4 for 10/- post.

Coder Unit Type 51a

This unit contains a small enclosed 12 volt D.C. motor which drives into a two stage gear box to give an O/P speed of 6 r.p.m., the O/P from the gear box turns a disc which in turn operates sets of contacts. There is also control relay and valve on small chassis with cover; in good condition. Price 25/- plus 4/6 post.

Power Unit Type 699a

1/P 200-250v, 50 c/s O/P 3V 30v D.C. at 1.5 amp & 80V, H.T. at 40 Ma x 6X3 & P.W. 200V. Max 1/2 amp. 1/2 amp. switch fitted; these were made to supply a number of the 61a units. Complete on chassis with outer cover in new condition. Price £25.0.0 plus 12/6 carriage.

B. SLATER

34 Lifford Street
Sheffield 9

E. R. NICHOLLS

Mail Order and Retail Shop
46 LOWFIELD ROAD
1 off SHAW HEATH, STOCKPORT
CRENSHIRE


RECEIVERS & COMPONENTS
(continued)

TRANSISTORS, UNMARKED, UNTESTED, 40 for 10/-, P. and P. 1/-, 4 packed post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. **K. R. WHISTON** (Dept. PRW), New Mills, Stockport.

TV CHASSIS, 110, with v.h.f. store soled, £5 including carriage. New 19in. TUBES with small spot burns. **VALVE SUPPLY LTD.**, Carlew St., Troo, Cornwall.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.**, Dept. PW7-9, 126 Hamleton Road, West Norwood, S.E.27. OlPay Hill 9166.

MARCONI CANADIAN RECEIVER No. 52

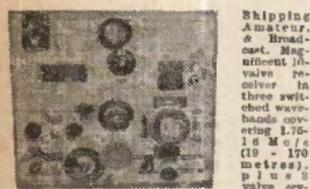

Shipping Amateur. 8 Brass cast. Magnificent in-voice receiver in three switched wave-bands covering 1.76-16 Mc/s (19-120 metres), plus 8 valve crystal oscillator, employing dual crystal to provide marker check at 10,100-1000 kc/s. One IF and two IF stages. Other features include: 47 and signal check meter. Internal S.A. speaker and two H/F outputs with switched control. EP-AP 6in. Noise Limiter, Filter, BFO. Heterodyne pitch control. Wide and Narrow Bandwidth Man. or AVC on CW & RT. Fast and Slow tuning with lock. Additional 08U Tuning (plus & minus). Size 15 x 14 x 1 1/2in. Fully leaved and working. A.C. Mains 200/240v. £14. Carr. 2/-.

No. 52 GROUND-STATION comprising Receiver, Transmitter and 12v. D.C. Power Unit, £27.10.0. Carr. £10.0. (Mainland only).

NATIONAL H.R.O. SENIOR RECEIVERS RT MODEL



4 VALVE 4 WATT AMPLIFIER



light. Valve inspection panel 19 x 7 x 7 in. Brand New in maker's carton, 7/6. Carr. 1/6.

TELEPHONIC AERIAL MASTS. Tubular steel copperplated, spray finish, ring end locking on each section provides for full or any height required. Notable all fixings and base locations. Bottom section 12in. diameter, 30in. (4 sections) Cloned 27in. Dia. Weight 74lb. 55/-, Carr. 5/-, 34lb. (6 sections) Cloned 24in. Dia. Weight 29lb. 70/-, Carr. 5/-, 16lb. (8 sections) Cloned 21in. Dia. Weight 17lb. 44/-, special price for quantities.

ROTARY TRANSFORMER. 12v. D.C. input, 250v. 15/-, output at 125 mA. Size 2 1/2 x 9 1/2in. Brand new 17/6. P. & P. 5/-.

R.F. ANTENNA TUNER (A.T.U.) Calibrated scale, length 160/80/40 metres. Limited number only. Brand new with instructions, 27/6. P. & P. 7/6. Complete list of other bargains 1/-, S.A.E. all enquiries. Credit Terms Available.

A. J. THOMPSON (Dept P.W.)
"HILING LODGE"
CODDICK, KITCHEN, HERTS.
Phone: CDDOOTE 242

BUILD

24 INTERESTING DESIGNS

with your own components and transistors on a printed-circuit chassis.

"EXPERIMENTAL" PRINTED CIRCUIT KIT

Contents

- (1) 2 Copper Laminate Boards 4" x 7" x 1/16"
- (2) Resist. (3) Resistor, (4) Resistor Solvent.
- (5) Cleanser Degreaser.
- (6) 16-page illustrated booklet.

"PRINTED CIRCUITS FOR AMATEURS"

containing full etching instructions. (7) Attractively bound 4" x 2 1/2" for a pocket Transistor Radio, Crystal Set, etc. Suite designs enclosed.

- (8) Miniature Radio Dial SW/MW/LW.
- (9) Miniature Radio Dial SW/MW/LW.

Also free with every kit.

(10) Essential Design Data and Constructional Details on easy-to-build

24 SUGGESTED PROJECTS

which you can build on a P.C. chassis made from this kit. Part Layouts, Circuit Diagrams, P.C. Chassis plans, Assembly Drawings, Photographs. Many recently developed very efficient designs.

- (1) Crystal set with hi-pass detector.
- (2) Crystal set with voltage-quadrupler detector.
- (3) Crystal set with dynamic load.
- (4) Crystal tuner with loudspeaker.
- (5) Carrier Power Conversion Receiver using the B.B.C. signal to bring in distant foreign stations. No 6V or 9V battery.
- (6) Split-Load Neutralized Double Reflex Pocket Loudspeaker Receiver. Uses only 3 transistors in a very sensitive and economical circuit.
- (7) Matchbox or Photocell Radio. Small receiver powered by a single photocell or mercury battery.
- (8) "TRIFLEXON" Triple Reflex with self-adjusting regeneration, variable bandwidth, amplified A.G.C. Uses only 3 transistors in cascade. Each transistor amplifies 5 times. Terrific gain. Excellent selectivity. The best circuit yet invented (Patent Pending). Simplicity of the TRF with the performance of the superhet. Makes possible the construction of extremely low-consumption subminiature radios.
- (9) Reel Battery Loudspeaker Amplifier. Employs photocells to charge a small accumulator. Entirely practical design.

3 SUBMINIATURE RADIO RECEIVERS

The smallest 3 designs yet offered to the Home Constructor anywhere in the World. Based on the "TriFlexon" circuit. Let us know if you know of a smaller design published anywhere. Features: Start-Ramp Radio. Size only 1.62" x 3.95" x .25". (1) Wrist-watch Radio, 1.15" x .95" x .25". (2) Ring-Radio, .70" x .70" x .55". (3) Bacteria-powered Radio. Runs on sugar or bread. (4) Radio Control Beacon. (5) Transistor P/P amplifier. (6) Reel Battery. (7) 1-valve amplifier. (8) Photoelectric Burglar Alarm. (9) Light-Seeking Animal, Guided Missile. (10) Spectroscopic Microscope. (11) Atmospheric Engine. (21) Metal Detector. (22) Simple Transistor Tester. (23) Home Body Radiation Detector. (24) Electronic Man/Woman Discriminator. Thermal Proximity Fuse, etc. P.C. Kit price 7/6. Post and pack 1/-.

Extra copper laminate available.

"YORK ELECTRICS"

181a, York Road, London, S.W.11.

Send S.A.E. for full details

RECEIVERS & COMPONENTS
(continued)

19 SETS (A sets complete) with Power Packs, Control Box and Conectors, tested and working R and T. £6/10/- plus 35/- carriage and packing. Sets only, £4, 20/- c. and P. Head Sets £7. **40 SETS**, new, unpacked complete with 2 Head Sets, Conectors, Hayreswick, £8/10/- carriage 17/6. **WALDEN**, Main Road Garage, South Green, Billerica, Essex.

RADIO-TV-ELECTRONIC COMPONENTS Bargain Prices

NEW TRANSISTORS
OC44, OC46, OC71, O.C.72, OC81m, OC81m, AF117
EF100, 500mA/8V each. Iron Dust Cores 4in. 1/- doz. Bin Low Loss Valve Holders, 1/4 doz. 4 pole 5-way Rotary switches 1/4 each. Fax Panels 6 x 4in. 10d. each. Miniature Condensers 4in. 10d. 10m. 50m. 100m. 100v. all 1/4 each. 1 Condensers 600v. 1/4 each. Miniature, 601, 602, 605, 606, 100 v. 6d. 6d. each. 30 mF, 20 v. 1/4 each. P22 Battery clips with leads 1/- each. Small Instrument Screws 50v. 6d. each. Small 8 soldering Irons 350v. 30 v. set 10/- each. 100mF Condensers 25 v. 6d. each. Edge-wise Volume Controls 5k, with switch, Jap replacement 2/8. Service sheets 2/- each. P. & P. 6d. please.

Maintenor Radio
222 GREAT WEST ROAD HOUNSLOW, MIDDLESEX

SILICON PLANAR Transistors, 18V, 200mW, 100mA max., $\beta=50$ to 300. NEP at 5/6, PNP at 7/-. Brand new. "By Return" service. **ELECTRO-VALUE**, 6 Mansfield Place, Ascot, Berkshire.

PATRICK & KINNIE
81 Park Lane, Hornchurch, Essex.
Romford 44472.

HIGH SPEED MAGNETIC COUNTERS (4x1 1/2in.) 6/12/24v. (scato white). 6/6 ea. P. & P. 1/-.

SANGAMO GEARED MOTORS. 1 R.P.M. 240v, 27/6 each.

40 WATT POWER AMPLIFIERS (E.M.), new boxed, 2 x K66 4 x EF37A, 11.11.0.0. P. & P. 15/-.

FIELD TELEPHONES TYPE "FF" (mint condition), 70/- per pair. P. & P. 10/-.

TELEPHONE HANDETS (latest type) smoke grey 10/- each. P. & P. 2/6.

AMPLIFIED TELEPHONE HANDETS. Built-in transistor amplifier and volume control. Red, ivory, green, black, 35/- each. P. & P. 2/6.

BULK COMPONENT PARCELS 100 capacitors (latest types) 50 pf to 1µf. 250 carbon resistors 4 and 1/2 watt transistor type.

250 carbon resistors 1/2 and 1 watt (all 5% to 10%).

150 hi-stab resistors 1/2, 1 and 2 watt. Exceptionally varied assortment any parcel 10/-, P. & P. inc.

3000 TYPE RELAYS, 10 for 25/-, P. & P. 2/6.

ELECTRIC CHECK METERS (mint condition), 40 amp, 20/- each. P. & P. 5/-.

1st GRADE TRANSISTORS, OC. 23 28/35 36 10/- each, OC. 42 44/45 71/72/73/76/77/81/82 3/- each, OC. 170 4/6 each. A. 128 4/6 each.

SAVBIT, 18 S.W.G. SOLDER, 1lb 7/6. **HEADSET & MIC MOVING COIL** 10/- Set P. & P. 2/6. **DLRS HEADPHONES**, 7/6 pair. P. & P. 1/6. **QUARTZ CRYSTALS** (glass encapsulated) 87G base 9.999 Kc/s or 32 Kc/s, 10/- each. P. & P. 1/6.

RECEIVERS & COMPONENTS

(continued)

SHORT OF MONEY? Turn your Relays and Contacts into cash. S.A.E. for details. 112 Groby Road, Glenfield, Leicesters.



CANADIAN MARCONI 52 RECEIVERS 1.75 to 16 Mc/s as previous adverts. 210.10.0 or with Z612 Power unit for 230v. A.C. E13.0.0, both carriage paid. Handbooks with circuit, 5/-, leaflet S.A.E.

LOUDSPEAKERS 10in. 3 ohm in wood case. Case soiled, 600 ohm Line Transformer, 25/- carriage paid.

CERAMIC Insulated 3 gang variables, 56 x 56 x 35 pF, 2/6, post 1/8.

POCKET WATCHES Ex-Government 15 Jewel Swiss movements, 50/- plus Reg'd. Post, 2/6.

(Carriage charges apply to England and Wales only).

Telephone: Worthing 3097

4042 PORTLAND ROAD, WORTHING

FOR SALE

MORSE MADE EASY!

The Famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum.

One student, aged 20, took only 13 DAYS, and another, aged 71, took only 6 WEEKS to obtain a G.P.O. Pass Certificate. If you wish to read Morse easily and naturally please enclose 8d. in stamps or two international reply coupons for full explanatory leaflet to G3GHS, 15 Green Ln., Purley, Surrey.

240= ELECTRIC POWER ANYWHERE

ANYTIME from 12= CAR BATTERY

with AMERICAN DYNAMOTOR UNIT

12v/12v output 2500 watts in 150 in 220 volts

Perfect for travelling. POWER TOOLS and all

essential A.C./D.C. ELECTRICAL EQUIPMENT, plus

wonderful results from ONLY 12= (plus delivery)

and several tests in full operating details

W.P. SCIENTIFIC PRODUCTS, CHELSEA, LONDON

W.P.

SPECIAL OFFER

GEVAERT TAPE, New, Boxed, 5 $\frac{1}{2}$, 600ft. with Stop and Leader Tapes, 9/- or 8 for 50/-, post paid.

GRUNDIG MA1 2 Transistor Pre-amps for Tape Monitoring or Microphone Boosters, 57/6 post paid.

LIST PRICE 4 GNS.

LEE ELECTRONICS

400 Edgware Road, Paddington 5521

Send for Free Lists and details of above

YUKAN SELF-SPRAY

YUKAN Aerosol spraykit contains 16 oz. fine quality, durable, easy instant spray. No stove baking required. Available in Grey, Blue, Gold, Bronze at 14/11 at our counter or 16/11, carriage paid, per publication self-spray can. **SPECIAL OFFER:** I can plus optional transferable snap-on trigger handle (value 1/2) for 18/11, carr. pd. Choice of 13 self-spray plain colours and primer (motor car quality) also available. Please enclose cheque or P.O. for total amount to:

YUKAN Dept. P.W./4 307a Edgware Rd., London, W.2. (Open all day Saturday, Closed Thurs. afternoon).

FOR SALE

(continued)

ELECTRIC SOLDERING-IRON



FANTASTIC BARGAIN OFFER

Lightweight Pistol Grip Handle 40 watt, 240/250v, A.C. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handy-ONLY 9/6

MAIL. A boon to model makers and a necessity for every wireless enthusiast. Offered to P & P you at this new amazing price.

C. H. SERVICE (Dept. P.W.)

Lusted Hall Lane, Tatsfield, Kent.

SPECIAL OFFER

1 watt S.T.C. 300 mc/s N.P.N. Silicon Planar, 100% Transistors limited stocks. £1 for 6.

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

5/- each. OC139, OC140, GET7, GET8, GET9, EX141, BY100, OA211.

SUN SOLAR CELL KITS

24 page Booklet on Experiments inc. 4 Sun Solar Cells 11/- set.

G.P.O. DIAL TELEPHONES

20/- each. 35/- pair.

Send 6d. for full lists:— inc., S.C.R., Zeners.

CURSONS

78 BROAD STREET
CANTERBURY, KENT

FOR SALE

(continued)

HAMMERITE

HAMMER PATTERN BRUSH PAINT FOR PANELS AND BOXES

* THE PATTERN IS IN THE TIN *
ALL YOU DO IS BRUSH IT ON!

24 oz. tins 7/8 1 gallon 28/-*

1 pint 7/8 1 gallon 55/-*

1 pint 15/- (sent by road)

Carriage: Orders up to 5/-, 9d; up to 10/- 1/8;

over 10/- 2/8.

Colours: Blue, Silver or Metallic Black.

Return of post service, Mon. to Fri.

From your component shop or direct from the manufacturer:

FINNIGAN SPECIALITY PAINTS (PW)

Mickley Square, Stockfield, Northumberland

Phone: Stockfield 2350

WANTED

WE BUY New Valves and Transistors. *Steady price.* A.D.A. MANUFACTURING CO., 416 Aldreton Road, Nottingham.

URGENTLY WANTED: New, Modern Valves, Transistors, Radios, Cameras, Tape Recorders and Tapes. Watches. Tools any quantity. S. N. WILLETTS, 16 New Street, West Bromwich, Staffs. Tel. 2392.

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. HUGGREN'S LTD., 2-4 Fawcett's Road, West Croydon.

WANTED VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

WANTED: Popular Brand New Valves. R.H.S., Stamford Road, 638 Great Horton Road, Bradford 7.

WE BUY New Valves for cash, large or small quantities, old types or the latest. Send details. Quotations by return. **WALTON'S WIRELESS STORES**, 16 Church Street, Wolverhampton.

MISCELLANEOUS

CONVERT ANY TV SET into an Oculiscope. Diagrams and instructions 12/8. **REDMOND**, 42 Dean Close, Portlisle, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classical and Swing.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

METAL WORK

METAL WORK: All types cabinets, chassis racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman St., Loughborough.

BOOKS & PUBLICATIONS

SURPLUS HANDBOOKS

19 set Instruction Handbook ..	8/6 P.P. 6d.
1155 Instruction Handbook ..	4/6 P.P. 6d.
H.R.O. Instruction Handbook ..	8/6 P.P. 6d.
82 set Instruction Handbook ..	5/- P.P. 6d.
35 set Instruction Handbook ..	3/6 P.P. 6d.
46 set Walkie-talkie circuit & notes	3/6 P.P. 6d.
68 set Walkie-talkie Instruction Handbook	5/- P.P. 6d.
Frequency Meter 80221 Instruction Handbook	3/6 P.P. 6d.
Wavemeter Class D Handbook Mr. L. H. Hill	3/6 P.P. 6d.
18 set Circuit Details & Notes A.E.S.D. Instruction Handbook	16/- P.P. 196d.
K.107 Instruction Handbook ..	5/- P.P. 6d.
GR.100 B.S. Receiver Handbook	8/6 P.P. 6d.
R1116A Circuit Diagram & Details	1/6 P.P. 6d.
R1294A Circuit Diagram & Details	1/6 P.P. 6d.
R1355 Circuit Diagram & Details RF 94, 95, 26 Circuit Diagrams, & Details	1/6 P.P. 6d.
Amplifier A1134 Circuit Diagram & Details	1/6 P.P. 6d.
Transmitter T1154 Circuit Diagram & Details (all notes)	2/- P.P. 6d.
Resistor Colour Code Indicators. Indicates the value of a resistor at a glance	1/6 P.P. 6d.

Instructional Handbook Supplies

Dept. PW, Talbot House, 28 Talbot Gardens Roundhay, Leeds, 3

EDUCATIONAL

RADIO OFFICERS see the world! Sea-going and shore appointments. Training vacancies during 1966-67. Granta syllable. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

CITY AND GUILDS (Electrical, etc.) on "Satisfaction or refund of fee" terms. Thousands of passes. For details of modern courses in all branches of Electrical Engineering, Electronics, Radio, TV, Automation, etc., send for 156-page handbook - FREE. B.I.E.T. (Dept. 159K), 29 Wright's Lane, London, W.8.

City and County of Bristol
BRISTOL TECHNICAL COLLEGE

Principal: E. Poole, B.Sc.Eng., M.I.Mech.E., M.I.Prod.E.

CAREERS IN RADIO & RADAR

Marine Radio Officers

2-year full-time course for young men aged 16 upwards, leading to 1st and 2nd class P.M.G. Certificates and B.O.T. Radar Maintenance Certificate.

Conversion Course (2nd class to 1st class).

R.T. Courses (for Full or Restricted Licence).

Training given on the latest types of Marine and Aircraft Equipment in newly equipped Laboratories at

THE SCHOOL OF MARINE RADIO & RADAR

Senior Lecturer: F. E. BARTROP

For details write to:

THE REGISTRAR

BRISTOL TECHNICAL COLLEGE
ASHLEY DOWN, BRISTOL 7

EDUCATIONAL

(continued)

RADIO OFFICERS' Training Courses. Write Principal, Newport and Monmouthshire College of Technology.

TRAIN FOR SUCCESS
WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 PARKGATE ROAD,
LONDON, S.W. 11.

SITUATIONS VACANT

TV AND RADIO: A.M.I.E.R.E., City and Guilds, R.T.E.B. Cert., etc. on "Satisfaction or refund of fee" terms. Thousands of passes. For details of Exams. and Home-training Courses (including practical apparatus) in all branches of Radio, TV and Electronics write for 156-page handbook - FREE. B.I.E.T. (Dept. 137K), 29 Wright's Lane, London, W.8.

RADIO AND TV Exam. and Courses by Britain's finest Home-study School. Coaching for B.I.E.R.E., City and Guilds Amateur's Licence, R.T.E.B. P.M.G. Cert., etc. FREE brochure from BRITISH NATIONAL RADIO SCHOOL, Russell Street, Reading.

A FULL-TIME TECHNICAL EXPERIENCE SALESMAN required for Retail Sales. Write, giving full details of age, previous experience and salary required, to the Manager, HENRY'S RADIO LTD., 38 Edgware Road London, W.2.

SITUATIONS VACANT

(continued)

A.M.I.Mech.E., A.M.I.E.R.E., City and Guilds, G.C.E., etc. Become a Technician or Technologist for high pay and security. Thousands of passes. For details of Exams. and Courses in all branches of Engineering, Building, Electronics, etc., write for 156-page handbook - FREE. B.I.E.T. (Dept. 159K), London, W.8

RADIO TECHNICIAN with a sound knowledge of at least three of the following types of equipment is required immediately for Meteorological Office Ocean Weather Ships: Single Side-band Transmitter, Radar (Navigational), Radar Height Finding, Echo Sounders and Radio Receivers, Automatic D.F., V.H.F. Recorders, Distant Telemetry Equipment. Salary scale £678-£1,304 per annum according to age, plus £120 per annum overtime allowance. Free food and accommodation provided on board ship. Applicants must be married, born British subjects. Full details from Short Captain, Ocean Weather Ship Base, Great Harbour, Greenock. Telephone Greenock 34221.

A book for every enthusiast...

TRANSISTOR
POCKET BOOK

by R. G. Hibberd, B.Sc., M.I.E.E.
Sen. M.J.E.E.E.

A comprehensive guide to the characteristics and use of the various types of transistor now available. The manufacture of the various types of transistor, up to and including the latest epitaxial planar, field of effect and metal-oxide silicon transistors, is described in detail in order to make clear the different characteristics of each. Includes notes on the use and handling of transistors, and chapters on solid state circuit techniques and recent developments.

304 pages 250 illustrations 25s.

From your bookseller, or in case of difficulty,
27s. from G. NEWNES LTD.,
SOUTHAMPTON STREET, W.C.2.

NEWNES



The Famous
E2A COMPASS
as in current use
in Jet Aircraft

This compass which is used on Direction Finders for small craft (see article in Practical Wireless July 1965) is also ideal for Yachts and cars. Noted for its accuracy and steadiness under all conditions, with vertical dial presentation and calibrated every 16 degrees. Liquid filled and gives a direct reading at any angle. Built-in correctors provide correction for co-efficients of expansion. Very popular with gliding enthusiasts & G.C. Very popular with the Government over 210. Our PRICE ONLY £217.8 P.P. 28d.

Send Catalogue now available free. Top quality matches, stop watches, Binoculars, Telescopes etc. Send 6d. postage.

UNITED TECHNICAL SUPPLIES LTD.
Dept. PW.29, Tottenham Court Road,
London, W.1. Telephone: Langham 1116/7

BARGAIN OFFER CORNER

MAINS TRANSFORMERS

Semi-automated drop thro' type. Pri. 300v. 220, 240v. Sec. 250v. 7 wave at 70ma & 6.5v. at 2 step. 4/4.

Stack size 3 x 2 1/2 x 1 1/2. **11/-** P. & F. 21.

PRECISION 6-MINUTE DELAY ACTION SWITCH Clockwork actuated. Made by Bunitis. Separate switching sections at intervals up to 6 mins. Each switch action designed for current loading up to 15 amps. at 250 volts. Suitable for photographic timer, sequence switching operations, etc. etc. Brand new and unused units offered at a fraction of their true value. OUR PRICE ONLY 24/- each. P. & F. 1/5. (3 or more post free). Special quotations for quantity. **HEAVY DUTY NON-INDUCTIVE D/F MICRO SWITCH**. Conservatively rated 10 amps at 250v. Standard one-hole fitting. Body size 1 1/2 x 1 in. deep inc. terminals 9/8 each. P. & F. 1/- (6 or more post free).

WON A.C. MAINS INDICATOR. For panel mounting, cut out size 1 1/2 x 1 in. deep inc. terminal. White case with less giving brighter light. For mains 200/240v. 2/8 each P.F. 5/1. (6 or more post free).

WYAIR AND KEENE SPEAKER AND CABINET FABRICS. Approx. 54in. wide. Usually 85/- yard. OUR PRICE 18/6 per yard length. P. & F. 2/6 (incl. own 3/4 S.A. in. for postage).

ACOS CRYSTAL MIKES. High imp. For desk or hand use. h.c. sensitivity 18/8. P. & F. 2/4.

TEL CRYSTAL STICK MIKE Listed at 45/-. OUR PRICE 18/6. P. & F. 2/4.

T.C.O. SUPPRESSOR CONDENSERS. 250v. A.C. .005 + .005 x 1. In tubular can 2in. long x 2in. dia. 2 for 8/- post free.

TRANSISTOR DRIVER AND O/P TRANSFORMERS. (Tapped 3 ohm and 10 ohm output). Plus 4 suitable Transformers giving approx. 1 watt output 25/- P. & F. 2/6.

3-0-3 GANG 500K TUNING CONDENSERS. 5 1/2 in. x 2 1/2 in. x 2 1/2 in. with built-in trimmer, 4/8, P. & F. 2/4.

MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 x 1 in. Output trans. tapped for 5 and 10 ohm output. 18/- pair. P. & F. 2/4.

BRAND NEW FLEESY. 12v. 4-pin non-syn. vibrators. Type 12 1/2 A.D. ONLY 8/6. P. & F. 1/6.

NEW TELESCOPE ARMILLAR. Comprising 10 sections heavily chromed rods. Closed 12in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, con. lead and plug. Suitable for F.M. or V.F. 18/6. P. & F. 2/4.

4-WAY NON-TANGLE TELEPHONE CABLE. Latest spring back coil type. Length 12m. to 30m. Complete with rubber trolley. 4/8 each. P. & F. 1/5.

SPECIAL BRAND NEW TRANSISTOR BARGAINS

OPT 16 (Matched Pair) 16/-, V16/10p, 10/-; OC71 8/-; OC76 8/-; AF17 12/-.
Set of Hillard 6 transistors OC16, 24—OC48 OC12D matched pair OC21 25/-, ORP12 Cadmium Sulphide Cell 10/8.

EDISWAN MAZDA

FXA101 6/8; 3-0-3 O.K. P. 2/6.
R.F.I. Pack 1—FXA109 Mixer; 2—FXA101 I.F. Amp. (Equip. OC44 and OC45). 10/8
R.F. 2—FXA101 I.F. Amp. 10/8
1—FXA109 Mixer. 2/6
L.F. Pack: Consisting of FXB118 Driver Matched pair FX171 mounted complete with heat sink (Equip. OC12 and OC13). 12/6
ALL TRANSISTORS POST FREE.

SPECIAL OFFER OF LEADING HI-FI MANUFACTURERS SURPLUS!

7-10 watt OUTPUT TRANSFORMERS to match pair of R126/2 in push-pull to 3 ohm output. ONLY 11/- P. & F. 2/6.

7-10 watt ULTRA LINEAR OUTPUT TRANSFORMERS to match pair of EC19/8 in push-pull to 3 ohm output. ONLY 13/- P. & F. 2/6.

SPECIAL MAFS TRANSFORMERS to match either of the above. Tapped primary. Secondary 200v. 20mA half wave and 6.5v. 2 amps. ONLY 12/6. P. & F. 2/6.

SPECIAL HARVERSON OFFER !!!

BRAND NEW HEAVY DUTY 12in. SPEAKERS Response 45 c/s-18 K/c/s. 14in. voice coil. Available in 8 or 16 ohms. Guaranteed full 16 watts British rating. Heavy cast aluminium frames. These are current production by world famous maker and as such are offered well below list price we are not permitted to disclose the name. LIMITED NUM. 12 1/2 x 8in. with high flux ceramic magnet 48/-; 16 ohm. 5in. P. & F. 6in. 2/-; 6in. 2in. 2/6; 10 and 12 in. 8/6 per speaker.

BRAND NEW 3 OHM SPEAKERS

12in. 12/8; 8in. 12/-; 6in. 2in. 2/6; 4in. 2/6; 2/8; 12in. 15 ohm 20/4; 10in. 6in. 2/6; 12in. 12 1/2 x 8in. with high flux ceramic magnet 48/-; 16 ohm. 5in. P. & F. 6in. 2/-; 6in. 2in. 2/6; 10 and 12 in. 8/6 per speaker.

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Maker's Original Packaging SINGLE PLAYERS

GARRARD 9P25 De Luxe. £12.10.6. Carr. 5/6

B.B. GUT with unit mounted pick-up arm. £4.5.5. Carr. 5/6

E.M.I. with unit mounted pick-up arm. £4. 9.6. Carr. 5/6

AUTO CHANGERS

LATEST B.B. GUTS Super 8in. mono. 28.2.8

B.S.R. UA15, 50.18.8; B.S.R. UA18, 50.18.5

GARRARD AT6. £9.10.0 Carr. 5/6 on each.

All the above units complete with 7 1/2 inch head and supplied stylus or be supplied with compatible stereo head for 12/6 extra.

SPECIAL OFFER

of the famous **COLLARO STUDIO 4-speed Semi Transcription Auto Changer Unit**, 200/250v. A.C. Really heavy duty motor and robust mechanism. Stereo wired. Supplied complete with mono cartridge and stylus. Offered at Bargain Price of £5.12.6. Carr. 7/6. Stereo version £6.12.6. ALSO small number of GARRARD Autolinn Changers, with plug-in head complete with Mono cartridge. To clear at £5.10.0 each or with Stereo cartridge 12/6 extra. Carr. 6/6.

NEW CARTRIDGE BARGAINS

MONETTE STEREO 105 CARTRIDGE. Stereo/LP/78 Complete with two styluses. Original list price 67/9. OUR PRICE 24/- P. & F. 1/4.

NEW 105 MONO COMPLETE. List price £11.0. Our price 18/6. P. & F. 2/4.

3 VALVE AUDIO AMPLIFIER MODEL HA34



Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis size 7in. x 4 in. d. x 4 1/2 in. h. Incorporates IC058 EL84, E2200 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass. Treble and volume controls. Negative feedback loop. Front panel can be detached. Output and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, £4.5.0/- P. & F. 2/6. wire and tested for only.

TYPE BEL 'FOUR' AMPLIFIER


3 VALVE 4 WATT USING EC088 EL84, E2200 VALVES
For A.C. mains 200/240.
Special features included:
● Heavy duty double-wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● All this builds on to a chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur construct with 100% success. ● Supplies complete with valve output transformer (3 ohm only), screened lead, wire, nuts, bolts, solder etc. (No extras to buy). **7/6** P. & F. 2/6.

Comprehensive circuit diagram, practical layout and parts list 9/6. (Free with Kit).

This kit although similar in appearance to HA34 employs entirely different and advanced circuitry.

STEREO AMPLIFIERS

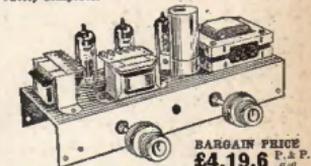Incorporates 2 EL24's and 1 E2200 heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



BARGAIN PRICE P. & F. **£4.19.6**

SUPER DE LUXE version of above incorporating EL250 valve separate bass and treble controls and full negative feedback. £5.5.5. P. & F. 6/6.

QUALITY RECORD PLAYER AMPLIFIER

A top quality record player amplifier. Size 7in. w. x 2 1/2 in. d. x 5 1/2 in. h. This amplifier was used in a 20 in. record player employs heavy duty double-wound mains transformer, IC058, EL84 E2200 valves separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Heavy built and tested.

PRICE 6/16 P. & F. 4/9.

ALSO AVAILABLE mounted on board with output transformer and 4in. speaker wire to fit into cabinet below. PRICE 38/6. P. & F. 5/9.

QUALITY PORTABLE R PLAYER CABINET

Truly modern build. Will take above amplifier and B.S.R. or GARRARD Antiochanger or single Record Player Unit. Size 18 x 14 x 9 1/2 in.

PRICE £39.6. Carr. 7/6

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT



Type TA1

● Peak output in excess of 13 watts. ● All standard British components. ● Built on printed circuit panel size 6 x 3in. ● Generous size Driver and Output Transformer. ● Output transformer tapped for 3 and 16 ohm speakers. ● Transistors (GZT114) or ST Mullard OC81D and matched pair of OC21 types for 3 v operation. ● Everything supplied, including clips, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram. 1/4- (Free with Kit). All parts sold separately.

SPECIAL PRICE £5. 8/- P. & F. 3/4.

Also ready built and tested £26/6. P. & F. 5/4. A pair of TA1's are ideal for stereo.

10/14 WATT HI-FI AMPLIFIER KIT

A component amplifier with an output of 14 watts f r e q 2 EL84's with 2 1/2 inch speaker reduction of 1/2 inch music and a p e e c h with negligible hum. Separate inputs for mike and gram, allow records shrouded section wound output transformer to match 3-15 oh speaker and independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 3 EL84's EC088 EF86 and E2200 rectifier. Simple instruction booklet 1/5. (Free with parts).

ONLY £6.19.6 P. & F. 8/0

All parts sold separately. £6.19.6 P. & F. 8/0

Also available ready built and tested complete with standard input sockets. £25.10.0. P. & F. 5/4. Carrying case for above 28/6. P. & F. 7/6.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985

Open all day Saturday Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station (Please write clearly)

PLEASE NOTE: P. & F. CHARGES QUOTED APPLY TO U.K. ONLY. P. & F. OVERSEAS ORDERS SHOWN EXTRA.

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE RIGHT HAND PAGE FOR MORE ITEMS

TEST METERS



20,000 O.P.V. MODEL TP 58. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +35. Size 3½" x 5¼" x 1½". £8.19.6.

2,000 O.P.V. MODEL TP 10. Reads A.C. and D.C. Volts up to 1,000 D.C. Current to 500mA; Resistance to 1 Meg.; Capacitance to 1µF; Decibels from -20 to +35; Output jack for Audio Measurements. Size 3½" x 5" x 1½". £5.19.6.

50,000 OHMS PER VOLT MODEL 500. Reads voltage up to 1,000 D.C. at 50,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. current to 10 amps. Resistance to 50 Megs.; Decibels from -20 to +55; Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3½" x 6½" x 2¼". £9.19.6.

50,000 OHMS PER VOLT TESTMETER MODEL 700. Reads A.C. and D.C. voltage up to 1,000 Alternating and Direct Current up to 10 amps. Resistance up to 50 Megohms, Decibels from -10 to +40dB. Internal buzzer for audible warning of short circuits or continuity and fitted with automatic overload protection for movement. Meter size 4½" x 2½", overall dimension 7¼" x 5¼" x 3¼". Has rigid handle which can be swivelled for use as a G.K. support. ONLY £17.19.6.

TRANSISTORIZED TEST EQUIPMENT. Fully guaranteed, brand new. By NOMOREX: 160 Kcs.—300 Mc/s. Signal Generator, £9.10.0. Resistance-Capacitance Bridge, £8.5.0. 1-10 villo D.C. Power Supply, £8.10.0. Audio Generator, 10/100,000 etc., £16.15.0. Inductance Bridge, £15.0.0.

VALVE VOLTMETER. D.C. Input Impedance 11 Megohms. 7 Voltage ranges, D.G. to 1,500 A.C. to 1,500 R.M.S., 4,200 Peak to Peak. Resistance 3 ohms to 1,000 Megohms. Constant zero setting for receiver alignment. Complete with A.C./D.C. probe and leads. Full illustrated details on request. ONLY £19.0.0 (Post 2/6).

FREQUENCY METERS TYPE LM. Frequency range 120-10,000 kc/s. In 2 bands. Type 1, United States Navy Model of the well-known BOZEL Frequency Meter, but has many additional features which increase its usefulness. Voltage stabilisation circuit and Crystal control ensure extreme accuracy and in addition it is fitted with an Internal Modulation switch to allow use as a Signal Generator. Size only 5¼" x 5¼" x 5¼". ONLY £15.

VARIABLE VOLTAGE TRANSFORMERS. Fully shrouded. Input 250 v. A.C. 50/60 cycles. Output 0-200 v. 2.5 amps. type £5.17.6. 0 amps. type £5. 10 amps. type £10.0.0. 20 amps. type £52.10.0.

STANDARD TRANSFORMERS
Vacuum impregnated, interlocked E.S. screen Universal mounting. Size 4in. x 3¼in. x 3¼in. ALL BRAND NEW 15/6 each. Post 2/6.
Type 1. 250-0-250 v. 50 mA. 5-5 v. 3. tapped at 1.4, 4, 8, 0.2 v. 3. tapped at 4 v. and 5 v.
Type 2. As above but 550-0-550 v. 50 mA.
Type 3. 30 v. 2.5 a. tapped at 12, 15, 30, and 24v. to give 3-4-5-6-9-10 v., etc.

HARRIS ELECTRONICS

(London) LTD.

138 GRAY'S INN ROAD
LONDON, W.C.1.

Telephone: TR 611111 7057

Please include carriage cost on ALL orders.
Trading hours 9 a.m.—6 p.m., Monday—Friday,
Closed Saturday, With 2 miles from High Holborn (King's Lane Station) and 5 mins. by bus from Chancery Cross.

PRICE

SPECIAL RADIO CHASSIS OFFERS

HI-FI CONTINENTAL STEREOPHONIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed autochanger. Complete £29.19.6. Chassis only 19! gns. Special terms available of £4.10.0 deposit followed by 18 monthly payments of £1.13.0 (total H.P. of £34.4.0) + 15% P. & P. Send £5.5.0 now.


IMPERIAL HI-FI STEREOPHONIC RADIOGRAM CHASSIS



The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons, Long-Medium-Short and VHF bands. Complete with two 10" loudspeakers plus a mono-stereo 4 speed automatic record changer. Complete 39! gns. Chassis only 27! gns.

Special terms available of £6.4.6 deposit followed by 24 monthly payments of £1.15.0 (total H.P. £44.4.6) + 17½ P. & P. Send £7.2.0 now.

HI-FI EMPRESS RADIOGRAM CHASSIS

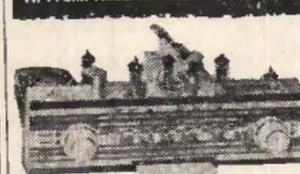

This fabulous 'Empress' Hi-Fi Radiogram chassis is offered complete with 10" loudspeaker plus 4 speed autochanger. At only 23 gns. this is the bargain of the year. Chassis only 15! gns. Special terms available of £3.12.6 deposit followed by 18 monthly payments of £1.6.7 (total H.P. £27.11.0) + 15% P. & P. Send £4.7.6 now.

All Lewis Radio equipment including valves are fully guaranteed for one year. Send your cheque or P.O. today while stocks last. Dept. P.46.

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.16. Telephone: PAL 3733/9666

SWLs · SWLs · SWLs · SWLs

Hark!

Hark!

-the DX is calling!



Special RX tuner
4½" x 3½" x 3½"

JOYSTICK

Variable Frequency ANTENNA SYSTEM

This revolutionary and pat. pend aerial system possesses the unique property of an even response over all frequencies between 1.2-30 Mc/s. Every JOYSTICK Aerial System is supplied complete with feeder and an aerial matching unit. Just connect your RX—it is ready to go and gives an unprecedented 3dB signal strength especially for 'lift' and 'wave' dwellers—EVEN FROM UNDERGROUND! Naturally the advantages of using the 'JOYSTICK' 'up-in-the-clear' are stress greater!

4,900 Joystick aerials all over the world have already shown that this is the first major break-through for 20 years in the field of aerials. The performance for such a compact unit (7" assembled) is staggering. Even the sceptics have been convinced once they have understood the basic principle and have followed the simple 'tune-up' procedure given in the detailed instructions.

New Joystick Range

There is now a whole new range of Joystick Aerial Systems—made to match your QTH, your rig and your pocket! The SYSTEMS cover SWL, T.X.I.N., indoor and outdoor mobile and even a new JOYSTICK Match only in the finest materials the SYSTEMS are reliable and permanent! Read all about them in our new brochure—

GUARANTEE: Partridge operate a rigid 100% Money Back Guarantee if you're not completely satisfied!

Read testimonials from all over the world! Four different receivers showed improved performance over a 'dipole' reports the U.S.A. C.Q. Magazine.

"Excellent results, Australia, Oeynho, Bost. Africa, as good strength although later weather conditions have been poor." W. Cummings, Lonsmouth, Scotland.

READ ALL ABOUT IT!

This ticket will bring you the new brochure by return of post.

PARTRIDGE ELECTRONICS LTD.
Caister House, Prospect Road,
Broadstairs, Kent. Tel. TRAFNET 62555

NAME


ADDRESS

.....

PRACTICAL WOODWORKING

MONTHLY 2/6

Nº 2 OUT
MARCH 10

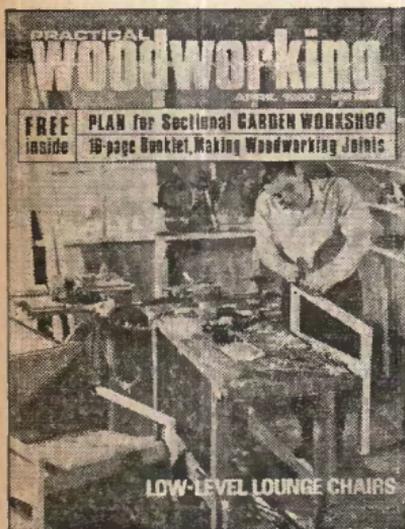

Also in the April issue

**LEISURE CHAIRS FOR
LOUNGE OR LOGGIA**

SUN LOUNGE FOR SMALLER HOUSE

BOW-FRONT WARDROBE

FLOWER-POT TROUGHS

BEDSIDE CUPBOARD

**WOODTURNING FOR PLEASURE
AND PROFIT**

**A NEW 'PRACTICAL' FOR
THE EXPERIENCED AMATEUR
AND THE BEGINNER**

Packed with fascinating new projects, new ideas and new techniques, PRACTICAL WOODWORKING, brings you the guidance you need to tackle any kind of woodworking job with the flair and finish of a professional.

FREE! 16-Page Booklet
**HOW TO MAKE
WOODWORKING JOINTS**

Covers every type from simple notched and tenon to modern glue-laminating techniques.

FREE! Construction Plan for
SECTIONAL GARDEN WORKSHOP
Full instructions on construction and erection.

EXTRA! Fold-out Sheet to Build
• **JOINER'S TOOL BOX**
• **FOLD-AWAY WORK BENCH**

EXTRA! Locks and Hinges Data Sheet

BIG DEMAND! MAKE SURE OF YOUR COPY - 2/6

D. & B. TELEVISION (WIMBLEDON) LTD.

131 KINGSTON ROAD · SOUTH WIMBLEDON · LONDON S.W. 19

Telephone: CHerrywood 3955

ALL BRAND NEW VALVES GUARANTEED 3 MONTHS

Postage and Packing on Valves 6d. each.


AZ31	10/6	EF90	7/-	PCF90	8/4	UCH81	7/8	6EP8	10/9
DAF91	7/10	EF86	7/-	PCF82	9/4	UCH82	8/8	6EP8	8/8
DAF99	7/10	EF86	9/4	PCF96	10/6	UCH88	10/8	6L1	15/6
DF01	6/8	EF89	7/-	PCF801	10/-	UP41	7/6	6L18	12/6
DF92	6/8	EP91	11/-	PCF802	10/-	UP42	9/-	6L18	9/8
DF96	7/10	EP92	11/-	PCF866	10/-	UP80	7/6	10C2	12/-
DK01	7/10	EP183	9/8	PC183	8/4	UP86	7/6	10F1	8/8
DK92	7/10	EL33	10/8	PC183	8/8	UP89	7/6	10F8	8/8
DK96	7/10	EL34	9/8	PC184	8/8	UL1	7/8	10F18	8/8
DL92	9/8	EL36	9/8	PC186	8/8	UL46	10/6	10F18	12/6
DL94	6/8	EL41	8/-	PL36	8/8	UL84	8/8	10F14	12/6
DL96	6/8	EL84	6/4	PL36	10/-	UY11	5/8	20F3	11/-
DY86	7/10	EM30	7/8	PL31	8/4	UY85	5/6	30F1	12/6
DY97	7/10	EM81	7/8	PL82	6/4	SV3	5/6	30F1	15/-
EABCO80	7/6	EM84	8/8	PL43	8/4	524	7/6	30F3	12/-
EAP49	5/6	EM85	10/-	PL88	7/-	6V8	7/7	30F4	13/-
EBO1	5/6	EV31	7/-	PL50	14/-	6X9	7/5	30P9	13/-
EBE33	11/8	EV86	7/-	PY33	9/8	K19	14/8	30C16	12/6
EB041	7/8	EZ40	6/8	PY90	9/8	U26	6/4	30C17	11/8
EB081	6/8	EZ41	5/4	PY81	10/-	U26	10/6	30C18	10/-
EBF80	7/-	EZ60	5/6	PY82	5/6	U181	9/8	30F5	10/-
EBF89	7/-	EZ61	5/6	PY83	5/6	U180	9/8	30F11	10/8
EC081	7/4	EZ90	5/-	PY88	5/6	U301	11/8	30G16	12/6
EC082	7/4	GZ80	11/-	PY80	7/-	U281	18/9	30G17	9/6
EC088	7/4	GZ84	11/-	PY801	7/-	U382	18/9	30G18	9/6
EC084	7/8	HBC90	6/4	UABC50	7/-	U301	18/9	30F4	12/-
EC086	7/8	FABCO90	7/8	UBC41	7/-	U09	8/8	30F19	12/6
ECF80	8/6	FC86	8/10	UBC81	7/-	U09	9/8	30F11	12/6
ECF88	13/-	PC088	8/10	UBF90	7/-	8F1	12/8	30F13	12/6
EMH42	8/6	PC97	7/8	UBF88	7/-	8F13	12/8	30F14	12/6
EM81	8/6	PC084	7/8	PC084	7/-	8F10	15/-	30F12	10/6
EM050	7/4	PC085	7/4	UC088	7/4	8F15	18/6	30F14	10/6
EM088	8/8	PC088	12/6	UCF89	9/4	8F28	20/6	30F14	10/6
EM088	10/8	PC089	10/8	UCH42	9/8	8F24	10/9	30F18	10/8
EM088	8/8	PC088	10/8						

We are open 9 a.m. to 6 p.m. Monday, Tuesday, Thursday and Saturday; 9 a.m. to 10 p.m. Friday. Closed all day Wednesday

SERVICE SHEETS TELEVISION !! ALL MAKES AND MODELS 4/- P. & P. 4d.

FAMOUS FOR THIRTY YEARS for
SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS

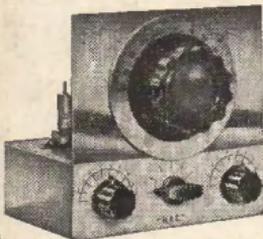

H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Home, etc.

IMPROVED 1966 RANGE

1-Valve model "OX", complete kit, Price 34/6
Customers say: "Definitely the best complete S.W. kit available at any price". This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and, of course, as all our products, fully guaranteed. **FULL RANGE** of other kits still available including the famous model "K", price 77/-. Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to:—

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. P.W.), 44 Old Bond St., London W.1

WORLD RADIO & TV HANDBOOK 1966, 28/-

by JOHANSEN, postage 1/8.

ABC's of Electronic Organs by Crowhurst. 16/-. P. & F. 1/-.
Electric Guitar Amplifier Handbook by Durr. 24/-. P. & F. 1/-.
Transistor Circuit Manual by Lytel. 35/-. P. & F. 1/8.
Transistor Electronic Organs for the Home Constructor by Douglas. 18/-. P. & F. 1/-.
Transistor Substitution Handbook, new ed. 15/6. P. & F. 1/-.
10 Ways to use your Signal Generator by Middleton. 18/-. P. & F. 1/-.
Practical Transistor Servicing, new ed. by Caldwell. 24/-. P. & F. 1/-.
Where possible 24 hours service guaranteed

UNIVERSAL BOOK CO.
12 LITTLE NEWPORT STREET,
LONDON, W.C.2
(adjoining Lisle Street)

DIGITAL COMPUTER

A simple digital Adder/Subtractor using switches and lamps only. A fascinating demonstration of Binary Arithmetic. Full circuit, wiring diagrams and notes on the Binary system. 5/6.
NOUETS AND GROSSES MACHINE Uses standard miniature switches and lamps only. This machine cannot be beaten. Full circuit, wiring diagram and instructions. 5/6.

1% High Stability Resistors
± watt 1%, 2/- each. Full range 10 ohms to 10 Meg. Many special values for meter multipliers etc. in stock.

1% Wirewound Resistors
1% 1 watt, 1 ohm to 5K, 3/- to 20K, 4/8; ± watt 3d. Your value wanted to order. Shunts down to 0.1 ohm.

High Resistance Phetnet, 10/-, post 1/-
100 Resistors, 1, 2 and 5% assorted, 9/8.
Signal Injector Kit, 10/-, post 1/-.

PLANET INSTRUMENT CO.

26 (W) DOMINION AVENUE, LEXXES

BBC2 (625 LINE) TV AERIALS



Maat Mounting Arrays, 9 element 45/- wide spaced high gain, 11 element 55/-; 14 element 62/6. **Wall Mounting with Cranked Arm 9 element 60/-** wide spaced, high gain, 11 element 67/8; 14 element 75/-. **Chimney Arrays Complete, 9 element 72/-**; wide spaced high gain, 11 element 80/-; 14 element 87/6. **Loft Arrays, 7 element 32/8**; wide spaced high gain, 11 element, with Tiltting Arm. 62/6; 14 element 70/-. All high gain units have special Multi-co Reflector. Low loss co-axial cable 1/6 per yard. UHF transistor pre-amps from 75/-.

BBC · ITV · F.M. AERIALS

BBC (Band 1), Telescopic lot 21/-, External 5/10 30/-.

ITV (Band 3), 3 Element lot array 25/-, 5 element 35/-, Wall mounting, 3 element 35/-, 5 element 45/-.

Combined BBC/ITV Lot, 1-3, 4/8; 1-5, 48/9; Wall mounting 1-3 55/3; 1-5, 63/9; Chimney 1-3, 63/9; 1-5 71/3.

UHF transistor pre-amps from 75/-.

F.M. (Band 5), Lot 5/10 12/6, "ITV" 90/- 3 element, 52/8. External units available Co-ax cable 9d. per ft. Co-ax plus, 1/8.

Outlet boxes 4/6, C.W.O. or C.O.D. P. 4/6. Send 5d. stamps for illustrated Home.

K.V.A. ELECTRONICS (Dept. P.W.)

27 Central Parade, New Addington

Surrey
L0D 2266

Your complete basic guide devoid of mathematics and circuitry

BEGINNER'S GUIDE TO COLOUR TELEVISION

by Terence L. Squires, A.M.Brit.I.R.E.



Explains fully how the signals are created in the television studios, how they are transmitted and the techniques used to receive and display them. Covers: Historical Outline - The Colour Signal - The Chrominance Signal - Colour Transmission - Receiving the Colour Signal - Domestic Aerial Systems - The Receiver Block Diagram - The SECAM Receiver etc.

128 pages, 58 diagrams
only 15s. net
from all booksellers

... or, in case of difficulty, 16s 3d by post from George Newnes Ltd., Tower House, Southampton Street, London W.C.2.

NEWNES

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDEGE, YORKS.

Telephone: Cleckheaton 2888

18 Set Receiver, 4 Valve Battery 8/4 6-9
mois. Clean condition 19/6. Post. 5/-
68 Set Receiver, 4 Valve Short Wave
Battery Set, New 15/6. P/P 6/-
500 Micro-Amp Meter from 18 Set Tx.
7/5. P/P 1/9.
New 500 Micro-Amp Meter from 68 Set Tx.
12/8. P/P 1/5.
Hairhead Eastern Slow Motion Drives.
Removed from units 6/- P/P 1/6.
Magic Eye with Holder, Six Units Octal
Base 2/6. P/P 1/5.
New Boxed Tube Unit, CR100, Complete
with Two small CRT Tubes VCRX283 and
VCRX286. Plus 21 small valves and 0-1ma.
meter. Relays removed, 87/-. Carr. 10/-
Reclaimed Tubes, Six months' guarantee.
AW43/90, 30/-, MW43/90, 30/-, MW43/88, 30/-,
CRM172, 30/-, CRM142, 17/-, 12" Tubes 10/-
17" tubes perfect but without guarantee,
17/- each. Carriage on any tube in G.B. 10/-
Specially Selected Nearly New Valves
with 8 months' guarantee. Single valves
Post. 1d.


PY33	6/-	807	5/-	EP91	2/-
PC081	8/6	ARP12	1/6	6K7	1/9
PCP30	5/6	ECL42	3/6	ECL3	3/6
PL26	8/-	ECC83	6/-	6V6	1/9
PL81	5/6	BCC82	4/3		

VALVE LIST

Ex Equipment, 3 months' guarantee.
Single Valves Post 7d.

EF86	1/6	KT88	5/-	6F14	5/-
BCL80	1/6	PCP80	2/-	10C2	5/-
EF91	9d.	PC084	2/-	10P19	2/6
EBB1	9d.	PCL82	4/-	10P14	2/-
EBF80	3/-	PCL83	3/-	20D1	2/-
ECC81	3/-	PCL84	3/-	20L1	5/-
ECC82	3/-	PCL55	3/-	20P1	4/-
ECC83	4/-	PZ30	5/-	20P4	8/6
EL84	5/-	PY81	1/6	U801	8/6
EY51	2/6	YF82	1/6	U826	5/-
EF50	1/-	PL81	4/-	U811	5/-
PY86	5/-	PL36	5/-	U191	5/-
6K25	5/-	PY33	5/-	U281	5/-
6U4	5/-	859	1/6	U282	5/-
6P25	5/-	8F1	1/-	U25	6/-

Motors removed from Washing Machines
4 h.p. with pulley, 26/-. Carriage 10/-
Hoover MK1, 15/-, Carriage 7/6, h.p. motor,
13 Amp. Double sockets, Brown Surface
Type, 3/-, Post 1/6, 6 for 18/-. Post Paid.
New Jap Earpieces complete with lead and
plug, 8 ohms, 3 or 6mm., 1/11 or 20/- per doz.
Post Free.
Diodes, Top grade. No duds 3/- per doz.
Post Paid.
Perfect Speakers removed from T.V. sets.
Round 3", 6/-, 6ola 6 x 4, 8/-, Goodmans
7 x 4, 5/-, 6" Round, 3/-, Philips 5" Round,
3/-. Plus Post on any Speaker 2/9, 6 x 4,
6" and 5" Round Speakers, 6 for 20/-, Post
Paid.

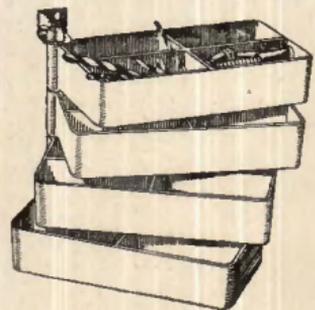

SWIVEL STORAGE RACKS. Ideal for
Nuts and Bolts, Resistors, etc. Unbreak-
able Plastic Trays 5 1/2" x 3" x 1 1/2" with Two
Divisions with Brackets for fixing to wall.

- 4 trays 6/-
- 6 Trays 9/-
- 8 Trays 12/-

P. & P. 1/4 any size.

JIGTOOLS, PENTYRCH, CARDIFF

LEWIS EQUIPMENT CABINETS OF DISTINCTION



Imperial

- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These Cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

FREE THE NEW LEWIS RADIO CATALOGUE

Designed to assist your choice of Cabinet.
The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE!
Please send your FREE cabinet catalogue.

NAME _____

ADDRESS _____

(Dept. P.46)

Capitals please

LEWIS radio

100 Chase Side, Southgate, London
Tel: Palmers Green 3733/9666

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel.: P.A.R. 5641/3/5
Please write for full catalogue

Z & IAERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office
When sending cash with order, please include 2/6 in p/c postage and handling
MINIMUM CHARGE 1/6. No C.O.D. orders accepted

Retail Shop:
85 TOTTERHAM COURT ROAD
LONDON W1
Tel.: L.A.H.A.M. 8403
Open all day Saturday

Table of electronic components including transistors, diodes, and tubes. Columns include part numbers, descriptions, and prices. Includes a 'First Quality Fully Guaranteed' logo and a 'CATHODE RAY TUBES' section.

TRANSISTORS table listing various transistor models and their prices.

DIODES table listing various diode models and their prices.

CATHODE RAY TUBES
3BT-1-A recommended for P.E. Diode Oscilloscope, 3rd dia. screen; 6.3v heaters. Max. EHT 1500V, 50/-
D07-5, 2nd screen; EHT 800v; 6.3v heaters, 50/-
89G Tube Base, 1/6
468A, 1st screen, EHT 800v; 4.0v heaters. Blue shot resistive screen suitable for photography, 60/-
B9 Tube Base, 1/6
5P7, 5th screen, yellow low persistence coating. Magnetic focusing and deflection, EHT 6000v. Exceptional brightness of the trace, 12/6. B14 Base, 8/6
SUB-CHASSIS EK YR 1934/5 AIRCRAFT TRANSMITTER-RECEIVER
1 Transmitter and Receiver Chassis (available in 100-250 Mc/s or 12.4-0.145 Mc/s, 15/-)
3 I.P. Chassis Type 676, 9.72 Mc/s, 15/- P.P. 5/- per chassis
These units are not in themselves complete and cannot be used as complete transmitter or receiver. They are however, eminently suitable for use as sub-units in Amplifiers, Tuners, etc.

PRACTICAL WIRELESS

blueprints

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-FEATURE BLUEPRINTS

SINGLE-FEATURE BLUEPRINTS

The Strand Amplifier } The PW Signal Generator }	5/-	The Tutor } The Citizen }	5/-
The Savoy VHF Tuner } The Mayfair Pre-amplifier }	5/-	The PW Pocket Superhet }	5/-
The Berkeley Loudspeaker Enclosure } The Luxembourg Tuner }	5/-	The PW 35-watt Guitar Amplifier }	5/-
The PW Troubadour } The PW Everest Tuner }	7/6	The Mini-amp }	5/-
The PW Britannic Two } The PW Mercury Six }	6/-	The PT Multimeter }	5/-
Beginner's Short Wave Two } S.W. Listener's Guide }	5/-	The Beginner's Short Wave Superhet }	5/-
Beginner's 10-watt Transmitter } Transmitting and Aerial Data... .. }	5/-	The Empire 7 Three-band Receiver }	5/-
PW "Sixteen" Multirange Meter }	5/-	Electronic Hawaiian Guitar }	5/-
Test Meter Applications Chart }	5/-	Progressive Short Wave Superhet }	5/-
The Celeste 7-transistor Portable Radio } The Spinette Record Player }	5/-		
Transistor Radio Mains Unit }	5/-		
7 Mc/s Transceiver }	5/-		

PLEASE NOTE that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

QUERY SERVICE

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 7th April, 1966 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, APRIL, 1966

16 PAGE TRANSISTOR LIST

Send 1/- stamp for new list
all types of semi-conductors.

1



2



3



4



5



6



7



8



9



10



11

NEW 1966 CATALOGUE 150 PAGES

Fully detailed and illustrated components, equipment.
Complete range of High Fidelity equipment in Stock.
All types and makes. 5000 Stock lines. The Finest
and largest Range available. A mine of information.

Price 6/- post paid.

FREE with Catalogue. 6/- Discount vouchers gives
2/- in pound discount on purchases.

CATALOGUE COSTS NOTHING AFTER USING VOUCHERS



(1) **GLOBEMASTER
MW/LW/SW PORTABLE**
Full 3-waveband tuning. Pushbutton
wavechange. Superhet printed circuit.
Black-chromed cabinet 11 x 7 1/2 x 3 1/2 in.
(SW 17-50 metres). Ear/Record sockets.
TOTAL COST £8.19.6 P.P.
TO BUILD 3/6.
* Building instructions on request.

(6) **VHF FM TUNER**
87/105 Mc's Transistor Superhet.
Geared tuning. Terrific quality and
sensitivity. For valve or transistor
amplifiers. 4 x 3 1/2 x 2 1/2 in.
TOTAL COST £6.19.6 P.P.
TO BUILD 2/6.
(Cabinet Assembly 20/- extra)
* Circuit and details on request.

10 AND 20 WATT TRANSISTOR MONO AND STEREO HI-FI UNITS

(2) **POWER AMPLIFIERS.** 10 watts
RMS output. 100mV input. 30c/s to
20kc/s — 1dB. 6 transistor. Push-pull.
Panel size 4 x 2 1/2 x 1 in. H/S 4 x 4 in.
TPA10/3 3.5 ohm spkr. **£5.10.0, p.p. 2/6**
TPA10/15, 12-16 ohm spkr.,
£5.19.6, p.p. 2/6
(Mains unit for 1 or 2 amplifiers,
59/6, p.p. 2/6)

(3) **PREAMPLIFIERS.** 8 input
selector. Treble, bass, volume, filter
controls. 1 1/2mV to 300mV inputs.
Battery operated or from Mains Unit.
Output up to 150mV RMS.

MP2 Mono 9 1/2 x 2 1/2 x 2 in. **£5.10.0, p.p.**
2/6 (brown and gold front panel 8/6).
SP4 Mono/Stereo, 9 x 3 1/2 x 16 in.,
£10.19.6, p.p. 3/6 (front panel plate 12/6)

The Finest High Fidelity at
Unbeatable Prices(4) **DEAC RECHARGE-
ABLE CELLS**Special offer at a fraction of
normal price. Brand new

- 3.6 volt 500 mA/H
1 1/2" x 1 1/2" diam 12/6
- 9.6 volt 225 mA/H
2 1/2" x 1" diam 20/-

HI-FI
WE CAN NOW
SUPPLY FROM
STOCK ALL MAKES
OF HIGH FIDELITY
EQUIPMENT
Special Parcel
Prices. Send list of
requirements for
quotation.

(9) **MICROPHONES**

- ★ Professional 50K ohms
Dm301 79/6
- ★ 50k Stick Dm107,
Dynamic 69/6
- ★ 100c Xtal Sock
with stand 32/6
- ★ BM3 Sock Mic. Xtal 47/6

(5) **BUILD A TAPE RECORDER**
Three speeds—3 watts.Complete kits with new "363" decks.
Supplied as preassembled sections.
Complete with portable cabinets and
Speaker—excellent quality.★ **TWO TRACK** ★ **FOUR TRACK**
£26 P.P. £30 P.P.
8/6 8/6(7) **5 WATT AMPLIFIER**6-Transistor Push-pull, 3 ohms, 6mV
into 1k. 12-18V supply. 27 x 2 x 1 1/2 in.
BUILT AND TESTED 79/6 P.P.
(optional mains units 64/- 2/-
p.p. 2/-). Leaflets on request.
New matching Preamplifier, 6 inputs,
treble/bass/selector/volume controls. 6-
10mV o/p. 9-18V supply. 79/6, p.p. 2/-(8) **REGENT-6****MW/LW POCKET RADIO**
6-transistor superhet. Geared
tuning. Push-pull output. Moulded
cabinet 5 x 3 x 1 1/2 in. Phone
socket. Leaflet on request.**TOTAL COST 85/- P.P.**
TO BUILD 2/-

MULTIMETERS

PT34	1k/V	39/6	TP55	20k/V	£5.19.6
M1	2k/V	49/6	EP30k	30k/V	£6.10.0
EP10	2k/V	75/-	EP50k	50k/V	£8.15.0
EP10k	10k/V	79/6	500	30k/V	£8.17.6
ITL-2	20k/V	89/6	EP100k	100k/V	£10.10.0
EP20k	10k/V	99/6			See catalogue for details

GARRARD DECKS — BRAND NEW FULLY GUARANTEED

1000 mono	£8 10 0	AT5 stereo	£8 0 0	AT90 loss cart	£11 10 0	AT5 mono	£2 19 6
1000 stereo	£8 19 6	SP20 loss cart	£10 10 0	AT50 mono	£11 19 6	AT6 Stereo	£8 19 6
2000 mono	£8 19 6	SP15 stereo	£11 19 6	AT50 stereo	£11 19 6	AT9 Derran	£11 19 6
2000 stereo	£7 20 0	BP25 stereo	£11 10 0	AT80 Derran	£14 10 0	Deezleed MkII	£17 0 0
3000lm stereo	£8 19 6	SP25 Derran	£11 19 6	LA350 loss cart	£85 0 0	(Chart. 3/- ext. any mod.)	

(11) **QUALITY MW/LW
SUPERHET TUNER**New printed circuit transistor design.
Output for any valve or transistor
amplifier. Full coverage with excellent
sensitivity and selectivity. 9 volt
operated. Complete with front panel
etc. Size 6" x 2 1/2" x 1 1/2".
TOTAL COST 79/6 P.P.
TO BUILD 2/-(10) **ROADSTER
MW/LW CAR RADIO**Supplied as Preassembled Panels.
Permeability tuned superhet. Push-
button wave-change. Push-pull out-
put. Fits any car. 7 x 4 x 2 in. 12 volt
(+) earth. Circuit on request.**ASSEMBLY £8.19.6 P.P.**
TOTAL COST 3/6
(Speaker/Baffle/Car Fixing Kit. 20/-)

HENRY'S RADIO LTD.

303 EDGWARE ROAD, LONDON W2
PADington 1008/9
Open Mon. to Sat. 9-6, Thurs. 1 p.m.
Open all day Saturday.● LET US QUOTE FOR PARTS
FOR YOUR CIRCUIT. SEND LIST OF
PARTS FOR QUICK REPLY. MOST
PARTS IN STOCK FOR ALL PUBLISHED
DESIGNS. LOWEST PRICES.