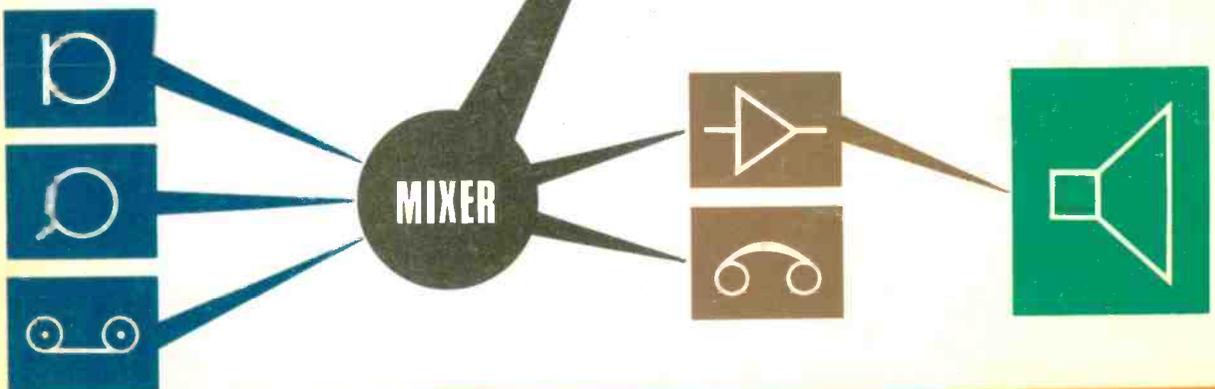


PRACTICAL WIRELESS

JUNE
1969

310

CONSTRUCT THIS AUDIO MIXER



ALSO
INSIDE

SLIMLINE SUPERHET

ADCOLA
PRODUCTS LIMITED
(Regd Trade Mark)

**THE RELIABLE
 SOLDERING INSTRUMENT!**



SEND COUPON FOR LATEST LEAFLET

**ADCOLA PRODUCTS LTD
 ADCOLA HOUSE
 GAUDEN ROAD
 LONDON SW4**

NAME

ADDRESS

.....

.....

PW170

JACKSON

—the big name in **PRECISION** components—

BALL DRIVES



Thousands of Jackson dual-ratio ball drives are in daily use. Type 4511DRF provides 6:1 fast ratio and 36:1 "reverse vernier" on one spindle. A flange for carrying a pointer, is ideal for use in receivers and measuring instruments. Other Jackson ball drives provide simple 6:1 reduction or combined 1:1 and 6:1 reverse vernier movements.

- *High torque. *Low backlash. *Simple fixing.
- *Take standard 0.25in spindles.
- *Utterly reliable of course!

**INTERNATIONAL LONDON
 ELECTRONIC COMPONENTS SHOW**

OLYMPIA MAY 20-23

See our range of variable Capacitors, Tuning Controls and Terminals on Stand E 221.

JACKSON BROS. (London) LIMITED
 Dept. PW, Kingsway, Waddon, Croydon, CR9 4DG
 Phone: (01-688) 2754-5 Grams; Wallfco, Croydon

US Office: M. SWEDGAL, 258 BROADWAY NY, NW 10007

17in.—£11.10.0

19in. **SLIMLINE**

SOBELL—24 Gns.

TWO-YEAR GUARANTEE

EX-RENTAL TELEVISIONS

**FREE ILLUSTRATED
 LIST OF TELEVISIONS**

17"–19"–21"–23"


WIDE RANGE OF MODELS

SIZES AND PRICES


DEMONSTRATIONS DAILY

**TWO-YEAR GUARANTEED
 REGUNNED TUBES**

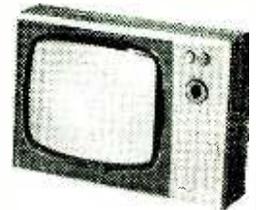70° and 90° 14in.—69/6, 17in.—89/6, 21in.—99/6, 110° 17in., 19in. and 21in.—99/6, 23° (not bonded)—119/6. Exchanged bowls. Carr. 10/6.



COCKTAIL/STEREOGRAM CABINET 19 gns.

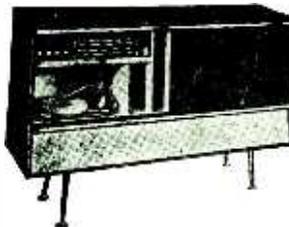

Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35½in., width 52½in., depth 14½in. Legs 1 gn. extra.

Speakers 6/6: 2"—75Ω. 2½"—35Ω. P. & P. 2/6. **Acos Mics.** 35/- Stand: Slick Mic. 2 gns. P. & P. 3/6. **Asstd. Condensers:** 10/- for 50. P. & P. 7/6. **Asstd. Resistors:** 10/- for 50. P. & P. 4/6. **Asstd. Controls:** 10/- for 25. P. & P. 7/6. **Transistors:** Mullard matched output kit 9/OC81D—2 OC81's. P. & P. FREE.

Ferrite Rods 3/6: 6", 8" x ¾" complete with LW/MW Coils. P. & P. FREE.
TRANSISTOR CASES 19/6. Cloth covered, many colours. Size 9½" x 6½" x 3½" P. & P. 4/6. Similar cases in plastic 7/6.
RECORD PLAYER CABINETS 549/6. Cloth covered, size 16½" x 14½" x 8". Takes any modern autochanger. P. & P. 7/6.
SINGLE PLAYER CABINETS 19/6. P. & P. 7/6.
STRIP LIGHT TUBES 3/9 each. 11" (284 mm.) 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting etc. 6 for £1. P. & P. free.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

Lasky's Radio

LASKY'S RADIO ESTABLISHED OVER
36
YEARS

THREE NEW TMK METERS

These meters by the famous TMK Co. of Japan incorporate the very latest developments in design and set a new standard in quality and accuracy. The new shape permits a more compact cabinet yet the meter size is actually increased! All have strong impact resistant cabinets with carrying handles and are complete with test leads, batteries and full instructions.

Model PL-436

20,000 O.P.V. Multitester for the amateur or professional. Features mirror scale and wood grain finish front panel. SPEC.: DC/V ranges: 0-6, 3, 12, 30, 120, 600V at 20K/O.P.V. AC/V ranges: 3, 30, 120, 600V at 8K/O.P.V. DC current: 50µA, 0-6, 60, 600mA. Resistance: 10K, 100K, 1M and 10M ohms end scale (65, 650, 6.5K and 65K ohms centre scale). Decibels: -20 to +57dB in four ranges. Operates on 2x1.5V U7 type batteries. Size: 5½ x 4½ x 2½in.




LASKY'S
PRICE

£7.19.6

Post
5/-

Model 5025

50,000 O.P.V. Multitester suitable for all professional and educational uses. Features a fantastic 57 measurement range cover (±2% accuracy on full scale DC). High speed range selection, polarity reversal switch and overload meter protection circuit. SPEC.: DC/V ranges: 0-125 to 1000V in 12 ranges (0-25 to 500V at 50K/O.P.V.). AC/V ranges 1.5V to 1000V in 10 ranges (1.5 to 500V at 5K/O.P.V.). DC current: 25µA to 10A. Ohms: 0 to 10M ohms. Decibels: -20 to +61.5dB in 10 ranges. Operates on 2x1.5V U7 type batteries. Size: 6½ x 5½ x 2½in.

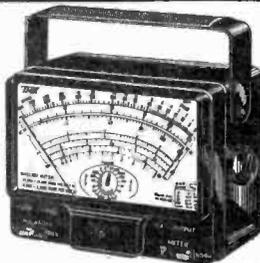

LASKY'S
PRICE

£13.10.0

Post
5/-

100,000 O.P.V. "LAB" Model

A highly accurate yet rugged Multitester using a 10µA meter hand calibrated to a DC accuracy of ±3% of full scale. Special features—ultra large meter scale 6½ x 3½in. incorporating an entirely new type of range selection panel which gives instant range identification without taking your eyes from the meter. An audible buzzer is provided for easy short testing. SPEC.: DC/V ranges: 0.5, 2.5, 10, 50, 250, 500, 1000V at 100K/O.P.V. AC/V ranges: 3, 10, 50, 250, 500, 1000V at 5K/O.P.V. DC current: 0-10, 100µA, 0-10, 100mA, 0-2.5, 10A. Resistance: 0-1K, 10K, 100K, 10M, 100M/ohms. Decibels: -10 to +49.4dB. Continuity test: Audible buzzer. Operates on 1x1.5V U9 and 1x1.5V B.154 type batteries. Cabinet size 7½ x 6½ x 3½in. Weight 4lb.



LASKY'S
PRICE

£19.10.0

Post
5/-

GET YOUR LASKY'S AUDIO-TRONICS PICTORIAL

FREE

16 colour pages in large 16 x 11in. format packed with 1,000's of items from our vast stocks. Hi-Fi, Radio, Electronics, Test equipment.

Send 1/- for post only and inclusion on our regular mailing list!

NEW LOW PRICE !!

SKYROVER Mk II COMMUNICATIONS RECEIVER



A completely new short wave receiver exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE6, 6BA6, 6AV6 and 6AR5 valves, gives highly sensitive reception and powerful gain.

Switch selected SW frequency range cover: 1.6 to 30 Mc/s in three separate bandspread ranges and full AM medium waveband cover in one range 550-1,600 Kc/s.

RF/O. Band selector. Power on indicator lamp. External antenna connections and mains fuse at rear. 8 ohms internal speaker plus standard 6mm jack socket for phones on front. For 220/240V AC mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9½ x 5½ x 5½ins. complete with mains lead and full instructions. Previously listed at £17.15.0 (A credit note for the difference in price will be given to customers who purchased this unit at the original price after Jan. 1st '69, on presentation of receipt).

LASKY'S
PRICE

£13.13.0

Post
5/-

MIDLAND Model 10-502 VHF AIRCRAFT BAND CONVERTER

An entirely new item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535 to 1605Kc/s, 88 to 108Mc/s respectively—with no electrical conversion or connection required. The Model 10-502 self powered by one 9V (PP3 type) battery is merely placed close to the receiving set and then tuned over 110 to 135Mc/s which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the vol. controls of each accordingly. The Model 10-502 has a smartly designed black plastic cabinet with brushed metal front panel and 18in. chrome telescopic antenna, size only 4x2½ x 2½in. (inc. knobs). Complete with battery and full instructions.




LASKY'S
PRICE

79/6

Post 5/-

TWO BAND PUSH BUTTON TRANSISTOR CAR RADIO MODEL CR-62

A high quality all transistor superbet car radio that really breaks the quality/price barrier. A unique feature of this set are the four M/W band station preselection buttons which you yourself set to your own four favourite stations—this is in addition to full M/W band cover over 535-1605 Kc/s and full L/W band cover over 150-300 Kc/s (IF frequency 455 Kc/s.) Externally adjustable aerial trimmers ensure maximum output. Six transistor (including one drift type) and one diode circuit provides powerful 2W output. The set is adjustable for use on either positive or negative ground 12V systems (external line fuse fitted). Standard mounting size 6½ x 5½ x 2½in.—front panel ½in. larger all round—finished in anodised aluminium with black push buttons. Complete with mounting brackets, full installation instructions and 2 baffle boards (for round or elliptical speaker). Fully guaranteed.

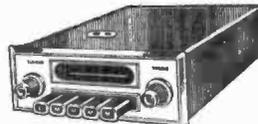

LASKY'S
PRICE

£10.19.6

Post 5/-
6 x 4in. dynamic
speaker 17/6 extra—
Post FREE

MANUAL TUNING MODEL OF CR-62 AVAILABLE. £7.19.6.
SPECIAL OFFER—LOCKING CAR AERIAL Model 83003 five section 42" extension heavy chrome telescopic wing mounting type with unique locking device to protect the antenna when closed. Complete with mounting bracket, lead and plug and two "keys". LASKY'S SPECIAL PRICE 38/6 Post Free with the CR-62. Post Sep. 2/6.

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271

Open all day, 9 a.m.—6 p.m. Monday to Saturday

33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel.: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday


118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789

Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

Open the pages of The RADIO CONSTRUCTOR

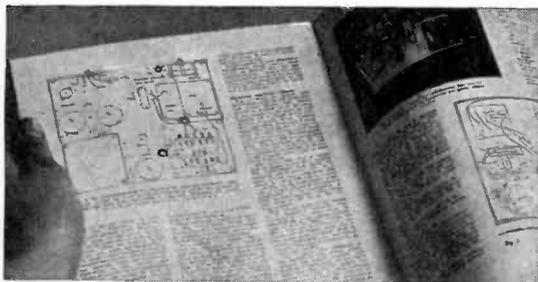this month for . . .
**A HOST OF CONSTRUCTIONAL
PROJECTS**



Articles include

WATER OPERATED ALARM

Using simple silicon semiconductor circuitry, this novel device sounds a bell to warn of excessive water level—cover feature.

★ ★ ★

LIGHT OPERATED RADIO SWITCH

★ ★ ★

PRINCIPLES OF METAL DETECTION

The first part of a 2 part article dealing with an application of electronics not normally encountered in the technical press.

★ ★ ★

MAINS POWER FOR TRANSISTOR EQUIPMENT

★ ★ ★

LOW-NOISE PRE-AMPLIFIER

This a.f. pre-amplifier is very simple in design, but can carry out a number of useful functions.


MAY ISSUE

RADIO CONSTRUCTOR

ON SALE NOW 3/-

PHOTOELECTRIC KIT

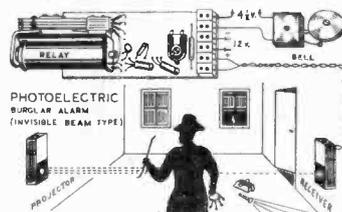CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
39/6

Postage and Pack. 2/6 (UK)
Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0
Australia, New Zealand
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit. Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 62 Radio, Electronic and Photoelectric Projects Assembled.



FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL
NO TECHNICAL KNOWLEDGE
REQUIRED

Only **28 Gns.** + P&P 17/6

H. P. terms available.
Dep. £9.16.0 & 12 monthly payments of 36/9 (Total H.P. £31.17.0).
Send £10.13.6 today.

Amplifier available separately at only 17 Gns.

FANTASTIC BARGAIN OFFER!


"TRANSCONTINENTAL" FULLY TRANSISTORISED STEREOPHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY**

10 Watts Total output **34 1/2 GNS.** 17/6

17 Transistors & 10 diodes
EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
H.P. available £12.1.6 dep. plus 18 monthly payments of 32/- (Total H.P. £40.17.6).

Send £12.19.0 today.

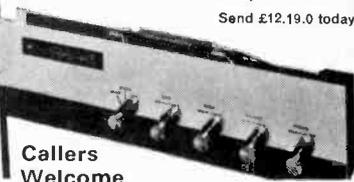

Callers
Welcome

POST
THIS
COUPON
NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name

Address

LEWIS radio

100 CHASE SIDE, SOUTHGATE, Dep. P609
LONDON, N.14. TELEPHONE PAL 3733/9666

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

RADIO ENGINEERING
Advanced Radio — Gen. Radio — Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Supply — Mining Elec. Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B., A.M.I.P.E., A.M.I.M.L., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

British Institute of Engineering Technology
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and if you are earning less than £30 a week you should send for your copy now—FREE and without obligation.



POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

WIRECOMP ELECTRONICS SALE MART

**BRAND NEW FAMOUS BRITISH
FM TUNER BARGAINS**

TRUVOX FM100 Transistorised Tuner

List price £34.17 **SALE PRICE £24.10.0** P. & P. 10/-

ALSO AVAIL. A FEW TRUVOX TSA 100 transistorised amps. List price £51.9.0. **SALE PRICE £37.10.0.** P. & P. 10/- and TRUVOX LS 100 loudspeaker systems. List price £26.0.0. **SALE PRICE £19.10.0.** P. & P. 10/- (per unit).

ARMSTRONG Model 224

List price £24.15.0. **SALE PRICE £19.0.0** P. & P. 10/-

Please note there are very limited stocks of these fine units

Hi-Sky HS-30 Cassette Recorder

High quality transistorised cassette recorder. Features include: Push button operation • Record level meter • Safety record button • Operates on 4xU11 type batteries • Complete with Real Leather case with carrying handle and accessory compartment. Dynamic remote control microphone and C-60 cassette. Brand new and boxed.

List Price £21.0.0 **SALE PRICE £17.10.0** P. & P. 6/6

FIRE/BURGLAR ALARMS

Type A. Industrial fire alarm. Emits loud warning note if air temp. exceeds 125°F, wall mounting. Operates on 2 x U2 type batteries. Size 6 x 2½ x 1½ in. Grey enamel finish.

SALE PRICE 22/6 P. & P. 2/6

Type B. Domestic fire alarm. As Type A but with louvered front and red crackle finish.

SALE PRICE 30/- P. & P. 2/6

Type C. Fire or burglar alarm. As types A and B but with alarm switch which may be connected in a door or window frame etc. Fire operation as types A and B. White enamel finish.

SALE PRICE 34/6 P. & P. 2/6

WIRECOMP SPECIALITIES FOR THE ENTHUSIAST

Special displays of radios, recorders, record decks, tuners, amps., meters, speakers, etc., etc. ALL faulty or damaged needing repair—

AT GIVE AWAY PRICES!

100's of component bargains from our easy to see and choose from self service racks.

100's OF OLD TYPE VALVES — 2/- each

ASSORTED TRANSISTORS 9d each. 7/6 per doz

Huge stocks of shop soiled and reconditioned second hand radios, record players, tape recorders, etc.

SPOT CASH PART EXCHANGES

WE OFFER THE HIGHEST RATES IN LONDON

There's something for everyone

COME AND LOOK TODAY (Open 6 days a week!)

ALL THESE ITEMS ARE AVAILABLE TO CALLERS ONLY

PERSONAL CALLERS TO:

48 TOTTENHAM CT. RD., W.1

Tel. 01-636 0647

MAIL ORDERS TO:

378 HARROW ROAD, PADDINGTON, LONDON, W.9

PLEASE NOTE: Owing to increased handling charges — MINIMUM Mail Order value £1 (including postage).

SPEAKER SYSTEMS

All cabinets are new and speakers are mounted on ¼ in. chipboard baffles. All speakers ex TV reconditioned hi flux magnet. All carefully tested before despatch.



THE CAXTON COLUMN
This is a column cabinet. 23½ x 54 x 5½ in. wide, fitted with 3 speakers. This will handle 8 watts and will improve the quality of any tape recorder, or record player. Finished in wood grain cloth and sandstone Vynair. A real bargain at 59/6. P. & P. 10/6.


THE MILTON A.
Hi-Fi Bookcase Cabinet. Size 9 x 5 x 6 in. with 6 in. speaker. Finished in Teak cloth with bold silk front 80/- P. & P. 4/6.



The Tennyson. Wedge shape for table or wall mounting 18½ x 16 x 8½ in. Fitted EMI 131 x 8 in. Speaker. Finished in Grey cloth with matching Vynair. £4.7.6 P. & P. 7/6.


DUO. Wedge shaped Speaker Cabinet. Size 7½ x 7½ in. Fitted 7 x 4 in. speaker. Covered in attractive two tone Vynair. Price 32/6. P. & P. 4/6.

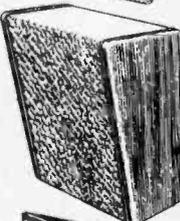THE IMP. Extension Speaker Cabinet. Wedge shaped, size 7½ x 6½ in. fitted 7 x 4 in. speaker.



THE SCOTT.

Table top or wall mounting Speaker. Size 16½ x 10½ x 5½ in., tapered as illustrated. Fitted 13½ x 8 in. Speaker with volume control. Finished in black cloth with matching grey Vynair. (Please state 3 P. & P. 4/6. or 15 ohm imp.) £4.5.0. P. & P. 7/6.

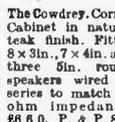

The Cowdrey Corner Cabinet in natural teak finish. Fitted 3 x 3 in., 7 x 4 in. and three 5 in. round speakers wired in series to match 15 ohm impedance. 26.8.0. P. & P. 8/6.



with attractive walnut Vynair front. Acos Mike 40, 18/6. Dyn. Mike DM-391, 30/-, CM21 Xtal, 12/6. Telephone Pick-up, 10/6. P. & P. 1/- Xtal lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-.

SPEAKERS: Elac Heavy duty Ceramic Magnets 11,000 line, 10 in. round, 10 x 6 in. 3 ohm, or 15 ohm, 48/6. P. & P. 3/6. 8 in. round 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I. 131 x 8 in. 3 ohm 45/-, 15 ohm 48/6. P. & P. 3/6. E.M.I. 8 in. tweeter, 17/6. P. & P. 1/6. E.M.I. 131 x 8 in. fitted two 2 in. tweeters, 15 ohms, 77/6. P. & P. 4/6. E.M.I. 131 x 8 in. (15 ohm) Hi-Fi Quality, 25.19.8. P. & P. 4/6. E.M.I. Woofers, 6½ x 6½ in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 18/6. P. & P. 1/- EAGLE Crossover units, 3 or 16 ohms, 18/- P. & P. 1/- Bakers 12 in., 25 watt, 16 ohm, 26.8.0. P. & P. 3/6.

TEAK PLINTH AND PERPEX DUST COVER for 8P25 etc. £5.5.0. P. & P. 5/- VYNAIR Widths from 40 to 54 in., 17/6 yd. off roll. P. & P. 1/9. 4 yard, 9/- P. & P. 1/9. Send 1/- stamps for samples.

SPEAKER MATCHING TRANSFORMERS 3, 7, 15 ohms, 8 watt, 11/6 P. & P. 1/6.

MICROPHONES: Xtal Hand Mikes. B1201 with stand, 54/6. P. & P. 3/6. ACOS Mike 45, 21/- ACOS Mike 40, 18/6. Dyn. Mike DM-391, 30/-, CM21 Xtal, 12/6. Telephone Pick-up, 10/6. P. & P. 1/- Xtal lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-.

FERROX RODS: 6 x ½ in., 2/6; 4 x ½ in., 2/-; 6 x ¾ in., 2/6; 8 x ¾ in., 3/- P. & P. 1/-

FERROX RODS WITH COILS, 4 x ½ in., 3/6; 8 x ½ in., 5/6; P. & P. 1/- each.

ROTARY SWITCHES: 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 5/6 each. P. & P. 1/-

TRANSISTOR SPEAKERS 8 ohm 2 in., 8/6. 3 in., 10/6. 3½ in., 12/6. P. & P. 1/-

CARTRIDGES

Stereo: Sonotone 9TA H/C Diamond 47/6. 9TA Sapphire, 37/6. 8TA Sapphire, 30/- Ronette 8106 Medium Output, 28/6. 8106 High Output 28/6. DC284 Stereo Compatible 22/6. Acos GP93/1 Sapphire, 37/6. GP94/1 Sapphire, 39/6. GP81 Diamond 42/- GP91 Stereo Compatible (High, Medium or Low Output), 25/- TA800 converts Philips AG3301, AG3306 to B.S.R. SX11. Plug-in head complete with cartridge 50/- TA700 equivalent to B.S.R. SX11, 35/- Japanese equivalent to B.S.R. TCS, 35/- Mono: Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/- S.R. TCRH Jap. equivalent, 16/6. Sonotone 2T88, 15/- Post and Packing 1/6. **EARPIECES WITH CORD** and 3-5 mm. plug, 8 ohm magnetic, 3/- 250 ohm, 4/- 180 ohm with clip, 6/6. Xtal. P. & P. 6d. **PIANO KEY PUSH BUTTON SWITCHES:** 7 button inc. mains on off, 6 banks of 6 P.C.O., 8/6. P. & P. 1/-

BROADWAY Electronics

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 Telephone 01-672 3984 (Closed all day Wednesday) (Few minutes from Tooting Broadway Underground Station)

TEST BIPOLAR AND FIELD EFFECT TRANSISTORS with the BOURNLEA DYNAMIC Transistor Tester

Engineers, servicemen and experimenters use this invaluable tester for • Checking • Matching • Selecting bipolar and field effect (depletion mode) transistors.

The BOURNLEA Tester measures • hfe (β) from 5 to 750 (NPN and PNP devices) • gmo (Yfs) from 0.5 to 75 mmhos (N- and P-channel FET's).

Sockets enable multimeter to be used for • Transistor and diode leakage • Zero bias FET drain current (IDSS) • Pinch-off Voltage (Vp), and many more tests.

Supplied complete with 9 Volt battery, leads and instructions. Price 15 gns. plus 5/- p. & p. C.W.O.

THE CARDON INSTRUMENT CO., Earls Colne, Colchester, Essex.




*Fine design
superlative
performance*

P.W. DOUBLE 12

As described in this month's Practical Wireless
*Top line integrated hi-fi stereo
amplifier featuring*

PEAK SOUND "CIR-KIT"

Peak Sound are indeed proud to be associated with this superb P.W. design and that so much of it is made possible because of Peak Sound products and design techniques. Basically, the "P.W. Double 12" demonstrates the value of using "Cir-Kit" in modern circuit board units either for single or prototype examples, but in this instance, Peak Sound have contributed much more to the success of this project. This includes the remarkable power amplifiers, the power pack and the ingeniously styled cabinet which almost assembles itself, it is so simple to build. Read about the "P.W. Double 12" in this issue right now. Then when you build this exciting new design be sure you do it with authentic, exact-to-specification Peak Sound kits as described.

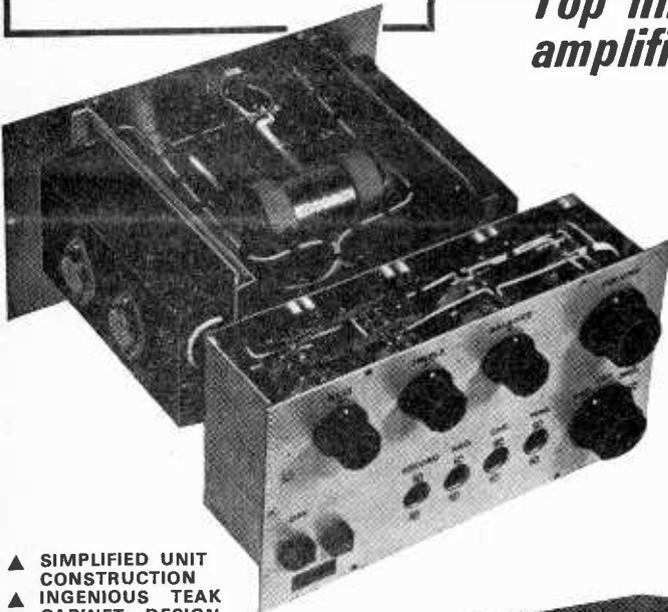

- ▲ SIMPLIFIED UNIT CONSTRUCTION
- ▲ INGENIOUS TEAK CABINET DESIGN
- ▲ PROFESSIONAL IN EVERY WAY AND MONEY SAVING TOO!

This is your "P.W. Double 12" shopping list

As you follow through stage by stage with P.W. these are the Peak Sound kits you will require. They are exact to specification. Transistors included.

2 Spools of "Cir-Kit" at 2/- each	4	0
2 Pre-amp and tone control kits	4	13
4 Pre-amp matrix boards	7	0
2 PA.12-15 Power Amplifier Kits	7	19
2 Heat Sink assemblies	12	0
2 P.A. matrix boards	8	0
1 PS.45K 45 volt power supply kit	4	10
1 Pack-flat afrormosia teak finished Cabinet kit	2	12
5 Controls as specified	2	0
TOTAL COST	£23	5 6

Metal work (make or buy), knobs, plugs and sockets, fuses etc. allow £3.0.0. From your local dealer.

Go to your Dealer NOW

for your authentic Peak Sound Kits. In case of difficulty, please send direct, giving the name and address of your usual supplier where possible and add 11/- postage for complete assembly, or 5/6 if without power pack.

TRADE ENQUIRIES INVITED

PEAK SOUND (HARROW) LTD., 32 ST JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, Phone EGHAM 5316



"Cir-Kit" is at the heart of building this fine design. Made from almost 100% pure copper with unique adhesive backing, it is the superb circuit builder for all requirements. In 5" spools, 1/8" wide, 2/- each.

"CIR-KIT" makes it possible!

▲ Abridged specification

Formation—Two pre-amp panels, two tone control panels, two power amplifier modules, power supply unit on chassis, housed within teak finished cabinet.
Controls—Bass and treble cut and lift based on Baxandall circuitry/Volume/Balance/ Rotary selector.
Input Sensitivity—Magnetic P.U.—(per channel) 2.5mV into 68kΩ. Ceramic P.U.—25mV into 27kΩ. equalised for flat response. Radio/Aux. 60mV.
HIGH OVERLOAD FACTOR ON ALL INPUTS.
Frequency Response—20Hz to 30KHz ± 1dB overall.

Output—12 watts per channel into 15Ω (8Ω speakers may be used).
Negative Feedback—43dB over each section.
Power required—45V D.C. (supplied by built-in power unit).
Cabinet—Afrormosia teak finish, pack-flat, easy to build kit. Size 9 1/2 x 5 1/2 in. high x 9 1/2 in. deep.
Transistors—Ultra low noise in pre-amp and tone control stages.
PERFORMANCE CHARACTERISTICS, PARTS REQUIRED, ETC., SEE OTHER PAGES IN THIS ISSUE

THESE PEAK SOUND PRODUCTS WILL HELP



PA.12-15 POWER AMPLIFIER

As specified for "P.W. Double 12" and available ready built complete with heat sink for mounting directly into position as described, but can also be used in other applications. Also available as a kit less heat sink and board.

Built **£5.19.6**

Kit (less heat sink, board and "Cir-Kit") **79/6**

Heat sink and baseboard assembly **10/-**
Please add 2/6 p/p either model if ordered direct, or 5/- for two.

ES. 10-15 BAXANDALL SPEAKER

This easy to build loudspeaker provides genuine hi-fi standards by the use of unique equalising principles. Frequency response 60-14,000Hz (100-10kHz ± 3dB). Easy-to-build kit including 18 x 12 x 10in cabinet.



£10.2.3

(Carr. 12/6). Leaflet available. + £1.2.9 P/Tax

THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25 x 14 x 10in. Complete Kit
★ Response 30-20,000 c.p.s. Impedance 15 ohms. **19 Gns.**
★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 6in. high flux 'middle range' speaker. (4) High efficiency tweeter. (5) Measured weight of woollen acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions.
DEMONSTRATIONS AT ALL BRANCHES.



R.S.C. STEREO/20 HI-FI AMPLIFIER

PROVIDING 10/14 WATT ULTRA LINEAR PEAK PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE. (7) valves ECC83, (2) ECL86, (4) EZ81. Frequency Response: ±2dB 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 30 millivolts max. Harmonic Distortion: 0.2%. ★ Four-position tone compensation and Input Selector Switch. ★ Stereo/Mono switch. ★ Neon panel indicator. ★ Handsome Perspex Frontplate. ★ Separate Bass and Treble controls. Output transformers are high quality sectionally wound. Outputs for 3 and 15 ohm speakers. Complete set of parts, point-to-point wiring diagrams and instructions. Or factory assembled with our usual 12 mths' gntee. 19 Gns. Or Dep. £4.10.0 and Carr. 12/6 9 monthly payments £2 (Total £22.10.0). Send S.A.E. for leaflet.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp./Tone Control Stages. Performance figures of factory built units: Hum level -70dB. Frequency response ±3dB 30-20,000c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 mV. Suitable for high impedance instruments. Crystal or Ceramic P.U.'s. Designed for Clubs, Schools, Theatre Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and 'Mike' can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. Carr. 12/6 **14 Gns.** Twin-handled perforated cover 27/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 17 Gns. **TERMS: Deposit £5.14.0 and 9 monthly payments of 31/3 (Total £19.15.3). Send S.A.E. for leaflet.**

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of 'mike' and gram, etc. etc. High sensitivity. 5 valves - ECC83 (2), EL84 (2), EZ81. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response ±3dB 30-20,000 c/s. Hum level -60dB. SENSITIVITY 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance instruments such as Electric Guitars etc. etc. Size approx. 12 x 9 x 7in. For A.C. mains 200-250v. 50 c/s. Output for 3 and 15 ohm spkrs. SAE for leaflet. Complete kit. **9 Gns.** Full instructions and point-to-point wiring diagrams. Carr. 11/6 (or factory built 12 Gns.) Twin handled metal cover 27/6. **TERMS ON ASSEMBLED UNITS:** Deposit 87/6 and 9 monthly payments of 22/-. (Total £14.5.6).

R.S.C. A11 TRANSFORMERISED VERSION OF above complete kit 9 Gns (Assembled 13 Gns)

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

An exceptional powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, etc. etc. **Peak OP rating 12in. Loudspeakers.** ★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or 'mikes'. Bass and Treble controls. **52 Gns.** Carr. 30/- or dep. £10.1.0 and 9 monthly payments of 25.11.9. (Total 57.9 gns.). Send S.A.E. for leaflet. **G100 100 watt peak output with pr. Columns and a Bass Unit. Inc. 8 speakers. R.S.C. Two 15". 99! gns.**

R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5 1/2 x 4 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 49/11 or assembled 59/11.

SELENIUM F.W. RECTIFIERS (Bridged)

All 6/12v. D.C. output. Max. A.C. input 18v. 1a. 3/11. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v. 50c/s. Screened

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.	15/11
250-0-250v., 60mA, 6-3v. 2a.	16/11
250-0-250v., 100mA, 6-3v. 2a.	21/9
250-0-250v., 100mA, 6-3v. 4a., 0-5-6-3v. 2a.	37/9
300-0-300v., 100mA, 6-3v. 4a., 0-5-6-3v. 2a.	37/9
300-0-300v., 130mA, 6-3v. 4a., c.t., 6-3v. 1a.	45/9
For Mullard 510 Amplifier	37/9
350-0-350v., 100mA, 6-3v. 4a., 0-5-6-3v. 2a.	47/9
350-0-350v., 150mA, 6-3v. 4a., 0-5-6-3v. 3a.	69/9
425-0-425v., 200mA, 6-3v. 4a., c.t., 5v. 3a.	69/9
425-0-425v., 200mA, 6-3v. 4a., 6-3v. 3a., 5v. 3a.	75/-
450-0-450v., 250mA, 6-3v. 4a., c.t., 5v. 3a.	87/9
TOP SHROUDED DROP-THROUGH TYPE	
250-0-250v., 70mA, 6-3v. 2a., 0-5-6-3v. 2a.	21/9
250-0-250v., 100mA, 6-3v. 3-5a.	25/9
250-0-250v., 100mA, 6-3v. 2a., 6-3v. 1a.	26/9
350-0-350v., 80mA, 6-3v. 2a., 0-5-6-3v. 2a.	27/9
250-0-250v., 100mA, 6-3v. 4a., 0-5-6-3v. 2a.	37/9
300-0-300v., 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	37/9
300-0-300v., 130mA, 6-3v. 4a., 0-5-6-3v. 1a.	44/9
Suitable for Mullard 510 Amplifier	37/9
350-0-350v., 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	37/9
350-0-350v., 150mA, 6-3v. 4a., 0-5-6-3v. 3a.	45/11
FILAMENT or TRANSISTOR POWER PACK Types	
6-3v. 1.5a. 7/8; 6-3v. 2a. 8/9; 6-3v. 3a. 10/9; 6-3v. 4a. 12/9; 12v. 1a. 8/9; 12v. 3a. or 24v. 1.5a. 21/9; 0-9-18v. 14a. 17/9; 0-12-25-42v. 2a. 29/9.	
CHARGER TRANSFORMERS 0-9-15v. 14a. 14/11; 24a. 17/9; 3a. 19/11; 5a. 23/9; 6a. 27/9; 8a. 33/9.	
AUTO (STEP UP/STEP DOWN) TRANSFORMERS	
0-110/120v. 200-230-250v. 50-80 watts 15/9	
150 watts, 29/11; 250 watts 49/9; 500 watts 99/9	
OUTPUT TRANSFORMERS	
Standard Pentode 5,000 Ω, 7,000 Ω to 3 Ω .. 8/9	
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω .. 12/9	
Push-Pull 10 watts 6V8 ECL86 to 3, 5, 8 or 15 Ω .. 22/9	
Push-Pull EL84 to 3 or 15 Ω 10-12 watts .. 21/9	
Push-Pull Ultra Linear for Mullard 510, etc. 37/9	
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω .. 35/9	
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω .. 69/9	
SMOOTHING CHOKES	
150mA, 7-10H, 250 Ω 12/9; 100mA, 10H, 200 Ω 10/9; 80mA, 10H, 350 Ω 8/9; 60mA, 10H, 400 Ω 4/11.	

BLACKPOOL AGENT APPOINTED O. & C. ELECTRONICS 227 CHURCH ST. R.S.C. HI-FI CENTRES LTD.

R.S.C. COLUMN SPEAKERS Covered in two-tone Rexline/Vynair. Ideal for vocalists and Public Address. 15 ohm matching. C57 15 watt inc. five 7 x 4in. speakers £7.19.11. Type C48S, 30 watts. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit 65/- and 9 monthly pmts 34/9 (Total £18.17.9) Carr. 10/- Type C418S, 30 watts. Fitted four 12in. 11,000 line 15 watt speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/- Or Deposit £4.13.6 and 9 monthly payments of 52/6 (Total £28.5.0). **16 Gns. 24 Gns.**

30 WATT HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group A 2 or 4 input, 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexline covered cabinet with handles. Attractive black/gold perspex face. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 3 gns. and Carr. 15/- 9 mthly payments of 39/8 (Total £21). **12/6**

12in. HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosia veneered Cabinets
15 Watt 11,000 lines £5.15.0 20 Watt 10,000 lines £8.19.9
3or15ohms. Carr 7/6 3or15ohms. Carr 8/9

LOUDSPEAKERS Limited number of heavy duty units at well below list prices.
Brand new, guaranteed. Terms available over 8% Carr. 10/- extra.

12in. 30 watt 6-8 ohms Normally approx. £12	£6.19.9	12in. 30 watt 15 ohms impedance Normally £10.10.0	15in. 40 watt 15 ohms Extra heavy 10 Gns. duty
---	---------	---	--

FANE "POP" 100 LOUDSPEAKER
18" 100 Watt
Fantastic power handling. Guaranteed 2 years. **19 Gns.** POST FREE

ARMSTRONG UNITS CLEARANCE
Stereo Amplifier 222 Our Price £25
AM/FM Tuner-AMP 277M Our Price £35

POWER PACK KIT Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200-250v. A.C. mains. Output 250v. 60mA 6-3v. 2a. Supplied with case in lieu of chassis 28/11. Or assembled 39/11. **24/11**

CLEARANCE LINES HIGH QUALITY 8" x 3" LOUDSPEAKERS 11/9

10000 Gauss 3 ohm only Post 2/-
14 WATT HI-FI AMPLIFIERS High sensitivity. Two separate inputs. Two vol. controls for mixing purposes. Separate Bass and Treble Controls. Valves ECC83, ECL86, ECL86, EZ80. Output for 15 ohm Loudspeaker. 200-250v 50 c.p.s. A.C. mains operation. Size approx. 8 x 8 x 6in. Factory built and fully guaranteed. Limited number to clear at **£7.19.11** Carr. 10/-

E.M.I. HIGH FIDELITY LOUDSPEAKERS 13" x 8" 15 ohms, Gauss 13,000 lines. Formed flexible P.V.C. cone surround for very low fundamental resonance. Range 30-15,000 c.p.s. Rating 10 watts. Limited number. **5 1/2 Gns.**

EXTENSION 'SPEAKERS 29/9 Cabinet size 12 x 8 x 5in. attractive grey lizard skin finish. Fitted high flux 5 watt 3 ohm speaker. **59/9** Mono Stereo **69/9**

PHONE AMPLIFIERS Speak and listen with both hands free. Standard dry battery operated. Attractive black moulded case. **59/9**

1 WATT TRANSISTOR AMPLIFIERS for 3-5 ohm Loudspeakers. Miniature size. Brand new boxed. Post free **37/9**

PRINTED CIRCUIT KITS for making printed circuits. Complete with 72 square (ms) laminated board and necessary fluids. Post 2/9 **12/9**

J.B. VHF/FM DIAL & DRIVE ASSEMBLIES ONLY 9/9 Complete with escutcheon. Size 7" x 4 1/2". Escutcheon 7 1/2" x 2 1/2". Post 2/9

TAPE RECORD/PLAYBACK AMPLIFIERS 4 watts output. Magic Eye Recording level indicator. For 3 ohm L/S. All normal facilities. Less Facia plate. For 200/250 A.C. mains. Carr. 8/6. **£8.15.0**

HEAVY DUTY 15in. 40 WATT LOUDSPEAKERS ONLY In substantial Rexline/Vynair covered cabinet. Carr. 15/- **14 Gns.**

MINI-8 HI-FI LOUDSPEAKER UNITS Teak or Afrormosia veneered cabinet, size approx. 10 1/2 x 6 1/2 x 7 1/2 in. Peak power handling 8 watts 3 ohms or 15 ohms. Clearance Price **59/11**

JASON VHF/FM TUNER DESIGNS Total cost of parts FMT1 **5 Gns.** FMT2 **£6.19.11.** JTV2 **9 1/2 Gns.** Please state channel

STEREO/TEN HIGH QUALITY AMPLIFIER 5 watts high quality peak output on each channel. Sensitivity 50 millivolts. Suitable all crystal or ceramic stereo cartridges. Ganged Bass and Treble Controls. Valves ECC83 (2), EL84 (2), EZ61. For 2-3 ohm speakers. Assembled with 12 months' guarantee Carr. 7/9 **£11.9.6**

6/12V CAR BATTERY CHARGERS Complete kit of parts with Ammeter and Circuit. Both models with variable charge rate selector. **4 amp 49/9 6 amp 69/9** All types 200-250v. A.C. Mains. Built 10/- extra.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewarts Road, London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

6/69

INTERNATIONAL CORRESPONDENCE SCHOOLS

F.A.L. Phase 32

You must hear this superb unit

15 + 15
WATT
HIGH
FIDELITY
OUTPUT



SOLID STATE STEREO AMPLIFIER

Recommended Retail Price **ONLY 35 Gns.**

- ★ Excellent performance
- ★ High grade components and transistors
- ★ Impressive technical specification
- ★ Attractive appearance
- ★ Modest cost

Housed in Teak veneered Cabinet, Switched selection of Mic., Magnetic P.U., Ceramic P.U., Radio Tuner, Tape Rec.

SEND S.A.E. FOR FULLY DESCRIPTIVE LEAFLET

Available from your local Hi-Fi Dealer

Wholesale and Retail enquiries to Manufacturers

FUTURISTIC AIDS LTD, 103 Henconner Lane, Leeds 13

BI-PRE-PAK LTD

222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0708) 46344

SPECIAL OFFER

Stock Clearance of Manufacturers Rejects. Limited Number UHF/VHF Tuner Units. Consisting of: 2 AF186 Transistors, Tuning Condensers, Coils and Comps etc.:

Price 5/- each

Post and Packing U.K. 2/6

Pak No.	NEW, UNMARKED, UNTESTED PAKS	Price
B78	12 Integrated circuits, Mixed types, data supplied with orders.	10/-
B80	8 Dual Transistors, Sil NPN Matched output pairs.	10/-
B82	10 OC35-OC81D-OC81 Transistors, Mullard glass types.	10/-
B83	200 Mixed A/F, E/F Sil Germ., NPN, PNP Transistors.	10/-
B84	100 Silicon diodes DO-7 Case, OA200 -OA202 Polarity marked.	10/-

Pak No.	NEW, TESTED AND MARKED PAKS	Price
B79	4 IN4007 Silicon Diodes, 1000 P.I.V. 1 Amp Min. Type.	10/-
B81	10 Reed switches Min. type with Coils and Magnets.	10/-
B85	24 Integrated circuits on panels. data of types sup. with orders.	10/-

Transistors	Price
AC126	2/4
AC127	2/4
AC176	4/-
AD149	10/-
AS Y29	5/-
BC107-9-9	4/6
BC171	3/-
BC172	3/-
BC173	3/-
OC22	6/-
OC23	6/-
OC28	7/6
OC28	5/-
OC28	10/-
OC35	5/-
OC44	1/11
OC45	1/9
OC71	2/6
OC83	4/-
OC139	2/6
OC140	3/6
OC201	3/-
OC271	10/-
BC108	3/6
BC109	3/6
2N4284	3/6
2N4285	3/6
2N4286	3/6
2N4287	3/6
2N4288	3/6
2N4289	3/6
2N4290	3/6
2N4292	3/6
2N3085	15/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

Send for our FREE lists and catalogue of all our products. Check your own equivalent with our free substitution chart.

Matched Set. NPN/ PNP AD161-AD162 Comp. pair Pak **10/- PR.** Complementary Set. NPN/ PNP Germ. trans., Pak F.3 **2/6 PR.**

NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/- CASH WITH ORDER PLEASE, add 1/- post and packing. OVERSEAS ADD EXTRA FOR AIRMAIL

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1

Tel: 01-636 3451




COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS

CARRIAGE 35/-

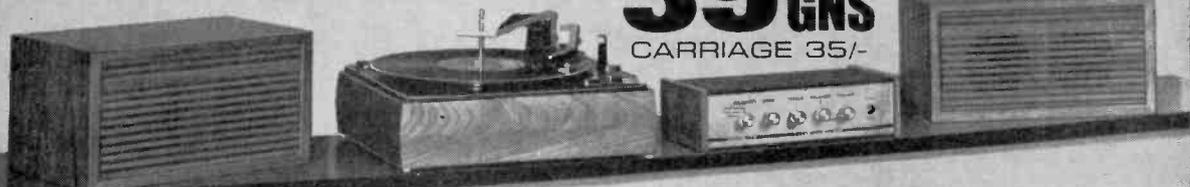

The Premier Stereo System consists of an all transistor stereo amplifier, Garrard Model 2025 auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor Amplifier has an output of 5 watts per channel with inputs for pick up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12" x 5 1/2" x 3 1/2" high (Amplifier available separately if required £14.19.6. Carr. 7/6).

GARRARD RECORD UNITS

1025 Stereo/Mono cart.	£7.19.6	
2025 Stereo/Mono cart.	£8.19.6	Teak Plinth with perspex cover as above £5.10.0.
3000 with 9TAHCD Carriage 7/6 extra	£9.19.6	Carr. 6/6 extra.
AT10 MKII less cart.	£13.19.6	
BP25 MKII less cart.	£11.19.6	

AP75 less cart.	£10.0.0	Teak Plinth with perspex cover as above £5.10.0.
8L75 less cart.	£29.0.0	£7.10.0. Carr. 7/6 ex.
8L95 less cart	£38.10.0.	Carrriage 10/- extra.

GOLDRING RECORD UNITS

GL68 less cart.	£22.7.0.	GL75 less cart.	£35.15.5.
Carrriage 10/- extra.			

PICK-UP CARTRIDGES

SHURE M3D (Stereo)	£7.10.0
B.S.O. 8P1 (Stereo)	£5. 5.0
PICKERING V15/AC2 (Stereo)	£8.10.0
SONOTONE 9TAHCD/Diamond (Stereo)	£2.15.0
ACOS GP93/1 (Mono compatible)	£1.13.5
ACOS GP93-1 (Stereo)	£2. 8.7
ACOS GP94-1 (Stereo)	£2.14.8
B.S.R. X3M (Mono compatible)	£1.18.5
B.S.R. X3H (Mono compatible)	£1.18.5
RONETTE 105 (Stereo)	£1.15.0
RONETTE 106 (Stereo)	£1.15.0

All complete with mounting brackets and instructions. Post and Packing 1/6 each.

WELLER SOLDERING TOOLS



"Expert" Solder Gun. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. 87/6 P. & P. 3/-. "Marksman" Soldering Iron. Lightweight, conventional 3/4" pencil bit. Ideal for regular bench use and all those jobs around the home. 25 watts. 240 volt. A.C. 31/6 P. & P. 2/-.

"PREMIER" TAPE CASSETTES



C60 Type 10/6
90 min.
C90 Type 15/-
90 min.
C120 Type 20/-
120 min.
P. & P. 1/-.

CASSETTE HEAD CLEANER
Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. 15/- P. & P. 1/-.




HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8ohm impedance. Complete with 6ft. lead and stereo jack plug. 59/6 P. & P. 5/-.

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low Imp. 25/- P. & P. 2/-.
MONO STETHOSCOPE SET Low Imp. 10/6 P. & P. 2/-.

"PREMIER" SPEAKER SYSTEM

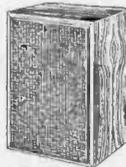Specially designed oiled teak cabinet with vinyl front. Size 12 1/2" high, 7 1/2" wide, 6 1/2" deep. Fitted 6 1/2" E.M.I. 8ohm Bass speaker with rolled surround and matching 3" E.M.I. tweeter. Fully lagged. £7.19.6. Carr. 7/6.



MULTI TESTERS

MODEL D14. A really versatile instrument that makes a handy pocket size tool. Measures AC or DC voltage in three ranges of 0-15-150-1000 volts. Resistance 0-100,000 ohms. Current 0-150 mA D.C. Size only: 3 1/2" x 2 1/4" x 1 1/4". Complete with battery, test leads and instructions 49/6. P. & P. 2/6.

POCKET SIZE MODEL. With wide-angle, levelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 19 Ranges: 0-5-25-50-250-500-2500 volts DC. 0-10-50-100-500-1000 volts AC. 0-50 uA-2.5 mA-250 mA DC. 0-8000 ohms-6 megohms, 10u uf-0.001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. £4.19.6. P. & P. 3/6.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	5/6	DT6 5 1/2" 1800' POLYESTER	22/6
TT3 3" 450' POLYESTER	7/6	TT6 5 1/2" 2400' POLYESTER	37/6
DT3 3 1/2" 600' POLYESTER	11/6	SP7 7" 1200' POLYESTER	12/6
SP5 5" 600' P.V.C.	8/6	LP7 7" 1800' P.V.C.	15/-
LP5 5" 900' P.V.C.	10/-	DT7 7" 2400' POLYESTER	25/-
DT5 5" 1200' POLYESTER	15/-	TT7 7" 3600' POLYESTER	50/-
LP6 5 1/2" 1200' P.V.C.	12/6		

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/6. TAPE CASES 5", 5 1/2", 7" 2/6.
Post and Packing 3" 1/-, 5", 5 1/2", 1/6, 7" 2/- (3 reels and over Post Free).



WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

All leading makes available including Rogers, Armstrong, Dulci, Wharfedale, Goodmans, Goldring, Shure, etc. etc.

SPECIAL OFFER

BALFOUR "PRINCESS"

4 Speed Autochanger fitted ACOS Mono Compatible 1/6 cartridge. Complete with TRAK BASE. ONLY £5.19.6. Carr. 7/6.



MONO GRAM AMPLIFIER

2 1/2 watts output. Uses EL84 valve, double wound mains transformer. Ideal for use with any record deck. Volume/On/Off and tone controls on flying leads. Output impedance 3 ohms. Size overall 6 1/2" w. x 5 1/2" d x 3" h. A.C. 200/240V. ONLY 49/6. P. & P. 5/-.

JULIETTE NA.5018 5 BAND 18 TRANSISTOR MAINS/BATTERY RADIO

Covers AM 540-1600Kc/s. Marine 1-4.6Mc/s. FM 88-102Mc/s. VHF 108-134Mc/s. PB 148-174Mc/s. Ferrite bar aerial for AM/MB. Telescopic aerial for FM/VHF/PB. 4" P.M. Speaker. Operates on AC 250v. or D.C. by four 1.5v. batteries. Size: 9 1/2" x 5 1/2" x 3 1/2". PREMIER PRICE 88 gns. P. & P. 10/-.



TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc. ONLY 49/6 P. & P. 4/-.



FOUR STATION INTERCOM. Master unit and 3 slaves. Ideal for office and home. Complete with battery and connecting wire £7.19.6 P. & P. 5/6.

Litesold

SOLDERING INSTRUMENTS



Have a look at your present soldering irons. Are they really giving you the performance and service you're paying for? Is there really a model suitable for your size of work? Or are you making do with a tiny bit in a big iron? Or vice versa? Do they have the cool, comfortable feel, the elegance, of a LITESOLD? Drop one on a concrete floor—does it survive? Can you easily and cheaply replace the bits? Can you service it yourself? Are the models you want available for any voltage? Are they listed at 32 shillings or so each, with discounts for quantity?

Yes? Then we must be preaching to the converted, for you are surely a LITESOLD user already.

Well, if you are, or even if you're not, you may be interested in the new PHILIPS ELECTROLYTICALLY IRON COATED BITS. They last up to 75 times longer than copper, and are a big advance on all previous iron coatings.

Please ask for literature L10

LIGHT SOLDERING DEVELOPMENTS LTD

28 Sydenham Road, Croydon, CR9 2LL

Telephone: 01-688-8589 & 4559



TRANSISTORS etc.

AC107	3/-	OC35	7/6
AC128	2/-	OC44	2/0
AF115	3/-	OC45	2/0
AF116	3/-	OC70	2/3
AF117	2/9	OC71	2/-
BFY18	4/6	OC72	2/3
BFY61	4/6	OC73	2/3
GET113	2/6	OC75	2/3
OA5	1/6	OC81	2/-
OA9	1/8	OC81D	2/-
OA81	1/6	OC82D	2/-
OA85	1/6	OC140	5/1
OA91	1/9	OC169	3/6
OC28	6/6	OC170	2/3
OC25	5/-	OC171	2/2
OC26	5/-	OC202	4/6
OC28	6/6	TK22C	1/6

Crystal Diodes—8 for 2/8. (7d.).

SILICON DIODE RECTIFIERS

BY100	800 pV	2/10
New 500 mA	250 pV	1/9
Avalanche 1 1/2 A	1200 pV	4/-
Six Amp Series	BY218 300 pV	3/6
	BY212 600 pV	4/6
	BY211 900 pV	5/-
	BY210 1200 pV	5/6
Millard Stack FW	Bridges	
12A 100 pV	39/6 (3/-)	
5 amp series	100 pV	7/6
	200 pV	9/-
	300 pV	12/-
	400 pV	12/-
	800 pV	25/-
10 amp series	50 pV	10/-
	100 pV	12/-
100 amp series	100 pV	12/-

available on request.

Midget Electrolytic Conds. Wire Ends

At 6d. each	0.8µF	25 volt
	2µF	150 volt
	4µF	150 volt
	640µF	2.5 volt
At 9d. each	2µF	300 volt
	4µF	150 volt
	8µF	12 volt
	16µF	16 volt
	30µF	10 volt
	100µF	6 volt
	125µF	4 volt
At 1/- each	16µF	250 volt
	50µF	10 volt
	100µF	12 volt
	200µF	10 volt
	320µF	10 volt
2000 MFD. 30V	4/-	
1500 MFD. 25V	4/-	

Also 8µF 350V 1/2, 25µF 25V 1/8 and 50µF 50V 1/8. Other electrolytics in current list. Postage, Packing and Insurance all above 7d. up to 3/- from 4-11, 12 and over paid.

2 GANG VAR. CONDENSERS: Mod., air-spaced, .0005 ea. sec. 5/- (1/-).

SUB-MINIATURE TRANSFORMERS Output (3Ω for OC72 etc.). Also Driver 2/8 each (7d.).

MULTIMETER: 20,000 Ω/V D.C., 10,000 Ω/V A.C. 0-5/25/50/250/500/1K volts D.C.

● 0-10/50/100/500/1K volts A.C. ● 0-50µA/2-5mA/250mA D.C. ● 0-8K Ω/6 meg Ω

● 10µF—0.01mfd/lmtd. ● -20 to +22dB. ● Complete with test leads and instructions.

● Over-load protected 1969 model with every refinement. \$4.7.6 (2/8). JUNIOR MODEL at 35/8 (1/6) 1000 Ω/V described in free list.

SOLDERING IRON, 81lm Mod. British High speed, 8 1/2 in., all parts replaceable, fully

guaranteed for professional, radio and general D.I.Y. use. 19/6 post free.

DIAMOND STYLII Replaces first TC3LP, TC3 and TC3LP/STEREO

COLLARO "O"; RONETTE BF40LP; GARRARD GC2LP and GC3LP; COOS GP68/87;

all at 7/6 each (6d.). ACOS GP91 ST/1P; BSR ST4 and ST9; SONOTONE 9TA and

9TAHC, PHILIPS AG3306. All at 13/6 (6d.).

SAPPHIRE all the above 7/6 types only, also ACOS GP37 at 3/6 each (6d.). ACOS

GP91 at 6/9 (6d.). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES, all fitted StylII and Standard fittings. Mono GP67/2, 13/6. ●

Mono de Luxe GP91/2, 17/-, ● Stereo Compatible—Mono which also plays Stereo records

monaurally with meter fitted. GP91/2, 19/6. ● Latest Stereo GP93, 22/-, ● Ceramic

Stereo, top quality for expensive outfit, GP94, 28/6 (all 1/-).

PP3 ELIMINATOR (A.C.) 17/6. (1/6) TWO STATION TRANS. INTER-COM. Excellent

baby alarm. Instant, easy fitting with leads, plugs and battery. All you require 52/6 (3/-).

TRANSISTORISED AMPLIFIERS, 3 watt, 9V operation, 45/6 (1/6); 7 1/2 watt, 6 trans.

24V operation, 67/6 (2/6).

Extra High Torque MINI-MOTOR, 4ft to 12V, 1 1/4 x 1/2 in. 5/- (3d.). 9,000 r.p.m.

MoCh. REV. COUNTER to 999, reset wheel, with T/recorders etc. 5/8 (1/-).

SUBSTITUTION BOXES, Capacitance 24/9 (1/6). Resistance 32/6 (1/6). Both full range and

complete. Full details in list.

TEST PRODS: Flexible, unbreakable 24" Red and Black leads, thin 4 1/2" prods, 1 1/2" plugs

4/9 (9d).

RECORDING TAPE: Finest quality British Mylar. STANDARD: 5in. 600ft. 7/3, 5 1/2in.

550ft. 8/9, 7in. 1200ft. 11/3, LONG PLAY 5in. 900ft. 10/-, 5 1/2in. 1200ft. 11/3, 7in. 1800ft.

18/-, (1/3 rest) 0.4m sec. list.

MICROPHONES—CRYSTAL MIC91, Desk, 16/3; MIC45, curved hand grip 17/3; Stick

"60" 20/3; Stick "39" 26/6 (1/6 each type). Cream plastic hand 7/6, or with "strut"

stand, switch and 2 leads with 2.5 and 3.5 plugs 11/-, Lapel (or hand) with clip 6/6 (1/-).

Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands,

25/- (1/6). DYNAMIC: Cream hand/table 14/- (1/-), MS10 50K Ω, 3 1/4 x 1/2 in. with Base,

Adaptor and Neck Cord 27/6 (2/6). MS11, similar, but fixed on flexible swan neck to switch-

fitted base 42/6 (2/6). DML32 Uni-directional, 50K/500 ohms imp, stand adaptor, very

high quality 6 1/2 x 2 x 1 1/4, \$5.9.6 (5/-).

GARDIOD DYNAMIC OMNI-DIRECTIONAL: Two recently introduced highly successful

mikes "SQUARE" 208, \$5.10.0. "BALL" type, 209, with built-in vol. control, switch

50K/500 ohms imp., \$5.17.6 (either type 5/-). Full details in list.

SPEAKERS: 12in round, fitted Tweeter, 6W, 3 or 15 Ω (state which), 25/6 (5/6); 2 1/2in. 3 Ω

6/6 (1/-); 3 x 4 heavy duty 3 Ω 13/6 (3/6) or for Stereo 32/6 pair, post etc. paid; 8 x 3in.,

3 Ω, 6/6 (1/-). Limited quantity powerful 2 1/2" PM transistor replacement speaker, high

ohms, excellent, 5/8 (1/-). HEADPHONE High Res. 2000 Ω ea. Earpiece 13/6 (1/6);

Stereo Dyn 8-16 Ω, 63/- (3/-); EARPIECES with lead etc., Min. Plug Magnetic 1/6;

Crystal 4/9 (either 7d.).

MICROPHONE INSERTS: Diameter 1.75in. or 0.9in either size 5/6 (6d.).

AERIALS, Car Types: Telescopic, vandal proof, locks retracted, 2 keys and all fittings,

25/8 (2/6) Motor driven, 12V, 6 section, complete \$7.10.0 (5/-).

FOR ALL PORTABLES and F.M. SETS. Telescopic 5 section 5 1/2-22in. with swivel, 5/-.

● 5-section 6 1/2-32in., no swivel screw hole in base, 6/6. ● 10-section 6 1/2-47 1/2in., no swivel,

screw hole in base, 12/6 (1/- all sizes).

SWITCHES: Standard toggle, metal, 250V 2A. One hole fixing: SPST 2/3, SPDT 2/9.

DPST 3/-, DPDT 3/3. Slide types. Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre

"off" 1/6. Reed magnetic on/off 1/9 (7d. each, all types). Rotary Switches etc. in list.

VIBRATORS: Famous makes only. 12 volt 4 pin non-synch 2/6. 12 volt 7 pin synch 10/-.

6 volt 7 pin synch 10/- (1/- each, all types).

MAINS NEON TESTER: Fly leads 2/- (7d.). Pocket screwdriver type 3/6 (6d). PLUGS: Std.

Jack, plastic body 2/- Screened 3/6. Sockets 1/6 (all 7d.). VALVE HOLDERS: B7G or

B2A, Moulded 4d. up to 4, 1/- over 4). CONNECTING WIRE: 5 coils asstd. coils each

5 yds. Solid Core 2/3, Flexible 2/6. Super thin for transistor wiring etc. 3/- (6d. all types,

per 5 coils). PICK-UP WIRE: Twin Super thin Flex, Screened, Sheathed, 1 1/2 yd. (6d. up

to 6 yds., over 6 yds. post free). TWIN MIKE CABLE: 1 1/2 yd. SINGLE MIKE CABLE:

7d. yd. Both flexible, screened and sheathed. ● FEEDER CABLE: TWIN R.F. bal. "ig. 8",

80 Ω, or flat 300 Ω transparent polythene insulated, either 6d. per yd. (all cables up to

three yards 8d. each additional yard, 1d. extra).

CURRENT LIST: Sent with all orders or free for a.s.c. details of cable, croc., clips and leads,

Continental din plugs for Grundig, Telefunken equipment, etc., dial, plug and sockets,

panel meters, record players and tape recording accessories, rectifiers, relays, wire wound

resistors. BATTERY CHARGERS test equipment, test prods, tape recorder, special trans-

istors, portable sets, car radio, more switches and other components, tools, Veroboard etc.,

etc. If interested in surplus equipment and units please say so. This advertisement cancels

all previous ones and lists supplied prior to April 30th.

R.F. INDICATOR, 5-Band, with meter antenna, monitoring crystal earpiece etc., 48/6

(1/6). Details in list.

RETRACTABLE FLEXIBLE LEADS. Space saving 'Curly', many uses in car and home: with

phono plug each end, 6 ft., 4/8; 12 ft., 7/9. With phono plug one end, phono socket

at other, 6 ft., 5/-, 12 ft., 8/6 (9d. on any).

FELSTEAD ELECTRONICS

(PW19)

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted. Charges apply to G.B. and Eire only. Overseas air or surface mail extra at cost. S.A.E. please for all enquiries.

Here's money-making repair data for over 1000 POPULAR MODELS

RADIO & TELEVISION SERVICING

This big RADIO & TELEVISION SERVICING repair library will help you speed up your repair work and increase your earnings. Packed with circuits, repair data and vital information it covers all the popular 1965-1969 TV's, Radios, Radiograms, Car Radios, Record Players and Tape Recorders—including the latest data on COLOUR TV.

Four volumes handsomely bound in maroon and gold. 2,180 pages written by a team of expert Research Engineers—there's no other publication like it! Speeds up repair work year after year. Examine this latest edition at home free for a week. Send no money—just post coupon below—there's absolutely no obligation to buy.

COLOUR TV


All aspects of Colour TV are covered—installing receivers, the explanation of new terms, adjustments on purity, colour balance, static and dynamic convergence, etc. The vital information in the colour section makes this repair library invaluable to the service engineer.

SERVICING DATA ON ALL THESE MAKES

Aiwa, Alba, Baird, Beogram, Beolit, Bush, Carousel, Cossor, Dansette, Decca, Defiant, Dynaport, Dynatron, Eddystone, Ekco, Elizabethan, Ever Ready, Ferguson, Ferranti, Fidelity, G.E.C., Grundig, H.M.V., Kolster-Brandes, Hitachi, Invicta, McMichael, Marconiphone, Masteradio, Motorola, Murphy, National, Newmatic, Pam, Perdio, Peto-Scott, Philips, Portadyne, Pye, Radiomobile, R.G.D., Regentone, Roberts' Radio, Sanyo, Sharp, Smith's Radiomobile, Sobell, S.T.C., Sony, Standard, Stella, Stereosound, Teletron, Thorn, Trans Arena, Ultra, Van Der Molen, World Radio.

SENT TO YOU BY POST ON

7 DAYS FREE TRIAL

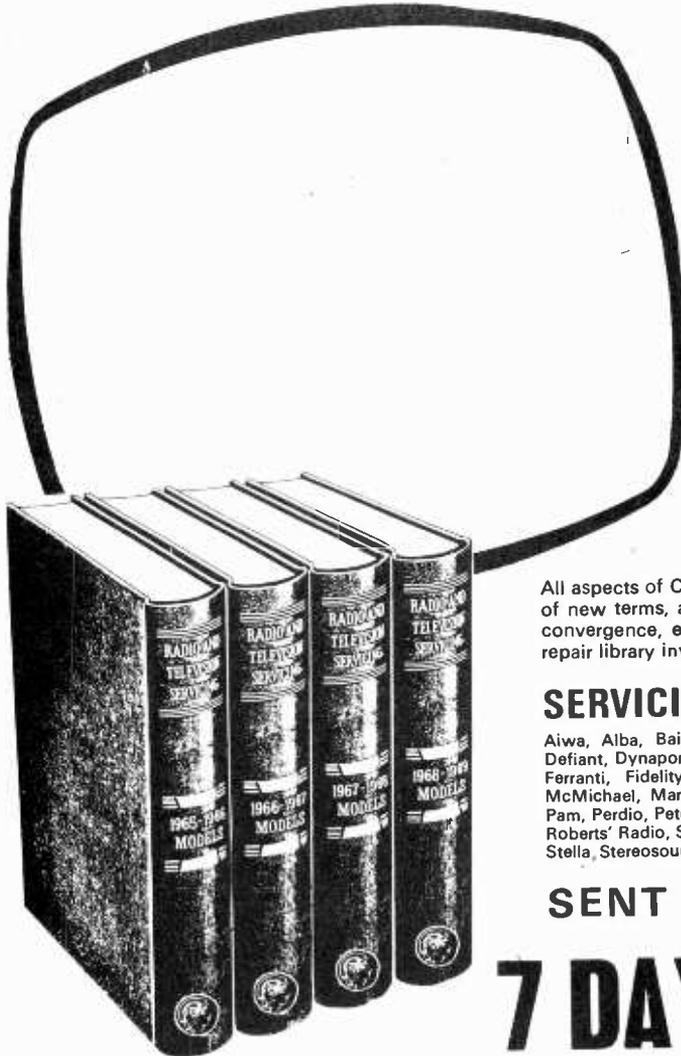

JUST OUT!

New 12th Edition of ELECTRICAL ENGINEER'S REFERENCE BOOK

Over 2,000 pages, more than 2,400 Diagrams, Photographs, and Tables. A comprehensive reference work on modern theory, practice, equipment and latest developments written by 75 leading experts.

Main Sections Include—

Theory and Calculations. Power Station Practice. Cables and Wires. Lighting, Heating Lifts. Motors, Wiring and Installation. Applied Electronics. Automatic Control. Computers. Latest I.E.E. Reg. requirements. Education, Training, City & Guilds, etc.



To: Buckingham Press Ltd., 18-19 Warren Street, London, W.1.

Please send RADIO & TV SERVICING—4 volumes, without obligation to buy if you accept my application. I will return the books in 8 days or post:

- Tick (✓) Full cash price of £18 or
 20/- deposit and 16 monthly payments of 20/- paying £17 in all.
 Also send me on 7 days trial Electrical Engineer's Reference Book. Cash price 26 6s. (or 12/- dep. 12 monthly payments of 10/- paying £6 12s. in all).

If you are under 21 your father must fill in coupon.

Full Name
(BLOCK LETTERS PLEASE)

Address

County

Occupation

Signature
RTV4/EERB/3999

Mr.
Mrs.
Miss

Please tick (✓) here

The address on left is
my/our property

Rented

unfurnished

Furnished accom.

Temporary

address

If none of the above
please answer here

AIR/SEA TRANS/REC. RESCUE

Compact VHF Trans./Rec. Fits in the pocket. Consists of Mike/Speaker, amplifier, aerial, transmitter and receiver. Were made to operate up to 100 miles depending on terrain. Operates from dry batteries. Completely self-contained. Cost Govt. over £50 each. Regulations state must not be operated in UK so please mention "For Dismantling purposes only" when ordering. Price £21.00 each, p. & p. 10/- Two sets for £35.00 post free. Four sets £8, carriage free. Bulk sale of 10 sets £15, carriage £1. Export enquiries invited.



PRECISION PANEL METERS

Brand new, boxed and fully guaranteed. With fixing nuts and bolts. Size approx. 3 1/2 in. square. 0-500 volts FSD. As used by leading laboratories. Ex-stock, only 35/-, p. & p. 5/- Two for £3, post free. **HEAVY DUTY POWER SUPPLY UNITS**
Bulk Purchase. Famous manufacture. Must have cost nearly £40 each. Input 200/250 volts 50c/s a.c. Output 250 volts d.c. at approx. 175m.a. 6-3/12 volts at approx. 4 amps a.c. Robust metal rack mounting cabinet, size approx. 19 x 15 x 8 in. Price only 85/-, carriage and insurance 15/- All units are fully fused and metered.

AIRCRAFT— PLUS GENERAL TELECOMMUNICATIONS BAND REC.

Listen to the thrills of Aircraft Pilots and Airports at work. Also Civil Depts, Fire and Ambulance services. Gas and electricity depts. Ideal for receiving 2 meter amateurs. Gives super reception within the range of all transmissions. A fully transistorised receiver covering 47-147mc/s VHF broadcasts. Robust attractive 2-tone finish metal cabinet size approx. 7 x 4 x 4 in. Operates from a 9 volt internal battery. Speaker or earphone output plus remote telescopic aerial. Only £8.19.8 carr. and insurance 10/6 C.W.O. or C.O.D.

SURPLUS BARGAINS HEAVY DUTY ACCUMULATORS

Type 1 (6 volt) 40AH. In metal cabinet. Size approx. 10 x 9 x 6 in. Complete with output socket, carrying strap. Brand new and unused. Worth £10 each. Our Price 55/-, carriage and insurance 15/-
Type 2 (6 volt) 16AH. In sturdy wooden cabinet with carrying strap. Worth £7 each. Brand new and boxed, only 32/6 each, p. & p. 12/6.
FIELD TELEPHONES
Type F. Housed in a portable wooden case. Ideal for indoor/outdoor communication up to 10 miles. Absolutely brand new. Price only £5.19.8 per pair, carriage and insurance 15/-
19 Set Headphones and Mike. Not new but in working order. Only 7/6 per set, p. & p. 4/6.
Tannoy Mikes. As new, 9/6 each, p. & p. 3/6 (heavy duty, ideal for P.A. work).
High Quality moving coil headphones and mike. Brand new, only 17/6, p. & p. 5/6. Suitable for most applications (cost approx. £3 per pair).

POWERITE UNIVERSAL BATTERY ELIMINATOR
BATTERY ELIMINATORS
AND STABILISED POWER PACKS

The most economical method of running transistorised equipment from AC mains. Power radios, record players, etc. MK. 1 model replaces all 9 volt batteries. Price only 35/- p. & p. 5/- MK. 2 model. Output 6 volts, 7 1/2 and 9 volts. STABILISED. This model is ideal for running Hi-Fi and test gear. Price only 85/- p. & p. 5/-



RUN YOUR 19 SET TX/RX FROM AC MAINS
We manufacture a brand new unit ready to operate all 19 Set Trans/Rec direct from the mains. Complete with full connecting instructions. Contained in an attractive steel cabinet. Price £6.10.0, carr. & ins. 10/-
RECEIVER VERSION ONLY £4.10.0 carr. & ins. 10/-
SHIPPING/80/160M BAND REC.
Listen to the worlds shipping, Hams at work. Covers the complete Maritime, and Trawler Band, plus top band and 80 m. Attractive hammer finished case, size 7 x 5 x 5 in. A neat little superhet. Fully transistorised. Works from 9 volt battery. Speaker or earphone output. Brand new from makers. PRICE £8.10.0, carr. 10/-

SMOOTHING UNITS
Beautifully made pieces of equipment. 12 volts or 24 volts d.c. input gives a fully smoothed fully regulated d.c. output. Worth £30 each. Robust metal cabinet with provision for standby battery. Brand new in maker's cartons. Price 65/-, p. & p. 15/-

COMMUNICATIONS RECEIVER TYPE T.R. G.D.X/20.C.

Brand new fully transistorised Communications Receiver. Specifications: 4 complete ranges 550 Kc/s to 30 Mc/s, covering all amateur bands, shipping and trawler bands, and broadcast bands. A highly efficient double tuned superhet, comprising R/F aerial tuning section, A.V.C. and built-in B.F.O. for C.W. or 88B reception. Ideal for fixed or mobile reception. Operates from Standard 9 volt battery, provided that fits internally. Gives over 1 watt audio output. With speaker and earphone output. Hammer finished robust steel case of pleasing modern design with all controls on well set-out front panel. Size approx. 9 x 7 x 6 in. British manufacture. Due to huge purchasing we can offer these excellent receivers at less than half their normal worth. Complete with handbook £16.10.0. Carr. and ins. 15/- Headphones if required 17/8, per pair, p. & p. 2/8.

NEW SHOP NOW OPEN

AT 88 BRIDGE END, MEADOW LANE, LEEDS 1.

OPEN 9-6 p.m. WEEK-DAYS AND SATS.

MINIATURE TRANSISTORISED B.F.O. UNIT

This is a miniature transistorised B.F.O. unit (tunable) that will enable your set to receive C.W. or S.S.B. reception. Compact, single hole fixing. This small unit will fit anywhere. Ideal for all Ex-Govt. Communication Receivers and most Commercial Types. Complete with fitting instructions. 49/8, post free.

19 SET CONTROL BOXES

Brand new and boxed 10/-, p. & p. 5/- Two for 27/8 post free. If purchased with 19 Set phones and mike, deduct 5/- from total.

MINIATURE MOVING COIL SPEAKERS

1 1/2 in. dia. Only 3/6 each, p. & p. 1/6. Two for 8/6 post free. 4 for 15/- post free.

12 VOLT HEAVY DUTY DPDT RELAYS

High current double pole contacts plus auxiliary low current contacts 12 or 24 volt operation. Up to 20 amp handling capacity. Worth nearly £3. Make ideal aerial changeover units, car, or house burglar alarms, switching relays. Size only 3 x 2 x 2 in. Price 17/8 each, p. & p. 2/6. 2 for 30/- post free.

RECTIFIER SALE 6/12 volt full wave bridge, 4 amps.

Brand new manufacturers surplus only 4/6 each, p. & p. 1/6. 2 for 10/- post free.

GLOBE SCIENTIFIC LTD Mail orders only to DEPT. P.W. 24 CAWOODS YARD, MARSH LANE, LEEDS 9

MARTIN IS HIGH-FIDELITY

The first and still the most satisfactory unit assembly system



F.M. TUNER



STEREO CONTROL ASSEMBLY

For many years now Martin Electronics have been producing highly efficient and dependable prefabricated module-type units for simple assembly into reasonably priced high fidelity systems. Many purchased at the time of the introduction of the Martin Audiokit system are in regular use to this day, completely justifying our claims for years of trouble-free service. No system gives you wider flexibility in the choice of units available than Martin and all equipment conforms precisely to stated specification. When new units

are introduced, they are designed for adding to those produced so far, making it easy and economical to extend and improve your existing Martin Audiokit set-up. Anyone can assemble Martin equipment with ease and the foreknowledge that when finished, he will be in possession of a true hi-fi assembly of the very best kind which looks and sounds completely professional in every way—and MARTIN AUDIOKITS remain as ever, the units that have true add-on ability.

AMPLIFIER SYSTEMS • TUNERS • RECORDERS

MARTIN HIGH-FIDELITY AUDIOKITS cover the widest possible range of requirements. They are available for Mono, and can be doubled up for conversion to stereo, or as complete stereo units. 3 ohm and 15 ohm systems. Special pre-amp for low output pick-ups—escutcheon panels to suit the arrangement you choose. Tuner is styled to match.

- UNITS INCLUDE:
- 5-stage input selector
 - Pre-amp tone controls
 - 10 watt amp. (3 ohms)
 - 10 watt amp. (15 ohms)
 - Mains power supply
 - F.M. Tuner

MARTIN ELECTRONICS
154 High Street, Brentford, Middlesex
Please send Audiokit Hi-Fi/F.M. Tuner/Record-
akits Leaflets. (Strike out items not wanted)

Name

Address

.....

PW6

Start by sending for leaflets at once Trade enquiries invited
MARTIN ELECTRONICS LTD. 154/5 HIGH STREET, BRENTFORD MIDDLESEX. ISLeworth 1161/2

LIND-AIR OPTRONICS LTD

See our vast range of Electronic Components at our new Component Centre 25 Tottenham Court Road




Battery Eliminator. Enables transistor equipment to be operated from AC mains. 6/9V 12v. output selector switch and on/off switch. Case size 4 x 2 1/2 x 2in. complete with mains lead, connecting leads and instructions. 59/6. P. & P. 3/6.

GARRARD DECKS



- SRP25 less cartridge 25. 9.6
- 1025 Stereo/Mono with cart. 47.19.6
- 2025 Stereo/Mono with cart. 48. 9.6
- 3000S Stereo/Mono with cart. 29.19.6
- 3000D Stereo/Mono with cart. 210.19.6
- SP25 less cartridge 210.19.6
- SP25 with Decca Deram cart. 217. 4.6
- SL35 less cartridge 212. 9.6
- SL55 with Decca Deram cart. 218.14.6
- Covers for above 22.10.0
- Bases for above 43. 0.0
- AP75 less cartridge 219.19.0
- SL75 less cartridge 223.19.6
- SL35 less cartridge 233.19.6
- Bases for above 241.9.6
- SPECIAL OFFERS**
- SP25 less cart., with base 213. 2.6
- P. & P. Decks 12/6, Cover 4/6, Base 4/6.
- P. & P. Deck/Cover/Base 17/-

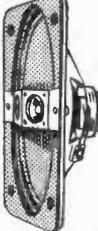EMI COMBINATION LOUDSPEAKERS. 13 1/2 x 9 1/2in. elliptical with two 2 1/2in. tweeters. 16 ohm impedance. Power handling 10 watts. Brand new and guaranteed. 99/8. P. & P. 7/6. (Also available without tweeters. 59/6. P. & P. 7/4.)



"HI-TONE" LOUDSPEAKER British made full range 10in. unit handles up to 10 watts. Ceramic magnet. Freq. response: 40-10,000 cps. Imp: 15Ω. Flux density: 10,000 lines. 49/6. P. & P. 4/6.



SOLDERING GUN

Comfortable grip with trigger control. "U" shaped 3/4in. bit to minimise wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use. 220-250 volts. 85 watt element. 49/8. P. & P. 3/6.

"ADASTRA" SOLDERING IRON. 30 watt. Employs its protective cover as a handle. AC 230/250v. With aft. lead. 12/6. P. & P. 2/6.

NEW-VEH AIRCRAFT BAND CONVERTOR. When placed within lin. of a MW band radio full coverage of V.H.F. Aircraft Band 108-135Mc/a. can be obtained. All transistor, 9v battery operation. Fully tunable 18in. x 7 section telescopic aerial. Size 4 x 2 1/2 x 1 1/2in. 79/6. P. & P. 3/6.



STEREO AMPLIFIERS

ORAL STEREO AMPLIFIER MODEL TS-135. SOLID STATE. 18 TRANSISTORS.




13.5 watts per channel. Free standing unit with black crockle case and satin alloy front panel. Specification: Frequency range 30c/s to 20Kc/s (±3dB). Harmonic distortion 2% at 10 watt (1Kc). Cross talk 45dB at 1Kc/s. Signal to noise ratio 60dB. 150mV, Taphead 4mV. Tone controls: Treble 10Kc/s at ±10dB. Loudness (medium frequency cut). Output impedance 8 ohms. Mains operated. Size 4 1/2 x 6 1/2 x 1 1/2in. Price £26.5.0. P. & P. 9/6.

DULCI STEREO AMPLIFIER MODEL 207



8 watts per channel. Integrated high fidelity transistor Stereo amplifier. An attractive free standing unit with provision for mounting in equipment cabinet. Finish Dark Grey vinyl simulated leather grain. Front panel satin alloy. Specification: Sensitivity, Radio/Tape 100mV into 1Mohm. Phono 100mV into 1Mohm. 3 position selector on front panel. Frequency response: 40c/s to 16Kc/s ±2dB. Separate bass and treble controls with boost and cut, balance control. Mono/Stereo Function switch (both channels work in parallel). Normally £23.2.0. LIND-AIR PRICE £19.19.0. Plus P. & P. 9/-.

S-DeC BREAD BOARD

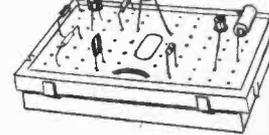

Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jigs and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.

4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £5.17.6. P. & P. 3/6.

SPECIAL PURCHASES

DE-LUXE STEREO HEADPHONES



With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000cps. With lead and stereo plug. Only 59/6. P. & P. 3/6.

NEW STEREO/MONO HEADPHONES

SDH-7. Soft rubber earpieces with slide switch for mono/stereo listening and ind. vol. controls. Impedance 8-16 ohm. Freq. response 25-15,000 cps. With lead and stereo plug. £6.6. P. & P. 3/6.



HI-TONE RECORDING TAPE

BRITISH MADE. TOP QUALITY		
J1001	3"	Long Play PVC 225ft. 5/8 P. & P. 1/2.
J1002	3"	Triple Play Poly 600ft. 10/8 P. & P. 1/2.
J1003	5"	Long Play PVC 960ft. 10/- P. & P. 1/8.
J1004	5"	Double Play Poly 1200ft. 15/- P. & P. 1/8.
J1005	5"	Long Play PVC 1200ft. 12/6 P. & P. 2/-
J1006	5"	Double Play Poly 1800ft. 22/6 P. & P. 2/-
J1007	7"	Standard Play PVC 1200ft. 12/6 P. & P. 2/6.
J1008	7"	Long Play PVC 1800ft. 17/6 P. & P. 2/6.
J1009	7"	Double Play Poly 2400ft. 25/- P. & P. 2/6.
J1010	7"	Triple Play Poly 3600ft. 50/- P. & P. 2/6.



NEW TRANSISTOR MODULES

E.1311. PHONO PRE-AMPLIFIER. Size 2 x 1 x 1/2in. Built-in R.I.A.A. characteristics enabling low output magnetic pick-up cartridges to be amplified up to 1 volt. Input 100Kohm: Gain 28dB: Max. output 3v: Max. input 50mV. Distortion 0-15% (at 1v level). Power supply 9-12v. 29/6. P. & P. 2/-.

E.1313. MICROPHONE PRE-AMPLIFIER. Enables a low output microphone to be used with an amplifier or radio. Input Imp. 100Kohms: Gain 28dB: Max. output 3v: Max. input 50mV: Distortion 0-15% (at 1v level): Freq. response 10Hz-50KHz. Power supply 9-12v. 29/6. P. & P. 2/-.

E.1318. DUAL LAMP FLASHER. A switch module for electronically alternating two miniature bulbs, 6V, 100-200mA. Ideal for models, toy boats and planes, displays, warning and security devices, communications signals, etc. Flasher time 1 sec: Power supply 6v DC: Current 150mA: Lamp 6v 150mA. 25/- P. & P. 2/-.

E.1315. ELECTRONIC ORGAN TONE OSCILLATOR. Used in conjunction with an organ keyboard, variable resistances and a 9 volt power supply, this module acts as the oscillator unit for an electronic organ. Tone Frequency: 200-1,000Hz: Output 80mW: Current 15mA. 25/- P. & P. 2/-.

E.1314. POWER AMPLIFIER. When used in conjunction with E.1311, E.1312 and E.1313 units this amplifier module produces about 300mW output for speaker connection (8-16 ohms), without necessity for an output transformer. Input Imp. 1,000 ohms: Gain 20dB: Output 300mW: Distortion 3% (at 200mW output level): Freq. res. 50Hz-10KHz. Power supply 9v. Current 20mA at no signal, 80mA at max. output. 29/6. P. & P. 2/-.


E.1317. MINIATURE MORSE TRANSMITTER. Will transmit to any adjacent AM Receiver, also makes a useful oscillator for trouble shooting. Audio tone 400c/s. Radio frequency range 400c/s to 30Mc/s. Power supply 3v DC. Current 35mA. 25/- P. & P. 2/-.

E.1312. TAP PRE-AMPLIFIER. Incorporating N.A. R.T.B. curve characteristics, this amplifies tape head signals up to 1 volt within the frequency range of 30Hz-15KHz. Input Imp. 100Kohm: Gain 25dB: Max. output 2v: Max. input 50mV: Distortion 0-15% (at 1v level): Power supply 9-12 volts. 29/6. P. & P. 2/-.

E.1316. MORSE CODE OSCILLATOR. A transistorised morse code oscillator (buzzer) to be used in conjunction with an operating key. Suitable for direct connection to a loudspeaker. Tone Freq. 400Hz: Power output 80mW: Power supply 3-9v.: Current 45mA. 25/- P. & P. 2/-.

Visit our Brand New Hi-Fi Demonstration Room, Tape Bar, Scientific Show of Microscopes, Binoculars, Telescopes also Watches at 18 Tottenham Court Road

COMPACT 2-WAY INTERCOMS

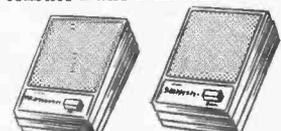

For table or wall mounting. Smart two tone grey cases size 3 1/4 x 1 1/4 x 3/4in. Complete with lead, staples and 9v battery. 55/- P. & P. 3/6.

LIGHT DIMMER AND SWITCH

600 watts. 250 v. Fully suppressed complete with control knob and fully assembled, less casing. Will fit most electrical fittings. Uses 4 silicon rectifiers, 2 transistors and 1 thyristor. Many other uses. £3.15.0 P. & P. 2/-.

MODEL MAKER'S MOTOR No. 15EN. Voltage 11.5v. Current 400mA. Torque 12g-cm. Body size 1 1/2" long x 1/2" dia. Shaft 7/16" dia. x 1/8" dia. Ideal for small models and toys. 5/6 each. P. & P. 1/3. 3 for 15/- P. & P. 2/6.

NEW TRANSISTOR CHECKER. For measuring alpha, beta and Ico. factors of transistors also for checking germanium and silicon diodes. Internal 9v. battery. Wide reading scale. Moulded case size 7 x 4 1/2 x 3 1/2in. Ranges: Alpha 0.7-0.9997; Beta 20-200; Ico 0.5-5,000A. Diode test: forward and reverse internal resistance. Resistances: 200 ohm-1 megohm. Complete with connectors and instruction booklet. £7.18.6. P. & P. 3/6.

SHIRA 62D MULTI-TESTER 20,000 o.p.v. DC voltage: 0-25-50-250-500-2.4K (20,000 ohms per volt). AC Voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50µA, 0-2-5mA, 0-250mA. Resistance: 0-6K, 0-6Mg (300 ohm and 30K at centre scale.) Capacitance: 10pf. to .001 mfd., .001µf to .1µf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1in. Complete with case 77/- P. & P. 3/6.

TTG.G1001 MULTITESTER in leather case. 20,000 o.p.v. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C Current 0.50µA, 0-250mA Resistance 0-60K, 0-6 Megohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 x 1in. 85/- P. & P. 3/6.

NEW-SINCLAIR IC-10 INTEGRATED CIRCUIT 10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONI.Y 69/8. P. & P. 1/6.

LIND-AIR OPTRONICS LTD
18, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.
Telephone: 01-580 2255/4532 7679
Shops open 9-6 pm. Monday to Saturday. Thursday until 7 pm.


ALL ORDERS TO Dept. PW669, 54a Tottenham Court Road, London, W1.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

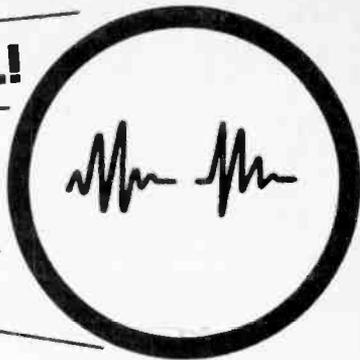


a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .

1

OWN and HANDLE a

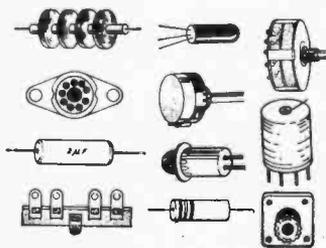
complete range of present-day **ELECTRONIC PARTS and COMPONENTS**



2

BUILD and USE

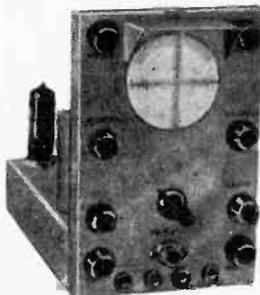
a modern and professional **CATHODE RAY OSCILLOSCOPE**



3

READ and DRAW and

UNDERSTAND CIRCUIT DIAGRAMS

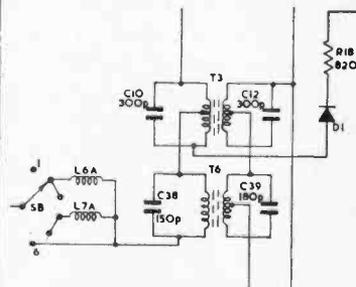

4

CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
 - TRANSISTOR EXPERIMENTS
 - AMPLIFIERS
 - OSCILLATORS
 - SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
 - COMPUTER CIRCUIT
 - BASIC RADIO RECEIVER
 - ELECTRONIC SWITCH
 - SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
 - D.C. EXPERIMENTS
 - SIMPLE COUNTER
 - TIME DELAY CIRCUIT
 - SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE

POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE PW 6

PRACTICAL WIRELESS

VOL 45 No 2

Issue 748

JUNE 1969

TOPIC OF THE MONTH

Standardisation

OBSERVANT readers will have noticed that P.W. is changing over from c/s to Hz. Much of industry has already made the change and most technical journals have followed suit, some of these decisions having been made, as was P.W.'s, not for choice but for conformity.

The idea was to honour the pioneer Hertz, celebrated for his work on radio waves. Thus changing 15kc/s for 15kHz makes some kind of sense, but 50c/s to 50Hz does not, for these are audio frequencies. Blumlein or another audio pioneer would have been a better choice!

But this is only one small item in the move towards Continentalisation (what an ugly word!), the abandoning of a perfectly understandable and descriptive term for one that is not. Already we are taking our medicine, if not our beer, in millilitres, our currency is being decimalised, temperature is given in both C and F and we are being generally geared to the Common Market, even if we never join that confederation.

This movement has led to outbreaks of midsummer madness and perhaps the choicest example was in a recent issue of a contemporary radio trade journal. In big bold headlines it was proclaimed that a certain maker's TV sets were now "metric ready". Reading on, it was discovered that this awe-inspiring term meant no more than that the cabinet dimensions were specified in centimetres instead of inches! So help us, it's true.

At least one other journal has abandoned inches per second for tape speeds in favour of metric figures. Here we find, for instance, that the fairly roundish $7\frac{1}{2}$ i.p.s. becomes 19.1cm, although the actual figure is 19.05cm. Some standard! Advertisements in the same journal show that the actual makers are still, however, specifying in i.p.s.

We are, though, all for standardisation in practical matters. For instance, the sooner everyone goes over to the DIN specifications for plugs and sockets the better. Then there will be no need for a caseful of odd leads carrying phono, coaxial, DIN, banana and "special" plugs and sockets. There are many fields in which acceptance of standard interchangeable components would be a blessing for everyone concerned. We'd like to see more of it. W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	95
News and Comment	96
Letters to the Editor	119
Practically Wireless by Henry	131
On the Short Waves by Christopher Danpure and David Gibson, G3JDG	132, 135
MW Column	140

CONSTRUCTIONAL

Comprehensive Audio Mixer by Andrew Dicks	98
P.W. Double-12, Part 3 by Hal Moorshead	102
Slimline Superhet by F. G. Rayer	113
Take 20 by Julian Anderson	120
Comprehensive Transistor Tester, Part 2 by J. A. Jebb	123

OTHER FEATURES


P.W. Guide to Components, Part 6 by M. K. Titman, B.Sc.	106
Transistor Output Stages by I. R. Sinclair	116
Aerials, Part 3 by A. J. Whittaker	127
Basic Semiconductor Technology, Part 2 by M. F. Docker, M.Sc.	136

JULY ISSUE WILL BE PUBLISHED
ON JUNE 6th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2. Phone: 01 836 4363. Advertisement Department: Fleetway House, Farringdon Street, London, E.C.4. Subscription rates, including postage: 42s. per year to any part of the world. ©IPC Magazines Ltd., 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

NEWS AND COMMENT...

NEW SOLDERLESS BREADBOARDS FROM S.D.C.

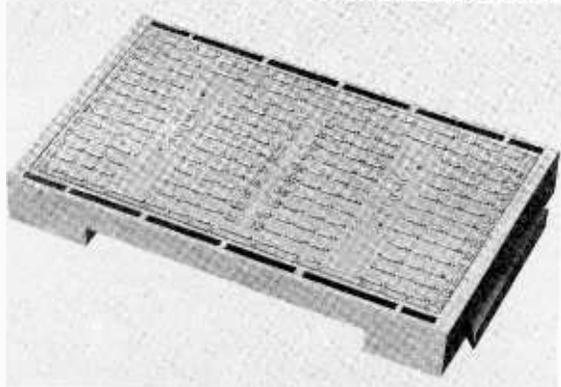

S.D.C. Products (Electronics) Limited, have extended their range of modular, solderless breadboarding systems to include two new DeCs specifically designed to accommodate integrated circuits as well as discrete components and to have an increased contact capacity—208 contact points per DeC—as compared to the original S-DeC.

The layout of the contacts consists of two panels of parallel rows of electrically linked contacts spaced 5mm. apart. This spacing enables short lead devices to be inserted directly into the boards. The new DeCs may be interlocked to give a stable area of breadboard of any desired size and each DeC has slots to accommodate two control panels.

The DeCs are formed from glass-filled nylon enabling temperature cycling tests to be carried out and contacts are of heavy gauge phosphor bronze in natural finish, in either silver plated or gold over nickel plated finish.

DeCs are supplied in two packs. The single pack contains one DeC, one control panel (with bushes for reducing the diameter of drilled holes in the panel) and a jig (for pre-forming components). The 6-DeC pack contains six DeCs, six control panels, sets of bushes and jigs, 50 x 1mm. plugs and eight links for joining power rails in neighbouring DeCs.

WHITBY TELEVISION AND VHF RADIO RELAY STATION

The BBC has placed an order for the construction of the building for the television and v.h.f. radio relay station which is being built to serve Whitby, Yorkshire.

This new relay station is being built near Abbey Lane, Whitby. It will transmit BBC 1 television on channel 4, with vertical polarisation, and v.h.f. radio on the following frequencies: Radio 2 89.6MHz, Radio 3 91.8MHz, Radio 4 94.0MHz.

PRESTON MOBILE RALLY

We of the Preston Amateur Radio Society are again basing our mobile rally on Kimberley Barracks, Deepdale Road, Preston, and this year's rally will be held on Sunday, 31st August, 1969.

For further details send s.a.e. to Press and Contest Sec.: Mr. G. Wright, 56 Queensway, Bamber Bridge, near Preston, Lancs.

BORDER AMATEUR RADIO SOCIETY

This new radio society has been formed to serve the Southern Borders and North Northumberland. The Secretary, J. Nairn, asks all who are interested to contact him at 5 Murrayfield, Gordon, Berwickshire or the Chairman, G. Shankie, GM3WIG. Meetings are held in the Cross Keys Hotel, Greenlaw.


TRISTAN CALLING

Mr. Roy Folgate whose callsign G3KDY is well known on the bands, will now have a new callsign—ZD9RF, for he is now resident on Tristan da Cunha, the volcanic island in the South Atlantic where he has taken up the post of Superintendent of Posts and Telegraphs.

"HEMEL HEMPSTEAD RADIO-NEWSLETTER"

This is the bi-monthly newsletter of the Pathfinder Radio Group. They also publish and circulate from time to time *Pathfinder DXer*. Since forming in 1964, the subscription has been free, but as from April 1969, the group are charging 10s. to new members. The *Hemel Hempstead Radio-Newsletter* is circulated in 9 European countries. For further details, s.a.e. to Alexander Lex-Arnold, c/o 13 Little Road, Hemel Hempstead, Herts.

MINI 15MHz OSCILLOSCOPE

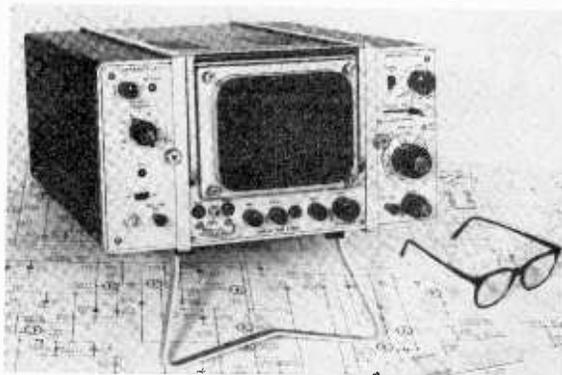

What is thought to be the smallest portable solid state oscilloscope of its sort with 15MHz bandwidth, has been announced by Dynamco and is available at £355.

It consists of a 7100 display unit, with a new 1Y7 single channel amplifier measuring only 2½in. and a new 1X6 timebase module, also of a similar width.

The 1Y7 is a general purpose single channel amplifier having a basic deflection factor of 50mV/division at full bandwidth and a maximum deflection factor of 5mV/division with a switched X10 a.c. coupled preamplifier. When the 1Y7 is used for horizontal deflection, the deflection factor remains the same and the frequency response is nominally d.c. to 4MHz—3dB.

The 1X6 timebase module is intended to provide, in a minimal width, most of the facilities required for general purpose applications. The calibrated sweep rates are 0.5µS/div. to 0.2secs/div. in 19 calibrated steps of 1, 2 and 5 sequence and a fine control provides continuous uncalibrated variation between steps and extends the range to 0.5secs/div.

A switched X10 magnifier gives a maximum sweep speed of 50nS/div.

NEWS AND COMMENT...

NEW FOR TWO-METRE FANS

Now joining the Hallicrafter CRX101 pocket-size solid-state aviation frequency receiver already available from Electroniques is the companion model CRX102.

Hallicrafters' CRX102 ranges from 144 to 174MHz (the high-band), tuning to the two-metre Amateur band.

Like the CRX101, it features a superhet circuit with three i.f. stages and five tuned circuits. It receives both a.m. and f.m. An r.f. stage boosts sensitivity and push-pull class B amplification combines high efficiency and power with long battery life (standard 9V battery).

Other features are: automatic gain control, telescopic aerial, provision for external aerial and earphones.

Price of the CRX102, like the 101, is £17 9s. 6d., plus 7s. 6d. postage. From Electroniques, Edinburgh Way, Harlow, Essex. (Harlow 26777.)

THE GOSCUT PISTOL-GRIP SHEAR

The Goscut single-handed shear, only six inches long from tip to tip, is adjustable to cut almost all sheet materials from paper to steel. It has three interchangeable blades. The blade bears down through a slot in a flat surface, so that the tool provides its own anvil or workbench. Close support at the point of cut prevents distortion or fracture of the material and leaves a clean-cut edge.

Adjustment of the slot width enables materials of varying thicknesses below $\frac{1}{8}$ in. to be cut. Cutting speed is about 30 seconds a foot run or a little longer for the heavier gauges of metal.

W. Norman Stevens, the Editor of PRACTICAL WIRELESS and Practical Television magazines opened the proceedings by welcoming readers to Caxton Hall and introducing Ian Nicholson of the Mullard Films and Lectures Division, and A. T. Collins, Managing Editor of the "Practical" group of magazines.

Ian Nicholson then introduced the film entitled, *It's the Tube that Makes the Colour*

which described the manufacture and operation of the Mullard Colour Screen colour tubes and also described how the pictures are received. It is being used in the BBC Trade Test Transmissions.

After the film, Mr. Nicholson delivered a lecture entitled "Purity, Convergence and All That". He explained that deviation from ideal picture reproduction occurs for one main reason—the fact that the three guns cannot all be mounted on the axis of the tube itself. It is because of this that geometrical errors between the three rasters that are produced and some means of correction must therefore be provided.

"It is with these means of correction that we are primarily concerned tonight", he said. "We find moreover that the prime components required to effect these corrections are all mounted externally around the tube itself. There is the magnetic shield, the deflection coil assembly, radial convergence magnets, the purity magnets and the blue horizontal or lateral shift magnets. The adjustment of static and dynamic convergence may at first seem rather complex but it is not nearly as difficult as it may appear. After all, purity adjustment consists merely of setting a couple of ring magnets for purity of colour near the screen centre. The position of the scanning coils should then be adjusted along the neck of the tube to give pure colours away from the centre. Static convergence is achieved simply by adjusting five permanent magnets on the tube neck to bring the red, blue and green beams together to give a white crosshatch pattern at the centre of the screen. Finally, dynamic convergence



VHF MOBILE TX TRANSISTORS

Two new high-gain, n-p-n silicon planar transistors announced by Mullard have been specially developed for use in v.h.f. mobile transmitters. Types BLY83 and BLY84, they are electrically equivalent to the TO-60 types BLY35 and BLY36 respectively.

Emitters in the new transistors are composed of several interdigitated structures, each with its own current-sharing resistor. Consequently, they are so robust electrically that they can be used in circuits containing no protection against aerial mismatch or variations in the supply voltage.

The transistors are enclosed in capstan type encapsulations that minimise lead inductance and lend themselves to efficient r.f. circuit design. They are designed primarily for use with a nominal supply voltage of 13.8V, and are intended for output stages—the BLY83 in a.m. and the BLY84 in f.m. transmitters.

12 VOLTS FROM 6

Philips new EN5013 transistor converter unit (suggested selling price £4 10s) enables a 12 volt car radio, when switched to negative earth, to be used in vehicles with a 6-volt electrical system.

The new converter unit has a power rating of 12 watts and can be inserted in the supply lead of the radio and operated with a separate on/off switch or, alternatively, wired to the radio switch so that it can be switched on/off with the radio.

is the manipulation of a dozen or so controls for the two line standards in a generally established sequence in order to bring the separate red, green and blue crosshatch line patterns together to give single white lines at the top, bottom and sides of the picture."

As yet there is no standardised terminology for the controls involved and each manufacturer has his own ideas about how and in what sequence these operations should be tackled—dependent usually on his own particular circuitry. Mr. Nicholson presented a broad picture of the principles involved in colour television receivers so as to make it easier to understand the individual service procedures.

After his talk, Mr. Nicholson opened the meeting to questions from the audience.

On the question of the kind of developments we can expect to see in the future of colour TV, Mr. Nicholson said the main developments would be in the use of integrated circuits which would give greater reliability and improved performance. Integrated circuits would be the subject of Filmshow '70 and Mullard Ltd are at present working on the production of the film.



A. T. Collins, W. N. Stevens and Ian Nicholson.

comprehensive



★ AUDIO ★ MIXER

ANDREW DICKS

MOST of the small audio mixers that are available to amateur audio enthusiasts have very limited applications. Many people who own these will have realised their incapability of accommodating all the various input sources that the amateur may use. One usually resorts to "hooking up" arrangements of attenuators, transformers and other devices to match sources to inputs.

The purpose of this mixer is to provide such comprehensive facilities that almost anything can be plugged into it without alteration. It is the wide range of available inputs that make this unit such a comprehensive piece of equipment. If good quality components are used the results will be no less than hi-fi and the price and appearance of finished unit will compare favourably with any commercially obtainable instrument.

General Principles

Broadly speaking, audio mixers may be classified into "active" or "passive" types. High quality devices are usually "active", that is, they incorporate some form of amplification. A block diagram of an "active" type of mixer is shown in Fig. 1, and the mixer to be described is based on this system. The inputs are fed to four emitter-followers which

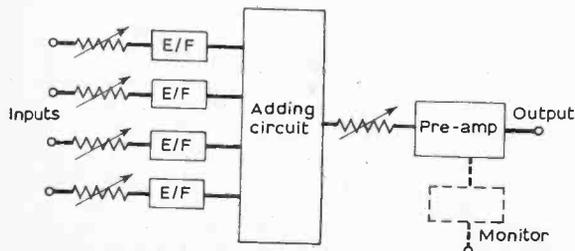


Fig. 1: Block diagram of an active mixer.

incorporate faders to control the level of each channel. The four sound channels are mixed by an adding circuit and the level of the composite signal is controlled by one master fader. The composite signal is then fed through a further stage of amplification to compensate for losses due to the adding circuits and attenuators.

The most difficult problem in designing audio circuits of this sort is the matching of input impedances and voltages. Fortunately, the matching of impedances is not too critical and values that are reasonably close will do, provided the voltage ratings match fairly well. The classes of impedances that are met with in practice are as follows:

- High (up to 2M Ω): crystal microphones, ceramic and crystal pick-ups.
- Medium (50k Ω): some magnetic and crystal microphones, tuner units, tape recorder outlets, magnetic pick-ups.
- Line (500 Ω): magnetic microphones.
- Low (3—30 Ω): magnetic microphones, loudspeakers.

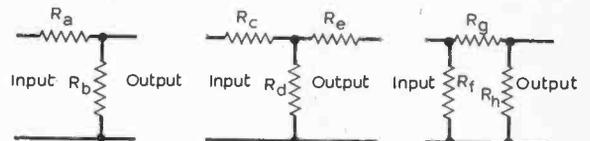


Fig. 2: Three types of resistive attenuator—L, T and π .

The easiest way of matching levels is to use attenuators. These can be purely resistive, the simplest of which are the L, T and π networks illustrated in Fig. 2. It is not proposed to discuss these circuits in detail as they can be found in standard textbooks, but suffice it to say that the L and T types of attenuator are used in this mixer.

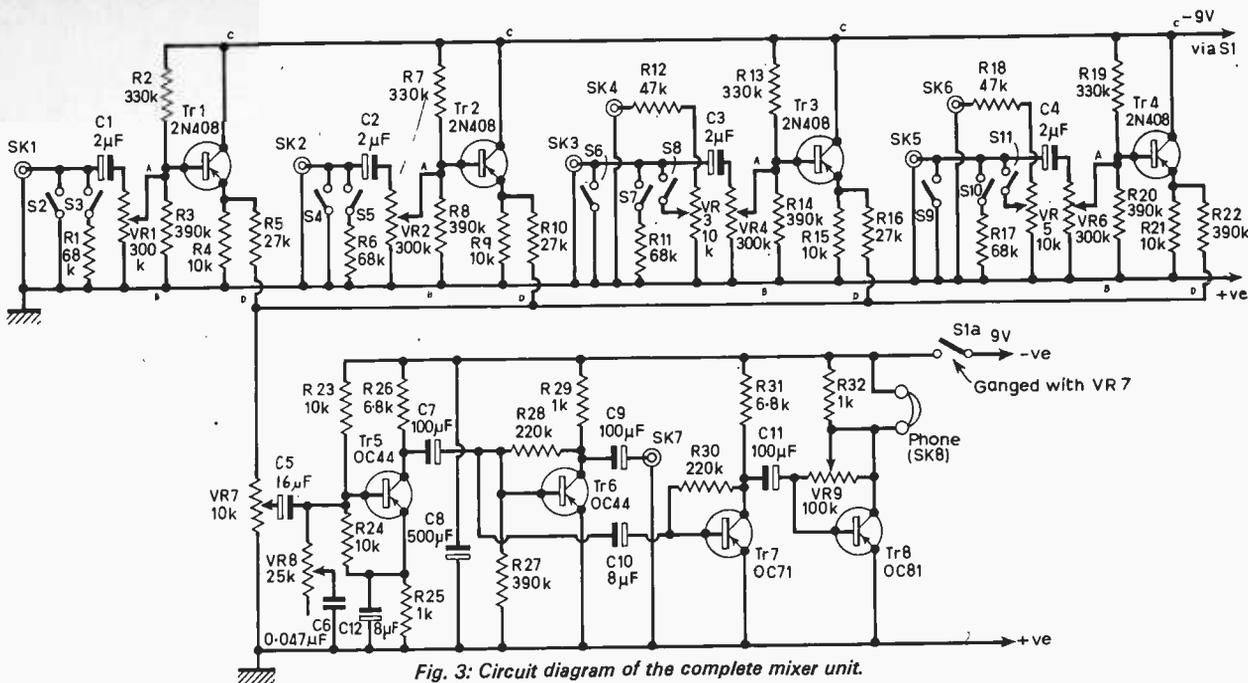


Fig. 3: Circuit diagram of the complete mixer unit.

Description and Specifications

The mixer is based on the idea outlined in Fig. 1; an additional facility has been incorporated (dotted lines) to enable the composite signal to be monitored using phones. The complete circuit of the unit is given in Fig. 3. A few points should be made regarding the input circuits—these are most prone to noise and for this reason only good quality components should be used for resistive attenuators. This also applies to the switches and electrolytic capacitors. The transistors used for the emitter follower stages are AC128 low noise a.f. types; these were found to be the most suitable low-priced transistors available.

The channels are mixed by a simple adding circuit and are given further amplification by Tr5 and Tr6, producing an output of up to 300mV at Sk7. The treble-cut control VR8 is perhaps a luxury item included primarily so that surface-noise on old records could be removed by cutting the upper frequencies. It will also be found useful when recording from a.m. radio.

The input sensitivities of the mixer are tabulated below:

Channels	Inputs	Sensitivity	Impedance
1, 2, 3, 4	Microphone	0.5mV	300kΩ
1, 2, 3, 4	Mic. or Mag. P.U.	5mV	50kΩ
3, 4	Crystal P.U.	100mV	50kΩ
3, 4	Radio, Tuner, etc.	200mV	100kΩ

Comparison of these impedances with the list of impedances given before shows that the mixer will accommodate a wide variety of inputs.

Plugs and Sockets

Before describing the actual construction of the mixer, it is worth while discussing plugs and sockets. Both professional bodies and amateurs are beginning to acknowledge the use of the German DIN system (Deutscher Industrie Normenausschus) for radio

and electronics. The commonly used plugs are the 3-pin, 5-pin, and loudspeaker 2-pin. The convention as agreed by DIN for wiring these is shown in Fig. 4,

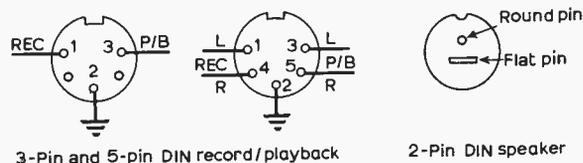


Fig. 4: Pin connections for 2, 3 and 5-pin DIN plugs.

and these should be followed although in particular cases it is advisable to check with the maker's instructions in case the pin order is non-DIN. The diagrams show the plugs as viewed from the free end or the sockets from the solder tags end. It should be noted that in each case, pin 2 is connected to earth. The 3-pin plug will fit the 5-pin socket and also the plugs are lugged so they are irreversible. The 5-pin sockets are used on the mixer so that inputs with 3-pin or 5-pin plugs may be used.

Construction

The complete mixer is housed in a compact wooden cabinet and to simplify construction this should be made first. The drilling of the various pieces is shown in Fig. 5. The base is made of ½ in. plywood and the side panels are of ¼ in. plywood. The side and front panels are fixed to the base with glue and screws, the other panels being fixed by suitable lengths of ¼ x ½ in. wooden strips; the top is made so that it can be screwed onto the side panels. The photograph shows how the cabinet looks when assembled. A sheet of Formica is glued to the top panel, which not only improves the appearance of the finished unit but also enables markings to be made in pencil which can easily be erased; this is useful for noting down volume levels etc.

In a design of this sort attention has to be paid

to screening so as to reduce noise, hum, and cross-talk. Screens made of 18 s.w.g. aluminium cover each of the emitter-follower stages, the details of which are also given in Fig. 5.

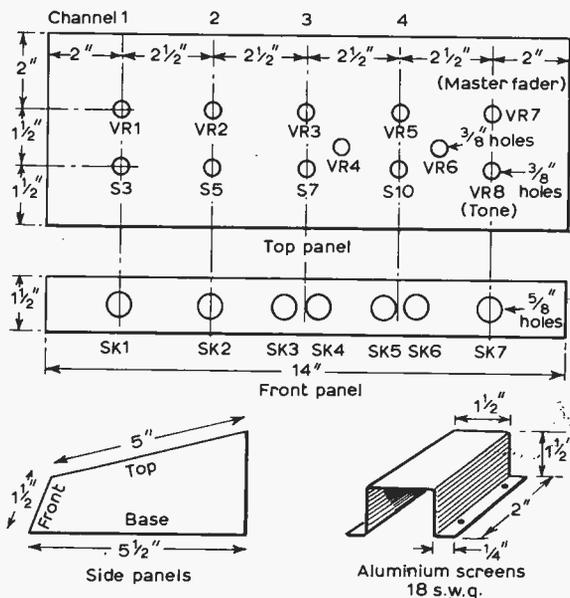


Fig. 5: Dimensions of cabinet, side panels and screens.

Most of the hardware is mounted on the top panel and so the switches and faders should be mounted first (see Fig. 7). The emitter-follower stages should be constructed next. These are most easily made on Veroboard, four of them being required and the wiring details are given in Fig. 6. It is perhaps a good idea to use different coloured wires for the connections A, B, C and D. Having made these stages, they can be secured to the top panel using screws and insulated washers. These are positioned as outlined in Fig. 7, when the main panel can then be wired up. Screened leads should be used to all of the sockets and to the input on the pre-amp. Fairly long leads should be used to connect

the sockets on the front panel to the top panel to enable the top panel to be easily removed should this become necessary. Once the top panel has been wired up the screens can be fitted over the emitter-follower circuits.

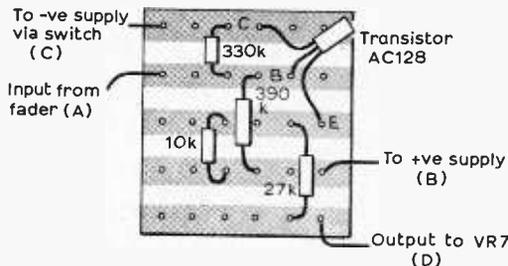


Fig. 6: Wiring of the emitter follower stages. Note the necessity for screened input and output leads.

The 5-pin sockets on the front panel are wired so that a 5-pin stereo source may be used and also to allow 3-pin plugs to be used. To do this, on each socket the tags 3 and 4 are connected together; tags 2 should be connected to the outer braid of the leads connecting to the top panel, and it is also advisable to connect the number 2 tags on each socket together and to take the positive battery supply to these tags. The output socket Sk7 is mounted on the rear of the cabinet.

The remainder of the circuit which consists of the pre-amplifier and the monitoring amplifier is assembled on a single piece of Veroboard which is then mounted on the base of the cabinet. The details of this board are given in Fig. 7 and the construction should present no problems.

The potentiometer VR9 can be mounted in a suitable position on the base of the cabinet; it is of the pre-set type and will vary the output to the phones. The output provided by this two-stage amplifier should be ample for most purposes.

When the amplifier has been made it can be screwed to the base of the cabinet and any remaining wiring completed.

Finally, the cabinet can be finished—the top

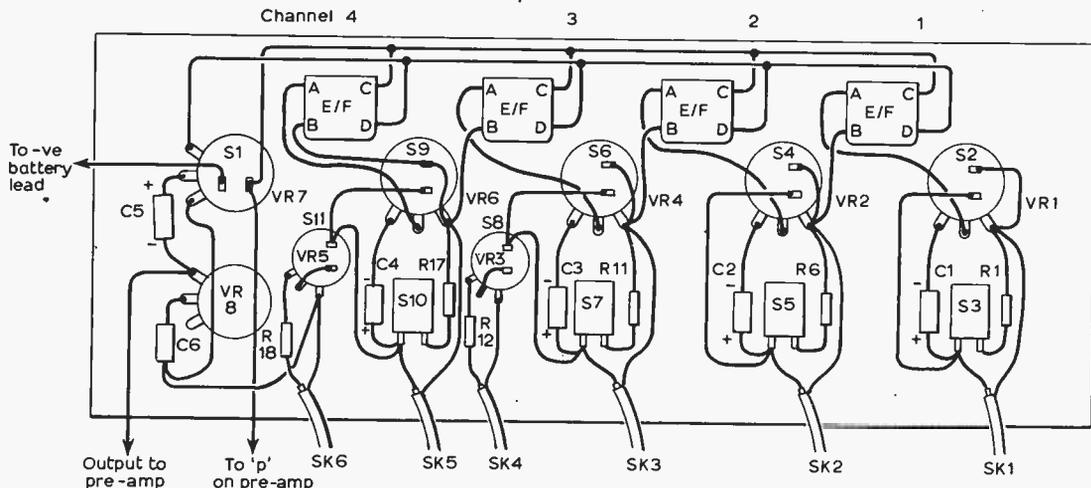


Fig. 7: Wiring of the main panel.

★ components list

Resistors:

R1	68kΩ	R17	68kΩ
R2	330kΩ	R18	47kΩ
R3	390kΩ	R19	330kΩ
R4	10kΩ	R20	390kΩ
R5	27kΩ	R21	10kΩ
R6	68kΩ	R22	27kΩ
R7	330kΩ	R23	10kΩ
R8	390kΩ	R24	10kΩ
R9	10kΩ	R25	1kΩ
R10	27kΩ	R26	6.8kΩ
R11	68kΩ	R27	390kΩ
R12	47kΩ	R28	220kΩ
R13	330kΩ	R29	1kΩ
R14	390kΩ	R30	220kΩ
R15	10kΩ	R31	6.8kΩ
R16	27kΩ	R32	1kΩ

All $\frac{1}{8}$ or $\frac{1}{4}$ W, 10%

Capacitors:

C1	} 2μF, 15V electrolytic
C2	
C3	
C4	
C5	16μF, 15V electrolytic

C6	0.047μF disc ceramic, 20V
C7	100μF, 15V electrolytic
C8	500μF, 15V electrolytic
C9	100μF, 15V electrolytic
C10	8μF, 15V electrolytic
C11	100μF, 15V electrolytic
C12	8μF, 15V electrolytic

Potentiometers:

VR1, VR2, VR4, VR6	300kΩ log., with switch
VR3, VR5, VR7	10kΩ lin., with switch
VR8	25kΩ log.
VR9	100kΩ lin.

Transistors:

TR1-4	AC128
TR5, TR6	OC44
TR7	OC71
TR8	OC81

Miscellaneous

Seven 5-pin DIN sockets; four s.p.s.t. toggle switches; Veroboard; 18s.w.g. aluminium; PP7 battery or equiv.; clips for battery; screened wire; plywood; Formica for cabinet; knobs etc.

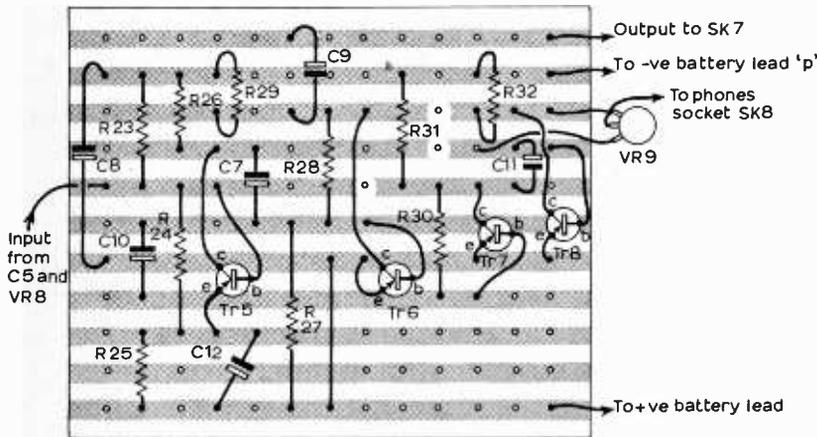


Fig. 8: Layout of the amplifier panel.

panel being fastened and the back panel screwed in place.

A 9V power supply is required and a PP7 power-pack will fit into the cabinet. Alternatively a simple power-supply can be made to run off the mains,

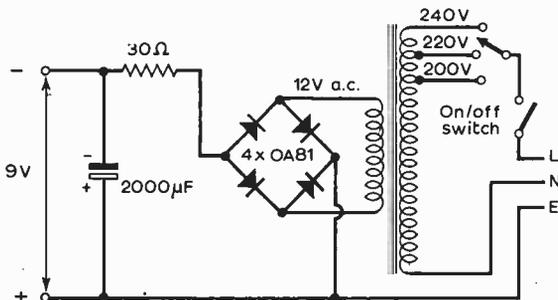


Fig. 9: A suitable power supply.

details being provided in Fig. 9. This should preferably be mounted in a separate case to prevent any mains hum being picked up by the circuits.


Testing

To test each of the channels a number of suitable sources are required. Plug a pair of head-phones into the phones socket and switch the mixer on by turning the master fader VR7 clockwise. Plug a microphone into socket Sk1, Sk2, Sk3 or Sk5 and turn on the appropriate channel.

For high impedance microphones (crystal) the appropriate toggle switch (S3, S5, S7 or S10) should be off and conversely on for lower impedances, the actual sensitivities having been previously given in the table. Adjust the faders to full volume then adjust the pre-set control VR9 so that a reasonable listening level is obtained without undue distortion. The attenuators VR4 and VR6 should be off when using microphones.

To use crystal pick-up, radio, tuner etc. channels 3 and 4 are used: plug a suitable source into Sk4 or Sk6 and turn on the attenuators VR4 and VR5; these can be adjusted to give a suitable volume level with the faders turned fully clockwise.

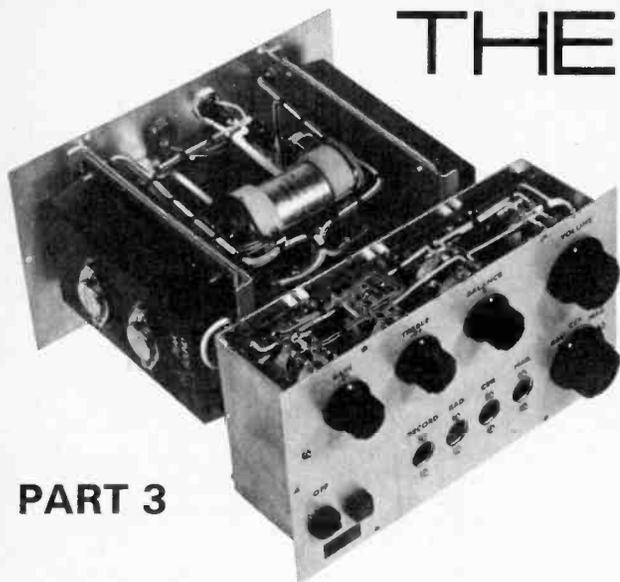Obviously the number of possible combinations of devices that can be used with this instrument is quite large and it would be pointless enumerating them all; the specifications given before will give the user a good idea of the range of applications for which this could be used. ■



THE P.W. DOUBLE-12 HI-FI AMPLIFIER

PART 3

HAL MOORSHEAD

IN THE PREVIOUS ARTICLES DETAILS WERE GIVEN ON THE CONSTRUCTION OF THE PREAMPLIFIER AND THE METALWORK FOR THE COMPLETE UNIT. THIS FINAL PART WILL DESCRIBE THE BUILDING OF THE MAIN AMPLIFIERS AND POWER SUPPLY AND A DESCRIPTION OF THE CABINET USED FOR THE PROTOTYPE.

As the P.W. Double-12 is a stereo unit obviously two main amplifiers are needed. As mentioned in the previous articles a wide range of ready built amplifiers are available at very small cost, in fact the cost of ready built units is so low that some readers may be suspicious of the claims made for them, but the author has tried several and found them excellent. For the reader who only requires a Hi-Fi amplifier and finds construction laborious ready built modules may be used. However, many constructors, like the author, prefer to build projects completely.

After considering several designs the one chosen finally was based on the Peak Sound P.A. 12-15 module, available either as a kit or as a ready built unit; this gives very high quality at a cost below buying the individual components. However a complete parts list and building details are given for anybody wishing to start from scratch.

The performance of the P.A. 12-15 easily exceeds the new European DIN standard for Hi-Fi amplifiers; specially selected high gain output transistors are used in closely matched pairs which, together with the high degree of negative feedback (43dB), contribute to the excellent performance figures which were given in some detail in the first part. In addition to having very good characteristics the module is easily built into a neat and compact unit.


The circuit

The theoretical circuit of one channel of the main amplifier is shown in Fig. 1. The circuit is a

fairly common configuration for Hi-Fi amplifiers and the method of working has been described before in PRACTICAL WIRELESS but for those unfamiliar with the basic operation a brief description will be given.

The signal from the preamplifier is fed to Tr1 (2N4289) which is arranged as a common emitter amplifier, the output is d.c. coupled to Tr2 which further amplifies the signal (again arranged as a common emitter amplifier) to drive the complementary pair of driver transistors Tr3 and Tr4. C5, which is connected from the collector to the base of Tr2, applies a.c. negative feedback and allows the top frequencies (above 50kc/s) to fall away. R10, TH1 and VR2 provide the correct base biasing for the complementary pair. The thermistor (TH1) alters the biasing to compensate for temperature changes.

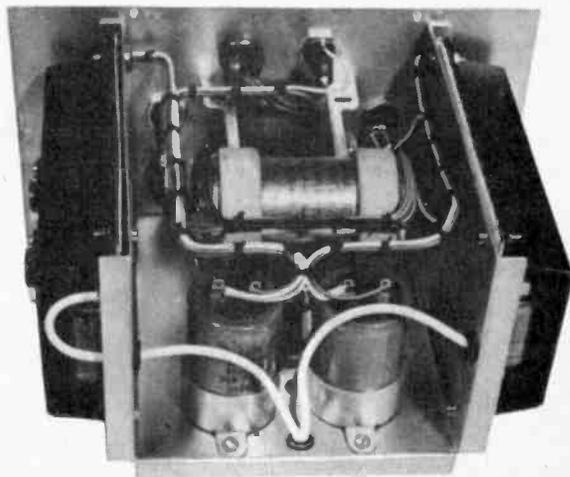The complementary pair act as phase splitters, each driving one of the power transistors Tr5 and Tr6 with half the signal, the two outputs appear together at the junction of R15 and the collector of



The chassis holding the power amplifiers on the side with the power supply and output capacitors in the centre.

Tr6. This combined signal is applied via C7, a 1,000 μ F capacitor to the loudspeaker.

Since the entire amplifier is directly coupled d.c. feedback is applied to stabilise the circuit from the output to the base of Tr1 via R2 and R11. Negative feedback is applied through C6 enhancing the performance and making the output more linear than it would be otherwise.

Construction

Like the preamplifier and tone control panels, the main amplifiers are built on a matrix board, 5 x 3 $\frac{1}{2}$ in., the interconnections being made using Cir-Kit self adhesive copper strip. First lay the strip following the layout in Fig. 2 observing the rules given in the first article. Insert the components and carefully solder. The output transistors are mounted on a heat-sink which covers the entire matrix board. It is necessary to insulate the bodies of these transistors (these are connected to the collector) from the heatsink using mica washers, first having spread both sides with a little silicon grease (provided in the kit) to ensure good heat conductivity.

The connections to the output transistors are taken by means of wires to the matrixed board; this is shown clearly in the photograph.


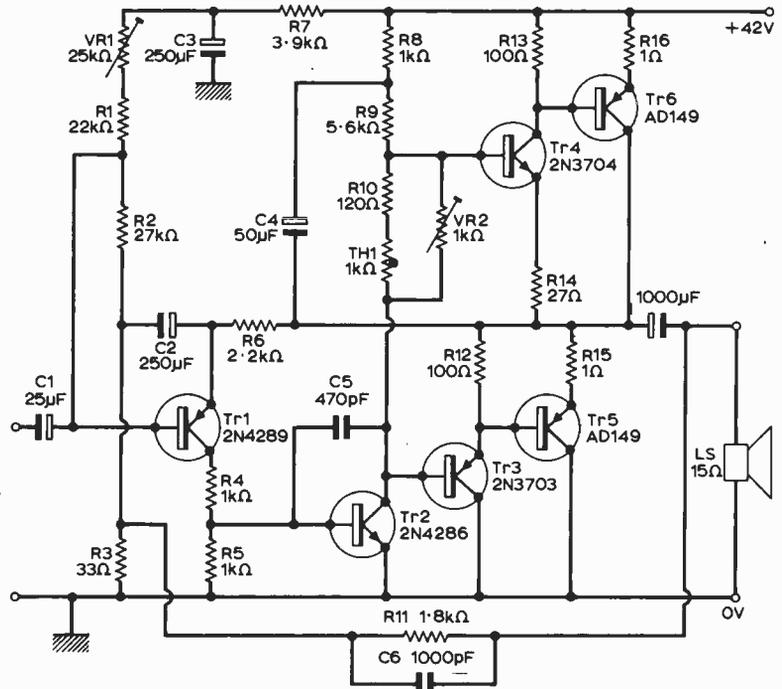


Fig. 1: The circuit of the power amplifier.

Fig. 2: The component layout of the power supply board. Like the preamp. panels they are mounted on matrix board and use Cir-Kit for interconnection.

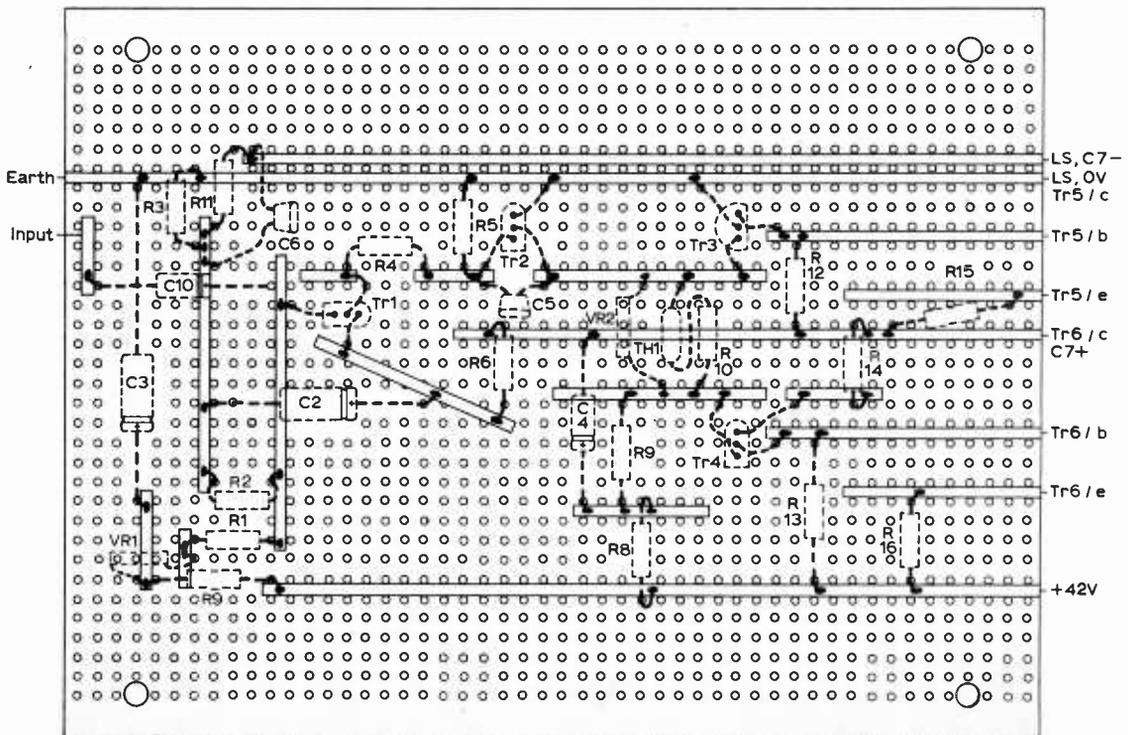

The power supply

The power supply shown in Fig. 3 is very simple and any mains transformer with a secondary of 33 volts at 2 amp. could be used. The bridge rectifier is composed of a single unit which is wired directly on to tags of the transformer. The mounting of the transformer, bridge rectifier and smoothing capacitor are clearly shown in the photographs of the unit; their layout is uncritical and self explanatory.

The 20V supply to the preamplifier section is taken from the output of the power supply (45V), the voltage being dropped by inserting a 5.6k Ω resistor in the supply line.

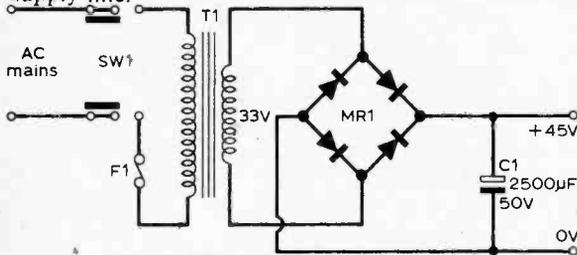


Fig. 3: The circuit of the power supply.

Interconnection

The outputs from the preamplifiers are wired directly to the power amplifier boards. The output from the amplifiers are taken to C7, the 1,000 μ F output capacitor and the other side of this is fed firstly back to the board providing negative feedback and secondly to the loudspeaker output socket through a fuse. It is important that a 1 amp. fuse is fitted into the loudspeaker circuit as shorting the output will damage the output transistors. The reader should refer to the metalwork (in the last issue) for the location of the fuse holders and the loudspeaker output sockets.

Setting up the power amplifiers

It will be noted that there are two preset potentiometers in the main amplifier circuits and it is important that these are correctly set. Before switching on set VR1 to the mid-position and VR2 to minimum resistance. Switch on and measure the voltage applied (this should be between 38 and 50V) to the amplifiers. Set VR1 so that the voltage between chassis and the amplifier side of C7 (1,000 μ F) is

★ components list

(POWER SUPPLY, MISCELLANEOUS AND EXTRA CIRCUITS)

Power Supply: Mains transformer, 250V primary 33V secondary, 2 amp; Silicon bridge rectifier (four BY100 rectifiers may be used if difficult to obtain); 1,000 μ F smoothing capacitor, 50V working; 1 amp. fuse holder.

Filter Networks: Top cut: 1k Ω , 15k Ω (both $\frac{1}{2}$ watt, 10%); 6,800pF; 2,200pF; double pole slider switch. Rumble filter: 0.47 μ F (or 1 μ F—see text); double pole slider switch.

Miscellaneous: Two 1 amp. fuses with fuse holders (for loudspeaker circuit), mains cable, wire etc.

half the applied voltage plus half a volt. Thus, if the applied voltage is 42V VR1 should be set to read 21.5V. VR2 should be set to provide an emitter current in Tr5 of 50mA in quiescent conditions, that is with no signal applied.

Additional features

MONO/STEREO SWITCH. Previously it was mentioned that a mono/stereo switch should not be necessary, but if one is required it is only necessary to fit a small slider switch to couple together the outputs from the preamplifier panels. There is plenty of room to fit the switch on to the front panel.

SCRATCH FILTER. Some constructors may want a scratch filter, especially when old records are played. The circuit shown in Fig. 4 provides a cut-off at 9kc/s at the rate of 8dB per octave and is switched in and out by means of a double pole slider switch (one section being used for each channel) which again may be fitted to the front panel.

RUMBLE FILTER. Although a cut-off at the lower frequencies is incorporated in the design, it is possible to fit a rumble filter giving a sharp cut-off at the lower frequencies. All that is necessary is to incorporate a slider switch which switches out C6 in the tone control panel and substitutes a 0.47 μ F capacitor in its place. This will begin to cut at 50c/s and cuts sharply below 30c/s. If a lower cut-off frequency is required a 1 μ F paper or polystyrene capacitor should be used, this will cut sharply below about 20c/s.


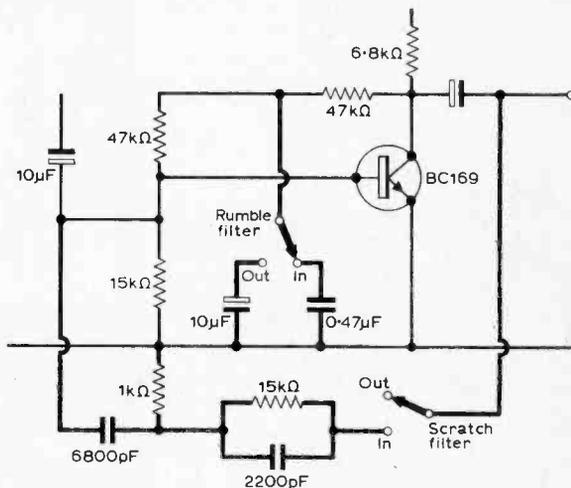


Fig.4: Additional circuitry for the scratch and rumble filters.

CORRIGENDA

In part one components list, the value of R4 in the preamplifier was given as 82k Ω : this should read 68k Ω as in the circuit diagram. Also all resistors in the preamp. and tone control circuits are $\frac{1}{2}$ watt, 10% miniature types. Alternatives to the BC169C were given and among these was the BC154; this is not suitable.

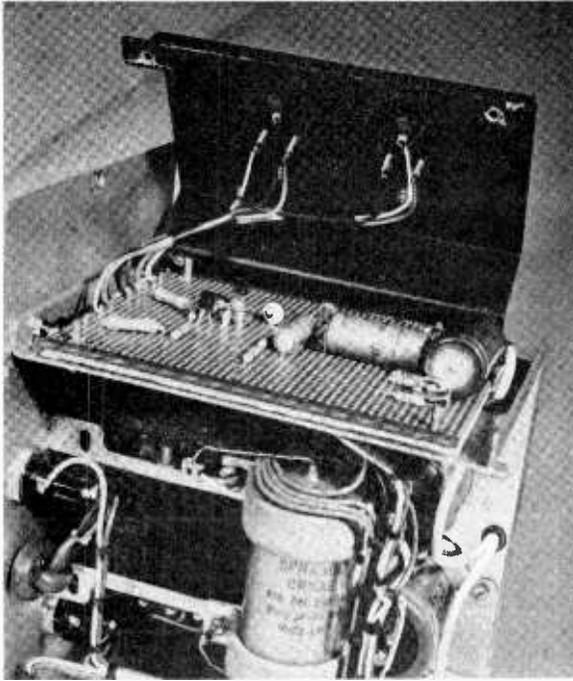In the second part the wiring of the input plugs was shown incorrectly. Numbering the pins 1-5 clockwise, on both the magnetic and ceramic inputs pins 1 and 2 should be joined together and pins 4 and 5 joined. In Part 2, Fig. 2, the spacing of the back panel from the bottom of the front panel is shown as $\frac{3}{8}$ in. This should read $1\frac{1}{2}$ in.



One of the power amplifiers with the heatsink raised.

★ components list

(MAIN AMPLIFIERS)

Resistors:

R1	22k Ω	R10	120 Ω
R2	27k Ω	R11	1.8k Ω
R3	33 Ω	R12	100 Ω
R4	1k Ω	R13	100 Ω
R5	1k Ω	R14	27 Ω
R6	2.2k Ω	R15	1 Ω 1 watt
R7	3.9k Ω	R16	1 Ω 1 watt
R8	1k Ω	VR1	25k Ω preset skeleton pot
R9	5.6k Ω	VR2	1k Ω preset skeleton pot

All resistors except R15 and R16 $\frac{1}{4}$ watt miniature, 10% tolerance.

Capacitors:

C1	25 μ F 25V	C5	470pF
C2	250 μ F 25V	C6	1,000pF
C3	250 μ F 50V	C7	1,000 μ F 50V
C4	50 μ F 25V		


Semiconductors:

Tr1	2N4289	Tr4	2N3704
Tr2	2N4286	Tr5 and Tr6	AD149
Tr3	2N3703		(All available from Peak Sound)

Miscellaneous:

Matrix board 5 x 3 $\frac{3}{4}$ in., Cir-Kit strip, TH1 (Thermistor) Siemens K151; Heatsink (Peak Sound), mica washers.

Fig. 5: A suggested design for the cabinet made from plywood.

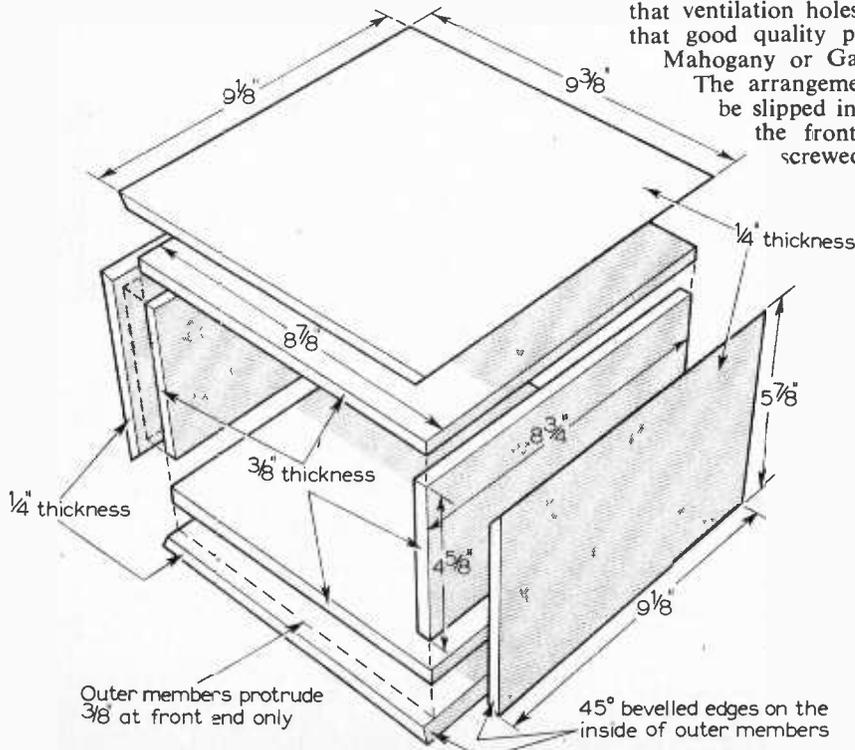

The cabinet

The cabinet for the Double-12 is extremely simple and can be made in an hour or two. The heat output from the unit, even at full output, is so small that ventilation holes are unnecessary. It is suggested that good quality plywood is used and if desired Mahogany or Gaboon-faced ply could be used.

The arrangement of the chassis enables it to be slipped into the cabinet, slightly recessing the front panel and allowing it to be screwed in. Details are shown in Fig. 5.

Conclusion

The P.W. Double-12, when completed, should be an excellent amplifier capable of faithfully reproducing the input. If used with good speakers, many of which are now available at reasonable prices, the builder will have an excellent Hi-Fi set-up at a very low cost. Any queries will be answered by the author if accompanied by a current query coupon and a stamped, self addressed envelope. ■

Due to pressure on space the second part of the PULSE CIRCUITS series has been held over till next month.

P.W. GUIDE TO COMPONENTS

PART 6

M. K. TITMAN, B.Sc. (Eng)

IN Part 5 last month basic transistor operation was outlined and the simple alloy-junction transistor described. This month we shall look at the more refined types of transistor giving improved performance.

Mesa Transistors

Drift transistors differ from alloy transistors in that the impurity concentration varies across the base region. This is achieved by *diffusing* the base region on to the main collector region and thus obtaining a greater concentration of impurity at the emitter, which is subsequently alloyed to the base region. The base thickness is carefully controlled and the varying concentration has the effect of a drift field which reduces the transit time of electrons or holes in the base region. The frequency response is considerably increased and operation up to 1,000Mc/s has been achieved.

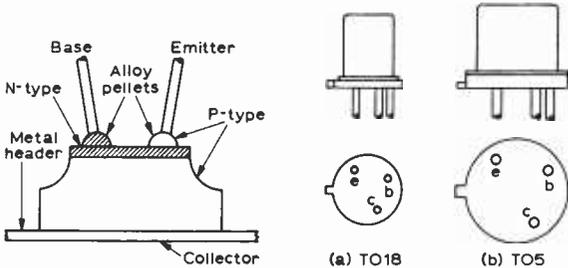


Fig. 1: Mesa transistor construction.

Fig. 2: Typical low-power transistor encapsulations.

Figure 1 shows a drift transistor construction which derives its name from its shape. This resembles a flat-topped mountain or mesa. In this construction a slice of p-type material is heated and placed in an atmosphere of n-type impurity such as aluminium until the aluminium has diffused into the slice to form an n-type base region. The base connection is made by alloying an n-type pellet whilst the emitter junction and connection is made by alloying a p-type pellet. The resulting p-n-p transistor is then bonded to a metal header which often forms part of the encapsulation to give good heat dissipation. The whole unit is hermetically sealed in a metal encapsulation of the familiar TO-5 or TO-18 style shown in Fig. 2 or for power transistors the TO-3 or TO-66 encapsulations shown in Fig. 3. Other encapsulations are used but these are almost regarded as the standard casings except for special purpose applications.

Mesa construction is used for both germanium and silicon transistors but as the diffusion of p-type impurities into n-type germanium is long and impractical germanium n-p-n transistors are not formed by diffusion techniques. Both p- and n-type diffusions are possible

with silicon and hence silicon transistors of either type are available. Also the double-diffused mesa construction shown in Fig. 4 is used extensively in order to control the emitter junction thickness and impurity level. And as the reverse leakage current is considerably lower and the maximum operating temperature considerably higher for silicon transistors they are rapidly superseding germanium transistors as general purpose devices.

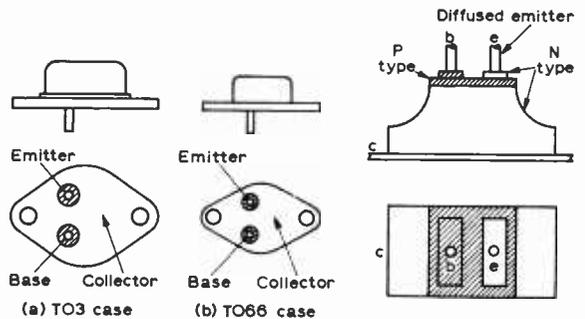


Fig. 3: Power transistor encapsulations.

Fig. 4: Double diffused silicon n-p-n transistor.

For power transistors the drift transistor construction brings difficulties due to secondary breakdown. This phenomenon is due to currents which flow in the transistor during switch-off. The current on rapid switch-off is localised at the circumference of the junction and in power devices the high currents cause the junction to break down. This effect is minimised if a drift field is not used and hence a homogeneous, rather than drift, epitaxial or surface layer is diffused. These homotaxial transistors using the mesa construction are used for power devices.


With the popularity of silicon mesa transistors a further step in construction was to produce transistors by diffusion techniques alone—using the production of silicon dioxide, which resists diffusion and is also a good insulator, to form the basis of a photographic and etching method of construction. This resulted in the planar epitaxial form of construction.

Planar Transistors

Planar transistors are formed by the epitaxial planar construction shown in Fig. 5. The name derives from planar, meaning in planes; and epitaxial, for surface. The technique starts with n-type material which forms the collector region. A silicon dioxide layer is then formed by passing superheated steam over the slice which ultimately will produce several hundred transistors. The silicon dioxide is selectively etched away and the base

SOLDER ON WITH

A N T E X

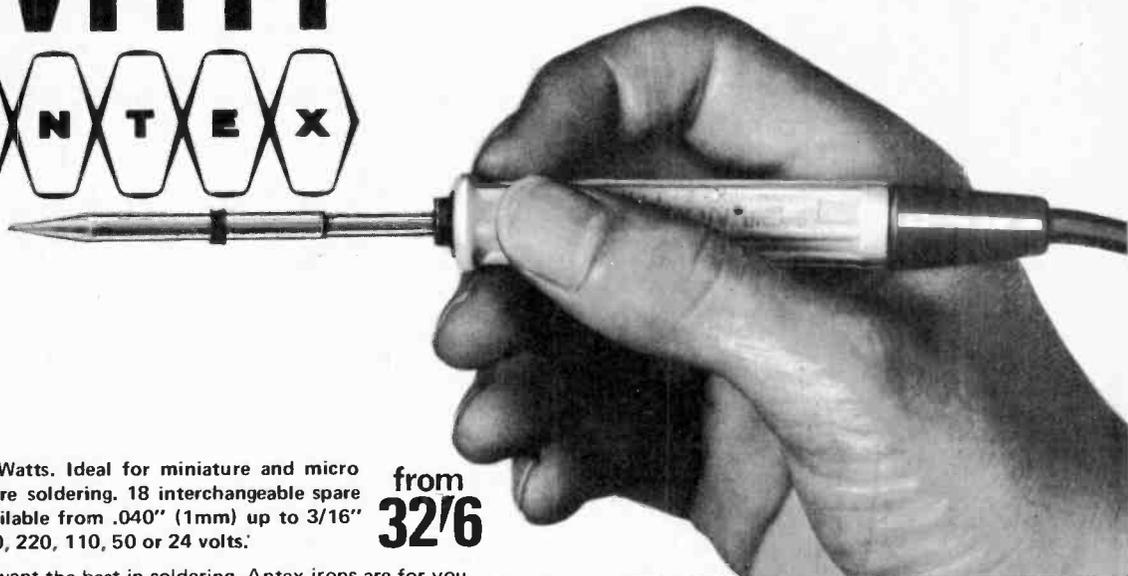

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. **from 32/6**

If you want the best in soldering, Antex irons are for you. Pin point precision, fingertip control, interchangeable bits that slide over the elements and do not stick, sharp heat at the tip, reliable elements and full availability of spares. World-wide users, both enthusiasts and professionals solder with Antex. It's time you joined them.

Antex soldering irons are stocked by quality electrical dealers, or order direct from Antex by sending Cash. A free colour catalogue will be supplied on request.

A N T E X

PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon
Telephone: Plymouth 67377/8. Telex 45296. Giro No.258 1000



Model CN 240/2
15 watts - 240 volts

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

31/-

Complete precision soldering kit



This kit—in a rigid plastic "tool-box"—contains everything you need for precision soldering.

- Model CN 15 watts miniature iron, fitted 3/32" bit.
- Interchangeable spare bits 3/32", 1/8", 3/16".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron
- Space for stowage of lead and plug

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

From Electrical and Radio Shops or send cash to Antex. **49/6**



G 18 watts. Ideal for miniature work on production lines. Interchangeable spare bits, 3/32", 1/8", 3/16", and 1/4". For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16". For 240, 220, 110 or 24 volts. from 35/-



ES 26 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4". Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. from 35/-



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" Very high temperature iron. Available for 240, 220, 110, 24 or 30 volts. from 42/6 Spare bits and elements for all models and voltages immediately available from stock.

- Please send me the Antex colour catalogue
 Please send me the following irons

Quantity	Model	Bit Size	Volts	Price
.....
.....
.....

To: Antex, Mayflower House, Plymouth, Devon

I enclose cheque/P.O./cash value
NAME
ADDRESS
P.W.6..... Telephone:

Fully guaranteed Individually packed VALVES

PERSONAL CALLERS WELCOME

Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders up to 10/-, 1/-; 10/- to £1, 2/-; over £1, 2/- per £1; over £3 post free. G.O.D. 4/- extra



ALL valves
guaranteed

A2134 8/-	ECF82 6/6	KT86 18/8	BG1-240A	UU5 7/6	X86 7/6	184 5/6	5A174G 5/6	6AC7 3/6	6CW4 18/6	77 6/6
AR23 5/6	ECR35 11/6	KT87 15/8	UP21 10/6	UY21 10/6	X76M 7/6	185 4/6	5B251M40/6	6AG5 2/6	6D6 3/6	78 5/6
ARP12 3/6	ECR81 5/6	KT76 2/6	SP1 28/6	UY41 7/6	X118 3/6	174 3/6	5B252M85/6	6AG7 6/6	6E5 8/6	80 5/6
ARTP1 6/6	ECR83 8/6	KT78 2/6	STV280/16	UY85 5/6	X145 3/6	223 3/6	5B254M40/6	6AH6 11/6	6EA8 9/6	81 9/6
ATF4 2/8	ECL80 7/6	KT263 7/6	V246A/1K	Y63 6/6	Y83 6/6	2D21 4/6	6B/255M	6A7 3/6	6E7 7/6	82 14/6
AZ1 9/6	ECL82 6/6	L63 6/6	190/-	Y65 4/6	3A4 4/6	35/-	6AK5 5/6	6F23 13/6	6F23 13/6	84 5/6
BD78 40/-	ECL83 10/6	MH4 5/6	VL8631 35/-	Z800 20/-	5B4WGA	5R4GY 9/6	6AK6 12/6	6FG2 7/6	6AX7 6/6	85A2 7/6
BL63 10/6	ECL86 8/6	MH1 8/6	VP23 3/6	Z801U 25/-	27/6	5T4 7/6	6AK7 6/6	6FG6 4/6	6AX7A 7/6	282A 85
BT35 15/-	ECL88 10/6	MH126 7/6	VP33 9/6	Z802U 18/-	3B7 5/6	5U4G 4/6	6AK8 6/6	6F7 6/6	10A7 7/6	307A 5/6
BT45 150/-	EF35 8/6	ML6 6/6	TR31 45/-	VR90 7/6	1232 30/-	3B24 14/6	6AL5 3/6	6FG8 5/6	12A7Y 10/6	313C 25/-
BT83 35/6	EF39 6/6	N34 8/6	TDO4-20	VR105/30	105GT 6/6	4D4 4/6	6AL5W 7/6	6FG12 4/6	12B26 6/6	337A 70/-
CV102 3/6	EF40 9/6	N78 15/6	TP22 5/6	VR150/30	1D8GT 6/6	3E29 50/-	6AM5 2/6	6FG15 5/6	12B27 3/6	368AS 30/-
CV103 4/6	EF41 9/6	OA2 6/6	TT11 3/6	VU89	1G6T 6/6	3Q4 8/6	6AM6 3/6	6FG17 5/6	12B28 3/6	393A 27/6
CV315 (masched)	EF42 13/6	OB2 6/6	TT15 55/-	W118 7/6	LLA 2/6	384 5/6	6AN5 20/6	6FG19 5/6	12C8 3/6	446 8/6
(pair) 120/-	EF60 4/6	OC3 6/6	W18 8/6	W18 8/6	LLC 7/6	3V4 6/6	6AN8 10/6	6GG6 9/6	12E1 17/6	703A 30/-
CV315 (Single) 50/-	EF85 6/6	OD3 6/6	TZ0502 4/-	W119 9/6	LLH4 4/6	5Z4G 7/6	6AG5W 9/6	6H8GT 1/6	12G7G 6/6	705A 20/-
CT31 7/6	EF86 6/6	OZ4A 5/6	TZ20 16/-	X65 5/6	LR5 6/6	5A173G 5/6	6A8 6/6	6H8 3/6	12K7GT 6/6	717A 9/6
D41 3/6	EF89 5/6	P41 7/6						6J4WA 12/6	12K8M 8/6	803 30/-
D77 3/6	EF91 3/6	PABC80 7/6						6J5 7/6	12Q7GT 5/6	807 9/6
DAL10 4/6	EF92 3/6	PC86 10/6	OA5 3/6	OC28 12/6	OC172 7/6	AD149 16/6	CR81/10 5/6	6J6GT 5/6	12R07 7/6	808 8/6
DAL90 7/6	EF95 5/6	PC90 9/6	OA7 4/6	OC29 15/6	OC20 7/6	AEY11 15/6	CR81/20 9/6	JK11A 12/6	12R27 3/6	813 75/6
DD41 4/6	EF183 6/6	PC97 9/6	OA10 3/6	OC35 10/6	OC201 10/6	AEY12 18/6	CR81/30/10/6	JK19A 22/6	12R37 3/6	816 35/6
DET20 2/6	EF184 7/6	PC98 9/6	OA27 2/6	OC38 12/6	OC202 12/6	AF114 6/6	CR81/35	JK21A 12/6	12R47 3/6	829B 5/6
DET25 10/6	EF187 7/6	PC99 9/6	OA70 2/6	OC39 5/6	OC203 12/6	AF115 6/6	CR81/40	JK50A 12/6	12R57 3/6	832A 45/6
DF91 3/6	EL31 15/6	PC189 10/6	OA71 2/6	OC41 6/6	OC204 17/6	AF116 6/6	CR81/45	JK50B 12/6	12S17GT/7/6	843 5/6
DF92 8/6	EL32 3/6	PCF80 6/6	OA72 2/6	OC42 5/6	OC206 17/6	AF117 5/6	MAT100 7/6	JK50C 12/6	12S27GT/7/6	866A 15/6
DF96 7/6	EL34 10/6	PCF84 9/6	OA73 2/6	OC44 4/6	OC207 17/6	AF118 10/6	MAT101 9/6	MPF102/11/6	12S37GT/7/6	866B 10/6
DK92 9/6	EL35 6/6	PCF86 9/6	OA79 2/6	OC45 3/6	OC208 17/6	AF124 7/6	CR83/20 6/6	MPF103/9/6	12S47GT/7/6	866C 10/6
DK96 8/6	EL38 24/6	PCF89 9/6	OA81 2/6	OC47 3/6	OC209 17/6	AF125 6/6	CR83/30	MPF104/10/6	12S57GT/7/6	866D 10/6
DL63 8/6	EL42 11/6	PCF80 9/6	OA90 2/6	OC48 3/6	OC210 17/6	AF126 6/6	CR83/35	MPF105/10/6	12S67GT/7/6	866E 10/6
DL92 4/6	EL50 9/6	PCF80 9/6	OA200 2/6	OC72 5/6	OC211 17/6	AF127 6/6	CR83/40	MPF106/10/6	12S77GT/7/6	866F 10/6
DL93 4/6	EL51 9/6	PCF80 9/6	OA202 2/6	OC73 6/6	OC212 17/6	AF128 6/6	CR83/45	MPF107/10/6	12S87GT/7/6	866G 10/6
DL94 6/6	EL51 9/6	PCF80 9/6	OA203 2/6	OC74 6/6	OC213 17/6	AF129 6/6	CR83/50	MPF108/10/6	12S97GT/7/6	866H 10/6
DL96 8/6	EL54 4/6	PCL81 9/6	OA204 2/6	OC75 6/6	OC214 17/6	AF130 10/6	CR83/55	MPF109/10/6	12T07GT/7/6	866I 10/6
DL110 12/-	EL55 5/6	PCL82 7/6	OA205 2/6	OC76 5/6	OC215 17/6	AF131 10/6	CR83/60	MPF110/10/6	12T17GT/7/6	866J 10/6
DY86 6/6	EL56 5/6	PCL83 10/6	OA206 2/6	OC77 6/6	OC216 17/6	AF132 10/6	CR83/65	MPF111/10/6	12T27GT/7/6	866K 10/6
DY87 6/6	EL59 20/6	PCL84 10/6	OA207 2/6	OC78 5/6	OC217 17/6	AF133 10/6	CR83/70	MPF112/10/6	12T37GT/7/6	866L 10/6
E90F 18/6	EM1 5/6	PCF86 9/6	OA208 2/6	OC79 6/6	OC218 17/6	AF134 10/6	CR83/75	MPF113/10/6	12T47GT/7/6	866M 10/6
E90C 8/6	EM8 7/6	PCL86 8/6	OA209 2/6	OC80 5/6	OC219 17/6	AF135 10/6	CR83/80	MPF114/10/6	12T57GT/7/6	866N 10/6
E91H 7/6	EM8 7/6	PCL86 8/6	OA210 2/6	OC81 5/6	OC220 17/6	AF136 10/6	CR83/85	MPF115/10/6	12T67GT/7/6	866O 10/6
E92CC 5/6	EM11 11/6	PL36 10/6	OA211 2/6	OC82 5/6	OC221 17/6	AF137 10/6	CR83/90	MPF116/10/6	12T77GT/7/6	866P 10/6
E180CC 7/6	ESU74 7/6	PL81 10/6	OA212 2/6	OC83 5/6	OC222 17/6	AF138 10/6	CR83/95	MPF117/10/6	12T87GT/7/6	866Q 10/6
E182CC 18/6	EV51 8/6	PL82 8/6	OA213 2/6	OC84 5/6	OC223 17/6	AF139 10/6	CR83/100	MPF118/10/6	12T97GT/7/6	866R 10/6
EL148 2/6	EY86 8/6	PL83 8/6	OA214 2/6	OC85 5/6	OC224 17/6	AF140 10/6	CR83/105	MPF119/10/6	12T07GT/7/6	866S 10/6
E476 7/6	EY88 8/6	PL84 8/6	OA215 2/6	OC86 5/6	OC225 17/6	AF141 10/6	CR83/110	MPF120/10/6	12T17GT/7/6	866T 10/6
EACB80 6/6	EY91 2/6	PL85 10/6	OA216 2/6	OC87 5/6	OC226 17/6	AF142 10/6	CR83/115	MPF121/10/6	12T27GT/7/6	866U 10/6
EAC91 3/6	EZ40 7/6	PX4 14/6	OA217 2/6	OC88 5/6	OC227 17/6	AF143 10/6	CR83/120	MPF122/10/6	12T37GT/7/6	866V 10/6
EAF42 9/6	EZ41 7/6	PX35 18/6	OA218 2/6	OC89 5/6	OC228 17/6	AF144 10/6	CR83/125	MPF123/10/6	12T47GT/7/6	866W 10/6
EB91 2/6	EZ80 5/6	PY33 9/6	OA219 2/6	OC90 5/6	OC229 17/6	AF145 10/6	CR83/130	MPF124/10/6	12T57GT/7/6	866X 10/6
ECB33 8/6	EZ81 5/6	PY81 5/6	OA220 2/6	OC91 5/6	OC230 17/6	AF146 10/6	CR83/135	MPF125/10/6	12T67GT/7/6	866Y 10/6
ECB34 8/6	FW500	PY82 5/6	OA221 2/6	OC92 5/6	OC231 17/6	AF147 10/6	CR83/140	MPF126/10/6	12T77GT/7/6	866Z 10/6
ECB35 8/6	FW500	PY83 6/6	OA222 2/6	OC93 5/6	OC232 17/6	AF148 10/6	CR83/145	MPF127/10/6	12T87GT/7/6	866AA 10/6
ECB36 8/6	FW500	PY84 6/6	OA223 2/6	OC94 5/6	OC233 17/6	AF149 10/6	CR83/150	MPF128/10/6	12T97GT/7/6	866AB 10/6
ECB37 8/6	FW4/800	PY85 6/6	OA224 2/6	OC95 5/6	OC234 17/6	AF150 10/6	CR83/155	MPF129/10/6	12T07GT/7/6	866AC 10/6
ECB38 8/6	FW4/800	PY86 6/6	OA225 2/6	OC96 5/6	OC235 17/6	AF151 10/6	CR83/160	MPF130/10/6	12T17GT/7/6	866AD 10/6
ECB39 8/6	FW4/800	PY87 6/6	OA226 2/6	OC97 5/6	OC236 17/6	AF152 10/6	CR83/165	MPF131/10/6	12T27GT/7/6	866AE 10/6
ECB40 8/6	FW4/800	PY88 6/6	OA227 2/6	OC98 5/6	OC237 17/6	AF153 10/6	CR83/170	MPF132/10/6	12T37GT/7/6	866AF 10/6
ECB41 8/6	FW4/800	PY89 6/6	OA228 2/6	OC99 5/6	OC238 17/6	AF154 10/6	CR83/175	MPF133/10/6	12T47GT/7/6	866AG 10/6
ECB42 8/6	FW4/800	PY90 6/6	OA229 2/6	OC100 5/6	OC239 17/6	AF155 10/6	CR83/180	MPF134/10/6	12T57GT/7/6	866AH 10/6
ECB43 8/6	FW4/800	PY91 6/6	OA230 2/6	OC101 5/6	OC240 17/6	AF156 10/6	CR83/185	MPF135/10/6	12T67GT/7/6	866AJ 10/6
ECB44 8/6	FW4/800	PY92 6/6	OA231 2/6	OC102 5/6	OC241 17/6	AF157 10/6	CR83/190	MPF136/10/6	12T77GT/7/6	866AK 10/6
ECB45 8/6	FW4/800	PY93 6/6	OA232 2/6	OC103 5/6	OC242 17/6	AF158 10/6	CR83/195	MPF137/10/6	12T87GT/7/6	866AL 10/6
ECB46 8/6	FW4/800	PY94 6/6	OA233 2/6	OC104 5/6	OC243 17/6	AF159 10/6	CR83/200	MPF138/10/6	12T97GT/7/6	866AM 10/6
ECB47 8/6	FW4/800	PY95 6/6	OA234 2/6	OC105 5/6	OC244 17/6	AF160 10/6	CR83/205	MPF139/10/6	12T07GT/7/6	866AN 10/6
ECB48 8/6	FW4/800	PY96 6/6	OA235 2/6	OC106 5/6	OC245 17/6	AF161 10/6	CR83/210	MPF140/10/6	12T17GT/7/6	866AO 10/6
ECB49 8/6	FW4/800	PY97 6/6	OA236 2/6	OC107 5/6	OC246 17/6	AF162 10/6	CR83/215	MPF141/10/6	12T27GT/7/6	866AP 10/6
ECB50 8/6	FW4/800	PY98 6/6	OA237 2/6	OC108 5/6	OC247 17/6	AF163 10/6	CR83/220	MPF142/10/6	12T37GT/7/6	866AQ 10/6
ECB51 8/6	FW4/800	PY99 6/6	OA238 2/6	OC109 5/6	OC248 17/6	AF164 10/6	CR83/225	MPF143/10/6	12T47GT/7/6	866AR 10/6
ECB52 8/6	FW4/800	PY100 6/6	OA239 2/6	OC110 5/6	OC249 17/6	AF165 10/6	CR83/230	MPF144/10/6	12T57GT/7/6	866AS 10/6
ECB53 8/6	FW4/800	PY101 6/6	OA240 2/6	OC111 5/6	OC250 17/6	AF166 10/6	CR83/235	MPF145/10/6	12T67GT/7/6	866AT 10/6
ECB54 8/6	FW4/800	PY102 6/6	OA241 2/6	OC112 5/6	OC251 17/6	AF167 10/6	CR83/240	MPF146/10/6	12T77GT/7/6	866AU 10/6
ECB55 8/6	FW4/800	PY103 6/6	OA242 2/6	OC113 5/6	OC252 17/6	AF168 10/6	CR83/245	MPF147/10/6	12T87GT/7/6	866AV 10/6
ECB56 8/6	FW4/800	PY104 6/6	OA243 2/6	OC114 5/6	OC253 17/6	AF169 10/6	CR83/250	MPF148/10/6	12T97GT/7/6	866AW 10/6
ECB57 8/6	FW4/800	PY105 6/6	OA244 2/6	OC115 5/6	OC254 17/6	AF170 10/6	CR83/255	MPF149/10/6	12T07GT/7/6	866AX 10/6
ECB58 8/6	FW4/800	PY106 6/6	OA245 2/6	OC116 5/6	OC255 17/6	AF171 10/6	CR83/260	MPF150/10/6	12T17GT/7/6	866AY 10/6
ECB59 8/6	FW4/800	PY								

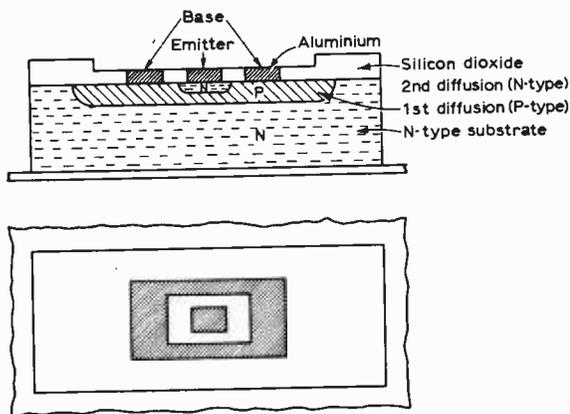


Fig. 5: Epitaxial planar transistor construction.

region formed by using a p-type impurity which diffuses where the silicon dioxide was removed. The slice is then re-oxidised to renew the dioxide layer and the emitter region etched away, an n-type diffusion then forming the emitter region. The slice is next diced into the separate transistor chips and the chips bonded to a metal header to which the lead-out wires are connected. The connections are joined to the lead-out wires by fine wires ultrasonic or heat bonded to the separate regions on the chip.

The whole device is encapsulated in a metal case of the TO-5 or power TO-3 type. Alternatively the chip is encapsulated in the new plastic encapsulations some of which are shown in Fig. 6. These plastic encapsulations are of very recent origin and have considerably lowered the price of industrial and commercial transistors but are at present not acceptable for military ratings.

The advantage of the planar construction is reliable control of physical parameters and hence better yields of the desired types of transistor. They have good high frequency characteristics, and by using a technique of producing multi-emitter regions to reduce the effects of

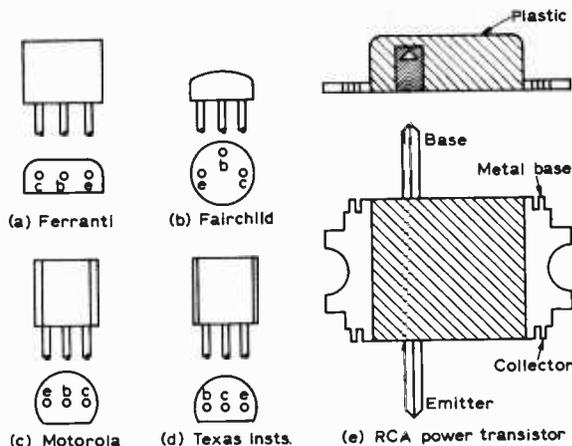


Fig. 6: Common epoxy resin encapsulations.

secondary breakdown high power operation can be obtained.

The construction shown in Fig. 5 is a low frequency device: for higher frequencies a more complex geometry is used.

Designation

With all transistors the device number is printed on the case. Initially, numbering was individual to each manufacturer as was the order and spacing of the lead-out wires. Now however some standardisation of casing in the TO-3, TO-5 etc. style has been achieved and lead-out wire connections are as shown in Figs. 2 and 4. Plastic cases have yet to be standardised.

Designations have standardised around the JEDEC system in the USA., such as the 2N1132 or 2N series, and in Europe the standard ACY, BFY etc. series. It is hoped that the European standard will prevail since the 2N series carries no meaning in the number whilst the European standard contains worthwhile information in the first two letters. The first letter indicates the material used in the construction and the second the general device type. The convention is detailed in Table 1.

Table 1: Standard Semiconductor Designations

First Letter	
A	Germanium
B	Silicon
C	Group III-V material
R	Photoconductive cells and Hall effect devices or materials
Second Letter	
A	Diode
C	A.F. transistor
D	Power transistor, a.f.
E	Tunnel diode
F	H.F. transistor
H	Field probe
K	Hall generator
L	H.F. power transistor
M	Hall generator (modulator or multiplier)
P	Control and switching device, low power
S	Switching transistor
T	Power control and switching device
U	Switching power transistor
Z	Zener diode

Parameters and Cost

Thousands of different types of transistor are produced and this profusion is bewildering to say the least. If however we examine the main circuit parameters we find that in all but the most specialised applications a great many are interchangeable. The fundamental parameters to be considered in connection with interchangeability are: (1) construction and material (n-p-n, p-n-p—Si, Ge); (2) maximum voltage ($V_{CE0 \text{ max}}$); (3) maximum current ($I_C \text{ max}$); (4) power rating (P_T); (5) frequency response (f_T); (6) current gain (h_{FE} , h_{ie} , α').

The construction and material are important since n-p-n and p-n-p transistors are not interchangeable unless all the transistors are reversed—together with polarised components and the supply voltage. Although silicon transistors can be used in place of germanium ones, often the bias supplies require alteration as the base emitter volt drop is 0.2-0.3V for germanium and 0.6-0.7V for silicon.

Provided the maximum voltage and current are not exceeded any transistor may be used and the frequency characteristics should match. Power rating is important and in general for the same case size silicon transistors can replace germanium types. Providing these require-

ments are met current gain matching can be determined by simple substitution.

In specialist applications, such as switching, the saturation volt drop $V_{CE\text{ sat}}$ is important but again substitution is usually a sufficient test.

Many transistors are interchangeable and the experimenter should never be deterred from trial and error as a means of determining whether an available type can be used.

Why there are so many different types is a question which is highly relevant. This is due to the large number of manufacturers and the yield of several types from each basic production unit. From this it can be seen that the cost of a transistor depends largely on the production yield, parameters and market requirement for a given type. Specialist devices are expensive but general purpose widely used transistors are cheap. Transistors with specialist parameters are often expensive simply because the demand is small. Therefore only popular devices should be used in circuit design.

General purpose low frequency transistors are available at 2s. 6d. to 5s. but £5 can be the price of similar devices. Power transistors range from 7s. to £2 for low frequency types but from £5 to £37 for high frequency working. Low power high frequency types are available at from 10s. to £10 for 1,000Mc/s. High voltage devices at low power are available from 4s. 6d. to £3. For silicon transistors generally n-p-n types are cheaper than p-n-p and plastic encapsulated devices are often half the price of their metal-cased counterparts.

The Future

As techniques improve and demand increases transistor prices will fall. Plastic encapsulation will find widespread application whilst the demand for germanium devices, except in specialist applications, will fall.

It is entirely probable that improved manufacture of f.e.t.s will considerably affect transistor usage whilst further inventions are likely to render obsolete the construction and application of transistors as we know them today.

TO BE CONTINUED

PRACTICAL TELEVISION

IN THE JUNE ISSUE

INTEGRATED CIRCUIT TV HEARING AID

A easy-to-assemble hearing aid which is completely independent of the TV set. Uses a high-impedance f.e.t. i.c. input stage.

A.G.C. FAULTS

A thorough survey of contrast and gain faults with rapid fault location guide.

EARLY TV CAMERA TUBES

An account of the development of the first broadcast-quality TV camera tubes.

VIDEO CIRCUIT TESTING

How to trace faults in the video amplifier, detector, interference limiter and tube biasing circuits.

ON SALE MAY 23

THE MW COLUMN

ALTHOUGH when we are talking about MW DX we are generally referring to signals from North or South America, Africa or Asia, there are some interesting and rare catches to be had within continental Europe. There are 34 distinct countries in Europe with MW broadcasting stations (two countries, San Marino and Liechtenstein have none) and of course many of these are easily heard even during daylight. During the evening the band is crammed with over a thousand stations and to pick out the unusual ones takes perhaps even more skill and patience than waiting until conditions are favourable for transatlantic signals.

Listen out for the Azores, Portuguese islands in the Atlantic with four stations, CSA97(836); CSB81 (1570); CSB80(1394) and the US Forces Station (1500). The Faroes, Danish islands north of the Shetlands, can sometimes be heard before close down at 2000 hrs. on 548. Iceland can be heard fairly easily over its LW stations but for the purist there are several MW stations, most of these are of flea-power but the stations on 665 and 737 are occasionally heard.

Gibraltar has been heard, but very rarely, on 1484, the International Common Frequency, broadcasting in English and Spanish. Although *Manx Radio* using only 50W is heard fairly well in Lancashire and North Wales on good equipment it can be heard during daylight throughout the country on 1295 when the BBC European Service on the same frequency is not on the air.

The only other countries that could possibly be classed as DX areas are Greece, Malta and Turkey. Greece broadcasting on 665, 728, 791 and 1007. There are several other low-powered stations but these are rarely heard. The *VOA* station on Rhodes can easily be heard on 1259 in a variety of languages. Turkey has two stations in Europe, a high power one on 701 and a 2kW one on 963. Malta can be heard occasionally through the BBC Relay on 1178 in Arabic but there are two other stations, *BFBS* on 1425 and *Radio Malta* on 1214; due to BBC *Radio 1* using 1214 *Radio Malta* would indeed be a prize catch.

Searching for these Europeans should be ideal for the enthusiast who doesn't fancy the idea of waiting till after midnight before even starting.

Radio Andorra on 701 is reported to be testing with English programmes after midnight and if this ever gets off the ground they may try to become a second *Radio Luxembourg*. Several of the European stations have English programmes in the late evening as a limited sort of overseas service, and all these will readily confirm and will send schedules. In the case of the Eastern European stations they will often send literature for years. The author is still receiving programme schedules, free records and competition forms from *Radio Budapest* even though only one report was sent—eight years ago!


European stations can also often provide a guide to the general conditions. If stations in Portugal and Spain are heard clearly the reception path across the Atlantic will usually be good. ■

Build yourself a quality transistor radio

backed by our after sales service!

roamer seven mk IV SEVEN WAVEBAND PORTABLE

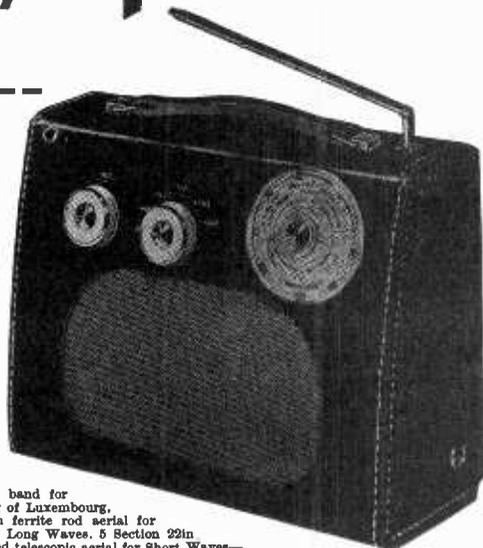
SEVEN TUNABLE WAVEBANDS—
MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.



pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 8½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).

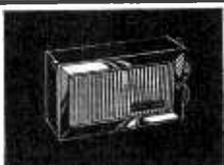

Total building costs
44'6 P. & P. 3/6

Extra M.W. band for easier tuning of Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push pull output. 7 transistors and 2 diodes including Micro-Alloy R.F. Transistors. Famous mark 7 x 4in. P.M. speaker for rich-tone volume. Air spaced ganged tuning condenser. Volume on/off control wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. First grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build.

Total building costs
£5.19.6 P. & P. 7/6 Personal Earpiece with switched socket for private listening 6/- extra.

Parts price list and easy build plans 3/- (Free with parts).

transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½in. x 1½in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
47'6 P. & P. 3/9

NEW LOOK melody six

TWO WAVEBAND PORTABLE

8 stages—5 transistors and 2 diodes. Covers Medium and Long Waves. Top quality 3½in. Loudspeaker for quality output and also with Personal Earpiece with switched socket for private listening. Two R.F. stages for extra boost. High "Q" Ferrite Rod Aerial. Push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 4 x 2in. Easy build plans and parts price list 2/- (FREE with parts).



Total building costs
69'6 P. & P. 4/3

super seven

THREE WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gilt fittings. The ideal radio for home or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 6/- extra.)



Total building costs
69'6 P. & P. 4/6

roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 6/- extra.)



Total building costs
79'6 P. & P. 4/6

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER SEVEN	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	SUPER SEVEN	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	MELODY SIX	<input type="checkbox"/>

Parts price list and plans for

Name

Address

PW6

* Calls side entrance Stylo Shoe Shop
* Open 10-1, 2.30-4.30 Mon-Fri. 9-12.30 Sat

another amazing newmart scoop purchase

A frustrated manufacturers French export order enables us to give you what is undoubtedly the finest package deal in this country today.

The world famous British made Deluxe Balfour 4 speed auto change record player deck (grey finish) incorporating an automatic stylus cleaner and unique arm locking device, compatible cartridge enabling you to play stereo records on mono without damage to the record, or for an extra 15/- you may have the stereo version of this cartridge. In addition there is supplied, at no extra charge, a 45 r.p.m. auto change adaptor which will enable you to dispense with the centres of your 45 r.p.m. records should you desire to do so. This unit is mounted on a magnificent luxury teak veneered plinth which will accept the Garrard SPC1 cover or similar type.



All this comes to you for the amazingly low price of **9½ gns.** (post and packing 10/-), which cuts normal prices by 50%. Deck with cartridge less plinth (template for cut out supplied) 7 gns. (post and packing 10/-). Remember this offer is exclusive to **NEWMART.**

NEWMART

ELECTRONICS Dept. JUN 9
30/32, Shudehill, Manchester 4. Tel: 061832 7710
15, Whitechapel, Liverpool. Tel: 051 236 0738

BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE,
150 REGENT ST., LONDON, W.1.

KING OF THE PAKS SUPER PAKS

Unequaled Value & Quality
BI-PAK NEW—UNTESTED
SEMICONDUCTORS

Satisfaction GUARANTEED In Every Pak, or money back.

PAK NO.	Description	Price
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N708	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 Watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	12 Silicon Rectifiers EPOXY BY126/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2S104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U22	10 1-Amp Glass Min. Silicon Rectifiers High Volts	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-Amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1 Amp SCR's TO-5 can up to 600 PIV CRSI/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise 2N3707	10/-
U32	25 Zener diodes 400mW DO-7 case mixed Vlt. 3-18	10/-
U33	15 Plastic case 1 Amp silicon rectifiers W4000 series	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

FULLY TESTED

AC107	3/6
AC126-7-8	2/6
AF116-117	3/6
AF139	10/-
AL102	15/-
BC107-8-9	5/-
BFY50-51-52	7/8
BBY26-7	3/6
BBY28-9	4/6
BSY95-95A	4/6
OC22-25	5/-
OC26-35	5/-
OC28-29	7/6
OC44-45	1/9
OC71-81	1/6
OC72-75	2/6
OC81D-92D	2/3
OC140	5/-
OC170	2/6
OC171	3/6
OC201	7/8
ORP12-60	8/6
OCPT1	8/6
OA5-10	1/9
OA47	2/-
OA70	1/8
OA79	1/9
OA81-85	1/6
OA91	1/3
OA95	1/9
OA290	3/-
OA302	3/6
2N696-7	5/-
2N708	3/6
2N2160	15/-
2N2646	15/-
2N2712	2/6
2N2926	2/6
MAT100-101	3/-
MAT130-121	3/6
ST140	3/-
ST141	4/-

SIL. RECTS TESTED

PIV	750mA	3A	10A	30A
50	1/-	2/9	4/3	9/6
100	1/8	3/3	4/6	15/-
200	1/4	4/-	4/6	20/-
300	2/3	4/6	6/6	22/-
400	2/6	5/6	7/6	25/-
500	3/-	6/-	8/6	30/-
600	3/3	6/6	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/6	12/6	50/-
1200	6/6	11/6	15/-	

PRINTED CIRCUITS

EX-COMPUTER
Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/- Plus 2/- P. & P.

UNIUNION

UT46 Eqvt. 2N2646, 7/6
Eqvt. TIS43

FET's

2N3819	10/-
2N3820	25/-
MPP105	8/-

AD161-162 NPN-PNP
Comp. Pair 12/6 pr.
28034 15/- ea.

TRANSISTOR EQUIVALENT BOOK

52 pages of Cross References for transistors and diodes, types include British, European, American and Japanese. Specially imported by BI-PAK 10/- each.

PLEASE NOTE.—To Avoid any further Increased Postal Charges to our Customers and enable us to keep our "By Return Postal Service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, Direct to our Warehouse and Despatch Department, postal address—BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and Packing 8/11/- per order. Minimum Order 10/-.

TESTED SCR's


PIV	1 AMP	7A	16A	30A
25		7/6		30/-
50	7/6	8/6	10/6	35/-
100	8/6	10/-	15/-	45/-
200	12/6	15/-	20/-	55/-
300	15/-	20/-	25/-	
400	17/6	25/-	35/-	80/-
500	30/-	40/-	45/-	95/-
600		40/-	50/-	

INTEGRATED CIRCUITS

I.C. Operational Amplifier with zener output.


Type 701C. Ideal for P.E. projects. 8 Lead TO-5 case. Full Data. Our Price 12/6 each. 5 off 11/- each. Large qty prices quoted for.

Fairchild Epoxy TO-5 8 Lead. I.C.	
uL800 Buffer	10/6
uL914 Dual Gate	10/6
uL923 J.K. Flip-Flop	14/-
I.C. Data Circuits etc.	1/8
Mullard I.C. Amplifiers	
TAA243 ORP.AMP.	70/-
TAA263 Min AF Amp	18/6
TAA293 G.P. Amp	26/-
RCA CA3020	
Audio Amp	30/-

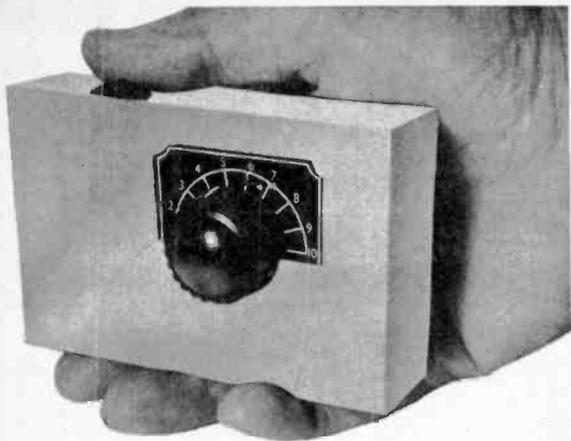

A
SLIMLINE
SUPERHET

F. G. RAYER
 ★★★

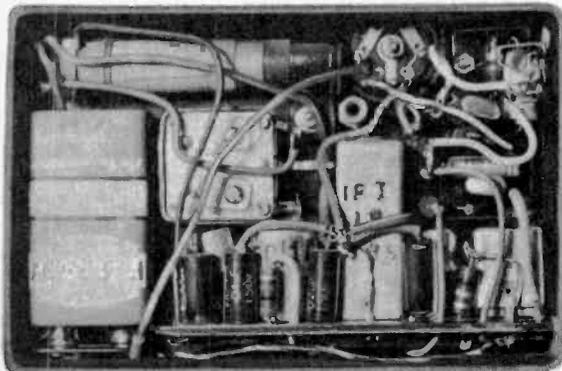

POCKET receivers often use reflexed t.r.f. circuits, and although these can give good results, some constructors may prefer a superhet. The one described here is built with standard and readily available transistor type components, and is approximately $4\frac{3}{8} \times 2\frac{7}{8} \times 1$ in. external dimensions, including battery. It is a 4-transistor superhet circuit giving excellent head-phone results.

Figure 1 is the circuit, the aerial L1 and oscillator coil L2 being tuned by a midget 192/78pF ganged capacitor, fitted with 15pF trimmers. AF117 transistors are used in mixer and i.f. stage, and IFT1 is double-tuned. IFT2 is single-tuned, and works into the emitter detector/amplifier Tr3. Automatic gain control bias to Tr2 is through R6. This type of circuit performs very well, and Tr4 is an audio amplifier, giving adequate output for phones or a personal earpiece.

The receiver is wired in three sections, and fitted together afterwards.

(1) $4\frac{3}{8} \times 2\frac{7}{8}$ in. front panel, carrying ferrite rod, volume control with switch, and ganged capacitor.

(2) Mixer and intermediate frequency amplifier, assembled on an insulated board $3\frac{1}{8} \times \frac{7}{8}$ in.

(3) Detector/audio amplifier, on a $1\frac{1}{2} \times 1$ in. board.

If alternative components are used, it would be wise to see that these will fit, as there is only a little free space.

Front Panel

The panel is wired as in Fig. 2, the mixer, i.f. and audio sections being omitted. VR1 is mounted with a small bolt so that it will project through a slot in the case side. VC1/2 is attached with two bolts.

The aerial listed is for a longer rod, and the ferrite rod actually needed here is $2\frac{3}{8}$ to $2\frac{1}{2}$ in. long, and $\frac{3}{16}$ in. in diameter. A piece this size was broken from a longer rod by gripping the rod quite tightly $2\frac{3}{8}$ in. from one end in a vice, and snapping it off. The rod is fixed by a band of insulating material, which passes round it at one end, and is secured with a bolt.

The aerial and oscillator coil L2 are of a type intended for 208pF aerial tuning, and 176pF with a series padder in the oscillator section. The ganged capacitor used here has an aerial section tag A, rotor tag E, and oscillator section tag O, Fig. 2, and alignment was found satisfactory. No series padder is used with L2. For the AF117 mixer transistor, the base coupling winding requires four turns. Aerials made for other transistors may have more turns here. If so, turns should be removed.

Leads to L1 can be solid wire, arranged to permit a little movement of L1 on the ferrite rod, if required later.

The Mixer/IF Section

A piece of $\frac{1}{16}$ in. paxolin sheet is cut and drilled to take the components as in Fig. 3. With the oscillator coil L2, a coloured dot is between pins 1 and 6. Pins on the i.f.t.s have closer spacing between 1 and 2, and 5 and 6. These components need to be fitted over holes so that the cores can be reached. Tags from the metal cans of L2, IFT1 and IFT2 are wired together and to the positive or "earth" line of the receiver.

Insulated sleeving should be placed on all leads. The transistors are fitted last, passing their leads down through the correct holes. Put on suitable pieces of sleeving, bend the leads over, and solder them to the other circuit points, afterwards snipping off unwanted wire. Be sure that transistor leads on top of the board cannot touch each other, or bare parts. Pieces of sleeving about $\frac{1}{4}$ to $\frac{3}{8}$ in. long can be put on these leads in advance.

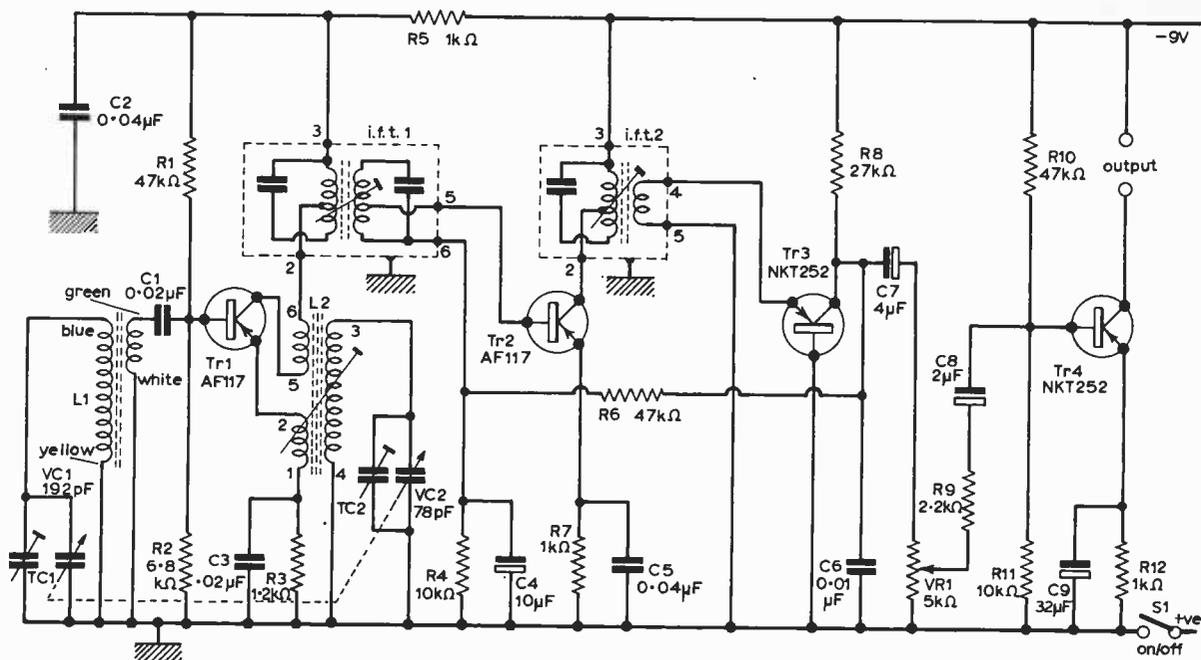


Fig. 1: Circuit of the Slimline Superhet, suitable for driving headphones or a personal earpiece.

The finished mixer/i.f. section is later attached to the panel by two small, countersunk 8BA bolts, which pass through the brackets in Fig. 3. These brackets are cut from thin metal, drilled, and soldered in place. One is soldered to the can tag of IFT1, while the second bracket is soldered to a can tag and pin 5 of IFT2.

C2, C3, C5, R3, R7, VC1/2 (E) and VR1/S1 are all joined near IFT1 (Fig. 3), and a lead passes down through the board to the earth (positive) line, Fig. 2.

When the mixer/i.f. section is fixed to the panel, the four adjustable cores can be reached with a suitable insulated tool.

C1 is wired to L1 green tag, and the earth circuits made to VC1/2 and VR1/S1, as mentioned (Fig. 2). A wire is prepared to run from pin 6 of IFT1 to R6. Other leads will run to the negative line at R8 and R10, and from the positive line of the i.f. section to positive on the audio circuit board.

Detector and Amplifier

Tr3 and Tr4 are on the audio amplifier board, Fig. 4. This is cut away to clear the milled rim of VR1. When this section is completed, it is mounted with a small bolt and spacer.

A lead passes from Tr3 emitter to pin 4 of IFT2. R6 is connected to pin 6 of IFT1. Leads run from C7 to VR1, and from C8 to R9, which is soldered directly to VR1 as in Fig. 2.

Battery negative goes to R8/R10, and also the mixer/i.f. section at pin 3 of IFT2. Battery positive is connected to S1, as in Fig. 2. The insulated strip, with snap fasteners, from an old battery can be used as battery connector. Remember to observe the polarity shown on the battery.

Two leads run from R10 (negative line) and the collector of Tr4. These connect to a miniature jack, for the headphones or a personal earpiece.

When the two small circuit boards have been fixed to the panel, the receiver should be tested, and i.f., aerial and oscillator circuits adjusted.

★ components list

Resistors:

R1	47k Ω	R7	1k Ω
R2	6.8k Ω	R8	27k Ω
R3	1.2k Ω	R9	2.2k Ω
R4	10k Ω	R10	47k Ω
R5	1k Ω	R11	10k Ω
R6	47k Ω	R12	1k Ω
VR1	5k Ω miniature log. pot. with switch		

All resistors $\frac{1}{2}$ watt 10%

Capacitors:

C1	0.02 μ F 150V Hunts miniature
C2	0.04 μ F 150V Hunts miniature
C3	0.02 μ F 150V Hunts miniature
C4	10 μ F 6V electrolytic
C5	0.04 μ F 150V Hunts miniature
C6	0.01 μ F 150V Hunts miniature
C7	4 μ F 6V electrolytic
C8	2 μ F 6V electrolytic
C9	32 μ F 6V electrolytic

VC1/VC2/TC1/TC2 Jackson Delemin 192/78pF with 15pF trimmers

Coils and Transformers:

L1	Weyrad RA2W (medium wave only)
L2	Weyrad P50/1AC
IFT1	Denco IFT 18/465
IFT2	Denco IFT 14/465

Transistors:

Tr1	AF117	Tr3	NKT252
Tr2	AF117	Tr4	NKT252

Miscellaneous:

$\frac{1}{16}$ in. sheet paxolin. Miniature jack and plug. PP3 battery. Knob, 1mm sleeving, etc.

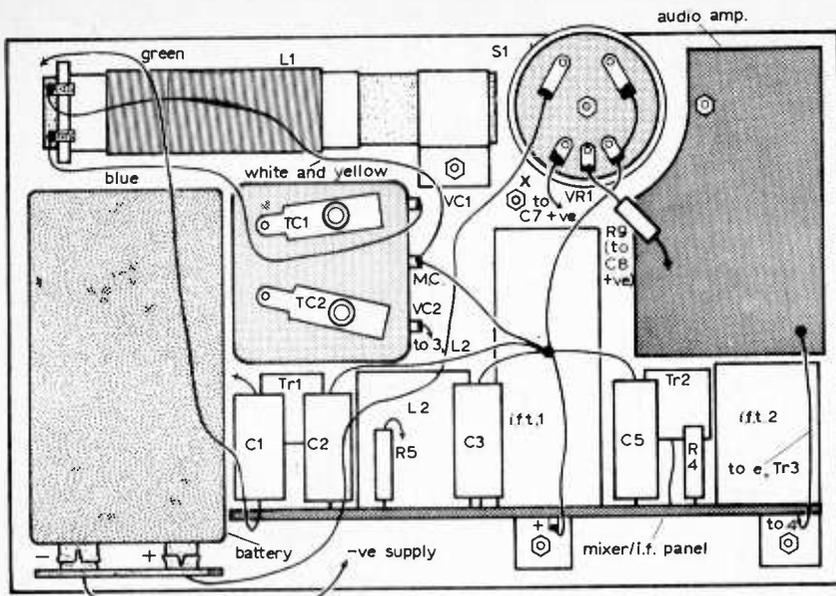


Fig. 2: General layout and inter-module wiring.

Alignment

A modulated 465kHz signal may be injected at the base of Tr1, and the cores of IFT1 and IFT2 rotated for best volume. If alignment is so far in error that no signals are obtained by this means, inject at 5 on IFT1 and adjust the core of IFT2. Then inject at 2 on IFT1 and adjust the second core. Afterwards inject at Tr1 base or collector, and adjust the first core of IFT1, and check adjustment of all cores.

To make these adjustments without a signal generator, tune in a transmission and rotate the cores for best volume. This is afterwards checked with a weak signal.

To align L1 and L2, first unscrew TC1 and TC2 about half-way. Set VC1/2 at maximum capacitance, and rotate the core of L2 to set the low-frequency band

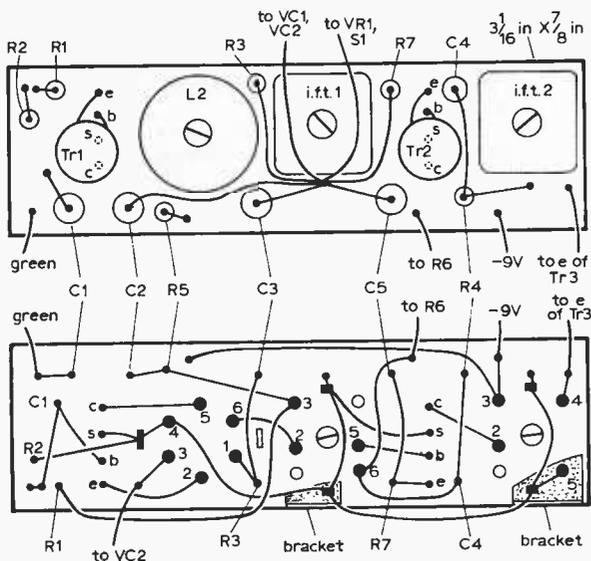


Fig. 3: The r.f. and i.f. amplifier component board.

edge to about 600kHz (or so that Radio 3 is tuned with VC1/2 nearly closed). At the same time move L1 on the rod for best results.

Open VC1/2 to near minimum capacity, and adjust TC1 and TC2 for best results with a 1,500kHz signal from the generator, or for reception of Radio Luxembourg.

Adjustments should be repeated, and checked over the band, for best results.

Case

Using $\frac{1}{8}$ in. thick paxolin throughout, the top and bottom of the case are cut to $4\frac{3}{8} \times \frac{7}{8}$ in., one piece being cut to clear VR1. The sides are $2\frac{1}{2}$ in. long by $\frac{7}{8}$ in. wide, and are cemented to the panel.

The terminal head X, Fig. 2, is fixed to the panel by means of a very short countersunk bolt. A screw is run into this terminal head from behind, to hold the back of the case.

Patterned material as used for covering boxes, etc., was cut to cover the front panel and sides, and to fold over about $\frac{1}{4}$ in. or so inside the case.

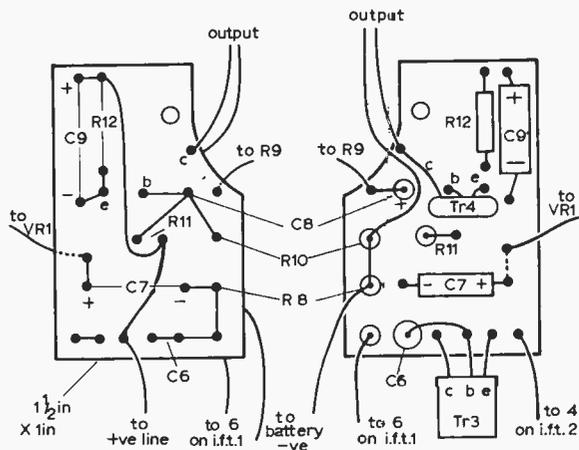


Fig. 4: The detector and audio stages.

Tuning Dial

The dial had white markings on a black background, from Set 6 (Dials) "Radio Constructor" panel transfers. The tuning knob is a $1\frac{1}{8}$ in diameter knob, with a white spot placed near the edge, to read against the tuning scale. A very small knob makes tuning rather critical.

The back of the receiver is $2\frac{1}{8} \times 4\frac{3}{8}$ in., with a hole drilled opposite terminal head X. Some small pieces of paxolin are cemented to the inside of the back, and rest inside the case when the back is in place. It is then held correctly in position by the single bolt.

MANY engineers who could build a valve amplifier without the need to refer to a circuit diagram feel totally lost when tackling transistor power output stages. Part of the trouble is due to the nature of the transistor, so easily damaged by excessive current and requiring heatsinks to avoid excessive temperature rise, and part to the confusing stream of different transistor characteristics which have been used in the past. This article attempts to clear up some of those difficulties.

The Need for Power Output

When an amplifier is used to drive the deflection plates of a cathode ray tube, the amplifier has to raise and lower the voltage on the plates, but, because the plates have no other connections, the amplifier does not have to supply any current. If the same amplifier had to raise and lower the voltage across a resistor, it would also have to raise and lower the current through the resistor, because the voltage across any resistor is its resistance times the current through it ($V=IR$), which is Ohm's law.


When an amplifier has to supply both voltage and current signals, and the maximum voltage signal occurs at the same time as the maximum current signal (as it must with a resistor) or nearly at the same time (with loudspeakers), then the amplifier is supplying power. This power can be measured in a variety of ways. If

oscilloscopes, will give readings for voltage and current which cannot be multiplied so readily, and a conversion table is given.

The need to supply both voltage and current restricts the sort of amplifier which we can use. Suppose, for example, we have a valve with an anode load of $100k\Omega$ and a line voltage of $1,000V$. Then with no current through the valve, the anode voltage is $1,000V$, and with $10mA$ flowing the anode voltage is $0V$. This stage can give a voltage signal of $1,000V$ but a current signal of only $10mA$, since these are the ranges of voltage and current available, so that it would be totally unsuitable for delivering large amounts of power to a load of 3 ohms (for example).

Matching Loads

Any amplifying device, valve or transistor, has an *internal impedance*, which measures its resistance to current flowing through it and in some cases restricts the amount of signal current flowing. When triode valves are used, the maximum power output is obtained when the load resistance R_l equals the internal resistance R_a . This piece of advice was so thoroughly drilled into the heads of designers in the valve era that it still persists even now that the use of triodes for output stages is practically obsolete. Pentode valves deliver a signal current that is almost constant despite changes in

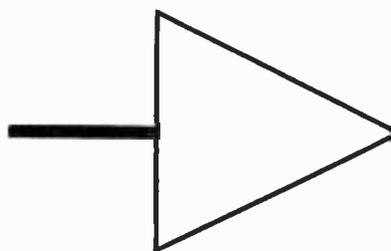

TRANSISTOR

the amplifier supplies its power to a resistor, the resistor will be heated by the power and the temperature rise can be used to measure the amount of power used or *dissipated*, provided we know what amount of power causes a given temperature rise. This method is often used for microwave amplifiers when other readings are difficult. Alternatively we may measure the voltage across the resistor and current through it with a meter which reads r.m.s. units and multiply the two together to give power. When volts d.c. are multiplied by amps d.c., the result is power in watts. R.M.S. meters are a.c. meters which are scaled so that the same multiplication gives the correct result in watts for a sine wave, but other waveforms, and other meters or cathode ray

anode voltage, which is another way of saying that they have a high internal impedance.

On the maximum power theory, they would require a very high load impedance for maximum power. This is true, but a *slightly* smaller power can be delivered at much less distortion into a smaller load, and this is the value of load recommended for such valves. Transistors are a separate case again; the signal current is almost independent of collector voltage (high impedance) but very high currents can pass at quite low voltages.

This point often causes confusion; the "high impedance" transistor passes high currents at low voltages, which *seems* to indicate low impedance, but we are talking of two different things. The impedance is represented by the change of current with collector voltage for a fixed bias; impedance = $\frac{\text{voltage change}}{\text{current change}}$.

When we bias the transistor full on and measure the voltage across it and the current through it and do the same sum of $\frac{\text{volts}}{\text{current}}$ we are simply measuring the resistance of the transistor to d.c., not to signals. This quantity should be called *Perveance*. It is well known to the user of transmitting valves used with positive grid voltages because it indicates the current which the valve can supply at low anode voltages.

All this means that our matching of transistors must be for best undistorted output and that it is unwise to

Table I

When using a meter which measures in peak volts and is scaled in R.M.S. volts (for example, any moving coil and rectifier type of meter).

Waveform	To find power
Sine	$V \times A$ as read on meter
Sawtooth	$2/3 \times V \times A$
Square	$2 \times V \times A$

bias a transistor hard on while the full line voltage is on the collectors, since a very high current will flow.

Single-ended Stages

When a single valve or transistor or a group wired in parallel is used to deliver power to a load, this is termed a *single-ended* stage. We bias such a stage so that the bias current is about half the maximum current we wish to take from the output, and we load so that the voltage at anode or collector is minimum (about 30V for a valve, 1V for a transistor) at maximum current. If the load we wish to use differs from the calculated ideal load, we use a transformer for matching, with a turns ratio $N:1$ equal to $\frac{\text{Primary load}}{\text{Secondary load}}$ where N is the ratio of primary turns to secondary turns. With valves, this procedure is quick and straightforward; with transistors, almost always impossible. To start with, when a valve is biased, and no signal is being amplified, there is power dissipated in the valve equal to anode voltage times anode current. This power appears when the current in the valve strikes the anode and heats it up; this heat must be lost by radiation, but does not affect the working of the valve, since electrons move through the vacuum unaffected by the temperature of their surroundings. When a transistor is biased in this way, the heat is generated inside the semiconductor crystal and

spreads throughout it. The effect of this is to make the crystal more conducting so that more heat is generated, and the situation can end up with the whole crystal melting, a catastrophe called *Thermal Runaway*.

A fair degree of protection can be obtained if the bias can also change with temperature, or can be regulated to keep the current fairly constant. This may involve a thermistor to reduce bias (Fig. 1) as temperature increases (the thermistor being attached to the transistor to short its temperature) or biasing with a network which holds the base at a constant voltage and using an emitter resistor so that any increase of emitter current automatically reduces bias (Fig. 2). The second method is better, since the emitter resistor can be chosen to prevent excessive current ever flowing, but the emitter resistor dissipates some power so that less can be used in the load.

Another method which has been used is to rectify some of the output signal and use it to increase the bias current when large signals are being amplified. In this way a low bias can be set for normal use without excessive distortion on large signals. This method, called *sliding bias*, is seldom seen due to the difficulties of setting the time constants of the rectifying circuit so that the response is quick enough to avoid undue distortion at the start of a loud passage and yet slow enough to avoid oscillation due to feedback of signal. A typical sliding bias circuit is shown in Fig. 3.

Single-ended output stages are wasteful in the sense

I. R. SINCLAIR

OUTPUT STAGES

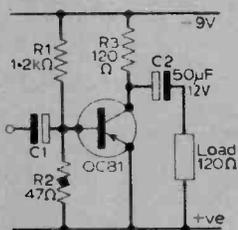


Fig. 1: A single-ended stage using thermistor compensation. If the voltage at A is less than half the line voltage, thermal runaway cannot cause damage. R3 may be used as the load if bias current can be passed through the load (not suitable for use with a loudspeaker)

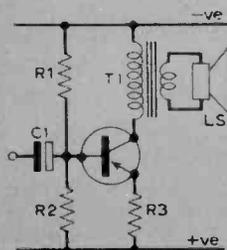


Fig. 2: A transformer coupled output stage. R3 is usually small, 1-10Ω, depending on the bias current so that about 0.5 volt is dropped across it. R1 and R2 are low value resistors, and R2 may be a thermistor for greater protection. R3 could be a torch bulb.

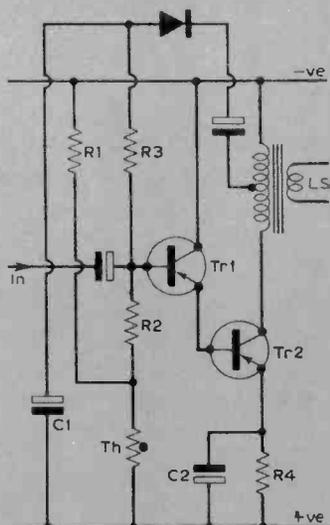


Fig. 3: A sliding bias amplifier. The current fed back by the rectifier must exceed the input signal current, and C1 must be chosen so that there is not too much time-lag between the signal and bias. Too small a value of C will cause severe distortion of low frequencies.

that the bias causes most of the wattage to be dissipated in the transistor and very little in the load, though they are fairly cheap in terms of component costs. Their main application is in car radios, where the bias current is only a small load on the power supply. When power is supplied by rectifying a.c., single-ended stages are seldom used because the large steady current demand makes it very difficult to obtain a supply free from mains hum.

Push-Pull Transformer—coupled

The basic circuit is shown in Fig. 4. The transistor may be biased in Class A, meaning a bias current of about half of the maximum signal current required, in

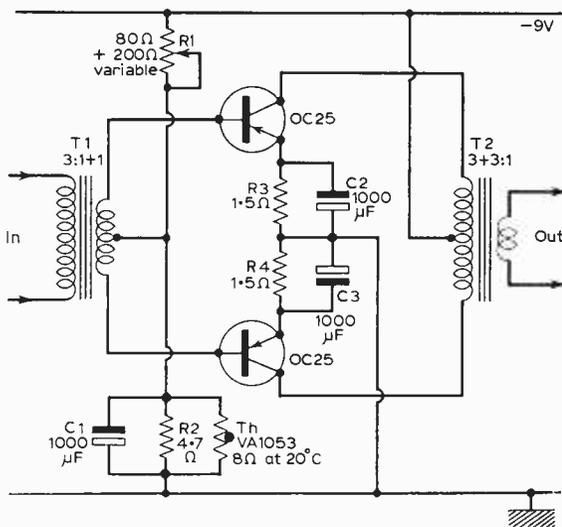


Fig. 4: A push-pull transformer coupled amplifier.

which case the disadvantages are the same as for the single-ended stage, excessive heat, danger of thermal runaway and large standing current drawn from the power supply. The use of push-pull does, however, avoid the hum from the power supply appearing in the output signal (provided it is not present in the input signal).

The bias can be reduced, so that the transistors work

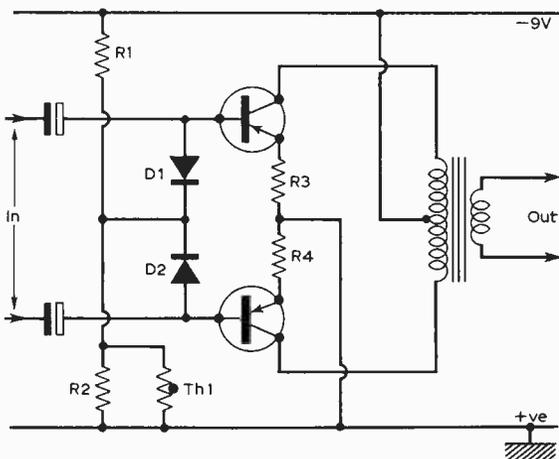


Fig. 5: A re-arrangement of Fig. 4 which is useful where a low supply voltage has to be used. The voltage at each collector becomes double the supply.

in Class AB, with both conducting but not passing as much as half of maximum signal current or in Class B where the bias current is almost zero, and each transistor conducts only when the signal input is in the forward direction of bias. The class AB circuit of Fig. 5 is capable of good results, and the transformer is easily made, yet this circuit does not seem to have been widely used, despite its very close resemblance to the equivalent valve circuit. Perhaps this has been due to the wide publicity given to circuits (dealt with later) which use no transformers, but which do not necessarily benefit thereby. The circuit of Fig. 5 is extremely useful where supply voltage is limited, as the effect of the transformer is to make the maximum voltage at each collector double the supply voltage.

Class B circuits can be used, but distort badly at low signal levels. They are useful in devices such as loud hailer or guitar amplifiers but not when close resemblance to the original sound is required.

The Totem-pole Circuit

Officially this circuit is known in this country as the "single-ended Push Pull", but the American name is much more descriptive. In outline, the circuit is as in Fig. 6. Two transistors are connected in series and driven

so that they conduct alternately. Such an arrangement could be used in Class A, but is usually used in Class AB or B, and is the output stage used in the majority of transistor amplifiers. No output transformer is required, though, in some American designs, an autotransformer output is used so that loads of different impedances can be used. When the load is coupled directly, one transistor connects the load to line voltage when conducting and the other connects the load to earth. In most designs, the load is the greatest impedance in the circuit, and very large currents can flow through the output transistors if a signal is applied to them with a low impedance load connected or the load shorted. For this reason, output circuits of this type need protection against excessive current, usually in the form of low ohmage resistors, fuses or lamps in the emitter of the output transistors.

Summing up the output power and transistor dissipation for transistors used in this circuit:

$$\text{Power Out} = \frac{V_c^2}{R_l} \quad \text{Power Dissipated} = A \times \frac{V_c^2}{R_l}$$

A is	Sine wave	"Music"	Square wave
	1/40	1/50	1/30

The Totem-pole circuit can be seen in three distinct forms, depending mainly on the way in which the input is applied: by a transformer, by driving transistors, or as a single phase input to a complementary pair output.

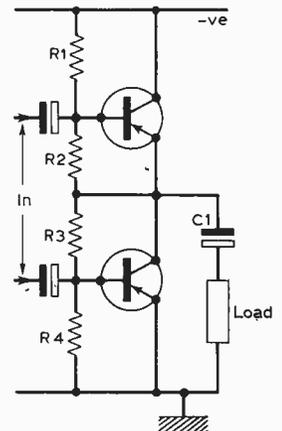


Fig. 6: A single-ended push-pull or totem-pole amplifier.

**NEXT MONTH: TRANSFORMERLESS
AMPLIFIERS AND THERMAL CALCULATIONS**

LETTERS

The Editor does not necessarily endorse the views expressed by correspondents.

Turning a deaf ear!

At the risk of making a complicated situation even more incomprehensible I would like to call attention to certain aspects of Mr. Iain Smith's letter published in February.

He states that, apart from certain cheap amplifiers which include a "loudness" control as a gimmick, many manufacturers provide this facility on their equipment under the *misconceived* notion that some compensation should exist to boost bass frequencies when the volume is reduced. In practice he suggests that this is not required because, for example, during a live concert if one moved from the front towards the back of the auditorium the sound would normally appear to fall with more noticeable loss in the lower frequency range. This, of course, is quite true. But then it presupposes that the situation is always of this form and that the intention is to make the sound seem a long way off whenever an amplifier has its gain reduced. It further suggests that it should be normal to shift the apparent sound source every time we adjust the volume control! And perhaps, even more ludicrously, that whenever an orchestra decides to play quietly it suddenly moves *en masse* to perform in some remote position outside the hall!

Fundamentally (provided we remain seated) none of these "loudness" distortions seem to occur during a live performance—why? We are all aware that an orchestra can deliberately create the illusion of playing a long distance away, but it can equally well play *quietly* and not give this impression. This, I suggest, is brought about by the effect of normal audition among the members of the orchestra; i.e. they are only able to create these effects by consciously monitoring (in conjunction with the conductor) the sounds they make and adjusting the amplitude accordingly. All these amplitude adjustments are necessarily made with reference to what the conductor's concept is of the sound produced by his orchestra playing at "full voice".

However, "we in our living rooms" cannot use the "full voice" reference without blowing several windows out, so naturally we keep the volume level much lower. By

doing this, though, we automatically change the reference point, but forget that our hearing response remains substantially the same. Therefore if, for example, we are listening to a recording of some music which up till now has remained at a satisfactory level, and then suddenly drops to a low intensity during a quiet passage, it will now sound far off and quite unrealistic. The only way in which this can be countered is by judicious use of a loudness control. It then matters little *where* the initial reference is.

Incidentally, Mr. Smith does not seem to mention that to a slightly less extent the ears' response *also* falls off with reduction in the intensity of treble. Most manufacturers take care of this in their design of loudness correction circuits.—G. C. Brown (*Hampshire*).

A lady replies

While leafing through my husband's copy of PRACTICAL WIRELESS, the contents of which are invariably beyond the comprehension of my housewife's brain, I noticed among the letters one concerning loudness control.

I would point out to any reader who considers that the further away one sits from an orchestra at a live performance, the less bass one hears, that this is not entirely true. Casting my mind back to my school days, when I was a regular concert-goer, it seems to me that one's distance from the orchestra is compensated for by the acoustics of the concert-hall. I am thinking in particular of the Free Trade Hall in Manchester, where our pocket money limited us to the cheapest seats, either the very back of the "Gods" or the front eight rows of the stalls. I can't honestly remember noticing any difference in the amount of bass that came over nor did it seem to me that the sound heard at the very back was murky or obscure, as Mr. Iain Smith suggests. This may, of course, be due to the fact that I am a music-lover, not an electronics enthusiast.

Having made this admission I would like to state my reasons for writing. My husband is at the moment, constructing a hi-fi unit, and since he asked my opinion as to whether the loudness control

was an improvement, I gave the matter a little consideration and now feel that I am as well qualified as most electronics experts and amateurs to state my views on what is, after all, a matter of individual taste.—Susan Jebb (*Warwickshire*).

The (w)hole truth?

That you should publish an article and a letter (B. R. Meredith, March P.W.) stating that hole theory is fiction shows editorial irresponsibility, I believe. To compare thermionic valve action to transistor action is as irrelevant as to compare the working of steam and diesel engines. It is a fact (unfortunately?) that the action of semiconductor devices cannot be explained *quantitatively* without holes. Current flow in semiconductors *does* take place by two distinct mechanisms. I can just believe that Mr. Meredith may be able to describe *qualitatively* transistor action without direct reference to holes. I defy him to produce a plausible explanation of the Hall Effect without introducing the concept of holes. Simple experiments based on this effect prove that there are indeed two different conduction processes in semiconductor materials.

It is certainly beyond the scope of your magazine to consider the band theory of solids in sufficient quantitative detail to demonstrate the existence of the hole. But you should not lead your readers astray by printing such dogmatic letters as Mr. Meredith's without comment.

I do not class myself as an "acknowledged expert": I am a third year undergraduate studying for the "Electrical Sciences Tripos".

I have read PRACTICAL WIRELESS regularly for about seven years. As a result, my interest in electronics has steadily increased. R. F. Pannett (*Trinity College, Cambridge*)

Anybody heard of these?

I recently acquired some TK31C JY and TK31C NB transistors and can find no reference to them in any of the books I have.

I wonder if any fellow readers could possibly supply me with simple circuits which use such devices?—J. Boot (38 Gowing Road, Hellesdon, Norwich, NOR 40M).

TAKE



JULIAN ANDERSON

A SERIES OF TRANSISTOR PROJECTS, EACH USING LESS THAN TWENTY COMPONENTS AND COSTING LESS THAN TWENTY SHILLINGS TO BUILD.

No. 2 an audio oscillator

WHEN building or testing equipment a source of sound is always useful. This can be supplied by all sorts of equipment, best of all a full range constant level audio oscillator, but a very simple source and one of the most useful is a transistor phase shift oscillator. Unlike the other commoner sine wave generators this uses only one transistor.

THE CIRCUIT

From the circuit diagram in Fig. 1 it will be seen that the output of Tr1 is taken from the collector and fed back to the base via a RC network comprising R1, R2 and R4 and C1, C2 and C3. The values of these components determines the output frequency. The network itself changes the phase at one particular frequency by 360° resulting in positive feedback and consequently oscillation. The losses in the network are quite high and a gain of 29 times must be obtained from the transistor for it to work. The transistor used in the prototype was an OC170, but almost any transistor giving enough gain could be used. The output impedance of the unit is high and if it is being used to feed into a transistor amplifier (where the impedances are generally fairly low) a 100kΩ resistor should be fitted in the lead to the equipment; with this the unit will still oscillate even if the ends are shorted.

The actual frequency can be calculated by the formula $f = \frac{\sqrt{6}}{CR}$ but it will be found that the internal resistances and capacities of the actual transistor used will alter this.

★ components list

Resistors:

R1 8.2kΩ	R4 4.7kΩ
R2 8.2kΩ	R5 6.8kΩ
R3 47kΩ	R6 820Ω

All resistors ½ watt miniature types.

Capacitors:

C1 2,000pF	C4 10μF 9V
C2 2,000pF	C5 0.01μF
C3 2,000pF	

Transistor OC170—see text.

9v Battery, Veroboard 1½ x 1½in., on/off switch.

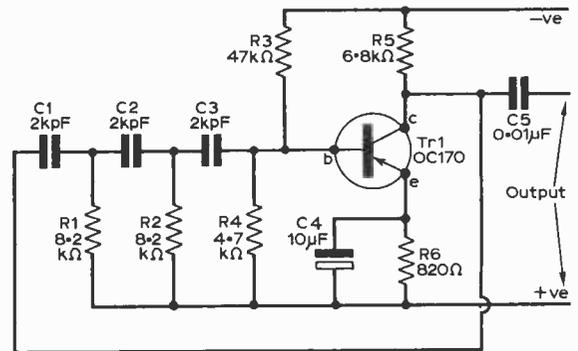


Fig. 1: The circuit of the phase shift oscillator. The voltage is 9v, supplied by any battery.

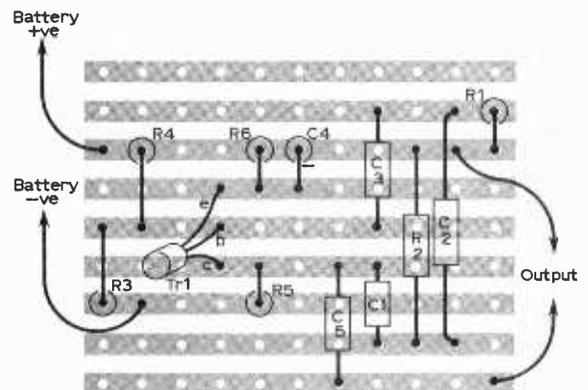


Fig. 2: The component layout; there are no breaks in the Veroboard copper strip.


If one is lucky enough to have an oscilloscope the unit may be used very successfully for tracing the waveform through an amplifier. In addition it may be used to feed a Schmitt trigger for producing square waves.

The actual building of the phase shift oscillator presents no problems, all the components can be mounted on a piece of Veroboard 1½ x 1½in.; no breaks are necessary in the copper strip.

If the unit is built into a copper tube about 1in. diameter, a small push button can be mounted at one end and a probe protruding from the other, an extremely useful audio signal injector will be added to your test gear.

"Listen in" on the World with HEATHKIT shortwave receivers

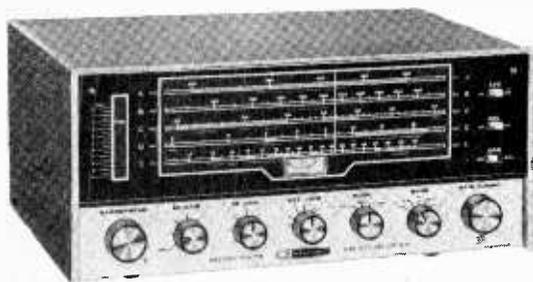TREAT YOURSELF TO A WORLD TOUR... *WITHOUT LEAVING HOME!*



GR-54

DELUXE 5 BAND SHORTWAVE RECEIVER GR-54


This receiver offers exceptional performance and many special features at such a low price. It covers 2MHz to 30MHz plus 550KHz to 1550KHz AM broadcast band and 150KHz to 420KHz aeronautical and radio navigation band. Receives AM/CW/SSB, 6 x 4in. PM speaker and sleek, "low-boy" styling. Operates on 115-230V 50Hz AC.

Kit K/GR-54 £44.0.0. Carr. 9/-

LOW COST 4 BAND SHORTWAVE RECEIVER GR-64

Makes an ideal present for the youngster. It has high performance features plus world-wide reception, shipping, aircraft, radio amateurs plus the popular medium broadcast band. It covers 1MHz to 30MHz plus 550KHz to 1620KHz AM, with sleek "low-boy" styling, operates on 115-250V 50Hz AC.

Kit K/GR-64 £22.8.0. Carr. 9/-

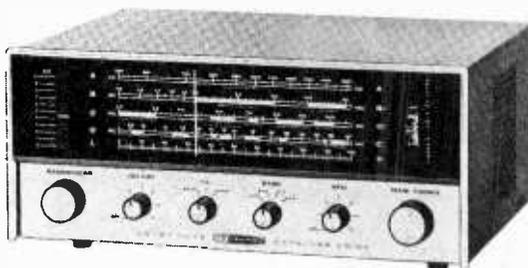

GR-64

GENERAL COVER-AGE RECEIVER GC-1U

A welcome traveller wherever you go! Covers 580 to 1550 KHz and 1.69 to 30MHz in 5 bands with calibrated bandsread scales for 80, 40, 20, 15 and 10 metre amateur bands. Completely solid state and self contained for portability. Operates on two internal PP6 batteries (not supplied) or 230V AC with a suitable power supply.

Kit K/GC-1U £38.8.0. Carr. 11/-



AMATEUR BANDS RECEIVER RA-1

Unequaled value for the radio amateur. Covers 160 to 10 metres. High quality lattice crystal filter for optimum communications selectivity. Optional 100KHz crystal calibrator plugs in inside receiver. 8 valve and 2 diode circuit. Operates on 115, 200-250V AC, 50Hz.

Kit K/RA-1 £39.16.0. Carr. 9/-



Free Catalogue!



See these models and many more in our 1969 catalogue. Models for Stereo/Hi-Fi, Industry, Education and the Home Workshop. Heathkit — the world's largest selling selection of electronic kits and equipment.



To
DAYSTROM LTD., Dept. PW-8, GLOUCESTER. GL2-8EE.

Please send me FREE CATALOGUE

NAME

ADDRESS

Prices and specifications may be subject to change without prior notice



FANTASTICALLY POPULAR

★ **TAPE** ★

We offer you fully tensilized polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. **TRY ONE AND PROVE IT YOURSELF**

Standard Play		Long Play	
3in. 150ft.	2/8	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,350ft.	25/-
5in. 1,200ft.	16/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,400ft.	27/-	Quadruple Play	
		3in.	600ft. 8/6

Postages 1/- each.
Post Free less 5% on three reels.
Quantity and Trade enquiries invited.
NOTE: Large tape stocks at all branches.

TUBES Highest Quality—Compare Our Prices

Garr. & Ins.	12/6	6 Months	18 Months
14in.	..	£2.10.0	£3.10.0
17in. & 19in.	..	£2. 5.0	£4. 5.0
21in. & 23in.	..	£3.15.0	£5.15.0

SATISFACTION GUARANTEED
Most Mullard, Masco, Cosor, Emitron, Emicope, Brimar, Ferrant types processed in our own factory.
NOTE: ALL tube orders only to Portsmouth branch please.

NEW and SPECIAL Lines at the keenest prices

AM/FM STEREO MULTIPLEX RECEIVERS
18 transistors, 9 diodes, 1 variable diode, 2 Silicon Rectifiers, Push-pull Stereo Amplifiers, FM Stereo Separation 15dB, AM Medium Wave 180-550 Metres. Power output 10W R.M.S., 280/240V A/C Mains. Beautiful wooden plinth case—approximately 15"(w) x 6"(h) x 9"(d). Controls: Function Switch, Balance, Base/Treble Control, Volume, Tuning, Fine Tuning. Special purchase enables us to offer these superb machines of famous make at a ridiculously low price. Unrepeatable offer at a fraction of list price... only 28 GNS. POST FREE.

- SHARP** RD504 Mains Battery Tape Recorder, List 26 gns **28 gns**
- HITACHI** SW/MAR/MW/LW Marine D/P Recorders **27 gns**
- GARRARD** 1025 Changers with Stereo Cartridge **£8 10s**
- JASON** 12in. Diecast full range twin cone Speakers **£4 10s**
- AJAX** Mains/Battery, AM/FM larger Radio **12 gns**
- WELESHERE** AM/FM High Sensitivity Black Leather **7 gns**
- HITACHI** WH897E All-Wave, full size. Excellent Short Wave **13 gns**
- HI-FI** By Leak, Wharfedale, Goodmans, WR, Dulci, Arona, Teleton, etc., etc.

All items previously advertised available. Huge Hi-Fi and Component stocks at all branches. Please call and view without obligation.



RETAIL BRANCHES:
LONDON, 10 Tottenham Court Rd. (MUS 2639)
PORTSMOUTH, 350-352 Fretton Road (Tel. 22034)
SOUTHAMPTON, 72 East Street (Tel. 25851)
BRIGHTON, 6 Queen's Road (Tel. 23975)

MAIL ORDER WAREHOUSE:
Devonian Court, Park Crescent Place, Brighton. (Tel. 880722)

BARGAIN PARCELS

Including variable condensers, i.l. coils, loudspeaker plug/sockets, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer choke, rectifier, transistors at a small fraction of list value. Due to heavy demand we now pack them in several sizes—be amazed—try one now.

- 3 lbs. (post 3/-)
- 5 lbs. (post 5/-)
- 14 lbs. (post 9/-)

Aerial Wire: Coils of 25 yds. solid core, 2/3 plus 1/- P. & P.

Battery Eliminators for Transistor Supplies. 9v., 7 1/2v., 6v., 28/6 plus 2/6 P. & P.

Condensers: Large range available from 6d. each.

Coax Sockets: Flush, 6d. plus 6d. P. & P.

Cartridges: Acos GP67/2G, 14/9; BSR TC8H, 30/-; TC8M, 28/6; X1M Inserts, 22/6, etc.

Ear Pieces: 2-5µ/m or 3-5µ/m Mag., 2/6 plus 1/- P. & P. 2-5µ/m or 3-5µ/m Crystal, 5/6 plus 1/- P. & P.

High Impedance Horns: 1 1/2 to 4 1/2 volt, ideal for alarms, 3/6 plus 1/- P. & P.

Loudspeakers: Large range. 2in. 8 ohm, 7/6; 4in. 8 ohm, 12/6; 5in. 8 ohm, 16/6 plus 2/- P. & P.

Transistors: Full range, i.e. OC44, OC45, OC71, OC82, 2/6; OC35, 9/-; Fet.MPF103, 9/6.

Transformers: 12 volt battery charger, £12.6. 250-0-250 volt 60mA, 18/9; 0-250 with 6-3 volt, 19/6 plus 3/6 P. & P.

Relays: 12 volt suitable for car alarm, 21/-; 6 volt AC, 28/6; 240 volt AC, 27/6 plus 3/- P. & P.

Ex. Govt. Panel Meters: 0-SM/A, 17/6; 0-300V AC/DC, 25/6 plus 2/7 P. & P.

Many other items, please send S.A.E. for free price list.

BOTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.
54 EGLINTON STREET, GLASGOW, G.5. Tel. 041 80Uth 2904
Member of the Lander Group

NEW FROM ILIFFE

110 SEMI-CONDUCTOR PROJECTS

For the Home Constructor

R. M. MARSTON, technical author and design consultant

This is a book which will appeal equally to the electronics amateur and to the professional engineer. 110 different circuits are described and the operation of each one is explained in simple and precise terms. The main feature of the book is that it fulfils a long-awaited need for readable information on these devices.

- CONTENTS**
- 30 Silicon-Planar Transistor Projects
 - 15 Field-Effect Transistor Projects
 - 20 Uni-Junction Transistor Projects
 - 15 Silicon Controlled-Rectifier Projects
 - 30 Integrated-Circuit Projects
 - 124 pages 110 illustrations
 - 25s net case 26s 4d by post
 - 18s net student edition 19s 4d by post

ILIFFE BOOKS LTD
42 RUSSELL SQUARE
LONDON, W.C.1

4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 18 gns. P. & P. 8/6 extra.


INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/8.

Transistor TELEPHONE AMPLIFIER

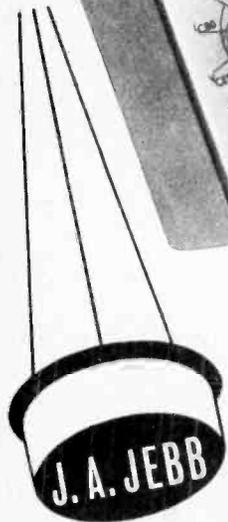Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 2/6. Full price refunded if not satisfied in 7 days.
WEST LONDON DIRECT SUPPLIES (P/W6)
168 KENSINGTON HIGH STREET, LONDON, W.8.



a comprehensive transistor tester

Last month the circuits for the transistor tester were given. This month the second part gives the constructional details and uses.

THE constant current supplies are the first things to be built and tested, as these are one of the most complicated parts of the apparatus. A meter is inserted in series with a resistor and a battery (preferably the battery to be used in the completed instrument), and the trimming resistor is adjusted to give approximately the right current. The resistor is now carefully shorted out, whereupon the current should not change.

Remember that the resistor used depends on the current range being tested, and that the electronics of the supply need about 6V to operate at all, so this fixes a maximum on resistor R_x depending on the battery voltage. For 30V, the resistor should be about $20k\Omega$ for 1mA, $2k\Omega$ for 10mA, 200Ω for 100mA. No overheating should occur, even on the 100mA range. Once this is completed, the switching circuitry is constructed.

The prototype was built in an Eddystone Box, type 6827P with the Veroboard circuit fastened to the lid by 2in. 6BA machine screws. The "function" switch and the current range switch were fixed to the lid first, and the Veroboard was positioned. 6BA machine screws were then passed through the Veroboard, secured with nuts, then further brass nuts were soldered to the frame of the switch. This secures the current switch to the board, and wiring can commence.

In view of the size and number of wafers required

for the function switch, this was built up around the circuit board with two wafers on one side and two on the other. The spacers are cut to accommodate the arrangement.

A battery carrier was made from four pieces of laminate board fixed to the inside of the box with 6BA screws and spring loaded to provide pressure on the ten penlight cells which provide the power. These cells will give 100mA for short periods with no trouble. The meter is a $100\mu A$ surplus type with a coil resistance of approximately $1k\Omega$.


Two transistor holders are provided for wire-ended transistors, one for JEDEC types and the other for European types. The difference is in the lead arrangements.

A holder for TO-3 type is fashioned from 4BA screws and miniature wander plug sockets. A 5-pin Philips plug is provided for connection via flying leads to transistors permanently fixed into equipment.

Diodes may be tested for forward and reverse resistance, and for type of semiconductor material by

inserting the diode into the collector and emitter sockets of one of the transistor holders, selecting I_{ceo} and 1mA on the switches (shunt the meter to 1mA). Operation of the polarity switch should give the result that the diode conducts one way, but not the other. Switching to V_{ce} should give the usual 0.2V or 0.7V reading depending on the diode construction.

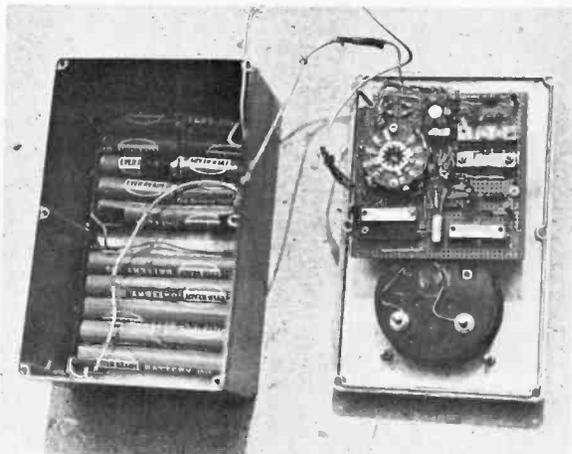The mode of operation of this device demands more complicated circuitry than is required for other types of tester, but it is felt that the tests offered are more



The interior of the transistor tester, note the batteries lain across the base and the way in which the Veroboard panel is sited.

valid and meaningful. Quite apart from this is the illustration of the techniques used in design of constant current sources, and also of the theory of transistor operation.

Operating instructions

1. Insert the device in the slot. The colours on the extension leads go: red = e black = b.

2. Having set switches to I_{ceo} and 1mA, select the polarity required, and shunt the meter. If the meter fails to register a reading, remove the shunt and repeat. If there is still no reading, replace the shunt, switch to 10mA, and press button. If there is no reading, remove the shunt. A perfect transistor will pass all tests.

3. (a) Set the switch to Vce (sat) and the other switch to 1mA. Press the button. Germanium may read 0.1V, silicon may read 0.5V.

(b) Set to 10mA. Germanium reads 0.25-0.4V, silicon reads 0.6-0.8V.

A short-circuited transistor always gives a low reading. An open-circuit

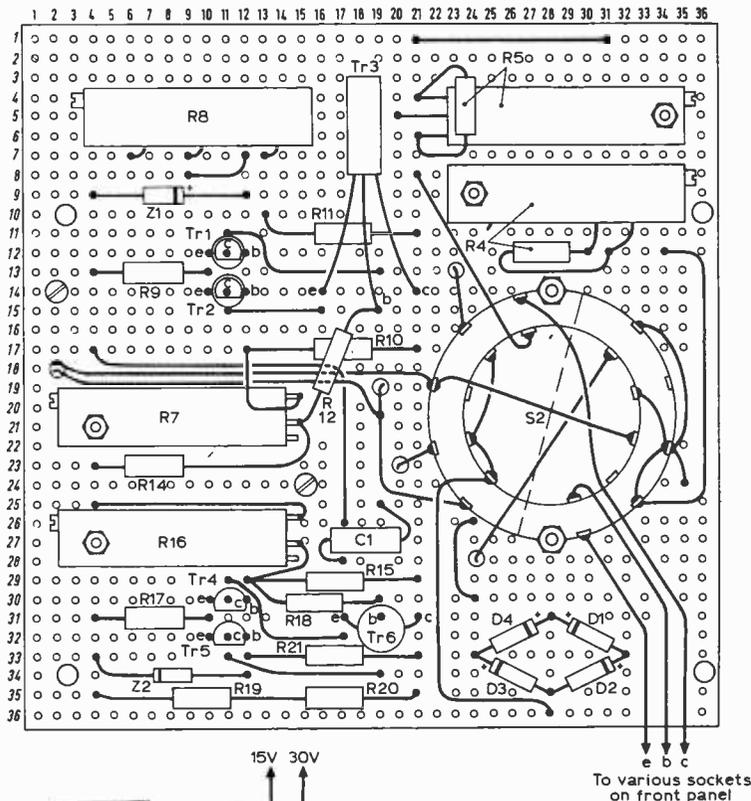


Fig. 1 (above): The location of the main components.

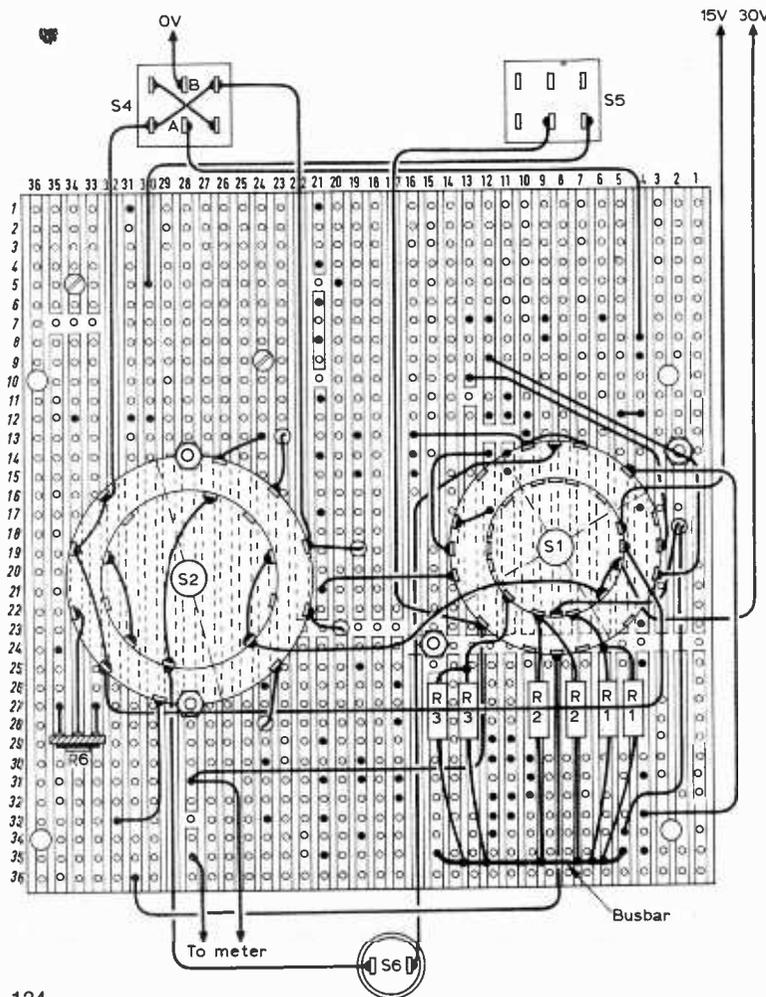


Fig. 2 (left): The copper side of the Veroboard showing the switch connections and the breaks in the laminate. Note that S6 was incorrectly labelled R5 in the circuit last month.

transistor always gives a very high reading.

4. Set to I_{cbo} , and use switches as for I_{ceo} . By noting which junction fails the leakage test (I_{cbo} tests collector/base, and I_{ceo} tests both) a fault may be traced to a particular junction, and the device used as a diode.

Testing Diodes

1. Set to I_{ceo} and 1mA, then shunt the meter. Insert the device or connect it to c and e terminals. Now switch on and operate the polarity switch. The diode will conduct one way and not the other. Remove the shunt and measure the leakage at 15V or 30V.

2. Set to Vce (sat) and 1mA. A germanium diode will give a reading 0.1-0.5V, depending on the current. A silicon diode will give 0.5-0.7, depending on the current.


PROTECT VALUABLE DEVICES



From thermal runaway or overheating. Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected; simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90°-190°F. or with the dial removed range setting is between 80 to 800°F. Price 10/-.


ROTISSERIE MOTOR

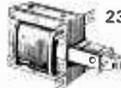Very powerful 7 r.p.m., operates from standard A.C. mains. 29/6, plus 3/6 P. & F.




230 VOLT SOLENOID
1 in. stroke. Size 2 1/2 in. x 2 in. x 1 1/2 in. 14/6, postage 2/9.

See in the Dark INFRA-RED BINOCULARS

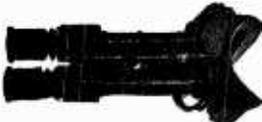

These infra-red binoculars when fed from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lenses for TV cameras—light cells, etc. (details supplied). The binocular form part of the Army night driving (Tabby) equipment. They are unused and believed to be in good working order but sold without a guarantee. Price £3.17.6, plus 10/- carr. and ins. Handbook 2/6.

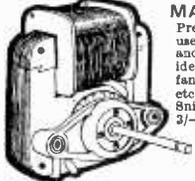

MAINS MOTOR

Precision made — as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.

16 RPM GEARED MOTOR

Made by Smith's Electrics, these are almost silent running, but are very powerful. They operate from normal to 240V. mains and the final shaft speed is 16 r.p.m. 15/-, Post & ins. 2/9.

MINIATURE WAFER SWITCHES



4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 38/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.




KETTLE ELEMENT

230/240V 1500 watt. Made by Best for kettles with 1 1/2 in. dia. hole including: Best, Besco, Chalfont, Davidson, Dimplex, Grafton, Hawkins, Jurymaid, Mirroware, Monogram, Pitco, Revco, Townen, Swan. Normally 32/6. Our price 15/- plus 2/6 post.

AC FAN

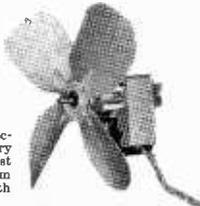Small but very powerful mains motor with 6 1/2 in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts from back or front with 4BA screws.



ELECTRIC CLOCK WITH 25 AMP. SWITCH

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Or available made up 29/6, plus 2/6 post.



HI FI BARGAIN

FULL FI 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address.
Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12in. over mounting lugs—Baffle hole 11in. diam.—Mounting holes 4, holes—1in. diam. on pitch circle 1 1/2 in. diam.—Overall height 5 1/2 in. A £6 speaker offered for only 23.9.6 plus 7/6 p. & p. Don't miss this offer.

THIS MONTH'S SNIP

G.E.C. 13A SOCKETS



Opportunity to re-equip your house or workshop, or if a contractor, to stock up for future jobs. We offer bakelite 13A sockets for flush or surface mounting made by the famous G.E.C., company and listed from 6/6 each. YOU CAN HAVE A BOX OF 12 flush type 24/-, surface type 29/6, post and ins. 4/6. (Gross or more carr., free).



PROCESS TIME CONTROLLER

Made by Smith's, motorised and mains driven, enables 15 A circuit to be started up to 18 hours in advance and to stay on for a period from 15 minutes to 3 hours. Totally enclosed in metal box with glass front and chrome surround. 49/6 plus 4/6 post and ins.

NICAD RECHARGEABLE BATTERIES



3-6V 500mA size 1 1/2 x 1 1/4 in. dia. type ref. DK2500 really powerful will deliver 1 amp for 1/2 hour. Regular price 32/6 our price 16/6 each. New and guaranteed. Other voltages available, single cell 1.2V 6/6. 5 cell 6V 29/6.

LAST CHANCE FOR THIS BARGAIN



CASSETTE LOADED DICTATING MACHINE

Battery operated and with all accessories. Really fantastic offer a British made £31 outfit for only 24.19.6, brilliantly designed for speed and efficiency—cassette takes normal spools, drops in and out for easy loading—all normal functions—accessories include: stethoscopic earpiece—crystal microphone has on/off switch—

FOR ONLY 99/6
telephone pick-up—DON'T MISS THIS UNREPEATABLE OFFER—**SEND TODAY £4.19.6 plus 7/6 post and insurance.** Foot switch 18/6 extra Spare Cassettes at 4/6 each, three for 10/-.

REPAIRABLE RADIOS

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2 in.—complete with soft leather zippered bag. Specification—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kcs. Sensitivity: 5 mv/m. Intermediate frequency: 465 Kcs, or 455 Kcs. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. These radios require attention. Circuit diagram is not available. Price only 17/6 each plus 2/9 post and insurance. 4 radios 23 post free.



VARYLITE

Will dim incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob 23.19.6.

INDICATOR LAMP

Panel mounting, consists of neon lamp in red Plastic lens with resistor in leads for mains operation. 2/6 each. 24/- dozen.

12V BLOWER

Heavy duty motor with centrifugal blower coupled to one end. Ideal for car heater. 12/6, plus 4/6 post.

TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six section, extends from 7 1/2 to 47in. Hoie in bottom for 6BA screw. 7/6.

MOVING COIL METER BARGAIN

Panel meters are always being needed and they are jolly costly when you have to buy them in a hurry—so you should take advantage of this offer: 2in. moving coil flush mounting meters only 9/6. These are actually R.F. meters and cost about £3 each but if you don't want them for R.F. then all you have to do is to remove the thermocouple and you will have a 2-3 mA. meter which you can make into almost anything by adding shunts or series resistor. New and unused.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (Class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

REED SWITCH

Suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simply glass encased switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 2/6 each, or 24/- dozen. Suitable magnets are 1/- each.

MINIATURE RELAY

American make—630 ohm coil 20-30 volt operation—2 pole change over 4/6 each, 48/- dozen.



SPRING COIL LEADS

as fitted to telephones, 4 core 2/6 each, 3 core 2/- each.

5A. 3 PIN SWITCH SOCKETS



An excellent opportunity to make that beach dis board you have needed or to stock up for future jobs. This month we offer 6 British made (Hircraft) bakelite flush mounting shuttered 5A switch sockets for only 10/- plus 3/6 post and insurance. (20 boxes post free.)

QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Havn. at bedside for tea, baby's food, etc. 18/6, post and insurance 1/6. 12v. car model also available.



HEADPHONES

Ex-W.D. unused and perfect, single with headband 4/6. Double with headband 9/6.
Multi Purpose Neox Test Unit. Robust, useful and instructive, tests insulation, capacity, continuity, resistor, volume controls, also acts as signal injector and L.T. fault finder, kit comprises neon indicator, 4-way wafer switch, ebouite tubes, resistors-condensers, terminals etc., with diagram, only 9/6, plus 2/- post and insurance.
Tuning Condenser, solid dielectric—0005mf. variable 2/6 each. 24/- dozen.
A.E.T. Fractional H.P. Motor. 200/250 v. 50/60 c.p.s. enclosed, continuous rating 1/40 h.p., ex. equipment. Perfect order, 19/6, plus 4/6.
Experimenting with ultra violet? Philips U.V. Lamp, 18/6; holder and control gear 18/6.
G.E.C. Black Light Tube for experiments and special lighting effects—40 watt 2ft. tubes only, 14/6 each; holders and control gear, 19/6, plus 4/6 post.
Clock Motor. 230v. 50 c.p.s. synchronous—self starting. 8/6.
Pentode Output Transformer. Standard size, 40-1, ex-equipment but O.K. 4/8 each, 48/- doz. Post paid.
E.H.T. Condenser. 0-1 mfd. 5 kV. 8/6 each.
Neon Mains Tester. 1/8 each, 12/- doz.
Flood Lamp Control. Our dim and full switch is ideal for controlling photo flood lamps; it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pairs or where circuit can be split exactly in half. Technically the switch is known as a double-pole change-over with off. Our price 4/6.
Sub-Miniature Silicon Diodes. General purpose type with gold-plated leads, 1/- each or 7/6 per dozen.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

ELECTRONICS (CROYDON) LTD
Dept PW 266 London Road, Croydon CR0-2TH
Also 102/3 Tamworth Road, Croydon

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets and Manufacturers' Manuals for most makes and types of Radios, Tape Recorders and Televisions.

Please complete order form below for your Service Sheet to be sent by return. To:

OAKFIELD ENTERPRISES

LIMITED

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1969 List now available at 2/- plus postage

If list is required indicate with X

From
Address

enclose remittance of
(and a stamped addressed envelope)
s.a.e. with enquiries please
MAIL ORDER ONLY (June PW)

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 37/6. 11 element, 45/-. 14 element, 52/6. 18 element, 60/-. Wall Mounting with Cranked Arm, 7 element, 80/-. 11 element, 87/-. 14 element, 75/-. 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6. 11 element, 55/-. 14 element, 62/-. 18 element, 70/-. Chimney Mounting Arrays, Complete, 7 element, 72/6. 11 element, 80/-. 14 element, 87/6. 18 element, 95/-. Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/-. State clearly channel number required on all orders.

BBC - ITV AERIALS




BBC (Band 1). Telescopic loft, 25/-. External S/D, 30/-. "H", 22.15.0.
ITV (Band 3). 3 element loft array, 30/-. 5 element, 40/-. 7 element, 50/-. Wall mounting, 3 element, 47/6. 5 element, 52/6. Combined BBC/ITV, Loft 1+3, 40/-. 1+5, 50/-. 1+7, 60/-. Wall mounting 1+3, 57/6; 1+5, 67/6; Chimney 1+3, 67/6; 1+5, 75/-.
VHF transistor preamps, 75/-.
COMBINED BBC1 - ITV - BBC2 AERIALS 1+3+9, 70/-. 1+5+9, 80/-. 1+5+14, 90/-. 1+7+14, 100/-. Loft mounting only. Special leaflet available.
F.M. (Band 2). Loft S/D, 15/-. "H", 32/6. 3 element, 55/-. External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/4. Outlet boxes, 5/-. Diplexer Crossover Boxes, 13/6. C.W.O. or C.O.D. P. & P. 6/-. Send 6d. stamps for illustrated lists.

Callers welcomed - open all day Saturday
K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE
LONDON ROAD, MITCHAM,
SURREY 01-648 4884

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

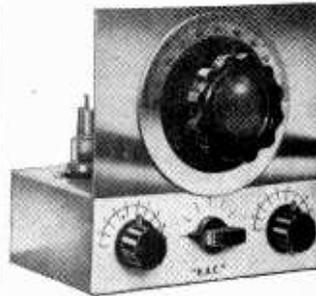

Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1969 RANGE

One-valve model "DX", complete kit—price 56/6 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-style drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP
Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY BASIC ELECTRONICS
Prices include Postage and Packing.

Signature
(If under 21 signature required of parent or guardian)

NAME
BLOCK LETTERS
FULL POSTAL ADDRESS

WHAT READERS SAY

"They certainly confirm everything your readers say about them and I am more than delighted with them. They will be of great value to me in my job as Hospital maintenance electrician." A. B., Birmingham.

"I am entirely satisfied with the books, they are everything you claim them to be." S.S., Cardiff.

"An extremely marvellous set of books." C.B., London.

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

AERIALS

A. J. WHITTAKER

PART 3—DIPOLE AERIALS

PARTS one and two in this series have described the basic theory of dipole aerials and the properties of vertical arrays when used for transmission of radio waves. This part will discuss effects of adding director and reflector elements to the basic dipole, and how to put the technique into practice by describing the construction of a v.h.f. loft aerial for receiving f.m. transmissions.

The Reflector Aerial

Consider Fig. 3.1, which is of a dipole "A" with the reflector "B" spaced $\frac{1}{4}$ wavelength behind. Assuming the dipole to be a transmitter aerial fed with r.f. energy, the action is as follows:

- (i) By the time that the voltage wave radiated from the main aerial "A" has reached the reflector "B" it has changed in phase by 90° ;
- (ii) The back e.m.f. in the reflector lags 180° on the cause producing it (i.e., the voltage radiated by "A");
- (iii) The reflector voltage, therefore, lags 270° behind the main aerial voltage;
- (iv) A phase lag of 270° is equivalent to a lead of 90° and so the reflector may be regarded as a directly energised aerial producing a radiated wave 90° or $\frac{1}{4}\lambda$ (λ wavelength lambda) in advance of the main aerial radiation;
- (v) As the reflector is a $\frac{1}{4}\lambda$ behind the main aerial, by the time the radiation therefrom has travelled through $\frac{1}{4}\lambda$ it is in phase with the main aerial and so augments the forward radiation;
- (vi) The polar diagram of radiation is a cardioid (Fig. 3.2):


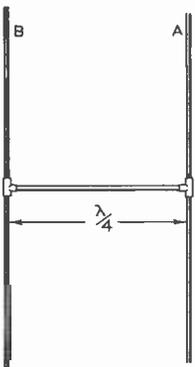


Fig. 3.1: A half-wave dipole with reflector.

Fig. 3.2: The radiation pattern for the aerial in Fig. 3.1.

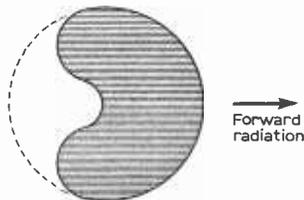

- (vii) A receiving aerial behaves in the same way but in reverse. The wavefront arriving at the main aerial induces a voltage into it. A $\frac{1}{4}\lambda$ after this, a voltage is induced into the reflector element. This sets up a current in it, and it re-radiates, the radiated wave lagging 180° on the cause producing it, implying that the

reflector radiation is again 270° lag on the main aerial voltage. As in the transmitter aerial, a lag of 270° is equivalent to a lead of 90° , and as the reflector element is $\frac{1}{4}\lambda$ behind the main aerial, its radiated field is in phase with it and so augments the forward pickup. The polar diagram is a cardioid and use may be made of this when siting the aerial to improve the signal-to-noise ratio.

Dipole with reflector and director

Figure 3.3 shows a dipole with director and reflector elements. The director augments the pickup in the dipole and adding several further improves the dipole gain. Owing to transformer action of directors and reflectors, however, this lowers the matching impedance to as little as 10 ohms.

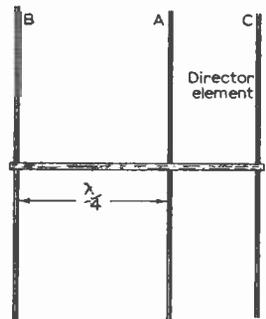


Fig. 3.3.

The Folded Dipole

The $\frac{1}{2}\lambda$ dipole is a balanced aerial requiring in practice a feeder wire of 75 ohms impedance to connect it to the receiver. As has just been mentioned, when reflectors and directors are coupled to it they lower the dipole input impedance, so to overcome this the dipole length is increased to a full wavelength and folded over. The feeder is now connected to the ends of the aerial which may be arranged, by adjustment of the reflector and director elements, to have an impedance of 75 ohms, thus avoiding the use of a matching element. The folded dipole behaves like two dipoles in parallel and an impedance step up of about 4/1 may be obtained.

The forward gain is seriously affected by the spacing of the reflector which is normally about $\frac{1}{4}\lambda$. A considerable change in the feed impedance also takes place when the spacing is varied. The reflector element is usually $\frac{1}{4}\lambda$ long but may be 0.475λ long for closer spacing than $\frac{1}{4}\lambda$.

Directors are usually about 0.43λ long and spaced about $\frac{1}{4}\lambda$ or less from the main dipole. If a number of directors are employed as in the Yagi array, making each progressively shorter in the direction of the transmitter broadens the bandwidth. For an aerial of 18 elements including the reflector and main dipole, the forward gain may be 14dB higher than a single dipole (i.e. about 4.5/1). The gain of a Yagi with one director and reflector is typically 8dB.

Construction of a practical v.h.f. aerial

A 3 element aerial for the reception of v.h.f. f.m.

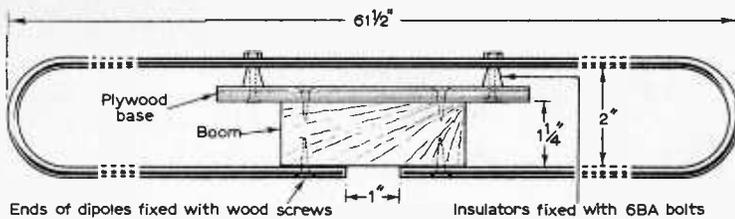


Fig. 3.4: The folded dipole.

Fig. 3.6: The complete aerial.


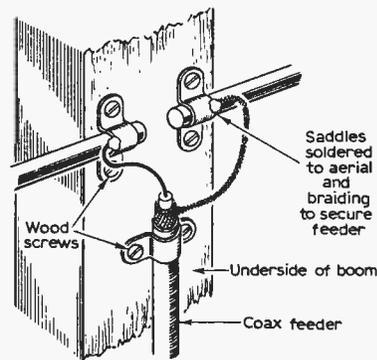
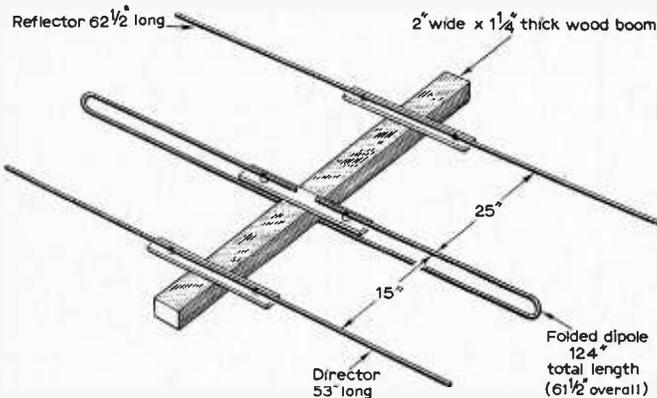


Fig. 3.5.

Fig. 3.7.

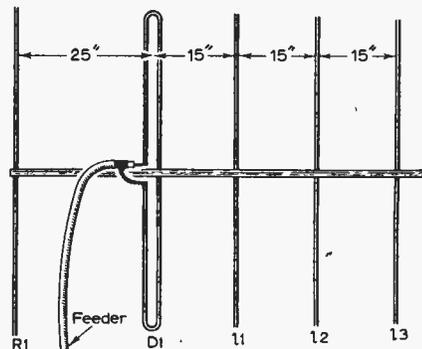

broadcasts, suitable for use in a loft, will be described.

The radiating element is a folded dipole, bent to the shape shown in Fig. 3.4. It is made from $\frac{3}{8}$ in. diameter copper tube, which can be bent by plugging the ends, filling it with sand, and folding it to the desired radius. The sand can then be emptied, and the ends flattened to seal the tube and provide a suitable surface for the terminal screws. All the dimensions are given in the sketch, and if these are carefully adhered to the aerial will tune to the mid-band frequency of 90Mc/s.

The reflector rod should be cut to $\frac{1}{2}\lambda$, which is about 62 $\frac{1}{2}$ in. This figure is calculated from the formula:

$$\frac{1}{2}\lambda \text{ element length (ft.)} = \frac{468}{\text{freq. (Mc/s)}}$$

This allows for the difference in velocity of electromagnetic waves in copper wire to the velocity in free space.

The director should be cut to a length of 0.43λ , which is about 54in. The ends of the reflector and director should be sealed off, and if the aerial is to be used out of doors, all elements should be painted.

Having prepared the aerial elements as above, they must be assembled on the wooden boom, which is cut from 2 x 1 $\frac{1}{4}$ in. timber to a length of 45in. The first operation is to mark off the centre of the boom at 22.5in. from one end, and attach to it, at right angles, a strip of plywood, 6 x 2 x $\frac{1}{4}$ in. After screwing it on, two holes should be drilled about 1in. from each end of the plywood to accommodate a plastic insulator pillar. These pillars are fastened to the folded dipole. The dipole can then be mounted, the ends to which the feeder is attached being fastened to the underside of the boom by two saddles fixed by woodscrews, as shown in Fig. 3.5.

In a similar fashion to the driven element, the


director is attached by cutting a piece of plywood 6 x 2 x $\frac{1}{4}$ in., and drilling a 6BA clearance hole, 1in. from each end to accommodate the insulated mounting pillars. The plywood should be screwed to the boom at a centre-to-centre distance of 15.5in. from the dipole, and the rod can then be screwed to the insulators. For the reflector repeat this operation, but space it from the dipole a distance of 25in.

The director and reflector rods should now be drilled with a 6BA clearance hole at a position 2in. either side of the centre line of the rod.

These holes are to accommodate the fixing screws for the insulating pillars to which these rods are fixed. The sketch shows the completed aerial, Fig. 3.6.

The insulated pillars may be made from Perspex, Paxolin, or any insulating material usually found in the workshop odds-and-ends box. The dimensions are given in the sketch.

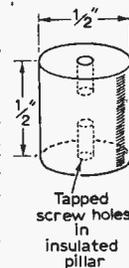The wooden boom was purposely made about 5in. longer than necessary to allow for possible adjustment of the reflector or director in the interests of getting the optimum matching conditions for the feeder.




Reception of VHF FM Stereo

For the reception of stereo broadcasts it is desirable to have an aerial system with more forward gain than the simple aerial described above. This may be quite simply done by adding more directors to the array, as shown in Fig. 3.7 which has two more director elements. These are cut progressively shorter in the direction of the transmitter to broaden the bandwidth. The boom will have to be lengthened to 75 in. to accommodate these extra directors.

TO BE CONTINUED

THE CLASSIC

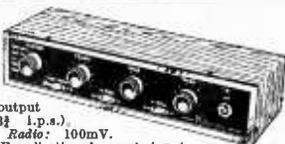Controls: Selector switch Tape speed equalisation switch (3½ and 7½ l.p.s.). Volume, Treble, Bass, 2 position scratch filter and 2 position rumble filter.



Specifications: Sensitivity for 10 watt output at 1KHz. *Tape head:* 3mV (at 3½ l.p.s.). Volume, Treble, Bass, 2 position scratch filter and 2 position rumble filter. *Mag. P.U.:* 2mV. *Cer. P.U.:* 80mV. *Radio:* 100mV. *Aux.:* 100mV. *Tape/Rec. output:* 100mV. Equalisation for each input is correct to within ± 2dB (R.I.A.A.) from 20Hz to 20KHz. *Tone control range:* Bass ± 13dB at 80 Hz. Treble ± 14dB at 15KHz. *Total distortion:* (for 10 watt output) < 1.5%. *Signal noise:* < -60dB. A.C. mains 200-250V. Built and Tested. Size 12½in. long, 4½in. deep, 2½in. high. Teak finished case. Price 8½ gns. + 7/6 p. & p.

DUETTO INTEGRATED TRANSISTOR STEREO AMPLIFIER

SPECIFICATION R.M.S. Power Output: 3 watts per channel into 10 ohms speakers. **INPUT SENSITIVITY:** Suitable for medium or high output crystal cartridges and tuners. Crosstalk better than 80mA at 1Kc/s. **CONTROLS:** 4-position selector switch (2 position mono and 2 position stereo). Dual ganged volume control. **TONE CONTROL:** Treble lift and cut. Separate on/off switch. A balance preset control is also incorporated inside amplifier, which is set to provide equal gain on both channels. The unit is fuse protected and offered in an elegantly styled teak finished case, size 10½" x 4½" x 2½" with contrasting front panel. Built and tested. Price 9 gns. plus 7/6 P. & P.

2½ watt ALL TRANSISTOR AMPLIFIER

AC mains 240V. Size 7" x 4½" x 1½". Frequency response 100 c/s—10 Kc/s Semi conductors, two OC 75's two AC 128's and two stabilizers AA129. Tone and volume controls on flying leads. £2.10.0 plus P. & P. 3/6. Suitable 8" x 5" 10,000 line high flux speaker, 18/6 plus 2/- P. & P.



50 WATT AMPLIFIER A.C. MAINS 200-250V

An extremely reliable general purpose valve amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organs, etc. Separate bass and treble controls. Output impedance 3, 8 and 15 ohms.

Price 27 gns. Plus 20/- p. & p.

X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: **Power Output** (into 3 ohms speaker) 10 watts. **Sensitivity** (for rated output): 1mV into 3K ohms (0-33 microamp). **Total Distortion** at 1KHz. at 5 watts 0-35% at rated output 1-5%. **Frequency Response:** Minus 3dB points 20Hz and 40KHz. **Speaker:** 3-4 ohms (3-15 ohms may be used). **Supply voltage:** 24V d.c. at 800mA (6-24V may be used).

Control assembly: including resistors and capacitors.

1. Volume: PRICE 5/-.
2. Treble: PRICE 5/-.
3. Comprehensive bass and treble: PRICE 10/-.

The above 3 items can be purchased for use with the X101.

Power Supplies for the X101:

P101 M (for mono) 35/- plus 4/6 p. & p.

P101 S (for stereo) 42/6 plus 4/6 p. & p.



Price 49/6 plus 2/6 p. & p.

THE RELIANT 10W SOLID-STATE HIGH QUALITY AMPLIFIER

SPECIFICATIONS

Output—10 watts

Inputs—1. -xrtl mic 10mV

2. -gram/radio 250mV

Frequency Response—(with tone controls central) Minus 3dB points are 20Hz and 40KHz.

Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220-250V. A.C. Size of chassis—10½" x 4½" x 2½".


A.C. Mains, 200-250V. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control for gram and mike. Built and tested. 8" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P.

Reliant Mk. I. 5½ gns. plus 7/6 p. & p.

As above less teak case.

Reliant Mark II. 6½ gns. plus 7/6 p. & p.

In teak finished case.

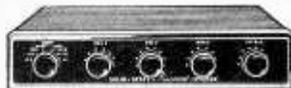

THE VISCOUNT

Integrated High Fidelity Transistor Stereo Amplifier

SPECIFICATIONS: Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monoral). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U., Tuner, Tape and Tape Rec. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency response: 40Hz-20KHz ± 2dB. Tone controls: (Baxandall type), separate bass and treble controls. Treble 13dB lift and cut at 15KHz. Bass 15dB lift and 25dB cut at 80Hz. Volume controls: Separate for each channel. A.C. Mains input: 200-240v. 50-60Hz. Size 12½ x 6 x 2½in. in teak-finished case. Built and tested.

PRICE 13½ Gns. Postage & Packing 7/6 extra.

Goods not despatched outside U.K. Terms C.W.O. All enquiries Stamped Addressed Envelope

RADIO & TV COMPONENTS (Acton) LTD

21c High Street, Acton, London, W.3.

All orders by post to our Acton address

323 Edgware Road, London, W.2.

THE DORSET (600mW output)



7-transistor fully tunable M.W.-L.W. superhet portable —with baby alarm facility. Set of parts. The latest modularised and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

MAINS POWER PACK KIT: 9/6 extra.

PRICE £5.5.0 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.

THE ELEGANT SEVEN MK. III (350mW output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price £4.9.6 plus 7/6 p. & p.

Circuit 2/6 FREE WITH PARTS.



CYLDON 2 TRANSISTOR U.H.F. TUNER

Brand new. Complete with circuit diagram.

£2.10.0 plus 1/- p. & p.

THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross over network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20Kc/s. Size 13½ x 8½ x 4½ inches. By famous manufacturer. List Price 47/. Our price 74/6 plus 5/- P. & P.

Similar speaker to the above without tweeters in 3 and 15 ohm 44/6 plus 5/- P. & P.

B.S.R. TD-2 TAPE DECK

This tape deck takes 6½in. spools complete with two-track heads. Size 13½in. long by 8½in. wide. £8.19.6 plus 7/6 p. & p.

RECORD PLAYER SNIP A.C. MAINS 240V

The "Princess" 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and insurance 7/6 extra.



CAR TRANSISTOR IGNITION SYSTEM

(by famous manufacturer)

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers etc.). PRICE £4.19.6. (post and packing 5/- extra).



POCKET MULTI-METER

Size 3½ x 2½ x 1½in. Meter size 2½ x 1½in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000 D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test prods, battery and full instructions, 42/6. P. & P. 3/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 18/- to every purchaser of the Pocket Multi-Meter.



FIRST QUALITY P.V.C. TAPE

5½" Std.	850ft.	11/6	5" L.P.	850ft.	12/-
7" Std.	1200ft.	13/-	3" T.P.	600ft.	12/-
3" L.P.	240ft.	5/6	5" T.P.	1800ft.	27/-
5½" L.P.	1200ft.	13/-	5½" T.P.	2400ft.	34/-
7" L.P.	1800ft.	20/-	7" T.P.	3600ft.	44/-
5½" D.P.	1800ft.	20/-	4" T.P.	900ft.	16/6

P. & P. on each 1/8.


MOTEK

3 Speed 2 track Tape Deck complete with heads, takes 7in. spool.

Incorporating 3 motors.

A.C. mains, 240 volts, listed at £21.0.0.

Our Price £9.19.6, plus 10/- P. & P.

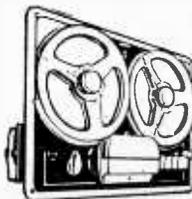


Bargain—Car Radios. Our Price 9 gns. Negative or positive earth (switched) fully transistorised (12v) medium and long waves. Speaker and fitting kit supplied at no extra cost. P/P 5/-.

DULCI HI-FI UNITS

The Dulci range of tuners and amplifiers offer exceptional quality at a sensible price.
Amplifiers: 207 and 207M. Tuners: FMT7 and FMT7s. SEND NOW FOR FULL DETAILS

Sonotone 9TA and 9TA/H.C. Diamond Cartridge brand new, boxed in manufacturers' carton 49/6 + 2/6 p/p. Acos GP 91-1 and GP 91-3 stereo compatible cartridges, new in sealed manufacturers' cartons 22/6 + 2/6 p/p.

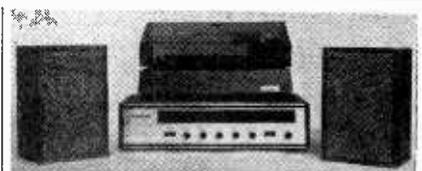TRIO Stereo Moving Magnet Cartridge Model AD76K. Diamond Stereo LP Stylus. Frequency response 20-20,000 c/s output. 7mv tracking pressure 2 grammes ± 0.5 gm. Fully guaranteed. Price 85/- p/p free.



The greatest HI-FI Budget system to-day—can't be beaten—price or quality anywhere—look at these great features—then compare.

Teleton F2000 tuner amp. AM-FM with multiplex decoder and A.F.C.—2 x 5w channels R.M.S. Bass Volume Treble Balance controls, a truly outstanding unit
Garrard SP 25 Mk II Transcription deck

£	s	d
43	1	0
15	11	11

Teleton SA 1003 matching speaker enclosures
Sonotone 9 TA Diamond Cartridge
Plinth and Perspex cover

9	5	0
4	2	0
7	0	0
£78 19 11		

Exclusively offered by WALDON at the remarkably low price of 63 gns.

BASF TAPE 25 % OFF

5" 600ft. 14/- 900ft. 19/- 1200ft. 30/-
5 1/2" 900ft. 19/- 1200ft. 24/- 1800ft. 39/-
7" 1200ft. 24/- 1800ft. 35/- 2400ft. 57/-

P. & P. 2/- per reel.—over £5 FREE

Bargain—Changer decks at lowest prices ever

GARRARD
Beautiful teak 1025 £8.9.0.
plinth and perspex 2025 £8.10.6.
cover to suit AT60 Mk. II £12.19.6.
these units SP25 Mk. II £12.9.0.
5 Gns. P. & P. Free 3500 with Son 9TA.HC diam. cart. £16.19.6.
Add 10/- p/p for each Garrard unit

HI-FI SPEAKER K12TC—12in. 12 watt

Offers an exceptionally smooth and extended response, with very low level of distortion from the specially designed twin diaphragms.
Frequency Response: 30-16,000Hz.
Impedance: 15-160Hm.

OUR SPECIAL PRICE 97/6
PLUS P. & P. 6/6

SPEAKER ENCLOSURES

Type: INFINITE BAFFLE
Model 8: 8" plus 3" tweeter
Model 13: 13" x 8" EMI
Both £4.19.6 each
Model 1012: 10" or 12" plus 4" tweeter
£7.19.6
All enclosures are in oiled teak, fully built.
Please add 8/- p. & p. on each enclosure

Bargain—Speakers, Hi-Fi—The Baker Selhurst Stalwart. 12in. round, 15 watt rating, 12,000 lines gauss, 15 ohms, response 45-13,000c/s. Bass resonance 40-50c/s, solid aluminium chassis. Our price £5.8.6.

p/p 6/6

Bargain — Speakers, Hi-Fi — The Baker Selhurst Guitar Group 25, 12in. round, 25 watt rating, 12,000 gauss, 15 ohms, response 30-10,000 c/s, solid aluminium chassis, heavy duty cone. Our price £5.8.6.

p/p 6/6

E.M.I. HI-FI SPEAKERS

SET 450: 13 x 8 with two built-in tweeters and cross-over unit. Our Price 99/6. 3 or 15 ohm, 10w, 40-13,000 Hz.
SET 850: 6" bass plus 3 1/2" tweeter and cross-over unit. 8 ohm, 10w, 65-20,000 Hz. 79/6.
SET 250: 5" heavy duty bass plus 3" tweeter and cross-over unit. 8 ohm, 6w, 80-20,000 Hz. 63/-.
Add 3/6 p/p for each speaker set

WALDON ELECTRONICS 707 Blackburn Road, Bolton, Lancs. Bolton 54280.



Fabulous Value


Fantastic Bargain Offer

STEREOPHONIC KUBA "ROYAL" RADIOGRAM

This radiogram chassis is offered complete with carefully matched loudspeaker system, two 10in. speakers, two 4in. Cone Tweeters and latest BSR UA70 Mono/Stereo record changer—a complete quality stereophonic radiogram at half normal price.
4 wavebands—AM/FM—8 piano keys control. 8 watt push-pull output per channel—frequency response 30-20,000 cycles. EASY TO INSTALL, NO TECHNICAL KNOWLEDGE REQUIRED
ONLY £79.19.6.

H.P. terms available. Deposit £26.13.2 and 24 monthly payments of 55/7 (total H.P. £93.7.2). Send £27.10.8 today, or write for free leaflet.

KUBA "IMPERIAL 666" STEREOPHONIC HI-FI RADIOGRAM CHASSIS—complete with two 10in. x 6in. speakers and the latest BSR Mono/Stereo record changer—a complete radiogram at half normal price. 4 Waveband AM/FM chassis with the very latest printed circuitry—7 push button control, 12 watts total output. Provision for stereo decoder. Only 49 1/2 Gns. plus P. & P. 17/6. EASILY FITTED. NO TECHNICAL KNOWLEDGE NECESSARY. H.P. available £17.6.6 deposit plus 24 monthly payments 36/2 (total H.P. £60.14.6). Send £18.4.0 today.

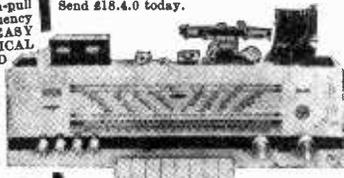

CALLERS WELCOME

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name
Address

LEWIS radio

100 CHASE SIDE, SOUTHGATE, Dept. P869A, LONDON, N14 TELEPHONE 01-886 3788/9086



Radio Communication Handbook

832 pages of everything in the science of radio communication. The Handbook's British origin ensures easy availability of components. The standard work in its field. 69s post paid

Amateur Radio Circuits Book

Dozens of clear, concise circuit suggestions with the basic constructional details. 120 spiral bound pages lie flat when open for convenience. 11s 6d post paid

Amateur Radio Techniques

All the good ideas are here. An anthology of the famous "Technical Topics" column from RADIO COMMUNICATION. Fascinating reading and an invaluable information source. 13s 6d post paid

All these and many more, plus free details of the **RADIO SOCIETY of GREAT BRITAIN** from 35 DOUGHTY STREET, LONDON, WC1

POST THIS COUPON NOW!

practically wireless

commentary by **HENRY**

HOW would you feel if the Time and Motion Study man came into your den with his stopwatch? More than a little aggrieved, I'll warrant. Perhaps a bit guilty about the clutter under the bench that you meant to clear up—was it last Michaelmas? Uneasily aware that reaching across for the soldering iron and sending the precariously perched valve rack toppling would not meet with his approval. Nervous about the habitual way one tips out the cocoa tin of hardware to search for a 6BA washer.

My own den, since Mrs Henry laid down the law about trailing wires and fire hazards, has expanded into the loft—where the aforesaid forewoman's incipient vertigo guarantees privacy. The rear bedroom, vacant since the Henry fledglings left the nest, is now a hi-fi centre, with equipment scattered around fairly neatly, and wires tucked away out of sight. Come to think of it, why did they fly away?

But I would hate to see Mr Slide-rule sniffing superciliously around my loft. I remember we had to saw laterally across the old washstand to get it through the hatch; its reassembly is as complete as need be, but technically imprecise. Have you ever tried to re-assemble a washstand that seems to be one of the reasons



The Time and Motion man with his stopwatch.

for Queen Victoria's lack of amusement? The fact that its slate top provides as good a base for turntable testing as one could hope to devise, and the handy little pot-sized cupboard whose door was not designed to shut, is just right for an easy cable entry, has nothing to do with efficiency or design. I feel sure Mr. David Michaelis would disapprove.

This gentleman is not a blood brother of our erudite contributor of the same name but a leading light in the TMS world. And the reason he finds himself immortalised by Henry is a trenchant article by Ann Batt of the *Daily Mail*, in which Mr. M. was quoted on the subject of women and housework.

"Would a man do six little batches of washing up in half an hour?" he asks. Not if he is wise enough to break the odd dish now and again, when asked. But that is not his point. He asserts that women "... toil on making a virtue out of hard slog by doing things the traditional way your mothers did instead of asking yourselves 'is there a better way?' There probably is; you just don't think".

Much of the way women work comes from learning in the manner that industry terms "Sitting by Nelly". That is, picking up the job as you go along, without specific training.

Be honest—when did you last remember to give that soldering iron bit a twitch, to make it easier to free when the time comes for replacement? How many pieces of your equipment are operating on supply lines stuffed into a socket and pinioned by the blades of another plug? Come to that, how much gear have you got multi-plugged to that single socket? Don't look at me—I'm only asking the questions.

My own home workshop would horrify Mr. Michaelis.



We had to saw across the old washstand.

Darn it, the place scares me at times. But even in our "official" workshop the den atmosphere persists and Nelly is lurking in every cluttered corner. One of our chaps still talks about "Anoids and Cathoids" because that was the way his mentor talked during his far-off apprentice days. Another has jumped gleefully for a recent exposition of transistor theory because he never really believed in "holes" anyway. Yet he manages to cope quite ably with repairs to semiconductor equipment.

And what about Henry's legacy from Nelly? Well, I think it must be a harkback to the Army days, when to leave a tool unattended was to invite its disappearance.

Perhaps we ought to ask Mr. Michaelis to take a long look at our dens. In one respect I know he is right. "A form of Parkinson's Law operates," he says, talking about working surfaces. "... your accumulated clutter responds to the stretchable space made available for it."

He could have been talking about the slate top of that old washstand. Maybe I can get Nelly to come and clear it up—one day!

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times GMT
Frequencies in kc/s

THE BROADCAST BANDS by CHRISTOPHER DANPURE

TIME certainly seems to fly when conditions are good, especially during the spring season when the h.f. bands are open until late evening. Here's a good DX-tip: have a listen to *R. Australia* on 15,240 from about 0600-0800. Power is only 10kW from the Shepperton transmitter. I always get good results, some days even better than the 100kW transmitter on 11,710.

During the past year when I have been writing this column I sometimes wonder what you readers think of the column, especially as to how useful you find the propagation predictions which are published each month. Do you find them useful? Let's have your comments please over this one, and any other suggestions you may have to help other people in their DX-ing and SWL-ing. Talking of SWL-ing and DX-ing, during the past few years there have been confusion in the use of these words. The translation which I believe is correct is that SWL-ing is listening generally to shortwave stations from all over the world, low and high power, but mainly to listen to specific programmes and taking interest in various countries, generally listening to shortwave radio to learn about the world and for entertainment. Now the DX-er or DX-ing is literally translated as "Distance listening", that is listening to stations outside the continent he resides in unless there are low power stations in his own continent, but generally listening to low power stations on the shortwave bands, and writing out reports to get as many QSL cards as possible. So how do you class yourself as a SWL or DX-er?

Over the past year I have tried to cater for both SWLs with new station schedules and for the DX-ers with short tips. But I seem to be providing more for the SWLs than the QSL card hunters, so come on you good DX-ers let's have those "heard and noted" lists of those stations you have heard in Latin America, Africa, Asia and Pacific Area like *R. New Zealand* and *R. Cordac*. I'll look forward to receiving your logs.

In the October 1968 column I listed all the programmes of interest to SWLs and DX-ers, so if you haven't got a copy of this list send 3s. postal order plus postage and ask for a copy of the October 1968 PRACTICAL WIRELESS. Now to bring this list of programmes up to date here are some alterations:

Sunday—DX-ing Worldwide *R. New York Worldwide* 1930-2000 on 21, 17 and 15Mc/s.

Monday—Delete all details for the *Deutsche Welle* DX-Programme.

Tuesday—Add *Deutsche Welle* DX-Programme every second Tuesday from 0810-0840, on 9,650 and 6,075; 1410-1440 on 11,765; 1710-1740 on 9,655 and 6,075.

Thursday—Add 0730-0745 *Trans World Radio* "DX-Special" on 7,295.

Friday—*Trans World Radio* "DX-Special" from Bonaire runs from 2055-2110.

Saturday—Delete details for *Trans World Radio* schedule.

Now here are some listening tips on new schedules commenced on 4th May.

EUROPE

Holland: *R. Nederland* is now operating on full schedule and has daily 80-minute transmissions in English. From 0630-0750 on 11,730 via Bonaire; 0800-0920 on 9,715 via Bonaire; 0930-1050 weekdays 21,480, 17,810 via Lopik; Sundays 9,715 and 5,980 via Lopik; 1400-1520 on 21,480, 17,810 and 6,020; 1830-1950 on 21,570 and 11,730 via Lopik; 15,220 via Bonaire. 2000-2120 on 9,715, 6,085 and 6,020 via Lopik; 2130-2250 weekdays on 15,425, 11,730 via Lopik; 0200-0320 on 11,730 via Bonaire; 0500-0620 on 11,730 and 9,715 via Bonaire. On Sundays the Happy Station programme is transmitted. The Spanish Happy Station programme is transmitted on Sundays at 2130-2250 on 9,715, 6,085 and 6,020 via Lopik and 17,810 via Bonaire; 2300-0020 on 15,425 and 6,020 via Lopik and 15,320 via Bonaire. 0030-0150 on 6,085 via Bonaire, 0200-0320 on 9,590 via Bonaire; 0330-0450 via Bonaire on 11,730.

Norway: *R. Norway* is now on their summer schedule from 0700-0830 on 25,730, 21,730, 21,655, 15,345 and 15,175; 1100-1230 on 25,730, 21,730, 21,655, 17,825 and 7,210; 1300-1430 on 25,730, 21,730, 21,670, 21,655, and 17,825; 1500-1630 on 25,730, 21,730, 21,670, 21,655 and 17,825; 1700-1830 same as 1500-1630; 1900-2030 on 25,730, 21,730, 21,670, 21,655 and 15,175; 2100-2230 on 25,730, 21,730, 21,655, 17,825 and 15,345; 2300-0030 on 21,655, 17,825, 15,345 and 15,175; 0100-0230 on 11,860, 11,850 and 11,735; 0300-0430 same as at 0100-0230.

AFRICA

South Africa: *Radio R.S.A.* has now altered the timings of some 50-minute transmissions. Now they run 0800-0850 on 21,535 and 17,825; 1000-1050 on 21,535, 17,825 and 15,220; 1600-1650 on 9,525 and 7,270; 1700-1750 on 21,535, 15,220, 9,525 and 7,270. The UK and Eire English transmission now runs from 1800-1850 on 21,500 and 17,795; 2100-2150 on 15,360 and 11,900. To North America from 2326-0320 on 9,705, 6,075 and 5,980. The general service to Africa now runs from 1100-1450 on 21,535, 17,805, 15,220 and 11,900.

Well that's about it for this month. Deadline for those DX-tips is 17th May. So until next month good listening and 73s.

ORGAN BUILDERS! SILICON N.P.N. TRANSISTORS TESTED AND APPROVED BY DESIGNER FOR USE IN "PRACTICAL ELECTRONICS" ORGAN CIRCUIT—1/6 each or 25 per 100.

LATEST LIST OF TRANSISTOR STOCK. ALL BRAND NEW AND TO MANUFACTURERS SPECIFICATIONS

NKT11	9/3	NKT402	19/3	BFX86	6/6	2N2221	8/6
NKT12	7/3	NKT403	16/-	BFX87	9/-	2N2221A	10/-
NKT17	5/-	NKT404	13/3	BFX88	7/3	2N2222	10/3
NKT73	5/-	NKT405	14/3	BFY50	5/-	2N2222A	19/6
NKT124	8/6	NKT406	13/3	BFY51	4/6	2N2287	9/3
NKT125	5/9	NKT420	40/-	BFY52	5/-	2N2388	4/6
NKT126	5/-	NKT451	13/3	BFY53	4/6	2N2389	4/6
NKT135	5/-	NKT452	12/6	BFY90	29/6	2N2398A	5/-
NKT137	6/6	NKT453	9/-	BSX19	4/6	2N2483	8/6
NKT210	5/9	NKT633F	6/6	BSX20	4/6	2N2484	10/9
NKT211	5/-	NKT613F	7/3	BSX60	16/6	2N2220A	10/9
NKT212	5/-	NKT674F	5/-	BSX81	10/-	2N2904	10/9
NKT213	6/6	NKT677F	4/6	BSY96A	3/9	2N2904A	12/-
NKT214	4/6	NKT713	5/-	2N696	5/-	2N2905	15/6
NKT215	5/-	NKT717	9/-	2N697	5/-	2N2906A	13/-
NKT216	10/-	NKT734	5/-	2N706	3/-	2N2906	13/6
NKT217	10/9	NKT736	6/6	2N706A	3/-	2N2908A	13/6
NKT219	5/-	NKT773	4/6	2N708	4/6	2N2907	14/-
NKT223	5/9	NKT781	5/-	2N709	11/6	2N2907A	20/9
NKT224	4/6	NKT10419	5/-	2N914	5/-	2N3053	5/9
NKT225	4/6	NKT10519	5/9	2N918	11/6	2N3055	20/9
NKT229	5/-	NKT10339	6/6	2N929	7/3	2C345	4/-
NKT237	7/3	NKT10439	7/3	2N930	9/-	2C371	4/-
NKT238	4/6	NKT12329	11/6	2N1131	8/6	2C378	4/-
NKT239	5/-	NKT12429	14/-	2N1132	10/-	OC22	10/-
NKT240	4/6	NKT13329	5/-	2N1302	4/6	OC204	6/-
NKT241	5/-	NKT13429	5/-	2N1303	4/6	OC44	6/-
NKT242	3/-	NKT33219	22/3	2N1304	5/-	OC45	6/-
NKT243	14/-	NKT16229	11/6	2N1305	5/-	ASZ17	10/-
NKT244	3/-	NKT20329	12/6	2N1306	6/6		
NKT245	3/9	NKT20339	8/6	2N1307	6/6		
NKT261	3/9	BC107	4/6	2N1308	8/6		
NKT262	3/9	BC108	3/-	2N1309	8/6		
NKT264	3/9	BC109	4/6	2N1613	5/9		
NKT271	3/9	BCY55	70/-	2N1711	6/6		
NKT272	3/9	BCY70	5/-	2N1833	12/6		
NKT274	3/9	BCY71	9/3	2N2217	7/3	25/49	5%
NKT275	3/9	BCY72	4/6	2N2217A	15/6	50/98	10%
NKT281	5/-	BDY20	22/3	2N2218	8/6	100/299	15%
NKT302	16/6	BFX28	11/6	2N2218A	10/-	300/999	20%
NKT304	12/3	BFX30	13/3	2N2219	13/3	1,000	25%
NKT351	11/6	BFX84	6/6	2N2218A	12/6		
NKT401	18/-	BFX85	8/-	2N2220	7/3	all one type	

UNMARKED TRANSISTORS (tested) similar to: 2N753 1/6, BSY26 1/6, BSX5 1/6, OC44 1/6, OC71 1/-, OC72 1/-, LIGHT SENSITIVE TRANSISTORS similar to: OCP71 2/- each, ORP12 CADMIUM SULPHIDE LIGHT-SENSITIVE RESISTORS 9/- each.

GIANT-SIZE SELENIUM SOLAR CELLS—PRODUCE UP TO 6mA AT 6 VOLTS FROM DAYLIGHT! 67mm. diameter 10/- each. 50mm. x 37mm., 2 for 10/-.

MULLARD POLYESTER CAPACITORS FAR BELOW COST PRICE! 0.001µF 400V 3d., 0.0015µF 400V 3d., 0.0018µF 400V 3d., 0.0022µF 400V 3d., 0.01µF 400V 3d., 0.15µF 160V 8d., 0.22µF 160V 8d., 0.27µF 160V 8d., 1µF 125V 1/-.

RECORD PLAYER CARTRIDGES. COMPLETE WITH NEEDLES GP67/2 Mono 15/-, GP91/3 Compatible £1, GP93/1 Crystal Stereo 25/-, GP94/1 Stereo Ceramic 25/-.

TRANSISTORISED SIGNAL INJECTOR KIT 10/-, SIGNAL TRACER KIT 10/-, CAR REV. COUNTER KIT 10/-.

VEROBOARD
 21 x 1" 0.15 matrix 1/3 5 x 3" 0.15 matrix 5/6 3" x 3" 0.1 matrix 4/9
 3" x 2" 0.15 matrix 3/3 17 x 2" 0.15 matrix 11/- 5 x 2" 0.1 matrix 4/7
 3" x 3" 0.15 matrix 3/11 17 x 3" 0.15 matrix 14/8 5 x 3" 0.1 matrix 5/6
 5 x 2" 0.15 matrix 3/11 3" x 2" 0.1 matrix 4/8
 Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins 3/6 for 36. Special Offer! Spot Face Cutter and 5 2" x 1" boards..... 9/8 only

PAPER CONDENSERS, Mixed bags 0.001µF to 5µF, 12/6 per 100. SILVER-MICA, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values, 10/- per 100.

RESISTORS. Mixed types and values. † to 1 watt, 6/6 per 100. 55/- per 1,000. Wire-wound resistors, 1 watt to 10 watts. Mixed values, 20 for 10/-. TRANSISTORS. Mixed, unmarked, mainly O.K. 7/6 for 50.

12 VOLT TRANSISTORISED FLOURESCENT LIGHTS. HALF NORMAL PRICE.
 8 Watt 12" tube. Reflector type £2.19.6. 15 watt 18" Batten type £3.19.6. IDEAL FOR CAMPING OR CARAVAN HOLIDAYS! A BRIGHT LIGHT FOR VERY LITTLE CURRENT!

ELECTROLYTIC CONDENSERS
 0.25µF 3 volt 4µF 4 volt 10µF 25 volt 64µF 9 volt
 1µF 6 volt 4µF 12 volt 20µF 6 volt 100µF 9 volt
 1µF 20 volt 4µF 25 volt 25µF 6 volt 320µF 4 volt
 1.25µF 16 volt 5µF 8 volt 25µF 12 volt 320µF 10 volt
 2µF 3 volt 6µF 6 volt 25µF 25 volt 400µF 6.4 volt
 2µF 350 volt 8µF 3 volt 30µF 6 volt All at 1/- each.
 2.5µF 16 volt 8µF 12 volt 30µF 10 volt 20 assorted
 3µF 25 volt 8µF 50 volt 50µF 6 volt (our selection)
 3.2µF 64 volt 10µF 6 volt 64µF 2.5 volt 10/-

Orders by post to:
G. F. MILWARD, DRAYTON BASSETT, NEAR TAMWORTH, STAFFS.

Please include suitable amount to cover post and packing. Minimum 2/- Stamped addressed envelope must accompany any enquiries. For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.

ELECTROVALUE

EVERYTHING BRAND NEW AND TO SPEC. NO SURPLUS

SPECIALIST SUPPLIERS OF TRANSISTORS

IN TYPES TO SUIT ALMOST ALL APPLICATIONS

- COMPETITIVE PRICES
- HIGH QUALITY COMPONENTS FOR TRANSISTOR CIRCUITS
- PEAK SOUND AS ADVERTISED
- CATALOGUE PACKED WITH UP TO THE MINUTE ITEMS AND INVALUABLE INFORMATION. Send 1/6 for your copy now.
- DISCOUNTS—10% on orders for components for £3 or more. 15% on orders for components for £10 or more.
- POSTAGE on order for £1. add 1/- . FREE on orders for £1 or over. Overseas orders welcome—Carriage charged at cost.

ELECTROVALUE

(Dept. PW), 32a ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY. Tel: Egham 5533 (STD 0784-3)

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates), the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME Block

ADDRESS Caps.

..... Please

6/69

BRITISH NATIONAL RADIO SCHOOL

TWENTY-EIGHT and twenty-one Mc/s are the bands which are usually the first to register dissatisfaction at lack of sunspots. However, with the sunspot count now on the decline, these bands are still pulling-in the stations. Strangely enough it is 21 which has been the more temperamental of the two and 28Mc/s has had some very good moments in the past month. Both bands seem to stay open longer in the evenings so how about a listen before you settle down to tea and telly?

Twenty metres is still a firm favourite in the s.w.l. DX stakes. From 1800 to 0600 it proved very lively with so much DX at times that it paid to have a countries list handy.

The 1f. end has also been busy with 80 metres providing some very good openings. Sadly, very few dared expose their ears to 40 metres where a mid-night-till-dawn session is usually very fruitful. How about a 7Mc/s month—go on, unsolder all the other coils in the receiver except those for 7Mc/s. You will probably hear a new country too if you persevere. Speaking of new countries and perseverance, Stew—W1BB has now worked over 100 countries on top-band so if 7Mc/s doesn't appeal try draping your earholes around 1.8—2.0Mc/s. Odd weak squeaks heard in this segment could well be G3JDG firing up the latest transistor r.f. oracle—or a ZL? just waiting for a report from you.

HEARD H.F.

Stephen Cole (Newport, Mon.), Trio JR60, Joystick, claims 28Mc/s r.f. s.s.b. emanating from—CR7DS, KR6KM, PY2HY, UA9CBW, XW8CS, 4X4HJ, 5A4TY, 5N2AAF, 9G1GG.

Meanwhile, back at the ranch, well, down in Gloucester, **Chris Witts** was loitering with his Trio JR-500s. Antenna used for lassooing the signals with a 100ft. end fed 30ft. from the terra firma. On 10 Chris hooked—KP4CL, PZ1DA, VE1ABF, VE3ETS, YN2RAC, ZC4TK, ZE1CX plus eight W's. On 21Mc/s his antenna reported signals from—CR4BB, HC1MG, IS1SCB, TF2WLM, VE3SQG, VK2FU, VK3VK, VK5GX, VQ9GA.

Over to Stourbridge in Worcestershire, where **Ron Shilvoek** states clearly, in writing, that he has only been DX-ing since his initiation in December 1968. A search on 21Mc/s with his Trio 9R-59DE and 60ft. end fed plus a.t.u. raised—CE3PT, CN8HL, CR6DP, EL9C, EP3REL, G3UHR/VO2, G8KL/W6, H18LA, HK3AUE, HK4TA, JX3DH, KP4ATS, KR6HB, PJ9PF, PY1DEM, VK3PX, VK4EF, VP2ME, VP8FL, WA6OET, WA8UYJ/KC4, W6GNP, W9BBR, YV3DA, YV5ANE, ZC4HS, ZE5JU, ZL1BEM, ZS3D, ZS4K, ZS5OB, ZS6EU, 4X4BO, 4X4RQ/AM, 5A4TY, 5N2AAU, 5Z4LX, 6W8DY, 6Y5LA, 8R1J, 9H1BI, 9Q5DA, 9X5AV.

T. Rumble (Wilts.), HA700 plus PR30 preselector, 100ft. long wire running N/S at 25ft. logged this lot on 28 Mc/s and on a.m. too—CT2AP, CX3BBU, K1ILT, K3VIG, VE2ABZ, VE3CLJ, WA1KEE, WA9PP, WB2CDX, W1LGS, W9DLZ, ZE1CB, 5A1TA.

If you are in the Bromley area of Kent, and you are an r.f. signal, watch out for **Simon Mummery's**

antenna. Those not so fortunate, and who saw it too late to miss it were—CN8CS, CR6CA, CR6LF, CR7IC, HS3DR, JA6AA, JA8ABH, JH1JUN, KV4FA, KV4SQ, SVØWI, VP7NA, YVØAB, ZS5XA—all 10 metres s.s.b. The same gear, B34 plus a.t.u. and 66ft. end fed, snared—CN8BB, EA9AQ, HC2OB, KH6GEL/P/W4, MP4BHG, SVØWN, VKØSL, VO1GL, ZS3LU.

NOT SO H.F.

It's no good, you just can't hide from those 20 metre signals. **L. Boucher** is down in Welsh Wales, but what happens when he switches on his R1155 and 68ft. end fed? Yes, that's right, s.s.b. signals on 20 from—CE3RY, CN8GE, CR4BK, CR6GA, VP5SK, VP8KD, VP8QR, VS6CO, VQ8CS, VU2GE, W6MWF, W7EPA, W7ZYC/MM (Survey ship *Discoverer*), ZB2BC, ZC4AK, ZD8Z, ZE1AA, ZL1ATX, ZL3AB, ZL4BX, ZS1BK, ZS6RM, 4X4KM, 5A4TR, 5A5TS, 5Z4AA, 7G1CG, 7P8YL, 7Z3AB, 9G1GD, 9H1M, 9J2GJ, 9K2AV, 9M2FR, 9Q5HF, 9X5AV.

HA350 plus PR30 plus RQ1OX plus 380ft. end fed plus **Robert James Dinning** plus 20 metres plus—CN8HO, CO2FA, CR7IZ, EP1VR, FP8CS, FR7ZG, HC2GU, KG4AA, KL7EG, KV4FC, KZ5AG, PJ2CB, OX3KG, SVØWEE, VE2AWE, VK2APC, VK3AIF, VP2GDL, VP8HS, VQ8BZ, VU2TP, XE3EB, ZE5JS, 5H3JL, 5U7AK, 5V4AP, 9H1M, 9K2CF, 9Y4AR.

Take away his B28, 20ft. indoor antenna, and **Roger Thackery** (Edinburgh), would never have heard—CE8AA, CT2AA, HI3AGS, HC2GU, LU6DZG, PJ2CB, PZ1BF, PY1MX, TN8VK, VE7PJ, VK3ARX, VK5MF, VKØKJ (Macquarie Is.), VP8JK, VP9CP, YV1EJ, ZS5TK, ZD8Z, 6W8DY, 6Y5GB, 7XØWW, 7X2ED, 8P6TV, 9Y4CP.

EVEN LESS H.F.

S. Teague (Worcs.), modified 19 set, 67ft. feeder with Joystick on the end, 80 metres s.s.b.—HB9KL, HV3SJ, K1KTH, MP4TAF, PJ2MI, TF3SD, VO1FG, VP2MK, VP9AT, W1CF, W4YAG, ZD8Z.

M. Pipes (Derby), "Trio RX", 66ft. end fed managed these on 160 metres—GD6IA, GM3VIO/A, HB9CM, OK1ACF, OK1TA, OK1ZW, OK2BGS, ON4WC, ZB2AY.


HAPPENINGS

Meetings, contests and gatherings for the merry month of May include: *May 3rd—4th* 2 metre contest (too late, it's happened); *24th—25th*, 432Mc/s contest; *24th—25th*, 1,296Mc/s contest (I didn't know anyone could live at the frequency). Mobile rallies include: *May 18th*, Northern MR near Leeds; *18th*, Thanet Radio Society's MR at Ramsgate; *June 1st*, A.R.M.S. rally at Old Warren Aerodrome; Biggleswade, Beds. (this will be a good 'un, see you there?); *June 1st*, Maidstone MR.

Deadline for logs is, as usual the 20th of the month. Keep the cans on, the antenna polished and the electricity bills high.

BASIC SEMICONDUCTOR TECHNOLOGY

PART TWO

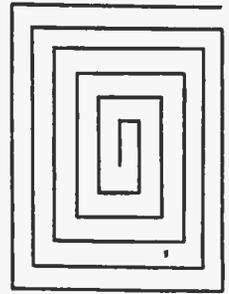

by M. F. DOCKER, M.Sc.

LAST month we showed that very pure materials were necessary for the manufacture of semiconductor devices. At present the most commonly used materials are germanium and silicon. However many devices are now being made using compounds of atoms with three and five valence electrons, such as gallium arsenide and indium antimonide, the so-called III-V compounds. These and other materials are showing great promise in device fabrication and undoubtedly their names will eventually become as common to the amateur as germanium and silicon are at present.

Germanium and silicon are each found in compound form and each needs to be very carefully purified before it can be used in a diode or transistor. Initially, chemical refining is carried out. Liquid compounds of the required element are prepared and these are then fractionally distilled in the same way that crude petroleum is distilled to separate the various compounds contained in it. This process provides a relatively pure compound which is then processed to yield the element.

Zone Refining

In order to obtain the one part in a thousand million parts purity which is required a process called zone purification which is very important to the semiconductor industry is used. When a vertical rod of the material is suspended in a bath of molten material of the same type, as shown in Fig. 1, impurities migrate to the liquid material to a certain extent. This is because the impurity is more soluble in liquid than in solid material. Thermal motion ensures that the impurity atoms move from the solid to the liquid and vice versa and as their solubility is greater in the liquid the number moving in the first way is greater than that moving in the second way.

The time required however is very long with this

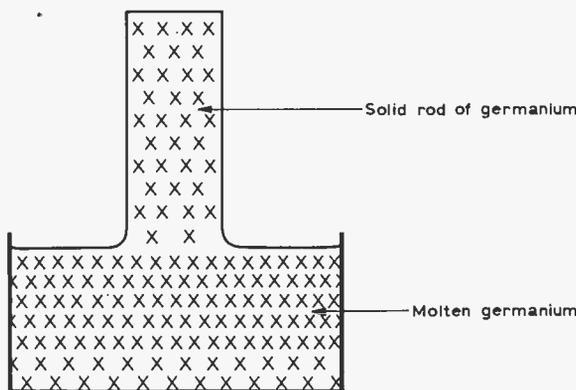


Fig. 1: Impurities concentrate more in molten than in solid germanium.

arrangement so that a different method is applied, the apparatus shown in Fig. 2 being used. A short r.f. heating coil is passed along a rod of the substance to be purified. This produces a short region of molten material which follows the coil along the rod and absorbs a proportion of the impurity present, carrying it to one end of the rod.

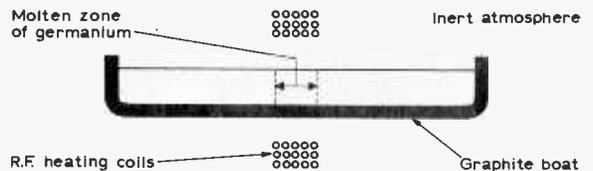


Fig. 2: Zone refining apparatus.

A single pass of the heating coil only reduces the impurity concentration by a certain fraction, this fraction depending on the type of impurity involved. In order to further purify the material the heating coil is swept along the rod several times, each pass resulting in a similar decrease in the impurity concentration. Many passes are required in order to obtain a sufficient degree of purification to permit semiconductor devices to be prepared from the material.

The various semiconductor materials tend to have different impurities depending on the ore from which they are refined. Silicon usually contains the element boron as an impurity, giving p-type material. The boron is very difficult to remove as the solubility of boron in liquid silicon is not very different from that in the solid. Consequently zone-refining is not very efficient in this case. A result of this technical difficulty was that early silicon devices had to be based on p-type material so that n-p-n silicon transistors were the first to make their mark on the market. These devices are still in general cheaper than the complementary p-n-p devices.

Crystal Defects

Having obtained a pure sample of the semiconductor, what else needs to be done to it before a transistor can be made? Last month it was shown that conduction could be due either to movement of electrons or to movement of holes; usually conduction is due to both but it is relatively easy to make one type predominate. The free current carriers in semiconductors only exist because very little energy is required to free them from their fixed positions in the crystal lattice. However there are various forms of binding which can result in the trapping of carriers and one of the most important of these is the presence of some form of crystal defect.

Defects can themselves be of many types, far too numerous to discuss here; however they often constitute discontinuities in the crystal lattice structure and this is equivalent to the presence of localised energy



If it's
components
you're after...



... you need the

HOME RADIO CATALOGUE

It's the finest, most comprehensive Catalogue we have ever produced—this latest edition. It has 330 pages, over 8,000 items listed, over 1,500 of them illustrated. Everything for the keen constructor—including tools and test gear. With each Catalogue we supply a 30-page Price Supplement, a bookmark giving electronic abbreviations, and an order form. All for only 8/6d plus 3/6 post, packing and insurance. Moreover, every catalogue contains 6 vouchers, each worth 1/- when used as directed.

POST THIS COUPON NOW
with cheque or P.O. for 12/-



Please write your Name and Address in block capitals

Name _____

Address _____



Home Radio (Components) Ltd. Dept. PW, 234-240
London Rd., Mitcham, CR4 3HD.


TO-3 PORTABLE OSCILLOSCOPE



3in. tube. Y amp. Sensitivity 1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF. X amp. sensitivity .9v p-p/CM. bandwidth 1.5 cps-800 KHZ. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHZ. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £35.0.0. Carr. 10/-.

R209 MK. II COMMUNICATION RECEIVER

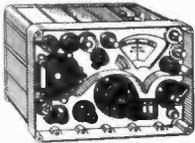11 valve high grade communication receiver suitable for tropical use. 1-30 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, BFO. Aerial trimmer, internal speaker and 12v. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. £12.10.0. Carr. 20/-.



TE-65 VALVE VOLTMETER



High quality instrument with 28 ranges. D.C. volts 1.5-1,500v. A.C. volts 1.5-1,500v. Resistance up to 1,000 megohms. 220/240v. A.C. operation. Complete with probe and instructions £17.10.0. P. & P. 6/-.

Additional probes available: R.F. 35/-, H.V. 42/6.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPS-1 MHz. Input imp. 2 meg Ω 25 pF. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240V A.C. Supplied brand new with handbook £22.10.0. Carr. 10/-.




TE-200 RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 Kcs-600 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140 x 215 x 170 mm.

TY75 AUDIO SIGNAL GENERATOR

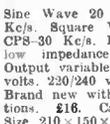

Sine Wave 20 CPS-200 CPS. Square Wave 20 CPS-30 Kcs. High and low impedance output. Output variable up to 6 volts. 220/240 volts A.C. Brand new with instructions. £16. Carr. 7/6. Size 210 x 150 x 120 mm.


LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER



2 pF-2000 mFd 2 ohms-200 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New £17.10.0 Carr. 7/6.

NOW OPEN IN EDGWARE ROAD

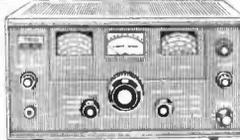Our new walk around shop is now open at 311 Edgware Road fully stocked with all Hi-Fi, Communication and Test Equipment. Call into your nearest shop—Edgware Road for all Equipment—Lisle Street for all Equipment and Components.




TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kcs/s to 30 Mc/s. continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 88B-CW • ANL • Variable BFO • 8 meter • Sep. bandspread dial • IF 455 Kcs/s • Audio output 1.6 W. • Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £42.10.0, carriage paid. TRIO COMMUNICATION TYPE HEADPHONES. Normally £5.19.6. OUR PRICE £3.15.0 if purchased with above receiver.

MARCONI TEST EQUIPMENT

EX-MILITARY RECONDITIONED. TE.144G STANDARD SIGNAL GENERATORS, 85 Kcs/s-25 Mc/s, £25 Carr. 30/-, T.F.858 VIDEO OSCILLATOR 0-5 Mc/s, £45 Carr. 30/-, T.F.195M BEAT FREQUENCY OSCILLATOR 0-40 Kcs/s, 200/250V. A.C., £20 Carr. 30/-, T.F.142E Distortion Factor Meter, £20 Carr. 20/-, All above offered in excellent condition, fully tested and checked. T.F.1100 VALVE VOLTMETER, Brand New, £50 T.F.1267 TRANSMISSION TEST SET, Brand New, £75 T.F.1371 Wide Band Millivolt Meter. Brand New, £50.

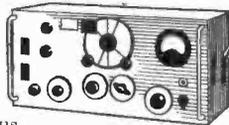


MULTIMETERS for EVERY purpose!

LAFAYETTE DE-LUXE 100K Ω /VOLT "LAB TESTER" Giant 6in. scale Built-in meter, protection 0/5/2.5/10/50/200/500/1,000V D.C. 0/3/10/50/250/500/1,000V A.C. 0/10/100 μ A/10/100/1,000 μ A/2.5/10/50/1K/10K/100K/10M/10M Ω -10 to 49-4dB £18.18.0. P. & P. 5/-.



TE-900 20,000 Ω /VOLT GIANT MULTIMETER mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V A.C. 0/25/12.5/10/50/250/1,000/5,000V D.C. 0/50 μ A/10/100/500 mA/10 amp. D.C. 0.2K/200K/20 MEG. OHM. £15. P. & P. 5/-.

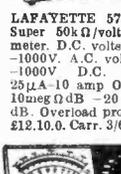MODEL AS-100D. 100K Ω /VOLT. 6in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V. D.C. 0/6/30/120/300/600V. A.C. 0/10 μ A/6/60/300 mA/2 amp. 0/2K/200K/2M/200M Ω -20 to +13dB. £12.10.0. P. & P. 3/6.




LAFAYETTE 57 Range Super 50k Ω /volt Multimeter. D.C. volts 12 mV-1000V. A.C. volts 1.5V-1000V D.C. current 25 μ A-10 amp Ohms 0-10meg Ω B -20 to +51 dB Overload protection. £12.10.0. Carr. 3/6.

MODEL TE-90 50,000 O.P.V. mirror scale overload protection. 0/3/12/60/300/600/1200V. D.C. 0/6/30/120/300/1200V. D.C. -0.8/60/600mA. D.C. 16K/160K/1.6/16meg Ω -20 to +63dB. £7.10.0. P. & P. 3/-.




PROFESSIONAL 20,000 Ω VOLT LAB. TYPE Multimeter. Automatic overload protection, mirror scale. Ranges: 1/10/50/250/500/1,000 volts. D.C. and A.C. 0-500 μ A, 10mA, 250mA Current: 0.20K, 200K, 2 megohm, Decibels: -20 to +22dB. £5.19.6. P. & P. 2/6.

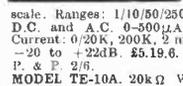MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30 μ A/3/30/300mA. 0/10K/100K/1.6M/16 Meg. Ω . £5.10.0. P. & P. 3/-.



MODEL TE-12 20,000 O.P.V. 0/0.6/6/30/120/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/80 μ A/8/60/600mA. 0/6K/600K/6Meg. 60 Meg. Ω 50pF. 0.2mFd. £5.19.6. P. & P. 3/6.

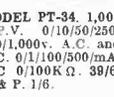MODEL PT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500M Ω . D.C. 0/100K Ω 39/8. P. & P. 1/6.



NEW CATALOGUE

Nearly 200 pages giving full details of a comprehensive range of COMPONENTS, TEST EQUIPMENT, COMMUNICATION EQUIPMENT AND HI-FI EQUIPMENT. Each section greatly enlarged and fully illustrated. Thousands of items many at bargain prices. Free Discount Coupons Value 10/-

SEND NOW—ONLY 7/6 P&P!

TE111. DECADE RESISTANCE ATTENUATOR



Variable range 0-11dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0-1d x B 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.06dB. Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-.

SINCLAIR EQUIPMENT

Z12 12 watt amplifier, 89/6 PZ4 Power Supply Unit 89/6 Stereo 25 Preamp. £9.18.6 Q14 Speakers £7.19.6 Micromatic Radio Kit. 49/6. Built 59/6. ALL POST PAID SPECIAL OFFER Two Z12 Amps, PZ4 Power Supply, Stereo 25 Preamp/liner, £22, or with two Q14 speakers, £37.

NEW SINCLAIR 2000 SYSTEM

35 watt Integrated Amplifier, £29, Carr. 5/-, Self-powered FM Tuner, £25, Carr. 6/-.

ECHO HS-606 STEREO HEADPHONES



Wonderfully comfortable. Lightweight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-17,000 cps. 8 ohm imp. 67/6 P. & P. 2/6.

AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmeq. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1 μ V-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.

FIELD TELEPHONES TYPE L

Generator ringing, metal cases. Operates from two 1.5V batteries (not supplied). Excellent production. £24.10.0 per pair. Carr. 10/-.



MARCONI CT/44/TF956

AF Absorption Wattmeter 1 μ Watt to 6 watts. £20. Carr. 10/-.

T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: -0.1/0.03/1/3/13/10/30/100/300V. R.N.S. 4cps. 2Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.10.0 Carr. 5/-.



AUTO TRANSFORMERS

0/115/230v. Step up or step down. Fully shrouded. 150 W. £11.2.6. P. & P. 3/6. 300 W. £2. 7.6. P. & P. 3/6. 500 W. £3.10.0. P. & P. 6/6. 1,000 W. £5.10.0. P. & P. 7/6. 1,500 W. £6.10.0. P. & P. 8/6. 3,000 W. £7.10.0. P. & P. 12/6. 7,500 W. £15.10.0. P. & P. 20/-.

G.W. SMITH & CO (RADIO) LIMITED

3 and 34, LISLE STREET, LEICESTER SQ., LONDON, W.C.2 01-437 8204
311, EDGWARE RD., LONDON, W.2 01-262 0387

OPEN 9 a.m. to 6 p.m. every day Monday to Saturday (Edgware Road) (Thu. Thurs.) Trade supplied.

(ALL MAIL ORDERS TO:- 3, LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2)

levels in the band gap. A sample of germanium may contain tens of thousands of dislocations in one c.c. of the crystal and a sample of silicon may contain millions of such discontinuities. The boundaries of individual crystallites also represent defects in the overall crystal structure. The presence of defects in semiconductors results in a large reduction of the lifetime of the current carriers as they soon become trapped—in the same way that a billiard ball moving on a rough table becomes caught in the undulations.

Crystal Growth

In order to remove these defects a single crystal is produced from the polycrystalline substance. There are several methods of doing this. The one most commonly used is probably the Czochralsky method which was developed in 1916. This involves the growth of a single crystal from a bath of molten semiconductor material as shown in Fig. 3. A small seed crystal is required and this is obtained by cutting very carefully from a polycrystalline sample a small single crystallite. This is then dipped into the melt and very, very slowly withdrawn, rates of between one-hundredth of a centimetre and sixty centimetres per hour commonly being used.

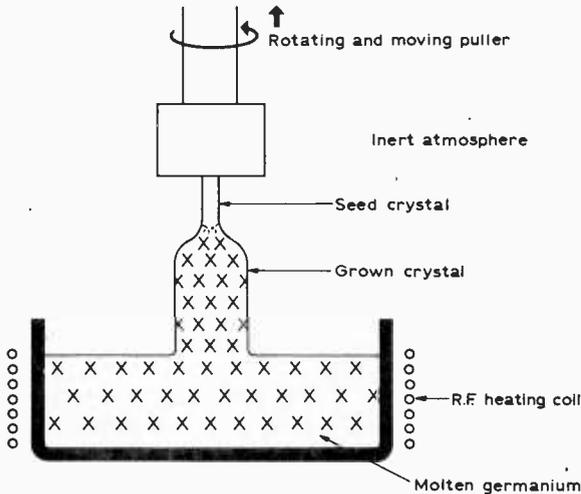


Fig. 3: The Czochralsky apparatus used to produce single crystals.

As the crystal is pulled out new material grows on to the seed. The atoms are deposited in the same orientation as that in the seed and in this way a long single crystal is produced. In order to help maintain a uniform growth rate the crystal is rotated at up to 200 r.p.m. on an axis along its length. Crystals of up to three inches diameter can be produced in this way, but more usually one-inch rods are made. This method can be used to produce single crystals of many different substances including germanium, silicon, gallium arsenide, copper, silver and lead.

In order to avoid the risk of impurities being introduced from the vessel containing the melt it is possible to produce a molten pool of the material in the solid polycrystalline substance by locally heating the required region with a beam of high energy electrons, the same crystal-pulling techniques being used as before.

Another method of making single crystals is the float-zoning process where a seed crystal is again required, but this time a slowly moving r.f. heating coil is used to produce the molten zone, in a similar way

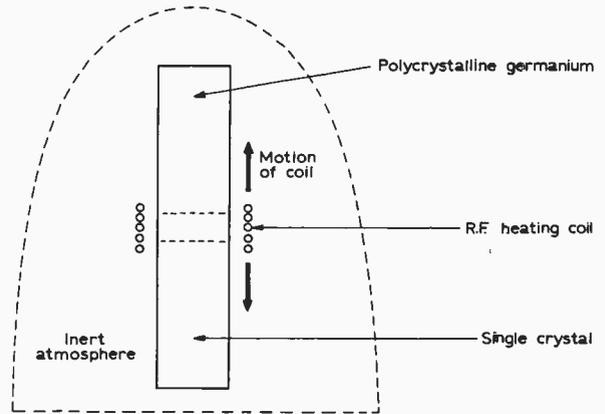


Fig. 4: Float zoning apparatus.

to that used in the zone refining apparatus. The seed crystal is placed at the bottom of the polycrystalline rod as shown in Fig. 4 and the r.f. coil placed around the rod just above the seed. It is slowly moved up the rod and as it moves the melted and then recrystallised material forms an extension of the original seed crystal. This method was developed at the Bell Telephone Systems laboratory during the 'fifties.

A further method is the Bridgman process in which the polycrystalline sample is slowly lowered through a furnace which is at a temperature above the melting point of the sample. As it comes out of the furnace it starts to recrystallise and a single crystal usually results. However in this method it is not so easy to control the orientation of the crystal faces.

Annealing of the single crystals is carried out to reduce the number of defects present in the lattice and consequently to improve the characteristics. This is done by cooling the single crystal very slowly so that defects have time to move out of the crystal.

Doping

Having obtained a pure single crystal of the material it is then necessary to add impurities! There are various ways of doing this and the different methods are used in the appropriate circumstances. Here only the problem of obtaining a uniform doping will be considered. It should be emphasised that the impurities in a semiconductor have to be very precisely controlled. The word impurity does not in this case mean something

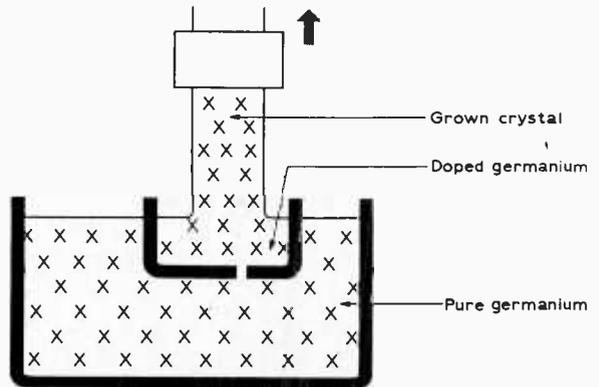


Fig. 5: The double-crucible method of growing doped crystals.

which is undesirable but an added atom which is different from the majority of atoms in the crystal.

Two important methods of doping are used. The first is the floating crucible in which there are two vessels, one having a small hole in its base (see Fig. 5). This contains pure material to which a small amount of the appropriate dope impurity has been added and floats in a quantity of pure material in the outer vessel. The system is used in conjunction with the Czochralsky method for producing single crystals and the resulting crystal has the required degree of doping. The reason for using the rather complicated apparatus is that if the dope were simply added to the melt the concentration of impurity in the crystal would vary as the crystal grew, the last part of the crystal to grow having a much higher doping level and consequently a lower resistivity than the rest. The double crucible compensates for this by keeping the impurity concentration constant as the crystal grows.

The second and perhaps the most important method is that of gas phase doping. This technique is used with the float-zoning method of preparing single crystals. Instead of carrying out the refining in a vacuum, the apparatus is surrounded with a gas containing the required doping atoms. The molten zone slowly absorbs some of the gas thus becoming doped. As the zone moves up the rod the doping proceeds, resulting in a uniform impurity concentration in the crystal.

The resistivity of the long round crystal is measured and it is then cut into thin slices about twenty-five thousandths of an inch thick and one inch in diameter. These are all lapped in order to provide smooth surfaces and finally they are chemically etched to remove damage, e.g. scratches, caused by the slicing process. After being carefully washed in very pure water they are ready to be used for the manufacture of devices. The final slice is about ten thousandths of an inch thick.

Growing Epitaxial Layers

Another manufacturing term which is seen frequently is "epitaxial" and very many devices are now manufactured using the epitaxial planar process. In order to obtain a device with high frequency capabilities it is necessary to use high resistivity material. However it is a disadvantage to make the whole device of this material because of the resultant high impedances. The epitaxial process starts with a low resistivity slice on to which a thin layer of high resistivity material is grown, the so-called epitaxial layer. The atoms deposited on the surface align themselves with the atoms in the crystal lattice so that they do not constitute crystal defects but are simple extensions of the crystal. The chemical reaction involved in the process is of the form:



Silicon tetrachloride reacts with hydrogen to liberate silicon at the surface of the slice. Doping is achieved by adding boron tribromide to the gases to produce p-type material or phosphorous trichloride for n-type material. A similar reduction reaction occurs, boron or phosphorous being deposited as impurity atoms in the epitaxial layer.


An individual transistor, diode, resistor and so on is called a device. An active device is one which can be used to amplify power; a passive device is one which produces no amplification, e.g. a resistor. Next month we shall describe methods of making diodes.

TO BE CONTINUED


NEXT MONTH IN P.W.

A.C.—D.C. METER

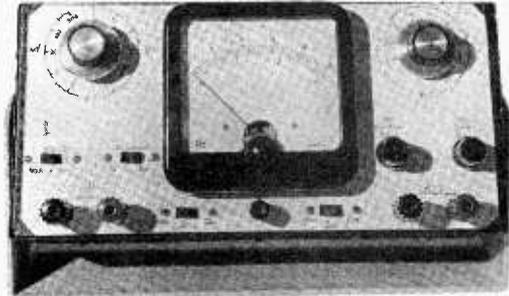Constructional article giving details of a sensitive multirange transistorised voltmeter for measuring a.c. and d.c. voltages. On a.c., the lowest range has an f.s.d. of 3mV and on d.c. 100mV.



A CALIBRATED SIGNAL GENERATOR

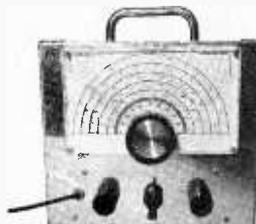

A constructional project which overcomes one of the main disadvantages of building test gear—calibration. This simple unit operates between 450Hz and 35MHz and by using the specified components,

calibration is simply a matter of copying from a chart provided in the article. The unit will provide modulated r.f., c.w. or a.f. signals.

PLUS OTHER CONSTRUCTIONAL PROJECTS AND REGULAR FEATURES


PRACTICAL WIRELESS

All in the JULY issue on sale June 6th

ORDER YOUR COPY NOW!

NEW! HSL.700 MONO TRANSISTOR AMPLIFIER

A really high fidelity mono-amp with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated pre-amplifier assembled on special printed sub-panel. AD181-AD182 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200-240v. Controls: Bass, Treble, Volume/on/off. Function selector for PU1, PU2, Tape, Radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9 1/2 x 5 1/4 in. high.

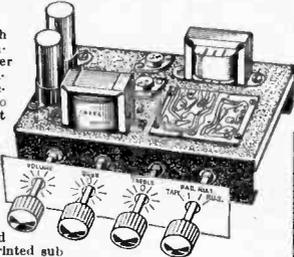

Performance figures:
Sensitivity—PU1-50mV, 50K input impedance.
PU2-110mV, 1 meg input impedance.
Tape—110mV, 1 meg input impedance.
Radio—110mV, 1 meg input impedance.
Output power measured at 1Kc—6.2 watts RMS into 3 ohms, 5.8 watts RMS into 15 ohm. Overall frequency response 30 c/s-16 Kc/s; Continuously variable tone controls; Bass, + 8 db to -12 db at 100 c/s. Treble, + 10 db to -10 db at 10 Kc/s.

The HSL.700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder pre amp but is also capable of being used in conjunction with a guitar by connecting to PU1 socket and the peak output power when used in the region of 15 watts. Supplied complete with knobs, attractive anodised aluminium front escutcheon panel, long spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions. Limited Number.

Our Special Price **£7.19.6** P. & P. 7/6.

BRAND NEW 3 OHM LOUSPEAKERS

5in. 14/-; 6in. 18/6; 8in. 27/-; 7 x 4in. 18/6; 10 x 6in. 27/6 E.M.I. 8 x 5in. with high flux magnet 21/-, E.M.I. 13 1/2 x 8in. with high flux ceramic magnet 42/- (15 ohm 45/-) E.M.I. 13 x 8in. with two built in tweeters and crossover network, 3 or 15 ohms 4 gns. P. & P. 5in. 2/-, 6in. 2/6 10 & 12in. 3/6 per speaker.

BRAND NEW 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiFux ceramic ferrobar magnet assembly 25.10.0. P. & P. 5/-
Guitar models: 25w. 25.0.0. 35w. 28.0.0. E.M.I. 8in. Heavy Duty Tweeters. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6
2in. "RA" TWIN CON LOUSPEAKER. 10 watts peak handling, 3 or 15 ohm, 35/-, P. & P. 3/6.

35 OHM SPEAKERS

3 1/2in. 12/6; 7 x 4in. 21/-, P. & P. 2/- per speaker.

LATEST COLLARO MAGNAVOC 363 STEREO TAPE DECK. Three speeds 4 track, takes up to 7in. spools. 216.00. Carr. 10/-

QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Only 49/6. P. & P. 8/6. Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser 35/-, P. & P. 3/6

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 18/6. P. & P. 1/6.
HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/-, P. & P. 1/6.
CARBON MIKE INSERTS. Brand new 2 1/2in. dia. 5/-, P. & P. 1/6.

NEW S.T.C. TYPE 25 MINIATURE RELAYS—18 volt-4 s/p, c/o contacts. 1 amp rating. Coil resistance 5,800 ohms. Size approx. 1 x 1 1/4 x 1 1/4 in. high. 8/6 each. P. & P. 1/6

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Size approx. 2 x 1 1/4 in. Only 8/6. P. & P. 2/6.

MAINS TRANSFORMER. Primary 200-240V two separate 1/2 amp secondaries giving approx 15V at 1 amp and 20V at 1/2 amp; secs. can be connected in series for 36V at 1/5 amp. Ideal for transistor power supplies. Drop through mounting. Stack size 2 1/2 x 3 1/4 x 1 1/2 in. 15/-, P. & P. 6/-

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. 11/-, P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6
MATCHED PAIR OF 21 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohm and 15 ohm output. 11/- pair plus 2/-, P. & P.

HIGH GRADE COPPER LAMINATE BOARDS 8 x 6 x 1/16 in. FIVE for 10/-, P. & P. 2/-.

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response ±3dB. 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 6 amp.

PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0. All Post Free.

Circuit diagram, construction details and parts list (free with kit) 1/8. (S. A. E.)

Official Stockists of all **PEAK SOUND HI-FI EQUIPMENT** including the **P. W. DOUBLE 12 STEREO AMPLIFIER** as featured in Practical Wireless April, May and June issues. Component pack as specified.

2 Spools of 'Cir-Kit'	4.0
2 Pre-amp and tone control kits	413.0
4 3 1/2in. x 2in. 'Cir-Kit' matrix	7.0
2 Boards 5" x 3"	8.0
2 PA.12-15 Power Amp Kits	27.19.0
2 Heat Sink assemblies	12.0
1 FS.45K v power supply kit	24.10.0
1 Pack flat aluminium cartr. finished	22.12.6
Cabinet kit	22.0.0
5 Controls as specified	22.0.0

Total cost **£235.6** Plus P. & P. 11/- (Excluding metal work, knobs, plugs and sockets and fuses).

SPECIAL PURCHASE! E.M.I. 4-SPEED PLAYER Heavy 8 1/2in. metal turntable. Low flutter performance 200/250 v. shaded motor (90 v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY 63/-, P. & P. 6/6.

QUALITY RECORD PLAYER AMPLIFIER MKII A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7" w. x 3" d. x 6" h. Ready built and tested. PRICE 75/-, P. & P. 6/-

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MKII Unit motor board size 14 1/2 x 12in. clearance 2in. below. 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD autochanger or Single Player Unit (except AT60 and 8P25). Size 18 1/2 x 15 x 8in. PRICE 78/6. P. & P. 8/6


FM/AM TUNER HEAD Beautifully designed and precision engineered by Dornier and Precision Wadsworth Ltd. Supplied ready fitted with twin-0005 tuning condenser for AM connection. Prealigned FM section covers 86-102 Mc/s. I.F. output 10-7 Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/6.
GORLER F.M. TUNER HEAD. 86-100 Mc/s. 10-7 Mc/s. I.F. 15/- plus 2/6 P. & P. (ECC85 valves, 8/6 extra)

3-VALVE AUDIO AMPLIFIER MODEL HA34 Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.5.0. P. & P. 6/-

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-; V15/10P. 10/-; OC71 5/-; OC76 6/-; AF17 3/6; 2G389 (NPN) 3/-; Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 25/-; ORP12 Cadmium Sulphide Cells 10/6. All post free.

DE LUXE STEREO AMPLIFIER

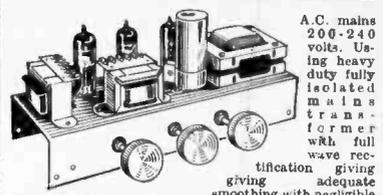

A.C. mains 200/240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: —2 x ECL86 Triode Pentodes, 1 x E280 as full wave rectifier. Two Dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A Dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs. Chassis size 11" w. x 4" x. Overall height including valves 5". Ready built and tested to a high standard. PRICE 8 gns. P. & P. 8/-

4-SPEED RECORD PLAYER BARGAINS Mains models. All brand new in maker's packing. E.M.I. MODEL 999 Single Player with unit mounted pick-up arm and mono cartridge 25.5.0 B.S.R. UA25 with latest mono compatible cart. 28.19.6 All plus Carriage and Packing 6/6

LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60 etc. Send S.A.E. for latest Prices! PLINTH UNITS cut out for Garrard Models, 1025, 2025, 2000, 3000, AT70, 8P25. With rigid perspex cover. OUR PRICE 5 gns. complete. P. & P. 8/6.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/80mm/78. Only 32/6. P. & P. 2/-
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/-, P. & P. 2/-
SONOTONE STABC compatible Stereo Cartridge with diamond stivus 50/-, P. & P. 2/-
FEW ONLY! ACOS High-G for EP and LP. Only 10/-, P. & P. 2/-

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TA1

- Peak output in excess of 11 watts.
- All standard British components.
- Built on printed circuit panel size 6 x 3in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers.
- Transistors (GET14 or 81 Mullard AC128D) and matched pair of AC128 p/c.
- 9 volt operation.
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 8/6 (Free with kit). All parts sold separately. SPECIAL PRICE 45/-, P. & P. 3/6. Also ready built and tested, 52/6. P. & P. 3/6.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, E280 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7" wide x 3" deep x 6" high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested, with valves and good quality output transformer. FEW ONLY.

OUR ROCK BOTTOM BARGAIN PRICE **49/6** P. & P. 6/-

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.9.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 29.5.0. P. & P. 8/6.

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon
Tube Station

HARVERSON SURPLUS CO. LTD.


170 HIGH ST., MERTON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Please write clearly
PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY.
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

Sinclair

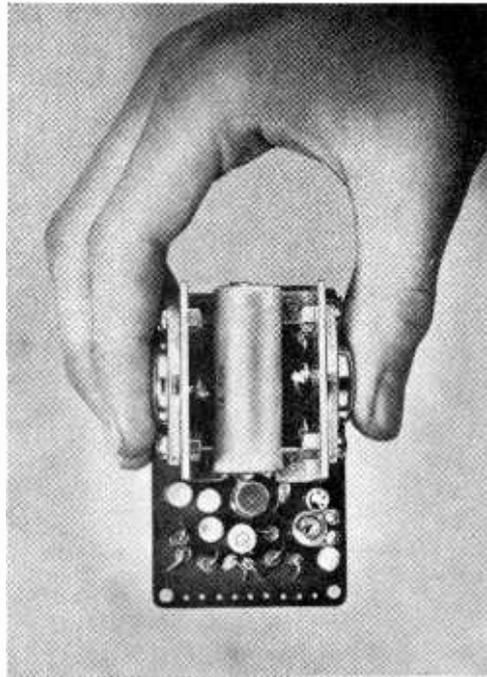

Z.12 - for all you want from any amplifier

The Z.12 is a most versatile integrated amplifier and pre-amp in which power, compactness and true high-fidelity standards are combined within a unit of very modest price. The most widely used unit of its kind in the world, the Z.12 has an output of 12W R.M.S. continuous sine wave (24W peak) or 15W music power (30W peak). It has Class B ultralinear output which can be fed into any loudspeaker from 3 to 15 ohms. (Two 3 ohm speakers can be used in parallel.) Frequency response—15 to 50,000Hz \pm 1dB; input sensitivity—2mV into 2 kilohms. The Z.12 will operate from any power source between 6 and 20V d.c. As such,

a car battery or the PZ.4 are eminently suitable, giving much wider than usual scope in the applications to which the Z.12 may be put. As well as hi-fi, these include systems for P.A. electronic guitars, organs, intercom systems, laboratory, education or industry. You will find the Z.12 in use in such instances again and again. The Sinclair Z.12 is supplied ready built, tested and guaranteed, complete with manual of circuits and instructions for matching it to your precise requirements. Two may be used in stereo when, with the Stereo 25 and PZ.4 together with two Q.14s, you will have an ideal high fidelity assembly.

89/6
+ P.T. Surcharge

Q.14 - the unique loudspeaker

New materials and original design techniques have been used to produce a speaker of fantastic quality at a most attractive price. Experts and reviewers have enthusiastically endorsed its performance. The shape and size of the Q.14 make it far more adaptable to its environment than is the case with conventionally styled speakers so that it is much easier to position this speaker in the room in which it is to be heard. The Sinclair Q.14 has a substantially flat frequency response

from 60 to 16,000Hz and outstandingly good transient response. It will comfortably handle up to 14W loading and is positively brilliant in stereo. Measuring 9 $\frac{1}{2}$ in. square by 4 $\frac{1}{2}$ in. deep, this loudspeaker is finished in matt black with solid aluminium bar trim. Try the Q.14 in your own home without delay. If you are not delighted with it, your money, including cost of return postage to Sinclair, will be refunded immediately.

£7.19.6
+ P.T. 2/11td
P.T. Surcharge



Stereo 25 de-luxe pre-amp/control unit

This is a very elegantly styled unit, which, although designed basically for use with the Z.12, is readily adaptable for use with any high quality power amplifier system. The switched input selector allows for Pick-up, Radio and Auxiliary and there are controls for bass cut and lift, treble cut and lift, volume and stereo balance. P.U. input is equalised to R.I.A.A. curve

from 50 to 20,000Hz \pm 1dB and the instructions manual provided gives matching details for pick-ups, shows how to connect up, etc. The front panel of the Stereo 25 is finished in brushed and polished aluminium embellished in black. The control knobs are in solid aluminium to match. Size $6\frac{1}{2}$ x $2\frac{1}{2}$ x $2\frac{1}{2}$ in. plus knobs. Supplied built, tested and guaranteed.

£9.19.6

PZ.4 - stabilised power supply unit

Designed specially to meet the power requirements for an assembly of two Z.12s and the Stereo 25, this heavy duty transistorized power supply unit has stabilised output of 18V d.c. at up to 1.5A. It is for a.c. mains operation 200/250V.

Supplied built, tested and guaranteed.

99/6

SINCLAIR MICROMATIC

Whether you buy your micromatic in kit form or built ready for use, you must not deny yourself the thrill of owning this fantastically small British receiver. Smaller than a matchbox, it has power range and selectivity that must be experienced to be believed. The high quality magnetic earpiece supplied with the set ensures excellent reproduction indoors and out. The Micromatic tunes over the medium waveband and has A.G.C. to counteract fading from distant stations. Bandpass tuning makes reception of Radio 1 easier; in fact you will find this set performing in some cases where other sets cannot be heard at all. The Micromatic is housed in a neat black case given an elegantly modern appearance by the attractive aluminium front panel and matching tuning control.

Kit in fitted pack with magnetic earpiece, instructions and free solder.

49/6 + 11d

Built, tested and guaranteed, inc. magnetic earpiece.

59/6 + 11d

Built, tested and guaranteed, inc. magnetic earpiece.

YOUR SINCLAIR GUARANTEE

should you not be completely satisfied with your purchase within 14 days of purchase your money will be refunded in full at once and without question. Full service facilities available to all purchasers.

Goods sent post free in U.K. and Overseas by surface mail. Air-freight charged at cost.

Please send POST FREE

NAME



ADDRESS

For which I enclose cash/cheque/ money order

PW.669

OCA-3 52731

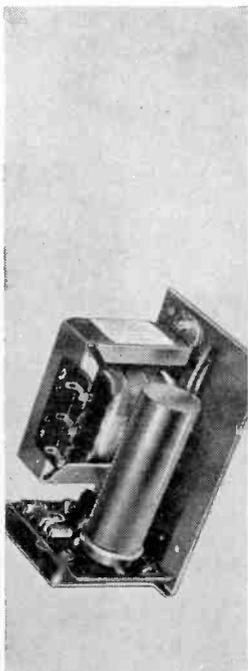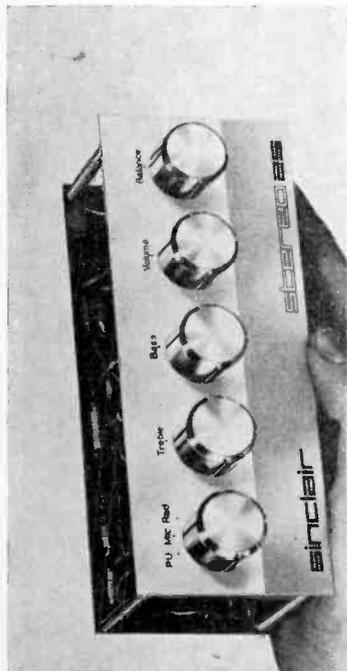SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE



The world's smallest personal radio



R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers

Tel. 769-0199/1649

1A7 7/0	6BQ7A 7/-	6K7G 2/-	9BW6 7/-	20P5 20/-	80 7/0	DF96 7/0	ECP80 6/0	EM80 7/0	PC97 8/0	RG5/50080/-	UP89 7/0
1D5 7/0	6BR7 12/-	6K7GT 4/0	10C1 12/0	25A6 6/0	85A2 7/0	DH77 4/0	ECP82 6/0	EM81 8/0	PC834 6/0	R130 40/-	UL14 12/-
1H5 7/-	6BR8 12/0	6K8M 11/0	10C2 12/0	25L8GT 7/-	160B2 11/0	DK32 7/0	ECH21 12/0	EM84 7/0	PC839 10/0	SP4 8/-	UL84 7/-
1ND5 6/-	6BS7 25/-	6K8G 3/-	10F1 14/0	25Y5 6/-	150C4 9/0	DK91 6/-	ECH35 11/0	ESU15020/-	PC189 10/0	SP41 3/0	UM80 5/0
1N5GT 8/-	6BW6 14/0	6K8GT 7/-	10F3 18/-	25Z4 6/0	801 8/0	9K92 9/-	ECH42 11/-	EY51 7/0	PCF80 6/0	SP61 3/0	U16 13/0
1R5 6/-	6BW7 18/-	6K25 15/-	10F9 10/0	25Z5 8/-	807 9/-	DK96 7/0	ECH41 5/0	EY86 7/-	PCF82 6/0	STV280/80	U17 13/0
184 5/0	6C4 5/-	6L1 12/-	10F18 8/-	25Z6 8/0	813UBA	DL66 25/-	ECH83 8/0	EZ35 6/-	PCF84 8/-	U25 95/-	U19 8/0
185 4/0	6C5G 5/-	6L6G 7/0	10L1 8/-	25D7 9/0	120/-	DL92 6/0	ECL80 7/-	EZ40 8/0	PCF86 9/-	UA25 19/0	U21 9/0
174 4/-	6C6 3/0	6L18 6/-	10LD11 10/0	30C1 6/0	813 8/0	DL93 4/-	ECL82 7/-	EZ41 9/0	PCF801 9/0	UA2160 12/0	U24 8/0
3A4 4/-	6C8G 6/-	6Q7G 6/-	10P13 13/0	30C15 15/-	866A 15/-	DL94 6/0	ECL83 10/0	EZ80 5/0	PCF802 9/0	T41 17/0	UY85 6/0
3C4 7/0	6CD80 24/-	6Q7GT 8/0	11E3 70/-	30C17 18/-	964 5/0	DL95 7/0	ECL86 9/-	EZ81 5/0	PCF805 15/-	TDD4 3/0	VMP40 17/-
9Q5 7/-	6CH6 7/0	68A8M 7/-	12A7 4/0	30C18 15/-	1625 6/0	DL96 7/0	ECLL800	GZ30 10/-	PCF806 13/0	U10 7/0	VP4B 25/-
384 6/0	6CW4 12/-	68C7 7/-	12A7T 6/-	30F15 12/-	4022AR07/-	DM70 6/-		GZ32 10/-	PCF808 15/0	U14 7/0	VR105/30
3V4 6/0	6D6 3/0	68G7 6/-	12AUG 5/0	30FL1 18/-	5783 12/-	DY86 6/-		GZ34 11/-	PCL82 7/0	U19 35/-	VR150/30
5R4QY 10/0	6E5 7/0	68H7 3/0	12AU7 5/0	30FL12 18/-	7193 20/-	DY87 6/0	EF9 20/-	GZ34 11/-	PCL83 10/0	U25 15/0	VR150/30
5U4G 4/-	6F1 12/0	68J7 6/-	12AX7 8/0	30FL14 15/0	7475 14/-	E980C 12/-	EF37A 7/-	KT36 11/-	PCL84 8/0	U26 15/0	VR150/30
5V4G 5/0	6F6G 8/-	68K7GT 4/0	12B6 6/-	30L15 17/-	A81 7/0	EA50 8/0	EF39 8/-	KT66 21/-	PCL85 9/0	U78 4/0	VT25 15/-
5Y3GT 6/-	6F8G 5/-	68L7GT 8/-	12BE6 8/0	30L17 17/-	ATP4 2/0	EABC80 6/0	EF50 5/-	KT81 85/-	PCL86 9/0	U191 13/0	VT31 80/0
5Z4G 7/-	6F8G 5/0	68N7GT 5/0	12CG8T 5/0	30P12 18/-	ATP5 12/-	EAP42 10/-	EF80 5/-	KT81 (7C5)	PEN44 20/-	U261 16/0	VU111 8/0
6/30L2 15/-	6F11 6/0	68Q7 7/0	12E1 20/-	30P19 15/-	ATP7 8/0	EB41 10/-	EF85 7/-	15N5A	PEN48 40/-	U301 12/0	VU120 12/0
6A7 15/-	6F13 6/0	6U4GT 12/-	12J5GT 2/0	30PL1 18/-	AU2 80/-	EB91 3/0	EF86 6/0	KT88 30/-	PEN45 7/-	U403 6/0	VU508 35/-
6A8G 12/0	6F14 12/0	6U5G 7/0	12J7GT 6/0	30PL13 18/0	AU5 8/0	EB93 8/0	EF89 5/0	KTW61 8/0	PEN46 4/-	U404 7/0	W81M 12/0
6AC7 4/-	6F23 16/-	6V6M 12/-	12K7GT 6/-	30PL14 15/0	AZ1 8/-	EB41 9/0	EF91 3/0	KTZ41 6/-	PL80 10/0	U901 23/0	X11-5 5/-
6AK5 5/-	6F24 14/-	6V6G 4/0	12K8GT 6/-	35A5 11/0	CB31 10/-	EB90 4/0	EF92 2/0	ML 17/0	PL81 8/0	UABC80 6/0	XF1-5 5/-
6AL5 4/0	6F25 15/-	6V6GT 6/0	12Q7GT 6/0	35L6 5/0	AZL1 10/-	EBF80 7/0	EF98 15/-	ML6 6/-	PL82 8/0	UAF42 10/0	XSG1-5 10/-
6AM5 2/0	6F28 14/-	6X4 4/0	128A7 8/-	35W4 4/0	CCH35 15/-	EBF83 9/-	EF183 6/0	MSP4 10/-	PL83 7/0	UBC41 9/0	Y63 7/0
6AM6 3/0	6G6 2/0	6X5G 4/0	128G7 6/0	35Z3 10/-	CL3 20/-	EBF89 6/0	EF184 7/-	MU14 7/0	PL84 7/-	UBC81 9/0	Tubes
6AQ5 6/0	6H6 3/-	6X5GT 6/-	128H7 3/-	35Z4GT 8/0	CY30 12/0	EBL1 14/-	EL32 3/0	MX40 12/0	PL600 14/0	UBF80 7/0	3EG1 65/-
6AS7G 10/-	6J5M 9/-	7B6 11/0	128J7 4/0	35Z5 6/0	CY31 8/0	EBL21 12/-	EL33 12/0	N78 19/-	FX4 14/-	UBF89 7/0	3FP7 29/-
6AT6 4/0	6J5G 4/-	7B7 7/0	128K7 4/0	37 6/0	DAC32 7/-	EBL31 27/0	EL34 10/0	N108 25/-	PY33 10/0	UC84 8/0	6CP1 55/-
6AU6 5/-	6J6GT 5/0	7C5 15/-	128R7 5/-	42 6/0	DAF91 4/0	ECC80 5/0	EL41 16/0	NGT1 6/-	PY81 5/0	UC85 7/0	ACV1526 40/-
6BA6 20/-	6J6 3/0	7C6 15/-	14H7 9/0	55 6/0	DAF96 7/0	ECC81 6/0	EL42 6/0	NGT7 80/-	PY82 5/0	UC86 8/0	CRI13100/-
6BB6 2/-	6J7M 8/0	7D5 8/-	19A05 5/-	60C5 6/0	DCC90 10/0	ECC82 5/0	EL44 4/0	OA2 6/0	PY83 7/0	UCH42 10/0	VCR97 35/-
6BA6 5/-	6J7G 6/-	7H7 8/0	20D1 10/-	50CD6G31/-	DF33 8/-	ECC83 6/0	EL80 6/0	OC3 7/-	PY80 9/0	UC81 7/0	VCR817B
6BE6 5/-	6J7GT 7/0	7H7 13/-	20P2 4/0	50LGT 6/0	DF70 9/0	ECC84 5/0	EL85 6/0	OZ4 4/0	PY801 9/0	UC182 7/0	46/-
6BH6 9/-	6K6GT 5/-	787 4/0	20L1 9/0	50P1 4/0	DP91 4/0	ECC85 5/0	EL80 20/-	PC86 11/0	R2 7/0	UC83 10/-	VCR517C
6BJ6 9/-	6K7M 6/0	7Y4 8/0	20P4 20/-	75 5/-	DF92 9/-	ECC88 7/0	EM34 21/-	PC88 11/0	R19 7/0	UF41 10/0	46/-

SPECIAL 24 HOUR SERVICE

OBSOLETE TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Express postage 9d. per valve.

Ordinary postage 6d. per valve.

C.W.O. No C.O.D.

Complete range of T.V. Tubes available from £4.5.0.

Manufacturers and Export Inquiries Welcome

**Special 24 Hour
Express Mail
Order Service**

SETS OF VALVES

DAF91, DF91, DK91, DL92 or DL94

DAF96, DF96, DK96, DL96 ..

20/- plus postage

29/- plus postage

TRANSISTORS

AC127 7/0

AF114 7/-

AF115 7/-

AF117 6/0

OC25 11/-

OC28 18/-

OC35 11/0

OC45 4/-

OC71 4/0

OC72 8/-

OC75 8/-

OC76 8/-

OC77 8/-

OC81 4/-

OC81D 4/-

OC81DM 4/-

OC82 6/-

OC82 6/-

OC82D 6/-

OC83 6/-

OC170 7/0

OC17A 8/-

OC200 7/0

SEND S.A.E. FOR LIST OF 2,000 TYPES

TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS
— 2 or 4 TRACK



Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Front panel alum and black—12 1/2 x 4 1/2 in. 200-250 A.C. Mains Trans. Off/On-Tone; Vol./Mic.; Vol./Gram.; Mic. Input; Gram. Input; Monitor; Valves 6BR7, ECC83, EM84, EL84 and Rect. 2 Track £10.10.0; 4 Track £12 (12/6 p. & p.). Ready for bolting direct to Magnavox deck.

FULLY BUILT STEREO AMPLIFIER. 2 x 3 watts, mains trans., metal rect., 2 x UCL82, 2 o.p. trans. for 3 ohm, vol/on-off, tone, balance, chassis type with 3 controls on front. 11 x 3 1/2 x 4 1/2 in. high. 26 (8/- p. & p.).

3W. PEAK PUSH-PULL OUTPUT AMPLIFIER. 200-250V A.C. E280, ECC83, 2—EL84, Bass, treble, vol/on-off, £7.12.6 (post paid). Size 12 x 3 1/2 x 5 1/2 in. high. For Record Player, Radio Tuner, etc. Mains Trans. o.p. trans. for 3 ohm.



6 PUSH-BUTTON STEREOGRAM CHASSIS



M.W. (S.W.1); S.W.2; V.H.F.; Gram; Stereo Gram; Vol; Tone; Mains Trans; 200-250 Volts; 2 o.p. for 3 ohm. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2 in. high. Dial silver and black 15 x 3 in. 190-550M; 18-51M; 60-187M; VHF 80-100 Mc/s. Valves—ECC85, ECH81, EP89, 2x ECL86, EM84 and Rect. Price £19.19.0, carr. paid. With Stereo Decoder fitted £27.10.0 extra.

GLADSTONE RADIO


66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses).
CLOSED WEDNESDAY.

FULL GUARANTEE. Aldershot 22240

STRONGHOLD
steel shelving
that adjusts
every inch of
its height!

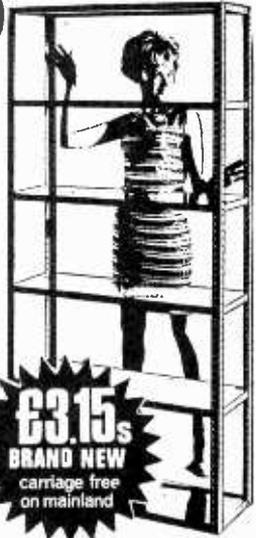Immensely strong—completely adjustable, every inch. Delivered free, mainland, with spanner provided for erection in minutes. Buy it by the bay! Cash with order
73" high x 34" wide x 12" deep unit with six shelves in heavy-gauge steel, stove enamelled grey or green!
£3.15s.—Brand New! See the rest of the N.C. Brown range!



£3.15s
BRAND NEW
carriage free
on mainland



N.C. BROWN LTD.

pacesetters in storage equipment

Send your FREE BROCHURE or Send (how many) bays of steel shelving @ £3.15s. in green grey (tick which)

Name.....
Address.....
Dept. PW Eagle Steelworks, Haywood, Lancs.
Tel: 69018, London: 25-27 Newton St. W.C.2.
Tel: 01-405 7931

DE LUXE PLAYERS

PORTABLE CABINET Anilux-Player. To fit standard 75/- trans. or autochanger.

BGS AMPLIFIER 3 WATT. Ready made and tested. This is a 2-stage unit using a triode pentode condenser coupled valve giving 3 watts output into a 3 ohm loudspeaker. Tone and volume controls mounted on chassis with knobs. Supplied with loudspeaker and valve UJL82. Frequency response 50-12,000 cps. **59/6**

AUTOCHANGERS MONO Ballour Princess 25.18.8
BBS Superdium UA25.28.18.6
UA70 Transcription 21.2.18.8
Garrard SRP2 26.18.8
Garrard SP25 MHII 21.18.8
3000 Stereo/Mono 21.2.18.8

All fitted LP78 stylus and pickup cartridge complete. Stereo/Mono pickup 20/- extra, except 3000.

GARRARD TEAKWOOD BASE WE.1. Ready cut out for mounting 1025, 8000, SP25, AT60, etc. **65/-**

GARRARD PERSPEX COVER 3PC.1. for WE.1



BARGAIN STEREO/MONO SYSTEM

Attractive Slim PLAYER CABINET with B.S.R. STEREO Autochanger 4 + 4 AMPLIFIER and TWO matched 6in. LOUDSPEAKERS Carr. 10/6 **£19.19.6.** (Only 4 pairs of wires to join.)

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V	2/3	100/25V	2/1
4/350V	2/3	150/25V	2/6
8/450V	2/3	500/25V	4/-
16/450V	3/-	8+8/450V	3/6
32/450V	3/9	16+16/450V	3/9
25/25V	1/9	16+16/450V	4/3
50/50V	2/-	32+32/350V	4/6

32+32+32/350V 8/6

SUB MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mF 15V 500, 1000mF 12V 50V; 2000mF 25V 7/-.

CERAMIC 500V 1pF to 0.01mF 9d. Disc 1/-.

PAPER 350V-0.1 9d; 0.5 2/6; 1mF 3/-; 2mF 150V 3/-.

500V-0.001 to 0.05 9d; 0.1 1/-; 0.2 1/6; 0.5 3/-; 1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1, 2/6.

SILVER MICA. Close tolerance 1%, 5-500pF 1/-; 560-2200pF 3/-; 2,700-5,600pF 3/6; 5,600pF-0.01 mid 9/- each.

NEON PANEL INDICATORS, 250V, AC/DC, 9/6.

RESISTORS. Preferred values, 10 ohms to 10 meg. 2/-; 1w, 1/2w, 1w, 20% 3d; 1/4w, 8d; 2w, 1/-; 1/2w, 10% 6d.

HIGH STABILITY. 1w, 1/2w, 10 ohms to 10 meg. 2/-; Ditto 5%. Preferred values 10 ohms to 22 meg. 9d.

8 watt 5/-
10 watt 5/-
16 watt 5/-

WIRE-WOUND RESISTORS 2/-
10K, 15K, 20K, 25K, 30K, 35K, 40K, 50K, 60K, 70K, 80K, 90K, 100K 3/-

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs 1 1/2 amp. 8/9; 2a, 11/3; 4a, 17/6.

CHARGER TRANSFORMERS, P. & P. 5/-. Input 200/250v. for 6 or 12v., 1 1/2 amps., 17/6; 2 amps., 21/-; 4 amps., 30/-

VALVE HOLDERS, 9d; CERAMIC 1/-; CANS 1/-.

BAKER 12in. DE-LUXE MKII LOUDSPEAKER

Suitable for any Hi-Fi System. Provides truly rich sound recreating the musical spectrum virtually flat from 25-16,000cps. Latest double cone with special "Ferrobac" ceramic magnet. Flux density 14,000 gauss. Bass resonance 32-38cps. 15W British rating. Voice coils available 3 or 6 or 15 **£9** Post ohms. Free

48 page Enclosure
Manual 5/ post paid

LOUDSPEAKER CABINET WADDING 18in. wide, 2/6 ft.

BAKER "GROUP SOUND" SPEAKERS—POST FREE

"Group 25" 12in. 15watt 6 gns.
"Group 35" 12in. 15watt 8 1/2 gns.
"Group 50" 12in. 15watt 18 gns.

ALL MODELS "BAKER SPEAKERS" IN STOCK

DE LUXE STEREO GRAM CHASSIS V.H.F. MW, SW 19-50m. SW 60-180m.

Marjo eye, push buttons. 6 valve plus rect. Size 15 x 7 1/2 x 6in. high. British made. Details S.A.E. **£22.10**

E.M.I. PICK-UP ARM Complete with mono cartridge 29/6; Xtal GP67 17/6; Stereo Ceramic 25/-; Powerpoint 60 15/-

CRYSTAL MIKE INSERTS

1 1/2 x 1/2 in. 6/6; A008 1 1/2 x 1/2 in. 9/6, BM3, 1" dia. 9/6

MOVING COIL MIKE with Remote Control Switch 19/6

PORTABLE TRANSISTOR AMPLIFIER PLUS DYNAMIC MICROPHONE

A self-contained fully portable mini p.a. system. Many uses—ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player. Amplifier, etc. Attractive rexine covered cabinet size 12 x 8 x 4in, with powerful 7 x 1/2 in. speaker and four transistor one watt power amplifier plus ultra sensitive microphone Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make. Only **90/-** Free

WEYRAD P50—TRANSISTOR COILS

RA2W 6in. Ferrite Aerial	Spare Cores	6d.
EAR with aerial coil	Driver Trans. LPD7A	9/6
Cap. P50/1A/3	Printed Circuit, PCA1	9/6
1rd. F. P50/2CC 470 k/1s.	J.B. Tuning Gang	10/6
S.F. P50/300	Weyrad Booklet	2/-

Telephone Choms 8 Aerials Gm. extends to 23in. 5/-
Ferrite Rods Only 8 x 1/2 in. 4/-; 8 x 1in. 5/-

VOLUME CONTROLS 80 Ohm Coax 8" rd.

10K spindles. Midset Size 5K, ohms to 2 Meg. LOG or LIN. 1/8, 1/4, 1/2, 5/8, 1, 1 1/2, 2, 3, 4, 5, 6, 8, 10, 15, 20, 30, 40, 50, 60, 80, 100, 150, 200, 300, 400, 500, 1000, 1500, 2000, 3000, 4000, 5000, 10000, 15000, 20000, 30000, 40000, 50000, 100000, 150000, 200000, 300000, 400000, 500000, 1000000, 1500000, 2000000, 3000000, 4000000, 5000000, 10000000, 15000000, 20000000, 30000000, 40000000, 50000000, 100000000, 150000000, 200000000, 300000000, 400000000, 500000000, 1000000000, 1500000000, 2000000000, 3000000000, 4000000000, 5000000000, 10000000000, 15000000000, 20000000000, 30000000000, 40000000000, 50000000000, 100000000000, 150000000000, 200000000000, 300000000000, 400000000000, 500000000000, 1000000000000, 1500000000000, 2000000000000, 3000000000000, 4000000000000, 5000000000000, 10000000000000, 15000000000000, 20000000000000, 30000000000000, 40000000000000, 50000000000000, 100000000000000, 150000000000000, 200000000000000, 300000000000000, 400000000000000, 500000000000000, 1000000000000000, 1500000000000000, 2000000000000000, 3000000000000000, 4000000000000000, 5000000000000000, 10000000000000000, 15000000000000000, 20000000000000000, 30000000000000000, 40000000000000000, 50000000000000000, 100000000000000000, 150000000000000000, 200000000000000000, 300000000000000000, 400000000000000000, 500000000000000000, 1000000000000000000, 1500000000000000000, 2000000000000000000, 3000000000000000000, 4000000000000000000, 5000000000000000000, 10000000000000000000, 15000000000000000000, 20000000000000000000, 30000000000000000000, 40000000000000000000, 50000000000000000000, 100000000000000000000, 150000000000000000000, 200000000000000000000, 300000000000000000000, 400000000000000000000, 500000000000000000000, 1000000000000000000000, 1500000000000000000000, 2000000000000000000000, 3000000000000000000000, 4000000000000000000000, 5000000000000000000000, 10000000000000000000000, 15000000000000000000000, 20000000000000000000000, 30000000000000000000000, 40000000000000000000000, 50000000000000000000000, 100000000000000000000000, 150000000000000000000000, 200000000000000000000000, 300000000000000000000000, 400000000000000000000000, 500000000000000000000000, 1000000000000000000000000, 1500000000000000000000000, 2000000000000000000000000, 3000000000000000000000000, 4000000000000000000000000, 5000000000000000000000000, 10000000000000000000000000, 15000000000000000000000000, 20000000000000000000000000, 30000000000000000000000000, 40000000000000000000000000, 50000000000000000000000000, 100000000000000000000000000, 150000000000000000000000000, 200000000000000000000000000, 300000000000000000000000000, 400000000000000000000000000, 500000000000000000000000000, 1000000000000000000000000000, 1500000000000000000000000000, 2000000000000000000000000000, 3000000000000000000000000000, 4000000000000000000000000000, 5000000000000000000000000000, 10000000000000000000000000000, 15000000000000000000000000000, 20000000000000000000000000000, 30000000000000000000000000000, 40000000000000000000000000000, 50000000000000000000000000000, 100000000000000000000000000000, 150000000000000000000000000000, 200000000000000000000000000000, 300000000000000000000000000000, 400000000000000000000000000000, 500000000000000000000000000000, 1000000000000000000000000000000, 1500000000000000000000000000000, 2000000000000000000000000000000, 3000000000000000000000000000000, 4000000000000000000000000000000, 5000000000000000000000000000000, 10000000000000000000000000000000, 15000000000000000000000000000000, 20000000000000000000000000000000, 30000000000000000000000000000000, 40000000000000000000000000000000, 50000000000000000000000000000000, 100000000000000000000000000000000, 150000000000000000000000000000000, 200000000000000000000000000000000, 300000000000000000000000000000000, 400000000000000000000000000000000, 500000000000000000000000000000000, 1000000000000000000000000000000000, 1500000000000000000000000000000000, 2000000000000000000000000000000000, 3000000000000000000000000000000000, 4000000000000000000000000000000000, 5000000000000000000000000000000000, 10000000000000000000000000000000000, 15000000000000000000000000000000000, 20000000000000000000000000000000000, 30000000000000000000000000000000000, 40000000000000000000000000000000000, 50000000000000000000000000000000000, 100000000000000000000000000000000000, 150000000000000000000000000000000000, 200000000000000000000000000000000000, 300000000000000000000000000000000000, 400000000000000000000000000000000000, 500000000000000000000000000000000000, 1000000000000000000000000000000000000, 1500000000000000000000000000000000000, 2000000000000000000000000000000000000, 3000000000000000000000000000000000000, 4000000000000000000000000000000000000, 5000000000000000000000000000000000000, 10000000000000000000000000000000000000, 15000000000000000000000000000000000000, 20000000000000000000000000000000000000, 30000000000000000000000000000000000000, 40000000000000000000000000000000000000, 50000000000000000000000000000000000000, 100000000000000000000000000000000000000, 150000000000000000000000000000000000000, 200000000000000000000000000000000000000, 300000000000000000000000000000000000000, 400000000000000000000000000000000000000, 500000000000000000000000000000000000000, 1000000000000000000000000000000000000000, 1500000000000000000000000000000000000000, 2000000000000000000000000000000000000000, 3000000000000000000000000000000000000000, 4000000000000000000000000000000000000000, 5000000000000000000000000000000000000000, 100, 15000000000000000000000000000000000000000, 200, 300, 400, 500, 1000, 1500, 2000, 3000, 4000, 5000, 100, 15000, 200, 300, 400, 500, 1000, 1500, 2000, 3000, 4000, 5000, 100, 15000, 200, 300, 400, 500, 1000, 1500, 2000, 3000, 4000, 5000, 100, 15000, 200, 300, 400, 500, 1000, 1500, 2000, 3000, 4000, 5000, 100, 15000, 200, 300, 400, 500, 1000, 1500, 2000, 3000, 4000, 5000, 100, 15000, 200, 300, 400, 500, 1000, 1500, 2000, 3000, 4000, 5000, 100, 15000, 200, 300, 400, 500,

PW DOUBLE 12

Described in this issue

BUY YOURS FROM TRS

All equipment supplied by TRS is exact to specification

	£	s.	d.
2 Spools of "Cir-Kit" at 2/- each	4	0	0
2 Peak Sound Pre-amp and Tone Control Kits	4	15	0
4 "Cir-Kit" Matrix Board	7	0	0
2 Peak Sound PA. 12-15 amp. units	7	19	0
2 Peak Sound Amp. Heat sinks	12	0	0
1 Peak Sound Power Unit PS.45K	4	10	0
1 Peak Sound Pack-flat cabinet kit	2	12	6
5 controls as specified	2	0	0
TOTAL	£22	19	6

Carriage and packing 12/6

TRS STEREO 4-4 a bargain in quality amplifiers

AMPLIFIER KIT #7.19.6 (p.p. 3/6) Integrated 5 transistor stereo amp based on newly developed Mullard 4 watt modules and BC.108 pre-amp. Suitable also for speakers from 3 to 15 ohms. With base and treble cut/boost. Response 60 to 14 KHz —3dB. This excellently engineered layout requires only wiring between controls and modules. Complete with metal chassis and simple teak-ended cabinet for instant assembly.

TRS POWER UNIT #2.5.0 (p.p. 2/6)

TRS SIMPLEX CABINET #1.17.6 (p.p. 2/6)

4 prs. DIN plugs and sockets if purchased separately, 15/-.

Complete kit inc. cabinet/power pack DIN plugs and socket.

£12.10.0 (Carr. 7/6)

MAKE YOUR OWN BOOKSHELF SPEAKER

With a set of matched speakers and cross-over from TRS. Comprises modern style high efficiency 5in. bass unit with special cone assembly, X-over and 2 1/2in. tweeter for mounting into your own cabinet or baffle system. Smooth response from 80 to 20,000 Hz. Loading up to 6 watts. Made by a world-famous manufacturer. A genuine bargain for only **79/6** (carr. 5/-).

TRS MULLARD AMPLIFIERS

STEREO 10-10 Kit with valves and passive control system. **KIT #18.10.0: BUILT #22.10.0** (carr. either 12/6).

2 x 2 VALVE PRE-AMP. Built with valves, dial, etc. **#18.19.6** (carr. 7/6).

5-10 MONO AMPLIFIER. Basic Kit, with valves, etc. 10 gms. Built **#13.0.0** (carr. either 7/6).

Basic Kit with passive control system, **#12.10.0**. Built 15 gms. (carr. either 7/6).

PRE-AMP 2 VALVE KIT #6.19.6. Built #9.10. (carr. either 5/6).

BASIS 5-10 AMPLIFIER AND 2 VALVE PRE-AMP Assembled, wired and tested, complete **#21.10.0** (carr. 10/-).

(S.A.E. brings details of range.)

WIRE WOUND RESISTORS—COATED TYPES

Stand. values 25 ohms—10,000 ohms, 5w, 1/8, 10w, 1/19, 15w, 2/8. SPECIAL VALUES 15K—35K ohms 5w, 2/6.

PRE-SET WIRE WOUND POTS. Slotted Knurled Knob TV Type 25 ohms—30Kohms 3/8. 50Kohms 4/6. Ditto carbon track 50K—2 Meg. 3/8.

SLIDER PRESETS 1w. 10K—2.2 Meg. 2/-, 10 ohms—5K 2/6.

STANDARD W/WOUND POTS. Long spindle. 100/50,000 ohms each 6/-, 100,000 ohms each 6/9.

VOLUME CONTROLS 1 1/2in. dia. Long Spindles. Famous make. All values 5,000 ohms—2 Megohms. Guaranteed 12 months. Log or Linear tracks. Less Sw. 3/6. DP 5w. 5/-, Log or Linear tracks. Centre tapped 1/2 Megohm Log, 1 Megohm less Sw. 5/-.

RESISTORS—Modern ratings, full range 10 ohms to 10 megohms, 10%, 1/2 w., 4d. ea.; 5% Hi-Stab. 1/2 w., 6d. ea. (below 100 ohms and over 1 meg., 6d. ea.). 1% Hi-Stab. 1/2 w., 1/8 ea. (below 100 ohms, 2/- ea.).

CONDENSERS Silver Mica. All values 2 pf. to 1,000 pf. 6d. ea. Disto ceramics 5d. Tab. 450v T.C.C. etc., .001 mf. to 0.1 mf./350 v. 10d., .05 mf. to 0.1 mf./500 v. 1/-, .25 T.C.C. 1/9, 5 T.C.C. 2/-. GLOSS TOL. S/MCS. 10% 5 pf.—500 pf. 2d. 600—5,000 pf. 1/-, 1% 2 pf.—100 pf. 11d. 100—250 pf. 1/2. 270—800 pf. 1/4. 800—5,000 pf. 2/-.

"CIR-KIT" "VEROBOARD".

SP25 De-Luxe single record player, diecast turntable. Less cartridge. **#12.10.6** (carr. 7/6).

GARRARD PLINTH WB1. In fine Teak for above units. (Pack. and carr. 5/-). 67/6

Clear-view rigid perspex cover (carr. 4/8), 65/-.

6 Valve AM/FM Tuner

Med. and V.H.F.—metal rectifier. Magic-eye, 3 push-button controls. Diode and high output sockets. Illuminated dial. Chassis 11 1/2 x 4 x 5 1/2in. Complete kit, inc. Power Pack A.C. mains **#12.0.0** (carr. 7/6). Circuit and construction details 4/6. Free with kit.

LISTS—Eight large printed pages, packed with bargain offers including difficult to find lines. Send 6d. for latest copy.

TRS RADIO

COMPONENT SPECIALISTS

Established 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Tel.: 01-684 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wednesdays

A few doors from Thornton Heath Stn. (S.R. Victoria section)



New Edition—Now Out

Thinking of High Fidelity—first read Goodman's 28 page High Fidelity Manual. It contains interesting articles on Stereo; an Introduction to High Fidelity; Stage-built systems; as well as full details of Goodman's High Fidelity audio products.

Send for your free copy

Please send me a free copy of Goodman's Manual

Name _____
Address _____ PW6

Goodmans Loudspeakers Limited

Axiom Works, Wembley, Middlesex. Tel: 01-902 1200

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 185, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for 17/6. DAF96, DF96, DK96, DL96, 4 for 26/-.

OZ4	4/6	20F2	13/6	DL35	5/-	EL84	4/9	PENA4	12/6	UC084	7/6
1A7GT	7/6	20P3	11/9	DL92	5/9	EL90	5/-	PEN38C15	-	UC085	6/9
1H6GT	7/6	20P4	18/6	DL94	5/9	EM80	5/9	PFL20012	6/6	UCF80	8/3
1N6GT	7/9	28U4GT11/6	DL96	7/-	EM61	6/9	FL35	9/9	UCF49	9/9	
1R5	5/6	30C1	6/9	DY36	5/9	EM84	6/6	PL31	7/8	UCB31	6/9
185	4/8	30C15	13/-	DY87	5/9	EM87	7/6	PL82	7/-	UCL82	7/3
1T4	3/9	30C17	16/-	EABC80	6/6	EY51	7/3	PL83	7/-	UCL83	11/6
384	5/9	30C18	9/-	EAF42	3/9	EY86	6/9	PL84	6/6	UF41	9/9
3V4	5/9	30F5	16/-	EB91	3/8	EZ40	7/6	PL500	13/-	UF80	7/-
5U4G	4/6	30FL1	12/6	EB33	7/6	EZ41	7/6	PL504	13/6	UF85	6/9
5Y3GT	5/9	30FL1214/6	EB41	6/8	EZ60	4/6	FL508	22/6	UF89	6/9	
5Z4G	7/6	30FL1410/6	EBF90	6/9	EZ81	4/9	PL802	14/6	UL41	10/6	
6/30L2	12/6	30L1	6/6	EBF89	6/8	GZ32	3/9	PM84	7/9	UL44	30/-
6AL5	2/3	30L15	14/-	ECC81	3/9	KT32	5/-	PK25	10/6	UL84	7/-
6AM6	3/6	30L17	15/6	ECC82	4/9	KT61	3/9	PY31	5/6	UM84	7/6
6AQ5	4/9	30P4	12/-	ECC83	7/-	KT66	15/-	PY32	10/-	UY41	7/-
6AT6	4/-	30P12	13/9	ECC84	6/6	MEL40015/-	-	PY33	10/-	U735	5/9
6AU6	4/9	30P19	12/-	ECC85	5/9	N78	14/9	PY81	5/3	VP4B	10/-
6BA6	4/6	30PL1	12/6	ECC80A12/6	6/6	PABC90	7/7	PY82	5/3	VP132121/-	3/6
6BE6	4/6	30PL13	15/6	ECCF80	7/-	PC86	10/3	PY83	5/3	Z77	3/6
6BJ6	7/-	30PL14	15/6	ECCF82	6/9	PC88	10/3	PY88	6/3	Transistors	-
6BW6	13/-	36L6GT	8/-	ECC85	6/9	PC96	3/6	PY900	7/6	AC107	3/6
6F13	3/6	35W4	4/6	ECC42	10/6	PC97	3/6	PY301	6/9	AC127	2/-
6X4	3/6	CL33	13/6	ECC49	3/9	PC90	3/6	R19	6/6	AT146	3/6
6F28	14/8	6063	12/6	ECC84	7/6	PC84	6/6	R20	12/6	AF103	15/-
6K7G	3/6	AC/VP210/-	-	ECL80	6/9	PC085	6/6	RE12	9/6	AF115	3/-
6K8G	4/8	AZ31	9/-	ECL82	6/9	PC088	9/9	U26	13/-	AF116	3/-
6L18	6/-	B729	12/6	ECL83	9/-	PC089	10/6	U26	12/-	AF117	3/6
6V6GT	6/6	CCR35	10/-	ECL86	5/6	PCF189	11/6	U47	13/6	AF124	7/6
6X14	3/6	CL33	13/6	ECC49	3/9	PCF50	5/9	U49	12/6	AT125	3/6
6XSGT	5/9	CY31	6/9	EF41	9/6	PCF82	6/-	U52	4/6	AF126	7/-
7B6	10/9	DAC32	7/8	EF80	4/9	PCF86	9/6	U78	3/6	AF127	3/6
7B7	7/-	DAF91	4/8	EF85	6/9	PCF80018/6	-	U191	12/6	OC26	5/6
7C6	6/9	DAF96	6/6	EF86	6/8	PCF801	7/-	U301	13/6	OC44	3/6
7Y4	6/6	DF33	7/9	EF89	5/8	PCF802	9/6	U801	19/6	OC45	3/6
10F1	15/-	DF81	2/9	EF91	9/6	PCF805	9/-	UABC90	6/3	OC71	3/6
10P13	15/6	DF96	6/-	EF94	4/9	PCF80811/6	-	UAF42	9/6	OC72	3/6
12AT7	3/9	DH77	4/-	EF183	6/-	PCF80810/6	-	UB41	6/6	OC75	3/6
12AU6	4/9	DH81	10/9	EF184	5/9	PL82	7/-	UBC41	3/6	OC81	3/3
12AU7	4/9	DK32	7/6	EH90	6/3	PCL38	9/-	UBC81	7/-	OC81D	3/3
12AX7	4/9	DK91	5/6	EL33	3/9	PL84	7/6	UBF80	6/-	OC82	3/3
12K8GT	7/-	DK92	9/3	EL34	9/6	PCL56	9/-	UBF89	6/9	OC82D	3/3
195G617/6	DK96	7/-	EL41	10/6	PCL86	3/6	UC92	5/-	OC170	3/6	

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

NEW PRICES ON NEW COMPONENTS

RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm.): Body: $\frac{1}{2}$ W; 8×2.8
 $\frac{1}{2}$ W; 10×4.3

Leads: 35

10% ranges; 10 Ohms to 10 Megohms (E12 Renard Series).
 5% ranges; 4.7 Ohms to 1 Megohm (E24 Renard Series).

Prices—per Ohmic value.

	each	10 off	25 off	100 off
$\frac{1}{2}$ W 10%	2d.	1/6	3/3	10/4
$\frac{1}{2}$ W 5%	2 $\frac{1}{2}$ d.	1/9	3/8	11/8
$\frac{1}{2}$ W 10%	2 $\frac{1}{2}$ d.	1/9	3/8	11/7
$\frac{1}{2}$ W 5%	3d.	2/-	4/-	12/10

CAPACITORS

Subminiature Polyester film, Modular for P.C. mounting. Hard epoxy resin encapsulation. Radial leads.

$\pm 10\%$ tolerance. 100 Volt Working.

Prices—per Capacitance value (μ F)

	each	10 off	25 off	100 off
0.001, 0.002, 0.005,		10 off	25 off	100 off
0.01, 0.02	6d.	4/3	8/4	30/-
0.05	8d.	6/-	12/6	41/8
0.1	10d.	7/1	15/6	51/-
0.2	1/2	10/-	20/10	68/6
0.5	2/-	17/6	37/6	125/-

Polystyrene film, Tubular, Axial leads. Unencapsulated. $\pm 5\%$ or $\pm 1\mu$ f tolerance. 160 Volt Working.

Prices—per Capacitance value (μ F)

	each	10 off	25 off	100 off
10, 12, 15, 18, 22, 27, 33,		10 off	25 off	100 off
39, 47, 56, 68, 82, 100, 120,		10 off	25 off	100 off
180, 220, 270, 330, 390	5d.	3/7	7/9	24/-
470, 560, 680, 820, 1,000,				
1,500	6d.	4/-	8/8	26/8
2,200, 3,300, 4,700, 5,600	7d.	5/-	10/10	33/4
6,800, 8,200, 10,000, 15,000	8d.	6/-	13/-	40/-
22,000	9d.	6/9	18/-	45/4

Polystyrene film, Tubular, Axial leads. Professional Grade. Hard Epoxy Resin encapsulation.

$\pm 1\%$ tolerance. 100 Volt Working.

Prices—per Capacitance value (μ F)—except where stated).

	each	10 off	25 off	100 off
100, 120, 150, 180	1/3	10/2	21/2	64/6
220, 270, 330, 390, 470,				
560, 680, 820	1/3	10/8	23/1	71/-
1,000, 1,200, 1,500,				
2,200, 2,700	1/6	13/10	29/11	92/-
3,300, 3,900, 4,700, 5,600	1/9	14/1	31/-	96/-
6,800, 8,200, 10,000, 12,000	1/9	15/2	32/10	101/-
15,000, 18,000	2/-	15/11	34/9	107/4
22,000, 27,000	2/3	17/3	37/10	115/-
33,000, 39,000	2/6	20/1	43/6	133/9
47,000, 56,000	2/9	22/1	47/10	147/4
68,000	3/-	24/9	53/8	165/4
82,000	3/3	26/1	56/6	173/9
0.1 μ F	3/6	27/5	59/4	182/8
0.12 μ F	3/9	30/3	65/10	202/-
0.15 μ F	4/3	34/2	73/7	228/-
0.18 μ F	5/-	37/10	81/11	252/3
0.22 μ F	6/-	47/-	101/10	313/4
0.27 μ F	6/9	53/9	116/8	358/4
0.33 μ F	7/3	58/10	126/11	390/-
0.39 μ F	7/9	65/-	140/10	433/4
0.47 μ F, 0.5 μ F	9/9	75/2	137/7	500/-

POTENTIOMETERS (Carbon)

Miniature, fully enclosed, rear tags, carbon brush wiper. Long life, low noise. Body dia., $\frac{1}{2}$ in. Spindle, $\frac{1}{16}$ in. $\frac{1}{2}$ W at $70^\circ\text{C.} \pm 20\%$ below $\frac{1}{2}$ M, $\pm 30\%$ over $\frac{1}{2}$ M. Lin. 100 ohms to 10 Megohms. Log. 5 Kohms to 5 Megohms.

Prices—per ohmic value

	each	10 off	25 off	100 off
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d.	7/1	14/7	46/8

SKELTON PRE-SET POTENTIOMETERS (Carbon)

High quality pre-sets suitable for printed circuit boards of 0.1in. P.C.M. 100 ohms to 5 Megohms (Linear only). Miniature: 0.3W at $70^\circ\text{C.} \pm 20\%$ below $\frac{1}{2}$ M, $\pm 30\%$ above $\frac{1}{2}$ M. Horizontal (0.7in. \times 0.4in. P.C.M.) or Vertical (0.4in. \times 0.2in. P.C.M.). Subminiature: 0.1W at $70^\circ\text{C.} \pm 20\%$ below 2.5 M, $\pm 30\%$ above.

Prices—per ohmic value

	each	10 off	25 off	100 off
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d.	7/1	14/7	46/8

JACK PLUGS

$\frac{1}{2}$ in. Type P1. Standard. Screened. Heavily chromed.

$\frac{1}{2}$ in. Type P2. Standard. Unscreened. Unbreakable moulded cover.

$\frac{1}{2}$ in. Type SE/P1. Side-entry version of P1 plug.

3.5 mm. Type P5. Standard. Screened. Aluminium cover.

3.5 mm. Type P6. Standard. Unscreened. Unbreakable moulded cover.

	each	10 off	25 off	100 off
P1	3/-	26/8	62/6	233/4
P2	2/6	23/4	54/2	200/-
SE/P1	3/6	30/10	66/8	280/-
P5	2/2	19/2	43/9	158/4
P6	1/8	15/-	33/4	116/8

JACK SOCKETS

$\frac{1}{2}$ in. Type S.5 Standard. Moulded body. Chrome insert.

3.5 mm. Type S.6. Specification as above.

Available with make/make, make/break, break/break, break/make contacts.

	each	10 off	25 off	100 off
S.5	2/9	25/-	56/8	216/8
S.6	1/6	13/4	33/4	100/-

ELECTROLYTIC CAPACITORS (Mullard). -10% to +50%.

Subminiature (all values in μ F)

	each	10 off	25 off	100 off
4V	8	32	64	125
6.4V	6.4	25	50	100
10V	4	16	32	64
16V	2.5	10	20	40
25V	1.6	6.4	12.5	25
40V	1	4	8	16
64V	0.64	2.5	5	10
Price	1/4	1/3	1/2	1/1

Small (all values in μ F)

	each	10 off	25 off	100 off
4V	800	1,250	2,000	3,200
6.4V	640	1,000	1,600	2,500
10V	400	640	1,000	1,600
16V	250	400	640	1,000
25V	160	250	400	640
40V	100	160	250	400
64V	64	100	160	250
Price	1/6	2/-	2/6	3/-

POLYESTER CAPACITORS (Mullard)

Tubular 10%, 160V: 0.01, 0.015, 0.022 μ F, 7d. 0.033, 0.047 μ F, 8d. 0.068, 0.1 μ F, 9d. 0.15 μ F, 11d. 0.22 μ F, 1/- 0.33 μ F, 1/3. 0.47 μ F, 1/6. 0.68 μ F, 2/3. 1 μ F, 2/8.

400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d. 6,800pF, 0.01, 0.015, 0.022 μ F, 7d. 0.033 μ F, 8d. 0.047 μ F, 9d. 0.068, 0.1 μ F, 11d. 0.15 μ F, 1/- 0.22 μ F, 1/6. 0.33 μ F, 2/3. 0.47 μ F, 2/8.

Modular, metalised, P.C. mounting, 20%, 250V: 0.01, 0.015, 0.022 μ F, 7d. 0.033, 0.047 μ F, 8d. 0.068, 0.1 μ F, 9d. 0.15 μ F, 11d. 0.22 μ F, 1/- 0.33 μ F, 1/5. 0.47 μ F, 1/8. 0.68 μ F, 2/3. 1 μ F, 2/9.

SEMICONDUCTORS: OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/- OC70, OC72, 2/3. AC107, OC75, OC170, OC171, 2/6. AF115, AF116, AF117, ACY19, ACY21, 3/3. OC140, 4/3. OC200, 5/- OC139, 5/3. OC25, 7/- OC35, 8/- OC23, OC28, 8/3.

SILICON RECTIFIERS (0.5A): 170 P.I.V., 2/9. 400 P.I.V., 3/- 800 P.I.V., 3/3. 1,250 P.I.V., 3/9. 1,500 P.I.V., 4/- (0.75A): 200 P.I.V., 1/6. 400 P.I.V., 2/- 800 P.I.V., 3/3. (6A): 200 P.I.V., 3/- 400 P.I.V., 4/- 600 P.I.V., 5/- 800 P.I.V., 6/-

SWITCHES (Chrome finish, Silver contacts): 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off 5/-. Toggle Switches: SP/ST, 3/6. SP/DT, 3/9. SP/DT (with centre position) 4/-. DP/ST, 4/6. DP/DT, 5/-

PRINTED CIRCUIT BOARD (Vero)

0.15in. Matrix: $3\frac{1}{2}$ in. \times $2\frac{1}{2}$ in., 3/3. $5\frac{1}{2}$ in. \times $2\frac{1}{2}$ in., 3/11. $3\frac{1}{2}$ in. \times $3\frac{1}{2}$ in., 3/11. 0.1in. \times $3\frac{1}{2}$ in., 5/6.

0.1 Matrix: $3\frac{1}{2}$ in. \times $2\frac{1}{2}$ in., 4/- 5in. \times $2\frac{1}{2}$ in., 4/6. $3\frac{1}{2}$ in. \times $3\frac{1}{2}$ in., 4/6. 5in. \times $3\frac{1}{2}$ in., 5/3.

SEND S.A.E. FOR 1969 CATALOGUE

DUXFORD ELECTRONICS (PE) 97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

(Visit us—at our new Mail Order, Wholesale and Retail Premises)

MINIMUM ORDER VALUE 5/-

C.W.O. Post and Packing 1/6

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. for insertion in the next available issue.

SITUATIONS VACANT

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

ENGINEERS. A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

RADIO TECHNICIANS

VACANCIES TO BE FILLED BY
OCTOBER 1969

A number of suitably qualified candidates are required for unestablished posts, leading to permanent and pensionable employment (in Cheltenham and other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to such candidates who can also offer "O" Level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications. A knowledge of Electro-mechanical equipment will be an advantage.

Pay according to age, e.g. at 19—£869 at 25—£1,130.

Prospects of promotion to grades in salary range £1,217-£2,038. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:


RECRUITMENT OFFICER (RT 37/54)

GOVERNMENT COMMUNICATIONS
HEADQUARTERS,
OAKLEY, PRIORS ROAD,
CHELTENHAM, GLOS. GL52 5AJ

EDUCATIONAL

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

EDUCATIONAL (continued)

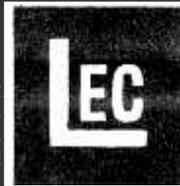

RADIO AND TELEVISION SERVICING RADAR THEORY AND MAINTENANCE TELECOMMUNICATIONS

This private College provides efficient theoretical and practical training in the above subjects. One-year day courses are available for beginners and shortened courses for men who have had previous training.

Write for details to:

The Secretary, London Electronics College, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373-8721

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam, home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV., automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541, INTERTEXT HOUSE,
LONDON, SW11

WANTED

DAMAGED AVO METERS, Models 7 & 8, any quantity. Send for packing instructions. **HUGGETT'S LTD.**, 2/4 Pawsons Road, West Croydon.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

WANTED: Popular Brand New Valves. R.H.S. Stamford House, 538 Great Horton Road, Bradford 7.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

WANTED (continued)

WANTED: New valves, transistors etc.; state prices. E.A.V. Factors, 202 Mansfield Road, Nottingham.

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

WANTED NEW VALVES, televisions, radios, grams, transistors, etc. **STAN WILLETTS**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

FOR SALE

£6,000 IN VOUCHERS GIVEN AWAY. See free Catalogue for details. Tools, materials, mechanical, electrical, thousands of interesting items. **WHISTON**, Dept. VW, New Mills, Stockport SK12 4HL.

PRECISION POTENTIOMETERS

Multi-turn, continuous or ganged from 25/-; carbon from 2/-. Also resistors, mains rectifiers, synchros, geared motors, chokes, capacitors, meters, microswitches, semiconductors. 8d. stamp catalogue. **F. HOLFORD & CO.**, 6 Imperial Square, Cheltenham.

THE IDEAL Panel Mounting Meter Movement for any Sensitive Test Meter etc. 200 Micro Amp F.S.D. 4 1/2in. x 4 1/2in. In clear plastic case. Our special price only 39/6d. P. & P. free. Limited number only. **WALTON'S WIRELESS STORES**, 55A Worcester Street, Wolverhampton, Staffs.

TOP TRADE DISCOUNTS FOR ALL

**COMPONENTS
VALVES
TUBES**

TRANSISTORS

Free Trade Catalogue
Engineers & Service Dealers Only

**WILLOW VALE
THE SERVICE DEPT.
WHOLESALEERS,**

4 The Broadway, Hanwell,

London, W.7

01-567 5400/2971

TELEVISION TUBES

Large stocks of television tubes, London's leading wholesale suppliers, all tubes complete with guarantee card. By return despatch. Terms: Cash with order, s.a.e. all enquiries.

14in. types. AW36/20, AW36/21, AW36/80, MW36/24, CRM141, CRM144, CME1402 etc.	£4 17 6
17in. types. MW43/80, AW43/80, CRM173, CME1702 MW43/69 CRM172, AW43/88, AW43/89, CME1703, CME1705 etc ...	£4 17 6
19in. types. AW47/90, AW47/91, CME1901, CME1903, CME1902, C19AH	£4 19 6
21in. types. AW53/88, AW53/89, CME2101, CME2303	£6 12 0
MW53/80, AW53/80, MW53/20, CRM211/2	£8 18 10
23in. types. AW59/90, AW59/91, CME2301, CME2303	£6 12 0
23in. Twin Panel. CME2306, A59-16W	£13 1 0
23in. Panorama. A59/11W etc.	£12 0 0
19in. Twin Panel. A47-13W, CME1906 etc.	£10 1 0
19in. Panorama. A47/11W etc.	£9 0 0

We stock all types of tubes.

Carriage and Packing 12/6d. per British Road Services.

Large stocks of valves, transistors components. L.O.P.T.'s, Electrolube, Servisol switch cleaner, Multicore solder. Service Tools.

WILLOW VALE ELECTRONICS LTD.

The Service Dept. Wholesalers, 4 The Broadway, Hanwell, London, W.6. Tel: 01-567 2971/5400
CATALOGUE TRADE ONLY. S.A.E. Please

YUKAN
SELF-SPRAY

Get these *air drying* **GREY HAMMER**
NOW! OR **BLACK WRINKLE**
(CRACKLE) Finishes

Yukan Aerosol spraybit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Finishes available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/6 as our counter or 14/6 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray can only) 12/6 carriage paid.

SPECIAL OFFER: I can plus optional transferable wrap-on trigger handle (value 5/-) for 18/6 carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

YUKAN, 307A, EDGWARE ROAD,
Dept. M/5, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

MORSE MADE EASY !!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, a.l.d. 01-660 2896 send 8d. stamp for explanatory booklet to:

89088 (BOX 11), 45 GREEN LANE, PURLEY, SURREY

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. **PHILPOTTS METAL WORKS LTD.,** Chapman Street, Loughborough.

BOOKS & PUBLICATIONS

GOVT. SURPLUS **WIRELESS EQUIPMENT HANDBOOK**

This useful Handbook gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment etc; also contained are some suggested modification details and improvements for the equipment. Incorporated in this revised edition is a surplus/commercial cross referenced valve and transistor guide. This book is invaluable to radio enthusiasts, radio clubs, universities and laboratories. The latest edition priced at 35/- per volume plus 5/- p & p is obtainable only from us at

GILTEXT (LEEDS) LTD

Dept. P.W., 24 Stansfield Chambers, Gt. George Street, Leeds 1.

s.a.e. with all enquiries, please. Extra postage for foreign orders.

BOOKS & PUBLICATIONS (continued)

SURPLUS HANDBOOKS

19 set Circuit and Notes	6/8 p/p 8d.
1156 set Circuit and Notes	6/6 p/p 8d.
H.R.O. Technical Instructions	5/6 p/p 8d.
38 set Technical Instructions	5/6 p/p 8d.
46 set Working Instructions	5/6 p/p 8d.
88 set Technical Instructions	7/- p/p 8d.
BC.221 Circuit and Notes	5/6 p/p 8d.
Wavemeter Class D Tech. Instr.	5/6 p/p 8d.
18 set Circuit and Notes	5/6 p/p 8d.
BC.1000 (31 set) Circuit and Notes	5/6 p/p 8d.
CR.100/B.28 Circuit and Notes	10/- p/p 8d.
R.107 Circuit and Notes	7/- p/p 8d.
AR.88D Instruction Manual	18/- p/p 8d.
82 set Circuit and Notes	6/6 p/p 8d.
Circuit Diagram 5/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.824, 22 set.	

52 set Sender and Receiver circuits 7/6 post free

Resistor colour code Indicator 2/6 p/p 8d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

FROM KAYE & WARD FUN WITH RADIO

BY GILBERT DAVEY

Edited by Jack Cox

The book of sound, tested designs for 'home made' beginners' radio sets written in straight forward, simple language for the modern, practically minded boy—though in fact suitable for any age of radio enthusiast just starting the hobby. 10in. x 7½in., 64pp., photos and diagrams, 16s. net.

194-200 BISHOPSGATE EC2

SERVICE SHEETS

SERVICE SHEETS. RADIO, TV. 5,000 Models. List 1/6. S.A.E. Enquiries. TELRAY, 11 Maudland Bank, Preston, Lancs.

RADIO, TELEVISION over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (1925-1969) for TELEVISIONS, RADIOS, TRANSISTORS, TAPE RECORDERS, RECORD PLAYERS, etc., by return post, with free fault-finding guide. Prices from 1/- Over 8,000 models available. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS)

Only 5/- each, plus large S.A.E.

(Uncrossed P.O.'s please, returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Mail order only.

MISCELLANEOUS

RHYTHM MODULES. Build your own rhythm box—simply, cheaply. Realistic sound guaranteed. S.A.E. for details. D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset.

ETCHED PRINTED CIRCUIT BOARD KITS. Full instructions 19/6 C.W.O. 'Circuit-tetch', 12 Cambridge Road, St. Albans, Herts.

MISCELLANEOUS (continued)

BUILD IT in a DEWBOX quality cabinet. 2in. x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

UFO DETECTOR CIRCUITS, data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed

65/- POST PAID

BIG BARGAIN PARCELS ONLY OF COMPONENTS 10/-

SALOP ELECTRONICS POST PAID
23 Wyle Cop, Shrewsbury, Shropshire. S.A.E. for lists

YOUR CALL SIGN ENGRAVED. White Letters Black Plate 6 x 1 1/2in. 5/6. 2 x 1/2in. Badge Pin, 4/-. Post Free. C.W.O. Workshops for Disabled, Northern Road, Cosham, Portsmouth. PO6 3EP.

ELECTRONIC SOUND and musical devices required for exploitation. Adequate finance available. Projects developed to pre-production stage required. Royalty payments guaranteed. Box 87

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 steps—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

ELECTRICAL

240 VOLT ELECTRICITY ANYWHERE



BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY
Exclusive World Scoop Purchase. The fabulous M.L. 8D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most Brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by DeKo-Remy. Not a midgeet converter, this magnificent machine is unobtainable elsewhere. Brand New and Fully Tested only £4.19.6 plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.
Dept. PW STANFORD ELECTRONICS, Bear Derby Road, North Fromensade, Blackpool, Lancashire.

MIGHTY MIDGET Converter
GIVES YOU 240v ELECTRICITY ANYWHERE

A marvellous unit giving 240 volts output from a 12 VOLT BATTERY. Runs AC/DC equipment, Lighting, shavers, fluorescent. Exceptionally low battery consumption. Made at tremendous expense for Govt. by famous manufacturer. Govt. Release/Scoop Purchase makes price NEW AND TESTED only 79/6. post/packing 10/6. Two units 28 post free, with full instructions to run TV, Drills, Power Tools, etc. Ideal for Caravans, Boat Owners, Campers.

Dept. P.W. GLOBE SCIENTIFIC LTD.
22/24 Cawoods Yard, Mill Street, Marsh Lane, Leeds 2.

AERIALS

Enthusiasts THE T.M.P. EXPERIMENTAL AERIAL KIT

A unique collection of alloy elements, dipoles, booms, clamps, mast reflectors, nuts & bolts, cables even a compass! etc., to make up various experimental aerials to cover all bands. This includes TV transmissions, SW for the radio amateur, VHF for BBC FM. Amateurs on 2 and 4 MTrs, Aircraft, Police etc., UHF for experiments on BBC 2 and Ultra High Frequencies. These Kits can be used indoor or outdoor. Robust construction with simplified detailed plans for easy assembly. *The Wonder T.M.P. Kit costs only 89/6—no extra for carriage.* Despatched to any address in UK within 7 days.
TUBULAR METAL PRODUCTS
7 LOWESMOOR TERRACE,
WORCESTER

RECEIVERS & COMPONENTS

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 1-20 watt, 12/6 Post Free. WHITSAM ELECTRICAL, 33 Drayton Green Road, West Ealing, W.13.

NEW VHF KIT

Receives Television Sound, Ambulances, Aircraft, Radio 2, 3 and 4 on VHF etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. The Kit comes with easy to follow instructions and circuit. Powered by 9v Battery. Complete with built in Jack Plug Socket for use with Earphones or Amplifier.

ONLY 57/- P. & P. FREE U.K. ONLY

Postal Orders, Cheques to Dept. P.W.1

Galleon Trading Co., 296A Lodge Lane, Romford, Essex

BRAND NEW ELECTROLYTICS, 15 Volt, 1, 2, 5, 6, 8, 10, 15, 20, 30, 40, 50, 100, 200 mfd. 7/6 per doz. postage 1/-. The C. R. Supply Co., 127 Chesterfield Road, Sheffield 8.

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/- P. & P. 2/-. With a guaranteed minimum of 85 transistors.

SPECIAL BARGAIN PACK, 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 65/- P. & P. 6/6. With a guaranteed minimum of 350 transistors.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4x OC28) 10/- P. & P. 2/-.
TRIM POTS, on 2in x 4in boards + other components. 100Ω, 500Ω, 15K, 20K. State requirements. 5 boards 10/- P. & P. 2/-.
NPN GERMANIUM 105 1 WATT POWER TRANSISTORS on small heat sink, on 2in x 4in panel. 5 for 10/- P. & P. 2/-.
POWER TRANSISTORS sim. to 2N174 ex eqpt., 4 for 10/- P. & P. 2/-.
POWER TRANSISTORS sim. to 2N174 on Finned Heat Sink (10D), 4 for £1. P. & P. 5/-.
LONG ARM TOGGLE SWITCHES ex eqpt. SPST 13/8 doz., DPST 15/- doz. P. & P. all types 2/- doz.
ORGAN BUILDERS' SPECIAL 500 TONS TRANSISTORS on panels. £4. P. & P. 6/-.
OVERLOAD CUT OUTS. Panel mounting in the following values... 5/- each. 2, 3, 4, 7, 10 amp. P. & P. 1/6.
MINIATURE GLASS NEONS, 12/6 doz. P. & P. 1/6.
150 PIV. 10 amp. DIODE BRIDGE RECTIFIERS on HEAT SINK. 12/- + 2/- P. & P. ea.
LARGE CAPACITY ELECTROLYTICS 4 1/2in, 2in diam. Screw terminals. All at 6/- each + 1/6 each P. & P.
4,000mF 72V d.c. wkg.
10,000mF 25V d.c. wkg.
6,600mF 45V d.c. wkg.
16,000mF 25V d.c. wkg.
25,000mF 12V d.c. wkg.

KEYTRONICS, 52 Earls Court Road London, W.8. Mail order only

RECEIVERS & COMPONENTS (continued)

D.I.Y.—All materials and components for construction of high fidelity loudspeaker systems (empty enclosures, BAF wadding, Tygan, Vynair fabric, cross-overs, etc.). Many other audio accessories and speaker kits. 6d. in stamps for lists. P. F. & A. R. HELME, Dept. PW, Summerbridge, Harrogate, Yorks.

BAKER & BAINES

for Television and F.M. Aerials

Examples of prices: FM Dipole 21/-, H 38/-, BBC dipole 30/-, X 38/-, H 42/-, 3 ele 69/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/6, 11 ele 57/6, Combined BBC/ITA 1 + 5 45/-, H + 5 69/-, X + 5 75/-, BBC2 8 ele 29/-, 14 ele 37/-, 18 ele 54/-, 22 ele 63/-.

All types generally available including accessories—prices include mounting clamps and postage.
11 Dale Crescent, New Tupton, Chesterfield.

SIGNAL INJECTOR. Transistorised square wave generator probe, British Made, only 19/6, P & P 1/6 S A E for details and lists WILSIC ELECTRONICS LTD., 6 Copley Road, Doncaster, Yorks.

TINY TRANSISTOR RELAY for model control, light switches, experiments etc. Only 1in. square, 330Ω coil, 30/- post free. H. R. RADIO, 174 Bramall Lane, Sheffield. S2 4RF.

BARGAIN LIST

Transistors OC70, OC71, OC72, OC45, OC171 at 8/- each. OC140, B8Y26, BYZ12, BYZ16 at 8/- each. Metal Rectifiers, 12v lamp contact cooled tube, 8/9 each. Metal Rectifiers, 12v 2amp at 8/6 each. Metal Rectifiers, 12v 4amp at 7/8 each. TV Metal Rectifiers, 250v 300mA at 4/6.
Edge-wise Volume Controls 5k Jap Replacements, 3/6 each. Panel Meters, new square Clear Plastic, 1.65 x 1.65 0-1ma Front at £1.0.0 each.
Panel Meters 500 micro amp at £1.4.0 each.
Toggle Switches SPST, 3/6. DPDT at 3/- each.
New Resistances small 1/2 watt, at 3d. each.
Transformers-Subminiature output 3 ohms for OC72 etc. at 2/6 each.
Transformers-Subminiature Driver for above at 2/6 each.
Jack Plugs Standard at 2/-, Jack Sockets at 1/6.
Pax Panels 6in. x 4in. x 1/16in. at 10d. 8in. x 6in. at 1/6 each.
Condensers 25mf 25v at 1/- 1/2in. Iron dust cores at 4d. per doz.
Miniature slide switches DPDT at 1/6 each.
Aluminium Panels 6in. x 4in. at 1/8. 8in. x 6in. at 3/- each.
Mail Order Only. Post & Packing 1/- S.A.E. for List.

HAIR SERVICES

38 GLOUCESTER ROAD, FELTHAM, MIDDLESEX

TELEVISION I.F. STRIPS (lead valves)

From BBC, 2 converters ideal for spares, contains smoothing capacitor, dropper resistors, 7 valve holders, I.F. transformers, coil formers, capacitors, resistors, diodes, tag strips, chokes, etc., etc., on chassis 11in. x 3 1/2in., no information or circuit. Brand new in boxes, 14/6.
MAINS TRANSFORMERS
250V input, output 10V at 500mA, 24V at 100mA, 32V at 10mA, size 2 1/2in. x 1 1/2in. x 1 1/2in. (drop through type) ideal for transistor power supply, 10/- post paid.
250V input, output 22V at 1 1/2A, size 2in. x 2in. x 2 1/2in., 11/- post paid.
MIXED bag of silver mica and ceramic capacitors, approx. 150, 10/- per bag.
ERIE Thyristors for drill speed controls 400 p.i.v. at 5A, 12/6.
HUNTS 0-1mfF, 350v paper capacitors, P.C. type, upright mounting, 8/6 doz., 15/- per 100, post paid per 100.
TUBULAR ceramic capacitors, P.C. type, 3-5pF and 500pF, only 6/- per 100, 1/8 doz.
MULLARD CAPACITORS 50 + 50 + 50mF, 350v, 6/-.
TRANSISTOR ELECTROLYTICS 2mf 6v, 4mf 6v, 20mf 6v, 50mf 6v, 100mf 6v, 8d. each, 100mF, 250v, 1/-, 400mF 15v, 500mF 9v, 8d., 1,000mF 50v can type, 4/-.
SPEAKER COVERING 7in. x 4in. perforated flexible plastic. Stimulated chrome on one side, 1/6 each 12/- doz.
HUNTS 2,500mfd. 50v, brand new, 6/6.
SILVER MICA capacitors 80pF size only 1/2in. x 1/2in. 200v, 4/- per 100.
UNMARKED 8X683 silicon diodes. 800 p.i.v. at 1 1/2 doz. Tested and guaranteed, 8d. each, 6/- doz.
GT46B equiv. to OC71, OC45, etc. 1/8 each, 12/- doz. Manufacturers marked, not rejects.
P.C. BOARDS 2 1/2in. x 3 1/2in. Ideal for mock-ups. Ready drilled and etched, 8/6 doz.
0.47mF, 30v, P.C. disc ceramics, 8/- doz., £1 per 100.
MAIL ORDER ONLY BAE FOR LISTS
Postal charges: up to £1 + 1/6; £1-£2 + 2/-; £2-£5 + 3/6; over £5 FREE.

A. J. H. ELECTRONICS

59 Waverley Road, The Kent, Rugby, Warwickshire.

RECEIVERS & COMPONENTS
(continued)

COMPLETE RANGE of Amateur, Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

BRAND NEW SEMICONDUCTORS

IN914 1/6	2N2005A 8/-	AC126 4/-	BCY39 6/6
IN916 1/6	2N2906 8/-	AC127 3/-	BCY70 5/6
IN4007 4/6	2N3906A 9/-	AC174 5/6	BCY71 5/6
1B021 4/-	2N2926	AC187 13/-	BD124 13/-
1B025 5/-	Green 3/6	AC188 12/-	BF115 4/6
1B130 2/6	Yellow 3/6	ACY17 5/-	BF167 6/6
AA119 2/-	Orange 3/-	ACY18 5/-	BF180 3/6
BY210 9/-	Red 2/9	ACY19 5/-	BF184 7/6
BY211 7/6	Brown 2/6	ACY20 5/-	BF194 6/6
BY213 5/-	2N3053 6/6	ACY21 5/-	BFX12 5/6
OA5 2/6	2N3054 12/6	ACY22 4/-	BFY13 5/6
OA79 1/9	2N3055 15/-	AD140 3/-	BFY50 4/6
OA81 1/6	2N3391 7/6	AD149 3/-	BFY51 4/6
OA85 1/6	2N3391A 6/-	AD161 7/6	BFY52 4/6
OA91 1/6	2N3393 6/6	AF114 5/-	BKX19 5/6
OA200 2/-	2N3702 4/-	AF116 5/-	BKX20 5/6
OA212 2/-	2N3703 4/6	AF117 5/-	BKX26 4/-
2N696 5/-	2N3704 5/6	AF124 5/-	BKX27 4/-
2N697 5/-	2N3705 4/6	AF126 5/-	BKX28 4/-
2N706 3/-	2N3706 4/-	AF127 5/-	BKX29 4/-
2N705A 3/-	2N3707 4/-	AF161 3/6	BKX95A 3/6
2N1302 4/6	2N3708 4/-	AF196 11/-	OC28 3/-
2N1303 4/6	2N3709 4/-	ASX28 5/6	OC35 7/6
2N1304 5/6	2N3710 4/-	ASX28 5/6	OC36 6/6
2N1305 5/6	2N3711 4/-	ASZ21 7/6	OC44 4/-
2N1306 6/6	2N3819 9/-	BC107 3/6	OC45 2/6
2N1307 6/6	2N3820 20/-	BC108 3/6	OC71 2/6
2N1308 5/-	2N3823 21/6	BC109 3/6	OC72 4/6
2N1309 3/-	2N4058 6/6	BC113 6/6	OC75 4/6
2N2147 17/6	2N4059 5/-	BC147 5/-	OC81 4/-
2N2148 12/6	2N4060 5/-	BC148 4/6	OC83 4/6
2N2160 14/6	2N4061 5/-	BC149 5/-	OC139 6/6
2N2989A 5/6	2N4062 5/6	BCY31 4/6	OC140 6/6
2N2946 11/6	40350 17/6	BCY32 7/6	OC202 3/6
2N2904 5/-	40361 12/6	BCY33 5/6	OC202 3/6
2N2904A 5/-	40362 14/6	BCY34 4/6	OC271 3/6
2N2905 8/-	AC107 6/6	BCY38 5/6	ORP12 3/6

Send 6d. stamp for complete list. Over 1,000 types Semiconductors in stock. Capacitors, Resistors and Pots also available.

A. MARSHALL & SON (London) LTD.

28 Cricklewood Broadway,
London, N.W.2
01-452 0161/3



with a Dewtron "NEW DIMENSIONS" 3-Dimensional effects amplifier. Gives Big Hall Stereo effect to most radios, tapes, etc. PLUS fully adjustable echo, vibrato and tone. 9 volt model, 8 gns. Speaker, 25/- extra. 6/12V car model, 10 gns. incl. speaker. Post and ins. 5/- either model. Write now—right now.

D.E.W. LTD.,
P.W., RINGWOOD ROAD, FERNDOWN, DORSET

MOBILE S.W. LISTENERS

The Halson Mobile Antenna for
AMATEUR RECEIVING and TRANSMITTING

The most efficient mobile All-Band Whip on the market. COILS FOR ALL BANDS. Complete with one coil £6.17.6, plus 3/6. Extra coils £3.17.6, plus 3/-.

From leading amateur radio stores or direct from the manufacturers:

HALSON ELECTRICAL SERVICES
Dover Road, off Ansdell Road,
Blackpool.

Est. 1943 **JOHNSONS** Tel: 24864

VHF and Short-Wave kits for the Amateur enthusiast and constructor. For 2 and 4 metres, the unique two transistor model SR2/P, 70-150Mc/s, 75/6, p.p. 4s. New super 5V all-wave, all-band kit, also "Mini-Amp" self-contained, cabinet, size a mere 4½ x 3½ x 2½. Write today, enclosing a stamped addressed envelope for interesting free literature, and details, direct to

JOHNSON'S (RADIO)
St. Martin's Gate, Worcester

SPECIAL FRINGE AREA BBC-2 & COLOUR TV AERIAL

Unbeatable Offer
ONLY 45/-
(Carr. 5/-)

For loft or roof fixing. Complete with mounting arm. State Channel required or nearest transmitter. Hundreds sold. Special low-loss co-axial cable 2/3 yd. Socket 2/6.

SPEAKER BARGAIN!
Famous English 12in. high flux, heavy cone, 10 watts speaker with built-in tweeter, excellent bass response. 15 ohms.
(P. & I. 5/6) **35/-**

ELECTRAMA Dept. PW86
1 GEORGE STREET, HAILSHAM, SUSSEX

PLEASE MENTION
"PRACTICAL WIRELESS"
WHEN REPLYING TO
ADVERTISEMENTS

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEGE, YORKS.
Tel. Cleckheaton 2866

Indicator Unit type 26
Size 12x9x9in. with outer case. Fitted with 2½" tube C.R.T. type CV1526. Nine B7G valves. Clean condition, but not tested. 32/6, p. & p. 10/-
Lumulator and Secant Gear Unit. Delight for the model maker. 12/6, p. & p. 8/6.
Silicon Rectifier 500mA, 500 P.I.V. No duds. 2/6, post paid. 24/- per dozen, post paid.

Jap Ear Piece. Magnetic 8 ohm. Small and large plug. 1/11, post paid.
Reclaimed TV tubes with six months guarantee. 17in. type AW43/88, AW43/80, 40/-; MW43/69, 30/-; 14in. types, 17/-; All tubes, 12/- carriage.

Speakers removed from TV sets. All PM and 3 ohms. 8in. round and 8x5in., 6/6, p. & p. 3/6.
6in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

6x4in., 3/-, p. & p. 3/-; 6 for 24/-, post paid.
7x4in., 5/-, p. & p. 3/-; 6 for 34/-, post paid.
5in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

Slot Speakers, 8x2½in., 5/-, p. & p. 3/-; 6 for 30/-, post paid.

Untested 12-channel 14in. TV sets, 20/-, carriage 15/-; Passenger train, double rate.
Untested Pye, KB, RDG, Ekko 17in. TV sets. Bush 17in. TV sets, 50/- each, carriage 15/-; Passenger train, double rate.

VALVE LIST
Ex Equipment 3 months' guarantee

Single Valves Post 7d., over 3 Valves p. & p. paid.			
10FL, EF90, EB91, ECL80, EF90, FY82, PZ50, 30P3. All at 10/- per dozen, post paid.			
6BP12 1/6	PCL82 5/-	6BW7 2/6	
EB91 9d.	PL36 5/-	6K7 1/9	
EF85 3/-	PL38 5/-	6U4 5/-	
EBF60 3/-	PL81 4/-	6V6 1/9	
EC081 3/-	PY33 5/-	6PZ8 5/-	
EC082 3/-	PY81 1/6	10P13 2/6	
EC083 4/-	PY82 1/6	18SBT 3/6	
ECL80 1/6	PZ80 5/-	20D1 3/-	
EF90 1/6	U191 5/-	20P1 5/-	
EF91 9d.	U281 5/-	30P3 2/6	
EY51 2/6	U288 5/-	30PL1 5/6	
EY86 6/-	U301 5/-	30P12 4/-	
PC34 5/-	U359 5/-	30F5 2/6	
PCF90 3/-	U381 5/-	30FL1 5/-	
PCL82 4/-	6B5 1/8	6/30L2 5/-	

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5 4/9	DY84 5/6	EZ80 3/9	PL600 12/9
1R5 4/3	DY87 5/6	EZ81 4/6	PL604 13/3
1T4 2/6	EAFC80 5/9	KT61 3/3	PY32 10/-
384 5/9	EB41 2/-	KT66 15/9	PY33 10/-
374 5/6	EBF80 6/-	N78 14/6	PY81 5/-
6AQ5 4/6	EBF89 5/9	PAB80 5/9	PY82 5/-
6L18 6/-	EC081 3/9	PC86 10/3	PY83 5/3
30C18 3/9	EC082 4/3	PC88 10/3	PY88 6/6
30FL1 12/6	EC083 4/9	PC97 7/3	PY800 7/3
30FL12 14/3	EC085 5/6	PC900 2/-	PY801 6/6
30FL14 10/3	ECH35 5/6	PC084 6/3	R19 9/6
30P4 11/6	ECH42 10/6	PC089 9/9	U26 12/9
30P19 11/6	ECH81 5/9	PC189 11/6	U26 11/6
30PL1 12/6	ECL80 6/3	PCF80 6/3	U191 12/3
OCX35 9/9	ECL82 6/3	PCF82 9/9	UAB80 6/9
CL33 17/6	ECL86 7/6	PCF81 6/9	UC81 3/3
DAC32 5/9	EF83 3/6	PCF805 5/9	UBF89 6/3
DAF91 4/3	EF80 4/9	PCF808 10/3	UC84 7/9
DAP96 6/3	EF85 5/-	PCL82 6/9	UC85 6/-
DF33 7/6	EF86 6/3	PCL83 9/9	UCF80 8/-
DF91 2/9	EF89 4/9	PCL84 7/-	UCH42 10/6
DF96 5/11	EF183 5/9	PCL85 6/9	UC81 7/-
DK32 6/9	EF184 5/6	PCL86 8/3	UCL82 6/9
DK91 4/9	EH90 6/-	PPL20012/-	UP41 9/6
DK96 6/6	EL33 3/3	PL36 9/3	UF89 6/6
DL85 4/9	EL41 10/3	PL81 7/-	UL41 10/3
DL92 5/9	EL84 4/6	PL82 6/9	UL84 9/6
DL94 5/6	EY31 7/3	PL83 6/9	UY41 6/6
DL96 6/9	EY86 6/-	PL84 6/3	UY85 5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling

MINIMUM CHARGE 2/6. No C.O.D. orders accepted.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANgham 8403
Open all day Saturday

OA2	6/-	6AK5	5/-	6BW7	12/-	6LD20	5/6
OA3	8/6	6AK6	11/6	6BZ6	6/-	6N7GT	6/6
OB2	6/-	6AL5	3/-	6BZ7	10/-	6P1	11/6
OB3	6/-	6AM4	22/-	6C4	6/6	6P25	13/-
OC3	6/6	6AM5	5/-	6C5GT	6/6	6P28	12/-
OD3	6/-	6AM6	4/-	6C6	4/-	6Q7	7/-
OM10	11/-	6AM8	8/-	6C8G	7/-	6RA7	7/-
1AX2	12/-	6AN8	10/-	6C9	17/8	6R67	6/-
1B3GT	7/-	6AQ5	6/-	6CB6	5/-	6R77	4/6
1C6GT	6/-	6AQ6	10/-	6CD6GA	6/-	6R77	7/6
1O4GT	8/-	6A35	6/-	6CG7	8/-	6RN7GT	5/6
1H5GT	7/-	6AR6	6/-	6CH6	11/-	6RQ7	7/-
1L4	3/-	6AR5	6/6	6CL6	9/-	6RB7	7/-
1R5	6/-	6AR6	7/-	6CL8	15/-	6R8	3/6
1R6	5/-	6AR7G	15/-	6CU6	12/-	6R8	3/6
184	4/6	6AT6	4/6	6CW4	12/-	6RGT	12/6
1T4	4/-	6AU4GTA	6/-	6CY5	7/-	6U8	8/-
1U4	8/-	6A25	6/-	6D3	7/6	6V8GT	6/6
1U5	8/6	6A26	5/-	6D4	17/8	6X4	4/6
1V2	9/-	6A28	10/-	6DC6	13/6	6X5GT	5/6
1X2B	7/-	6AV6GTA	12/6	6DK6	8/-	6X8	11/6
1Z2	25/-	6AV6	5/6	6DQB	11/-	6Y6G	11/6
2C28A	8/-	6AV6	5/6	6DQ8	15/-	6Z5	13/6
2C40	8/-	6AW2A11/-	6/-	6DT8	8/-	6Z7	20/-
2C3	8/-	6AX4GTA	8/-	6E8	11/-	6Z8	20/-
2C4	12/-	6A25	6/-	6E8	11/-	6Z8	20/-
2D21	6/-	6AX6GT	12/6	6F7	9/-	6Z8	20/-
2E26	27/6	6AX7	10/-	6F7	9/-	6Z8	20/-
2X2	5/-	6AX7	10/-	6F7	9/-	6Z8	20/-
3A4	4/6	6B6	15/-	6F7	9/-	6Z8	20/-
3B38	40/-	6B6	15/-	6F7	9/-	6Z8	20/-
3C4	7/6	6B6	15/-	6F7	9/-	6Z8	20/-
3R4	6/-	6BA7	15/-	6F7	9/-	6Z8	20/-
3V4	6/6	6BC5	3/6	6F7	9/-	6Z8	20/-
4B32	30/-	6B6	15/-	6F7	9/-	6Z8	20/-
BR4G	10/-	6BF6	15/-	6F7	9/-	6Z8	20/-
OU4G	5/6	6BF6	15/-	6F7	9/-	6Z8	20/-
5U4G	7/-	6BF7	12/-	6F7	9/-	6Z8	20/-
5U8	8/-	6BG6G	11/-	6F7	9/-	6Z8	20/-
5Y3GT	5/6	6BH6	8/-	6F7	9/-	6Z8	20/-
5Z3	8/-	6B76	8/-	6F7	9/-	6Z8	20/-
5Z4G	7/-	6BK4	20/-	6F7	9/-	6Z8	20/-
6R02L	14/-	6BK7A	9/-	6F7	9/-	6Z8	20/-
6A8G	5/6	6BL7GTA	6/-	6F7	9/-	6Z8	20/-
6AB4	9/6	6B76	8/-	6F7	9/-	6Z8	20/-
6AB7	4/-	6BN6	7/6	6F7	9/-	6Z8	20/-
6AC7	4/-	6BN8	8/-	6F7	9/-	6Z8	20/-
6AD4	15/-	6BQ6GT	6/-	6F7	9/-	6Z8	20/-
6AP4A	6/-	6BQ7A	12/-	6F7	9/-	6Z8	20/-
6AG5	3/-	6B76	8/-	6F7	9/-	6Z8	20/-
6AG7	6/6	6B76	8/-	6F7	9/-	6Z8	20/-
6AH6	10/-	6BR5	12/6	6F7	9/-	6Z8	20/-
6AJ6	9/-	6BR7	25/-	6F7	9/-	6Z8	20/-
6A78	5/8	6BW6	12/6	6F7	9/-	6Z8	20/-

First Quality Fully Guaranteed



ELECTRONIC VALVES

Combined effect of increase in Purchase Tax and S.E.T. and import restrictions forced us to introduce an increase of 1d. per shilling which must be added to the total of each order.

12BY7	10/-	30FL13	8/-	812A	60/-	E83F	20/-
12C06	12/-	30FL14	14/6	813	75/-	E88C	23/-
12DQ7	10/-	30L1	6/-	837	15/-	E88CC	12/6
12E1	20/-	30L15	16/-	868A	14/-	E130L100	10/-
12E14	52/6	30L17	16/-	884	10/-	E180F	17/6
12K5	10/-	30P12	15/-	5670	10/-	EAF80110	10/-
12K8	8/-	30P19	14/-	5751	11/-	EABC80	6/-
12Q7GT	5/6	30PL1	15/-	5783	12/-	EB33	8/-
12SAG7	4/6	30PL13	17/6	5886	40/-	EB41	8/6
12S7	6/6	30P15	17/6	6020	27/6	EB33	6/-
12S7GT	6/6	35A5	10/-	6146	27/6	EBF80	6/6
12S8	12/-	35B5	12/-	6197	20/-	EBF83	8/-
12S8GT	6/6	35C5	6/6	6360	25/-	EBF89	6/6
12S9	5/6	35D5	12/-	6390	40/-	EBL1	12/-
12S9GT	6/6	35E5	12/-	6390	40/-	EBL1	12/-
12T1	18/-	35F5	12/-	6390	40/-	EBL1	12/-
12T1GT	6/6	35G5	12/-	6390	40/-	EBL1	12/-
12T2	18/-	35H5	12/-	6390	40/-	EBL1	12/-
12T2GT	6/6	35I5	12/-	6390	40/-	EBL1	12/-
12T3	18/-	35J5	12/-	6390	40/-	EBL1	12/-
12T3GT	6/6	35K5	12/-	6390	40/-	EBL1	12/-
12T4	18/-	35L5	12/-	6390	40/-	EBL1	12/-
12T4GT	6/6	35M5	12/-	6390	40/-	EBL1	12/-
12T5	18/-	35N5	12/-	6390	40/-	EBL1	12/-
12T5GT	6/6	35O5	12/-	6390	40/-	EBL1	12/-
12T6	18/-	35P5	12/-	6390	40/-	EBL1	12/-
12T6GT	6/6	35Q5	12/-	6390	40/-	EBL1	12/-
12T7	18/-	35R5	12/-	6390	40/-	EBL1	12/-
12T7GT	6/6	35S5	12/-	6390	40/-	EBL1	12/-
12T8	18/-	35T5	12/-	6390	40/-	EBL1	12/-
12T8GT	6/6	35U5	12/-	6390	40/-	EBL1	12/-
12T9	18/-	35V5	12/-	6390	40/-	EBL1	12/-
12T9GT	6/6	35W5	12/-	6390	40/-	EBL1	12/-
12T10	18/-	35X5	12/-	6390	40/-	EBL1	12/-
12T10GT	6/6	35Y5	12/-	6390	40/-	EBL1	12/-
12T11	18/-	35Z5	12/-	6390	40/-	EBL1	12/-
12T11GT	6/6	35A6	12/-	6390	40/-	EBL1	12/-
12T12	18/-	35B6	12/-	6390	40/-	EBL1	12/-
12T12GT	6/6	35C6	12/-	6390	40/-	EBL1	12/-
12T13	18/-	35D6	12/-	6390	40/-	EBL1	12/-
12T13GT	6/6	35E6	12/-	6390	40/-	EBL1	12/-
12T14	18/-	35F6	12/-	6390	40/-	EBL1	12/-
12T14GT	6/6	35G6	12/-	6390	40/-	EBL1	12/-
12T15	18/-	35H6	12/-	6390	40/-	EBL1	12/-
12T15GT	6/6	35I6	12/-	6390	40/-	EBL1	12/-
12T16	18/-	35J6	12/-	6390	40/-	EBL1	12/-
12T16GT	6/6	35K6	12/-	6390	40/-	EBL1	12/-
12T17	18/-	35L6	12/-	6390	40/-	EBL1	12/-
12T17GT	6/6	35M6	12/-	6390	40/-	EBL1	12/-
12T18	18/-	35N6	12/-	6390	40/-	EBL1	12/-
12T18GT	6/6	35O6	12/-	6390	40/-	EBL1	12/-
12T19	18/-	35P6	12/-	6390	40/-	EBL1	12/-
12T19GT	6/6	35Q6	12/-	6390	40/-	EBL1	12/-
12T20	18/-	35R6	12/-	6390	40/-	EBL1	12/-
12T20GT	6/6	35S6	12/-	6390	40/-	EBL1	12/-
12T21	18/-	35T6	12/-	6390	40/-	EBL1	12/-
12T21GT	6/6	35U6	12/-	6390	40/-	EBL1	12/-
12T22	18/-	35V6	12/-	6390	40/-	EBL1	12/-
12T22GT	6/6	35W6	12/-	6390	40/-	EBL1	12/-
12T23	18/-	35X6	12/-	6390	40/-	EBL1	12/-
12T23GT	6/6	35Y6	12/-	6390	40/-	EBL1	12/-
12T24	18/-	35Z6	12/-	6390	40/-	EBL1	12/-
12T24GT	6/6	35A7	12/-	6390	40/-	EBL1	12/-
12T25	18/-	35B7	12/-	6390	40/-	EBL1	12/-
12T25GT	6/6	35C7	12/-	6390	40/-	EBL1	12/-
12T26	18/-	35D7	12/-	6390	40/-	EBL1	12/-
12T26GT	6/6	35E7	12/-	6390	40/-	EBL1	12/-
12T27	18/-	35F7	12/-	6390	40/-	EBL1	12/-
12T27GT	6/6	35G7	12/-	6390	40/-	EBL1	12/-
12T28	18/-	35H7	12/-	6390	40/-	EBL1	12/-
12T28GT	6/6	35I7	12/-	6390	40/-	EBL1	12/-
12T29	18/-	35J7	12/-	6390	40/-	EBL1	12/-
12T29GT	6/6	35K7	12/-	6390	40/-	EBL1	12/-
12T30	18/-	35L7	12/-	6390	40/-	EBL1	12/-
12T30GT	6/6	35M7	12/-	6390	40/-	EBL1	12/-
12T31	18/-	35N7	12/-	6390	40/-	EBL1	12/-
12T31GT	6/6	35O7	12/-	6390	40/-	EBL1	12/-
12T32	18/-	35P7	12/-	6390	40/-	EBL1	12/-
12T32GT	6/6	35Q7	12/-	6390	40/-	EBL1	12/-
12T33	18/-	35R7	12/-	6390	40/-	EBL1	12/-
12T33GT	6/6	35S7	12/-	6390	40/-	EBL1	12/-
12T34	18/-	35T7	12/-	6390	40/-	EBL1	12/-
12T34GT	6/6	35U7	12/-	6390	40/-	EBL1	12/-
12T35	18/-	35V7	12/-	6390	40/-	EBL1	12/-
12T35GT	6/6	35W7	12/-	6390	40/-	EBL1	12/-
12T36	18/-	35X7	12/-	6390	40/-	EBL1	12/-
12T36GT	6/6	35Y7	12/-	6390	40/-	EBL1	12/-
12T37	18/-	35Z7	12/-	6390	40/-	EBL1	12/-
12T37GT	6/6	35A8	12/-	6390	40/-	EBL1	12/-
12T38	18/-	35B8	12/-	6390	40/-	EBL1	12/-
12T38GT	6/6	35C8	12/-	6390	40/-	EBL1	12/-
12T39	18/-	35D8	12/-	6390	40/-	EBL1	12/-
12T39GT	6/6	35E8	12/-	6390	40/-	EBL1	12/-
12T40	18/-	35F8	12/-	6390	40/-	EBL1	12/-
12T40GT	6/6	35G8	12/-	6390	40/-	EBL1	12/-
12T41	18/-	35H8	12/-	6390	40/-	EBL1	12/-
12T41GT	6/6	35I8	12/-	6390	40/-	EBL1	12/-
12T42	18/-	35J8	12/-	6390	40/-	EBL1	12/-
12T42GT	6/6	35K8	12/-	6390	40/-	EBL1	12/-
12T43	18/-	35L8	12/-	6390	40/-	EBL1	12/-
12T43GT	6/6	35M8	12/-	6390	40/-	EBL1	12/-
12T44	18/-	35N8	12/-	6390	40/-	EBL1	12/-
12T44GT	6/6	35O8	12/-	6390	40/-	EBL1	12/-
12T45	18/-	35P8	12/-	6390	40/-	EBL1	12/-
12T45GT	6/6	35Q8	12/-	6390	40/-	EBL1	12/-
12T46	18/-	35R8	12/-	6390	40/-	EBL1	12/-
12T46GT	6/6	35S8	12/-	6390	40/-	EBL1	12/-
12T47	18/-	35T8	12/-	6390	40/-	EBL1	12/-
12T47GT	6/6	35U8	12/-	6390	40/-	EBL1	12/-
12T48	18/-	35V8	12/-	6390	40/-	EBL1	12/-
12T48GT	6/6	35W8	12/-	6390	40/-		



Interested in cutting your motoring costs?

You can save a considerable amount of money by tackling some of the car maintenance jobs yourself and the **PRACTICAL MOTORIST ANNUAL** is designed specially to help you. Authoritative articles and step-by-step instructions show you how to maintain the engine, ignition, cooling, carburation, transmission, suspension and steering, brakes, tyres, bodywork, electrics, etc., and give advice on simple tuning.

With holidays in mind there is a most helpful section on camping and caravanning.

EVERY MOTORIST NEEDS THE

PRACTICAL

motorist

Now on sale 3/6

annual

PRACTICAL WIRELESS

Query Service

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) **We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

QUERY COUPON

This coupon is available until 6th June, 1969 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, JUNE 1969

ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

SOLID STATE-HIGH FIDELITY AUDIO EQUIPMENT


Mono or Stereo Audio. Equipment developed from Dinsdale Mk II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM £15.5.0

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately.

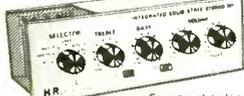SEND FOR FREE BROCHURE (No. 21) TODAY!
DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



MA7 MONO
£8.10.0

For complete listening satisfaction choose either the—

OR THE STEREO MA8 POST PACKING 5/- EITHER MODEL

£16.10.0

OPTIONAL MAINS UNIT PS20 62/6d. p.p. 4/-

Illustrated leaflets 12 and 14 FREE on request.

INTEGRATED TRANSISTOR AMPLIFIERS MA66 12 WATTS STEREO

We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways—with fantastic power and quality with far greater adaptability, with freedom for battery or mains operation.


ELECTRONIC ORGANS KITS TO BUILD YOURSELF AND COMPLETE UNITS.

THE MAYFAIR

A completely new development in portable electronic musical instruments and a new field for the home constructor. The 'MAYFAIR' produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 165 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive veneer covered cabinet with carry handle.

Deferred terms available
COMPLETE KIT
Deposit £25.0.0,
12 monthly payments of £7.
TOTAL £113.0.0

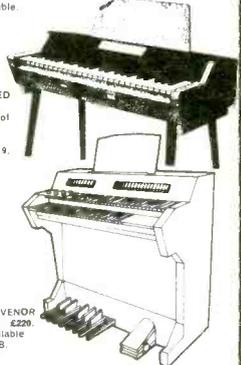BUILT AND TESTED
Deposit £30.0.0 and
12 monthly payments of £9.
Total £144.0.0
THE MAYFAIR
99 GNS. Brochure 9.



THE GROSVENOR

THE GROSVENOR is designed for the more ambitious musician and has a much wider range than most commercial organs. It comprises 24 octave (48 note) keyboards and a thirteen note pedal board. It has four pitches (i.e. 8ft., 4ft., 2ft., 1ft.) on the upper or solo keyboard, three pitches (i.e. 16ft., 8ft., 4ft.) on the lower or accompaniment keyboard, two pitches (i.e. 16ft., 8ft.) on the pedal board. Variable sustain on the solo keyboard and variable vibrato on both keyboards. It has 15 voices in the solo tone-forming unit, 10 voices in the accompaniment tone-forming unit and 4 voices in the pedal tone-forming unit. All components and kit sections are available separately including the OAK CONSOLE at £95.10.0.

THE GROSVENOR
Kits from £220.
Terms available
Brochure 9B.

PRACTICAL ELECTRONICS - ELECTRONIC ORGAN KIT

We are able to supply parts as described in Practical Electronics. Details on request.

ORGAN COMPONENTS. Complete range in stock. 49 and 61 note keyboards. ● 2 to 5 pair Gold Contacts. ● Coils and Chokes. ● Reversion Springs and Units. ● Stop Tabs and Assemblies. ● Pedal Boards. ● Rhodium and Gold Clad Wire. Also printed circuits, etc. Complete ranges for Transistorised Organs. Ask for Price List with Details. Leaflet 8B.

All enquiries to: ORGAN DEPT. Mr. ELVINS

DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations.

TOTAL COST **£6.19.6** P.P. 4/6

TO BUILD Send for Brochure 1

NEW MODELS NOMBREX TRANSISTORISED Test Equipment

MODEL	PRICE	Leaflet
29s RF. Gen.	£ 21 0 0	25
29x Xtal RF Gen.	29 10 0	25
30 Audio Generator	19 10 0	24
31 R.F. Generator	12 10 0	25
32 C.R. Bridge	10 10 0	26
33 Inductance Bridge	20 0 0	29

QUALITY CAR RADIOS

A precision engineered car radio that's perfect company for long hours—the road that quick button operation for immediate station selection and choice of Medium or Long wave frequency. Output of 3½ watts ensures crisp top quality sound even at high motoring speeds. Includes full accessories and instructions.

POSITIVE/NEGATIVE EARTH PRICE £12 12 0 p.p. 4/6

MANUAL as above £8.19.6 but with single MW/LW Push Button

MULLARD 1 WATT AMPLIFIER

PORTABLE TRANSISTOR UNIT with volume control. Many uses—Intercoms, Bab' Alarms, Guitar Practice Telephone or Record Player Amplifier. Optional Rexine covered Wood cabinet 12 x 9 x 4 12 6 7 x 4 in speaker 17/6 Uses P99 battery

45/- p.p.

Ask for Leaflet 2

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNAVOX DECK you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre amplifier which comes to you assembled on its printed circuit board—in fact every thing needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER which when built will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.



2 Track 36 gns. 4 Track 39 gns.

P.P. 22/6 either model. Kit comprises: Deck, Amplifier, Cabinet and speaker, with MICROPHONE 7 in x 1 200 Hz tape spool. ALL UNITS AVAILABLE SEPARATELY. Value £60. ASK FOR BROCHURE 6

VHF FM SUPERHET TUNER MKII

A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and with the decoder stereophonic broadcasts. There is no doubt about it—VHF FM gives the real sound. Excellent stability economically priced. TOTAL COST £8.19.6 (CABINET 20/-)

ASK FOR LEAFLET 3.

MANUFACTURERS—DISTRIBUTORS

We publish a QUANTITY SEMI-CONDUCTOR BULLETIN listing over 500 different devices available FROM STOCK in medium to large quantities at KEEN PRICES coupled with PROMPT DELIVERIES. TO OBTAIN YOUR COPY WRITE TO US (on Company Headed Notepaper please) requesting our SEMI-CONDUCTOR BULLETIN. For TELEPHONE QUOTATIONS, PHONE (01) 723 1008/9 Extn. 4 (01) 723 0401 Extn. 4

MAINS AND BATTERY DECK

● 3 speed 9 volt dec—brand new, complete with mono cartridge. Special offer price 40/-, p.p. 3/6. ● Stereo mains version 82/6 p.p. 3/6.

NEW—MALLORY LONG LIFE MERCURY BATTERIES

50% OFF LIST PRICES
RM12 1.35 volts 3500 mAh OUR PRICES 5/- each
Size 2in. x 1in. dia. RM602 10.25 volts 350 mAh
Pack of 8. Size 2 1/2in. x 1in. dia.
OUR PRICE 10/- each
Easily split into eight 1.35v cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required.
QUANTITIES AVAILABLE

GARRARD RECORD DECKS




BRAND NEW All below list price

	£ s. d.
2025 Mono/Stereo	8 8 0
3000 LM with 9T/AHC	9 19 6
SP25 Mk II	11 19 6
AT60 Mk II	13 10 0
3500 Mono/Stereo	12 19 6
401	28 10 0
AP75	17 17 0
SL55	11 19 6
SL65	14 14 0
SL75	29 0 0
SL95	35 0 0
L70 Mk II	12 12 0

Send for New 8-Page Brochures
Complete range of accessories available

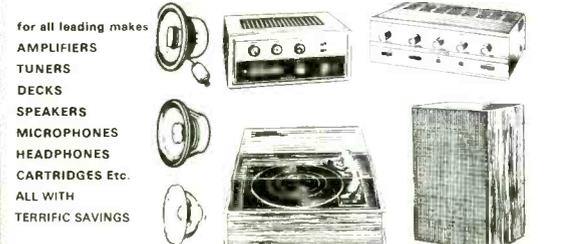VISIT OUR NEW HI-FI CENTRE AT 309 EDGWARE ROAD, AND SAVE UP TO £25 ON SEPARATE UNITS OR THE SYSTEM OF YOUR CHOICE



IT WILL PAY YOU TO PAY US A VISIT! COMPLETE SYSTEMS FROM £46—SAVE £12.10.0 SEND FOR NEW DETAILED HI-FI PRICE LIST 16/M.

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)

The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE

Complete with 10/- worth discount vouchers

FREE WITH EVERY COPY

• 32 pages of transistors and semi-conductor devices, valves and crystals.
• 210 pages of components and equipment.
• 70 pages of microphones, decks and Hi-Fi equipment.

6,500 ITEMS

320 BIG PAGES



Send today 7/6 Post etc 2/-

HENRY'S RADIO LTD (HR)

OPEN MON-SAT, 9 a.m.-6 p.m. THURS, 9 a.m.-1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008/9
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963