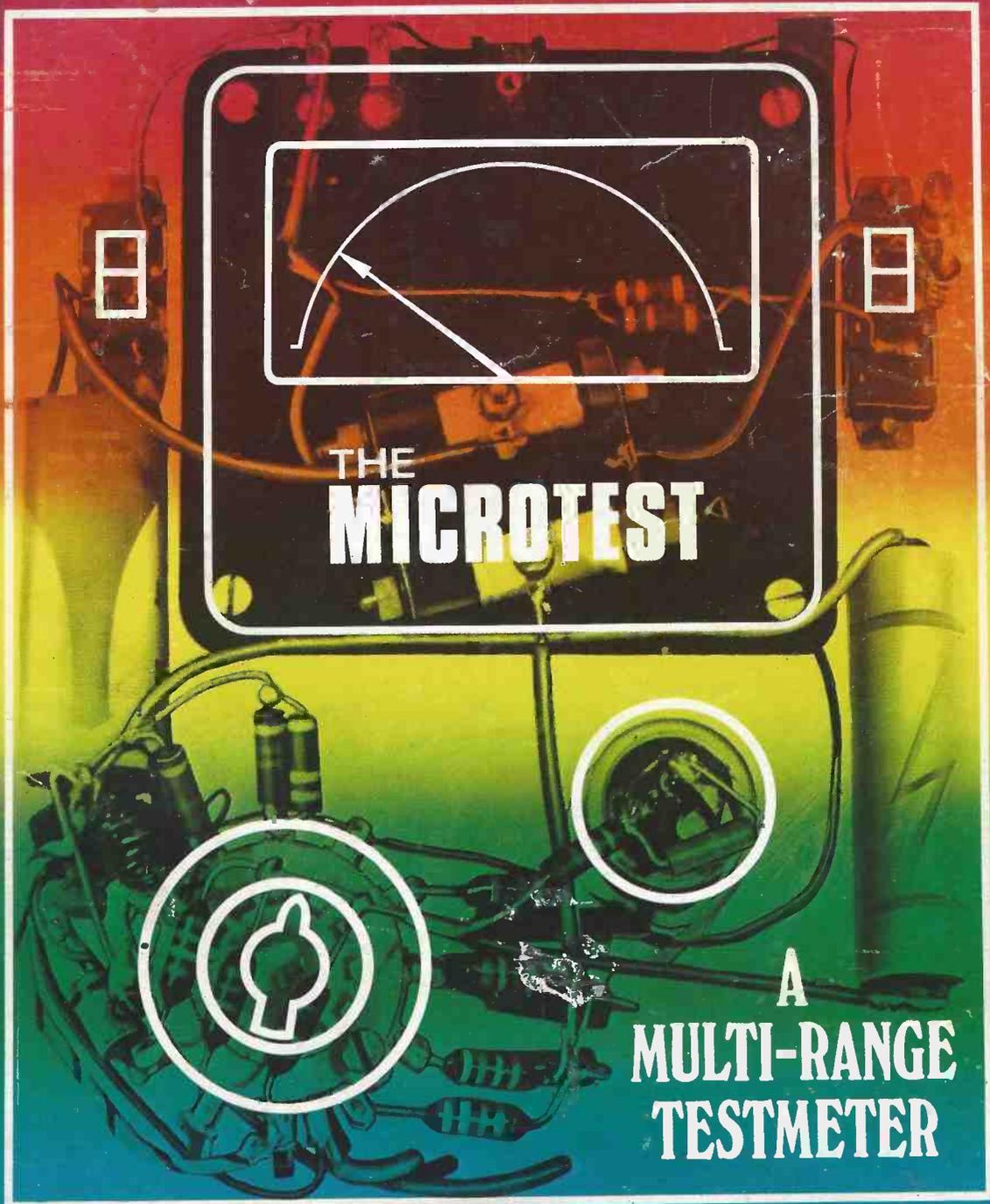


PRACTICAL WIRELESS

FEBRUARY
1970

310




THE
MICROTTEST

A
MULTI-RANGE
TESTMETER

ADCOLA

PRODUCTS LIMITED
(Regd Trade Mark)

THE RELIABLE SOLDERING INSTRUMENT!

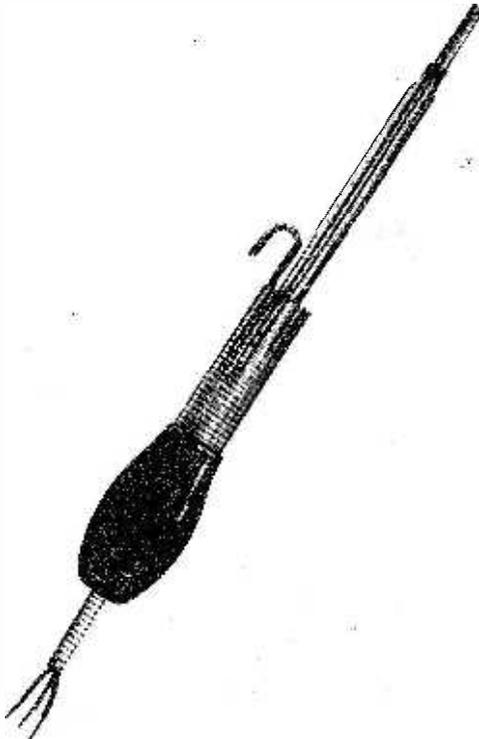

SEND COUPON FOR LATEST LEAFLET

ADCOLA PRODUCTS LTD
ADCOLA HOUSE
GAUDEN ROAD
LONDON SW4
Telephone 01-622 0291/3

NAME

ADDRESS

.....

.....

PW177


JACKSON BROTHERS

have acquired the manufacturing rights of

WAVEMASTER

VARIABLE CAPACITORS

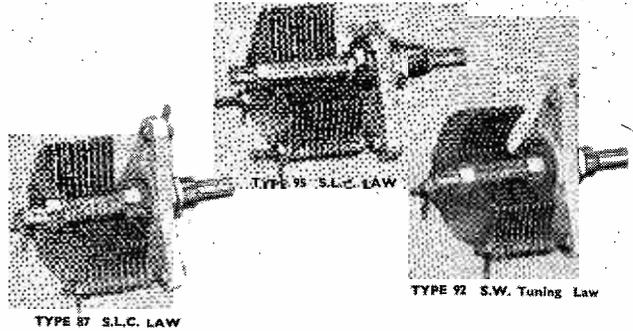'Wavemaster' variable capacitors have brass vanes and a single ceramic end plate. All have .248" spindles, extended both ends for ganging by means of our Universal Couplings. All are designed for S.W. working and for one hole fixing. 6mm spindles to order if required. Various capacitances. Largest vane packs 300 pF .017 air gap, 50 pF 0.64 air gap.



Type 87 S.L.C. Law
Plain bearings $\frac{3}{8}$ "
fixing bush front
area $1\frac{1}{2}$ " w. x $1\frac{1}{4}$ " h.

Type 95 S.L.C. Law
Ball bearings $\frac{7}{16}$ "
dia. fixing bush
front area $1\frac{1}{8}$ " w. x
 $1\frac{1}{2}$ " h.


Type 92 Modified S.L.C. Law (S.W. Turning)
Plain bearings $\frac{3}{8}$ " dia.
fixing bush front
area $1\frac{1}{2}$ " w. x $1\frac{1}{4}$ " h.

JACKSON BROTHERS (London) LTD

Kingsway, Waddon, Croydon, CR9 4DG. 'Phone: (01-688) 2754-5
U.S. Office:- M. Swedgal, 258 Broadway, New York. N.Y. 10007

PHOTOELECTRIC KIT

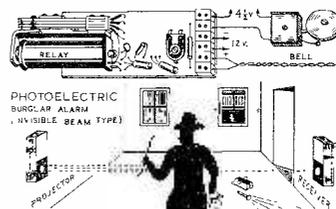CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
39/6

Postage and Pack. 2/6 (UK)
Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0
Australia, New Zealand
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT


CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photo-cell receiver for use with Junior Photoelectric Kit. Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

Just published!

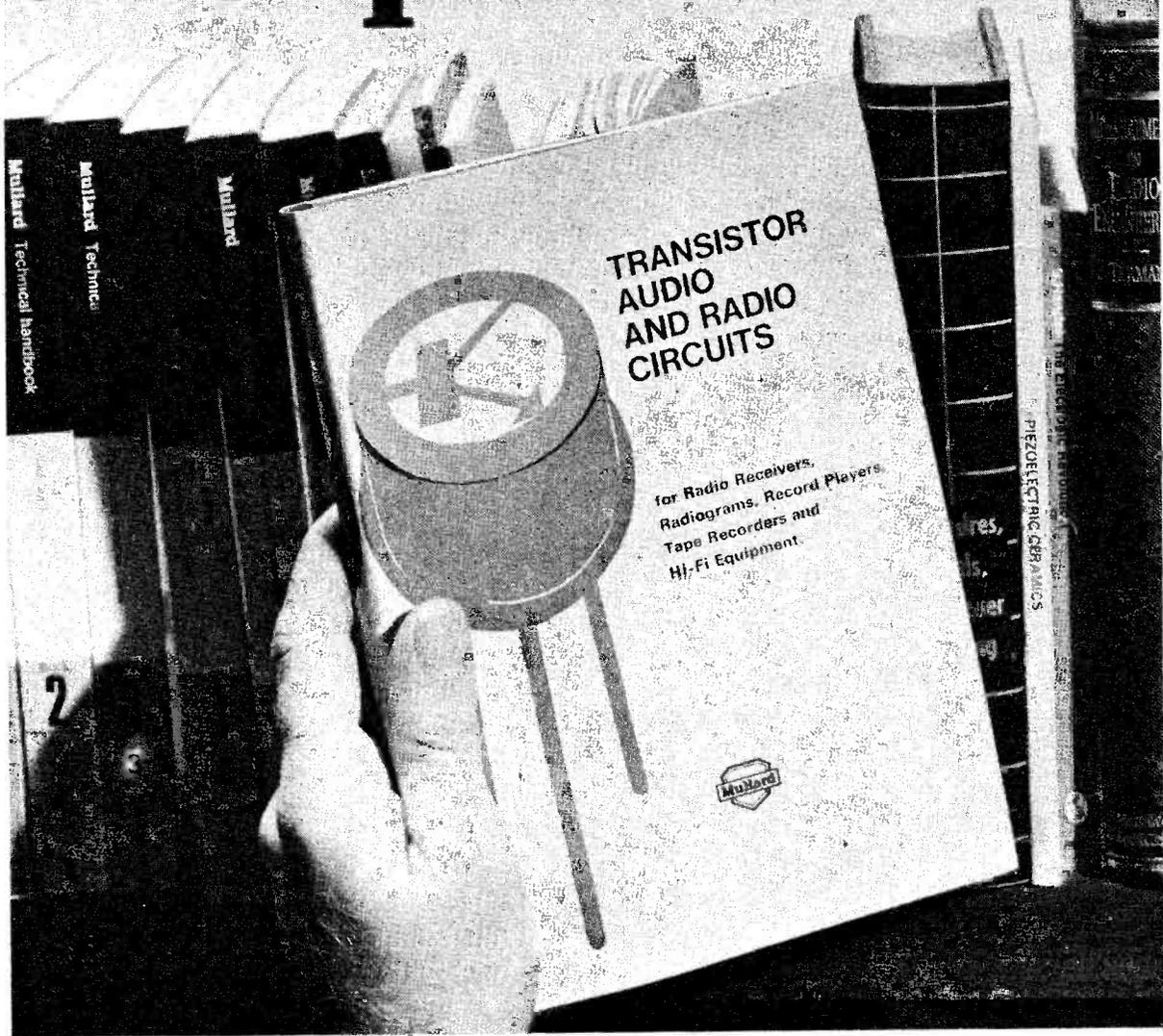

Produced by experts for Engineers, Students and Enthusiasts

This is the book you've been waiting for! Over 200 information-packed pages. Circuits for audio amplifiers, record players, tape recorders, f.m. tuners and portable radio receivers up to hi-fi standards, all designed and proven in Mullard laboratories.

Mullard publications are renowned for the technical authority of their contents and the clarity and style of their presentation.

'Transistor Audio and Radio Circuits' is another outstanding example—there's bound to be a big demand.

It's handy sized and strongly bound. Tremendous value at 30/-.

Get your copy from your local radio retailer, bookshop or direct from Mullard (cash with order) 32/- per copy including postage and packing.


Mullard

Mullard Limited, Distributor Sales Division,
Mullard House, Torrington Place, London W.C.1.

Lasky's

EXCLUSIVE HI-FI STEREO TUNER AMP. OFFER THE MT-65 CHASSIS

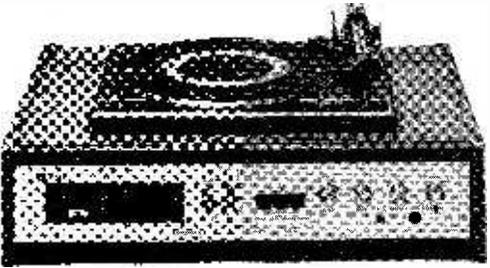
Solid state AM/FM multiplex tuner with FET front-end/17+17 watts stereo amplifier by world famous manufacturer. Frequency response 20-45KHz. Inputs—2.3mV mag. p/u and 140mV tape play. Tape record output. Controls: Left/right volume, bass, treble, loudness, monitor. Tuning meter and stereo beacon. Stereo phone jack. Machined stainless steel front panel. Overall size 20 x 3 3/8 x 16in.



LASKY'S PRICE £78.0.0 CARRIAGE 12/6
DE-LUXE "COMPACT" PACKAGE OFFER LASKY'S
PACKAGE PRICE £132.0.0
 U.K. carriage 40/-
 All units avail. separately

MT-65 Chassis	£78 0 0
GARRARD AP-75 3-speed Single Player	£23 16 7
AUDIO DEVELOPMENT AD-90K Magnetic Cartridge	£5 18 6
3 WEARDEALE DAVTON Speaker Systems	£38 0 0
"Compact" Teak Cabinet (as shown)	£7 10 0
TOTAL RECOMMENDED LIST PRICE	£151.5.1

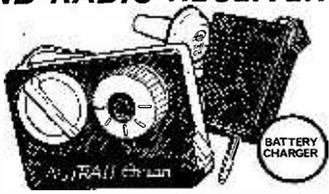SCOOP! THE WORLD'S SMALLEST 6 TRANSISTOR TWO WAVEBAND RADIO RECEIVER Over 10,000 sold The Astrad ORION



Made to the highest space-age standards—this remarkable micro-set measures only 1 11/16 x 1 13/16 x 5 1/16 in. yet it contains 6 transistors and other components combined in a photo etched circuit, only 2 x 1/2 in.; tuning capacitor, ferrite rod aerial, battery, v. wave band selection switch, etc. Output to a high impedance crystal earpiece, giving ample volume (automatically adjusted) and clear tone. Brief tech. spec.: Waveband coverage—Medium wave 525 to 180 kc/s. Long wave 150 kc/s to 498 kc/s. Sensitivity: 36mV max. Selectivity—10dB (at 30 kc/s de-tuning). Power source: 1 x 1.4V Mercury battery. The Orion is supplied fully built and tested complete with battery, left and right fitting earphone supports and attractive black and ivory plastic carrying case—the Orion is an ideal gift for all, providing a constant source of enjoyment without disturbing others.

LASKY'S PRICE ONLY 39/6 Post 2/6
 Extra rechargeable battery 2/6
 *NOTE: The battery we supply with the Orion is a rechargeable type. Charger units are available enabling you to recharge the battery from AC Mains 250/240V supply.

PRICE 19/6 extra Post Free with radio—otherwise 2/-.

NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE at RECORD LOW PRICES

3in. Message tape, 150ft.	2 6	5 1/2in. Standard play, 850ft. PVC.	11 6
3in. Message tape, 225ft.	3 9	5 1/2in. Long play, 1200ft. Mylar . . .	15 0
3in. Message tape, 300ft.	7 6	5 1/2in. Triple play, 2400ft. Mylar . . .	45 0
3 1/2in. Triple play, 600ft. Mylar . . .	10 0	7in. Standard play, 1200ft. Acc.	12 6
4in. Triple play, 900ft. Mylar . . .	17 6	7in. Standard play, 1200ft. Mylar . . .	12 6
5in. Double play, 1800ft. Mylar . . .	15 0	7in. bar	12 6
5in. Long play, 900ft. Acetate . . .	10 0	7in. Long play, 1800ft. Mylar . . .	19 6
5in. Standard play, 600ft. PVC . . .	8 6	7in. Double play, 2400ft. Mylar . . .	25 0
5in. Triple play, 1800ft. Mylar . . .	25 0	7in. Long play, 1800ft. Acetate . . .	15 0
5 1/2in. Double play, 1800ft. Mylar . . .	22 6	7in. Triple play, 3600ft. Mylar . . .	50 0
5 1/2in. Long play, 1200ft. Acetate . . .	12 6		

P. & P. 1/- extra per reel. 4 reels and over Post Free. Special quotes for quantities.

Garrard

SL55 with J2006 stereo cartridge
£11.19.6 Post 5/-



AUTOCHANGERS

1025 less cartridge	£6.9.6
1025 with GCM1 mono cart- ridge. Stereo compat.	£6.19.6
2025CT with 97A stereo diamond cartridge	£8.17.6
AT60 Mk II less cartridge	£13.5.0
SL65B less cartridge	£15.19.6
SL75B less cartridge	£22.0.0
SL95B less cartridge	£24.0.0
AT0 Mk II less cartridge	£13.19.6
BSR UA 47 less cartridge	£5.19.6

SINGLE PLAYERS

AP75 with AD176K magnetic cartridge	£21.10.0
--	----------

AP75 less cartridge	£18.10.0
SP25 Mk II less cartridge	£11.19.6
SRP22 Mains model less cartridge	£16.12.10
SRP22 Battery model less cartridge	£7.15.3
TRANSCRIPTION DECKS	£28.0.0
401	
GARRARD BASES	
WB1 £3.16.11; WB4 Mk II	£5.12.6
WB5	£5.19.6
CLEARVIEW PERSPEX COVERS	
SPC1 £3.14.1; SPC4 Mk II	£4.8.10

Postage on all above 5/-.

DENSHI BOARD KITS EXPERIMENTAL AND EDUCATIONAL CIRCUIT SYSTEM



The DENSHI BOARD system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all! Basically the system comprises a slotted circuit board into which plug-in components and bridge pieces are set to produce up to 30 different circuits. The components are encapsulated in transparent plastic blocks bearing the appropriate circuit symbol and value thus enabling even the complete novice to visually grasp the fundamentals of circuitry after only a few moments study. In addition each DENSHI BOARD KIT comes complete with an 80 page manual of circuits and data.

THESE ARE JUST A FEW OF THE CIRCUITS YOU CAN BUILD IN MINUTES:

VARIOUS RADIO RECEIVERS, AMPLIFIERS, MORSE CODE PRACTICE DEVICE, CONTINUITY TESTER, SIGNAL INJECTOR, SIGNAL TRACER, WIRELESS MICROPHONE ETC., ETC.

DENSHI BOARD KIT SR-1A comprises: Base board; tuner block; 4 resistors; choke coil; transformer; 2SA transistor for RF; 2 diodes; 3 capacitors; battery block; morse key; antenna lead; crystal earphone; various bridge and connecting pieces. This kit permits the building of 18 basic circuits.


LASKY'S PRICE 87/6 Post 3/6

DENSHI BOARD KIT SR-2A as SR-1A but with the following additional parts: 2SB transistor for AF; 2 resistors; 1 capacitor; crystal microphone; test probes; electrode additional connecting pieces; 9V battery. This kit permits the building of 30 basic circuits

LASKY'S PRICE £6.2.6 Post 2/6

NEW! FOSTER "Criterion" MkII

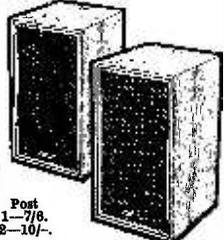2 SPEAKER TWO WAY BOOK-SHELF SPEAKER SYSTEM



Another high quality sub-miniature bookshelf system from Foster. The "Criterion" Mk. II is a sealed infinite baffle type enclosure using 5 1/2 in. bass/mid-range woofer with rolled cloth edge and a 2 1/2 in. HF cone type tweeter. The compact cabinet is constructed of 1/2 in. laminate with handsome oiled walnut veneer finish and black woven acoustic gauze front panel with satin chrome edge insert. SPECC: Frequency range 90-20,000Hz. Power handling 10 watts. Impedance 8 ohms. HF crossover. Screw leg connections at rear. Size 12 1/2 x 7 1/2 x 6 1/2 in. The performance of the "Criterion" is superior to many larger and more expensive units and at Lasky's exclusive price offers absolutely unbeatable value.

Post 1-7/6. 2-10/-.

LASKY'S PRICE £9.10.0 or £17.10.0

Lasky's

1970 JUST PUBLISHED AUDIO TRONICS

28 PAGES, MANY IN COLOUR

36 YEARS ESTABLISHED

The 1970 edition of Lasky's famous Audio-Tronics catalogue is now available - FREE on request. The 28 tabloid pages - many in full colour are packed with 1000's of items from the largest stocks in Great Britain, everything for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories plus LASKY'S AMAZING MONEY SAVING VOUCHERS WORTH OVER £25.0.0. All the goods shown in the "Audio-Tronics" catalogue are available from any of our branches or by Mail Order to any address in the U.K. or Overseas - bringing the benefits of shopping at Lasky's to you in the comfort of your home. A ¼-Million customers have already received their copy of the "Audio-Tronics" catalogue.



Send for your copy now.

SEND TODAY

Your name and address and 1/6d for post only and inclusion in our regular mailing list.

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271

Open all day, 9 a.m.—6 p.m. Monday to Saturday

33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel.: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789

Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewarts Road, London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

1/70

INTERNATIONAL CORRESPONDENCE SCHOOLS




RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.

LTA 15 WATT AMPLIFIER

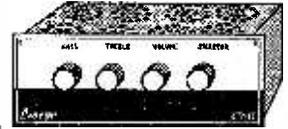
HIGH FIDELITY OUTPUT SWITCHED INPUTS FOR GRAM, 'MIKE', TAPE, AND RADIO
Frequency Response 10-40,000 cps-3dB. Bass Control+17dB to-16dB at 40cps. Treble Control+17dB to-14dB at 14Kcs. Hum and Noise-80dB. Harmonic Distortion 0.2% at rated output. Output for 3-8-15 ohm Loudspeakers.



Recommended Retail Price **£18. 10. 0.**
Size 9½ x 3½ x 5½ in. approx.

PTA30 HI-FI PUBLIC ADDRESS AMPLIFIER

A SUCCESSOR TO OUR POPULAR CONCHORD 30 WATT UNIT
Input Sensitivity 2 mv (max.)
Output 30 watts.
Output Sockets for Loudspeaker or combination of Speakers with total impedance between 3 ohms and 30 ohms. Three individually controlled Inputs for mixing purposes. Housed in fully enclosed stove enamelled steel case. Controls Vol. (1) Vol. (2) Vol. (3) with mains switch, Treble 'lift', and 'cut'. Bass 'lift' and 'cut'.

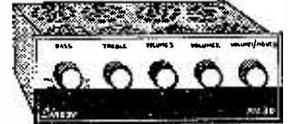

Recommended Retail Price **£23.**
Size 12 x 3½ x 6 in. approx.

AN IDEAL UNIT FOR VOCAL AND INSTRUMENTAL GROUPS, SUITABLE FOR ANY KIND OF 'MIKE' AND INSTRUMENT PICK-UP, ALSO FOR RADIO, TAPE OR GRAM.

If required an attractive wood cabinet with veneer finish can be supplied for any model.
Prices from **70s.**

Please send a stamped addressed envelope for full descriptive details of above units, also TUNER/AMPLIFIERS STEREO and MONO.

AVAILABLE FROM YOUR LOCAL HI-FI DEALER
Wholesale and Retail enquiries to:

LINEAR PRODUCTS LTD,
Electron Works, Armley, Leeds

MARCONI CR 150/2 double Superhet receiver 1.5-22Mc/s AM/CW/SSB operation Xtal Filter, BFO fast/slow motion tuning 'S' Meter, etc. Good condition. Tested and working. **£22.10.0.** P.P. 30/-

R209 RECEIVER, AM/CW/FM, 1-20Mc/s, Four bands, Vernier tuning, 12 volt DC input. Tested and working. **£13.10.0.** P.P. £1.

COMPUTER BOARDS, Min 30 transistors and diodes and res.etc. 10 boards, 10/- and P.P. 2/6; 25 boards **22/6** and P.P. 4/6.

HEADPHONES, Chamois padded, low impedance. Moving coil, magnetic microphone, new ex W.D., rare type, limited stock. **25/-** per pair and 3/6 P.P.

AERIALS, new condition, extending to 11ft fully open; whip type: 12/6 and P.P. 3/6. Whip aerials, 12ft collapsible type; used condition. **10/-** and P.P. 3/6 Bases for above 5/- and 2/6 P.P.

BARGAIN PARCELS. 14 lb. 29/- and 6/6 P.P.; 28 lb. 55/- and 12/6 P.P.; 56 lb. 90/- and 25/- P.P. Contain Pots., Res., Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value saves **£££s.** LUCKY DIP SERVICE.

FURZHILL BEAT FREQUENCY OSCILLATOR, 0-10Kc/s, 110/250 volt. Good condition; complete with spares. **£5.10.0** and 25/- P.P.

VHF RECEIVER TYPE 715, less crystal 60-100Mc/s, can be operated on 2 or 4 meters or made tunable 12 volt input; not tested, complete with valves and speaker. **£3.0.0** and **£1 P.P.**

VIBRATOR POWER SUPPLY TYPE 69 by BCC for 69 T/R. Small compact 12V input gives 250V DC at 80mA and 12V output. Good condition. **25/-** and 7/6 P.P.

MOBILE POWER UNITS by **PYE** for the C12 T/R. Power output is 400V DC at 140mA and 300V DC at 100mA. Good condition. **£3.10.0** and **£1 P.P.**

INSULATION TESTERS. Bench or fieldwork; speed clutch; new condition, complete with leather case; 500V, 500 megohms. **£20** and 12/6 P.P. Also 1000V 1000 megohms with case. **£23** and 12/6 P.P.

CRYSTALS AS NEW. Hc8U 5.345; 5.055; 5.030; 5.005; 4.945; 4.875; 4.840; 4.795; 4.580; 4.660; 4.520; 4.510; 2.300; 2.295 Kc/s and 10 x J 465 Kc/s. All at 10/- and 1/6 P.P.

METERS/MOVING COIL EX EQUIPMENT. Good condition; all from 0-10mA, 30mA, 50mA, 100mA, 500mA. All 2½in. round **10/-** ea and 5/- P.P. from 0-1mA, 5mA, 15 amp D.C., 20 amp D.C., 40 amp D.C. All 2in. round. **10/-** ea and 5/- P.P.

A. H. THACKER

Radio Dept.
HIGH ST., CHESLYN HAY, Nr. WALSALL,
STAFFS.

COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS

CARRIAGE 35/-

The Premier Stereo System consists of an all transistor stereo amplifier, Garrard Model 2025 auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

SPECIAL OFFER CARTRIDGES

	SHURE List Price	Premier Price
M3D	£8.10.6	£6.19.6
M44-5	£14.9.1	£10.10.0
M44C	£12.19.5	£9.8.0
M44E	£17.8.4	£13.19.6
M56E	£20.15.1	£15.15.0
M75-6	£17.8.4	£13.19.6
M75E	£25.18.10	£21.0.0

AUDIO TECHNICA

A.T.7S stereo	£22.0.0	£15.0.0
A.T.7X elliptical	£25.0.0	£18.0.0

Post and Packing 1/6 each

"NOVA" TRANSISTOR STEREO AMPLIFIER

A superb stereo amplifier offering every facility for the hi-fi enthusiast. Output 10 watts per channel. Frequency response 40-20,000 Hz. 3dB. Inputs for radio, P.U. Ceramic, P.U. Magnetic Tape, Separate bass and treble controls, Volume and Balance controls Mono/Stereo Switch. Also features headphone socket and tape output. Teak case with attractive illuminated front panel. Size 14 1/2 x 9 x 3 1/2 in. A.C. 200/250V.



WONDERFUL VALUE AT 25 Gns. Carr. 10/-.

PICK-UP CARTRIDGES AT MONEY SAVING PRICES!

GOLDRING G800 (Stereo)	£8.19.6
SONOTONE STAHC/D (Stereo)	£2.15.0
ACOS GP91/LSC (Mono compatible)	£1.13.5
ACOS GP93-1 (Stereo)	£2. 8.7
ACOS GP94 (Stereo)	£2.14.8
B S R X3M (Mono compatible)	£1.16.5
B S R X3H (Mono compatible)	£1.16.5
RONETTE 105 (Stereo)	£1.15.0
RONETTE 106 (Stereo)	£1.15.0

All complete with mounting brackets and instructions. Post and Packing 1/6 each.

WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

All leading makes available including Rogers, Armstrong, Dulci, Wharfedale, Goodmans, Goldring, Shure, etc. etc.



E.M.I. 13 x 8 in. HI-FI SPEAKERS

Fitted two 2 1/2 in. tweeters and crossover network. Impedance 8 and 15 ohms. Handling capacity 10 watts. Brand new.

99/6 P. & P. 7/6

Also available without tweeters

49/6 P. & P. 7/6



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.

59/6 P. & P.

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/6.
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/6.



"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped - attractively boxed

LP3 3" 250' P.V.C.	5/6	LP6 5 1/2" 1200' P.V.C.	12/6
TP3 3" 450' POLYESTER	7/6	DT6 5 1/2" 1800' POLYESTER	22/6
DT3 3 1/2" 600' POLYESTER	11/6	TP6 5 1/2" 2400' POLYESTER	37/6
SP5 5" 800' P.V.C.	8/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	DT7 7" 2400' POLYESTER	25/-
DT5 5" 1200' POLYESTER	15/-	TT7 7" 3600' POLYESTER	50/-

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/9. TAPE CASES 5", 7" 2/6.
Post and Packing 3" 1/-, 5", 5 1/2" 1/6, 7" 2/-, (3 reels and over Post Free).

"NOVA" 5 WATTSPER CHANNEL STEREO AMPLIFIER.

Specification as above. £18 18 6. Carr. 10/-.

SAVE NEARLY £5!

Premier Stereo System with "NOVA" 10 watt Stereo Amplifier as above. 45 Gns. Carr. 35/-.

VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 1/2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono plugs output. Attractive teak wood grain finish case.



MONO MODEL 59/6 STEREO MODEL 69/6 P. & P. 2/6.

VERITAS V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds.



34/6 P. & P. 1/6.

JULIETTE NA.5018 5 BAND 18 MAINS BATTERY RADIO

Covers AM 540-1600Kc/s. Marine 1.6-4.6Mc/s. FM 88-108Mc/s. VHF 108-134Mc/s. PB 148-174Mc/s. Ferrite bar aerial for AM MB. Telescopic aerial for FM/VHF PB. 4" P.M. Speaker and BFO switch. Operates on AC 250v. or D.C. by four 1.5v. batteries. Size: 9 1/2" x 5 1/2" x 3 1/2".

PREMIER 39 GNS. P. & P. 10/-.



MULTI TESTERS

"TEST 7". A really versatile instrument that makes a handy pocket size tool. Measures AC or DC voltase in three ranges of 0-15-150-1000 volts. Resistance 0-100,000 ohms. Current 0-150 mA D.C. Size only: 3 1/2" x 2 1/2" x 1 1/2" Complete with 59/6 P. & P. battery test leads and instructions.




POCKET SIZE MULTI-TESTER With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 19 Ranges: 0-5-25-50-250-500-2500 volts DC. 0-10-50-100-500-1000 volts AC. 0-50uA-2.5 mA-250 mA DC. 0-8000 ohms-6 megohms, 10uA, uA-0-001 mid-1 mid-20 to +22dB. Complete battery, test lead and instructions. £4.19.6 P. & P. 3/6.



TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc.

65/- P. & P. 4/-.

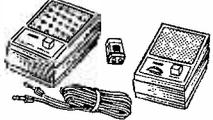

FOUR STATION INTERCOM. Master unit and 3 slaves. Ideal for office and home. Complete with battery and connecting wire £7.19.6 P. & P. 5/6.

"PREMIER" TAPE CASSETTES



C60 (60 min.) 7/6

THREE FOR 21/-


C90 (90 min.) 12/6

THREE FOR 36/-

C120 (120 min.) 17/6

THREE FOR 51/-

P. & P. 1/-.

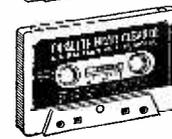

CASSETTE HEAD CLEANER

Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. 11/6 P. & P. 1/-.

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W1 Tel: 01-636 3451



A LONG COOL LIFE

for your valuable components with the
S.D.C. DeC range of SOLDERLESS breadboards

S-DeC Available as single packs with accessories and control panel @ 29/6d or the DeCSTOR double pack containing 2 S-DeCs, accessories, control panel, all in a plastic storage container. Only 67/6d. A 4 DeC pack is available, only 117/6d.

T-DeC Now available to the amateur. 208 connection points. 38 independent junctions. Accommodates I.Cs using standard carriers. Three times the capability for only twice the price! Unit pack with control panel 50/-d.

µ-DeC Primarily for use with integrated circuits; further details on request.



T-DeCs, S-DeCs and Accessories are all obtainable

from leading suppliers throughout the U.K.

In case of difficulty complete the coupon and mail without delay.

Post to:

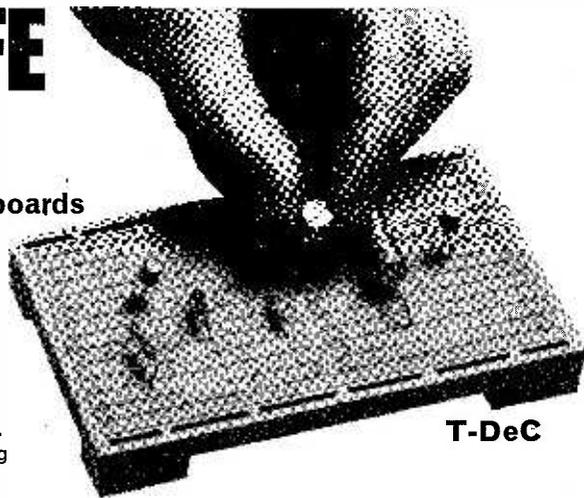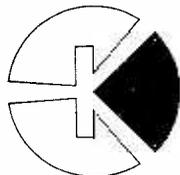S.D.C. Electronics (Sales) Ltd.,
34, Arkwright, Astmoor Industrial Estate,
Runcorn, Cheshire. Tel: Runcorn 5041



T-DeC


Please send me:

.....T-DeC PackS-DeC Single Pack
.....DeCSTOR Pack4-DeC Pack

Tick here if you require further details of the µ-DeC
I enclose PO/Cheque/Money Order value £ | | d.
Money refunded if not satisfied.

Name.....

Address.....

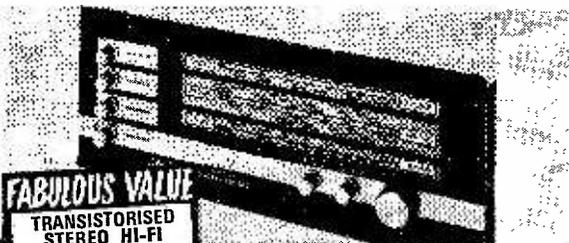

FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Sarsnade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier—only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL
NO TECHNICAL KNOWLEDGE REQUIRED

Only **28** Gns. + P&P 17/6

Credit terms available, first monthly payment £3.6.2 followed by 9 monthly payments of £3.6.2. (Total "Credit Sale" Price £33.1.8). Send £4.3.8 today.

FANTASTIC BARGAIN OFFER!

"TRANSCONTINENTAL"


FULLY TRANSISTORISED STEREOGRAPHIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price ONLY

10 Watts Total output **£36.10.0** P&P 17/6
17 Transistors & 10 diodes

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
Credit Terms available. First monthly payment £4.2.2 followed by 9 monthly payments of £4.2.2.

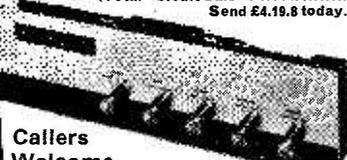(Total "Credit Sale" Price £41.1.8.)
Send £4.19.8 today.



Callers Welcome

BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—obtainable from your local Retailer

Trade enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:

VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

A MUST FOR THE HI-FI PERFECTIONIST AUDIO ADAPTOR UNITS

TYPE AAU-2. Provides switching between 2 pairs of speakers and 1 pair of Stereo Headphones to 1 stereo Amplifier, which can be either switched singly or simultaneously.

TYPE AAU-3. Provides switching between 3 Stereo inputs to a common Amplifier input. A general purpose unit suitable for pick-ups, tuners, mics, tape, etc.; 2 inputs at rear and 1 via front DIN socket. Rear inputs are alternately switched to front socket for feeding external equipment.

TYPE AAU-4. Provides Stereo Record/Replay connections between 2 Stereo or Mono Tape Recorders, to 1 Stereo Amplifier. One Recorder can be permanently installed in the cabinet with amplifier, connected via the rear sockets. The other can be used externally, and be connected to the front socket as required.

TYPE AAU-TV Provides a ready means of connecting external equipment to a TV receiver with complete safety.

We stock all the above and many other units manufactured by M.A.C. Ltd.

Write for full details to
W. E. C. LTD. (AW)

74 THE STREET, ASHTEAD, SURREY

POST THIS COUPON NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name.....
Address.....

LEWIS radio 100 CHASE SIDE, SOUTHGATE, Dep. P170
LONDON, N.14. TELEPHONE PAL 3733/9868

There's Something for Everyone in the NEW HEATHKIT CATALOGUE!



- GUITAR PRACTICE AMPLIFIER
- ELECTRONIC METRONOME
- AMBASSADOR SPEAKERS
- AUTO-TUNE-UP METER
- AIRCRAFT MONITOR RECEIVER
- CAR RADIO
- TECHNICIANS LOW-COST 'VVM'
- SEVERN AM/FM RADIO
- FABULOUS STEREO HI-FI COMPACTS
- STEREO RECORD PLAYER
- D.I.Y. SPEAKER SETS
- GENERATORS
- POWER SUPPLIES
- D.I.Y. RADIOGRAM PACKS
- MANY OTHER MODELS TOO NUMEROUS TO MENTION

Send for this
FREE Catalogue
and see for yourself, Today!



DAYSTROM LTD
GLOUCESTER
GL2-6EE

TO DAYSTROM LTD, GLOUCESTER GL2-6EE

Please send me my free copy of the 1970 HEATHKIT CATALOGUE

NAME

ADDRESS

51/2B

Complete stereo system – £29-10

The new Duo general-purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION:-

Impedance 10 ohms. It incorporates Goodmans high flux 6" x 4" speaker and 2½" tweeter. Teak finish 12" x 6½" x 5½". 4 guineas each. 7/6d. p. & p. Type 2 as type 1. Size 17½" x 10½" x 6½". Incorporating 10½" x 6½" bass unit and 2½" tweeter. 3 ohms impedance 5½ guineas plus 7/6 p. & p. 7/6d. p. & p.

Garrard Changers from £7.19.6d. p. & p. 7/6d.

Cover and Teak finish Plinth £4.15.0d. 7/6d. p. & p.

The items illustrated can be purchased together for £29-10.

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

SPECIFICATION:-

R.M.S. power output: 3 watts per channel into 10 ohms speakers.

INPUT SENSITIVITY: Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1 Kc/s.

CONTROLS: 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.

TONE CONTROL: Treble lift and cut. Separate on/off switch. A preset balance control.

Duetto

Integrated Transistor Stereo Amplifier

£9-10
plus 7/6d.
p. & p.



The above 5 items can be purchased together for £29.10 + £1.10.0 p. & p.

The Classic

£9 plus 7/6 p. & p.

Controls: Selector switch Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume, Treble, Bass, 2 position scratch filter and 2 position rumble filter.



Specification: Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape head: 3mV (at 3½ i.p.s.). Mag. P.U.: 2mV. Cer. P.U.: 80 mV. Tuner: 100mV. Aux.: 100mV. Tape/Rec. output: Equalisation for each input is correct to within ±2dB (R.I.A.A.) from 20Hz to 20KHz. Tone control range: Bass ±13dB at 60Hz. Treble ±14dB at 15KHz. Total distortion: (for 10 watt output) <1.5%. Signal noise: <-60dB. A.C. mains 200-250v. Built and tested. Size 12½in. long, 4½in. deep, 2½in. high. Teak finished case.

The Viscount

£14.5 plus 7/6 p. & p.

Integrated High Fidelity Transistor Stereo Amplifier. Specification—Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo), P.U., Tuner, Tape and Tape Rec. out. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency Response: 40Hz-20KHz ±2dB. Tone Controls: Separate bass and treble controls; treble, 13dB lift and cut (at 15KHz); Bass, 15dB lift and 25dB cut (at 60Hz). Volume Controls: Separate for each channel. A.C. Mains Input: 200-240V. 50-60Hz. Size: 12½" x 6" x 2½" in teak finished case. Built and tested.

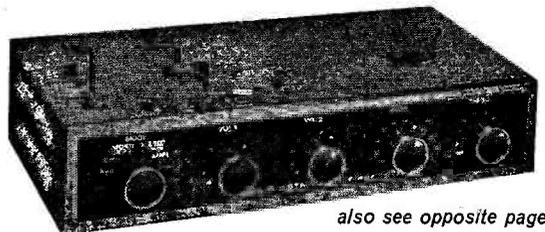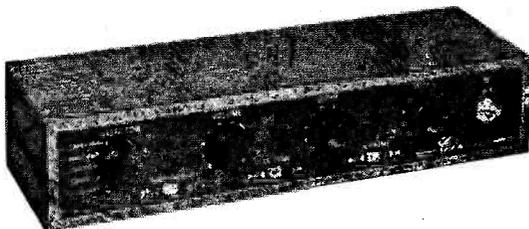VISCOUNT MARK II for use with magnetic pick-ups specification as above. Fully equalised for magnetic pick-ups. Suitable for cartridges with minimum output of 4mV/cm/sec. at 1kc. Input impedance 47k. £15.15 plus 7/6 p. & p.



also see opposite page



SPECIAL OFFER!

Complete stereo system comprising BALFOUR 4-speed autoplatter with stereo head, 2 Duo speaker systems, size 12in. x 6½in. x 5½in. Plinth (less cover) and the DUETTO stereo amplifier. All above items

£20 plus 20/- p. & p.

NEW COMPLETE HI-FI STEREO SYSTEM - £39

comprising SP 25 Garrard Mk II with diamond cartridge, Viscount Mk I amplifier, two type 2 speakers, plinth and cover

£39 plus £2 p. & p.

AUDIO EFFECTS

5 SHAW LANE HALIFAX YORKS.

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

REVERBERATION AMPLIFIER. Self-contained transistorised battery operated. An entirely different approach to sound reproduction. Normally sound reproduction from a single source has a flat, one-dimensional effect. With this unit proper sound delay through reverberation tones are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc. in and the output into your amplifier. Supplied in a beautiful walnut cabinet. 7½ x 3 x 4½ in. £10.4.0. P.P. & Ins. 6/-.



with box, power socket, cables, etc. In kit form with easy to follow instructions £8.9.6. Ready built £9.4.6 plus 5/6 P.P. & Ins.

VOX SWITCH. This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. HIGH and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions, 42/6. Ready built, tested and guaranteed, 62/6 plus 2/6 P.P.


METRONOME UNIT. Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6 post paid. Ready built in an attractive black and white polythene case 37/6 post paid.

MORSE OSCILLATOR. PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speakers. In kit form 17/6 post paid. Ready built in similar case as above, 25/- post paid.

JUST ARRIVED IN STOCK. Texas transistors. Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 6/6 post paid.

Free lists with every order. For lists only send 1/6 (deductible from first order).

SURPLUS EX GOVT. BARGAINS

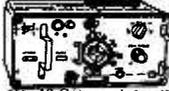

AMPLIFIER RF NO. 2 MK III. Increases output of 19 set to 25 watts. Brand New. 12v operation. 75/-, Carr. 15/-.

No. 19 Sets and Ancillary Equipment available.

12v D.C. Power Units 50/-, Carr. 10/-, 12/24v D.C. Power Units with Vibrator MK II No. 2, 70/-, Carr. 10/-.

H/MIG SETS. Used 15/-, New 22/6, P. & P. 5/-.

Mains P.S.U.'s for 19 TM/RC 26.15.0, Carr. 10/-. R.F. Antenna Tuner (ATU) 25/-, P. & P. 5/-.




COLLINS TCS RECEIVER 7 valve Int. Octal Covers 1-5-12 Mc/s Tunable RF.A.F.B.F.O. Power required 240v D.C. 80 MA 12v1-25A. £8.10.0. Carr. 15/-.

GR100 RECEIVERS. Amateur Shipping Broadcast. 60Kc/s, Carr. 50/-.

B.41 RECEIVER. LF Version of B.40. Coverage 15Kc/s-700Kc/s. Mains Operation. As new 28.10.0, Carr. 30/-.



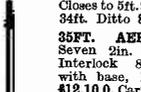R.200 MK II COMMUNICATION RECEIVERS. 11 valve. Covers 1-20Mc/s. 4 bands. AM/FM. CW. BFO. 12v DC. Internal Power Supply. Tested. £13.10.0, Carr. 15/-.



TELESCOPIC MASTS. 20ft. Closes to 5ft. 9in. 70/- Carr. 15/-.

34ft. Ditto 80/-, Carr. 15/-.

35FT. AERIAL MASTS. Seven 2in. dia. sections. Interlock 8in. Complete with base, Nylon Guys. £12.10.0. Carr. 20/-.

TELE SP FIELD TELEPHONES. Communication up to 10 miles. Tested with batteries. £5.15.0 pair, Carr. 20/-.

LIVINGSTONE LAB TRANSISTOR AMPLIFIER. 50 watts R.M.S. Size 14½ x 9 x 4in. With mains p.s.v. Size 16 x 9½ x 9½ in. 22 Gns., Carr. 20/-.

A.J. THOMPSON (Dept. P.W.)

"Eiling Lodge", Cotdicote, Hitchin, Herts. Phone: Cotdicote 242

C.W.O. Carriage charges apply to mainland only.

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

The Ideal, economical and safe way of running Transistor Radios, Record Players, Tape Recorders, Amplifiers etc. from A.C. Mains. All units are completely isolated from mains by double wound transformer ensuring 100% safety.

PLUS-3 MAINS UNIT


Provides three separate switched output voltages 6v., 7½v. and 9v. DC. attractive case with indicator light, mains lead output socket, plug and lead. Size 4 x 3½ x 2½ in.



57/6 P. & P. 2/6 (Extra lead with DIN plug for Cassette Recorders 7/6)

POWER PLUS MAINS UNIT

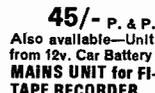for Cassette Tape Recorders using 7½v. Complete with DIN plug for recorder power socket. Can also be supplied for a 6-volt output complete with suitable plug. (Please state make, model and voltage required.)



45/- P. & P. 2/6 Also available—Unit to run your Cassette Recorder from 12v. Car Battery 32/6. P. & P. 2/6.

MAINS UNIT for FI-CORD 202A TAPE RECORDER P. & P. 5/- £4.15.0

MAJOR POWER PLUS MAINS UNITS

For single outputs, 6v, 9v, 12v, 18v, 33/6. For two separate outputs, 4½v + 4½v, 6v + 6v., 9v + 9v. 42/6. P. & P. 2/6 per unit. (Please state outputs reqd.)

R.C.S. PRODUCTS (RADIO) LTD. (Dept. P.W.), 31 Oliver Road, London, E.17



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

... carefully written ...

... I am very satisfied with these carefully written and well expressed manuals ... A.W., Shanklin.

... valuable assistance ...

... Your valuable assistance has enabled me to find a good position as a Radio and TV Engineer ... D.S., Bristol.

... they are invaluable ...

... I find that as a base for a course in Electronics they are invaluable and I have yet to find anything even to approach the same standard ... H.N., Rotherham.

A TECH-PRESS PUBLICATION

■ To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

■ Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

■ Tick Set required (Only one set allowed on free trial)

■ BASIC ELECTRICITY BASIC ELECTRONICS

Prices include Postage and Packing.

■ Signature _____ (If under 21 signature required of parent or guardian)

■ NAME _____

■ BLOCK LETTERS _____


■ FULL POSTAL ADDRESS _____

POST NOW FOR THIS OFFER!!

LIND-AIR OPTRONICS LTD

See our vast range of Electronic Components and Accessories at our enlarged Component Centre 25 Tottenham Court Road

MAINS KEYNECTOR SAVES TIME — SAFELY !

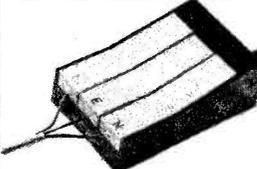

One mains "Keyconnector" instantly and safely connects electrical appliances to mains supply without the use of a plug. A number of appliances may be used simultaneously up to the full 13 amp rating of this device. A red light glows when "live". The "Keyconnector" is fused and has its own robust switch which is interlocked to prevent connections when "live". Invaluable to handymen, servicemen, demonstrators, etc.

39/6 P. & P. 3/-

VHF AIRCRAFT BAND CONVERTER
When placed within 1in. of a MW band radio full coverage of VHF Aircraft Band 108-135 Mc/s. can be obtained. All transistor, 9v battery operation. Fully tunable 18 1/2 in. x 7 section telescopic aerial. Size 4 x 2 1/2 x 1 1/2 in. 79/6 P. & P. 3/6.



MODEL MAKER'S MOTOR
No. 15RN. Voltage 11.5v Current 400mA. Torque 12g-cm. Body size 1 1/2" long x 3/4" dia. Shaft 3/16" long x 1/16" dia. Ideal for small models and toys. 5/6 P. & P. 1.3.3 for 15/-, P. & P. 2/6.



DE-LUXE STEREO HEADPHONES
With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug. Only 59/6 P. & P. 3/6.



Battery Eliminator
Enables transistor equipment to be operated from AC mains. 6/9 1/2 v. output.
Selector switch and on/off switch. 100mA. Case size 4 x 2 1/2 x 2in. complete with mains lead, connecting leads and instructions 55/6 P. & P. 3/6



SINCLAIR IC-10 INTEGRATED CIRCUIT
10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONLY 59/6 P. & P. 1/6.



SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v. at 0.5 amp. 16/6 P. & P. 2/6.

HI-TONE RECORDING TAPE

BRITISH MADE. TOP QUALITY					
J1001	3"	Long Play PVC	250ft.	5/6 P.	& P. 1/2
J1002	3"	Triple Play Poly	600ft.	10/6 P.	& P. 1/2
J1003	5"	Long Play PVC	900ft.	10/- P.	& P. 1/8
J1004	5"	Double Play Poly	1200ft.	15/- P.	& P. 1/8
J1005	5 1/2"	Long Play PVC	1200ft.	12/6 P.	& P. 2/-
J1006	5 1/2"	Double Play Poly	1800ft.	22/6 P.	& P. 2/-
J1007	7"	Standard Play PVC	1200ft.	12/6 P.	& P. 2/6
J1008	7"	Long Play PVC	1800ft.	17/6 P.	& P. 2/6
J1009	7"	Double Play Poly	2400ft.	25/- P.	& P. 2/6
J1010	7"	Triple Play Poly	3600ft.	50/- P.	& P. 2/6



Visit our Brand New enlarged Hi-Fi Demonstration Room, Tape, Record Bar and Scientific Show of Microscopes, Binoculars, Telescopes and Watches at 18/19 Tottenham Court Road

TRANSFORMERS

AUTO WOUND TRANSFORMERS

All Winding Voltage Ratings and Tapping 0-115-200-220-240v except MT113-0-115-210-240v.

MT113	20W	Size 2 1/2 x 1 1/2 x 1 1/2 in.	Wgt 11oz	Price 12/6	P & P 2/6
MT64	75W	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 11b 14oz	Price 21/9	P & P 4/6
MT4	150W	Size 3 1/2 x 2 1/2 x 3 in.	Wgt 31b	Price 33/-	P & P 6/-
MT65	200W	Size 3 1/2 x 4 1/2 x 3 in.	Wgt 41b	Price 39/6	P & P 6/-
MT66	300W	Size 4 x 4 x 3 1/2 in.	Wgt 61b 7oz	Price 59/4	P & P 6/-
MT110	400W	Size 4 1/2 x 4 1/2 x 4 in.	Wgt 111b	Price 85/-	P & P 10/-
MT67	500W	Size 5 1/2 x 4 x 4 1/2 in.	Wgt 121b 8oz	Price 89/-	P & P 10/6
MT83	750W	Size 4 1/2 x 5 1/2 x 5 1/2 in.	Wgt 13 lb 4oz	Price 95/7	P & P 10/6
MT84	1000W	Size 4 1/2 x 5 1/2 x 5 1/2 in.	Wgt 16 lb	Price 142/2	arr. ex.
MT83	1500W	Size 5 1/2 x 5 1/2 x 6 1/2 in.	Wgt 21b 9oz	Price 170/6	Carr. ex.
MT94	1750W	Size 5 1/2 x 6 1/2 x 6 1/2 in.	Wgt 31b	Price 195/-	Carr. ex.
MT95	2000W	Size 7 x 5 1/2 x 8 1/2 in.	Wgt 40lb	Price 211/2	Carr. ex.
MT73	3000W	Size 6 1/2 x 7 1/2 x 8 1/2 in.	Wgt 45lb 8oz	Price 300/-	Carr. ex.

LOW VOLTAGE 12 VOLT RANGE

Primary 200-250v—Secondary 12v					
MT111	0.5 Amp	Size 3 x 2 1/2 x 1 1/2 in.	Wgt 11oz	Price 15/3	P & P 2/6
MT71	2 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 11b	Price 19/-	P & P 3/9
MT69	4 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt 21b	Price 28/-	P & P 6/-
MT70	6 Amp	Size 4 x 2 1/2 x 2 1/2 in.	Wgt 31b	Price 39/-	P & P 6/-
MT72	10 Amp	Size 3 1/2 x 4 1/2 x 4 in.	Wgt 61b 3oz	Price 51/-	P & P 9/-
MT115	20 Amp	Size 4 1/2 x 4 1/2 x 4 in.	Wgt 111b 13oz	Price 95/-	P & P 9/-
MT187	30 Amp	Size 5 1/2 x 4 1/2 x 4 1/2 in.	Wgt 161b 12oz	Price 180/-	P & P 13/6

LOW VOLTAGE 24 VOLT RANGE

Primary 200/250v. Secondary 24v					
MT58	1 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt 11b. 7oz	Price 23/9	P & P 4/6
MT114	3 Amp	Size 2 1/2 x 3 x 3 in.	Wgt 31b 6oz	Price 38/-	P & P 6/-
MT72	5 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 51b 12oz	Price 53/10	P & P 6/-
MT17	8 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 71b 8oz	Price 72/7	P & P 9/-
MT115	10 Amp	Size 4 1/2 x 4 1/2 x 4 in.	Wgt 111b 13oz	Price 95/-	P & P 11/-

LOW VOLTAGE 30 VOLT RANGE

Primary 200/250v. Secondary Tapped 12-15-20-24-30					
MT112	0.5-Amp	Size 3 1/2 x 2 1/2 x 1 1/2 in.	Wgt 11b 4oz	Price 17/4	P & P 3/9
MT79	3 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 21b	Price 23/-	P & P 6/-
MT20	3 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 41b 6oz	Price 46/2	P & P 6/-
MT51	5 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 61b 8oz	Price 60/9	P & P 9/-
MT88	8 Amp	Size 5 1/2 x 3 1/2 x 4 1/2 in.	Wgt 91b 6oz	Price 92/4	P & P 11/-
MT89	10 Amp	Size 5 1/2 x 4 1/2 x 4 1/2 in.	Wgt 121b 2oz	Price 103/6	P & P 11/-

LOW VOLTAGE 50 VOLT RANGE

Primary 200-250v SECONDARY TAPPED 19-25-33-40-50v					
MT102	0.5 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 11b 11oz	Price 21/3	P & P 6/-
MT104	2 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 51b	Price 45/8	P & P 6/-
MT106	4 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 71b 4oz	Price 77/7	P & P 9/-
MT118	8 Amp	Size 5 1/2 x 5 1/2 x 4 1/2 in.	Wgt 181b 9oz	Price 132/-	P & P 13/6
MT119	10 Amp	Size 6 1/2 x 5 1/2 x 6 1/2 in.	Wgt 191b 12oz	Price 165/-	P & P 15/6

LOW VOLTAGE 60 VOLT RANGE

Primary 200/250v. Secondary 24-30-40-48-60					
MT124	0.5 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt 21b 4oz	Price 24/-	P & P 6/-
MT127	2 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 51b 6oz	Price 52/10	P & P 6/-
MT123	4 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 101b 6oz	Price 99/-	P & P 11/-
MT122	10 Amp	Size 6 1/2 x 5 x 6 1/2 in.	Wgt 231b 2oz	Price 152/-	Carr. ex.

MAINS H.T. RANGE

Model	Power	Primary	Secondary	Size	Price P & P
MT1AT	250-0-250v	80MA 6-3v 3-5A	5/6-3v 1A	3 1/2 x 3 x 3"	33/- 6/-
MT6AT	250-0-250v	100MA 6-3v 3.5A	5/6-3v 1A	4 x 3 1/2 x 3 1/2"	38/3 6/-
MT110	250-0-250v	120MA 6-3v 3-5A	5/6-3v 1A	4 x 4 x 3 1/2"	44/9 6/-
MT11AT	300-0-300v	100MA 6-3v 3-5A	5/6-3v 1A	4 x 3 1/2 x 3 1/2"	37/9 6/-
MT12AT	300-0-300v	120MA 6-3v 4A	5/6-3v 1A	4 x 3 1/2 x 3 1/2"	46/2 9/-
MT33AT	300-0-300v	150MA 6-3v 4A	5/6-3v 1A	4 x 5 x 3 1/2"	59/4 9/-
MT2AT	350-0-350v	80MA 6-3v 3-5A	5/6-3v 1A	4 x 3 1/2 x 3 1/2"	38/6 6/-
MT7	350-0-350v	100MA 6-3v 3-5A	5/6-3v 1A	4 x 3 1/2 x 3 1/2"	42/4 6/-
MT8	350-0-350v	120MA 6-3v 3-5A	5/6-3v 1A	4 x 3 1/2 x 3 1/2"	50/- 6/-

BATTERY CHARGER TYPES

Primary Voltage 200-250v. Secondary 6-12v. (Rectifier not included)					
MT45	1.5 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt 11b 9oz	Price 21/9	P & P 4/6
MT46	2 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt 11b 4oz	Price 25/4	P & P 6/-
MT47	3 Amp	Size 4 x 2 1/2 x 3 1/2 in.	Wgt 31b 8oz	Price 28/4	P & P 6/-
MT5	4 Amp	Size 4 x 3 x 3 1/2 in.	Wgt 31b 11oz	Price 33/-	P & P 6/-
MT78	5 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt 51b 4oz	Price 42/-	P & P 6/-
MT86	6 Amp	Size 4 1/2 x 3 1/2 in.	Wgt 51b 12oz	Price 48/-	P & P 6/-
MT48	7 Amp	Size 4 x 4 x 3 1/2 in.	Wgt 61b	Price 56/7	P & P 9/-
MT146	8 Amp	Size 3 1/2 x 4 x 4 in.	Wgt 61b 4oz	Price 75/-	P & P 9/-
MT49	9 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 71b 8oz	Price 99/-	P & P 9/-
MT147	10 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt 91b 3oz	Price 105/-	P & P 9/-
MT50	12.5 Amp	Size 5 1/2 x 4 1/2 x 4 1/2 in.	Wgt 111b 14oz	Price 125/-	P & P 11/-

Amperages are D.C. when used with nominal selenium bridge rectifiers

MAINS ISOLATING RANGE ALSO AVAILABLE

TTC.C1001 MULTITESTER in



leather case. Overload protection. 20,000 ohm AC volts 10, 50, 250 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-60K, 0-6 Megohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 in. 85/- P. & P. 3/6.

SHIRA 62D MULTITESTER 20,000 ohm

DC voltage: 5-25-50-250-500-2.5K (20,000 ohms per volt). AC Voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5mA, 0-250mA. Resistance: 0-6K, 0-6Mg (300 ohm and 30K at centre scale). Capacitance: 10f to .001 mfd. .001 uF to 1 uF. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 in. 71/- P. & P. 3/6

S-DEC BREAD BOARD

Solderless breadboard panels, for fast reliable component connections. Single Decks, One S-Deck with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-Deck" giving construction details for a variety of circuits. 29/6 P. & P. 2/6. 4-Deck KIT Four S-Decks with two Control Panels, Jigs and Accessories and the booklet "Projects on S-Deck" all contained in a strong attractive plastic case. Ideal for the professional user. 45/6 P. & P. 3/6.

GARRARD DECKS



SRP22 less cartridge	85.9.6
1025 Stereo/Mono with cart.	86.19.6
2025 Stereo/Mono with cart.	87.19.6
3005 Stereo/Mono with cart.	89.19.6
3000D Stereo/Mono with cart.	110.19.6
SP25 less cartridge	111.19.6
SP25 with Decca Deram cart.	117.4.6
SL55 less cartridge	111.19.6
SL55 with Decca Deram cart.	117.4.6
SL65 less cartridge	114.9.6
Covers for above	12.19.6
Bases for above	12.10.0
AP75 less cartridge	118.18.6
SL95 less cartridge	138.19.6
Bases for above	14.19.6

SPECIAL OFFER!

SP25 less cart., with base £13.10.0
P. & P. Decks 12/6, Cover 4/6, Base 4/6. P. & P. Deck/Cover/Base 17/-.

MINIATURE SOLDERING IRON

British made and designed for use with transistor circuitry but ideal for many other uses. AC 240v. 18 watt. Length 7 1/2 in. 1/2" slide on bit. Price 32/6 P. & P. 2/-.

LIND-AIR OPTRONICS LTD

18/19, 25 & 53 TOTTENHAM CT ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Shops open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

ALL MAIL ORDERS

To Dept. PW20,
54a Tottenham Court Road,
London, W1.

Sonotone 9TA and 9TA/HC. Diamond Cartridge brand new, boxed in manufacturers' carton 49/6 plus 2/6 p/p. Acos GP 91-1 and GP 91-3 stereo compatible cartridges, new in sealed manufacturers' cartons 22/6 plus 2/6 p/p.

BASF TAPE 25% OFF

5in. 600ft. 14/- 900ft. 19/- 1200ft. 30/-
5 1/2in. 900ft. 19/- 1200ft. 24/- 1800ft. 39/-
7in. 1200ft. 24/- 1800ft. 35/- 2400ft. 57/-
P/P 2/- per reel—over £5 FREE

SPECIAL PURCHASE

12in. 15 watt HI-FI LOUDSPEAKERS

Made by famous British manufacturer to very high standards, heavy duty cast chassis, twin cone construction, smooth extended range, with very low level of distortion.—Response 35-17,500Hz.—impedance 15 ohms—flux, 11,000 gauss.

WALDON 97/6 each plus 6/6 P. & P.

E.M.I. HI-FI SPEAKERS

SET 450: 13 x 8 with two built-in tweeters and cross-over unit. Our Price 69/6 3 or 15 ohm, 10W, 40-13,000Hz.

SET 850: 6 1/2in. bass plus 3 1/2in. tweeter and cross-over unit. 8 ohm, 10W, 65-20,000Hz. 79/6

SET 250: 5in. heavy duty bass plus 3in. tweeter and cross-over unit. 8 ohm, 6W, 80-20,000Hz. 65/-

Add 5/6 p/p for each speaker set.

TRIO Stereo Moving Magnet Cartridge Model AD76K. Diamond Stereo LP Stylus. Frequency response 20-20,000c/s output. 7mV tracking pressure 2 grammes ± 0.5 gm. Fully guaranteed. Price 85/- p/p free.

GARRARD UNITS

	£	s	d
SP25 Mk. II ..	11	9	6
AP75	17	19	6
SL65	14	9	6
*3500	11	9	6

*Denotes including Sonotone 9TA-Stereo/Diamond Cartridge. Elegantly styled plinth and cover to suit the above units. From 5 gns. Please add 10/- p/p each on all above items.

SPEAKER ENCLOSURES


Designed to accept the full range of E.M.I. loudspeakers. Beautifully styled in teak.

Prices from **89/6** each.

25 WATT GROUP SPEAKERS

Guitar group 25. 12in. round, heavy duty cone, with solid aluminium chassis, 15 ohms imp. 12,000 gauss. Response 30-10,000c/s. OUR SPECIAL PRICE

£5.9.6 plus 6/6 P. & P.

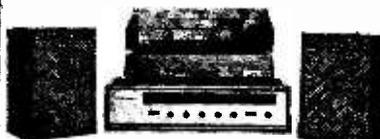

The greatest budget system available today—can't be beaten—price or quality anywhere—look at these great features—then compare:

Teleton FZ000 Mk. II. Tuner amp. Latest version with all the new features. Tuning indicator—fused circuit protection. AM-FM fitted multiplex, A.F.C. 2 x 5 watts per channel. A truly outstanding unit.

Garrard 3500 (Auto/single). Latest in the great new Garrard range, provides facilities and controls that are usually found only on much more expensive units

Teleton SA1003 matching speaker systems

Sonotone 9TA stereo cartridge with diamond styli—a perfect match

Plinth/Cover elegantly styled

Plugs and Leads all supplied

Normal Retail Price **£78 19 8**

Exclusively offered by **WALDON 63 gns** + 25/- at the remarkably low price of **63 gns** Carr.

All items may be purchased separately.

WALDON ELECTRONICS, 707 Blackburn Road, Bolton, Lancs. Bolton 54280

PLEASE ENCLOSE 2/- IN STAMPS WITH ENQUIRIES



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 15/-

A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	3/-*
Size 5 (Ill. ustra- ted)	Savbit	18	3/-*
15	60/40	22	4/-*

*Recommended Price

THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 15/-

INVALUABLE FOR STRIPPING FLEX. THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER,

easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6

VALVES

SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS IR5, 185, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94, Set of 4 for 18/6, DAF96, DF96, DK96, DL96, 4 FOR 26/6

OZ4	4/6	12K8GT	7/3	7/6	EF183	5/9	PCF808	14/9	UBC41	9/-
1A7GT	7/6	12N7GT	7/3	7/6	EF184	5/6	PC181	8/9	UBF80	5/9
1HS2T	7/3				EH90	8/3	PC182	7/-	UBF89	5/9
1NS5T	7/9	19B6G	17/6	17/6	EL33	8/9	PC183	9/-	UC92	5/-
1R5	5/9	20F2	13/6	13/6	EL34	9/6	PC184	7/6	UC84	7/-
1SS	4/3	20P3	11/9	11/9	EL41	10/6	PC185	9/-	UCC85	7/3
1T4	2/9	20P4	18/6	18/6	EL84	4/9	PC186	8/3	UCH80	7/3
354	6/-	2516GT	5/-	5/-	EL90	4/6	PEN4A	12/6	UCH42	12/-
3V4	6/-	25U4GT	11/6	11/6	DY8	5/9	PFL200	11/9	UCH81	6/3
5Y3GT	5/9	30C1	6/6	6/6	DY87	5/9	EM80	7/6	UCL82	6/9
5Z4G	7/6	30C15	13/-	13/-	EAB380	6/6	EM81	7/6	UCL83	11/6
630L2	12/-	30C17	16/-	16/-	EAF42	10/-	EM84	6/6	UF41	10/6
6A15	2/3	30C18	14/-	14/-	EB91	2/3	EM87	7/6	UF80	7/6
6AM6	2/9	30F5	16/-	16/-	EBC33	8/-	EY51	7/6	UF85	6/9
6A05	4/6	30FL1	13/9	13/9	EBC41	9/6	EY86	6/6	UF89	6/9
6A76	4/-	30FL12	14/6	14/6	EBF80	6/9	EZ40	8/-	UL41	10/9
6A06	4/6	30FL14	14/9	14/9	EBF89	6/3	EZ41	8/-	UL44	20/-
6B16	8/6	30L1	6/6	6/6	EC81	3/9	EZ80	4/6	UL84	7/-
6BE6	4/9	30L15	14/-	14/-	EC82	4/9	EZ81	4/9	UM84	6/6
6B16	8/6	30L17	15/6	15/6	EC83	7/-	GZ32	8/9	UY41	7/6
6BW6	13/-	30P4	12/-	12/-	EC85	5/-	GZ34	9/9	UY85	5/9
6F13	3/6	30P12	13/9	13/9	EC91	3/-	KT61	8/9	VP48	10/-
6F14	9/-	30P19	12/-	12/-	EC804	16/-	KT66	16/-	W119	7/-
6F23	14/3	30P11	13/9	13/9	ECF80	6/6	N78	17/6	Y83	5/9
6F25	13/-	30PL13	15/6	15/6	ECF82	5/9	PABC80	7/-	Y88	6/9
6J6	3/-	30PL14	15/6	15/6	ECH35	6/-	PC86	10/3	Y80	7/6
6K7G	2/6	35L6GT	8/6	8/6	ECH42	13/6	PC88	10/3	Y801	6/9
6K8G	2/9	35W4	4/6	4/6	EC181	5/9	PC96	8/6	R20	12/6
6L18	6/-	35ZAGT	5/-	5/-	EC183	8/3	PC97	8/6	U25	13/-
6SN7GT	4/3	60S3	12/6	12/6	EC184	7/6	PC90	7/6	U26	12/-
6V6G	3/3	AC/VP2	10/-	10/-	ECL80	6/9	PCC84	6/6	U47	13/6
6V6GT	6/6	AZ31	9/6	9/6	ECL82	6/9	PCC85	6/-	U49	13/6
6X4	4/3	B729	12/6	12/6	ECL83	8/6	PCC88	9/-	U52	14/6
6K35GT	5/9	CCH35	13/6	13/6	ECL86	8/-	PCF89	10/6	U78	4/3
7B7	7/-	CL33	18/6	18/6	EF37A	6/6	PC189	11/6	U191	12/6
7C6	6/9	CY31	6/9	6/9	EF39	4/9	PCF80	6/6	U193	8/6
10F1	14/-	DAC32	7/3	7/3	EF41	10/9	PCF82	6/6	U251	14/6
10F18	7/-	DAF91	6/3	6/3	EF80	4/6	PCF86	11/6	U301	10/6
10P13	18/6	DAF96	6/6	6/6	EF85	5/3	PCF200	13/6	U329	14/6
12A17	3/9	DF33	7/9	7/9	EF86	6/3	PCF800	13/6	U801	19/6
12A16	4/9	DF91	2/9	2/9	EF89	5/3	PCF801	6/9	UAB80	6/6
12A17	4/9	DF96	6/6	6/6	EF91	2/9	PCF802	9/-	UAF42	10/3
12AX7	4/9	DH77	4/-	4/-	EF94	4/6	PCF805	14/-	UB41	6/6

READERS RADIO


85 TORQUAY GARDENS, REDBRIDGE, ILFORD,

ESSEX.

Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra

peak sound englefield

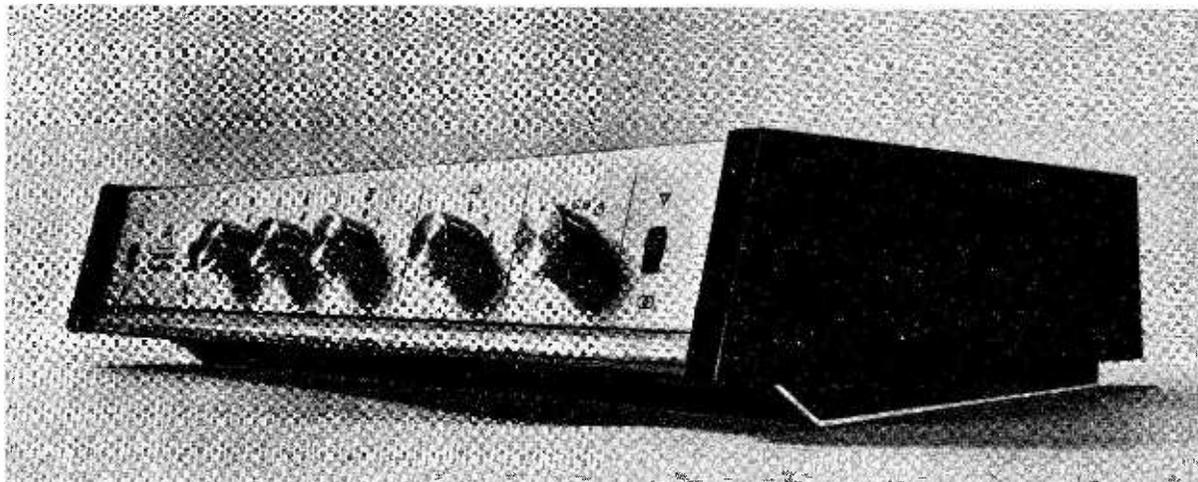

developed out of the highly successful PW. 12-12 and now in complete kit form to save you still more.

The Peak Sound Englefield is a system offering great flexibility whilst providing cost-performance ratios which have never been bettered in high fidelity. Here top-flight circuitry is housed in a cabinet of elegantly original styling which is both beautiful and completely practical front and back. Now we carry design standards further by offering a 12+12 watt version completely in kit form. The resultant specification surpasses that even of the original PW.12+12 which again was based on Peak Sound design. In this Englefield kit, printed circuit boards are supplied for you to mount the components on. Standards of input sensitivity and overload factor on all channels as well as filter performance are all improved. By giving you the satisfaction of building the Englefield this way, you save considerably and finish with a completely professionally styled instrument. Go to your dealer and start building now, or send direct for delivery by return in case of difficulty.

and this is the Peak Sound Specification Guarantee

Peak Sound guarantee that their equipment meets all specifications as published by them and that these are written in the same terms as used in equipment reviews appearing in this and other leading British hi-fi journals. Audio output powers are quoted at continuous sine wave power in terms of Root Mean Square values (R.M.S.) into stated loads at stated frequencies.

The specification that tells you everything (See guarantee)

Using two Peak Sound PA. 12-15's, driven simultaneously at 1 KHz from 240 V. mains supply.
 Output per channel: 11 watts into 15Ω: 14 watts into 8Ω.
 Frequency bandwidth: 10Hz to 45 KHz for 1dB at 1 watt.
 Total Harmonic Distortion at 1 KHz at 10 watt into 15Ω—0.1%.
 Input sensitivities: Mag. PU.3.5 mV. R.I.A.A. equalized into 68KΩ: Tape, 100mV linear into 100KΩ: Radio, 100mV linear into 100KΩ.
 Overload factor: 29dB on all input channels.
 Signal/noise ratio: —65dB on all inputs.
 Vol. control at max.
 Controls: Volume, Treble, Bass, Low-pass Filter. Mono/Stereo: On/off; Balance.
 Complete kit of parts including cabinet assembly, knobs, transistors, well-prepared instructions and wire to length, colour coded and stripped at ends as well as built-in mains power supply. (Post free in U.K.)
£32.12.6

Englefield assembly as above, but in easy-to-put-together modules. (Post free in U.K.)
£38.9.0

Peak Sound ES.10-15 BAXANDALL LOUD-SPEAKER. Fantastic performance and value. Ideal with your Englefield. Cabinet 18"x12"x10" natural teak finish. Ready built—18½ gns. Parts available separately for building yourself with appreciable saving. Leaflet on request.

peak sound

PEAK SOUND (HARROW) LTD., SAINT JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY. Egham 5316

To Peak Sound, Saint Judes Road, Englefield Green, Egham, Surrey

Details of Englefield systems, please send.....

Name

Address

PW2

Write your stockist's name and address in margin below and cut out with coupon if necessary

R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

30 WATT OUTPUT

- * Goldring Transcription Turntable on Plinth
 - * Shure or Goldring 800Hz Magnetic Pick-up Cartridge
 - * Super 30 Amplifier in veneered housing
 - * Pair of Stanway II Loudspeaker Units
- Special total price. Four fully wired units ready to "plug-in". Carr. 30/-
TERMS AVAILABLE ALL PACKAGE OFFERS

86 Gns.

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround for low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.

HF100D 10"	15W	£5.79
HF510L 5"	10W	£7.9
HF801D 8"	8W	£9.9
HF812D 8"	10W	£5.50
HF120D 12"	15W	£5.50

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled acoustic damping. Ported where appropriate, credit terms available.



DORCHESTER Size 16x11x9in. Appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13x8in. Dual Cone spkr. Imp. 3 or 15 ohms. **£8.19.9**

STANWAY II Size 20x10x9 1/2 in. Rating 10 watts. Inc. Fane 13x8in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

GLOUCESTER Size 25 x 16 x 10in. 12in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Frequency range 40-20,000 c.p.s. Impedance 15 ohms. **12 1/2 Gns.**

E2 CABINET Size 17" wide. 14 1/2" deep, 11 1/2" high. Cut for TA12, Super 15, Super 30 and other amplifiers. "Roll over" transp. plastic cover. Satin Teak or Afrormosia veneer finish. Inc. carr. **8 Gns.**

MOTOR BOARDS cut for Garrard Turntables and many other units. Price **12/9**

R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. —2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble "Hifi" and "cut" controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. Carr. 7/6
Or factory built with 12 months' guarantee. **£8.19.9**

Matching as recommended for optimum performance. Send for coloured brochure showing other money-saving offers.

30 WATT OUTPUT

- * Garrard SP25 Mk II Turntable on Plinth
- * Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
- * Super 30 amplifier in veneered housing
- * Pair Stanway II Speaker Units
- * Four fully wired units ready to "plug-in". Special total price **76 Gns. Carr. 30/-**



EXTREMELY ATTRACTIVE PLINTHS finished in Teak or Afrormosia veneer. Transparent plastic cover.

RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover Ready to plug into Amplifier or Tape recorder.

RP2C Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. **23 Gns.**

RP5C Garrard 2025 Auto Unit fitted Garrard GCS 23 Stereo Cartridge with diamond tip. inc. carr. **15 Gns.** Other types available with Magnetic cartridges and with alternative design plinths.

R.S.C. PLINTHS


for Record Playing units cut for Garrard 1025, 2025, 3000, AT60, SP25 etc. Available with transp. plastic cover. Inc. Carr. **5/9**

Available with transp. plastic cover. Inc. Carr. **6 Gns.**

INTEREST CHARGES REFUNDED On Credit Sales settled in 3 months.

R.S.C. TA12 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL. Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, "Mike" etc. * 3 separate switched input sockets on each channel * Separate Bass and Treble controls * Slide Switch for mono use * Speaker Output 3-15 ohms * For 200-250v. A.C. mains * Frequency Response 30-20,000 c.p.s. —2dB * Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise —70dB * Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV. Output rating I.H.F.M. * Handsome brushed silver finish Facia and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 months' guarantee. £17 Gns or Deposit £5.2.6 and 9 monthly pymts 34/- (Total £20.8.0) or Afrormosia veneer housing 20/- Gns. Dep. £5.10.6 and 9 monthly payments £2.1.7 (Total £24.4.9).

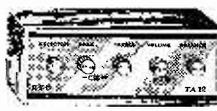

AUDIOTRINE HI-FI SPEAKER SYSTEMS Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Or Senior 15 Watt inc. HF126 15,000 line Speaker £6.15.0. Carr. 6/6

LINEAR L10 HIGH FIDELITY 10W AMPLIFIER with separate Pre-amp. Magnet P.U. matching. To clear **10 Gns**

HI-FI SPEAKER ENCLOSURES Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approximate. Inc. carr. **£4.14.6**

JES Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. **£5.15.0**

SE8 For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. **£6.19.6**

SE10 For outstanding results. SE12 For excellent performance with 12in. Hi-Fi speaker and Tweeter. Size 24x15x10in. P.td. **£5.19.6** Size 25 x 16 x 10in. **£6.19.9**

R.S.C. TFMI SOLID STATE VHF/FM RADIO TUNER

Total cost of parts with detailed wiring diagrams & instructions. Inc. Carr. **14 Gns.**

Or factory built 18 gns. Or in Teak finished cabinet as illustrated. 21 gns. Terms: Deposit £6.1.0 and 9 monthly payments 2 gns. Total **£24.19.0**



* High-sensitivity. * 200-250v. A.C. Mains operation. * Sharp A.M. selection. * Drift-free reception. * Output ample for any amplifier (approx. 500 m.v.). * Simple alignment instructions. * Output available for feeding tuning meter. * Output for feeding Stereo Multiplexer. * Tuner head using silicon Planar Transistors. * Designed for standard 80 ohm co-axial standard of performance and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry. Only high grade transistors and components used. A quality product at considerably less than the cost of comparable units. Stereo version, all parts 20 gns. inc. carr. Assembled **23 gns. inc. carr.**

R.S.C. SUPER 30 MKII HIGH FIDELITY STEREO AMPLIFIER

High Grade Components Specifications comparable with units costing considerably more.

TRANSISTORS 9 high quality types in each channel.

OUTPUT 10 Watts R.M.S. continuous into 15Ω (per channel). 15 Watts R.M.S. continuous into 3Ω.

INPUT SENSITIVITIES Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5 mV.

FREQUENCY RESPONSE ±2 dB. 10-20,000 c.p.s.

TREBLE CONTROL +17 dB to —14 dB at 10 Kc/s.

BASS CONTROL +17 dB to —15 dB at 50 c/s.

HUM LEVEL —80 dB.



Employing Twin Printed Circuits. 200/250v. A.C. mains operation. **HARMONIC DISTORTION** 0.1% at 10 watts 1,000 c.p.s.

CROSS TALK 52 dB at 1,000 c.p.s.

CONTROLS 5 Position Input Selector, Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.

INPUT SOCKETS (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic, or Tape Head. (Operation of Input Selector assures appropriate equalisation).

CHASSIS Strong Steel construction. Approx. 12 3 x 8in.

FACIA PLATE Attractive design in rigid Perspex. Spun silver finish matching control knobs as available.

COMPLETE KIT OF PARTS Carr. 15/-

Point to point wiring diagrams and detailed instructions. Eminently suitable for use with any make of Pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first-rate ancillary equipment. Unit factory built. **29 Gns.**

or Deposit £7.5.0 and 9 monthly payments 58/9 (Total £33.13.9) or in Teak or Afrormosia veneer housing 32 Gns. Carr. 15/- Terms: Deposit £7.3.6 and 9 monthly payments of 66/6 (Total £37.2.0). Send S.A.E. for leaflet.

R.S.C. SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER

Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. Carr. 12/6 or factory built 15 1/2 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9) or in Teak or Afrormosia veneered housing. **19 Gns.**

- BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agents) O. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gt. Western Arcade 021-236-1279 (Half-day Wed.)
- DERBY** 26 Osmonson Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries. Branches open all day Sats.

MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252 **LEEDS**
- 73 Dale St. (Half-day Wed.) Tel. CENtral 3573 **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**
- 60A Oldham Street (Half-day Wed.) Tel. CENtral 2778 **MANCHESTER**
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**
- 41 Blackett Street (Opp. Fenwick's Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25 x 14 x 10in. Complete Kit **20 Gns.**
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms
 ★ Performance comparable with units costing Carr. 12/6 considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £5.10.6 and 9 monthly payments 39/- (Total £23.1.0).
DEMONSTRATIONS AT ALL BRANCHES




R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output, with Pre-amp. Tone Control Stages. Performance figures of factory built units: Hum level - 70dB. Frequency response ± 3dB 30-20,000/c.s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36mV. Suitable for high impedance microphones, Crystal or ceramic P.U.'s. Designed for Clubs, Schools, Theatres, Dance Halls or

Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring **15 Gns.** 12/6 diagrams and instructions.
 Twin-handled perforated cover 27/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 18 gns. TERMS: Deposit £6.3.0 and 9 monthly payments of 34/- (Total £21.9.0). Send S.A.E. for leaflet.

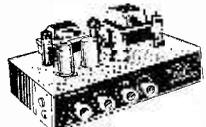R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER



PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of "mike" and gram, etc., etc. High sensitivity, 5 valves - ECC83 (2), EL84 (2), EZ81. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response ± 3dB 30-20,000 c/s. Hum level - 70dB. SENSITIVITY 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments such as String Bass, Electronic Guitars, etc. Size approx. 12 x 9 x 7in. For AC mains 200-250v. 50 cps. Output for 3 and 15 ohm spkrs. SAE for leaflet. Complete kit. **9 1/2 Gns.** Full instructions and point-to-point wiring diagrams. Carr. 11/6 (or factory built 12 1/2 gns.). Twin handled metal cover 27/6. TERMS ON ASSEMBLED UNITS. Deposit 9/6 and 9 monthly payments of 23/- (Total £15.6.6)

RSC A11 TRANSISTORISED VERSION of above complete kit 9 Gns. (Assembled 13 Gns.)

R.S.C. BASS-REGENT 50 WATT AMPLIFIER



An exceptionally powerful high quality all - purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak O-P rating. **12in. Loudspeakers.**
 ★ Two extra heavy duty 12in. Loudspeakers.
 ★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. Carr. 30/- or **55 Gns.** dep. £13.4.9 and 9 monthly payments of £5.11.9. (Total 60 1/2 gns.). Send S.A.E. for leaflet.
 G100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Speakers). 99 1/2 gns.

R.S.C. BATTERY MAINS CONVERSION UNITS



Type BM1 battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 52/6 or assembled 3 Gns.

SELENIUM RECTIFIERS

F.W. (Bridged) All 6/12v. D.C. output. Max. A.C. input 18v. Ia. 4/3. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.



6/12V CAR BATTERY CHARGERS

Complete kit of parts with Ammeter and Circuit. Both models with variable charge rate selector. **4 amp 49/9 6 amp 69/9**
 All types 200-250v. A.C. Mains. Built 10/- extra.

14 WATT HI-FI AMPLIFIERS

High sensitivity. Two separate inputs. Two vol. controls for mixing purposes. Separate Bass and Treble Controls. Valves ECC83, ECL86, ECL86, EZ80. Output for 15 ohm Loudspeaker. 200-250v. 50 c.p.s. A.C. mains operation. Size approx. 8x8x6in. Factory built and fully guaranteed. Limited number to clear at **£7-19-11** Carr. 10/-

FANE POP 30c LOUDSPEAKERS

12in. 8-15Ω, 25 watts R.M.S. continuous. Dual cone. Carr. free

£5-19-9




R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair, ideal for vocalists and Public Address, 15 ohm matching. C57 15 watts inc. five 7 x 4in. speakers £7.19.11. TYPE C45 25/30 WATTS. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit 67/- and 9 **16 Gns.** monthly payments 34/9 (Total £18.19.9). Carr. 10/-.
 TYPE C412S, 50 WATTS. Fitted four 12in. 11,000 line 15 watt **26 Gns.** speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/-.
 Or Deposit £5.17.6 and 9 monthly payments of 54/6 (Total £30.7.0).

30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Group. A 2 or 4 input, 2 vol. control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output ratings. Strong Rexine covered cabinet with handles. Attractive black/gold perspex fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 5 gns. and 9 **19 Gns.** 12/6 monthly payments of 39/8 (Total 22 gns.)

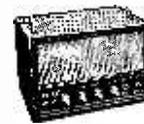

F.A.L. 'Phase Fifty' PUBLIC ADDRESS AMPLIFIER

Solid State Circuitry. 50 Watts Peak Output, 3 separately controlled inputs for mixing purposes. Separate Bass and Treble Controls. Output for loudspeakers 3-30 ohms. Suitable for Dynamic, Ribbon or Crystal Mikes. For Clubs, Theatres, Restaurants, Hotels, Schools, etc. For Vocal or Instrumental Groups. Send S.A.E. for leaflet. **29 GNS.**

HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosa veneered Cabinets. L12 12" 20 Watt £13 13" x 8" 10 Watt 10,000 lines £4-19-9 15 ohms. Carr. 8/9 £8-19-9 3 or 15 ohms. Carr. 7/6



FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous, 2 years' guaranteed. High Flux 14,000 line ceramic magnets. Heavy cast chassis.

'POP' 100 18" 100 Watt 21 GNS. Carr. free	'POP' 60 15" 60 Watt 12 GNS. Carr. free	'POP' 50 12" 50 Watt 10 GNS. Carr. free
--	--	--

POWER PACK KIT

Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit 200/250v. A.C. mains, Output 250v. 60mA, 6-3v. 2a. Supplied with case in lieu of chassis 32/11. Or assembled 44/- **28/11**

MINI-8 HI-FI Loudspeaker Units Special Offer

Teak or Afrormosa veneered cabinet, size approx. 10 1/2 x 6 1/2 x 7 1/2 in. Carr. **69/11**
 Peak power handling 8 watts 3-5 ohms.

WIREGOMP ELECTRONICS

LONDON'S LEADING BARGAIN SPECIALISTS

FOR THE RADIO • HI-FI & ELECTRONICS ENTHUSIAST

Special displays of radios, recorders, record decks, tuners, amps., meters, speakers, etc., etc. ALL faulty or damaged needing repair—
AT GIVE AWAY PRICES!

100's of component bargains from our easy to see and choose from self service racks.

100's OF OLD TYPE VALVES — from 2/- each

ASSORTED TRANSISTORS 9d each. 7/6 per doz

Huge stocks of shop soiled and reconditioned second hand radios, record players, tape recorders, etc.

SPOT CASH PART EXCHANGES

WE OFFER THE HIGHEST RATES IN LONDON

There's something for everyone
COME AND LOOK TODAY (Open 6 days a week!)
ALL THESE ITEMS ARE AVAILABLE TO CALLERS ONLY

PERSONAL CALLERS TO:
48 TOTTENHAM CT. RD., W.1 Tel. 01-636 0647

Kinver for Components

LINEAR INTEGRATED CIRCUITS FOR ALL YOUR REQUIREMENTS

Sinclair type IC-10	59/6 net
Plessey SL403A 3 Watt Audio Amplifier	49/6
G.E. type PA230 Low Level Amplifier	21/-
G.E. type PA234 1 Watt Audio Amplifier	23/-
G.E. type PA237 2 Watt Audio Amplifier	34/-
G.E. type PA246 5 Watt Audio Amplifier	57/-
RCA type CA3000 D.C. Amplifier	54/9
RCA type CA3011 Wide Band Amplifier	20/-
RCA type CA3020 3 Watt Wide Band Amplifier	32/-
RCA type CA3028A Differential Cascode Amp. (120 MHz)	20/-
RCA type CA3029 Operational Amplifier	55/2
RCA type CA3035 Ultra High Gain Amplifier	30/-
Mullard type TAA265 A.F. Amplifier	15/9
Mullard type TAA293 General Purpose Amplifier	21/8
Mullard type TAA310 Record/Playback Pre-Amplifier	32/-
Mullard type TAA320 MOS L.F. Amplifier	13/5
G.E. type 2N5306 Darlington Pair	11/6
G.E. type D1311 Programmable Unijunction Transistor	10/8



ADD 1/- each to the above i.c.s. for data sheets if required. Data sheets may be purchased separately at 1/6d. each, post free. Issued free with SL403A & IC-10. Not available separately for IC-10.

1 WATT AMPLIFIER MODULE TYPE PCM 1

This amplifier unit is a printed circuit module incorporating the popular and well tried PA234 amplifier. The unit is a COMPLETE AUDIO AMPLIFIER and requires no external components, you simply connect an 18 volt power supply and a 15 or 16 ohm speaker or headphone, even the supply smoothing capacitor and the output capacitor are included in the dimensions, including capacitors, are 2 1/2" x 3" x 1 1/2". The input for 1 watt output at 1 kHz is typically 300mV into 100 kohms.

This unit is available at only 36/- net, complete with descriptive leaflet or 70/- net per pair. Send for free leaflet.

TRANSISTORS

ACY17	8/8	BC212L	3/9	OC26	9/-	2N1308	9/6
ACY18	4/5	BC213L	3/9	OC28	9/-	2N1309	9/6
ACY19	5/3	BC214	4/-	OC35	9/-	2N2906	13/-
ACY20	4/6	BCY70	5/4	OC36	9/-	2N2924	4/4
ACY21	4/11	BCY71	10/4	OC71	3/9	2N2925	5/3
ACY22	2/10	BCY72	4/6	OC72	3/9	2N2926	3/-
ACY23	18/-	BD121	17/-	OC75	3/9	2N3053	6/8
ACY40	3/5	BF184	7/6	OC81D	3/9	2N3055	19/6
ACY41	4/4	BF194	7/-	OC170	3/9	2N3702	3/6
ACY44	8/7	BFY50	5/-	OC171	3/9	2N3703	3/3
ASY26	6/2	BFY51	4/6	2N696	4/9	2N3704	3/9
ASY27	8/2	BFY52	4/6	2N697	4/9	2N3705	3/4
ASY28	6/2	BSY95A	3/11	SN706	3/3	2N3707	4/-
ASY29	8/8	MJ481	27/3	2N1132	10/9	2N3708	2/5
BC107	3/7	MJ491	32/11	2N1302	3/11	2N3819	18/9
BC108	3/7	TIP121	17/-	2N1303	3/11	2N3820	18/9
BC109	3/3	TIP32A	23/-	2N1304	5/-	2N3826	5/11
BC182L	3/2	1S44	1/9	2N1305	5/-	2N4058	4/6
BC183L	3/5	1S49	2/6	2N1306	6/5	2N4059	3/5
BC184L	2/2	1S850	3/9	2N1307	6/5	40408	14/11

2N2160 Unijunction 14/11.

DIODES

AA119	3/6	OA91	1/3	1N82A	9/6	IS134	5/3
AA111	2/6	OA202	2/9	1N87A	4/6	IS940	1/4-
AA215	3/3	1N34A	4/-	1N914	2/-		
BA Y38	3/9	1N60	4/-	1S44	1/8		
OA47	2/-	1N64	4/-	IS131	3/-		

VEROBOARD

2 1/2" x 5" in	0.1	0.15
2 1/2" x 5" in	4/9	4/2
2 1/2" x 3 1/2" in	4/2	3/5
3 1/2" x 5" in	5/6	5/6
3 1/2" x 3 1/2" in	4/9	3/11
17" in x 2 1/2" in	10/6	
17" in x 3 1/2" in	14/8	

PLAIN VEROBOARD

(Uncoopered)
(0.15 in Matrix only)

2 1/2" x 5" in	3/8
2 1/2" x 3 1/2" in	3/8
17" in x 2 1/2" in	7/6
17" in x 3 1/2" in	9/8
17" in x 5" in	14/8
Cutter	7/3
Pin Insertion Tool (0.15)	9/6
Pin Insertion Tool (0.15)	9/6
Packet of 36 pins (0.1)	3/11
Packet of 36 pins (0.15)	3/11

EDGE CONNECTORS

FOR USE WITH VEROBOARD

16 way, 0.15in pitch	4/6 each
24 way, 0.15in pitch	6/9 each
24 way, 0.10in pitch	6/9 each
36 way, 0.10in pitch	8/7 each

INTERNATIONAL RECTIFIERS HANDBOOKS

HB10 Rectifier Engineering Handbook	16/9
HB20 Zener Diode Handbook	16/9
HB30 Solar Cell and Photocell Handbook	16/9
HB40 SCR Handbook	20/-

PHOTOCELLS

IR CS-120	19/8
Mullard Type ORP12	9/-

ZENER DIODES

IS2030 Series (400mW 3.3V to 15V)	4/8
Z1100-C Series (1 Watt 3.9V to 27V)	7/11

CARBON VOLUME CONTROLS (POTENTIOMETERS)

Linear or log function type are available in the following values: 5k, 10k, 25k, 100k, 250k, 500k, 1M, 2M.
Available in the following types: Single Pots 3/- each
Single Pots with DP switch 5/3 each
Ganged pots 8/6d each.
Standard Skeleton pots, linear, Horizontal or Vertical mounting, available in the following values, 100, 220, 470, 1K, 2.2K ... to 4.7M 1/- each.

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the fast, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book —'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, Aldermaston Court, Aldermaston, Berkshire.

To: B.I.E.T., Dept. 372B, ALDERMASTON COURT, ALDERMASTON, BERKS.

I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 164-page book.

name.....
address.....
age.....



COMPONENTS CATALOGUE 2/- Post Free (Inland)
P & P 1/6 inland, overseas at cost (min. 10/-). Cash with order please, discounts may be deducted as follows: order over £5—10%, order over £10—15%, excluding net items. Trade orders—net 30 days. Please send SAE with enquiries. CALLERS WELCOME, Open 9.00 a.m.—12.50 p.m. 2.00 p.m.—5.00 p.m. Weekdays and Saturday Mornings 9.00 a.m.—12.50 p.m.

KINVER ELECTRONICS LTD
STONE LANE KINVER STOURBRIDGE WORCS
Telephone: KINVER 2099

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mkl WITH VARIABLE TONE CONTROL


7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs

£6.19.6

Parts Price List and Easy Build Plans 5/- (FREE with parts).

P & P 7/6.

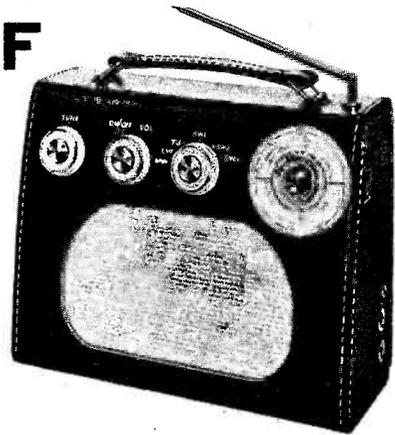


roamer seven mkliv

SEVEN FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Five Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

Total building costs

£5.19.6

P. & P. 7/6

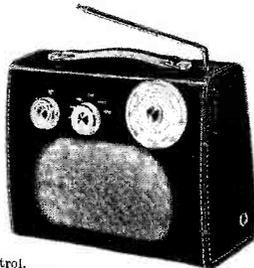


NEW! trans eight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.

Total building costs

89'6

P & P 5/6

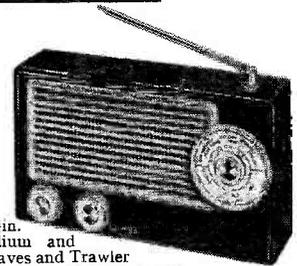

pocket five


MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs

44'6

P. & P. 3/6

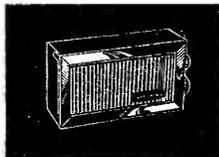

transona five


MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs

47'6

P. & P. 3/9

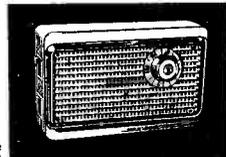

roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/-. (FREE with parts).

Total building costs

79'6

P. & P. 4/6



RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for

Name


Address

PW14

* Callers side entrance Stylo Shoe Shop

* Open 10-1, 2.30-4.30 Mon-Fri. 9-12 Sat

CAR LIGHT FLASHERS

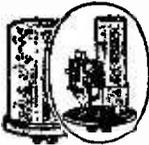

Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset). Housed in strong plastic case. Flashing rate between 60-120 per minute. 12V DC operation. Maximum load 6 amps. Size 2-11/16in. dia. x 4in. Supplied brand new at a fraction of original cost. 6/6 each P. P. 2/6. (3 for 17/6 P. P. 4/6).

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. £5.19.6. Carr. 7/6. Or brand new with accessories. £7.19.6. Carr. 7/6.

CLASS D WAVEMETERS No. 2

Crystal controlled. 1.2-19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. £12.10.0. Carr. 30/-.

R209 MK II

COMMUNICATION RECEIVER
11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O., aerial trimmer, internal speaker and 12V. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. £15.0.0. Carr. 20/-.



TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5-5 Mc/s. Sensitivity 35mV/CM. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.



MARCONI
T/44/TF956
AF Absorption
Wavemeter

1 1/2 watt to 6 watts.
£90. Carr. 10/-.

GEARED MAINS MOTORS



Paralux type SD19 230/250V. A.C. Reversible. 30 r.p.m. 40 lb./ins. Complete with capacitor. Excellent condition. 99/6. Carr. 10/-.


AVO 48A. Perfect order with set of shunts and resistances. £12.10.0. P. & P. 7/6.

TO-3 PORTABLE OSCILLOSCOPE



3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-15 MHz. Input imp. 2 meg Ω 25pF. X amp. sensitivity 0.9v p-p/CM. Bandwidth 1.5 cps-500KHz. Input imp. 2 meg Ω 20pF. Time base 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £85.0.0. Carr. 10/-.

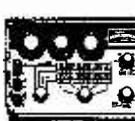TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE




A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 meg Ω. G. Ranges ±1%. L. L. H. HENRYS 6 Ranges -2%. C. 10pF ±1110mFd. 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:1110. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. £20. P. & P. 5/-.

UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6 **13 gns.**



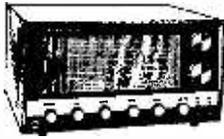TRIO JR.310 New Amateur Band 10-80 Metre Receiver in stock. £77.10.0.



LAFAYETTE SOLID STATE HAG00 RECEIVER 5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 160 Kc/s-400 Kc/s and 550 Kc/s-30 Mc/s FET front end • 2 mechanical filters • Huge dial • Product detector • Variable BFO • Noise limiter • 8 meter • 24in Bandspread • 230V. A.C./12V. D.C. neg. earth operation • RF gain control. Size 16in. x 9 1/2in. x 8 1/2in. Weight 18 lbs. EXCEPTIONAL VALUE. £45. Carr. 10/- S.A.E. for full details.




TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kc/s to 30 Mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit, 4/8 ohm output and phone jack. SSB-CW • ANL • Variable BFO • 8 meter • Sep. bandspread dial • IF 455 Kc/s • Audio output 1.5 W. • Variable RF and AF gain control. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £42, carriage paid. TRIO COMMUNICATION TYPE HEADPHONES. Normally £5.19.6. OUR PRICE £8.15.0 if purchased with above receiver.

TRIO JR. 500SE 10-80 Metre Receiver £69.10.0


LAFAYETTE HA-300 SOLID STATE AMATEUR COMMUNICATION RECEIVER Six bands 3.5-4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54Mc/s. Dual conversion on all bands. 2 x 455 Kc/s mechanical filters. FET front end, product detector, variable BFO, 100Kc/s crystal calibrator. 'S' Meter. Huge slide rule dial. Operation 230V AC or 12V DC. Size 15 x 9 1/2 x 8 1/2in. Complete with instruction manual. £27.10.0 Carr. Paid. 100Kc/s crystal 39/6 extra.

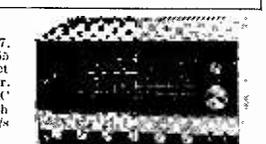TRIO TS 510 AMATEUR TRANS-CEIVER with speaker and mains P.S.U. £212. IN STOCK!



RCA COMMUNICATIONS RECEIVERS AR88D

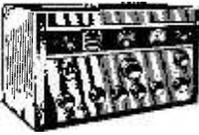Latest release by ministry BRAND NEW in original cases. 110-250V. A.C. operation. Frequency in 6 Bands. 635 Kc/s-32 Mc/s continuous. Output impedance 2-5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price £27.10.0. Carr. £2.




LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £27.10.0. Carr. 10/-.



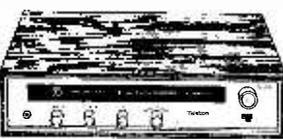TELETON MODEL CR-10T AM/FM STEREO TUNER AMPLIFIER



A new model from Teleton. 31 solid state devices. 4+4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600KHz FM 88-108MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFC switch. Stereo headphone socket. Size 13 1/2" x 3 1/2" x 9 1/2" approx. PRICE £34.0.0. Carr. 7/6.

CLEAR PLASTIC PANEL METERS

First grade quality Moving Coil panel meters. Type MR 39S. 1 1/2" dia. square fronts.

500-0-500μA	27/6	50mA	27/6	150V. D.C.	27/6
1mA	27/6	100mA	27/6	300V. D.C.	27/6
1.0-1mA	27/6	150mA	27/6	500V. D.C.	27/6
2mA	27/6	200mA	27/6	750V. D.C.	27/6
5mA	27/6	300mA	27/6	15V. A.C.	27/6
10mA	27/6	500mA	27/6	50V. A.C.	27/6
50-0-50μA	37/6	750mA	27/6	150V. A.C.	27/6
100μA	37/6	1 amp	27/6	300V. A.C.	27/6
100-0-100μA	35/-	2 amp	27/6	500V. A.C.	27/6
200μA	35/-	5 amp	27/6	5meter 1mA	32/-
500μA	40/-	20mA	27/6	VU meter	42/-


FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET

Variable Voltage Transformers

Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 50-60 cycles. Output full variable from 0-250 volts. Bulk quantities available. 1 amp. -£5.10.0; 2.5 amp. -£8.15.0; 5 amp. -£9.15.0; 8 amp. -£14.10.0; 10 amp. -£18.10.0; 12 amp. -£21.0.0; 20 amp. -£27.0.0.



CRYSTAL CALIBRATORS NO. 10

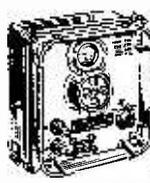

Small portable crystal controlled wavemeter. Size 7 x 7 1/2 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V. D.C. 0.3A. Excellent condition. 89/6. Carr. 7/6.

SOLARTRON CD.711S.2 OSCILLOSCOPES

Double beam. D.C. to 9Mc/s. Perfect order. £65. Carr. 50/-.

TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0.1/0.03/1/3/1.5/10/30/100/300V. R.N.S. 4cps. 1-2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.10.0. Carr. 5/-.



LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Mc/s. on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. £12.10.0. Carr. 10/-.

TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/-.

Additional probes available. R.F. 35/-, H.V. 42/6.

COSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.C. coupled. Band width 1Kc/s. Perfect order. £25. Carr. 30/-.

AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmec. Frequency coverage 20-50 Mc/s. AM CW FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.

EDDYSTONE VHF RECEIVERS

Model 770R. 19-165 Mc/s. Excellent condition. £150.



TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800Hz modulation. 5 1/2 x 5 1/2 x 3 1/2in. Complete with instructions and leads. £7.19.6. P. & P. 4/-.

Generator ringing, metal cases. Operates from two 1.5V batteries (not supplied). Excellent condition. £4.10.0 per pair. Carr. 10/-.

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded. 150 W. £2.2.6. P. & P. 3/6. 300 W. £2.19.6. P. & P. 4/6. 500 W. £4.10.0. P. & P. 6/6. 1,000 W. £8.10.0. P. & P. 7/6. 1,500 W. £7.19.6. P. & P. 8/6. 7,500 W. £15.10.0. P. & P. 20/-.

G. W. SMITH & CO (RADIO) LTD. Also see opps. page

**Fully guaranteed
Individually packed
VALVES**

PERSONAL CALLERS WELCOME
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.



**ALL valves
guaranteed**

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders up to 10/-, 1/-; 10/- to £1, 2/-; over £1, 2/- per £1; over £3 post free. C.O.D. 4/- extra

TRANSISTORS, ZENER DIODES etc.

<p> CY31 7/- EF36 3/6 DAF96 7/9 EF37A 7/6 DF96 7/6 EF39 6/0 DF92 9/0 EF41 12/6 DK96 7/6 EF80 5/- DL92 6/6 EF83 9/6 DL94 6/6 EF85 9/6 DM70 6/- EF86 6/6 DY86 6/- EF86 6/3 DY87 6/6 EF89 5/3 EABC80 6/6 EF91 3/- EAF42 10/- EF92 2/6 EB91 2/- EF95 5/- EBC33 8/- EF183 6/6 EBC41 10/6 EF184 7/- EBC81 6/6 EF800 20/- EBF80 7/6 EF812 15/6 EBF83 8/6 EFL200 15/6 EBF89 6/- EL34 10/6 FCC81 6/- EL41 11/6 FCC82 5/9 EL42 10/6 ECC83 5/6 EL84 4/9 ECC84 6/- EL85 8/6 ECC86 7/6 EL86 8/6 ECC88 7/- EL90 6/- ECC189 9/9 EL95 7/- ECF80 6/6 EL500 12/- ECF82 6/6 EL8035 17/- ECF83 12/6 EM51 5/- ECF801 12/6 EM80 7/6 ECF802 12/6 EM84 7/- ECF803 12/6 EM87 11/- ECH84 7/6 EY51 8/- ECH35 11/- EY81 7/- ECH42 13/- EY86 7/- ECH81 5/9 EY88 8/6 ECH83 10/9 EY89 8/6 ECH200 12/6 EZ80 5/- EC180 9/- EZ21 5/- EC182 6/6 EZ34 10/6 EC183 10/6 KT66 27/6 EC186 8/6 N78 25/- </p>	<p> OA2 6/- OB2 6/- PA8C80 7/6 PC77 6/6 PA05 2/6 OA10 3/- OA30 2/- OA70 2/- OA71 2/- OA79 1/9 OA81 1/6 OC35 10/- OA200 1/9 OC38 8/6 OA202 2/- OC44 4/- OA210 7/6 OC45 2/6 OA211 9/6 OC70 3/- OA2200 11/- OC71 2/6 OA2201 10/- OC72 4/6 OA2202 10/- OC73 11/- OA2206 8/6 OC75 6/- OA2207 9/6 OC76 5/- OA2208 7/6 OC81 4/- OA2213 6/6 OC81D 3/- OA2223 10/- OC81DM 3/- OA2225 10/- OC82 5/- </p>	<p> U26 14/6 U27 8/- U191 14/- U194 11/6 U301 20/- U302 13/6 U303 13/6 U304 12/- U305 10/9 U306 10/9 U307 10/9 U1000 10/9 </p>	<p> OC16 15/- OC22 8/- OC25 7/6 OC26 6/6 OC29 15/- OC32 10/- OC35 10/- OC38 8/6 OC42 4/- OC45 2/6 OC70 3/- OC71 2/6 OC72 4/6 OC73 11/- OC75 6/- OC76 5/- OC81 4/- OC81D 3/- OC82 5/- U141 11/6 U184 6/6 U185 7/6 U186 8/6 U187 8/6 U188 8/6 U189 8/6 U466 8/6 U467</p>
--	--	---	---

ELECTROVALUE

Everything brand new and to specification • Large stocks • Good service

RESISTORS :

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	100Ω-220KΩ	E12	18	16	14
C	1/8W	5%	4.7Ω-1MΩ	E24	2.5	2	1.75
C	1/4W	10%	4.7Ω-10MΩ	E12	2.5	1.75	1.5
C	1/2W	5%	4.7Ω-10MΩ	E24	3	2.25	2
MO	1/2W	2%	10Ω-1MΩ	E24	9	8	7
C	1W	10%	4.2Ω-10MΩ	E12	4	3.25	3
WW	1W	10% + 1/20Ω	0.22Ω-3.3Ω	E12	15d all quantities		
WW	3W	5%	12Ω-10KΩ	E12	15d all quantities		
WW	7W	5%	12Ω-10KΩ	E12	15d all quantities		

Codes : C = carbon film, high stability, low noise.
MO = metal oxide, Electrofit TR5, ultra low noise.
WW = wire wound, Plessey.

Values : E12 denotes series: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades.
E24 denotes series: as E12 plus 1.1, 1.3, 1.6, 2, 2.4, 3, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1 and their decades.

Prices are in pence each for each ohmic value and power ratings. (Ignore fractions of one penny on total resistor order.)

COLVERS 3 WATT WIRE-WOUND POTENTIOMETERS :

10KΩ, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1KΩ, 1.5KΩ, 2.5KΩ, 5KΩ, 10KΩ, 15KΩ, 25KΩ, 50KΩ. Price only 5/6 each.

CARBON TRACK POTENTIOMETERS : Double wiper ensures minimum noise level. Long plastic spindles each
Single gang linear: 220Ω, 470Ω, 1K etc. to 2.2MΩ 2/6 Log/Anti-log: 10K, 47K, 1MΩ only 8/6
Single gang log: 4K7, 10K, 22K, etc. to 2.2MΩ 2/6 Dual anti-log: 10K only 8/6
Dual gang linear: 4K7, 10K, 22K etc. to 1MΩ 8/6 Any type with ½ amp. double pole mains extra 2/3
Dual gang log: 4K7, 10K, 22K etc. to 2MΩ 8/6 switch

FETS n-channel low cost general purpose 2N5163, 25 volt, only 5/- each.
Audio/r.f. Texas 2N3819 9/-, Motorola 2N5459 (MPF105) 9/6 each.

NEW PLESSEY INTEGRATED CIRCUIT POWER AMPLIFIER TYPE SL403A. Only 57/- each. Operates with 18V power supply. Sensitivity 20mV into 20MΩ, 3 wats into 7.5Ω. Applications data with two or more. PE Nov. 69 Stereo Amplifier kit less metal work £11/18/- NET complete.

30 WATT BAILEY AMPLIFIER COMPONENTS :

Transistors for one channel £7/5/6 list, with 10% discount only £6/11/0.
Transistors for two channels £14/11/0 list, with 15% discount only £12/7/5.
Capacitors and resistors for one channel list £2.
Printed circuit board free with each transistor set.
Complete unregulated power supply kit £4/17/6 mono or stereo, subject to discount.
Complete regulated power supply kit £9/5/- subject to discount. Further details on application.

SINCLAIR IC.10 Integrated Circuit Amplifier and Pre-amplifier. This remarkable monolithic integrated circuit amplifier and pre-amp now available from stock. The equivalent of 13 transistor/18 resistor circuit plus 3 diodes and the first of its kind ever. It is d.c. coupled and applicable to an unusually wide range of uses as detailed in the manual provided with it. As advertised, post free 59/6 NET.

CARBON SKELETON PRE-SETS. Small high quality, type PR. Linear only, 100Ω, 220Ω, 470Ω, 1KΩ, 2KΩ, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1MΩ, 2MΩ, 5M, 10MΩ vertical or horizontal mounting, 1/- each.

S-DeCs put an end to "birdsnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only 30/6 post free. Compact T-DeC, increased capacity, may be temperature-cycled T DeC only 51/- post free.

CAPACITORS: All new stock

High ripple current types:
2000μF 25V 7/4; 2000μF 50V 11/4; 5000μF 25V 12/6; 5000μF 50V 21/11; 1000μF 100V 16/3; 2000μF 100V 28/9; 5000μF 70V 36/-; 5000μF 100V 58/3; 1000μF 50V 8/2; 2500μF 64V 15/5; 2500μF 70V 19/6.

Medium elecs.

Axial leads. Values (μF/V):
50/50 2/-; 100/25 2/-; 100/50 3/9;
2/6; 250/25 2/6; 250/50 3/9;
500/25 3/9; 1000/10 3/-; 500/50 4/6; 1000/25 4/6; 1000/50 6/-; 2000/25 6/-.

Small elecs

Axial leads: 5/10, 10/10, 25/10, 50/10 1/- each, 25/25, 47/25, 100/10, 220/10 1/3 each.

PEAK SOUND ENGLEFIELD KITS

Brilliant new styling and available in two forms: Stereo 15 watts per channel In kit form with complete amplifier and pre-amplifier modules and power supply. Build it 12+12 or 25+25' Output per channel into 15Ω, 12 watts R.M.S. Price £38/4/- net

25 WATTS PER CHANNEL. As above but Output per channel into 15Ω, 25 watts R.M.S. Price £53/15/- Net

Brief specification: Total harmonic distortion 0.1%. Inputs: Magnetic, Ceramic, Tape, Radio Signal to noise ratios: Better than 60dB all inputs. O/load factor 28dB all channels.

ENGLEFIELD CABINET to house either above assemblies (as illustrated) £6 Net. OTHER PEAK SOUND PRODUCTS AS ADVERTISED.

MULLARD Sub-min electrolytic C426 range: Price 1/3 each. Axial leads, Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

Wavechange switches: 1P 12W; 2P 6W; 3P 4W; 4P 3W long spindles, 4/9 each. Slider switches, double pole double throw, 3/- each.

BARGAINS IN NEW TRANSISTORS

All power types supplied with free insulating sets

2N696	5/6	2N5192	25/-
2N697	5/6	2N5195	29/3
2N706	2/9	40406	16/3
2N1132	9/9	40408	14/6
2N1302	4/-	AC126	6/6
2N1303	4/-	AC127	6/-
2N1304	4/6	AC128	6/-
2N1305	4/6	AC176	11/-
2N1306	6/9	ACY22	3/9
2N1307	6/9	ACY40	4/-
2N1308	8/9	AD140	19/-
2N1309	8/9	AD149	17/6
2N1613	6/-	AD161	16/- pr.
2N1711	7/-	AD162	
2N2218	9/3	AF118	16/6
2N2147	18/9	AF124	7/6
2N2369A	6/9	AF127	7/-
2N2646	10/9	BA102	9/-
2N2924	4/3	BC107	2/9
2N2925	5/3	BC108	2/6
2N2926R	2/6	BC109	2/9
2N2926O	2/6	BC147	4/3
2N2926Y	2/3	BC148	3/3
2N2926G	2/6	BC149	4/3
2N3053	5/6	BC153	10/-
2N3054	14/3	BC154	11/-
2N3055	16/6	BC157	3/9
2N3391A	5/6	BC158	3/6
2N3702	3/6	BC159	3/9
2N3703	3/3	BC167	2/6
2N3704	3/9	BV168	2/3
2N3705	3/5	BC169	2/6
2N3706	3/3	BC177	6/3
2N3703	4/-	BC178	5/8
2N3708	2/9	BC179	6/-
2N3709	3/-	BD121	18/-
2N3710	3/3	BD123	24/3
2N3711	3/11	BF178	10/6
2N3904	7/6	BFX29	10/9
2N3906	7/6	BFX85	8/3
2N3731	23/-	BFX88	7/9
2N3820	25/6	BFY50	4/6
2N3325	10/6	BFY51	4/3
2N3794	3/3	BSX20	3/9
2N4286	3/3	MJ480	21/-
2N4289	3/3	MJ481	27/-
2N4291	3/3	MJ491	30/-
2N4292	3/3	P346A	5/9
2N4410	4/9	V405A	7/9

MAIN LINE AMPLIFIER KITS as advertised. Prices Net. Authorised dealer.

COMPONENT DISCOUNTS :

10% on orders for components for £5 or more.
15% on orders for components for £15 or more.
(No discount on net items.)

POSTAGE AND PACKING :

Free on orders over £2.
Please add 1/6 if order is under £2.
Overseas orders welcome; carriage charged at cost.

ELECTROVALUE

(Dept. PW. 2) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY.

Telephone: Egham 5533 (STD 0784-3)
Open 9 - 5.30 Sats. 1 p.m.

IF YOU HAVE A HOME RADIO CATALOGUE

Ordering components is easier and quicker with our new

Credit Account Service




Just a
phone call
away

Our aim in life at Home Radio Components Ltd. is to make *your* life happier and less complicated! To this end we have recently introduced a Credit Account Service, one advantage of which is that you can order components by telephone *any time, any day*. If you phone out of shop hours a recording machine will take your message for us to deal with as soon as we open shop next day.

There are *other* advantages to the new Service—if you want to order by post we provide Order Forms and *Prepaid* Envelopes. You settle your account just once per month. We stipulate *no* minimum order value. Of course for ordering your components you first need our Catalogue, and after you have been in the Service 12 months we regularly send you an up-to-date catalogue—FREE!

For full details of our Credit Account service just drop us a line or phone 01-648 8422.

IF YOU HAVEN'T...

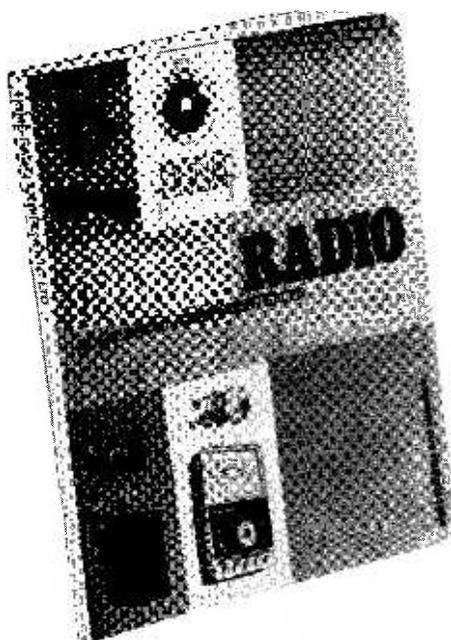

Whether or not you want to use the Credit Account Service described above, you certainly need the Home Radio Components Catalogue if you construct or repair radio and electronic gadgets. The catalogue has 350 pages, lists 8000 components and has over 1500 illustrations. It contains 6 vouchers, each worth 1/- when used as indicated. Post the coupon with 12/- (8/6 plus 3/6 postage and packing) and we will send a catalogue by return of post. By the way, we supply *free* a 30-page Price Supplement and a Bookmark giving electronic abbreviations.

Please write your Name and Address in block capitals

NAME.....

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. PW,
234-240 London Road, Mitcham, Surrey CR4 3HD



PRACTICAL WIRELESS

VOL 45 NO 10

Issue 756

FEBRUARY 1970

TOPIC OF THE MONTH

The point is...

FOR as long as we can remember, Practical Wireless has offered a readers' postal query service. In a measure, of course, we are obliged, at least morally, to do all we can within reason to help out readers with problems relating to articles and projects which have been published in these pages. Nothing in this world is perfect, however; sometimes readers think we fall short of their ideal and sometimes we feel that readers expect too much. It might be helpful to consider what is involved, especially to newer readers.

First of all, cost. Even if a reader submits a query strictly to the rules, enclosing a prepaid envelope plus a query coupon, it can cost several shillings to process a reply, taking into account all the time and expenses involved. In fact, to answer a query costs us more than we get from the sale of a magazine! This is why we cannot guarantee a reply if the rules are broken.

Secondly, the time factor. Many queries can be dealt with immediately. Others involve a good deal of research, which may mean telephone calls and letters to manufacturers, etc. Also, in order to provide the best possible service, many queries are dealt with by a panel of outside specialists.

Thirdly, feasibility. We cannot be held responsible for poor workmanship!

Fourthly, terms of reference. Don't write asking for formulae or valve and transistor characteristics that can be obtained from standard data books; don't ask us to modify a P.W. design to suit a personal requirement. Of course, we cannot undertake to run a free professional advisory and design service.

Fifthly, procedure. All queries should conform to the rules: i.e., query coupon, SAE, etc. We regret that technical queries cannot be answered over the telephone.

Sixthly, period of validity. We cannot guarantee to answer queries relating to projects published more than two years ago.

We are constantly trying to improve the turn around in readers' queries, but the sheer volume often endangers the aims to provide a quick and effective advice service. We are fully conscious of the help often needed and we will continue to do everything possible to sort out the difficulties. All we ask in return is that readers try to appreciate just how much is involved in running a free query service.

W. N. STEVENS—Editor.

NEWS AND COMMENT

Leader	751
News and Comment	752
MW Column <i>by C. Molloy</i>	774
Practically Wireless <i>by Henry</i>	782
Club Spot	783
On the Short Waves <i>by Malcolm Connah and David Gibson, G3JDG</i>	789
Letters to the Editor	798

CONSTRUCTIONAL

The Microtest Multi-range Meter <i>by C. Marshall</i>	754
I.C. of the Month, A.M. Radio <i>by L. A. J. Ireland</i>	758
The Chelmer Six <i>by R. L. Graper</i>	766
Repairing Loudspeakers <i>by H. C. Bennet-Clark, B.Sc., Ph.D.</i>	771
The Two-Fifty Transmitter <i>by A. S. Carpenter, G3TYJ</i>	776
Panoramic Receiver for 160 to 80 Metres, Part 2 <i>by D. Bollen</i>	779
Take 20, 1W Amplifier <i>by Julian Anderson</i>	784
'S' Meter for the Clubman Receiver <i>by J. Thornton- Lawrence, GW3JGA</i>	785
I.F. Crystal Filter <i>by F. G. Rayner G3OGR</i>	805

OTHER FEATURES

Repairing Transistor Radios <i>by V. Capel</i>	761
Home and Dry <i>by F. G. Sadler, G3UZ</i>	775
Basic Semiconductor Technology, Part 9 <i>by M. F. Docker, M.Sc.</i>	793
P.W. Guide to Components, Part 14 <i>by M. K. Titman, B.Sc.</i>	801

March issue will be published on
February 6th

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

NEWS...

NEWS...

NEWS...


First London rally

We hear from Mr. A. P. Teale, G3SGT, the Hon. Sec. of the Ealing and District Amateur Radio Society, G3UUP, that the Society will be holding a Mobile Rally at the Hanwell Community Association on May 10th, 1970.

It is thought that this will be the first time a rally has been held in London and it is hoped that it will prove to be a large and successful one with attendance figures in excess of 500.

The Automobile Association will do the signposting (15 signposts in all) and have their own exhibition caravan at the sight. In the main hall there will be many other trade stalls. The Rally address will be: Hanwell Community Association, Westcott Crescent, Hanwell, London, W.7. Further details may be obtained by sending a s.a.e. to Bill Teale, G3SGT, 16 Whitestile Road, Brentford, Middlesex.

Low pass filters

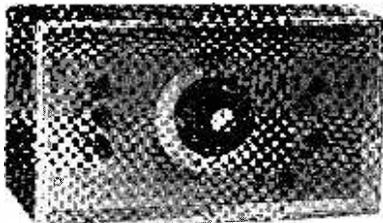

Lionmount & Co. Ltd., are now manufacturing Low Pass Active Filters which can be varied continuously throughout the pass-band.

Two types are available, one of which covers the range 1kHz to 10kHz in one band—the other being a switched-band version covering the frequency range of 1Hz-10kHz in four switched bands. The designs are based on 9th order Butterworth or Chebyshev configuration and can realise 80 dB/decade attenuation at cut off.

The filters will accept an input voltage of $\pm 10V$. peak and may be loaded with a minimum of 2000 ohms. *Lionmount & Co. Ltd., Belleview Road, New Southgate, London, N.11.*

Interlocking boxes



Liden Products (Whitewood) Ltd introduce their storage boxes which interlock with each other. By sliding these in and out numerous permutations can be made. The all-round grooving allows for several boxes to be joined up. The boxes are provided with holes at the back for wall fixing; a slot in the front for inserting identification labels and removable plastic divider in each box. They are available in grey or white.

The measurements are: $2\frac{1}{4}$ x $4\frac{1}{4}$ in. and the width for the large box is 4in. Small boxes cost 2s. 6d. and large boxes 4s. 6d.

The Gunn effect

An article on Gunn effect devices and their applications, originally published in Mullard Technical Communications, is now available as a pamphlet.

It contains an explanation of the Gunn effect, describes the construction of the device and gives advice on the design of oscillator cavities for Gunn devices. Factors affecting stability are discussed and information is given on noise, frequency locking and pulsed operation.

Requests for the pamphlet should be made on company-headed notepaper to *I.E.D./Valves Sales, Mullard Limited, Mullard House, Torrington Place, London, W.C.1.*

Pathfinder radio group


We have been informed by the organiser of the Pathfinder Radio Group, Mr. Lex-Arnold, that the Group is temporarily inactive due to reorganisation. Membership applications will be dealt with as and when the Group is re-formed.

The sound of Eumig


Eumig have announced the Mark S 712D projector which takes Super-8, single and standard-8 sound films, has an f1.6 15/27mm zoom lens, and costs only £110 15s 5d.

There is a combined record and playback amplifier with an integrated circuit (the first time that i.c.'s have been used in an amateur sound movie projector). Amplifier line-up is: type TAA 310 i.c., two 2N5172 transistors, two BC148B transistors, a complementary pair AC187K/188K, two DAX13 diodes, one MV1 varistor, a B832001P/130E thermistor and a type BY164 silicon bridge rectifier.

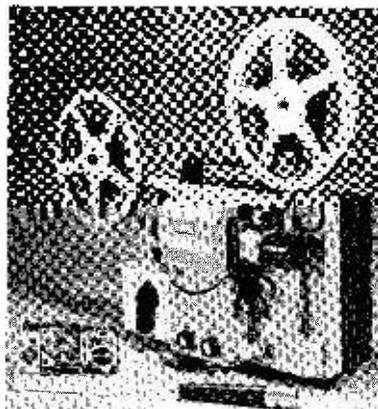The frequency range on edge-stripped film is 80-8,000Hz at 18 frames per second and 75-10,000Hz at 24 f.p.s. Signal to noise ratio is 40dB.



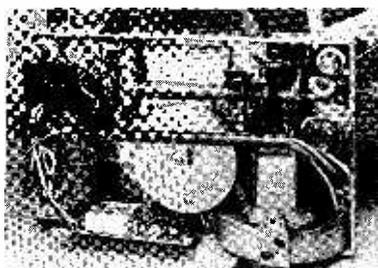
The Eumig S 712D. Below, viewed from the back, the amplifier is seen mounted under the central flywheel.



**...TALKING OF PROJECTORS,
DON'T FORGET THE P.W.
FILMSHOW.**

NEWS... NEWS... NEWS...

How your cassettes are recorded

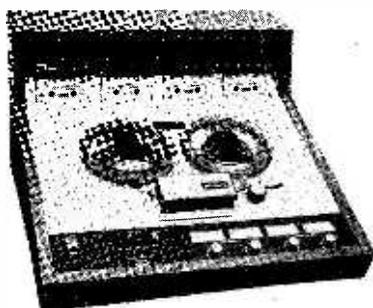

Fraser-Peacock Ltd., announce that they have been appointed sole distributors for the Infonics range of high-speed tape duplicating equipment.

As well as reel-to-reel equipment, a new reel-to-Philips cassette duplicator is now available. The machine shown will make four 1-hour programmes (C 60 cassette) in four minutes.

In addition to their reel-to-reel service, the company are now able to offer a high-speed cassette copying service. *Fraser-Peacock Associates Ltd., 94 High Street, Wimbledon Village, London, S.W.19.*

FET F.M. tuner

Tripletone announce their Solid State FET F.M. Tuner which uses a dual gate f.e.t., minimising drift and giving improved signal/noise performance. The outputs are fed via emitter followers.

The tuner can be supplied in mono form to which the decoder board can be plugged in at a later date. Price of the Stereo Mk. 2 F.M. Tuner is £37 19s. 10d. including PT complete with decoder. The mono version costs £31 9s. and the decoder unit separately is £8. Both models are available without teak case at £35 1s. 3d. and £28 13s. 9d. respectively. *The Tripletone Manufacturing Co. Ltd., 241a The Broadway, Wimbledon, S.W.19.*

Mullard pocket data book

We hear from Mullard that stocks of their 1969 Pocket Data Book are now exhausted. It is regretted therefore that no further orders can be accepted. Preparations for the 1970 edition are, however, in hand and a further announcement will be made in due course.

V.H.F./F.M. reception on band II

With the announcement by the Minister of Posts and Telecommunications (G.P.O.) of the next twelve Local Broadcasting Stations, it is appropriate to draw attention to the need for suitable aerials and properly adjusted v.h.f. receivers.

The BBC recently completed an analysis of complaints of unsatisfactory v.h.f. reception received during 1968/69 and this shows that more than 50% of complaints were due to the use of inadequate aerials or to faulty or maladjusted receivers.

Class 'B' stereo

Welbrook Engineering and Electronics Ltd. have released two new stereo amplifiers both incorporating an entirely new design of output circuit.

For further details on the amplifiers, model W.30 priced at £52 and model W.20 priced at £42, contact *Welbrook Engineering and Electronics Ltd., Brooks Street, Stockport, Cheshire, SK1 3HT.*

Readers are cordially invited to the
Practical Wireless and Practical Television Filmshow
(in collaboration with Mullard Ltd.)

at

Caxton Hall, Caxton Street, London, S.W.1
(Great Hall Site)

on

Friday 6th March, 1970

7-15 p.m. for 7-30 p.m.


W. N. Stevens, Editor Practical Wireless and Practical Television
will be in the chair

The film this year is entitled "Something big in Microcircuits"
and the principal speaker will be Mr. Ian Nicholson of Mullard Ltd.

THE MICROTEST

a multi-range test meter

C. MARSHALL

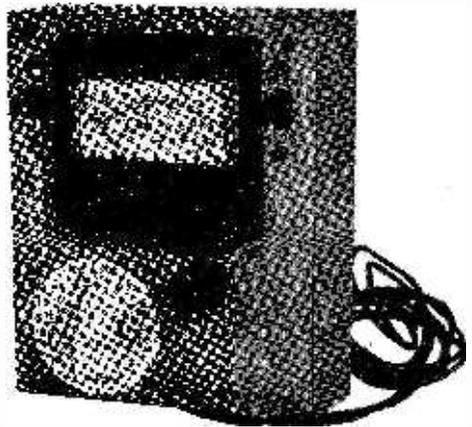

IT is generally true that the more accurate a multi-meter is, the larger it will be and the greater will be its cost. For many home constructors both space and money are severely limited, and they are usually forced into either buying or making a small, cheap multimeter. The accuracy of such a meter is limited partly by the short-scale length which limits the reading accuracy, and partly because of the limited number of ranges which are provided. This latter failing means that many readings must be taken near the zero end of the scale where the accuracy is greatly reduced.

This article begins by discussing some of the factors which limit the accuracy of a multimeter, then describes a multimeter which reduces the effects of these limitations by providing many more ranges than usual but without using any non-standard switches. The Microtest is both small and inexpensive, but maintains a high standard of accuracy comparable to instruments costing much more.

MULTIMETER ACCURACY

The most common measurement made by a multi-meter is that of voltage, although the same sources of error also affect the measurement of current. The voltmeter is basically a high sensitivity current meter in series with a high resistance, and there are five sources of error associated with such an arrangement.

1. The voltmeter may draw current from the voltage source it is required to measure, and this may affect the voltage being measured. This situation can best be improved by reducing the full scale current required by the meter. It is normally difficult to obtain meters more sensitive than $50\mu\text{A}$ f.s.d. and this is the sensitivity that is used in the Microtest.

2. The meter scale on anything but the most expensive meters is normally a mass-produced linear scale, but unfortunately the actual meter deflection may not be exactly linear, thus causing an error in reading. This error is usually greatest at about centre scale, but its magnitude is seldom quoted in advertisements for meters of the type intended for this instrument. Its effect is normally lumped together with the next source of error to give an overall accuracy figure for the meter.

3. The meter required for the Microtest has a nominal sensitivity of $50\mu\text{A}$ f.s.d., but unless the meter is individually calibrated (and thus expensive), its actual sensitivity will differ from the nominal value. The magnitude of this error is normally given so as to cover both the f.s.d. error and the non-linearity error, and is typically about 2% of the

reading, although it is often quoted as the same percentage of the full-scale reading.

4. The most important source of error in a multi-meter is the error involved in reading what the meter deflection actually is, and this is the real limitation on the smallness of a multimeter. A typical $2\frac{1}{2}$ inch square meter has a scale length of about 3 inches, and with a fine knife-edge pointer it should be possible to read the meter to within $\pm 0.5\mu\text{A}$, or 1% f.s.d. The scale markings are normally so coarse that any improvement on this would be difficult. It may be thought that an error of 1% should hardly be called "most important", and this would be true if the error were to remain at a constant 1% over the whole scale, but unfortunately this is not the case: the error is a fixed $0.5\mu\text{A}$ at all points on the scale.

Most multimeters provide ranges which increase in multiples of ten, such as 10V, 100V, 1000V etc. If it were required to use such a meter to read a voltage of 101V, then this would have to be measured on the 1000V scale, and the meter deflection would be only about 10% full scale. When making this reading our fixed error of $0.5\mu\text{A}$ causes an error of no less than 10%, which is far from being unimportant. If however the ranges were grouped closer together so that it was never necessary to make a reading at less than 25% full scale, then this error is kept to the much more satisfactory level of 4%.

The ideal system would be to have the ranges increasing in multiples of $\sqrt{10}$ each time, giving full scale deflections of 1V, 3.16V, 10V, 31.6V, etc, and a maximum error of about 3%, but unfortunately meters with suitable scales are not generally available in the price range required. However a reasonable compromise can be made by having ranges of 1V, 2.5V, 10V, 25V, etc, where the maximum error is 4%. A scale divided into 100 equal divisions will give easy reading on all ranges. To provide coverage from 1V to 1000V f.s.d. using these scales would normally require seven positions of the range switch, and for a similar coverage of current ranges from $100\mu\text{A}$ to 2.5A would require a further ten positions. Although it is not impossible to obtain eighteen way switches, they are very expensive, and a much simpler solution is possible. If ranges are provided on the switch in the usual scale-of-ten series, and a separate two way switch is used to change the meter sensitivity to give the intermediate 25V ranges, then only nine range positions are needed to give the required coverage, leaving three other positions of a standard twelve way switch for resistance ranges. This is the method used in the Microtest to provide increased accuracy for a given meter size, with fewer compo-

nents and reduced cost. The actual circuits used are described later.

5. The final source of error comes from the multiplier resistors themselves, and these are the components over which the constructor has the most control. These can be obtained to almost any required accuracy, and 1% resistors are the ones recommended for this circuit. A higher accuracy would greatly increase the cost without a great increase in meter accuracy, because of the other sources of error. If a somewhat lower performance is satisfactory then 2% resistors could be used instead. In order that the accuracy of the meter should not change with age, it is important that high stability resistors should be used throughout.

We have therefore three sources of error affecting the accuracy of our multimeter: a sensitivity error of 2%, a multiplier error of 1%, and a reading error of $0.5\mu\text{A}$, which is at worst a 4% error. The maximum error should therefore not be greater than 7% at the worst case and 4% at the best. Fortunately, because these sources of error may be of differing signs the actual error is likely to be very much less than this, and it can be shown that a better estimate of the maximum error is given by taking the square root of the sum of the squares of the individual errors. This gives an error of 4.6% at the worst case and 2.5% at full scale, which is quite adequate for most construction and repair work.

As a comparison, if the accuracy of reading had been improved by doubling the scale length of the meter (and at least doubling its cost), and ranges were provided in the usual scale of ten, then the worst case accuracy would have been 5.5%. A ready built meter costing about £10 would not be expected to be better than about 3% accurate.

When a.c. voltages are being measured with a multimeter, the resistance of the bridge rectifier is in series with the multiplier, and this can cause additional errors on the low voltage ranges. On the Microtest, 1V and 2.5V a.c. ranges are provided with the intention that these be used only for indicating the presence of a small signal, not for making accurate measurements at these levels. The rectifier can cause gross non-linearity of the scales, and the maximum error on these ranges can easily be as high as 20%. Similar remarks would also apply to any other multimeter providing such ranges without the use of an amplifier. It is most important that this limitation is realised when using the Microtest.

THE CIRCUIT

The full circuit is shown in Fig. 1, and this will be studied in its separate functions.

Most of the circuitry is fairly standard, except for the two way switch associated with the meter which is used to change the sensitivity of the meter. With the switch in the x1 position the series and shunt resistors have no effect. If the meter is of 1000 ohms internal impedance (a typical value) the meter will

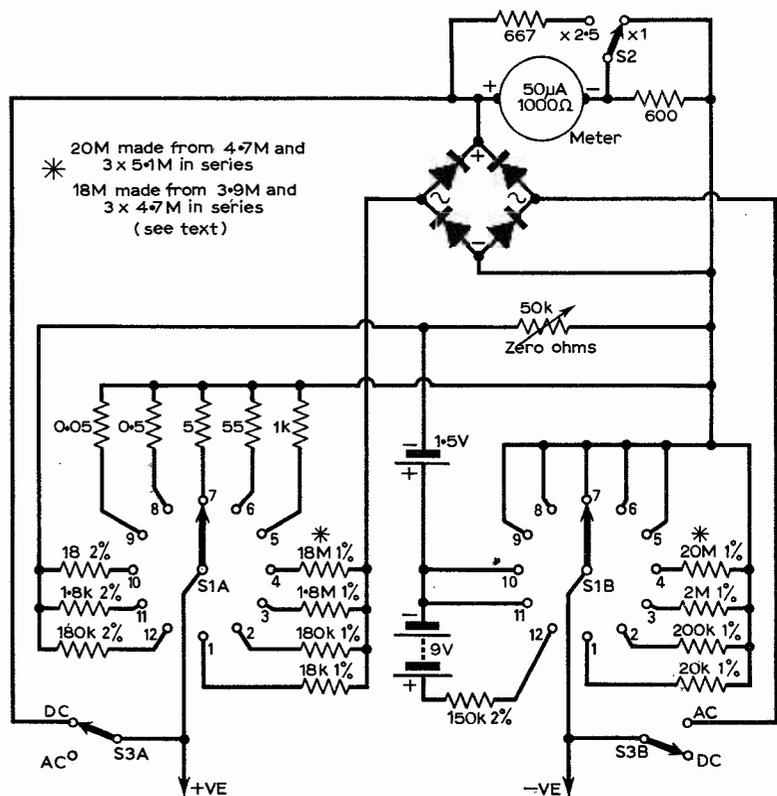


Fig. 1: The complete circuit of the Microtest.

read full scale when $50\mu\text{A}$ passes through it (voltage ranges) or when 50mV is applied across it (current ranges). When the switch is moved to the $\times 2.5$ position, a shunt is placed across the meter which reduces the sensitivity to $125\mu\text{A}$ f.s.d. The series resistor reduces the voltage sensitivity of the shunted meter to 125mV f.s.d. These two adjustments have the effect of multiplying the voltage or current required for full scale deflection on any range by 2.5. This function may be used on any voltage or current range provided by the meter, but not on the resistance ranges.

One small disadvantage of this feature should be pointed out here. When the Microtest is being used to measure a voltage on the $\times 2.5$ range, then the current drawn from the voltage source for full scale deflection will be $125\mu\text{A}$, giving a sensitivity of only $8\text{k}\Omega/\text{V}$, compared to $20\text{k}\Omega/\text{V}$ on the x1 range. If the source being measured is of a high internal impedance, then different readings would be obtained according to which range was being used for the measurement because of the different loadings imposed on the source. For most measurements this effect causes negligible error, but it is important to be aware that it can occur in certain cases.

The range switch S1 is a two-pole twelve-way switch and for most convenience in use it should be the type without a stop, to allow continuous rotation. A ceramic switch with silver plated contacts would be the best from the point of view of reliability, but a paxolin wafer switch costing only a few shillings can give many years good service before the contacts wear. Once again a compromise is necessary between cost and performance, and it is worth spending some time deciding just what sort of performance you

require from your Microtest, then spending accordingly.

S1b switches in the d.c. multiplier resistors and the appropriate batteries for the resistance ranges. S1a switches the shunts for the current ranges, and the multipliers for the a.c. voltage ranges and the ohms ranges. All the multipliers are standard values at 1% tolerance and little difficulty should be experienced in obtaining them. The a.c. voltage multipliers are chosen so that the meter reads r.m.s. voltage for a sine wave input; for other input waveforms the meter will read 1.11 times the average voltage.

The 1000V multipliers on the a.c. and d.c. ranges will have to withstand up to 2500V when the $\times 2.5$ function is used. While this does not exceed the power rating of the resistors, it does exceed their voltage rating of about 750V. To get round this problem each of these multiplier resistors is made up from four separate resistors so as to divide the voltage load between them. Under no circumstances should fewer resistors be used, and even so, care must be taken when wiring up the Microtest to provide a good clearance between the high-voltage multipliers and the other components.

The bridge rectifier used in the original Microtest was a surplus unit advertised simply as a $50\mu\text{A}$ meter rectifier. Almost any meter rectifier will work in the circuit, but in order to keep the scale linear a metal oxide rectifier of the type intended for use at $50\mu\text{A}$ should be used. The leakage resistance of the bridge should be as high as possible or the meter sensitivity will be reduced. The addition of the bridge rectifier introduces an error of up to 2% on all a.c. voltage measurements.

The current ranges provided are of perfectly standard form, each range being obtained by a separate shunt. The resistance quoted for the shunts on the circuit are approximate values only, and are given for 1000 ohm meter. In practice the shunts have to be individually adjusted to give the required ranges, and this process is described in more detail below. A $50\mu\text{A}$ range was not provided on the original Microtest, $100\mu\text{A}$ being the most sensitive range. The reason for this was simply the lack of available positions on the range switch. If a $50\mu\text{A}$ range were considered essential, it could easily be provided, but only at the expense of, say, the 1A range.

Three resistance ranges are provided, these having 18Ω , $1.8\text{k}\Omega$ and $180\text{k}\Omega$ as the centre scale readings. These three ranges are adequate to cover the full range of preferred values of resistance, and to give reasonable indications down to 0.1Ω . Using standard 2% resistors for the resistance ranges will give an accuracy of between 5% and 10% over the useable portion of the scales, which is about as good as any other multimeter. For increased accuracy of measurement other techniques such as a bridge have to be employed. The accuracy of the resistance range is not greatly dependent upon the battery voltage, but these should be renewed as soon as their voltage begins to fall to prevent the possibility of their leaking into the case and damaging other components.

A few words about the choice of meter would not be amiss here, as this is the heart of the instrument. Within reason it is usually worth getting the most expensive meter you can afford, as its accuracy will increase with price. There would be little point in getting a meter bigger than about 4 inches square or the instrument would hardly warrant the Microtest; about 3 inches square would seem to be a reasonable compromise between cost and performance. The scale

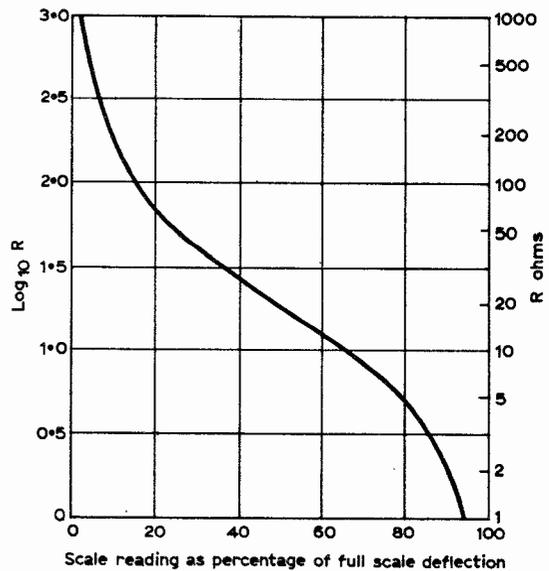


Fig. 2: Resistance measurements can be calculated from a graph stuck on the bottom of the case.

is best divided into 100 equal divisions, marked 0-10. A fine knife edge pointer will greatly increase the accuracy of reading the meter. The resistance scale may be either drawn directly onto the meter's scale plate if great care is taken, or a calibration graph may be attached to the back of the Microtest. A graph suitable for either purpose is given in Fig. 2.

CONSTRUCTION AND TESTING

The component layout of the Microtest is in no way critical, except that high current leads should be kept as short as possible to avoid unwanted voltage drops. Because the actual size and layout of the instrument will depend to a large extent on the meter chosen for the Microtest, no details are given of the cabinet construction or component layout. The prototype used a three inch square meter, and the whole instrument was built into a Formica box $4\frac{1}{2}'' \times 5\frac{1}{2}'' \times 1\frac{1}{2}''$ deep. Either the front or back of the instrument should be easily removable to enable the batteries to be changed when necessary.

All the multipliers and shunts are mounted directly onto the range switch to minimise their lead length. The shunt and series resistors used to change the meter sensitivity are mounted directly onto the multiplier switch, and the bridge rectifier is mounted on the a.c./d.c. switch. The batteries can be held in place by small sponge pads on the lid of the case. Contact is made to the 9V battery by a snap connector, and to the 1.5V battery by two small brass contacts fixed to the case. The "ohms-zero" control should preferably be a wire-wound control for reliability.


The Microtest should first be built omitting the current shunts and the $\times 2.5$ multipliers. No provision is made in the circuit for accurately setting the voltage ranges, but if a high accuracy meter is available it is worth getting an estimate of the accuracy of the Microtest by comparing the readings of the two instruments when they are reading the same voltage. The accuracy should be within the limits stated in the first section. If such a comparison is not possible then it must be assumed that the error is zero when using the instrument.

The $\times 2.5$ multiplier must now be added. Using

any convenient voltage source such as a twelve volt battery in series with a $50k\Omega$ variable resistor, set the Microtest and the variable resistor until the meter reads full scale on the 10V range. The multiplier switch should be set to $\times 1$. Now without altering any other components, select a resistor or a number of resistors so that when soldered directly across the meter terminals the reading drops from 10V to 4V.

While the meter is still set up reading 10V full scale the $100\mu A$ shunt can be prepared by the same technique. This time a resistor is required that will reduce the meter deflection to half scale (5V), and again this should be done as accurately as possible. When selected it should be wired directly onto the range switch in the correct position for the $100\mu A$ range. The series resistor of the $\times 2.5$ multiplier can now be selected.

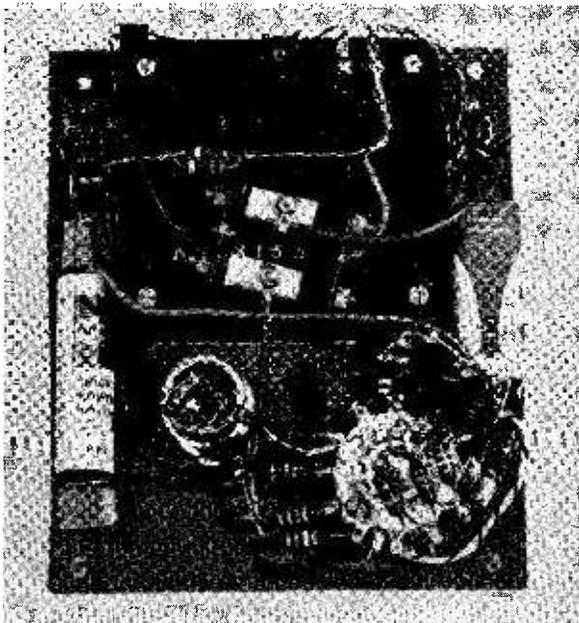Connect a 9V battery, $100k\Omega$ variable resistor and the Microtest set to read $100\mu A$ all in series, and adjust the variable resistor until the meter reads full scale. Now try a number of resistors in the multiplier position until one is found which gives a meter reading of $100\mu A$ in the $\times 1$ position and $40\mu A$ in the $\times 2.5$ position. This resistor may then be left in



An interior view of the prototype.

position, completing the setting up of the range multiplier. This will have a negligible effect on the accuracy of the voltage ranges.

There are two methods of adjusting the three remaining current shunts. The simplest and most accurate method is to use a calibrated meter in series with the Microtest, then adjusting the appropriate shunt until the two instruments read exactly the same. All adjustments should be carried out at the current required to give full scale deflection of the Microtest. Great care must be taken to ensure that the full current is never passed through the meter except when the shunt is firmly soldered into place, or the meter will be severely, if not fatally, damaged. The 1A shunt should be made from wire no thinner than 22swg, or it will be burnt out when the 2.5A passes through it. The other shunts are not particularly critical as the currents involved are small. A

few feet of thin copper wire should be sufficient for the 100mA shunt and two 10 ohm resistors in parallel form the basis of the 10mA shunt.

The alternative method of calibration is to use one range of the Microtest to set the current being used to calibrate the next range up. This method is not to be recommended if the first method is possible, because errors gradually creep in during the calibration, and the 1A range can easily be as much as 10% in error. A regulated supply of at least 30V in series with an appropriate value of variable resistor is used as the current source.

Initially the meter is set to read $250\mu A$ f.s.d. and the current adjusted to exactly this value. This setting should be continually checked during the next stage. Wire in an appropriate value resistor as a 1mA shunt, then turn to this range. With the multiplier switch set to $\times 1$, adjust the 1mA shunt until the meter reads exactly $250\mu A$. The 1mA range is now calibrated, and this range may now be used to set the reference current to 2.5mA, which is used in turn to calibrate the 10mA range. This process is repeated until all the shunts are correctly adjusted. It is then worth repeating the whole process to check the final accuracy. When using the meter it is important that all the ranges should agree with one another at the points where they overlap. When these shunts are finally set to your satisfaction, the Microtest is ready for use.

★ components list

Resistors

1% high stability types

18k Ω , 20k Ω , 180k Ω , 200k Ω , 1.8M Ω , 2M Ω , 3.9M Ω , 4x4.7M Ω , 3x5.1M Ω .

2% high stability types

18 Ω , 1.8k Ω , 150k Ω , 180k Ω .

High stability types selected for use as shunts

5 Ω , 55 Ω , 600 Ω , 680 Ω , 1k Ω .

Zero-ohms potentiometer, 50k Ω wirewound.

Switches

2 pole 12 way rotary.


2 pole 2 way slide type.

1 pole 2 way slide type.

Miscellaneous

Batteries: 1.5V U16, 9V PP3; Rectifier: 50 μA bridge meter type; Meter movement: 3in. square moving coil.

No meter will remain accurate for long if it is regularly overloaded: the needle will get bent and the coil will be damaged. To avoid such accidents with any multimeter always begin making a measurement with the meter set to the highest range, then working down. When making current measurements, do not change ranges while the meter has a high current flowing through it, as it is possible for the shunt to be disconnected for an instant as the switch is moved, and in that instant the meter may be damaged. Provided the Microtest is treated, like all other sensitive instruments, with care and respect, it will provide many years of useful service, repaying its cost many times over. ■

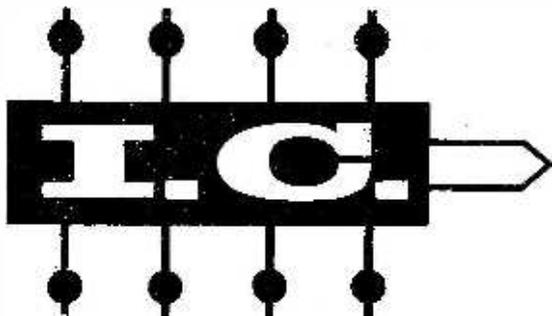

OF THE MONTH

L.A.J. IRELAND

Number 4

The Mullard TAD100, a.m. tuner and preamp.

IN January of 1968 Mullard introduced their TAD100 linear i.c. which was principally designed for use in medium and long wave portable receivers although the frequency response of the circuit was such that it could also be used as a 10.7MHz i.f. amplifier and audio preamp. in f.m. receivers. In addition to many of the passive components required in an ordinary radio set the circuit also incorporates all the active elements as far as the audio driver stage. Different output stages can therefore be chosen to suit individual requirements. This month's article describes how the TAD100 may be used in a medium wave receiver giving an audio output of about 500mW.

The complete receiver circuit is shown in Fig. 1. The first three transistors are used in the front end of the receiver with the first stage of the long-tailed pair transistors acting as an r.f. amplifier and the second stage as mixer. A separate transistor is used as the local oscillator with the oscillator signal injected at the base of Tr2 and the i.f. produced extracted at its collector. The block filter type LP1175 is the only selectivity element used to extract the 470kHz signal but it provides sufficient attenuation and bandwidth as three conventional i.f.t.'s.

Due to the emitter follower action of Tr4 and Tr5 the input impedance of the i.f. amplifier is very high and the three stages are arranged in a d.c. feedback circuit to the base of Tr3. Tr7 acts as the detector with the audio signal appearing across its emitter resistor and it also supplies the a.g.c. voltage for controlling the bias of Tr1.

Due to its stability and flexibility the differential amplifier or long-tailed pair arrangement forms the basic circuitry in most linear i.c.'s and where previously it would have been economic madness to use extra discrete transistors the i.c. comes into its own. Even in the audio stages of the TAD100 this is evidenced with the use of four transistors in the preamp and driver stages. The audio signal from the volume control is applied to the base of Tr9 which is diode connected to the Darlington pair Tr10 and Tr11. Overall negative feedback of up to 20dB can very neatly be applied to the base of Tr8 thereby providing good stability under a wide range of operating conditions. The only two other active elements used in the set are the complementary output pair of transistors Tr12 and Tr13 and these are directly coupled to the i.c. driver stage and deliver 500mW into a 15 ohm speaker.

Continued on page 765

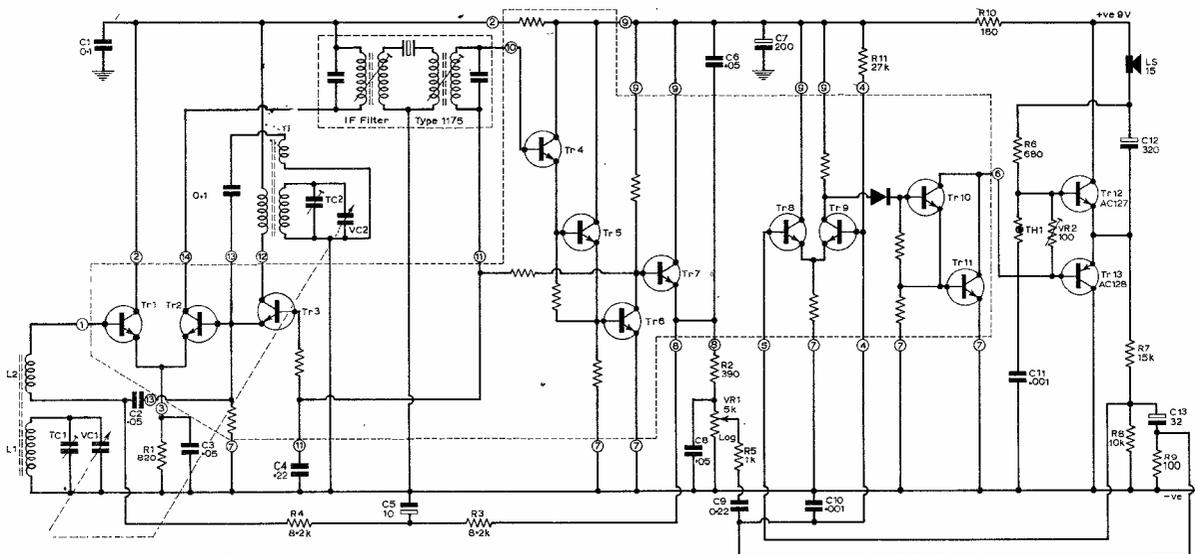


Fig. 1: A practical circuit for a m.w. radio using the TAD100 and an i.f. filter type 1175. The thermistor and C11 junction should be shown connected to the base of Tr13.

4! brings you a mountain of components at manufacturers' prices

The serious amateur should never be without this comprehensive price list and guide to semiconductors and electronic components from RCA, IR, SGS, Emihus, Semitron, Keyswitch, Plessey, Morganite, Litesold and others (together with manufacturers' application data) which you can buy direct from us at *manufacturers' prices* e.g. **IN914 1/3d.**

IN916 1/11d. **2N697 4/5d.** **2N706 2/3d.** **2N706A 2/9d.** **2N929 5/8d.**
 2N1613 4/8d. **2N3011 9/1d.** **2N3053 6/2d.** **2N3055 15/9d.** **3N140 15/3d.**
BFY50 4/8d. **BFY51 3/9d.** **BSY27 18/-**
BSY95A 3/3d. **C407 4/6d.** **CA3012 18/3d.** **CA3014 25/6d.** **CA3020 25/9d.**
OA200 1/9d. **OA202 1/11d.**




Build the NEW Mainline Audio Amplifier kits - UP TO 70 WATTS

The result of the combined resources of SGS and RCA, these quasi circuits set new standards in quality and performance. Each kit is complete with circuit diagram, all semiconductors, resistors, capacitors and printed circuit board.

12A	£7. 0. 0.
25A	£8. 5. 0.
40A	£9. 0. 0.
70A	£10.10. 0.

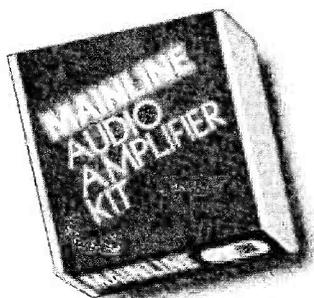Any two will make an outstanding stereo equipment.



To: Mainline Electronics Limited, Thames Avenue, Windsor, Berkshire

I enclose 4/-. Please send me your price list and guide

I am interested in Amp Mainline Audio Amplifier Kits. Please send me full data

I am interested in receiving data on preamplifier & power supply kits

NAME _____ ADDRESS _____

(A member of the ECS Group of Companies)

PW270

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government 38 CHALCOT ROAD, LONDON, N.W.1 Telephone 01-722-9090

EXPRESS POSTAL SERVICE, SAME DAY DESPATCH BY FIRST CLASS MAIL.
All goods are offered subject to the standard three month guarantee.

OA2	5/9	6F1	8/9	12AX7	4/6	306	13/19	EB91	2/3	EM80	7/6	PCCR06	15/6	UBL21	9/2	W729	10/-	BA129	2/6	OA47	2/-
OB2	6/-	6F6G	4/9	12AY7	9/9	807	11/19	EB41	9/6	EM81	7/6	PCFR8	6/6	UC92	5/6	X24	16/6	BA130	2/4	OA70	3/4
OZ4	4/6	6F6M	12/6	12BA6	6/-	956	2/6	EB81	5/9	EM84	6/6	PCF82	6/3	UCC84	8/-	X41	10/9	BCY10	5/-	OA73	3/4
IA3	4/6	6F12	3/6	12BE6	5/9	1821	10/6	EB90	4/-	EM85	11/-	PCF84	8/-	UCC85	6/9	X61	5/9	BCY12	5/-	OA79	1/9
IA5	5/6	6F13	3/6	12BF7	6/-	5763	10/6	EB91	5/6	EM87	7/6	PCF86	9/-	UCF80	8/3	X63	5/6	BCY33	5/-	OA81	1/9
IA7GT	7/3	6F15	3/6	12BE1	7/6	6060	5/6	EB90	6/9	EY51	7/6	PCF87	16/-	UCF81	6/6	X66	12/6	BCY34	4/6	OA85	1/6
IC1	5/6	6F18	7/6	12BF7	6/-	7193	10/6	EB89	6/3	EY83	8/3	PCF80	13/-	UCF82	13/-	X65	5/6	BCY38	4/6	OA90	2/6
IC2	9/-	6F23	13/3	12JGT7	6/6	7475	4/6	EBF89	6/3	EY84	7/6	PCF81	7/-	UCF83	10/6	X64	12/6	BCY39	4/6	OA91	1/9
IC3	7/-	6F24	11/9	12K5	10/-	A1834	20/-	EBC11	11/-	EY86	6/6	PCF85	11/6	UCF84	13/-	X101	30/6	BCY38	5/6	OA96	4/6
IC5	4/9	6F25	13/-	12K7GT	5/9	A2134	10/6	ECS3	12/6	EY87	6/6	PCF86	11/6	UCF85	10/6	X109	26/6	BCY38	5/6	OA96	4/6
ID5	6/9	6F28	14/-	12QGT7	4/6	A3042	15/-	ECS4	6/-	EY88	7/6	PCF87	12/6	UCF86	9/6	X119	6/6	BCY39	4/6	OA99	2/6
ID6	9/6	6F32	3/6	12S7GT	6/6	ACZPEN	19/6	ECS6	12/6	EY91	3/6	PCF88	12/6	UCF87	10/6	X119	6/6	BCY39	4/6	OA99	2/6
IFD1	6/6	6G6G	2/6	12S7GT	6/6	ACZPEN	19/6	EC86	12/6	EY91	3/6	PCF88	12/6	UCF87	10/6	X119	6/6	BCY39	4/6	OA99	2/6
IFD9	4/3	6HG6T	1/9	12SG7	3/6	ACZPEN	19/6	EC88	12/6	EY91	3/6	PCF88	12/6	UCF87	10/6	X119	6/6	BCY39	4/6	OA99	2/6
IG6	6/-	6J5G	3/9	12SH7	3/6	DD	19/6	EC92	6/6	EZ40	7/6	PCF84	7/6	UCF86	9/6	Z32	4/6	BC107	4/6	OA200	1/6
IHG5T	7/-	6J5GT	4/6	12S7	4/6	ACZPEN	19/6	ECC31	15/6	EZ41	8/6	PCF85	11/6	UCF87	10/6	Z32	4/6	BC108	3/6	OA202	2/6
ILA	2/6	6J6	3/6	12SK7	4/6	AC/PEN	5/6	ECC32	4/6	EZ40	4/6	PCF86	9/6	UCF88	10/6	Z32	4/6	BC113	5/6	OA210	9/6
ILDS	6/9	6J7G	4/9	12S7GT	7/6	AC/PEN	19/6	ECC33	31/6	EZ81	4/6	PCF87	12/6	UCF89	10/6	Z32	4/6	BC115	5/6	OA211	13/6
ILNS	8/-	6J7GT	6/6	12S7GT	9/6	AC/PEN	19/6	ECC34	29/6	EY81	3/6	PCF88	12/6	UCF90	10/6	Z32	4/6	BC116	5/6	OA220	12/6
INSGT	7/9	6K7G	2/6	14S7	15/-	ACTH	19/6	ECC40	9/6	FC4	12/6	PCF81	15/-	UCF91	10/6	Z32	4/6	BC119	9/6	OA220	12/6
IP1	7/-	6K7GT	4/6	18	12/6	ACTH	19/6	ECC81	3/9	FW4/500	6/6	PEN45	7/-	UCF92	10/6	Z32	4/6	BC121	6/6	OA219	9/6
IP10	5/9	6L1	19/6	19A05	4/9	ACTH	19/6	ECC82	4/6	FW4/800/10	12/6	PEN45DD	12/-	UCF93	10/6	Z32	4/6	BC122	6/6	OA220	12/6
IP11	5/9	6L6GT	7/9	19H1	40/-	ACTH	19/6	ECC83	4/6	GZ20	7/-	PEN45	12/-	UCF94	10/6	Z32	4/6	BC123	6/6	OA221	13/6
IS5	5/6	6L7	12/6	20F1	13/6	ACTH	19/6	ECC84	5/6	GZ23	9/6	PEN45	12/-	UCF95	10/6	Z32	4/6	BC124	6/6	OA222	13/6
IS4	4/9	6L8	6/-	20F2	20/5	ACTH	19/6	ECC85	8/-	GZ23	12/6	PEN45	12/-	UCF96	10/6	Z32	4/6	BC125	6/6	OA223	13/6
IS5	4/3	6L9	19/-	20F4	14/6	ACTH	19/6	ECC86	8/-	GZ24	10/6	PEN45	12/-	UCF97	10/6	Z32	4/6	BC126	6/6	OA224	13/6
IT4	2/9	6LD20	9/6	20L1	13/6	ACTH	19/6	ECC88	7/-	GZ27	14/6	PEN45	12/-	UCF98	10/6	Z32	4/6	BC127	6/6	OA225	13/6
IU4	5/9	6N7GT	6/6	20P1	17/6	ACTH	19/6	ECC91	3/9	H30	5/6	PEN/AD	12/-	UCF99	10/6	Z32	4/6	BC128	6/6	OA226	13/6
IU5	5/9	6P1	12/-	20P3	18/-	ACTH	19/6	ECC89	9/6	HABC80	8/-	PEN/AD	12/-	UCF100	10/6	Z32	4/6	BC129	6/6	OA227	13/6
LD5	12/6	6P25	12/6	20P5	18/-	ACTH	19/6	ECC90	9/6	HL13C	4/6	PEN/AD	12/-	UCF101	10/6	Z32	4/6	BC130	6/6	OA228	13/6
2D13C	7/-	6P26	12/6	20P5	18/-	ACTH	19/6	ECC91	9/6	EC808	27/6	PEN/AD	12/-	UCF102	10/6	Z32	4/6	BC131	6/6	OA229	13/6
2D21	5/6	6P28	25/-	25L6GT	5/6	ACTH	19/6	ECC92	6/6	HL14	3/9	PEN/AD	12/-	UCF103	10/6	Z32	4/6	BC132	6/6	OA230	13/6
2X2	4/9	6Q7G	6/6	25Y5	6/6	ACTH	19/6	ECC93	6/6	HL41DD	19/6	PEN/AD	12/-	UCF104	10/6	Z32	4/6	BC133	6/6	OA231	13/6
3A4	3/6	6Q7GT	8/6	25Y5G	8/6	ACTH	19/6	ECC94	6/6	HL42DD	8/-	PEN/AD	12/-	UCF105	10/6	Z32	4/6	BC134	6/6	OA232	13/6
3A5	10/-	6R7	7/6	25Z2G	6/6	ACTH	19/6	ECC95	6/6	HN309	27/4	PEN/AD	12/-	UCF106	10/6	Z32	4/6	BC135	6/6	OA233	13/6
3BT	5/6	6R7	7/6	25Z2	7/6	ACTH	19/6	ECC96	6/6	HL13C	4/6	PEN/AD	12/-	UCF107	10/6	Z32	4/6	BC136	6/6	OA234	13/6
3D6	3/9	6SA7GT	7/6	30D4	20/5	ACTH	19/6	ECC97	6/6	EC88	27/6	PEN/AD	12/-	UCF108	10/6	Z32	4/6	BC137	6/6	OA235	13/6
3Q4	6/6	6SA7	7/6	30C1	6/6	ACTH	19/6	ECC98	6/6	EC88	27/6	PEN/AD	12/-	UCF109	10/6	Z32	4/6	BC138	6/6	OA236	13/6
3Q5GT	6/-	6SC7GT	6/6	30C15	13/6	ACTH	19/6	ECC99	6/6	EC88	27/6	PEN/AD	12/-	UCF110	10/6	Z32	4/6	BC139	6/6	OA237	13/6
3S4	5/9	6S7	6/6	30C17	16/6	ACTH	19/6	ECC100	6/6	EC88	27/6	PEN/AD	12/-	UCF111	10/6	Z32	4/6	BC140	6/6	OA238	13/6
3V4	5/9	6S7	6/6	30C18	11/6	ACTH	19/6	ECC101	6/6	EC88	27/6	PEN/AD	12/-	UCF112	10/6	Z32	4/6	BC141	6/6	OA239	13/6
3Y4	5/9	6S7	6/6	30C19	11/6	ACTH	19/6	ECC102	6/6	EC88	27/6	PEN/AD	12/-	UCF113	10/6	Z32	4/6	BC142	6/6	OA240	13/6
4R4G	8/9	6SK7GT	4/6	30F11	15/6	ACTH	19/6	ECC103	6/6	EC88	27/6	PEN/AD	12/-	UCF114	10/6	Z32	4/6	BC143	6/6	OA241	13/6
5U4G	4/9	6SN7GT	4/6	30F12	16/6	ACTH	19/6	ECC104	6/6	EC88	27/6	PEN/AD	12/-	UCF115	10/6	Z32	4/6	BC144	6/6	OA242	13/6
5V4G	7/6	6SO7GT	7/6	30F13	8/6	ACTH	19/6	ECC105	6/6	EC88	27/6	PEN/AD	12/-	UCF116	10/6	Z32	4/6	BC145	6/6	OA243	13/6
5Y3GT	5/6	6S5	3/6	30F14	12/6	ACTH	19/6	ECC106	6/6	EC88	27/6	PEN/AD	12/-	UCF117	10/6	Z32	4/6	BC146	6/6	OA244	13/6
5Z3	8/-	6U7G	7/6	30L1	6/3	ACTH	19/6	ECC107	6/6	EC88	27/6	PEN/AD	12/-	UCF118	10/6	Z32	4/6	BC147	6/6	OA245	13/6
6A3	7/6	6Z4G	7/6	30L15	10/6	ACTH	19/6	ECC108	6/6	EC88	27/6	PEN/AD	12/-	UCF119	10/6	Z32	4/6	BC148	6/6	OA246	13/6
6/30L2	12/6	6V6G	3/6	30L17	15/6	ACTH	19/6	ECC109	6/6	EC88	27/6	PEN/AD	12/-	UCF120	10/6	Z32	4/6	BC149	6/6	OA247	13/6
6A8G	5/6	6X4	4/3	30P4	12/6	ACTH	19/6	ECC110	6/6	EC88	27/6	PEN/AD	12/-	UCF121	10/6	Z32	4/6	BC150	6/6	OA248	13/6
6A7C	3/6	6X5GT	5/6	30P4MR	17/6	ACTH	19/6	ECC111	6/6	EC88	27/6	PEN/AD	12/-	UCF122	10/6	Z32	4/6	BC151	6/6	OA249	13/6
6A5G	3/6	6Y6G	8/6	30P12	13/9	ACTH	19/6	ECC112	6/6	EC88	27/6	PEN/AD	12/-	UCF123	10/6	Z32	4/6	BC152	6/6	OA250	13/6
6A15	8/6	6Y7G	12/6	30P19	12/6	ACTH	19/6	ECC113	6/6	EC88	27/6	PEN/AD	12/-	UCF124	10/6	Z32	4/6	BC153	6/6	OA251	13/6
6A3S	5/6	7A7	12/6	30P13	15/6	ACTH	19/6	ECC114	6/6	EC88	27/6	PEN/AD	12/-	UCF125	10/6	Z32	4/6	BC154	6/6	OA252	13/6
6AK6	6/-	7AN7	6/3	30P15	15/6	ACTH	19/6	ECC115	6/6	EC88	27/6	PEN/AD	12/-	UCF126	10/6	Z32	4/6	BC155	6/6	OA253	13/6
6AK8	6/-	7B6	10/9	30P14	15/6	ACTH	19/6	ECC116	6/6	EC88	27/6	PEN/AD	12/-	UCF127	10/6	Z32	4/6	BC156	6/6	OA254	13/6
6AL5	2/3	7B7	7/6	30P15	15/6	ACTH	19/6	ECC117	6/6	EC88	27/6	PEN/AD	12/-	UCF128	10/6	Z32	4/6	BC157	6/6	OA255	13/6
6AM5	2/6	7C6	6/6	35A3	9/6	ACTH	19/6	ECC118	6/6	EC88	27/6	PEN/AD	12/-	UCF129	10/6	Z32	4/6	BC158	6/6	OA256	13/6
6AM6	3/3	7D6	15/6	35A5	15/6	ACTH	19/6	ECC119	6/6	EC88	27/6	PEN/AD	12/-	UCF130	10/6	Z32	4/6	BC159	6/6	OA257	13/6
6AOS	5/6	7F8	12/6	35D6	12/6	ACTH	19/6	ECC120	6/6	EC88	27/6	PEN/AD	12/-	UCF131	10/6	Z32	4/6	BC160	6/6	OA258	13/6
6AR6	20/-	7H7	5/6	35L6GT	8/6	ACTH	19/6	ECC121	6/6	EC88	27/6	PEN/AD	12/-	UCF132	10/6	Z32	4/6	BC161	6/6	OA259	13/6
6AT6	4/-	7R7	12/6	35W4	4/6	ACTH	19/6	ECC122	6/6	EC88	27/6	PEN/AD	12/-	UCF133	10/6	Z32	4/6	BC162	6/6	OA260	13/6
6A8G	5/6	7V7	5/6	35Z3	10/6	ACTH	19/6	ECC123	6/6	EC88	27/6	PEN/AD	12/-	UCF134	10/6	Z32	4/6	BC163	6/6	OA261	13/6
6AV6	5/6	7Y4	6/6	35Z4GT	4/6	ACTH	19														

REPAIRING TRANSISTOR RADIOS

V. CAPEL

PART 1

THE cheap transistor radio can often pose something of a headache for the professional engineer. All repairs take time, and sometimes an elusive fault can take more time than a straightforward fault on a television receiver. The situation is aggravated by a lack of service information and spares where, as is more often than not, the radio is imported. A repair bill can result which is a large proportion of the original cost of the set, and the owner naturally thinks he is being had.

Because of this, many dealers understandably refuse to accept these cheaper radios for re-
pair. Amateur repairers not having to make their time pay may agree to have a go, often later to wish they had not!

In general, it is prudent to set a time limit of say a quarter of an hour and if the fault cannot be located in this time, the set should be returned to the owner as being beyond economic repair. This calls for quick, short-cut methods of diagnosis and repair, some of which may be frowned upon if used with conventional equipment, but which in many cases would be the only alternative to refusing the repair. We should add that these remarks do not apply to the better class transistor radio which is backed by spares service and technical information. These should, of course, be serviced in the normal way.

A common fault is for the receiver to be completely dead. While in theory a number of things could be responsible, in practice a few faults crop up with almost monotonous regularity, so these can be checked first.

Batteries that have been left in cause corrosion of the contacts which of course remains when the owner fits new batteries. Often the trouble is nothing more than poor battery contact due to this cause. The remedy is obvious.

Another very common source of trouble is the on/off switch. Generally an integral part of an edge-type volume control, they are impossible to repair economically and the only course is to fit a complete new control. Fortunately, the value of the volume control seems to be standardised at $5k\Omega$, and a number of component firms make controls that will fit. The main consideration is physical size, if too large it will jam in the case aperture, and if too small, will not reach far enough through. The disposition of the contacts may not line up with the original on the printed panel but this can usually be overcome by bending some of the contacts and soldering a section of copper wire to those that may not reach. A few controls have the switch mounted externally in which case a repair can often be made by adjusting the switch contacts.

A quick test can be made on both battery contacts and switch by taking a voltage reading at some convenient point on the print, from an earth point, say one of the coil screening cans to one of the tags on the output or driver transformer. This should show almost full battery voltage, if it is

much less, there is a high resistance in series, possibly corroded battery contacts or faulty switch.

Correct voltage measured here means we must look further. Scratching the volume control terminals with the meter probe and the meter switched to the ohms range should produce crackling in the loudspeaker, and if so, suggests that the fault is in preceding stages. No crackling means trouble in driver or output circuit. Open-circuit loudspeaker speech coils are not at all uncommon, especially the higher impedances, so this is worth checking next; failing this, check earphone socket shorting contacts.

MECHANICAL DAMAGE

Often the radio has been subject to a fall and a frequent result is that the output or driver transformer is partly wrenched from its position in the print. A casual glance may not indicate this but sometimes one or more of the fine wires coming from the windings are broken away from their terminal posts. Whenever there is trouble in this end of the set, it is always worthwhile to make a visual examination of the transformers, especially the lead-out wires.

If the set is lively from the volume control onwards, flicking the waveband switch may produce clicks, which would suggest that the i.f. stages are working and that the mixer and r.f. stages should be investigated first. It is still possible for the i.f. stages to be at fault, but the odds are on the previous ones.

If the trouble appears in the first stage it is wise to check the connections to the ferrite aerial coils. The rod is not always rigidly mounted, and any mechanical shock could easily strain the fine wires from the coils to the print. In many cases these wires are left long enough by the makers to facilitate adjustment by sliding along the rod, but this slack may already be taken up by a previous alignment. Broken aerial wires are very common and can give rise to several faults. Complete lack of signals is one, where the broken lead is common to both wavebands or as is sometimes the case, where there are more than one broken. Often it leaves one waveband dead and sometimes produces a rather puzzling symptom of breakthrough from one band into the other. Thus the light programme on 1500 metres is superimposed on the BBC London or Welsh Home service.

A close look at the components mounted on the printed panel would not come amiss. Look for vertically mounted parts that are leaning over at an angle, suggesting they may have been forced and either damaged or pulled from their printed connection. Components mounted near the battery compartment are particularly prone to this sort of trouble by suffering from the attempts of a ham-handed owner to replace the batteries! A probe at any likely looking suspect with an insulated tool will confirm the suspicion.

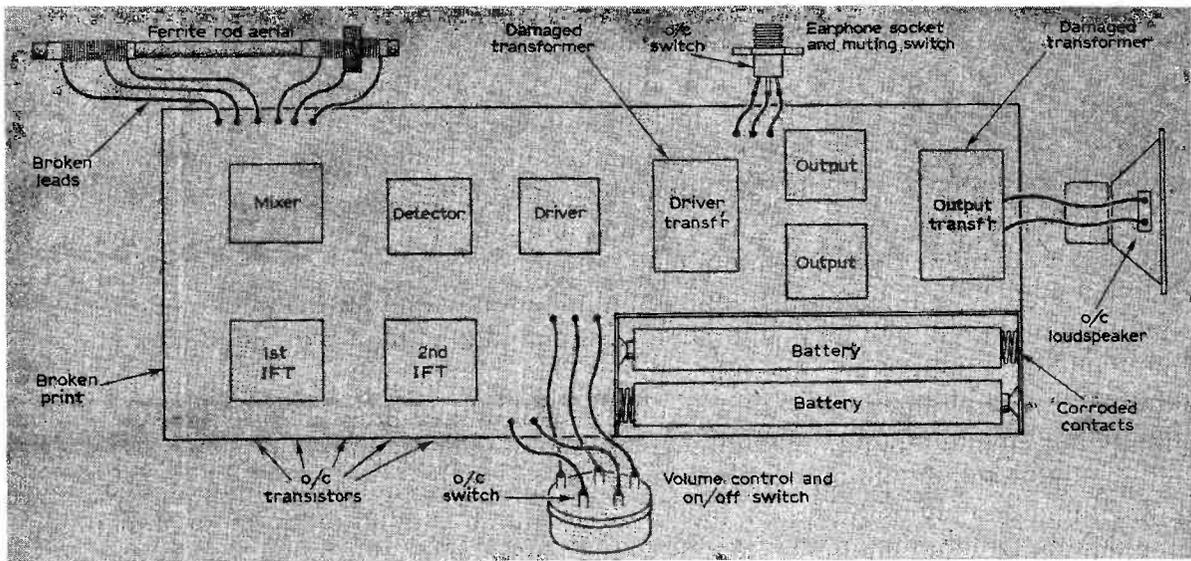


Fig. 1: The most common faults in a normal a.m. transistor radio.

The rough tests we have described followed by a visual check of the suspected part of the circuit will take just a matter of a few minutes. Many faults will come to light by this means. Remember that a large proportion of troubles with portable transistor radios are mechanical in origin.

Next, after these checks, the most likely possibilities to investigate are printed circuit faults or defective transistors. This is where the meter must be used again and voltage measurements taken. We will have already roughly isolated the section of the receiver in which the trouble lies, so now collector, base and emitter voltages of transistors within that section can be measured. If service information is not to hand, exact readings cannot be compared with correct figures, however in most cases defects can be quickly spotted.

Collector voltages are generally not less than about three-quarters of the battery voltage except in audio stages where the collector is directly coupled to the base of the following stage. Where two batteries or a tapped battery is used, the full voltage is often only applied to the output stage and perhaps the driver, the rest of the circuit being supplied from one battery or section.

Base and emitter voltages vary considerably according to the circuit from a few tenths of a volt to over one volt. The main thing is to compare the base voltage with the emitter. Assuming germanium p-n-p transistors, the base must be slightly more negative than the emitter, so a difference of one or two tenths of a volt should be measured. A higher base voltage could be due to an internal leak or an open-circuit bottom bleeder resistor to the base. A low base voltage could indicate an open-circuit top resistor. No emitter voltage is the result of an open-circuit transistor, unless of course the emitter has no series resistor. A high emitter and base voltage with a low collector voltage

betrays excessive current due to internal leakage.

Some confusion can result when taking voltage readings as to which point to measure from, as some sets have positive earths and others negative. It is usually the most straightforward practice to ignore the earth and to clip the positive lead of the meter to the battery positive terminal taking all readings from there.

If a transistor appears to be at fault, it is not always necessary to remove it in order to try a replacement. This takes time, and more time is wasted re-fitting it if it is not the trouble, to say nothing of possible damage by soldering (it is usually impossible to use a heat sink). In most cases, just connect a substitute in parallel with the suspect, on the print side of the board and without cutting the wires. If the set works, then the old one can be removed and the replacement fitted properly, if not, little time is wasted. The old one seems to have little effect on the working except where it is drawing excess current. In such case, just disconnect the collector wire.

Many imported sets use transistors with type numbers that mean little to the average engineer. An equivalent list is very handy if available. If not,

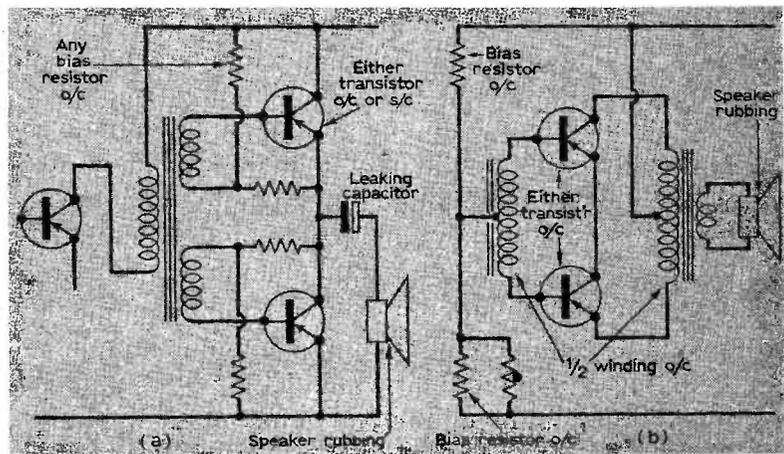


Fig. 2: Faults associated with the two commonest output stages.

Wharfedale Unit 3 build-it-yourself high fidelity loudspeaker kit



A big success right from the word 'Go', the Wharfedale Unit 3 kit gives you a genuine hi-fi speaker system at a very low cost. Thousands of satisfied buyers will confirm how simple it is to build: assembly instructions are easy to follow, and include plans of two different cabinets.

Each kit contains:

- 8" Speaker covering the bass and middle ranges.
- Wharfedale tweeter with Cellulose Acetate Butyrate dome and plastic diffuser.
- Electrical cross-over unit.
- Acoustic wadding, wiring etc.

The bookshelf speaker you can build yourself

The Unit 3 kit can be built into two cabinet sizes: in the smaller cabinet the system gives faithful reproduction of all musical sounds from 65—17,000 Hz; in the larger cabinet the range is increased from 40—17,000 Hz. Power handling capacity 15 watts; impedance 4—8 ohms.

Recommended retail price, including purchase tax, only £10:19:6. Write for detailed leaflet, or see your dealer to-day.



RANK WHARFEDALE LIMITED, IDLE, BRADFORD, YORKSHIRE



BRAND NEW FULLY GUARANTEED TRANSISTORS & DEVICES

1N4001	2/1	2N4292	3/1	2N51	19/4	CRS130	8/1	D49	3/1
1N4002	2/3	2N4292	3/1	2N51	19/4	CRS135	8/1	D410	2/1
1N4003	2/6	40361	12/1	2N51	19/4	CRS140	9/6	D470	2/1
1N4004	3/1	40362	13/6	2N51	19/4	CRS105	6/1	D470	2/1
1N4005	3/1	23001	10/1	2N51	19/4	CRS120	6/1	D470	2/1
1N4006	4/1	25002	10/6	2N51	19/4	CRS230	7/6	D473	2/1
1N4007	1/6	25003	9/6	2N51	19/4	CRS330	8/6	D474	2/1
1N4148	1/9	25005	15/1	2N51	19/4	CRS340	18/1	D475	2/1
1N4785	10/1	25012	25/1	2N51	19/4	CRS400/40	29/6	DA81	2/1
2G210	12/6	25012A	22/6	2N51	19/4	CRS1025AF	7/1	DA85	2/6
2G240	49/6	25013	20/1	2N51	19/4	CRS25/025	15/1	DA86	4/1
2G301	4/1	25013A	25/1	2N51	19/4	DD006	3/9	DA91	1/6
2G303	4/6	25017	15/1	2N51	19/4	DD058	6/1	DA93	2/1
2G303	5/1	25018	17/6	2N51	19/4	DD190	12/6	DA200	1/9
2G308	7/6	25020	50/1	2N51	19/4	DD226A	7/6	DA202	2/1
2G308	7/6	25024	50/1	2N51	19/4	DD262A	3/9	DA210	6/1
2G309	6/1	25025	60/1	2N51	19/4	DK110	1/6	DA211	9/6
2G339A	3/1	25026	100/1	2N51	19/4	DT3200	7/6	DAZ200	11/1
2G371	4/6	25027	12/6	2N51	19/4	GET105	5/1	DAZ201	10/6
2G374	5/6	25036	25/6	2N51	19/4	FST2/0	3/6	DAZ202	10/6
2G381	5/1	25102	10/1	2N51	19/4	FST3/1	3/1	DAZ203	8/6
2G382	6/1	25103	12/6	2N51	19/4	FST3/1	3/1	DAZ204	8/6
2G378A	4/6	25104	12/6	2N51	19/4	FST3/1	4/1	DAZ205	8/6
2G383	5/1	25131	7/6	2N51	19/4	FST3/8	6/1	DAZ206	8/6
2G304	4/6	25301	6/1	2N51	19/4	FST305 AF	3/6	DAZ207	8/6
2G405	5/1	25302	7/6	2N51	19/4	GET102	6/1	DAZ208	6/6
2N454	15/1	25303	10/1	2N51	19/4	GET103	4/6	DAZ209	6/6
2N458	20/1	25305	15/1	2N51	19/4	GET105	8/6	DAZ210	6/6
2N503	9/6	25320	9/1	2N51	19/4	GET106	10/1	DAZ211	6/6
2N599	12/6	25321	9/1	2N51	19/4	GET110	5/1	DAZ212	6/6
2N601	3/6	25322	10/1	2N51	19/4	GET111	4/1	DAZ213	6/6
2N606	4/6	25323	10/1	2N51	19/4	GET112	4/1	DAZ214	6/6
2N607	5/1	25324	10/1	2N51	19/4	GET113	3/1	DAZ215	6/6
2N608	6/1	25325	10/1	2N51	19/4	GET114	4/1	DAZ216	6/6
2N706	1/6	25302	8/6	2N51	19/4	GET115	9/6	DAZ217	6/6
2N706A	2/6	25303	10/1	2N51	19/4	GET116	9/6	DAZ218	6/6
2N707	12/6	25312	9/6	2N51	19/4	GET117	9/6	DAZ219	6/6
2N708	3/1	25701	8/6	2N51	19/4	GET118	6/1	DAZ220	6/6
2N711	7/6	25710	8/6	2N51	19/4	GET119	6/1	DAZ221	6/6
2N711A	7/6	25724	50/1	2N51	19/4	GET120	6/1	DAZ222	6/6
2N721	11/1	25731	8/6	2N51	19/4	GET121	6/1	DAZ223	6/6
2N743	4/1	25732	8/6	2N51	19/4	GET122	6/1	DAZ224	6/6
2N744	4/1	25733	9/6	2N51	19/4	GET123	6/1	DAZ225	6/6
2N753	5/1	25743	50/1	2N51	19/4	GET124	6/1	DAZ226	6/6
2N865	12/6	25801	6/1	2N51	19/4	GET125	6/1	DAZ227	6/6
2N914	4/6	AA129	4/1	2N51	19/4	GET126	6/1	DAZ228	6/6
2N916	4/6	AA178	8/6	2N51	19/4	GET127	6/1	DAZ229	6/6
2N918	7/6	AA179	8/6	2N51	19/4	GET128	6/1	DAZ230	6/6
2N919	4/1	AA172	5/1	2N51	19/4	GET129	6/1	DAZ231	6/6
2N920	5/1	AA212	4/1	2N51	19/4	GET130	6/1	DAZ232	6/6
2N922	8/6	AA213	2/1	2N51	19/4	GET131	6/1	DAZ233	6/6
2N930	7/6	AA217	2/1	2N51	19/4	GET132	6/1	DAZ234	6/6
2N1090	6/1	JAC126	5/1	2N51	19/4	GET133	6/1	DAZ235	6/6
2N1091	4/6	JAC127	5/1	2N51	19/4	GET134	6/1	DAZ236	6/6
2N1131	6/1	AC127Z	12/6	2N51	19/4	GET135	6/1	DAZ237	6/6
2N1132	6/1	AC128	5/1	2N51	19/4	GET136	6/1	DAZ238	6/6
2N1133	4/6	AC153	4/1	2N51	19/4	GET137	6/1	DAZ239	6/6
2N1303	4/6	AC154	3/1	2N51	19/4	GET138	6/1	DAZ240	6/6
2N1304	3/1	AC169	3/1	2N51	19/4	GET139	6/1	DAZ241	6/6
2N1305	3/1	AC176	3/1	2N51	19/4	GET140	6/1	DAZ242	6/6
2N1306	5/1	AC187	3/1	2N51	19/4	GET141	6/1	DAZ243	6/6
2N1307	5/1	AC188	6/1	2N51	19/4	GET142	6/1	DAZ244	6/6
2N1308	8/1	AC189	6/1	2N51	19/4	GET143	6/1	DAZ245	6/6
2N1309	5/1	AC184	4/1	2N51	19/4	GET144	6/1	DAZ246	6/6
2N1420	10/6	AC195	5/1	2N51	19/4	GET145	6/1	DAZ247	6/6
2N1483	9/6	AC199	4/1	2N51	19/4	GET146	6/1	DAZ248	6/6
2N1613	5/1	AC21	4/6	2N51	19/4	GET147	6/1	DAZ249	6/6
2N1614	17/6	AC22	3/6	2N51	19/4	GET148	6/1	DAZ250	6/6
2N1660	15/1	AC23	3/6	2N51	19/4	GET149	6/1	DAZ251	6/6
2N1660	15/1	AC24	3/6	2N51	19/4	GET150	6/1	DAZ252	6/6
2N1660	15/1	AC25	3/6	2N51	19/4	GET151	6/1	DAZ253	6/6
2N1660	15/1	AC26	3/6	2N51	19/4	GET152	6/1	DAZ254	6/6
2N1660	15/1	AC27	3/6	2N51	19/4	GET153	6/1	DAZ255	6/6
2N1660	15/1	AC28	3/6	2N51	19/4	GET154	6/1	DAZ256	6/6
2N1660	15/1	AC29	3/6	2N51	19/4	GET155	6/1	DAZ257	6/6
2N1660	15/1	AC30	3/6	2N51	19/4	GET156	6/1	DAZ258	6/6
2N1660	15/1	AC31	3/6	2N51	19/4	GET157	6/1	DAZ259	6/6
2N1660	15/1	AC32	3/6	2N51	19/4	GET158	6/1	DAZ260	6/6
2N1660	15/1	AC33	3/6	2N51	19/4	GET159	6/1	DAZ261	6/6
2N1660	15/1	AC34	3/6	2N51	19/4	GET160	6/1	DAZ262	6/6
2N1660	15/1	AC35	3/6	2N51	19/4	GET161	6/1	DAZ263	6/6
2N1660	15/1	AC36	3/6	2N51	19/4	GET162	6/1	DAZ264	6/6
2N1660	15/1	AC37	3/6	2N51	19/4	GET163	6/1	DAZ265	6/6
2N1660	15/1	AC38	3/6	2N51	19/4	GET164	6/1	DAZ266	6/6
2N1660	15/1	AC39	3/6	2N51	19/4	GET165	6/1	DAZ267	6/6
2N1660	15/1	AC40	3/6	2N51	19/4	GET166	6/1	DAZ268	6/6
2N1660	15/1	AD140	11/1	2N51	19/4	GET167	6/1	DAZ269	6/6
2N1660	15/1	AD149	12/6	2N51	19/4	GET168	6/1	DAZ270	6/6
2N1660	15/1	AD161	7/6	2N51	19/4	GET169	6/1	DAZ271	6/6
2N1660	15/1	AD162	7/6	2N51	19/4	GET170	6/1	DAZ272	6/6
2N1660	15/1	AD163	7/6	2N51	19/4	GET171	6/1	DAZ273	6/6
2N1660	15/1	AD164	7/6	2N51	19/4	GET172	6/1	DAZ274	6/6
2N1660	15/1	AD165	7/6	2N51	19/4	GET173	6/1	DAZ275	6/6
2N1660	15/1	AD166	7/6	2N51	19/4	GET174	6/1	DAZ276	6/6
2N1660	15/1	AD167	7/6	2N51	19/4	GET175	6/1	DAZ277	6/6
2N1660	15/1	AD168	7/6	2N51	19/4	GET176	6/1	DAZ278	6/6
2N1660	15/1	AD169	7/6	2N51	19/4	GET177	6/1	DAZ279	6/6
2N1660	15/1	AD170	7/6	2N51	19/4	GET178	6/1	DAZ280	6/6
2N1660	15/1	AD171	7/6	2N51	19/4	GET179	6/1	DAZ281	6/6
2N1660	15/1	AD172	7/6	2N51	19/4	GET180	6/1	DAZ282	6/6
2N1660	15/1	AD173	7/6	2N51	19/4	GET181	6/1	DAZ283	6/6
2N1660	15/1	AD174	7/6	2N51	19/4	GET182	6/1	DAZ284	6/6
2N1660	15/1	AD175	7/6	2N51	19/4	GET183	6/1	DAZ285	6/6
2N1660	15/1	AD176	7/6	2N51	19/4	GET184	6/1	DAZ286	6/6
2N1660	15/1	AD177	7/6	2N51	19/4	GET185	6/1	DAZ287	6/6
2N1660	15/1	AD178	7/6	2N51	19/4	GET186	6/1	DAZ288	6/6
2N1660	15/1	AD179	7/6	2N51	19/4	GET187	6/1	DAZ289	6/6
2N1660	15/1	AD180	7/6	2N51	19/4	GET188	6/1	DAZ290	6/6
2N1660	15/1	AD181	7/6	2N51	19/4	GET189	6/1	DAZ291	6/6
2N1660	15/1	AD182	7/6	2N51	19/4	GET190	6/1	DAZ292	6/6
2N1660	15/1	AD183	7/6	2N51	19/4	GET191	6/1	DAZ293	6/6
2N1660	15/1	AD184	7/6	2N51	19/4	GET192	6/1	DAZ294	6/6
2N1660	15/1	AD185	7/6	2N51	19/4	GET193	6/1	DAZ295	6/6
2N1660	15/1	AD186	7/6	2N51	19/4	GET194	6/1	DAZ296	6/6
2N1660	15/1	AD187	7/6	2N51	19/4	GET195	6/1	DAZ297	6/6
2N1660	15/1	AD188	7/6	2N51	19/4	GET196	6/1	DAZ298	6/6
2N1660	15/1	AD189	7/6	2N51	19/4	GET197	6/1	DAZ299	6/6
2N1660	15/1	AD190	7/6	2N51	19/4	GET198	6/1	DAZ300	6/6
2N1660	15/1	AD191	7/6	2N51	19/4	GET199	6/1	DAZ301	6/6
2N1660	15/1	AD192	7/6	2N51	19/4	GET200	6/1	DAZ302	6/6
2N1660	15/1	AD193	7/6	2N51	19/4	GET201	6/1	DAZ303	6/6
2N1660	15/1	AD194	7/6	2N51	19/4	GET202	6/1	DAZ304	6/6
2N1660	15/1	AD195	7/6	2N51	19/4	GET203	6/1	DAZ305	6/6
2N1660	15/1	AD196	7/6	2N51	19/4	GET204	6/1	DAZ306	6/6
2N1660	15/1	AD197	7/6	2N51	19/4	GET205	6/1	DAZ307	6/6
2N1660	15/1	AD198	7/6	2N51	19/4	GET206	6/1	DAZ308	6/6
2N1660	15/1	AD199	7/6	2N51	19/4	GET207	6/1	DAZ309	6/6
2N1660	15/1	AD200	7/6	2N51	19/4	GET208	6/1	DAZ310	6/6
2N1660	15/1	AD201	7/6	2N51	19/4	GET209	6/1	DAZ311	6/6
2N1660	15/1	AD202	7/6	2N51	19/4	GET210	6		

or if the type is not listed, then fit anything which is in the same class (mixer, r.f., a.f. or output). Unlike valves, transistors have a high degree of compatibility and in the field of the cheap portable radio, any minor differences in performance are unimportant, it might even be better than the original! Certainly it is uneconomic to spend time trying to chase exact equivalents even if there are such. The output stage is the only one where some thought may have to be exercised in choosing a replacement, and alteration of the base forward bias may be required. After replacing such, check for distortion and that the quiescent current is reasonable for the type of set.

This brings us to perhaps the most troublesome and frustrating fault to locate, print faults. These may be dry joints between print and components or hair-line cracks in the print itself.

Bending and flexing the panel will often make the fault come and go although not necessarily indicate where it is. Gentle prodding around will sometimes bring it to light, but not always. Another way of tackling the trouble is to take a voltage reading around the suspected area, then flex the panel to see if there is any change in value. This can be repeated at various points, and any change discovered followed up through connecting print and components.

DISTORTION

Another very common complaint is distortion. In by far the majority of cases, the trouble is in the output circuit, so diagnosis should not take so long as with some other faults. First of all though, check the battery voltage. Even if it is claimed to be a new battery, it could have been left switched on when not in use, not an uncommon occurrence.

The usual source of trouble is failure of one half of the push-pull output pair. If the series configuration is used, take voltage readings to find if the collector of the bottom transistor and the emitter of the top one are about half of the battery voltage. If this mid-point is in fact either higher or lower by any marked extent from the half value, most likely one of the transistors is either open-circuit or partially so, or has a high leakage, depending on whether the voltage is high or low and which transistor is defective. The quickest and cheapest course is to replace both transistors. Before doing so though, just check the base-bias resistors, and take another measurement with the speaker disconnected. The capacitor feeding the speaker may be leaky and cause an abnormal voltage reading, disconnecting the speaker will remove the leakage return path and restore correct voltage if this is the cause of the trouble.

If the output stage is of the normal transformer push-pull type, voltage readings will not be a great help. Defective transistors will not have a great effect on voltage because of the low series impedances. Voltages should be measured of course, to make sure that bias is present and the output transformer windings are continuous. If these are in order, the quickest way of checking the transistors is to short the base to emitter of each in turn with a screw-driver blade. When both transistors are working correctly, the result will be distortion and a drop in volume. Shorting a defective one will have little or no effect, while shorting its companion will stop the set working completely or nearly so.

Thus the faulty transistor can be quickly located

and replaced. Discretion can be used as to whether it is deemed necessary to replace the other as well. If only one is replaced, then the replacement should be of the same type.

A frequent cause of distortion is the loudspeaker. Trouble is due to the speech coil rubbing the pole pieces of the magnet. This is not always easy to identify as it can sound very much like distortion originating in the output stage. It is usually worse at low volume settings, because the rubbing tends to be masked at higher volumes. Often it can be felt by gently pushing the cone in and out with the finger tips, but this is not always decisive. Hooking up another speaker is the best test. Impedance is not too critical, a 3-ohm can be used in place of an 8-ohm for testing, but a series resistor should be used in a 30-ohm circuit. A 15-ohm speaker is very useful for bench testing if one can be acquired, as it can be used with almost any circuit.

Distortion can be traced to other causes than the output circuit. The driver stage can be responsible and even the pre-detector stages. These however are rarer and will have to be tackled by voltage measurements and other conventional servicing techniques.

TO BE CONTINUED

I.G. OF THE MONTH

—continued from page 758

★ components list

Resistors

R1	820 Ω	R7	15k Ω
R2	390 Ω	R8	10k Ω
R3	8.2k Ω	R9	100 Ω
R4	8.2k Ω	R10	180 Ω
R5	1k Ω	R11	27k Ω
R6	680 Ω		

All resistors, ½ watt, 10% types

VR1 5k Ω pot. with switch

VR2 100 Ω preset pot.

Capacitors

C1	0.1 μF	C8	0.05 μF
C2	0.05 μF	C9	0.22 μF
C3	0.05 μF	C10	0.001 μF
C4	0.22 μF	C11	0.001 μF
C5	10 μF 6V	C12	320 μF 12V
C6	0.05 μF	C13	32 μF 12V
C7	200 μF 12V		

VC1, VC2 208pF + 176pF ganged tuning capacitor.

TC1, TC2 trimmer capacitors associated with above

Semiconductors

TAD100 Integrated circuit

Tr12 AC127

Tr13 AC128


Miscellaneous

L1, L2, medium aerial on ferrite rod suitable for 208pF tuning with secondary; T1, oscillator coil Weyrad type P50/1AC; I.F. filter type LP 1175; TH1, VA1077; Loudspeaker 15 Ω type.

The sensitivity of the receiver is very good giving a performance comparable to an equivalent eight transistor quality receiver using conventional discrete components. In addition the TAD100 integrates the major portion of the set providing a far more reliable and rugged receiver. ■

the CHELMER SIX

R. L. GRAPER

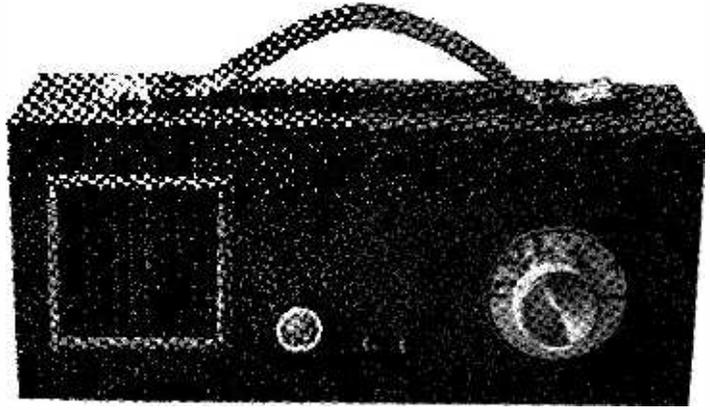

THE author's first attempts at transistor set construction were not very successful, mainly through being too ambitious with miniaturisation. The sets made were mixtures of reflex circuits, employing home wound ferrite aerials with feed-back windings, but they could not be relied upon for stability, and reproduction quality was far removed from that easily obtainable with a modern superhet which may be built for little extra cost.

The author decided to adhere strictly to the superhet circuitry recommended by Weyrad and Mullard, which has stood the tests of time and reliability. There are a few slight deviations from some components used due to lack of availability of the original items, but the performance of the substitutes is well up to standard. The chassis design, and layout of the components was, however, arranged by the author to give a really robust set, yet one which could be removed from its cabinet in a few seconds.

In fact the "Chelmer Six" is one hole fixing in its cabinet, the only control needing attachment being the tuning knob. To achieve this simplicity the speaker is mounted on the chassis, and the volume control and switch are mounted on two brass studding pedestals. No fixing screws are necessary, as four turnbuttons inside the cabinet press the chassis panel firmly against the front panel of its cabinet.

The circuit

The full circuit is shown in Fig. 1. The signal received in the ferrite aerial is tuned by VC1, the aerial section of the ganged capacitor. The signal is then fed into the mixer/oscillator Tr1 via the small coupling coil on the aerial. The signal, now at i.f., passes on to two stages of i.f. amplification. The amplified signal is then fed by the third i.f. transformer to the detector diode, D1, where the audio signal is extracted.

This signal is tapped off by the 5kΩ potentiometer VR1, the volume control. The signal passes on to Tr4, the driver stage, and on to the phase-splitting driver transformer T2. The push-pull amplifier consists of Tr5 and Tr6. The much amplified signal is then fed to the loudspeaker via the output transformer T2. There is, of course, an a.g.c. system, R5 and C3, which controls the bias of Tr2.

One detail that must be explained is a series resistance of 100Ω, R21. This allows a faint signal to be received immediately the set is switched on, thus acting as a safety precaution to prevent one unwittingly leaving the set on when not in use.

Construction

The main component board drilling plan is shown



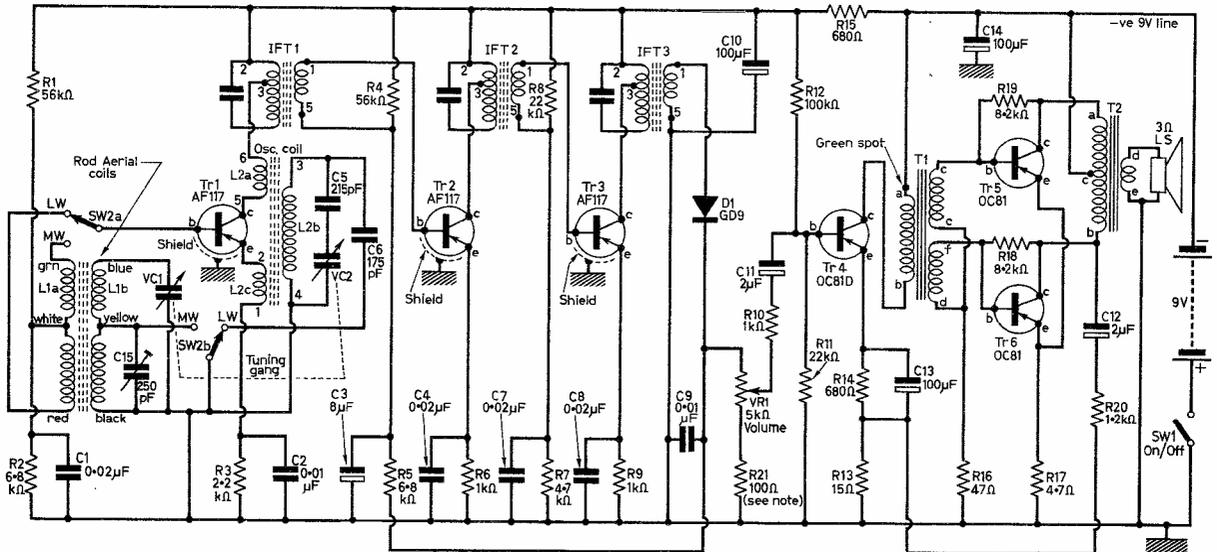



Fig. 1: The complete circuit of the six transistor two waveband Chelmer Six.

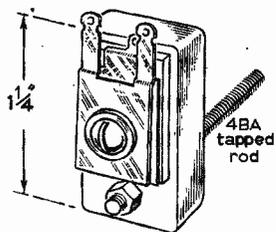

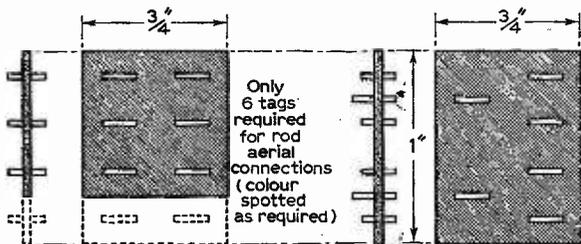This padder can be omitted if the correct value of 175pF is available. Difficulty was experienced in obtaining this exact value so a 250pF variable was used, but adjustment of long-wave section was found to be very tricky.



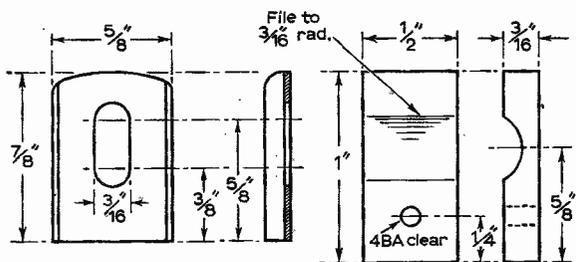Main panel drilled for tags which project through



Material: Perspex

Chassis rear feet 2 off, from brass curtain rail

Also required: 6 pieces of 4BA tapped rod, each 2 1/2 long and 36 4BA nuts

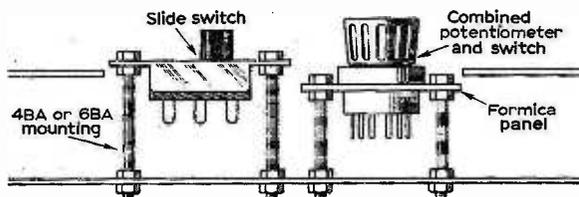


Fig. 4: Details of the sub panels, control mountings, chassis feet and l.w. trimmer capacitor support. Tag panel A is shown on the left, panel B on the right.

The author drilled lots of small holes at random all over the panel, which may be found useful if the constructor finds that an odd wire needs to be passed through the panel. This drilling should, of course, be done before actually mounting the components on to the panel.

Wiring

With the circuit diagram Fig. 1 and the wiring plan Fig. 6 to refer to, the constructor should find no difficulty as there is plenty of space available. The author prefers the method of laying resistors and capacitors flat on or near to the panel, rather than the more conventional method of mounting these components vertically. Make sure that all the electrolytic capacitors are correctly connected for polarity. It is best to solder the transistors on last, the triangular arrays of screws on tag panel B being provided to allow all other components to be put into position and wiring completed first. Colour spot

marking beside these pins is useful to avoid mistakes when the transistors are soldered on finally. The spot marks should be put on both sides of the panel.

Care is needed when soldering to the i.f. transformer and oscillator coil pins, which should be gripped with a pair of thin nosed pliers to form a heat-sink.

The potentiometer with its incorporated switch is a little tricky to wire up and colour coding beside the small tags might be an idea to avoid mistakes. Note also the colour coded and numbered tags on panel A (Fig. 4) which tie up on the circuit with the leads taken from the ferrite rod aerial.

A little extra spacing is needed, incidentally, at each side of the tuning capacitor to avoid the grub screws of the extension spindle, these project slightly, and free rotation of the control is essential.

Fig. 6 gives an idea of the length of the various wires required. Wires not connected are shown crossing, and only where a black dot is shown are the wires soldered together.

The Weyrad transformer LFDT3 has a split secondary, and there is a correct way of wiring it so the author advises the reader to study the Weyrad literature before connecting it. The colour code spot denotes the start of the primary.

Alignment

A signal generator is, of course, the ideal instrument to use for alignment, but an alternative procedure is feasible, and will be described.

1. Switch the set to m.w.
2. Set the aerial and oscillator trimmers to mid-point.
3. Use tuning scale to set tuning capacitor to correct position for the local station.
4. Adjust the oscillator coil core to bring this station in at the correct point on the tuning scale.
5. Tune to a weak signal anywhere in the band, preferably one not subject to fading, and adjust the i.f. transformer cores for maximum output. This will ensure that the i.f.s. are peaked for maximum gain.
6. Tune to the high frequency end of the band and adjust the oscillator trimmer to bring the station in line with the scale calibration.
7. Tune to other end of band and adjust the medium wave coil on the ferrite rod for maximum gain.
8. Repeat steps 5 and 6 until adjustment of one end has no effect on the other.
9. Switch the set to l.w.
10. Tune in Radio 2 on 1500m. and adjust l.w. aerial winding for maximum volume.
11. Trim C15 to obtain maximum volume of Radio 2.

Use the correct trimming tool; a thin brass strip mounted in an insulating handle. The brass strip should pass right through the full length of the slot in the iron cores of the transformers and oscillator coil. Do not use an ordinary screwdriver for these adjustments or the lugs will break up and jam in the thread.

The scale used is that issued by Weyrad for use in conjunction with their rod aerial RA2W. Unless the set is incorporated in its cabinet, on to which the scale is glued, the alignment adjustments will have to be delayed until the cabinet is completed.


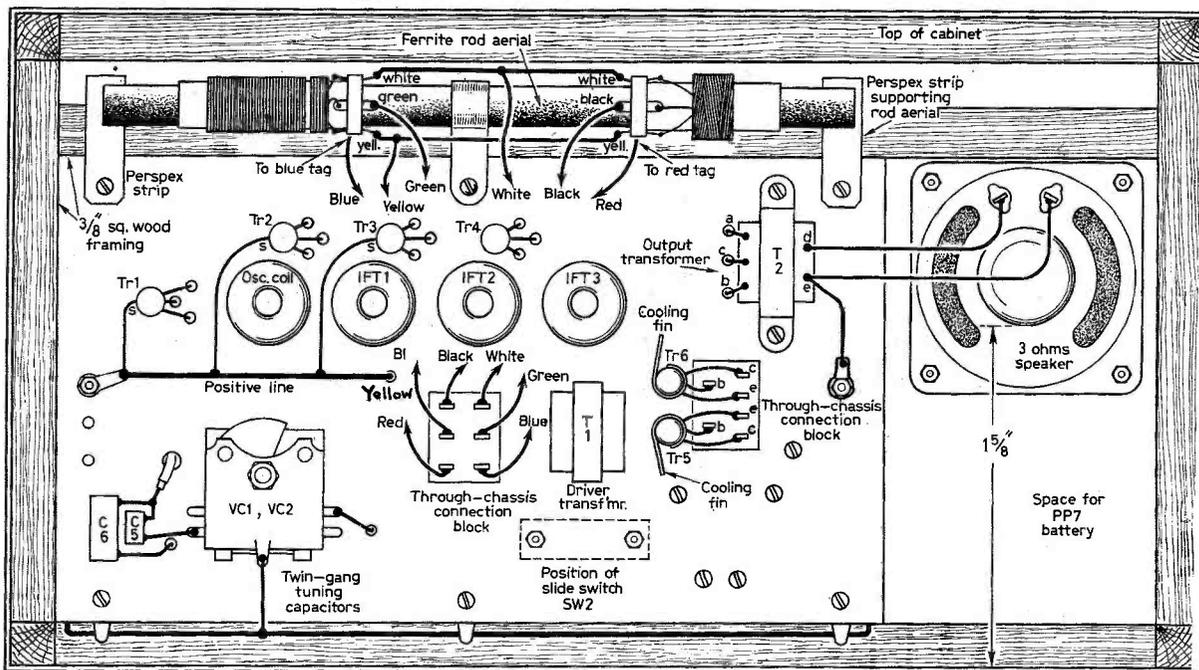


Fig. 5: (above) The component layout viewed from the rear of the case, the drilling plan is shown in Fig. 2.

Fig. 6: (below) The main wiring diagram.

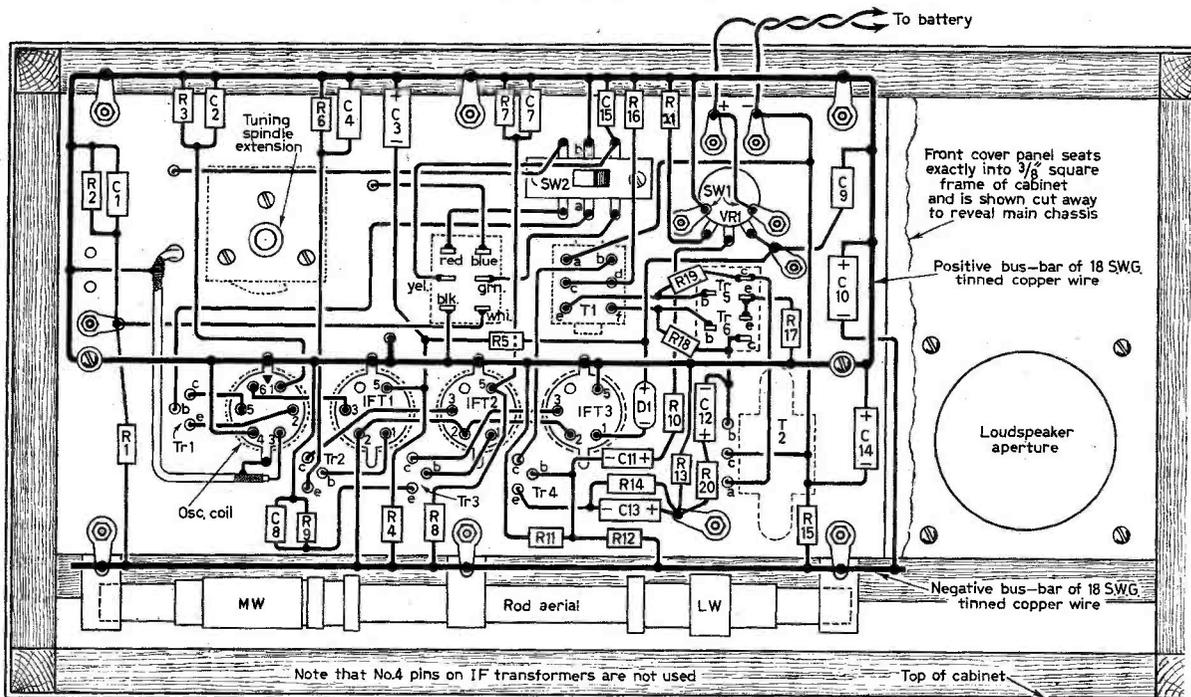

The cabinet

The author has always favoured plastic laminate material, such as Formica, for radio cabinets. The material is light and very strong, so that when built on a light section wood frame it cannot warp. Further it can be obtained in many attractive colours.

When the panels are cut out they should be fastened together with adhesive tape and trimmed up to make exact pairs. Unbind and bevel all the edges at 45°, which makes a neat cabinet with flush edges. On the front panel a frame of 3/8 in square stripwood is next glued, spaced from the edges to a distance equal to the thickness of the material. The frame thus formed need not be

★ components list

Resistors

R1 56k Ω	R12 100k Ω
R2 6.8k Ω	R13 15 Ω
R3 2.2k Ω	R14 680 Ω
R4 56k Ω	R15 680 Ω
R5 6.8k Ω	R16 47 Ω
R6 1k Ω	R17 4.7 Ω
R7 4.7k Ω	R18 8.2k Ω
R8 22k Ω	R19 8.2k Ω
R9 1k Ω	R20 1.2k Ω
R10 1k Ω	R21 100 Ω
R11 22k Ω	

All resistors $\frac{1}{4}$ watt, 10% tolerance
VR1 5 k Ω log. potentiometer with switch

Capacitors

C1 0.02 μ F	C9 0.01 μ F
C2 0.01 μ F	C10 100 μ F, 12V
C3 8 μ F, 12V	C11 2 μ F, 12V
C4 0.02 μ F	C12 2 μ F, 12V
C5 215pF, 2% ceramic	C13 100 μ F, 12V
C6 175pF, 2% ceramic	C14 100 μ F, 12V
C7 0.02 μ F	C15 250pF trimmer
C8 0.02 μ F	

VC1, VC2 208+176pF tuning capacitor. Jackson type "00".

Inductors

L1 Ferrite rod aerial, 6in. x $\frac{7}{8}$ in., Weyrad RA2W
L2 Weyrad P50/1AC oscillator coil (red spot)
IFT1, 1FT2 Weyrad i.f. transformers type P50/2CC (white spot)
1FT3 Weyrad i.f. transformer type P50/3CC (blue spot)
T1 Driver transformer. Weyrad LFDT3 or Radiospares T/T1
T2 Output transformer. Radiospares T/T2

Semiconductors

Tr1 AF117	Tr5 OC81	} matched pair
Tr2 AF117	Tr6 OC81	
Tr3 AF117	D1 GD9, OA81, OA91, etc.	
Tr4 OC81D		

Miscellaneous

Loudspeaker 2 $\frac{1}{2}$ in. diameter 3 Ω or 8 Ω , SW2, 2 pole 2 way slide switch; paxolin sheet; 4BA brass studing; battery clips; Formica for case etc.—see text for case materials.

mitred to 45°, but the lengths should be exact and tried out before glueing. The top panel should also be fitted with a $\frac{3}{8}$ in. wood frame but only on rear edge. The end panels and bottom may be left out until after assembly before glueing on the remaining strengthening stripwood pieces.

Before actual assembly of the panels into box form it is best to cut out the large hole for the loudspeaker in the top right hand side of the front panel.

Assembly is quite simple. Treat the outside faces of the $\frac{3}{8}$ in. wood framing with Evostik and after a short drying time bring the panels together to form the box shape. Then cut the lengths of $\frac{3}{8}$ in. stripwood for the sides, and lengths of $\frac{1}{2}$ in. square wood for the battery holder and glue them in individually. Four screw holes only are necessary for the back panel cover which can be countersunk. The best method of getting the correct position for drilling out the clearance holes for capacitor spindles and that for the potentiometer knob is to spot at each centre with Indian ink. The chassis can then be carefully inserted until the spindle and knob touch, leaving a black dot on the panel. The large hole for the potentiometer knob can then be marked with compasses, cut out by means of a fretsaw and piercing saw blade.

The front panel of the chassis should fit neatly inside the frame of the front panel of the cabinet. A piece of speaker fabric can be glued inside, over the speaker aperture to improve the appearance and exclude dust.

The carrying strap was cut from lin. plastic material, and the cross strips from Formica.

The set described has been in use continuously for several months, and yet no maintenance has so far been necessary. ■

PRACTICAL WIRELESS and PRACTICAL TELEVISION

FILM SHOW

Caxton Hall, Caxton Street
London S.W.1

Friday, March 6th, 1970
at 7.30 p.m.

Come and spend an interesting evening (free tea and sandwiches), which will include a colour film entitled SOMETHING BIG IN MICRO-CIRCUITS. Ian Nicholson of Mullard Ltd., will be the principal speaker. W. N. Stevens, Editor, Practical Wireless and Practical Television will be in the chair.

A vacancy exists on the editorial staff of

PRACTICAL WIRELESS

Required to prepare articles from authors copy through to final printing. Knowledge of modern electronics and editorial procedure essential. Applicants are invited to write to the Managing Editor, Practical Wireless, Tower House, Southampton St., London W.C.2. giving full details.

REPAIRING LOUDSPEAKER CONES

H.C. BENNET-CLARK, B.Sc., Ph.D.

I WAS recently asked for advice about an old 12in. loudspeaker that had suffered from the attentions of house-proud mice. The mice had succeeded in removing most of the cone but the voice coil, leads and inner cone support were intact. (Fig. 1.)

I suggested that the unit should be returned to the makers for re-coning, but the owner was horrified to learn that this would cost at least £2 and probably £4. He bought a new low-cost 12in. unit for 32s. and presented me with the relics of a first-class loudspeaker.

This presented such a challenge that I decided to try to make an entirely new cone, incorporating some ideas I have had on this subject.

A BIT OF THEORY

The problem is that the cone should be as light and rigid as possible and also be very free to move. Some of the best loudspeakers use expanded plastic foam diaphragms, constrained by a soft plastic roll surround that is very free of distortion and coloration over a band from maybe 40Hz to 2kHz, but a tweeter is also needed.

Alternatively, a soft corrugated paper cone can produce sound over the whole audio band, but this is achieved because the cone does not vibrate as a whole at the highest frequencies; only the centre moves and h.f. radiation may be improved by fitting a small inner cone to the voice coil. This type of speaker generally gives a rather poorer performance than is realised with separate l.f. and h.f. units.

In production, the cones for both types of speaker are stamped or cast in a mould. Obviously, it is unrealistic to try to make a mould for a single loudspeaker and the amateur must try to build cones in a different manner, not losing sight of the need for lightness, strength, and a flexible surround.

There must be thousands of old loudspeaker units lying around unused because the cones are damaged. Any of these is a suitable subject for restoration and the methods suggested should make a unit with a very good performance.

MAKING THE OUTER CONE

The first thing with any unit is to remove most of the old cone; this may sound drastic, but it makes things far easier. Remove the paper or felt gasket from the chassis and remove the old cone surround from the chassis. Trim the cone to leave a rim about $\frac{1}{4}$ in. wide around the coil former and leave a support for the voice coil leads. (Fig. 2.) You must be very careful of the voice coil leads; if you wreck them it is very difficult to save the speaker.

The outer cone is made from a sheet of thin good quality paper. I used tracing paper, but good lightweight drawing paper is also suitable. This must be marked out in such a way as to make a suitable shaped cone. In the case of a 12in. Good-

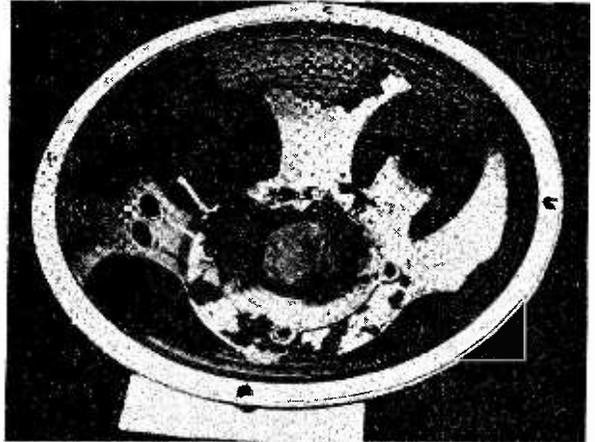


Fig. 1: The 12in. Goodman's loudspeaker attacked by mice. The cone has been destroyed, but the coil assembly is intact.

man's which has a fairly steep cone of about 105° , this can be made from a circle of 6in. radius, with a sector of 90° removed. (Fig. 3.) There are various tips that will assist you in making a suitable paper cone. Do not use the sheet of high quality paper for this experiment—use brown paper.

Draw a circle of 6in. radius and inside that draw concentric circles of radius $5\frac{1}{2}$ in., $5\frac{1}{4}$ in., 5in., and in the middle of $\frac{3}{4}$ in., 1in., $1\frac{1}{4}$ in., $1\frac{1}{2}$ in. radius (as in Fig. 3). Draw in a radius and cut along this, cut around the outside circle and around the innermost circle. This will give you a variable sized cone former, which can be pinned or glued temporarily and offered up to the voice coil.

The aim is to make a template for the final cone. By adjusting the amount of overlap the cone can be made more or less acute and you should aim to make it fit with a gap of about $\frac{1}{4}$ in. all round the


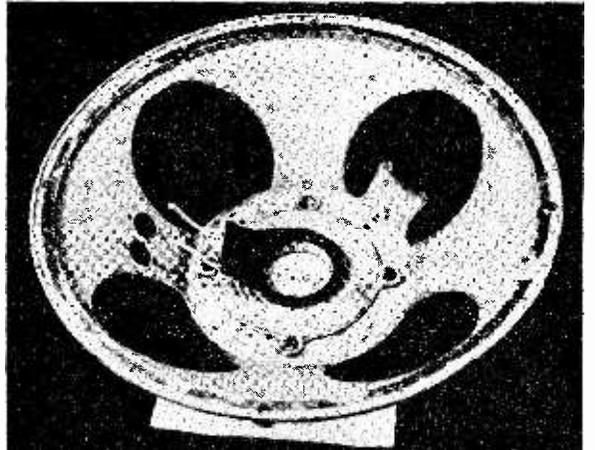


Fig. 2: The cone is trimmed and tidied up. The surround is removed entirely.

Fig. 3: Diagram showing how a sheet of paper should be marked out to make a suitable cone for a 12in. speaker. The detailed dimensions will depend on the speaker, but this will serve as a guide.

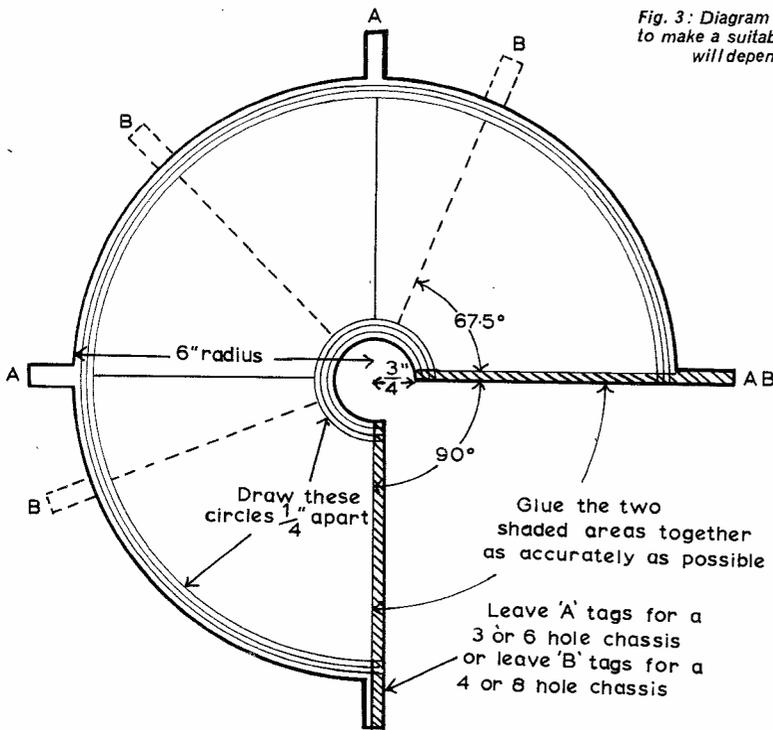

inside of the chassis level with the rim. The outer diameter can be trimmed to size by cutting all round one of the lines that you draw. The inner diameter should be made a snug fit around the outside of the voice coil former, again by trimming all round inside the template, using the lines as a guide. Then mark the template to indicate the degree of overlap required to get the correct angle.

The template for a 12in. Goodman's unit is shown in Fig. 3. Very conveniently, the cone is made by cutting out a 90° sector. The outer radius is about 6in. and the inner radius about 3in. After marking out the circles with compasses, mark out a series of radii as is shown in the diagram: these and the tags "A" and "B" are used later to align the cone in the chassis. I have drawn the cone template so as to suit either a 6-hole chassis or a 4 or 8-hole chassis. If the chassis has 3 or 6 holes, draw in the radii and tags shown as full lines in the diagram. For a 4 or 8-hole chassis, 3 equidistant lines should be drawn, as shown dotted and the tags "B" should be made. Cut out the paper and glue it up using the overlap and the various circles as guides: if you do this, it should be truly conical.

Obviously, if the loudspeaker had a flatter cone, requiring a sector of only 60° to be removed, the "A" radii should be spaced 100° apart or the "B" radii 75° apart.

Now you must attach the paper cone to the existing voice coil. This job must be done perfectly as it is the basis for the final cone. I used balsa wood cement spread pretty thickly on the old cone and then offered up the new paper cone, fitting it, rather like a motor tyre so that the lines drawn around the new cone were concentric with the voice coil. While setting, the cone was held in place by Sellotape between the chassis and the tags on the edge of the cone.

When the glue has set, it is an advantage to fit

an extra layer to the inside or apex of the cone: this inner cone can be about 1in. wide and serves to strengthen the attachment of the new cone to the voice coil.

SUSPENDING THE CONE

The edge suspension should be firm enough to support the coil in the magnet but flexible enough to allow free movement of the cone. Suitable materials for the suspension are chamois leather (expensive), cloth or polyurethane foam. A sheet of foam, 15in. square and 1/8in. thick costs 7d at Woolworths, but be careful to get the thinnest material!

This foam is marked out into a ring of the same outside diameter as the chassis and an inside diameter about 1/2in. smaller than the new cone.

The new cone is temporarily suspended by attaching the tags on

its edge to the chassis. In doing so, ensure that the cone is circular and centred (I found that it was a help to put a disc into the cone to shape it: try a 7in. gramophone record), the chassis holes can be used as guides.

The foam surround is cut into 4, 6 or 8 equal sectors and two opposite sectors are glued to the chassis using Copydex adhesive. The inner edges of these sectors are then glued to the cone. After the glue has set, test that the cone moves freely. Continue thus until a complete surround has been built and replace the gasket strips (Fig. 4).

STRENGTHENING THE CONE

The thin paper cone will be far too flexible for hi-fi purposes. It can be made very much more rigid by reinforcement with expanded polystyrene

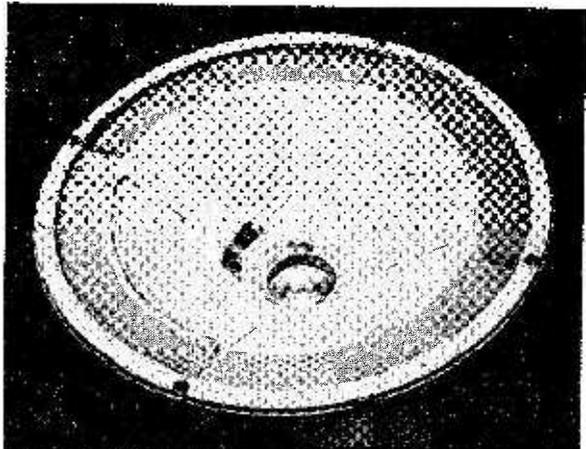


Fig. 4: The thin paper cone is suspended at its edge by polyurethane foam. The centre is reinforced and guide lines help in centring the cone.

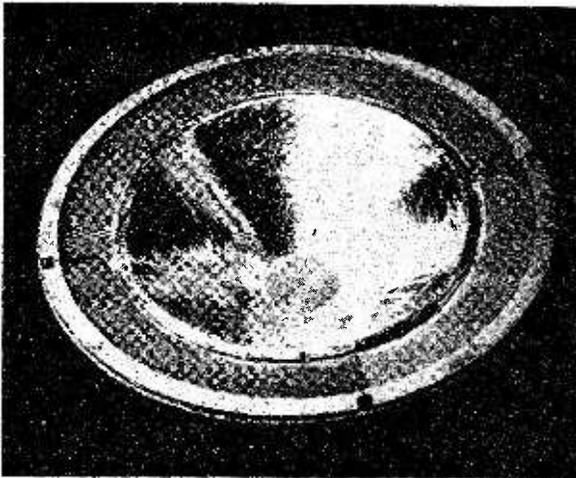


Fig. 5: The finished bass unit. The cone has four layers of polystyrene foam and is finished with aluminium foil.

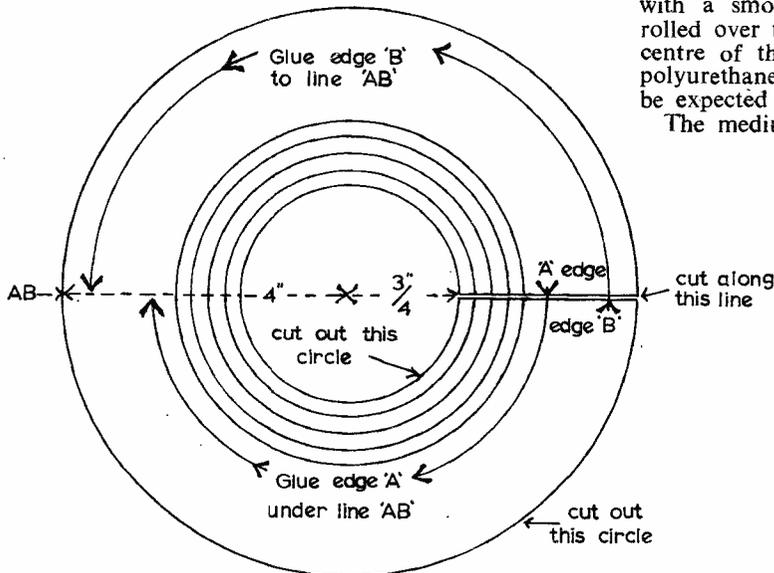


Fig. 6: Diagram showing how a sheet of card should be cut and glued to form a small h.f. radiator for the centre of the large cone.

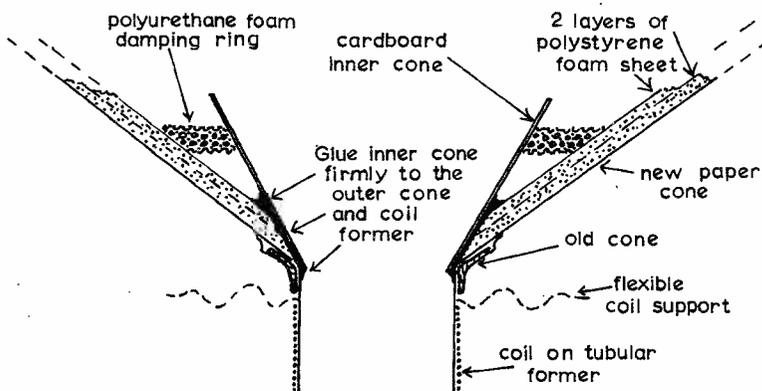


Fig. 7: Diagram showing the fitting of the h.f. radiator cone to the large cone and the siting of a damping ring of polyurethane foam.

foam. The foam can be bought as a roll of household insulation costing about 6s 11d for 33ft. x 3ft. x 2mm. This very light material is cut to the same shape as the cone template (Fig. 3) and divided into three or four sectors. The sectors are then glued around the inside of the thin paper cone. This glueing must be as strong as possible and I suggest you use either Copydex or Britfix balsa cement (many glues dissolve polystyrene—carry out a test).

At this point you must decide whether you want a hi-fi bass unit or a medium quality full range unit. For hi-fi you need a rigid cone, but this will not respond well above 2kHz. For medium quality, the cone may be less rigid but should be fitted with an auxiliary high frequency cone at the centre.

The rigid l.f. cone is made by adding three further layers to the cone. The gaps between the sectors of succeeding layers should be staggered for strength. These layers are glued on with Copydex. The cone is finished off with a layer of aluminium cooking foil, again cut to the template and glued with Copydex. This foil is rolled down on to the cone with a smooth object to ensure adhesion and is rolled over the inside and outside of the cone. The centre of the cone is finished with a dust cap of polyurethane foam (Fig. 5). This speaker should not be expected to perform well above 2kHz.

The medium quality full range version uses only two layers of polystyrene foam and no aluminium skin. It is fitted with a laminated inner cone of 60° angle. This accessory cone is made from a circle of radius 4in. marked out as in Fig. 6. Use thin card, similar to postcard, and mark out a series of guide-rings $\frac{1}{4}$ in. apart; these will help in fitting the cone to the voice coil. Cut along a single radius and fold the two cut edges, one inside and one outside the cone to form the double cone. Glue it carefully all over with Copydex.

As the purpose of this small cone is to radiate directly from the coil, it must be fastened firmly to the polystyrene foam around the apex of the large cone, until the small cone is a snug fit on the large cone and edge of the coil former (see Fig. 7). Then trim the apex of the small cone, using the guide-rings to ensure concentricity, until the cone apex is only slightly smaller than the large cone. Then glue the small cone on to the large cone and coil former with balsa cement.

Practical experience shows that thin cones of this type have undesirable resonances. These can be damped to a great extent by fitting a ring of polyurethane foam between the h.f. cone and the main cone. This should be made of $\frac{1}{4}$ in. thick foam (Woolworths, again cut in a ring of outside radius 2 $\frac{1}{4}$ in. and inside radius 1 $\frac{1}{4}$ in. and fitted over the inner cone as in

★ components list

Materials required	Approximate cost
1 sheet tracing or drawing paper 15in. x 20in.	6d.
1 roll polystyrene foam wall covering 33ft. x 2ft. x 2mm.	6s.11d.*
(You only need about 3ft. of this, so you can scrounge it!)	
1 tube balsa wood cement (Britfix)	1s. 3d.
1 tube Copydex	2s. 6d.
1 sq. ft. of domestic foil (L.F. unit only)	2s. 9d.*
(Give the rest to your wife!)	
8in. square of card 0.015in. thick (Full range unit only)	
1 sheet polyurethane foam 15in. x 15in. x $\frac{1}{8}$ in.	7d. Woolworths.
1 sheet polyurethane foam 6in. x 6in. x $\frac{1}{8}$ in. (Full range unit only)	7d. Woolworths.
	14s. 9d. or 12s. 7d.
* You can restore about ten loudspeakers from these packages!	
Tools	
Pencil, ruler, protractor, pair of compasses and scissors.	

Fig. 7; this is not glued in place. An appropriate circle of foam should be cut and glued inside the inner cone to protect the pole of the magnet from dust.

The main problems are that the new cone may be eccentric or may not be firmly glued to the voice coil. This is very easily tested by feeding the speaker with between 3 and 10 watts of 50Hz signal; for a 3 Ω speaker, 4 to 6 volts; or for a 15 Ω speaker 8 to 12 volts from a transformer will provide this power. The cone should vibrate through about $\frac{1}{8}$ in., but should not set up a scraping noise in the process. If the speaker can stand this usage, it should stand domestic music!

For various purposes, it is useful to find the bass resonant frequency; unfortunately, you will need an a.f. generator and an amplifier for this. Connect an a.c. voltmeter across the loudspeaker and feed from the amplifier via a 15 Ω to 30 Ω resistor. Resonance causes the loudspeaker impedance to rise and thus the voltage across the voice coil rises and the point at which this voltage is maximum is the resonant frequency. Alternatively, the resonance can be seen as a greatly increased amplitude of cone movement. When designing a new enclosure, the resonance is used to assist in tuning the enclosure and so the value should be noted carefully.

If the finished cone causes rubbing on the poles of the magnet, it is a comparatively simple task to re-align it; the site of friction can be observed and the whole cone pulled to and fro to free the coil. After the correct pull has been found, the foam surround can be freed from the cone and re-glued appropriately.

The instructions given here hold for a typical 12in loudspeaker with a pole piece of about 1 $\frac{1}{4}$ in. diameter. For other units, appropriate adjustments to the dimensions will have to be made.

If you do not have a tweeter or crossover unit, the wide range medium fidelity unit can be used without further modification.

For the best results, the l.f. unit is preferred. My speaker responds very smoothly from 50Hz to 1.5kHz, and is flat over this range to \pm about 5dB. The bass resonance is 32Hz. ■

THE MW COLUMN

DURING the winter months there is quite a lot of DX on the medium waves from about 1500 hrs. GMT onwards. Stations reported recently include Taiwan 750 KHz; Bagdad 760; *Radio Irana* Teheran 895 (closes down at 1930 hrs.); Anwhei China on 940; Kermanshah Iran 985; *AIR* Calcutta on 1130; *VOA* Okinawa 1178 (behind Horby Sweden); Kabul Afghanistan 1280; China 1290; Teheran 1325; Kuwait 1345; Ahwaz Iran 1390. The *VOA* station in Malalos in the Philippines on 920 was transferred recently to the Philippines government and is now called the Voice of the Philippines, it has programmes in English and signs off at 1600 hrs. Later in the evening a number of interesting African stations can be heard. Tenerife in the Canaries is usually a prominent signal on 620 KHz. Monrovia in Liberia on 629 is more difficult but has been logged. EAJ103 *Radio Sahara* in El Aioun is on 656; Dakar in Senegal on 764 is generally strong after Sottens closes down; EAK92 Las Palmas Canaries is on 827 mixed with EAJ1 Barcelona: EFJ57 in Tenerife is now on 894 after moving recently from 872; EAJ202 *Radio Villa Cisneros* in Spanish Sahara is on 998; *Radio Atlantico* Las Palmas on 1097 is behind EFE14 Madrid; Conakry Guinea on 1403 is invariably a strong signal with African music after 2300 hrs.; Funchal Madeira 1529 is sometimes audible before close down at 2300 hrs.

A number of European MW stations broadcast special programmes in English for DXers. *Sweden Calling DXers* is on 1178 KHz at 2300 hrs. GMT on Tuesdays, *Radio Portugal* has a DX programme on Mondays on 755 and 1161 at 2300 hrs. and on 1412 at 2315 hrs. Recently, *Deutschlandfunk* on 1268 has started *DX Circle* at 1800 hrs. on alternate Wednesdays. This programme is introduced by Alan Thompson of the World DX Club. *Radio Andorra* 701 KHz now has a nightly programme of pop music and announcements in English starting at midnight GMT. Reports are requested and should go to PO Box 1, Andorra.

The writer is often asked by newcomers how they can find North America on the MWs. At this time of the year, the easiest station to locate is CBA Moncton New Brunswick, an outlet of the *Canadian Broadcasting Corporation* on 1070 KHz. *Paris II* on the same frequency closes down at 2300 hrs. GMT nightly and when the path is open CBA should be audible after the Paris carrier is switched off. If it is not heard by 2330 hrs. then conditions are below average and a further attempt should be made a few days later, conditions do vary. Other stations that have been logged recently between 2300 hrs. and midnight GMT are VOCM on 590 in St. John's, Newfoundland; WOR New York City on 710; WABC also in NYC on 770; WHDH Boston on 850; CJON St. John's Newfoundland on 930; WINS in NYC on 1010; WBAL Baltimore on 1090 and WNEW 1130 in NYC. When conditions are good numerous NA stations can be heard up to 0300 hrs. when interference starts to become troublesome.

CHARLES MOLLOY

home and dry!


F.G.SADLER, G3UZ

THERE is one item that seems to have escaped discovery, and I have never seen in print, and that is "How to buy and get into the shack, unbeknown to the wife, new gear". I have been around this country and abroad visiting other "Hams" at various times and during this period, have picked up quite a few hints and tips on this subject, and for what they are worth I will try to pass them on.

First tip is to get the XYL to pay a visit to her mother and as soon as she is out of the way, go out and buy a new bit of gear. As soon as you arrive home place it on the bench with other equipment, if after a time she happens to spot it, do not worry, you can get away with it in nine cases out of ten, by saying: "Haven't you seen that before dear, it has been laying on the bench for years." I know this can work very well, as, just after the war, I got rid of XYL as described above, and straightaway went down to radio dealer and bought a R1155 receiver. I had to carry it about two miles to my home, but I was so pleased about it all, it seemed to me as light as a feather!

Tip No. 2, again you are thinking about a piece of new gear, first thing to do is to get your best friend, who by the way is also a "Ham", to pay you a visit then after he has been there for about half an hour and just as the XYL is bringing a cup of tea

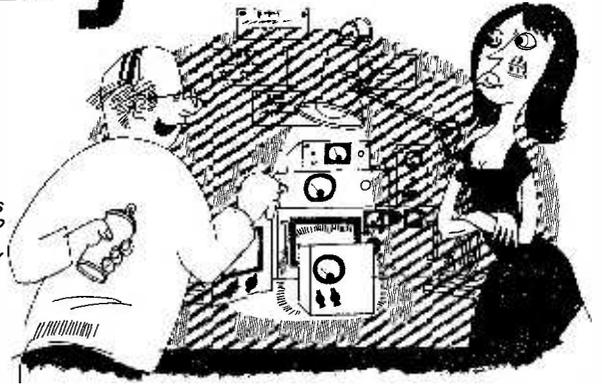"I reckon this paint is wonderful, don't you? Just feel the surface, it's bone dry!"



into shack, let him drop the remark that he has a bit of useless gear at home that he intends to throw out, you up and say (while wife listens) as a great favour to him you will take it off his hands for spare parts.

As soon as XYL is out, bring in gear, place on bench, when she arrives home again, take her in shack, show her gear with the remark, "What a good chap that Fred is to be sure, look dear he has even brought it around". One look at it, and she will reply "Another bit of rubbish, I expect". Alas it is a sad state of affairs that wives think this way but you've got your new piece of gear!


No. 3 tip and best of all, to my way of thinking, was passed to me by a friend who resides in Eire, and this is how it goes.

When you come home from work, and you are having your meal, get your copy of PRACTICAL

WIRELESS out and start to read it. Suddenly you read out to the XYL, an advert., contained therein relating to "So and So quick drying paint". "I must get a tin of that" you say and you do so.

Now you have got your new gear, which you have hidden under cover of bench, so straight to the shack you go, open up the tin of paint, and paint an old cabinet. When this has been done (door and windows have been kept shut whilst doing the job so the smell of the paint cannot get out), put new gear on bench, stick old repainted cabinet under bench, then rush out of shack, to living room where XYL is reading paper and say: "Come and have a look at the job I have just painted." When she gets into the shack the smell of paint is really awful, however, do not let her go back to her newspaper yet. Just say: "I reckon this paint is wonderful, don't you? Just feel that shiny surface dear, it is bone dry." Though she may feel the top of gear, she will not take much notice of it being new as she will want to get away from smell of paint, so once again you have run out as a winner!

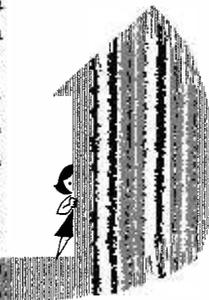If later on, she does happen to see it and asks about it, and where it came from you can always turn around to her and say "Why you little silly billy, that's that bit of old gear I painted up, don't you remember?" Well, Mr. Editor, I have done my best to help other "Hams" in their painful ordeals, and I sincerely trust they have happier times buying their gear.




When smuggling a new piece of gear into the shack, make sure the XYL is not lurking round the corner!

The TWO-FIFTY TRANSMITTER

A S CARPENTER G3TYJ

2-50

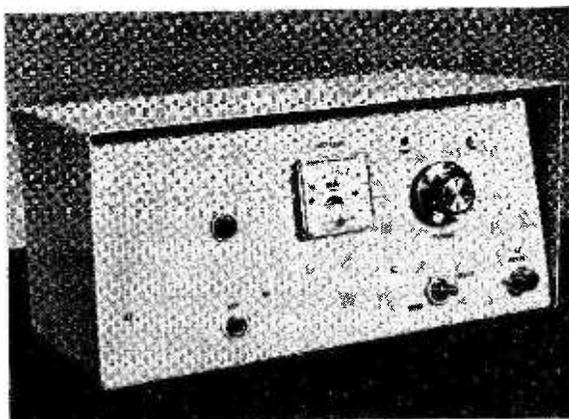

NOW that the 2-metre (144-146MHz) amateur band is usable by GPO-licensed G8 (Class B) call-signs additional to Class A licensees, a reasonably potent v.h.f. transmitter design may be of interest to readers. All parts used in the transmitter are readily obtainable and the total building cost, when every item has to be purchased, is in the region of £10.

When operated in the author's preferred mode, viz. A1 (c.w.) emission the transmitter will run at up to 40W input from a 300V d.c. supply rail voltage and at 25W input from 250V d.c.; running the

transmitter from a h.t. rail voltage lower than 250V is not recommended, except perhaps for preliminary setting-up operations.

Current requirements are 200mA (minimum) plus 3 amps from a 6.3V a.c. source for the heaters and panel warning lamp. A complete power supply unit (PSU) should be provided as an outboard item.

The transmitter keying socket is associated with the penultimate r.f. stage but the final valve is fully protected during "key-up" conditions by fitment of a clamp valve. Provision is also made for type A3 emission (phone) working via an external modulator;

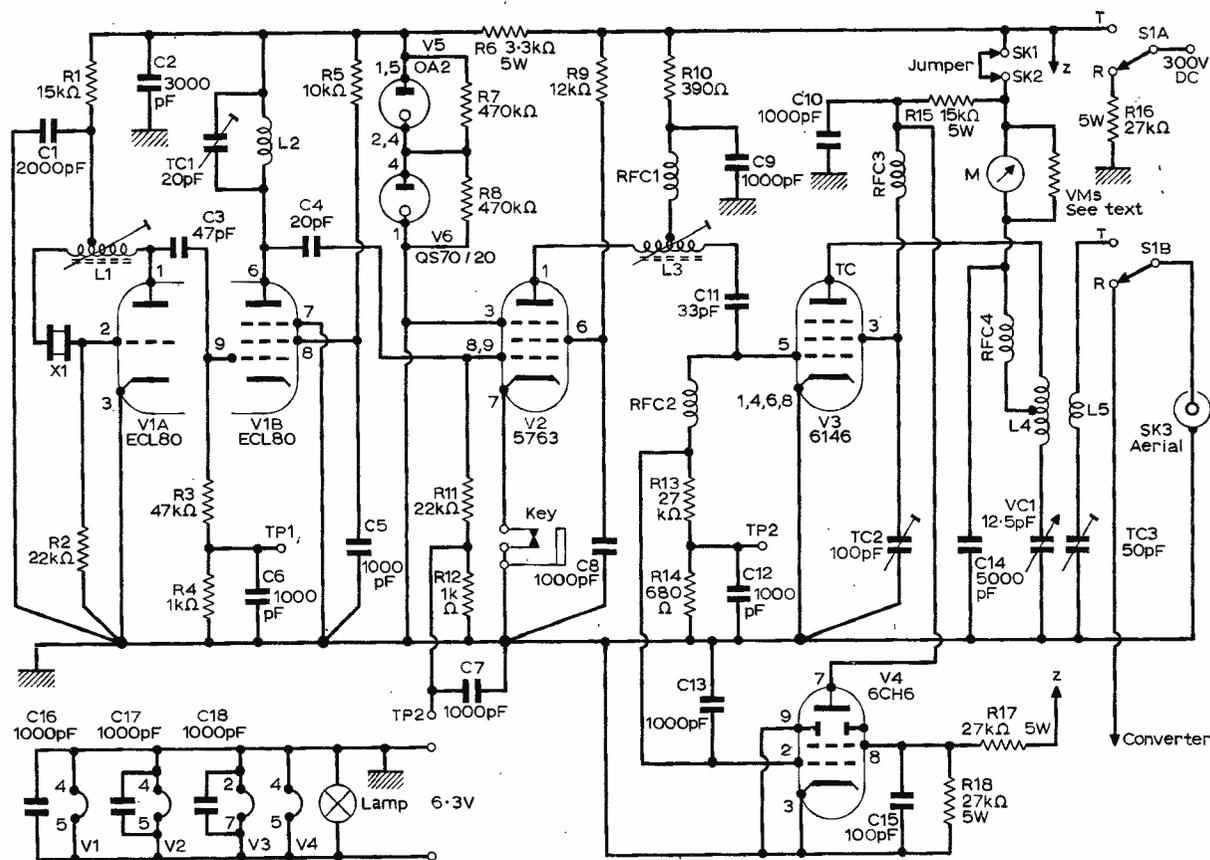


Fig. 1: The complete circuit of the transmitter.

anode and screen modulation requires audio power of some 15W and must be provided by a separate unit. Clamp valve modulation, although not so effective as preferred anode and screen systems, can possibly be used; this does confer simplicity and a suggestion regarding it will be made later.

CIRCUITRY

The complete circuit of the "Two-Fifty" transmitter is given in Fig. 1 where the required final output in the 2-metre band is secured via multiplied oscillations generated initially at a nominal frequency of 8MHz and obtained via a crystal. The crystal oscillator coil L1 in conjunction with the triode section of V1a is tuned to the third crystal harmonic in the 24MHz region; this is injected into the pentode grid circuit of V1b. Output multiplied to 72MHz is available at the pentode anode and is developed across coil L2. The 5763 valve, V2 then doubles the 72MHz input applied to it and signals in the 144MHz band are developed at the pi-tuned anode-grid coil Lc. The PA valve, a 6146, then raises the signals to a suitable level for transmission.

Output is taken from a small link coil, L5, wound centrally within series-tuned coil L4. In the PA stage choke RFC3 and trimmer CT2 are neutralising items whilst the pair of sockets SK1-2 fitted in d.c. supply circuit permit modulation to be applied to both anode and screen from an external unit.

The PA anode meter *M* is useful as a current monitor but for more precise tuning-up an absorption type wavemeter is preferred; meter *M* in the prototype is a 5mA f.s.d. item shunted to read 0-150mA. The shunt value required is 0.2 ohms approximately for the particular movement used and this is made up by winding some fine enamelled copper wire on to a $\frac{1}{8}$ in. former and checking the panel meter to f.s.d. against an external test meter appropriately driven to 150mA.

PA PROTECTION

The drive voltage present at the "earthy" end of choke RFC2 when the transmitter is operating is in connection with the control grid of clamp valve V4, but biasing it to cut-off; V4 is thus normally inoperative. If the voltage developed across R13-14 by drive disappears at any time however, the clamp valve conducts heavily and a large voltage drop occurs across R15 as extra current is drawn; the 6146 valve screen voltage then falls low and the valve is protected. The clamp valve thus immediately offers itself as a keying safety device which can operate in sympathy with the Morse characters keyed. The valve specified for the clamp operation is a 6CH6 but any small output pentode capable of accommodating a current capacity of 40mA or so is suitable.

Keying the transmitter causes h.t. voltage fluctuations thus it is essential to stabilise the supply to V1; series-connected stabiliser valves V5 and V6 enable this to be done satisfactorily. A single OA2 stabiliser valve can be tried but this does reduce the available h.t. potential to V1 to 150V. A type QS70/25 can be used in place of the QS70/20 specified, provided base differences are noted at the wiring-up stage. Series resistor R6 should be so chosen that current taken by the stabiliser valves does not exceed 20mA under any circumstances.

★ components list

Resistors:

R1	15k Ω	R12	1k Ω
R2	22k Ω	R13	27k Ω
R3	47k Ω	R14	680 Ω
R4	1k Ω	R15	15k Ω , 5W
R5	10k Ω	R16	27k Ω , 5W
R6	3.3k Ω , 5W	VM _s	See text
R7	470k Ω	R17	} 27k Ω , 5W
R8	470k Ω	R18	
R9	12k Ω	All $\frac{1}{2}$ W, 20% except	
R10	390 Ω	where stated	
R11	22k Ω		

Valves:

V1	ECL80	V4	6CH6
V2	5763		(or see text)
V3	6146 Brimar	V5	OA2
		V6	QS70/20

Capacitors:

C1	2,000pF ceramic	C13	1,000pF ceramic
C2	3,000pF ceramic	C14	5,000pF
C3	47pF ceramic	C15	1,000pF ceramic
C4	20pF ceramic	C16	1,000pF ceramic
C5	1,000pF ceramic	C17	1,000pF ceramic
C6	1,000pF ceramic	C18	1,000pF ceramic
	(feed through type)	VC1	12.5pF variable
C7	1,000pF ceramic	CT1	20pF air-spaced trimmer
C8	1,000pF ceramic	CT2	100pF trimmer
C9	1,000pF ceramic	CT3	50pF air-spaced trimmer type C801 or similar
C10	1,000pF ceramic		
C11	33pF ceramic		
C12	1,000pF ceramic		
	(feed through type)		

Miscellaneous:

Key socket, self-closing type; Modulation input sockets (2); Coaxial-type aerial socket; DPDT switch; Valveholders (see text), B9A (3), B7G (2), I.O. (1); panel and chassis material; Meter, miniature panel type 0-5mA (see text) or 0-150mA.

SWITCHING

The function switching of the "Two-Fifty" transmitter is simply, if crudely, done by means of S1A-B, one section being used for h.t. purposes and the other for aerial change-over. A more refined method of switching r.f. may be desirable but since the system seems to work to date it is retained. Resistor R16 is fitted as a current "bleeder" during "receive" periods. On/Off switching proper is associated with the external PSU.

LAYOUT AND CONSTRUCTION

Layout of v.h.f. equipment requires care and it is thought that the layout adopted can hardly be improved upon since it affords short, direct wiring. Wiring-up should follow normal v.h.f. practice with a single chassis connecting point being used for each stage; thick connecting wire of solid core—

say 18s.w.g.—is required. Ceramic valveholders must be used for V1, V2 and V3; a metal ring should be associated with the V3 valveholder and tags No. 1, 4, 6 and 8 should be soldered directly to it with short lengths of 18s.w.g. copper wire.

COIL WINDING

All coils are wound by hand and full details are given below:

Coil No.	Frequency MHz	Turns	Wire s.w.g.	Coil former and spacing etc.
L1	24	25	30 enam.	$\frac{3}{8}$ in. dust-cored former, turns close wound, tapped 5 turns from X1 end.
L2	72	4	16 t.c.	$\frac{1}{2}$ in. air-cored, turns spaced wire thickness.
L3	144	$3\frac{1}{2}$	16 t.c.	$\frac{3}{8}$ in. dust-cored former, turns spaced wire thickness, centre tapped.
L4	144	4	16 t.c.	$\frac{3}{8}$ in. air-cored, turns spaced wire thickness $\times 2$. Tapped centrally.
L5	—	1	22 t.c.	$\frac{3}{8}$ in. air-cored, P.V.C. insulated and inserted centrally in L4.

Note: t.c. = tinned copper wire. enam. = enamelled copper wire.

RF chokes RFC1 and RFC2 can be v.h.f. types or some 100 turns of fine enamelled copper wire may be wound on to a $1M\Omega$ resistor. For choke RFC3 40 turns of 36d.s.c. copper wire are close-wound on to a $\frac{1}{2}$ in. diameter air-cored former whilst choke RFC4 consists of 50 turns of 30s.w.g. enamelled copper wire close-wound on to a $1\frac{1}{2}$ in. length of ball-pen barrel approximately $\frac{3}{4}$ in. diameter.

TESTING

Initially the oscillator should be checked with a low h.t. voltage applied and with V2 and the insulated jumper to sockets SK1-2 removed. A test meter set to read 0-10mA connected from TP1 to chassis (chassis +ve meter prod) should indicate when the core of L1 is adjusted; the core is first adjusted for maximum meter indication then rotated to slightly disengage the windings and until the meter reading falls by a small amount. Failure to make this adjustment may result in the oscillator going

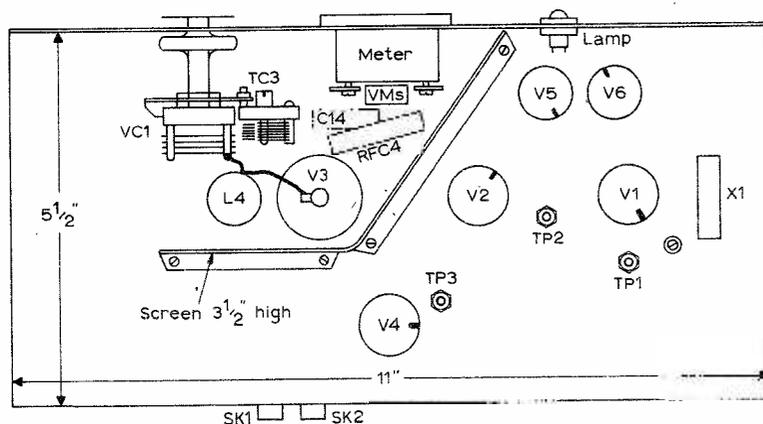


Fig. 2: The above-chassis layout.

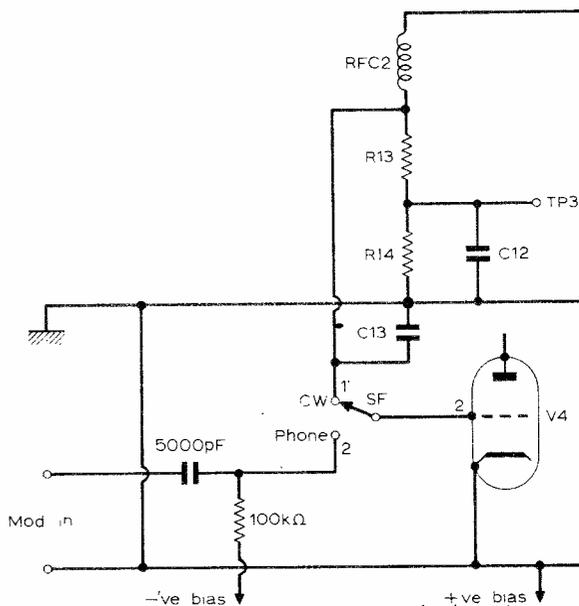


Fig. 3: Suggested modification to permit clamp type modulation.

“dead” when switched on next time. An absorption type wavemeter should now show the circuit to be operative at the crystal frequency $\times 3$, viz. in the 24MHz region. With V2 plugged in, the meter is moved to TP2 and CT1 adjusted for maximum indication after which L2 is checked with a wavemeter for output in the 72MHz region. At TP3 the core of L3 is set for maximum meter indication and a wavemeter check at 144MHz made. If VC1 is now rotated the test meter at TP3 should show little or no change as L4 is tuned through resonance but in practice a sharp downward kick may be observed; when this occurs CT2 needs to be reset and should be adjusted to provide but the smallest change in reading when the test is repeated.

With the function switch S1 set to receive an insulated jumper can be applied to sockets SK1-2, a low-wattage lamp applied to the aerial socket and power applied. The lamp should glow when S1 is moved to “Transmit” and when VC1 is adjusted for lowest panel meter reading—say 100mA.

When the key jack-plug is inserted—or the keying contacts opened—the panel meter reading should fall very low and the lamp should go out. If this does not occur either the clamp valve is not functioning or the 6146 valve has “taken off”; this can be checked by momentarily touching the tapping point of L1 with a screwdriver blade whereupon the lamp should dim and then recover from the disturbance.

The current passing through the stabiliser valves should also be checked; if they remain unlit resistor R6 is too high in value.

—continued on page 781

A PANORAMIC RECEIVER for 160 to 80 METRES

BY D. BOLLEN

PART 2


Last month the theory and circuit of the Panadaptor were given. This month's article deals with the construction.

PANORAMIC RECEIVER CONSTRUCTION

USING Fig. 6 as a guide, drill a $5\frac{1}{2}$ in. \times 7in. s.r.b.p. panel to take the tuning capacitor mounting screws, B9A coil holders, i.f. transformer tags, VR4, C12, the bias battery, and all turret tags. Also, holes to take the aluminium bracket screws and the two wires going to the diode tuner panel. Insert and rivet all turret tags before mounting the above components on the s.r.b.p. panel. Complete coil holder and i.f. transformer wiring using Fig. 6b as a guide, but ignore for the time being all connections to the converter controls and diode tuner panel.

The next stage is to make up the diode tuner panel on either 0.1in. matrix Veroboard, with 21×30 holes and copper strips running parallel to the longest side, or else plain drilled s.r.b.p. or the same matrix with copper wire or Cir-Kit strips on the underside. Insert and wire up diode tuner components as shown in Fig. 7, and take care to observe the correct diode polarities.

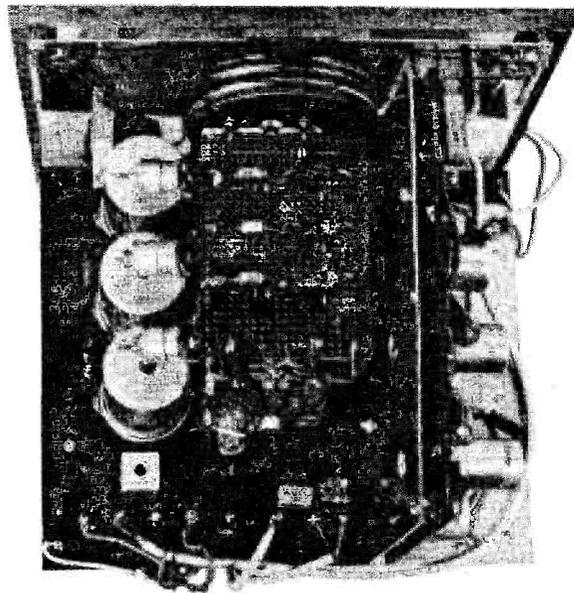Four short 18s.w.g. copper wire legs will serve to mount the diode tuner panel on top of the



Top view of the Panadaptor—compare this with Fig. 6.

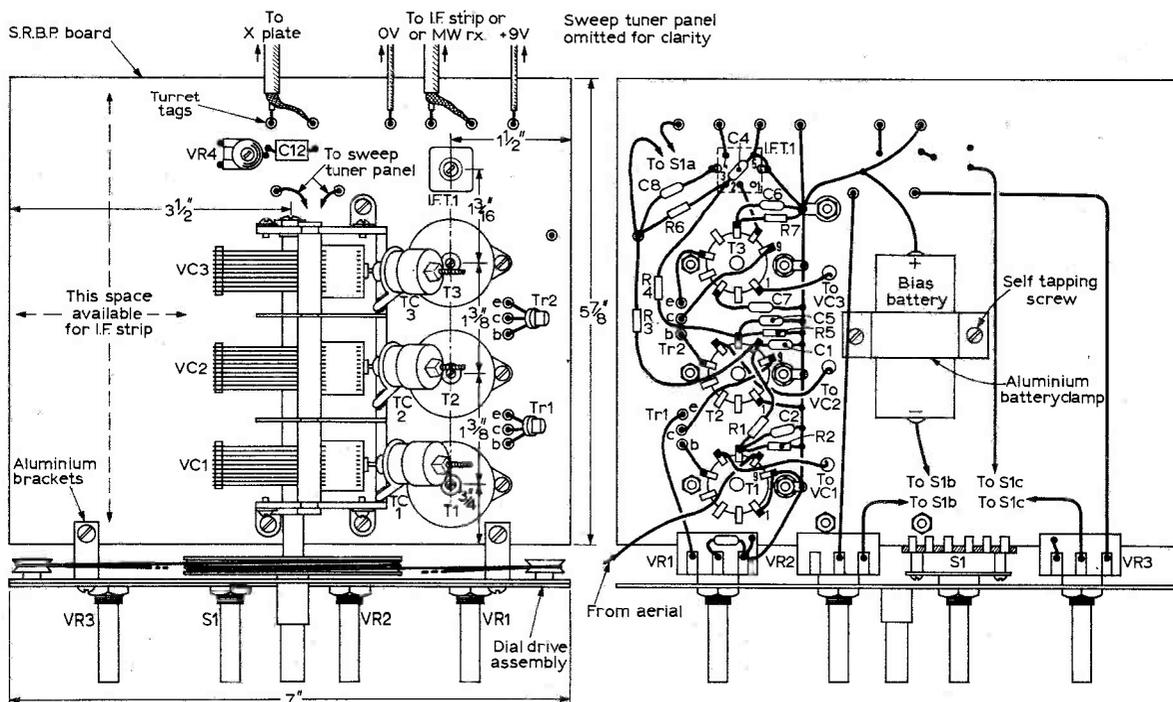


Fig. 6: The layout and wiring diagram.



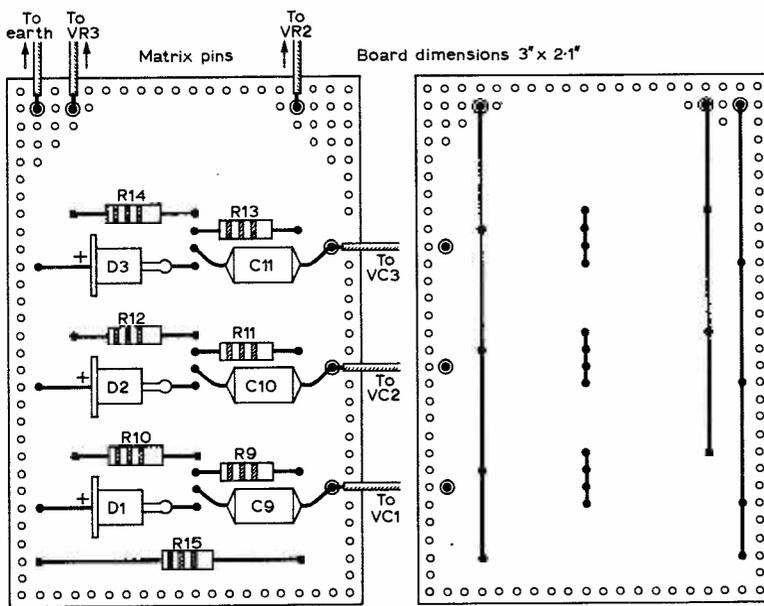


Fig. 7: The component layout and wiring of the sweep tuner panel.

(a) Details of converter chassis

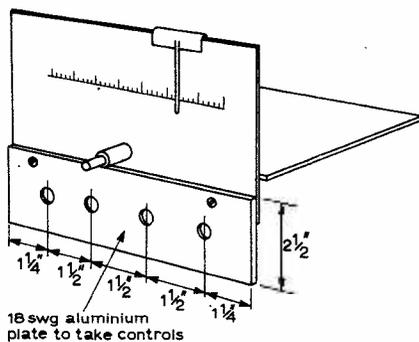

18swg aluminium plate to take controls

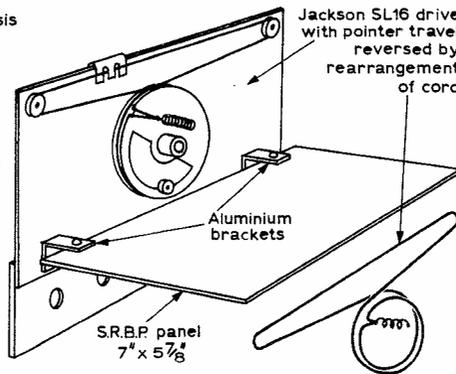

(b) Method of mounting "sweep" tuner panel on top of tuning capacitor

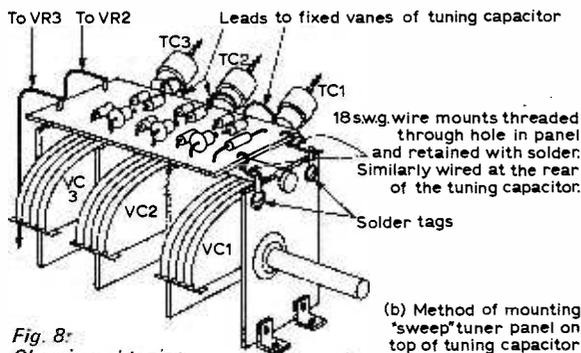


Fig. 8: Chassis and tuning constructional details.

converter tuning capacitor, for details see Fig. 8b. Solder tags (4BA) to accept the ends of the wire legs are screwed to the tuning capacitor frame by means of the tapped holes provided. After offering up the tuner panel, solder the legs to the solder tags.

Make up and drill an 18s.w.g. aluminium plate to take the converter controls, according to Fig. 8a.

The plate is bolted to the tuning scale drive assembly with two 4BA screws and nuts, which also serve to secure the aluminium brackets on the main s.r.b.p. converter panel. If it is desired to have a tuning scale with the lowest frequency on the left-hand side, it will be necessary to lengthen the drive cord and then re-wind it as shown in Fig. 8a. Whichever way the drive cord is wound, a clockwise rotation of the tuning knob gives a natural deflection of signals on the oscilloscope display to the right, and the band-spread control VR2 works similarly.

After mounting the converter controls VR1, VR2, VR3, and S1, offer up the tuning capacitor spindle and s.r.b.p. converter panel to the scale drive assembly, then complete final wiring.


COUPLING ARRANGEMENTS

If a transistor medium wave portable receiver is to hand, this can be employed as a mixer-i.f. strip without any modification, by feeding the output from the converter straight to the aerial socket of the receiver, and by taking an output straight from the receiver detector diode to the oscilloscope Y amplifier. The resistor R8 shown in Fig. 4 can be inserted if instability is experienced. A slightly better


arrangement is shown in Fig 9a, where switching is included after the diode detector to prevent the loud, rasping note of the sweep input being relayed to the headphones or loudspeaker. Note also the use of a 10mH r.f. choke in series with lead from the oscilloscope X terminal, to reduce harmonic interference from the timebase flyback, which can be especially troublesome on Top Band.

A problem likely to be encountered when the converter output is coupled to a medium wave receiver via the ferrite aerial winding is that, with the ferrite aerial still in circuit, it may be difficult to avoid spurious medium wave signals, especially after dark. Figure 9b gives an alternative method of coupling which removes the ferrite aerial from circuit. Where the ferrite aerial has a separate base winding, the circuit of Fig. 9c can be employed.

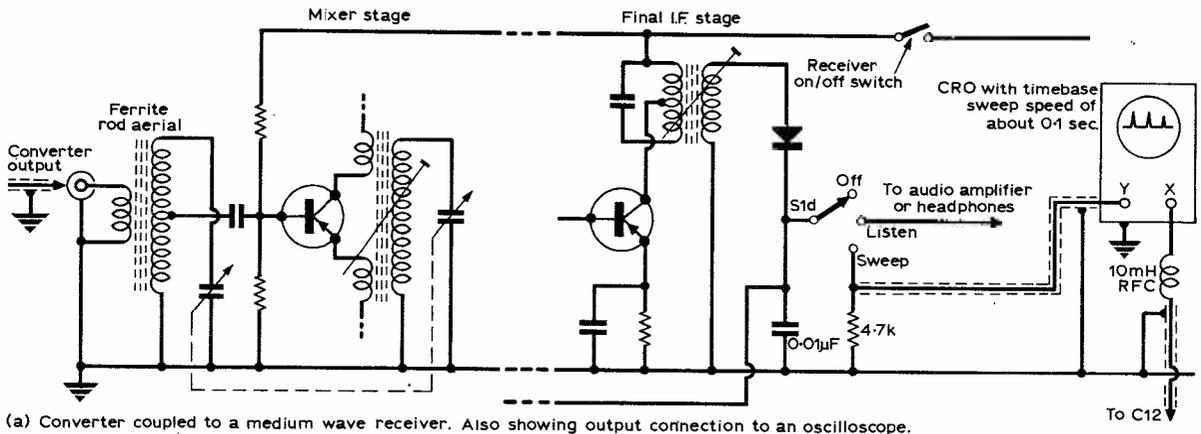
If a transistor receiver is not available for use with the converter, a 1.6MHz i.f. strip will have to be constructed, or purchased as a module. To achieve a performance comparable to that obtained with a mixer stage and 465kHz i.f. strip, the 1.6MHz i.f. strip should have three stages of amplification. A way of connecting the first i.f. stage to the converter output is shown in Fig. 9d.



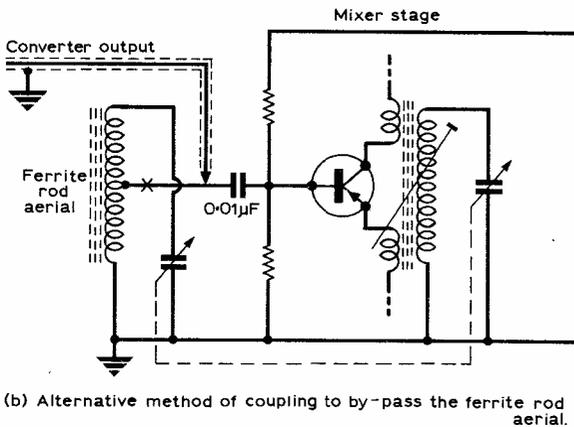
(a) Converter coupled to a medium wave receiver. Also showing output connection to an oscilloscope.



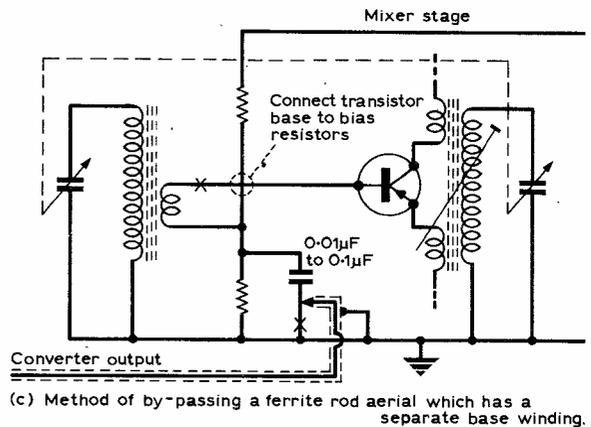(b) Alternative method of coupling to by-pass the ferrite rod aerial.



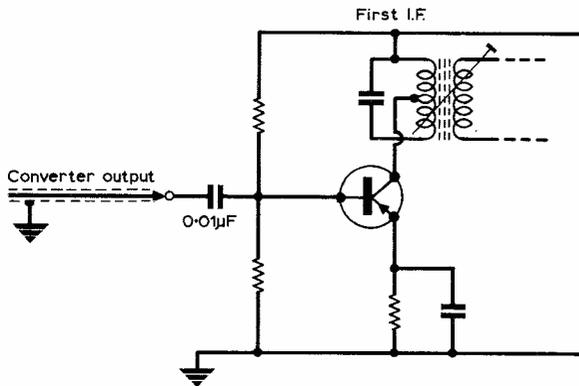(c) Method of by-passing a ferrite rod aerial which has a separate base winding.



(d) Converter coupled to a 1.6MHz I.F. strip.
Fig. 9: Coupling arrangements for the Panadaptor—see text for explanations.

When the medium wave receiver or 1.6MHz i.f. strip employs p-n-p transistors its supply rail will, of course, be at negative potential, which will conflict with the power requirements of the n-p-n transistor converter. However, in the interests of stability as well as simplicity, it is preferable anyway to employ two batteries, one for the converter and one for the receiver or i.f. strip.

Next month's final part will describe the alignment procedure and show the traces given on an oscilloscope by the prototype.

THE TWO-FIFTY TRANSMITTER

continued from page 778

Although in no way comparable to anode-and-screen modulation a clamp valve system can be tried when the simple additional switchery around SF in Fig. 3 is suggested. Negative bias—3 or 4 volts—sufficient to bring the panel meter pointer to about half-scale is needed. Modulation from a simple 2- or 3-stage speech amplifier using say 12AX7s and with a crystal microphone should swing the screen potential of the 6146 valve in sympathy with the input signals. Adequate space exists on the transmitter chassis for the inclusion of such a simple modulator. It must be appreciated however that no practical tests with this form of modulation have been made.

So far no mention has been made of the actual crystal frequency except to say that it should be in the 8MHz region; it should of course be selected in relation to the particular area in which the transmitter is to be used. The 144-144.10MHz region is a nationwide c.w. segment but for phone working the 2-metre Band Plan zonings should be observed; it is also necessary to keep clear of various Services guard channels.

Final loading into the station aerial can follow preferably using as an aid an absorption type wave-meter; the setting assigned to trimmer CT3 can then be found which affords optimum performance. ■

practically wireless commentary by HENRY

Obvious Innit?

Half the fun of reading the glossier technical magazines comes from their correspondence columns. Professor Pundit begs for space to point out that the formula for interactive floating feedback given by J. Sproggs in his otherwise interesting article contained the sort of popular error usually attributed to inattentive schoolboys. The parsing factor, given as $10^{-2}Z_{sup}$, had been proved 0.0072% too large in detailed experiment by the Capanfish Laboratories in 1937, and verified by independent field research.

Well, of course, Sproggs is not the man to take that lying down and he parries smartly to the effect that the learned Professor should have taken more trouble to read right through the offending article, where, in para 4 of Page 391 he would have seen that parsation was indeed compensated by factor K. Mr. S. goes on to say that he is surprised that Prof. P. should have seen fit to use the now discredited Binnacle Assessment. It was to be hoped, for the sake of the professor's pupils, that the bulk of his teaching was not based on such fallacious argument.

Thoroughly incensed, the Prof. fights back, quoting armsful of sources, and Sproggs caps him with reference to recent spin-off researches from the NASA programme. He implies that the Prof.

has his head buried too deeply in the historical sand.

It goes on for a few months, with others joining in to add their weight or villify; with the inevitable red herring letter (which Henry always suspects the Editor to have written himself), until a terse *'This correspondence is now closed'* allows us to concentrate on another argument that has sprung up.

Half the trouble with these 'frank exchanges' is lack of communication. Words are a treacherous form of communication, especially when used to discuss a subject as beset by different standards as electronics. Or, worse, high fidelity audio, where one man's power is another man's fixation.

Just at present there rages an argument about the relative merits of Class A and Class B operation of push-pull transistorised output stages. The protagonists have been polite, so far. Gordon J. King has recently been experimenting with amplifier assessment, and concludes that crossover distortion is such a subjective matter that by the time you have got down to the low levels where you doubt the validity of your instruments, the noise level of the amplifier masks instrumental interpretation anyway. Agreed! There does not seem much point in donning ear-phones to listen to your hair grow.

Taking a practical example of a 20-watt amplifier (r.m.s., we presume?) with the good noise figure (overall noise relative to full power output) of 78dB . . . *You will already have noted that we needed to qualify two of our parameters—that's how it goes with hi-fi lads . . .* he works out the maximum distortion measurable by the usual methods, and finds that this gives a ratio to the noise level of 2900:18 (44dB, or 0.65%).

From which we conclude that it is virtually impossible to measure low-level distortion at power around the 10mW mark (for the



Listening to your hair grow.

aforementioned amplifier) as the distortion falls into noise.

Let's come down a bit to where the air is not refined. Down to information retrieval, in fact. That formidable term simply means being able to flip over the pages until you find the data you want. My back numbers of PW are well-thumbed and dog-eared by this process because I had no way of finding the information I wanted except a vague jog of the memory and a patient flip. Now you would think that someone as erudite as Marshall McLuhan would see the value of browsing.

But, No Sir, in Dewline Newsletter he talks about communications and says: *'To go on building nineteenth century spaces for the storing and dissemination of classified information is perfectly natural. It is also fatal.'* He goes on to advocate microfilmed books, available to all at the touch of a button, extracts appearing on your TV screen.

If the Dewline extract had appeared in one of our technical glossies, McLuhan would soon have been challenged. What seems obvious to the dogmatist can be torn to pieces by the terriers of technical readership. He has overlooked the basic point about books—that all the information is under one's hand; that browsing can turn up related facts as we subconsciously do our ferreting.



His head buried in the sand.



BROMSGROVE & DISTRICT AMATEUR RADIO CLUB G3VGG

THE club was formed in January 1965 when John Harvey, a keen SWL, decided to put a CQ in the local newspaper calling any radio enthusiasts to a meeting at the Bromsgrove Co-op Hall. Twelve chaps turned up for the first meeting.

Among them was the Late Jack Casey, G8JC. Jack was a great help in helping to form the rules of the club and getting the finances organised. The present chairman Jack Gwynne, G2CLN has held that office right from the first meeting and has played a major part in the development of the club. G2CLN has been a source of inspiration to the members in getting club projects organised and also in helping with RAE lectures.

Other founder members include the present treasurer, John Harvey and J. Dufrane (Hon. Sec.). Since then the club has made great strides, a prominent landmark was the acquisition of a club shack. January 1st 1967 saw every able-bodied member armed with paints, brushes, tools, etc. and in a short time work benches and an "operating table" were fixed up. Now the shack boasts a top band Tx and various Rx sets for members' use. In addition, the club, using its call sign G3VGG takes part in various contests.

NFD is a very popular event and at the present rate of progress we should win the event in 1975! VHF and f.m. in particular is becoming very popular and a club project organised by G2CLN is for a 2m f.e.t. converter. The club has operated portable on 2m on the Clee Mills.

A very popular event is the annual mobile picnic: this is a true picnic and the aim is to cater for the wives and kids as well as the amateurs. This year's picnic on August 31st was held in the grounds of Hartlebury Castle, near Kidderminster, talk-in stations operating on 2m and top band.



A group of members at the finish of the 1967 N.F.D. event

Other outdoor activities include several exhibition stations put on at local fetes and flower shows.

The club's newsletter is edited by Ray Young and his XYL.

Licensed members include Howard, G3NOY; Robin, G3WNT; Hugh, G3VHL; Ian, G3WUG; Ken, G810 and several perspiring RAE candidates.

For SWL members the club runs a logging contest—each month a specified band with points for number of calls logged. A trophy has been presented by G2CLN to be awarded to the winner at the end of the year.

Club meetings are held every second Friday of the month at the Co-op Hall in Bromsgrove, talks and demonstrations with film shows, etc. Visitors are welcomed.

Details from Jack Dufrane, Hon. Sec., 44 Hazelton Road Marlbrook Bromsgrove, Worcestershire.



ISSUES WANTED

... September 1967 issue of Practical Television.—R. H. Taylor, 7 Antrobus Close, Sutton, Surrey.
... the issues of P.W. containing part 2 onwards of the Spectreophon article by I. J. Kappel (March 1964 on).—E. J. Thornton, Townley Hall, Burnley, Lancashire.
... February 1963 issue of P.W. which contains details of the General Purpose Communication Receiver by R. F. Graham.—W. Butterworth, 50 Kinder Avenue, Hazelhurst, Ashton-under-Lyne, Lancs.
... February 1966 issue of P.W.—James Beveridge, 18 Braeside, Haugh of Urr, Castle Douglas, Kirkcubrightshire.

... issues of P.W. from May 1966 to February 1967; from November 1967 to January 1968 and the March and April 1968 issues. Dates inclusive.—M. Donald, 116 Moncks Spur Road, Redcliffs, Christchurch 8, New Zealand
... June 1964 issue of P.W. please state price.—45 Victoria Street, Burton-on-Trent, Staffs.

... loan of these issues of P.W.: April and May 1966 and September to December 1967. Also would like Tape correspondent interested in SWL and of 16 years of age.—Kevin Piper, 113 Hawthorn Road, Bognor Regis, Sussex

... sell or lend March and April 1967 issues of Practical Television.—R. A. Jackson, 228 Woodside View, Honington, Bury St. Edmunds, Suffolk.

... February 1968 issue of Practical Television.—Michael Camilleri, 18 St. Anthony Street, Valletta, Malta.

... February 1968 issue of Practical Television containing the article Scope from an old TV Chassis.—J. P. Thurgood, Moorfield, North Cowton, Northallerton, Yorks
... the Practical Wireless magazine dated May 1963 containing the Double Conversion Communications Receiver.—Keith Portman, 23 Fell Wilson Street, Warsop Mansfield, Notts.

... August and September 1961 issues of P.W.—John Watson, 20 Watson Road, Sheffield, 10.

... November and December 1964 issues of P.W. describing the 10-5 Receiver.—P. Hudson, 338 Bennett Street, Long Eaton, Nottingham, NG10 4JD.

... January 1967 issue of P.W. containing details of the "Explorer".—S. Kendall, "Handsel", Peel Crescent, Ashton, Chester.

... Practical Wireless March and April 1966 containing mods to the 19 set.—A. M. Laird, The Tower, Patra Road, Kirkmichael, Ayrshire.

... copies of P.W. from October 1953 to July 1954 containing the P.W. Electronic Organ.—A. D. Varley, "Belfairs", 252 Liverpool Road, Penwortham, Lancs. PR1 0LY.

... P.W. June 1967 and P.E. July 1966, June 1967 and July 1967.—C. M. Davis, 1 Willesden Road, Hughesdale 3166, Victoria, Australia.

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build

IT was not many years ago that virtually all transistor amplifiers consisted of a driver transistor feeding its output into a phase-splitting transformer which powered a couple of output transistors which in turn fed their output to an output transformer. Things have changed, however; firstly with the introduction of cheap pairs of complementary transistors and secondly the rapid rise in the price of transformers against the general trend of price reductions in the electronic component field.

It is now possible to build a really simple transformerless amplifier giving an output of between 750mW and 1W feeding into a 3Ω speaker which costs well under £1. The quality is *not* high fidelity but it does compare favourably with the better quality transistor radios. The supply voltage shown, 9V, is about the lowest that this type of amplifier will operate from. However, a greater output can easily be achieved merely by increasing the supply to a maximum of 20V—no circuit modifications are necessary.

The Circuit

Tr1 acts as a high gain amplifier feeding a complementary pair; one of the output transistors amplifies the positive going signal which appears at the collector of Tr1, while the other takes care of the negative going signal.


The circuit is a very common type but most recommend the use of 15Ω or even higher impedance speakers. 3Ω speakers are, however, far more common and are generally cheaper and the component values have been chosen to ensure that this impedance speaker can operate with the circuit. If higher impedance speakers are already available they may, of course, be used, but this will be at the expense of volume.

Considerable heat is dissipated from the output transistors—especially when using a supply in excess of 9V—and adequate heat sinks are imperative. The larger types of battery should be used as the current drawn at full output can be as much as 150mA—far too much for the PP3, etc.

The Complementary Pair

Several complementary pairs of transistors were tried and all worked perfectly including an unmarked pair retailing at 3s. 6d. including postage and packing from Bi-Pre-Pak Ltd. These transistors are germanium types and are matched, but the gain of one pair is not necessarily the same as another; three pairs were built into circuits, one low gain, one high gain and the other chosen at random—all worked well.

No. 10 ONE WATT AMPLIFIER

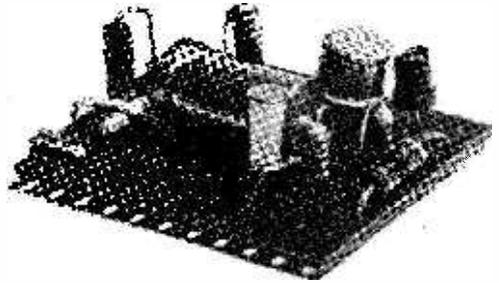

The prototype is constructed on a small piece of Veroboard but almost any method of construction should be satisfactory.

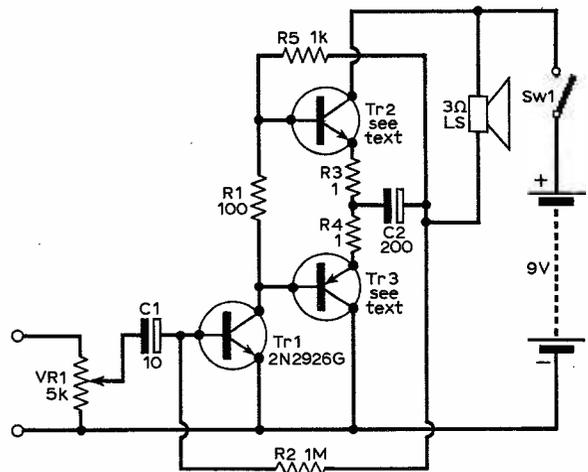


Fig. 1: The circuit diagram of the Take 20 amplifier.

★ components list

R1	100Ω	10%, ¼Watt	3d.
R2	1MΩ	"	6d.
R3, R4	1Ω	"	3d.
R5	1kΩ	"	3d.
C1	10μF 25V	1s. 2d.
C2	200μF 25V	1s. 3d.
VR1	5kΩ log.	3s. 0d.
Tr1	2N2926G	2s. 6d.
Tr2, Tr3 pair†	2s. 6d.
3Ω Loudspeaker*	3s. 0d.
						14s. 8d.


† Bi-Pre-Pak Ltd.

* Ex TV set speaker, Padgetts Radio Store, see advertisements for addresses.

Prices are only a guide.

Construction and layout are absolutely straightforward and so no layout diagram is shown. The prototypes, one of which is shown in the photograph, were built on Veroboard, but there is no reason why pin board or even tag board should not be used.

'S' METER for the CLUBMAN RECEIVER

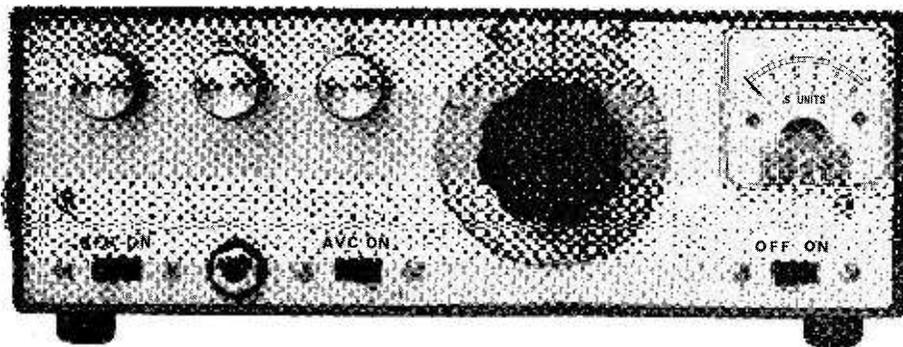

J. THORNTON LAWRENCE GW3JGA

READERS' letters which have been received in connection with the series of "Clubman" receiver articles, (PRACTICAL WIRELESS, January to July 1968), indicate that an "S" meter would be a desirable addition to the receiver. A simple circuit has therefore been developed and tested in the prototype, and will be described here. It is suitable for use in the Mk II version onwards, and could pos-

sibly be used in other transistor receivers having similar i.f. circuits.

The main requirements of an "S" meter circuit are that it should give a sensible indication of signal strength and, for transistorised equipment, it should have a low current consumption.

Circuit Description

The "S" meter circuit (Fig. 44) operates from the a.g.c. line of the receiver. It consists of two silicon transistors Tr12 and Tr13 connected as a "long-tailed pair". The base of Tr12 is connected to the receiver a.g.c. line on the i.f. panel at D5-9, the junction of R12, R13, C13 etc. (see P.W. March 1968, Page 831, Fig. 23) and the base of Tr13 is connected to the slider of the "zero" control VR4. A current is fed to both emitters via R37 and the "S" meter itself is in the collector circuit of Tr12.

With no input signal, the base of Tr12 is at approximately -0.9 volts, with respect to chassis. VR4 is adjusted so that Tr13 is conducting all the current supplied by R37 and no current is passing through Tr12 to the meter. In the presence of any signal, a positive voltage is developed at the detector diode causing the base of Tr12 to become less negative. This results in Tr12 conducting and allowing the current supplied by R37 to flow through the collector of Tr12 to the meter. The increase of meter current with increase of input signal is approximately logarithmic, which will give a linear scale for the meter when this is calibrated in decibels. The particular meter used is a MR38P "S" meter which is scaled in "S" units and in dB above S9.

It is usual to make each "S" unit equal to a 4dB increase in signal. Unfortunately the "S" units and dB markings on the scale are not linear and do not agree exactly with the changes of input signal. However, the error is sufficiently small over the major portion of the scale to be neglected for most practical purposes. The meter indication has been found to agree well with "S" reports based on personal estimation of the received signal.

The graph in Fig. 45 shows the relationship between input signal and "S" meter reading for the Clubman II and Clubman III with its r.f. stage.

The position and mounting of the meter depends on personal requirements. It is obviously easier to

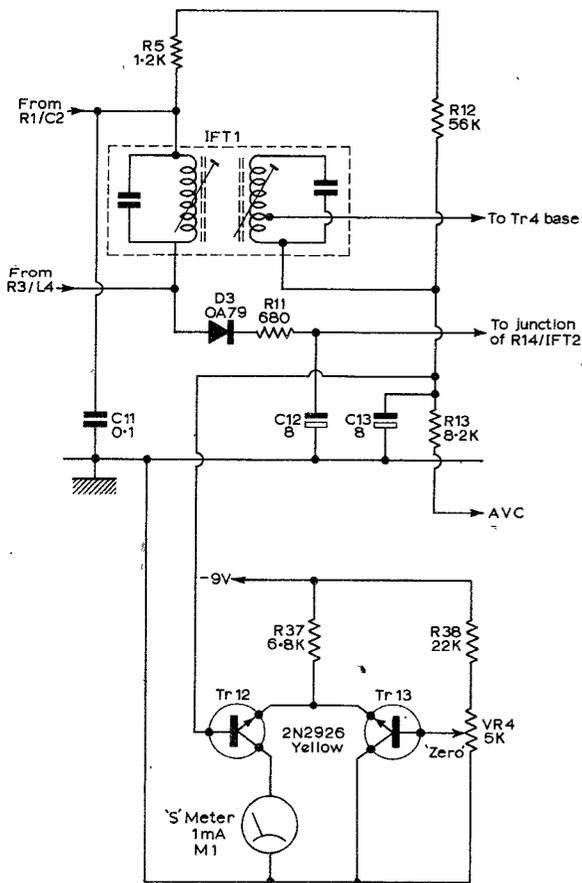


Fig. 44: 'S' meter circuitry as fitted to the Clubman Mk. II receiver.

Input Signal μ V

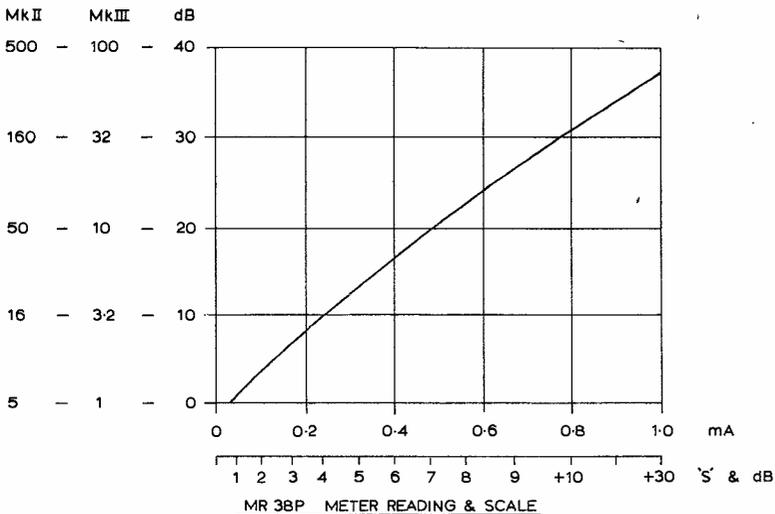


Fig. 45: Graph showing input signal/'S' meter readings for Mk. II and Mk. III Clubman.

- a - 6 BA Clearance
- b - 1 1/2" dia.

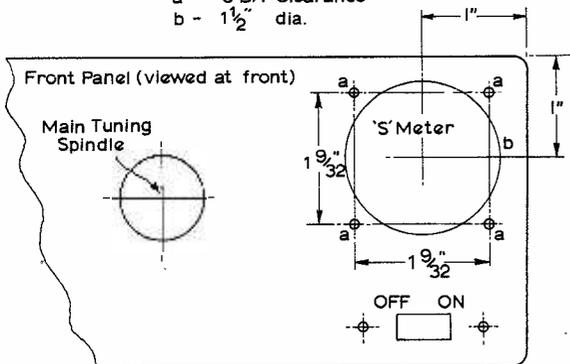


Fig. 46: Front panel drilling for the 'S' meter.

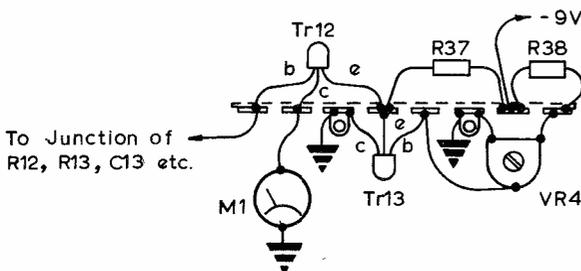


Fig. 47: Component layout and wiring for the 'S' meter circuitry.

mount the meter externally if the receiver is already built. The meter could be housed, for example, in a small metal or plastic box. Alternatively, it is possible to fit the meter at the right-hand side of the front panel of the Clubman II, as shown in Fig. 46. With the meter in this position, the clearance between the meter case and the oscillator coil L4, 5 and 6 is very small and it is necessary to remove the coil screening can. If the receiver is about to be constructed, the oscillator coil holder

could be positioned 1/4 in. further back to give the necessary clearance. In the Clubman III etc., the r.f. tuning control is in the position required by the meter. The more experienced constructor will find it still possible to fit the meter to the front panel but it is necessary to dispose of the separate r.f. tuning control. This may be done by replacing the two-gang tuning capacitor VC1, VC2 and the single r.f. tuning capacitor VC4 with a three-gang unit, e.g. Wingrove & Rogers, C73-23. The capacitance law of this unit is different to the Jackson one used originally and a new dial will be required. The use of a three-gang tuning capacitor in the Clubman V, with the d/f loop aerial, is not recommended due to difficulties in getting the loop aerial to track the main tuning circuits. The "S" meter circuit may be built on a small tagstrip under the

chassis as shown in Fig. 47, or on Veroboard and mounted in some convenient position.

★ components list

Resistors:

- R37 6.8k Ω , 1/2 watt, 10% carbon
- R38 22k Ω , 1/2 watt, 10% carbon.
- VR4 5k Ω , skeleton preset, or similar.

Semiconductors:

- Tr12 2N2926
- Tr13 2N2926

Meter:

- M1 MR38P "S" Meter (1mA)

'S' Meter Adjustment

With no signal input to the receiver, the "S" meter zero control VR4 should be adjusted so that the pointer indicates just off the zero end of the scale, about 50 microamps (0.05 milliamps). This ensures that the meter indicates even the weakest of signals and does not have a "dead" zone at zero. ■


BINDERS AND INDEX

Don't let your copies of PRACTICAL WIRELESS become torn and dirty: hard-cover binders are available at 14s. 6d. from:

**BINDING SECTION,
IPC MAGAZINES, LTD.,
SOUTHAMPTON STREET,
LONDON, W.C.2.**

Indexes to Vol. 43, 1967-8, are also available at 1s. 6d.

These prices include post and packing.

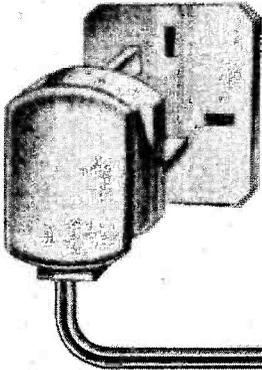

plug in


the smallest soldering iron available

Antex irons will give you fingertip control for precision soldering of small component and transistors.

Send for one if your local shop cannot supply, or send for our 16 page colour catalogue by completing the coupon below.



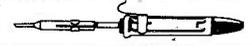CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. from **32'6**



15 Watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits: 1/8", 3/16", and 1/4" available. For 240, 220 or 110 volts. **32'6**



20 Watts. Fitted with 1/4" bit. Interchangeable spare bits: 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From **35'**



25 Watts. Fitted with 1/8" bit. Interchangeable bits: 3/32", 3/16", and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From **35'**



40 Watts. Fitted 5/16" bit. Interchangeable bits: 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 12 volts. From **42'6**

Spare bits and elements for all models and voltages immediately available from stock.

Complete precision soldering kit



- This kit—in a rigid plastic "tool-box"—contains
- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits: 1/8", 3/16", 1/4"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

From Electrical and Radio Shops or send cash **49'6** to Antex.



Model CN 240/2
15 watts - 240 volts
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **31'**



PRECISION MINIATURE SOLDERING IRONS
Antex, Mayflower House, Plymouth, Devon.
Telephone: Plymouth 67377/8.
Telex: 45296. Giro No. 2581000.

Please send me the Antex colour catalogue
 Please send me the following irons

Quantity	Model	Bit Size	Volts	Price
.....
.....

I enclose cheque/P.O./cash value
.....
NAME
ADDRESS
.....

PE3

MADE IN ENGLAND
ACTUAL SIZE

LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on ½ in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.




COWDREY FIVE. Specially designed Corner Cabinet 20½ x 13 x 7½ in. deep. Finished in natural teak veneers with Vynair front. Fitted rubber feet. Five speaker units 15 ohms. Impedance handles 15 watts). £6.6.0 P. & P. 8/6 each.



ADASTRA DOUBLE 5 stereo solid state amplifier housed in handsome cabinet veneered in natural teak. Size 11½ x 6 x 5½ in. 10 Transistors—power output 5 watts peak per channel. 220-240V AC. Output impedance 12 to 15 ohms (our Cowdrey speaker system eminently suitable). Smart blue escutcheon. £14.14.0. P. & P. 10/6.

SCOTT. This elegant tapered cabinet 10½ x 16 x 5½ in. deep is attractively finished in black cloth with striped grey Vynair front. Suitable for table or for wall mounting. Fitted with 13½ x 8 in. speaker unit and volume control. 3 or 15 ohms impedance—please state impedance required. £4.5.0. P. & P. 7/6d each. Fitted with E.M.I. 45 x 8 in. speaker unit and twin tweeters. 15 ohms impedance, capacity 10 watts. 30/- extra.

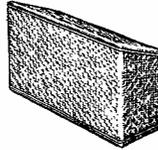


SPEAKERS: Elac Heavy duty Ceramic Magnets 11,000 line. 10in. round, 10 x 6in. 3 ohm or 15 ohm, 48/6. P. & P. 3/6. 8in. round 15 or 3ohm, 42/6. P. & P. 3/6. E.M.I. 13½ x 8in. 3ohm, 45/-, 15ohm 48/6. P. & P. 1/6. E.M.I. 3in. tweeter 17/6. P. & P. 1/6. E.M.I. 13½ x 8in. fitted two 2½in. tweeters. 15ohm 77/6. P. & P. 4/6. E.M.I. 13½ x 8in.



CAXTON COLUMN. This is a column cabinet 23½ x 5½ x 5½ in. deep finished in wood grain cloth with sandstone Vynair front. Keyhole slot for wall mounting. Fitted with three speaker units. 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at 59/6d. P. & P. 10/6d. each.

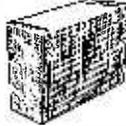ELF. An extension speaker of quality 9 x 5½ x 3½ in. deep veneered in natural teak with smart gold and brown Vynair front trimmed in white. Fitted with 3 ohm speaker unit mounted on ½ in. baffle. Exceptional value 37/6d. P. & P. 3/9d. each.



IMP. Wedge shaped extension speaker 7½ x 6½ x 4 in. (max.). Covered in walnut wood grain cloth with foam Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only 25/6d. P. & P. 3/9d. each.

(15 ohm) Hi-Fi quality £5.19.6. P. & P. 4/6. E.M.I. Woofers, 6½ x 6½ in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/- EAGLE Crossover units 3 or 10 ohms, 16/-, P. & P. 1/- Bakers 12in., 25 watt 15 ohm £6.6.0. P. & P. 3/6.

CANCELS PREVIOUS LIST

TEAK PLINTH AND PERSPEX DUST COVER for SP25 etc. £5 5 0 P. & P. 5/-.

VYNAIR. Widths from 40 to 54in., 17/6 yd. off roll. P. & P. 1/9. ¼ yard, 9/-, P. & P. 1/9. Send 1/- stamps for samples.

SPEAKER MATCHING TRANSFORMERS. 3, 7, 15 ohms, 8 watt, 13/6. P. & P. 1/6.

MICROPHONES: Xtal Hand Mikes. B1201 with stand, 54/6. P. & P. 3/6. Dyn. Mike DM-391, 30/-, CM21 Xtal, 12/6. Telephone Pick-up, 10/6. P. & P. 1/-, Xtal label Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-.

FERROX RODS: 6 x ½ in., 2/6; 4½ x ¾ in., 2/-; 6 x ¾ in., 2/6; P. & P. 1/- each.

FERROX RODS WITH COILS. 4½ x ¾ in., 3/6; 8 x ¾ in., 5/6. P. & P. 1/- each.

ROTARY SWITCHES: 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each. P. & P. 1/-.

TRANSISTOR SPEAKERS 8 ohm 2 in., 8/6, 3 in., 10/6. P. & P. 1/-.

CARTRIDGES. Stereo: Sonotone 9TA H/C Diamond, 47/6. 9TA Sapphire, 37/6. STA Sapphire, 30/-, Ronette S105 Medium Output, 28/6. S106 High Output, 28/6. DC284 Stereo Compatible, 22/6. Acos GP93/1 Sapphire, 37/6. GP94/1 Sapphire, 39/6. GP81 Diamond, 42/-, GP91 Stereo Compatible (High, Medium or Low Output), 25/-, TA800 converts Philips AG3301, AG3306 to B.S.R. SX1H. Plug-in head complete with cartridge, 50/-, TA700 equivalent to B.S.R. SX1M, 35/-. Japanese equivalent to B.S.R. TC8s, 35/-, P. & P. 1/6.

Mono: Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/-, B.S.R. TC8H Jap. equivalent, 26/-. Sonotone 2TSS, 15/-, P. & P. 1/6.

EARPIECES WITH CORD and 3.5mm. plus, 8 ohm magnetic, 3/-, 250 ohm, 4/-, 180 ohm with clip, 6/6. Xtal. P. & P. 6d.

PIANO KEY PUSH BUTTON SWITCHES. 7 button inc. mains on off. 6 banks of 6 P.C.O., 8/6. P. & P. 1/-.

BROADWAY Electronics (Few minutes from Tooting Broadway Underground Stn)

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 01-672 3984 (Closed all day Wednesday)

4-STATION INTERCOM



£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price £10.19.6. P. & P. 8/6 extra.

INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

TELEPHONE AMPLIFIER



59/6


Why not boost business efficiency with this incredible De-luxe Telephons Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P/W)
189 KENSINGTON HIGH STREET, LONDON, W.8.

Keynector

A REVOLUTIONARY PRODUCT

cuts out plugs

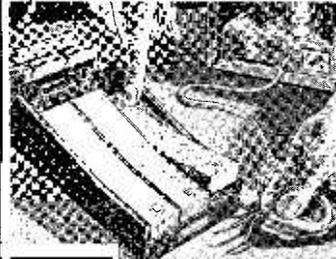

SAFEST & QUICKEST WAY TO CONNECT ELECTRICAL EQUIPMENT TO THE MAINS



No plugs—no sockets—no risk of bare wires. To connect anything electrical, from an oscilloscope to an electric drill, simply open the fuse housing, depress the keys, insert the wires and close the housing. A neon light on the front of the Keynector glows to indicate proper connection. Multi-parallel connections can be made up to 13 amps. Keys are colour coded and lettered LEN for quick identification. The Keynector casing is in two-tone plastic and measures 5 x 3 x 1½ in. Price 39/6, plus 5/- p. & p.

E. B. INSTRUMENTS
DIVISION OF ELECTRONIC BROKERS LTD.
49-53 PANCRAS ROAD, LONDON, N.W.1.
Telephone: 01-837 7781

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND LONDON WC2

Make	Model	Radio/TV

1969 List available at 2/- plus postage If list is required indicate with X

From

Address

enclose remittance of.....
(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (February PW)

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT • Frequencies in kHz

THE BROADCAST BANDS Malcolm Connah

BY the time that you read this a tragic event may have occurred in the world of Shortwave radio. I am referring to the cessation of foreign language broadcasts from the *Voice of Denmark*. Originally scheduled for the 1st. April 1970, the date of closure was brought forward to the 1st. January 1970.

The decision was taken by the Danish Radio Committee and two reasons were given: (1) very few people listen to the *Voice of Denmark* (although 3,000 letters were received in the last half year); (2) The Danish Radio and Television Service has to cut its budget (although the Shortwave department costs only 345,000 D. Kr. annually, which is a fraction of the cost of one of the expensive TV productions).

If you have any loggings of *Radio Denmark* which you have not used for reception reports I suggest that you use them now and include a plea to keep the station open. Rodney Baggaley wrote to me from Daventry suggesting that protests should also be sent to the Director-General of Danmarks Radio at the following address:—Mr. Hans Sølvhøj, The Director-General, Danmarks Radio, Radio House, Copenhagen, Denmark.

In the past several stations have made similar decisions only to have them reversed by the large number of protests from shortwave enthusiasts from all over the world. Please act as soon as possible and we may yet be able to save this excellent station from extinction.

Worldwide QSL Card Poll

The results of this poll, which was conducted by the Cellardyke Short Wave Radio Group to find the shortwave station which has issued the best QSL card since January 1967, arrived just too late for inclusion in the last issue. Votes were received for nearly fifty stations and the top five with the number of votes in parentheses were:—

- 1) Radio Portugal (62)
- 2) Radio Australia (48)
- 3)=Radio RSA (47)
- 3)=Radio Nederland (47)
- 5) Radio Canada (46)

Congratulations to *Radio Portugal* who emerged as clear winners.

The poll was also used to determine what details were thought to contribute to an ideal QSL card. The results indicated that date, time and frequency were regarded as essentials. The next most popular detail was transmitter power followed by transmitter location, reporter's name, genuine signature on the QSL, etc.

Africa

Nigeria: The *Voice of Nigeria* in Lagos has dropped 11770 for the English broadcast to Europe and has now been noted on 7275, 15365 and 21455 from 0600 to 0730.

Seychelles: F.E.B.A. test transmissions are scheduled for 0030-0330 on 15165; 1300-1630 on 17755 and 1700-2000 on 21635 using a power of 3 kW. Reports should be sent to F.E.B.C., Box 234, Victoria, Seychelles or to F.E.B.A., Sky Waves, St. Paul's Road, Woking, Surrey. Taped reports should preferably be sent to the British address.

Asia

Cyprus: As reported last month the Cyprus Broadcasting Corporation continues to transmit with a power of 30 kW on 15260 and 17875. From the 1st. November they introduced the new frequency of 11910. The station issues a very good multi-coloured QSL card.

Syria: *Radio Damascus* has returned to the frequency of 15165 for its broadcasts in German at 1830. French at 1900 and English at 2030.

Europe

Greece: *Radio Athens* has news in French, German and English at 0715-0730, 1115-1130, 1315-1330 and 1830-1845 on 9605 and 11720; 1730-1745 and 1945-2000 on 15345 and 17745; 2200-2215 and 2300-2315 on 11720 and 15345.

South America

Brazil: *Radio Piratininga*, Sao Paulo, has a religious programme in English, Monday-Friday, at 2100-2115 called "Lesson for Life." The frequencies are announced as 6025 and 11745.

Ecuador: The *Voice of the Andes*, HCJB, is testing on 21460 to Europe from 1800 to 2145.

El Salvador: El Salvador has announced that it is going to have an international service. The broadcast will be from 0300 on 9555 and the languages used will be Spanish, French and English.

Mexico: A new station is *Radio Mexico*, XERMX, Apt. 20100, Mexico City 20. The station has been heard testing from 2350 to 0300 on 11720 with announcements in English, French, German and Spanish.

THE AMATEUR BANDS

David Gibson, G3JDG

GOOD news this month for the ten metre fans. The band has been providing some very good openings and quite a large number of eager hearing utensils have been frantically logging most continents. Signal levels have varied and it must be admitted that some of the signs from further afield have been down in the 5 and 4 range.

One item of interest for those who like tuning in to something a bit different. Why not tune down between 28 and 27MHz and eavesdrop on the American citizens band? Some of these stations have to be heard to be believed. Seriously though, the citizens band does give an excellent indication of just how much the band is open, particularly towards W land.

As might be expected, the fifteen metre band opened up with ten and some very good openings here too. Down another notch on twenty things have been quite good but surprisingly enough it is ten metres which has provided the majority of DX signals. Twenty has been open at times but mostly to S. America with good sigs from PY and surrounding districts. Africa, too, has done quite well on twenty from the s.w.l. in Britain's point of view.

Forty and eighty have had their moments but mostly Europeans (EUs) logged at this QTH. One or two W stations made it through the QRM on forty and in the W segment of eighty.

Topband hasn't fared too well. Lots and lots of QRM/QRN and the best for the month was only GW and GM. No W stations were logged on c.w. Anyone hear any W-type tweets down the l.f. end?

Logland

On to the field where lovely logs grow. This one was cared for by **John Moore** (Leicester) and is an all-band edition. Envious readers should (like me) gnash CQ on their teeth while reading—160: GM3ONS/A, GM3UYF, GM3WDF GW3RBM.

80: CT1GD, JW1CI (Bear Is.), KV4FZ, OY1X, UA9KAX, VE1IE, VP2VP, W1EBC.

40: EA6BN, PJØDX, WA2ZAA.

20: CT2AK, DU1BEN, ET3ZU, FG7TI/P/FS7, FG7XT, HK3RQ, HK4AXZ, HZ1AB, JA8EL, JW1CI, KP4AST, KR6NR, KV4FZ, KZ5DA, LU8DF, OD5BZ, PJØDX, PY1NBF, TA2SC, TG9UZ, TF2WLN, VE1SH, VE2DHF/YV1, VE5US, VP2VI (Tortola), VP7DL, VP8KD, VS6DR, YV1EJ, ZS5XA, 4X4UF, 5A1TL, 5H3LV, 8P6AZ, 9H1BL, 9Y4AA.

15: CR7IZ, DU1FH, F6ABP/FC, JA3LVT, JA8QN, KH6SP, KL7MF, OD5FA, PJØDX, PZ1CU, TG9F, UA9FU, VE2AFC, VE3BMB, VE5XC, VE7TL, VP2VP, VK6US, W7RM, ZS6AR, 4M1A (Venezuela ?), 4X4KT, 9Q5GV, 9Y4AA.

10: CN8DW, CN8HD, CR6LV, CT2AS, CX7BF, EP2BQ, ET3USA, HC1RF, HK4DF, K6NA, KV4AD, KZ5AT, LU2QT, MP4BBA, OA1BT, OA4PF, OD5BZ, PJ1AA, PJØDX, PY1NBF, PZ1DB, UAØBP, VE1ATC, VE2AYW, VE3BIZ, VO2AP, VP2VI, VS6AL, VS6DR, VUØDK, W6ESI, XW8CR, ZS5DC, 4Z4HF, 5Z4ALS, 9H1BP.

All this bunch on s.s.b. picked up with the aid of a 60ft. end fed and a CR100/2.

A. Woodland (Somerset), confesses to usually listening to non-amateur type stations (some people have no shame) but admits to weakening while ill. His receiver is a Hammarlund SP600JX (suddenly I'm green) and the aerial a V-beam 40ft. up plus a 72ft. vertical "condensed" into 41ft. (Good Gawd!) Stations logged on ten metres include—CE3OE, CR6CA, EP2BQ, GC4LI, HK4DF, JA1AEA, JA2CLI, JA4FRB, JA6YCU, JA7BCR, JA8PMK, KA9MF, KH6SP, KR6VX, KV4FZ, KZ5CD, K6CM, K6KGU, K7AB, LU7FAG, LU8DKA, LX1BW, MP4BL, OA1OX, OA4PF, OD5EP, PJØDX, VE6AUT, VE6ADX, VE7AGZ, VE8YM, VK6US, VP2GBL, VP9BU, VP9EP, W6ABN, W6EJJ, WA6EPQ, W7AC, W7GUX, XE1WS, XW8CS, YN1HS, YV6GL, ZE1CY, ZE1JU, 6Y5DW, 8P6CX, 9Y4AA. All these on s.s.b.

A. Crooks (Leicester), recently had his RA1 serviced and peaked up. It showed its appreciation by teaming up with a PR30 and 45ft. end fed to hook these on 15 s.s.b.—CX1JM, JW1CI, KØVBX, K5QHS, JA2KKZ, TF3EA, UD6BD, VE6XF, VE7HN, VP8KO, (S. Orkneys), W6ZQI, W7GVA, WF2LIB, ZS5JY, 9I5EJ (Zambia).

B. Hughes (Worcester), JR5OOSE, dipole, had a quick squint at 20 and came up with—CR7DS, CR6IK, CR4BC, JX8IL, LAØAD, SVØWN, TG9EP, TR8MC, VUØGE, VK9KY, (Cocos Keeling), VK2BKM/VK2 (Lord Howe Is.), VP2GLE, VR1L, ZS2MI, 6W8BD, 9V1PA, 9X5AA.

All these on s.s.b. except ZS2MI on Marion Island who was a.m., just shows what you can receive without a b.f.o.

A. Lister (London), CR7OA, home brew pre-selector and 150ft. end feed informs that ZL's are loitering on 3.8MHz from 0600-0700. Fifteen with this set up raised—AP2AGC, CT1GD, EA6BN, IS1LIO, KP4KBS, KV4FZ, LG5LG, LX1JES, PY1MT, TF2WKO, VE3ZO, VO2DAL, VO8CR, dozens of W's, ZS6QK, 4X4LN, 5A3JR, 9Q5FM, 9Q5AE. On eighty, Adrian's best were five ZL's and he managed VK2WX on ten metres.

R. Hall (Belfast) modified AR88D, 50ft. end fed; listens at weekends. The last session on twenty s.s.b. produced—AP5HQ, CR6IK, CT1WB, FP8AP, HK3RQ, HR1KAS, JA9AG, KC4CL, KZ5NG, OZ7TF, PJ1AA, TF2WKI, VE3CBG, VK6RU, VP7DL, 3Z3AMZ, 4X4OS, 6Y5SR, 8R1UC, 9H1M, 9K2CF, 9N1MM, 9Y4UV to mention just a few.

NEWS of contests—

According to my diary, contest lovers will be out of luck for the cold days in January. I can find only two with February not faring very much better.

January 10-11th., AFS contest; 31-Feb. 1st., French c.w. contest.


Logs for the Amateur Bands, with stations in alphabetical order, must arrive before the 18th. of each month. Logs only to: 5 Edward Close, St. Albans, Herts.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

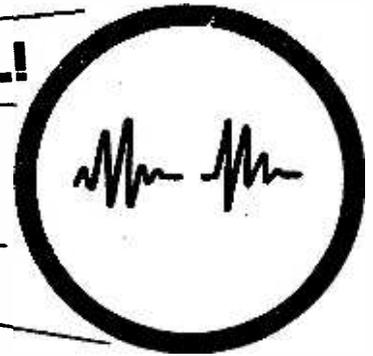


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

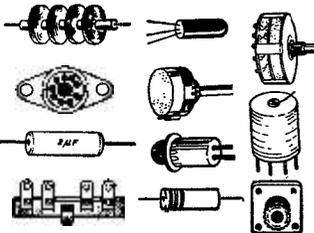complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

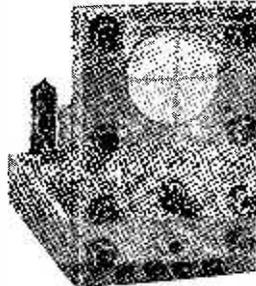a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND **CIRCUIT DIAGRAMS**

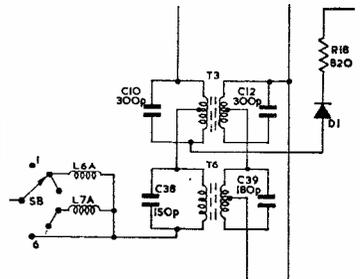

4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
 - TRANSISTOR EXPERIMENTS
 - AMPLIFIERS
 - OSCILLATORS
 - SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
 - COMPUTER CIRCUIT
 - BASIC RADIO RECEIVER
 - ELECTRONIC SWITCH
 - SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
 - D.C. EXPERIMENTS
 - SIMPLE COUNTER
 - TIME DELAY CIRCUIT
 - SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW1

FAN HEATER

Three position switch to suit changes in the weather. Each up for full heater (2½ kW), switch down for half heat (1½kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cutout. Complete kit £3.15.0. Post and ins. 7/6 or similar 2½kw made up heater £4.5s. Post & ins. 7/6.



FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube cnds, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-sized, mostly resin filled. Kit A—15-20w. 19/6. Kit B—30-40w. 19/6. Kit C—80 w. 23/6. Kit E—65 w. 19/6. Kit MF1 is for 6in., 9in. and 12in. miniature tubes. 19/6. Postage on Kit A, B and 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

BLANKET SWITCH

Double pole with neon let into side so luminous in dark. Ideal for dark room light or for use with water-proof elements in plastic case. 5/6 each, 3 heat model 7/6.



HIGH CAPACITY ELECTROLYTICS

Brand new, not ex equipment. 100 mfd 25v. 1/3 each. 12/- doz. 200 mfd 25v. 1/6 each. 15/- doz. 500 mfd 12v. 2/- each. £1.1.0 doz. 1,000 mfd 12v. 2/- each. £1.0.0 doz. 5,000 mfd 12v. 4/9 each. £2.8.0 doz. 10,000 mfd 6v. 5/9 each. £3.0.0 doz. 10,000 mfd 15v. 8/6 each. £4.10.0 doz. 15,000 mfd 10v. 10/6 each. £4.10.0 doz. 60,000 mfd 8v. 2/- each. £10.0.0 doz. 70,000 mfd 13v. 40/- each. £20.0.0 doz.

TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7½ to 47in. Hole in bottom for 6BA screw. 7/6.

TOGGLE SWITCH

3 amp 250v with fixing ring 1/6 each 15/- doz.



80 OHM BALANCED ARMATURE EAR PIECE

Usable as microphone or loudspeaker, 4/6 each.

MINIATURE EAR PIECE

As used with imported pocket radios 1/6 ea. 15/- doz.

ISOLATION SWITCH

20 Amp D.P. 250 volts. Ideal to control Water Heater or any other appliance. Neon indicator shows when current is on. 4/6. 48/- per dozen.



FLEX BARGAINS

Screened 3 Core Flex. Each core 14/0076 Copper PVC insulated and coloured. The 3 cores laid together and metal braided overall. Price £3.15. per 100 yds. coil.

15 Amp 3 Core Non-kink Flex. 70/0076 insulated coloured cores, protected by tough rubber sheath. Black cotton braided with white tracer. A normal domestic flex as fitted to 3 Kw. fires. Regular Price 3/6 per yd. 50 yd. coil £4.10.0, or cut to your length 2/6 per yard.

10 Amp 3 Core Non-kink Flex. As above but cores are 28/0076 Copper. Normal Price 2/6 per yd. 100 yd. coil £7.10.0, or cut to your length 1/9 yd.

6 Amp 2 Core Flex. As above, but 2C ores each 23/0076 used for Vacuum Cleaners, Electric Blankets, etc. 39/6 100 yd. coil.

15/20 AMP CONNECTORS

Polythene insulated 12 way strip 2/6 each 24/- doz.



13 AMP FUSED SWITCH

Made by GEC. For connecting water heater etc., into 13 amp ring main. Flush type 3/6 each 30/- doz. Metal boxes for surface mounting 1/6 each 15/- doz.


REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types.

Miniature. 1in. long x approximately ¼in. diameter. Will make and break up to ½ amp up to 300 volts. Price 2/6 each. 24/- dozen. Standard 2in. long x 3/16in. diameter. This will break currents of up to 1 amp, voltages up to 250 volts. Price 2/- each. 18/- per dozen. Flat. Flat type. 2in. long, just over 1/16in. thick, approximately ¼in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp, 200 volts. Price 6/- each. £3 per dozen. Small ceramic magnets to operate these reed switches 1/3 each. 12/- dozen.

'GLADIATOR' 2. WAVE BAND TRANSISTOR RADIO

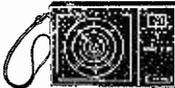7 transistor, 2 wave band (medium and long) pocket radio with carrying handle and ear. Plug. These radios use a ferrite slab aerial and a conventional superhet circuit with built in moving coil speaker. Completely built up, ready to play. Offered at less than importers price due to bankers purchase. A remarkable bargain. 39/6 plus 3/6 post and insurance



MINIATURE EXTRACTOR FAN

Beautifully made by famous German Company. P.A.P.S.T System, 230/240 A.C. Mains operated, size 3½in. x 3½in. x 2in. Made for instrument cooling but ideal to incorporate in a cooker hood, etc. 65/-



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box with heavy cable and 13 amp plug. Supplied complete with 6 feet of take standard 13 amp fused plug. Similar panels advertised at £5. Our price kit of parts 39/6 Plus 3/6 Post and insurance. Made Up 45/- Plus 4/6 Post and insurance.



Horstmann "Time and Set" Switch

(A 15 amp Switch) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price 29/6. p. & ins. 4/6.

24 HOUR TIME SWITCH

Mains operated. Adjustable Contacts give 2 on/off per 24 hours. Control rated 15 amps. Repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 with Perspex cover, plus 3/6 postage and insurance, a real snip which should not be missed.



PROTECT VALUABLE DEVICES FROM THERMAL RUNAWAY OR OVER-HEATING

Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having them operate in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg. F. or with the dial removed range setting is between 80 to 800deg. F. Price 10/-



BATTERY OPERATED TAPE DECK WITH Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2in. deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4½ volts. Supplied complete with 2 spools ready to install. Record, Replayhead is the sensitive M4 type intended for use with transistor, amplifier. Price 79/6. Post and insurance 4/6.



ATLAS SLIMLINE FLUORESCENTS

THE TWENTYLITE & TWIN FORTY



A Fluorescent lighting unit made by the famous Atlas company, with super silent polyester filled choke and radio suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. Measures 2ft. long. Is ideal in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer. 39/6 with tube. Assembled ready to install. Postage and insurance 6/6 extra.

1 WATT AMPLIFIER & PREAMP

5 transistors—highly efficient, made for use with tapehead G4 but equally suitable for microphone or pick up—limited quantity 39/6. Full circuit diagram, also shows tape controls 5/-




VARYLITE

Will dim incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob £3.19.6.



FULL F1 12 INCH LOUSPEAKER.

This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in. Mtd on 12in. dia. holes 4. Baffle hole 11in. Diam.—Mounting holes 4. holes —¼in. diam. on pitch circle 1½in. diam.—Overall height 5½in. A £6 speaker offered for only £3.9.6 plus 7/6. p. & p. Don't miss this offer. 15in. 30 watt £7.19.6. 17in. 100 watt £24.10.0.

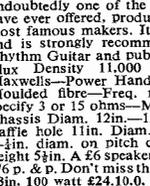

DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 10/- each, plus 3/6 post and insurance, 6 or more post free.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 1 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.



AC FAN

Small but very powerful mains motor with 53in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6. post 4/6. Mounts from back or front with 4BA screws.

750 MICRO AMP MOVING COIL METER

2½in. ex W.D. but brand new and unused 19/6.

0.0005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each. 24/- doz.



HEAT & LIGHT LAMP

275W. internally mirrored bulb with b.c. end for putting into lamp holder 19/6 each plus 4/6 postage and insurance.

COPPER CLAD ELEMENT

1250 watts—4ft. long but bent to U shape. ideal for overhead heater—just mount reflector above. 12/6 each, plus 4/6 post. £6 doz. post paid.

Battery Record Player. Made by Collaro. This is made up on a unit plate with speed selector and pick-up. The turntable is a heavy one and measures approximately 9½ins. Pick-up is fitted with the famous "Studio" cartridge. Price 69/6. Postage and insurance 6/6.

E.H.T. Condenser, 28Kv. 0.0011 mfd. Suitable for transmitting test conditions 6A at 300k/c. Bakelite case. 18/6 each.

85 Watt Tubular Element. Very well made unit. The element is wound on a porcelain former then encased in a brass tube encased with beaded leads 12in. long. Normal mains voltage. Price 5/- each or 54/- per doz.

Press to Make Switch. Double pole, 5 amp contacts or can be used as single pole, 10 amp, contacts 250 volt working. Single hole fixing. 2/6 each, 24/- dozen.

Door Switch. Contacts open when plunger is depressed. Prevents lights being left on. 15 amp contacts, 230 volt working. Made by Arrow. 3/6 each, 36/- dozen.

Rotary Appliance Switch. 16 amp, 230 volt on moulded ceramic base. Operated by pointer knob (not supplied). 2/- each, 18/- per dozen. 1/40th h.p. Motor. Made by the French (Cassor) Company. This is an excellent totally enclosed motor, powerful enough to operate small lathe, drilling machine, washing machine, etc. It's speed is 1,450 r.p.m. Made for normal 50 cycle. 230/250 volts. Main totally enclosed, size 2½ x 3½in. dia. with 1in. of ¼in. spindle. Price 19/6 plus 4/6 postage and insurance.

THERMAL CUTOUT

A miniature device ¼in. dia. on one screw fixing mount—can be used for motor over-heat protection—fire alarm—soldering iron switch off, etc., etc.—15 amp contacts open with flame—radiant or conducted heat. 1/6 each, 15/- doz. £5 10.0.

THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 30-80°F. 9/6 plus 1/6 post. Suitable box for wall mounting. 5/-, P. & P. 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjust this from 50-550°F. Internal screw alters the setting so this could be adjustable over 30° to 1000°F.

Suitable for controlling water, furnace, oven, kiln, immersion heater or to make flame-stat or fire alarm. 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16 yd 10/-) is wound round the pipes. 7/6. P. & P. 1/-.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6. plus 1/6 post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks. Thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developed and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/- plus 2/- post and insurance.

Type "G". We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16 yd 10/-) is wound round the pipes. 7/6. P. & P. 1/-.

Type "H". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6. plus 1/6 post.

Type "I". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks. Thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developed and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/- plus 2/- post and insurance.

Type "J". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks. Thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developed and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/- plus 2/- post and insurance.

Type "K". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks. Thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developed and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/- plus 2/- post and insurance.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.


ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH

Also 102/3 Tamworth Road, Croydon

BASIC SEMICONDUCTOR TECHNOLOGY

PART NINE

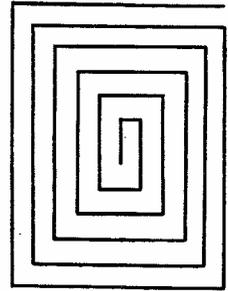

by M.F. DOCKER, M.Sc.

SINGLE semiconductor devices can be produced easily nowadays. They are rugged, stable and efficient. An early thought was why not put several devices on to one chip so that even more space saving could be achieved, not to mention the other advantages of this method. The advent of planar technology, where devices are produced by diffusion from one side of the chip only, brought this idea to economic feasibility in the form of integrated circuits.

The Planar Process

The techniques used to produce a planar epitaxial transistor and the diode counterpart are the same as those used to produce integrated circuits and it is convenient to discuss them together at this point. As was explained some time ago an epitaxial layer is one which has been produced on the surface of a silicon chip in such a way that its crystal structure is the same as that of the underlying layer or substrate. It is possible to produce an epitaxial layer of intrinsic p- or n-type material depending on the requirements.

An essential part of the process of producing devices by this method is that of masking the areas which are not to be affected by the various diffusion processes that are to take place. The method most commonly used is that of silicon dioxide masking. After a layer of epitaxial silicon has been grown on the surface of the crystal a layer of silicon dioxide (SiO_2) is produced over this either by an electrolytic oxidation (anodising) or by chemical deposition of silicon dioxide by oxidation of an organic silicon compound (tetraethyl orthosilicate). The uniform layer of silicon dioxide can then be etched with hydrofluoric acid to expose sites for later diffusion processing to take place. In order to locate the regions to be diffused, photolithographic techniques are used. A layer of photoresist is painted on to the slice, a suitable mask is used to protect the required pattern, and unexposed photoresist is removed to leave a mask which is resistant to hydrofluoric acid. Following this it is possible to etch the exposed regions to reveal the epitaxial layer into which dopant atoms can be diffused to produce the devices.

When producing a single silicon planar epitaxial diode it is only necessary to expose one region, although generally several hundred diodes are produced on a single wafer. If an n-type epitaxial layer has been grown then a diffusion of p-type impurity into the exposed region will produce a graded junction diode structure as seen in Fig. 1, where the various stages in the production of a single diode are shown in detail. In order to provide an ohmic contact to the n-type region it is necessary

to go through the processes of photolithography and etching once more in order to allow a heavy diffusion of n^+ -type dopant to provide a cathode contact. Finally, metallising is carried out to provide contact to the n^+ - and p-type regions, and leads are attached to these regions after the slices have been cut to separate the individual diodes. The current and voltage ratings of the devices depend as always on the geometry of the arrangement and on the doping levels used. A compromise between the speed, capacity and maximum rating of the devices has to be made in order to suit the individual requirements.

Advantages of the epitaxial planar process described are numerous. The devices are produced by diffusion from one side of the chip only, simplifying manufacturing techniques; the epitaxial layer has reproducible properties which are uniform across the surface of the wafer, and it is possible to produce high resistivity material in this way. Of course, not only diodes are produced in this manner; resistors, capacitors, transistors and field effect transistors can all be produced by the planar process.

Isolation in I.C.s

Integrated circuits usually include several of the different devices on the same chip. The problem which now arises is that of isolation of one device from another to avoid unwanted circuit interconnections. Two processes are commonly used to achieve this. First, the use of two back-to-back diodes can be conveniently obtained in integrated circuit form. Both diodes are arranged to be reverse

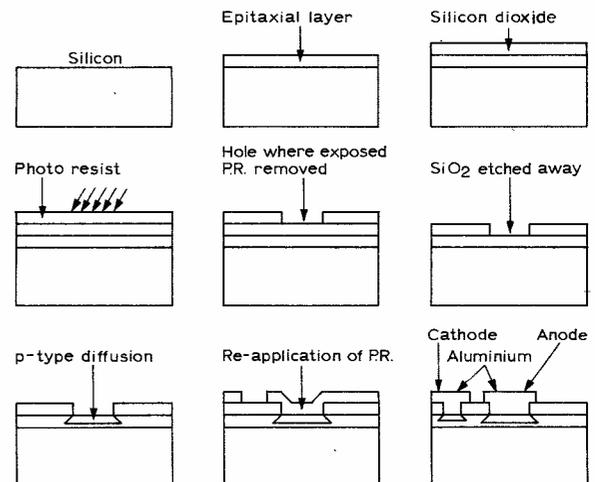


Fig. 1: Planar technology: the stages involved in the manufacture of an epitaxial planar diode.

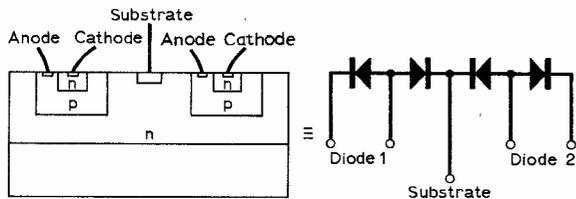


Fig. 2: Integrated circuit isolation achieved by means of back-to-back diodes.

biased all the time the circuit is in use. This reduces the coupling between the devices to that across a reverse biased diode, namely, several tens of megohms with a parallel capacitance of a few picofarads. Fig. 2 shows two diode structures in an integrated circuit together with this isolation arrangement. The diodes in this case are produced by double diffusion. In order to provide isolation with this arrangement the substrate has to be held more positive than any other point in the integrated circuit, and, of course, with a p-type substrate the substrate has to be made negative.

The second method is to produce isolated pockets of epitaxial material inside regions of polycrystalline material surrounded by thin layers of silicon dioxide. The method of achieving this is somewhat involved, but the important consideration is that the lifetime of the charge carriers in such polycrystalline material is very short. Hence the conductivity is very low so that good isolation is achieved. This method is not used so extensively in manufacturing because of the extra number of steps required in the process. Back-to-back diode isolation provides sufficient immunity to interference for the majority of applications.

Devices can be made in a similar way, not using an epitaxial layer but simply by carrying out diffusion into the surface of the substrate. These devices are called planar devices, sometimes abbreviated to just planar. They are also passivated with silicon dioxide in a similar way to that in which the planar epitaxial devices are treated, as described below.

Integrated Circuit Components

Capacitors are required in many circuits, but unfortunately they are difficult to fabricate in integrated circuit form. It is relatively easy to produce small value capacitors, as described in a previous article, using the capacitance of a reverse biased diode. In this way capacitors of up to 0.001 microfarad can be made. Larger values have to be obtained in other ways, either by use of external capacitors or by using electronic methods of multiplying the diode capacitance.

Another method of producing capacitors is by utilising the capacitance across the silicon dioxide layer. During the diffusion processes involved in making the integrated circuit a layer of high conductivity silicon is produced where the capacitor is required. Subsequently a layer of silicon dioxide is grown over this and finally a layer of metal is put on top to produce the second electrode. An advantage of this structure is that the capacitor produced is non-polar, that is it can be used with voltages applied in either direction.

The other passive element which can be fabricated using the diffusion process is the resistor. Since

very thin sheets of high resistivity epitaxial material are available it is possible to produce resistors simply by placing two contacts on to a suitably shaped region of the epitaxial layer. There are two ways a given resistor can be made. First, a long wide resistor can be used; secondly, a short thin resistor may be used. The choice depends on several factors including the accuracy required and the power which the resistor will have to dissipate. The important factor determining the resistance is the aspect ratio of the resistor, that is, of course, the ratio of the length to the width of the resistor. It is possible to produce resistors with values up to 20,000 ohms, but it is very difficult to make the value of the resistor exactly equal to the circuit requirements. To overcome this difficulty the circuit of an integrated unit is designed so that its operation depends not so much on the absolute value of each resistor but on their relative values. Thus, in bias chains a potential divider is used rather than a single series resistor. This is because the relative values are determined by the mask shape whereas the absolute values depend strongly on the characteristics of the epitaxial layer. It is practical to produce resistor values accurate to within 10%, but ratios can be obtained with an accuracy better than 2%.

It is not practical to use or produce inductors using integration techniques. Consequently if it is essential to use these components they have to be provided externally to the circuit. However, using active filter techniques it is possible to dispense with the inductor in many circuit arrangements. In this way it is possible to produce filter circuits using only resistors and capacitors and yet attain very high Q values.

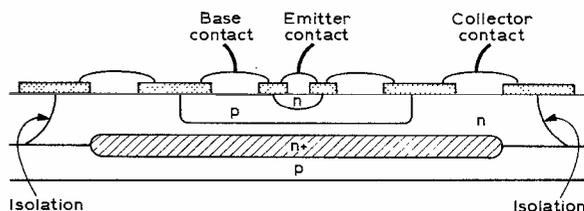


Fig. 3: Construction of an integrated circuit planar epitaxial transistor.

Bipolar transistors are produced in integrated circuits by multiple diffusion techniques. For instance, an n-p-n silicon epitaxial transistor, as shown in Fig. 3, could be produced in an integrated circuit by the following processes common to all diffusion device production. A layer of epitaxial n-type silicon is grown over a clean p-type silicon wafer. This epitaxial layer later becomes the collector of the transistor and because of this it has a high resistivity or low impurity concentration. After suitable oxide masking, photolithography and etching, a p-type diffusion is carried out to produce the base region and also in integrated circuits to produce the isolation region previously described. During the diffusion an oxide layer is regrown over the exposed region. Subsequently this is re-etched in the position of the emitter and an n-type diffusion is carried out to produce a low resistivity emitter with the resultant high injection efficiency. Finally a layer of silicon dioxide is grown over the device completely in order to passivate it against atmospheric contamination, and small areas are

INCREASE YOUR KNOWLEDGE



Established 1891


MANY COURSES TO CHOOSE FROM incl.
RADIO & TV ENGINEERING & SERVICING,
TRANSISTOR & PRINTED CIRCUIT SERVICING,
CLOSED CIRCUIT TV, ELECTRONICS,
NUMERICAL CONTROL ELECTRONICS,
TELEMETRY TECHNIQUES, CONTROL SYSTEMS,
ELECTRONICS FOR AUTOMATION,
COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

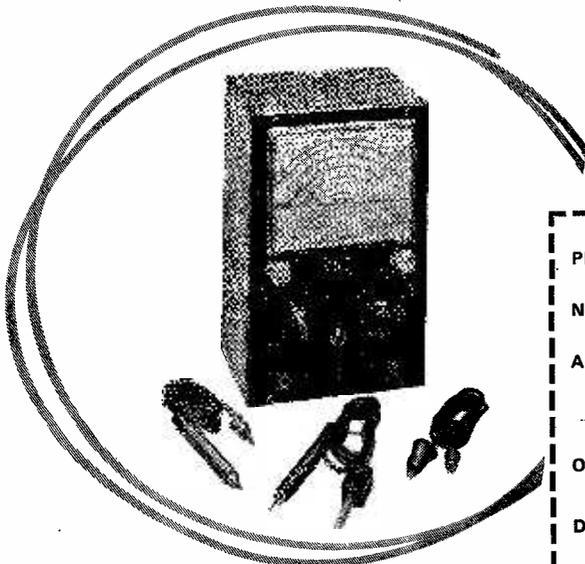C. & G. Telecommunication Technicians' Certs
C. & G. Electronic Servicing
R.T.E.B. Radio/TV Servicing Certificate
P.M.G. Certificates in Radiotelegraphy
Radio Amateurs' Examination
General Certificate of Education, etc

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments, incl. professional-type valve volt meter (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME


ADDRESS

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEXT HOUSE, PARKGATE ROAD, London, SW11
2/70

DISCOSOUND

NEW DISCOSOUND PRE-4

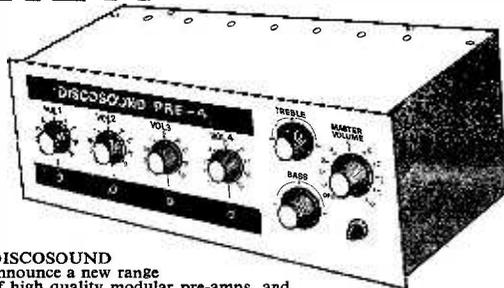

DISCOSOUND announce a new range of high quality modular pre-amps, and main amplifiers which offer a wide range of facilities to suit all types of applications.

Model Pre-4. This is a four channel fully mixable pre-amp, with separate treble, bass and master volume controls, and is completely self powered. All four inputs are by standard jack socket on the front panel with the addition of inputs 3 and 4 being duplicated on the back panel, with two paralleled outputs also featured for versatility in use.

Specification:

Inputs.	Vol. 1.	10 mv at 50k Ohms	} Other Impedances can be made to special order.
	Vol. 2.	10 mv at 50k Ohms	
	Vol. 3.	50 mv at 500k Ohms	
	Vol. 4.	50 mv at 500k Ohms	

Frequency Response: 30—20,000 HZ \pm 3db.

Signal/Noise Ratio: -65db.

Treble: continuously variable 20db. at 100 HZ.

Bass: continuously variable 20db. at 10 KHZ.

Output: variable up to 1 volt RMS at 25k Ohms.

Size: front panel 12½ × 5½ cut out required 11½ × 4½.

Completely built and tested.

PRICE £18.0.0 inc. P. & P.

NEW DISCOSOUND 70 MAIN AMPLIFIER

This is a 70 watts RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features, full automatic overload protection against short or open circuits. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound PRE-4, or can be used with any other high quality pre-amp control unit.

Specification:

Power Output: 70 watts RMS into 8 Ohms.

Frequency response: 20—20,000 Hz \pm 2db.

Harmonic distortion: less than 0.5% at 70 watts RMS.


Input Impedance and Sensitivity: 700 mv at 20-30k Ohms.

Size: 7" × 9" × 6".

Completely built and tested on steel Chassis.

PRICE £30.0.0 inc. P. & P.

DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

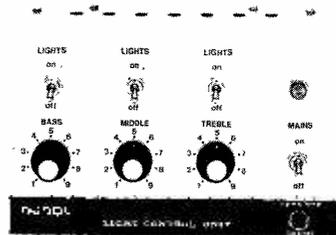

3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation.

Completely built and tested.

PRICE £37.10.0 inc. P. & P.

NEW RANGE OF COMPLETELY BUILT & TESTED MODULES USING P.C. BOARDS. FIRST GRADE COMPONENTS AND SILICON TRANSISTORS THROUGHOUT

Model 106F. 4 channel mixer with separate bass and treble controls. Complete with pots, connecting diagram, etc. Power requirements 18 volts D.C.

Specification:

Vol. 1.	10 mv at 50k Ohms	} Other Impedances can be made to order.
Vol. 2.	10 mv at 50k Ohms	
Vol. 3.	50 mv at 500k Ohms	
Vol. 4.	50 mv at 500k Ohms	

Frequency: 30—2,000 Hz \pm 3db.

Signal/Noise: -65db.

Output: variable up to 1 volt RMS.

PRICE £7.0.0 inc. P. & P.

Model 100SP. 2 channel mixer with separate bass, treble and master volume controls. Fibre-glass P.C. board complete with pots, connecting diagrams etc. Power requirements 18 volts D.C.

Specification:

Vol. 1/2 can be from 50k upwards. Please state requirements. All other details as 106F.

PRICE £5.0.0 inc. P. & P.

For full details of these and all Discosound Products write direct to:—

DISCOSOUND, 170 ALBION ROAD, LONDON, N.16. Tel: 01-254 5779

Full money back guarantee if returned within 10 days.

All Discosound Products are guaranteed for 12 months.

Demonstrations given at any time.

etched away to allow metallising of the required external contacts.

One point not yet mentioned is the presence of the n^+ region in the collector layer. This is provided to give a uniform field across the collector to base junction, effectively lowering the collector output impedance.

Logic and Linear I.C.s

It should now be apparent that most semiconductor devices can be produced in integrated circuit form and thus circuits of high complexity can be produced on a single chip of silicon. The procedures involved in producing optimisation of the manufacturing techniques for a given circuit are very involved, but in most cases it is possible to arrange that an integrated circuit will perform the desired function as well as its discrete component counterpart.

There are basically two types of integrated circuit available and these can conveniently be classified as "logic" and "linear" circuits. The difference between the two classes is that the logic circuits are used in applications where they are required to give yes/no types of output, whereas linear circuits are expected to give an output which has some continuous relationship with the input signal. In this context linear is used somewhat inappropriately as it in fact covers circuits with feedback which results in their output varying with the input signal but in a far from linear manner.

Types of Logic Circuit

The logic circuits are of very varied type. The first solid state logic circuits made were combinations of resistors and diodes and they performed numerous gating functions. Fig. 4 shows an "and" gate using these elements. If A and B are at the +5V level then C will also be at the +5V level, otherwise C will be at the zero level. Notice that if A and B are open circuit C assumes the high state.

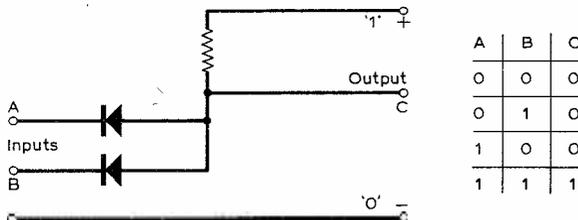


Fig. 4: Simple diode-resistor logical AND gate with corresponding truth table.

Following on from this start there have evolved Resistor Transistor Logic (RTL), Diode Transistor Logic (DTL), Transistor Transistor Logic (TTL), Emitter Coupled Logic (ECL), Emitter Emitter Coupled Logic (E^2 CL) and MOST logic circuits. Each of these types has its own advantages as seen in the following examples. RTL has a medium speed of operation which means that when a logical switch is made to the input the output follows this change within about 20 nanosec and the circuit also has a fairly low power consumption, each gate taking about 10mW. DTL is somewhat faster than RTL, especially when the nonsaturating type of logic is used so that all the transistors are in the active state rather than being either fully on or off. TTL

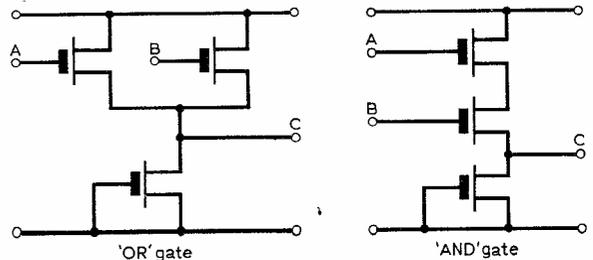


Fig. 5: MOST logic gates.

has a very long propagation delay. Emitter coupled logic has a very short propagation delay but has a large dissipation per gate. E^2 CL is mainly used in the central processors of computers; it has an even shorter delay, typically one or two nano-seconds.

The final arrangement considered here is the MOST logic circuit which consists of arrays of MOS transistors. A MOST logical "and" and "or" gate are shown in Fig. 5. The advantage of this circuit type is that it is relatively cheap to make in highly complex arrangements as no isolation is required between the elements. They are slow but happily consume very little power.

Thus, there is a trade off between the speed of operation of the logical element and the power dissipation per gate. This is an important criterion for the circuit designer and the ideal system would use a combination of the different types to achieve maximum efficiency.

The final article in this series will describe the different linear circuits which are available and also the principles underlying thick and thin film circuit manufacture.

TO BE CONTINUED

PRACTICAL TELEVISION

in the FEBRUARY issue

★ CAPACITOR TESTER

Specially designed for the service engineer, providing clear and rapid readings of capacitance values, leakage conditions if any and changes in capacitance and leakage with applied voltage.

★ LINE OUTPUT STAGE TUNING

If you've ever wondered just why the line output stage is tuned to the third harmonic of the fundamental frequency, this aspect of line output stage mystique is fully explained.

★ LUMINANCE STAGES

A detailed look at the luminance circuitry used in colour receivers, including grey-scale tracking, beam limiting, flyback suppression and so on.

★ TV RECEIVER SERVICING

Servicing the Philips 210 series dual-standard hybrid chassis.

PLUS ALL THE REGULAR FEATURES on sale

JANUARY 23rd

LETTERS

The Editor does not necessarily endorse the views expressed by correspondents

Air wave wasters

Recently I have heard a large amount of discussion on the BBC World Service on Commercial Radio in Great Britain. As you probably know, Australia has had commercial radio ever since broadcasting began. I think therefore that I am qualified to pass judgement on these nuisances and air-wave wasters.

I listen to many commercial radio stations in Australia and can state that what I have heard has been nothing but a programme format of continuous pop, high-powered advertisements rapped down the listener's throat and news that is often inaccurate. The number of advertisements is fantastic. For instance, in one quarter-hour on the local radio station up here (8DN-1240kHz) there was *one-half* of a gramophone record played (a latest pop of course) and all the rest of the time was taken up with advertisements.

I think therefore, that these air-wave wasters should be banned from cluttering up the air-waves and government radio should be developed to the point of having a service not unlike the BBC.
Terry Robinson (*Darwin, Australia*).

A few memories

As a reader of your excellent magazine for more years than I care to recall, together with some of its early contemporaries which did not make the grade, your editorial article of issue 751 September 1969, encouraged me to write to you for the first time.

Needless to say I heartily applaud the sentiment of your article, we do with the advent of the i.c. have chance once again to rationalise, human nature being what it is, however, I wonder if the nettle will be grasped?

Whilst pondering on this matter and the extent to which the art of radio construction has changed my mind went back to the halcyon days of the spaghetti resistance, Lewcos coils, Telsen, dutch R. valves, and all the last word gadgetry which was per-

petrated upon the somewhat bewildered constructor even in those early days. I feel certain that some of your more senior readers must recall the "Magic" indoor aerials, the Loewe valves, and even then the attempts at integrated circuitry, I seem to recall that one could purchase a large black box which contained a transformer coupled amplifier, and which had three valve holders mounted upon its top, all one required was the ability to wire up an H. F. section and Voila! a wireless set.

In my opinion the period from the early twenties up to the late thirties was a fascinating one in the development of radio, and I write to ask if it would be possible for a series of articles with pictures and circuitry of constructional projects of the period could be printed, even small articles of the period would I feel raise a smile, and probably the wry comment that little is really new under the sun.

In closing I should like to do something that I have intended to do for so many years, that is to thank you for a very well produced magazine which has remained a real constructors magazine for so long. Long may you flourish.
R. C. Armet (*Transvaal, Republic of South Africa*).

[I would like to hear from readers who would like to see reprints of parts of 1920-1930 articles.]—Editor

Ban the speaker!

Nowadays one reads of semiconductor devices being used to produce coherent light, etc. but nowhere can I find any reference to their being used to produce sound. This surprises me as I remember witnessing this phenomenon in 1964 whilst playing around with a set of transistors. (These transistors came boxed in a set and were, I believe, of Italian manufacture. They were encased in black-painted metal cans.)

I had built a crystal set at this time and was using the transistors to amplify the signal sufficiently to feed a loudspeaker. Being a

newcomer to electronics at this time and entirely ignorant of circuitry I remember that in the three transistor amplifier lash-up I employed a separate battery for each transistor! Unorthodox as this procedure was, it worked well and to my great delight the strains of music obligingly came blasting out of the speaker! On removing the speaker, however, to make some adjustment or other, I noticed that I could still hear the music! The volume was not as high as with the speaker connected but was still at a comfortable level. My first thought was that the sounds were emanating from the speaker transformer core (a large, ex-TV item) but this was not the case. The sound source was the transistors themselves. I cannot now recall if one or all of the transistors were "sounding-off," but at least one of them was. I believe the actual sound came from the transistor cans which, as mentioned above, were metal and rang when "pinged" with a finger nail, but what caused them to vibrate I have never been able to ascertain.

I should be extremely grateful if any of your readers can collaborate this phenomenon or offer any explanation as to how it could have occurred.—**J. B. Jobe** (*Worcester*).

Marconi station

I thought that some history of the above station might be of interest to readers. It was opened in 1910 and was an outstanding landmark round these parts. It could be seen for many miles with its 400ft. aerials standing along the slopes of Cafn Dee mountain near Caernarvon.

With the advance of modern developments the old station went out of commission in 1939 and the aerials were pulled down.

During the First World War, the first wireless transmission ever sent to Australia from this country was transmitted from this station by Lloyd George to Hughes, another Welshman who was Prime Minister of Australia at the time.—**H. Roberts** (*Caernarvon, N. Wales*).

CODAR CR.70A

Communications Receiver 540-10 metres




The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £21 the CR.70A is outstanding value for money. In four stable ranges, the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the short wave and international amateur bands up to and including 10 metres, where the rapidly improving conditions that now prevail allow the regular reception of world-wide call-signs!

The CR.70A has a high 'Q' aerial input stage using exclusive CODAR COIL air space inductor. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt AC mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5½" x 7½" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months! New model has separate direct output socket for feeding tape recorder, Hi-Fi equipment, etc.


20 gns.

Carriage 7/6 extra

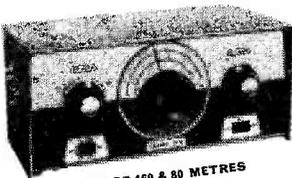
- *Ideal for SWLs
- *5 valves (inc. two twin triodes) giving 7 valve line-up
- *Excellent on amateur and shipping frequencies
- *Calibrated signal strength meter (illuminated)
- *Automatic volume control
- *Separate B.F. oscillator for morse and S.S.B. signals
- *Two speed vernier tuning
- *Separate output for recording etc.



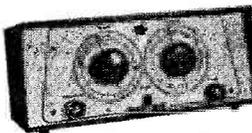
T23 RECEIVER FOR 150 & 80 METRES AMATEUR BANDS
 Transistors, bandspread 1.8-2Mc/s and 3.5-9 Mc/s 12 volts, only 8" x 4" x 3". Ideal portable, mobile or home receiver. Efficient BFO, printed circuits. ONLY £15.17.6. Carr. 4/6.



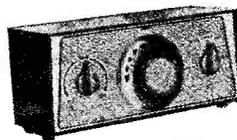CR45 MAINS T.R.F. SHORT-WAVE RECEIVER
 World wide reception. *Separate electrical hand-receiver. *3 slow motion drives. *Output 3 watts spread. *3 valves ECC81, EL84, EZ80. For 2/3 ohm speaker. *Valves ECC81, EL84, EZ80. Size 12" x 9" x 7". CODAR-KIT CR.45K with 3 coils (10-26, 28-75, 60-176 metres). £9.15.0. Carr. 6/-, or ready built CR.45 £11.19.6. Carr. 6/-, Extra coils 5/4 each.



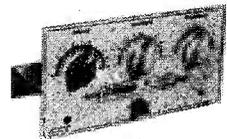R.F. PRE-SELECTOR MODEL P.R.30
 1.5-30Mc/s
 Provides up to 20dB gain plus substantial image rejection. Improved signal/noise ratio and selectivity. Power requirements 100-250 volts 12mA H.T. 6.3 volts, .3 amp L.T. Size 8½" x 5" x 4". Ready built complete with cables, plugs and instructions £5.19.6. Carr. 4/6. Self-powered P.R.30X £7.19.6. Carr. 4/6.



MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER
 *Can be built in one evening. *Complete with valve, one coil 25-75 metres and 4 page instruction manual. Price £2.9.0. Carr. 3/-. Extra coils 5/4.

CRC

CODAR RADIO COMPANY
 UNIT 1, MEADOW ROAD, INDUSTRIAL ESTATE,
 EAST WORTHING, SUSSEX. WORTHING 37315

World-wide Mail Order Service

Please supply (tick as required)
 I enclose cheque/ M.O./P.O. value of £.....
 8d stamp enclosed for leaflets

NAME _____

ADDRESS _____

POST ORDER FORM TODAY

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	5/7
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	6/-
Rod Aerial	RA2W		12/6
Driver Transformer	LFDT4/1		9/6
Output Transformer	OPT1		10/6
Printed Circuit	PCA1		9/6

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	7/6
T41/2E	2nd I.F. Transformer	7/6
T41/3T	3rd I.F. Transformer	10/6
T41/3T	B.F.O. Coil	10/6

Details of these and our other components are given in an illustrated folder which will be supplied on request with 4d. postage please.

WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.
—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers

Tel. 769-0199/1649

LA7 7/9	6BQ7A 7/-	6K7M 8/6	7Y4 3/6	20P5 20/-	80 7/6	DF96 7/6	ECF82 6/6	EM80 7/6	PC97 8/8	RG5/50080/-	UF89 7/6
LD5 7/6	6BR7 12/6	6K7G 4/6	7C4 2/6	25A5 5/9	85A2 7/6	DF77 4/8	ECH21 12/6	EM81 8/8	PCC84 6/6	S130 40/-	UL41 12/-
1BE5 7/-	6BR8 12/6	6K8 2/9	7D1 12/6	25B4 7/6	150C4 3/8	DK91 6/-	ECH42 12/6	EM82 7/6	PCC89 10/6	SP4 8/-	UL64 7/-
ILD5 6/-	6BS7 25/-	6K8 2/9	7D2 12/6	25Y5 6/-	150C4 3/8	DK91 6/-	ECH42 12/6	EM83 8/6	PC189 10/6	SP41 5/6	UM80 5/6
IN5GT 8/-	6BW6 14/6	6K8M 11/6	7D1 14/9	25Z4 6/3	801 9/6	DK92 9/-	ECH81 5/9	EY51 8/-	PCF80 6/6	SP61 5/-	UU6 21/-
IR5 6/-	6BW7 13/-	6K8G 3/-	7D2 18/-	25Z5 8/-	807 9/-	DK96 7/9	ECH83 8/6	EY56 7/9	PCF82 6/6	STV280/80	UU7 21/-
1R4 5/6	6C4 5/-	6K8GT 7/-	7D3 10/6	25Z6 8/6	813USA 120/-	DL66 25/-	ECL80 5/9	EZ35 6/-	PCF84 8/-	ST25 95/-	UU8 21/-
1R5 4/6	6C5G 5/-	6K25 15/-	7D4 8/-	25Z7 8/6	813USA 120/-	DL66 25/-	ECL82 7/-	EZ41 9/6	PCF86 9/-	ST2150 12/6	UU9 8/3
3A4 4/-	6C6 3/9	6L1 12/-	7D5 8/-	30C1 6/9	813 75/-	DL92 6/3	ECL83 10/3	EZ80 5/6	PCF801 9/6	STV280/80	UU9 8/3
3A4 4/-	6C6G 6/-	6L6G 7/9	7D6 12/6	30C1 6/9	813 75/-	DL94 6/9	ECL86 9/-	EZ81 5/6	PCF802 9/6	T41 17/6	UY4 8/6
3Q4 7/9	6CD6G 24/-	6L18 6/-	7D7 12/6	30C17 18/-	954 5/3	DL95 7/9	ECL86 9/-	EZ81 5/6	PCF805 15/-	TDD4 8/6	UY5 8/5
3Q5 7/-	6CH6 7/6	6Q7G 6/-	7D8 7/6	30C18 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/-	U10 7/6	VMP44 17/6
3Q4 6/3	6CW4 12/-	6Q7GT 8/6	7D9 7/6	30C18 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF805 15/6	U14 7/6	VP4B 25/-
3V4 6/9	6E5 7/6	6SCT 7/-	7E1 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
5R4GY 10/6	6E1 12/6	6SCT 7/-	7E2 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
5U4G 5/6	6E5G 8/-	6SCT 7/-	7E3 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
5V4G 8/-	6E5G 8/-	6SCT 7/-	7E4 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
5Y3GT 6/-	6E5G 8/-	6SCT 7/-	7E5 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
5Z4G 7/-	6E11 6/6	6SLTGT 6/-	7E6 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6/90L2 15/-	6E13 6/6	6SN7GT 5/6	7E7 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6A7 15/-	6E14 12/6	6SQ7 7/6	7E8 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6ASG 12/6	6E23 18/-	6U4GT 18/-	7E9 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AC7 4/-	6E24 14/-	6U5G 7/6	7F0 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AK5 5/-	6E25 15/-	6V6M 12/-	7F1 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AM5 4/6	6E28 14/-	6V6G 4/6	7F2 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AM6 3/6	6E32 2/9	6V6GT 6/6	7F3 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AQ5 6/3	6E36 2/6	6X4 4/8	7F4 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AS7G 16/-	6H6 3/-	6X5G 4/8	7F5 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AM6 3/6	6J5M 9/-	6X5GT 6/-	7F6 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AT6 4/9	6J5G 4/-	7B6 11/8	7F7 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6AU6 5/6	6J5GT 5/6	7B7 7/6	7F8 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6B4G 20/-	6J6 3/6	7C5 22/6	7F9 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6B8G 2/-	6J7M 8/6	7C6 15/-	7F10 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6BA5 5/6	6J7G 6/-	7D5 8/-	7F11 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6BE6 5/6	6J7GT 7/6	7D7 6/8	7F12 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6BH6 8/-	6K6GT 5/-	7E7 13/-	7F13 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30
6B76 9/-	6K7 1/9	7E7 45/-	7F14 20/-	30C19 15/-	1625 6/6	DL96 7/9	ECL86 9/-	EZ81 5/6	PCF806 13/6	U19 35/-	VR105/30

Manufacturers and Export Inquiries Welcome
OBsolete TYPES A SPECIALITY
 QUOTATIONS FOR ANY VALVE NOT LISTED
 Express postage 9d. per valve.
 Ordinary postage 6d. per valve. C.W.O. No C.O.D.
 Tube postage 7/6 each

TUBES

14 inch	..	24 0 0
17 inch	..	24 5 0
19 inch	..	28 0 0
21 inch	..	26 10 0
23 inch	..	212 0 0
27 inch	..	28 0 0

SETS OF VALVES
 DAF91, DF91, DK91, DL92 or DL94 .. 19/- plus postage
 DAF96, DF96, DK96, DL96 .. 27/6 plus postage

TRANSISTORS

AC127 5/-	OC25 8/-	OC71 2/6	OC81 4/-	OC82D 6/-
AF114 5/-	OC28 8/-	OC72 6/-	OC81D 4/-	OC83 6/-
AF115 5/-	OC35 8/-	OC75 6/-	OC81DM 4/-	OC170 7/-
AF116 5/-	OC44 8/-	OC76 6/-	OC82 6/-	OC71 6/-
AF117 5/-	OC45 2/6	OC77 8/-	OC82 6/-	OC200 7/6

SEND S.A.E. FOR LIST OF 2,000 TYPES

P.W. GUIDE TO COMPONENTS

PART 14

M. K. TITMAN, B.Sc. (Eng)

Field Effect Transistors

There are two basic forms of construction used in the manufacture of field effect transistors (f.e.t.s). The resulting devices are known as junction f.e.t.s and insulated gate f.e.t.s. It will be convenient to examine each type separately.

Junction f.e.t.

The junction f.e.t. is a device utilising a single p-n junction with a structure very similar to the unijunction transistor which is a related device. The basic structure is illustrated in Fig. 12 and consists of a bar of n-type

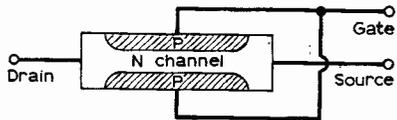


Fig. 12: Basic structure of a junction F.E.T.

semiconductor, usually silicon, with a p-type region on either side of the bar. The n-type portion between the p-type regions is called the channel and current flows through the channel from drain to source. Now if the diode formed between the p-type region, termed the gate, and the source is reverse biased by a negative potential on the gate, an electric field is set up in the channel which restricts the current flow through it. If the voltage is sufficiently negative all current flow is inhibited through the channel. The bias voltage for zero current is called the pinch off voltage (V_p).

The operation of an f.e.t. depends on an input through a reverse-biased diode and therefore the f.e.t. characteristically has a very high input impedance ($\sim 10M\Omega$). As with other semiconductor devices p-type and n-type materials can be reversed to give a p-channel f.e.t. with an n-type gate, and in this case the potential on the gate is reversed. The symbols for n-channel and p-channel f.e.t.s are shown in Fig. 13 together with the biasing voltages for normal operation. It should be remembered that the arrow direction indicates the diode forward current direction and hence potentials are such as to reverse bias the diode.

At this point most of us with valve experience will

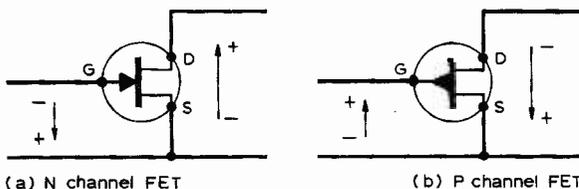


Fig. 13: B.S. preferred symbols and applied polarities for junction F.E.T.'s.

have noted the similarity between valves and f.e.t.s. In fact the n-channel f.e.t., which is by far the most commonly available f.e.t., is strikingly similar both in voltage polarities, as shown in Fig. 14, and characteristics, shown in Fig. 15. Unlike the valve however the maximum drain to source voltage is limited by breakdown characteristics, whilst f.e.t. transconductance ($\frac{I_{DS}}{V_{GS}} \approx gm$) varies with bias voltage (V_{GS}) and is a maximum at $V_{GS}=0$. The transconductance is more linear than for conventional transistors.

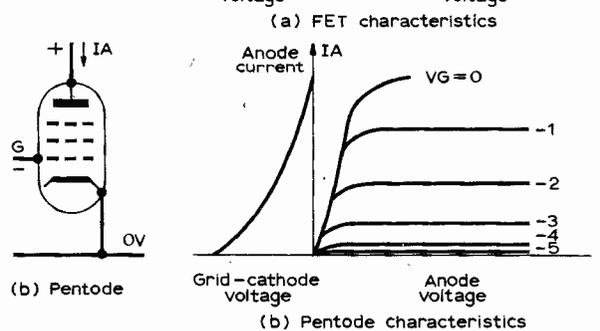
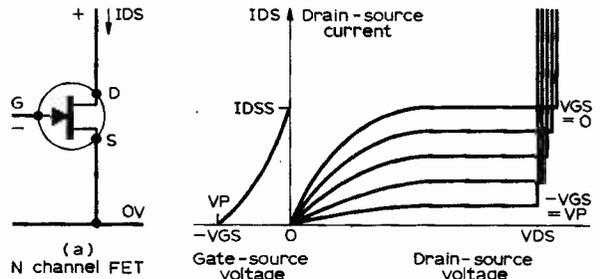


Fig. 14: (left) Comparison of F.E.T. and pentode symbols. Fig. 15: (right) Comparison of F.E.T. and pentode characteristics.

Manufacturer's parameters for f.e.t.s usually include the items shown in Table 2, which also includes typical ranges of values for n-channel devices. Other parameters include maximum reverse transfer capacitance at 0.5-10pF and noise figures between 1-5dB. These are usually only important for critical applications.

Field effect transistors are used for many applications including microphone preamplifiers, d.c. differential amplifiers, r.f. amplifiers in v.h.f. radio circuits, switching circuits and instrument input amplifiers. At present they are used in circuits which particularly require the special features of low noise levels and high input impedance. The extremely low drift currents of $1pA$ ($10^{-12}A$) per $^{\circ}C$ and high input impedances make them particularly suitable for use in input and buffer circuits.

Table 2: Typical f.e.t. parameters

Parameter	Symbol	Typical values
Max. gate-source voltage	V _{gso}	20-50V
Max. drain-source voltage	V _{ds}	20-100V
Drain-source current at V _{gs} =0	I _{dss}	0.5-100mA
Max. pinch off voltage V _{gs} =V _p	V(p) _{gs} V _{gs(off)}	2-10V
Max. gate current	I _{gss}	0.1-10nA
Transconductance	g _m	0.25-30mA/V

Typical input characteristics of an f.e.t. preamplifier are Z_{in}>1MΩ, C_{in}>10pF, noise voltage <0.5mV and bandwidth >100MHz.

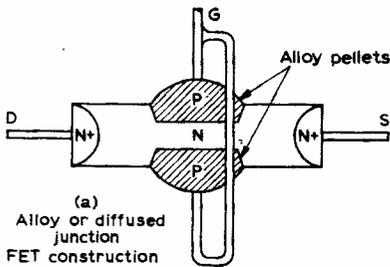


Fig. 16a: Alloy or diffused junction F.E.T. construction.

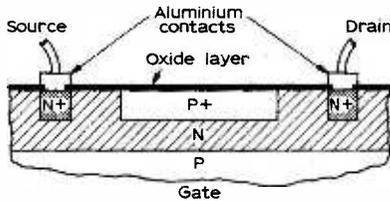


Fig. 16b: Planar junction F.E.T. construction.

Figure 16 illustrates the two basic forms of junction f.e.t. construction which are used at present. The alloy construction of Fig. 16(a) is still the most common where p-type pellets are alloyed to either side of an n-type slice. The geometrical outline is also used for diffused junction f.e.t.s. As with conventional transistors planar construction, using the more accurate photographic techniques, is used increasingly in close tolerance f.e.t. manufacture, and this form of construction is illustrated in Fig. 16(b).

A special form of construction used to obtain good high frequency characteristics is illustrated in Fig. 17 and this device is known as a tectron. Indium is deposited on the surface of an n-type slice etched to receive the plating. The result is a thin channel region of small area giving low capacitance and therefore good high frequency characteristics. The structure is however electrically and thermally less robust and is at present rather uncommon.

As with conventional transistors the encapsulation of

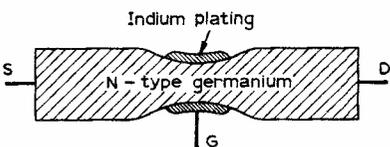


Fig. 17: Tectron construction.

f.e.t.s is mainly of the popular TO-18 or TO-5 types. A plastic encapsulation is shown in Fig. 18 but as the lead out connections are still unstandardised the precise terminal designations should be obtained from the manufacturer.

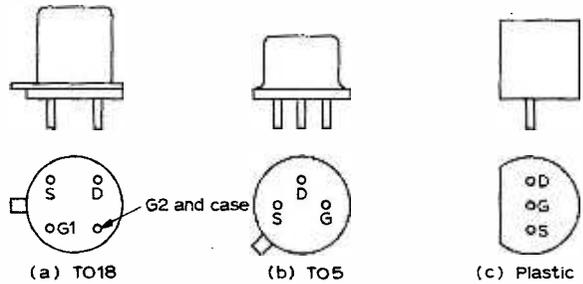


Fig. 18: F.E.T. encapsulations.

We have now examined the junction field effect transistor and should consider the second basic form of construction known as insulated gate f.e.t. It is interesting to note that it was experiments with crude constructions to obtain the insulated gate f.e.t., or unipolar transistor as it was then known, that led to the discovery by Shockley of the conventional or bipolar transistor. The insulated gate f.e.t. was therefore a forerunner of the modern transistor but it is only with the discovery of planar epitaxial techniques that the insulated gate or metal-oxide semiconductor (m.o.s.) transistor has been a practical proposition in terms of noise and gain.

Insulated Gate f.e.t. or Metal-Oxide Semiconductor Transistor (m.o.s.t.)

Metal-oxide semiconductor transistors (m.o.s.t.s) are constructed with p- or n-type semiconductor channels. In place of the reverse biased p-n junction which provides the controlling electric field, the field is formed through an extremely thin insulated junction. The insulation is provided by a silicon dioxide layer which acts as an efficient insulator. The basic form of construction is similar to that shown in Fig. 12 for a junction f.e.t. except that the junction is formed between a metal connection and the p- or n-type channel. The insulation is silicon dioxide thermally grown by passing steam over the basic chip. The basic symbol for a m.o.s.t. is shown in Fig. 19.


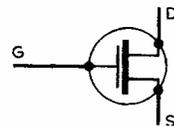


Fig. 19: Insulated gate (or M.O.S.T.) symbol.


The m.o.s.t. has properties which are peculiar to insulated gate structures. Two basic modes of action are possible. Firstly the depletion mode in which current normally flows through the channel but is reduced by channel width depletion until zero current flows at maximum gate voltage. The second mode of operation is known as the enhancement mode and in this mode the device is normally off but is turned on up to saturation point by increasing gate potentials. The enhancement mode is achieved by altering the end connections and type of channel material so that the path between the drain and source appears as back-to-back diodes and the gate potential increasingly reduces the blocking effect. It is clear from this that all junction f.e.t.s belong to the depletion mode of operation since the gate p-n junctions must be reverse biased.

—continued on page 806

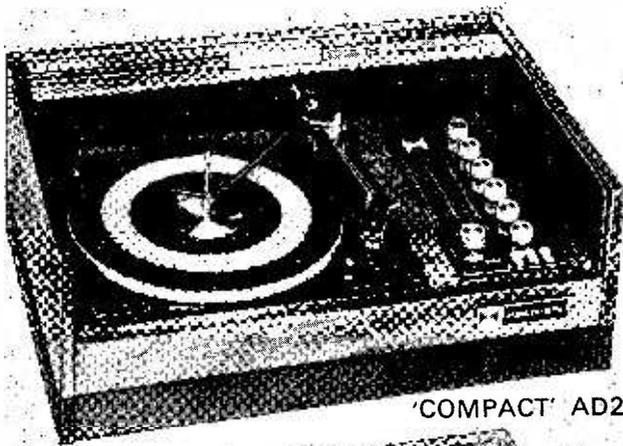
Heathkit for the new "Compact" Sound of the 70's



'COMPACT' AD27

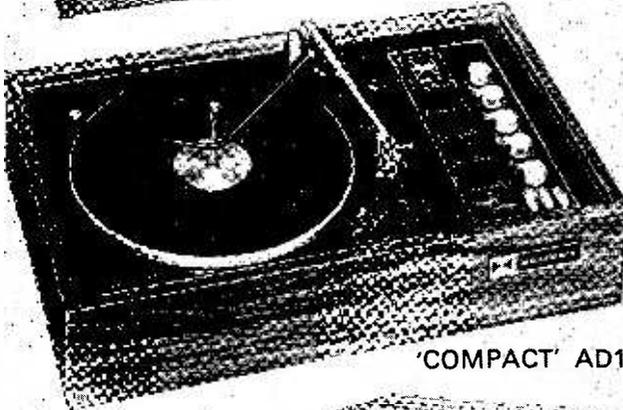

'COMPACT' AD17

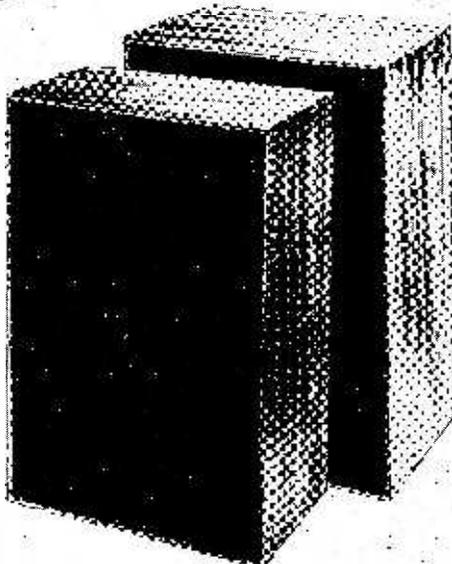

AMBASSADOR SPEAKERS

The fabulous stereo "Compacts" Models AD-17 and AD-27 are setting the pace in hi-fi for the 1970's. They offer outstanding value and performance. The AD-17 comprises a BSR MA-65 turntable/Shure M44-MB magnetic cartridge and a 10 watt (RMS) per channel stereo amplifier all mounted on a Teak or Walnut plinth.

Kit Price £54. Carr. 13/-

The AD-27 is similar but uses the MA-70 turntable and includes an FM stereo tuner. In this case the "plinth" is better described as a small cabinet. It has the additional features of a "Roller Shutter" lid and is available in Teak or Walnut.

Kit Price £82. Carr 13/-

Heathkit offer many excellent loudspeaker systems the new "Ambassador" Hi-Fi loudspeaker is winning many friends. Its cabinet is supplied ready assembled and finished in selected Teak or Walnut veneers to harmonise with other current Heathkit hi-fi equipment. It uses three loudspeaker units a 12in. bass, 5in. mid range and a 1in. Dome Pressure Tweeter.

Kit Price £29.16.0 Carr. 15/-

The complete Heathkit hi-fi range of stereo amplifiers, tuner/amplifiers, FM tuners, Stereo "Compacts", loudspeaker systems and ancilliary hi-fi equipment are all described and illustrated, many in full colour. In a wonderful free catalogue.

**Send for the
FREE Catalogue
and see for
yourself . . .
Today !**

TO DAYSTROM LTD., GLOUCESTER, GL2-6EE

Please rush me details of the latest Heathkit Hi-Fi Models

NAME.....

ADDRESS.....

51/2A



DAYSTROM LTD
GLOUCESTER
GL2-6EE

COMET Hi-Fi DISCOUNT WAREHOUSE

- ALL ITEMS OFFERED ARE FULLY GUARANTEED AND BACKED BY COMET.
- OPEN TO THE PUBLIC 9 to 5.30 p.m. daily (8 p.m. Wed., Thurs. and Friday evenings) and 5 p.m. Saturdays.
- COMPLETE FREE PRICE LIST CONTAINING OVER 800 ITEMS ON REQUEST.

	Rec. Retail Price	Comet Price
AMPLIFIERS		
ARENA 210 Amplifier ..	£34 13 0	£28 0 0
ARMSTRONG 521 25 watts per channel ..	£52 0 0	£44 0 0
DULCI 207 Stereo Amplifier ..	£25 0 0	£17 0 0
DULCI 207M Stereo Amplifier takes magnetic P/U ..	£30 0 0	£20 19 6
GOODMANS Maxamp ..	£54 0 0	£41 19 6
New LEAK Stereo 30 Plus ..	£53 0 0	£43 19 6
New LEAK Stereo 30 Plus in teak case ..	£59 10 0	£47 19 6
New LEAK Stereo 70 ..	£63 0 0	£49 19 6
LEAK Stereo 70 in teak case ..	£69 10 0	£56 4 6
New LEAK Stereo 70 Plus in teak case ..	£69 10 0	£54 19 6
LINEAR LT.66 Stereo Amplifier ..	£18 18 0	£13 19 6
QUAD 33 Pre-amplifier ..	£43 0 0	£35 19 6
QUAD 303 Stereo Main Amplifier ..	£55 0 0	£46 19 6
ROGERS Ravensbourne 50 watt Stereo ..	£59 10 0	£48 19 6
ROGERS Ravensbourne in teak case ..	£64 0 0	£52 13 6
ROGERS Ravensbrook ..	£44 0 0	£36 19 6
ROGERS Ravensbrook in Teak Case ..	£49 0 0	£38 19 6
TELETON 203E ..	£28 7 6	£20 15 6
TRUVOX TSA.200 ..	£54 12 0	£39 19 6
TUNERS		
ARENA 211 Stereo with decoder ..	£39 10 0	£33 19 6
ARMSTRONG 523 FM ..	£52 9 0	£44 19 6
ARMSTRONG 524 FM ..	£40 4 6	£34 19 6
ARMSTRONG M8 Stereo decoder ..	£9 10 0	£7 19 6
DULCI FMT.7 FM ..	£22 1 0	£17 19 6
DULCI FMT.7S FM Stereo Tuner ..	£31 0 0	£25 5 0
GOODMANS Stereomax AM/FM Stereo Tuner ..	£82 10 5	£71 19 6
LEAK Troughline Tuner with multiplex ..	£51 10 6	£39 19 6
LEAK Stereofetic Chassis form ..	£56 11 0	£45 19 0
LEAK Stereofetic in teak case ..	£64 14 4	£52 19 6
QUAD Stereo FM ..	£51 0 0	£44 19 6
ROGERS Cadet Mark III Tuner ..	£20 12 6	£17 13 0
ROGERS Ravensbourne Tuner with Decoder ..	£61 17 9	£52 12 6
TRUVOX FM 200/1C with decoder ..	£60 11 10	£45 19 0
TUNER/AMPLIFIERS		
ARENA 2400 with Decoder ..	£90 6 0	£69 19 6
ARENA 2500 complete with Decoder ..	£97 0 0	£79 0 0
ARENA T1500F AM/FM Stereo Tuner/Amplifier ..	£72 9 0	£59 19 6
ARENA T900 AM/FM Stereo Tuner Amplifier ..	£303 9 0	£258 0 0
ARMSTRONG 525 25 watts per channel FM ..	£87 16 9	£74 19 6
ARMSTRONG 526 25 watts per channel AM/FM ..	£98 15 6	£85 19 6
ARMSTRONG 127 ..	£43 19 9	£37 19 6
(Teak Case for 127) ..	£3 17 0	£3 10 0
(NEW) GOODMANS Model 3000 with stereo decoder ..	£77 14 7	£66 19 6

	Rec. Retail Price	Comet Price
TANDBERG soly Super 10/71 Tuner/Amplifier AM/FM and 2 short wavebands ..	£75 18 0	£65 18 0
TELETON MX 990 Stereo Tuner/Amplifier with AM/FM Multiplex Stereo Radio c/w two Speakers, each Speaker containing 8in. bass, 2in. tweeter ..	£64 13 2	£48 19 6
TELETON F.2000 AM/FM Stereo Tuner/Amplifier 2 x 5 watts RMS with silicon transistors ..	£51 0 0	£37 19 6
TELETON R.8000 AM/FM Stereo Tuner/Amplifier 2 x 8 watts RMS, complete with 2 speaker boxes ..	£60 19 6	£49 19 6
TELETON C.M.S. 300 with turntable and two speakers ..	£105 15 0	£79 19 6
TELETON CMS.400 AM/FM Multiplex Tuner/Amplifier with 2 speaker boxes and turntable ..	£126 0 0	£89 0 0
TELETON 7ATI Stereo Tuner/Amplifier AM/FM 50 watts RMS Stereo Decoder and F.E.T. ..	£133 0 0	£89 0 0

THE GOODMAN 3000 MUSIC AUDIO SUITE
A complete Audio Suite with Stereo Radio, complete with Speakers, Turntable and magnetic cartridge. All Wired and ready to go. Beautifully finished in Teak. Rec. Retail Price £140.9.0. **COMET PRICE £111.0.0.**

CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

	Rec. Retail Price	Comet Price
SPEAKERS		
ARENA HT 21 ..	£10 10 0	£9 5 0
ARENA HT 7 ..	£19 19 0	£17 0 0
ARENA HT 10 ..	£22 1 0	£18 19 6
ARENA HT 20 ..	£32 11 0	£26 19 6
ARENA HT 26 ..	£78 15 0	£65 19 6
BOWERS & WILKINS DM3 A and W ..	£63 0 0	£53 6 0
BOWERS & WILKINS DM3 M ..	£69 10 0	£58 16 0
BOWERS & WILKINS PZH ..	£94 10 0	£81 5 6
CELESTION D1ton 10 ..	£21 3 2	£17 5 0
CELESTION D1ton 15 ..	£31 3 7	£25 19 6
DULCI AS3 Speaker ..	£8 8 0	£6 19 6
GOODMANS Maxim ..	£20 7 9	£15 19 6
GOODMANS Mezzo II ..	£30 18 0	£24 19 6
GOODMANS Magnum-K ..	£40 2 0	£32 19 6
GOODMANS Mirimba ..	£24 0 1	£19 19 6
GOODMANS Mambo ..	£22 5 6	£18 11 9
GOODMANS Loudspeaker System Model 2005 (per pair) ..	£25 0 0	£21 0 0
KEF Celeste ..	£29 0 0	£23 19 6
KEF Concord ..	£43 10 0	£34 19 6
LEAK Sandwich ..	£43 10 0	£34 19 6
LEAK Mini-Sandwich ..	£29 15 0	£23 19 6
QUAD Electrostatic ..	£66 0 0	£57 19 6
TRUVOX LS200 ..	£22 7 3	£17 19 6
WHARFEDALE New Airedale ..	£69 10 0	£57 14 0
WHARFEDALE Denton ..	£18 0 0	£13 19 6
WHARFEDALE Super Linton ..	£21 10 0	£17 19 6
WHARFEDALE Melton ..	£29 10 0	£23 19 6
WHARFEDALE New Dovedale 3 ..	£39 10 0	£31 19 6

	Rec. Retail Price	Comet Price
WHARFEDALE Rosedale ..	£55 0 0	£43 19 6
WHARFEDALE UNIT 3 Speaker Kit ..	£10 19 6	£8 19 6

Most types of chassis, speakers, cross-over networks, etc., available ex stock.

TURNTABLES

	Rec. Retail Price	Comet Price
ARENA SP.25 complete with base and cover ..	£30 19 0	£24 19 6
GARRARD SP.25, Mark II ..	£15 11 4	£11 19 6
GARRARD AP.75 ..	£23 16 0	£16 19 6
GARRARD SL.55 ..	£13 17 9	£11 12 6
GARRARD SL.65 ..	£19 6 5	£14 9 6
GARRARD SL.75 ..	£35 12 5	£25 19 6
GARRARD SL.95B ..	£45 9 1	£33 19 6
GARRARD 401 ..	£31 14 2	£26 10 0
GARRARD 3000 fitted with GKS 25/Cartridge ..	£13 18 3	£ 9 19 6
GARRARD 3500 fitted with GKS 25/Cartridge ..	£15 15 0	£10 19 6
GOLDRING GL69 ..	£25 1 6	£21 5 0
GOLDRING 69P ..	£33 11 9	£28 19 6
GOLDRING Lenco GL.75 ..	£36 8 2	£27 19 6
GOLDRING 75P inc. cover ..	£46 18 8	£38 0 0
GOODMANS Model 3025 complete with magnetic Cartridge ..	£37 14 9	£32 19 6
THORENS TD.125 ..	£69 11 2	£53 19 6
THORENS TD.150A Mark II ..	£41 14 9	£32 19 6
THORENS TD.150AB Mark II ..	£45 10 7	£34 19 6
THORENS TD.124/II ..	£46 15 10	£42 0 0

Bases, plinths and covers stocked to suit all the above turntables.

HI-FI STEREO TAPE DECKS AND TAPE RECORDERS

	Rec. Retail Price	Comet Price
AKAI X-360 4-track ..	£339 0 0	£284 0 0
AKAI X-360D deck 4-track ..	£290 0 0	£243 0 0
AKAI 1710 4-track without accessories ..	£109 0 0	£89 19 6
AKAI 1800 4-track ..	£158 0 0	£133 0 0
AKAI 1800SD 4-track ..	£199 0 0	£167 0 0
AKAI 4000D deck 4-track ..	£87 10 0	£75 10 0
FERGUSON 3324 Twin Track ..	£33 14 0	£24 19 6
FERGUSON 3226 Four Track ..	£46 6 0	£29 19 6
GRUNDIG TK124 ..	£41 18 6	£36 19 6
GRUNDIG TK144 ..	£47 13 1	£39 19 6
GRUNDIG TK149 ..	£55 18 10	£47 19 6
MARCONI 4218 Stereo Tape Recorder ..	£89 11 2	£69 19 6
MARCONI 4238 4-track Tape Recorder ..	£58 11 0	£49 19 6
TRUVOX R52 & R54 3-speed 2-track ..	£77 5 1	£52 2 0
TRUVOX PD 102 Stereo Tape Deck ..	£114 15 3	£79 0 0

PICKUP ARMS

	Rec. Retail Price	Comet Price
GOLDRING Lenco L75 ..	£12 6 6	£10 10 0
GOLDRING Lenco G65 ..	£7 13 6	£6 10 0
SME 3009 with S2 shell ..	£31 6 3	£24 19 6
SME 3012 with S2 shell ..	£33 7 3	£26 19 6

COMET DISCOUNT WAREHOUSE

Reservoir Road, Clough Road, Hull. Tel 407906
68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055

Customers are welcome to call personally.
Ample Car Parking facilities

Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.
Add 9/- for post and packing on all orders. Make cheques, Money Orders payable to "COMET".

I.F. CRYSTAL FILTER



F.G. RAYER

RECEIVERS in the higher price range often have a crystal filter to give a very considerable increase in selectivity compared with transformers, thus reducing interference from adjacent transmissions. The simplest type of filter is that with a single crystal and variable phasing. The filter described here was fitted as an addition in the all-wave "Progressive Superhet" (March 1969 issue) but could equally well be included in other home-constructed, surplus, communications-type receivers.

Figure 1 is the circuit, and uses the centre-tapped i.f. transformer listed, numbers being for the pins of this component. This i.f.t. is intended for 465kHz, but was found to be satisfactory anywhere in the 455-470kHz range.

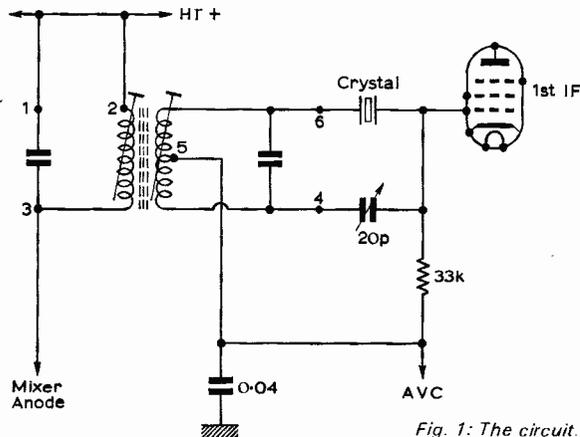


Fig. 1: The circuit.

The crystal was 464.75kHz, obtained from the supplier listed. There is no need to use this exact frequency, as all the i.f.t.s are later aligned on the crystal frequency.

When the 20pF variable capacitor is adjusted to balance the stray crystal circuit capacitance a symmetrical response curve similar to that at A in Fig. 2 is obtained. The crystal has a Q very much higher than that of an ordinary tuned circuit, so the response curve is very sharp, giving high selectivity. F is the crystal frequency. The ordinary tuned circuits of the other i.f.t.s help to reduce the response

★ components list

Type IFT11/465/CT i.f. transformer (Denco, Clacton, Ltd., 357/9 Old Road, Clacton-on-Sea, Essex).

Crystal, 464.75kHz or similar (Henry's Radio. Ltd., 303 Edgware Road, London, W.2).

33k Ω $\frac{1}{4}$ -watt resistor.

20pF or similar miniature air-spaced variable capacitor.

Insulated extension spindle, coupling, bush etc. (Home Radio, 187 London Road, Mitcham, Surrey.)

at the wider skirt frequencies, $F1$ and $F2$.

If the variable capacitor is adjusted slightly, changes in phase produce the notch shown at B: this is a frequency at which there is minimum response. The position of this rejection notch can be varied by adjusting the phasing capacitor, and can be moved to the other side of the resonant frequency F . The normal selectivity of the other i.f. tuned circuits helps compensate for the hump and extended skirt of B.

Maximum selectivity may be increased by reducing the value of the 33k Ω resistor, or reduced by increasing the resistor value. Selectivity with the circuit balanced (A, Fig. 2) is too great for normal reception, so for this purpose some means of cutting out the crystal or reducing its effect becomes necessary. The best method is to short out the crystal with a low-loss low-capacitance switch connected with short leads, but there are other ways such as adjusting the phasing capacitor well off optimum setting or bending one corner of a moving plate so that the capacitor shorts when closed. These methods avoid the switch but leave a secondary dip from the crystal when tuning.

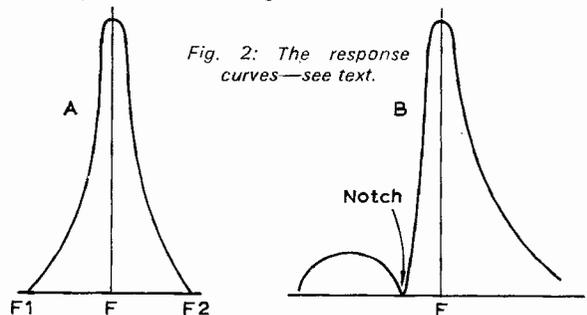


Fig. 2: The response curves—see text.

In the receiver mentioned, the first i.f.t. is removed and the centre-tapped type fitted in its place. The phasing capacitor is mounted on paxolin, fixed to the chassis with brackets. A $\frac{1}{4}$ in. dia. insulated extension rod is attached to the capacitor spindle with a coupling, and passes through a bush placed in the "R.F./L.F. Gain" control position, this potentiometer being moved to the right of the panel above the chassis.

With other receivers, a well-screened layout is best, to avoid stray coupling round the crystal, thereby reducing its efficiency. The layout should also permit short wiring. Some commercial receivers have the phasing capacitor fitted to the panel, with only an insulated bush, but this can cause misalignment because of hand capacitance effects.

For best possible results alignment is quite critical, and is best done by tuning-in a quite strong, steady signal, such as that from a BBC transmitter.

With the crystal in circuit and the phasing capacitor about half closed, tune slowly through the signal, observing the S-meter or a meter temporarily placed in the h.t. circuit to one i.f. stage.

A very sharp peak should be seen, with a

broader but similarly strong response at a second but near frequency. The sharp peak is from the crystal, and broad peak from the i.f. tuned circuits.

Tune to the sharp peak, and adjust all the i.f.t. cores slightly for best results. As this is done, the second broad peak will disappear, and signal strength at the sharp peak will rise considerably.

Careful tuning will now probably show a response similar to that at B, Fig. 2. Adjust the phasing capacitor until this changes to that at A. Reduce signal input (a *very short* aerial can be used to do this) and carefully touch-up the i.f.t. cores.

With all i.f.t.s tuned exactly on the crystal, and the latter balanced, observation of the S-meter will give a response like that at A. If the receiver is tuned slightly above or below a carrier, adjustment of the phasing capacitor one way or the other should be found to place the carrier in the rejection notch, B, so that it almost completely disappears.

As the receiver i.f. has been modified, the oscillator cores and trimmers should be touched up, for best results on each band.

Maximum selectivity is primarily for c.w. only, the passband being too narrow for speech. However, when operating in a congested amateur or other band, selectivity can be degraded somewhat by adjusting to obtain the curve B, meanwhile placing the notch so as to reduce interference. This allows a great improvement in the reception of voice transmissions. ■

P.W. GUIDE TO COMPONENTS

continued from page 802

Insulated gate f.e.t.s are commonly of the depletion type and can be directly substituted with junction f.e.t.s of the same effective channel type. Gate currents are of course considerably lower and gate-source bleed resistors can be as high as 1,000M Ω and mainly depend only on external leakage requirements. The principal disadvantage of m.o.s. transistors is the high noise levels which are associated with the insulated gate and which preclude their use in small signal circuits.

Field effect transistors therefore are an extremely useful alternative to conventional bipolar transistors. They are encapsulated in similar cases to transistors, and where heavy current devices are required an interdigitated or multichannel device is used. At present plastic encapsulated, wide tolerance junction f.e.t.s (n-channel) are available from 5s. whilst closer tolerance f.e.t.s, both n- and p-channel, are usually available from £1 to £20. Insulated gate f.e.t.s are of the same order of price. Since the vast majority of f.e.t.s are junction n-channel devices it would be wise for the amateur to use these widely available and hence cheaper devices.

TO BE CONTINUED

QUERY COUPON

This coupon is available until 6th February 1970 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, FEBRUARY 1970

NEXT MONTH IN

PRACTICAL WIRELESS

TWELVE TRANSISTOR RECEIVER

A real communications type receiver with continuous coverage from 550kHz to 30MHz in four switched bands. Incorporated in the design are a variety of features found only in the best sets—switched a.g.c., S-Meter and B.F.O.

The problem of tackling a set of this complexity is overcome to such an extent that it can truly be classed in the beginners range. The set initially starts as a six transistor receiver and will provide excellent coverage in this form, but it builds up to a twelve transistor plus four diode set with the features mentioned above.

METAL DETECTOR

This article describes the principles of metal detection including the limitations of amateur types and goes on to describe a practical circuit which in addition to being useful for locating house wiring etc. can give endless hours of fun. In the described form the metal detector should cost under 50s. including headphones but a cheaper and simpler version making use of a standard radio set is also described.

BOOKSHELF SPEAKER

The "Decibella" speaker enclosure contains a woofer and a tweeter, frequencies above 3kHz being fed to the tweeter and below 3kHz to the woofer. A series L-C crossover network is employed.

Size of the enclosure is 13 x 8in. with a depth of 8½in. and fed from a 10 Watt amplifier, two of these units will give really good stereo listening.



PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" FEATURES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES

Don't miss your copy of the March issue of Practical Wireless—on sale 6th February—price 3s.

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-236 8080. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia, Malawi and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2 2s 0d.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

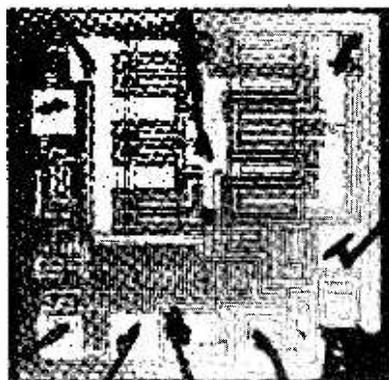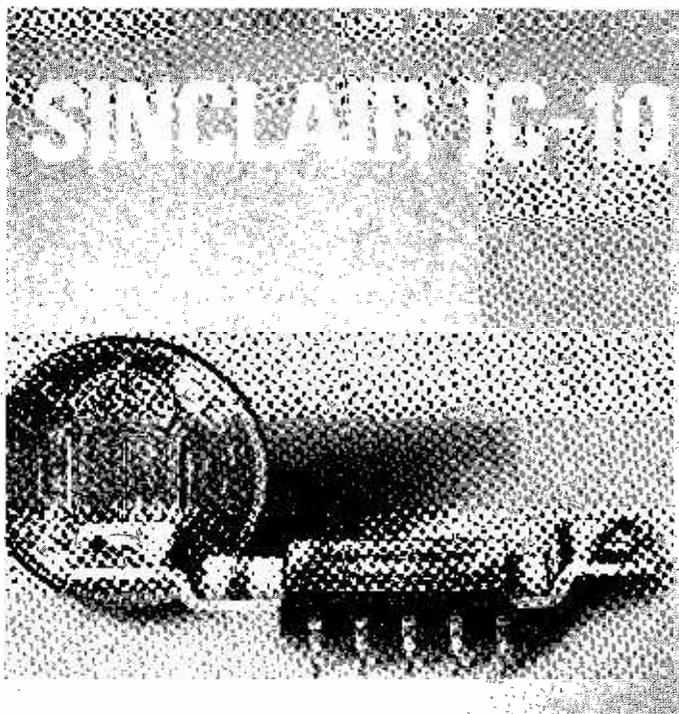MONOLITHIC INTEGRATED CIRCUIT HIGH FIDELITY AMPLIFIER AND PRE-AMP



the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output of 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 zenor diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of the usual tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required for producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. It also enables us to give a 5 year guarantee on each IC-10 knowing that every unit will work as perfectly as the original and do so for a lifetime.

■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz ± 1 dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

SINCLAIR

IC.10 *with IC.10 manual and 5 year guarantee* **59/6**

POST FREE


sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET ROAD · CAMBRIDGE
Tel. 0233-52731

NEW

20 WATTS
(40 WATTS PEAK)

**HIGH
POWER**

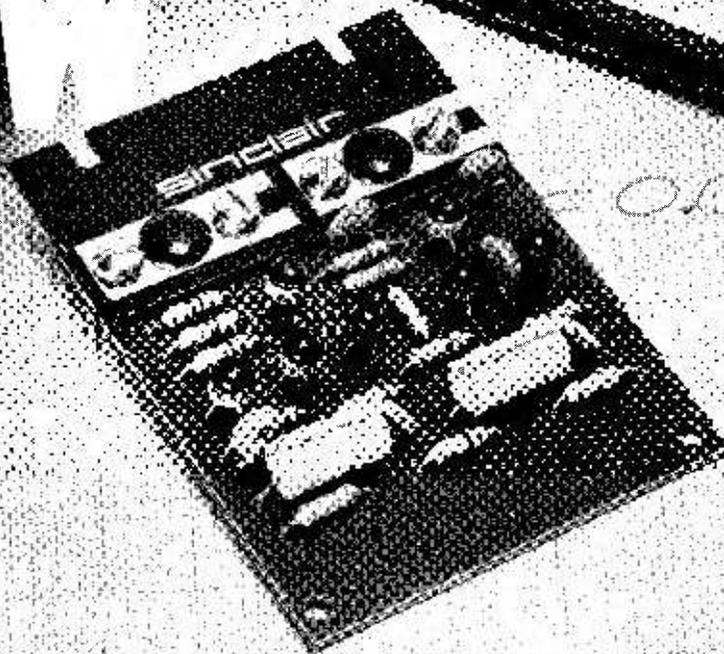

Z.30


THE WORLD'S LOWEST DISTORTION HIGH FIDELITY AMPLIFIER.

For four years, the Sinclair Z.12 dominated the constructor world, being the best selling unit of its kind this side of the Atlantic. Excellent as it was, the new Sinclair Z.30 is still better. Half the size of the Z.12, it has more than twice the power, very much greater gain and a level of distortion 50 times lower. This incredible figure results from using over 60dB of negative feed back with a constant current load to the driver stage obtained by incorporating a two transistor circuit in place of the more usual boot-strapping. 9 silicon epitaxial planar transistors are used to provide enormous power (up to 20 watts RMS continuous sine wave, 40 watts peak). The circuitry of this marvellous amplifier allows it to be operated from any voltage from 8 to 35 to perfection.

At all output levels, distortion is only 0.02%. This puts true laboratory standards into the hands of every user of a Z.30. Two Z.30s and a new Stereo Sixty will make a stereo assembly of such perfection that it could not be bettered in its class no matter how much you spent. But the Z.30 has an enormous variety of applications, particularly where quality, precision and reliability are essential. Yet this brilliant new Sinclair design costs not a penny more than its famous predecessor.

APPLICATIONS

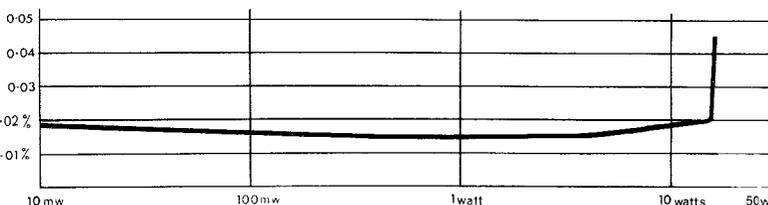Hi-fi amplifier; car radio amplifier; record player amplifier fed directly from pick-up; intercom; electronic music and instruments; P.A.; laboratory work, etc. Full details for these and many other applications are given in the manual supplied with the Z.30.



SPECIFICATIONS

Power output: 15 watts R.M.S. into 8 ohms using a 35 volt supply; 20 watts R.M.S. into 3 ohms using a 30 volt supply.

Output: Class AB.

Frequency response: 30 to 300,000Hz \pm 1dB.

Distortion: 0.02% total harmonic distortion at full output into 8 ohms and at all lower output levels.

Signal-to-noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms.

Damping factor: > 500.

Loudspeaker impedances: 3 to 15 ohms.

Power requirements: From 8 to 35V. d.c. (The Z.30 will operate ideally from batteries if required).

Size: 3½ x 2½ x ½ inches.

*Built, tested and guaranteed,
with circuits and instructions
manual*


89/6

sinclair


SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD, CAMBRIDGE Tel: 0223 52731

NEW

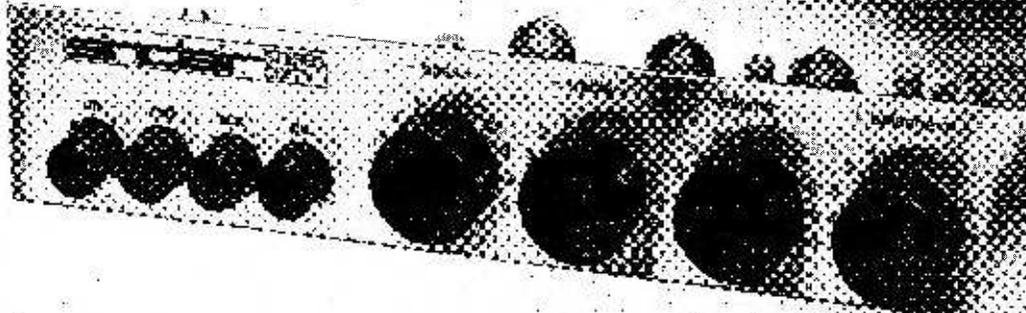


STEREO SIXTY PRE-AMP & TONE CONTROL UNIT

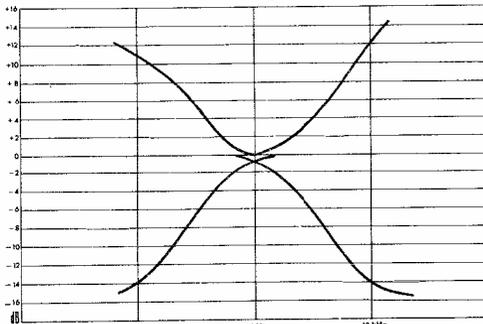

Curves to show bass and treble cut and boost

Ready built, tested and
guaranteed with
instructions

£9.19.6

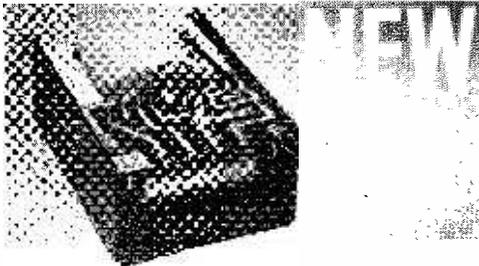

sinclair

This attractive and completely new unit is intended for use with two new Z.30 amplifiers to provide the finest possible standards of stereo reproduction. Four press buttons and four rotary controls are used to provide on-off, three input selectors and Volume, Bass cut/boost, Treble cut/boost and Stereo balance. The on-off button also switches the power amplifiers. The front panel in brushed aluminium is flush mounted to the cabinet front, it being necessary only to drill holes to accommodate the controls. Rear adjustable brackets hold the chassis tight to the cabinet. The very latest ganged rotary controls are used to afford compactness and extra long working life free from noise.

The Stereo-60 may also be used with 2 IC-10's or any other high performance amplifiers.

SPECIFICATIONS

- Inputs sensitivities—Radio—up to 3mV
Magnetic Pickup—3mV; correct to R.I.A.A. curve ± 1 dB; 20 to 25,000 Hz.
Ceramic Pickup—up to 3mV; Auxiliary—up to 3mV.
- Output—250mv.
- Signal-to-noise ratio—better than 70dB.
- Channel matching—within 1dB.
- Tone Controls—TREBLE +15 to -15dB at 10kHz. BASS +15 to -15dB at 100Hz.
- Power consumption 5mA.
- Front panel—brushed aluminium with black knobs and controls.
- Size $8\frac{1}{2} \times 1\frac{1}{2} \times 4$ ins.

PZ.5 POWER SUPPLY UNIT

A new heavy duty mains power supply unit designed specially to drive two Z.30s and a Stereo Sixty. New compact design. **£4.19.6**

Q.16 Loudspeaker and Micromatic on next page.


To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE
Please send

NAME
ADDRESS
.....
.....
For which I enclose cash/cheque/ money order	PW2/70

SINCLAIR Q.16

new elegance in an
outstanding loudspeaker

All the superb features which went to make the Sinclair Q.14 have been incorporated in the new Q.16 which gives an exciting new opportunity for you to match your Sinclair equipment with modern decor. Employing the same well proven acoustic system in which materials, processing and styling are used in such a radical and successful departure from conventional design, the new Q.16 presents an entirely new appearance with its attractive teak surround and all-over special cellular foam front chosen as much for its appearance as for its ability to pass all audio frequencies without loss. The Q.16 is compact and slim. Its new styling makes it eminently suitable for shelf mounting, but it is no less versatile than its famous predecessor. Listen to a pair of Q.16s in stereo and marvel at the standards of quality and clarity they give.

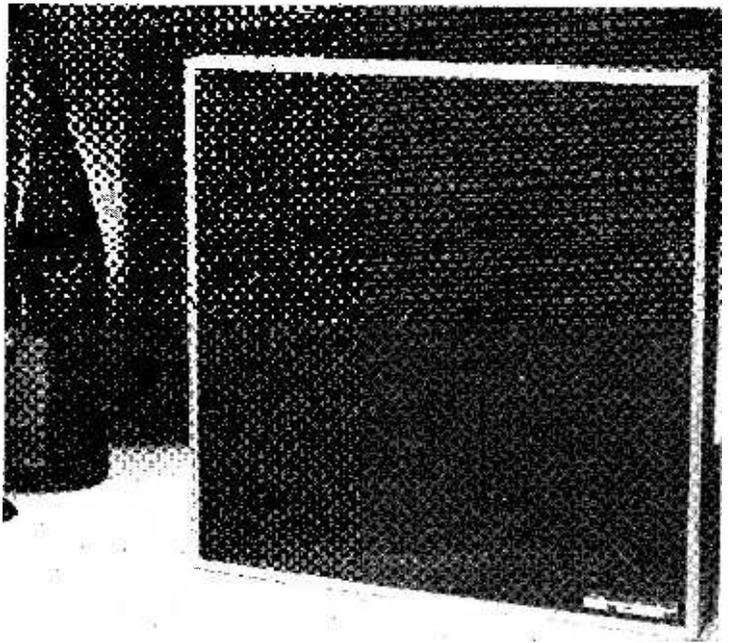


The Q.16 will handle loading up to 14 watts R.M.S. and presents an 8 ohm impedance to the amplifier output. Frequency response extends from 60 to 16,000Hz with exceptional smoothness. A specially designed driver system is used in a sealed and contoured pressure chamber to ensure good transient response at all frequencies. Size: 9 $\frac{1}{2}$ " square \times 4 $\frac{3}{4}$ " deep from front to back.

£8.19.6

POST FREE

SINCLAIR MICROMATIC

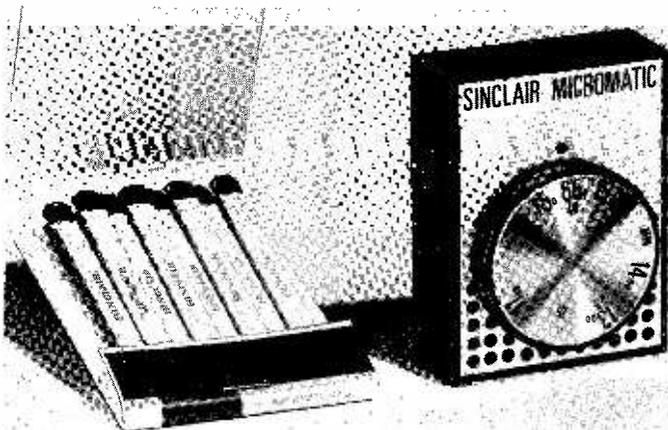The world's most
successful miniature
radio



SPECIFICATIONS—Size: 1 $\frac{13}{16}$ " \times 1 $\frac{1}{16}$ " \times $\frac{3}{8}$ " (46 \times 33 \times 13mm). **Weight incl. batteries:** 1 oz. (28-35gm) approx. **Tuning:** Medium wave band with bandspread at higher frequency end. **Earpiece:** Magnetic type. **Case:** Black plastic with anodized aluminium front panel, spun aluminium dial.

Complete kit incl. earpiece, case, solder and instructions in fitted pack. **49/6**
Plus 11d. P.T. surcharge
Ready built, tested and guaranteed, with earpiece. **59/6**
Plus 1/1d. P.T. surcharge
Mallory Mercury Cell RM675 (2 req.) 2/9 each

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation much easier than with many larger sets. The plug-in magnetic earpiece which matches exactly with the output provides wonderful standards of reproduction.

Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wrist-watch, and dependable under the severest listening conditions.

USE THIS COUPON FOR MICROMATIC AND Q.16 ORDERS

SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET RD., CAMBRIDGE
Tel: 0223 52731

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE
Please send


NAME

ADDRESS

For which I enclose cash/cheque/
money order

PW.170

6 PUSH-BUTTON STEREOGRAM CHASSIS

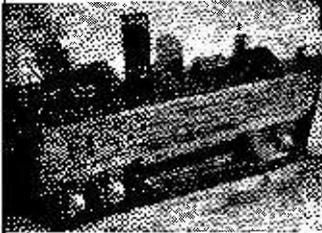

M.W.: S.W.1.: S.W.2.: V.H.F.:
 Gram: Stereo Gram: Vol;
 Tone; Mains Trans; 200-
 250 Volts; 2 o.p. for 3 ohm.
 Also operates with
 two speakers on Radio. Chassis
 size: 15 x 7 x 6 1/2 in. high. Dial
 silver and black 15 x 3 in. 190-
 550M; 18-51M; 60-187M;
 VHF 86-100 Mc/s. Valves:
 ECC85, ECH81, EF89, 2 x
 ECL86, EM84 and Rect.
 Price £19.19.0, carr. paid.
 With Stereo Decoder fitted
 £8 extra.

STEREO AMPLIFIER type HV—
 2 x 3 Watts

Fully built. On off. sep. vol. and tone each
 channel 12 x 4 1/2 x 6 in. high. EZ80. 2 x ECL86;
 for 3 ohm speakers, double wound main trans;
 fixing flanges and base plate, suitable for crystal
 cart, tuner etc. £6.10.0 (8/- p. x p.)



STEREO AMPLIFIER type RC—
 2 x 3 Watts

Fully built. 2 x UCL82, metal rect; ganged vol.
 and tone cont; on-off. balance. 11 x 3 1/2 x 4 in.
 high. Double wound mains trans. with supporting
 brackets. For 3-ohm speakers. £6 (8/- p. & p.).



MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short. Gram. 200-250v AC
 Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in.
 Double wound mains transformer 5 valves ECH81
 EF89, EBC81, EL84, EZ80. Price £10.12.6.
 (7/6 p. & p.) Output trans. for 3-ohm speaker.



BAKERS' Selhurst Speakers. 12 in., cast frame, 3, 8 or 15 ohm (state which).
 Group 25 (25 watt) for guitars, etc. £6.6.0: Stalwart 45-13,000 cps, 15W
 £6.6.0; de Luxe Mk2 dual cone 25-16,000cps. 15W £9 (all carr. paid) less
 10% for 2 speakers.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240
 CLOSED WEDNESDAY. S.A.E. for enquiries please.

YOUR CAREER in
**RADIO &
 ELECTRONICS ?**

Big opportunities and big money await the qualified man
 in every field of Electronics today—both in the U.K. and
 throughout the world. We offer the finest home study
 training for all subjects in radio, television, etc., especially
 for the CITY & GUILDS EXAMS (Technicians' Certificates);
 the Grad. Brit. I.E.R. Exam.; the RADIO
 AMATEUR'S LICENCE; P.M.G. Certificates; the
 R.T.E.B. Servicing Certificates; etc. Also courses in Tele-
 vision; Transistors; Radar; Computers; Servo-mech-
 anisms; Mathematics and Practical Transistor Radio course
 with equipment. We have OVER 20 YEARS' experience
 in teaching radio subjects and an unbroken record of
 exam. successes. We are the only privately run British
 home study College specialising in electronics subjects only.
 Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME Block


ADDRESS Caps.

Please
 1/70

BRITISH NATIONAL RADIO SCHOOL

BETTER Bargains
 Service
 FROM TRS

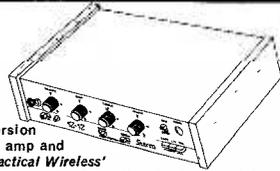BUILD THIS FINE
 VERSION OF THE
 PW.12-12 WITH A
 TRS KIT



T.R.S. have produced their own kit version
 of this outstanding combined stereo amp and
 pre-amp. It conforms precisely to 'Practical Wireless'
 excellent circuit but is styled for a flatter, more conventional cabinet which
 will be available shortly. Kit includes two-tone front panel and control knobs,
 components and transistors.

Inputs—Mag. P.U. (R.I.A.A.) 2-5mV into 68 Kohms; Ceramic P.U. and
 Radio; Response 20Hz to 30KHz ±1dB. Output—12 watts per channel.
 R.M.S. into 15 ohms.

Power Amplifier & Pre-amp

Kit complete. £24.10.0 (Carr. 7/6) Kits available separately.
 less cabinet. S.A.E. brings list.

AMPLIFIERS

Styled and kitted by T.R.S., using quality com-
 ponents, including valves or transistors as
 necessary and excellent instructions. Backed by
 T.R.S. service.

MULLARD 5-10. Basic kit (requires pre-amp). Input Sensitivity—40mV;
 Response 20Hz-15KHz ±1dB; Output 10 watts R.M.S. at 3 or 15 ohms.
 KIT £10.10.0. BUILT £13.0.0 (Carr. either, 7/6).

MULLARD 2 VALVE PRE-AMP. Switching for 5 inputs; bass/treble/
 volume controls, etc. Sensitivity at input—4mV max. into 80K-1 Megohm;
 Response 20-25,000Hz ±1dB. KIT £6.19.6. BUILT £9.10.0 (Carr. either 5/6).

MULLARD 10-10 STEREO AMPLIFIER. Input sensitivity—210mV
 per channel; Response 12Hz-35KHz ±3dB; 10 watts R.M.S. output per channel
 into 3 or 15 ohms. KIT £18.10.0. BUILT £22.10.0 (Carr. either 12/6).

Basic Kit (no panel or controls) £17.0.0. Built £21.0.0. Pre-amp must be
 used here.

MULLARD 2+2 STEREO PRE-AMP with same characteristics per
 channel as mono pre-amp (+ balance). BUILT £13.19.6 (Carr. 7/6).

T.R.S. 4x4 ECONOMY STEREO. Modular assembly. With cabinet
 power supply and Din plugs £12.10.0 (Carr. 7/6).

SINCLAIR PRODUCTS AS ADVERTISED

TUNERS

T.R.S. 6 VALVE AM/FM. Self-powered, large scale; push-buttons. Magic
 eye. Med. Wave and F.M. Diode output per tape. COMPLETE KIT £12.10.0
 (Carr. 7/6).

T.R.S. FM TUNER. Transistors, Inter-station suppression, A.F.C. etc.
 Modular assembly. Modules, chassis, drive etc. come to £15.15.0 (Carr. 7/6)
 Cabinet to match T.R.S. 4+4 £1.17.6 (Carr. 2/6)
 Power supply £2.5.0 (Carr. 3/-)
 Decoder for Stereo £10.10.0 (Carr. 2/6)

GRAMO UNITS & PLINTHS

GARRARD SP.25 MK. II. Manual: Arm and 10 1/2 in. die-cast t/table, cueing
 device, etc. less cartridge. Brand new in maker's carton £12.7.6.

GARRARD LM.2025. With Sonotone 9TA/HC Stereo Cartridge and lift
 control £10.19.6 (Carr. 7/6)
 Garrard WB.1 Plinth £3.7.6 (Carr. 5/-)
 Garrard CLEARVIEW Cover SCP.1 £3.5.0 (Carr. 4/6)
 Garrard Scandinavian Type Plinth £5.5.0 (Carr. 5/-)

ALWAYS IN STOCK

Resistors in all values; wire-
 wound resistors; volume controls log or linear, 10K-2meg. Mono 3/6 (with
 switch 5/-). Stereo 8/6 (with switch, certain values 10/6). Log/antilog balance
 controls, capacitors and electrolytics; Vinalr speaker covering 48in.—22/6
 yd; Bondacoust 48in. x 1in. thick 7/- yd.; Veroboard; Cir-Kit; valves; trans-
 istors. S.A.E. with enquiries please.

TRS RADIO COMPONENTS
 70 BRIGSTOCK ROAD,
 THORNTON HEATH,
 SURREY

Open Sats. • 7 min. Thornton Heath • Phone:
 Close early Weds. Stn. (Southern) 01-684 2188

SOLDERING IRONS?

Whatever your particular application we are almost certain to have just the tool for the job.

ADAMIN—featherweight instruments with the slip-on bits and the big performance.

LITESOLD—the best-selling seven-model range of top-quality 'conventional' irons.

THERMOSTATIC CONTROL?
The new LITESTAT instruments are surely the most advanced available — at not so advanced prices.

You ought to get the whole story. Ask for catalogues L10. Free.

LIGHT SOLDERING DEVELOPMENTS LTD
28 Sydenham Road, Croydon, CR9 2LL
Telephone: 01-688-8589 & 4559



TRANSISTORS etc.			SILICON DIODE RECTIFIERS		Midget Electrolytic Conds. Wire Ends	
AC107	3/-	OC35	9/-	BY100	800 pV	2/10
AC126	2/-	OC44	2/-	Avalanche	14A	1/9
AF115	3/-	OC45	2/-		1200 pV	4/-
AF116	3/-	OC70	2/3	Six Amp Series		
AF117	2/9	OC71	2/-	BYZ13	300 pV	3/6
BFY18	4/6	OC72	2/2	BYZ11	900 pV	4/6
BFY51	4/-	OC73	2/9	BYZ10	1200 pV	5/6
GE1113	2/6	OC75	2/2	Mullard Stack FW Bridge		
OA5	1/6	OC81	2/-	12A	100 pV	39/6 (3/-)
OA9	1/8	OC81D	2/-	THYRISTORS		
OA47	1/9	OC82D	2/3	5 amp series		
OA81	1/6	OC140	5/-	100 pV	7/6	
OA85	1/6	OC169	3/6	200 pV	9/-	
OC23	6/6	OC170	2/6	300 pV	10/6	
OC25	6/-	OC171	2/2	400 pV	12/-	
OC26	7/6	OC202	4/6	800 pV	25/-	
OC28	8/6	TK22C	1/6	10 amp series		
				50 pV	10/-	
				100 pV	12/-	
				100 amp series prices available on request.		
				2000 MFD.	30V	4/6
				1500 MFD.	30V	4/6

Additional Transistors—AF147 and AF150, 24V. Larger envelope, 4 leads, collective current 10mA, gain 70—47 each. AF149—gain 225—4/6 each. Also 8x F 35V 1/2.5W 50V 50V 1/9. Other electrolytics in current list. Postage, Packing and Insurance all above 1/- up to 11, 12 and over charges paid. 2 GANG VAR. CONDENSER: Mod., air-spaced, .0005 ea. sec. 5/- (1/-), 3 GANG, 7/6 (1/-). SUB-MIN TRANSFORMERS: Output (Ω for OC72 etc.) 2/6. Driver 2.9 (up to 4.3). 1-1 MFLTR: 20,000 Ω/V D.C., 10,000 Ω/V A.C., 50/500/1K volts D.C., 0-10/50/100/500/1K volts A.C., 0-50A/2.5mA/250mA D.C., 0-6K Ω/6 meg Ω, 10μF—100mfd/1mfd. ●—20 to +22dB. ●Complete with test leads and instructions. ●Over-load Protected 1970 model with every refinement, £4.10.0 (2/6). JUNIOR MODEL at 47/6 (2/6) 1000Ω/V described in free list.

SOLDERING IRON. Slim Mod. British High speed, 8in., all parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use, 19/6 (1/6).

DIAMOND STYL Replacements for BSR TC8LP, TC8/S and TC8LP/GARRARD GC2LP STEREO COLLARO "C"; RONETTE BF40LP; PHILIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304) state whether 4in. or 3in., all at 13/6 (1/-).

SAPHIRE all the above 7/6 types only, also ACOS GP37 at 3/3 each (1/-), ACOS GP91 at 7/6 (1/-). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES All fitted Styls and Standard fittings. Mono which also plays Stereo records monaurally with min. wear, GP91/SC, 21/-. ●Largest Stereo GP93, 24/6. ●Ceramic Stereo, top quality for expensive outfits, GP94, 38/6 (all 1/-).

PP3 ELIMINATOR (A.C.) 17/6 (1/6). **TWO STATION TRANS. INTER-COM.** Excellent baby alarm. Instant, easy fitting with leads, plugs and battery. All you require 52/6 (3/-).

TRANSISTORISED AMPLIFIERS. 3 watt, 9V operation, 45/6 (1/6); 7 1/2 watt, 6 trans, 24V operation, 67/6 (2/6).

Extra High Torque MINI-MOTOR, 4 1/2 to 12V, 1 1/2 x 7/16in. 5/- (1/-), 9,000 r.p.m. SUBSTITUTION BOXES. Capacitance 25/6 (1/6). Resistance 32/6 (1/6). Both full range and complete. Full details in list.

TEST PRODS: Flexible, unbreakable 24in. Red and Black leads, thin 44in. prods, 14in. plugs 4/9 (1/-). Croc. Clips: Plated with screw, or with red/black handles, 6d. each, 5/- doz. (1/-).

RECORDING TAPE Finest quality British Mylar. **STANDARD:** 5in. 600ft. 7/3, 5in. 850ft. 8/9, 5in. 1200ft. 11/3, 7in. 1800ft. 18/- (1/3 reel). Still the finest quality and value obtainable.

MICROPHONES—CRYSTAL, MIC91, Desk, 16/3; MIC45, curved hand grip 17/6; Stick "60" 20/3; Stick "39" 26/6 (1/6 each type). Cream plastic hand type 7/6, or with "strut" stand, switch and 2 leads with 2-5 and 3-5 plugs 12/6 (1/3). Lancel (or hand) with clip 6/6 (1/-). Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands, 25/- (1/6). **DYNAMIC:** Cream hand/table 15/6 (1/6). MS10 50K Ω, 3 1/2-in. with base, Adaptor 37/6 (2/6). MS11, similar, but fixed on flexible Swan neck to switch-fitted base 42/6 (2/6). DM128 Uni-directional, 50K/600 ohms imp. stand adaptor, very high quality 6 1/2 x 2 x 1 1/2in. £5.9.6 (5/-). **CARDIOID DYNAMIC OMNI-DIRECTIONAL:** Two highly successful mikes "SOLARE" 209, 210, 211, 212, 213, 214, 215, 216, 217, 218, 219, with built-in vol. control, switch 50K/600 ohms imp., £5.17.6 (either type 5/-). Full details in list.

MICROPHONE INSERTS: Diameter 1.75in. or 0.9in., either size 5/6 (1/-). **SPEAKERS:** 12in. round, fitted Tweeter, 6W, 3 or 15 Ω (state which), 37/6 (5/6); or for stereo, 80W (charges paid); 2in. 3 1/2 x 6 1/2 (1/-); 6 1/2 x 4 heavy duty 3 1/2 x 1 1/2 (3/6) or for Stereo 3 1/2 x 6 1/2 pair (charges paid). Limited quantity powerful 2in. PM transistor replacement speaker, high ohms, excellent 5/9 (1/-). **HEADPHONES** High Res. 200Ω ea. earpiece, 18/6; Stereo Dyn 8-16Ω 63Ω (3/-). **EAR-PIECES** with lead and 3.5mm. jack plug, magnetic 6; Crystal jack up to 3.5mm (1/- on either). State if 2.5mm. plug required. (Crystal 3.5mm. only).

AERIALS, Car Types: Telescopic, vandal proof, locks retracted, 2 keys and all fittings, 22/6 (2/6). Motor driven, 12V, 5 section, complete 47.10.0 (5/-).

FOR ALL PORTABLES AND SETS. 7-Section, no swivel, screw hole in base, 6/6. ●10-section 6 1/2-47 1/2in., no swivel, screw hole in base, 12/6. **DISAPPEARING** 8 section, swivel fixing assembly, 6 1/2-33in. 10/- New 6 section 5 1/2-25 1/2in., screw hole in base, no swivel 4/- (1/- all sizes).

SWITCHES: standard toggle, metal, 250V 2A. One hole fixing: SPST 2/3, SPDT 2/9, DPST 3/-, DPDT 3/3. Slide type, Sub-min. DPDT 1/6 each, Small DPDT 3 way, centre "off" 1/9. Reed magnetic on/off 1/9 (up to three, 1/-; 1d. each all additional). Rotary Switches etc. in list.

VIBRATORS: Famous makes only. 12 volt 4 pin non-synch. 4/6. 12 volt 7 pin synch. 12/6. 6 volt 7 pin synch. 12/6 (1/- each, all types). No other types available.

MAINS NEON TESTER: Fly leads 2/-, Pocket screwdriver type 3/6. **PLUGS:** Std. Jack, plastic body 2/3. Screened 3/-, VALVE HOLDERS: BYG or B9A, Moulded 6d. (all above, 1/- to three). **CONNECTING CABLES:** 5 coils assid. coils, each 5 yds. Solid Core 2/6. Flexible 3/-, Super thin for transistor wiring (1/- all types per 5 coils). **PICK-UP WIRE:** Twin Super thin Flex, Screened, Sheathed, 1 1/2 yd. (6d. up to 6 yds., over 6 yds. post free). **TWIN MIKE CABLE:** 1 1/2 yd. SINGLE MIKE CABLE 3/6. Both flexible, screened and sheathed. (Up to 3 yds. 8d., each additional yard 1d. extra).

R.F. FIELD INDICATOR, 5-band with antenna, monitoring crystal carpiece, visible indicator etc. 48/6 (1/6). Details in list.

RETRACTABLE EXTENSIBLE LEADS. Space saving "Curly", many uses in car and home; with phono plug each end, 6ft., 4/6; 12ft., 7/9; With phono plug one end, phono socket at other, 6ft., 5/-, 12ft., 8/6 (1/- each all types).

CAR RADIO: Splendid new All-British dash-mounting radio using Mullard transistors and circuit. M. and L. wave. Separate speaker and battery. Absolutely complete, for + or - chassis, £11.11.0 (6/6). A huge success since introduction.

CURRENT LIST: Sent with all orders or free for s.a.c. details of cable, croc. clips and leads, Continental din plugs for Grundig, Telefunken equipment, etc., dials, plugs and sockets, namers, record player and tape recording accessories.

BATTERY CHARGERS: test equipment, terminals, tape recorder, special transistors, portable sets, more switches and other components, tools, Veroboard etc., etc. This advertisement cancels all previous ones and lists supplied prior to December 31st, 1969.

FELSTEAD ELECTRONICS

(PW27) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted, and a minimum charge of 1/- is now made. Charges apply to G.E. and Eric only. Overseas orders welcomed. Air or surface mail at cost, sent at buyer's risk, unregistered and uninsured unless specified and min. insurance/ reg. fee of 3/2 sent.

S.A.E. please for all enquiries, otherwise regret cannot be replied to.

DE LUXE PLAYERS

PORTABLE CABINET As illustrated. To fit standard player or autochanger **75/-**
RCS AMPLIFIER 3 WATT
 Ready made and tested.

This is a 2-stage unit using a triode pentode condenser coupled valve, giving 3 wats output into a 3 ohm loudspeaker. Tone and volume controls mounted on panel. Supplied with knobs, loudspeaker and valves UCL2.2.UY85



Post 5/6 each item

Frequency response 50-12,000 cps. Sensitivity 200mV.

59/6 AUTOCHANGERS MONO Balfour Princess £5.5/6 BSR Superslim UA25 £6.19/6

SINGLE PLAYERS MONO BSR Mini Changer £8.19/6 EMI Junior Mains £2.19/6 AUTOCHANGERS STEREO Garrard SRP 22 £6.19/6 BSR Superslim £7.19/6 SINGLE PLAYERS STEREO Garrard 1025 £7.19/6 Garrard SP25 MkII £12.19/6 Garrard 3000 £12.19/6

GARRARD TEAKWOOD BASE W.B.I. Ready cut **77/6** out for mounting 1025, 3000, SP25, AT60, etc. **GARRARD PLASTIC COVER SPEC.1** for W.B.I. BASE. Durable tinted attractive appearance. **65/-**

E.M.I. PICK-UP ARM, complete with mono cartridge 29/6; XTAL GP67 17/6; Stereo Ceramic 35/-; ACOS LP only 10/6.

CRYSTAL MIKE INSERTS
 1 1/2" dia. 6/6; ACOS 1 1/2" dia. 12/6; BM3 1" dia. 9/6
QUALITY RIBBON MIKE with GOOSENECK £11.11/0
CRYSTAL HAND MIKE High Output 12/6

A self-contained fully portable mini P.A. system. Many uses—Ideal for Parties, or as Baby Alarm, or as Telephone or Record Player, Amplifier, etc. Attractive rexine covered cabinet, size 12 x 9 x 4in., with power-ful 7 x 4in. speaker and four transistor one watt power amplifier plus ultra sensitive microphone. Uses PP3 battery. Brand new in makers' carton with full makers' guarantee. Only **90/-** Post Free World famous make



WEYRAD P50—TRANSISTOR COILS

RA2W 6in. Ferrite Aerial with car aerial	12/6	Spare Cores	6d.
O.C. P50/1AC	5/4	Driver Trans. LFDT4	9/6
I.F. P50/2CC 470kc/s	5/7	Printed Circuit, PCA1	9/6
3rd I.F. P50/3CC	6/6	J.B. Tuning Gans	10/6
Telescopic Chrome Aerials 6in. extends to 23in.	5/-	Weyrad Booklet	2/-
Ferrite Rods only 3 x 1/4in. 4/- 6 x 1/4in. 5/-			

VOLUME CONTROLS

Long spindles, Midset Size 5K, ohms to 2 Meg. LOG of LIN. L/S 3/4, D.P. 5/16, STEREO L/S 10/16, D.P. 1/4, Edge S/L, S.P. Transistor 5/16	80 Ohm Coax 8d. yd. BRITISH AERIALITE AERIAL-5K SPACED 40 yd. 10/- 60 yd. 30/- FRINGE/LOW LOSS Ideal 625 lines. 1/6 yd
WIRE-WOUND 3-WATT POTTS. TV Type. Knurled Knob Values 10Ω to 30K. Cap 30K to 2meg. 4/6	WIRE-WOUND 3-Watt Standard Size Pots. Long Spindle 10 OHMS to 100K 7/6

VEROBOARD 1/5 MATRIX
 2 1/2 x 5in. 3/8, 2 1/2 x 3 1/2, 3 1/2 x 3 1/2, 3 1/2 x 5in. 5/2. EDGE CONNECTORS 16 way 5/-, 24 way 7/6
 PINS 36 per packet 3/4. FACE CUTTERS 7/6.
 S.R.P.B. Board 0.15 MATRIX 2 1/2in. wide 6d. per lin. 3 1/2in. wide 9d. per lin. 5in. wide 1/- per lin. up to 17in.
 S.R.P.B. undrilled 1/2in. Board 10 x 8in. 3/-
 BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides. 7 x 4in. 5/6; 9 x 7in. 6/6; 11 x 3in. 6/6; 11 x 7in. 7/6; 13 x 9in. 9/6; 14 x 11in. 12/6; 15 x 14in. 15/-
 ALUMINIUM PANELS 18 s.w.g. 12 x 12in. 6/6; 14 x 9in. 5/6; 12 x 8in. 4/6; 10 x 7in. 3/6; 8 x 6in. 2/6; 6 x 4in. 1/6.

Q MAX CHASSIS CUTTER


Complete: a die, a punch, an Allen screw and key
 1in. 16/- 1 1/4in. 17/6 1 1/2in. 19/6 1 3/4in. 24/- 2 1/4in. 44/3
 1in. 16/- 1 1/4in. 19/6 1 1/2in. 20/6 1 3/4in. 29/- 2 1/4in. 57/3
 1in. 16/9 1 1/4in. 19/6 1 1/2in. 21/6 2in. 39/- 1in.s. 36/6

1 1/4in. DIAMETER WAVE-CHANGE SWITCHES.
 2p. 2-way, or 2p. 6-way, or 3p. 4-way 4/6 each.
 1p. 12-way, or 4p. 2-way, or 4p. 3-way 4/6 each.
 1in. Diameter Wavechange "MAKITS" 1p. 12-way, 2p. 6-way, 3p. 4-way, 4p. 3-way, 6p. 2-way, 1 wafer 12/-, 2 wafer 18/-, 3 wafer 24/-, 4 wafer 30/-, 5 wafer 36/-. TOGGLE SWITCHES, sp. 2/6; sp. dp. 3/6; dp. 3/6; dp. 4/6.

ALL PURPOSE HEADPHONES
 H.R. HEADPHONES 2000 ohms Super Sensitive. 35/-
 LOW RESISTANCE HEADPHONES 3-5 ohms. 39/6
 DE LUXE PADDED STEREO PHONES 8 ohms. 79/6

"THE INSTANT"

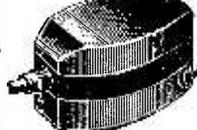BULK TAPE ERASER AND RECORDING HEAD 42/6 Post 2/6
DEMAGNETISER 200/250 v A.C. Leaflet S.A.E.
 Minimum Post and Packing 2/6.



RADIO COMPONENT SPECIALISTS
 Full List 1/- Written guarantee with every purchase. (Export: Remit cash and extra postage.)

BARGAIN STEREO/MONO SYSTEM
 Attractive Slim PLAYER CABINET with B.S.R. Stereo Autochanger, 3 valve Stereo Amplifier, two 6 1/2in. LOUD-SPEAKERS. (Only 4 pairs of wires to join). Carr. 10/6. S.A.E. for details **£19.19.6**

NEW TUBULAR ELECTROLYTICS

2/350V .. 2/3 100/25V .. 2/7	8/600V .. 9/6
4/350V .. 2/3 250/25V .. 2/6	16/600V .. 12/6
8/450V .. 2/3 500/25V .. 4/-	16+16/500V .. 7/6
16/450V .. 3/- 8+8/450V .. 3/6	50+50/350V .. 7/-
32/450V .. 3/9 8+16/450V .. 3/9	60+100/350V 11/6
25/25V .. 1/9 16+16/450V 4/3	32+32+32/350V 8/-
50/50V .. 2/- 32+32/350V 4/6	100+50+50/350V 9/6

SUB-MINI. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mF 15V 7/- 500, 100mF 12V 3/6; 2000mF 25V 7/-, CERAMIC. 500V 1pF to 0.01mF, 9d.
 PAPER 350V-0.1 9d. 0.5 2/6; 1mF 3/4; 2mF 150V 3/- 500V-0.001 to 0.05 9d; 0.1 1/1; 0.25 1/6; 0.5 3/6.
 1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 0.047, 0.1, 2/6.
 SILVER MICA. Close tolerance 1%, 5-5000pF 1/-; 560-2,200pF 2/-; 2,700-5,600pF 3/6; 6,800pF 0.01 mfd 6/- each.
TWIN GANG, "0-0" 20pF+176pF, 10/6; 365pF, miniature 10/6; 500pF standard with trimmers, 12/6; 500pF midset less trimmers, 7/6; 500pF slow motion standard 9/-; small 3-gang 500pF 19/6. Single "0" 365pF 7/6. Twin 10/6.
SHORT WAVE, Single 10pF, 25pF, 50pF, 75pF, 100pF, 160pF, 200pF, 10/6 each.
TUNING, Solid dielectric 100pF, 300pF, 500pF, 7/- each. TRIMMERS, Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF 750pF, 1/9; 100pF 2/6.
RECTIFIERS CONTACT COOLED +wave 60mA, 7/6; 85mA, 9/6.
SILICON BYZ13, 6/-; BY100, 10/-
 Full wave Bridge 75mA 10/-; 150mA 19/6; TV rects. 10/-
NEON PANEL INDICATORS 250mv. AC/DC Red. Amber 4/6.

RESISTORS, Preferred values, 10 ohms to 10 meg
 1 w. 1/4 w. 1 w. 20% 3/4; 1 1/2 w. 8d. 2 w. 1/1; 1 w. 10% 6d.
HIGH STABILITY, 1/4 w. 1 1/2 w. 10 ohms to 10 meg. 2/- Ditto 5% Preferred values 10 ohms to 22 meg., 9d.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 2/- each; 3 watt, 0.5 ohms to 8.2 ohms, 2/-
BRAND NEW TRANSISTORS 6/- each
 OC71, OC72, OC81, OC44, OC45, AF117
 MAT100, 79; MAT105, MAT170; MAT121, 8/6.
REPANCO TRANSISTOR TRANSFORMERS
 TT45, Push Pull Drive, 9:1 CT, 6/-; TT46 Output, CT 8:1 6/-; TT49 Interstage, 4.5:1, 6/-; TT52 Output 3 ohms, 20:1 6/-; TT23/4 PAIR 10 watt Amp. Transformers and circuit 35/-.

TRANSISTOR MAINS POWER PACKS, FULL WAVE
 9 volt 500mA. Size 4 1/2 x 2 1/2 in. Metal case. Crackle finish. Output terminals. On/off switch **49/6**
 Half Wave 9 volt 50mA. Size 2 1/2 x 1 1/4 in. Snap terminals 32/6.
 9 volt 500mA. TRANSFORMER ONLY. 2 1/2 x 1 1/4 x 1 1/4 in. 10/6.

MAINS TRANSFORMERS

250-0-250 50 mA. 6.3v. 2 amps. centre tapped	19/6
250-0-250 80mA. 6.3v. 3.5 a. 6.3v. 1a. or 5v. 2a	35/-
350-0-350 80mA. 6.3v. 3.5 a. 6.3v. 1a. or 5v. 2a	35/-
500-0-500 120mA. 6.3v. 4a. C.T.; 6.3v. 2a	45/-
MINIATURE 200v. 20mA. 6.3v. 1a 2 1/2 x 2 1/4 in.	12/6
MIDGET 220v. 45mA. 6.3v. 2a. 2 1/2 x 2 1/2 in.	17/6
HEATER TRANS. 6.3v. 1 1/4, 8/6; 6.3v. 4a. 12/6	
Ditto, tapped sec. 1.4v. 2, 3, 4, 5, 6, 3v. 1 1/2amp. 12/6	
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30v. at 2a. 35/-	
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. 35/-	
AUTO TRANSFORMERS 0.15-230v. Input/Output. 60w. 18/6; 150w. 35/-; 500w. 92/6; 1000v. 195/-	
CHARGER TRANSFORMERS. Input 200-250v. for 6 or 12v. 1 1/2amp. 22/-; 4 amp. 35/-	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. Output. 1 1/2 amp 8/9; 2 amp. 11/3; 4 amp. 17/6.	

COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE 2/-
OUTLET BOXES, SURFACE OR FLUSH 4/6.
MINIATURE TWIN FEEDERS 1 1/4 in. 80 ohms or 300 ohms.
JACK SOCKET Std. open-circuit 2/6, closed circuit 4/6;
 Chrome Lead Socket 7/6. Phono Plugs 1/-, Phono Socket 1/-
JACK PLUGS Std. Chrome 3/1; 3.5mm Chrome 2/6.
DIN SOCKETS Chassis 3-pin 1/6; 5-pin 2/-, DIN SOCKETS Lead 3-pin 3/6; 5-pin 5/-, DIN PLUGS 3-pin 3/6; 5-pin 5/-
VALVE HOLDERS, 9d., CERAMIC 1/-; CANS 1/-

T.S.L. LOUDSPEAKER CROSSOVER HLP2

2-way crossover for 8 or 15 ohm speakers and tweeters, 3 phono input/output sockets.
 Made to sell OUR PRICE **22/6**
 at 42/- Post 2/6

Tape Spools 2/6. Tape Splice 5/-. Leader Tape 4/6.
 Reuter Tape Heads for Collaro models 2 track 2 1/2" pair.
PHOTO-ELECTRIC RELAY SYSTEM, 240v. AC.
 Exciter and relay unit with infra red filter.
 For counting, door signals, alarms, etc. **£12** Post Free

MINI-MODULE LOUDSPEAKER KIT

10 WATT 65/- CARRIAGE 5/-
 Triple speaker system combining on ready cut baffle, 1/2in chip-board 18in x 8in. Separate Bass, Middle and Treble Loudspeakers and crossover condenser. The heavy duty 5in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm.

TEAK VENEERED BOOKSHELF ENCLOSURE
 16 x 10 x 9in. Modern Scandinavian fluted **94/6** Post 5/- front design for Mini-Module

ALL MODELS "BAKER SPEAKERS" IN STOCK




BAKER SPEAKER £8

30-14,500 c.p.s., Hi-Fi double cone woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 Gauss and a total flux of 145,000 Maxwells. Bass Response 45 cps. Rated 20 wats. Voice coils available 3 or 8 or 15 ohms. PRICE £8. or Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions **£10.19.6**

BAKER "GROUP SOUND" SPEAKERS — POST FREE
 "GROUP 25" "GROUP 35" "GROUP 50"
 12in. 12in. 15in.
 25 watt 6 gns. 35 watt 8 gns. 50 watt 18 gns.
TEAK HI-FI SPEAKER CABINET, Fluted wood front.
 For 10 or 12in round. Loudspeaker £8.10.0
 For 13 x 8in. or 8in round Loudspeaker £4.14.6
 For 10 x 6in. or 6in. round Loudspeaker £3.16.6
LOUDSPEAKER CABINET WADDING 18in wide, 2/6ft.

Goodmans Tweeter 3 1/2in 3 ohm 35/-, EMI 2 1/2in 8 ohm 17/6, Horn Tweeters 2-18kc/s, 10W 150hm 29/6, Crossover 16/6, LOUDSPEAKERS P.M. 3 ohms, 2 1/2in, 3in, 4in, 5in, 5 x 2 1/2in, 7 x 4in 17/6 each; 6 1/2in 22/6; 8 x 5in, 2 1/4 x 8 1/2in, 5in, 10 x 6in 30/-; 10in and 12in, Double cone 3 or 15 ohm 39/6, E.M.I. Double Cone 13 1/2in, 3 or 15 ohm 10 in. 45/-, DITTO Twin tweeters and X/over, 3 or 8 or 15 ohm 10w 79/6, SPECIAL OFFER: 8 ohm, 2 1/2in; 6 x 4in; 8 ohm 2 1/2in, 2 1/2in. 15/6 EACH 2 w. 6 x 4in x 30 ohm; 3in; 15 ohm 12in. 7 x 4in, 8 x 5in.
 8in. LOUDSPEAKER UNITS 3 ohm 27/6; 15 ohm 30/-; ELAC 8in. De Luxe Ceramic 3 ohm 45/-; 15 ohm 50/-
 8in. LOUDSPEAKER TWIN CONE 3 ohms 35/-; 15 ohm 39/6, OUTPUT TRANS. EL84 etc. 4/6; MIKE TRANS. 50L 3/9, SPEAKER COVERING MATERIALS. Samples Large S.A.E.

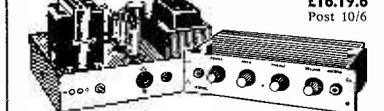THE FAMOUS "MULLARD 510" £16.19.6 Post 10/6



Main power, amplifier and 2 valve pre-amplifier. Silver grey face panel. Volume, treble, bass controls, Function switch: Radio, Tape 1, Tape 2, Mic., Gram LP, Gram 78, Tape output socket. Valves: 2 x EL84, 3 x EF86, 1 x ECC83, 1 x EZ81. Ultra linear Farnok output transformer, 20 db negative feedback, 10 watts rms. mono 3 and 15 ohm output. Brand new. Guaranteed.

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES
 45-page Eagle catalogue 5/- Post free

BARGAIN AM TUNER, Medium Wave **79/6**
 Transistor Superhet, Ferrite aerial, 9 volt.

BARGAIN DE LUXE TAPE SPLICER, Cuts, trims joins for editings and repairs. With 3 blades **17/6**

BARGAIN 4 CHANNEL TRANSISTOR MIXER
 Will mix musical highlights and sound effects to recordings mix Microphone, records, tape and tuner with separate controls into single output. 9volt. **59/6**

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. Ready built. Printed Circuit. Calibrated slide dial tuning. Size 6 x 4 x 2 1/4in. 9 volt. **£6.19.6**

BARGAIN 3 WATT AMPLIFIER, 4 Transistor Push/Pull Ready built, with volume control. 9v. **69/6**

★ RADIO BOOKS ★ (Postage 9d.)

Practical Transistor Receivers	5/-
Practical Radio Inside out	4/6
Super-sensitive Transistor Pocket Radio	3/6
Radio Valve Guide Books 1, 2, 3 or each 5/- No. 5 ea.	6/-
T.V. Fault Finding 405/625 lines	8/6
Shortwave Transistor Receivers	5/-
Transistor Communication Sets	6/-
Modern Transistor Circuits for Beginners	7/6
Sub-Miniature Transistor Receivers	5/-
Wireless World Radio Valve Data	9/6
International Radio Stations Guide	2/6
Receive foreign TV programmes by simple modifications	5/-
Valves, Transistors and Diodes equivalents Manual	10/6

3 inch MOVING COIL METERS BRITISH MADE
 Various calibrations/movements, 500 Micro-amp! 1 Milliamp; 50-0-50 Microamp, etc. S.A.E. for list **37/6**

BRAND NEW QUALITY EXTENSION LOUDSPEAKER

Handsome plastic cabinet 20ft. lead and adaptor. For any radio, intercom, tape recorder, etc. 3 to 15 ohms. Size: 7 1/2 x 5 1/2 x 3in. POST 2/6. **30/-**

CALLERS WELCOME. CUSTOMERS FREE CAR PARK.
337 WHITEHORSE ROAD, WEST CROYDON
 Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)
 Buses 133 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665

BOOKS BY G. A. BRIGGS

OVER A QUARTER OF A MILLION COPIES SOLD SINCE 1948

AERIAL HANDBOOK (second edition)

176 pages, 144 illustrations.

PRICE (semi-stiff cover) 15/- (16/6 post free).

Cloth bound 22/6 (24/- post free).



CABINET HANDBOOK

112 pages, 90 illustrations

PRICE (semi-stiff cover) 7/6 (8/6 post free).

Cloth bound 15/- (16/6 post free).



AUDIO BIOGRAPHIES

344 pages, 64 contributions from pioneers and leaders in Audio. Cloth bound.

PRICE 25/- (27/- post free).



MUSICAL INSTRUMENTS AND AUDIO

240 pages, 212 illustrations. Cloth bound.

PRICE 32/6 (34/6 post free).



LOUDSPEAKERS

Fifth edition—336 pages, 230 illustrations
Cloth bound.

PRICE 30/- (32/6 post free).



A TO Z IN AUDIO

224 pages, 160 illustrations. Cloth bound.

PRICE 15/6 (17/- post free).



PIANOS, PIANISTS AND SONICS

190 pages, 102 illustrations. Cloth bound.

PRICE 18/6 (20/- post free).



ABOUT YOUR HEARING

132 pages, 112 illustrations

PRICE (semi-stiff cover) 15/6 (16/6 post free)

Cloth bound 22/6 (24/- post free).



LETTERS FROM ABROAD

I have recently been going through eight of your books and they have been a feast of information. I have been like a dog with eight tasty dishes, not knowing which one to tackle first but nipping about and sampling each one.

Somerset, Sept. 69

Having read the majority of your 'Bibles on Hi Fi', of such a remarkably 'hi' standard, I eagerly await a copy of your Cabinet Handbook.

London N22, Nov. 69

Please send orders and enquiries to:—

**RANK WHARFEDALE BOOK DEPT. B.W.S.
13 WELLS ROAD ILKLEY YORKS**


Telephone: ILKLEY 4246

Published by:

RANK WHARFEDALE LTD IDLE BRADFORD YORKSHIRE

F.A.L. 'PHASE 100'

Public Address Amplifier

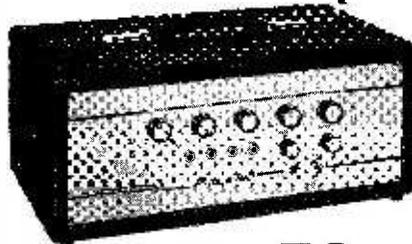

A superb solid state A.C. Mains unit for vocal and Instrumental groups and General Public Address use.

59 Gns

Recommended Retail price

- ★ 70 Watts RMS Output
- ★ Output matching for speakers from 3-30 ohms
- ★ 4 separately controlled inputs plus master
- ★ Separate Bass and Treble Controls
- ★ Frequency Response 20c.p.s. to 30 Kcs
- ★ High Sensitivity

Send S.A.E. for fully descriptive leaflet

Available from your local Dealer

Wholesale and Retail enquiries to Manufacturers

FUTURISTIC AIDS LTD, 103 Henconner Lane, Leeds 13

M. & B. RADIO

15a HUNSLET ROAD, LEEDS LS10 1JQ

Telephone: 0532-35649

STEREO CABINETS. A beautifully finished polished wood cabinet supplied in original carton. Size approx. 22 x 16 x 8in. New 47/6 plus 6/6 carriage.



TELEMETERS. A well finished cabinet containing lots of useful items for the constructor. Endless tape unit and tape head, 2 motors, auto and mains transformers, miniature valve I.F. strip etc. Ideal for modifying or stripping. 77/6 plus 7/6 carr.



STETHOSCOPE HEADSETS. Brand New. Ideal for stereo or mono. Low impedance. 27/6 plus 3/6 pp.

MICROPHONES. Radiotelephone type, used. 5/- plus 2/- pp.

SPRING LOADED aerial base sections. New 6/6 plus 1/6 pp.

TRANSISTORISED 2 METER CONVERTERS. Please state preference of I.F. frequency when ordering. £7.15.0 plus 5/- pp. 4 metre models available at the same price. VHF Marine band model £8.5.0 plus 5/- pp.

VHF MOBILE TX/RX. Miniature valve xtal controlled transmitter with 12 volt transistorised power unit. Internal speaker. Double conversion receiver easily modified to tuneable. Ideal for 4 metres. £9.10.0 plus 27/6 carriage.

MODULATION TRANSFORMERS. scr522 type. 7/6 plus 2/- pp.

AERIAL CHANGE OVER RELAYS 12 volt. Used 4/- plus 1/6 pp.

60 UNTESTED DIODES 2/6 plus 1/- pp.

60 UNTESTED TRANSISTORS 5/- plus 1/- pp.

2-3W. INTEGRATED CIRCUIT AMPLIFIERS. Tested £1, plus 1/- pp.


USED TESTED VALVES, QQV03/10 6/-, 6AQ5 3/-, 6BJ6 1/6, ECC83 2/6. 5U4 6/-, all plus 1/6 pp.

LOTS OF OTHER EQUIPMENT

PLEASE SEND 6d. PLUS S.A.E. FOR LIST

MONO TRANSISTOR AMPLIFIER HSL-700

A really high fidelity monoaural amplifier with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier supply for AC mains 200-240v. Controls: Bass, Treble, Volume/on/off. Function selector for P.U.1, P.U.2, Tape, Radio. The HSL-700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9 1/2 x 5 1/4 x 4 in. Sensitivity: P.U.1-50mV/v, 56K input impedance.

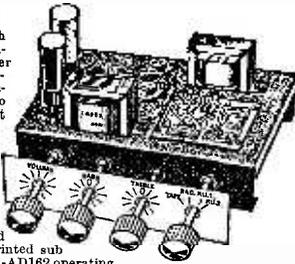

P.U.2-110mV/v, 1 meg input impedance. Tape-110mV/v, 1 meg input impedance. Radio-110mV/v, 1 meg input impedance. Output power measured at 1Kc-6.2 watts RMS into 3 ohms, 5.8 watts RMS into 15 ohm. Overall frequency response 30 c/s-18 Kc/s: Continuously variable tone controls; Bass, + 8 db to - 12 db at 100 c/s. Treble, + 10 db to - 10 db at 10 Kc/s. The HSL-700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, full circuit diagram and operating instructions.

Our Special Price **£7.19.6** P. & P. 7/6.

LOUDSPEAKER BARGAINS

5in. 3 ohm 16/- P. & P. 3/7. 7 x 4in. 3 ohm 21/- P. & P. 4/- 10 x 6in. 3 ohm 27/6 P. & P. 6/- E.M.I. 5 in. 3 ohm with high flux magnet 21/- P. & P. 4/- E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 45/-) P. & P. 6/- E.M.I. 13 x 8in. 3 or 15 ohm with two inbuilt tweeters and crossover network 4 gns. P. & P. 6/7.
BRAND NEW. 12in. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly 25.10.0 P. & P. 7/6. Guitar magnets: 25w. 28.0.0. 35w. 28.0.0. E.M.I. 8 1/2in. HEAVY DUTY TWEETERS. Power/ceramic magnet. Available in 3 or 3 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.
12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 15 ohm 37/6. P. & P. 6/-

35 OHM SPEAKERS

3 1/2in. 14/- P. & P. 2/6; 7 1/2in. 21/- P. & P. 4/-
80 OHM MOVING COIL SPEAKERS
High Flux Magnet. 2 1/2in. dia. 12/- each. P. & P. 1/6.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 18/6. P. & P. 1/6.
HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/- P. & P. 1/6.
HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity. 39/6 P. & P. 2/6.

FYE MICROSWITCHES S/P. C/O. Lever roller action. Rating 250v. AC at 5 amps. Size approx. 1 1/2 x 1/2 x 4/8 each. P. & P. 1/- (6 or more post free).
HONEYWELL MICROSWITCHES. S/P. C/O. Push button action. Rating 250v. AC at 15 amps. Size approx 1 1/2 x 1 1/2 x 5/8 each. P. & P. 1/- (6 or more post free)

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7in. to approx. 56in. Maximum diameter 7in. 10/- each. P. & P. 1/6. 6 section Lacquered Brass. Extends from 6in. to 22 1/2in. approx. Maximum diameter 1 1/2 in. 5/- each. P. & P. 1/6.

TRANSFORMER BARGAINS!

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations: 0-5-10-15-20-25-30-35-40-50w. half wave at 1 amp. or 10-20-30-40-50-60-80-100-120-150-200-240v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price 32/6. P. & P. 6/-.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. 11/- P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA 12/6 P. & P. 2/6.

BRAND NEW MAINS TRANSFORMERS for Bridge Rectifier. Pri. 240v. AC. Sec. 240v. at 50mA and 6.3v. at 1.5 amp. Stack size 2 1/2 x 3 1/2in. 10/6. P. & P. 3/6. (Special quotations for quantities.)

BRAND NEW! FARMERCO MAINS TRANSFORMERS Primary 110v. Secondary 350-0-350v. 100 mA and 6.3v. at 2 amps, 6.3v. at 2 amps and 6.3 v. at 1 amp. Conservatively rated. Fully impregnated Electrostatic screen. Suitable for vertical or drop through mounting. Overall size 4 1/2 x 3 1/2 in. Weight 8 lb. Limited number only at 37/6. P. & P. 8/6.

SPECIAL OFFER!!

Your opportunity to acquire a first class HI-FI LOUD-SPEAKER SYSTEM at an extremely moderate price! Beautifully made teak finish enclosure with most attractive Tygan front. Size 16 1/2" high x 10 1/4" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 15 ohm impedance.

OUR PRICE WHILE LIMITED STOCKS LAST

8 GNS.

Carriage 10/-

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class HI-FI Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W, mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 410.0p.

PRICES: AMPLIFIER KIT £10.10; POWER PACK KIT £3.0; CABINET £3.0. All Post Free. Also available STEREO 8+8 MK II above but 10 watts per channel. PRICES: AMPLIFIER KIT £12. POWER PACK KIT £3.10. Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).

Official stockists of all PEAK SOUND HI-FI EQUIPMENT*

including the P.W. DOUBLE 12 STEREO AMPLIFIER as featured in Practical Wireless April, May and June issues. Component pack as specified. Total cost £23.5.0 Plus P. & P. 1/6. (Excluding metalwork, knobs, plugs and sockets and fuses).



SPECIAL PURCHASE!


E.M.I. 4-SPEED PLAYER Heavy 3 1/2in. metal turntable. Low distortion performance 200/250 v. shaded motor (90 v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY 63/- P. & P. 6/6.

QUALITY RECORD PLAYER AMPLIFIER MKII

A top quality record player amplifier employing heavy duty double wound mains transformer, EC83, EL84, E230 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in deep x 6in. high. Ready built and tested. PRICE 75/- P. & P. 6/-.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

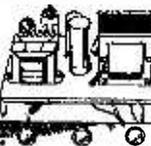DELUXE QUALITY PORTABLE R/P CARRIER MKII Cutout motor board size 14 1/2 x 12in. clearance 3in. below. 5 1/2in. above. Will take amplifier and any B.S.R. or GARRARD autochanger or Single Player Unit (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 79/6. P. & P. 9/6.



3-VALVE AUDIO

AMPLIFIER HA34 MK II. Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E230 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.15.0. P. & P. 6/-.


EST. "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/- V1510p 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G389 (NPN) 3/-; Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 25/-; ORP12 Cadmium Sulphide Cells 10/6. All post free.

YVAINR AND REXINE SPEAKER AND CABINET FABRICS. Approx. 54in. wide. Usually 35/- yard. Our PRICE 15/- per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

POWERFUL COMPACT MOTOR for 6-9v. Battery operation approx 25 mA. Made originally for "Staar" and "Greencoat" record player decks. Built in constant speed device. Ideal for models etc. Overall size approx 1 1/2 x 1 1/2 x 7/8 each. P. & P. 1/6 (3 or more Post Free)

DE LUXE STEREO AMPLIFIER

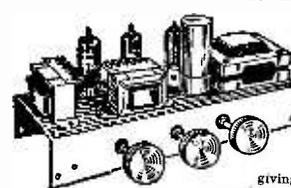

A.C. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: —2 x ECL86 Triode Pentodes, 1 x E230 as full wave rectifier. Two Dual pentodes are provided for bass and treble control, giving bass and treble boost and cut. A Dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV/v. For full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs. Chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. PRICE 85/- P. & P. 8/-.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing. B.S.R. UA25 with latest mono compatible cart. £619.6 All plus Carriage and Packing 6/6

LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60 etc. Send S.A.E. for latest Prices!


PLINTH UNITS cut out for Garrard Models, 1025, 2025, 2000, 3000, AT60, SP25. With transparent plastic cover. OUR PRICE 5 gns. complete. P. & P. 8/6.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. Only 32/6. P. & P. 2/-.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/- P. & P. 2/-.

SONOTONE 9TACH compatible Stereo Cartridge with diamond stylus 50/- P. & P. 2/-.

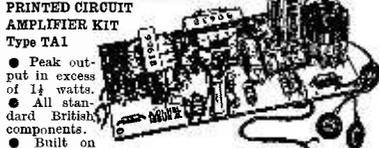HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT



Type TAI
● Peak output in excess of 1 1/2 watts.
● All standard British components.
● Built on printed circuit panel size 5 x 3in.
● Generous size Driver and Output Transformers.
● Output transformer tapped for 3 ohm and 15 ohm speakers.
● Transistors (GET114 or S1 Mullard AC128D and matched pair of AC128 o/p). ● 9 volt operation.
● Everything supplied, wire, battery clips, solder, etc.
● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/- P. & P. 3/-
● Also ready built and tested, 52/6. P. & P. 3/-.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 8-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up: EL84s, ECC83, EF86 and E230 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.9.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets. £9.5.0. P. & P. 8/6.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, E230 rectifier and ECL86 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. FEW ONLY.
OUR ROCK BOTTOM BARGAIN PRICE **49/6** P. & P. 6/-

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Please write clearly
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



MICRO SWITCH
5 amp. changeover contacts.
1/9 each, 18/- doz.



SUPPRESSOR CONDENSER TCC
.1 mfd. 250 v. A.C. working metal case with fixing lug. 1/9 each, 18/- doz.

Tubular Type by Phillips
500W. 29/6 plus 4/6 post and insurance.


BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at 27/6 each we offer these while our stocks last at only 12/6 each.

DIAMOND H OVEN THERMOSTAT
Type 20 with capillary tube and sensor. 20 amp A.C. type as fitted to many cookers adjustable by control knob (not supplied) 12/6 each.

BLACK LIGHT

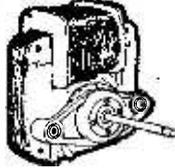G.E.C. tube for experiments and special lighting—40 watt 2ft tubes only 18/6 each. Holders and control gear 19/6, postage on single item 4/6 inc. insurance, or both items ordered together postage 6/6 inc. insurance.



MAINS MOTOR

Precision made—used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snp at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.

INSTRUMENT MOTOR WITH GEARBOX

Made by famous Smiths Company. Very powerful, although only quite small. Overall dimensions approx. 1 1/2 in. deep by 2 in. dia. Following models available. Please specify required speed. Revs. per hour 2—8—12. Revs. per hour 1, 2, 4, 6, 12, 20, 30. Revs. per minute 1, 2, 3, 4, 6, 8, 15, 30, 60, 17 1/2 each.



DRILL CONTROLLER

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Made up model 37/6 plus 2/6 p. & p.



WAFER SWITCHES TO YOUR REQUIREMENTS

Standard Size 1 1/2 wafer—silver plated 5 amp contact standard 1/2" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	10 way	12 way
1 pole	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
2 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
3 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
4 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
5 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
6 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
7 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
8 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
9 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
10 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
11 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
12 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6

Switches up to 10/6 each are from stock—others 7 days.

TANGENTIAL HEATER UNIT



Winter is coming but act today and you won't dismay. This heater unit is the very latest type, most efficient and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor impeller, 2 kw. element and 1 kw. element allowing switching 1, 2 and 3 kw. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs on/off switch. 79/6, postage & insurance 6/6. Don't miss this.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

SOLDER GUN

A must for every busy man. Gives almost instant heat; also illuminates job. 100 watt 220/240v. 39/6 (saves you over 30/-), post & ins. 4/6. BIG JOB 250 watt model 99/6 (saves you over £3.10.0), post and ins. 6/6.



BURGLAR ALARM KIT

Protect your home and family by frightening away the intruder. With our circuit a mains operated bell rings loudly directly the door or window is opened. Kit comprises 12 reed switches, 12 magnets, relay mains transformer and bell with circuit. Price 49/6.

Mains Transistor Power Pack

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (Class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

THE ERGOTROL UNITS

These units made by the Mullard Group for operating and controlling d.c. Motors and equipment from A.C. mains. Thyristors are used and these supply a variable d.c. resulting in motor speed control and operating efficiency far superior to most other methods. The units are contained in wall mounting cabinets with front control panel on which are fuses—push buttons for on/off and the variable thyristor firing control. Four models are available—all are brand new in makers' cases: Model 2410 for up to 5 amps £17.10.0, 2411 10 £27.10.0, 2413 45 £47.10.0, 2415 80 £95.0.0.

Note: 2415 is a floor mounting unit.

RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. 29/6—twin stethoscope instead of earpiece 11/- extra—post and ins. 2/9.



ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH
Also 102/3 Tamworth Road, Croydon

THE RSGB AMATEUR RADIO CALL BOOK

1970 edition containing 120 pages.

Complete up to date listing of all amateur stations in the U.K. and Eire together with much operating information including beam headings and list of prefixes.

7s 3d post paid

over
16,000

copies sold

Now in its
second printing

Radio Communication Handbook

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. The standard work in its field.

69s post. paid

World at Their Fingertips

The first and only complete story of the evolution of Amateur Radio to be published. An entertaining and instructive account of notable events and progress from the first days up to the present period. This book is published in two styles: a hardbound version and a paperback. Both contain 308 pages and are profusely illustrated. De-luxe hardbound version 50s, paperback 14s 6d (both post paid)

Obtainable from:

RADIO SOCIETY of GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1

17in.—£11.10.0 TWO-YEAR GUARANTEE 19in. BBC 2 EX-RENTAL TELEVISIONS FERGUSON 39 Gns.


FREE ILLUSTRATED LIST OF TELEVISIONS

17"—19"—21"—23"
Wide range of models, sizes and prices


Carr. ins. on all sets 30/-
DEMONSTRATIONS DAILY

TWO-YEAR GUARANTEE REGUNNED TUBES

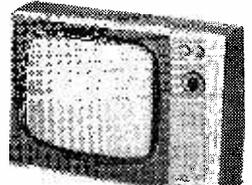70° and 90° 14in.—69/6, 17in.—69/6, 21in.—99/6, 110° 17in., 19in. and 21in.—99/6, 23° (not bonded)—119/6. Exchanged bowis. Carr. 10/6.



COCKTAIL/STEREOGRAM CABINET 15 gns.

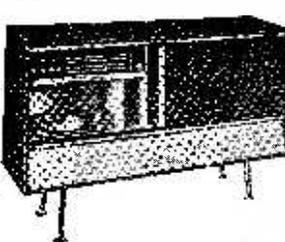

Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35 1/2 in., width 52 1/2 in., depth 14 1/2 in. Legs 1 gn. extra.

Speakers 10"-1: 3 1/2"—25Ω, 4"—10Ω. 7" x 4" —3Ω. Brand new. P. & P. 2/6 Asstd. Condensers: 10/- for 50. P. & P. 7/6. Asstd. Resistors: 10/- for 50. P. & P. 4/6. Asstd. Controls: 10/- for 25. P. & P. 7/6. Transistors: Mullard matched output kit 9/6-OC81D—2 OC81's. P. & P. FREE.

Ferrite Rods 3/6: 6", complete with LW/MW Coils. P. & P. FREE.

TRANSISTOR CASES 19/6. Cloth covered, many colours. Size 9 1/2" x 6 1/2" x 3 1/2" P. & P. 4/6. Similar cases in plastic 7/6.

RECORD PLAYER CABINETS 49/6. Cloth covered, size 16 1/2" x 14 1/2" x 8". Takes any modern autochanger. P. & P. 7/6.

SINGLE PLAYER CABINETS 19/6. P. & P. 7/6.

STRIP LIGHT TUBES 3/9 each, 11" (284 mm.) 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting etc. 6 for £1. P. & P. free.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, London, E12 Tel. 01—478 6001/2/3

SEMICONDUCTORS

BRAND NEW AND FULLY GUARANTEED

1N914	1/6	2N2905A	8/	ACV22	4/	BD124	21/6	MJ490	22/6
1N916	1/6	2N2906A	8/	AD128	4/	BD124	12/	MJ491	22/6
1N921	4/	2N2923	4/	AD140	8/	BF115	5/	MPP102	8/6
1N925	5/	2N2924	4/	AD149	11/6	BF117	10/6	MPP103	7/6
1N113	3/	2N2924	4/	AD161	7/6	BF167	5/6	MPP104	7/6
1N126	2/6	2N2925	3/6	AD162	7/6	BF173	7/6	MPP105	8/
1N121	2/6	2N2926	3/	AF114	5/	BF180	7/	NK10013	8/6
1N130	2/6	Yellow	2/9	AF116	5/	BF181	6/	NK1216	4/
1N131	2/6	Orange	2/9	AF117	5/	BF184	7/6	NK1261	8/6
1N132	2/6	2N3011	12/6	AF118	12/6	BF194	5/	NKT261	4/
1N44	2/	2N3053	6/6	AF124	4/6	BFX12	4/6	NKT262	4/
2N301	4/	2N3053	6/6	AF125	4/6	BFX13	4/6	NKT264	4/
2N302	4/	2N3054	12/6	AF126	4/	BFX29	12/6	NKT271	4/
2N303	4/	2N3055	15/	AF127	3/6	BFX30	9/	NKT272	4/
2N371	3/	2N3702	3/6	AF139	7/6	BFX33	19/6	NKT274	4/
2N686	4/6	2N3703	4/6	AF181	8/6	BFX43	8/6	NKT275	4/
2N697	5/	2N3704	4/6	AF186	11/	BFX44	8/6	NKT281	5/6
2N698	4/6	2N3705	4/	AF239	7/6	BFX84	7/6	NKT403	15/
2N706	2/6	2N3706	4/6	AF212	8/6	BFX85	9/	NKT404	12/6
2N706A	2/6	2N3707	4/	ASV26	5/6	BFX86	6/6	NKT406	15/
2N708	4/	2N3708	3/6	ASV27	8/6	BFX87	6/6	NKT613	6/6
2N929	5/6	2N3709	3/6	ASV28	5/6	BFX88	5/	NKT674	5/
2N930	7/	2N3710	4/	ASV29	5/6	BFY10	4/6	NKT677	5/
2N1080	6/6	2N3711	4/	ASZ20	7/6	BFY17	4/6	NKT718	5/
2N1091	6/6	2N3819	9/	ASZ21	7/6	BFY18	4/6	NKT773	5/
2N1131	6/6	2N3820	20/6	BAV13	2/6	BFY19	4/6	NKT774	6/
2N1132	6/6	2N4058	5/6	BAV16	2/6	BFY20	12/6	NKT20329	8/6
2N1362	3/6	2N4059	5/	BAV31	1/6	BFY41	10/	NKT80111	
2N1303	3/6	2N4060	5/	BAV38	3/6	BFY43	12/6		15/6
2N1304	4/6	2N4061	4/6	BC107	3/6	BFY50	4/6	NKT80112	
2N1305	4/6	2N4062	4/6	BC108	3/6	BFY51	4/6		19/6
2N1306	5/	2N4254	8/6	BC109	3/6	BFY52	4/6	NKT80113	
2N1307	5/	2N4255	8/6	BC118	6/6	BFY77	11/6	OA5	2/6
2N1308	6/	2N4285	3/6	BC116	12/6	BFY80	12/6	OA9	2/
2N1309	6/	2N4286	3/6	BC118	6/6	B8A19	3/6	OA70	1/6
2N1307	5/6	2N4286	3/6	BC125	11/	B8A20	3/6	OA73	2/
2N1613	5/6	2N4287	3/6	BC126	11/	B8A20	3/6	OA79	1/6
2N1711	6/6	2N4289	3/6	BC147	3/6	B8A26	7/6	OA81	1/6
2N1889	6/6	2N4291	3/6	BC148	3/6	B8A27	10/6	OA85	1/6
2N1893	8/6	2N4292	3/6	BC149	3/6	B8A28	6/	OA90	1/6
2N2142	15/	40361	12/6	BC167	3/6	B8A29	13/6	OA91	1/6
2N2147	14/6	40362	14/6	BC168B	3/6	B8A29	13/6	OA95	1/6
2N2160	14/6	3N128	18/6	BC168C	3/6	B8A29	4/	OA200	2/
2N2163	5/6	3N140	19/6	BC169B	3/6	B8A29	4/	OC26	6/6
2N2183A	5/6	3N141	21/6	BC169C	3/6	B8A29	4/	OC28	8/6
2N2194A	5/6	3N142	16/6	BC121	5/	B8A38	4/6	OC35	6/6
2N2217	6/6	AAZ13	2/	BCY30	5/6	B8A39	4/6	OC36	6/6
2N2218	6/6	AAZ15	2/6	BCY31	5/6	B8A40	6/6	OC44	4/
2N2219	6/6	AAZ17	2/6	BCY32	7/6	B8A51	8/6	OC45	2/6
2N2220	5/	AC107	*6/	BCY33	4/	B8A52	9/	OC71	2/6
2N2221	5/	AC126	4/	BCY34	4/6	B8A53	8/6	OC72	2/6
2N2222	6/6	AC127	5/	BCY38	4/6	B8A54	10/6	OC75	4/6
2N2308	5/	AC128	4/	BCY39	7/6	B8A55A	3/6	OC81	4/6
2N2369	5/	AC176	5/	BCY42	3/	BY100	4/6	OC83	4/6
2N2369A	5/6	AC187	12/	BCY43	3/	BYX10	5/6	OC81D	4/6
2N2539	4/6	AC188	12/	BCY54	7/6	BYZ10	9/	OC84	5/
2N2540	4/6	ACY17	5/	BCY70	4/6	BYZ11	7/6	OC139	6/6
2N2646	11/6	ACY18	5/	BCY71	8/6	BYZ12	6/	OC140	6/6
2N2904	8/	ACY19	5/	BCY72	4/	BYZ13	5/	OC200	6/6
2N2904A	9/	ACY20	5/	BD116	35/	MJ480	20/6	OC201	7/6
2N2905	8/	ACY21	5/	BD121	17/6	MJ481	27/6	OC202	10/6

MULLARD INTEGRATED CIRCUITS

FCH211 Hexuple DFL Inverter Gate	28/6
FCH221 Triple 3 Input DFL Line	28/6
FCJ101 3 Input JK Flip Flop	35/
TAA241 Operational Amplifier	47/6
TAA243 Operational Amplifier	47 6
TAA 263 Linear AF Amplifier	18/6
TAA320 Most LP Pre-amplifier	15/6

SPEAKERS (3 ohm)

10" - 6"	37/6
9" - 4"	23/6
8" - 5"	19/6
7" - 4"	15/6
5" - 3"	12/6
3" 9/6, 5" 14/6, 8" 27/6, 12" 39/6.	

Post and Packing 2/9

A. MARSHALL & SON
 28 CRICKLEWOOD BROADWAY, LONDON N.W.2
 01-452 0161/2/3 CALLERS WELCOME
 Post & Packing U.K. only, 1/6. Europe 10/-, Commonwealth (Air) 13/-.

THYRISTORS

1 AMP: 50V 5/-, 100V 5/6, 200V 7/-, 400V 9/6.
 3 AMP: 50V 6/-, 100V 7/6, 200V 8/-, 400V 10/6.
 ZENERS. 11 WATT 2.7-33V 4/6, 400m w 3.0-33V 5/-.

INTEGRATED CIRCUITS - R.C.A.

CA3005 30/-, CA3011 20/-, CA3012 25/-,
 CA3013 30/-, CA3014 30/-, CA3018 25/-,
 CA3019 25/-, CA3020 27/6, CA3021 42/6,
 CA3022 85/-, CA3023 27/6, CA3024 27/6,
 CA3028A 25/-, CA3028B 35/-, CA3035 35/-,
 (CA3036 20/-).
 PAIRCHILD
 L900, 914 11/-, L923 14/-.
 DATA SHEETS FOR RCA DEVICES 2/- per type.

Presets std. horiz. or vert. 1/6
 Potentiometers, Log Lin 3/3 each

MFD	V	Price	MFD	V	Price	MFD	V	Price
1	15	1/6	25	10	1/6	200	6-4	1/9
1	40	1/6	25	25	1/6	200	16	2/
2	15	1/6	25	50	1/6	250	25	2/9
2	350	2/-	32	15	1/6	250	50	3/9
2-5	16	1/9	32	450	1/6	320	10	1/6
4	15	1/6	40	6-4	1/6	400	16	2/9
4	40	4/6	40	16	1/6	500	6	2/6
4	350	2/3	50	12	1/6	500	25	3/9
5	15	1/6	50	25	1/6	500	50	4/9
6-4	6-4	1/9	50	50	2/-	640	16	3/6
8	18	1/6	64	25	1/6	1000	12	3/9
8	40	1/6	80	6-4	1/6	1000	16	4/
8	450	3/-	80	16	1/6	1000	55	5/6
10	15	1/6	100	6-4	1/6	1000	50	7/6
10	25	1/6	100	12	1/6	2000	25	8/6
12-5	25	1/9	100	25	1/6	2000	50	12/6
16	18	1/6	100	50	2/6	2500	25	9/6
25	6-4	1/6	125	4	1/6	3000	25	12/6

VEROBOARD		RESISTORS	
-15 Matrix -1 Matrix		1 watt 10%, 4d.	
21"	3 3/8	3/6	4/
21"	5"	4/3	4/9
31"	3 3/8	4/3	4/9
31"	5"	5/6	5/6
21"	17"	12/6	12/6
31"	17"	16/-	21/6
Cutter	9/		1 watt Metal Oxide, 1/6



and work at the nerve centres of civil aviation

The National Air Traffic Control Service of the Board of Trade needs Radio Technicians to install and maintain the very latest electronic aids at Civil Airports, Air Traffic Control Centres, Radar Stations and specialist establishments. Vacancies exist in various parts of the United Kingdom.

This is responsible demanding work (for which you will get familiarisation training) involving communications, computers, radar and data extraction, automatic landing systems, and closed-circuit television. It offers excellent prospects with ample opportunities to study for higher qualifications in this fast-expanding field.

If you are 19 or over, with at least one year's practical experience in telecommunications, fill in the coupon now. Preference will be given to those having ONC or qualifications in Telecommunications.

Salary: £985 (at 19) to £1,295 (at 25 or over); scale maximum £1,500 (higher rates at Heathrow). Some posts attract shift-duty payments. The annual leave allowance is good and there is a non-contributory pension scheme for established staff.

Complete this coupon for full details and application form:
 To: A. J. Edwards, C.Eng., M.I.E.E., M.I.E.R.E., Room 705, The Adelphi,
 John Adam Street, London WC2 marking your envelope 'Recruitment'

Name

Address

PW/B2

Not applicable to residents outside the United Kingdom.

NATCS

National Air Traffic Control Service

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

FOR SALE

FANTASTIC SALE. 1,000 of the following Amplifier Kits to clear:

	List price	Sale price	P.8
5 watts	£3.15.0	£1.17.6	9V
7 watts	£6.19.0	£2.7.6	9V
10 watts	£8.19.0	£2.17.6	9V

M. GLEAVES & BROTHER, 28 Wenny Estate, Chatteris, Cambs.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

135 COPIES "P.W." July 1953 to Jan 1965 plus odd circuits, etc. £6. GRAY, 229 Trentham Road, Stoke, ST3.4EJ.

YUKAN SELF-SPRAY

Get these *air drying* **GREY HAMMER** *OR* **BLACK WRINKLE** finishes *NOW!*

Yukan Aerosol sprays contain 16 oz. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 16/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Flat finish (12 oz. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/3 for 15/11 carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

307A, EDGWARE ROAD,
Dept. M/1 **YUKAN, LONDON, W.2.**

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations. We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

MORSE MADE !!

FACT NOT FICTION. If you start **EASY** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognize the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to: **GG8CS (BOX 11), 46 GREEN LANE, FURLEY, SURREY**

P.T.F.E. SLEEPING, 25 yds, five different colours: 3/- A. ROGERS, 137 Queen's Parade, Scarborough.

MISCELLANEOUS

SPEAKER CABINET BARGAIN



Beautifully finished in Teak veneer. Size 16 x 8 x 6 in. Great value at **ONLY 67/6 each**, p.p. 7/6 or two at 62/6 each, p.p. 10/6 pair.

NEW RELEASE. Bass Guitar Speakers. 12", 25Watt. Heavy Duty cast chassis. 15 Ohm. Suitable for all High Power applications. Limited Number at 5 Gns, p.p. 7/6. Send SAE for comprehensive Hi-Fi lists.

ALBION ELECTRONIC SUPPLIES

Dept 3
16 ALBION ROAD, BIRCHINGTON, Kent

MISCELLANEOUS

(continued)

ETCHED PRINTED CIRCUIT BOARD KITS. Full instructions 19/6 C.W.O. 'Circuit-etch', 12 Cambridge Road, St. Albans, Herts.

BUILD IT in a DEWBOX quality cabinet. 2in.x 2½in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

THE NEW

ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

6 OR 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent, etc. Fully transistorised, low battery drain. Unbeatable at **£2.19.6** post paid.

or in kit form **50/-**

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **65/- POST PAID**

SALOP ELECTRONICS Callers welcome
23 Wyle Cop, Shrewsbury, Shropshire S.A.E. for lists

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Rickmond, Surrey.

EXPRESS ROTARY SWITCHES. Switches for Mullard audio circuits, also switches made to customers own specifications. For details and price list, write or phone to 189 Edgware Road., London W.2. Tel. 01-723 4455.

MUSICAL MIRACLES. Send S.A.E. for details of Rhythm Modules, versatile bass-pedal unit, self-contained with unique effects, kits for waa-waa pedals. Also new 50µA meters, 25/- post paid. HURRY. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

POWERFUL TWO WAY MURPHY TRANSMITTER/RECEIVER AND MURPHY ROVER MOBILE TRANSMITTER/RECEIVER INCLUDING 30 FOOT ROOF TOP AERIAL. COST IN EXCESS OF £400. 25 MILE RANGE. £150. BILLERICAY 51261.

COMPLETE HI FI STEREO KIT, under 30 hours use. Connoisseur 2-speed turntable, Decca fss stereo pick up, mono head, Audiomaster c/v, Altobass-Mullard main amplifier, Audiomaster stereo tape recorder/replay, Collard deck fitted Miniflex 4-track heads, Pye FM tuner. Cost £300. Any sensible offer, J. BERRISFORD, Bolts Cross Cottage, Peppard, Henley, Oxon.

MISCELLANEOUS

(continued)

BARGAIN PACKS. 200 assorted springs, nuts, washers, screws. Popular sizes, 7/6 including postage. Cohaven Industrial Estate, Ripley, Derbyshire.

PRINTED CIRCUITS Prototype, Medium and Batch Production of all types of circuits, Design and layout facilities available. Brooklands Plating Co., Spices Yard, South End, Croydon. Tel. 01-688-2128.

A CORNUCOPIA OF COMPONENTS! Scarce valves, selected TV components, Educational and Projects Kits, speakers and cabinets, transistors. Resistors all values ½ watt 3d. each. State your requirements. S.A.E. for details. MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

JOURNAL OF PARAPHYSICS Russian experiments: telekinesis ("mind-over-matter"); brainwaves actuate electronic relays; transistor UFO detectors; finger-visibility; hyperspace; time-reversal; tachyons ("faster than light") etc. S.A.E. for list. 20s. for back issues. Paraphysical Laboratory, Downton, Wilts.

BOOKS & PUBLICATIONS

SURPLUS HANDBOOKS

19 set Circuit and Notes	6/8 p/p 6d.
1155 set Circuit and Notes	6/8 p/p 6d.
H.R.O. Technical Instructions	5/6 p/p 6d.
38 set Technical Instructions	5/6 p/p 6d.
46 set Working Instructions	5/6 p/p 6d.
88 set Technical Instructions	7/- p/p 6d.
BC.221 Circuit and Notes	5/6 p/p 6d.
Wavemeter Class D Tech. Instr.	5/6 p/p 6d.
18 set Circuit and Notes	5/6 p/p 6d.
BC.1000 (31 set) Circuit and Notes	5/6 p/p 6d.
CR.100/B.28 Circuit and Notes	10/- p/p 9d.
R.107 Circuit and Notes	7/- p/p 6d.
AR.88D Instruction Manual	18/- p/p 6d.
62 set Circuit and Notes	6/6 p/p 6d.
Circuit Diagram 5/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.	
52 set Sender and Receiver circuits 7/6 post free	

Colour code indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

WANTED

WE BUY New Valves and Transistors. State price: A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

WANTED NEW VALVES, televisions, radiograms, transistors, etc. STAN WILL-ETTS, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WANTED
(continued)

AVO METERS, MODELS 8 & 9, ANY QUANTITY, ANY CONDITION, ALSO WEE MEGGERS. SEND FOR PACKING INSTRUCTIONS. HUGGETT'S LTD., 2/4 PAWSONS ROAD, W. CROYDON.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.**

SERVICE SHEETS

SERVICE SHEETS, RADIO, TV, 5,000 Models. List 1/6. S.A.E. Enquiries. **TEL-RAY, 11 Maudland Bank, Preston, Lancs.**

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. **THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.**

SERVICE SHEETS (1925-1969) for TELEVISIONS, RADIOS, TRANSISTORS, TAPE RECORDERS, RECORD PLAYERS, etc., by return post, with free fault-finding guide. Prices from 1/-. Over 8,000 models available. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO, 54 London Road, Bexhill, Sussex.**

RADIO, TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.**

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 10/- each, plus large S.A.E.
(Uncrossed P.O.'s please, returned if service sheets not available.)

C. CARANNA

71 BEAUFORT PARK LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request.

Mail order only.

EDUCATIONAL

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London, E.C.1.**

EDUCATIONAL
(continued)



**RADIO AND TELEVISION SERVICING
RADAR THEORY AND MAINTENANCE
TELECOMMUNICATIONS**

This private College provides efficient theoretical and practical training in the above subjects. One-year day courses are available for beginners and shortened courses for men who have had previous training.

Write for details to:
The Secretary, London Electronics College, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373-8721

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. **B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.**

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs) R.T.E.B., etc. Many non-exam courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON, SW8

SITUATIONS VACANT

Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1970 and in subsequent years.

Specialist training courses lasting approximately nine months, according to the trainee's progress, are held at intervals. Applications are now invited for the course starting in September 1970.

During training a salary will be paid on the following scale:—

Age 21	£ 800 per annum
22	855 " "
23	890 " "
24	925 " "
25 and over	965 " "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade I scale:—

Age 21	£ 965 per annum
22	1025 " "
23	1085 " "
24	1145 " "
25 (highest age point)	1215 " "

then by six annual increases to a maximum of £1,650 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad. Applicants must normally be under 30 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or F.M.G. qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:—

RECRUITMENT OFFICER, Government Communications Headquarters, Oakley, Priors Road, CHELTENHAM, Glos. GL52 5AJ Tel: No. Cheltenham 21491 Ext 2270

SITUATIONS VACANT
(continued)

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept 137K), Aldermaston Court, Aldermaston, Berks.**

Trainee Radio Technicians

A Progressive Career in the Field of Radio and Electronics

Applications are now invited for an intensive training course of two years, leading to appointment as a fully qualified **RADIO TECHNICIAN**, with further prospects of progression to the Telecommunication Technical Officer Class.

Generous Pay and Conditions while under training.

Candidates must be over 16 and under 21 years of age as at 7 September, 1970, on which date training commences.

Minimum educational qualifications required are passes at GCE 'O' Level in English Language, Mathematics and PHYSICS (already held or expected to be obtained in the Summer, 1970). Equivalent passes in Scottish or Northern Ireland Certificates and CSE Grade I passes are also acceptable.

Closing date for receipt of applications: 27 February, 1970.

Apply for full details and application form to:—

The Recruitment Officer (TRT/37), Government Communications Headquarters, Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ

HENRY'S RADIO LTD.
303 EDGWARE ROAD, LONDON, W.2

HAVE THE FOLLOWING VACANCIES IN THEIR ORGANISATION.

Sales Assistants
Young man with good general knowledge of electronic components required for our retail sales dept. Please Phone 723 1008/9 Extn. 1.

Sales Assistants Hi-Fi Dept.
Young man with a good general knowledge of HIGH FIDELITY EQUIPMENT required for our retail HI-FI SALES DEPT. Please contact Mr. STEVENS, Telephone 723 6963.

SKILLED OR SEMI-SKILLED ENGINEER required for service electronic department of large photographic importers. Congenial conditions, interesting work, good salary and L.V's. For appointment telephone 253-8031 Mr. Vassey.

SITUATIONS VACANT (continued)

ENGINEERS, A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

ELECTRICAL

**240 VOLT
ELECTRICITY
ANYWHERE**



BEST EVER 200/240 VOLTS "MANS" SUPPLY FROM 12 VOLT CAR BATTERY
Exclusive World Scoop Purchase. The fabulous Mk. 2D American Heavy Duty Dynamo Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, A.C. Fluorescent Lighting and all 200/240 volt Universal A.C./D.C. mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested, only £4.19.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details. Dept. PW STANFORD ELECTRONICS, Rear Derby Road, North Promenade, Blackpool, Lancashire.

RECEIVERS & COMPONENTS

A. J. H. ELECTRONICS 59 Waverley Road, The Kent, Rugby Warwickshire. Tel. Rugby 71066

Postal Charges:— Under £1+1/6, Between £1 & £3+2/3, — Under £3 & £5+3/4, Over £5 post free unless stated.

P.C. BOARDS stripped form modern radio equipment but have the corners cut off at the request of the manufacturer:—

P.C.1: R. F. UNIT 2R.F. stages using AFZ11, GEX66 or equivalent as crystal mixer, for use with 3rd overtone crystals, not supplied. FREQ. 32-54 Mc/s can be altered to 70 Mc/s by changing capacitors across tuned circuits. With circuit £1.0.0. each (BRAND NEW UNUSED).

P.C.2: 10.7 Mc/s I.F. strip 3 AF114 transistors 3 neutralised stages of amplification, each stage screened, coils wound in pot cores, 4" x 3 1/2" £1.0.0. each with circuit.

P.C.3: 2nd MIXER OSCILLATOR board converts 10.7 Mc/s to 455Kc/s 2 transistors OC171 osc. GET887 or equivalent 455 Kc/s I.F. amplifier miniature wire ended crystal 11.155 Mc/s. 12/6 each with circuit.

P.C.4: 455 Kc/s A.M. I.F. AMPLIFIER 5, GET 887s, 2, NKT223A, 5 diodes, with built in noise limiter (that really works) supplied with filter 2 1/2" x 6" £1.17.6. with circuit.

P.C.5: MODULATOR driver board with speech compressor, 300-3500c/s 4 transistors NKT223A, 2 1/2" x 6" with circuit £1.0.0. each. RECTIFIER ASSEMBLY 4 silicon diodes HS3108 800 piv @ 165 mA diode 2102 2 resistors, 1 R.F. choke, 1 25 mfd. 50 vvw electrolytic BRAND NEW 4/6 each.

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hy-stab, Vitreous, 1-20 watt, 15/- Post Free. **WHITSAM ELECTRICAL**, 33 Drayton Green Road, West Ealing, W.13.

BRAND NEW ELECTROLYTICS, 0.5, 1, 2, 5, 8, 10, 15, 20, 30, 40, 50, 100, 200 mfd., 8/- per dozen, postage 1/-. The C.R. Supply Co., 127 Chesterfield Road, Sheffield 8.

RECEIVERS & COMPONENTS (continued)

NEW FULL SPECIFICATION DEVICES. Integrated Circuits complete with data: GE PA230 Audio Preamplifier 18/6 each; GE PA234 1W Audio Amplifier 17/6 each; GE PA237 2W Audio Amplifier 32/6 each; MEL 11 Photo Darlington Amplifier 9/6 each. High quality low cost plastic transistors: GE 2N5172 NPN 200mW Transistor 1/9 each; ME 0412 PNP 200mW Transistor 3/9 each. Westinghouse guaranteed plastic rectifier: IN4820 1.5A 400V Si Rectifier 2/6 each. C.W.O. P. & P. 1/- per JEF ELECTRONICS, York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only.

HI-FI loudspeaker systems for the home constructor, cabinet kits, the new range of Peerless speakers, speaker kit systems and cross-over networks. BAF wadding, speaker fabric (samples on request) and all other necessary components. Send 5d in stamps to: **AUDIOSCAN**, Dept. PW, 4 Princes Square, Harrowgate, Yorks.

COMPLETE RANGE of Amateur Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in. packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/-, P. & P. 2/-. With a guaranteed minimum of 35 transistors.

SPECIAL BARGAIN PACK, 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 55/-, P. & P. 7/6. With a guaranteed minimum of 350 transistors.

GIANT PANELS, 5 1/2in. x 4in., min. 20 transistors, 9 x 56 µH inductors, resistors, diodes, etc. 3 for £1. P. & P. 2/-.

As above, only 21 transistors, 70 diodes, 62 min. 1/2 th.W resistors. 3 for 25/-, P. & P. 2/-.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-, P. & P. 2/-.

TRIM POTS. On 2in x 4in boards + Ta caps and other components. Ideal for organ keyboard tuning etc. 100Ω, 500Ω, 15K., 20K. State requirements. 5 boards 10/-, P. & P. 2/-.

NPN GERMANIUM TO5 1 WATT POWER TRANSISTORS. On small heat sink, on 2in. x 4in. panel. 5 for 10/-, P. & P. 2/-.

POWER TRANSISTORS. Sim. to 2N174 ex-eqnt. On Finned Heat Sink (10D), 4 for £1. P. & P. 5/-.

DIODES. Ex eqpt., Silicon, 150 PIV, 10 amp. 4 for 10/-, 150 PIV, 20 amp. 4 for £1. Post free.

MINIATURE GLASS NEONS, 13/6 doz.

PAPST FANS. Powerful Extractor/Blower fans. 4 1/2in. x 4 1/2in. x 2in. 230/250V. 100 c.f.m., 2,800 r.p.m. Weight 2 1/2 lb. 12 oz. 50/- post free.

SPRAGUE POLYESTER. 0.22µF 250V small capacitors. 5/- doz. P. & P. 1/-.

SPRAGUE ELECTROLYTICS. 4µF 150V. 5/- doz. P. & P. 1/-.

TANTALUM CAPS. 2.2µF 50V. 8/- per doz P. & P. 1/-

NEW MIXED COMPONENTS
150 High stab. resistors 5% and better. 12/6. P. & P. 1/-.
250 mixed resistors 1/4W + 1/2W. 12/6. P. & P. 1/-.

Large handful of mixed capacitors. 12/6. P. & P. 1/-.

LARGE CAPACITY ELECTROLYTICS 4 1/2in., 2in. diam. Screw terminals. 7/8 each post free. 4,000µF 72V d.c. wkg.

4 1/2in. x 2in. Plessey 1,500µF 150V d.c. wkg. 8/- each. 3in. x 1in. Plessey 2,000µF 25V d.c. wkg. 6/- each.

KEYTRONICS, 52 Earls Court Road
London, W.8. Mail order only
Tel. 01-478 8499

Closed Circuit T.V. Systems

Complete systems comprise Camera with lens & Vidicon Control unit and 8 1/2" Monitor, 50ft camera cable & mains cables in working order with circuits. Made by Peto Scott & Fye. Price £85 plus £3 carr.

V.H.F. Radio Telephone Units

Hudson boot mounting type uses 16 valves and 14 Transistors, 80 to 100 Mc/s channel single in working order with circuits. See Jan. P.W. or write for full details.

Price £15 plus 10/- carr.

Test Set Type 276

Contains mains P.U. 200/250v I/P O/P 300v at 100 Ma & 6.3, uses 5Z4, 2 chokes, valves EF50x10, also pots, swts, fuses, etc., in good condition in transit case.

Price £3.5, plus 10/- carr.

Transistor Invertors

I/P 12v D.C. + or - Ea O/Ps 250v D.C. smoothed at 100 Ma & -25v in case, good condition.

Price £3 plus 4/6 post.

Amplifier I.F. N.B.W.

These are a narrow bandwidth tunable 45 Mc/s I.F. amp intended to work with a 45 Mc/s I.F. strip, it is possible to select a 50Kc portion of a 4.5 Mc/s bandwidth the I/P of 45 Mc/s being converted to 20 Mc/s then back to 45 Mc/s. These can be tuned from the front panel, fitted mains P.U. for 230v and monitor meter in good condition with circ and plugs.

Price £4 plus 12/6 carr.

I.F. Unit Type 215

This is a 5-stage 45 Mc/s I.F. amp with valves EF50x6 complete with coax and power plug, can be used with above. Ex equipment.

Price 15/- plus 5/- post.

MOD Kits

These contain 8 group boards 2" wide with approx 130 conds & resistors, 11 to 24 way. All parts can be removed, top quality brand new boxed.

price 12/6 plus 3/- post.

Meters

Edgewise reading type 1 Ma scale 0 to 2,000yds linear, 10 divisions, overhaul, size 3x1x3 1/2", also 500 Ua scale 0 to 5 2 1/2 O.S.D. single hole fixing, both ex equipment tested.

Price both types 17/6 plus 2/6 post.

Mains Transformer

Pria 230v 50c/s Sec., 350-, 310-0-310-350v at 220Ma 5v 6a, 6.7 5a, 6.3, 3a twice, 6.3 1a twice, potted ex equip.

Price 35/- plus 7/6 carr.

Matching choke 10H, 250 Ma, 17/6.

12 or 24v DC Supply Units

I/P 200/250v O/P 12v D.C. twice at 3 amps on each circ will give 24v 3a or 12v 6a, with circ and connections. In used condition.

Price £3-5 plus 10/- carr.

Radio Telemeter Units

I/P 230v. these are a low-freq radio unit with 6 valves, speaker, tape head with tape loop, 2 motors, swts, etc. Complete in neat cabinet, with circ and mods for Radio 2.

Price £3-5 plus 10/- carr.

Control Unit 595.

Contains 2 500Ua 2" meters, 3 Yax swts, Variac 1500c/s type can be used on 6.3v 50c/s, 4 pots, 12 misc res, etc new in case.

Price 50/- plus 10/- carr.

A. H. SUPPLIES, 57 Main Road, SHEFFIELD, S9.5HL.

Shop open Mon., Wens, Fri & Sat.
Carriage applies to U.K. Mainland only.

Stella Nine Range Cases

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES which are made to fit Standard

Width	Depth	Alloy Chassis		
		4" Height £ s. d.	6" Height £ s. d.	7 1/2" Height £ s. d.
6 1/2"	3 3/8"	12 6	15 0	18 0
6 1/2"	4 1/8"	13 6	18 0	1 0 0
8 1/2"	3 3/8"	15 0	1 0 0	1 1 0
8 1/2"	6 1/8"	1 1 0	1 6 6	1 11 3
10 1/2"	7 1/8"	1 8 6	1 15 6	1 18 9
12 1/2"	3 3/8"	1 1 0	1 6 6	1 11 0
12 1/2"	5 1/8"	1 8 0	1 14 0	1 17 6
12 1/2"	8 1/8"	1 16 0	2 3 0	2 7 3
14 1/2"	8 1/8"	1 5 0	1 11 6	1 14 0
14 1/2"	9 1/8"	2 3 0	2 15 9	2 18 5
16 1/2"	6 1/8"	1 18 6	2 6 3	2 11 6
16 1/2"	10 1/8"	2 10 0	3 5 0	3 11 9

Cases—Post 4s. 6d. per order.
Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/2" Walls

	s. d.	s. d.	s. d.	s. d.	
6" x 3"	5 6	10" x 7"	8 6	14" x 8"	7 3
6" x 4"	5 9	12" x 3"	6 9	14" x 9"	14 3
8" x 3"	6 6	12" x 5"	7 6	16" x 6"	10 9
8" x 6"	7 9	12" x 8"	10 9	16" x 10"	16 0

Chassis—Post 3s. 0d. per order.
Discounts available on quantities.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases
46 LOWFIELD ROAD
STOCKPORT - CHESHIRE
Tel: 061-480 2179

BARGAIN PARCELS

Any 5, 9/-; 10, 14/-; 100, £5.10.0 from the following:
ECC82, ECL80, EF80, EF85, EF183, EBF89, EB91, EY86, PCC84, PCC89, PCF80, PCL82, PCL83, PCL84, PL36, PL81, PY33, PY81, PY82, U191, 6-30L2, 30FL1, 30F5.

U.H.F. AERIAL BOOSTER

Transistorised, cavity tuned, high-gain. All uhf channels. Complete with battery and lead. 69/-, p. & p. 1/-, VELCO ELECTRONICS, 62 Bridge Street, Ramsbottom, Bury, Lancs.

NEW VHF KIT

Receives Television Sound, Ambulances, Aircraft, Radio 2, 3 and 4 on VHF, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. The Kit comes with easy to follow instructions and circuit. Powered by 9v Battery. Complete with built-in Jack Plug Socket for use with Earphones or Amplifier.

ONLY 57/-, P. & P. FREE U.K. ONLY.

Postal Orders, Cheques to:

Dept. P.W.7.

Galleon Trading Co., 298A Lodge Lane, Romford, Essex.

EMSAC FOR ANTENNA SYSTEMS AND CONVERTERS.

Please send s.a.e. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting. ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD., Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

COMMUNICATION RECEIVERS: R107 £15, R209 (6 volt) £12, PCR2 LW, MW, and 6-22 mc/s, fitted internal mains PSU, LS and BFO, £12, PCR2 unmodified £8. Carriage paid. For R209 and PCR2's add £1 deposit on returnable crate. GOLLEDDGE, G3EDW, Glen Tor, Torrington, Devon. (Phone 2411).

TO HELP THE HOME CONSTRUCTOR. Heathkit now make available our surplus Resistors, Capacitors, etc. at Bargain prices. Send for lists, E. Moyle, Daystrom Ltd., Gloucester.

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. PHIL- POTTS METAL WORKS LTD., Chapman Street, Loughborough.

AERIALS

BAKER AND BAINES

All aerials available—Engineered to a high standard. Specials and DX made to order. BBC dipole 30/-, H 42/-, 3 ele 89/-, 4 ele 120/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/5, 11 ele 57/6, 13 ele 71/-, ITA double 8 112/-, 11 ele 140/-, 13 ele 159/-, Combined BBC/ITA D+5 45/-, D+8 52/-, H+5 65/-, X+5 75/-, BBC2—ITV2 8 ele 29/-, 14 ele 37/-, 18 ele 54/-, 22 ele 63/-, double 22 ele 142/-, FM dipole 21/-, H 38/-, 3 ele 65/-, All aerials suitable for mounting where space permits. Special high-gain loft BBC1/ITA for confined space with pole, joist bracket and swivel joint 37/-, Co-ax low loss 1/3 per yard—Ultra low loss 2/3 per yard. Co-ax plugs 1/4. Band I/III d-plexers 8/3, I/II/III triplexers 13/6. Feed BBC1—ITA—BBC2 all down the same co-ax using pair matched UHF/VHF d-plexers, 21/3 pair. Chimney lashings 15/-, 19/-, 5ft. cranked arm pole 10/4. 3ft. arm 6/3. 16ft. x 2in. poles 59/-, Clamps, couplers, etc. Signal boosters BBC2 97/6. Combined BBC1/ITA 75/6. All cathode Ray Tubes Brand New not rejuvenated (full 2 years guarantee) at sensible prices 14in. £6, 17in £6, 19in. £7.15.0, 21in. £7.15.0, 23in. £9, Twin Panel 19in. £12, 23in. £15.7.6. Ringguard 19in. £10.9.0, 23in. £13.14.0. SAE for full details please. Most Television Valves available Brand New for extra performance 3 months guarantee, 15% off standard price. SAE will bring full lists. Carriage: Aerials paid. Accessories—according to weight. TV Tubes 12/6. Insurance 5/- extra. Valves 9d. 11 Dale Crescent, Tupton, Chesterfield.

GIANT 10/- SALE

YES 10/- IS ALL YOU PAY!! ALL PACKS ARE POST PAID, ALL DELIVERIES BY RETURN OF POST OR YOUR MONEY BACK PLUS FREE GIFT!!

- | | | | | |
|------|------|--------------------------|--|------|
| Pack | ES1 | <input type="checkbox"/> | EXPERIMENTORS PARCEL—2LBS WEIGHT ASSORTED ELECTRONIC COMPONENTS INCL. PART MADE EQUIPMENT | 10/- |
| | ES2 | <input type="checkbox"/> | 200 ASSORTED RESISTORS—CARBON, WIRE-WOUND, HIGH STABS, LARGE & MINIATURE TYPES | 10/- |
| | ES3 | <input type="checkbox"/> | 75 ASSORTED CAPACITORS—SILVER MICA'S, DISC CERAMICS, PAPERS, ELECTROLYTICS, ETC. | 10/- |
| | ES4 | <input type="checkbox"/> | 100 MIXED TRANSISTORS, DIODES, RECTIFIERS, ETC. MANUFACTURERS REJECTS. GOOD PERCENTAGE USEABLE | 10/- |
| | ES5 | <input type="checkbox"/> | 10 PRINTED CIRCUIT BOARDS CONTAINING TRANSISTORS, DIODES, RESISTORS, CAPACITORS, ETC., ETC. | 10/- |
| | ES6 | <input type="checkbox"/> | PRINTED CIRCUIT LAMINATE—DOUBLE & SINGLE SIDED COPPER—3/4 LB OF GOOD SIZED OFFCUTS FOR | 10/- |
| | ES7 | <input type="checkbox"/> | 20 ASSORTED COILS & INDUCTORS COIL FORMERS FERRITES IFT'S ETC. | 10/- |
| | ES8 | <input type="checkbox"/> | 8 ASSORTED CARBON & WIRE WOUND POTENTIOMETERS & PRESETS (SOME WITH SWITCHES) | 10/- |
| | ES9 | <input type="checkbox"/> | 5 ASSORTED SWITCHES INCLUDING MULTI—WAFER (YAXLEY ETC.) TYPES & SOME TOGGLE SWITCHES | 10/- |
| | ES10 | <input type="checkbox"/> | 3 ASSORTED RELAYS OF VARIOUS VOLTAGES & RESISTANCES G.P.O. & INDUSTRIAL TYPES | 10/- |
| | ES11 | <input type="checkbox"/> | 10 SUB-MINIATURE NEON BULBS WIRE ENDED PLUS ONE MAINS NEON INDICATOR PANEL MOUNTING | 10/- |
| | ES12 | <input type="checkbox"/> | 10 TRANSISTOR SOCKETS TO TAKE 3 OR 4 WIRE TRANSISTORS | 10/- |

IT'S EASY TO ORDER FROM ELECTROSPARES BY MAIL—JUST FOLLOW THESE INSTRUCTIONS FOR YOUR PARCEL BY RETURN OF POST

1. Please PRINT your name and full address clearly in box:—
2. Place a cross (X) in the square beside the pack you require.
3. Tear out this advertisement.
4. Enclose 10/- for each pack ordered. Remember NO POST CHARGES to pay.
5. Post your order to:—

ELECTROSPARES, POST BOX 48,
BRENTWOOD, ESSEX

(Please note: This offer limited to United Kingdom only.)
(No C.O.D.—Mail orders only—only items advertised are stocked.)

REMEMBER—ELECTROSPARES WILL SEND BY RETURN OF POST OR YOUR MONEY BACK PLUS A FREE GIFT—ELECTROSPARES

SPECIAL FREE OFFER!!

ORDER 10 PACKS (ANY 10) & SEND ONLY £4 10s GET ONE PACK OF YOUR CHOICE FREE OF CHARGE

Name

Number & Road

Town

County

I enclose £ s for..... packs as indicated X

Cheque/Cash/Postal Orders.



ELECTRAMA
FANTASTIC
SPEAKER BARGAIN
Famous English, 12" high
flux, heavy cone, 10 watts
speaker with built-in tweeter,
3 or 15 ohms. **39/6**
(P. & I. 4/9) (P. & I. 6/9)
2 for 70/- (P. & I. 6/9)




NEW RELEASE
HI-FI COLUMN
SPEAKER CABINET
Beautifully made. Suitable for
7-12" speakers. Rose-
wood finish. Screwed and
glued. Attractive grey cloth
front measures 24" x 13" x
10" with tweeter hole above.
Mark 11 **95/-** C.drr.
de luxe model **10/-**
With 12" speaker as adver-
tised above **£6.5.0.** (carr. 10/-)



LATEST
RELEASE!
EVER READY

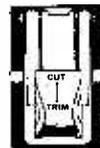RE-CHARGEABLE NICKEL
CADMIUM CELLS
1.25 v 1.6 A.H. **29/6**
Size 2 1/4" high x 1 1/4" dia.
1.25 v 0.45 A.H. **18/-**
9 v equiv. PP3 **39/6**
P & P 1/9 on each
CHARGERS AVAILABLE—send S.A.E.
for details.



TAPE SPLICER/
EDITOR
19/6

4 TRANSISTOR AUDIO
AMPLIFIER (1 watt)
Output 8 or 16 ohms.
3 1/2" x 2 1/2" x 1 1/2"
Dept. PW12, 15 High St., Hailsham, Sussex



NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting
bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 37/6.
11 element, 45/-, 14 element, 52/6, 18
element, 60/-, **Wall Mounting with**
Cranked Arms, 7 element, 60/-, 11 element,
Cranked Arms, 7 1/2 element, 82/6.
87/-, 14 element, 75/-, 18 element, 82/6.
Mast Mounting with 2in. clamp, 7 element,
42/6, 11 element, 55/-, 14 element, 62/-, 18
element, 70/-, Chimney Mounting Arrays,
Complete, 7 element, 72/6, 11 element, 80/-,
14 element, 87/6, 18 element, 95/-, Complete
assembly instructions with every unit. **Low**
Loss Cable, 1/6 yd. U.H.F. Preamps from
75/-, State clearly channel number required
on all orders.

BBC · ITV AERIALS



BBC (Band 1), Tele-
scopic loft, 25/-, External
S/D, 30/-, "H" £2.15.0.
ITV (Band 3), 3 element
loft array, 30/-, 5
element, 40/-, 7 element
50/-, Wall mounting, 3 element,
47/6, 5 element,
52/6. Combined BBC/
ITV, Loft 1+3, 40/- 1+5,
50/-; 1+7, 60/-; Wall
mounting 1+3, 57/6; 1+5,
67/6; Chimney 1+3, 67/6;
1+5, 75/-.
VHF transistor pre-
amps, 75/-.


COMBINED BBC1 - ITV - BBC2
AERIALS, 1+3+9, 70/-, 1+5+9, 80/-,
1+5+14, 90/-, 1+7+14, 100/-, Loft mounting
only. Special leaflet available.
F.M. (Band 2), Loft S/D, 15/-, "H", 32/6.
3 element, 55/-, External units available.
Co-ax. cable 5d., yd. Co-ax. plugs, 1/4.
Outlet boxes, 5/-, Diplexer Crossover Boxes,
13/6. C.W.O. or C.O.D. P. & P. 6/-. Send 6d.
stamps for illustrated lists.

Callers welcomed - open all day Saturday

K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE
LONDON ROAD, MITCHAM,
SURREY 01-648 4884

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

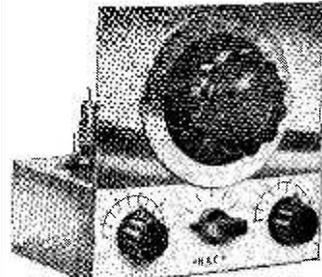

Famous for over 25 years for Short-Wave Equipment
of quality, "H.A.C." were the Original
suppliers of Short-Wave Receiver Kits for the
amateur constructor. Over 10,000 satisfied
customers—including Technical Colleges, Hos-
pitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1970 RANGE

One-valve model "DX", complete kit—price 58/6
(Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve
S.W. Kit available at any price. America and
Australia received clearly at good volume." This
kit contains all genuine short-wave components,
drilled chassis, valve, accessories and full instructions.
Ready to assemble, and of course, as all our
products—fully guaranteed. Full range of other
S.W. kits including the famous model "K" and
"K plus" (illustrated above.) All orders despatched
by return. (Mail order only.) Send now for a
descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE,
YORKS. Tel. Heckmondwike 4285
Indicator Unit Type 26, Size 12x2x9in.
With Outer Case fitted with 2 1/2in. CRT Type
CV1526 9 B7G Valves. Fair condition but
not tested. 32/6, p. & p. 10/-.

Aircraft Sighting Head with Gyro Unit.
Condition fair. 18/6, carriage B.R.S. 12/-.
Small 12-way Plug and Socket, 1/6 each, p.p.
1/-, 15/- per doz. p.p. 3/6. Ex unit.

Panel of 19 mixed pots, 5/- post paid. Ex unit.
Panel of Resistors and Condensers, 8/- per
doz. post paid. Ex unit.

Bombsight Computers containing a large
selection of gears. A delight for the
model maker. 55/- carriage paid.
Complete untested 17 inch T.V. Sets 12
channel 50/-, 15/- carriage.

Model Makers Motor with Train of Gears.
24 volts. Will run off 12 or 6 volts at slower
speeds. 5/-, post and packing 3/6.

Speakers removed from T.V. Sets. All PM
and 3 ohm. 6in. round 3/-, p. & p. 3/-;
6 for 24/-, post paid. 6 x 4in. 3/-, p. & p. 3/-;
6 for 24/-, round paid. 5in. round 3/-, p. & p.
3/-; 6 for 24/-, post paid. 7 x 4in. 5/-, p. & p.
3/-; 6 for 34/-, post paid. Slot Speakers
8 x 2 1/2in. 5/-, p. & p. 3/-; 6 for 30/-, post paid.

Reclaimed T.V. Tubes, with 6 months'
guarantee 17in. Type AW43/80, AW43/88
40/-, MW43/69 30/-, 14in. Type 147/-.
All Tubes 12/- carriage.

Silicon Rectifier 500mA 800 PIV, 2/6
post paid. 24/- per dozen, post paid.

Jap Earpiece. Magnetic 8 ohm. Small and
Large Plug 1/11 post paid.

G.P. Diodes 3/6 per dozen, post paid.

Top Grade Mylar Tapes, 7in. Standard 11/6,
7in. Long Play 14/-, 7in. Double Play 19/6.
5in. Standard 7/9, 5in. Long Play 10/-,
plus post on any tape 1/9.

VALVE LIST—Ex Equipment, 3 months' guarantee
Single Valves Post 7d., over 3 Valves p. & p. paid

ARP12	1/6	PCL82	4/-	6B8	1/8
EB91	9d.	PCL83	5/-	6BW7	2/6
EF85	3/-	PL86	5/-	6K7	1/6
EF80	3/-	PL88	6/-	6U4	5/-
EC081	3/-	PL81	4/-	6P28	5/-
ECC82	3/-	PY33	5/-	10P13	2/6
ECC83	4/-	PY81	1/6	185BT	8/8
ECC84	4/-	PY82	1/6	20D1	3/-
ECL80	1/6	PZ30	5/-	20P1	5/-
EF80	1/6	U191	5/-	20P2	2/6
EF80	1/6	U281	5/-	30FL1	5/-
EF91	9d.	U282	5/-	30P12	5/-
EY86	5/-	U301	5/-	30F5	2/6
PC084	2/-	U329	5/-	30FL1	5/-
PCF80	2/-	U261	5/-	6/30L2	5/-

Est. 1943 **JOHNSONS** Tel: 21784

New! CV2—a unique triple-purpose
VHF kit for the Amateur enthusiast.
Integrated converter, receiver, and
tuner-feeder. Fantastic single trans-
istor performance! Comprehensive kit
of high grade parts with three coils
covering 80-178MHz, 9v battery, etc.,
together with simplified diagrams and
instructions. Price complete, £4, post,
packing and insurance paid, direct
from makers. S.A.E. for literature.

JOHNSON'S (RADIO)
St. Martin's Gate, Worcester

Please mention
PRACTICAL
WIRELESS
when replying to
advertisements

NEW VALVES!

Guaranteed and Tested
24-HOUR SERVICE

1R5	5/6	DI 96	6/9	EY51	6/9	PI 504	13/3
1S5	4/3	DY86	4/9	EY86	5/9	PY32	10/-
1T4	2/9	DY87	4/9	EZ80	3/9	PY33	10/-
3V4	5/9	EABC80	5/9	EZ81	4/6	PY81	5/-
3Y4	5/9	FBC33	7/9	KT61	8/3	PY82	5/-
6X01.2	11/6	EBG41	9/3	KT66	15/9	PY83	5/6
6AQ5	4/3	EBF80	6/-	N78	14/6	PY88	6/6
6V6G	3/-	EBF89	5/9	PABC80	6/9	PY800	6/3
2516GT	4/6	ECC82	4/-	PC86	10/3	PY801	6/3
30FL1	13/6	ECC83	4/9	PC88	10/3	R19	6/3
30F1	12	ECC85	5/-	PC97	8/3	U25	12/9
30P4	11/6	EC435	5/6	PC900	7/-	U26	11/6
30P19	11/6	EC442	10/6	PC834	6/3	U191	12/-
30PL1	13/6	EC481	5/9	PC839	8/11	U193	8/6
30PL13	14/9	FC180	6/6	PCF80	5/11	U251	14/-
CC35	13/-	EC182	6/3	PCF801	6/6	U301	10/-
CL33	17/6	EC186	7/6	PCF802	8/6	U329	14/-
DA632	6/9	EF37A	6/-	PC182	6/9	UABC80	6/3
DAF91	4/3	EF39	4/6	PC183	8/9	UBC41	8/3
DAF96	6/3	EF80	4/6	PC184	7/-	UBF89	6/3
DF33	7/6	EF85	4/9	PCL85	8/6	UCC85	7/3
DF91	2/9	EF86	6/3	PC186	8/-	UCH81	6/-
DF96	6/3	EF89	4/9	PFL200	11/-	UCL82	6/9
DK32	6/9	EF183	5/6	PL 86	9/3	UF41	10/6
DK91	5/6	EF184	5/3	PL81	7/6	UF89	6/-
DK96	6/6	EH90	6/-	PL82	5/9	UI41	10/3
DI35	4/9	EI 33	8/3	PL83	6/3	UI84	6/3
DI92	5/9	EI41	10/3	PL84	6/6	UY41	7/-
DI94	5/9	EI 84	4/9	PI 500	12/9	UY85	5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d.
per valve extra. Any parcel insured against damage in transit
6d. extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

VALUE ALL THE WAY

QUALITY-TESTED PAKS

6 Matched Trans. OC44/45/81/81D	10/-
20 Red Spot AF Trans. PNP	10/-
16 White Spot RF Trans. PNP	10/-
5 Silicon Rects. 3 A 100-400 PIV	10/-
2 10 A Silicon Rects. 100 PIV	10/-
2 OC1 140 Trans. NPN Switching	10/-
1 12 A SCR 100 PIV	10/-
3 Sil. Trans. 28303 PNP	10/-
2 200 Mc/s Sil. Trans. NPN BSY26/27/10	10/-
3 Zener Diodes 1W 33V 5% Tol.	10/-
4 High Current Trans. OC42 Evt.	10/-
2 Power Transistors 1 OC25 1 OC35	10/-
3 Silicon Rects. 400 PIV 250mA	10/-
4 OC75 Transistors	10/-
1 Power Trans. OC20 100V	10/-
10 OA202 Sil. Diodes Sub-min.	10/-
2 Low Noise Trans. NPN 2N929/30	10/-
1 Sil. Trans. NPN VCB 100 ZT86	10/-
8 OA81 Diodes	10/-
4 OC72 Transistors	10/-
4 OC77 Transistors	10/-
5 Sil. Rects. 400 PIV 500mA	10/-
5 GET884 Trans. Evt. OC44	10/-
5 GET883 Trans. Evt. OC45	10/-
2N708 Sil. Trans. 300Mc/s NPN	10/-
3 GT31 LF Low Noise Germ. Trans.	10/-
6 IN914 Sil. Diodes 75 PIV 75mA	10/-
8 OA95 Germ. Diodes Sub-min. IN69	10/-
3 NPN Germ. Trans. NKT773 Evt.	10/-
2 OC22 Power Trans. Germ.	10/-
2 OC25 Power Trans. Germ.	10/-
4 AC128 Trans. PNP High Gain	10/-
4 AC127/128 Comp. pair PNP/NPN	10/-
2 2N1307 PNP Switching Trans.	10/-
7 CG62H Germ. Diodes Evt. OA71	10/-
3 AF116 Type Trans.	10/-
12 Assorted Germ. Diodes Marked	10/-
4 AC126 Germ. PNP Trans.	10/-
4 Silicon Rects. 100 PIV 750mA	10/-
3 AF117 Trans.	10/-
7 OC81 Type Trans.	10/-
3 OC71 Trans.	10/-
5 2N2926 Sil. Epoxy Trans.	10/-
5 OC71 Type Trans.	10/-
2 2S701 Sil. Trans. Texas.	10/-
10 A 600 PIV Sil. Rects. 1S45R	10/-
3 BC108 Sil. NPN High Gain Trans.	10/-
2 2N910 NPN Sil. Trans. VCB 100	10/-
2 1000 PIV Sil. Rect. 1-5A RS53310A/F	10/-
3 BSY95A Sil. Trans. NPN 200Mc/s	10/-
3 OC200 Sil. Trans.	10/-
2 GET880 Low Noise Germ. Trans.	10/-
4 AF139 PNP High Fred. Trans.	10/-
3 NPN Trans. 1 ST141 & 2 ST140	10/-
4 Madt's 2 MAT100 & 2 MAT120	10/-
3 Madt's 2 MAT101 & MAT121	10/-
3 OC44 Germ. Trans. AF	10/-
3 AC127 NPN Germ. Trans.	10/-
1 2N3906 Sil. PNP Trans. Motorola	10/-
2 Sil. Power Rects. BYZ13	15/-
1 Sil. Power Trans. NPN 100Mc/s	15/-
TK201A	15/-
2 2N1132 PNP Epitaxial Planar Sil.	10/-
3 2N697 Epitaxial Planar Trans. Sil.	15/-
4 Germ. Power Trans. Evt. OC16	15/-
1 Unijunction Trans. 2N2646	15/-
2 Sil. Trans. 200Mc/s 60Vcb ZT83/84	15/-
1 Tunnel Diode AEY11 1050 Mc/s	15/-
2 2N7126 Sil. Epoxy Planar HFE225	15/-
8 BY100 Type Sil. Rects.	20/-
25 Sil. and Germ. Trans. Mixed, all marked. New.	30/-

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS

NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2S104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Rectifiers like BC108	10/-
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors 2G300 Ser. & OC71	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min.	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces	20/-
U29	10 1-amp SCR's TO-5 can up to 600 PIV CR51/25-600	20/-
U31	20 Sil. Planar NPN Trans. low noise AMP 2N3707	10/-
U32	25 Zener diodes 400mV D07 case mixed Volts. 3-18	10/-
U33	15 Plastic case 1 amp Silicon Rectifiers IN4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4	10/-
U35	25 Sil. Planar Trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN Trans. TO-5 BFY 501/51/52	10/-
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2S322	10/-
U38	20 Fast Switching Sil. Trans. NPN, 400 Mc/s 2N3011	10/-
U39	30 RF Germ. PNP Trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
U41	30 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP Trans. TO-1 NKT767 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

NEW LOW PRICE TESTED S.C.R.'s.

1 A	3 A	7 A	16 A	30 A
(TO-5 case)	(TO-66 case)	(TO-48 case)	(TO-48 case)	(TO-48 case)
PIV each	each	each	each	PIV each
50	4/5	9/6	10/6	25
100	5/-	6/6	10/6	50
200	7/-	7/6	11/6	100
400	8/6	9/6	13/6	180
600	10/6	11/6	15/6	250
800	12/6	14/-	18/-	300

2 Amp POTTED BRIDGE RECTIFIERS
200 V. 10/- | 600 V. 15/- | 800 V. 20/-

TRANSISTOR EQVT. & SPECIFICATION BOOK (German publication). A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- ea.

PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- p. & p.

PLEASE NOTE. To avoid any further increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organized and streamlined our Dispatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Dispatch Department, postal address: BI-PAK SEMICONDUCTORS, Dispatch Dept., P.O. BOX 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-.

SIL. RECTS. TESTED

PIV 750mA	3A	10A	30A
50	1/-	2/9	4/3
100	1/3	3/3	4/6
200	1/9	4/-	4/9
300	2/3	4/6	6/6
400	2/6	5/6	7/6
500	3/6	6/6	8/6
600	3/3	6/9	9/-
800	3/6	7/6	11/-
1000	5/-	9/3	12/6
1200	6/6	11/6	15/-

TRIACS

VBOM 2A	6A	10A
(TO-1)	(TO-66)	(TO-8)
100	14/-	15/-
200	17/6	20/-
400	20/-	25/-
VBOM=Blocking voltage in either direction.		

LUCAS 35A SIL RECTS. Branded 400 PIV. Special Price, stud type, flying lead, 22/6 each.

SILICON HIGH VOLTAGE RECTIFIERS

10 Amp, 3kV (3000 PIV) Stud Type with Flying Leads. 16/- each

UNIUNION

UT46. Evt. 2N2646. Evt. TIS43. BEN3000 5/6 EACH 25-99 5/- 100 UP 4/-

NPN Silicon PLANAR BC107/8/9, 2/- each 50-99, 1/10 100 up, 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

PNP Sil. Plastic Trans. Similar to 2N3702, untested but fully tested, 1/6 each, 25-99, 1/3 each 100 up, 1/- each.

INTEGRATED CIRCUITS

BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)

BP709C, Operational amplifier, 15/- each.
BP701B, Operational amplifier (with Zener output), 12/6 each.
BP702C, Operational amplifier (with direct output), 12/6 each.
BP501, Wide band amplifier 18/- each.
BP521, Logarithmic wide band amp, 14/- each.
BP20/C, General purpose amplifier, (TO-5 8lead), (voltage or current amp.), 12/6 each.

I.C. Operational Amplifier with Zener output. Type 701C. Ideal for P.E. Projects, 8 lead TO-5 case. Full data.
Our price 12/6 each 5 off 1/1 each. Large Qty. Prices quoted for AS USED IN 'P.E.' PROJECTS

AMPLIFIER AS USED IN 'P.E.' PROJECTS



Identical encapsulation and pin configuration to the following: SL402-3 IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

OTHER MONOLITHIC DEVICES

BP424, Zero voltage switch, 8/6 each. This device is a monolithic I.C. that acts as combined threshold detector and trigger circuit for controlling a triac. It is designed to pulse the gate of a thyristor at the point of zero supply voltage, and therefore eliminates any frequency interference when used with resistive loads.
D13D1 Silicon Unilateral switch, 10/- each.
A Silicon Planar monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuit details available on request. FAIRCHILD (U.S.A.) RTUL MICROLOGIC INTEGRATED CIRCUITS

Epoxy case T8-5 lead temp. range 15°C to 55°C. UL900, Buffer, 9/9 each. UL914, Dual two-input gate, 9/9 each. UL923 J-K-flip-flop, 13/- each.
Complete data and circuits for the Fairchild I.C.'s available in booklet form priced 1/6.
MULLARD I.C. AMPLIFIERS
TAA243, Operational amplifier, 70/- each.
TAA263, Linear AF amplifier, 15/9 each.
TAA 293, General purpose amplifier, 21/- ea.
CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS
Audio Power Amplifier, 30/- each.
CADDIUM CELLS
ORP12, 8/6.
ORP60, ORP61, 8/- each.
PHOTO TRANS.
OC71 Type, 8/6

AD161 NPN

AD162 PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS. For mains driven output stages of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

HIGH POWER SILICON PLANAR TRANSISTORS
TEXAS 2503A NPN VCB 100 1c4A (T. 15Mc) VCE100 Prot. 40V VEBE hFE(min.) 60 15/- each.

2N3055 115 WATT SIL. POWER NPN. OUR PRICE 12/6 EACH.

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-16V, 400mV (DO-7 Case) 1/6 ea. 1-5W (SO-Hat Stud) 5/- ea. All fully tested. 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS CODED and Guaranteed

Pak No.	EQVT
T1	2 2G371A OC71
T2	2 2G374 OC75
T3	8 2G374A OC81D
T4	8 2G381A OC81
T5	8 2G381A OC81
T6	8 2G344A OC44
T7	8 2G345A OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G417 AF117

All 10/- each pack

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 5/- ea.

120V CB NIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N893 FULLY TESTED AND CODED. NDI20 1-24, 3/6 each. TO-5 NPN 25 up 3/- each.

Sil. trans. suitable for P.E. Organ, Metal TO-18 Evt. ZTX300 1-18 Any Qty.

FREE One 10/- Pack of your own choice free with orders valued 44 or over

NPN DIFFUSED SILICON PHOTO-DUODIODE TYPE IS701 (2N2175) or Tape Readout, high switching and measurement indicators. 50V, 250mV. OUR PRICE 10/- EACH. 50 OR OVER 8/6. EACH. FULL DETAILS.

FET'S
2N 3819 8/-
2N 3820 25/-
MPF105 8/-

LOW COST F.E.T.'s Fully Tested, Guaranteed Parameters equit. to 2N3819, MPF102, 2N-5459, 1-24, 7/6 each; 25-99, 6/3 each; 100 up, 5/6 each. Coded FE19. Full data sent TO-72 case.

BI-PAK MONOLITHIC DIGITAL CIRCUITS

BP305A, 6-input AND gate, 9/6 each.
BP314A, 7-input NOR gate, 9/6 each.
BP315A, Dual 3-input NOR gate, 9/6 each.
BP316A, Dual 2-input NOR gate (expandable), 9/6 ea.
BP20A, 1-Kbitary element, 11/6 each.
BP322A, Dual 3-input OR gate, 9/6 each.

GIRO No. 338-7006



500, Chesham House,
150 Regent Street,
LONDON, W.1.

KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office
 When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 2/6. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

OA2	6/6	6AT6	5/-	6DS4	15/-	6Z4	5/6
OA3	9/-	6AU4GT4		6EA8	11/-	9BW6	8/6
OB2	6/6		9/-	6EH7	6/6	10C2	10/-
OB3	10/-	6AU5GT		6FJ7	7/-	10D1	8/-
OC3	7/-		22/6	6EW6	12/-	10D2	8/-
OD2	6/6	6AU6	5/-	6F6	14/-	10F1	20/-
IB3GT	7/6	6AV5GT4		6F6G	5/-	10F9	10/-
IL4	3/6		13/-	6F11	6/6	10F18	8/-
IN5GT	8/6	6AV6	9/-	6F12	4/6	10L1	8/-
IO5GT	10/-	6AW8A	11/-	6F13	7/6	10LD11	11/-
IR4	6/6	6AX5GT		6F14	12/-	10P13	11/-
IR5	7/-		13/-	6F15	11/-	10P14	20/-
IR6	5/6	6BA6	4/6	6F18	8/-	12A5	10/6
IR5	5/6	6BE6	5/6	6F22	6/6	12AC6	7/6
IT4	4/6	6BF5	16/-	6F23	15/6	12AD6	7/6
IU4	6/6	6BF6	9/6	6F24	13/6	12AH7GT	
IU5	9/6	6BG6G	12/6	6F25	15/-		
IV2	9/6	6BH6	8/6	6F26	18/-	12AL5	5/-
IX3B	7/6	6BK6	8/6	6F28	14/-	12AQ5	8/-
2CW4	12/-	6BK4	21/-	6F29	6/6	12AT6	5/6
2D21	6/6	6BK7A	10/-	6F30	7/6	12AT7	6/6
3A4	4/-	6BL7GTA		6G4	9/6	12AU6	5/6
3A5	10/-		12/-	6J5GT	6/6	12AU7	6/6
3A8GT	10/-	6BN4	7/6	6K7	8/6	12AV6	6/6
3Q4	8/-	6BN4	13/-	6K6GT	10/-	12AV7	9/6
3Q5GT	8/6	6BN5	8/6	6K7	6/6	12AX4GTB	
354	7/6	6BN6	8/6	6K8G	6/-		
3V4	8/6	6BQ5	5/6	6K23	10/-	12AX7	6/6
5R4Y	11/-	6BQ6GTB		6K25	15/-	12AY7	13/6
5U4G	6/6	6B07A	13/-	6L6GT	9/6	12B4A	16/6
5U4GB	7/6	6BR7	17/-	6L8	6/6	12B4B	6/6
5Y3GT	6/6	6BR8	13/6	6L20	6/6	12BE6	6/6
5Z3	9/6	6BS7	26/-	6N7GT	7/6	12BH7	6/6
5Z4G	7/6	6BW6	16/6	6P1	12/-	12BY7	6/6
5Z4GT	8/6	6BW7	13/6	6P28	12/6	12C8	6/6
6S0L2	15/6	6BK6	5/-	6Q7	6/6	12C16	15/6
6A8G	6/6	6BR26	6/6	6R7G	7/6	12J5GT	4/6
6AB4	6/6	6C4	6/-	6S2	8/-	12K5	10/-
6AC7	4/6	6C5GT	7/6	6S4A	11/-	12K7GT	7/6
6AF4A	9/6	6CA4	5/6	6S4T	7/6	12K8	10/-
6AG7	7/6	6CA7	10/6	6S6G	6/6	12Q7G	5/6
6AH6	10/-	6CB6	10/6	6S17	7/6	12S7	5/6
6A8	5/6	6CD6GA		6SK7	6/6	12S7G	5/6
6AK5	6/6		23/-	6L17GT	6/6	12SH7	5/6
6AK6	11/6	6C67	9/6	6SN7GT	6/6	12S7J	5/6
6AL3	8/6	6CH6	11/-	6S07	8/-	12SK7	8/6
6AL5	3/6	6CL6	10/6	6SR7	7/6	12SL7GT	8/6
6AM5	5/6	6CL6	13/6	6U4GT	12/6	12S07	8/6
6A05	6/6	6CV5	8/6	6V8	7/6	12S7R	7/6
6A06	10/6	6CV7	12/-	6G6GT	6/6	14S7	16/6
6AR5	6/6	6D3	8/6	6X4	5/-	20D1	9/6
6AR6	6/6	6DC6	13/6	6X5GT	8/6	20L1	20/-
6AS5	7/6	6DK6	8/6	6X8	11/-	20P1	10/-
6AS7G	16/-	6DQ6B	12/-	6Y6G	12/-	20P3	12/-

First Quality Fully Guaranteed



BRAND

ELECTRONIC VALVES

20P4	20/-	85A2	7/6	DY70	12/-	ECH83	8/6
20P5	20/-	90A0	48/-	DY86	6/6	ECH84	9/6
25C5	9/6	90AV	48/-	DY87	7/6	ECL80	9/6
25C6	9/6	90C1	12/-	DY802	10/-	ECL81	8/6
25L6GT	7/6	90C2	25/-	E55L	55/-	ECL82	6/6
30A1	8/6	90C3	25/-	E130L	90/-	ECL83	12/6
30A2	8/6	807	9/6	E180F	19/-	ECL84	11/-
30A3	8/6	811A	30/-	E280F	42/-	ECL85	10/6
30C1	6/6	812A	65/-	EABC80	6/6	ECL86	8/6
30C15	15/6	866A	14/-	EAF4	10/-	EFC3A	9/6
30C17	16/6	6080	27/6	EAF801	9/6	EFC39	8/6
30C18	15/6	6146	30/-	EBC33	9/6	EFC40	10/6
30F5	17/6	6146B	47/6	EBC41	10/6	EFC42	12/6
30F11	15/6	6267	6/6	EBC8T	6/6	EFC44	14/6
30F12	18/6	6360	25/6	EBC90	5/6	EFC45	13/6
30F13	10/6	6939	42/-	EBC91	6/6	EFC46	13/6
30F14	15/6	7199	15/6	EBC92	6/6	EFC47	13/6
30L1	7/6	7586	25/6	EBC93	6/6	EFC48	13/6
30L15	17/6	7591A	20/-	EBC94	6/6	EFC49	13/6
30L17	17/6	9002	6/6	EBC95	6/6	EFC50	13/6
30P12	16/6	9003	10/6	EBC96	6/6	EFC51	13/6
30P18	7/6	AZ31	10/6	EBC97	10/6	EFC52	13/6
30P19	15/6	B11	16/6	EBC98	12/6	EFC53	13/6
30PL1	15/6	CBL31	17/6	EBC99	6/6	EFC54	13/6
30PL13	18/6	CCL33	17/6	EC92	6/6	EFC55	13/6
30PL14	17/6	CY31	7/6	EC93	9/6	EFC56	13/6
35A3	10/6	DAF41	11/6	EC94	9/6	EFC57	13/6
35A5	11/6	DAF91	5/6	EC95	9/6	EFC58	13/6
35B5	13/6	DAF92	9/6	EC96	11/6	EFC59	13/6
35C5	7/6	DAF96	7/6	EC97	11/6	EFC60	13/6
35D5	13/6	DC90	9/6	EC98	6/6	EFC61	13/6
35L6GT	9/6	DF96	7/6	EC99	6/6	EFC62	13/6
35W4	5/6	DK40	10/6	EC99	6/6	EFC63	13/6
35Z3	11/6	DK91	7/6	EC99	6/6	EFC64	13/6
35Z4G	5/6	DK92	9/6	EC99	6/6	EFC65	13/6
35Z5GT	7/6	DK96	8/6	EC99	6/6	EFC66	13/6
50L6GT	8/6	D195	5/6	EC99	6/6	EFC67	13/6
50A5	13/6	D191	5/6	EC99	6/6	EFC68	13/6
50B5	7/6	D192	7/6	EC99	6/6	EFC69	13/6
50C5	7/6	D193	4/6	EC99	6/6	EFC70	13/6
50C6GT	30/-	DL94	8/6	EC99	6/6	EFC71	13/6
50L6GT	8/6	D195	5/6	EC99	6/6	EFC72	13/6
83A1	14/6	D196	7/6	EC99	6/6	EFC73	13/6
85A1	25/-	DM70	6/6	EC99	6/6	EFC74	13/6

EL85	8/6	PC88	13/6	PL508	17/6	U404	7/6
EL86	8/6	PC97	8/6	PL509	30/-	U801	20/6
EL90	6/6	PC900	9/6	PL802	16/6	UA80	6/9
EL91	7/6	PC854	7/6	PL803	14/6	UAF41	10/6
EL95	7/6	PC85	8/6	PL180	11/6	UAF42	10/6
EL360	23/-	PC88	12/6	PM84	9/6	UB41	11/6
EL803	17/6	PC89	10/6	PX4	30/-	UBC41	9/6
EL821	11/6	PC189	11/6	PX25	30/-	UBC81	8/6
EL822	18/6	PC805	17/6	PY31	5/6	UBF80	7/6
EL80	15/6	PC806	17/6	PY32	11/6	UBF89	7/6
EM34	16/6	PC800	15/6	PY33	12/6	UBL1	10/6
EM71	12/6	PCF80	6/6	PY80	6/6	UBL21	12/6
EM80	8/6	PCF82	6/9	PY81	6/6	UC92	6/6
EM81	8/6	PCF84	9/6	PY82	6/6	UC95	8/6
EM84	7/6	PCF86	11/6	PY83	7/6	UCF80	10/6
EN11	6/6	PCF87	16/6	PY88	8/6	UCF81	11/6
EN91	6/6	PCF80	15/6	PY500	20/6	UCH42	13/6
EY51	8/6	PCF801	10/6	PY800	10/6	UCH43	12/6
EY80	9/6	PCF802	10/6	PY801	10/6	UCH81	6/6
EY81	8/6	PCF805	15/6	PZ30	7/6	UCL81	11/6
EY83	11/6	PCF806	13/6	QQV02-6		UCL82	7/6
EY84	10/6	PCF808	15/6	QQV03-10		UCL83	12/6
EY86	8/6	PCH200	14/6	QQV03-10		UD143	15/6
EY87	8/6	PC181	10/6			UF9	11/6
EY88	8/6	PC182	7/9	QQV03-20A		UF11	10/6
EZ35	5/6	PC183	13/6	UF41	10/6	UF41	10/6
EZ40	9/6	PC184	8/9	UF42	12/6	UF42	12/6
EZ41	9/6	PC185	9/6	UF43	11/6	UF43	11/6
EZ80	5/6	PC186	9/6	UF80	7/6	UF80	7/6
EZ81	5/6	PC188	17/6	UF85	8/6	UF85	8/6
EZ90	5/6	PC180	17/6	UF89	7/6	UF89	7/6
FW4500/33F		PC1801	15/6	UL41	12/6	UL41	12/6
G547X	5/6	PD500	30/6	UL84	6/6	UL84	6/6
GY501	16/6	PF40D	8/6	SU2150A		UM4	8/6
GZ30	7/6	PEN36C	13/6			UM84	4/6
GZ31	6/6	PEN45	7/6	TT21	15/6	UY1N	10/6
GZ32	9/6	PEN45DD		TT22	50/6	UY11	11/6
GZ33	16/6			TT22	50/6	UY21	11/6
GZ34	11/6			U17	10/6	UY41	3/6
HBC80	8/6	PEN383	10/6	UR20	6/6	UY82	10/6
HBC90	5/6	PEN384	10/6	U120	13/6	UY85	6/6
HBC91	6/6	PEN43DD		U25	15/6	VP23	6/6
HF93	6/6			U26	15/6	VP41	7/6
HF94	6/6	PEN4A	8/6	U31	9/6	VP133	15/6
HF95	6/6	PF66	11/6	U37	30/6	VR750	9/6
HF96	6/6	PF818	17/6	U50	6/6	VR105/30	7/6
HL94	8/6	PL1200	14/6	U52	6/6	VR150/30	6/6
KT66	27/6	PF33	7/6	U76	5/6	U33	10/6
KT88	33/6	PL36	11/6	U78	5/6	U39A	10/6
MSPENT		PL81	9/6	U81	13/6	U111	10/6
		PL82	9/6	U91	15/6	U120	15/6
		PL83	8/6	U101	7/6	U153	10/6
		PL84	7/6	U281	8/6	W729	12/6
		PL302	15/6	U282	8/6	Z309	10/6
N78	21/6	PL302	15/6	U301	11/6	Z329	17/6
PABC80	8/6	PL504	16/6	U403	10/6	Z803U	17/6
PC86	11/6						

INTEGRATED CIRCUIT AMPLIFIERS

CA3005 RF Amplifier. with 100mc/s bandwidth. Max. dissipation 26mW. For use as RF amplifier, balanced mixer, product detector or self-oscillating mixer. 27/6

CA3012 wide Band Amplifier (up to 20mc/s), suitable as IF Amplifier for VHF/FM receivers. 22/6

CA3020 General Purpose Audio Amplifier of 550mW output. 30/6

CA3036 Buffer amplifier consisting of two 'super-alpha' pair of transistors suitable for stereo pick-up systems. 19/6

The above four I.C.'s are in TO5 encapsulation.

PA222 Audio Amplifier providing a max. output of 1.2 watts. 65/6

PA234 Audio Amplifier providing a max. output of 1 watt. 27/6

PA237 2 watts Audio Amplifier. 40/6

The above three I.C.'s are in epoxy moulded double four-line package.

MC1709CG General Purpose operational amplifier in TO-99 case. 40/6

TAA263 3-stage direct coupled amplifier for use from DC to 600kc/s; 70mW dissipation. Output 10mW into 150Ω load. 15/6

TAA293 3-stage amplifier with connection brought out to the individual leads. Bandwidth 600kc/s. 160mW dissipation. Output 10mW into 150Ω load. 20/6

TAA320 MOST input stage followed by a bi-polar transistor stage. 200mW dissipation. 13/6

TAD100 Integrated AM receiver circuit containing all active components, except output stage, required to build a complete receiver. 45/6

SL403A 3 watts Audio Amplifier into 7.5Ω Loudspeaker. Operating voltage 18V. Overvoltage protection. 49/6

Data sheets are available for all the above I.C.'s.

OUR NEW C

VALUABLE NEW HANDBOOK

FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

RADIO ENGINEERING
Advanced Radio — Gen. Radio — Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

ELECTRONIC ENG.
Advanced Electronic Eng. — Gen. Electronic Eng. — Applied Electronics — Prac. Electronics — Radar Tech. — Frequency Modulation — Transistors.

ELECTRICAL ENG.
Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Supply — Mining Elec. Engineering.

MECHANICAL ENG.
Advanced Mechanical Eng. — Gen. Mechanical Eng. — Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work — Welding — Eng. Pattern Making — Inspection — Draughtsmanship — Metallurgy — Production Eng.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

AUTOMOBILE ENG.
Advanced Automobile Eng. — Gen. Automobile Eng. — Automobile Maintenance — Repair — Automobile Diesel Maintenance — Automobile Elec. Equipment — Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

British Institute of Engineering Technology
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

INCLUDING TOOLS

Basic Practical and Theoretical Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy *now*—FREE and without obligation.



POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS


WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

HENRY'S RADIO LTD.

ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES


BUILD A QUALITY 4 TRACK TAPE RECORDER

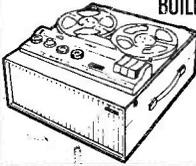

To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on it's printed circuit board - in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises: Deck, Amplifier, Cabinet and speaker, with microphone, 7" 1200 ft. tape and spare spool. ASK FOR BROCHURE 6. TODAY'S VALUE £60. PRICE 39 gns. p.p. 22/6. NOTHING ELSE TO BUY

SCOOP! STAAR RECORD PLAYER

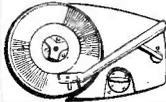Deck plays 33, 45, 78, R.P.M. records. 9 volt operated, with mono cartridge. BRAND NEW... as illustrated.



PRICE 59/6.
p.p. 3/6.
Send for leaflet No. 2.




MULLARD 1 WATT AMPLIFIER

Portable Transistor Unit/ideal for Intercoms, Baby Alarms, Telephone Record Players or Guitar Practice. 9 Volt 5 transistors with volume control, output 3 ohms. Ideal for use with STAAR RECORD DECK. PRICE 45/-. p.p. 2/6.

OTHER ITEMS. Suitable 7 x 4 inch. 3 ohm speaker 17/6 p.p. 1/6. Rexine covered cabinet 12 x 9 x 4 12/6 p.p. 2/6. P.P. 9 volt battery 3/9. Write for leaflet No. 2.

GARRARD RECORD DECKS

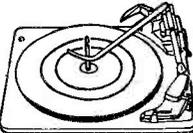

All the latest models BRAND NEW and guaranteed - TERRIFIC SAVINGS!

- *2025 STEREO £ 7.18.6.
- *2025TC DIAMOND. 9TAH.C. £ 9.18.6.
- *3000 STEREO 9TAH.C. £ 9.18.6.
- *SP 25 Mk.II £11.19.6.
- *SL 55 £11.19.6.
- *A70 Mk.II. £12.10.0.
- *AT 50 K.II. £13.10.0.
- *SL 66 £14.14.0.
- AP 75 £18. 0.0.
- 401 £28. 7.6.
- SL 75 £29. 0.0.
- SL 95 £35. 0.0.
- GL 75 GOLDRING £33. 0.0.
- GL 75 P " £45. 19.0.

ALSO IN STOCK - THORENS - Lenco - B.S.R. Carriage/insurance 7/6 extra on any model. WBA BASES £3.19.6. PERSPEX COVERS £3.10.0. *Special offer base and cover available for these models at £4.15.0. Carriage 5/-. Complete range of Cartridges/Pilnths/Covers. SEND FOR 6 PAGE BROCHURE 16/17 TODAY.

BUILD YOURSELF A QUALITY RADIO



New printed circuit design with full power output. Fully tuneable on both mw/w. bands. 7 Mullard transistors, Fitted 5" speaker, Room Filling Power. All easy to build with terrific results. All local and continental stations. Complete detailed instructions. TOTAL COST £6.19.6. p.p. 4/6. Ask for Leaflet No. 1.

TRANSISTORS DIODES RECTIFIERS

WE HAVE THE MOST COMPREHENSIVE STOCK IN GREAT BRITAIN. NEW 1969 LIST OF 1000 TYPES. SEND FOR FREE COPY TODAY (LIST 36) Whether you require one or 1000, devices we can fulfill your order from stock. For quantity quotations telephone. (011 723 040) Ex. 4. or (01) 402 6923.

HENELEC 5-5 STEREO AMPLIFIER

Excellent low priced British designed Stereo Amplifier for use with Record Decks, Mike, Tuners. 16 transistor mains operated. Output 5+5 watts for 8-15 ohm speakers. Black, silver and wood finish, size 13" x 3" x 6". PRICE £13.10.0. p.p. 7/6. (Leaflet on request). Complete Stereo System 5-5. Garrard 2025 stereo, 5-5 Amplifier, Pilnith/Cover. Two 10 watt speakers with tweeters in polished cabinets. Usual price £47.0.0. OUR PRICE £39.10.0. p.p. 20/-. ASK FOR BROCHURE 13



SINCLAIR EQUIPMENT

The SINCLAIR IC-10 is the worlds first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself has an output power of 10 watts, yet with an overall size of 1 x 0.4 x 0.2 in.

IC-10 Integrated Circuit Amplifier	59/6	OTHER TYPES OF	
Stereo 80	£9.19.6.	INTEGRATED CIRCUITS	G.E. PA246* 52/6
P25 Power Supply	£4.19.6.	RCA CA3014	SL402 45/0
O16 Loud Speaker	£8.19.6.	RCA CA3020	SL403 Pressey 49/6
P21 Amplifier	89/6	RCA CA3028	S.G.S. UL1910 10/0
P2 A Power unit	99/6	RCA CA3036	S.G.S. UL1900 10/0
Stereo 25	£9.19.6.	Sinclair I.C. 10.	S.G.S. UL1914 11/0
O14 Speaker system	£7.19.6.	G.E. PA230*	Mullard TAA263 15/0
All post paid, delivery from stock.		G.E. PA231*	20/0
		G.E. PA237*	37/6

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS. 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound.

PARTS TOTAL COST £6.19.6. DECODER £5.19.6. ASK FOR LEAFLET No. 3. (FOR STEREO)



HENRY'S RADIO Fully Illustrated Catalogues

A ALL TYPES OF ELECTRONIC COMPONENTS TEST EQUIPMENT KITS BUILT UNITS



B HIGH FIDELITY & GENERAL AUDIO EQUIPMENT CATALOGUE

COMPREHENSIVE · CLEAR · CONCISE · CATALOGUES
A Over 300 pages fully detailed and illustrated with more than 6,000 stock items. Everything for amateur and professional use. Complete with 5 vouchers 10/- value, for use with purchases. ORDER AS CATALOGUE A. PRICE 7/6. p.p. 2/-

B New audio and high fidelity catalogue. 120 pages containing ideas and equipment for every application. Special low prices for all leading makes. Plus 12/6 extra discount voucher. ORDER AS CATALOGUE B. PRICE 7/6. p.p. 1/-

WHY NOT SEND AWAY TODAY!


AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dinsdale Mk. II - each unit or system will compare favourably with other professional equipment selling at much higher prices.

£11.12.6. to £38.17.6. (all units available separately).


THE FINEST VALUE IN LOW COST HIGH FIDELITY - CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS.

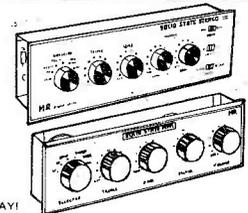SEND FOR BROCHURES No. 12/14 and 21 TODAY!



Hi-Fi equipment to suit EVERY POCKET

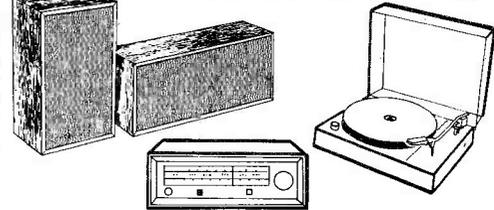HIGH FIDELITY AUDIO EQUIPMENT CATALOGUE 5/- p.p. 1/-



VISIT OUR NEW HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of - AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS - IT WILL PAY YOU TO PAY US A VISIT. AUDIO SYSTEMS £40 - £300 TO SUIT EVERY POCKET. DEFERRED TERMS AVAILABLE. SEND FOR ILLUSTRATED BROCHURE 16/17. TWO DEMONSTRATION ROOMS

ELECTRONIC ORGANS

COMPLETE KITS FOR THE HOME CONSTRUCTOR

STAR FEATURES:
*ALL TRANSISTOR PRINTED CIRCUIT DESIGNS.
*BRITISH DESIGN. *STEP BY STEP DETAILED INSTRUCTIONS. *GIVES UP TO 50% ON COMMERCIAL EQUIVALENT. *EVERYTHING SUPPLIED DOWN TO THE LAST ITEM. *FULL AFTER-SALES SERVICE & ADVICE. *CREDIT SALE & H.P. TERMS AVAILABLE.

We are pleased to offer the choice of FOUR British designs from a single manual portable at £99 THE MAYFAIR for light or classical music - to a two manual five octave de-luxe model with OAK CONSOLE from £285 for the serious musician.

*These kits are the result of years of research and design and offer the best that is essential to good organ designs, coupled with excellent value are within the reach of most pockets. No technical skill or knowledge is required in construction, with the aid of the STEP BY STEP illustrated manuals will produce an instrument that will be a delight to own and use and will give years of trouble free entertainment for the whole family.

SEND FOR ILLUSTRATED BROCHURES 9/10/11 TODAY! When in LONDON · CALL IN, SEE, HEAR, PLAY FOR YOURSELF.

Organ Demonstration Room 1st Floor. PRACTICAL ELECTRONICS ORGAN - ORGAN COMPONENTS

We are able to supply all items for this series, details on request.

Start building for as little as £10

MODELS FROM £99 - £350.

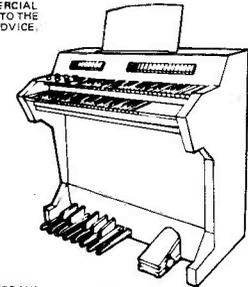


ILLUSTRATION of GROSVENOR ELECTRONIC ORGAN

Built models available from £124.

HENRY'S RADIO LTD.

Mail Order Dept., Components, Organ Dept.
303 EDGWARE ROAD, LONDON W.2.
Telephone: 01-723 1008/9


High Fidelity and Equipment Centre
309 EDGWARE ROAD, LONDON W.2.
Telephone: 01-723 6963

OPEN MON-SAT 9am-6pm THURS 9am-1pm

PRACTICAL WIRELESS

FEBRUARY
1970

30

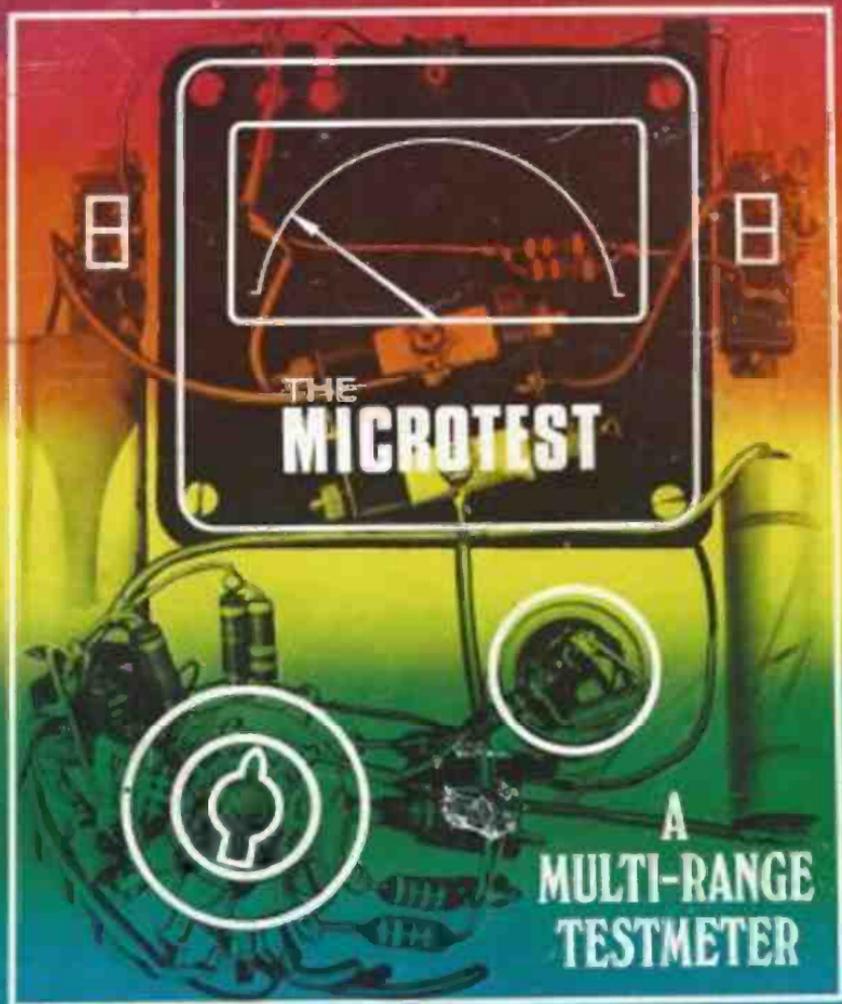

A
MULTI-RANGE
TESTMETER