

# PRACTICAL WIRELESS

AUGUST  
1970

3/6

## MODULAR

## 3-Band Short Wave

## RECEIVER



also featuring:-

## ELECTRONIC METRONOME



and...  
VERSATILE  
HAM  
TRANSMITTER  
'GENETRACER'  
TESTER

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard  $3/16"$  (4.75 mm) diameter, detachable copper chisel-face bit\*.

Standard temp.  $360^{\circ}\text{C}$  at 23 watts.

Special temps. from  $250^{\circ}\text{C}$ — $410^{\circ}\text{C}$ .

**\*Additional Stock Bits**  
(illustrated) available

### COPPER

**B 38**  $1/4"$  — 3.2 mm CHISEL FACE

**B 14**  $3/32"$  — 2.4 mm CHISEL FACE

**B 24**  $1/16"$  — 4.75 mm SCREWDRIVER FACE

**B 12**  $3/32"$  — 4.75 mm EYELET BIT

**B 58**  $1/2"$  — 5.34 mm CHISEL FACE


### LONG LIFE

**B 42 LL**  $1/16"$  — 4.75 mm CHISEL FACE

**B 38 LL**  $1/4"$  — 3.2 mm CHISEL FACE

**B 14 LL**  $3/32"$  — 2.4 mm CHISEL FACE

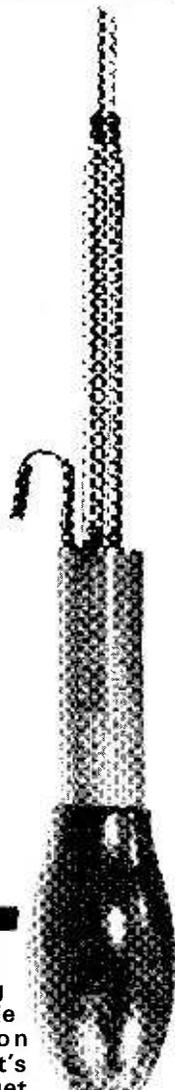**B 44 LL**  $1/16"$  — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.




**ADCOLA PRODUCTS LTD.,**  
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

\*  
Write for price list and catalogue

# JACKSONS

Radio and Electronic Components  
(Made in England)

## SL 16 DRIVE

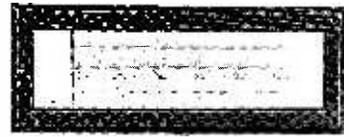

General Purpose Slide Rule Drive. Calibrated 0—100. Aluminium Scale. With provision for individual calibration. Scale Length  $4\frac{3}{8}"$ . Black Escutcheon  $7\frac{1}{4}" \times 2\frac{3}{8}"$  overall. Fitted with Glass. Smooth 10:1 reduction.

Price 26/-



It's reliable if it's made by JACKSON!

MADE IN ENGLAND

**JACKSON BROS. (LONDON) LTD.**


Dept. RCm, Kingsway-Waddon Croydon, CR9 4DG  
Telephone 01-688 2754

Telegrams Walfilco, Croydon

U.S. Office: M. Swedgal, 258 Broadway, New York, N.Y. 10007
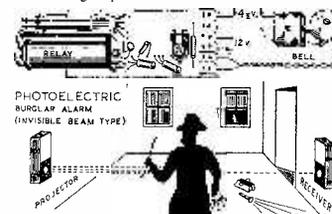
## PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



**PHOTOELECTRIC KIT**  
39/6

Postage and Pack. 2/6 (UK)  
Commonwealth:  
SURFACE MAIL 3/6  
AIR MAIL £1.00  
Australia, New Zealand,  
S. Africa, Canada and U.S.A.  
Also Essential Data Circuits  
and Plans for Building  
10 Advanced Designs

### INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

### LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

### JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm. Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs".

Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

### JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

## YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

# TMK METER KITS

These meter kits by TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinet is supplied with the meter, scale and movement and the range selector in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional, circuit and operating instructions.

## MODEL 200

20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale.



Large 3 1/2 in. meter. Full scale accuracy: DCV and current: ±2%, ACV: ±3%, resistance ±3%. Special 0-5V DC range for transistor circuit measurements.


### SPECIFICATION

- DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV.
- ACV: 0-8-30-120-600-1,200V at 10K/OPV.
- DC Current: 0-8 0-6-800mA.
- Resistance: 0-10-K 100K-1M-10M ohms (50-500-5-5K at mid-scale).
- Capacitance: 0-0.02-0.2μF (AC V range).
- Diacibles: -20 to +63dB.
- Output: 0.05μF blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet. Size 5 1/2 x 3 1/2 in. Complete with test leads.

**KIT PRICE ONLY 92/-** Post 3/6

# WHARFEDALE

## UNIT 3 SPEAKER KIT

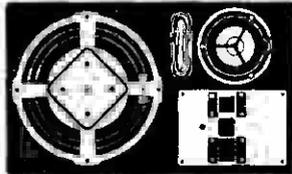

3in tweeter uses new Wharfedale "AcoustiDrene" dome diaphragm. Crossover unit Crossover freq. 1,750Hz. ALL accessories, acoustic wadding, mounting bolts, wire, etc., are supplied, you provide the cabinet to suit your needs. 8in. Bass/Mid. range speaker employing a powerful magnet assembly with diecast chassis and Fiberglass roll surround. The Wharfedale Unit 3 speaker kit can be constructed by anybody and with a suitable cabinet.

net will provide a highly sophisticated system giving true Hi-Fi reproduction from 40-17,000Hz. Impedance 4/8 ohms. Max. power handling 15W.

**£11.19.6 each** Post 5/- **£20 per pair** Post 10/-

## UNIT 4 SPEAKER KIT

2 speakers (12in. Bass and 3in. Treble) to give full range, balanced reproduction. Frequency response of 45-17,000Hz when housed in suitable cabinet. Superior 4-element crossover unit ensures optimum performance from each speaker.

**£16 each** Post 5/- **£30 per pair** Post 10/-

## UNIT 5 MONITOR SYSTEM KIT


3 speakers (12in. Bass, 5in. M.-R. unit, 1in. Treble) give clean, smooth performance. Frequency response of 40-20,000Hz when housed in suitable cabinet. Unique mechanical electrical 6 element crossover unit.

**£23.10 each** Post 7/6 **£42.10 per pair** Post 15/-

# TTC HEADPHONES
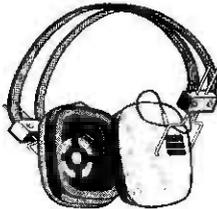
## MODEL G-III

Yet another outstanding TTC product which gives you exceptional value plus super quality. These stereo phones use two 3in low imp. high flux density dynamic reproducers. Freq. Res. 25-15,000Hz. Fitted with foam cushioned adjustable earpads for super listening comfort. Imp. 8 ohms, matching 18 ohms. Max. input 0-5W. Complete with 36in shielded grey cable. Pearl grey finish with double spring headband.



**ONLY 63/-** Post 3/6

# USA MADE CASSETTES

## AT LASKY'S BUDGET PRICES

C80	7/8 each post 7/-	35/- post 2/-	65/- post 3/-
C90	12/8 each post 7/-	57/8 post 2/-	115/- post 3/-
C120	17/8 each post 7/-	85/- post 2/-	165/- post 3/-

# Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271  
 33 TOTTENHAM CT. RD, LONDON, WIP 9RB. Tel: 01-636 2605  
 Open all day, 9 a.m.-6 p.m. Monday to Saturday  
 109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812  
 152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833  
 Open all day Thursday, early closing 1 p.m. Saturday


**HIGH FIDELITY AUDIO CENTRES**  
 42-45 TOTTENHAM CT. RD, LONDON, WIP 9RD. Tel: 01-580 2573  
 Open all day, 9 a.m.-4 p.m. Monday to Saturday  
 118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789  
 Open all day Saturday early closing 1 p.m., Thursday



**ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821**

# EXCLUSIVE

# DIGITAL CLOCK SCOOP!

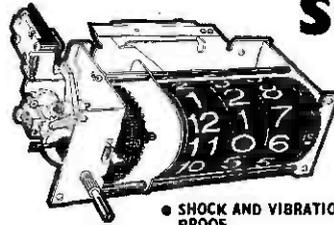

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light etc. at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall) from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBBS.

**LASKY'S PRICE £6.19.6** Post 3/6  
 SPECIAL QUOTATIONS FOR QUANTITIES

# Audio Development



## AD-309K

PRECISION PICK-UP ARM COMPLETE WITH AD-76K MAGNETIC CARTRIDGE

The new AUDIO DEVELOPMENT precision pick-up arm—ready fitted with the outstanding AD-76K magnetic cartridge is constructed of brass throughout, heavily chrome plated; uses needle and miniature ballface bearings; both coarse and fine balance adjustment is provided. The fixed head has standard 1/2 in. mounting centre and is finished in black enamel with chrome fitting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 295mm; media to pivot length 223mm; offset angle 24°; overhang 10mm. Requires angle 7/16in dia. mounting hole.

**LASKY'S PRICE £9.19.6** POST 3/6  
**AUDIO DEVELOPMENT AD-76K**  
 Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms/0.5 gm. Replacement stylus type Y.960S 5/16.  
**AUDIO DEVELOPMENT AD-96K**  
 Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms. Replacement stylus type JS.P1 4 1/2 in., post free.

# Audio Tronics 70

## LASKY'S PRICE £9.19.6 POST 3/6

**AUDIO DEVELOPMENT AD-76K**  
 Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms/0.5 gm. Replacement stylus type Y.960S 5/16.


**AUDIO DEVELOPMENT AD-96K**  
 Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms. Replacement stylus type JS.P1 4 1/2 in., post free.

**£5.18.6** Post Free

# Audio Tronics 70

The 1970 edition of Lasky's Audio-Tronics catalogue is available FREE on request. Packed with 1000's of items for the Radio and Hi-Fi enthusiast. Electronics Hobbyist, Servicemen and Communications Ham. Covers every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories plus Lasky's amazing money saving vouchers worth over £25. **SEND TODAY.** Send your name, address and 3/- for post and inclusion of your name on our regular mailing list

**This month's voucher worth 50/-**

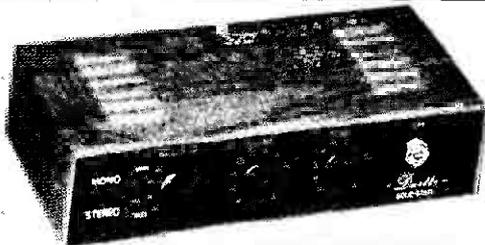

£9.10. plus 7/6 p. & p.

**Controls:** Selector switch Tape speed equalisation switch (32 and 74 l.p.s.). Volume, Treble, Bass, 2 position scratch filter and 2 position rumble filter.

**Specification:** Sensibilities for 10 watt output at 1KHz into 3 ohms. *Tape head:* 3mV (at 3 1/2 l.p.s.). *Mag. P.U.:* 2mV. *Cer. P.U.:* 80mV. *Tuner:* 100mV. *Aux.:* 100mV. *Tape/Rec. output:* Equalisation for each input is correct to within  $\pm 2$ dB (R.I.A.A.) from 20Hz to 20KHz. *Tone control range:* Bass  $\pm 13$ dB at 60Hz. Treble  $\pm 14$ dB at 15KHz. *Total distortion:* (for 10 watt output)  $< 1.5\%$ . *Signal noise:*  $< -60$ dB. A.C. mains 200-250V. Built and tested. Size 12 1/2 in long, 4 1/2 in deep, 2 1/2 in high. Teak finished case.


### THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer, with matching vinyl grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION—

Impedance 3, 8 or 10 ohms (please state requirement). It incorporates Goodmans high flux 6in x 4in speaker and 2 1/2in speaker. Teak finish 12in x 6 1/2in x 5 1/2in. 4 guinea each. 7/8 p. & p.

### 50 WATT AMPLIFIER

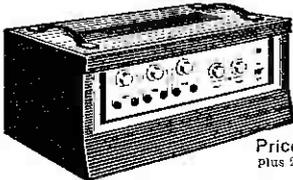

A.C. Mains 200-250V


Price £28.10 plus 20/- p. & p.

An extremely usable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

#### TECHNICAL SPECIFICATIONS

3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. **SENSITIVITIES AND INPUT IMPEDANCES:** Channels 1 and 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 and 4 300mV at 1M. Suitable for most high output instruments (gram, tuner, organ, etc.). Input

### THE RELIANT

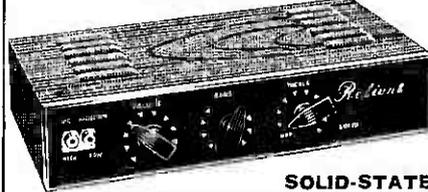

#### SOLID-STATE GENERAL PURPOSE AMPLIFIER

##### SPECIFICATIONS

Output—10 watts. Output impedance—3 to 4 ohms. Inputs—1. -xtal mic 10mV. **Tone Controls:** Treble control range  $\pm 12$ dB at 10KHz. 2. -gram/radio 250mV. Bass control range  $\pm 13$ dB at 100Hz. **Frequency Response:**—with tone controls central. Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than 60dB. **Transistors:**—4 silicon Planar type and 3 Germanium type. **Mains input:**—230/250V. A.C. Size of chassis—10 1/2 in x 4 1/2 in x 2 1/2 in. For use with Std. or L.P. records, musical instruments, all kinds of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram, and mike. Built and tested.

##### RELIANT Mk. I

As above less teak case  
£6.10 plus 7/6 P. & P.

##### RELIANT Mk. II


In teak finished case  
£7.5 plus 7/6 P. & P.

sensitivity relative to 10V output. **TOSE CONTROLS ARE COMMON TO ALL INPUTS:** Bass Boost +12dB at 50Hz. Bass Cut—13dB at 60Hz. Treble Boost +11dB at 15 KHz. Treble Cut—12dB at 10 KHz. With bass and treble controls central—3dB points are 30 Hz and 20 KHz. **POWER OUTPUT:** For speech and music 30 watts rms, 100 watts peak. For sustained music 45 watts rms, 90 watts peak. For sine wave 30.5 watts rms, nearly 60 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.18% at 1KHz. Output to match into 8 or 16 ohm speaker system. **NEGATIVE FEEDBACK** 90dB at 1KHz. **SIGNAL TO NOISE RATIO** 60dB. **MAINS VOLTAGES** adjustable from 200-250V A.C. 50-60Hz. A protective fuse is located at the rear of the unit. Output-impedance 3, 8 and 16 ohms.


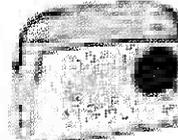
### The ELEGANT SEVEN Mk. III (350m W Output)

7-transistor fully-tunable M.W.—L.W. superhet. Portable Set of 4. Complete with 4 components, including 2 x 7 pinched and drilled printed circuit board—back printed for foolproof construction. **MAINS POWER PACK KIT:** 9/6 extra. Price £5.5.0 plus 7/6 P. & P. Circuit 2/6 FREE WITH PARTS



### The DORSET (600m W Output) Price £5.5.0 plus 7/6 P. & P.

Circuit 2/6 FREE WITH PARTS

7-transistor fully tunable M.W.—L.W. superhet portable—with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Size: 12 x 8 x 3in. **MAINS POWER PACK KIT:** 9/6 extra


### QUALITY MAINS TRANSFORMER

Input 240 volts. **OUTPUT (All RMS values):** 4 windings of 11.5 volts connected in series total 46 volts at 4.5 amps (conservatively rated). The following combinations may be used. 1. 230-23 volts. 2. 46 volts. Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price 35/- plus 7/6 P. & P.


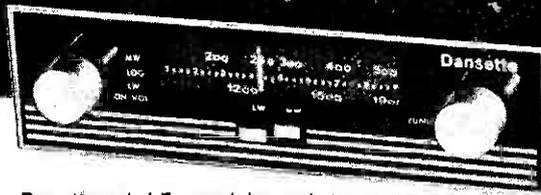
# LIQUIDATED STOCK DANSETTE TOURISTE MK3 CAR RADIO



Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold complete for £15.4.6.

SET OF PARTS

£6.6.0

Circuit diagram 2/6. Free with parts

plus 7/6 P. & P.

Speaker, baffle and fixing kit 25/- extra plus 4/- P. & P. Postage free when ordered with parts.

See top of previous page for address


RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED

# R+TV

**RADIO & TV COMPONENTS (Acton) Ltd.**  
 21c High Street, Acton, London W.3.  
 Also at 323 Edgware Road, London, W.2.  
**ALL ORDERS BY POST TO OUR ACTON BRANCH**  
 Terms C.W.O. All enquiries S.A.E.
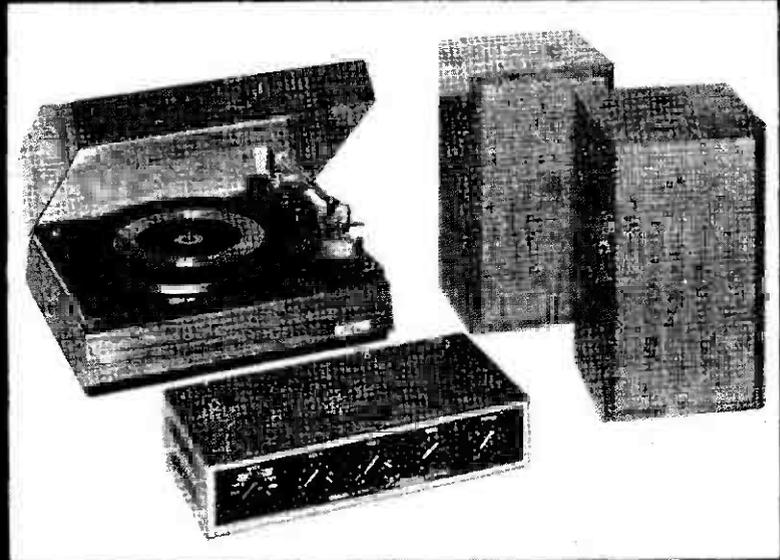
## Complete Stereo System £41

**WITH VISCOUNT F.E.T.**  
 FIELD EFFECT TRANSISTORS AMPLIFIER



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. Mk I amplifier on which full details are given below, the famous Garrard SP 25 Mk II (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers. Measuring 17½in x 10½in x 6½in, the Duo type 2 speakers are beautifully finished in teak veneer with matching wynaïr grills. They incorporate a 10½in x 6½in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo speaker system is also available separately at £8.6.0 each, plus 15/- p. & p.

Complete stereo system £41 plus £2.10. p. & p.

### The Viscount F.E.T. Mk I £14.5 plus 7/6 p. & p.

**Specification**—Output per channel 10 watts r.m.s. Frequency bandwidth 20 Hz to 20 kHz + 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5% Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

**Signal to noise ratio**—70db on all inputs (with vol. max). **Controls**—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass ± 14db at 60 Hz. Treble (with D.P.S. on off) ± 12 db at 10 KHz. Tape recording output sockets on each channel. Size 12½in. 6in. 2½in. in teak-

finished case. **BUILT & TESTED.** MkII (MAG P.U.) £15.15 plus 10/- p. & p. Specification same as Mk. 1, but with the following inputs. Mag. P.U. CER. P.U. Tuncr. Spec. on Mag. P.U. 3mV at 1 kHz Input Impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max).

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

### The £29-10-0 Stereo system

The Duetto is a good quality stereo amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

**SPECIFICATION**—R.M.S. power output 3 watts per channel into 10 ohms speakers.

**INPUT SENSITIVITY.** Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

**CONTROLS:** 4-position selector switch (2 pos. mono and 2 pos stereo) dual ganged volume control.



**TONE CONTROL** Treble lift and cut Separate on off switch. A preset balance control.

Duetto integrated transistor stereo Amp. Garrard Changer from Cover and teak finish plinth Duo Type 1 speakers (see opp. page) The above items purchased together

£9.10.0 + 7/6 p&p.  
 £7.19.6 + 7/6 p&p.  
 £4.15.0 + 7/6 p&p.  
 ea. £4. 4.0 + 7/5 p&p.  
 £29.10.0 + £1.10 p&p.



# COMET

## Hi-Fi DISCOUNT WAREHOUSES

- All items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Complete Free price list of over 800 items on request.



Customers Welcome

Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.

Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday, Thursday & Friday.

	Rec. Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>		
ARENA 210 Amplifier ..	£34 13 0	£28 0 0
ARMSTRONG 621 ..	£52 0 0	£42 19 6
DULCI 207 ..	£25 0 0	£17 0 0
DULCI 207M ..	£30 0 0	£20 19 0
GOODMANS Maxamp ..	£54 0 0	£44 19 6
LEAK Stereo 30 Plus ..	£53 0 0	£43 19 6
LEAK Stereo 30 Plus ..		
In teak case ..	£59 10 0	£47 19 6
LEAK Stereo 70 ..	£65 0 0	£52 19 6
LEAK Stereo 70 In teak case ..	£71 10 0	£56 19 6
LINEAR LT.66 ..	£18 18 0	£15 19 6
METRO SOUND ST 20 ..	£32 0 0	£25 19 6
PHILIPS RH 591 ..	£72 0 0	£59 19 6
PHILIPS RH 592 ..	£48 0 0	£37 19 6
PHILIPS RH 580 ..	£26 0 0	£19 19 6
PIONEER SA500 ..	£62 1 11	£45 0 0
PIONEER SA700 ..	£98 0 0	£74 19 6
PIONEER SA900 ..	£134 2 0	£99 19 6
PIONEER Reverberation ..	£45 9 11	£35 19 6
QUAD 33 Pre-amplifier ..	£43 0 0	£36 19 6
QUAD 303 Main Amplifier ..	£55 0 0	£48 19 6
ROGERS Ravensbourne ..	£59 10 0	£46 19 6
ROGERS Ravensbourne (cased) ..	£64 0 0	£49 19 6
ROGERS Ravensbrook ..	£44 0 0	£38 19 6
ROGERS Ravensbrook (cased) ..	£49 0 0	£39 19 6
SINCLAIR 2000 ..	£30 9 0	£24 19 6
TELETON 203E ..	£28 7 6	£19 19 6
TRUVOX TSA. 200 ..	£54 12 0	£43 19 6

	Rec. Retail Price	Comet Price
<b>TUNERS</b>		
ARENA F211 ..	£39 10 0	£33 19 6
ARMSTRONG 623 AM/FM ..	£52 0 0	£44 19 6
ARMSTRONG 624 FM ..	£40 4 6	£34 19 6
ARMSTRONG M6 decoder ..	£9 10 0	£7 19 6
DULCI FMT.75M ..	£22 1 0	£17 19 6
DULCI FMT.75 Stereo ..	£31 0 0	£23 5 0
GOODMANS Stereomax ..	£62 10 8	£51 19 6
LEAK Stereoletic Chassis ..	£59 18 0	£51 19 6
LEAK Stereoletic in teak case ..	£87 3 6	£59 19 6
PHILIPS RH 690 ..	£39 0 0	£31 19 6
PIONEER TX600 AM/FM ..	£77 18 9	£63 19 6
PIONEER TX900 AM/FM ..	£163 13 10	£128 0 0
QUAD Stereo FM ..	£51 0 0	£39 19 6
ROGERS Ravensbourne ..	£61 17 9	£48 19 6
ROGERS Ravensbrook ..	£45 0 2	£39 19 6
ROGERS Ravensbrook (cased) ..	£51 5 3	£42 19 6
SINCLAIR 2000 ..	£26 14 6	£19 4 6
TRUVOX FM 200/1C ..	£60 11 10	£39 19 6

All above tuners are complete with MPX stereo decoder

	Rec. Retail Price	Comet Price
<b>TUNER/AMPLIFIERS</b>		
ARENA 2400 ..	£90 0 0	£71 19 6
ARENA 2600 Stereo AM/FM ..	£111 6 0	£94 0 0
ARENA 2700 Stereo ..	£105 0 0	£85 0 0
ARENA T1500F ..	£72 0 0	£59 19 6
ARENA T9000 ..	£303 9 0	£258 0 0
ARMSTRONG 925 ..	£87 16 9	£68 19 6
ARMSTRONG 926 ..	£98 15 8	£79 19 6
ARMSTRONG M6 decoder ..	£9 10 0	£7 19 6
GOODMANS 3000 ..	£77 14 7	£66 19 6
PHILIPS RH851 ..	£174 19 6	£154 19 6
PHILIPS RH790 ..	£125 0 0	£101 19 6
PHILIPS RH891 ..	£83 0 0	£70 10 0
PIONEER KX330 AM/FM/SW ..	£78 12 4	£62 19 6
PIONEER SX770 AM/FM ..	£160 8 6	£129 19 6
PIONEER SX990 AM/FM ..	£194 14 8	£155 0 0
TELETON F.2000 ..	£51 0 0	£37 19 6
TELETON TATI ..	£133 0 0	£85 0 0
TELETON R4200 ..	£51 15 0	£42 19 6
TELETON CR/10T ..	£39 0 0	£29 19 6
TELETON TF550 ..	£74 0 0	£56 19 6

All above Tuner Amplifiers are complete with MPX decoder

### CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

	Rec. Retail Price	Comet Price
<b>PICKUP ARMS</b>		
GOLDRING Lenco L75 ..	£12 6 6	£10 10 0
GOLDRING Lenco L69 ..	£9 5 9	£7 0 0
SME 3009 with S2 shell ..	£31 6 3	£25 19 6
SME 3012 with S2 shell ..	£33 7 3	£28 19 6

## DELIVERY BY SECURICOR within 72 hours

All in-stock items value over £50 delivered by Securicor within 72 hours. (Add 12/- only for Securicor delivery) All Goods fully insured against loss or damage whilst in transit.

	Rec. Retail Price	Comet Price
<b>TURNTABLES</b>		
ARENA SP25 with base, cover ..	£22 1 0	£17 19 6
GARRARD SP25, fully wired with Goldring 8800 magnetic cartridge, complete with base, plinth and cover ..	£25 1 6	£21 5 0
Special price ..	£20 19 6	
GARRARD SP.25 Mk II ..	£19 11 4	£10 19 6
GARRARD AP.75 ..	£23 16 0	£17 19 6
GARRARD SL.65 ..	£13 17 9	£11 12 6
GARRARD SL.65B ..	£18 6 5	£14 9 6
GARRARD SL.75B ..	£26 12 5	£20 19 6
GARRARD SL.95B ..	£45 9 1	£37 19 6
GARRARD 401 ..	£31 14 2	£26 10 0
GARRARD SL.72B ..	£30 2 0	£24 19 6
GARRARD 3500 with GKS Cartridge ..	£15 15 0	£11 19 6
GOLDRING GL.69 ..	£25 1 6	£21 5 0
GOLDRING 69P ..	£33 11 9	£28 19 6
GOLDRING GL.75 ..	£36 8 2	£29 18 6
GOLDRING 75P ..	£46 18 8	£38 19 6
GOLDRING Covers for 69P and 75P ..	£4 4 3	£3 8 0
GOODMANS 3025 ..	£27 14 6	£22 19 6
PHILIPS 226 ..	£19 19 6	£16 19 6
PHILIPS GA146 ..	£29 19 8	£24 16 0
PHILIPS 217 ..	£22 0 8	£27 6 0
PHILIPS 202 Electronic ..	£84 0 0	£54 0 0
THORENS TO.125 ..	£75 17 8	£59 19 6
THORENS 125AB ..	£120 3 11	£89 19 6
THORENS 150A Mk II ..	£43 12 7	£32 19 6
THORENS 150AB Mk II ..	£47 5 7	£40 19 6
THORENS TO.124/11 ..	£45 15 10	£39 19 6

Bases, plinths, and covers stocked.

	Rec. Retail Price	Comet Price
<b>SPEAKERS</b>		
ARENA HT 27 ..	£18 18 0	£13 19 6
ARENA HT 28 ..	£17 17 0	£12 19 6
ARENA HT 21 ..	£10 10 0	£9 5 0
ARENA HT 7 ..	£19 19 0	£17 0 0
ARENA HT 10 ..	£22 1 0	£18 19 6
ARENA HT 20 ..	£32 11 0	£26 19 6
ARENA HT 26 ..	£78 15 0	£65 19 6
B & W DM3 ..	£63 0 0	£53 6 0
B & W P2H ..	£94 10 0	£79 0 0
B & W DM ..	£32 0 0	£26 19 6
CELESTION Ditton 10 ..	£21 3 2	£17 5 0
CELESTION Ditton 15 ..	£29 0 0	£22 10 0
CELESTION Ditton 25 ..	£39 17 0	£49 0 0
DULCI AS 3 ..	£8 0 0	£6 19 6
GOODMANS Malesia ..	£57 0 0	£48 19 6
GOODMANS Maxim ..	£20 7 9	£16 19 6
GOODMANS Mezzo II ..	£33 18 0	£23 10 0
GOODMANS Magnum-K ..	£40 2 0	£29 19 6
GOODMANS Marimba ..	£24 0 1	£19 19 6
GOODMANS Mamba ..	£22 5 6	£17 19 6
GOODMANS 3005 (pair) ..	£25 0 0	£21 0 0
KEF Calista ..	£29 0 0	£22 10 0
KEF Concord ..	£43 10 0	£33 19 6
KEF Concerto ..	£53 10 0	£44 19 6
KEF Cresta ..	£22 3 4	£19 19 6
LEAK Sandwich ..	£45 10 0	£34 19 6
LEAK Mini-Sandwich ..	£29 15 0	£22 19 6
LOWTHER Acousia (with PM7) ..	£45 10 0	£38 7 6
LOWTHER Acousia (with PM7) ..	£53 0 0	£45 19 6
LOWTHER Ideal Baffle ..	£35 10 0	£29 17 8
QUAD Electrostatic ..	£86 0 0	£52 19 6
PHILIPS RH 481 ..	£11 0 0	£9 2 6
PHILIPS RH 482 ..	£21 0 0	£14 19 6

	Rec. Retail Price	Comet Price
<b>WHARFEDALE Speakers</b>		
Alredale ..	£69 10 0	£57 14 0
Denton ..	£19 0 0	£14 19 6
Super Linton ..	£22 10 0	£18 10 0
Melton ..	£29 10 0	£22 19 6
Dovedale 3 ..	£59 10 0	£29 18 8
Roadside ..	£59 10 0	£48 19 6
<b>WHARFEDALE UNIT</b>		
3 Speaker Kit ..	£11 19 6	£9 19 6
WHARFEDALE UNIT 4 Speaker Kit ..	£16 0 0	£13 10 0
WHARFEDALE UNIT 5 Speaker Kit ..	£23 10 0	£19 19 6

	Rec. Retail Price	Comet Price
<b>CHASSIS SPEAKERS</b>		
GOODMANS Axielle 8 ..	£7 2 1	£5 13 6
GOODMANS Twinzietta 8 ..	£8 0 7	£6 8 0
GOODMANS Axiom 10 ..	£8 8 0	£6 14 0
GOODMANS Axiom 201 ..	£12 10 0	£9 7 6
GOODMANS Axiom 301 ..	£17 18 0	£13 8 6
GOODMANS Audiom 91 ..	£11 6 8	£8 9 6
GOODMANS Audiom 81 ..	£16 7 0	£12 6 6
GOODMANS Audiom 81 ..	£27 12 0	£20 14 0
GOODMANS Audiom 81 ..	£31 5 0	£23 8 6
GOODMANS Audiom 91/100 ..	£34 17 0	£26 9 6
GOODMANS ARU 180 ..	£37 13 8	£2 18 6
GOODMANS ARU 280 ..	£3 17 8	£2 18 6
GOODMANS ARU 480 ..	£5 5 4	£4 1 3
GOODMANS ARU 172 ..	£3 17 8	£2 18 6
GOODMANS Trebax 100 ..	£7 9 0	£5 11 6
GOODMANS Trebax 5K/20KL ..	£8 8 0	£6 6 0
GOODMANS Midax ..	£11 4 0	£8 8 0
GOODMANS Titanator ..	£3 1 4	£2 6 0
<b>GOODMANS Crossover</b>		
Networks X0/950/5000 ..	£8 8 7	£6 6 0
GOODMANS Crossover Networks XD/950 ..	£6 7 9	£4 15 9
GOODMANS Crossover Networks X0/5000 ..	£2 6 0	£1 14 6
<b>WHARFEDALE 8 inch Bronze/RS/DD ..</b>		
	£4 8 0	£3 13 6
<b>WHARFEDALE Super 8/RS/DD ..</b>		
	£7 12 0	£6 6 0
<b>WHARFEDALE Super 10/RS/DD ..</b>		
	£12 14 0	£10 10 0
<b>WHARFEDALE WMT 1 Matching Transformer ..</b>		
	16 9	13 6

	Rec. Retail Price	Comet Price
<b>HI-FI STEREO TAPE DECKS AND TAPE RECORDERS</b>		
AKAI 150D ..	£130 2 4	£109 0 0
AKAI X-360 ..	£339 0 0	£284 0 0
AKAI X-360D deck ..	£290 0 0	£243 0 0
AKAI 1800 ..	£109 0 0	£91 0 0
AKAI 1800SD ..	£158 0 0	£133 0 0
AKAI 1800SD ..	£199 0 0	£167 0 0
AKAI 4000 ..	£124 18 0	£99 19 6
AKAI 4000 D deck ..	£289 19 6	£242 19 6
ALBA R222 Battery/Mains ..	£50 5 0	£29 19 6
BUSH TP 69 Cassette Tape Recorder ..	£27 15 8	£24 19 6
FERGUSON 3824 Twin Track ..	£33 14 0	£24 19 6
FERGUSON 3246 ..	£41 14 0	£32 19 6
FERGUSON 3247 4-track ..	£47 1 0	£37 19 6
FERGUSON 3244 Stereo 4-track ..	£97 18 0	£79 19 6
GRUNDIG C200 Cassette ..	£37 19 0	£29 19 6
GRUNDIG TK 120 Continental ..	£29 5 0	£25 19 6
GRUNDIG TK 124 ..	£44 18 0	£34 19 6
GRUNDIG TK 144 ..	£49 19 8	£39 19 6
GRUNDIG 149 ..	£57 12 8	£47 19 6
MARCONI 4218 Stereo tape Recorder ..	£89 11 2	£69 19 6
PHILIPS 3302 Cassette Tape Recorder ..	£28 7 0	£21 19 6
PHILIPS 4302 Twin Track Auto ..	£35 17 6	£25 19 6
PHILIPS 4307 4-track ..	£49 10 0	£38 19 6
PHILIPS N4404 (4 track stereo) ..	£83 0 0	£68 19 6
PHILIPS N4407 Stereo ..	£105 0 0	£89 19 6
PHILIPS N4308 ..	£80 10 0	£69 19 6
TELETON FXB 570D Stereo TRUVOX PD 102 ..	£52 10 0	£43 19 6
Stereo Tape Recorder ..	£114 15 3	£79 0 0

# COMET Hi-Fi DISCOUNT WAREHOUSES


Reservoir Road, Clough Road, Hull HU6 7QD. Tel 407906  
 also at 68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055

Customers are welcome to call personally. Ample Car Parking facilities

Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Comprehensive Hi-Fi Catalogue available 5/-

# COMPLETE STEREO SYSTEM

FOR ONLY **39 GNS**  
CARRIAGE 35/-

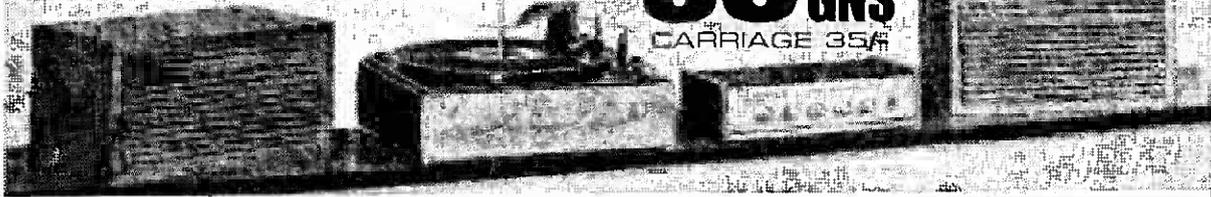

**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier, Garrard 2025 T/C manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on off, stereo mono switch. Brushed aluminium front panel Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

**PREMIER STEREO SYSTEM "TWO"**  
As system "ONE" above but with Garrard 8F23.  
**PREMIER PRICE 45 Gns.** Carr. 35/-



## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, acid or humidity. High polished splices free finish. Smooth output throughout the entire audio range. Double wrapped-attractively boxed.

LP3 3" 850' P.V.C.	5/6	LP6 5 1/2" 1200' P.V.C.	12/8
TP3 3" 450' POLYESTER	7/6	DT6 5 1/2" 1800' POLYESTER	22/8
DT3 3 1/2" 800' POLYESTER	11/6	TT6 5 1/2" 2400' POLYESTER	37/6
SP5 5" 800' P.V.C.	8/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	LP7 7" 1800' P.V.C.	15/-
DT5 5" 1200' POLYESTER	15/-	DT7 7" 2400' POLYESTER	25/-
		TT7 7" 3600' POLYESTER	50/-

TAPE SPOOLS 3" 1/2, 5", 5 1/2", 7", 1 1/2, 2" (3 reels and over Post Free).  
Post and Packing 3" 1/2, 5", 5 1/2", 1 1/2, 7", 2" (3 reels and over Post Free).



**TAPE CASSETTES**


C60 (60 min.)	7/6	3 for 21/-
C90 (90 min.)	12/6	3 for 36/-
C120 (120 min.)	17/6	3 for 51/-

P. & P. 1/-

**CASSETTE HEAD CLEANER**  
Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. **11/6** P. & P. 1/-  
All cassettes can be supplied with library cases at 6d. extra each
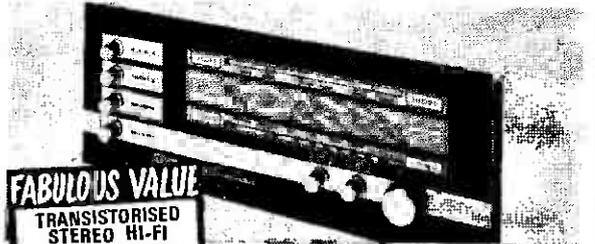
# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



**FABULOUS VALUE**  
**TRANSISTORISED STEREO HI-FI RECORDER PLAYER**  
Build your own Hi-Fi Record Player with the Sereade fully transistorised amplifier which comes complete with 2-10" x 8" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer. Advanced solid state amplifier only 4 1/2" deep. 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50 15,000 c/s. EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED  
Only **28 Gns.** + P & P 17/6  
Credit terms available. First monthly payment £3.6.2 followed by 9 monthly payments of £3.8.2. (Total "Credit Sale" Price £33.1.8). Send £4.3.8 today.

## FANTASTIC BARGAIN OFFER!

**"TRANSCONTINENTAL" FULLY TRANSISTORISED STEREPHONIC RADIOGRAM CHASSIS**  
Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price ONLY  
10 Watts Total output **£36.10.0** P & P 17/6  
17 Transistors & 10 diodes  
EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY  
Credit Terms available. First monthly payment £4.2.2 followed by 9 monthly payments of £4.2.2. (Total "Credit Sale" Price £41.1.8). Send £4.19.8 today.




Callers Welcome
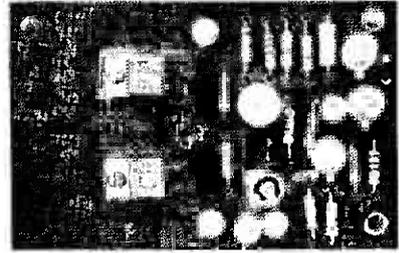
## newbury SOUND EQUIPMENT

20 Watts RMS for 86/- + 2/6 P.P. FREE ON TWO MODULES

THE 6T9 POWER AMPLIFIER WITH INTEGRAL PRE-AMPLIFIER USES THE LATEST R.C.A. PLASTIC OUTPUT TRANSISTORS—ENABLING OUTPUTS OF 20 WATTS MUSIC TO BE OBTAINED FROM A 3 1/2" x 2 1/4" (9.5cm x 6.6cm) CIRCUIT BOARD—RECOMMENDED FOR ECONOMY HI-FI, P.A. APPLICATION OR GUITAR AMPLIFIERS.



- 10-30,000 Hz @ 10 Watts ± 1dB
- Distortion 0.25% typical at 15 Watts.
- Power Gain 80dB.
- 35 Volt operation.
- Load Impedances 3-15 ohms.
- Six Transistor, two Diodes.
- Top quality components throughout.

**POWER AMPLIFIER 3T1 19/6**  
500mW for 40mV input 35-45,000 Hz  
**ORGAN MODULE 3T1 17/6**  
Will act as Oscillator or Divider up to 6000 Hz  
**MULTI-PURPOSE PRE-AMPLIFIER 19/6**  
9-24V gain variable to 40 dB  
**DUAL VOLTAGE PRE-AMPLIFIER 17/6**  
9-24V, 200-500V 25 dB gain.  
**TACHOMETER MODULE (any car at all) 18/6**

POST & PACKAGE 1/-

ALL THESE MODULES ARE ENCAPSULATED AND WILL MOUNT ON VERBOBOARD

**ALL NEWBURY MODULES ARE DESIGNED TO BE INTERCONNECTED WITH EASE**  
NEWBURY SOUND EQUIPMENT, 21 LANCASTER CT. LANCASTER AVENUE, S.E.27

We welcome your application problems, but please send an S.A.E. with your enquiry.

**POST THIS COUPON NOW!**

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name: \_\_\_\_\_  
Address: \_\_\_\_\_

**LEWIS radio** 100 CHASE SIDE, SOUTHGATE, DEP. P870 LONDON, N.14. TELEPHONE 886 3733/8666

# LST

## ELECTRONIC COMPONENTS LTD.

### BETTER QUALITY, SERVICE, PRICES & LARGEST STOCKS

A1617/3	40/-	AM006	10/-	BD119	15/-	BSY95	3.2	NKT163	6/-	NKT351	10/-	OC70	2/6	04320	7.3	2N2148	12/6	3N140	15/3
AA30	1/7	AS26	4/5	BD121	18/-	BSY95A	2/11	NKT164	6/-	NKT352	17/6	OC71	3/-	04323	6/6	2N2160	14/9	3N141	14/6
AA313	3/2	AS27	6/1	BD123	21/6	BSW41	8/6	NKT165	6/-	NKT361	20/-	OC72	4/6	04324	6/3	2N2218	6/3	3N142	10/9
AC107	7/7	AS28	4/5	BD124	12/-	BSW70	5/6	NKT201	6/-	NKT362	20/-	OC74	8/-	04326	4/3	2N2368	3/4	3N143	13/3
AC126	5/-	AS29	6/-	BOY29	20/8	BY127	4/-	NKT202	6/-	NKT401	14/8	OC75	4/6	04329	4/7	2N2369	3/4	3N152	17/3
AC127	4/-	AS21	7/6	BF115	3/-	CI106F	5/-	NKT203	6/-	NKT402	15/-	OC76	5/6	04344	5/3	2N2370	3/11	AA119	2/-
AC128	9/6	AUY10	30/-	BF152	13/8	C111	18/-	NKT205	6/-	NKT403	14/9	OC77	5/6	04347	5/6	2N2371	15/-	BA110	6/-
AC128	4/-	B181	10/-	BF154	10/-	C111E	12/-	NKT206	6/-	NKT404	13/-	OC81	4/6	04348	4/3	2N2348	10/-	BA110	6/-
AC176	5/-	B2M	12/6	BF159	15/-	CR1-051C	8/-	NKT208	6/-	NKT405	11/-	OC81D	3/-	04360	6/6	2N2712	6/-	BA111	18/-
AC181	12/-	B3M	15/-	BF163	9/-	CR1-401C	10/-	NKT210	4/2	NKT406	9/11	OC82	5/-	04361	9/6	2N2713	5/6	BA112	6/-
AC188	12/-	B108	2/6	BF167	5/-	D13T1	10/-	NKT211	3/9	NKT420	28/11	OC82D	3/-	04362	11/6	2N2904A	9/9	BA115	1/6
ACY17	5/3	BA111	6/-	BF173	6/-	FST13-BAF	4/-	NKT212	3/9	NKT441	9/11	OC83	4/6	04370	6/-	2N2955A	15/1	BA130	3/-
ACY18	4/-	BAX13	1/6	BF178	10/6	MJ480	20/6	NKT213	4/7	NKT454	9/6	OC84	5/6	04372	6/3	2N2922	4/-	BYX10	3/-
ACY19	4/-	BC107	2/9	BF179	12/6	MJ481	27/-	NKT214	3/5	NKT453	6/8	OC123	7/-	04408	10/3	2N2925	6/-	BYX36,150	2/6
ACY20	3/10	BC108	2/9	BF180	22/6	MJ490	22/6	NKT215	3/7	NKT603F	4/8	OC139	5/-	04462	11/3	Green	2/-	BYX36,300	2/10
ACY21	3/10	BC109	2/9	BF181	6/6	MJ491	29/6	NKT216	7/6	NKT613F	5/2	OC140	7/-	04467	18/6	2N2926	18/6	BYX35,600	3/9
ACY22	3/9	BC113	5/-	BF184	7/-	MPF102	9/6	NKT217	9/-	NKT654F	4/2	OC170	5/-	04602	7/-	Yellow	2/-	BYZ10	9/-
ACY27	3/6	BC116	8/-	BF185	8/-	MPF103	7/8	NKT218	6/-	NKT673	6/8	OC171	6/-	04602	2/2	Orange	2/-	BYZ12	6/-
ACY28	3/8	BC118	5/-	BF194	3/6	MPF104	7/8	NKT219	4/7	NKT676	5/-	OC200	8/3	04602	3/9	Orange	2/-	BYZ13	5/-
ACY29	7/8	BC125	11/-	BF200	10/6	MPF105	8/-	NKT221	7/-	NKT677F	3/10	OC201	9/6	04633A	5/-	2N2923	6/-	EA403	3/6
ACY30	7/6	BC126	11/-	BF274	7/6	NKT11	5/6	NKT222	6/-	NKT703	8/-	OC202	18/-	046371	3/-	Brown	2/-	EC401	5/-
ACY31	4/7	BC134	5/-	BFX13	5/-	NKT12	5/6	NKT223	5/-	NKT713	3/10	OC203	7/6	04667B	3/-	3N3053	4/5	EC402	4/6
ACY34	3/9	BC135	6/-	BFX29	6/2	NKT32	6/-	NKT224	3/7	NKT717	3/10	OC204	8/-	04674	5/-	2N3054	12/6	EB383	3/8
ACY35	3/8	BC136	8/-	BFX34	8/-	NKT42	6/-	NKT225	3/6	NKT734	4/11	OC205	9/-	04682	5/-	2N3055	15/-	OA5	3/8
ACY36	3/9	BC137	8/6	BFX44	8/-	NKT43	6/-	NKT226	11/-	NKT735	6/2	OC206	10/6	04682A	2/6	2N3235	28/6	OA10	6/-
ACY39	12/-	BC138	12/-	BFX84	5/2	NKT72	3/9	NKT227	6/8	NKT773	3/7	DC207	7/6	2N388A	15/-	2N3331A	1/6	OA17	1/8
ACY40	3/-	BC140	13/3	BFX85	6/9	NKT73	3/7	NKT228	6/8	NKT774	8/-	OCPT1	19/6	2N404	4/6	2N3392	5/-	OA70	1/8
ACY41	3/-	BC147	2/9	BFX86	4/11	NKT101	6/-	NKT229	3/11	NKT0013	8/8	ORP12	9/6	2N696	3/7	2N3393	3/-	OA73	1/8
ACY44	9/-	BC148	3/3	BFX87	5/11	NKT102	6/-	NKT231	5/11	NKT0419	3/10	ORP60	8/-	2N697	3/10	2N3525	21/6	OA79	1/8
AD140	11/-	BC149	8/-	BFY88	5/3	NKT103	6/-	NKT232	6/-	NKT0519	4/5	ORP61	8/-	2N698	6/-	2N3702	2/6	OA81	1/8
AD149	11/6	BC154	12/-	BFY18	15/-	NKT104	6/-	NKT233	5/9	NKT0539	4/7	ORP63	8/-	2N706	2/4	2N3703	3/5	OA85	1/8
AD161	6/-	BC167	3/6	BFY50	4/6	NKT105	6/-	NKT238	4/-	NKT0439	5/5	P346A	3/9	2N706A	2/6	2N3704	3/2	OA90	1/8
AD162	6/-	BC168	3/9	BFY51	3/9	NKT106	6/-	NKT239	4/-	NKT12329	8/5	RAS310AF	6/-	2N708	3/3	2N3705	2/3	OA91	1/8
ADT140	12/6	BC169	3/9	BFY52	4/6	NKT107	6/-	NKT240	3/10	NKT12429	10/8	RAS308AF	15/-	2N709	3/10	2N3706	2/3	OA95	1/8
ADZ17	32/-	BC171	2/3	BFY53	3/2	NKT108	6/-	NKT241	3/9	NKT13329	3/11	RS220F	4/-	2N711	7/6	2N3707	2/10	OA200	2/-
AF102	12/6	BC182L	2/3	BFY60	2/3	BFY60	2/3	NKT242	3/11	NKT13429	3/11	S1M	19/-	2N711A	7/6	2N3708	1/10	OA202	2/-
AF106	7/8	BC183L	1/10	BFW57	8/-	NKT109	10/6	NKT243	18/-	NKT16229	2/5	S4M	33/6	2N743	4/8	2N3709	2/-	OA211	8/-
AF114	5/-	BC184L	3/4	BFW58	5/6	NKT122	10/-	NKT244	3/11	NKT20326	6/8	ST140	3/-	2N744	6/-	2N3710	2/6	OA224	18/-
AF115	5/-	BC212L	3/4	BFW59	5/-	NKT123	9/6	NKT245	3/11	NKT20339	6/4	ST141	5/-	2N911	10/-	2N3711	2/6	OA227	10/-
AF116	5/-	BCY10	10/-	BFW60	4/6	NKT124	6/6	NKT262	4/3	NKT35219	15/9	ST2	9/9	2N914	3/11	2N3819	7/-	SD19	7d
AF117	5/-	BCY12	12/-	BLY47	3/13	NKT125	4/5	NKT263	4/8	OC19	19/-	T107	9/9	2N918	8/5	2N3820	18/9	TD716	12/-
AF118	8/10	BCY30	5/-	BS05	10/-	NKT126	4/6	NKT264	4/3	OC20	19/6	T104	19/9	2N929	5/3	2N3826	6/-	IN34A	4/-
AF121	8/-	BCY31	5/6	BSX19	10/6	NKT127	10/6	NKT265	5/6	OC22	8/-	TIP3A	12/6	2N930	6/-	2N3866	25/-	IN60	4/-
AF124	4/2	BCY32	10/6	BSX20	3/3	NKT128	10/6	NKT270	6/-	OC23	8/-	TIP32A	14/10	2N931	6/11	2N4031	15/6	IN64	4/-
AF125	4/2	BCY33	4/-	BSX21	7/6	NKT129	8/6	NKT271	2/10	OC24	6/-	V205	20/-	2N1132	7/9	2N4058	3/4	IN82A	9/6
AF126	3/6	BCY34	5/-	BSX60	12/7	NKT135	8/1	NKT272	2/10	OC25	7/6	V405A	9/3	2N1302	3/7	2N4051	1/-	IN87A	4/6
AF127	3/8	BCY38	6/-	BSX61	7/1	NKT137	8/1	NKT273	3/8	OC26	6/6	40250	10/9	2N1303	3/7	2N4052	4/6	IN91A	5/-
AF178	9/6	BCY40	10/-	BSX76	4/-	NKT143	10/6	NKT274	2/10	OC28	12/-	40309	8/-	2N1306	4/11	2N4287	3/-	IN91A	1/8
AF179	11/6	BCY42	4/-	BSX77	4/-	NKT142	10/6	NKT275	3/4	OC29	15/-	40310	8/-	2N1305	4/11	2N4288	3/-	IN4148	1/9
AF180	12/6	BCY43	4/-	BSX78	6/6	NKT143	9/6	NKT276	3/6	OC31	9/-	40311	6/-	2N1306	4/11	2N4289	3/-	IS44	1/9
AF181	8/6	BCY54	7/6	BSY27	4/-	NKT144	8/-	NKT79A	2/6	OC36	12/6	40312	9/6	2N1307	6/-	2N4290	3/-	IS103	4/3
AF186W	9/-	BCY70	3/10	BSY29	5/-	NKT151	6/-	NKT281	3/-	OC41	4/6	40314	7/3	2N1308	6/-	2N4291	3/-	IS113	4/6
AF186G	9/-	BCY71	7/8	BSY32	5/-	NKT153	6/-	NKT301	18/-	OC42	4/6	40315	7/3	2N1309	6/3	2N4292	3/-	IS130	2/6
AF238	7/6	BCY72	3/2	BSY36	5/-	NKT154	6/-	NKT302	12/5	OC43	4/6	40316	9/3	2N1613	4/5	2N4871	6/9	IS131	2/6
AFY19	22/6	BCZ17	8/8	BSY37	5/-	NKT161	6/-	NKT303	17/6	OC44	3/-	40317	7/3	2N1711	5/1	2S104	12/6	IS132	3/-
AFZ11	8/-	BCZ11	7/6	BSY38	4/-	NKT162	6/-	NKT304	8/10	OC45	3/-	40319	18/9	2N247	16/3	IN128	13/9	IS20R	1/1

**BC107/8/9 2/9**  
NPN Planar transistors  
BC107  
4/9 25+2/5 100+2/2  
BC105 25+2/3 100+2/2

**2N3819 7/-**  
Texas FET  
25+ 6/- 100+ 5/3

**SILICON RECTIFIERS**  
1 Amp Miniature Moulded Junction Rectifiers.

P.V.	1-24	25-99	100+
1N4001	50	1/6	1/5
1N4002	100	2/-	1/10
1N4003	200	2/6	2/4
1N4004	400	2/9	2/6
1N4005	600	3/-	2/11
1N4006	800	3/6	3/3
1N4007	1000	3/9	3/4

**NEWS NEWS NEWS NEWS**  
L.S.T. Electronic Components Limited are proud to announce their official appointment by Newmarket Transistors Ltd.-All Newmarket products now available at Industrial User prices. All R.C.A. Semiconductors and integrated circuits now also available from L.S.T. at reduced prices. Many Mullard General Electric and other types also in stock at Industrial User prices and better. And what's more our Retail catalogue is free to all. Ixora Transistors, Mullard Capacitors, Veroboard, Resistor coils and other misc. components at low prices. In large quantities. Official International Rectifier Semiconductor Centre stockists.

**2N4071 4/9**  
Mullard and General Electric  
25+ 9/- 100+ 6/-

**ADI161/2 10/-**  
Siemens/Telefunken  
NPN PNP output pair  
25+ 9/- 100+ 6/-

**DISCOUNT** - Quantities of different 1N4000 series may be combined to qualify for the quantity discount prices quoted. Example: 10x1N4001 1/8, 10x1N4002 1/10, 5x1N4007 4/9 (25 total pieces).  
In the event of any 1N4000 series going temporarily out of stock we reserve the right to send higher voltage types at no extra charge. 1000+ & over prices on application.

**INTEGRATED CIRCUITS**  
Some R.C.A. Linear types

CA3005	23/6	CA3022	25/-	CA3041	21/9
CA3011	14/9	CA3023	25/3	CA3042	21/9
CA3012	17/9	CA3026	20/-	CA3043	27/6
CA3013	21/9	CA3028A	14/9	CA3044	24/-
CA3014	24/9	CA3028B	21/-	CA3045	24/6
CA3018	18/9	CA3035	24/6	CA3046	15/2
CA3020	25/3	CA3036	14/6	CA3048	40/9
CA3021	31/3	CA3038	16/9	CA3051	26/9

**2N3055 15/-**  
1N5 watt silicon power transistor  
25+ 13/- 100+ 11/-

**OC71 19/4**  
Mullard and General Electric  
25+ 18/- 100+ 14/-

Application notes for CA series 2 6d. per copy.  
IC10 Sinclair Audio Amp 59¢  
PA230 GE IC 1 Watt Amp 20/-  
PA237 GE IC 2 Watt Amp 32/6  
PA246 GE IC 5 Watt Amp 52/6  
PA424 GE IC Zero Voltage  
TAA263 Mullard Linear 15/-  
TAA293 Mullard Gen. Purp. 20/-  
TAA310 Record/Playback Amp 30/-  
TAA320 MOS LF Amplifier 13/-  
TAD100 Mullard IC receiver 45/-  
3N84 GE Silicon controlled switch 26/-  
SL403A Plessey 3 Watt Amp 42/8  
SL702C Plessey Linear 25/8  
Data sheets 1/- (SL403A 2/6d. IC10 data not sold separately)  
**FAIRCHILD MICRO-LDGC**

uL900	9/9	9/-	8/-
uL914	9/9	9/-	8/-
uL923	12/6	11/9	11/-

Data and circuits (5 pages) 2/6. DIL. adapters/spreaders 1/

### BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000 Hz; Square 18-50,000 Hz  
Output max. 10 dB (10 K ohms)



Operation internal batteries  
Attractive 2-tone case 7 1/2" x 5" x 2"  
Price \$17.10.0. Carr. 3/8.

### CLASS D WAVEMETERS

A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. \$5.19.0. Carr. 7/8. Or brand new with accessories. \$7.19.0. Carr. 7/8.

**CLASS D WAVEMETERS No. 2**  
Crystal controlled. 1.2-19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. \$12.10.0. Carr. 30/-.

### R209 MK II COMMUNICATION RECEIVER

11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/PM operation. Incorporates precision vernier driver, B.F.O. aerial trimmer, internal speaker and 12V. D.C. internal power supply. Fully tested and checked. \$15.0.0. Carr. 20/-.



### TYPE 13A DOUBLE BEAM OSCILLOSCOPES

An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 2.5 Mc/s. Sensitivity 33mV/CM. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. \$22.10.0. Carriage 30/-.



### MARCONI T/44/TP956

AE Absorption  
Wattmeter  
1 μwatt to 6 watts.  
\$20. Carr. 10/-.



### SOLARTRON CD 711S2 Double Beam Oscilloscopes

D.C. to 9 Mc/s. Perfect order \$55. Carr. 50/-


### TO-3 PORTABLE OSCILLOSCOPE

3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω 250P. X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5 cps-800KHz. Input Imp. 2 meg Ω 200P. Time base. 5 ranges 10 cps-300 KHz. Synchronisation. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 10 1/2 lb. \$20/240V. A.C. Supplied brand new with handbook. \$37.10.0. Carr. 10/-.


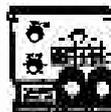
### TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-111 meg Ω 6 Ranges ±1% L1 μH - 111 HENRYS 6 Ranges -2% to C. 10pF - 1110pF 6 Ranges ±1% TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2" x 5" x 2in. \$20. P. & P. 3/-.




### UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kcs-30 Mc/s. Incorporates B.F.O. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6. **13 gns.**


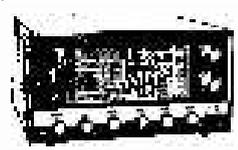
### TRIO TR-310 New Amateur Band 10-80 Metre Receiver in stock. \$77.10.0.



**LAFAYETTE SOLID STATE HA600 RECEIVER**  
5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 160 Kcs-400 Kcs and 550 Kcs-30 Mc/s FET front end • 2 mechanical filters • Huge dial • Product detector • Variable BFO • Noise limiter • 8 meter • 24in Bandspread • 230V. A.C./12V. D.C. neg. earth operation • RF gain control. Size 15in. x 9 1/2in. x 8 1/2in. Weight 1 1/2 lbs. EXCEPTIONAL VALUE. \$45. Carr. 10/- S.A.E. for full details.

### LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER

Six bands 3-5-4, 7-7.3, 14-14.36, 21-21.45, 28-29.7, 50-54 Mc/s. Dual conversion on all bands. 2 x 456 Kcs mechanical filters. FET front end, product detector, variable BFO, 100Kc/s crystal calibrator. '8' Meter. Huge slide rule dial. Operation 230V. A.C. or 12V. D.C. Size 15 x 9 1/2 x 8 1/2in. Complete with instruction manual. \$57.10.0 Carr. Paid. 100Kc/s crystal 39/6 extra.

### VARIABLE TRANSFORMERS

Input 230V. A.C. 50/60 cs.  
Output variable 0-260V.

BENCH MOUNTING	
1 amp	\$5.10.0.
2 1/2 amp	\$8.15.0.
5 amp	\$9.15.0.
PANEL MOUNTING	
1 amp	\$5.10.0.
2 1/2 amp	\$8.12.0.

### B.C. 221 FREQUENCY METERS

latest release  
125 KHz-20 MHz  
Excellent condition  
Fully tested and checked and complete with calibrator chart.  
\$27.10.0 each. Carr. 10/-



### TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kcs to 30 Mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW • AM • Variable BFO • 8 meter • Sep. bandspread dial • IF 455 Kcs • Audio output 1.5 W. • Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size 7 x 18 x 16in. With instruction manual and service data. \$42. carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES.** Normally \$5.19.6. **OUR PRICE \$3.15.0** if purchased with above receiver.

### TRIO JR. 500SE 10-80 Metre Receiver £69.10.0



### TRIO TS 510 AMATEUR TRANS- CEIVER with speaker and mains P.S.U. \$212. IN STOCK!

**RCA COMMUNICATIONS  
RECEIVERS AR88D**  
Latest release by ministry BRAND NEW in original cases. 110-250V. A.C. operation. Frequency in 6 Bands. 535 Kcs-32 Mc/s continuous. Output impedance 2-5-600 ohms. Incorporating crystal filter. noise limiter, variable BFO, variable selectivity, etc. Price \$25.0.0. Carr. \$2.

### LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 102-174 Mc/s. Fully tunable or crystal controlled (not supplied for fixed frequency operation). Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. \$37.10.0. Carr. 10/-.



### TELETON CR-10T AM/FM STEREO TUNER AMPLIFIER



A new model from Teleton. 31 solid state devices. 4 + 4 watt output. Input for ceramic/crystal cartridge. Frequency range AM 540-1600KHz FM 88-108MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFC switch. Stereo headphone socket. Size 13 1/2" x 8 1/2" x 9 1/2" approx. PRICE \$34.0.0. Carr. 7/6.

### CLEAR PLASTIC PANEL METERS


First grade quality Moving Coil Panel meters. Type MR 38P. 1 1/2in. square fronts.

500-0-500μA	27/6	50mA	27/6	150V. D.C.	27/6
1mA	27/6	100mA	27/6	300V. D.C.	27/6
1.0-1mA	27/6	150mA	27/6	500V. D.C.	27/6
2mA	27/6	200mA	27/6	750V. D.C.	27/6
5mA	27/6	300mA	27/6	15V. A.C.	27/6
10mA	27/6	500mA	27/6	50V. A.C.	27/6
750mA	27/6	3V. D.C.	27/6	150V. A.C.	27/6
1 amp	27/6	10V. D.C.	27/6	300V. A.C.	27/6
2 amp	27/6	15V. D.C.	27/6	500V. A.C.	27/6
5 amp	27/6	20V. D.C.	27/6	8 meter 1mA	32/-
200μA	35/-	100V. D.C.	27/6	VU meter	42/-
500μA	40/-				

FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET

**Variable Voltage TRANSFORMERS**  
Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 50-60 cycles. Output full variable from 0-260 volts. Bulk quantities available.  
1 amp - \$5.10.0; 2.5 amp - \$6.15.0; 5 amp - \$9.15.0;  
8 amp - \$14.10.0; 10 amp - \$18.10.0; 12 amp - \$21.0.0;  
20 amp - \$27.0.0.

### CRYSTAL CALIBRATORS NO. 10

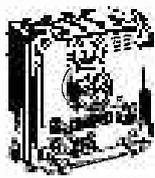

Small portable crystal controlled wavemeter. Size 7 x 7 1/2 x 4 1/2in. Frequency range 500 Kcs-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V. D.C. 0.3A.

### TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: -01/-003/1/3/1/3/10/30/100/300V. R.N.S. 4cps-1.2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. \$17.10.0 Carr. 5/-.



### LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/230V. A.C. Supplied in perfect order. \$12.10.0 Carr. 10/-.


### TE-65 VALVE VOLTMETER

High quality instrument with 25 ranges. D.C. volts 1-10-1500V. A.C. volts 1.5-1500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with Probe and instructions. \$17.10.0. P. & P. 6/- Additional probes available: R.F. 42/8. H.V. 50/-


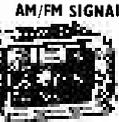
### COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.C. coupled. Band width 1Kc/s. Perfect order. \$25. Carr. 30/-.



### AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airtec. Frequency coverage 20-80 Mc/s. AM CW/PM. Incorporates Precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. \$45. Carr. 20/-.

### EDDYSTONE VHF RECEIVERS Model 770R. 10-165 Mc/s. Excellent condition. \$150.

### RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

6 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 2 sec to 100 μs/sec/cm. Supplied complete with all accessories and instructions \$37. Carr. paid



**TE-16A Transistorised  
Signal Generator.** 6 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 1/2 x 3 1/2 x 3 1/2in. Complete with instructions and leads. \$7.19.5. P. & P. 4/-.

### HOSIDEN DH-08S DE-LUXE STEREO HEADPHONES

Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead and stereo jack plug \$7.19.5. P. & P. 2/6.



### AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.  
150 W. \$2. 2.6. P. & P. 3/6.  
300 W. \$3. 5.0. P. & P. 4/6.  
500 W. \$4. 10.0. P. & P. 6/6.  
1,000 W. \$7. 10.0. P. & P. 7/6.  
1,500 W. \$11.9.0. P. & P. 8/6.  
7,500 W. \$15.10.0. P. & P. 20/-.

**G. W. SMITH  
& CO (RADIO) LTD**  
Also see oppo. page

**ARF-100 COMBINED AF-RD SIGNAL GENERATOR**



**A.F. SINE WAVE**  
20 - 200,000 c/s.  
Square wave 20 - 30,000 c/s. O.P.P.  
HIGH IMP. 21V.  
P/1000 Ω 2.5V. P/P  
T/100 Kc/s-300  
Mc/s. Variable R.F.  
Mod. Variable R.F.  
attenuation lit/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod on R.F. 220/240V. A.C. £32.10.0. Carr. 7/6.

**TE-20 RF SIGNAL GENERATOR**

Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable J.F. attenuator. Operation 200/240V. Brand new with instruction. £15.0.0. P. & P. 7/6. S.A.S. for details.



**PEAK-SOUND PRODUCTS.** Full range of Amplifiers, Kits, Speakers, in stock.

**TE22 SINE SQUARE WAVE AUDIO GENERATORS**

Size: 20c/s to 200 kc/s on 4 bands. Square: 20c/s to 50 kc/s. Output impedance 1,000 ohms. 200/240V. A.C. Supplied brand new and guaranteed with instruction manual and leads. £12.10.0. Carr. 7/6.



**MARCONI TP149E DISTORTION FACTOR METERS.** Excellent condition. Fully tested. £20. Carr. 15/6.

**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER**

2 pF-2000 mFD 2 ohms 200 meg-ohms. Also checks impedance, turns ratio, insulation. 200/230V. A.C. Brand New £17.10.0. Carr. 7/6.



**TO-2 PORTABLE OSCILLOSCOPE**

A general purpose low cost accuracy oscilloscope for everyday use. Y axis Bandwidth 2 CPS-1 MHz. Input Imp. 2 meg Ω 20 P.F. Illuminated scale. 2in. tube. 110 x 150 x 230mm. Weight 5lb. 220/240 V. a.c. Supplied brand new with handbook. £22.10.0. Carr. 10/6.



**ADVANCE TEST EQUIPMENT**

Brand new and boxed in original sealed cartons  
**J1B. AUDIO SIGNAL GENERATOR.** 15 c/s to 50 Kc/s. Sin. wave. Output 600 ohms or 5 ohms £20.0.0.  
**VK79. UHY MILLIVOLT METER.** 100 Kc/s to 1,000 Mc/s. A.C. 10µV to 3v. D.C. 10 mV to 3v. Current 0.01 mA to 0.3 mA. Resistance 1 ohm to 10 megohms. £125.0.0.  
**TT15. TRANSISTOR TESTER.** Full range of facilities for testing PNP or NPN transistors in or out of circuit. £27.10.0. Carrriage 10/- per item.

**HOSIDEN DHOAS 2-WAY STEREO HEADSETS**




Each headphone contains a 2 1/2in. woofer and a 1/2in. tweeter. Built in individual level controls. 8 Ω Imp. 25-15,000Ω/s with cable and stereo plug. £5.10.0. P. & P. 2/6.

**BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR**



New high quality portable instrument. Size 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price £27.10.0. Carr. 6/-

**Latest Catalogue**

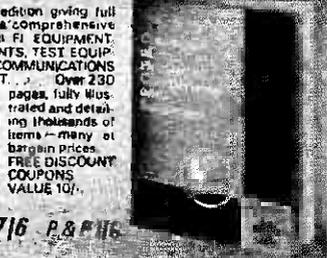

SEND NOW—ONLY 7/6 P&H

**GARRARD**

FULL CURRENT RANGE OFFERED BRAND NEW AT FANTASTIC SAVINGS

1065 stereo	£719.6	SL75B	£25.00
40 Mk II stereo	£83.0	AP75	£13.00
3022/7C stereo	£8.17.8	SL75	£25.10.0
3000 stereo	£8.10.8	SL75B	£25.00
SP25 Mk II	£11.9.8	SL05B	£25.00
SL55	£11.12.6	A70/11	£11.19.8
SL65II	£14.19.8	401	£25.00

Carriage 7/6 extra each item.  
**TEAK PLINTHS & PERSPEX COVERS**  
1. For SP25, SL65, SL55, 3000, 3025 T/C 2035, 1000. £4.10.0  
2. For AP75, SL75, SL05 £5.10.0  
3. For SP25 etc. to operate with lid in place £5.10.0.  
Carriage 7/6 extra each type. Full range of Garrard accessories available.



**SPECIAL OFFERS:**

Garrard SP25 fitted Goldring 8800 cartridge and wooden plinth. Total list price £22.8.6.

**OLK PRICE £19.15.0 Carr. 10/-**

**GOLDRING 8800 fitted Goldring 8800 cartridge complete with deluxe base and cover.**  
Total list price £20.10.0.

**OLK Carr. £39 Carr. 10/-**

**RTCE9 4-TRACK TAPE DECK**

British Made Speeds 1 1/2", 3 1/2", 7 1/2" P.B. Marriot Heads. 7" reel size. Push Button controls, fully automatic. Size 13" x 10" x 1 1/2" above unit plate. 4 1/2" below. Full instructions. £13.19.8 Carr. 7/6



**MULTIMETERS for EVERY purpose!**

**TE-51. NEW 20,000 Ω/VOLT MULTIMETER** with overload protection, and mirror scale. 0/850/120/1,200V. A.C. 0/300/60/300/600/1,200V. D.C. 0/50/10/12/300mA. D.C. 0/50K/16 meg. ohm. 0/25. P. & P. 2/6

**MODEL AS-100D. 100K Ω/VOLT.** Sin. mirror scale. Built-in meter protection. 0/8/12/60/20/300/600/1,200V D.C. 0/8/30/120/300/600V. A.C. 0/10/10/60/80/300 mA/10 meg Ω. 0/25/200K Ω. -20 to +17dB. £12.10.0. P. & P. 3/6.

**MODEL TE-90 50,000 Ω/V** mirror scale overload protection 0/3/12/60/300/600/1200V. D.C. 0/6/30/120/300/1200V. D.C. 0/6/30/60/300 mA. D.C. 15K/100K/1.6/16meg Ω. -20 to +68dB. £7.10.0. P. & P. 3/6.

**MODEL TE-70. 30,000 Ω/V.** 0/3/12/60/300/600/1200V D.C. 0/6/30/120/600/1200V A.C. 0/30/10/30/300mA. 0/15K/160K/1.6/16 Meg Ω. £5.10.0. P. & P. 3/6.

**MODEL FT-34. 1,000 Ω/V.** 0/10/50/120/300/600/1,000V AC and D.C. 0/10/100/600mA D.C. 0/100K Ω. 30/6. P. & P. 1/6.

**TE-800 20,000 Ω/VOLT GIANT MULTIMETER** mirror scale and overload protection. 6in full view meter. 2 colour scale. 0/2.5/10/120/1,000/5,000V. A.C. 0/25/12.5/10/30/250/1,000/5,000V. D.C. 0/50/50/110/100/500mA/10 amp. D.C. 0.2K/200K/10 MEG. OHM. £15. P. & P. 3/6.

**LAFAYETTE 57 Range Super 50K Ω/Volt Multi-meter** D.C. volts 12 mV - 1000V. A.C. volts 1.5V - 1000V. D.C. current 25µA - 10 amp. Ohms 0 - 10 meg Ω dB - 20 to +81 dB. Overload protection £12.10.0. Carr. 3/6.

**MODEL TE-300. 30,000 Ω/V.** Mirror scale, overload protection. 0/3/12/60/300/1,200V d.c. 0/6/30/120/300/1,200V A.C. 0/30/10/30/300mA/160K/160K/800K/8 meg. -20 to +68 dB. £5.19.8. P. & P. 3/6.

**MODEL TE-12. 20,000 Ω/V.** 0/0.6/6/30/120/600/1,200/3,000/6,000V. D.C. 0/8/20/120/600/1,200V. A.C. 0/10/10/60/300mA/160K/160K/800K/8 meg. 100 Meg Ω 50P/0.3mFD. £5.19.8. P. & P. 3/6.

**SAVE UP TO 33% OF HI-FI EQUIPMENT**  
Send for discount price list

**AVO CT471A MULTIMETER**

Battery operated, fully transistorised Sensitivity 100µΩ/V. Measures A.C./D.C. Voltages 12mV to 1,200V. A.C./D.C. Current 12uA to 1.2 Amp. Resistance 12 ohm to 120 mΩ. 11F, 11HF, 11HF Voltages with multiplier 4v to 400v up to 50 Mc/s. 40mV to 4v up to 1,000 Mc/s. Offered in perfect condition. £55 each. Carr. 10/-

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**

Operative over amazingly long distances. Separate call and cross to talk buttons. 3-wire connection. 100% of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £8.19.8. P. & P. 3/6.



**SINCLAIR EQUIPMENT**

Project 60. Package offers:  
2 x 230 amplifier, stereo 60 pre-amp. P25 power supply. £19.0.0. Carr. 7/6. Or with P26 power supply £21. Carr. 7/6.  
1 x 230 amplifier, stereo 60 pre-amp. P26 power supply. £21.10.0. Carr. 7/6.  
Transformer 4 1/2 230V extra. Add to any of the above £4.17.5 for active filter unit and £6 for a pair of Q16 speakers. All other Sinclair Products in stock. 2,000 amplifier £28. Carr. 7/6. Neoteric amplifier £48. Carr. 7/6.

**SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS**

Compact and pin mounting. Ideal for control of amps, drills, electrical appliances etc. Input 250/240V. A.C. Output continuously variable from 30V-230V. Model MR 2305 5 amp 14 x 45 x 43mm £27.6 Model MR 2310 10 amp 95 x 45 x 60mm £11.19.8 Postage 2/6

**TE111. DECADE RESISTANCE ATTENUATOR**  
Variable range 0-114dB Connections: Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB), accuracy: 0.3dB. + indication dB x 0.1 Max input power less than 1W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 6/-

**RECORDING HEADS**  
COSMOCORD 1-track head. High imp. record/playback 65-. Low imp. erase 20/-  
MARRIOTT 1-track heads. High imp. record/playback 85-. Low imp. erase 20/- Post extra.

**AMERICAN TAPE**

First grade quality American tapes. Brand new. Discount on quantities.  
3in. 225ft. L.P. acetate ..... 3/6  
3 1/2in. 600ft. T.P. mylar ..... 10/-  
5in. 900ft. 1/4" acetate ..... 15/6  
5in. 900ft. L.P. acetate ..... 15/-  
5in. 1,200ft. D.P. mylar ..... 18/-  
5in. 1,200ft. L.P. acetate ..... 12/6  
5in. 1,200ft. L.P. mylar ..... 18/-  
5in. 1,800ft. D.P. mylar ..... 22/6  
5in. 2,400ft. T.P. mylar ..... 28/6  
7in. 1,200ft. 1/4" acetate ..... 15/6  
7in. 1,600ft. L.P. acetate ..... 18/-  
7in. 1,800ft. L.P. mylar ..... 20/-  
7in. 2,400ft. D.P. mylar ..... 25/-  
7in. 3,000ft. T.P. mylar ..... 45/-  
Postage 2/- Over £3 Post paid.

**TAPE CASSETTES**

Top quality in plastic library boxes.  
C90 90 min 18. 3 for £4/8  
C90 90 min 18. 3 for 90/-  
C120 120 min 18/- 3 for 42/6  
Cassette Head Cleaner 11/8 Post Extra.

**G.W.SMITH & CO. (RADIO) LTD**  
3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to -  
147, Church Street, London, W.2  
Tel: 01-262 4562  
(Trade supplied)

# R.S.T. VALVE MAIL ORDER CO.

## BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.  
—5.30 p.m.  
Closed Sat. 1.30—2.30 p.m.  
Open Daily to Callers

Tel. 769-0199/1649

1A7	7/9	6BR8	12/6	6K7GT	4/8	10C1	20/-	25L6GT	7/-	150B2	11/6	DK92	7/8	ECH35	11/6	EY86	7/-	PCF80	6/9	PY801	9/6	UCL83	10/-
1D5	7/6	6B87	28/-	6K8	2/8	10C2	12/8	25V5	6/-	150C4	9/8	DK91	6/8	ECH42	13/-	EZ35	6/-	PCF82	6/9	R2	7/6	UF41	10/6
1E5	7/-	6B86	14/6	6K8M	11/8	10P1	14/8	26Z4	6/8	801	9/8	DK92	9/-	ECH81	5/8	EZ40	9/-	PCF84	8/-	R19	7/9	UF99	7/6
1LD5	6/-	6B87	13/-	6K8C	3/-	10P2	15/-	26Z5	6/8	813	9/8	DK92	7/8	ECH85	8/8	EZ41	9/8	PCF85	9/8	R35/500	9/8	UL41	12/6
1N6GT	8/-	6C4	5/-	6K8GT	7/-	10P9	10/8	26Z6	8/8	813USA	8/8	DL66	25/-	ECL80	7/-	EZ80	6/8	PCF801	9/8	R136	40/-	U84	7/6
1B5	6/-	6C5G	5/-	6K26	16/-	10P18	3/-	28D7	9/3	120/-	DL92	6/8	ECL82	7/-	EZ81	5/8	PCF82	9/8	SP4	8/-	UM80	6/8	
1B4	5/6	6C6	3/9	6L1	12/-	10L1	8/-	30C1	6/9	813	75/-	DL93	4/-	ECL83	10/8	EY501	15/-	PCF805	15/-	SP41	3/8	U6	21/-
1B5	4/6	6C8G	6/-	6L6G	7/8	10LD11	10/8	30C15	15/-	866A	15/-	DL94	6/8	ECL86	9/-	GZ30	10/-	PCF806	13/-	SP61	3/8	U7	21/-
1T4	4/-	6CD6G	24/-	6L18	9/-	10P13	13/8	30C17	16/-	964	5/8	DL95	7/8	ECL8080	8/8	GZ32	10/-	PCF808	15/8	SPV80/80	8/8	U8	21/-
2A4	4/-	6CH6	7/8	6Q7G	6/-	11P3	7/8	30C18	15/-	1225	6/8	DL96	7/8	ECH88	8/8	GZ34	11/-	PCL82	10/8	SP62	3/8	U9	3/8
2Q4	7/8	6CW4	13/8	6Q7GT	8/8	12AT6	4/8	30F5	17/-	4022AR	67/-	DM70	6/-	EP3A	20/-	HN309	11/-	PCL83	10/8	SU25	19/8	UY21	6/8
2Q5	7/8	6D6	3/9	68A7M	7/-	12AT7	6/-	30FL1	15/-	5763	12/-	DY86	6/-	EP39	7/-	HN309	11/-	PCL84	18/8	SU2150	12/8	UY41	8/8
2B4	6/8	6E5	7/8	68C7	7/-	12AU6	5/8	30FL12	19/-	7193	2/-	DY87	6/6	EP41	10/-	KT61	22/8	PCL85	9/8	T41	17/8	UY85	6/8
2V4	6/9	6P1	12/6	68G7	6/-	12AU7	5/8	30FL14	16/8	7475	14/-	EB80C	12/-	EP50	6/-	KT66	30/8	PCL86	9/8	TDD4	8/8	VP4G	17/-
2B4G	10/8	6P5G	8/-	68H7	2/3	12AX7	6/8	30L15	17/-	A61	3/6	EA50	3/6	EP80	4/8	KT81	35/-	PD500	28/-	U10	7/8	VP4B	25/-
2U4G	5/6	6P6G	5/-	68J7	9/-	12BAG	6/-	30L17	17/-	ATP4	3/6	EAB80	3/6	EP85	7/-	KT81 (7C5)	PEN44	20/-	U14	7/8	VR105/30	8/8	
2V4G	6/-	6P8G	5/6	68K7GT	4/9	12BEG	6/8	30P4	22/8	ATP5	12/-	EAF42	10/-	EP86	6/6	PEN45	22/8	PEN46	20/-	U19	35/-	VR150/30	8/8
2Z4G	7/-	6P13	6/8	68N7GT	5/8	12E1	20/-	30P19	15/-	ATP7	8/6	ED41	10/-	EP89	5/8	KT88	24/-	PEN46	4/-	U26	15/8	VT25	15/-
6/30L2	15/-	6P14	12/6	68Q7	2/8	12F5G	2/6	30P1L	16/-	AU5	8/8	EC83	8/8	EP92	2/6	KTZ41	6/-	PL36	10/9	U78	4/8	VU111	9/9
6A7	15/-	6P23	14/6	6U4GT	12/-	12J7GT	6/8	30P1L3	18/6	AZ1	8/-	EP84	9/8	EP98	15/-	ML4	17/8	PL81	9/8	U191	13/8	VU120	12/6
6A8G	12/6	6P24	14/-	6U5G	7/8	12K7GT	7/-	30P1L4	19/-	AZ1	10/-	EP80	4/9	EP183	6/8	ML6	7/8	PL82	8/8	U281	16/8	VU608	35/-
6AC7	4/-	6P25	15/-	6V6M	12/8	12R5GT	8/-	35A5	12/8	CB131	15/-	EPF50	7/8	EP184	7/-	MSF4	10/-	PL83	7/8	U301	12/8	XLM	18/6
6AK5	5/-	6P28	14/6	6V8G	12/8	12T7GT	8/-	35L8	9/-	CEH35	15/-	EPF83	9/8	EL32	3/6	ML14	7/8	PL84	7/-	U403	6/8	XP1-5	8/-
6AM4	4/6	6P32	2/9	6V8GT	6/8	12P47	8/-	35W4	4/6	CL33	20/-	BF89	6/8	EL33	12/6	MX40	12/6	PL500	14/6	U404	7/8	XP1-5	5/-
6AM8	6/8	6G6	3/6	6X4	4/8	12SG7	6/-	35Z3	10/-	CV450	25/-	EBL1	14/6	EL34	10/6	N78	19/-	PL604	18/6	U801	23/8	XSG1-5	110/-
6AQ5	6/8	6E6	3/-	6X5G	4/8	12SH7	3/-	36Z4GT	8/6	CY30	12/6	EBL21	12/6	EL38	22/6	NG18	25/-	PL508	28/-	UAB80	6/8	Y63	7/8
6A87G	15/-	6B3M	9/-	6X5GT	6/-	12S7	3/9	35Z5	3/9	CY31	8/6	EBL31	27/8	EL41	11/-	NGT1	3/6	PL509	28/-	UAF42	10/8	Y63	7/8
6AT6	4/9	6B3G	4/-	7B6	11/8	12SK7	4/8	37	6/8	DA32	7/8	EC90	7/8	EL42	11/8	NGT7	5/8	PL602	18/8	UB41	30/8	ZEG1	65/-
6AT6G	5/-	6B5GT	8/-	7B7	9/8	12SR7	5/-	42	6/8	DAF91	4/6	EC81	5/-	EL84	4/9	OA2	6/-	PK4	24/-	UB81	3/8	ZFP7	20/-
6B4G	20/-	616	3/8	7C5	22/6	14E7	5/6	50B6	6/8	DAF96	7/8	EC82	5/9	EL95	7/8	OC3	5/-	PK25	27/8	UBF80	7/8	ZCP1	65/-
6B8G	2/-	617M	6/8	7C6	15/-	19AQ5	5/-	50C5	6/3	DCO90	20/-	EC83	5/8	ELL80	20/-	OC4	4/8	PK33	10/9	UBF89	7/8	ZCV1528	65/-
6BA6	5/-	617G	6/-	7D5	8/-	20D1	10/-	50CD6G	31/-	DF33	8/-	EC84	5/8	EM34	16/-	PC86	11/8	PK41	5/8	UC84	3/8	ZACR131100	8/8
6B6E	5/-	617GT	7/8	7H7	6/8	20P2	14/-	50L6GT	8/-	DF70	9/-	EC85	5/-	EM80	7/8	PC88	11/8	PK82	5/8	UC85	5/8	ZCR97	45/-
6B86	9/-	6K5GT	8/-	7R7	13/-	20L1	20/-	75	9/8	DF91	4/-	EC88	7/8	EM81	12/8	PC97	8/8	PK83	7/-	UC86	6/8	ZCR97B	45/-
6B9E	9/-	6K7	1/9	7S7	45/-	20P4	20/-	78	5/-	DF92	3/8	ECF80	6/8	EM84	7/8	PC98	6/8	PK84	7/8	UC87	10/8	ZCR97C	45/-
6B9A	7/-	6K7M	6/8	7Y4	8/8	20P5	20/-	80	7/8	DF95	7/8	ECF82	6/8	ESU150	20/-	PC99	10/8	PK85	7/8	UC88	11/8	ZCR97D	45/-
6BR7	17/-	6K7G	2/-	9BW6	7/-	25A6	5/9	85A2	7/8	DH77	4/9	ECH21	12/6	EY51	7/8	PC189	10/6	PK89	8/8	UC82	7/8	ZCR97E	45/-

Manufacturers and Export Inquiries Welcome

OBSCURE TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Express postage 9d. per valve.

Ordinary postage 6d. per valve. C.W.D. No C.O.D.

Tube postage 10/- each

Special Express Mail Order Service

### VALVES & TRANSISTORS

2G414	6/0	AC128	4/6	AF113	12/-	OA10	3/-	OC36	8/6	OC77	8/-	OC122	12/6
2N1305	5/-	AC176	6/2	BC108	3/8	OA20	2/-	OC38	12/6	OC78	8/-	OC123	4/4
2N2147	15/8	ACY18	4/-	BC109	3/8	OA29	2/-	OC39	17/-	OC81	4/8	OC129	7/6
2N2369A	5/-	ACY27	5/-	BY51	6/-	QAZ242	4/6	OC70	3/8	OC81D	3/8	OC170	5/6
2N2696	6/8	ACY28	4/-	BY90	12/6	QAZ246	4/6	OC71	3/-	OC81M	5/8	OC171	6/-
2N2926	3/-	ACT39	12/6	BY100	4/8	OC16	15/0	OC72	4/-	OC82	3/8	OC172	7/8
2N3705	4/-	AD149	12/-	GET114	4/-	OC19	8/6	OC73	7/8	OC82D	3/8	OC200	5/8
2N3819	8/-	AD161	7/8	GJ7M	6/8	OC20	20/-	OC74	4/8	OC83	4/6	OC201	8/8
AC107	5/8	AD162	7/-	NKT274	4/9	OC28	12/6	OC75	4/8	OC84	4/8	OC202	8/8
AC127	6/-	AF117	4/6	NKT713	7/8	OC35	6/3	OC76	3/-	OC114	7/8	OC203	6/-

SEND S.A.E. FOR LIST OF 3,000 TYPES

## LOOK AT THESE PRICES

### CARTRIDGES

Acos GP87-2, GP91-38C 22/6; Acos GP93-1 24/8;  
Acos GP94-1 22/6; Sonotone 9TAHO 20/6; All  
above in makers cartons; Japanese Stereo 16/-

### 1 WATT AMPLIFIER

Complete with volume control, rectifier, smoothing  
cct, fully transistorised, OUR PRICE 27/6

### PLUGS & SOCKETS

Phono plugs, red, white, yellow, green, grey, blue,  
black 11d 9/- per doz; Coaxial plugs, aluminium 1/6;  
Coaxial couplers 1/-; 2 pin DIN plugs 3/-; 3 pin  
DIN plugs 3/-; 5 pin DIN plugs 3/8; 2 pin, 3 pin  
DIN sockets 1/6; wander Plugs 6d; sockets 8d;  
Banana plugs 1/6, sockets 1/-; 3.5mm J/Plugs 1/6 &  
3/8; Standard J/Plugs with solder terminals 2/-;  
Chrome 3/-; Side Entry J/Plugs black and chrome  
4/8; Insulated sockets, c/ect 3/8, o/ect 5/8.

### ELECTROLYTIC CAPACITORS

4uF, 150v 9d; 8uF 500v, 3/-; 8uF 12v 10d; 8uF +  
8uF 450v 4/3; 10uF 150v 9d; 12uF 25v 9d; 16uF  
150v 2/9d; 16uF + 16uF 450v 4/8; 20uF 10v 9d; 50uF  
40v; 100uF 9v 9d; 100uF 12v 9v; 150uF 12v 9d;  
320uF 9v 1/-; 1500uF 20v 3/8; 2000uF 30v 4/2;  
5000uF 25v 10/-; 10000uF 25v 15/-; 20000uF  
30v 21/-.

### MICROPHONES

Acos Mic 45 22/8; Acos Mic 60 18/11; Planet CM70  
30/-; Hand Mike 15/-; Shure 201 25; Shure 444  
210.10.0.


### VALVES

FY81 7/2; PCL82 7/8; EF183 9/-; EF184 9/-.

## GEORGE FRANCIS (Dept PW),

98 Balderton Gate, Newark, Notts.  
Telephone: Newark 4783.

## The Unique MULTI-MINI TWIN-VICE

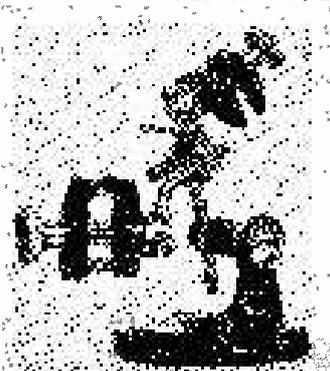

An extra "Pair of hands" for  
those tricky jobs

ASSEMBLY—SOLDERING—  
GLUING—WIRING—DRILLING  
ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5-18-0 (4/6 P & P)

ALSO AVAILABLE

SINGLE VICE: £3-7-6 (3/- P & P)

COVENTRY MOVEMENT CO LTD.  
BURNSALL ROAD, COVENTRY  
CV5 6BU STD O203-74363

## UNREPEATABLE PRICE

DESPITE RECENT INCREASES

# SAVE NEARLY 20%

LATEST NEW & IMPROVED "JULIETTE"  
NA5018A COMMUNICATIONS RECEIVER  
(with AFC and BFO)  
5 BAND MAINS/BATTERY SOLID STATE  
PORTABLE RECEIVER



LIST PRICE £44.17.0  
OUR  
PRICE 34 gns.  
(cash only) + 9/- p/p  
Limited quantity


- AM Band: 540-1600 Kc's Full Meter wave cover.
  - Marine Band: 1.6-4.6 Mc's Shipping Hams. SW, etc.
  - FM/VHF: 88-108 Mc's Radios 2, 3, 4; TV Sound, Public Services, etc.
  - Aircraft 108-134 Mc's (improved sensitivity); Airlines and Ground Control
  - PB (High VLF Band): 148-174 Mc's TV Sound, Fire, Ambulance, etc., Taxis, Shipping, Fuel Boards, Oil
- Rigs, Gas and Electric Boards, Local Hams, Industrial and Commercial Mobiles, Military aircraft etc. (DEPENDENT ON LOCALITY).
- FEATURES—4" Dynamic PM Speaker. Directional telescopic VHF aerial. Internac Ferrite rod aerial. Illuminated Dial, size 9 1/2" x 4 1/2". Weight 4 1/2 lbs. Impressive and sturdy design in Chrome and Black Leather. Ultra sensitive transistor circuit. Earpiece and Socket. Leather carrying and shoulder straps. Batteries incl. (STANDARD EVER READY TYPE).

RETAIL TRADERS SUPPLIED  
Enquiries to wholesale dept.  
STOCKTON PARTNERS (DEPT. PW)  
BRIGHLOWGATE, GRIMSBY, Lincs.  
Tel: 0472 58815/64196

Imports, Wholesale Electronic Equipment Distributors



# LIND-AIR AUDIO

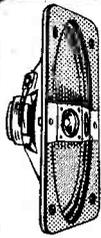

E.M.I.

## COMBINATION LOUDSPEAKERS

13 1/2" x 8" elliptical with two tweeters 8 ohm impedance; power handling 10W. Brand new guaranteed. Lind Air

Price **89/6** P. & P. 7/6.

## HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

J1001 3"	L.P. PVC 295ft.	5/6	P & P 1/2
J1002 3"	T.P. Poly 600ft.	10/6	P & P 1/2
J1003 3"	L.P. PVC 900ft.	10/-	P & P 1/8
J1004 3"	D.P. Poly 1200ft.	15/-	P & P 1/8
J1005 3 1/2"	L.P. PVC 1200ft.	12/6	P & P 2/-
J1006 3 1/2"	D.P. Poly 1800ft.	22/6	P & P 2/-
J1007 7"	S.P. PVC 1200ft.	12/6	P & P 2/6
J1008 7"	L.P. PVC 1800ft.	17/6	P & P 2/6
J1009 7"	D.P. Poly 2400ft.	25/-	P & P 2/6
J1010 7"	T.P. Poly 3800ft.	50/-	P & P 2/6
C90 Cassette (Library cased)		8/6	P & P 1/-
C90 Cassette (Library cased)		13/-	P & P 1/-
C120 Cassette (Library cased)		18/-	P & P 1/-



## DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 25-13,000 cps. With lead and stereo plug.

**59/6** P. & P. 3/6.

## VHF AIRCRAFT BAND CONVERTOR

When placed within line of a MW band radio full coverage of VHF Aircraft Band 108-135 Mc/s. can be obtained. All transistor. 9v battery operation. Fully tunable 18 1/2" x 7" section telescopic aerial. Size 4 x 2 1/2 x 1 1/2 in.



**79/6** P. & P. 3/6.

## C1001 MULTI-TESTER



Overload protection. 20,000 ohm. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-60K, 0-6 Meg ohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 x 1 in. Complete with leather case **85/-** P. & P. 3/6.

## NEW! STP.800 8-TRACK STEREO CARTRIDGE HOME PLAYER

TELETON STP. 800 8-TRACK STEREO CARTRIDGE HOME PLAYER A complete solid state unit ready to plug in and play. Hi Fi reproduction at 3 1/2 i.p.s. Player unit incorporates Volume, tone and balance controls and push button track selector. Size 14 1/2" x 10 1/2". Matched speakers size 11" x 8" x 5 1/2" each.




LIND-AIR PRICE **49 GNS.** Carr. 3/0

## 62D MULTI-TESTER

20,000 p.p.v. DC voltage 5-25-50-250-500-2.5 K (20,000 ohms per volt). AC voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5 mA, 0-250 mA. Resistance: 0-6K, 0-6 M; (300 ohm and 30K at centre scale). Capacitance: 10f. to .001 mfd. .001 uf to .1 uf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1 in. **71/-** P. & P. 3/6.



## S-DEC BREADBOARD

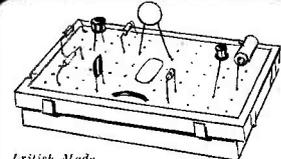

British Made Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-Dec with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-Dec" giving construction details for a variety of circuits. 29/6. P. & P. 2/6. 4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-Dec" all contained in a strong attractive plastic case. Ideal for the professional user. **£5.17.6** P. & P. 3/6. T-DeC KIT **£5.17.6** P. & P. 3/6.

## LIND-AIR LA.20




A fantastic stereo amplifier made exclusively for Lind-Air and represents considerable advance in solid state stereo amplifiers. Inputs for gram and radio tuner and provision for direct tape recording. Attractive and modern panel with bass, treble balance and volume controls also on/off and stereo/mono switch. Output 5W per channel music power. Frequency response 40-20,000Hz 8-16 ohm speaker matching. Size 16 1/2" x 14" x 4".

LIND-AIR **£24** P. & P. PRICE 10/-

## SINCLAIR IC-10 INTEGRATED CIRCUIT

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. **ONLY 59/6** P. & P. 1/6. SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v. at 0.5amp. **16/6** P. & P. 2/6.

## WHARFEDALE SPEAKER KITS

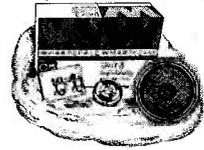

Complete with all components for building into suitable cabinets.

- Unit 3 Kit **£11.10.6** each **£21** per pair
  - Unit 4 Kit **£18.0.0** each **£28** per pair
  - Unit 5 Kit **£23.10.0** each **£36** per pair
- P. & P. 10/- each 15/- pair


## TELETON SAQ203 TRANSISTOR STEREO AMPLIFIER



Superb quality hi-fi. 10 watts per channel music power. Inputs for gram (Magnetic and Crystal), Tuner and Auxiliary, Tape Record output. Controls: Volume, Balance, Bass, Treble. Attractive oiled walnut cabinet and brushed aluminium front panel. List Price **£28.7.0**


LIND-AIR PRICE **22 Gns.** P. & P. 10/-

## SAVE ON AKAI!

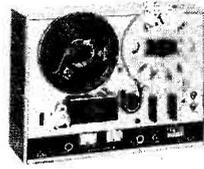

AKAI 4000 Stereo Tape Recorder List Price **£124.18.0** (as illus.) OUR PRICE **99 Gns.** Carr 30/- AKAI 4000D STEREO TAPE DECK List Price **£89.19.1** OUR PRICE **69 Gns.** Carr 30/-

## SPECIAL LIND-AIR OFFER!

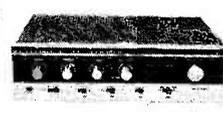

ROTEL 100 AMP STEREO AMPLIFIER. Fully transistorised with all facilities for the home hi-fi system. List price **£45**

LIND-AIR PRICE **£37.10.0.** Carr. 10/-

## Garrard HI-FI TURNTABLES



- 2025 T/C with stereo cartridge... **£8.19.6**
  - 3000 with Sonotone **£10.19.6**
  - 9TAHCD stereo cartridge... **£10.19.6**
  - SP25 Mk II... **£10.19.6**
  - SL65B... **£15.19.6**
  - Base and cover for above... **£5.19.6**
  - AP75... **£13.10.0**
  - SL72B... **£24.19.6**
  - SL75B... **£28.7.0**
  - SL95B... **£39.9.0**
  - 401... **£25.10.0**
  - Base and cover for above... **£8.19.6**
  - F. & P. Decks 12/6. Base & Cover 10/- Deck/Base/Cover 17/6.
- SPECIAL OFFERS!  
SP25 MkII with base **£14.10.0**. P. & P. 15/-  
SP25 Mk II with Sonotone 9TAHCD cartridge and base **£15.15.0**. P. & P. 15/-  
Sonotone 9TAHCD cartridge **£2.15.0** P. & P. 1/6.

**18/19, 25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.**  
**Telephone: 01-580 2255/4532/7679**  
**Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.**

All Mail Orders and correspondence to Dept L5/8, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

# R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

★ Super 30 Amplifier (15 + 15 watt) in veneered housing  
★ Goldring Transcription Turntable on Plinth  
★ Shure or Goldring Magnetic Pick-up Cartridge  
★ Pair of Stanway II Loudspeaker Units  
Special total price. Four fully wired units ready to "plug-in". Carr. 30/-.

**86 Gns.**

TA12 Amplifier (8.5 + 8.5 watt) in veneered housing. Garrard 3000 4 sp. Autochanger unit on plinth. Sonotone 97A P.U. cartridge. Pair of Dorchester Loudspeaker units.  
Special Total Price **47 1/2 Gns.** Carr. 25/-.

Matching as recommended for optimum performance. Send for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



EXTREMELY ATTRACTIVE PLINTHS finished in Teak or Afrormosia veneer. Trans plastic cover.

★ Super 30 amplifier (15 + 15 watt) in veneered housing  
★ Garrard SP25 Mk II Turntable on Plinth  
★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus  
★ Pair Stanway II Speaker Units  
Four fully wired units ready to "plug-in". Special total price **76 Gns.** Carr. 30/-.

★ TA12 Amplifier (8.5 + 8.5 watt) in veneered housing  
★ Garrard SP25 Mk II 4 sp. player unit on plinth  
★ Goldring CS90 Ceramic P.U. Cartridge **53 Gns.**  
★ Pair of Dorchester Loudspeaker Units.  
Special total price Carr. 25/-.

Or Dep. £10.03 and 9 monthly payments £5.15.5 (Total 58 gns.). Transparent plastic cover 3 gns. extra. **TERMS AVAILABLE ALL PACKAGES OFFERS**

## AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. "L" indicates Roll Rubber cone surround. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.

HF510L	5"	10W	49/9	HF120	12"	15W	79/9
HF801D	8"	8W	54/3	HF180D	12"	15W	89/9
HF102D	10"	10W	67/11	HF128	12"	15W	£5.15.0
HF100D	10"	15W	£4.19.9	HF128D	12"	15W	£5.15.0
HF105DL	10"	10W	62/6				

### HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. credit terms available.

**DORCHESTER** Size 16 x 11 x 9in. approx. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High Flux 13x9in. Dual 8W. 18. 19.9  
Cone spkr. Imp. 3 or 15 ohms. Carr. 7/6

**STANWAY II** Size 20x10x9in. approx. Rating 10 watts. Inc. Pane 13x8in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet.

High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

### R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER



200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.8% at 1,000 c.p.s.

'lift' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 50V. Output rating I.I.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 3 1/2 in. Attractive brushed silver finish. Plastic plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring **7 Gns.** Carr. 7/6 OR FACTORY BUILT with 12 months' guarantee. £8.19.9

### RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

**RP2C** Garrard SP25 Mk II (with heavy turntable) fitted Garrard CS23 Stereo Cartridge with diamond tip, Plinth & Cover as RP2C. **15 Gns.**

**RP5C** Garrard 2025 Auto Unit fitted Garrard CS23 Stereo Cartridge with diamond tip, Plinth & Cover as RP2C. **15 Gns.**

Limited number of CLEARANCE LINES in leading makes of Hi-Fi equipment at Branches only

### R.S.C. PLINTHS



for Record Playing units, cut for Garrard 1025, 2025, 3000, A760, SP25 etc. **3 gns.**  
AVAILABLE WITH TRANSPARENT PLASTIC COVER **6 gns.**

INTEREST CHARGES REFUNDED

On Credit Sales settled in 3 months.

### LINEAR L10 HIGH FIDELITY 10W AMPLIFIER 10 Gns.

with separate Pre-amp Magnetic P.U. matching. To clear

### R.S.C. TA12 MKII 6.5 + 6.5 WATT STEREO AMPLIFIER FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'Mficc' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities 1) 300mV (2) 50mV (3) 100mV (4) 2mV. Output rating H.F.M. ★ Handsome brushed silver finish. Facia and knobs. Complete kit **13 1/2 Gns.**



FACTORY BUILT with 12 month gntee 17 Gns or Deposit £5.2.6 and 9 mthly pmts 34/- (Total £20.8.6). Or in Teak or Afrormosia veneer housing 20 1/2 Gns. Dep. £5.10.6 and 9 monthly payments £2.1.7 (Total £24.4.9).

### AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. OR SENIOR 15 WATT INC. HF126 15,000 line 15ohm Speaker £6.15.0. Carr. 9/9

### HI-FI SPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 5/- per enclosure  
**JES** Size 16 x 11 x 9in. Pressurised. Gives £4.14.6 pleasing results with any 5in. Hi-Fi speaker.  
**SE2** For optimum performance with any 5in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. £5.15.0  
**SE10** For outstanding results SE12 For exult primce with 12in. with 10in. Hi-Fi 'spkr' £5.19.9  
Size 24x15x10in. P't'd. Size 25 x 16 x 10in. £6.19.9

### THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25x14x10in. COMPLETE KIT **20 Gns**  
★ Response 30-20,000 c.p.s. Impedance 15 ohms  
★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 6in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £5.10.6 and 9 monthly payments 39/- (Total £23.1.0). DEMONSTRATIONS AT ALL BRANCHES



### R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

★ High-sensitivity. ★ 200-250v. A.C. Mains operation. ★ Sharp A.M. Rejection x 3. ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm coaxial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at considerably less than the cost of comparable units. Factory built 18 gns. Or in Teak finished cabinet as illustrated 21 gns. Terms: Deposit 261.0 and 9 monthly payments. 2 gns. Total £24.19.0. Stereo version. 23 1/2 gns. Carr. 10/6 extra



## R.S.C. SUPER 30 MKII HIGH FIDELITY STEREO AMPLIFIER

High Grade Components Specifications comparable with units costing considerably more.

TRANSISTORS 9 high quality types in each channel.  
OUTPUT 10 Watts R.M.S. continuous into 15Ω (per channel). 15 Watts R.M.S. continuous into 3Ω.  
INPUT SENSITIVITIES Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5 mV.  
FREQUENCY RESPONSE ± 2 dB. 10-20,000 c.p.s.  
TREBLE CONTROL +17 dB to -14 dB at 10 Kc/s.  
BASS CONTROL +17 dB to -15 dB at 50 c/s. HUM LEVEL -80 dB.  
HARMONIC DISTORTION 0.1% at 10 watts 1,000 c.p.s.



Employing Twin Printed Circuits. 200/250v. A.C. mains operation. **CROSS TALK** 52 dB at 1,000 c.p.s.  
**CONTROLS** 5 Position Input Selector. Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.  
**INPUT SOCKETS** (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).  
**CHASSIS** Strong Steel construction. Approx. 12 x 8 x 8in.

**FACIA PLATE** Attractive design in rigid plastic silver background black lettering. Silver finish matching control knobs as available.  
Eminently suitable for use with any make of pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first rate ancillary equipment.

**COMPLETE KIT OF PARTS** 22 gns. Point to point wiring diagrams Carr. 15/- and detailed instructions. Carr. 15/-  
**UNIT FACTORY BUILT** 29 gns. With 12 months guarantee. or Deposit £7.5.0 and 9 monthly payments 58/9 (Total £33.13.9) or in Teak or Afrormosia veneer housing 32 Gns. Carr. 16/-.

### R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BMI An all-day battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 52/6 or **ASSEMBLED 8 Gns.**  
**SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER** Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. **12 1/2 gns.** Carr. 12/6 OR FACTORY BUILT 15 1/2 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9) Available in Teak or Afrormosia veneered housing. 19gns.



### PARTIRIDGE "JOYSTICK" SHORT WAVE AERIALS AND TUNERS AT ALL BRANCHES (S.A.E. for full list)

- BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM 30/31 Gt. Western Arcade 021-236-1279 (Half-day Wed.)
- DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
- GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Henconer Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries.  
Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420 LEICESTER
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) TELLS LIVERPOOL Tel. 28252
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 LIVERPOOL
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 LONDON
- 60A Oldham Street (Half-day Wed.) CENTRAL 2778 MANCHESTER
- 106 Newport Rd. (Half-day Wed.) CENTRAL 47096 MIDDLESBROUGH
- 41 Blakett Street (Opp Fenwick's Store) NEWCASTLE UPON TYNE (Half-day Wed.) Tel. 21469
- 13 Exchange Street (Castle Market Bldgs.) SHEFFIELD (Half-day Thursday) Tel. 20716

**R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER** Highly sensitive. Push-Pull high output, with Pre-amp. Tone Control Stages. Performance figures of factory built units: Hum level—70dB. Frequency response  $\pm 3dB$  30-20,000c/s. Sectionally wound output transformer. All high grade components. Valves E186, E189, ECC83, 907, 907, GZ34. Separate Bass and Treble Controls. Sensitivity 36mV. Suitable for high impedance microphones. Crystal or Ceramic P.U.'s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.P. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **15 Gns.** Carr. 12/6

Twin-handled perforated cover 35/-. Supplied factory built with EL34 output valves. 12 months' guarantee for 18 Gns. **TERMS:** Deposit £6.3.0 and 9 monthly payments of 34/- (Total £21.9.0). Send S.A.E. for leaflet.

**R.S.C. All HIGH FIDELITY 12-14 WATT AMPLIFIER**

**PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP.** Two input sockets with mixing facilities High sensitivity. 5 valves. Independent Bass and treble controls. Frequency response  $\pm 3dB$  30-20,000 c/s. Hum level—60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.'s. High Impedance "mikes". For Musical Instruments etc. Std. A.C. mains. For 3 & 15 ohm spkrs. **91 Gns.** SAE for leaflet. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6. Twin handled metal cover 35/-. Price Factory built 131 gns. or Deposit 99/6 and 9 monthly payments of 26/-. (Total £18.13.6).

**ESD KIT TRANSCRIBED VERSION** of above complete kit 9 Gns. (Assembled 18 Gns.)

**30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP** A 4 input, 2 volume control Hi-Fi unit with Separate Bass and Treble controls. B.V.A. valves. Peak output rating. Strong Rexine covered cabinet with handle. Attractive black/gold fascia panel. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm **19 Gns.** Carr. 12/6. Dep. 5 gns. & 9 monthly payments of 39/9 (Total 29 gns.)

**FANE ULTRA HIGH POWER LOUDSPEAKERS** All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis. All prices carr. free

<b>'POP' 100</b> 18" 100Watt 14,500 gauss 8/15Ω <b>21 GNS.</b>	<b>'POP' 60</b> 15" 60 Watt 14,000 gauss 8/15Ω <b>12 GNS.</b>	<b>'POP' 50</b> 12" 50 Watt 14,000 gauss 15Ω <b>10 GNS.</b>
--	---	---

**FANE LOUDSPEAKERS 'POP' 30C**  
12" 25 Watt Dual cone 15Ω  
**£5-19-9** Carr. free

**F.A.L. P.A. AMPLIFIERS** PHASE 50 **29 GNS.** PHASE 100 **59 GNS.**  
S.A.E. for leaflets.

**R.S.C. COLUMN SPEAKERS** Covered in Rexine and Vynair, ideal for vocalists and Public Address. 15 ohm matching.

**TYPE C48S 25/30 WATTS.** Fitted four 8in. high flux 8 watt speakers. Overall size approx. 48 x 10 x 6in. **16 Gns.** Carr. 10/-

Or deposit 67/- and 9 monthly payments 34/9 (Total £18.19.9).

**TYPE C412S 50 WATTS.** Fitted four 12in. 11,000 line 15 watt speakers. Overall size 56 x 14 x 9in. approx. **26 Gns.** Carr. 15/-

Or Deposit £5.17.6 and 9 monthly payments of 54/6 (Total £30.7.0)

**HIGH QUALITY LOUDSPEAKERS**

In Teak or Alrosmosia veneered Cabinets

**L13 13" x 8" 8-10 Watt** 10,000 lines 3 or 15 ohms. Carr. 7/6

**TYPE L12 12" 20 Watt** 10,000 lines 15 ohms. Carr. 8/9

**R.S.C. BASS-REGENT 50 WATT AMPLIFIER**

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram. radio, tape. Peak Output rating.

★ Two extra heavy duty 12in. Loudspeakers.  
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

**55 Gns.** Carr. 30/- or dep. £18.4.9 and 9 monthly payments of £5.11.9. (Total 604 gns.) Send S.A.E. for leaflet.

G100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Speakers). 99½ gns.

**R.S.C. MAINS TRANSFORMERS FULLY GUARANTEED** Interleaved and Impregnated. Primaries 200-250v. 50c/s. Screened MIDGET CLAMPED TYPE 2½ x 2½ x 2½in.

250v., 60mA, 6.3v. 2a	17/11
250-0-250v., 60mA 6.3v. 2a	18/11
<b>FULLY SHROUDED UPRIGHT MOUNTING</b>	
250-0-250v. 100mA, 6.3v. 2a, 0-5-6.3v. 2a.	24/9
250-0-250v. 100mA, 6.3v. 2a, 0-5-6.3v. 3a.	39/9
300-0-300v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a.	39/9
300-0-300v. 130mA, 6.3v. 4a, c.t., 6.3v. 1a.	
For Mullard 510 Amplifier	47/11
350-0-350v. 100mA, 6.3v. 2a, 0-5-6.3v. 3a.	39/9
350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a.	47/9
425-0-425v. 200mA, 6.3v. 4a, c.t., 5v. 3a.	89/9
425-0-425v. 200mA, 6.3v. 4a, 6.3v. 3a, 5v. 3a	93/9
450-0-450v. 250mA, 6.3v. 4a, c.t., 5v. 3a.	99/9
<b>TOP SHROUDED DROP-THRO' TYPE</b>	
250-0-250v. 70mA, 6.3v. 2a, 0-5-6.3v. 2a.	23/9
250-0-250v. 100mA, 6.3v. 3.5a.	27/9
250-0-250v. 100mA, 6.3v. 2a, 6.3v. 1a.	28/9
350-0-350v. 80mA, 6.3v. 2a, 0-5-6.3v. 2a.	29/11
300-0-300v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a.	39/9
300-0-300v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a.	39/9
300-0-300v. 130mA, 6.3v. 4a, 0-5-6.3v. 1a.	
Suitable for Mullard 510 Amplifier	46/9
350-0-350v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a.	39/9
350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a.	46/11
<b>FILAMENT OR TRANSFORMER POWER PACK</b>	
Types 6.3v. 1.5a. 8/9; 6.3v. 2a. 9/9; 6.3v. 3a. 13/9; 6.3v. 6a. 22/9; 12v. 1a. 9/11; 12v. 3a. or 24v. 1.5a. 23/9; 0.9-18v. 12a. 19/11; 0-12-25-43v. 2a. 31/9	
<b>CHARGE TRANSFORMERS</b> 0.9-15v. 11a. 15/9; 24a. 19/11; 5a. 21/11; 6a. 25/11; 6a. 29/9; 5a. 36/9.	
<b>AUTO (Step Up/step DOWN) TRANSFORMERS</b>	
0-110/120v. 200-230-250v., 50-80 watts 19/9; 150 watts, 33/6 250 watts 49/9; 500 watts 105/-	
<b>OUTPUT TRANSFORMERS</b>	
Standard Pentode 5,000Ω or 7,000Ω to 3Ω	8/9
Push-Pull 8 watts EL34 to 3Ω or 15 Ω	14/9
Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15 Ω	24/9
Push-Pull EL34 to 3 or 15 Ω 10-12 watts	23/9
Push-Pull Ultra Linear for Mullard 510, etc.	39/9
Push-Pull 15-15 watts sectionally wound 6L6, KT66, etc., for 3 or 15 Ω	35/9
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω	59/9
<b>SMOOTHING CHOKES</b> 150mA, 7-10H, 250Ω 12/9; 100mA, 10H, 200Ω 10/9; 80mA, 160Ω, 350Ω 8/9; 60mA, 10H, 400Ω 7/11.	
<b>SELENIUM RECTIFIERS F. W. (Bridged)</b>	
All 6/12v. D.C. output. Max. A.C. input 18V. 1a. 4/8. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.	

**YOURS FREE FOR 7 DAYS**

**The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

**WHAT READERS SAY**

*'Everything is clearly set out ...'*  
... I am well pleased with this pictorial system. Everything is clearly set out in diagrams, ... L.P., Co. Armagh.

*'... very pleased with the set ...'*  
... I was very pleased with the set of Basic Electronics. Please send Basic Electricity ... D.W., Margate.

*'... how understandable your books are ...'*  
... Pleased to say how understandable your books are, I now have a sound knowledge of the subject ... A.A., Hull.

A TECH-PRESS PUBLICATION

**POST NOW FOR THIS OFFER!!**

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS

Prices include Postage and Packing.

Signature \_\_\_\_\_  
(If under 21 signature required of parent or guardian)

NAME \_\_\_\_\_  
BLOCK LETTERS

FULL POSTAL ADDRESS \_\_\_\_\_

# Adamin

## MICRO SOLDERING INSTRUMENTS

A range of micro soldering instruments combining high performance with really small dimensions and providing exceptional versatility.

Weighing about ½ oz. (less flex) these miniature tools ensure the utmost accuracy and safety in use, resulting in consistently high standards of soldering with minimum operator fatigue.

Ultra-slim unbreakable nylon handles give a cool, comfortable grip for sustained delicacy of operation.

Slip-on bits are fitted over the element shaft, so absorbing all the heat produced and giving high performance with rapid heating and recovery. A wide range of interchangeable tip sizes is available to suit different types of work.

There are six ADAMIN models to choose from, 5 to 24 watts, in voltages from 6v. to 240v.

Please ask for leaflet A/10.

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL  
Telephone 01-688 8589 and 4559



**FREE LIST! SEND S.A.E. FOR BUMPER FLOG LIST**

**★ FANTASTICALLY POPULAR JASON TAPE ★**

We offer you fully tensilised polyester mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, isolated or cheap imports **TRY ONE AND PROVE IT YOURSELF.**

Standard Play		Long Play	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5¾in. 900ft.	10/6	5¾in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5¾in. 2,400ft.	34/-
5¾in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,100ft.	27/-	Quadruple Play	
		3in. 600ft.	8/6

**BARGAIN SPRING SALES AT ALL BRANCHES**

- ★ LONDON (MUS 2639) 10 Tottenham Court Road
- ★ PORTSMOUTH (Tel. 22034) 350-352 Fratton Road
- ★ SOUTHAMPTON 72 East Street (Tel. 25851)
- ★ BRIGHTON (Tel. 23975) 8 Queen's Road

Postages 1/- reel.  
Post Free less 5% on three reels.  
Quantity and Trade enquiries invited.

All mail orders to DEVONIAN COURT, PK. CRES. PLACE, BRIGHTON (Tel 680722)

## RADIO COMMUNICATION HANDBOOK

over 22,000 copies sold

Now in its second printing

The standard work in its field

832 pages of everything in the science of radio communication. The handbook's UK origin ensures easy availability of components. **69s post paid**

## Amateur radio circuits book

by George Jessop, G6JP

Second edition; reprinted 1970

Designed to meet the needs of the home constructor and experimenter. A comprehensive collection of up-to-date circuits covering a wide variety of applications. **13s 4d post paid**

## THE VHF-UHF MANUAL

By George Jessop, G6JP

A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA. **23s post paid**

Obtainable from:  
**RADIO SOCIETY of GREAT BRITAIN**  
35 DOUGHTY STREET, LONDON, WC1N 2AE

## BAKER 12in. MAJOR £9

The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30.17,000 cps with tweeter, crossover, baffle 19 x 12½in. and instructions. **£11.10.0**

Send 4d Stamp for Further Details

**Baker Reproducers Ltd**  
Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

# BI-PAK SEMICONDUCTORS

**NEW LOW PRICED TESTED S.C.R.'s**  
 1A 3A 7A 6A 30A  
 (TO-5) (TO-66) (TO-48) (TO-48)  
 case) case) case) case)  
 PIV each case each case PIV each  
 50 4/6 5/- 9/6 10/6 25 20/-  
 100 5/- 6/6 10/6 12/6 50 23/-  
 200 7/- 7/6 11/6 15/- 100 28/-  
 400 8/6 9/6 13/6 18/- 200 32/-  
 600 10/6 11/6 15/6 25/- 400 35/-  
 800 12/6 14/- 18/- 30/- 800 80/-

**PRINTED CIRCUITS EX-COMPUTER**  
 Packed with semiconductors and components, 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- p. & p.

**TRANSISTORE QV.T. & SPECIFICATION BOOK** (German publication). A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

**2N3060 NPN SIL. DUAL TRANS.** CODE D1699 TEXAS. Our price 5/- ea.  
**120VCE NIXIE DRIVER TRANSISTOR.** Sim. HBX21 & C407, 2N1893 FULLY TESTED AND CODED ND120, 1-24, 8/6 each. TO-5 NPN 25 up 8/- each.

Sil. trans. suitable for P.E. Organ, Metal TO-18 Eqt. Any Qty. **ZTX300 1/-**

**MULLARD I.C. AMPLIFIERS**  
 TAA243, Operational amplifier, 70/- each.  
 TAA263, Linear AF amplifier, 18/6 each.  
 TAA293, General purpose amplifier, 21/- each.

**CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS**  
 Audio Power Amplifier, 30/- each.

**SIL. REJECTS TESTED**  
 PIV 750mA 3A 10A 30A  
 50 1/- 2/9 4/3 9/6  
 100 1/3 3/3 4/6 15/-  
 200 1/9 4/- 4/9 20/-  
 300 2/3 4/6 6/6 22/-  
 400 2/6 5/6 7/6 25/-  
 500 3/- 6/- 8/6 30/-  
 600 3/3 6/9 9/- 37/-  
 800 3/6 7/6 11/- 40/-  
 1000 5/- 9/3 12/6 50/-  
 1200 6/6 11/6 15/-

**TRIACS**  
 VBOM 2A 6A 10A  
 (TO-1) (TO-66) (TO-88)  
 100 14/- 15/- 22/6  
 200 17/6 20/- 28/-  
 400 20/- 25/- 35/-  
 VBOM=Blocking voltage in either direction.

**2N3055 115 WATT SIL. POWER. NPN.** OUR PRICE 12/6 EACH

**FULL RANGE OF ZENER DIODES**  
 VOLTAGE RANGE 2-18V. 400mV (DO-7 Case) 2/8 ea. 1-5W(T op-Hat) 3/8 ea. 10W. (SO-18 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

**BRAND NEW TEXAS GERM. TRANSISTORS** Coded and Guaranteed.  
 Pak No. EQVT  
 T1 8 2G371A OC71  
 T2 8 2G374 OC75  
 T3 8 2G374A OC81D  
 T4 8 2G381A OC81  
 T5 8 2G382T OC82  
 T6 8 2G344A OC44  
 T7 8 2G345A OC45  
 T8 8 2G378 OC78  
 T9 8 2G399A 2N1302  
 T10 8 2G417 AF117  
 All 10/- each pack

# SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality  
 Satisfaction GUARANTEED in Every Pak, or money back.

- Pak No.**
- U1 120 Glass Sub-min. General Purpose Germanium Diodes .. 10/-
  - U2 60 Mixed Germanium Transistors AF/RF .. 10/-
  - U3 75 Germanium Gold Bonded Diodes sim. OA6, OA47 .. 10/-
  - U4 40 Germanium Transistors like OC81, AC128 .. 10/-
  - U5 60 200mA Sub-min. Sil. Diodes .. 10/-
  - U6 30 Silicon Planar Transistors NPN sim. B5Y95A, 2N706 .. 10/-
  - U7 16 Silicon Rectifiers Top-Hat 750mA up to 1,000V .. 10/-
  - U8 60 Sil. Planar Diodes 250mA OA/200/202 .. 10/-
  - U9 20 Mixed Volts 1 watt Zener Diodes .. 10/-
  - U11 30 PNP Silicon Planar Transistors TO-5 sim. 2N1132 .. 10/-
  - U13 30 PNP-NPN Sil. Transistors OC200 & 2S104 .. 10/-
  - U14 150 Mixed Silicon and Germanium Diodes .. 10/-
  - U15 25 NPN Silicon Planar Transistors TO-5 sim. 2N897 .. 10/-
  - U16 10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV .. 10/-
  - U17 30 Germanium PNP AF Transistors TO-5 like ACY17-22 .. 10/-
  - U18 8 6-Amp Silicon Rectifiers BY213 Type up to 600 PIV .. 10/-
  - U19 25 Silicon NPN Transistors like BC108 .. 10/-
  - U20 12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV .. 10/-
  - U21 30 AF Germanium alloy Transistors 2G300 Ser. & OC71 .. 10/-
  - U22 30 Mat's like MAT Series PNP Transistors .. 10/-
  - U24 20 Germanium 1-amp Rectifiers GJM up to 300 PIV .. 10/-
  - U25 25 300mC/s NPN Silicon Transistors 2N708, B5Y27 .. 10/-
  - U26 30 Fast Switching Silicon Diodes like IN914 Micro-min. .. 10/-
  - U28 Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces 20/-
  - U29 10 1-amp SCR's TO-5 can up to 600 PIV CR61/25-600 .. 20/-
  - U31 20 Sil. Planar NPN trans. low noise Amp 2N3707 .. 10/-
  - U32 25 Zener diodes 400mW D07 case mixed Volts, 3-18 .. 10/-
  - U33 15 Plastic case 1 amp Silicon Rectifiers IN4000 series .. 10/-
  - U34 30 Sil. PNP alloy trans. TO-5 BCY28, 2S302/4 .. 10/-
  - U35 25 Sil. Planar trans. PNP TO-18 2N2906 .. 10/-
  - U36 25 Sil. Planar NPN trans. TO-5 BFY 30/51/52 .. 10/-
  - U37 30 Sil. alloy trans. SO-2 PNP, OC200 2S322 .. 10/-
  - U38 20 Fast Switching Sil. trans. NPN. 400 Mfcs 2N3011 .. 10/-
  - U39 30 RF Germ. PNP trans. 2N1303/5 TO-6 .. 10/-
  - U40 10 Dual trans. 6 lead TO-5 2N930 .. 10/-
  - U41 25 RF Germ. trans. TO-1 OC45 NKT72 .. 10/-
  - U42 10 VHF Germ. PNP trans. TO-1 NKT667 AF117 .. 10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

# I.C. AMPLIFIER

Identical encapsulation and pin configuration to the following: SL402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 80/- each. 100 up 25/- each.

**AD161 NPN AD162 PNP**  
 MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS. For mains driven output stages of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

**UNIUNION UT46.** Eqt. 2N2646 Eqt. TIS43. BEN3000 5/6 EACH 25-99 5/- 100 up 4/-

**NPN Silicon PLANAR BC107/8/9, 2/-** each 50-99, 1/10 100 up, 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

**PNP DIFFUSED SILICON PHOTODUODIODE TYPE 15701 (2N1275) or Triac** (2N1275) or Triac. High switching and measurement indicators, 50V, 250mV. OUR PRICE 10/- EACH 50 OR OVER 8/6 EACH. FULL DETAILS.

**FE7's**  
 2N 3819 ..... 8/-  
 2N 3820 ..... 25/-  
 MPF105 ..... 8/6

# BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital SN74N Series fully coded, brand new to manufacturers' specifications. Dual in-line plastic 14 and 16 pin packages.

BI-PAK Order No.	Description	Price and qty. prices
		1-24 25-99 100 up
BP00=SN7400N	Quad 2-Input NAND GATE	6/6 5/6 4/6
BP01=SN7401N	Quad 2-Input NAND Gate—OPEN COLLECTOR	6/6 5/6 4/6
BP04=SN7404N	HEX INVERTER	6/6 5/6 4/6
BP10=SN7410N	Triple 3-Input NAND GATE	6/6 5/6 4/6
BP20=SN7420N	Dual 4-Input NAND GATE	6/6 5/6 4/6
BP30=SN7430N	Single 8-Input NAND GATE	6/6 5/6 4/6
BP40=SN7440N	Dual 4-Input BUFFER GATE	6/6 5/6 4/6
BP41=SN7441AN	BCD to decimal decoder and NIT Driver	22/6 20/- 17/6
BP42=SN7442N	BCD to decimal decode (TTL 0/1)	22/6 20/- 17/6
BP50=SN7450N	Dual 2-Input AND/OR/NOT GATE—expandable	6/6 5/6 4/6
BP53=SN7453N	Single 8-Input AND/OR/NOT GATE—expandable	6/6 5/6 4/6
BP60=SN7460N	Dual 4-Input—expandable	6/6 5/6 4/6
BP70=SN7470N	Single JK Flip-flop—edge triggered	9/- 8/- 7/-
BP72=SN7472N	Single Master Slave JK Flip-flop	9/- 8/- 7/-
BP73=SN7473N	Dual Master Slave JK Flip-flop	10/- 9/- 8/6
BP74=SN7474N	Dual D Flip-flop	10/- 9/- 8/6
BP75=SN7475N	Quad Bistable Latch	11/- 10/- 9/6
BP76=SN7476N	Dual Master Slave Flip-flop with preset and clear	11/- 10/- 9/6
BP83=SN7483N	Four Bit Binary Adder	26/- 22/6 20/-
BP90=SN7490N	BCD Decade Counter	22/6 20/- 17/6
BP92=SN7492N	Divide by 12 4 Bit binary counter	22/6 20/- 17/6
BP93=SN7493N	Divide by 16 4 Bit binary counter	22/6 20/- 17/6
BP94=SN7494N	Dual Entry 4 Bit Shift Register	22/6 20/- 17/6
BP95=SN7495N	4 Bit Up-Down Shift Register	22/6 20/- 17/6
BP96=SN7496N	5 Bit shift register	24/- 21/- 18/6

Data is available for the SN74N Series of Integrated circuits in booklet form, price 2/6

**BRAND NEW FULL TO MANUFACTURERS' SPECIFICATION**  
 BP709 Operational Amplifier, dual-in-line 14 pin package = SN72709 and similar to MIC709 and ZLD709C 10/6 9/- 8/-  
 This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

# INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work, on testing some will be found perfect.

PAK No.	PAK No.	PAK No.
UIC00=5 x 7400N .. 10/-	UIC42=5 x 7442N .. 10/-	UIC80=5 x 7480N .. 10/-
UIC01=5 x 7401N .. 10/-	UIC50=5 x 7450N .. 10/-	UIC82=5 x 7482N .. 10/-
UIC02=5 x 7402N .. 10/-	UIC61=5 x 7461N .. 10/-	UIC83=5 x 7483N .. 10/-
UIC03=5 x 7403N .. 10/-	UIC60=5 x 7460N .. 10/-	UIC85=5 x 7485N .. 10/-
UIC04=5 x 7404N .. 10/-	UIC70=5 x 7470N .. 10/-	UIC90=5 x 7490N .. 10/-
UIC05=5 x 7405N .. 10/-	UIC72=5 x 7472N .. 10/-	UIC92=5 x 7492N .. 10/-
UIC10=5 x 7410N .. 10/-	UIC73=5 x 7473N .. 10/-	UIC93=5 x 7493N .. 10/-
UIC20=5 x 7420N .. 10/-	UIC74=5 x 7474N .. 10/-	UIC94=5 x 7494N .. 10/-
UIC40=5 x 7440N .. 10/-	UIC75=5 x 7475N .. 10/-	UIC95=5 x 7495N .. 10/-
UIC41=5 x 7441AN .. 10/-	UIC76=5 x 7476N .. 10/-	UIC96=5 x 7496N .. 10/-
		UICX1=20 x ass't'd 74's .. 30/-

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

# DUAL-IN-LINE LOW PROFILE SOCKETS

14 AND 16 Lead Sockets for use with Dual-in-Line Integrated Circuits.  
**Order No.**  
 TS014 14 pin type .. 1-24 25-99 100 up  
 TS015 14 pin type .. 7/6 6/- 5/3  
 TS016 16 pin type .. 10/- 8/6 7/9

# FAIRCHILD (U.S.A.) I.C.'s

**RTL Micrologic Circuits**  
 Epoxy case To-5 temp range 15°C to 55°C. Qty. prices each  
 μL 900 Buffer .. 1-11 12-24 25-99 100 up  
 μL 914 Dual two-input GATE .. 9/8 8/- 7/6 6/6  
 μL 923 J-K Flip-flop .. 9/8 8/- 7/6 6/6  
 Full data and circuits for ICS in Booklet form price 1/6 each.  
 μA703E Linear RF-IF AMPLIFIER .. 11/- 10/- 9/- 8/8  
 PLASTIC CASE TO-5 6 lead up to 100 m/cs.

# MOTOROLA DIGITAL I.C.'s

**MDTL dual in-line package.**  
 Type MCRP expandable dual 4-input NAND Power Gate .. 10/- each  
 Type MCR45P Clocked Flip-flop .. 15/- each  
 FULL DATA SUPPLIED WITH UNITS


Please send all orders direct to our warehouse and despatch department.  
**BI-PAK SEMICONDUCTORS**  
**P.O. BOX 6, WARE, HERTS.**  
 Postage and packing add 1/-. Overseas add extra for Airmail. Minimum order 10/- Cash with order please.

# LOOK!

**PRACTICAL!**

**VISUAL!**

**EXCITING!**

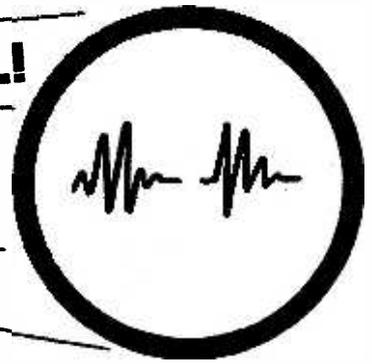


*a new 4-way method of mastering*

# ELECTRONICS

*by doing — and — seeing . . .*

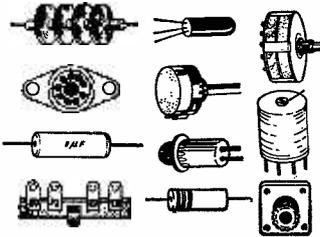
## 1 ▶ OWN and HANDLE a

complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



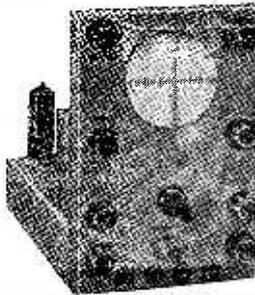
## 2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**



## 3 ▶ READ and DRAW and

**UNDERSTAND** **CIRCUIT DIAGRAMS**

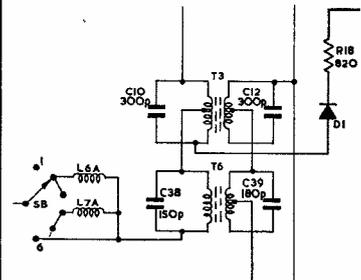

## 4 ▶ CARRY OUT OVER **40** EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE P.W.8

# PRACTICAL WIRELESS

VOL 46 NO 4

Issue 762

AUGUST 1970

## TOPIC OF THE MONTH

### Learn while you build

**E**XPERT gardeners are said to have 'green fingers' which implies that they have some magic touch. In the same way, there are service technicians who, seemingly by some sort of telepathy, have an uncanny knack of quickly looking over a faulty piece of equipment, then pointing an accusing finger and saying "C5 has gone down".

The same kind of thing happens in the area of amateur home construction. Some seem to have it, others do not. But although it is obvious that some constructors are neater and cleverer than others, and some people can "de-bug" a project quicker and more effectively than others, it would be wrong to put this down to fate or any other ethereal influence.

Real success in such realms as radio construction is rarely accidental; it is usually achieved only by a combination of common sense and thoughtful application. An enthusiast passes the barrier between the absolute novice and competent constructor when he begins not only to build equipment but starts to puzzle out exactly what each component does and what effect each component has on others. Only by acquiring a solid working knowledge of each individual item will the enthusiast be able to get the optimum performance from his project and to clear up any troubles which may subsequently arise.

One often hears that certain pieces of equipment, such as portable transistor radio receivers, use "standard circuits". This may appear to be superficially true, but in actual practice, variations are legion. These may be minor in character, the basic "blocks" being almost identical, but it is these minor variations which (if fully understood) will give the enquiring hobbyist a much better insight into the whys and wherefores of circuit design.

Basic circuitry can be learnt from text books, but no amount of reading will substitute for practical work; on the other hand practical work will not advance the constructor's knowledge unless he takes the trouble to work out what a circuit is, what it is supposed to do, and how. He should want to know why a certain component is where it is, and why it has a certain value. He should also want to know what might happen should that component become faulty.

W. N. STEVENS—*Editor.*

**SEPTEMBER ISSUE WILL BE PUBLISHED  
ON AUGUST 7**

## NEWS AND COMMENT

Leader	265
News . . . News . . . News . . .	266
Letters to the Editor	285
On the Short Waves by <i>Malcolm Connah and David Gibson, G3JDG</i>	286, 287
MW Column by <i>Charles Molloy</i>	293
CQ! CQ! CQ! CQ! CQ! CQ!	293

## CONSTRUCTIONAL

Genetracer by <i>J. B. Willmott, A.I.P.R.E.</i>	268
Versatile 5/50 Transmitter by <i>F. G. Rayer, G3OGR</i>	272
Electronic Metronome by <i>M. Wallis</i>	279
I.C. of the Month, MC1303 Stereo Preamp & MC1304 Decoder by <i>L. A. J. Ireland</i>	283
Modular 3-Band Short Wave Receiver by <i>R. F. Graham</i>	288
Audio Expander Compressor by <i>C. R. Bradley</i>	294
Take 20, Signal Injector by <i>Julian Anderson</i>	310

## OTHER FEATURES

Project Autumn	271
Sums plus Circuits equals Understanding Part 5 by <i>Leslie Moore</i>	309
Going Back by <i>Colin Riches and Arthur Dow</i>	313

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, St. Queen Street, London W.C.2.

# NEWS... NEWS... NEWS...

## Listeners Club Ceases

Now in its fourth year of service, the Listeners' Club of Radio New York Worldwide has ceased operation.

Irwin Belofsky, the President of the Club, says that they have found it impossible to continue publishing *Radio Worldwide*, their magazine, without a tremendous financial loss. It is a loss incurred through rising costs in postage, print, etc., and these could not be covered through membership dues or advertising.

All Listeners Club members with unexpired subscriptions will, however, receive the balance of their membership in issues of a new publication, *Radio Today*.

## Vero Strip




Vero Electronics Ltd., of Chandler's Ford, Hampshire, have recently introduced a new type of terminal board which has been designed as a simple and inexpensive mounting strip for discrete components. These can be mounted across the width of the board or alternatively along its length to effect cross-connection.

The mechanical and electrical specifications of the materials used enable the board to withstand a maximum working voltage of 2kV, whilst still maintaining an insulation resistance of one hundred thousand megohms between adjacent copper pads. These features make the board suitable for all applications where a conventional tag strip or group board might be used.

The dimensions of the strip are such that they can be mounted in standard die-cast boxes.

A number of terminal pins are also available which can be used in conjunction with the Vero strip where such additional facilities are required. *Vero Electronics Limited, Industrial Estate, Chandler's Ford, Hampshire, SO5 3ZR.*

## B.B.C. Radio Birmingham

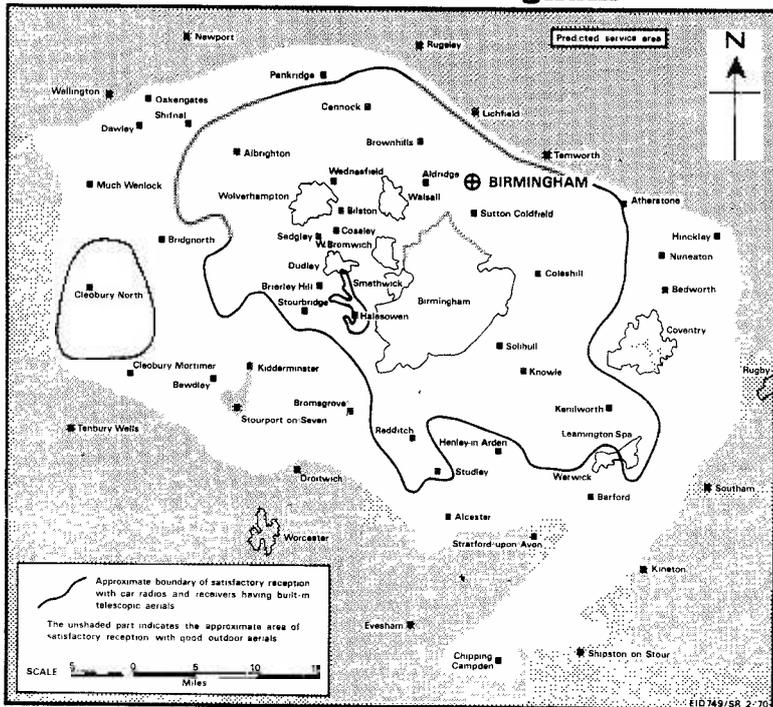

This v.h.f. service transmits on 95.6MHz, horizontal polarisation. Maximum e.r.p. is 5.5kW with a directional aerial.

The transmitter is sited at BBC Sutton Coldfield. Inner and outer service area boundaries correspond to average field-strength contours of 60 and 52dB (relative to 1 microvolt per metre) respectively for a receiving aerial height of 30 feet. The field strength at a particular site may differ by as much as 10dB from that indicated.

## Otley Radio Society

The Chairman of the Otley Radio Society, M. T. George-Powell, G3NNO, informs us that the membership has increased and the Society recently moved to larger premises so that they will be able to hold lectures, slide shows etc. The Society meets every Tuesday evening and on March 19th members visited the Yorkshire TV studios in Leeds. Further details about the meetings may be obtained from: *The Chairman, 82 Forest Avenue, Harrogate, York.*


## Loudspeaker Kits

Richard Allan Ltd. announce details of three loudspeaker kits. They have made a special study of the needs of the D.I.Y. individual and believe that they have met all the requirements.

The kits are complete in every


sense and contain B.A.F. wadding and foam underlay cut to size and a postcard giving a choice of any three Vynairs. Receipt by Richard Allan of the card giving the user's choice enables them to post him the Vynair by return post. Shown in the photograph is the "Twin Assembly".

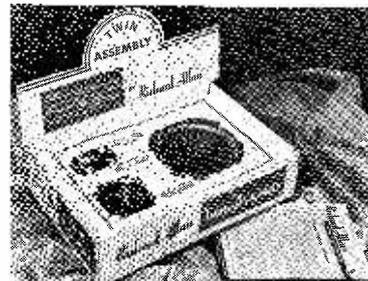For further details contact *Richard Allan Ltd., Bradford Road, Gomersal, Cleckheaton, Yorkshire.*



# NEWS... NEWS... NEWS...

## Keeping Track

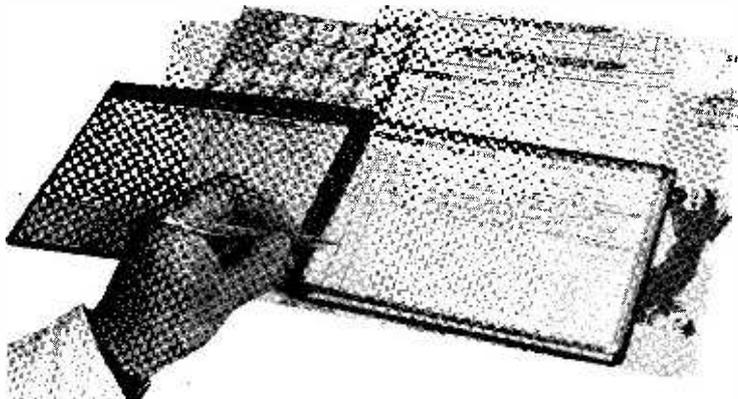


A new useful accessory for record collectors is a unique system for cataloguing and locating gramophone records easily. The system comprises:- luxury padded simulated pigskin book containing 12 clear P.V.C. slip-in pockets in which are kept specially pre-printed index records which can be completed by the user. The index is provided in pad form, each set comprises:- 25 pre-printed Index Pages, 3 Records Wanted Pages and 3 Contents

Pages; pairs of self-adhesive circular labels numbered 1-100 for attaching to record sleeves; 40 plain self-adhesive labels enabling printed headings of the Index Pages to be covered neatly to provide for hand or typewritten headings. The system can be expanded to 999 records and can also be used for recorded tape.

Made by the *Bib Division, Multicore Works, Hemel Hempstead, Herts.* retail price, including tax, is 34s.
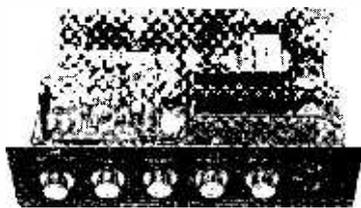
## Stereo Amplifier from F.S. Electronics



This amplifier has been designed as an optimum between the simple and sophisticated units presently available, to give performance and looks required by present day living rooms at a moderate cost. This unit is due for export to Czechoslovakia as a solid British product housed in a  $\frac{3}{4}$ in. polished cabinet with a choice of woods and front panel colours. Inputs are available for Ceramic/Crystal and Magnetic cartridges, with an Auxiliary input for Radio Tuner or Tape Replay.

Outputs consist of a low impedance Tape Record and Twin

speakers.

Specification is as follows:  
**Ceramic Input:** 50mV sensitivity, velocity loaded, R.I.A.A. corrected.

**Magnetic Input:** 2.5mV sensitivity, velocity loaded, R.I.A.A. corrected.

**Auxiliary Input:** 100mV into 110K, flat response, ie 20Hz-20kHz  $\pm 2$ dB.

**Tape Output:** 150mV flat response.

**Speaker Output:** 6 watts Music Power into 4 ohms per channel.

**Tone Controls:** Base  $\pm 10$ dB at 20Hz-20kHz. Treble  $\pm 15$ dB at 20kHz.

**Signal/Noise:** Better than 50dB on all inputs. Aux. input 60dB.

**Overall Distortion:** 1.5%.

The amplifier retails at £32 10s and the power output modules can be supplied separately at £3 16s each.

*F.S. Electronics Ltd., 93A Balderton Gate, Newark, Notts.*

## Club Notes

... Meetings of the Chester & District Amateur Radio Society are held at the Y.M.C.A., Chester at 8 p.m. every Tuesday except the first Tuesday of each month which is Nett Night. Recent meetings included lectures on Short Wave Listening and Aerials, visit to BBC, junk sale, and talk entitled On to Square Two by G3ATZ. Further gen from: Alan S. Warne, G8AYW, 113 Queens Road, Vicars Cross, Chester.

... Derby & District Amateur Radio Society are holding their Mobile Rally on Sunday, August 16th. at Rykneld School, Bedford Street, Derby. There will be talk-in stations from 10 a.m. to 3 p.m. G3ERD/A on 160m., G2DJ/A on 4m. and G8DBY/A on 2m. Further gen from: T. Darn, G3FGY, Sandham Lodge, Sandham Lane, Ripley, Derby.

... Stourbridge & District Amateur Radio Society, in collaboration with the Llanfair-Welshpool railway set up a radio station at the Llanfair-Caereinion terminal station on July 4th. They operated between 12 noon and 6 p.m. on 80m. using the call GW601/P. Further gen on the Society from: Sheila Clift, G8BYE, Manorways, 49 Manor Lane, Halesowen, Worcs.

## Radio & TV Course

The Stonebridge Evening Institute, Brentfield Road, London, N.W.10. are holding a Radio & TV Course. It will be held on Tuesdays and Thursdays (7p.m.-9p.m.) commencing 22nd and 24th. September 1970. Fees for a course lasting 30 weeks for two evenings per week are £4. Session ends on 28th. May 1971. The course covers theory and some practical work. Enrolment will take place during the week 14th. to 17th. September 1970 or readers may enrol now by writing to: 44 Worcester Crescent, Mill Hill, London, N.W.7. Cheques and P.O.'s should be made payable to "The Brent Borough Treasurer".

# genetracer


J. B. WILLMOTT A.I.P.R.E.

## A USEFUL AID TO SPEEDY FAULT FINDING

WHAT the serviceman requires is some quick method of "seeing" (or hearing) what is actually happening to the signal passing through any part of equipment under investigation. The sophisticated approach to this requirement is to use an oscilloscope, on the screen of which the actual signal at the test point can be displayed.

But few radio enthusiasts possess such an instrument and the necessary ancillary items such as a wobulator and calibrated signal generator, which are required to utilise the full potential of an oscilloscope.

A very effective substitute is the use of the procedure known as "signal tracing". Basically, this can be approached in two ways, either an artificial signal can be injected into the equipment under test, at any given point, and the result listened to on the equipment's own speaker, or, alternatively, a sensitive signal tracer can be connected to any suitable point in the equipment being tested, and the signal at that point "picked off" by the tracer,

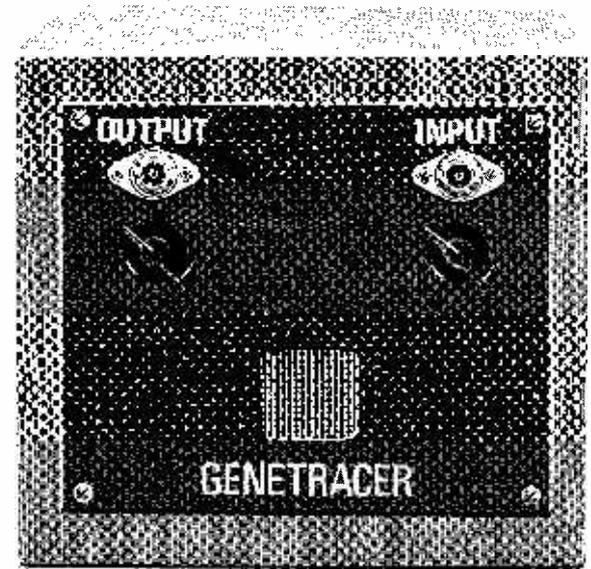

demodulated if necessary (r.f. or i.f. signals), and given sufficient a.f. amplification to produce an audible signal in the speaker built into the tracer itself.

Both systems have their merits and the instrument about to be described combines both functions. If the output socket be connected, preferably by a short length of coaxial cable, to the equipment under test, a wideband signal extending from r.f. to a.f. frequencies can be injected at any desired level by adjustment of the output gain control, and a steady audio note (of about 1 kHz) will be heard from the speaker of the equipment being tested, if all is in order onwards from the point of injection.

Alternatively, if the input socket is connected to the equipment being tested, the tracer will reproduce in its own speaker, a faithful rendering of the signal existing at the test point. It is in fact possible, indeed often useful, to utilise both functions simultaneously.

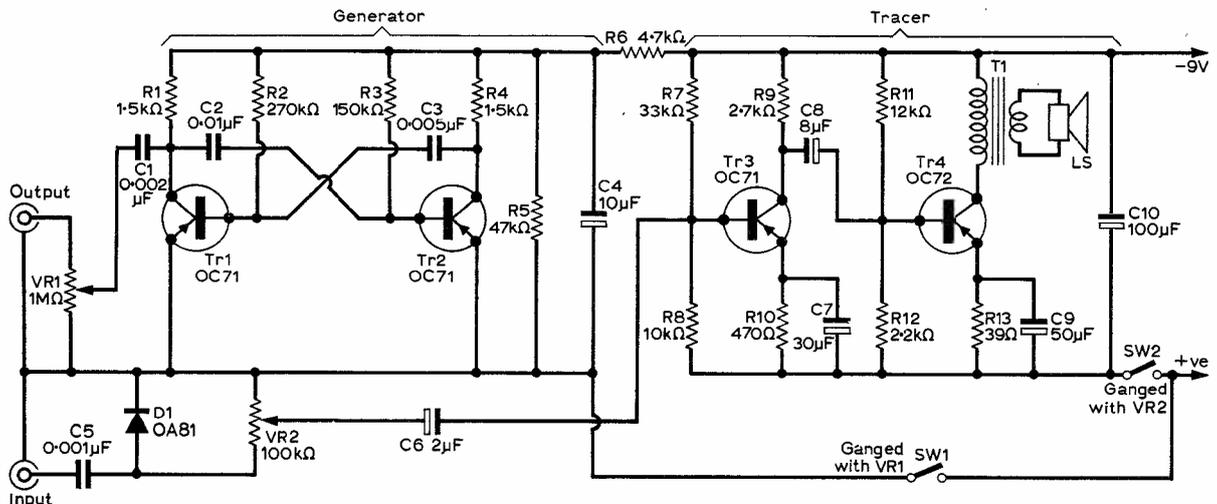


Fig. 1 : Circuit of the Genetracer. The "generator" and the "tracer" are built on separate circuit boards

For example, a signal can be injected at the grid of a valve, and the amplified signal "heard" on the tracer's speaker by connecting the input socket to the anode circuit of the same valve. Thus absence of signal, lack of gain, or distortion arising within the stage under investigation, can be quickly discerned.

Once the faulty stage has been located in this way, voltage and/or resistance checks of all components directly connected thereto will usually show what is amiss.

## Circuit

Referring to Fig. 1, it will be seen that the "generator" portion of the instrument comprises the familiar cross-coupled multivibrator circuit, using Tr1 and Tr2. The "tracer" function is carried out by the D1, Tr3 and Tr4 circuitry.

The instrument is in fact constructed as two separate units, on paxolin component boards, powered from a common 9V battery (type PP3 or similar). The full 9V is not necessary for the multivibrator "generator" and so this part of the circuit is fed from a potential divider network (R6 and R5) giving about 6V.

This has all the advantages of printed circuit wiring, yet is much easier for the amateur constructor to reproduce.

For those who have not previously used this material, it comprises a thin strip of pure copper, protected when bought by a plastic backing which when peeled away leaves the adhesive copper strip ready for fixing to any smooth insulating surface. The copper strip is easily cut, bent, or otherwise shaped, to meet circuit needs.

It is already prepared for soldering, and the leads of the various components are bent over and soldered on with a quick application of hot iron and cored solder in the usual way.

Figures 2 and 3 show the component layouts used in the prototype, and it is recommended that these should be adhered to. The drawings are actual size and, for ease of construction, it is suggested that tracings of these be made. A tracing can then be temporarily fixed to the surface of a paxolin panel, and the drilling of all connecting points (shown by a black dot), and component mounting holes made, using the tracing as a template. Holes,  $\frac{3}{16}$  in. diameter, are required for the mounting of the gain controls VR1 and VR2.

All other holes should be small enough to just accommodate the lead out wires from the various

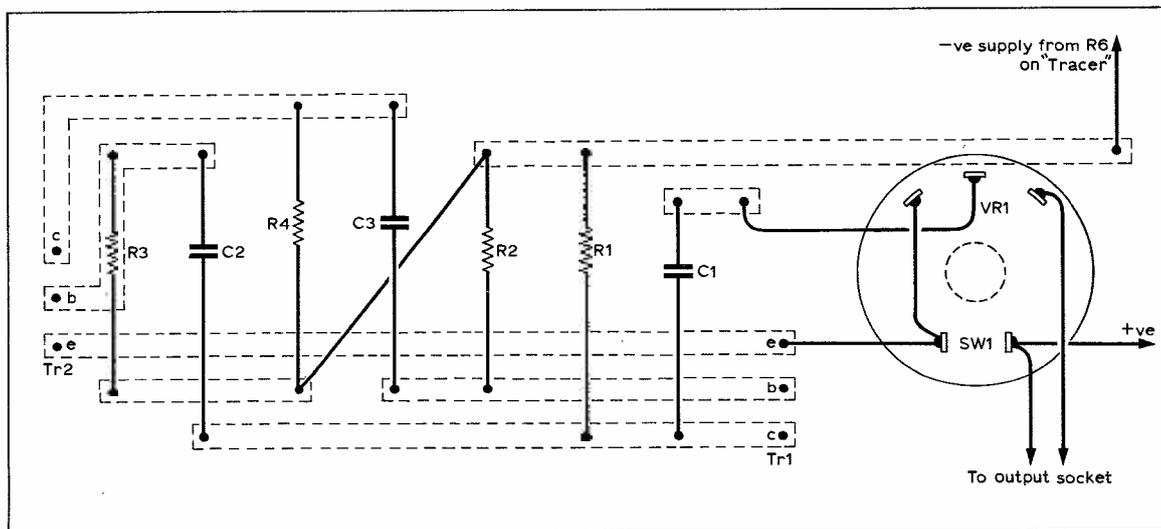


Fig. 2 : Full scale layout of the "generator" circuit board

The circuits of both units are entirely conventional, and standard readily obtainable transistors and components are used throughout. A simple Class A single-ended transistor output stage is used in the "tracer" as a large output is not required.

## Construction

For ease of construction and general neatness of the completed units, the popular method of mounting all components on one side of a  $\frac{1}{16}$  in. thick paxolin panel, with their connecting wires protruding through holes to the other side of the panel, and there connecting them to adhesive "Cir-Kit" copper wiring strips, has been adopted.

resistors, capacitors, etc. Note that the coaxial input and output sockets are mounted on the front control panel (also of paxolin) of the instrument, not on the component panels. Connection to these sockets is thus delayed until the panels have been completed, and fixed to the  $\frac{3}{16}$  in. thick wooden spacers glued to the rear surface of the control panel.

The speaker is also mounted on the control panel and, for neatness, is provided with a small square of "fret" fabric.

The Cir-Kit strips are shown in Figs. 2 and 3 as actually lying on top of the component lead out holes, done for the sake of clarity. Actually, the strips should be affixed so that they run just clear of the holes, the component wires then being bent over at right angles (which helps to anchor them in position) and soldered to the appropriate strips.

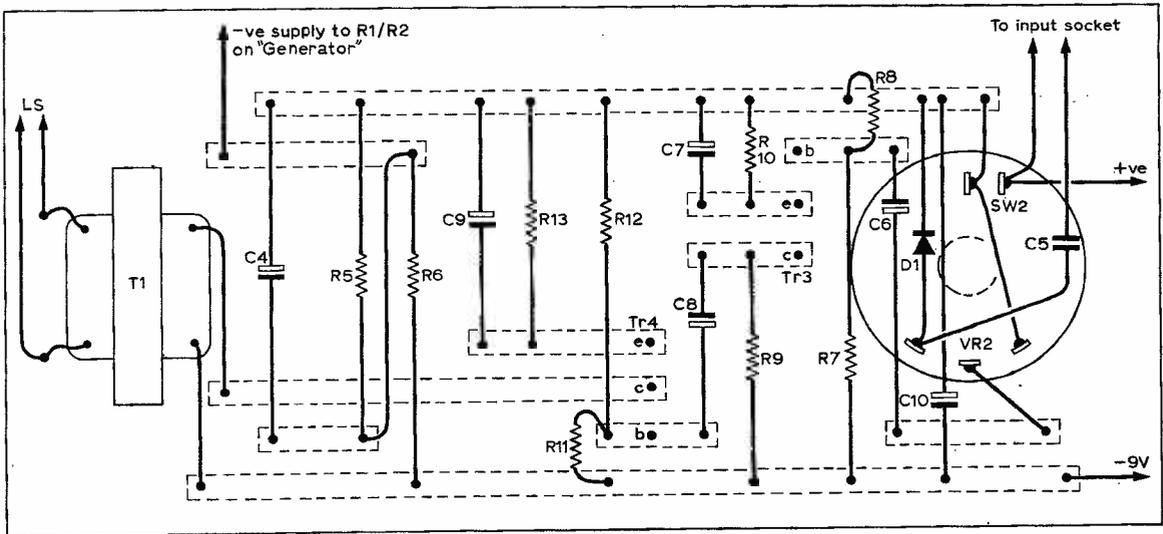


Fig. 3: Layout of the "tracer" circuit board, also full scale

Take care to ensure that the electrolytic capacitors are correctly placed with regard to polarity markings. The transistors should not be soldered into place until all other wiring has been completed on the panels. When soldering the transistor and diode leads take care to use an effective heat sink.

It helps if coloured sleeving is slipped over the transistor leads before connecting them into circuit, a suitable colour code being red for collector, yellow for emitter, and blue for base. Note especially that in the case of Tr3 and Tr4, the relative positions of "b", "c" and "e" are not identical on the component board.

When the two panels have been completed, and checked for correct assembly and wiring, they may be fixed to the spacing strips secured to the control panel by small wood screws. The photograph of the completed assembly shows what is required.

Connect the speaker to the output transformer secondary T1, and connect the input and output sockets to the respective gain controls as shown in Fig. 4.

The battery leads, terminating in a suitable press stud connector to fit the PP3 battery, and composed of red and blue flexible wire, can now be connected. The diagonal interconnection between the tracer and generator panels should also be completed at this stage.

The completed unit is housed in a simple rectangular box of a size to suit the front panel, and about 4in. deep from front to rear. This depth is not required to house the instrument, but rather to provide stability when stood upright on the bench. It is a good plan to fix four small rubber feet at the corners of the base. The actual method of construction and the materials used are left to the discretion of the constructor.

Two lengths of test lead should now be prepared comprising some 12in. to 18in. of TV type coaxial cable, one end of each lead being terminated in a coaxial plug. The other ends should have outer braiding and inner conductor separated for about 6in., and crocodile clips fitted. These form the most convenient means of connecting the instrument leads to the equipment under test.

### Testing

To test the completed instrument, plug the test leads into the input and output sockets, and connect the ends of the test leads together, i.e., braiding to braiding and inner to inner. Switch on both the generator and tracer units and, by adjusting the gain controls, the output from the generator can be clearly heard in the tracer's speaker.

—continued on page 305

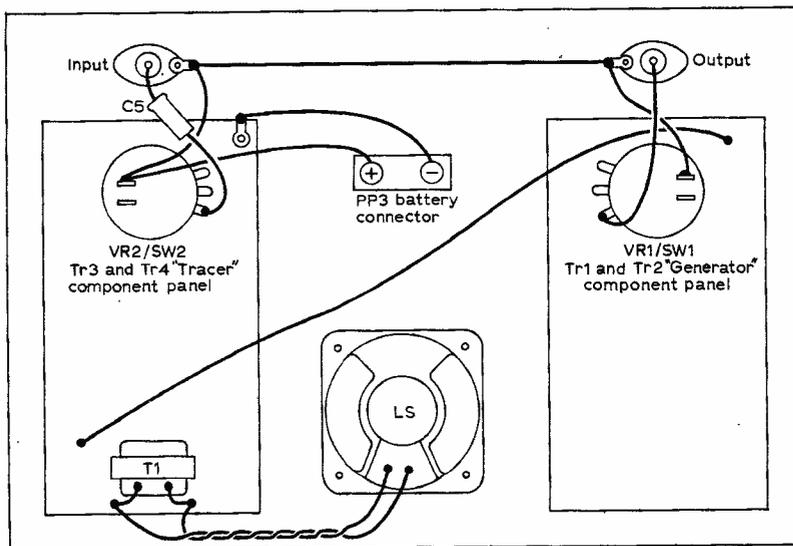


Fig. 4: Interconnection of the circuit boards after mounting in cabinet.

# PROJECT Autumn

Readers of Practical Wireless are invited to submit articles for publication and to compete for the Practical Wireless "Designer's Trophy"



- ### RULES.
1. Articles submitted for the competition should conform to the general style of material published in Practical Wireless and must describe the operation and construction of a piece of radio, audio or test equipment that has been designed and built by the author.
  2. Articles should, preferably, be typed using double spacing, leaving wide margins, and on one side only of each sheet. Circuit diagrams and any other drawings should be on separate sheets and numbered to agree with the text. Author's roughs must be clear enough to permit re-drawing. Component lists must also be separate and laid out to the standard PW format.
  3. Photographs of the equipment are desirable and should be in black and white, sharp and clear. Each photograph should be identified by sticking a piece of paper on the back rather than by writing on the photograph itself.
  4. Components used in the design must be readily available from retail sources.
  5. An entry form, properly completed, must accompany each article submitted. There is no limit to the number of articles submitted by any one author.
  6. Articles must reach the Editor, Practical Wireless, Old Fleetway House, Farringdon Street, London, E.C.4. by the first post on Monday, November 2nd 1970 with the envelope and title sheet clearly marked "Project Autumn". A stamped, self-addressed envelope must accompany each entry.
  7. All entries submitted will be considered by a panel of judges and the Editor's decision on all matters arising will be final. The Editor will require authors of winning entries to submit the equipment to him immediately on request for final assessment by the panel.
  8. Employees and staff of Practical Wireless are not eligible for entry to this competition.
  9. The winner of the competition will receive and retain outright the Practical Wireless "Designer's Trophy 1970". Other prizes will be awarded to the best runners-up. Any article published will be paid for at normal rates.

## ENTRY FORM

## "Project Autumn"

Full Name .....

Address .....

.....

.....

Title of Article .....

.....

If my article does not win a prize I should like it:-


(a) to be considered for publication in the usual way\*

(b) to be returned to me.\*

Signature ..... Date .....

\*delete as required

PA-PW-8

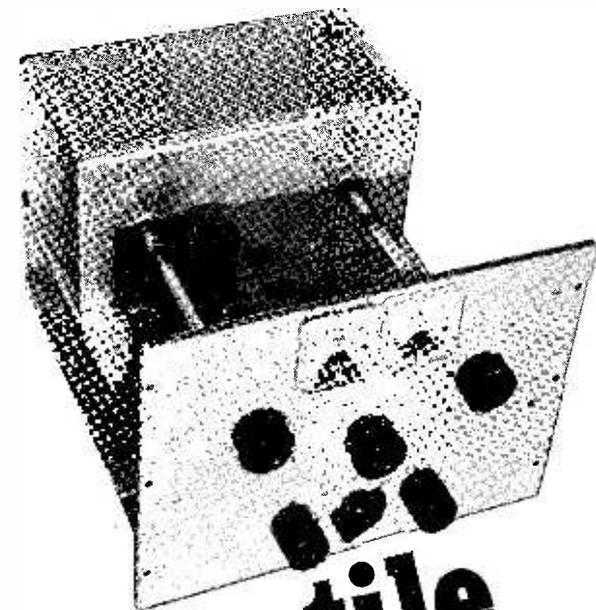

**versatile**


# TRANSMITTER

## BUFFER AMPLIFIER

This is V2, a 5763, and the stage operates as a doubler for 80m, a straight-through amplifier/buffer on 40m, a doubler on 20m, a tripler on 15m, and a doubler for 10m.

In each case S4 selects suitable anode coils, so that the anode circuit can be tuned to the frequency at which transmitter output is to be obtained. This allows the power amplifier V3 to work straight through on all bands.

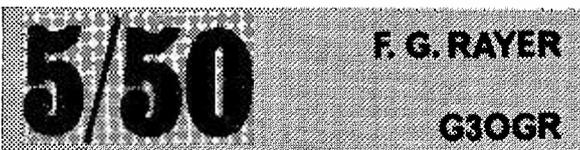This arrangement was found to provide better than 3mA grid drive on all bands, and considerably more on the l.f. bands. The combinations of untuned anode circuit in V1, and frequency multiplication, were found to give good stability on all bands.



**T**HIS transmitter is VFO controlled, and operates on the 80, 40, 20, 15 and 10m amateur bands. A power input of about 40 to 60 watts, according to the h.t. supply, proves very useful, and a single switch selects any band.

Fig. 1 shows the circuit, and the following details should help when checking operation and tuning up.

## VARIABLE FREQUENCY OSCILLATOR

V1, a 6CH6, is a Clapp type oscillator, with the voltage stabilised screen grid acting as a virtual anode for the oscillator circuit. L1 tunes 1.75-1.9MHz, and is selected by S1 and S2, output frequency being doubled for the 3.5-3.8MHz band. C1, with TC1 and the core of L1, allow adjustment of band coverage. The anode circuit of V1 is electron coupled, and is untuned on this band, R4 being the anode load.

For the higher frequency bands, S1 and S2 select L2, which has TC2 and C2, VC1 being the main variable tuning capacitor as before. The fundamental range is now approximately 7.7-3MHz, and this with harmonics allows complete coverage of the 7, 14 and 21MHz bands, and coverage from 28-29.2MHz on 10 metres. As all these ranges are direct harmonics, calibration is simplified.

For 7MHz, R4 provides an untuned anode load. L3 is resonant at about 7.1MHz, and is brought in by S3, for the 14 and 21MHz bands. For 28MHz, L4 is in circuit, and is tuned to about 14.5MHz, so that the output from the anode of V1 is doubled in frequency.

## POWER AMPLIFIER

This is a v.h.f. type power beam tetrode, a 6146, operated at 100mA anode current. This corresponds to 40 watts input with a 400V supply, 50 watts with 500V, and 60 watts with 600V. It has also been used with 300V (30 watts) with excellent results.

Bias is obtained by grid current through R8. Here, 2mA grid current provides 44V bias and normal operation is with about 2mA to 2.5mA grid current. Since lack of grid current can rapidly damage the 6146 the grid meter is permanently in circuit.

When changing frequency, h.t. is applied to V1 and V2 by closing the "Tune" switch, and VC2 is then adjusted for suitable grid current. When this has been done, the 2-pole transmit/receive switch applies h.t. to all stages.

R.F.C.3 with R10 forms a parasitic suppressor. Anode current is shown by the 150mA meter. The switch S5 and tapped coil L10 allow 5-band coverage. VC3 is for anode tuning, and VC4/5 is the output capacitor of the pi-network, and allows the p.a. to be loaded by a range of impedances.

TC3 with L11 forms a series tuned harmonic trap, which in certain circumstances will be useful when interference is being caused to t.v. reception.

## MODES OF OPERATION

The transmitter was built for use with a 30 watt modulator, which permits modulation of V3 anode and screen grid. This is a very trouble-free and satisfactory method, and one which will give excellent results without any special care in adjustment.

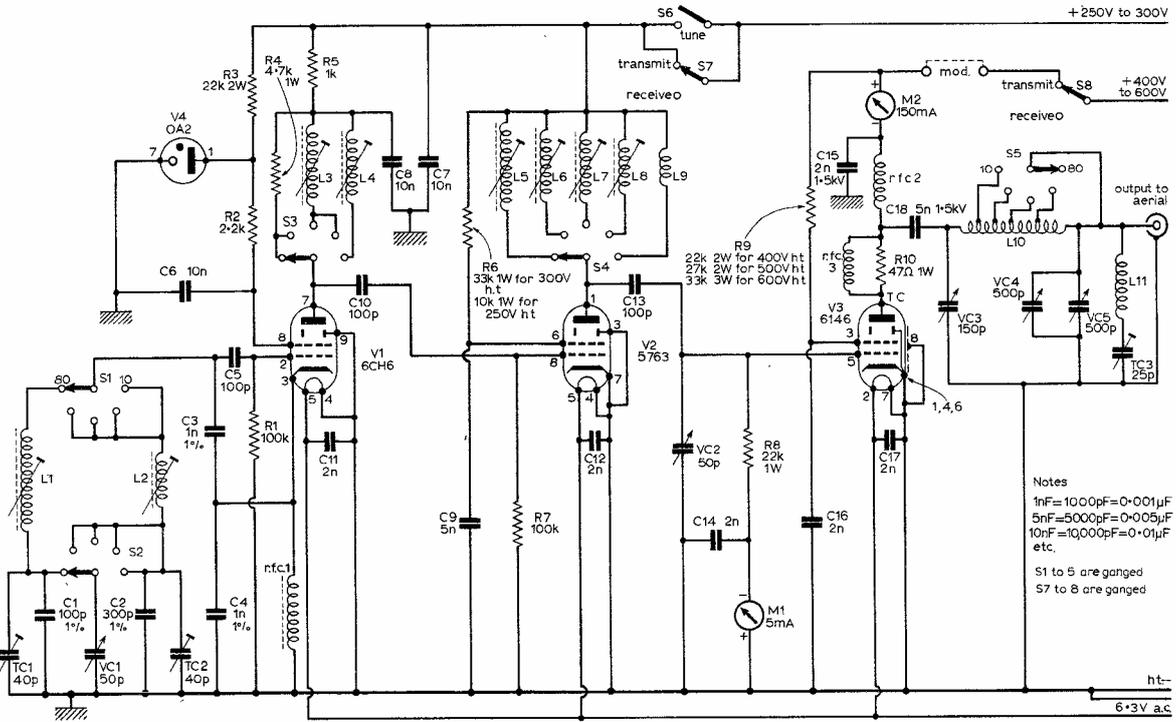


Fig. 1: Complete circuit diagram of the 5-band transmitter.

The connection to R9 can be broken, and screen grid modulation used. This has the advantage that an ordinary audio amplifier, giving about 2-4 watts output, will readily modulate the transmitter but r.f. output is reduced, so correct and full aerial loading is essential, to avoid distortion.

Though the transmitter was intended for telephony working on all bands, cathode and other forms of keying have been found satisfactory for c.w. It is also possible to substitute an inexpensive 807 for the 6146.

### CONSTRUCTION

VC1, C1, C2, TC1 and TC2, with L1 and L2, occupy an enclosed box on top of the chassis, Fig. 2. To simplify metal work, the front and both sides of this box are formed from an 8x2in. universal chassis runner. Segments are cut from each flange 2½in. from the end.

The runner is then bent at right angles at these points, to form a member 3x2½in. L1 and L2 are mounted, and also the ball-drive for VC1. VC1 is fitted to a bracket bolted to the runner.

This assembly is then bolted to the chassis in the position shown in Fig. 2, and is completely wired. Leads pass down through the chassis from L1 and L2, to S1 and S2. VC1 is also wired to S2.

TC1 and TC2 are ceramic trimmers, on brackets bolted to the chassis. A piece of aluminium 4½x3in. is bent to form the coil box top and back, ¼in. forming a flange to bolt to the chassis. This part is attached to the box flanges by self-tapping screws. Holes allow TC1 and TC2 to be reached.

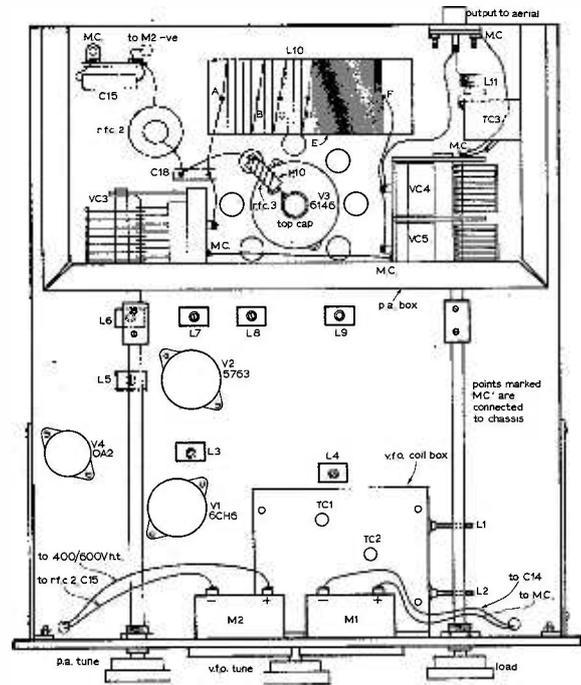


Fig. 2: Plan view of transmitter chassis.

## VFO ANODE CIRCUIT

A universal chassis runner  $11 \times 2$  in. has its flanges cut  $3\frac{1}{2}$  in. from the ends, so that it can be bent into a box  $3\frac{1}{2} \times 3\frac{1}{2}$  in. This is bolted to the chassis and chassis front in the position in Fig. 3, and contains V1 holder, L3, L4, etc.

R.F.C.1 is supported on a tag strip. All wiring associated with S1/S2, C3, C4, C5 and V1 should be stout and rigid. A tag strip also anchors R2 and R5. S3 is wired to select R4, L3 or L4.

C10 is inside this box, and a lead passes through the box to tag 8 of V2. This and R7 are positioned as in Fig. 3. The box is closed by cutting a plate  $3\frac{1}{2} \times 3\frac{1}{2}$  in. and fixing it to the flanges with self-tapping screws.

## BA ANODE CIRCUIT

Coils L5/L6/L7/L8 and L9 are selected by the wafer S4, and are tuned by VC2. C7 should be on short leads from VC2 to L9, while C13 is directly connected from S4 to V3, with a short wire to VC2. A coupler and long shaft operate VC2.

S4 is arranged so that very short leads are possible to the h.f. range coils, especially L8 and L9. All other wiring needs to be reasonably short and direct.

## POWER AMPLIFIER STAGE

Cathode and r.f. circuits in this stage should be wired with 16 s.w.g. or stouter conductors. Tags 1, 4, 6, 7 and 8 are well earthed, see Fig. 3. A tag strip supports R8 and C14, a lead passing from here to the grid current meter. A tag strip near the rear of the chassis is used for h.t. and other connections, and allows easy disconnection of R9 for screen grid modulation.

The p.a. and anode circuit components occupy a box  $8\frac{1}{2} \times 4\frac{1}{2} \times 4$  in. high, Fig. 2. This was purchased ready made (see component list). A number of holes are punched in the chassis around the holder for the 6146. The box is finally closed with perforated metal or similar material, holes being punched in this for TC3 and the co-axial output socket.

VC3 and VC4/5 are joined by a stout lead, and earthed to the chassis. R.F.C.3 is 5 turns of 18 s.w.g. wire, wound to  $\frac{3}{8}$  in. diameter, and stretched to occupy about  $\frac{1}{2}$  in. R10 is in the centre of R.F.C.3, and both are soldered directly to the anode cap clip of the 6146. All leads to VC3, C18 and L10 should be very stout and short.

A tag strip holds R.F.C.3. The output socket is bolted to a bracket in contact with the chassis, and is wired to VC4/5. TC3 is held with a small bracket and L11 is fitted directly between TC3 and the output socket, as shown.

## INDUCTORS

L1 is a medium wave type dipped coil with unwanted windings and some turns removed until 1.75MHz is reached with VC1 closed. L2 is 11 turns of 24 s.w.g. enamelled wire close-wound on a  $\frac{1}{2}$  in. diameter former. L3 is 50 turns of 32 s.w.g. enamelled wire, and L4 is 17 turns, both on  $\frac{1}{2}$  in. diameter formers.

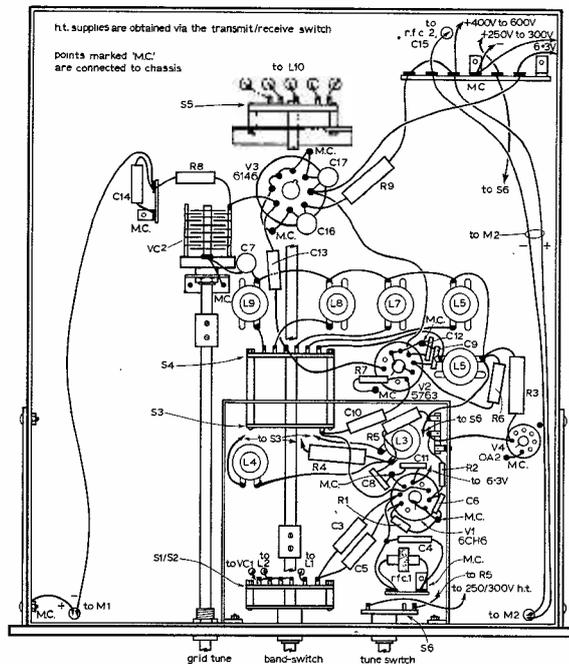


Fig. 3: Underneath the chassis showing main wiring.

L5 has 65 turns of 34 s.w.g. enamelled wire, and L7 has 14 turns of 32 s.w.g. all close-wound on  $\frac{1}{2}$  in. diameter cored formers. L8 has nine turns of 26 s.w.g., spaced by the wire diameter, and L9 has eight turns of 26 s.w.g., also spaced by the wire diameter. Both formers are  $\frac{1}{2}$  in. diameter, and L8 has a core, but not L9. If necessary, the inductance of L9 can be reduced by spreading the turns.

L1 should tune from 1.75-1.9MHz, with a trifle to spare, and L2 from about 7.7-3MHz. This can be checked by applying h.t. to V1 only, with R4 in circuit, and listening for the v.f.o. signal with a receiver. Final calibration is by adjusting the cores of L1 and L2, in conjunction with trimmers TC1 and TC2. The v.f.o. should be adjusted in conjunction with the 100kHz harmonics from a crystal marker when all construction is finished.

L3, with stray circuit capacitances, should be tunable to 7MHz. This can be shown by grid current through R7 or R8, or by using a wavemeter. L4 is similarly tunable to 14MHz. When the transmitter is tested, the cores of L3 and L4 can be rotated slightly for maximum p.a. grid current around the middle of the respective bands.

L5 should tune to about 3.6MHz with VC2 about half closed. L6 is resonant at about 7MHz with VC2 about one-third closed.

The cores of both L7 and L8 are adjusted so that 14MHz and 21MHz can be tuned with VC2 only slightly closed. No core was used with L9, and the winding is adjusted so that VC2 is almost at minimum capacitance at 29MHz.

If L8 and L9 have insufficient inductance, and resonance on 21 and 28MHz bands is only obtained with VC2 near maximum, grid current will be reduced. If the coils are adjusted as explained, it will not be possible to tune to wrong harmonics with VC2.

A grid-dip meter should be used to check that each anode coil L5 to L9 operates on the correct harmonic, when first aligning the buffer-amplifier, with h.t. off. Since V1 provides 7MHz output for 14MHz and 21MHz, and 14MHz output for 28MHz, wrong tuning of the anode circuit of V2 is unlikely.

Final adjustments to the cores of these coils must be made by observing grid current on the grid current meter, V3 being in position, but anode and screen grid voltages being removed from this stage.

## TANK COIL

This is wound on a paxolin tube  $3\frac{1}{2}$  in. long and  $1\frac{1}{2}$  in. in diameter subsequently mounted on 6BA bolts with extra nuts, to be  $\frac{3}{4}$  in. clear of the chassis. The ends A and F, and tappings B, C, D, and E, Fig. 2, are on the underside of the coil, so that leads to wafer S5, Fig. 3, are short.

Some 16 s.w.g. wire is anchored at A, and four turns are wound with a pitch of 8 turns-per-inch. The wire is taken along to allow a  $\frac{1}{4}$  in. space, and two more turns are wound. After another  $\frac{1}{4}$  in. space, three turns are wound, and the wire is anchored at D. Stout leads are securely soldered at B and C. The coil is finished by winding 22 turns of 20 s.w.g. wire from D to F, these turns occupying  $1\frac{1}{4}$  in. Tapping E is a short loop seven turns from D.

F is connected directly to S5 rotor tag. B, C, D and E are connected so that turns in circuit are as follows: 10 metres, 4; 15m, 6; 20m, 9; 40m, 16; 80m, whole coil.

## POWER SUPPLIES

V1 and V2 draw current from a separate h.t. supply of around 250/300V. A 230V supply was found to give a minimum grid current of 3mA on all bands, with R6 reduced to 10k $\Omega$ . The supply should be able to provide 60mA, so a receiver-type power pack is thus generally suitable.

The h.t. for V3 can depend somewhat on the modulator power or available supplies. For high-level modulation, an audio output of about one-half the p.a. input is required. Modulator circuits actually used had 2 $\times$ 6V6 for 15W of audio, 2 $\times$ 6L6 for 20W, and 2 $\times$ 807 for 30W.

For screen grid modulation, R9 is disconnected from the positive line, and receives modulated h.f. from a small amplifier. A single 6BW6 or similar output stage is quite adequate. The p.a. anode is then supplied from a higher voltage source—preferably 500/600V.

## BANDSWITCH

S1/S2 is a 2-pole 5-way wafer and S3, S4 and S5 are each single-pole 5-way wafers. S3 and S4 are mounted on the box, Fig. 3, with long bolts and spacers. S5 is fixed to a bracket near V3 and immediately under L10.

The shaft is a long insulated  $\frac{1}{4}$  in. diameter rod (see component list) with flats filed to engage with the holes in the rotating part of the wafers. A hole in the rear of the chassis allows this rod to be pushed in from the back, and through each wafer. A coupler connects it with the metal shaft of S1/S2.

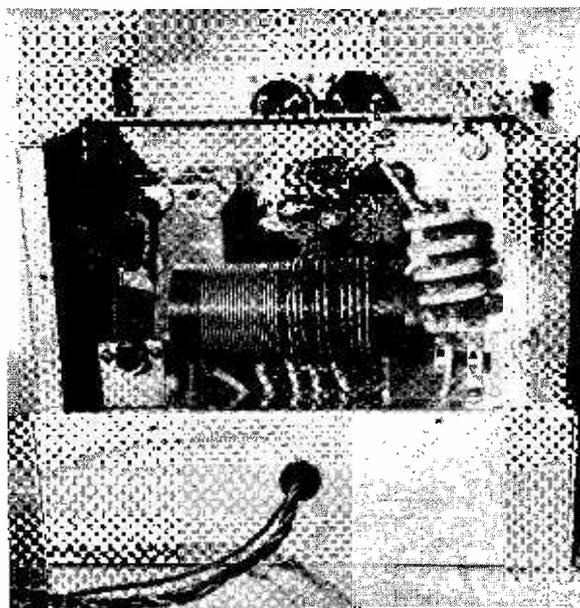


Fig. 4: View of p.a. compartment at rear of chassis.

A switch in which tags are progressively shorted all round is often used for a pi-tank of the type shown in Fig. 1. R.F. output was measured on all bands with such a wafer, and again with an ordinary single-pole 5-way wafer, and no measurable difference could be observed. In view of this, the ordinary 5-way wafer seems suitable.

## FUNCTION SWITCHING

The "Tune" switch applies h.t. to V1/V2 only, to allow adjusting transmitter frequency, and tuning for grid current. The 2-way T/R switch applies h.t. to both V1/V2 and to V3. This was arranged by having the T/R switch on the power-pack/modulator.

Should the high voltage supply be from a separate h.t. transformer, h.t. may be taken off the p.a. and modulator valves by placing an h.t. on/off toggle switch in the mains supply to this transformer. (The transformer must then be for h.t. supply only, and not include rectifier, heater or other supplies.)

The actual method of h.t. switching is not important, provided h.t. can be applied to V1 and V2 separately, with V3 off. It should not be possible to apply h.t. to V3, with V1 and V2 inoperative.

If the T/R switch has extra poles, these may be used to operate an aerial change-over relay, or to switch the aerial directly from receiver to transmitter. With the latter method, switch wiring should be done with co-axial cable, and the receiver aerial input should be earthed on transmit, to reduce stray r.f. at the receiver.

## OPERATION

V3 anode circuit must always be tuned to resonance, by VC3, as shown by a dip in anode current. A check is most readily made on 80m, with an artificial load such as a 60 watt domestic lamp plugged

into the output socket or connected across VC4/5.

With h.t. on V1/V2 only, VC2 is rotated for about 2.5mA grid current. VC4/5 is at maximum capacity. H.T. is applied to V3, and VC3 at once adjusted for minimum anode current. This minimum is raised by reducing VC4/5, simultaneously re-adjusting VC3 for minimum current. When this minimum has reached 100mA the lamp should light brightly.

Working on the other bands is similar, except that tuning becomes more critical. For the h.f. bands, VC3 should be at almost minimum capacity.

R.F. output for screen grid modulation will be much less than with high level modulation, and the p.a. must be loaded in the manner described until the anode current dip found with VC3 is very flat.

## ★ components list

### Resistors:

R1	100kΩ ½W	R7	100kΩ ½W
R2	2.2kΩ ½W	R8	22kΩ 1W
R3	22kΩ 2W	R9	22kΩ 2W*
R4	4.7kΩ 1W		27kΩ 2W*
R5	1kΩ ½W		33kΩ 3 E*
R6	33kΩ 1W	R10	47Ω 1W
	(10kΩ for 250V)		* see text

### Capacitors:

C1	100pF 1% S.M.	C10	100pF mica
C2	300pF 1% S.M.	C11	0.002μF 500V disc
C3	1000pF 1% S.M.	C12	0.002μF 500V disc
C4	1000pF 1% S.M.	C13	100pF mica
C5	100pF 1% S.M.	C14	0.002μF 500V disc
C6	0.01μF 500V disc	C15	0.002μF 1.5 kV
C7	0.01μF 500V disc	C16	0.002μF 500V disc
C8	0.01μF 500V disc	C17	0.002μF 500V disc
C9	0.005μF 500V disc	C18	0.005μF 1.5kV
TC1	40pF ceramic trimmer		
TC2	40pF ceramic trimmer		
TC3	25pF double spaced variable		
VC1	50pF air spaced variable		
VC2	50pF air spaced variable		
VC3	150pF double spaced variable		
VC4/5	2 x 500pF ganged variable		

### Switches:

S1/2	2 pole 5 way wafer	} 'Bandswitch'
S3/4/5	1 pole 5 way wafer	
S6	Single pole single throw rotary. 'Tune'	
S7/8	2 pole 2 way "T/R Switch"	

### Valves:

V1	6CH6 with B9A holder and screen.
V2	5763 with B9A holder and screen.
V3	6146 with octal holder, low-loss or ceramic.
V4	OA2 with B7G holder.

### Metalwork:

Chassis 10½ x 9 x 2½in. Type K (H. L. Smith & Co.)  
 Chassis 8½ x 4½ x 4in. Type P (H. L. Smith & Co.)  
 2 Panel brackets 4 x 4in. Type C (H. L. Smith & Co.)  
 Panel, 10 x 7in. (H. L. Smith & Co.)  
 Universal chassis runner 8 x 2in. (Home Radio)  
 Universal chassis runner 11 x 2in. (Home Radio)  
 Perforated metal 9 x 8½in.  
 Sheet metal for covers, etc.

### Miscellaneous:

R.F.C.1. 2.5 mH midget cored choke.  
 R.F.C.2. 2.6mH choke, (Denco RFC9).  
 R.F.C.3. and L1-11 see text.  
 Panel meters, 0-5mA and 0-150mA.  
 Slow motion drive, knobs, 3 panel bushes, 3 shaft couplers, ½in. insulated rod.  
 Tag strips, co-axial socket.

Switching should be so arranged that screen voltage cannot be applied to the 6146 unless anode voltage is also present.

It is essential that the power amplifier is not left operating off-tune, or with insufficient grid current, as this will rapidly damage the valve.

The transmitter is best operated into a low impedance load, such as a multiband dipole with 75 ohm feeder, or a tuner feeding an all-band aerial.

## HARMONIC TRAP

This is a series-tuned acceptor, using L11 and TC3. A very closely spaced midget capacitor is not suitable except when working into low impedances.

L11 is best adjusted with a grid-drip meter, so that TC3 gives resonance on the particular channel required. L11 will usually be from about 5 turns ¼in. in diameter and ½in. or so long, up to 14 turns close-wound ¼in. in diameter. It can be 16 s.w.g. wire, self-supporting.

The best method of adjustment is to operate the transmitter into a dipole or 75 ohm non-reactive load, adjusting VC4/5 for the correct p.a. input. With power off and TC3 about half closed, check the resonant frequency with the grid dip meter, and adjust L11 as required. Then with power on, rotate TC3 while observing any interference to t.v. reception. Actual trouble in this direction depends on the siting and type of aerials, efficiency of earthing, strength of the t.v. signal, and other factors.


## CALIBRATION

The ball drive is fitted with a transparent cursor and hair-line. Calibration on 3.5-3.8MHz is for the 80m band only. The 5.5, 6.5 and 7.5MHz points can be found by listening to the second harmonic of the v.f.o. on the receiver, beating with 100kHz harmonics from a 100kHz crystal.

Calibration on the 20, 15 and 10m bands is obtained by direct multiplication from 40m, so these four bands are marked simultaneously. L2 core and TC2 are adjusted for suitable coverage, with 7MHz obtained when VC1 is almost fully closed. This is also 14, 21 and 28MHz. In the same way, 7.1MHz corresponds to 14.2MHz, 21.3MHz, and 28.4MHz. ■
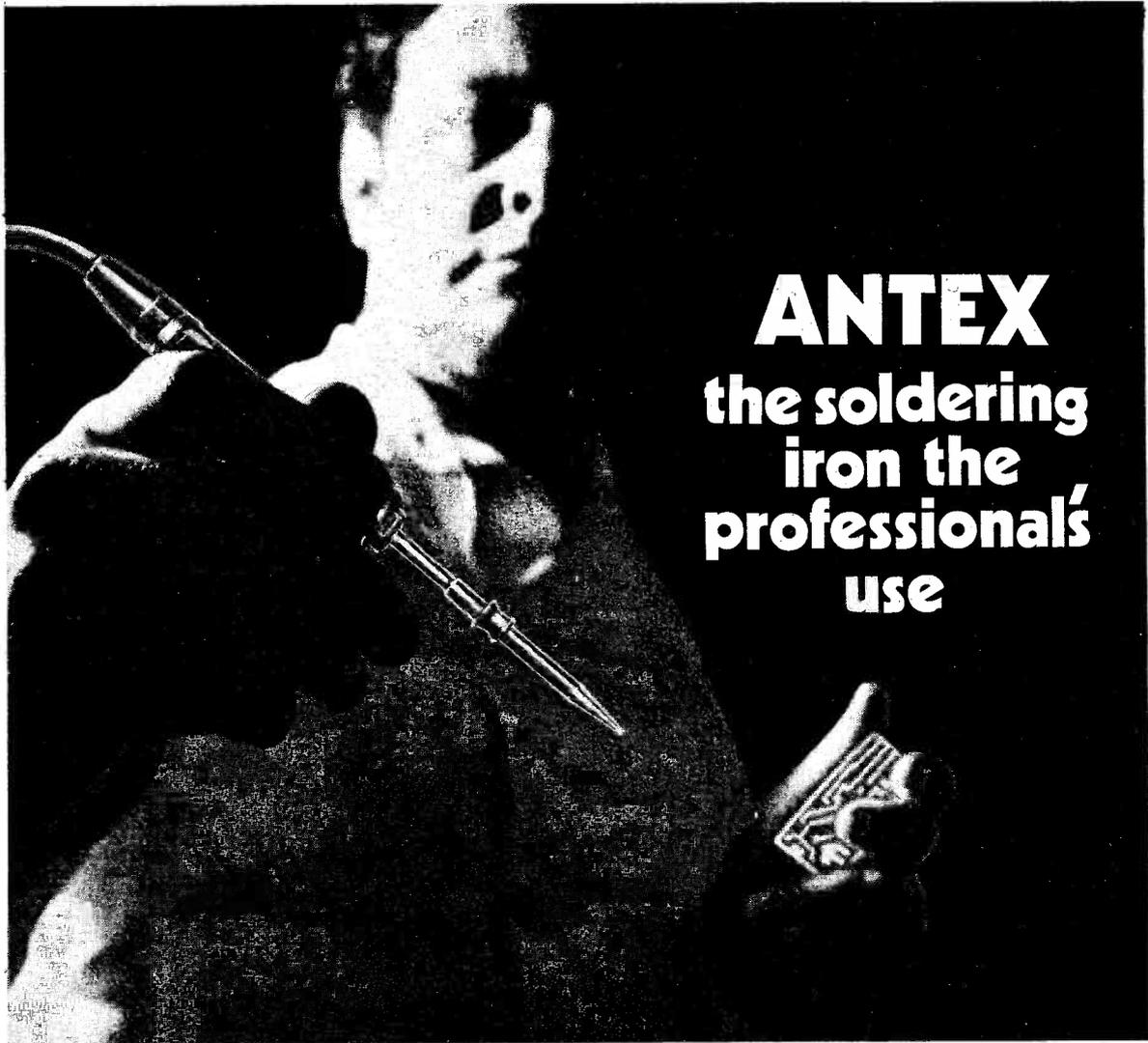
## LATE PUBLICATION OF PRACTICAL TELEVISION

We apologise to readers of our sister magazine Practical Television for the late appearance of the June and July issues, due to a dispute at the printers. We are doing our best to publish the August issue on time but this may also be a little late.



# ANTEX

## the soldering iron the professionals' use



6-16 watts. Fitted 3/32" bit for miniature work up to production level. Interchangeable spare bits 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/6



2-28 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 3/16" and 1/8" available. For 240, 220, 110 volts. From 38/6




15-25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production work. For 240, 220, 110, 24 or 12 volts. From 38/6



7-40 watts. Fitted 3/16" bit. Interchangeable bits 1/4", 3/16", 1/8" and 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6. Spare bit elements for all models and voltage units readily available from stock.

### Complete precision soldering kit

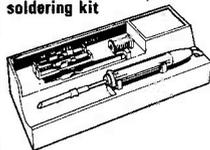

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box"—contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits 1/8", 3/16".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**



### Model CN 240/2 15 watts - 240 volts

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

**31/6**



### PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon. Telephone: Plymouth 67377/8. Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

PW8

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
 THE VALVE SPECIALISTS Telephone 01-722 9090  
 SAVE POSTAL COSTS! CASH AND CARRY BY CALLERS WELCOME

0A2	5/9	6BA6	4/6	6P26	12/-	12AV6	5/6	30P4	12/-	AC2PEN/	DL510	9/6	
0B2	6/-	6BE6	4/6	6P28	25/-	12AX7	4/6	30P4MR		DD	DM70	6/6	
0Z4	4/6	6B16	7/6	6Q7	6/6	12AY7	9/9		17/8	AC6PEN/7/6	DM71	7/6	
1A3	4/6	6B16	6/6	6Q7G	6/6	12BA6	6/-	30P12	13/9	AC/PE/5	DW43506/6	6/6	
1A5	5/-	6R05	4/6	6R7	11/-	12BB6	5/-	30P19	12/9	AC/PE/7	DW45008/8	8/6	
1A7G	7/6	6BQ7A	7/-	6R7G	7/-	12BH7	6/-	30P11	13/9	AC/PE/10	DY8	6/6	
1C5	4/6	6BR7	15/6	6SA7GT	7/-	12BL	17/-	30P11	12/9		DY8	6/6	
1D5	7/6	6BR8	12/6	6SA7M	7/-	127GT	6/6	30P113	15/6	AC/TH110	EM84	6/6	
1D6	9/6	6BS7	25/6	6S7GT	6/6	12K5	10/6	30P114	15/6	AC/TP	EM85	6/6	
1FD1	6/6	6BZ6	14/3	6S7GT	6/6	12K7GT	6/6	30P115	15/6	AC/VP/210/6	EM87	7/6	
1FD9	4/6	6BWT	13/6	6SH7	3/-	12QGT	6/-	35A3	10/-	AL60	EM87	7/6	
1G6	6/-	6BZ6	6/-	6S7J	6/6	12SA7GT	6/-	35A5	15/-	ARP	EM87	7/6	
1H5GT	7/-	6C6	3/9	6SK7GT	4/6	8/-	35D5	12/6	ATP4	2/3	E192CC22/6	EM87	7/6
1L4	2/6	6C9	14/6	6SN7GT	4/6	128C7	5/-	35L6GT	8/6	AZ1	EA50	1/8	
1LD5	6/-	6CD6	23/-	6SQ7GT	7/6	128G7	4/6	35W4	4/6	AZ31	EA76	13/-	
1L5	8/-	6C6H	7/-	6U4GT	12/-	128H7	3/-	35Z3	10/-	AZ41	EAL31	3/-	
1NG6T	7/9	6CL9	8/6	6U7G	10/6	128J7	4/6	35Z4GT	4/9	B86	EAL31	3/-	
1R5	5/6	6CWT	12/6	6V6G	8/6	12SK7	6/6	35ZGT	6/-	CL33	EAL31	3/-	
1R4	4/6	6D3	7/6	6V6GT	6/6	12SQ7GT	6/6	50B5	7/6	CV6	EAL31	3/-	
1R5	4/6	6D3	3/-	6X4	4/3	14H7	6/6	50C5	6/3	CY1C	EA42	10/6	
1U4	5/9	6F1	12/6	6X5GT	5/-	14H7	15/-	50C6	6/3	CY1C	EA42	10/6	
2D21	6/6	6E6	12/6	6Y7G	10/6	19AQ5	4/9	50D6GT	9/-	D63	EA42	10/6	
3A5	10/-	6E6G	5/-	7B6	12/6	19H1	4/9	72	6/6	D77	EA42	10/6	
3B7	5/4	6E12	3/3	7B7	7/-	20D1	13/-	85A2	8/6	DC93	EA42	10/6	
3D6	3/6	6F13	3/6	7C6	6/-	20D4	20/5	85A3	8/6	DAF91	EA42	10/6	
3Q4	7/6	6F15	10/6	7E8	12/6	20P2	14/6	90A9	8/6	DAF96	EA42	10/6	
3Q5GT	6/-	6F18	7/6	7H7	5/6	20L2	20/6	90AV	8/6	DCC90	EA42	10/6	
3S4	5/9	6P23	14/3	7R7	13/-	20P1	17/6	90CG	34/6	DD4	EA42	10/6	
3V4	6/3	6P24	13/6	7V7	5/-	20P3	18/6	90CV	33/6	DF3	EA42	10/6	
5R4G	10/6	6E25	13/6	8P3W6	7/-	20P4	18/6	90C1	16/6	DF81	EA42	10/6	
5U4G	5/6	6P28	14/6	8D7	15/6	20P5	20/6	150B2	14/6	DF96	EA42	10/6	
5V4G	7/6	6P32	3/-	10C1	25/-	25L6GT	5/6	150C2	5/9	DF97	EA42	10/6	
5Y3GT	5/6	6H6GT	3/-	10C2	10/-	25Y5	6/-	201	20/6	DH63	EA42	10/6	
5Z3	9/-	6J5G	3/9	10D1	8/-	25Y6	8/6	302	16/6	DH76	EA42	10/6	
5Z4G	7/-	6J6	3/9	10D2	14/7	25Z4G	6/-	303	16/6	DH77	EA42	10/6	
6J0L2	12/-	6J7G	4/9	10F1	15/-	25Z5	8/-	305	16/6	DH83	EA42	10/6	
6A8G	6/6	6J7GT	6/6	10F2	15/6	25Z6	8/6	306	16/6	DH101	EA42	10/6	
6AC7	3/6	6K7G	2/6	10F8	7/-	30C1	6/6	807	11/9	DH107	EA42	10/6	
6AG5	4/6	6K7GT	4/6	10L1D110	11/6	30C15	13/-	956	2/-				
6AK5	5/6	6K8G	4/6	10P13	13/6	30C17	18/-	1821	10/6	DK32	7/3		
6AK6	6/-	6L1	19/6	10P14	20/-	30C18	14/-	5763	10/6	DK40	10/6		
6AL5	2/3	6L6GT	7/9	12A6	12/6	30F5	16/-	6060	5/6	DK91	5/6		
6AM3	2/6	6L7GT	1/6	12A8	7/6	30FL1	13/9	7193	10/6	DK92	9/6		
6AQ3	6/6	6L7G	6/6	12AB6	12/6	30FL2	15/6	7475	14/6	DK96	9/6		
6AR2	2/6	6L19	27/6	12AB6	12/6	30FL2	15/6	A1834	20/6	DL3	6/6		
6AT6	4/6	6LD20	9/6	12A7E	4/6	30FL14	14/6	A2134	19/6	DL35	4/9		
6AU6	5/-	6N7GT	6/6	12A7J	3/9	30L1	6/6	A3042	15/6	DL92	5/9		
6AV6	5/6	6P1	12/-	12A7U	4/9	30L15	13/9	AC2PEN		DL94	5/9		
6B8G	2/6	6P25	12/-	12A7V	4/6	30L17	15/6		19/6	DL96	7/-		

ECX82	4/6	EL33	12/-	KT61	12/-	PCL85	9/-	R18	10/-	U19	34/6	
ECX83	4/6	EL34	10/6	KT63	5/-	PCL86	8/6	R19	7/6	U22	7/9	
ECX84	6/6	EL37	17/3	KT66	17/3	PCL89	15/6	R20	11/9	U26	13/-	
ECX85	5/6	EL41	11/-	KT74	12/6	PEN36C15	15/6	R22	7/6	U26	11/6	
ECX86	8/-	EL42	10/6	KT76	12/6	PEN45	7/-	RK34	7/6	U31	9/-	
ECX88	7/-	EL41	10/-	KT88	34/-	PEN46DD	12/6	SP42	12/6	U33	29/6	
ECC189	9/6	EL33	7/6	KTW6112/6			15/-	SP61	8/3	U35	16/6	
ECC80412/-	EL34	4/9	KTW6212/6			PEN46	4/-	TH4B	10/-	U37	34/11	
ECC807	27/6	EL35	8/-	KTW63	6/-	PEN46DD		TH233	7/-	U45	16/6	
ECC809	6/6	EL36	8/6	L63	3/9			TR290	6/6	U47	15/6	
ECC82	6/6	EL91	4/6	LN152	7/6	PEN4A119/6		UAB380	6/6	U49	11/9	
ECC86	9/-	EL95	5/3	LN309	10/-	PLS/DD		UAF42	10/3	U50	6/6	
ECC804	EM80	7/6	LN319	13/9			4020	17/6	UB41	6/6	U52	5/6
ECC812	EM81	7/6	LN339	13/9	PFL20011/9				UB41	9/6	U76	4/3
ECC812/6	EM84	6/6	LZ329	6/6	P633	19/6			UCB81	7/6	U78	4/3
ECC85	5/9	EM85	11/6	M162	12/6	L36	9/6		UCB80	5/9	U107	18/3
ECC87	EM87	7/6	M16014/9		PL31	19/6			UCB80	5/9	U191	12/6
ECC81	5/9	EY81	7/6	MHL4	12/6	PL31A	10/6		UBL21	9/6	U251	14/3
ECC83	8/-	EY81	7/6	MHLD612/6		PL82	6/6		UC92	5/6	U281	8/-
ECC84	7/6	EY83	11/6	MUL2/144/-		PL83	6/6		UCC84	8/-	U282	8/-
ECC80	7/6	EY84	10/-	MX40	12/6	PL84	6/6		UCC85	7/3	U301	11/-
ECC82	6/6	EY86	6/6	N78	40/3	PL302	12/6		UCF80	8/3	U329	14/6
ECC83	5/9	EY87	6/6	N166	27/10	PL500	13/6		UCF21	9/6	U403	6/6
ECC84	12/-	EY88	8/6	N308	17/6	PL504	13/6		UCF40	12/6	U404	7/6
ECC85	11/-	EY91	3/9	N339	25/-	PL505	28/9		UCH81	6/6	U501	19/6
ECC86	8/-	EZ35	5/-	P61	10/6	PL508	27/10		UCL82	7/6	U4200	7/6
ECC1800	EZ40	7/6	PABC80	7/3	PL509	28/9			UCL83	10/6	VP4B	10/6
EZ41	8/6	PC86	10/3	PL502	15/-	UF41	10/6		VP13C	7/6		
EZ20	4/6	PC88	10/3	PM34	7/9	UF42	9/6		VP41	7/6		
EZ21	4/9	PC85	9/3	PS32	10/6	UF80	6/9		VR75	24/6		
EZ30	4/3	PC97	8/6	PS31	10/6	UF85	6/9		VR105	6/6		
EW45006/6	PC90	7/6	PS30	6/6	UF86	9/6			VR150	6/6		
GZ30	7/6	PC84	6/3	PI81	5/3	UF89	6/9		VR61A	7/6		
GZ32	9/6	PC85	6/6	PI82	5/3	UL41	10/6		VU111	7/3		
GZ33	12/6	PC88	9/3	PI83	5/9	UL46	12/6		VU120	12/6		
GZ34	10/6	PC89	6/6	PI84	6/6	UL34	6/6		VU120A12/6			
GZ37	14/6	PC189	10/6	PS301	12/6	UM80	6/6		VU135	7/6		
HAB380	6/6	PC80	6/6	PS302	7/6	URIC	10/6		W76	6/9		
HL41DD	PC82	6/6	PS301	6/9	US5	7/6			W101	26/2		
HL42DD	PC82	6/6	PZ30	9/6	US8	14/6			W107	8/6		
HL43DD	PC86	12/9	QV0310	10/6	UU9	7/6			W229	12/6		
HL44DD	PC86	12/9	QV0310	10/6	UX12	4/9			X41	10/6		
HN309	27/6	PCF290	13/3		Q8750	24/-			UY1N	9/6	X61	5/9
HVR2	10/6	PCF801	7/-		Q8750/15	12/6			UY21	9/6	X65	10/6
HVR2A10/6	PCF802	9/6			RS159/15	12/6			UY41	7/6	X66	10/6
IW3	5/6	PCF805	14/6						UY85	5/9	X101	30/6
1W4/350	5/6	PCF806	11/6						U10	9/6	XE3	25
1W4/500	6/6	PCF808	14/6						R10	15/6	U12/14	7/6
KT2	5/-	PCF200	12/3						R11	19/6	U16	15/6
KT8	6/6	PCF2	7/3						R16	34/11	U17	5/6
EL190	7/6	KT41	19/6						R16	34/11	U17	5/6
EL32	3/6	KT44	20/6						R17	17/6	U18/20	10/6

All goods are new and subject to the maker's guarantee. We do not handle manufacturers' seconds, nor rejects, which are often described as "new and tested" but have a limited and unreliable life. Business hours Mon.-Fri. 9-5.30 p.m. Sats. 9-1 p.m. Terms of business. Cash with order only. Post/packing 6d. per item. Orders over 25 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 6d. extra. Complete catalogue of valves, transistors and components with conditions of sale, price list, post free. No enquiries answered unless S.A.E. enclosed for reply.

## Kinver for Components

SILICON TRANSISTORS FOR HIGH QUALITY EQUIPMENT							
BC107	3/3	BD123	24/3	TIP32A	23/-	2N3055	15/9
BC108	3/3	BDY20	24/3	TIR44	1/9	2N3702	3/3
BC109	3/3	BF184	7/6	TIR49	2/6	2N3703	3/3
BC158	7/6	BF194	7/6	TIR50	3/9	2N3704	3/9
BC182L	3/-	BFX29	9/6	2N696	4/6	2N3705	3/4
BC183L	3/-	BFX44	9/6	2N707	4/6	2N3707	3/4
BC184L	3/-	BFX85	8/6	2N706	3/-	2N3708	2/5
BC212L	3/9	BFY50	4/6	2N1132	10/9	2N3819	7/9
BC213L	3/9	BFY51	4/6	2N2906	13/-	2N3820	15/9

# ELECTRONIC metronome

M. WALLIS



**T**HE project described here has a number of uses. First, it will operate as a conventional metronome, that is it can be used to provide the time for playing musical instruments. It may also be used as a short-duration timer or in a situation when using a clock is impractical such as in a dark-room. A similar circuit has been used by the author as a bird scarer; after two years of being without a single ripe cherry from a tree in the garden, a more powerful version was waterproofed and placed at the foot of the tree. A healthy click every few seconds succeeded in keeping the crop intact.

It is possible to build a cheaper metronome than the one described here using one PNP and one NPN transistor (such a circuit was described in *Take 20 No. 3, Practical Wireless, July 1969*) but this type, although it has several uses, suffers from inaccuracy due to the beat being dependent on the supply voltage and to a lesser extent on the ambient temperature. The circuit used here is very stable and overcomes these inaccuracies by using a unijunction transistor.

The metronome may be calibrated very accurately and once this is done the settings can be relied upon. When the battery voltage falls the output level drops but the beat timing is unaffected.

## THE CIRCUIT

The circuit for the metronome is shown in Fig. 1 and consists of a 2N2646 unijunction transistor operating as a relaxation oscillator. The second transistor, a BC108 in the prototype, simply boosts the output though it is being operated more as a switch rather than as an amplifier.

The operation of the unijunction has been described in past issues of the magazine and for those interested in its operation these should be consulted.

When no voltage is applied to the circuit the emitter junction of the u.j.t. will be at earth potential as the capacitor has no charge on it, but as the unit is switched on

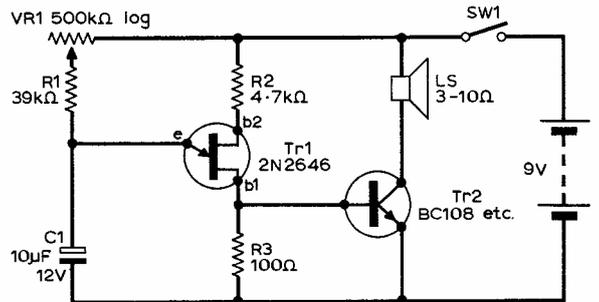


Fig. 1: The circuit of the metronome

C1 charges up through VR1 and R1 so that voltage at the emitter of Tr1 rises.

When this junction reaches a certain level Tr1 starts to conduct and C1 is discharged through R3. At the same time current flows between b1 and b2


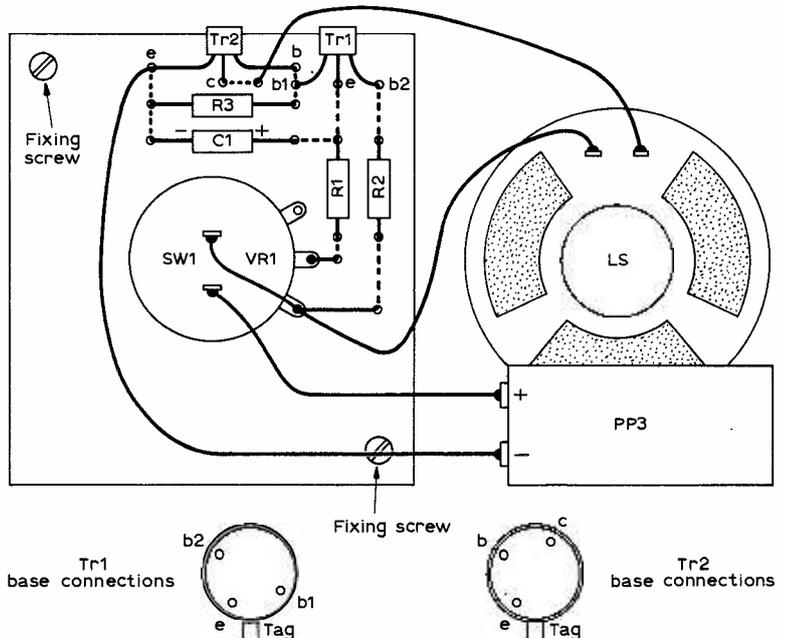


Fig. 2: The component layout and transistor base connections

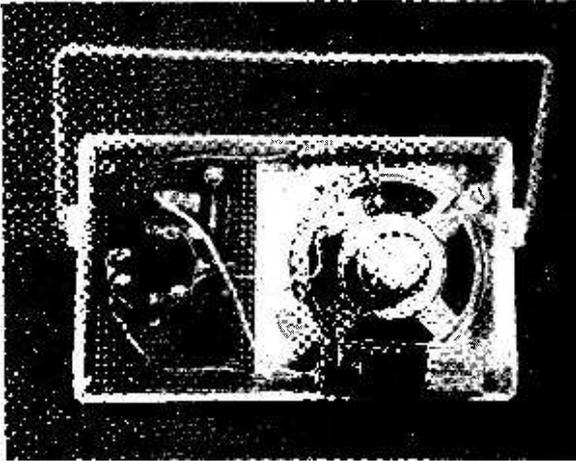

*Internal view of the completed metronome*

and the voltage at  $b_1$  rises.

However, as C1 has discharged the unijunction is switched off and the voltage rapidly falls. All this takes place very quickly and all you actually get is a series of pulses across R3.

Tr2 is connected with its emitter grounded, its base directly connected to Tr1  $b_1$  and the loudspeaker acting as the collector load. When Tr1 is not conducting the base of Tr2 is negative so no current flows but when Tr1 is producing the pulses Tr2 is switched on and the pulse is transferred to the loudspeaker, giving a healthy click.

The timing of the beats depends on the time constant of VR1 plus R1 and C1 and a wide range of frequencies are possible by altering VR1. The values in the circuit cover beats from 4 per second to one every 4 seconds and this should cover most music and timing requirements. For other ranges C1 can be changed—for faster beats reduce C1, for longer ones increase the value.

It is an easy matter to set the control accurately and this has been done on the prototype at the one second setting, this being very useful for timing applications.

VR1 can be either a linear or logarithmic type, but to give more control over the faster beats a log. type was chosen.

Almost any silicon NPN transistor can be used for Tr2, including the cheap surplus types.

The output volume is almost entirely dependent upon battery voltage, but a PP3 delivering 9V gives a pretty healthy click.

## CONSTRUCTION

The prototype was built in a transistor radio case and many readers will recognise it. Several kits were based on this case and they are still advertised separately from time to time. If this type is not available local component suppliers often have surplus transistor radio cases and most of these should be suitable. The advantage of using such a case is that it will have a speaker grill and mounting facilities for the circuit board.

Apart from the loudspeaker and the battery, all components are mounted on a drilled paxolin board. Figure 2 shows the component layout and this should be fairly easy to follow. ■

## NEXT MONTH IN

# PRACTICAL WIRELESS

### THE 'VIBRASONIC' PW25-50 GUITAR AMPLIFIER

Suitable for use with two guitars or a portable electronic organ the amplifier's built-in mixing system also allows the use of a microphone. Utilising the latest silicon transistorised power modules with loudspeakers tailored for the reproduction of musical instruments the Vibrasonic will deliver a genuine 50 watts (r.m.s.) of output power. Featuring a brand new 'tone tremulant' system with a visual tremulant indicator the amplifier will appeal to all music lovers.

### LOW BAND VHF CONVERTER

The monitoring of signals from the USA on the 35MHz paging band has proved to be a very good guide to radio conditions. This simple converter can be fed into any receiver capable of tuning to 5MHz and used to maintain a daily watch on propagation.

### ORGAN PEDAL BASS UNIT

This unit can be used with any portable electronic organ having no pedal bass and it is entirely self-contained. It provides 8ft. or 16ft. or 8+16ft. pitch with flute or clarinet voicing. Feeds into any amplifier and tunable to your own instrument. An extra feature is the drum brush rhythm circuit operating on all pedals.


### PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" FEATURES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES

Don't miss your copy of the September issue of Practical Wireless —on sale 7th August—price 3s. 6d.

# DISCRETE


# or

# IC's

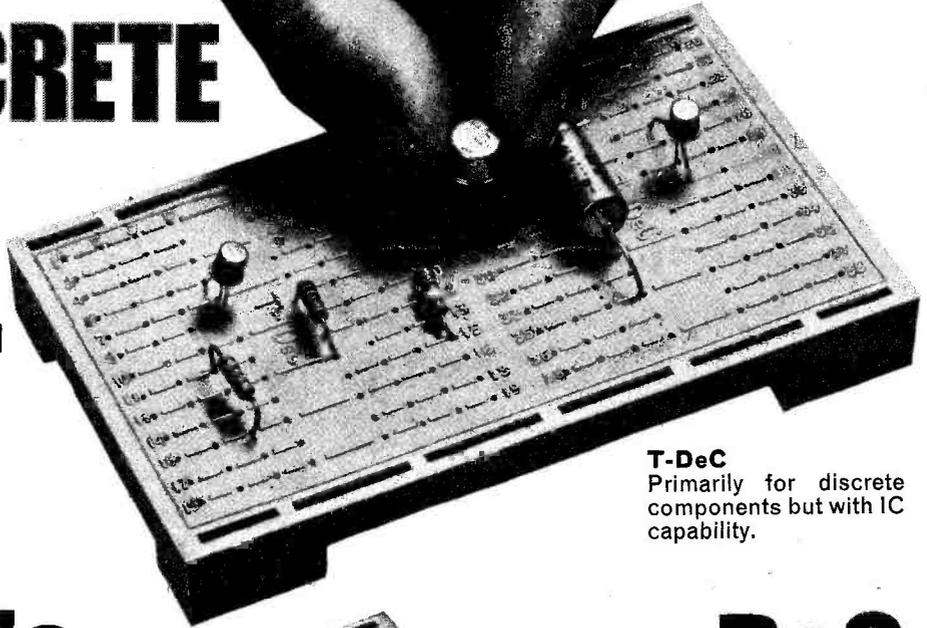
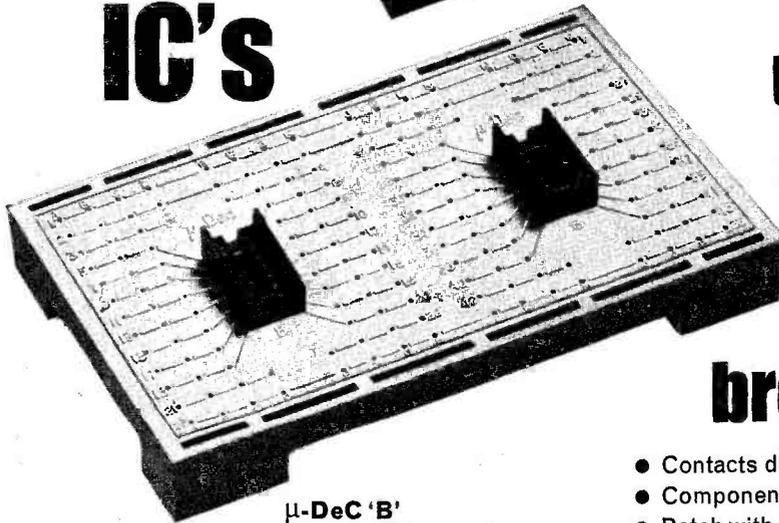
### T-DeC

Primarily for discrete components but with IC capability.




### $\mu$ -DeC 'B'

The board to use if breadboarding with one package type.

If breadboarding with a variety of packages use  $\mu$ -DeC 'A' general purpose breadboards.
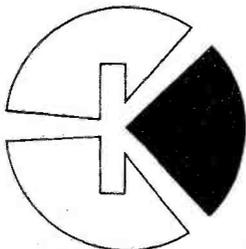
# use DeC solderless modular breadboards


- Contacts designed for maximum life.
- Components inserted directly into board.
- Patch with ordinary wire.
- Modular, for economy and maximum use.
- Modules link to form any size of breadboarding.
- Slots accommodate heat sinks and control panels.
- Control panel supplied with every DeC.
- DeC's may be temperature cycled.
- Contacts available in a range of surface finishes.
- All contacts numbered for reference.
- All connection points shown on surface of DeC.



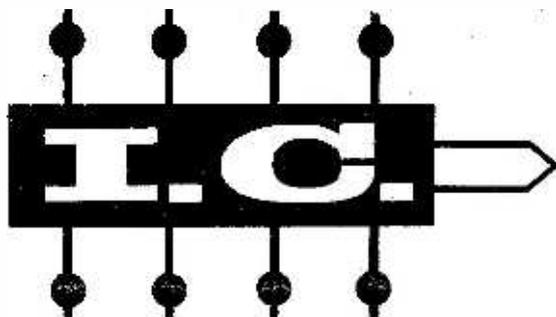**S.D.C. ELECTRONICS (SALES) LTD.**

34 Arkwright, Astmoor Industrial Estate, Runcorn, Cheshire. Tel: Runcorn 5041.





# OF THE MONTH

L.A.J. IRELAND

Number 10

MC1303 Stereo Preamplifier/MC1304 Decoder

As long ago as December 1967 "P.W." carried a report, with full assembly details, on an f.m. tuner incorporating a special-purpose linear integrated circuit, the R.C.A. type CA3014, as the i.f. amplifier stage. Since then other manufacturers have introduced competing f.m. i.f. amplifier i.c.s, and now there are also available units to perform the other functions required in a hi-fi audio system. This month two of them are considered, a stereo decoder and the audio preamplifier to follow it.


## MC1304 Stereo Decoder

First, the stereo decoder, a Motorola unit type MC1304. With a handful of resistors, capacitors and coils this unit takes a "pilot tone" type multiplex stereo signal from the discriminator stage of an f.m. tuner and sorts out the separate right and left

channels to the extent to which right and left channels differ at any given moment.

The difference is actually transmitted in the form of an amplitude modulation of a subcarrier at 38kHz, and therefore a decoder is analogous to a t.r.f. receiver tuned to this frequency, followed by a matrix which produces the separate channels from the now known sum and difference signals. There is one final complicating factor; to conserve bandwidth the sidebands only of the 38kHz a.m. subcarrier are allowed to contribute to the frequency modulation. The "suppressed carrier" must be provided if a conventional a.m. detector is to function, and this is in fact produced in the decoder with the assistance of a 19kHz "pilot tone" accompanying the sum signal.

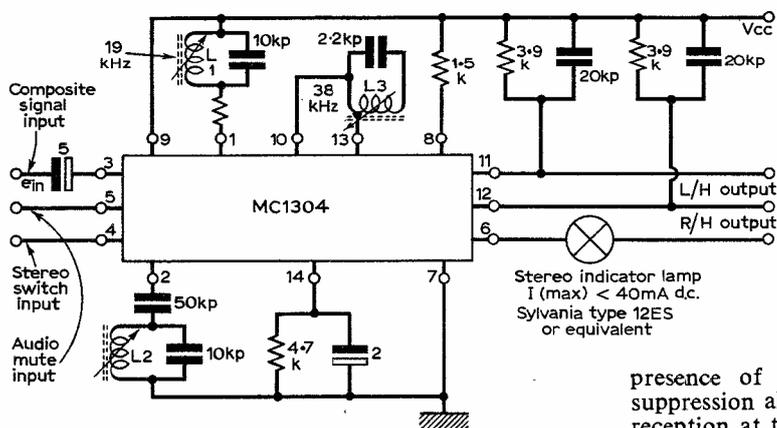
To these essential functions the MC1304 adds a few "optional extras" in the form of a lamp driver output, activated by the pilot tone to indicate the



Left: The external circuitry required for full stereo decoder facilities using the MC1304. The righthand side of the indicator lamp goes to the 12V supply. Lefthand channel output is between pin 11 and earth and righthand channel output between pin 12 and earth. With a supply voltage of 12V the resistor at pin 8 should be changed to 2.7kΩ.

channels to feed the audio stages of the receiver system. As many readers will know, the pilot tone system of stereo f.m. transmission was chosen by the broadcasting networks since it is "compatible," i.e. can be received as a mono signal on a standard f.m. receiver. This is because the primary signal is the average of the two stereo channels. However, the demodulated stereo signal also contains components at a frequency beyond the limits of aural sensitivity which carry the difference information, determining

presence of a stereo signal, together with stereo suppression allowing comparison of stereo and mono reception at the touch of a switch. A similar system allows complete audio muting, switching the receiver into a stand-by mode. Like the stereo preamp type MC1303, described below, the MC1304 is supplied in a standard 14 lead dual in-line epoxy package, and the circuit and application diagrams should enable the experienced constructor to achieve success with this unit. Layout of the decoder system is not critical, as the highest frequency occurring is the upper sideband of the 38kHz suppressed carrier a.m. signal. In regard to matching this unit to the circuitry of the f.m. tuner, the input impedance is typically 12kΩ,

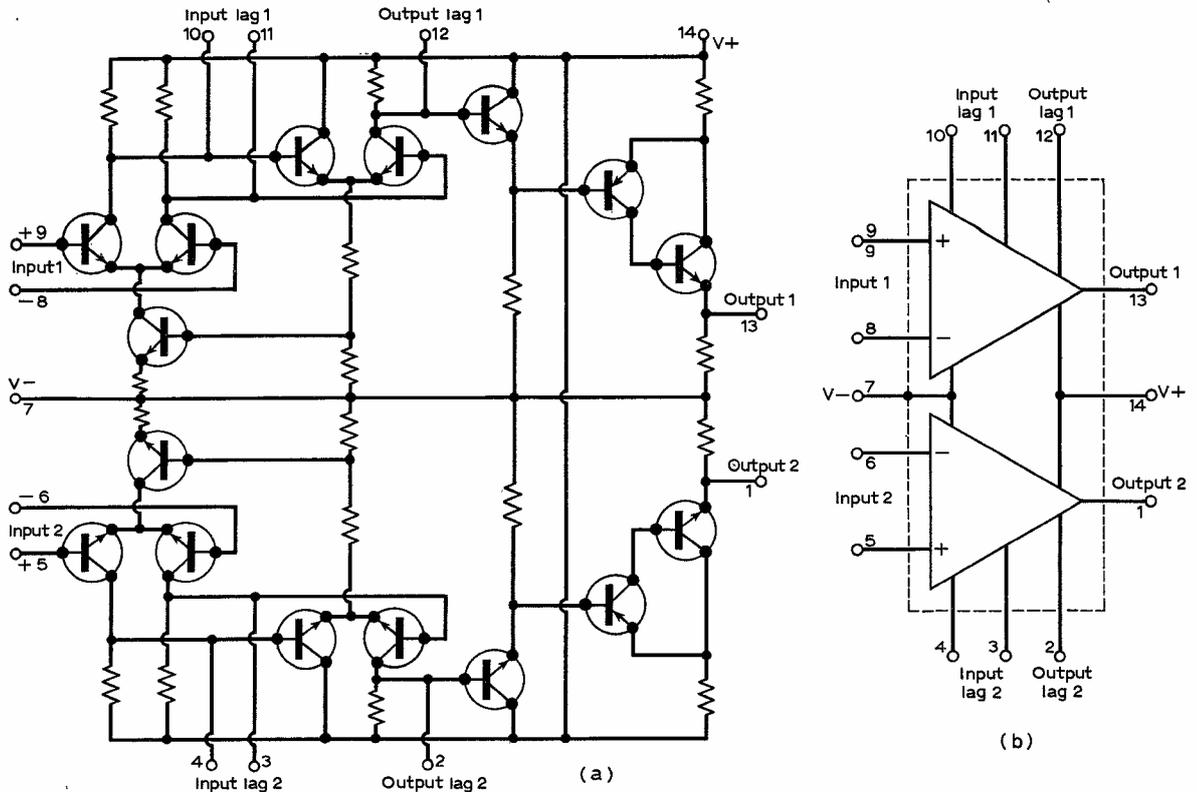

Left: Circuit of MC1303, stereo preamplifier unit. Right: Simplified diagram of the preamplifier.


and with this light loading of the discriminator stage of the tuner, no difficulty should be experienced. (One point, however, the satisfactory operation of a stereo decoder presupposes that the tuner had the specified bandwidth for f.m. reception, which must allow for a 75kHz frequency deviation. This is assured in conventional circuits with 10.7MHz i.f. and discriminator circuits, but may not be available in pulse-counting type tuners, with their very low i.f. frequencies, even though a particular specimen appears fully satisfactory in its mono performance.)

The output for each channel of the decoder is taken from the collector of a common emitter transistor stage, so that the only constraint on the audio amplifier following it is that its input impedance should not be too low. However, any standard stereo preamp will have an input impedance of 50kΩ or greater, so again no difficulty in matching should be experienced. For standard applications elegant and effective output stages to follow the decoder, with power levels in the range of 0.5 to 2 watts per channel, can be provided with i.c.s already mentioned in the pages of this magazine, such as the R.C.A. CA3020 or the General Electric (USA) PA237.
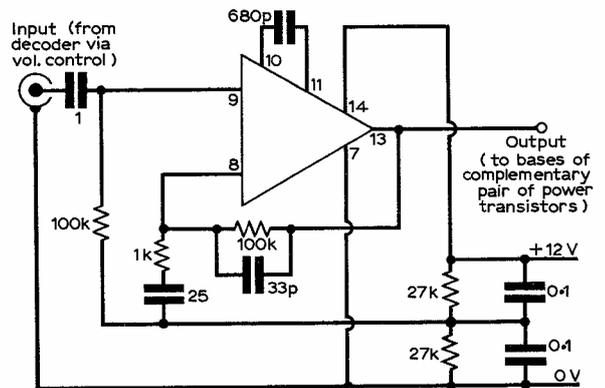
### MC1303 Stereo Preamplifier

Motorola intend their MC1303 preamp to drive an output stage using discrete power transistors to a level of ten watts per channel or greater. The circuit is a development of an industrial dual operational amplifier, the MC1535, and as such provision is made for operation from a dual power supply, which gives both positive and negative inputs to the unit as well as an earth reference. For single source

operation, as would be provided in the amateur circuit and for compatibility with the decoder, the base bias to the input transistors is drawn from a potential divider. The output level will then also be approximately one-half of the supply voltage, and correct for direct coupling to the bases of a complementary output transistor pair of the appropriate power rating.



Typical circuit of one channel of a stereo preamplifier built around the MC1303.

The power supply unit will be a standard system chosen with regard to the requirements of the output stage, with suitable decoupling for the preamp and decoder. Neither this nor the tone control circuits, also conventional, should provide any difficulty for the competent constructor. ■

## Very interesting

Your correspondent J. B. Jobe (Feb. 1970) describes a phenomenon which I remember witnessing a couple of years ago when servicing a receiver.

I cannot remember the make of the set, though I know it was of foreign manufacture. Its owner had complained of no response from the volume control, although the sound was of reasonable quality and at a reasonable level.

Upon dismantling the set, I immediately noticed that one of the loudspeaker leads had come adrift, though at the time I thought this had occurred during dismantling.

However, after having duly fitted a new potentiometer, I switched the set on before I had connected the speaker and music miraculously emanated from . . . somewhere!

Unfortunately pressure of work precluded me from pursuing the matter at the time, so I wired up the L.S. and forget about it until I read Mr. Jobe's letter.

In retrospect, I know that the sound could not have come from the speaker transformer and I seem to remember suspecting the transistors at the time, though I do not remember whether they were "canned" or not.

As for explaining the phenomenon, I'm afraid I cannot! I am in the process of experimenting with various makes and types of transistors in an effort to reproduce the effect but so far without success. Dare we hope for speaker-less radios in the future?

—David A. Evered, (Roath Park, Cardiff).

## Some views

I write first to say how much I agree with your Editorial comment in the April 1970 issue of P.W.

The recent decisions by the broadcasting authorities have all been negative to a high degree, and it has always been my opinion that they seem intent on filling up m.w. channels, especially since the outrageous affair of the "pirates" being kicked off the air (although I am by no means a whole-hearted supporter of piracy!).

It seems that an important part of our cultural and entertainment facilities are being used as a political and financial pawn in the hands of the authorities.

My second point is entirely removed from the first and concerns the availability of components and the shops that supply them.

I recently decided to build the "Injectrace" in the Dec. 1969 issue and as I was anxious to get optimum performance from it, I decided to buy new components throughout instead of consulting my "odd-box". Having made a special journey to London to obtain the components for this, you can imagine my dismay and outrage when half the bits were as obtainable as Moondust! In one shop I was informed with great authority that the capacitors (Mylar) were no longer available as the firm called Mylar had "gone bust" six months ago. In another shop I was asked what circuit the capacitors were for and when I showed them the circuit in P.W. I was treated to a long tirade of abuse directed at P.W. and its staff who "didn't ought to specify fings cos the manufacturer sent em a free sample or two", (or words to that effect). In a very well-known shop I stood for 7½ minutes awaiting service whilst the assistants discussed in great detail the latest pop music.

The assistants in one well-known shop have the annoying habit of putting all one's purchases in a paper bag and not showing to one *before* doing so. This resulted in my coming away one or two items short. One could of course check them at the counter but this would be after paying as they are so quick to take the money.

Several other minor things happened all adding up to a very frustrating day, after which I resolved firmly to shop from the excellent small men who advertise in P.W., by post.—Paul Newman (Aylesbury, Buckinghamshire).

## Oldest in the world?

South Africa may claim to have the oldest ham net in the world in the Early Morning Gang (sic),

which is international in character and has been in existence since 1935. It is also one of the most informal, and although I as an associate and short wave listener have known it for 12 years, I have not sounded the depths of its traditions, customs and "deep mysteries".

From the chairman, affable O. M. Ted (ZS6 William Ida), Johannesburg, I learn that the only founder member is O. M. Bill (Horizontal Willie) who resides symbolically enough in Vereeniging, Transvaal, where the Treaty of Vereeniging was signed in 1902 restoring full peace to South Africa and establishing the Union.

Bill Yapp sets the pace for the amusing mimicry of the EMG (which must *never* be called a group) by claiming to reside in "the depths of the River Vaal" from which he emerges with a gurgling of water (recorded on a tape recorder) to give his matinal greeting.

The Early Morning Gang is only heard in the mornings between 0400 GMT and 0600 on the 40-metre band (7056.3 kHz), on a.m., and migrates to 3600 kHz during the South African winter. It is a very far flung gang and has members in Cape Town (1,000 miles from Johannesburg) Bulawayo, Rhodesia, East London, C. Province, Lesotho, Botswana and Swaziland. Among its members are farmers, a retired hotel keeper, a pharmaceutical expert, a retired mining official, and one nursing sister, who is the only YL. Most of the members put out a pretty good signal, and the gang has been heard in many parts of Africa, and sometimes in Australia and South America. On Christmas mornings as many as 42 hams in Southern Africa have exchanged greetings within the EMG, and passing of the "over" has been expertly handled by the chairman assisted by veterans with more than 20 years membership.

It has dozens of faithful listeners each morning and has officially awarded Five Star Listener status to two for their services in sending in reports.

I'm one, so that's why I've written this.—Hector Watt (Johannesburg).

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**T**HE arrival of spring always seems to drag DXers out of their shacks and put them to work in the garden or around the house. One DXer who remained in his shack was **J. G. Sowerby** of Stranraer and he was suitably rewarded when he heard Radio New Zealand. His equipment is a Lafayette HA600 with either a Joystick or an external long-wire.

This is a case of the early bird catching the worm as reception occurred at 0500 GMT with news followed by music and talks until close-down at 0545. The broadcast is beamed to the Pacific Islands on several frequencies but only 15280 is audible in this country.

**Geoffrey Gilham** of London S.E.12 has, once again, used his Eddystone EC10 and Trio 9R59D to good effect and sent in the following log:

- 4935 *Radio Poti*, Brazil with light music at 0220
- 4835 *Radio Mali* with news in French at 2015
- 4870 *Dahomey* with radio play at 1939
- 4890 *Radio Baré*, Brazil at 2315
- 15125 *BED60*, Taiwan in English at 1802
- 15440 *DZF8*, FEBC in English at 1530

A new reporter this month is **Mervyn Winters** of County Antrim whose equipment consists of an AR88D and a 12 foot whip aerial. His list of two dozen stations has been severely pruned by your scribe but among the better catches were:

- 6095 *Radio Baghdad*, Iraq in English at 2000
- 9545 *Accra*, Ghana in English at 2045
- 11730 *R. Nederland*, Bonair in English at 0625
- 11915 *HCJB*, Ecuador in English at 0900
- 15020 *Radio Hanoi*, Vietnam in English at 2000
- 15160 *Radio Ankara*, Turkey in English at 2200
- 15165 *Radio Damascus*, Syria in English at 1930
- 15345 *Radio Kuwait* in English at 1830
- 21480 *RSA*, South Africa in English at 1750
- 21485 *Radio Australia* in English at 2310

Another regular reporter is **T. R. Gibbs** of Swindon. His report this month contained the following loggings:

- 3322 *Radio New Guinea* at 1200
- 7135 *Radio Peking* in German from 2000 to 2030
- 9715 *Cyprus B.C.* from 1900 to 2000
- 11855 *RTA*, Algeria at 1600
- 15270 *Radio Sudan* (J) with 11835) from 1715 to 1800

**Philip Batt** of Littleborough, Lancashire is another new reporter, his equipment is a PCR3 receiver and a 92 foot long-wire at 15 feet elevation. His log included:

- 7105 *Radio Tirana*, Albania at 0015
- 7110 *All India Radio* at 2115
- 11995 *Teheran*, Iran at 2010
- 15335 *Deutsche Welle*, Kigali relay at 0659
- 15365 *R.N. Espana*, Canary Is. in Spanish at 1910

Times • Frequencies  
in GMT • in kHz

## THE BROADCAST BANDS

Malcolm Connah

- 15400 *Radio Kiev* at 1935
- 15405 *Voice of Nigeria* at 1815
- 17750 *Radio Pakistan* in English at 0900
- 17825 *NHK, Tokio*, Japan in English at 0900
- 21600 *Radio Australia* at 0620

**Raymond Peart** of Worcestershire used his Spidola transistor receiver and 100 foot long-wire to send in his first report to the column:

- 6135 *Radio Warsaw*, Poland at 1830-1900
- 7210 *Radio Norway*, English news, 1200-1230
- 7219 *Radio Nederland*, Happy Station at 0930
- 9605 *Radio Prague* in English at 1730-1830
- 9665 *Radio Switzerland* Calling at 1830
- 9770 *Austrian Radio* with news in English, 1300-1400
- 17705 *Radio Havana*, Cuba in English at 2010-2138

**Roy Patrick** of Derby has sent in some very interesting items of news including:

*Radio Pyongyang* has been heard by Roy at 1900 in a frequency of 6540 with programmes in English.

*Radio Mexico* is now using two frequencies, according to Roy these are 9745 and 15135kHz.

**Malcolm Robinson** of Liverpool sent me the schedule of *Radio RSA*, South Africa which reads as follows:

*English: Daily Transmission to:—*

U.K. and Ireland from 1756 to 1850 still using the 21480 and 15250 outlets.

Africa General from 1056. Heard at good strength on 25790 and 21535 also with unheard outlet of 15220; and from 1450 to 1550 heard on 21535 and unheard on 15220. An additional outlet on Saturdays and Sundays on 11900 is in use from 1056 to 1450.

*Monday-Saturday Transmissions to:—*

North-West Africa from 0645 to 0658 heard on 21535 and 17805 and unheard on 15220 and 11900.

*Afrikaans: Monday-Saturday Transmissions to:—*  
Rhodesia, Malawi and Zambia from 0600 to 0613 heard on 17805 and 15220, also broadcasting on 11900 and 9525.

*Sundays to:—*

East and Central Africa from 0656 to 0950. Heard on 25790 also broadcasting on 15220.

*French: Monday-Saturday to:—*

Central and North Africa from 0630 to 0643 heard on 21535 and 17805 also outlets on 15220 and 11900.

*Potuguese: Monday-Saturday to:—*

Angola from 0615 to 0628 heard on 17805 also with outlets on 15220, 11900 and 9525.

We have been asked to point out that in the report on page 57 in the May 1970 issue, the reference to the Codar CR70A was not intended to be detrimental. It was not intended as a report on the receiver and reception was of course governed by conditions.

# THE AMATEUR BANDS

David Gibson, G3JDG

**R**EAD all about it. Who is GB3WRA? Why are strange call signs coming from PY land? Who has a 21-mile antenna buried in ice?

Listen out on all bands 160-10 metres on Saturday, September 5, for GB3WRA. This will be a special station located at High Wycombe, Bucks, for the annual Wycombe show. Visiting amateurs and s.w.l.s welcome.

Brazilian stations apparently used the prefixes ZV, ZW, ZX, ZY and ZZ for the CQ WW contest because the contest was for prefixes. You begin to wonder if a countries list or a callbook is really of much use these days.

**John Moore** (Leicester), relates the strange saga of KC4AAD who is located near the U.S. base "Byrd" some 650 miles from the South Pole at 120°30'W, 79°54'S. Are you sitting comfortably? Then I'll begin. This station has a 21-mile dipole which is resonant at just under 1kHz and is used on 3kHz for experimental purposes. Quick, get the hi-fi out, you might log him. Apparently some five years ago the antenna, all 21 lovely, dangly miles of it, was lying on the ice. Now, it is four feet below the surface. Anyone at the North Pole is advised to be on the lookout for a long piece of wire which should be through in about another seven million years' time.

**J. Leaver** (Lancs), home brew s/het, 100ft wire wound round the loft, a.t.u., has sent in a fantastic topband log which is 99.893% c.w. Among the stations heard, which includes 30 OK and 13 OL stations are: DL9KRA, EI9BG, GI3JEX, GI6TK (s.s.b.), GM3BGW, GM3LQI/P, GM3SVK, GW3TUG, GW3ZEY, OK1ABK, OK2BMR, OK3TCA, OK5TOL, OL1AUL, OL2ANK, OL4AMF, OL5AMA, OL6AKP, OL8ANL, PA0PN, 5B4NZ, 9H1BL. Would-be c.w. sleuths are advised to QRX 1.85MHz down to band-edge.

**Steve Ireland** (Kent), PW Clubman, 19-set variometer, 67ft end fed, says best time to listen for DX on 80 is 2130, especially the net on 3.795MHz. Steve's best on the band are: CN8HD, CT2AK, CR6IV, EP2DX, HB0LL, OY2X, OD5BA, PY1HA, PY7BFN, PZ1AH, SM6CNS/MM, TA2E, W4RDD/P/VP9, W2NIN, K3JH, XE7KS, YV0AI, ZC4CB, ZM2BCG, 4X4KT, 4X4YM.

I've heard of "A little bird" whispering in someone's ear, but when it comes to 14MHz, the PCR3 'belonging to **P. Batt** (Lancs), takes a lot of beating. The 22ft 45° "vertical" is connected via a 70ft single wire feeder and an a.t.u. Proof of this r.f. pudding is: AX2AYE, AX3AD, AX3LAF, AX4SD, CE3OE, EP40E, HP1MD, K4ZL, KP4CM, KV4AB, LU5B, PY1BSC, PY7ARM, VK5RFJ, VK7WH, VP2DOE, VP2VO, VR1IC, VE3CU, VE4SK, YV3US.

Messrs **Anderson, Roberts** and **Apperley** have confessed! Their chemistry master is none other than G3XMM. Heard on 21MHz on the guv's HRO and 80ft end fed: AX3DCR, DU1CH, EL2AI, EP2KB, G3PAC/W9, HR2HHP, HV1CN, JA6MDD, JA8DGR, KR6HR, LU5XE, MP4MBB, MP4TDR, PY2EIR, SV1CZ, VE3EQA, VP7CG, VP9GE, VU2DK, YV1SA, ZM1AIX, ZS6AL, ZX1MB, ZX2DVH, 9Y4MM all on s.s.b.

**A. Crooks** (Leicester), RA1 plus PR30, 45ft end

fed also reports a series of interesting squeaks on 21MHz s.s.b. Andy's log reads: CR4BC, CR6GA, CR7IZ, EA8GZ, EL2BZ, EP2DX, HS3ACP, JA1SQI, JA1YGM, JA4AOF/MM (near the Phillipines), JA5ARU, JA6MS, JA9IL, JH1BLX, JW7UH, KP4ES, OA4LM, OI3NY PY4BLH, TG9RR, TJIAR, UA0SU, VO1FX, VU2KV, VU2OLK, ZS2PX, 4X4BR, 6W8BD, 9H1CB.

**Gear**—CR100/2, 60ft end fed. Listener—**J. Moore** (Leicester). Log: AX3VK, CR6GA, CR6MH, CR7BB, CX7BF, DU1FH, FG7XL, FL8MB, HK3VA, HS5ABD, HT1HSM, JA1HTM, JA2EQ, JA4FRB, KV4AD, KZ5JW, LU2DEK, LU5DDM, LU9NA, OA4LM, OD5BZ, PJ9JR, PY2HT, PY8IL, UH8BX, UL7GAW, VE3MR/4X4, ZE1AA, ZE3JO, ZS6AL, ZV2CK, ZY2RZ, ZZ1CAD, 4S7PB, 4Z4HF, 5J3WO, 5Z4LS, 7Q7LZ, 9H1BA, 9J2PV all on ten metres s.s.b.

It's all happening on two metres. **N. Richardson** sends in an impressive log which included F1BCI/P located some 10km south of Calais. Nicholas is in Bucks, and uses an 8-element Yagi, Garex converter, PR30 and CR7OA tuning 28-30MHz.

"Keep up the good work in printing 2 metre logs in PW," says **S. Carter** (Staffs), while **Glyn Richards** (Isle of Wight), admits to riding his trusty 4-over-4 slot fed on the 144MHz trail. The JXX converter and GC-1U got these a.m. stations which are between 120 and 180 miles away: G3GZJ (c.w.), G3PWJ, G8CSU/P, GW3CBY, GW3ITZ/P, GW3OXD/P, GW3NWR, GW3VKL/P.

From France, Glyn logged: F1AAD/A, F1TE/P (both in Cherbourg), F1BCI/P (Calais), F3LP (Le Havre), and from further afield—HB9AEN/P.

Mobile rallies in July include: July 5th, Cornish ARC rally at St. Ives; 5th, ARMS rally at RAF/USAF air base, Alconbury (highly recommended); 12th, Upton Mobile Rally, Upton-upon-Severn, Worcs; 19th, Mobile Rally at Scarborough; 26th, White Rose rally at Leeds; 26th, Saltash rally; August 2nd, Mobile picnic at Bristol; August 9th, Woburn Abbey mobile rally; August 9, Mobile picnic at Stratford-upon-Avon.

Deadline for logs for The Amateur Bands this month is the 15th.

## RSGB EXHIBITION 1970

PRACTICAL WIRELESS  
PRACTICAL TELEVISION

Visit our Stand at the Show where we shall be glad to meet our readers and their friends.

SEE OUR LATEST DESIGNS  
including

LIGHT BEAM TELEPHONE  
VIBRASONIC GUITAR AMPLIFIER  
ORGAN PEDAL BASS UNIT


WHEN?

Wednesday Aug. 19th to Saturday Aug. 22nd  
10 a.m. to 9 p.m. daily

WHERE?

The Royal Horticultural Society's New Hall,  
Greycoat Street, Westminster, London, S.W.1  
(Nearest Station—Victoria)

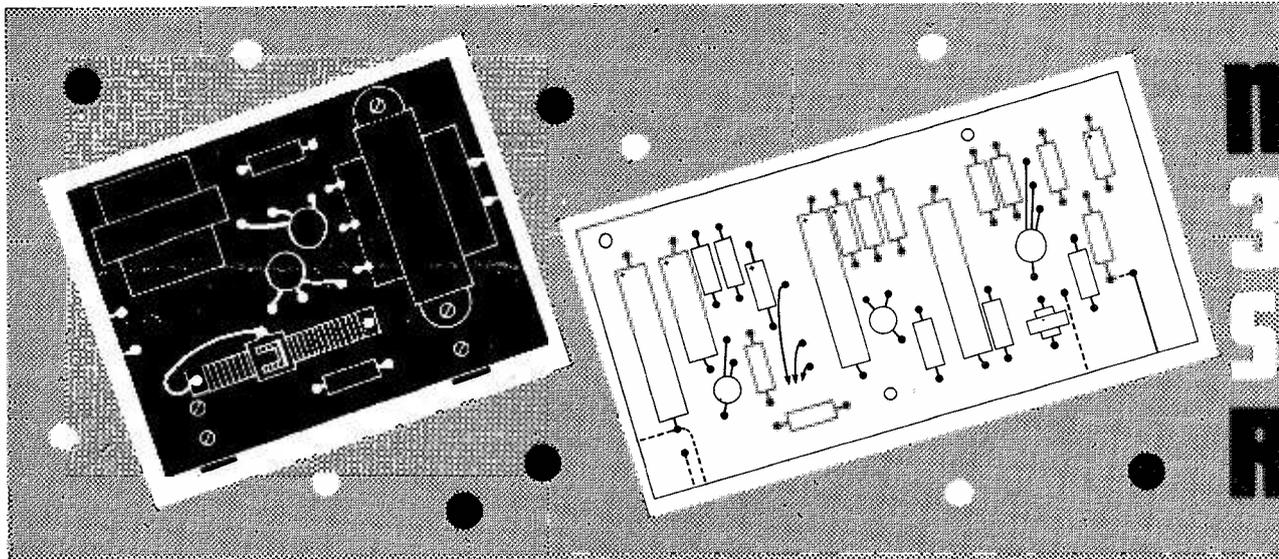BE CAREFUL . . . !!! NOTE THE DATE  
THE SHOW'S EARLY THIS YEAR!



As is well known, a t.r.f. type receiver is capable of surprisingly good results, when correctly operated and circuit design is very much simpler than with a superhet.

The receiver described here covers approximately 1.3MHz to 20MHz or 230 to 15 metres, in three switch selected wavebands. The OC81D output stage gives very good headphone volume, from a large number of transmissions. Coverage includes the 160m and 80m amateur bands, ship and other frequencies, as well as the more usual short wave bands.

A push-pull output stage can be added to boost

volume for loudspeaker reception. This stage is in the form of an optional module which can be plugged into the receiver output socket.

### Circuit

This is shown in Fig. 1, with the coil for one band only. The remaining two coils are wired in the same way as that shown.

VC1 is the main tuning or band-setting capacitor and the small capacitor VC2 is for bandsreading.

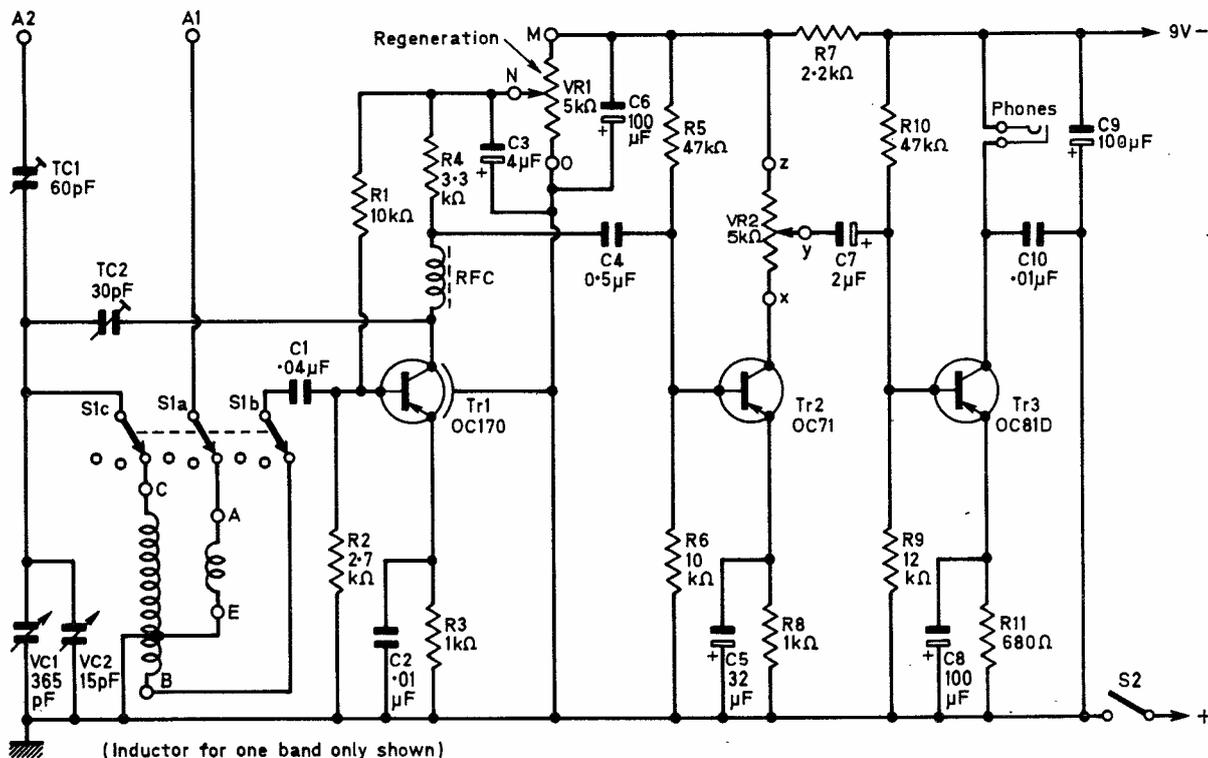


Fig. 1: Circuit of receiver. The circuit of the additional audio module is shown in Fig. 7.

# MODULAR -Band Short Wave RECEIVER



R. F. GRAHAM

Its full rotation covers only a narrow band of frequencies. In use, VC1 is set for a band required, such as the 25m or 31m band, and this is tuned with VC2. The tuning "rate" with VC2 is about the same as that which would be obtained with a 20:1 reduction drive on VC1, and this method is inexpensive, convenient, and easy from the building point of view. These capacitors need not have the exact values shown.

Each inductor has a tuned section C to E, base coupling E to B, and aerial coupling A to E and 3-pole 3-way switch brings in the coil required. Alternative aerial sockets are fitted, A1 is better with a reasonably long aerial and when an earth is available. A2 is used in other circumstances, and has a small series capacitor TC1.

An OC170, Tr1, is used as a regenerative detector, with feedback through TC2 and regeneration control

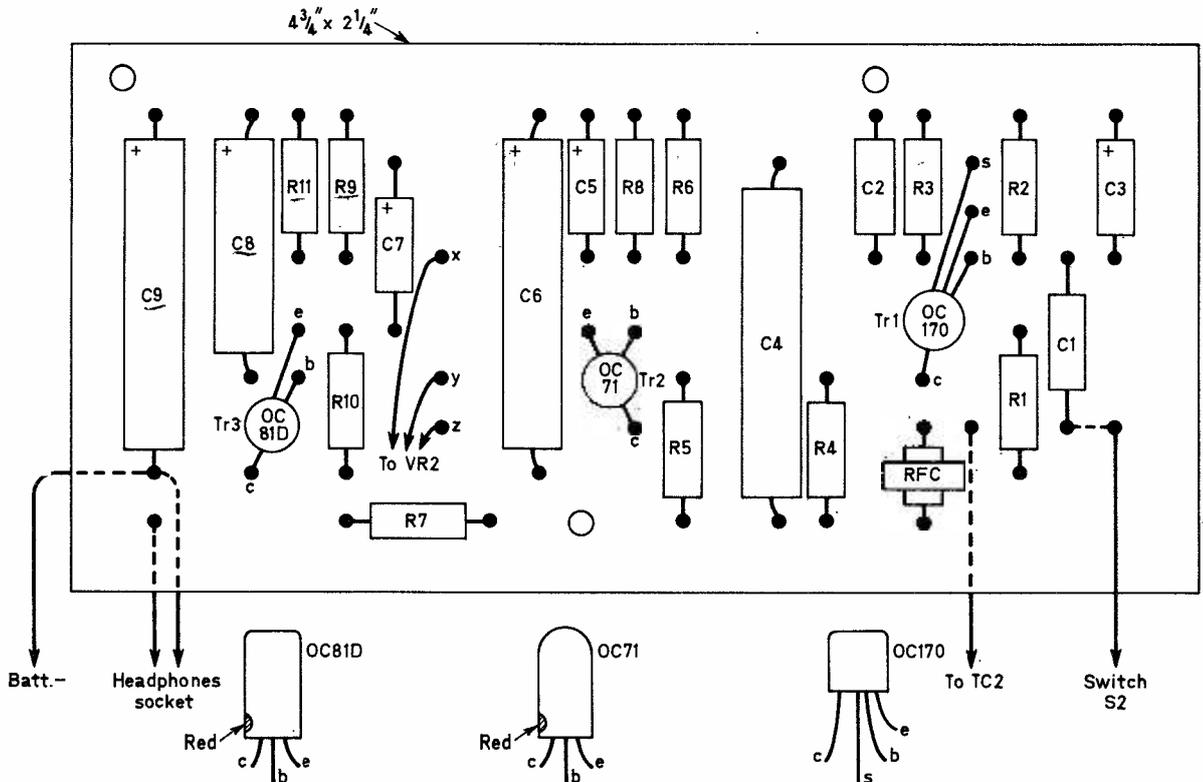


Fig. 2: Top view of circuit board and identification of transistor connections.

VR1. For proper results with a t.r.f. receiver, proper regeneration on all frequencies is absolutely essential, and this circuit was found to perform well.

The output of the detector is coupled to an OC71, Tr2, first audio amplifier, and VR2 is the audio gain control. Tr3, an OC81D, is intended for use with medium impedance (500Ω) headphones. A single earpiece or miniature personal earphone not being very suitable for regular s.w. listening.

### Circuit Board Module

Most of the components are assembled upon a ready perforated insulated board about  $4\frac{3}{4} \times 2\frac{1}{4}$  in. which is later fixed to the chassis by three bolts, two of which provide earth returns.

Fig. 2 is the top of the board. The easiest method is probably to insert the resistors and capacitors a few at a time, spreading the wire ends so that they do not fall out. The board is then turned over, and the leads are cut to suitable length, and soldered. Check all component values as they are fitted, and note that the larger capacitors have their polarity indicated, as shown.

Fig. 3 is the underside of the board. Where wire connections are necessary, some 22 s.w.g. tinned copper or similar wire is used. Insulated sleeving is put on all leads which may touch other bare wires or joints. Two tags are placed as in Fig. 3, and are common to the positive or earth circuit and chassis. These tags are tightly held by nuts or  $\frac{1}{2}$  in. long bolts.

When the circuit board is fixed to the chassis, put an extra nut on each bolt, so that the board is about  $\frac{1}{4}$  in. clear of the chassis. The bolts then pass through holes in the chassis, and further nuts are put on and locked tight. Bare joints and wires should be clear of the metal chassis, but a piece of card can be put under the circuit board, to avoid any possible short circuit.

Transistor connections are shown in Fig. 2, and it may be found helpful to put thin coloured sleeving on the wires to help identify them. Red may be used for the collector, black for the base, and some other colour for emitter leads. The wires are left at such a length that the transistors are about  $\frac{1}{2}$  in. clear of the circuit board.

A number of flexible leads run from the circuit board, for connections to the volume control and elsewhere. It is helpful to identify these wires by using coloured sleeving, or by employing thin coloured flex.

A lead from C1 passes directly down through the chassis to the bandswitch, Fig. 4. Leads from VR1 go down through a common hole, as do leads from VR2. Take a flexible lead from C9, for battery negative, and solder on a negative battery fastener. Run leads from C9 and OC81D collector which go to the headphones socket.

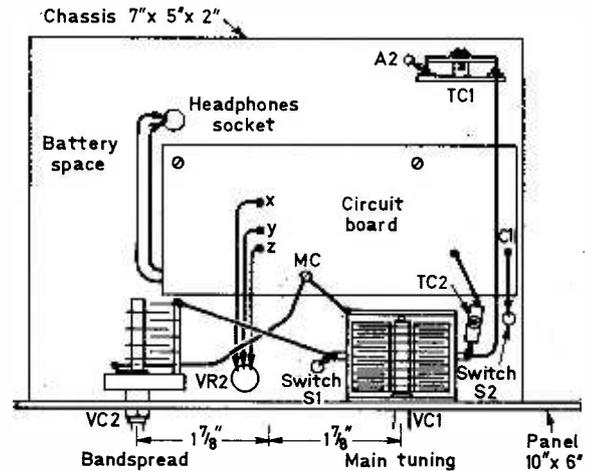


Fig. 4 : Top view of chassis and circuit board.

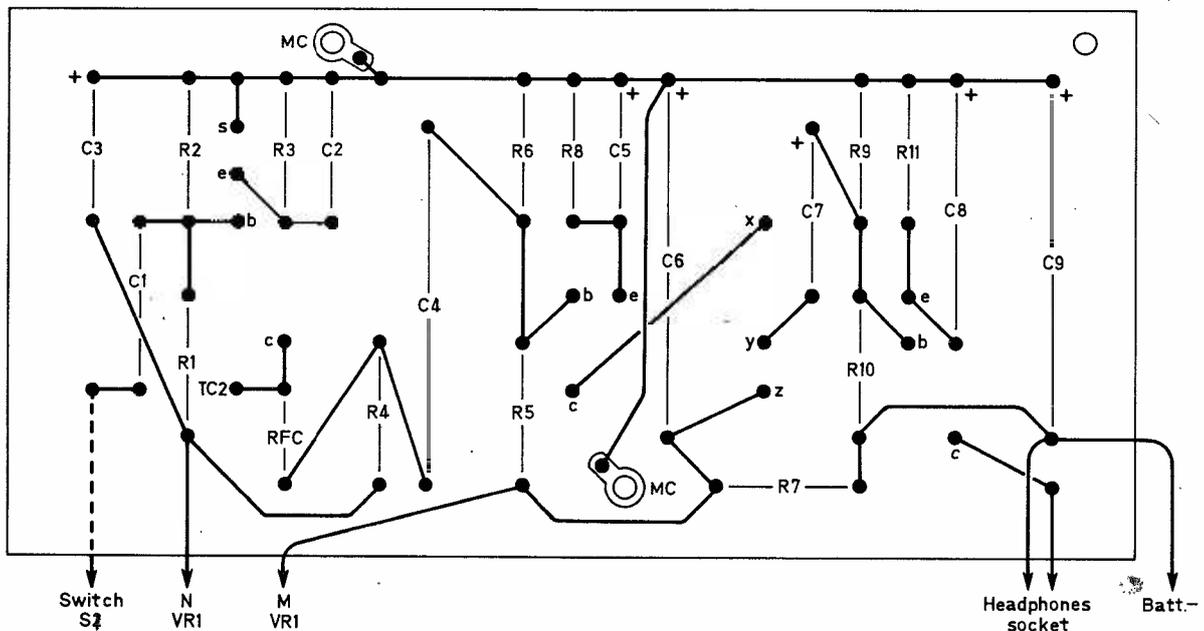


Fig. 3 : Bottom view of circuit board showing interconnection of components.

## Chassis

The chassis has flanges to which the panel is bolted as in Fig. 5, and Fig. 4 shows how the circuit board is fitted. The rotor connections for both VC1 and VC2 run to a tag MC, in Fig. 4. A further tag, under the chassis on this bolt, is the earth return point for the coils, Fig. 5.

TC1 is soldered to the insulated tags of a tag-strip, Fig. 4, and TC2 is soldered directly to one of the stator tags of VC1. A lead from the other stator tag passes directly down through the chassis to the band-switch.

The tags of VR1 and VR2 are lettered, and must, of course, be correctly connected to the circuit board. The metal chassis is the common positive or earth return. A lead with a positive battery fastener is soldered to the switch incorporated in VR2, as in Fig. 5.

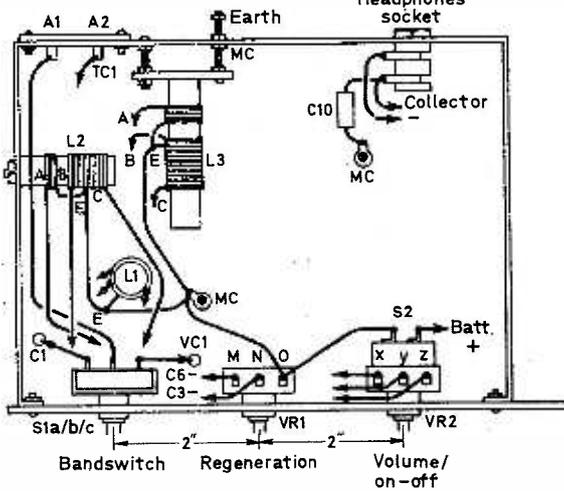


Fig. 5: Bottom view of chassis and wiring of coils and controls.

The cabinet listed has an inner flange, so the chassis has to be mounted a little high, as in Fig. 6, to clear this. With a receiver of this kind, a metal case is helpful in avoiding hand-capacity effects.

## Coils and Calibration

The three coils are wound in the same way, except for the numbers of turns. L1 and L2 are on  $\frac{1}{2}$ in. diameter insulated formers,  $1\frac{1}{2}$ in. long, and L3 is wound on a ferrite rod 2in. long and  $\frac{3}{8}$ in. in diameter. Paxolin tubes can be mounted by cutting discs of insulating material, and cementing these in one end. A small bolt will then fix the coil to the chassis.

All windings for L2 are of 32 s.w.g. enamelled wire, turns wound side by side. Fix the wire at C, Fig. 5, near one end of the tube, by passing it through small holes, or cementing it. Wind on 34 turns. Bare the wire and form a loop E, continue for a further 4 turns in the same direction, and finish at B. Leave the wire ends long enough to reach the switch. Solder the wire on at E, leave about  $\frac{1}{8}$ in. space, and wind 7 turns, finishing at A.

With all coils C goes to VC1 (via switch), E to chassis and earth line, B to transistor base (via switch and C1), and A to aerial, again via the switch.

The highest frequency coil L1 has 15 turns from C to E, and 3 turns from E to B, of 22 s.w.g. enamelled wire. E to A is 4 turns.

The lower frequency coil L3 is wound on a ferrite rod to reduce the number of turns required. C to E is 27 turns, and E to B is  $1\frac{1}{2}$  turns, of 24 s.w.g. double

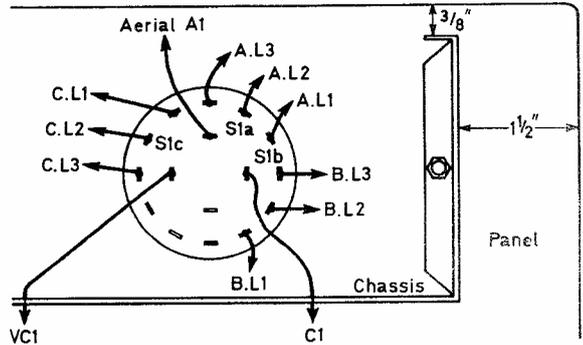


Fig. 6: Position of chassis relative to panel and bandswitch connections

cotton-covered wire. E to A is 7 turns of 32 s.w.g. enamelled wire. The end of the ferrite rod is a tight push fit in a hole in a strip of paxolin, and is cemented here. It is then mounted with two bolts, as in Fig. 5.

Fig. 6 shows the rotary switch connections, as seen from behind. (This is actually a 4-pole switch, with one pole unused. To avoid any chance of a mistake here, L2 only can be wired in, and the receiver tested with the switch in its central position. If the wrong tags are used for any coil or connection, the receiver cannot function.

VC1 and VC2 are fitted with large knobs and dials calibrated 0-100. VC1 is secured with three bolts, which must be very short to avoid fouling the plates. A small bolt was fitted above each dial, with its slot vertical and filled with paint, so that the dial numbers can be logged. Dial readings of VC1 for the various bands are given below. These are only a guide, because the home-wound coils and other factors will influence coverage.

	Freq.	Dial
Band 1.	20MHz	10
	15	20
	10	38
	8	55
	6	90
Band 2.	8MHz	12
	6	20
	4	40
	3	70
Band 3.	4MHz	15
	3	25
	2	50
	1.6	68
	1.3	95

## Operation

With a t.r.f. receiver, adjustment of the regeneration is of the greatest importance. If there is little or no regeneration, almost no signals will be heard, and tuning will be very flat, but as regeneration is

increased, a point is reached where sensitivity and selectivity improve enormously. This shows that the detector is approaching the point where it will begin to oscillate. Optimum results are with regeneration so adjusted that the receiver is *just* failing to oscillate. Advancing regeneration further will cause whistles when tuning through signals, and an almost complete loss of signals.

Initially, TC2 is almost wholly unscrewed. When VR1 is rotated slowly in a clockwise direction, background noise should begin to increase, and signals heard. If oscillation occurs when tuning through a signal back off VR1 very slightly. If regeneration up to the oscillating point cannot be obtained on some frequencies, screw down TC2 a little.

TC1 should normally be fairly well open, except for a very short aerial. If TC1 is screwed down, and a long aerial attached, the damping introduced may prevent regeneration, and may cause flat tuning.

Current drain is about 6-8mA or so, and any 9V battery is satisfactory.

### Push-pull Amplifier Module

This amplifier, Fig. 7, can be plugged into the t.r.f. short wave receiver, to obtain speaker reception. No changes are needed to the receiver. The jack plug is put in the receiver headphones socket, audio signals being taken to the primary of the driver transformer T1. The plug also provides the supply voltage for the output stage.

### ★ components list

#### Resistors

R1	10kΩ	R8	1kΩ
R2	2.7kΩ	R9	12kΩ
R3	1kΩ	R10	47kΩ
R4	3.3kΩ	R11	680Ω
R5	47kΩ	R12	1.5kΩ
R6	10kΩ	R13	50Ω WW (Home Radio VR 101)
R7	2.2kΩ	R14	4-7Ω

All 1/4W 10% except R13

VR1 5kΩ linear pot. VR2 5kΩ linear pot with switch.

#### Capacitors

C1	0.04μF 150V	C6	100μF 12V
C2	0.01μF 150V	C7	2μF 6V
C3	4μF 12V	C8	100μF 6V
C4	0.5μF 150V	C9	100μF 12V
C5	32μF 6V	C10	0.01μF 150V
VC1	365pF (Home Radio No. VC1A)		
VC2	15pF (Home Radio No. VC26D)		
TC1	60pF pre-set (Home Radio)		
TC2	30pF pre-set (Home Radio)		

#### Semi-Conductors

Tr1	OC170	Tr3	OC81D
Tr2	OC71	Tr4/5	OC81 matched pair

#### Miscellaneous

S1a-b-c, 3P3W rotary switch (Home Radio WS17). Transformer T1 (Weyrad LFDT4). Transformer T2 (Weyrad OPT1). 2 Dials, 2 3/4in dia. (Home Radio KN2). Chasis components, aluminium plate 7 x 5in (Home Radio CU168), 2 sides 5 x 2in (Home Radio CU134), 1 side 7 x 2in (Home Radio CU136). Miniature R.F. choke 2.5 mH. Case 10 x 6 x 6in (Electroniques 'Dinkicase'). Headphones jack and plugs. Paxolin panel 3 x 2 1/4in. Eyelet board.

R12 and R13 set the base operating conditions for the pair of output transistors, and R13 is a miniature pre-set resistor. This allows easy adjustment for best results with any pair of output transistors of the type shown, or similar type.

The amplifier module is mounted on two small brackets which form the positive or chassis return. This connection is essential. If the amplifier is not fixed to the chassis in this way, a lead must be provided here to complete the circuit. In this case, the amplifier could be in the speaker cabinet.

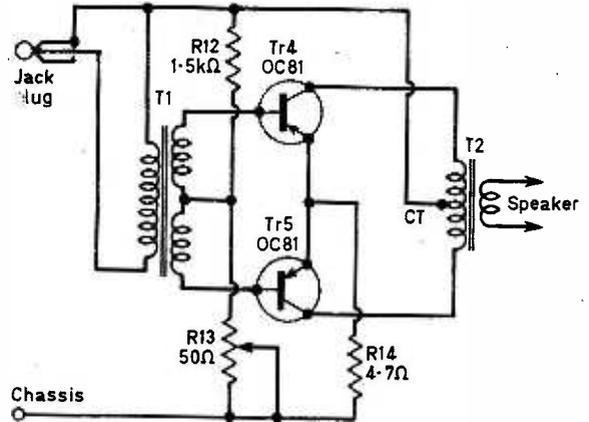


Fig. 7 : Circuit of amplifier module.

The components are mounted on an insulated board about 3 x 2 1/4in., Fig. 8. Provide a short flexible lead from the slider of R13, to one end, as shown. One tag of the driver transformer T1 is identified by a green dot, and this should be placed as in Fig. 8. Flexible leads run from the primary to the jack plug. Connect the plug in such a way that the negative circuit is correctly made when it is inserted.

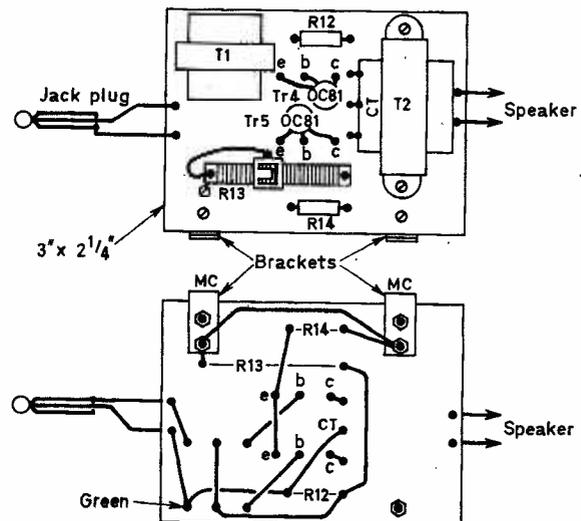


Fig. 8 : Views of amplifier circuit board. Care must be taken to ensure correct wiring of jackplug.

Flexible leads from T2 run to the speaker, which should be a reasonably large 2Ω or 3Ω model, fitted in a cabinet, or attached to a baffle board. The amplifier is attached to the receiver by the two brackets, and stands vertically behind the receiver circuit board.

When the amplifier is in use, a PP9 or similar large 9V battery is more suitable. Temporarily, place a 100mA or similar meter in series with one battery lead. Set R13 to minimum resistance and plug the amplifier plug into the receiver headphones socket. When the receiver is switched on, the meter should show about 8-10mA. Move the slider of R13 to increase its resistance until the current rises about 2mA to 4mA above the original figure.

Subsequently R13 may be re-adjusted, if necessary, for best results with a signal tuned in. Current should not be over 15mA or so with no signal, rising to 30-40mA with good volume. The best setting for R13 depends somewhat on the individual transistors.

Headphones can be used as before, when wanted, by withdrawing the amplifier plug, and inserting the headphone plug. This puts the push-pull amplifier completely out of use. ■



...buy or borrow manual of Stern-Clyne Veritone STP-1 stereo Tape Preamp.—S. Stubbs, 49 Neil Lane, Manchester, M21 2SH.  
 ...mods and official handbook for the No. 19 set Mk. 3.—F. G. Shepherd, 16 Frances Road, Purbrook, Portsmouth, Hants.  
 ...details of the WS 19 and ancillaries (operating procedure etc).—A. Howard, 2 Castle Close, Raffley Estate, Kings Lynn, Norfolk.  
 ...any information at all on the T18D23 full-wave rectifier.—R. Collins, 39 Cadogan Gardens, South Woodford, London, E.18.  
 ...any information regarding the c.r.t. indicator unit type 26.—R. A. Carter, 2 Wolsingham Drive, Acklam, Middlesbrough, Teeside.  
 ...information and details on converting Ferguson 12in. TV into an oscilloscope.—I. Dyche, 49 Marlowe Drive, Whitecross, Herts.  
 ...circuit and constructional details of an a.t.u. which covers Top Band and Eighty. Also buy or borrow December 1961 issue of P.W.—Martin Swift, 341 Walsall Road, Stone Cross, West Bromwich, Staffs.  
 ...information on the indicator unit c.r.t. type 26 ref. 10Q/16058. Information particularly required is on plug connections, power requirements, circuit diagram etc.—L. K. Ferguson, 49 Bulloil Road, Kempston, Leeds.  
 ...circuit and any other information on Indicator Unit c.r.t. type 26 A.M. reference 10Q/16058. I am also in need of a power supply for the unit which requires 80V at 400-2240Hz and would be glad to hear from anyone who has any ideas on this.—M. K. Dakin, 145 The Broadway, Norton, Stourbridge, Worcs.  
 ...circuit diagram of the P. W. Monophonic Electronic Organ's Professional Amplifier.—C. W. G. McGiffie, 10 Bryn-Awel, Bryntirion Hill, Bridgend, Glamorgan, South Wales.  
 ...information on the Elliott Multiversal Testing Set, No. D474763 (this may be serial number). It is a Wheatstone bridge, insulation tester and fault localisation unit.—L. O. Tully, 120 Victoria Street, Fairfield 4103, Brisbane, Australia.  
 ...manual or circuit diagram of the ex-Govt. signal generator CT53. I understand that these were manufactured by different contractors but the maker of my one is H. C. Atkins of S.W.6.—The Occupier, 145 Brighton Road, South Croxson, Surrey.  
 ...any information at all on surplus R103 Mk. 2 receiver.—J. M. Gunter, 65 Hamilton Road, Taunton, Somerset.  
 ...v.h.f. receiver type R1392D. I would like to purchase the i.f. transformer on the right of the chassis looking from the front.—L. K. Ferguson, 49 Bulloil Road, Kempston Beds.  
 ...name of supplier of resistance line cord 3-way, 0.3 amp to reduce 240V a.c. to 112V a.c. I also have many copies of P.W. for disposal.—R. G. Clark, 101 Warrnam Court Road, Carshalton, Surrey.  
 ...any gen. at all re echo sounder type 621 made by Rikoh.—John Bartlett, 35 Brambleton Avenue, Farnham, Surrey.  
 ...diagrams and service sheet for Korting Mk. 112 tape recorder.—R. Stansfield, 23 Well Walk, Hampstead, London, N.W.3.  
 ...details on how to convert a TV set into an oscilloscope.—R. Johnson, 44 Queenborough Road, Halfway, Sheppey, Kent.  
 ...any gen on an old radio receiver—the Osram Four New Music Magnet.—P. Shea, 17 Granbleton Park, Belfast, 9.  
 ...handbook of the Trio 9R-59 receiver.—G. L. Hill, BRS31721, 51 Halffields Lane, Gunthorpe Estate, Peterborough.  
 ...details on improving the s.s.b. on an AR88.—G. McKindry, 29 Whitehurst, Bearsden, Glasgow, Scotland.  
 ...information, circuit or handbook and any useful mods for the R.3673.—A. Howard, 2 Castle Close, Raffley Estate, Kings Lynn, Norfolk.  
 ...loan or purchase handbook for BC454 Command receiver.—A. Rawlings, 37 Kingswood Avenue, London, N.W.6.  
 ...information on use or purchase of manual on Simon SP5 tape recorder.—P. C. Hill, 42 Church Road, Bishopsworth, Bristol, BS13 8JW.  
 ...gen on using VCR139A or CV1588 c.r.t. for an oscilloscope. Also the socket for the CV1588.—A. Kitchen, Rosery, Star, Shipham, Somerset.

# THE MW COLUMN

**M**EDIUM-WAVE stations in Europe operate on channels spaced 9kHz apart as laid down in the Copenhagen Plan. There are a number of African and Asiatic stations in the gaps between these channels and these can be heard during the evening before the majority of Europeans close down. A selective receiver of communications standard is an advantage for this type of DX while a loop aerial is helpful in cutting down splash from adjacent channels. *Baghdad* Iraq 760kHz can be located between West Germany on 755 and Sottos 764. The programming is in Arabic though it sometimes broadcasts western music before closedown at 22.30 GMT. Occasionally there is a 1kHz heterodyne on this station caused by *COA* 759kHz in the Portuguese island of Sao Tome West Africa. Sandwiched between USSR on 890 and Milan on 899 is EFJ57 *Radio Juventud de Canarias* Tenerife on 895kHz. This station relays news from *Radio Nacional Espana* and specialises in serious music until sign-off at midnight. Deir el Zor 959kHz Syria has Arabic programmes until 2230hrs and can be found just below Paris 962kHz. Other stations to look for on these 'split' frequencies include *Riyadh Saudi Arabia* on 588; *Jerusalem* 677; *Kermanshah Iran* 985; *Kuwait* 1345; BBC Eastern Relay in the Persian Gulf on 1410. *Urumchi* in western China is a regular on 1525 with Russian propaganda and jamming. Two long wave Asiatics logged recently are *Tselinograd* in Kazakstan behind Warsaw 227kHz and *Ashkhabad* 375kHz, both at 2200hrs.

A mystery Greek-speaking station has been heard just out-of-band on 1610kHz. It was first reported to Sweden Calling DXers by a listener in Austria and further information has just come to hand in a letter from Angelo Coppola of Naples who has logged it several times after sunset. The programmes are mainly Greek folk music and the identification sounds like *Radiophonikos Stathmos Chidas*. Has anyone heard this station? There is nothing listed on 1610, the highest MW channel being 1603.

Stations along the east coast of North America can be logged for about one hour before sunrise during July. European interference is light at this time owing to the approaching daylight from the east while QRM from inland North America is absent, enabling stations that would be classed as 'difficult' in winter, to be heard. Look for *WHAM* Rochester NY on 1180; *WLIB* New York City 1190; *KCW* Moncton N.B. 1220; *WSYB* Rutland Vermont 1380; *WNJR*, the all-negro station in Newark N.J. 1430; *CBG* Gander Newfoundland 1450; *WHEC* Rochester NY 1460; *WPTR* Albany NY 1540 mixed with *ZNSI* Nassau Bahamas. Those right on the top of the band are usually prominent, such as *WSFR* Ft. Lauderdale Florida 1580; *WSMN* Nashua N.H. and *WAKR* Akron Ohio, both on 1590 and *CJRN* Niagara Falls Ontario 1600. Nearer home on the periphery of Europe are three A.F.R.T.S. stations not normally heard except at sunrise in summer. These are *Kenitra* Morocco 1484; *Lajes Terceira* Azores 1500 and *Tripoli* 1594.

CHARLES MOLLOY

# AUDIO EXPANDER COMPRESSOR


C.R. Bradley

ALMOST every audio source can benefit from a degree of compression or expansion of the volume range. The unit described here provides a variable amount of compression or expansion with low distortion and can be added to almost any sound system. It can be an additional 'luxury' control (like the tone controls) in a hi-fi system, or it can have more important uses in tape recording, pop music and radio communication as will be described. It can also be used to sustain notes played on an electric guitar, or give a tape recorder automatic level control.
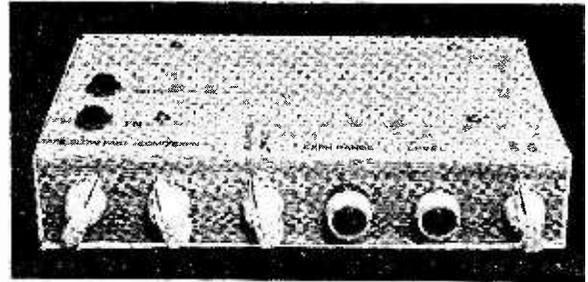
## PRINCIPLE

The level of an audio signal may be controlled by passing it through a stage with variable gain. A simple example is the volume control in a radio receiver, if we can regard it as a stage on its own—see Fig. 1a. When the slider is at the bottom end of the track, the gain of the stage is zero and the output signal is zero. When the slider is at the top end of the track, the gain is unity (disregarding loading effects) and the output signal is maximum. The range of gain is 0 to 1 and it is controlled by mechanical action on the control spindle. Note that if the slider is left in a certain position, say half way along the track (gain =  $\frac{1}{2}$ ), the *dynamic range* (volume range) of the signal is not affected. Thus if the input level doubles the output level doubles also, regardless of the control setting (except at zero of course).

Now suppose the volume control in Fig. 1a could be turned up when the input level is low and turned down when the level is high, all this to be done automatically without noticeable delay. The output level could then be held constant in spite of wide variations in the input level. This would be *volume compression* or reduction of the dynamic range. Conversely, if the volume control could be turned



down when the input level is low and turned up when the level is high we would get *volume expansion* or exaggeration of the dynamic range.

Either of these processes can properly be called a.v.c. (automatic volume control). The circuit in a radio receiver which maintains a constant r.f. input to the detector is sometimes misnamed the a.v.c. circuit; it is more correctly a.g.c. (automatic gain control) applied to an r.f. stage, whereas a.v.c. is

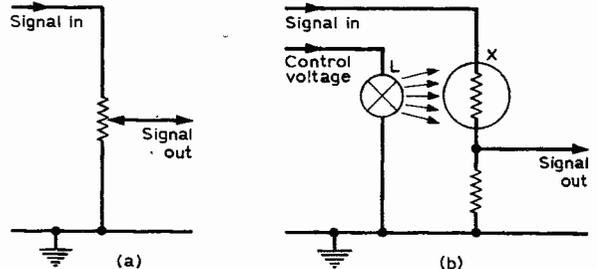


Fig. 1: A standard volume control and a simple method of audio expansion or compression using an L.D.R.

a.g.c. applied to an a.f. stage.

It might be thought possible to obtain volume compression or expansion by driving the volume control in Fig. 1a with a servo motor. Unfortunately, any practical mechanical linkages would have significant inertia and friction and the system would be too slow to keep up with fast volume changes. Therefore it is necessary to design a stage whose gain can be controlled electrically. But before considering all-electric stages, the circuit in Fig. 1b provides an interesting use of light for a.v.c. X is a cadmium sulphide photocell and L is a lamp mounted close to it. The lamp brilliance depends on the control voltage. When the control voltage is high the lamp shines brightly and the resistance of

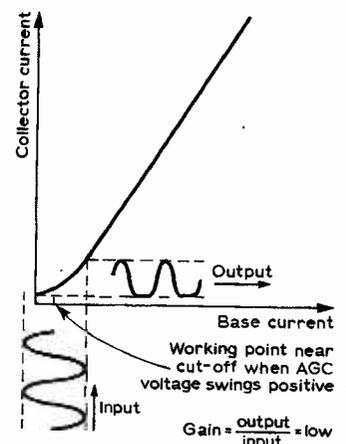
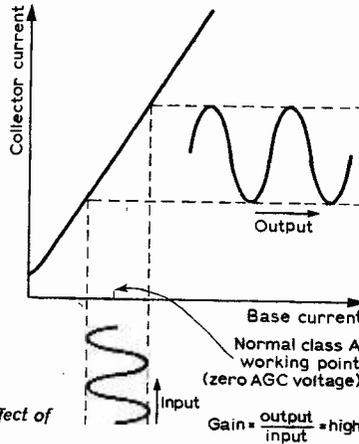
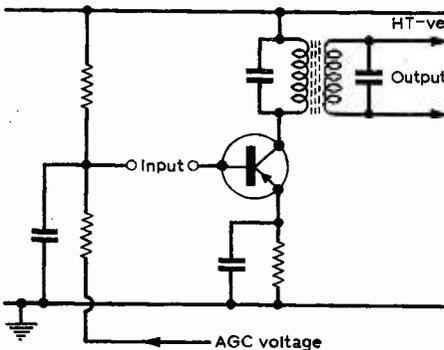


Fig. 2: Radio receiver a.g.c. circuit and graphs showing effect of a.g.c. on gain.

X is low, resulting in a high output level. When the control voltage is low the lamp shines dimly and the resistance of X is high, resulting in a low output level. This arrangement is often used in remote volume control applications and in some audio compressor and expander circuits. The lamp and photocell can be bought as a single sealed unit for this use. After experiment, this circuit was discarded in favour of the circuit to be described because the power consumption of the lamp is high and the relation between the control voltage and the output level is very non-linear. Also the heat mass of the lamp filament and the photocell characteristics introduce a delay in response.

## VARIABLE GAIN STAGES

The gain of a class A amplifier stage can be varied by moving the bias toward cut-off. This is a type of gain control used in radio a.g.c. circuits—see Fig. 2. This circuit has the disadvantage of severe distortion of the output waveform when the stage is near cut-off. In a tuned r.f. stage this distortion is tolerable as the next tuned circuit will eliminate harmonics and restore the sine waveform. But the distortion is excessive for a full range a.f. stage, particularly in an audio compressor where the stage would be biased near cut-off when the input signal was at maximum.

Another circuit which was investigated is shown in Fig. 3. This is a long tailed pair where the audio signal is passed through one of the transistors (Tr2). When the control voltage swings negative, Tr1 turns

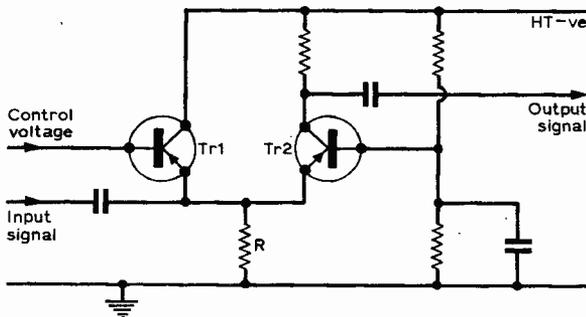


Fig. 3: Two transistors connected as a long tailed pair can control dynamic range but only at low input levels.

on. As Tr2 base is held at constant potential, the increased voltage drop across R biases Tr2 toward cut-off and the audio signal is attenuated. This circuit gives a good performance but the input signal must be small to avoid distortion.

The final choice of circuit is shown in Fig. 4. It

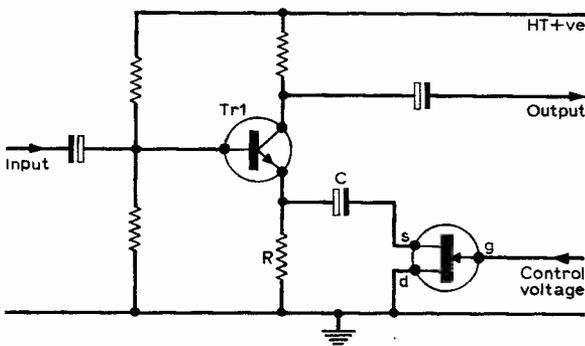


Fig. 4: The basic control circuit used in the final circuit.

is a conventional common emitter amplifier with a field effect transistor placed in series with the emitter bypass capacitor. The f.e.t. is used as a variable resistor controlled by the gate voltage. When the gate voltage is zero, the source-to-drain resistance is low and Tr1 emitter is fully decoupled by C. When the gate voltage swings negative, the resistance rises so that the decoupling action of C on Tr1 emitter is reduced. The gain of the stage is now reduced by negative feedback from the unbypassed emitter resistor R.

It will be noticed that the f.e.t. is being used to control alternating current. The circuit was first tried with an additional resistor from h.t. positive to the f.e.t. source to give a steady d.c. bias. This was discarded when it was found that as the f.e.t. is basically a symmetrical device, it can be used on a.c. In this circuit the source and drain leads can be swapped with no great effect on performance, although one arrangement is slightly better with the low cost f.e.t. specified—which is not specified as a symmetrical type in any case.

The main advantage of this circuit is the low distortion over a wide range of signal level. The transistor is always biased in class A where distortion is minimum. Unlike any of the previous circuits, the distortion *reduces* as the gain is reduced; this is due to the increased negative feedback from R. This makes it particularly suitable for an audio compressor. The transistor and the f.e.t. also provide useful amplification of the audio signal and the control voltage respectively.

## COMPRESSOR CIRCUIT

The arrangement for audio compression is shown in Fig. 5. The output signal is sampled by a single stage amplifier A. This provides a signal across R1 which is rectified by D to give a negative-going voltage across the diode load R2. Audio frequency components are smoothed by C1 to produce the steady control voltage which is fed to the f.e.t. gate. Since the gate impedance of the f.e.t. is very high, the attack/decay time of the compressor is determined by the values of R3 and C2. The graph in Fig. 6 illustrates the action of compression. When the input signal is low, the f.e.t. gate voltage  $V_g$  is between 0V and -2V and the transistor gives a high gain.

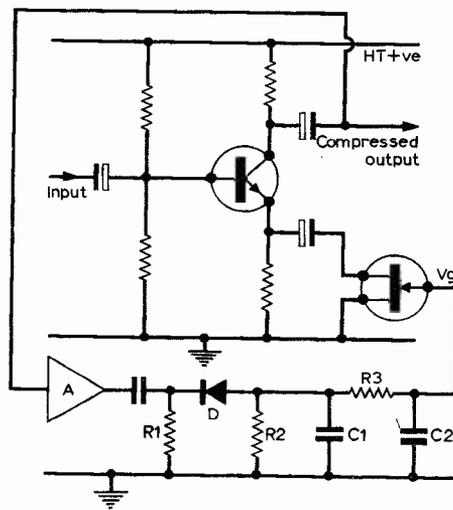


Fig. 5: The compressor circuit principle.

When the input signal level rises so that the gate voltage passes from  $-2V$  to  $-3V$  the gain is progressively reduced. Higher signal levels cannot be further compressed as the f.e.t. has already blocked all the emitter decoupling. However, distortion due to clipping only sets in with very high signal levels.

The flattish portion of the solid curve in Fig. 6

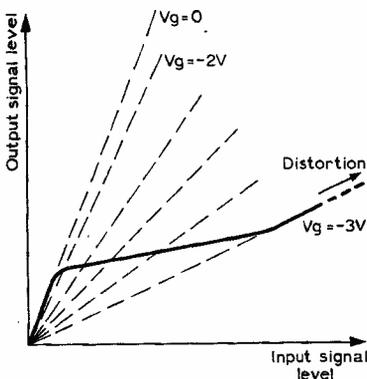



Fig. 6: The dashed lines on the graph show the audio stage gains at different f.e.t. gate voltages for the circuit in Fig. 5.

shows the range of compression. The higher the gain of amplifier A the flatter it will be and the greater will be the degree of compression. As A samples the compressed output and not the input signal, the circuit cannot 'over compress' strong signals no matter how high the gain of A, i.e. it is impossible for the curve to slope downwards from left to right.

It must be understood that the non-linearity of the curve in Fig. 6 does not cause harmonic distortion in the output signal as it represents a non-linear *volume* response, not instantaneous response. The time constant  $R3/C2$  is chosen so that the gate voltage does not change appreciably during even the longest (bass) audio cycles. The instantaneous response curve at any time is one of the dashed lines in Fig. 6, and these are linear.
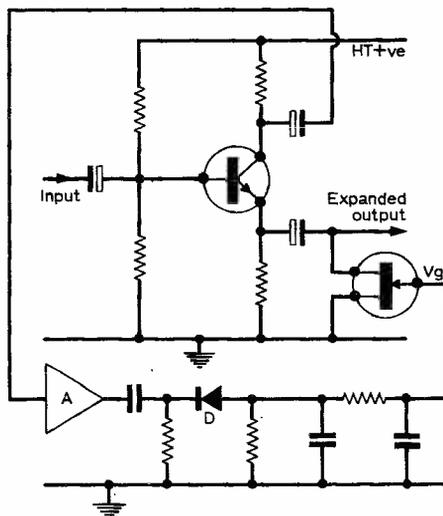
## EXPANDER CIRCUIT

Although audio expansion has simply the reverse effect of audio compression, the circuit design is not as simple as this might suggest. We might try to use the circuit in Fig. 5 but with a negative bias on the f.e.t. gate and the diode D reversed. The transistor would then give a low gain on weak signals and a high gain on strong signals, as desired. Unfortunately a positive feedback loop exists. A strong signal causes the gate voltage to swing towards zero which increases the gain; this increases the signal sampled by A which drive the gate voltage further towards zero and so on. The arrangement gives a squelch action illustrated in Fig. 7a i.e.: signals below a threshold level are amplified with low gain and signals above the threshold level are amplified with high gain.



Although squelch has its own uses it is not the kind of volume expansion required.

The same arrangement is more workable if the signal sampled by A is the unexpanded input signal; this removes the positive feedback loop. However, a very high gain is required in A and the expansion proves to be very non-linear (Fig. 7b).

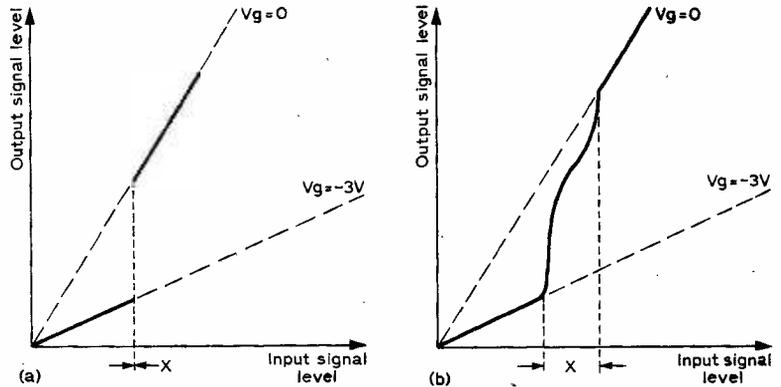


Fig. 7: Volume expansion characteristics of circuits discussed in text. In (a) expansion operates over an infinitely small range; in (b) the range is real but expansion is non-linear.

The solution to the requirement for linear volume expansion over a wide range is shown in Fig. 8. This is in fact the volume compression circuit with the output taken from a different point. When the input signal level is low, the f.e.t. gate voltage is near zero and therefore the source to drain impedance is low compared to the output impedance of Tr1 acting as an emitter follower. Hence the output level is low. When the input signal level is high, the f.e.t. gate is driven negative and the source to drain impedance is high; hence the gain of the circuit increases to unity. Amplifier A is part of a negative feedback loop as it samples the *compressed* signal at Tr1 collector; this feedback ensures linear expansion of the signal.

## FINAL CIRCUIT

The final compressor/expander circuit is shown in Fig. 10. The variable gain stage is formed by Tr1 and Tr2 (f.e.t.) with S1 selecting compression or expansion. The compressed signal at Tr1 collector


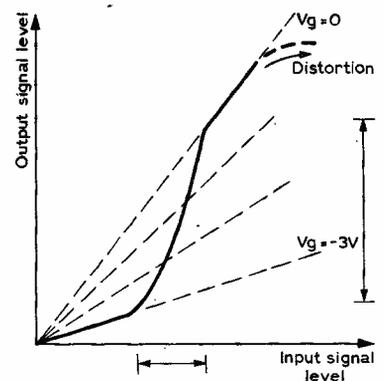
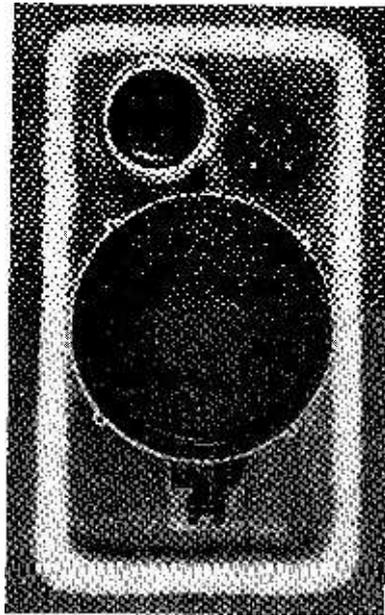


Fig. 8: (left) Expansion circuit principle. Fig. 9: (above) The arrows on the graph show how a small range of volume in the input is expanded to a wider range.
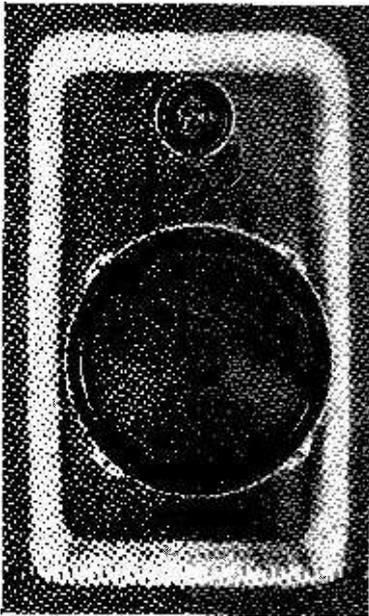
# Two new Build-it-yourself speaker kits from Wharfedale

"Why don't you produce kits for bigger speakers?"  
people asked us when Unit 3 proved such a success.  
We hope you'll like our answer—Unit 4 (2-speaker floor

standing system) and Unit 5 (3-speaker monitor system).  
So if you're a high fidelity enthusiast who enjoys  
building his own equipment, send for details.



## Unit 4 full range floor standing system.

2 speakers (12" Bass and 3" Treble)  
to give full range, balanced  
reproduction.

Frequency response of 45-17,000  
Hz. when housed in suitable cabinet.

Superior 4-element crossover unit  
ensures optimum performance  
from each speaker.

Rec. Retail Price £16-0-0

All kits include speakers, crossover network, acoustic  
wadding, mounting bolts and connecting wire, together  
with full assembly instructions. No expert technical  
knowledge needed.



## Unit 5 the monitor system you can build yourself.

3 speakers (12" Bass, 5" Mid-Range  
unit, and 1" Treble) give clean,  
smooth performance.

Frequency response of 40-20,000  
Hz. when housed in suitable cabinet.

Unique mechanical/electrical 6  
element crossover unit.

Rec. Retail Price £23-10-0.



■ ■ ■ ■ ■ CUT HERE ■ ■ ■ ■ ■

**To: Rank Wharfedale Ltd., Idle, Bradford.**

■ Please send me leaflets describing your speaker kits.

■ Name (Block capitals, please).....

■ Address.....

.....


P.W.7/7

the true sound in High Fidelity



Rank Wharfedale Ltd.,  
Idle · Bradford · Yorkshire

Fig. 10: The complete circuit of the audio expander/compressor. Components within the dotted line are mounted on the P.C. board.

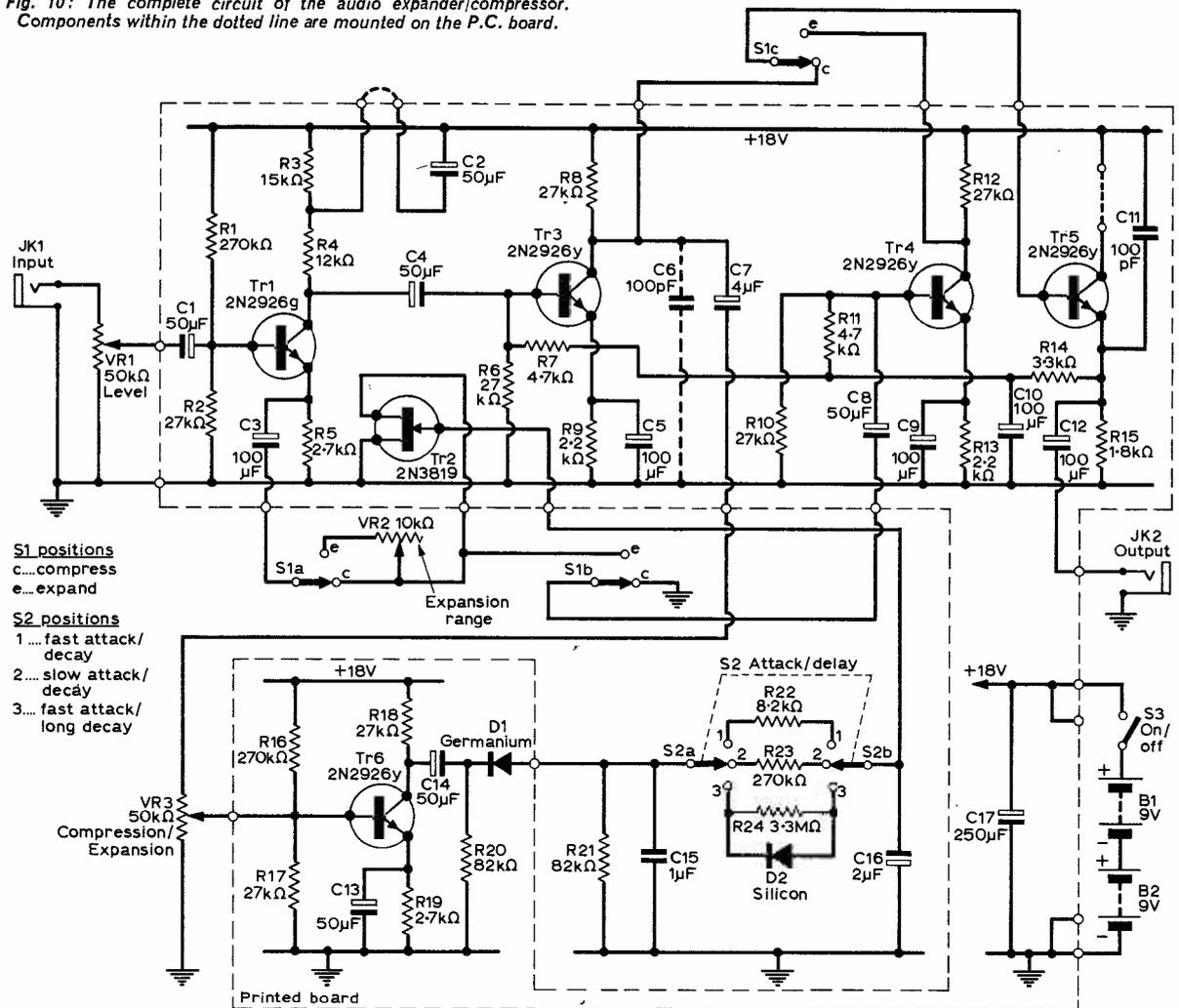

is amplified by Tr3 and fed via C7 and VR3 to Tr6 which is the amplifier A in Fig. 4. The degree of compression (or expansion) is controlled by VR3. The signal at Tr6 collector is rectified by D1, smoothed by C15 and fed to the f.e.t. gate via one of the sets of time constant components selected by S2.

For compression, the signal at Tr3 collector is also taken directly to the base of emitter follower Tr5 which provides a low impedance output on JK2; in this mode Tr4 has no function.

For expansion, the signal at Tr1 emitter is used as described in Fig. 8. This signal is taken through VR2 and C8 to Tr4 base. The signal at Tr4 collector is taken directly to the base of output stage Tr5. The potentiometer VR2 works only on expansion; its resistance forms a potential divider with the varying source-to-drain resistance of the f.e.t. and it is used to set the range of expansion. All the transistors are working as Tr3 is still delivering a compressed signal to Tr6.

Base bias for both Tr3 and Tr4 is provided via R14 from Tr5 emitter; Tr5 forms a d.c. feedback pair with either Tr3 or Tr4 on compression or expansion respectively.

It is possible to experiment with the time constant components selected by S2 to obtain any desired

attack/decay characteristic; some quite complex networks might be used here to obtain a particular result. The values of R22 to R24 shown in Fig. 10 have been chosen to give the following choice of characteristics in conjunction with C16. In position 1 of S2, C16 can rapidly charge and discharge through R22. The compressor/expander therefore has as fast a response to volume changes as is possible without feedback arising from audio frequencies reaching Tr2 gate. In position 2 of S2, R22 is replaced by a higher value R23 resulting in a slower response. Position 3 of S2 gives a special attack/decay characteristic intended for automatic level control use with a tape recorder (S1 switched to compression).

The compressor responds very quickly to an increase in signal volume when forward current flows in D2 to charge C16 negatively, but C16 can only discharge very slowly through R24 as the leakage current of the f.e.t. gate is negligible. Hence the f.e.t. gate voltage depends on the peak volume level. This characteristic is ideal for the purpose since volume peaks are quickly brought down to a constant level to avoid over-modulating the tape, but the gain does not increase much during lower level sound passages. Thus the dynamic range of the material recorded is not greatly affected.

## BSR 4-SPEED SUPERSLIM AUTO RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 13 1/2" x 11 1/2" x 4 1/2". Above motor board 3 1/2" below 2 1/2". AC 200/250V.



with STEREO/MONO XTAL £6.19.6 Post 5/6

BSR UA70 Stereo/Mono Transcription Auto Changer. Calibrated Stylus Pressure. £12.19.6

BSR Minioplayer UA60 Stereo/Mono. £7.19.6 Size 12 x 8 in. AC 200/250V. Post 5/6.

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk II £14.19.6. AT80 Mk II £14.19.6. Model 3000 £12.19.6. Post 5/6.

RECORD PLAYER PORTABLE CABINET Space for amplifier and autochanger. Post 5/-.

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made and tested. A 2-stage unit using triode pentode valve, giving 3 watts output. Tone and volume controls. Isolated mains transformer. With 400mA loudspeaker and valves 6X12, 6Z80. Frequency response 50-12,000 cps. Sensitivity 200mV. 5/6. 89/6

R.C.S. TEAKWOOD BASE. Ready cut out for mounting (State player make and model) 77/6

R.C.S. PLASTIC COVERS FOR ABOVE BASES. Durable tinted plastic, attractive appearance. 77/6

EMI PICK-UP ARM. Complete with mono cartridge 29/6.

EMI JUNIOR 4 SPEED RECORD PLAYER. Mains operated motor, turntable and pick up complete. Post 5/6. 59/6

HI-FI PICK UP CARTRIDGES. GP94 55/-; GP93 45/-; GP91 30/-; GP67 19/6. ACOS L.P. only 10/6. All standard fixing complete with stylus.

### CRYSTAL MIKE INSERTS

1 1/2" dia. 6/6. ACOS 1 1/2" dia 12/6. BMS3, 1" dia. 9/6.

## PORTABLE AMPLIFIER

Portable mini p.a. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive resin covered cabinet, size 12 x 9 x 4 in., with powerful 7 x 4 in. speaker and four transistor one watt power amplifier. Uses PP3 battery Brand new in Maker's carton with full maker's guarantee. World famous make.



Only 75/- Post 5/-

### WEYRAN P50-TRANSISTOR COILS

RA2W Ferrite Aerial 12/6 Spare Cores ..... 6d.  
Osc. P50/LAC ..... 5/4 Driver Trans. LEDT4 ..... 9/6  
L.F. P50/BCC 470 kc/s. 5/7 Printed Circuit, PCAL ..... 9/6  
3rd LF. P50/SCC ..... 6/- J.B. Tuning Gangs ..... 10/6  
P51/1 or P51/2 ..... 5/7 Weyran Booklet ..... 2/-  
P51/3 ..... 6/- OPTI ..... 10/6  
Ferrite Rod 8 x 1/4 in. 4/-, 6 x 1/4 in. 5/-.

### VOLUME CONTROLS

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 3/-, D.P. 5/-  
STEREO L/S 1 1/2". D.P. 15/-  
Edge SK. SP. Transistor, 5/-  
WIRE-WOUND 3-WATT POTS. WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 Ohm to 30 K. LONG SPINDLE 10 OHMS to 100 K. 8/- Carbon 30 K to 2 meg. 5/-

### VEROBOARD 0.15 MATRIX

2 1/2 x 5 in. 3/8. 2 1/2 x 3 1/2 in. 3/8. 3 1/2 x 3 1/2 in. 3/8. 3 1/2 x 5 in. 5/2. EDGE CONNECTORS 18 way 5/-, 24 way 7/8. PINS 36 per packet 3/4. FACE CUTTERS 7/8.  
S.R.B.P. Board 0.15 MATRIX 3 1/2 in. wide 6d. per lin., 3 1/2 in. wide 9d. per 1 in.; 5 in. side 1/- per lin. (up to 17 in.). S.R.B.P. undrilled 1 in. Board 10 x 5 in. 3/-.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 3 1/2 in. sides. 7 x 4 in. 6/-; 11 x 3 in. 7/6; 14 x 7 in. 9/6; 13 x 5 in. 10/6; 15 x 14 in. 15/-; 20 x 7 in. 8/6; 14 x 11 x 3 in. 14/6.  
ALUMINIUM PANELS 18 s.w.g. 12 x 12 in. 6/6; 14 x 9 in. 5/6; 12 x 8 in. 4/6; 10 x 7 in. 3/6; 8 x 6 in. 2/6; 6 x 4 in. 1/6.

1-inch DIAMETER WAVE-CHANGE SWITCHES. 2-p. 2-way, or 2-p. 2-way, or 3-p. 4-way 4/6 each. 1-p. 12-way, or 4-p. 2-way, or 4-p. 3-way 4/6 each. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 12/-, 2 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 36/-.  
TOGGLE SWITCHES, sp. 2/6; sp. dl. 3/6; dp. 3/6; dp. dt. 4/6.

### ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms Super Sensitive. 35/-  
LOW RESISTANCE HEADPHONES 3-5 ohms. 39/6  
DE LUXE PADDED STEREO PHONES 8 ohms. 79/6

### "THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



200/250 v. A.C. Leaflet S.A.E.

Post 2/6

## ★ GENERAL PURPOSE TRANSISTOR PEE AMPLIFIER BRITISH MADE ★

for Mike, Tape, P.U., Guitar  
Battery 9-12v. or H.T. line 200-300V D.C. operation. Size 1 1/2" x 1 1/2" x 1". Response 2 c.p.s. to 25 Kc/s. 26 db gain. For use with valve or transistor equipment. Full instructions. Brand new. Guaranteed. 17/6 each  
Details S.A.E.

NEW TUBULAR ELECTROLYTICS	CAN TYPES
2/850V .. 2/ 100/25V .. 3/	18-18/500V 11/-
4/350V .. 2/6 250/25V .. 2/6	50-50/350V 7/6
8/450V .. 2/6 500/25V .. 4/-	60-100/350V 11/6
16/450V .. 3/- 8-8/450V .. 3/6	32-32/250V 3/6
32/450V .. 4/- 8-16/450V .. 4/-	32-32/450V 6/6
25/25V .. 2/- 18-18/450V 5/-	32-32+32/850V 0/9
50/50V .. 2/- 32-32/50V 5/-	100-50+50/850V 9/6

SUB-MIN. ELECTROLYTICS 1, 2, 4, 8, 16, 25, 50, 100, 200F 15V. 2/-; 500F 15V 3/6; 1000F 15V 5/6; 2000F 15V 7/6. CERAMIC 1P/F to 0.01 MF, 8d. Silver Mica 2 to 5000P.F. 9d. PAPER 350V-0.1 9d. 0.5 2/6; 1mF 3/-; 2mF 150V 3/-; 500V-0.001 to 0.05 8d.; 0.1 1/-; 0.25 1/6; 0.47 5/6; 1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1, 2/6. SILVER MICA. Close tolerance 1% 2.2-500pF 1/6; 500-2,200 pF 2/-; 2,700-5,300pF 4/-; 6,300pF-0.01, mill 6/-; each. TWIN GANG. "0-0" 208pF+176pF. 1 1/2". Slow motion drive 365+365 with 25+25pF, 1 1/2"; 500pF slow motion, standard 9/-; small 3-gang 500pF 22/-.

SHORT WAVE. Single 25 pF 11/-  
CHROME TELESCOPIC AERIAL 23in. 5/-  
TUNING. Solid dielectric. 500pF, 500pF, 7/- each.  
RESISTORS. Compression 10, 50, 70P 1/-; 100P 150pF, 1/6; 250P 1/6; 600P, 750P, 2/-; 1000 P, 2/6.  
RECTIFIERS CONTACT COOLED 1/2 wave 60mA 7/6; 85mA 9/6. SILICON BYZ13 6/-; BY100 10/-.  
Full wave Bridge 75mA 10/-; 150mA 19/6; TV rects. 10/-.  
NEON PANEL INDICATORS 250V AC/DC Red, Amber 4/-.  
RESISTORS. Precision 10, 100, 1000 Ohm 10 cent. 1/4; 1 w. w. w. 20%; 3d. 1 1/2; 5d. 2 w. w. 1/-; 1 w. 10% 6d. HIGH STABILITY. 1 w. 1% 10 ohms to 10 meg. 2/-.  
Ditto 5% Preferred values 10 ohms to 22 meg. 9/-.  
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K. 2/- each; 25 watt. 1 ohm to 3.2 ohms 2/-.

## Q MAX CHASSIS CUTTER


Complete: a die, a punch, an Allen screw and key  
1 in. 16/-; 1 1/2 in. 17/6; 1 1/2 in. 18/6; 1 1/2 in. 24/-; 2 1/2 in. 24/6; 3 in. 19/6; 3 1/2 in. 19/6; 4 in. 19/6; 4 1/2 in. 21/6; 5 in. 21/6; 5 1/2 in. 21/6; 6 in. 21/6; 6 1/2 in. 21/6; 7 in. 21/6; 7 1/2 in. 21/6; 277 in. 21/6; 277 1/2 in. 21/6;
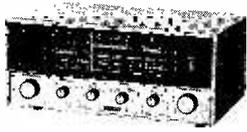
# Never Built a Kit Before?

Why not prove how easy it is the HEATHKIT way.  
Build one of these beginner kits.



**Stereo Record Player**  
Kit K/SRP-1 £27.6.0  
Carr. 11/-




**Economy SW Receiver**  
Kit K/GR-64 £24.16.0  
Carr. 9/-



**Deluxe Car Radio**  
Kit K/CR-1 (less Spk.)  
£12.12.0  
Carr. 5/-



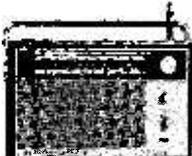**Versatile Service VVM**  
Kit K/IM-18U £16.14.0  
Carr. 5/-



**Severn AM/FM Radio**  
Kit K/Severn £18.18.0  
Carr. 5/-



**Car Tune-up Meter**  
Kit K/ID-29 £17.8.0  
Carr. 5/-



**Model Builders Tacho**  
Kit K/GD-69  
£11.0.0  
Carr. Paid



**D.I.Y. 2-Speaker System**  
Kit K/SCM-3 (less cab)  
£12.6.0  
Carr. 6/-

## Many more kits in the FREE CATALOGUE

Please send me FREE Catalogue.

NAME .....

ADDRESS .....

Post Code .....

25/8

**HEATH (GLOUCESTER) LTD.**

**GLOUCESTER GL2-6EE**




a Schlumberger Company

**HOME RADIO (Components) Ltd.,**  
Dept. PW., 234 London Road, Mitcham CR4 3HD.  
Phone 01-648 8422.



- A** Purchase a Home Radio Catalogue, using the Coupon below. Please enclose a cheque or postal order for 12/6 (8/6 plus 4/- packing & postage). Your catalogue will be sent by return of post.
- B** Choose your components. In the Home Radio Catalogue over 8,000 components are listed and more than 1,500 illustrated. A comprehensive index helps you to locate your requirements easily.
- C** Join our Credit Account Service. Full details are enclosed with every catalogue.
- D** Order your components. Having joined our Credit Account Service, you may order either by phone or post. If you phone out of office hours, a recording machine takes your message.
- E** Get started on that project! Whether it's constructing or servicing work, the fact that you can obtain the right components easily, without having to chase from shop to shop, will put you in the right frame of mind to make a better job of it.

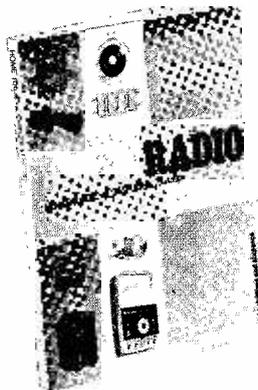

Whether or not you want to use the Credit Account Service mentioned above, you certainly need the Home Radio Components Catalogue, if you construct or repair radio, television and electronic gadgets. By the way, the catalogue contains six vouchers, each worth a shilling when used as instructed, and with the catalogue we supply a 30-page Price Supplement and a Bookmark giving electronic abbreviations.

**Post the Coupon today, with 12/6**

*The price of 12/6 applies only to catalogues purchased by customers residing in the U.K.*

Please write your Name and Address in block capitals

Name .....

Address .....



**HOME RADIO (Components) LTD.,**  
Dept. PW., 234-240 London Rd., Mitcham, CR4 3HD

The value of R24 can be increased to give an even longer discharge time for C16. The combination of R24 and silicon diode D2 (low leakage) can be replaced by a germanium diode (higher leakage) but this prevents any experimentation with R24.

## CONSTRUCTION

Most of the components are carried on a printed circuit board shown in Fig. 11. The board and the controls are mounted in a two piece aluminium box (see Fig. 12) for effective screening. The author used a separate component for the ON/OFF switch S3; this results in a rather large number of knobs on the front of the unit and it might be preferable to have a third 'OFF' position on S1. In this case S1 would need to be a 4-pole 3-way type.

Arrangements have been made for readers to obtain the printed board ready made and drilled

from the suppliers listed in the parts list. If making the board oneself, the pattern of conductors shown in Fig. 11 should be traced and the resist painted on the copper in a mirror image of the pattern.

The transistor types used, viz: 2N2926 (popular plastic silicon planar) and 2N3819 (general purpose f.e.t.) are available cheaply from advertisers in the magazine. Ensure that the electrolytic capacitors and the semiconductors are wired with correct polarity as indicated in Fig. 11. All components should be soldered quickly and with short leads. The germanium diode D1 is the only component where particular care should be taken to avoid heat damage. The wiring between the board and the controls should be short and the indicated leads screened as shown. All earth connections are made to a common point, the body of VR1.

The inclusion of C11 should be sufficient to ensure stability if the layout is followed.

If instability arises due to poor layout or the use of higher gain transistors, a 100pF capacitor C6 can be added between earth and Tr5 base (connect at S1) or in the position shown on the printed circuit (normally unoccupied). The compressor/expander should remain stable even with an overload input.

Two links are shown on the printed circuit. When the link between C2 negative and R3/R4 is made, the gain of the unit is reduced slightly but the range of compression or expansion is increased. The link between Tr5 collector and the positive line may be opened to measure Tr5 collector current. This should be around 3.5 mA in both compress and expand positions of S1.

Under some conditions, it may be possible to drive the circuit into low frequency oscillation when VR3 is fully on (clockwise). Some improvement in this, and in the circuit's recovery time from an extreme overload, can be found by wiring a low-wattage 2.7V zener diode across C16 (positive to positive).

## USE

For compression, the unit is set up as follows. Start with S1 at COMPRESS, VR1 (LEVEL) anticlockwise and VR3 anticlockwise. Feed the


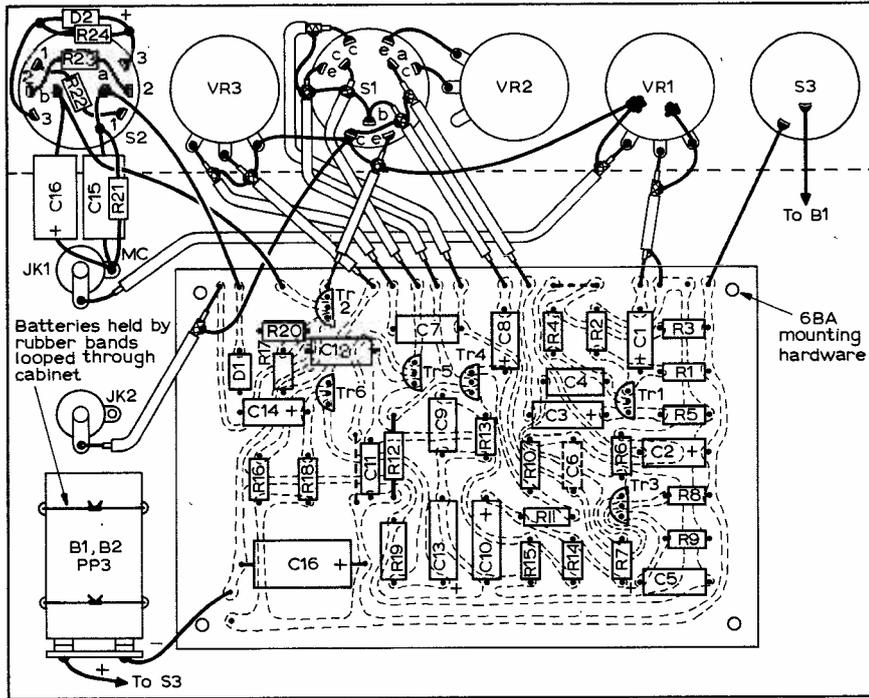


Fig. 11: The component layout. Using the recommended P.C. board makes for easy construction and a neat final layout.

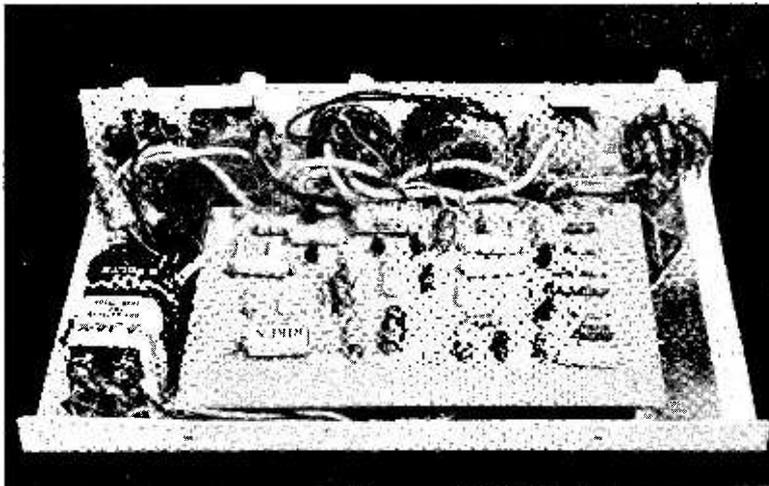

◀ Interior view of the completed project. Compare this with Fig. 11.

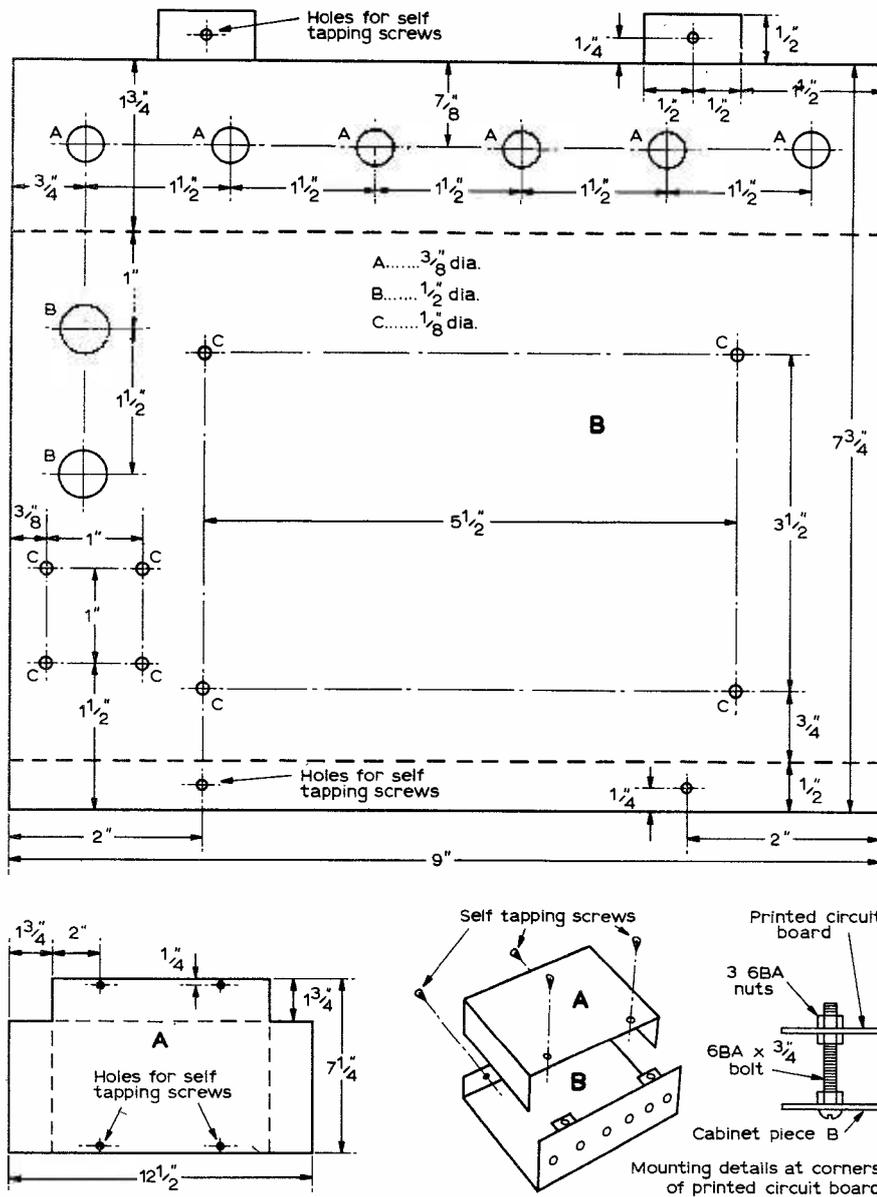


Fig. 12: The cutting and drilling details of the two piece aluminium cabinet.

signal input to JK1. The unit can be driven by a dynamic microphone, electric guitar, magnetic pick-up, tuner, etc. A crystal microphone or pickup can also be used but a resistor of 47kΩ to 220kΩ should be put in series with JK1 to reduce distortion. The output at JK2 may be fed to any valve or transistor amplifier. Advance VR1 (LEVEL) until the lowest level sound passages are reproduced at the desired volume. Then advance VR3 until the louder passages are sufficiently compressed.

Expansion is a little harder to set up as VR1, VR2 and VR3 have interdependent effects. With S1 at EXPAND and VR3 anticlockwise, set VR2 for the desired range of expansion, from slight (anticlockwise) to extreme or 'squelch-like' (clockwise). Advance VR1 until the lowest level sound passages are just audible. Then advance VR3 until the louder passages are sufficiently expanded.

If a voltmeter is available, the voltage across C16 can be monitored. Note that the internal resistance of a moving coil voltmeter will affect the attack/decay times. A change in signal level is expanded or compressed when it causes a voltage change in the range 1.8V to 2.5V d.c.

## APPLICATIONS

Volume compression can be applied usefully to almost any audio signal where full reproduction of the dynamic range is not essential. Compression reduces the demands made on audio equipment and on the listener. In the extremes, 'loud' sounds are prevented from causing overload distortion while 'quiet' sounds are not lost. The use of compression for tape recorders has already been mentioned and is a great help when recording 'wild' sounds out of doors. Some further applications are described below.

Compression is useful in a public address system as it compensates for poor microphone technique. Intelligibility is improved and this may enable the amplifier to be used at lower gain with consequently less risk of feedback howls.


Compression can be used in radio communication to increase 'talk power' (intelligibility) over a noisy channel. It is preferable to speech clipping as it does not introduce harmonic distortion. A combination of compression and clipping would give excellent intelligibility over a poor quality speech link.

Compression can be useful to the hard of hearing who may need to listen to radio or television at an uncomfortably high volume (to others) in order to hear everything. If the dynamic range of the material is compressed, the annoyance caused to others by peak sound levels is reduced.

Compression is used in commercial record making where the dynamic range of the material to be recorded exceeds the range that can be cut on the record. Pop music often employs a high degree of compression; in this way the 'backing' sound can be recorded at full level without drowning out the singer. Even the most idolised groups usually provide live performances which seem 'weak' compared with their recorded offerings; compression can provide

# DISCOSOUND

## DJ DISCO-AMP

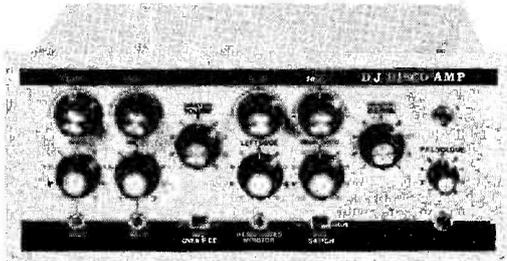

The DJ Disco-amp has been designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

The pre-amp section features independent inputs and volume controls for two mics with separate bass, treble and master volume, plus two independent inputs and volume controls for turntables, again with separate bass, treble and master volume controls.

A complete Pre-fade listen (P.F.L.) cueing monitor section is also featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half so that mic announcements may be made over the music without altering the volume controls.

The power amplifier section has an output of 70 watts R.M.S. into 8 ohms and has elaborate protection against thermal, short or open circuit. The unit is designed for panel mounting.

### SPECIFICATION


Output power	70 watts R.M.S. $\pm$ 1db at 8 ohms.
Frequency response	30-20,000 Hz $\pm$ 3 db.
Harmonic distortion	Less than 1% at full output.
Signal/noise ratio	Better than - 65db.
Speaker impedance	8-16 ohms.
Headphone impedance	8-16 ohms.
Bass control	Variable 20 db at 100 Hz.
Treble control	Variable 20db at 10 kHz.
Inputs:	Mic 1 & 2 5 mV at 50 K ohms.
turntable	1 & 2 100mV at 1 meg ohm.

50 ohm or 600 ohm mic inputs may be ordered at extra cost.  
Size: Front Panel 16 $\frac{1}{2}$ " x 7". Cut out 15 $\frac{1}{2}$ " x 6". Fuses: A.C. 1.5 amp (B.S.) mounted on back panel.

**PRICE £85.0.0 inc. P & P.**
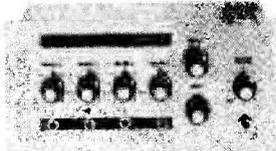
## DISCOSOUND PRE-4


This is a four channel fully mixable pre-amp, with separate treble, bass and master volume controls, and is completely self powered. All four inputs are by standard jack socket on the front panel with the addition of inputs 3 and 4 being duplicated on the back panel, with two paralleled outputs also featured for versatility in use. Frequency response: 30-20,000 Hz  $\pm$  3db. Signal/Noise Ratio: -65db. Size: front panel 12 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " cut out required 11 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ ". Completely built and tested.



**PRICE £18.0.0 inc. P & P.**

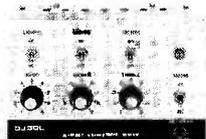
## DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation. Completely built and tested



**PRICE £37.10.0 inc. P & P.**

## DJ 70S INTEGRATED MIXER-AMPLIFIER

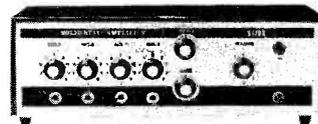

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70 watts R.M.S.) a frequency response (30-20,000 Hz  $\pm$  3db) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs etc., or anywhere that high quality high output is required. Size: 15 $\frac{1}{2}$ " x 5" x 6".

**PRICE £55.0.0 inc. P & P.**

Also available DJ105S 30 watt P.A. Amplifier. Similar specification to above.

**PRICE £35.0.0 inc. P & P.**

## DISCOSOUND 70 MAIN AMPLIFIER

A 70 watts RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000 Hz  $\pm$  2db. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound PRE-4, or can be used with any other high quality pre-amp control unit. Size: 7" x 9" x 6". Completely built and tested on steel Chassis.

**PRICE £30.0.0 inc. P & P.**

*For full details of these and all Discosound Products write direct to:—*

**DISCOSOUND, 122 BALLS POND ROAD, LONDON, N.1. Tel: 01-254 5779**

Full money back guarantee if returned within 10 days.

All Discosound Products are guaranteed for 12 months.

Demonstrations given at any time.

# ELECTROVALUE

EVERYTHING BRAND NEW & TO SPECIFICATION • LARGE STOCKS

## BARGAINS IN NEW SEMICONDUCTORS all power types supplied with free insulating sets

1N914	1/3	2N3706	3/3	40512	45/8	BC147	3/8	BFY61	4/3
1N3754	4/-	2N3707	4/-	40602	9/8	BC148	3/3	BX520	3/9
1N4148	1/9	2N3708	3/-	AC107	14/8	BC149	3/8	BY164	10/-
1N6054	4/-	2N3709	3/-	AC126	6/6	BC153	10/-	BY288	3/6
1S940	1/-	2N3710	3/6	AC127	6/-	BC154	11/-	CI06B1	14/6
2N696	0/6	2N3711	3/11	AC128	6/-	BC157	3/9	MC140	5/-
2N697	5/6	2N3731	24/-	AC176	11/-	BC158	3/6	MJ480	21/-
2N706	2/9	2N3794	3/8	ACY22	3/9	BC159	3/9	MJ481	27/-
2N1302	4/-	2N3819	9/8	ACY40	4/-	BC167	2/6	MY491	30/-
2N1303	4/-	2N3820	25/6	AOY41	5/-	BC168	2/3	MFP102	7/6
2N1304	4/6	2N3904	7/6	AD142	14/3	BC169	2/6	NKT403	15/6
2N1305	4/6	2N3906	7/6	AD149	17/6	BC177	6/3	NKT405	15/-
2N1306	6/9	2N4088	5/3	AD181/AD182	7/-	BC178	5/8	OA47	1/9
2N1307	6/9	2N4059	4/-	(matched) 18/- pr	7/-	BC179	6/-	OA90	1/3
2N1308	8/9	2N4080	4/3	AF114	7/-	BC182L	4/3	OA91	1/3
2N1309	8/9	2N4061	4/3	AF115	7/-	BC183L	2/3	OA95	1/3
2N1613	6/-	2N4062	4/3	AF116	6/6	BC184L	2/6	OA99	3/-
2N1711	7/-	2N4284	3/3	AF117	6/6	BC186	8/6	OA200	1/11
2N2147	18/9	2N4286	3/3	AF124	7/6	BC212L	5/-	OA202	2/-
2N2218	9/3	2N4289	3/3	AF127	7/-	BC213L	5/-	OC71	5/6
2N2270	12/9	2N4291	3/3	AF138	9/6	BC214L	6/3	TP1E1A	17/6
2N2484	13/6	2N4282	3/3	AF180	18/6	BCV70	5/3	TP32A	23/6
2N2646	10/9	2N4410	4/9	AF239	9/9	BD121	18/-	TI843	10/6
2N2904	11/-	2N5062	12/3	AF228	6/6	BD123	24/3	ZTX300	3/6
2N2924	4/-	2N5163	5/-	ASY27	8/3	BD124	16/-	ZTX301	3/6
2N2925	4/6	2N5192	25/-	ASY28	6/6	BF167	8/6	ZTX302	4/6
2N2926	2/3	2N5195	28/3	B0041	15/-	BF178	10/6	ZTX303	4/6
2N3033	5/6	2N5467	9/9	BA102	9/-	BF180	12/-	ZTX304	6/9
2N3054	14/3	2N5458	9/9	BA166	4/-	BF194	7/-	ZTX500	5/-
2N3055	16/-	2N5459	9/9	BA130	4/6	BF195	7/6	ZTX501	5/-
2N3225	10/9	40250	14/3	BA145	5/6	BFX29	10/9	ZTX502	6/9
2N3663	11/6	40361	12/6	BC107	2/9	BFX84	7/5	ZTX503	5/-
2N3702	3/6	40362	16/-	BC108	2/6	BFX85	8/3	ZTX504	5/-
2N3703	3/3	40409	19/3	BC109	2/9	BFX87	8/3	ZTX505	12/-
2N3704	3/9	40408	14/6	BC125	12/-	BFX88	6/9	ZTX530	5/5
2N3706	3/5	40480	37/-	BC126	12/-	BFY50	4/6	ZTX531	6/9

## PEAK SOUND PRODUCTS

### ENGLEFIELD CABINET KITS

Build it 12 + 12 or 25 + 25



Stereo amplifier in modular kit form 12 watts per channel £38/9/-; 25 watts £58/15/- Cabinet kit only £6. These prices nett.  
As recently reviewed in Hi Fi Sound.

### BAXANDALL SPEAKER SYSTEM

Designed by Peter Paxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 16Ω 69RM109 speaker Unit. Kit £18/12/- nett; built £19/8/8 nett.

### STEREO AMPLIFIER S.A. 10-10.

Developed from the very successful SA.8-8 amplifier giving first class stereo amplification featuring separate volume controls for each channel, bass and treble controls, 10 watts per channel into 5 to 8Ω. Kit £19/7/6 nett; built £24/16/8 nett. Suitable 8Ω wide range speakers available £13/15/- each nett.

### MAINLINE AMPLIFIER KITS

RCA/868 designed main amplifier kits. Input sensitivity 500-700mV for full output into 8Ω. Power Kit price including power supply components kit

12W	140/- nett	98/-
25W	185/- nett	N/A
40W	195/- nett	115/1
70W	210/- nett	131/-

### 30 WATT BAILEY AMPLIFIER KIT

Special summer reduction (to Sept. 30th 1970 only) Sensitivity 1.2V for full output into 8Ω Transistors for one channel £7/5/8 list; £6 only nett. Transistors for two channels £14/11/- list £11 only nett. Capacitors and resistors (metal oxide) 30/- per channel nett. Complete unregulated power supply kit 37/6 nett

### ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 80V 4/6 each 1W: 6.8V to 82V 9/- each 1.5W: 4.7V to 75V 12/- each Clip to increase 1.5W rating to 3 watts (type 266F) 9d.

### CARBON TRACK

#### POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level. Single gang linear 220Ω to 2.2MΩ 2/6  
Single gang log 4.7KΩ to 2.2MΩ 2/6  
Dual gang linear 4.7KΩ to 2.2MΩ 8/6  
Dual gang log 4.7KΩ to 2.2MΩ 8/6  
Log/Antilog 10K, 47K, 1MΩ only 8/6  
Any type with 1/4 D.P. mains switch, extra 2/6  
Please note: only decades of 10, 22 and 47 are available within ranges quoted.

### CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 200K, 470K, 1M, 2M2, 5M, 10MΩ Vertical or horizontal mounting 1/- each.

### COMPONENT DISCOUNTS

10% on orders for components for 25 or more. 15% on orders for components for 115 or more (No discount on nett items).

### POSTAGE AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82Ω-220KΩ	E12	18	16	15
C	1/8W	5%	4.7Ω-330KΩ	E24	2-5	2	1-75
C	1/4W	10%	4.7Ω-10MΩ	E12	2-5	2	1-75
C	1/2W	5%	4.7Ω-10MΩ	E24	3	2-5	2-25
C	1W	10%	4.7Ω-10MΩ	E12	6	5	4-5
MO	1/2W	5%	10Ω-1MΩ	E24	3		7
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12		15d all quantities	
WW	3W	5%	12Ω-10KΩ	E12		15d all quantities	
WW	7W	5%	12Ω-10KΩ	E12		18d all quantities	

Codes: C = carbon film high stability low noise  
MO = metal oxide Electrosl TR5 ultra low noise  
WW = wire wound Plessey.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1d. on total resistor order)

### MULLARD polyester C280 series

250V 20%: 0-01; 0-022; 0-033; 0-047 8d ea. 0-068; 0-1 9d ea., 0-15 11d., 0-22 11-, 10%; 0-33 1/5, 0-47 1/3, 0-68 2/3, 1μF 2/9, 1.5μF 4/2, 2.2μF 4/9.

### MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 1/3 each  
Values (μF/V): 0-04/64; 1/40; 1-6/25; 2.5/16; 2.5/84; 4/10; 4/40; 5/64; 8.4/64; 6.4/28; 8/4; 8/40; 10/25; 10/18; 10/64; 12.5/25; 15/40; 20/16; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/25; 50/64; 50/25; 50/40; 64/4; 64/10; 80/25; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 160/25; 200/64; 200/10; 250/4; 320/25; 320/64; 400/4; 500/2.5.

### LARGE CAPACITORS

High ripple current types: 1000/25 5/8; 1000/50 8/2; 1000/100 16/3; 2000/25 7/4; 2000/50 11/4; 2000/50 11/4; 2000/100 22/8; 2500/64 15/8; 2500/70 19/8; 5000/25 12/6; 5000/50 21/11; 5000/100 58/3; 10000/15 17/-; 10000/25 24/6; 10000/50 44/-; 10000/70 61/-.

### MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 2/-; 100/25 2/-; 100/50 2/6; 250/25 2/6; 330/25 2/6; 500/50 3/9; 500/25 3/9; 500/50 4/6; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-.

### SMALL ELECTROLYTICS

Axial leads: 4.7/10; 4.7/25; 5/50 1/- ea. 10/10; 10/25; 10/50; 33/10; 50/10 1/- ea. 25/25; 25/50; 47/25; 100/10; 220/10 1/3 ea.

## INTEGRATED CIRCUIT AMPLIFIERS

SINCLAIR IC10 complete with instruction book giving amplifier circuit details and range of applications. 50/6 nett.

FLESSEY SL403A only 48/6 each. 3W into 7.5Ω for 18V supply. Application data sent with two more.

## WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W 4/9 each

## SLIDER SWITCHES D.P.D.T.

3/- each

## NEON INDICATOR LAMPS

all 200/250V. Square bezel, red only 3/9  
Round chrome bezel red, amber, clear 4/9 each

Toggle switches, 250V a.c. 1.5A. chrome dolly and chrome milled nut S.P.S.T. 3/9; S.P.D.T. 4/5/9; D.P.D.T. 5/9; S.P.D.T. centre off 5/-.

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only 30/- Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC only 50/- post free. Full range stocked.

# ELECTROVALUE

(Dept. PW.8) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY.  
Hours: 9-5.30: Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3) Telex 264475

some improvement here. The usual technique seems to be to overload amplifiers and speakers to a ludicrous extent, presumably to achieve volume compression by extreme clipping! A local pop group has been experimenting with a prototype of the compressor/expander and are enthusiastic about it. The effect of extreme compression on the sound of an electric guitar is to sustain the notes played; the

## ★ components list

### Resistors:

R1	270k $\Omega$	R13	2.2k $\Omega$
R2	27k $\Omega$	R14	3.3k $\Omega$
R3	15k $\Omega$	R15	1.8k $\Omega$
R4	12k $\Omega$	R16	270k $\Omega$
R5	2.7k $\Omega$	R17	27k $\Omega$
R6	27k $\Omega$	R18	27k $\Omega$
R7	4.7k $\Omega$	R19	2.7k $\Omega$
R8	27k $\Omega$	R20	82k $\Omega$
R9	2.2k $\Omega$	R21	82k $\Omega$
R10	27k $\Omega$	R22	8.2k $\Omega$
R11	4.7k $\Omega$	R23	270k $\Omega$
R12	27k $\Omega$	R24	3.3M $\Omega$

All resistors  $\frac{1}{4}$  watt, 10% tolerance.

VR1	50k $\Omega$ 10g.
VR2	10k $\Omega$ 10g.
VR3	50k $\Omega$ 10g.

### Capacitors:

C1	50 $\mu$ F 6V	C9	100 $\mu$ F 6V
C2	50 $\mu$ F 10V	C10	100 $\mu$ F 6V
C3	100 $\mu$ F 6V	C11	100 $\mu$ F ceramic
C4	50 $\mu$ F 10V	C12	100 $\mu$ F 10V
C5	100 $\mu$ F 6V	C13	50 $\mu$ F 6V
C6	100pF ceramic	C14	50 $\mu$ F 10V
	—see text	C15	1 $\mu$ F paper
C7	4 $\mu$ F 15V	C16	2 $\mu$ F 6V
C8	50 $\mu$ F 10V	C17	250 $\mu$ F 20V

### Switches:

S1	3-pole 2-way rotary
S2	2-pole 3-way rotary
S3	Single pole on/off (or see text)

### Semiconductors:

Tr1	2N2926G (green)
Tr2	Texas 2N3819 (f.e.t.)
Tr3	2N2926Y (yellow)
Tr4	2N2926Y (yellow)
Tr5	2N2926Y (yellow)
Tr6	2N2926Y (yellow)
D1	OA70, OA91 or any germanium diode.
D2	1N914 or any silicon diode.

### Miscellaneous

JK1, JK2, jack sockets; B1, B2, PP3 9V batteries; printed circuit board\*; knobs; battery clips etc.

\* The printed wiring board is available from: Walsall Timing Developments Ltd., Hall Lane, Walsall Wood, Staffs for 10s. post paid. Delivery 7-10 days.

result is more like an organ than a guitar. Compression also removes the need to change the amplifier gain between playing accompaniment and single note solos.

Compression has a side effect of worsening the apparent signal to noise ratio of an audio system. This happens because hum and noise are amplified at high gain during silent passages when they are most noticeable.

Volume expansion is not quite as useful as compression as most audio material already has a wide

dynamic range. It can be used to counteract previous volume compression when replaying records or tapes. Expansion has a remarkable side effect of improving the apparent signal to noise ratio of an audio system. This is because the gain is only high when the signal level is high, and hum and noise are not very noticeable at this time. This effect reduces the fatigue of listening to short wave signals against a noisy background, although any fading will be exaggerated.

If VR2 is set for the maximum degree of expansion, the circuit behaves similarly to a squelch. The usefulness of squelch in muting radio receiver noise when no signal is present has already been described in Practical Wireless October 1969. ■

## GENETRACER—continued from page 270

It is recommended that the instrument be tested on a radio receiver in known working order, first injecting a signal from the "generator" at the control grid (valve receivers) or base (transistor receivers) at each stage in turn, listening to the resultant response in the receiver's speaker.

## ★ components list

### Resistors:

R1	1.5k $\Omega$	R7	33k $\Omega$
R2	270k $\Omega$	R8	10k $\Omega$
R3	150k $\Omega$	R9	2.7k $\Omega$
R4	1.5k $\Omega$	R10	470 $\Omega$
R5	47k $\Omega$	R11	12k $\Omega$
R6	4.7k $\Omega$	R12	2.2k $\Omega$
		R13	39 $\Omega$

All  $\frac{1}{4}$ W 10%

VR1/SW1 1M $\Omega$  pot. with switch  
VR2/SW2 100k $\Omega$  pot. with switch

### Capacitors:

C1	0.002 $\mu$ F 500VW mica
C2	0.01 $\mu$ F 150VW ceramic
C3	0.005 $\mu$ F 150VW ceramic
C4	10 $\mu$ F 15VW electrolytic
C5	0.001 $\mu$ F 500VW mica
C6	2 $\mu$ F 15VW electrolytic
C7	30 $\mu$ F 15VW electrolytic
C8	8 $\mu$ F 15VW electrolytic
C9	50 $\mu$ F 15VW electrolytic
C10	100 $\mu$ F 25VW electrolytic

### Semi-conductors:

Tr1, 2, 3	OC71
Tr4	OC72
D1	OA81

### Miscellaneous:

Paxolin panels: 1 off 10 x 8in x  $\frac{1}{16}$ in. 2 off 6 x 2 $\frac{1}{2}$ in. x  $\frac{1}{16}$ in. Reel of "Cir-Kit" adhesive connector strip.  
T1—Transistor output transformer OC72 to 3 $\Omega$  speaker. Speaker, 3 $\Omega$  impedance. PP3 battery and connector. 2 control knobs. 2 Coaxial sockets, chassis mounting. 2 Coaxial plugs. 2 lengths TV coaxial cable about 12 to 18in long. 4 crocodile clips.

Now switch off the "generator", switch on the "tracer", and listen to the signal at the input and output of each stage in the receiver, on the tracer's own speaker. Finally, try the effect of injecting a signal from the "generator" at the input side of a receiver stage, simultaneously listening to the output in the "tracer's" speaker. ■

SUMS

plus

CIRCUITS

equals

UNDERSTANDING

# PART 5 (FINAL)

LESLIE MOORE

## FEEDBACK

THE operation of amplifying circuits with feedback can be analysed quite simply using a few basic principles. Figure 5.1 shows an amplifier of gain 'A' with a feedback network which has a gain, or attenuation, of 'B'.

Because most amplifiers have negative feedback we will assume that the voltage fed back will be subtracted from the input voltage, and by algebraic manipulation we arrive at the formula.

$$V = V_{IN} - B \times V_O \dots\dots\dots(1)$$

This means that the voltage actually fed into the amplifier is less than the voltage supplied.

We can say that because the amplifier has a gain of A,

$$V_O = A \times V \dots\dots\dots(2)$$

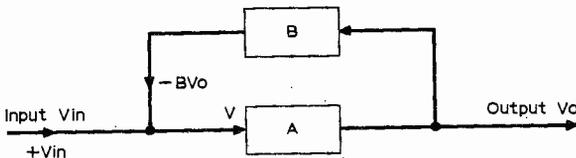


Fig. 5.1. Basic circuit of a feedback network

As we require a relationship between the output,  $V_O$ , and input,  $V_{IN}$ , we must manipulate the terms in equations (1) and (2) to contain only constants and variables  $V_{IN}$  and  $V_O$ .

From equation (2),  $V = \frac{V_O}{A} \dots\dots\dots(3)$

and substituting equation (3) into equation (1) gives:

$$\frac{V_O}{A} = V_{IN} - B \times V_O$$

rewriting

$$V_O \left( \frac{1}{A} + B \right) = V_{IN} \therefore V_O \left( \frac{1+AB}{A} \right) = V_{IN}$$

$$\therefore \frac{V_O}{V_{IN}} = \frac{A}{1+AB} = \text{gain with negative feedback}$$

From this formula it would appear that the application of negative feedback would reduce gain.

e.g. if  $A = 100, B = \frac{1}{100}$

$$\frac{V_O}{V_{IN}} = \frac{100}{1+1} = 50$$

This is a disadvantage. However, a very important advantage of applying negative feedback can be demonstrated quite easily.

Bandwidth was defined as the frequency range between the half power points. Suppose at the 3dB point of an amplifier the power gain was 50

$$\text{or} = 10 \log_{10} 100 - 10 \log_{10} 2 \\ = 20 - 3\text{dB}$$

Now at the same frequency with negative feedback applied, the amplifier gain would be

$$\text{Gain} = 10 \log_{10} \frac{A/2}{1 + A/2B}$$

If  $B = \frac{1}{100}$  then gain with feedback becomes:-

$$10 \log_{10} 50 - 10 \log_{10} \left( 1 + \frac{1}{2} \right) \\ = 16.99 - 1.76\text{dB}$$

It can be seen by comparing the amplifier gains at the same frequency, the reduction of gain with feedback applied is only 1.76dB, indicating that the -3dB point occurs at a higher frequency at the upper half power point and a lower frequency at the lower half power point. Therefore, although the mid-band gain has been reduced, bandwidth has been increased.

It would seem logical that by applying positive feedback gain would increase and bandwidth reduce. This is so, in fact if sufficient positive feedback is applied to an amplifier, gain would be so far increased and bandwidth reduced that the amplifier would become unstable and produce oscillations. This is not a particularly good way of producing oscillations of predetermined signals—there are numerous other more reliable methods.

## Oscillators

Oscillators which produce sinusoidal waveforms, can, in general, be simplified to an amplifier and feedback network as shown in Fig 5.2.

Usually the amplifier will produce an output voltage 180° out of phase with an input voltage. For oscillations to be self sustaining the feedback network should produce the amplifier's input voltage from its output voltage, therefore the feedback network should also produce a 180° phase shift to compensate for amplifier phase shift. Another governing factor is that any losses which are present in the feedback network must be compensated for by the amplifier gain.

—continued on page 309

### MICRO SWITCH

5 amp. changover contacts, 1/9 each, 18/- doz. 15 amp Model 2/- each or 21/- doz.



### TOGGLE SWITCH

3 amp 250v. with fixing ring, 1/8 each, 15/- doz.

### CONSTRUCTORS PARCEL

1. Plessey miniature 2 gang tuning condenser with built in trimmers and wave gang switch. 2. Ferrite slab aerial with coils to suit the above tuning condenser. 3. Circuit diagram giving all component values for 6 transistor circuit covering full medium wave and the long wave band around Radio 2. The three items for only 7/6d which is half of the price of the tuning condenser alone.

### 10 AMP 24V BATTERY CHARGER

Ideal unit for garage, boat station etc. £22.10.0d. each plus carriage and cost.

### BEHIND THE EAR DEAF-AID

Made by a very famous maker. Thoroughly overhauled, cleaned and re-conditioned. Guaranteed 6 months. Regular price around £50. Our price £20.10.0d.

### ISOLATION TRANSFORMERS 200-250 Mains

A must if you work on mains equipment. Prevents accidents and shocks even in damp conditions. Input and output separately screened by connection block. 100 watt £23.10.0. 250 watt 25.

### SLOW MOTION DRIVERS

For coupling to tuning condensers etc. One end .5in. shaft, the other end fits to a .5in. shaft with grub screws. Price 4/6 each 48/- dozen.

### LARGE PANEL MOUNTING MOVING-COIL METERS

Size 5in. x 4in. Centre zero 200-0-200 micro amp made by Sangamo Weston. Regular price probably £8. Our price 59/6. ditto but 100-0-100 79/6.

### A.C. Ammeter 0-5 amps. flush mounting—moving iron. Ex equipment but guaranteed perfect 29/6.

### CIRCUIT BOARDS

Heavy copper on 3/32 paxolin sheet ideal for making power packs etc. as sheet is very strong and thick enough to allow copper to be cut away with hacksaw blade. 5in. x 5in. 1/6 each. 15in. x 5in. 4/6d. each.

6KVA Auto-transformer in ventilated sheet steel case—110v-140v-170v-200v-230v. Ex equipment but guaranteed perfect £19.10.0. carriage at cost.

### PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.



### REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

- Miniature.** .5in. long x approximately .4in. diameter. Will make and break up to 1A up to 300 volts. Price 2/6 each. 24/- dozen.
- Standard.** 2in long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each. 18/- dozen.
- Flat.** Flat type, 2in. long, just over 1/16in. thick, approximately .5in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each. 23 per dozen.
- Small ceramic magnets to operate these reed switches 1/9 each. 18/- dozen.

### 0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/8 each, 24/- doz.



### SUB-MINIATURE MOVING COIL MICROPHONE

as used in behind the ear deaf aids Acts also as earphone size only .5in. x .5in. x .5in. Regular price probably £3 or more. Our price 19/6. Note these are ex-equipment but if not in perfect working order they will be exchanged.

**Chart Recorder Motor.** Small 2" diameter (approx) instrument motor with fixing flange and spindle (1/4" long, 1/4" diameter) integral gear box gives 1 rev per 24 hours. 19/6.

**Ignition (E.H.T.) Transformer** made by Parmeko Ltd., Primary 240V 50 cps. Secondary 5KV at 23 mA. Size approx. 4 1/2" x 3 1/2" x 2 1/2" thick. 29/6 plus 4/6 p. & p.



### 12V EXTRACTOR FAN BY DELCO

Ideal for ventilation in Caravan, Car or Boat. 6 Bladed 6" diameter fan inside heavy duty cylinder with 3 point fixing flange. 5 1/2" diameter fixing hole. Length approx. 8 1/2". Exceptional bargain 27/6 plus 5/6 post and insurance.

4 Push Switch. Ideal to control fan Heater, etc. 3 on switches and 1 off. Contacts rated at 15 amp on all switches. 4/6 each, 48/- doz.

### INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. The ICs are all single silicon chip General Purpose Amplifiers. Regular price of which is well over £1 each. Full circuit details of the ICs are included and in addition you will receive a list of 50 different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only £23 post paid; or list at all data 10/- post free. Credited when you order IC's value of 50/- and upwards.



### 24 HOUR TIME SWITCH

Mains operated. Adjustable Contacts give 3 on/off per 24 hours. Contracts rated 15 amps, repeating mechanism so ideal for shop window control, or to switch ball lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 with Perspex cover, plus 3/6 postage and insurance, a real snip which should not be missed.



### DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets and on/off switch with neon warning light (in metal box). Takes standard 13 amp fused plugs. Supplied complete with 7 feet of heavy cable. 39/6 wired up, ready to work plus 4/6 post & insurance. 5 amp 3 pin model 25/-, 15 amp 3 pin model 45/-

### BARGAIN OF THE YEAR

#### MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2 in.—complete with soft leather zipped bag. Specification:— Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kc/s. Sensitivity: 5 mv/in. Intermediate frequency: 455 Kc/s or 455 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly offered without guarantee except that they are new. Price only 24/6 plus 2/6 post 6/ for £7 post free.



#### THE 5-5 WATT STEREO AMPLIFIER

Made by one of our most famous makers for a de-luxe player. This amplifier has a quality of reproduction much better than average. Using a total 16 transistors and a generously sized mains power pack. Controls include bass, treble, balance and volume. Suitable for 8-16 ohm impedance speakers with crossovers for tweeter mid-range and bass thus giving option of 1, 2 or 3 speakers per channel. Offered at about one third of its original price only £9.19.6d. plus 6/6d post and insurance.

### OUT OF SEASON BARGAIN

#### 3kW TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 59/6. 2kW. Model as above except 2 kilowatts 39/6. Postage and insurance 6/6. Don't miss this.



### THIS MONTH'S SNIP

#### AUTO ELECTRIC CAR AERIAL

With dashboard control switch—fully extendable to 40" or fully retracted. Suitable for 12v positive on Neg earth—supplied complete with fitting instructions and wired rear dashboard switch £5.18.6d. plus 5/-.



#### 1 HOUR MINUTE TIMER

Made by famous Smiths company, this has a large clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch 22/6.



#### 3 STAGE PERMEABILITY TUNER

This Tuner is a precision instrument made by the famous "Coydon" Company for the equally famous Radomobile Car Radio. It is a medium wave tuner (but set of long wave coils available as an extra, (if required) with a frequency coverage 1620 Kc/s-625 Kc/s and intended to operate with an I.F. value of 470 Kc/s. Extremely compact (size only 2 1/2 x 2 1/2 in. thick) with reduction gear for fine tuning. Snip price this month 12/6, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier. Post Free.



### RECORD CHANGER BARGAIN

THE "PRINCESS" 4 SPEED AUTOMATIC RECORD CHANGER. Will take up to ten records which may be mixed, stylus brush cleans stylus after each playing, other features include pick-up height adjustment and stylus pressure adjustment. Beautifully styled and really fine looking, this is a high class expensive instrument, but you can purchase this month for only 49/6 + 5/6 p. & p. One point—these changers have been to France and back and the journey may have loosened screws or otherwise put them slightly out of adjustment. However, with each we supply 16 page service manual and fault finding chart with which you could completely rebuild the changer. So don't miss this real bargain which is available until the end of August. 49/6 + 10/6 p. & p. 200-240V.



Where postage is not stated then orders over 25 are post free. Below 25 add 2/9 Semiconductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

### NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts. 1/8 each, 18/- doz. Plastic push-rod suitable for operating, 1/- each, 9/- doz.



### COMPUTER MULTI-CORE CABLES

12, 14/0076 copper cores, each one insulated by coloured P.V.C. then separately screened, the 12 metal braided cores laid together and P.V.C. covered overall making a cable just under 1/4 in. dia. but quite pliable. Price 7/6 per ft. Any length cut. Other sizes available 7 core 5/- ft., 6 core 4/- ft. 4 core 3/6 ft.

### INSULATED TERMINAL HEADS

Make your own terminal and save half the cost 2BA 6d. each 5/- doz. 4BA 5d. each 4/- doz.

### MAINS TRANSFORMER BARGAIN

Normal mains primary 250v tapped 230v—10M secondary 250-0-350 @ 150MA, 100v @ 20MA. 6.3v @ 3A 4v @ 2A—upright mounting size 5 x 4 x 3 1/2 approx. Price 35/- plus 7/6 post, etc.

### RING MAIN (13 amp) SPUR BOX


for joining water heaters—clocks and all auto devices to ring main—white bakelite, fused, made by G.E.C. 2/- each 18/- doz.
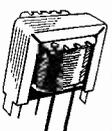
### 250v 150 amp CHANGE OVER SWITCH

Double pole with centre off—suitable reversing or series parallel circuits—useful for heating control and to prolong life of flood lamps—2/6 each 24/- doz.



Instrument Knobs. 1/2 in. dia. head with 1/2 in. shank for slotted 1/2 in. spindle, 9d. each, 8/- dozen. Ditto but with metal disc, 1/- each, 11/- dozen.



Midget Output Transformer. Ratio 140:1. Size approx. 1 1/2 in. x 1/2 in. x 1/2 in. primary impedance 450 Ohm. Secondary by flying leads. 4/6 each, 48/- doz.



Midget Input Transformer. Ratio 80:1. Size approx. 1 1/2 in. x 1/2 in. x 1/2 in. Primary impedance 132 Ohm. Printed circuit board connection. 5/6 each. 23 doz.



4-Gang Air Spaced Tuning Condenser for AM/FM circuits. AM rf section 200 pf sec section 80 pf both with trimmers.—FM rf section 8.5 pf sec section 1.2 pf—integral slow-motion drive 9/6 each.

### Mains Connector. A quick way to connect equipment to the mains safely and firmly—L, N, and E. coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire up to four 7.026 cables. 12/6 each.



### DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions and full instructions 19/6, plus 2/6 post and insurance. Made up model also available 37/6 plus 2/6 p. & p.



### CONTROL DRILL SPEEDS

### ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



**ELECTRONICS (CROYDON) LTD**  
Dept. PE, 266 London Rd., Croydon CRO 2TH  
Also 102/3 Tamworth Road, Croydon

The  
**RADIO  
CONSTRUCTOR**

**JULY ISSUE**  
features  
**The GLOBE RANGER**



**4-BAND SUPERHET**

This communications-type design offers reception over two short wave ranges, medium and long waves and incorporates a b.f.o. stage and an i.f. gain control. The complications of oscillator and aerial tuned circuit wiring are eradicated by the use of a ready-wired 4-band coilpack.

**'DISCOVERY' S.W.  
RECEIVER**

This design was featured in our March issue and proved to be a popular design for beginner constructors. In Further Notes, simple modifications are described which result in the addition of bandspread and headphone reception.

**PLUS**


- **OTHER PROJECTS  
AND FEATURES**
- **DATA SHEET No. 40**
- **ANNUAL INDEX**

**ON SALE NOW 3/6**

Copies may also be obtained direct from the Publishers 4/- including postage.  
Published by:

**Data Publications Ltd.  
57 Maida Vale, London, W.9**

**DIMMASWITCH**

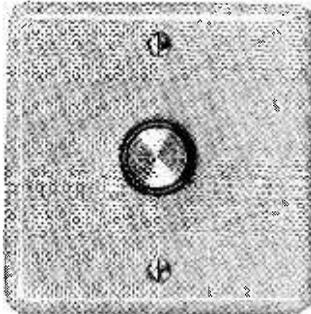

This is a dimmer of standard size in ivory and chrome to replace modern light switches without wiring change—controls 40-600V, 200/250V at 50Hz. of all lights except fluorescents.

Two models are available with on/off switch to control from maximum to zero.

DS500/2 at £3.12.6d. with clockwise or reverse dimming, with the switch at full reverse rotation.

DS500/2/P at £3.18s. uses a patented switch giving on/off control at any position of dimming.

Both are available in D.I.Y. kit form at 10/- less. Fuse protection is available at 2/6d. extra.

Please send C.W.O. to:

**DEXTER & COMPANY**

ULVER HOUSE, 19 KING STREET,  
CHESTER CH1 2AH  
Tel: Chester 25883

As supplied to H.M. Government Depts., Hospitals, Local Authorities, etc.

**NEW RANGE U.H.F. TV AERIALS**

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
Loft Mounting Arrays, 7 element, 40/-, 11 element, 47/6, 14 element, 55/-, 18 element, 62/6. Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6, 11 element, 55/-, 14 element, 62/-, 18 element, 70/-, Chimney Mounting Arrays, Complete, 7 element, 72/6, 11 element, 80/-, 14 element, 87/6, 18 element, 95/-, Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/-, State clearly channel number required on all orders.

**BBC - ITV AERIALS**



BBC (Band 1). Loft, 25/-, External S/D, 30/-, "H", £2.15.0. ITV (Band 3). 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 50/-, 5 element, 55/-, Combined BBC/ITV: Loft 1 + 3, 40/-; 1 + 5, 50/-; 1 + 7, 60/-; Wall mounting 1 + 3, 60/-; 1 + 5, 70/-; Chimney 1 + 3, 70/-; 1 + 5, 80/-, VHF transistor pre-amps, 75/-.

COMBINED BBC1 - ITV - BBC2 AERIALS 1 + 3 + 9, 70/-, 1 + 5 + 9, 80/-, 1 + 5 + 14, 90/-, 1 + 7 + 14, 100/-, Loft mounting only.

F.M. (Band 2). Loft S/D, 17/6, "H", 35/-, 3 element, 57/6. External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/6. Outlet boxes, 5/-, Diplexer Crossover Boxes, 17/6. C.W.O. or C.O.D. P. & P. 6/6. Send 6d. stamps for illustrated lists.

Callers welcomed — open all day Saturday

**K.V.A. ELECTRONICS (Dept. P.W.)**  
40-41 MONARCH PARADE  
LONDON ROAD, MITCHAM,  
SURREY O1-648 4884

**AUDIO EFFECTS**  
5 SHAW LANE, HALIFAX YORKS

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.  
**AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT.** No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils 2T, 0.5 to 1.54 Mhz 3T, 1.67 to 5.3 Mhz 4T, 5.0 to 15 Mhz 5T, 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 3 volt battery. Easy step by step instructions. Complete Kit, £8.19.6 plus 5/6 P. P. & Ins. Extra ranges 12/- per range.

**POWER CONTROLLER.** Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3kW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions 26/9. Ready built £9.4.6 plus 5/6 P. P. & Ins.  
**REVERBERATION AMPLIFIER.** Self contained transistorised battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2in x 3in x 4 1/2in. £10.4.0 plus 6/- P. P. & Ins.

**VOX SWITCH.** This sound operated switch is ideal for mobile TX work, record switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 42/6. Ready built, tested and guaranteed. 62/6, plus 2/6 P. P.

**METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive black and white polythene case. 37/6 post paid.

**MORSE OSCILLATOR.** PC board, transistors, high sub. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 25/- post paid.

**STRAIGHT FROM THE PRESS.** Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi Tape, etc. etc. 32/6 post paid.

**JUST ARRIVED IN STOCK.** Texas transistors. Complimentary symmetry. Driver. NPN. PNP output. The set of three ONLY 6/6 post paid.

Free lists with every order. For lists only send 1/6 (deductible from first order).

**NEW VALVES!**  
Guaranteed and Tested  
24-HOUR SERVICE

1B5 5/6	DL35 4/9	EL33 9/8	FL84 8/-
1B5 4/3	DL92 5/9	EL94 4/9	FL60 12/9
1T4 2/9	DL94 5/9	EY81 7/-	FL504 13/3
3B4 5/9	DL96 7/8	EY86 6/3	PY22 10/-
3V4 5/9	DY86 5/3	EZ80 4/3	PY83 10/-
6/30L2 11/6	DY87 5/3	EZ81 4/6	PY81 5/-
6AQ5 4/3	EA8C0 5/9	KT61 9/3	PY82 5/6
2SL6GT 4/6	EBC83 7/9	KT66 16/6	PY88 5/6
30C18 13/6	EB341 9/3	N78 17/-	PY88 6/6
30FL12 12/6	EBF80 6/6	PC86 10/3	PY800 7/6
30FL12 14/3	EBF89 5/9	PC88 10/3	PY801 6/3
30L15 12/9	ECC81 3/6	PC97 7/9	R19 6/9
30P4 11/9	ECC82 4/6	PC900 7/-	U25 12/9
30FL15 15/-	ECC83 4/9	PC884 6/3	U26 11/6
30FL14 14/6	ECC85 5/-	PC885 5/-	U28 11/6
30P19 11/9	ECH85 5/6	PCF80 5/11	U281 14/-
30PL12 12/6	ECH81 5/9	PCF801 6/6	U329 14/-
CC835 13/-	ECL80 6/6	PCF802 8/9	UAB80 6/6
CL83 17/6	ECL82 6/3	PCF805 12/9	UBC41 8/3
DAC32 6/9	ECL86 7/6	PCL82 6/9	UBF89 6/3
DAF91 4/3	EF87A 6/3	PCL83 11/9	UC85 7/3
DF96 7/8	EF89 4/6	PCL84 5/6	UC81 6/6
DF83 7/6	EF80 4/6	PCL85 8/6	UCL82 6/9
DF91 2/9	EF85 5/9	PCL86 8/-	UF41 10/6
DF96 7/-	EF86 6/3	PFL20011/6	UF89 6/-
DK82 6/6	EF89 4/9	PL86 9/3	UL41 11/9
DK91 5/6	EF183 5/6	PL81 8/-	UL84 6/3
DK92 8/3	EF184 6/-	PL82 5/9	UY41 7/-
DK96 7/8	EH90 6/-	PL83 6/3	UY85 5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any insured parcel against damage in transit 6d. extra. Office address, no callers.

**GERALD BERNARD**  
83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON, N.16

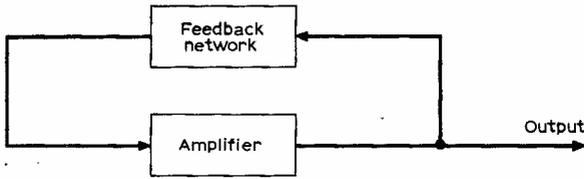


Fig. 5.2. Feedback network employed to produce an oscillator

Figure 5.3 shows the circuit diagram of a CR feedback network oscillator which can be analysed as follows.

R at the input of the amplifier should include the transistor input resistor and the biasing resistors in parallel. This circuit consists of a single stage amplifier providing a 180° phase shift and a 3-stage CR feedback network.

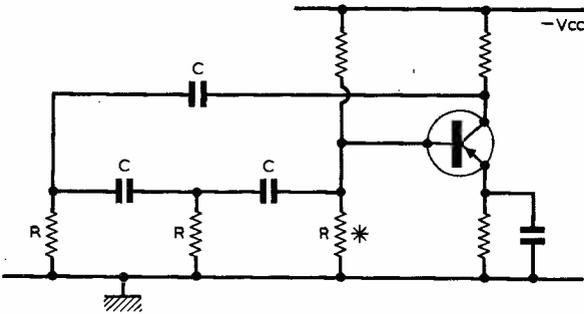


Fig. 5.3. Typical oscillator circuit utilising a CR feedback network

Neglecting the effects of the individual CR networks loading each other, each CR network will produce a 60° phase change as indicated by the vector diagram in Fig 5.4.

$$\text{Tangent } 60^\circ = \frac{\sqrt{3}}{1} = \frac{V_C}{V_R} = \frac{X_C}{R}$$

$$\text{but } X_C = \frac{1}{2\pi f C}$$

$$\therefore \sqrt{3} = \frac{1}{2\pi f CR}$$

therefore the frequency of oscillation,

$$f = \frac{1}{2\sqrt{3}\pi CR}$$

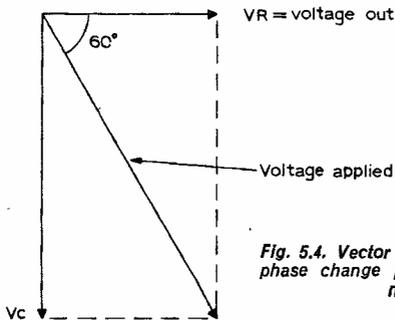


Fig. 5.4. Vector diagram showing 60° phase change produced by the CR network

For this circuit it can be shown that the amplifier must have a gain of slightly more than 29 to compensate for losses in the network.

The Wien bridge oscillator shown in Fig 5.5 is perhaps the most widely used for frequency generator circuits in test equipment as a wide range of frequencies can be generated by varying C and R values.

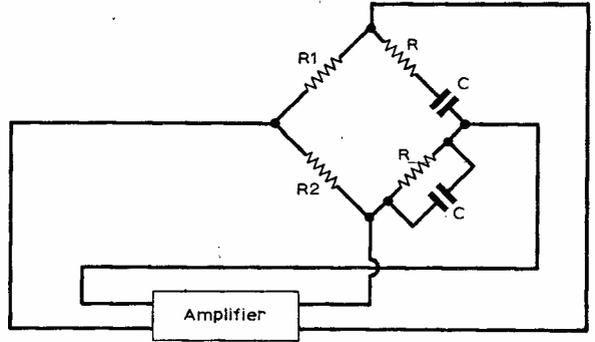


Fig. 5.5. Basic circuit of the Wien bridge oscillator

It can be shown by making the appropriate circuit assumptions that frequency of oscillation is given by:

$$f = \frac{1}{2\pi CR}$$

## Relaxation Oscillators

These are circuits which again involve feedback in amplifiers, but here switching of current flow is obtained by CR network feedback rather than by producing sinusoidal oscillations. Fig 5.6 shows the basic circuit.

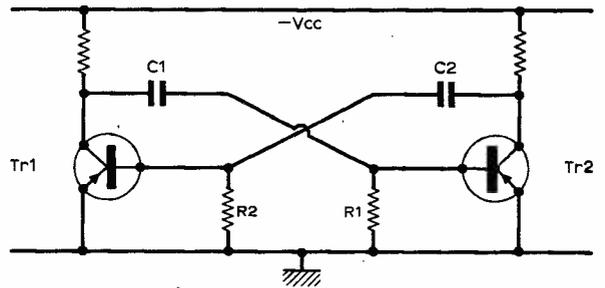


Fig. 5.6. Relaxation oscillator using two feedback networks C1R1 and C2R2

The time taken for switching is half the periodic time of the waveform. This time can be obtained from the equations discussed in the last article.

$$\text{Periodic time} = 2 \times 0.693 \times CR = 1.386CR$$

or approximately 1.4CR

$$\therefore \text{frequency} = \frac{1}{1.4CR}$$

This type of circuit, although used in logic circuits in the main, is often used in electronic organs, the keyboard used to switch different values of C<sub>1</sub> and R<sub>1</sub> into the circuit thus providing the different notes. Filter circuits are sometimes used to filter out some of the higher harmonics to give a purer sound.

So far these articles have shown that mathematics applied to electronics can remove all the guesswork normally encountered in circuit designing and building. It is now up to the reader to put these principles into practice not only in the workshop but in understanding radio and electronics a little more clearly. ■

# TAKE 20

JULIAN ANDERSON

**A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build.**

ONCE a piece of equipment has been built, it is often necessary to provide some form of signal input with which to test it. I am sure many of you use the trick of tapping the audio from either the loudspeaker or the volume control of a transistor radio. This is fine where an audio signal is required but will not help where r.f. is needed. For this type of equipment radio broadcasts can often be used but if this does not work you will not know if something is wrong or if the equipment is just not sensitive enough.

It is however very easy to build a signal injector which produces a basic audio signal which is so distorted that the harmonics reach way up into the r.f. spectrum.

Various types of oscillator will do this but the one described here will achieve all the others do and the cost will be under 10s.

## THE CIRCUIT

The transistor is connected in the common emitter mode with base bias being provided by R1. The collector load comprises a radio frequency choke which has two capacitors, themselves in series, connected across it. C1 and C2 are 0.1 $\mu$ F each so that the effective capacitance across the choke will be 0.05 $\mu$ F. The junction of these capacitors is connected to the base via a 1,000pF capacitor which starts and maintains the oscillation.

By coupling far too much positive feedback to the input, a grossly distorted waveform is achieved, this being necessary to produce the harmonics.

In operation for radio frequency usage, the choke itself will radiate the harmonics to be picked up on any tuned circuit and it is only necessary to place the injector near the equipment. For audio purposes C4 taps off the output and this can be coupled to the equipment under test via some form of probe.

A huge variety of transistors can be used for Tr1, we are using a 2N2926 here only for economy; the frequency response should be over 10MHz otherwise the higher harmonics will not be produced. PNP transistors, if used, of course require that the battery polarities be reversed.

Component layout should prove to be easy, a small piece of Veroboard will take all the components and make the finished article neat.

Just a few lines on test equipment. Many beginners seem to ignore this feeling that, since it is rarely used, it is a waste of time and money. I am sure that many constructors who are frustrated by early failures drop the hobby for this reason. If they had

## No. 16 SIGNAL INJECTOR

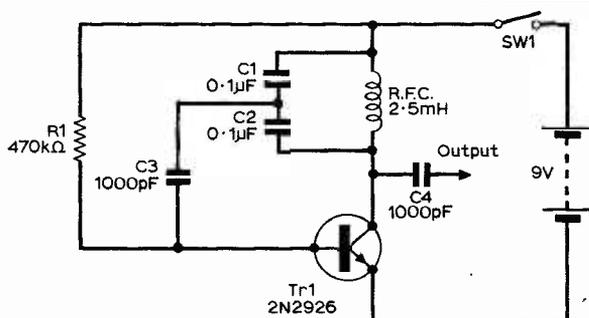


Fig. 1: The circuit diagram of the signal injector.

### ★ components list

R1	470k $\Omega$ 1/4 watt 10%
C1	0.1 $\mu$ F
C2	0.1 $\mu$ F
C3	1000pF
C4	1000pF
R.F.C.	2.5mH radio frequency choke
Tr1	2N2926

paid proper attention to it and realised that test equipment will often sort out troubles in seconds that would otherwise take hours they would still be with us. Good test equipment enables one to churn out projects quickly and of a high standard but even the simplest types, such as that described here, is very useful. ■

## PRACTICAL WIRELESS QUERY SERVICE

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard textbooks. In order to prevent unnecessary disappointment, prospective users of the service should note that:

- We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.
- We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.
- It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.
- We regret we are unable to answer technical queries over the telephone.
- It helps us if queries are clear and concise.
- We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

## QUERY COUPON

This coupon is available until 7th August 1970 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, AUGUST 1970

# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

## NEW! roamer eight mk1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs

**£6.19.6**

Parts Price List and Easy Build Plans 5/- (FREE with parts).

P & P 7/6.




## roamer seven mk1v

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Five Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Fanoms make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

Total building costs

**£5.19.6**

P. & P. 7/6

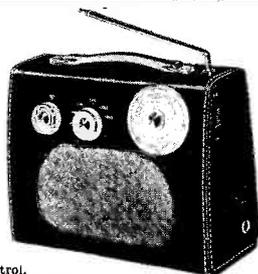

## NEW! trans eight


SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.

Total building costs

**89'6**


P & P 5/6

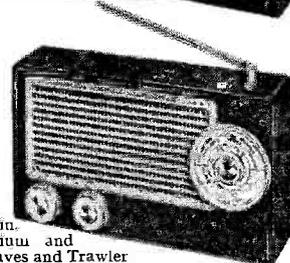
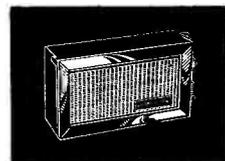
## pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2 in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs


**44'6**

P. & P. 3/6
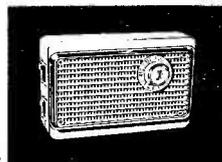
## transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**47'6**

P. & P. 3/9

## roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2 in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts).



Total building costs

**79'6**

P. & P. 4/6

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....


PW.20

\* Callers side entrance Stylo Shoe Shop

\* Open 10-1, 2.30-4.30 Mon-Fri. 9-12 Sat
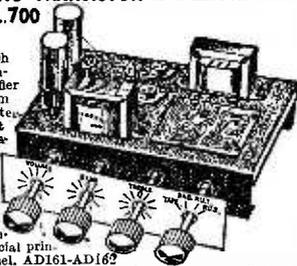
## MONO TRANSISTOR AMPLIFIER HSL.700

A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200-240v. Controls: Bass, Treble, Volume on/off, Function selector for P.U1, P.U2, Tape, Radio. The HSL700 is strongly constructed on rigid steel chassis bronze hammer enamel finish. Size 9 1/2 x 5 x 4 1/2 in. high.



Sensitivity: P.U1-50mV, 56K input impedance. P.U2-10mV, 1 meg input impedance. Tape-10mV, 1 meg input impedance. Radio-110mV, 1 meg input impedance. Output power measured at 1Kc-6.2 watts RMS into 3 ohms. 5.8 watts RMS into 15 ohms. Overall frequency response 30 c/s-18 Kc/s; Continuously variable tone controls: Bass, +8db to -12db at 700c/s. Treble, +10db to -10db at 10Kc/s. The HSL700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front case/cover panel, long spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.

Our Special Price **£7.19.6** P & P. 7/6

### LOUDSPEAKER BARGAINS

2 1/2" 4 ohm 10W, P. & P. 1/6 5/6. 3 ohm 15W, P. & P. 3/- 7 x 4in. 3 ohm 2W, P. & P. 4/- 10 x 6in. 3 ohm 27/6, P. & P. 6/- E.M.I. 8 x 5in. 3 ohm with high flux magnet 26/-, P. & P. 4/- E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 46/-), P. & P. 6/- E.M.I. 13 x 8in. 3 or 15 ohm with two built tweeters and crossover network 54/-, P. & P. 6/- BRAND NEW, 12in. 15W. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiFiux ceramic ferrobar magnet assembly 25.10.0. P. & P. 7/6 Guitar models: 25w. 26.0.0. 35w. 28.0.0. E.M.I. 3in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6. P. & P. 2/6. 12in. "BRA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm 27/6, P. & P. 6/-.

### 35 OHM SPEAKERS

3 1/2in. 14/-, P. & P. 2/6; 7 x 4in. 21/-, P. & P. 4/- VYNAIR AND RESINE SPEAKER AND CABINET FABRICS. Approx. 54in. wide. Usually 35/- yard. OUR PRICE 15/- per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

MAGNAVOX DESK TYPE MOVING COIL MICROPHONE. Medium impedance. Brand New. Special Price 42/- P. & P. 2/-

BALANCED ARMATURE EARPHONE. Approx 70 ohm impedance. Can be used as ultra sensitive mike or speaker. ONLY 8/6, P. & P. 1/6.

CRYSTAL MIKES. High Imp. for desk or hand use. High sensitivity. 13/6, P. & P. 1/6.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/-, P. & P. 1/6.

HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity. 29/6, P. & P. 2/6.

HONEYWELL MICROSWITCHES, S/P, C/O. Push button action. Rating 250v. AC at 15 amps. Size approx. 1 1/2 x 1 1/2 x 1/2 in. 5/- each. P. & P. 1/6 (6 or more post free).

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 140pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 Kc/sec I.F. Size approx. 2 1/2 x 1 1/2. Only 9/6, P. & P. 2/6.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7in. to approx. 50in. Maximum diameter 1/2 in. 10/- each. P. & P. 1/6. 6 section Lacquered Brass. Extends from 6in. to 22 1/2 in. approx. Maximum diameter 1/2 in. 5/- each. P. & P. 1/6.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-10-10, 20-0-20, 30-0-30v, at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. Price 85/-, P. & P. 6/6.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 0-9-9 at 500mA. 14/-, P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 17/6, P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6, P. & P. 3/6. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 22/6, P. & P. 2/6.

BATTERY CHARGER TRANSFORMERS. 200/240v. input. Nominal output for 6 or 12v. batteries 3 amps. Size approx. 3" x 2 1/4" x 2 1/4". Brand New. Price 21/-, P. & P. 5/6.

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4 in. FIVE for 10/-, P. & P. 2/6.

## STOCKISTS OF SINCLAIR EQUIPMENT

Z.30 Amplifier 89/6 p. & p. 2/6.

ST20 Pre. Amplifier 29 19 6 p. & p. 5/-

EZ5 Power Supply 24 19 6 p. & p. 3/6.

EZ6 Power Base 27 19 6 p. & p. 6/6.

IC.10 Integrated Circuit 89/6 p. & p. 2/-.

### SPECIAL OFFER !!

**HI-FI LOUDSPEAKER SYSTEM**  
Beautifully made teak finish enclosure with most attractive Tygan-Uynair front. Size 16 1/2" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" base unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 15 ohm impedance.

8 Gns. Carriage 10/-

## TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speaker from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response  $\pm 3dB$ . 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -15dB. Negative feedback  $\pm 15dB$  over main amp. Power requirements 25V at 6 amp. **PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £2.0.0. All Post Free.** Also available STEREO 10 + 10. As above but 10 watts per channel. **PRICES: AMPLIFIER KIT £12; POWER PACK KIT £3.10.0.** Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.).

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR AMPLIFIER

For P.U. Tape, Micro, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 17/6, P. & P. 2/6.

### SPECIAL PURCHASE!

#### E.M.I. 4-SPEED PLAYER

Heavy 8 1/2 in. metal turntable. Low flutter performance 200/250v. shaded motor (90v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY 68/-, P. & P. 6/6.

### QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE 25/-, P. & P. 6/6. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 27/6, P. & P. 7/6. **DELUXE QUALITY PORTABLE R/P CABINET MK II.** Uncut motor board size 14 1/2 in. clearance 3in. below. 6 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 79/6, P. & P. 9/6.

### 3-VALVE AUDIO AMPLIFIER HA34 MK II.


Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm wide range tone controls and now with improved cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0, P. & P. 6/-.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6, P. & P. 6/-.

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high. Input AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. FEW ONLY. **55/- P. & P. BARGAIN PRICE**

## DE LUXE STEREO AMPLIFIER

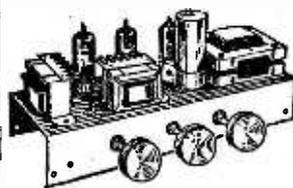

A.C. mains 200-240 v. U.T. 1 n.g. heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 x ECL86 Triode Pentodes, 1 x EZ80 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 200mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w. x 4" d. Overall height including valves 5". Ready built and tested to a high standard. PRICE 8 gns. P. & P. 8/-.

### 4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. **SPECIAL OFFER!** Famous GARRARD 3500 fitted Sonotone 9TAHC Diamond Stereo Cartridge. List price over £16. Limited Number at £10. Carr. 8/6.

**LATEST B.S.R. C109/AR1 4-SPEED AUTOCHEANGER.** With latest mono compatible cartridge 86.19.6. Carr. 6/6. With stereo cartridge 77.18.6. Carr. 6/6.

**LATEST GARRARD MODELS.** All types available 1025, 2025, SP25, 3000, AT60 etc. Send S.A.E. for latest Prices! **PLINTE UNITS** cut out for Garrard Models, 1025, 2025, 2000, 3000, AT60, SP25. With rigid transparent plastic cover. Special design enables unit to be used with cover in position. OUR PRICE 25.15.0 complete. P. & P. 8/6

**LATEST ACOS GPH1/13C** mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. 30/0. P. & P. 1/6.

**SONOTONE 2539** High output Stereo Cartridge. T/O stylus for Stereo/LP/78. Complete with universal mounting bracket. List Price 48/7.

OUR PRICE 25/-, P. & P. 1/6. **SONOTONE 9TAHC** compatible Stereo Cartridge with diamond stylus 50/-, P. & P. 2/-.

**LATEST BONNETTE 730 STEREO COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. 22/6, P. & P. 2/-.

**LATEST BONNETTE T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/-, P. & P. 2/-.

### HIGH GAIN 4 TRANSISTOR MONO CIRCUIT AMPLIFIER KIT

Type TA1  
Peak output in excess of 1 1/2 watts. All standard British components. Built on printed circuit panel size 6 x 6 in. Generous size Driver and Output Transformers. Output transformer tapped for 8 ohm and 15 ohm speakers. Transistors (GET114 or 81 Mullard AC128D and matched pair of AC128 o/p). 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive ease to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-, P. & P. 3/-.** Also ready built and tested, 52/6, P. & P. 3/-.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EZ80 and EZ80 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.9.6, P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 29.5.0, P. & P. 8/6.

**BRAND NEW TRANSISTOR BARGAINS.** GET 15 (Matched pair) 15/-; V15/10p 10/-; OCT1 5/-; OCT6 6/-; AP17 3/6; 20339 (NPN) 3/-; Set of Mullard 6 transistors OC44, 2-OC46, AC128D matched pair AC128 25/-; ORP12 Cadmium Sulphide Cells 10/6. All post free.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985


SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

# GOING BACK...

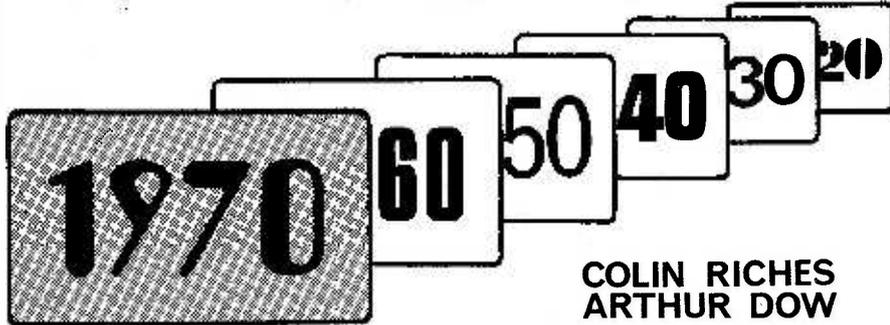

**COLIN RICHES  
ARTHUR DOW**

## Vintage Radio Society

In connection with our previous notes on the possible formation of a VRS we have had an offer from a reader to compile a list of those people who have a genuine interest in the collection and preservation of "vintage" radio equipment. All communications direct to: Mr. K. Lancaster, 40 Great Gardens Road, Hornchurch, Essex.

It is of interest at this point to raise the question as to just what constitutes "vintage" radio equipment. In our view the term should apply to equipment produced prior to 1930 by which time broadcasting had become firmly established in this country and the basic design of radio receivers more or less stabilised.

However, would readers care to express their own views on this matter?

## Radiograms

"According to the latest reports Captain Amundsen, at present *en route* to survey the Arctic region, will broadcast Eskimo music to the world." . . . 1922 . . . *possibly more pleasing to the ear than some of today's pop!*

"One of the simplest ways of cutting down atmospherics is to lower the aerial." . . . 1932.


"Increasing the height of the aerial is often as effective as adding another valve." . . . 1932. . . . *your move!* . . .

"America promises us a new method of waging war in her promised production of a giant airship capable of carrying large numbers of pilotless gliders laden with bombs. These gliders would be guided to the spot at which it was desired to drop bombs by means of a wireless ray." . . . 1922 . . . *but what about anti-missile missiles??*


"How Germany does it . . . in Germany the listening tax is paid monthly and its collection from set-owners is made by the postman on his rounds. The annual cost is approximately 30s. Radio pirates are discovered by the municipal chimney-sweeps who in the course of their daily duties visit all houses, flats and apartments. It is their duty to notify all wireless receivers to the local authorities." . . . !! . . . . 1932. . . . *M of P & T to note . . . using postmen that is, not chimney sweeps!*

. . . in addition to the Post Office Licence it is also

necessary to have a licence from Marconi's Wireless Telegraphy Co., for the use of their patents. The home constructor is not immune from this levy . . . if you construct a receiver for your own use and make use of any of the above company's patents you should write to them for a licence plate which will be supplied on payment of the royalty. If in doubt send them a wiring diagram of the receiver. The Post Office Licence is 10s. per annum, the Home Constructors Marconi Licence is 12s. 6d. and Manufacturers Licence is 5s. per valve!! . . . 1932 . . . *we should be grateful that this at least has been dropped! !*

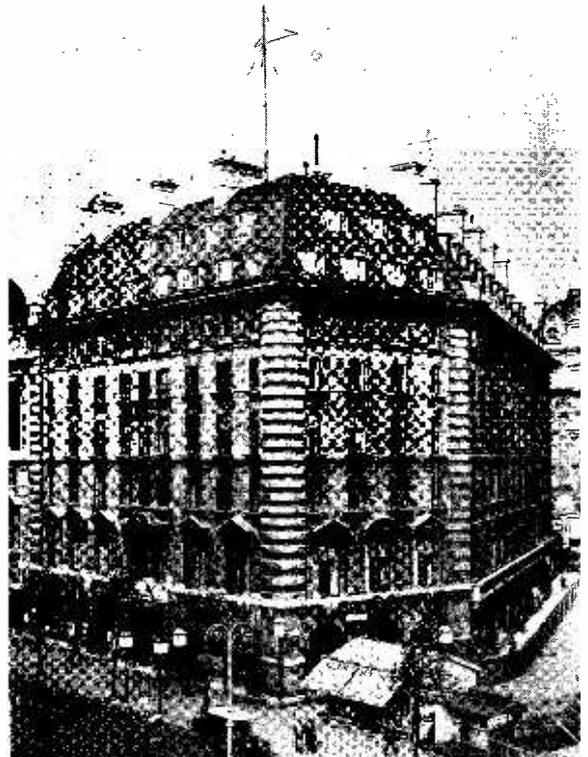

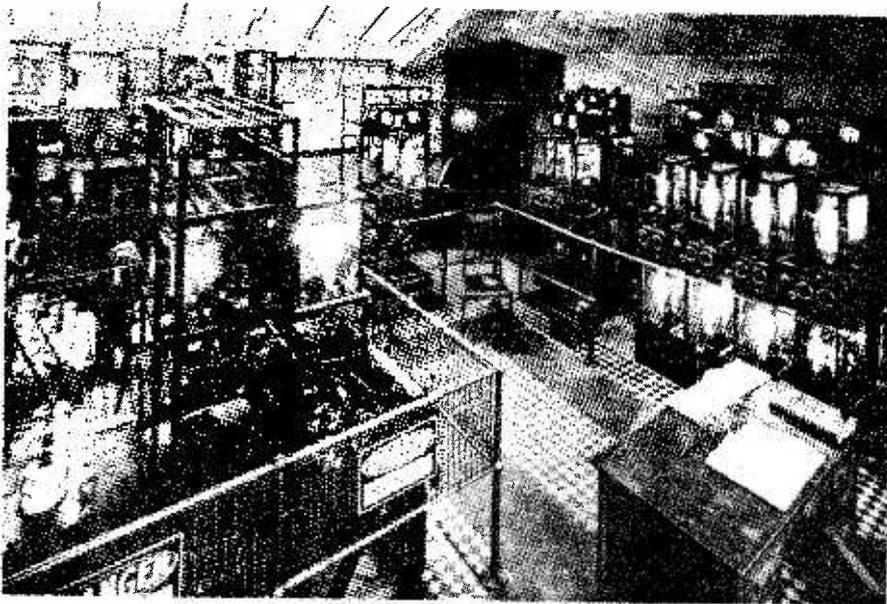*In 1922 the first broadcasts, as we know them today, took place from Marconi House in the Strand in London. Initially the power used was only 100 watts but this was soon increased to 1.5kW. The British Broadcasting Company came into being in December the same year and in a matter of months a network of eight 1.5kW stations, similar to 2LO, were operational around the country.*



A first glance at the transmitter hall of 2LO gives the impression of many mighty kilowatts but in fact it was only 1.5kW. On the right are the early audio stages and modulator with the master oscillator in the centre background. The power supply with its transformers and valve rectifiers is on the left.

## Readers Comment

... Recently I sorted out one of the old 2V triodes and made a single valve reaction set. The coil was home-wound on a former made from a toilet roll. The results were fantastic. (*J. Taylor, Lancashire.*)

... I got the wireless "bug" in 1920 when I was given some odd pieces of World War 1 surplus equipment. (*F. H. Osborn, G2CVO, London, E.4.*)

... I constructed a John Scott Taggart design delivering 12W of audio and had the police hammering on the door at 2 a.m. (*B. Richardson, Nottingham.*)

... I clearly remember several of your crystal receiver designs. (*Raymond A. Hounslow, Carlton, Bedford.*)

... I collect old wireless components and still have the Vol. 1, No. 1 issue of Practical Wireless. (*Alan Barnes, Yorkshire.*)

... The years which P.W. has survived are clear proof of quality. I have many fond memories of its earlier days. (*Maurice Dean, Sheffield.*)

... Wireless has been the No. 1 all-devouring interest for me since I was 11 in 1932. I collect books, magazines and components from the much earlier days of wireless. (*Basil D. Van Der Syde, M.S.E.R.T., Dorset.*)

... I still have many magazines dating back to the early days and would not part with them for all the world. (*B. Richardson, Nottingham.*)

... I built my first wireless receiver at the end of the First World War. (*Norman Gilbertson, Southampton.*)

... My first receiving licence was a Constructor's Licence issued in 1924. (*E. C. Parker, Middlesex.*)

... I have taken P.W. since the first issue and would like to see some early designs of transmitters. (*John R. Davidson, G3FG, Surrey.*)

These are but just extracts from some of the many letters we have received on the subject of the early days of radio.

## Testing 'Phones

Back in 1922, this was an inexpensive way to test your earphones: "The two leads from the earphones are connected to the two terminals of an ordinary electric bell. No battery whatever is put in the circuit. The clapper is pressed forward to the bell and then quickly released. It will vibrate several times before coming to rest. A similar vibration will take place and will be plainly heard in the phones. The explanation of the action is that there is a small amount of magnetism in the magnet of the bell when it is not connected to the battery which usually works it. When you cause the armature of the bell to vibrate the magnetism is disturbed and sets up currents in the coils of the magnet core. These currents work the diaphragms of your phones, and you hear a sound agreeing with the vibration of the armature of the bell."


## ... So What's New?

"Various means have been designed for the purpose of operating the 'change-over' switch automatically. de Forest used an electromagnet which was energised by a delicate contact inserted in the microphone mouthpiece.


"This contact was closed by the actual air pulses from the mouth and the electromagnet thereupon moved a pivoted switch so as to break the receiving circuit and couple the transmitter to the aerial."  
... VOX 1923!

"In response to a query from a reader concerning the operation of station 5HY the owner of the station, Mr. Baynham Honri, writes to say that his station is licensed for 10 watts but that he actually uses from 4 to 6 watts only on 440 and 200 metres."

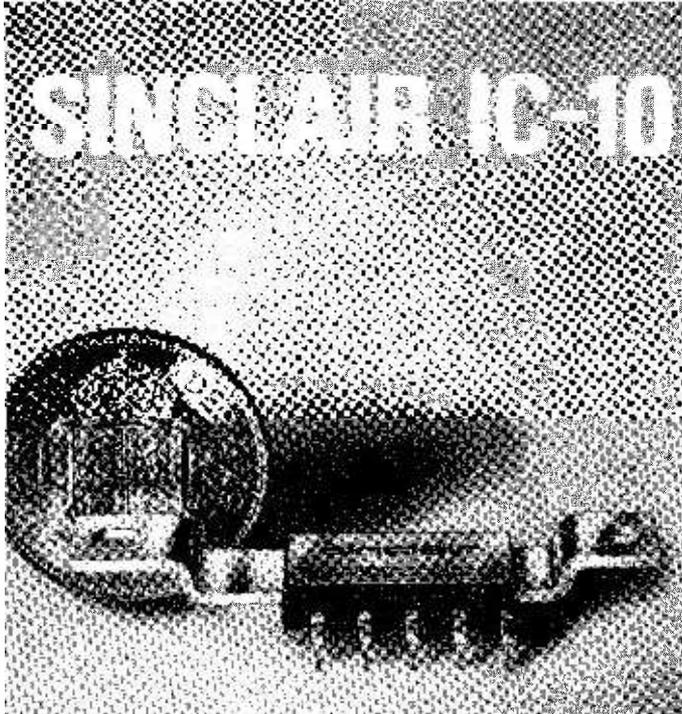... January 1923. ... Readers may be interested to know that Mr. Honri is still very much alive and is the author of the monthly feature "Underneath the Dipole" in our "sister" magazine Practical Television.


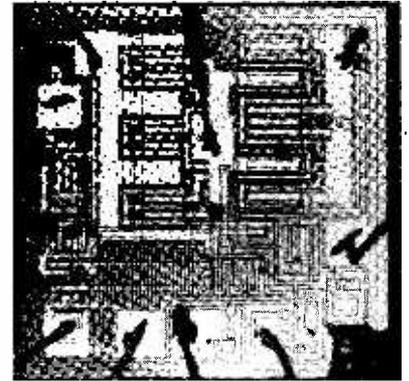
## MONOLITHIC INTEGRATED CIRCUIT HIGH FIDELITY AMPLIFIER AND PRE-AMP



### the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output of 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 Zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required as part of the process of producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. This enables us to cover every IC-10 with the Sinclair guarantee of reliability.

#### ■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz $\pm$ 1dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

#### ■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

#### ■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

SINCLAIR

**IC.10** with *IC.10 manual* **59/6**

POST FREE

**sinclair**

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD · CAMBRIDGE  
Telephone 0223 52731

# Project 60

## laboratory-standard high fidelity modules

**Sinclair Project 60** comprises a range of modules which connect together simply to form a complete stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare in overall performance. Now with the addition of three new modules to the range, the constructor has choice of assemblies with either 20 or 40 watts output per channel, with or without filter facilities.

The modules are: 1. The Z-30 and Z-50 high gain power amplifiers, each of which is an immensely flexible unit in its own right. 2. The Stereo 60 pre-amplifier and control unit. 3. The Active Filter unit with both high and low audio frequency cut-offs. 4. The PZ-5 and PZ-6 power supplies. A complete system could comprise, for example, two Z-30's, one Stereo-60, and a PZ-5. The PZ-6 is stabilised and should be used where the highest possible continuous sine wave rating is required. An A.F.U. may be added as required. In a normal domestic application, there will be no significant difference between using a PZ-5 or PZ-6 unless loudspeakers of very low efficiency are being used, in which case the PZ-6 will be required. For assemblies using two Z-50's there is the

new PZ-8 stabilised supply unit to ensure maximum performance from these more powerful amplifiers.


All you need to assemble your Project 60 system is a screwdriver and soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly. Project 60 modules have been carefully designed to fit into virtually all modern plinth or cabinets and only holes need be drilled into the wood of the plinth to mount the control unit and the A.F.U. Any slight slip here will be covered by the aluminium front panels of these two units.

The Project 60 manual gives all the building and operating instructions you can possibly want, clearly and concisely. Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future as the latest additions to the range show. A stereo F.M. tuner is next to come. These and all other modules we introduce will be compatible with those already available and may be added to your system at any time. And because Sinclair are the largest producers of constructor modules in Europe, Project 60 prices are remarkably low.

SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD CAMBRIDGE

Telephone 0223 52731

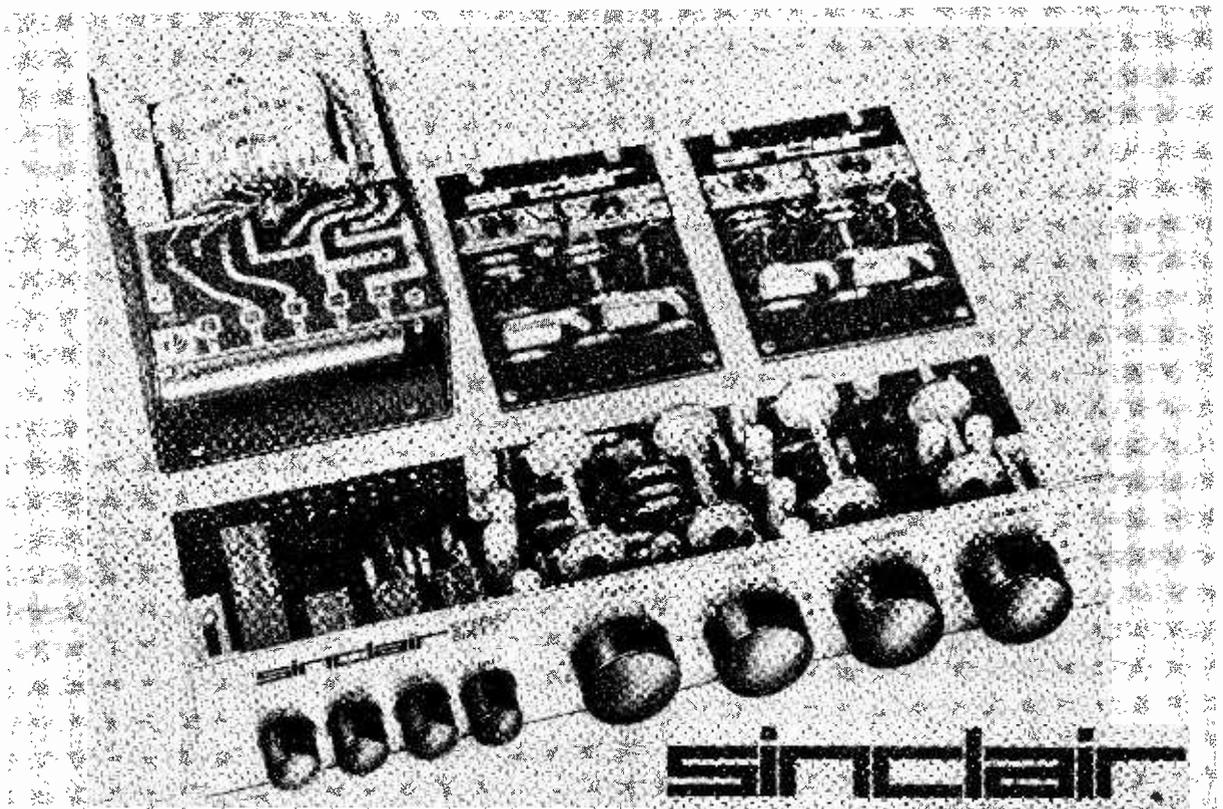



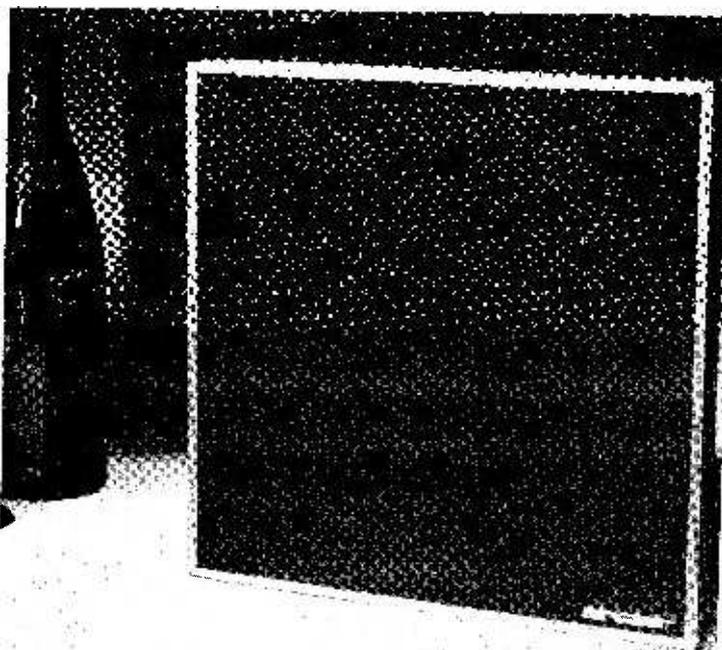
# SINCLAIR Q.16

new elegance in an  
outstanding loudspeaker

All the superb features which went to make the Sinclair Q.14 have been incorporated in the new Q.16 which gives an exciting new opportunity for you to match your Sinclair equipment with modern decor. Employing the same well proven acoustic system in which materials, processing and styling are used in such a radical and successful departure from conventional design. This speaker presents an entirely new appearance with its attractive teak surround and all-over special cellular foam front chosen as much for its appearance as for its ability to pass all audio frequencies without loss. The Q.16 is compact and slim. Its new styling makes it eminently suitable for shelf mounting, but it is no less versatile than its famous predecessor. Listen to a pair of Q.16s in stereo and marvel at the standards of quality and clarity they give. At the price this Sinclair speaker represents outstanding value as you will discover the moment you see and hear it.




The Q.16 will handle loading up to 14 watts R.M.S. and presents an 8 ohm impedance to the amplifier output. Frequency response extends from 60 to 16,000Hz with exceptional smoothness. A specially designed driver system is used in a sealed and contoured pressure chamber to ensure good transient response at all frequencies. Size: 9 $\frac{3}{4}$ " square  $\times$  4 $\frac{3}{4}$ " deep from front to back.

**£8.19.6**

POST FREE
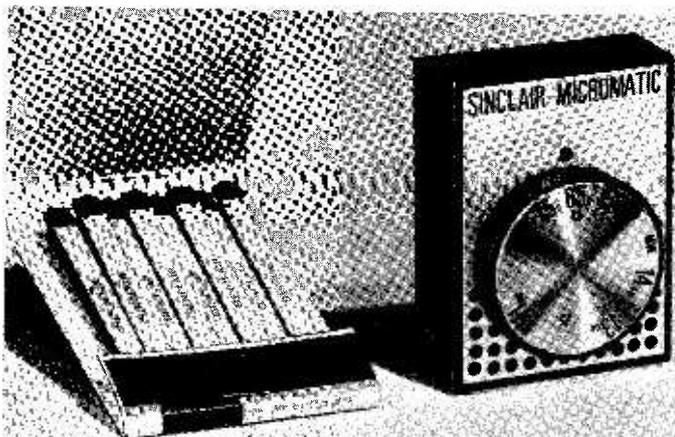
# SINCLAIR MICROMATIC

*The world's most  
successful miniature  
radio*



**SPECIFICATIONS**—Size: 1 $\frac{13}{16}$ "  $\times$  1 $\frac{7}{16}$ "  $\times$   $\frac{1}{2}$ " (46 $\times$  33 $\times$  13mm). **Weight incl. batteries:** 1 oz. (28.35gm) approx. **Tuning:** Medium wave band with bandspread at higher frequency end. **Earpiece:** Magnetic type. **Case:** Black plastic with anodized aluminium front panel, spun aluminium dial.

Complete kit incl. earpiece, case, solder and instructions in fitted pack.  
Ready built, tested and guaranteed, with earpiece.

**49/6**

**59/6**

Mallory Mercury Cell RM675 (2 req.) 2/9 each

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation much easier than with many larger sets. The plug-in magnetic earpiece which matches exactly with the output provides wonderful standards of reproduction.

Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wrist-watch, and dependable under the severest listening conditions.

## SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

**sinclair**

**SINCLAIR RADIONICS LIMITED**

22 NEWMARKET ROAD, CAMBRIDGE

Tel: 0223 52731

To: SINCLAIR RADIONICS LTD., 22, NEWMARKET RD., CAMBRIDGE  
Please send

NAME .....

ADDRESS .....

For which I enclose cash/cheque/  
money order

PW 870

# VALVES

**SAME DAY SERVICE  
NEW! TESTED! GUARANTEED**


**SETS** 1R5, 1A5, 1T4, 3A4, 3V4, DAF91, DF91, DK91, DL92, DI84.  
Set of 4 for 1S/6, DAF95, DF 95, DK95, DL99, 4 FOR 27/-.

024	4/0	20P3	11/8	DK96	7/8	EL35	17/6	PCL82	7/8	UBF80	5/8
1A7GT	7/8	20P4	18/8	DL35	5/-	EL41	11/-	PCL83	12/-	UBF89	6/8
1B6GT	7/8	26L6GT	5/-	DL92	5/8	EL84	4/8	PCL84	7/8	UCC84	7/-
1N6GT	7/8	25C4GT11/8		DL94	6/3	EL90	4/8	PCL85	9/-	YCC85	7/8
1R5	5/8	30C1	6/8	DL95	7/8	EL900	12/6	PCL86	8/8	UCF90	7/8
1R6	4/8	30C15	13/-	DY86	5/8	EM60	8/6	PCL88	14/6	UCB42	12/6
1T4	2/8	30C17	16/-	DY87	5/8	EM81	8/6	PCL800	15/8	UCB61	8/8
3S4	5/8	30C18	13/6	FABC80	6/8	EM64	6/8	PEN44	8/6	UCL83	7/8
3V4	6/3	30F6	18/-	EAF42	10/-	EM67	7/8	PFL20011/8		UCL83	11/8
5Y3GT	5/8	30FL1	12/8	EB01	2/3	EY61	7/8	PL56	3/8	UF41	10/6
5Z4G	7/8	30FL12	14/6	EB133	7/-	EY86	6/8	PL81	5/8	UF85	6/8
6AL5	2/3	30FL14	14/6	EBC41	8/8	EZ40	8/-	PL82	6/8	UF89	6/8
6AQ5	2/3	30LL	0/8	EBY80	6/8	EZ41	8/-	PL83	6/8	UL41	12/-
6AM6	2/8	30LL15	12/-	EBY89	6/3	EZ80	4/6	PL84	6/8	UL44	20/-
6AQ6	4/8	30LL17	15/8	ECC81	8/8	EZ81	4/8	PL800	13/-	UL84	7/-
6AT6	4/-	30P4	12/-	ECC82	4/8	EZ82	8/8	PL604	13/8	UM80	4/8
6AU6	4/8	30P12	13/8	ECC83	7/-	KT41	13/8	PL606	23/8	UM94	4/8
6BA6	4/8	30P19	12/-	ECC85	8/-	KT61	9/8	PM84	7/8	UY41	7/6
6BE6	4/8	30P11	13/8	ECC80A	12/-	KT68	18/8	PX25	23/6	UY85	5/8
6BJ6	8/8	30P13	18/8	ECLF30	6/8	LN350	14/6	PY32	10/-	VP4B	15/8
6C6G	4/8	30P14	14/6	ECLF82	6/8	N78	17/6	PY33	10/-	W77	3/8
6F18	3/8	26L6GT	8/8	ECH85	8/-	P61	10/-	PY81	5/8	W119	7/-
6F14	9/-	35W4	4/8	ECH42	13/6	FABC80	7/-	PY82	5/8	Z77	2/8
6F23	14/3	36Z4GT	5/-	ECH61	5/8	PC85	10/8	PY84	5/8	Transistors	
6F28	13/-	30E2	12/8	ECH82	8/8	PC85	10/8	PY88	6/8	AC107	8/8
6J5G	4/8	807	9/-	ECH84	7/8	PC95	8/8	PY800	7/8	AC127	8/8
6K7G	2/8	AC/V P215/8		ECL86	7/-	PC97	8/-	PY801	7/8	AD140	7/8
6K6G	2/8	A231	9/8	ECL92	8/8	PC800	7/8	R19	6/8	AF116	3/8
6BN7GT	4/3	B749	18/-	EOL80	8/-	PCC84	6/8	R20	12/6	AF116	3/8
6V6G	3/3	B729	12/8	EP47A	8/8	PCC85	6/8	U26	13/-	AF117	4/-
6V9GT	6/8	CCH35	15/8	ECH83	5/8	PCC88	6/8	U28	12/-	AF125	3/8
6X4	4/3	CL33	18/6	EF41	11/8	PCC89	10/8	U47	13/6	AF127	8/8
8XDGT	5/8	CY31	6/8	EF80	4/8	PCC189	10/8	U49	13/6	OC26	5/-
10F1	14/-	DAC32	7/8	EF85	6/3	PCC805	13/-	U78	4/3	OC41	2/8
10F18	7/-	DAF91	4/8	EF86	3/8	PCF80	8/8	U191	12/6	OC45	2/8
10P13	12/-	DAF98	7/8	EF89	5/3	PCF82	8/8	U195	8/6	OC71	2/8
12A7T	8/8	DF23	7/8	EF91	2/3	PCF86	10/-	U291	14/8	OC72	2/8
12A7G	4/8	DF81	2/8	EF94	4/8	PCF806	13/6	Y801	10/8	OC75	2/8
12A7U	4/8	DF96	7/8	EF163	5/8	PCF501	6/8	U329	14/8	OC81	2/8
12A7X	4/8	DH77	4/-	EF1P4	6/8	PCF802	8/-	U801	19/8	OC81D	2/8
12K8GT	7/8	DK22	7/8	ER90	8/3	PUF803	13/8	VABC80	6/8	OC82	2/8
12B66GT17/8		DK91	5/8	EL33	8/8	PCF808	12/8	UAF42	10/3	OC82D	2/8
20F2	18/8	DK92	8/8	EL34	8/8	ZCF808	14/8	UBC41	8/-	OC170	4/8
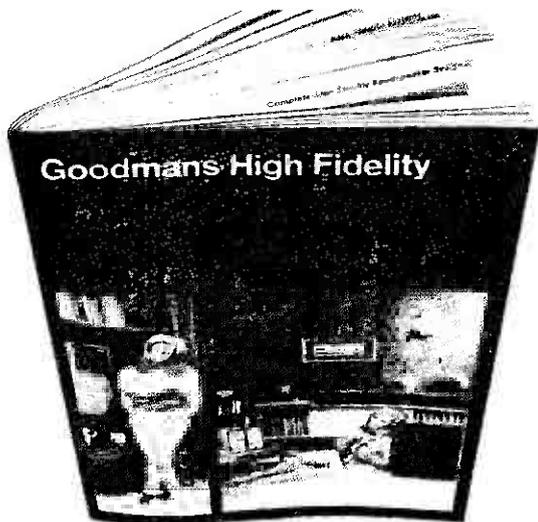
## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6s. extra



### Let us give you the facts

From cover to cover Goodman's Manual is packed with fascinating articles on Stereo; a beginners guide to High Fidelity; Stage-built Systems; complete details of Goodman's High Fidelity Audio products. 28 pages you can't afford to miss... and it's yours FREE!

**Please send me a free copy**


Name \_\_\_\_\_

Address \_\_\_\_\_

8/70



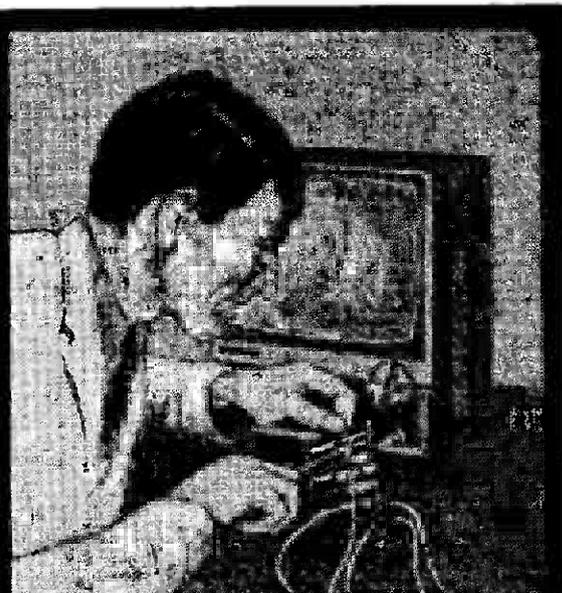**Goodmans Loudspeakers Limited**  
Axiom Works, Wembley, Middlesex, Tel: 01-902 1200



## Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full-time 2 year College Diploma Course which gives a thorough fundamental training for radio and television engineers starts on 2nd September, 1970.

The course includes theoretical and practical instruction on Colour Television receivers and is designed to cover the syllabus of the new City and Guilds Radio, Television and Electronics Technicians' Course. Pembridge College diplomas are awarded to successful students.

The way to get ahead in this fast growing industry —an industry that gives you many far-reaching opportunities—is to enrol now. Minimum entrance requirements 'O' Level, Senior Cambridge or equivalent in Mathematics and English.

**To: The Pembridge College of Electronics (Dept. PW15), 34a Hereford Road, London, W.2**

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME.....

ADDRESS.....




# M. & B. RADIO

38 BRIDGE END, LEEDS 1

Telephone: 0532-35649

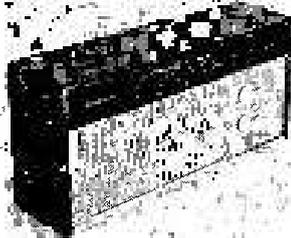VHF FM/MW/LW TRANSISTOR RADIO BRAND NEW. 10 transistor plus 4 diode table model of well known British manufacture. The highly polished wood cabinet, speaker and pre-assembled chassis are supplied separate and only require fitting together and the 2 speaker connections making. CHASSIS & CABINET £9.10.0. SPEAKER 25/- carr. paid.



STC STEREO/MONO HEADPHONES. Brand new lightweight high quality comfortable padded headphones for stereo or mono use. Weight 10 oz. 20 c/s to 20 Kc/s 300 ohms per earpiece. Supplied with details of matching circuit for 15 ohms using only 3 resistors. 54/- plus 4/- pp. 12 VOLT TRANSISTOR INVERTERS. 12vdc input, 270vdc at 150mA approx output. Transformer 2in x 2in x 1 1/2in mounted on aluminium case 1 1/2in x 2 1/2in x 4in. Weight 15oz. 65/- plus 4/- pp.

TRANSISTOR MODULATOR PRE-AMP PANEL. BRAND NEW 4 transistors plus 1 diode. 4 1/2in x 2 1/2in. Fitted with pre-set microphone gain control and mod filter. Originally used to drive an NKT404 which drove a pair of NKT404s. Supplied brand new c/w circuit of complete modulator. 22/6d plus 1/6 pp.

TRANSISTOR AUDIO AND MUTING PANELS. Brand new set of 3 panels. Audio panel with transistor gate originally used to drive an NKT404 output transistor. 2 muting panels with Schmitt trigger circuit to operate the gate on the audio panel. 8 transistors in all. Supplied with full circuit 22/6d plus 2/6 pp.

455Kc/s FM I.F. PANEL. Brand new but faulty 6 transistor panel usually low in gain. 12/6 plus 1/6 pp.

HAND TELEPHONES. Brand new radiotelephone type press to talk handsets. 12/6 plus 1/6 pp.

VHF AERIAL C/O RELAYS. Used but OK. 6 or 12v. 4/- plus 1/6 pp  
60 UNTESTED MIXED TRANSISTORS 5/- plus 1/- pp.  
60 UNTESTED MIXED DIODES 2/6 plus 1/- pp.

USED TESTED VALVES. 12AX7/ECC83 2/6. 6BJ6 1/6. 6AQ5/EL90 2/6. ECF80 2/-, 6AT6 1/6.

ALSO VARIOUS VHF EQUIPMENT IN STOCK  
S.A.E. AND 6d. STAMP FOR LISTS



## RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.



**LT55 6 WATT AMPLIFIER**  
A HIGH FIDELITY UNIT PROVIDING EXCELLENT RESULTS AT MODEST OUTPUT LEVELS.

Recommended **£10**  
Retail price  
Size 9 1/2 x 2 1/2 x 5 1/2 in. Approx.  
Controls (5) Volume, Bass, Treble, Mains Switch, Input Selector Switch.

Sensitivity 5 mv (max).  
Frequency Response 30-20,000 cps—2dB  
Harmonic Distortion 0.5% at 1,000 cps  
Output Rating I.H.F.M. 6W  
Input Sockets for "Mike," Gram and Radio Tuner/Tape Recorder.  
Suitable for speakers 3-15 ohms.

### LT66 12 WATT STEREO AMPLIFIER

A TWIN CHANNEL VERSION OF THE LT55 PROVIDING UP TO 6 WATTS I.H.F.M. HIGH FIDELITY OUTPUT ON EACH CHANNEL.

Switch Input Facilities  
Socket (1) Tape or crystal PU  
(2) Radio Tuner (3) Ceramic PU Microphone.

Controls (6) Volume, Bass, Treble, Balance, Mains Switch, Input Selector Switch, Stereo/Mono Switch.

Facia Plate Rigid Perspex with black/silver background and matching black edged knobs with silver finish centres.



Recommended **18 gns**  
Retail price  
Size 12 x 3 1/2 x 6 in. Approx.

If required an attractive wood cabinet with veneer finish can be supplied for any model

PLEASE SEND A STAMPED ADDRESSED ENVELOPE FOR FULL DETAILS OF ABOVE UNITS

AVAILABLE FROM YOUR LOCAL HI-FI DEALER

Prices From **70s.**

Wholesale and Retail enquiries to:

**LINEAR PRODUCTS LTD, Electron Works, Armley, Leeds**

# If you can put a 'Yes' in every box, you might just make a RADIO TECHNICIAN in Air Traffic Control

An all consuming interest in telecommunications

At least one year's practical experience in telecommunications, preferably with 'ONC' or 'C and G' technical qualifications

A highly developed sense of responsibility

Willingness to undergo a rigorous programme of training

Aged 19 or over

To the right man, the National Air Traffic Control Service offers the prospect of an interesting and steadily developing career as a Radio Technician in air traffic control.

The work involves the installation and maintenance of some of the very latest electronic equipment at civil airports, radar stations and other specialist establishments all over the country. Important today, the job will become increasingly vital as Britain's air traffic continues to grow, and prospects for promotion are excellent. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over). Scale maximum £1590 (higher rates at Heathrow). The annual leave allowance is good, and there is a non-contributory pension for established staff.

If you feel you can meet the demands of this rather special job—and you have a strong determination to succeed—you are invited to complete the coupon below.

Send this coupon for full details and application form.  
To: A J Edwards, C Eng, MIEE, The Adelphi,  
Room 705, John Adam Street, London WC2,  
marking your envelope "Recruitment"

Name

Address

PWT/G1

Not applicable to residents outside the United Kingdom

# NATCS

National Air Traffic Control Service



## SITUATIONS VACANT

**RADIO TECHNICIANS** with sound knowledge of at least three of the following types of equipment required immediately for Meteorological Office Ocean Weather Ships: MF, HF, VHF and UHF, Single and Double side-band transmitters, Radar (Navigational), Radar (Height finding), Radio Receivers, MF and VHF, Auto DF, Digital telemetering equipment, Low voltage servo-recorders, Loran and echo sounders.

Salary Scale £885-£1500 per annum according to age (£1295 at 25 age point), plus £162 per annum overtime allowance. Liberal leave allowance. Free food and accommodation provided on board ship. Applicants must be natural born British Subjects.

Full details from Shore Captain, Ocean Weather Ship Base, Great Harbour, Greenock. Telephone 24391.

# Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1971 and in subsequent years.

Specialist training courses lasting approximately nine months according to the trainee's progress are held at intervals. Applications are now invited for the course starting in January 1971.

During training a salary will be paid on the following scale:—

Age 21	£848 per annum
22	£906 " "
23	£943 " "
24	£981 " "
25 and over	£1,023 " "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade 1 scale:—

Age 21	£1,023 per annum
22	£1,087 " "
23	£1,150 " "
24	£1,214 " "
25 (highest age point)	£1,288 " "

then by six annual increases to a maximum of £1,749 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad. Applicants must normally be under 35 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:—

**RECRUITMENT OFFICER,  
Government Communications  
Headquarters,  
Oakley, Priors Road,  
Cheltenham, Glos. GL52 5AJ  
Tel: No. Cheltenham 21491 Ext 2270**

## EDUCATIONAL

**RADIO OFFICER** training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.



## TELEVISION

This private College provides efficient theoretical and practical training in Radio and TV Servicing. One-year day courses, commencing in Sept., January and April, are available for beginners, and shortened courses for men who have had previous training. Write for free prospectus to:—  
**London Electronics College, Dept. LX/4, 20 Penywern Road, Earls Court, London, S.W.5 Tel. 01-373 8721**

## SITUATIONS VACANT

**ENGINEERS. A TECHNICAL CERTIFICATE** or qualification will bring you security and much better pay. Etem. and adv. private postal courses for C.Eng., A.M.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept 137K), Aldermaston Court, Aldermaston, Berks.

## UNIVERSITY OF SOUTHAMPTON INSTITUTE OF SOUND AND VIBRATION RESEARCH

Person required to help with development and operation of instrumentation systems for noise and vibration measurement, including analysis of data and routine maintenance of equipment. Salary on scale—either £456-£771 or £905-£1273 with supplementary allowances for qualifications. Please write stating date of birth, experience and qualifications and giving the names of two referees to the Deputy Secretary, The University, Southampton, SO9 5NH, quoting ref: PW.

## EDUCATIONAL (continued)

**BECOME** "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

## EDUCATIONAL (continued)

### TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE,  
STEWARTS ROAD, LONDON. SW8

**CITY & GUILDS** (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. **B.I.E.T.** (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

## BOOKS & PUBLICATIONS

### SURPLUS HANDBOOKS

19 set Circuit and Notes .. ..	7/0 p/p 9d.
1155 set Circuit and Notes .. ..	7/0 p/p 9d.
H.R.O. Technical Instructions .. ..	6/0 p/p 9d.
38 set Technical Instructions .. ..	6/0 p/p 9d.
46 set Working Instructions .. ..	6/0 p/p 9d.
88 set Technical Instructions .. ..	7/6 p/p 9d.
BC.221 Circuit and Notes .. ..	6/0 p/p 9d.
Wavemeter Class D Tech. Instr. ..	8/6 p/p 9d.
18 set Circuit and Notes .. ..	6/0 p/p 9d.
BC.1000 (31 set) Circuit and Notes ..	6/6 p/p 9d.
CR.100/B.28 Circuit and Notes ..	10/6 p/p 1/-
R.107 Circuit and Notes .. ..	7/6 p/p 9d.
AR.88D Instruction Manual .. ..	6/0 p/p 9d.
62 set Circuit and Notes .. ..	7/0 p/p 9d.
Circuit Diagram 5/6 each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1194, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.	
Colour Code Indicator .. ..	2/8 p/p 9d.
52 set Sender and Receiver circuits 3/- post free	

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

### INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,  
28 TALBOT GARDENS, LEEDS 8

## SERVICE SHEETS

**SERVICE SHEETS** (1925-1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/-. Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. **Hamilton Radio**, 54 London Road, Bexhill, Sussex.

**SERVICE SHEETS**, Radio, TV, etc. 8,000 models. List 2/-. S.A.E. enquiries. **TELRAY**, 11 Maudland Bank, Preston.

**RADIO, TELEVISION** over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

**SERVICE SHEETS** (75,000) 5/- each: please add loose 4d. stamp: callers welcome: always open. **THOMAS BOWER**, 5 South Street, Oakenshaw, Bradford.

# TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

**OAKFIELD ENTERPRISES**  
LIMITED  
30 CRAVEN STREET, STRAND  
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From

Address

enclose remittance of

(and a stamped addressed envelope)  
s.a.e. with enquiries please

**MAIL ORDER ONLY (February PW)**

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 5/- each, Manuals from 10/- plus large S.A.E.

(Uncrossed P.O. s please. original returned if service sheets not available.)

**C. CARANNA**  
71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.


Free TV fault tracing chart or TV list on request with order.

Mail order only.
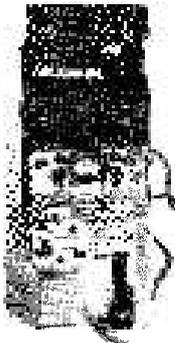
## RECEIVERS & COMPONENTS

**COMMUNICATIONS RECEIVERS:** Ex-Govt. bargains in the £10 to £20 range. Example: B40, 640 kHz-30.5 MHz, cleaned, checked, aligned, with circuit information, £17. Carriage 40/- (England, Wales). Deposit on crate 30/-. Also Murphy CAS and Pye CAT first-class ex-navy receivers, B41, CR300, PCR2 and others. Money back guarantee. Calibrators, VTVMs, headphones, components, at competitive prices. SAE details. Phone any time. Callers welcome.—P. R. GOLLEDGE, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

**GIEGER COUNTERS LATEST GOVERNMENT RELEASE, OF THESE EXCEEDINGLY POPULAR AND WELL KNOWN CONTAMINATION METERS.** Which were intended for use, should the need arise, by the Civil Defence etc.



These are new or virtually as new, being shelf stored only, and are complete with all parts including, Carrying Haversack, Cable and Probe, Instructions for use.

This Model incorporates a plug in Vibrator Power unit, instead of the normal Battery Holder, thereby using four standard Maltory R.M.12 R. Long Life Batteries. (Not supplied.)

The unit is completely portable, being made in Cast Aluminium, making it extremely light and strong. Every part is completely sealed and watertight. List Price £70.

SUPPLIED AS ABOVE IN MAKER'S CARTON COMPLETE AND TESTED 90/- POST 10/-, TWO CARRIAGE PAID.

**J. H. TOWNEND**  
21 THE ROUNDWAY, MORLEY,  
NR. LEEDS, YORKS.

## Stella Nine Range Cases

Manufactured in Black, Grey, or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

### LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7 1/2" Height
£ s. d.	£ s. d.	£ s. d.	£ s. d.	£ s. d.
6 1/2"	3 1/2"	15 0	18 0	1 1 6
6 1/2"	4 1/2"	16 3	1 1 6	1 5 0
8 1/2"	3 1/2"	18 0	1 5 0	1 5 0
8 1/2"	6 1/2"	1 5 0	1 11 9	1 17 0
10 1/2"	7 1/2"	1 14 6	2 2 6	2 6 0
12 1/2"	3 1/2"	1 5 0	1 11 9	1 17 6
12 1/2"	5 1/2"	1 14 0	2 2 0	2 5 6
14 1/2"	8 1/2"	2 3 0	2 11 6	2 15 6
14 1/2"	3 1/2"	1 10 0	1 17 6	2 2 0
14 1/2"	9 1/2"	2 11 6	3 7 0	3 10 0
16 1/2"	6 1/2"	2 6 0	2 15 6	3 1 9
16 1/2"	10 1/2"	3 0 0	3 18 0	4 6 0

Cases—Post 4s. 6d. per order.  
Discounts available on quantities.

### CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases.		All 2 1/2" Walls	
s. d.	s. d.	s. d.	s. d.
6" x 3"	6 6	10" x 7"	10 3
6" x 4"	6 9	12" x 3"	8 0
8" x 3"	7 9	12" x 5"	9 0
8" x 6"	9 3	12" x 8"	12 9
		16" x 10"	19 0

Chassis—Post 3s. 0d. per order.  
Discounts available on quantities.

### E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases  
46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE  
Tel: 061-480 2179

### CONSTRUCTOR UNITS

**R.F. Generator.** Supplied with coils, tuning cap., switch and details for wiring and calibration. Covers 150KH/z to 30MH/z. 89/6 + 3/6 pp.

**A.F. Unit.** Osc. operates at 2 freq's. for A.F. R.F. checks, connects as amp. for continuity checks Dual freq. square wave o/p for audio/HiFi tests. Provides modulation for R.F. unit. 39/6 + 3/6 pp. S.A.E. for Details, Tweed Electronics (PW), 9 The Green, Hatfield Peverel, Chelmsford, Essex.

### NEW MODEL V.H.F. KIT MK2

Our latest Kit improved design and performance plus extra Amplifier Stage receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4 etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

ONLY 68/- P. & P. FREE U.K. ONLY

### "AUDIO 1" 3 WATT AMPLIFIER

Ready built, tested and guaranteed. Very attractive Cabinet in black leatherette with light grey front, size 10" x 4 1/2" x 4". Fitted large speaker, Jack Socket and Volume Control. Many uses e.g. Radio Kit Amplifier, Intercom, Record Player, Public Address or even Crystal Set Amplifier. **OUR PRICE ONLY 97/- P. & P. 4/6d.**



### EXTENSION SPEAKER CABINET

The same Cabinet that houses our Amplifier. **ONLY 26/- P. & P. 3/-** Or with fitted Speaker 34/- P. & P. 3/6d.

Cheques, Postal Orders to:

Dept. P.W.,  
Galleon Trading Co., 298A Lodge Lane,  
Romford, Essex

## VALVE BARGAINS

Any 5, 9/-; 10, 14/-; 100, £5 10s from the following:

ECC82, ECL80, EF85, EF183, EBF89, EB91, EY86, PCC84, PCC89, PCF80, PCF86, PCL82, PCL83, PCL84, PL36, PL81, PY35, PY81, PY82, PY800.

## AERIAL BOOSTERS 59/-

Three types of High Gain Transistorised pre-amplifiers all at the same price UHF 625 Type L45, Tunable over the complete UHF Stations VHF 405 Type L12 with Separate Tuning for Band 1 and Band 2. Please state channel numbers.

**FM UHF RADIO PRE-AMPLIFIER** SAE for Full Details. All complete with battery and leads, 7 day money back guarantee if not satisfied

**VELCO ELECTRONICS, 62 BRIDGE ST. RAMSBOTTOM, BURY, LANCs.**

### AMAZING VALUE

#### NEW BRANDED FULL SPEC. DEVICES

Plessey SL402A Preamp & 2W Amp. 40/-  
GE PA234 1W Audio Amplifier 17/6  
GE PA237 2W Audio Amplifier 32/6  
RCA 40669 8A 400V Triac 24/-  
RCA 40583 Trigger Diode 5/3  
GE D40C1 4W Darlington Amp. 13/6

Notes supplied FREE with orders.

P. & P. 1/- per order. Overseas 7/6  
Cash with order. Mail order only.

### JEF ELECTRONICS (P.W.8)

York House, 12 York Drive, Grappenhall, Warrington, Lancs.

Money back if not satisfied.

### A CORNUCOPIA OF COMPONENTS!

Scarce valve, selected T.V. components, Speakers, Cabinets, Computer panels—long leads NOT printed circuits. Transistors, resistors—new and recovered. State requirements. S.A.E. (F.S.) for details. **MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.**

**COMPLETE RANGE of Amateur Aircraft, Communications receivers.** Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

**TRANSFORMERS.** Rewound, Prototypes supplied capacity for small quantity runs. S.A.E. please. Katcliffe, 18 Beech Avenue, Thongsbridge, Huddersfield, Yorks.

## LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 1/2 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.




**CAXTON COLUMN.** This is a column cabinet 23 1/2 x 8 1/2 x 52 in. deep finished in black or wood grain cloth with blue Vynair front. Key-note slot for wall mounting. Fitted with three speaker units, 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at 59/6d. P. & P. 11/- each.

**SPEAKERS:** E.M.I. 1 1/2 x 8 in. 3 ohm, 45/-, 15 ohm 48/6. P. & P. 5/6. E.M.I. 3 in. tweeter 17/6. P. & P. 2/6. E.M.I. 1 1/2 x 8 in. fitted two 2 1/2 in. tweeters. 15 ohm 77/6. P. & P. 5/6. E.M.I. 1 1/2 x 8 in. (15 ohm) hi-fi quality £5.19.6. P. & P. 5/6. E.M.I. Woofers. 6 1/2 x 6 1/2 in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/8. P. & P. 1/-. EAGLE Crossover units 3 or 16 ohms, 17/4. P. & P. 1/6. Bakers 12 in., 25 watt 15 ohm £6.6.0. P. & P. 5/6.

**VYNAIR** Widths from 40 to 54 in., 15/- yd. off roll. P. & P. 4/9. 3 yard, 8/-, P. & P. 1/9. Send 1/- stamps for samples.

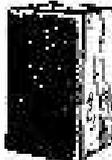**ELF.** An extension speaker of quality, 9 x 5 1/2 x 3 1/2 in. veneered in natural teak with smart gold and brown Vynair front trimmed with white. Fitted re-conned 5 in. 30hm speaker. The baffle is half inch thick. A real bargain at 37/6. P. & P. 4/9.



**BROADWAY ELECTRONICS** (N1. Tooting Broadway Underground Stn)  
92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 01.672 3984 (Closed all day Wed.)

**CARTRIDGES:** Stereo: Sonotone 8TA H/C Diamond, 47/6. Ronette S105 Medium Output, 28/6. S106 High Output, 28/6. Acos GP23 1 Sapphire, 37/6. GP94 1 Sapphire, 39/6. GP91 Stereo Compatible (High, Medium or Low Output), 25/-, TA800 converts Philips AG3301, AG3306 to B.S.R. SX1H. Plug-in head complete with cartridge, 50/-, TA700 equivalent to B.S.R. SX1M, 35/-, Japanese equivalent to B.S.R. TC8s, 35/-, P. & P. 1/6. Mono: Acos GP67/2 will replace Collo and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/-, B.S.R. TC8H Jap. equivalent, 26/-, P. & P. 1/6.

**EARPIECES WITH CORD** and 3.5mm. plug, 8 ohm magnetic, 3/-, 250 ohm, 4/-, 180 ohm with clip, 6/6. Xtal. P. & P. 6d.


**PIANO KEY PUSH BUTTON SWITCHES.** 7 button inc. mains on off, 6 banks of 6 P.C.O., 8/6. P. & P. 1/6.

**THE SHELLEY.** Size 21 x 11 x 6 in.

An extremely elegant speaker system made of 12 m.m. chipboard covered with teak leathercloth with dark Vynair front (send S.A.E. for cloth samples). This unique system uses three ex T.V. speaker 6 1/2 in round for the Bass, 3 x 3 in for the Middle and 2 in round for Treble. Carefully matched and tested. Will handle 10-12 watts and will match 8 ohms impedance. If preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4 19 6 plus 12/9 P. & P. **MATCHING TRANSFORMER** for 15 ohms 16/- post free.



## 4-STATION INTERCOM

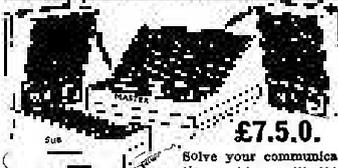

£75.0.

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in deluxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price £11.19.6. P. & P. 8/6 extra.

## INTERCOM BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.



59/6

Why not boost your business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days. **WEST LONDON DIRECT SUPPLIES (P/W4)**  
169 KENSINGTON HIGH STREET, LONDON, W.8.

**BRAND NEW ELECTROLYTICS,** 15/16V, 0.5, 1, 2, 5, 8, 10, 20, 30, 40, 50, 100 mfd, 8-5d. E12 series 5% resistors. Carbon Film 1/4W 10Ω to 1MΩ, 1-5d. Wirewound 5W 15Ω to 15KΩ, 10d, postage 1/-. The C. R. Supply Co., 127 Chesterfield Road, Sheffield 8.

**AUDIOSCAN-HI-FI** loudspeaker systems for the home constructor, cabinet kits, new range of Peerless speakers, speaker kit systems and cross-over networks. BAF wadding and all necessary components. Free speaker fabric samples on request. Send 9d in stamps to: **AUDIOSCAN, Dept. P.W.**, 4 Princes Square, Harrogate, Yorks.

**EMSAF FOR ANTENNA SYSTEMS AND CONVERTERS.** Please send s.a.e. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting. **ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD.,** Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

### HI-FI EQUIPMENT

**SHURE GOLDRING** Cartridges Post Free. G800, M44 5/7 £7.17.6. M31 £5.5.0. M44E £8.19.6. M55E £9.19.6. M75E/2 £16.10.0. GARRARD SP25/2 £10.17.6. AP 75 £16.17.6. p. & p. 7/6. Ultimate Electronics, 38 Achilles Road, London, N.W.6. Mail Order Only.

### AERIALS

#### BAKER AND BAINES

**BBC** dipole 30/-, H 42/-, 3 ele 89/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/5, 11 ele 57/6. **ITA** doubles 8 ele 112/-, 11 ele 140/-, 13 ele 159/-. Combined BBC/ITA D+5 45/-, D+8 52/-, H+5 69/-, X+5 75/-, Combined Loft Special D+5 with loft pole and fixings 37/-, **UHF Aerials BBC/ITA** 14 ele 37/-, 18 ele 54/-, 22 ele 63/-, Double 22 ele 142/-, **CO-AX** low loss at 1/3 and 2/3, Co-Ax plugs 1/4. **Diplexers—Triplexers—Matched UHF/VHF Diplexers, VHF/UHF Amps 75/-, Poles, Lashing, Clamps, Couplers, etc.** Postage Paid inland on aerials. Extra on accessories. Please state channels when ordering.

11 Dale Cres., Tupton, Chesterfield.

### ELECTRICAL

240 VOLT  
ELECTRICITY  
ANYWHERE



**BEST EVER 200/240 VOLTS "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scoop Purchase. The fabulous Mk. 12D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere.

Brand New and Fully Tested, only £59.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

Dept. PW, **SCIENTIFIC PRODUCTS**  
Rear Derby Road, North Fromenade,  
Blackpool, Lancashire.


Est. 1943 **JOHNSONS** Tel: 24864

New! **CV2**—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

**JOHNSONS (RADIO)**  
St. Martin's Gate, Worcester  
WR1 2DT

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

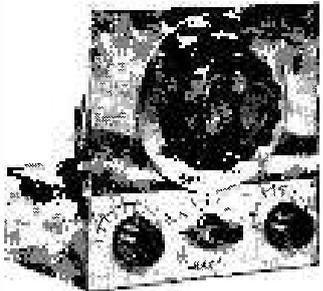

Famous for over 35 Years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

#### IMPROVED 1970 RANGE

One-valve model "DX", complete kit—price 66/6 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits including the famous model "K" and "K plus" (illustrated above.) All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1

## SEMICONDUCTORS

BRAND NEW AND FULLY GUARANTEED

1N914	1/6	2N2923	3/6	AD162	7/6	BD192	24/-	MPP102	8/6
1N916	1/6	2N2924	3/6	AF114	5/-	BD142	18/6	MPP103	7/6
18021	4/-	2N2926	3/6	AF116	5/-	BF115	5/-	MPP104	7/6
18025	5/-	2N2926	3/6	AF117	5/-	BF117	9/6	MPP105	7/6
18113	3/-	" Green	3/6	AF118	12/6	BF167	6/6	NKT0013	8/6
18120	2/6	" Yellow	2/6	AF124	4/6	BF173	6/6	NKT216	6/6
18121	2/6	" Orange	2/6	AF125	4/6	BF180	7/6	NKT217	8/6
18130	3/6	2N3011	6/6	AF126	4/6	BF181	6/6	NKT261	6/6
18131	2/6	2N3053	5/6	AF127	3/6	BF184	6/6	NKT282	4/6
18132	2/6	2N3054	11/-	AF139	7/6	BF194	4/6	NKT284	4/6
1844	2/-	2N3055	15/-	AF181	8/6	BF195	5/6	NKT271	4/6
18920	2/-	2N3702	3/6	AF186	9/6	BF197	8/6	NKT272	4/6
24301	4/-	2N3703	4/6	AF239	8/6	BF244	8/6	NKT274	4/6
24302	4/-	2N3704	4/6	AS235	5/6	BF261	13/6	NKT275	4/6
24303	4/-	2N3705	4/6	AS237	7/6	BF263	4/6	NKT281	5/6
24308	6/-	2N3706	4/6	AS258	5/6	BF229	8/6	NKT403	15/-
24371	3/-	2N3707	4/6	AS259	5/6	BF230	9/6	NKT404	12/6
2N606	4/-	2N3708	3/6	AS220	7/6	BF235	19/6	NKT405	15/-
2N607	4/-	2N3709	3/6	AS221	8/6	BF243	7/6	NKT613	6/6
2N608	4/-	2N3710	4/-	BA109	6/6	BF244	7/6	NKT674	6/6
2N705	7/6	2N3711	4/-	BAX13	1/6	BF284	6/6	NKT677	5/6
2N706A	3/6	2N3819	7/-	BAX16	1/6	BF285	7/-	NKT713	5/6
2N708	3/6	2N3820	19/6	BA231	1/6	BF286	6/6	NKT773	5/6
2N980	5/6	2N3905	7/6	BA233	3/6	BF287	6/6	NKT781	6/6
2N1121	5/6	2N4058	5/6	BC107	3/-	BF288	5/6	NKT20329	8/6
2N1132	6/6	2N4059	5/6	BC108	3/-	BF243	12/6	NKT801115	6/6
2N1302	6/6	2N4060	4/6	BC109	3/6	BF250	4/6	NKT801219	6/6
2N1303	6/6	2N4061	4/6	BC113	5/6	BF251	4/6	NKT801322	6/6
2N1304	4/6	2N4062	4/6	BC116	7/6	BF252	4/6	OA5	3/6
2N1305	4/6	2N4284	3/6	BC118	6/6	BF276	8/6	OA9	2/6
2N1306	5/6	2N4285	3/6	BC123	11/-	BF290	13/6	OA70	1/6
2N1307	6/6	2N4286	3/6	BC126	11/-	BKX19	8/6	OA73	1/9
2N1308	6/6	2N4287	3/6	BC147	3/6	BKX20	3/6	OA79	1/6
2N1309	6/6	2N4288	3/6	BC148	3/6	BKX21	7/6	OA81	1/6
2N1507	5/6	2N4289	3/6	BC149	3/6	BKX28	9/6	OA85	1/6
2N1613	5/6	2N4291	3/6	BC167	3/6	BKX27	9/6	OA90	1/6
2N1711	5/6	2N4292	3/6	BC168B	2/6	BKX28	6/6	OA91	1/6
2N1889	6/6	40381	12/6	BC189C	3/6	BKX29	13/6	OA95	1/6
2N1893	6/6	40382	12/6	BC193	2/6	BKX26	8/6	OA99	2/6
2N2102	14/-	3N123	18/6	BC190C	2/6	BKX27	8/6	OA202	2/6
2N2147	14/6	3N140	19/6	BC192L	4/6	BKX28	3/6	OC26	6/6
2N2148	12/6	3N141	19/6	BC212L	4/6	BSY29	8/6	OC28	12/6
2N2160	11/6	3N142	19/6	BCY30	5/6	BSY28	4/6	OC29	15/-
2N2183	9/6	AAZ13	2/6	BCY31	5/6	BSY39	4/6	OC35	8/6
2N2194A	4/6	AAZ15	2/6	BCY32	7/6	BSY40	6/6	OC36	12/6
2N2217	5/6	AAZ17	2/6	BCY33	7/6	BSY41	6/6	OC44	4/6
2N2218	6/6	AC107	6/6	BCY34	4/6	BSY22	6/6	OC45	2/6
2N2219	6/6	AC126	4/6	BCY35	4/6	BSY33	7/6	OC71	2/6
2N2220	5/6	AC127	5/6	BCY39	8/6	BSY34	8/6	OC72	2/6
2N2221	5/6	AC128	4/6	BCY40	7/6	BSY35A	2/6	OC75	4/6
2N2222	6/6	AC176	5/6	BCY42	3/6	BY100	4/6	OC81	4/6
2N2368	3/6	AC217	12/6	BCY43	2/6	BY110	8/6	OC82	4/6
2N2369	3/6	AC188	12/6	BCY54	6/6	BY210	9/6	OC81D	4/6
2N2369A	4/6	ACY17	5/6	BCY70	4/6	BY211	7/6	OC84	5/6
2N2369B	4/6	ACY18	5/6	BCY71	8/6	BY212	6/6	OC139	6/6
2N2440	4/6	ACY19	5/6	BCY72	3/6	BY213	5/6	OC140	6/6
2N2446	11/6	ACY20	5/6	BDY20	22/6	MJ480	18/6	OC200	6/6
2N2904	8/6	ACY21	5/6	BDY16	22/6	MJ483	25/6	OC201	9/6
2N2904A	8/6	ACY22	4/6	BD121	13/6	MJ490	20/6	OC202	12/6
2N2905	8/6	ADY26	4/6	BD123	16/6	MJ491	27/6	OC271	8/6
2N2905A	9/6	AD140	8/6	BD124	12/6	MJE20	17/6	ORP12	12/6
2N2906	6/6	AD149	11/6	BD131	24/-	MJE21	17/6	ORP61	10/-
2N2906A	6/6	AD161	7/6						

### PLESSEY INTEGRATED CIRCUITS

SL402A	42/6
SL403A	42/6
Data Sheets	2/-

### MULLARD INTEGRATED CIRCUITS (LINEAR)

TAA241	32/6
TAA242	35/-
TAA243	30/-
TAA293	15/6
TAA298	15/6
TAA300	35/-
TAA310	25/-
TAA320	14/6
TAA350	35/-
TAA435	22/6
TAA521	22/6
TAA522	22/6
TAA511	88/-
TAB101	19/6
TAD100	39/6
TAD110	39/6
Data Sheets 1/-	
(Free with I.C.s.)	

### HEATSINKS

TO-18, TO-5, TO-1, 1/-	
FINNED FOR ONE	8/6
TO-3	8/6
FINNED FOR TWO	12/5
TO-3	8/6

### THERMISTORS

R55 (8°C)	25/6
R53 (1K)	25/6
Various Mullard	
Thermistors in stock.	
Send 2/6 for new comprehensive catalogue, P.P. for Components 1/6 per order.	

### THYRISTORS

1 AMP: 50V 5/-, 100V 5/6, 200V 7/-, 400V 9/6.  
 3 AMP: 50V 8/-, 100V 7/6, 200V 8/-, 400V 10/6.  
 ZENERS, 1 1/2 WATT 2.7-33V 4.6/16 WATT 39-100V 7/6.  
 400mW 3-0-33V 4/-, 1 Watt, 2.4V-200V 7/6.

### INTEGRATED CIRCUITS - R.C.A.

CA3005 28/6, CA3011 18/6, CA3014 27/-, CA3015 19/-,  
 CA3018 19/-, CA3020 27/-, CA3020A 37/-, CA3022 27/6,  
 CA3026 21/-, CA3028A 18/6, CA3028B 24/-, CA3029 19/6,  
 CA3036 18/6, CA3041 25/-, CA3042 25/-, CA3044 27/-,  
 CA3046 19/6, CA3048 45/-, CA3050 39/6, CA3052 36/6.  
 PARALLEL

L900, 914 9/6, L923 12/6, L709C 30/6, L709C 21/-,  
 L710C 21/-, L716C 56/-.  
 DATA SHEETS FOR RCA DEVICES 2/- PER TYPE.  
**G.E. INTEGRATED CIRCUITS**  
 PA230 22/6, PA234 26/6, PA237 35/-, PA246 57/6.  
 Data Sheet 1/-.

Presets std., horiz. or vert.  
 Potentiometers, Log/Lin 2/3 each  
 Twin-ganged Pots Log and Lin. 7/6

MPD V	Price	MPD V	Price	MPD V	Price	
1	40	1/8	25	25	1/8	
2	15	1/8	25	50	1/8	
2	350	2/6	32	15	1/8	
2	5	1/8	32	450	5/6	
4	15	1/8	40	64	1/8	
4	350	2/6	50	18	1/8	
5	15	1/8	50	25	1/8	
5	15	1/8	50	25	1/8	
6	4	25	1/8	60	50	2/-
8	18	1/8	64	25	1/8	
8	40	1/8	80	16	1/8	
8	430	3/6	100	64	1/8	
10	15	1/8	100	15	1/8	
12.5	25	1/8	100	35	2/-	
16	18	1/8	100	50	2/6	
25	64	1/8	125	4	1/8	
25	10	1/8	200	64	1/8	

VERBOARD		RESISTORS	
13 Matrix	1 Matrix	1/2 watt 5%, 5d.	1 watt 10%, 6d.
2 1/2in. x 3 1/2in.	3/5	4/6	2.5 watt 5%, 1/6
2 1/2in. x 5in.	4/3	4/9	5 watt 5%, 2/6
3 1/2in. x 3 1/2in.	4/8	5/6	10 watt 5%, 2/6
3 1/2in. x 5in.	5/6		1 watt 5%, 3d.
3 1/2in. x 17in.	16/6		1 watt M.O. 2%, 1/9
3 1/2in. x 17in.	16/6		
Cutter 9/-	Veropina (Bag 50) 5/-		

## A. MARSHALL & SON

25 CRICKLEWOOD BROADWAY, LONDON N.W.2  
 TELEX 21492 01.452 0161/2/3 CALLERS WELCOME  
 Post & Packing U.K. only 1/6. Europe 6/-. Commonwealth (Air) 13/-

## AMPLIFIER FOR MAGNAVOX TAPE DECKS — 4 TRACK CAN BE USED FOR 2-TRACK



Chassis 12 1/2 x 5 1/4 x 4 1/2 in. high. Plastic front panel finished in Black and "Silver". 200-250 A.C. Record/Playback amp. switch; On/Off-Tone. Vol./Me.; Vol./Gram. Mic. Input; Gram. Input; Valves 6BR7; 12AX7; 6BM8; EL84 and EZ80. Separate Output Transformer (Already wired to amp). PRICE £12 (10/- P. & P.). 3-ohm speaker 7" x 4" 16/- extra.

### STEREO AMPLIFIER type HV — 2 x 3 Watts

Fully built. On off sep. vol. and tone each channel 12 x 4 1/2 x 6 in. high. EZ80, 2 x ECL86; for 3 ohm speakers, double wound main trans; fixing flanges and base plate, suitable for crystal cart, tuner etc. £8.10.0 (8/- p. & p., 200-250V. A.C.) Superior version — separate base, treble & vol each channel with mono/stereo switch 15/- extra.



### STEREO AMPLIFIER type RC — 2 x 3 Watts for 200-250V. A.C.

Fully built. 2 x UCL82, metal rect; ganged vol and tone cont; on-off balance. 11 x 3 1/2 x 4 in. high. Double wound mains trans. with supporting brackets. For 3-ohm speakers. £6 (3/- p. & p.)



### MONO GRAM CHASSIS 3 WATT

Wave band long-med short. Gram., 200-250V A.C. Ferrite aerial Chassis 13 x 7 x 6 in. Dual 13 x 4 in. Double wound mains transformer 5 valves ECH81, 6F89, EBC81, EL84, EZ80. Price £10.12.6 (7/5 p. & p.) Output trans. for 3-ohm speaker

NEW TAPE AMPLIFIER for 4 track B.S.R. Deck TD2. Mains and output Trans. 10" x 6" x 4" overall. Rect: OC83, EL84, Mike and Gram Inputs. £7.5.0. (10/- p. & p.) For 3-ohm speaker. (For 200-250V. A.C.)

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.  
 (2 mins. from Station and Buses), FULLY GUARANTEED. Aldershot 22240  
 CLOSED WEDNESDAY. S.A.E. for Enquiries please.

# YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates), the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME .....

ADDRESS .....

Please 1/70

## BRITISH NATIONAL RADIO SCHOOL

# BI-PRE-PAK LTD

DEPT 10, 722-724 WEST ROAD, WESTCLIFF ON SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

## FULLY TESTED AND MARKED

41:107	3/-	OC120	3/-
41:126	2/6	OC171	8/-
41:127	3/6	OC200	2/6
41:128	2/6	OC201	7/-
41:176	2/6	9G301	2/6
41:177	2/-	2G303	2/6
41:114	4/-	2N1302.3	4/-
41:115	3/6	2N1304.5	5/-
41:116	3/6	2N1306.7	6/-
41:117	3/6	2N1308.9	7/-
41:239	12/6	2N3819 P&T	9/-
41:186	10/-	2N3844A	5/-
41:189	10/-	Power	
41:190	4/-	Transistors	
41:191	7/6	OC20	10/-
41:192	3/6	OC23	10/-
41:193	3/-	OC26	8/-
41:194	3/-	OC28	8/-
41:195	3/-	OC30	7/6
41:196	3/-	OC32	7/6
41:197	2/6	AD149	10/-
41:198	2/6	AUY 10	10/-
41:199	2/6	AA102	15/-
41:200	2/6	AA103	15/-
41:201	2/6	AA104	15/-
41:202	2/6	AA105	15/-
41:203	2/6	AA106	15/-
41:204	2/6	AA107	15/-
41:205	2/6	AA108	15/-
41:206	2/6	AA109	15/-
41:207	2/6	AA110	15/-
41:208	2/6	AA111	15/-
41:209	2/6	AA112	15/-
41:210	2/6	AA113	15/-
41:211	2/6	AA114	15/-
41:212	2/6	AA115	15/-
41:213	2/6	AA116	15/-
41:214	2/6	AA117	15/-
41:215	2/6	AA118	15/-
41:216	2/6	AA119	15/-
41:217	2/6	AA120	15/-
41:218	2/6	AA121	15/-
41:219	2/6	AA122	15/-
41:220	2/6	AA123	15/-
41:221	2/6	AA124	15/-
41:222	2/6	AA125	15/-
41:223	2/6	AA126	15/-
41:224	2/6	AA127	15/-
41:225	2/6	AA128	15/-
41:226	2/6	AA129	15/-
41:227	2/6	AA130	15/-
41:228	2/6	AA131	15/-
41:229	2/6	AA132	15/-
41:230	2/6	AA133	15/-
41:231	2/6	AA134	15/-
41:232	2/6	AA135	15/-
41:233	2/6	AA136	15/-
41:234	2/6	AA137	15/-
41:235	2/6	AA138	15/-
41:236	2/6	AA139	15/-
41:237	2/6	AA140	15/-

## NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits. Date and Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN Sil. in TO-9 can	10/-
B82	10	OC45, OC81D and OC81 Trans. Mullard glass type	10/-
B83	200	Trans. Makers rejects. NPN/PNP Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
B86	150	High quality Germ Diodes. Min. glass type	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC49, OCS1, etc	10/-
B88	50	Sil. Trans. NPN, PNP, equivalent to OC209/1, 2N706A, BSX95A, etc	10/-
B80	10	7 Watt Zener Diodes. Mixed voltages	10/-
H5	16	1 Amp. Plastic Diodes, 50-1,000 Volts. 6 large, 10 small	10/-
H6	40	250mW. Zener Diode DO-7 mm. Glass Type. AV.40% Good.	10/-

## NEW TESTED & GUARANTEED PAKS

B4	4	Photo Cells, Sun Batteries 3 to 5 volt. 5 to 2 ma	10/-
H1	4	BY127 Silicon Recs. 1000 P.V.V. 1 amp. Plastic. Replaces the BY 100	10/-
B74	4	1N4007 Sil. Rec. Diodes. 1.000 P.V.V. 1 amp. Plastic.	10/-
B81	10	Reed Switches, mixed types, large and small	10/-
B83	2	58Ps Light Sensitive Cds. Light Res. 400 Ω Dark 1M Ω	10/-
B91	8	NKT163/164 PNP Germ. TO 5 equivalent to OC44, OC45	10/-
B83	4	NPN. Sil. Trans. AO6 BSX20 2N2969 500 MHz, 360mW	10/-
B93	5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ	10/-
B75	5	2N3136 PNP Sil Trans. TO 18, HFE 100-300 IC, 600mA, 200MHz	10/-
B98	10	XB119 and XB102 equiv. to AC125, AC156, OCS1/2, OC71/2, NK271, etc.	10/-
H4	250	Mixed Resistors, Post and packing 2/-	10/-
H7	40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-
H9	2	OCPT1 Light Sensitive Photo Transistors	10/-

**FREE!** Packs of your own choice up to the value of 10/- with orders over £4.

## RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductor and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give more information on the transistors

**PI PLEASE ASK FOR PAK P.I. ONLY 10/-**  
2/- P. & P. on this Pak

Complimentary Set NPN/PNP Germ. Trans. Pak F3. **2/6 PAIR**

**P.O. RELAYS 8 FOR 20/-**  
Various Contacts and Coil Resistances. Post & Packaging 5/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS and CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART

NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order OVERSEAS AND EXTRA FOR AIR MAIL

## "DRAGS IN STATIONS I NEVER NEW EXISTED" (SWL G. WHYTE, ABERDEEN) THE STICK THAT DOES THE TRICK!!!

WA2WOR, NEW YORK 23 SAYS CAN NOW OPERATE 160M FROM CENTRE OF N.Y.C. PLUS EXCELLENT PERFORMANCE H.F. BANDS.



SWL J. D. THOMPSON, 13 OLD PARK ROAD, DOVER, KENT SAYS: "FRANKLY I AM ASTONISHED BY THE ABILITY OF THE JOYSTICK—SURROUNDED AS I AM IN A BUILT UP AREA—IN A VALLEY WITH CONSIDERABLE HILLS AROUND ME" (JOYSTICK INDOORS!)

"CERTAINLY THE ANSWER TO ANTENNA PROBLEM FOR APARTMENT DWELLERS".

VARIABLE FREQUENCY ANTENNA

## ALL BAND - WORLD RECORD AWARD WINNING AERIAL - JUST 7 ft. 6 ins. LONG!

Obtainable from:—  
**R.S.G. BI-FI CENTRES at:**  
**BERMINGHAM,** 61 Western Parade  
**BRADFORD,** 10 N. Parade  
**DARLINGTON,** 18 Priestgate  
**DERBY,** 16 Osaston Rd.  
**EDINBURGH,** 183 Leith St.  
**GLASGOW,** 226 Argyle St.  
**HULL,** 91 Ferguson St.  
**LONDON,** 5-7 County Rd.  
**LEICESTER,** 32 High St.  
**LIVERPOOL,** 73 Dale St.  
**MANCHESTER,** 60a Oldham St.  
**MIDDLEBROUGH,** 106 Newport Rd.  
**NEWCASTLE/TYNE,** 41 Blackett St.  
**SEEFIELD,** 13 Exchange St.  
**LONDON** 238 Edgware Rd.  
**LASKY'S RADIO at:**  
**LONDON,** 207 Edgware Rd.  
 33 Tottenham Ct. Rd.  
 152-3 Fleet St.  
**G. W. SMITH & CO. at:**  
**LONDON,** 3 & 34 Lisle St. WC2  
 311 Edgware Rd. W2  
**IMHOF'S (Edgworths Dist.) at:**  
**LONDON,** New Oxford St. WC1  
**AND AT:**  
**ABERDEEN,** L. Hardie, 542 George St.

**ASHFORD (MIDDLE),** Echford Comm. Rath Ryland Huntley, 13 Old Bond St.  
**BIRMINGHAM,** Amateur Electronics Chas. H. Young Ltd.  
**BOURNE MOUTH,** Forresters Nat. Radio  
**BRADFORD,** Radio Ham Shack, Godwin St.  
**BRIGHTON,** Arthur Sallis, Gardener St.  
**BURNLEY,** Tristralgar Supplies  
**GARDEN,** Wessex Radio, Cathays  
**CHELMSFORD,** Radio Service, New St.  
**CHESTERFIELD,** J. & A. Tweedy Ltd.  
**EDINBURGH,** F. Brown & Co. Geo. V. Bdge.  
**EXETER,** Electrosure Ltd. Fore St.  
**FRASERBURGH,** Murray Mackie  
**GLASGOW,** RME Surplus Supplies  
**GOODMAYES,** Unique Radio, Facade  
**GT. YARMOUTH,** The Record Shop  
**HALIFAX,** Albert Hind Ltd.  
**HARTLEPOOL,** Specialist Radio  
**HERNE BAY,** Furaya's  
**HUDERSFIELD,** Radio Cast Ltd.  
**HULL,** Short Wave, Newland Ave.  
**LEFORD,** Radio Dev. Clayhall Ave.  
**IPSWICH,** Eagle Elect. (Dunsiae).  
**LEICESTER,** S. May, 12-14 Church Gate  
**LIVERPOOL,** Stephens-James, Priory Rd.  
 Super Radio (Whitechapel)

**LONDON,** City Radio, Ealing W5.  
 Newbury Radio, Forest Gate  
 R.T. & I. Elect. Ashville Rd. E11.  
**LUTON,** Coventry Radio, Dunstable Rd.  
**NEWCASTLE/LYME,** Sydney T. Chadwick  
**NEWCASTLE/TYNE,** Richey & Freeman  
**NEWPORT (MON.),** K. F. Paull, Dock St.  
**NEWQUAY,** R. V. Henning Ltd.  
**NORWICH,** Radionatics, St. Benedicts St.  
**NOTTINGHAM,** Pete's Elect. Arkwright St.  
**OLDHAM,** The Electronic Centre, The Mumps  
**PLYMOUTH,** Radioparts, 3 Market Way  
**PRESTON,** Croftilm, 46 Friargate  
**BOMFORD,** Newbury Rdo. 129 North St.  
**SARROUGH,** Derwent Rdo. Hillcrest Ave.  
**SOUTHAMPTON,** Frank Victor, Northam  
**S. SHIELDS,** J. R. Gough Elect. Incey St.  
**SUNDERLAND,** Red Radio Shop, Cowtree Rd.  
**SWANSEA,** W. J. Holt, Oxford St.  
**WESTCLIFF-ON-SEA,** Radio Const. Co.  
**WORCESTER,** Jack Porter, College St.  
**WOLVERHAMPTON,** Lings Rdo. Snow Hill  
**WOthingh.** G.W.M. Rdo. Ford Rd.  
 or from:  
**PARTRIDGE ELECTRONICS LTD., (PWA),**  
**BROADSTAIRS, KENT.** Tel: Thanet 62835

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel. PARK 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office  
When sending cash with order, please include 2/6 in £ for postage and handling  
MINIMUM CHARGE 2/6. No C.O.D. orders accepted

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel. LA.Ngham 8403  
Open all day Saturday

PLEASE NOTE THAT THE VALUES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

0A2	6/6	6A16	5/-	6F18	8/-	10P9	10/-	EF504	20/-	EF94	5/6	FFS18	17/-	1301	11/6
0A8	9/6	6A76	6/-	6F22	6/6	10F18	8/-	EF811	15/-	HR90	6/6	PL2001/1	6/6	U408	10/-
0B2	6/6	6A78A	11/-	6F23	16/6	10L1	8/-	EF812	15/6	HL92	7/6	PL3	7/6	U404	7/6
0C3	10/-	6B4A	4/6	6F24	13/6	10L1D11	11/-	EF814	13/6	HL94	8/-	PL36	11/-	U801	20/-
0C8	7/6	6B29	5/6	6F25	13/6	10P13	11/-	EK90	5/6	KT66	27/6	PL81	9/6	UABC80	6/9
0D8	6/6	6B29	16/6	6F26	7/6	10P14	20/-	EL34	10/6	K788	38/-	PL82	9/6	UA4A1	10/-
1B3GT	7/6	6B6G	12/-	6F28	14/-	12A25	9/6	EL36	9/6	N78	2/6	PL83	8/6	UA4Z	10/6
1L4	3/6	6B6G	12/-	6F29	14/-	12A26	7/6	EL41	11/-	P4BC80	8/6	PL87	7/6	UB41	11/-
1R4	4/6	6B16	8/6	6F30	7/6	12A26	7/6	EL42	11/6	PC88	13/-	PL302	15/-	UBC41	9/6
1R5	7/6	6B36	8/6	6F4	9/6	12A15	8/-	EL81	10/6	PC97	8/6	PL300	15/-	UBC81	8/6
184	5/6	6BK7A	10/-	6F37GT	6/6	12A25	8/6	EL82	8/6	PC900	9/6	PL304	18/-	UBF60	7/6
185	5/6	6BL3	7/6	6F37	6/6	12A26	8/6	EL83	8/6	PC884	7/6	PL308	17/6	UBF89	7/6
1P4	4/6	6B16	8/6	6K6GT	10/6	12A27	6/6	EL84	8/6	PC85	8/6	PL309	30/-	UBL1	10/-
1U4	6/6	6B16	8/6	6K7	6/6	12A26	5/6	EL85	8/6	PC85	8/6	PL309	30/-	UBL2	10/-
1U5	9/6	6B35	5/6	6K8G	6/6	12A27	6/6	EL90	6/6	PC89	10/6	PL302	14/-	UC92	6/6
1Y2	9/6	6BR8	13/-	6K23	10/-	12A26	8/6	EL91	5/6	PC8189	11/-	PM84	9/6	UC85	8/6
1X2R	7/6	6B87	28/-	6K23	15/-	12A27	9/6	EL95	7/6	PC806	17/-	PY31	5/6	UCF90	10/6
2D2I	6/6	6B16	18/-	6L6GT	9/6	12A27	9/6	EL96	7/6	PC806	17/-	PY33	13/6	UCY21	11/-
3A4	4/6	6B7	13/6	6L7	6/6	12A27	9/6	EL97	7/6	PC806	17/-	PY80	6/6	UCY42	13/6
3B28	4/6	6B16	18/-	6L8	6/6	12A27	9/6	EL98	7/6	PC806	17/-	PY81	6/6	UCY43	13/6
3BP1	65/-	6B26	6/6	6L20	6/6	12A27	9/6	EL99	7/6	PC806	17/-	PY82	6/6	UCY81	6/6
3Q4	8/6	6C4	6/6	6N7GT	7/6	12A27	9/6	EL99	7/6	PC806	17/-	PY83	7/6	UCY81	6/6
384	7/6	6C5GT	7/6	6P1	12/-	12B20	6/6	EL99	7/6	PC806	17/-	PY84	7/6	UCY82	7/6
3V4	8/6	6C4	5/6	6P25	21/-	12B17	6/6	EL99	7/6	PC806	17/-	PY85	7/6	UCY83	7/6
3R4GY	11/-	6C47	10/6	6P26	12/6	12B17	10/6	EL99	7/6	PC806	17/-	PY86	6/6	UCY84	7/6
3C4D	6/6	6C47	10/6	6P27	12/6	12B17	10/6	EL99	7/6	PC806	17/-	PY87	6/6	UCY85	7/6
5U4BR	7/6	6C6GA	6/6	6R7G	7/6	12K7GT	7/6	EL99	7/6	PC806	17/-	PY88	6/6	UCY86	7/6
5V4G	8/6	6C7	28/-	6S2	8/6	12Q7G	5/6	EL99	7/6	PC806	17/-	PY89	6/6	UCY87	7/6
5Y3GT	8/6	6C7	28/-	6S4	11/-	12R27	7/6	EL99	7/6	PC806	17/-	PY90	6/6	UCY88	7/6
5Z3	9/6	6C16	11/6	6S7	7/6	12R27	7/6	EL99	7/6	PC806	17/-	PY91	6/6	UCY89	7/6
62AGT	8/6	6C16	10/6	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY92	6/6	UCY90	7/6
63012	15/6	6C16	12/6	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY93	6/6	UCY91	7/6
6A6A	9/6	6C17	8/6	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY94	6/6	UCY92	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY95	6/6	UCY93	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY96	6/6	UCY94	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY97	6/6	UCY95	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY98	6/6	UCY96	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY99	6/6	UCY97	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY100	6/6	UCY98	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY101	6/6	UCY99	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY102	6/6	UCY100	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY103	6/6	UCY101	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY104	6/6	UCY102	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY105	6/6	UCY103	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY106	6/6	UCY104	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY107	6/6	UCY105	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY108	6/6	UCY106	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY109	6/6	UCY107	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY110	6/6	UCY108	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY111	6/6	UCY109	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY112	6/6	UCY110	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY113	6/6	UCY111	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY114	6/6	UCY112	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY115	6/6	UCY113	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY116	6/6	UCY114	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY117	6/6	UCY115	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY118	6/6	UCY116	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY119	6/6	UCY117	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY120	6/6	UCY118	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY121	6/6	UCY119	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY122	6/6	UCY120	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY123	6/6	UCY121	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY124	6/6	UCY122	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY125	6/6	UCY123	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY126	6/6	UCY124	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY127	6/6	UCY125	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY128	6/6	UCY126	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY129	6/6	UCY127	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY130	6/6	UCY128	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY131	6/6	UCY129	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY132	6/6	UCY130	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY133	6/6	UCY131	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY134	6/6	UCY132	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY135	6/6	UCY133	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY136	6/6	UCY134	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY137	6/6	UCY135	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY138	6/6	UCY136	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY139	6/6	UCY137	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY140	6/6	UCY138	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY141	6/6	UCY139	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY142	6/6	UCY140	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY143	6/6	UCY141	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY144	6/6	UCY142	7/6
6A6A	9/6	6C17	12/-	6S7	6/6	12R27	7/6	EL99	7/6	PC806	17/-	PY145	6/6	UCY143</	

# VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

## On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

## WHICH OF THESE IS YOUR PET SUBJECT?

**RADIO ENGINEERING**  
Advanced Radio — Gen.  
Radio — Radio & TV  
Servicing — TV Eng. —  
Telecommunications—Sound  
Recording — Automation —  
Practical Radio — Radio  
Amateurs' Exam.

**ELECTRICAL ENG.**  
Advanced Electrical Eng. —  
Gen. Electrical Eng. —  
Installations — Draughts-  
manship — Illuminating Eng. —  
Refrigeration — Elec.  
Electrical Science — Elec-  
trical Supply — Mining Elec.  
Engineering.

**CIVIL ENGINEERING**  
Advanced Civil Eng. — Gen.  
Civil Eng. — Municipal  
Eng. — Structural Eng. —  
Sanitary Eng. — Road Eng. —  
Hydraulics — Mining —  
Water Supply — Petrol Tech.

**ELECTRONIC ENG.**  
Advanced Electronic Eng. —  
Gen. Electronic Eng. —  
Applied Electronics — Prac.  
Electronics — Radar Tech. —  
Frequency Modulation —  
Transistors.

**MECHANICAL ENG.**  
Advanced Mechanical Eng. —  
Gen. Mechanical Eng. —  
Maintenance Eng. — Diesel  
Eng. — Press Tool Design —  
Sheet Metal Work—Welding  
— Eng. Pattern Making —  
Inspection — Draughtsman-  
ship — Metallurgy — Pro-  
duction Eng.

**AUTOMOBILE ENG.**  
Advanced Automobile Eng. —  
Gen. Automobile Eng. —  
Automobile Maintenance —  
Repair — Automobile Diesel  
Maintenance — Automobile  
Elec. Equipment — Garage  
Management.

"WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?  
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B.,  
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,  
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT.  
OF EDUCATION, ETC.

**British Institute of Engineering Technology**  
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

## THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT  
CAREER - GUIDANCE

PRACTICAL INCLUDING  
EQUIPMENT TOOLS

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.**

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy *now*—FREE and without obligation.



## POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT,  
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....


WRITE IF YOU PREFER NOT TO CUT THIS PAGE

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**

# HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES
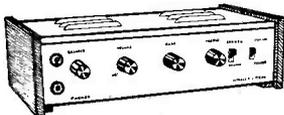
## COMPLETE STEREO SYSTEM FOR £39-10-0

**HENELEC 5-5 STEREO AMPLIFIER.** Inputs for ceramic cartridge. Aux./Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12½ x 3½ x 6½. Fitted headphone socket. Complete system comprises 5.5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10watt speakers, twin tweeters and crossover with polished wood cabinets 18" x 11" x 7". Also plinth and cover.



- COMPLETE STEREO SYSTEM (Rec. Price £50), £39-10-0 p.p. 20/-
- AMPLIFIER ONLY £13-19-6, p.p. 7/6
- TE1035 RECOMMENDED STEREO PHONES 39/6

## BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

PARTS TOTAL COST £6.19.6, p.p. 3/6  
DECODER £3.19.6 (FOR STEREO) p.p. 3/-  
ASK FOR BROCHURE No. 3.



New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.

## BUILD YOURSELF A QUALITY RADIO



Total cost £6.19.6, p.p. 6/6

Ask for Leaflet No. 1.

## SINCLAIR EQUIPMENT

Z30 75/- each, stereo 60 £8-10-0, PZ5 79/6,  
PZ6 £6-19-6, Z50 £5-9-6, PZ8 £5-19-6.

### SPECIAL OFFER

2 of Z30, stereo 60, PZ5 (usually £23-10) or with PZ6 in place of PZ5 £21


# £19

Complete range of amplifiers and preamplifiers in stock. All detailed in catalogue above.
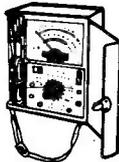
## TEST EQUIPMENT FOR YOUR HOME



AF105 50k/v multimeter (illus.), price £8-10, p.p. 3/6, leather case 28/6,  
200H 20k/v multimeter price £3-17-6, p.p. 3/-, case 12/6  
TE20D RF Generator (illus.), price £15, p.p. 7/6  
TE21D Matching Audio Generator, price £17, p.p. 17/6  
TE65 Valve Voltmeter, price £17-10-0, p.p. 7/6  
Full details and complete range in catalogue



## SLIM POCKET TEST GEAR

- SIGNAL INJECTOR 35/- p.p. 1/6
- SIGNAL TRACER 29/6 p.p. 1/6

**NEW** WORLD'S LOWEST COST STEREO MAGNETIC CARTRIDGE O/P 7mV, 20 c/s-20 Kc/s. Diamond Stylus. Fits most decks. Recommended. Price 79/6 p.p. 2/6.

## HI-FI equipment to suit EVERY POCKET



# FREE

Stock List No. 1617 on request

Choose from 100 complete stereo systems—Complete range of individual units also in stock. Demonstrations all day.

## 100 STEREO SYSTEMS

LOW CASH AND CREDIT/HP PRICES (Credit terms from £30 purchase-callers only).



## HENRY'S LATEST CATALOGUE

New print. Now 350 pages.

- ★ COMPONENTS, TEST GEAR
- ★ EQUIPMENT, MODULES
- ★ SPECIAL OFFERS ETC. ETC.

Everything for the constructor

Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-



## WHY NOT SEND AWAY TODAY?

## NEW 25watt and 50watt RMS SILICON AMPLIFIERS

### LOOK AT THE SPECIFICATIONS!

- 0.3% Distortion at full power
- -1db 11c/s to 40kc/s at full power
- Response -1db 11c/s to 100kc/s

PA25 10 Silicon Thyristors Differential input, 25watts rms into 8ohms, 700mV input. Size only 5" x 3" x 2". 4-hole fixing. Supplied with edge connector and harness.

PA50 12-Transistor Version, 50watt rms into 3 to 4ohms

MU442 Power supply for one or two PA25 or one PA50


● PA25 £7-10-0, ● PA50 £9-10-0, ● MU442 £6

### NEW! STEREO FET SELF POWERED PREAMPLIFIER

MODEL FET154

Inputs for mag. Pickup, Tuner/Aux., Tape in and out. Response 20 c/s to 30kc/s. Output adjustable up to 1 volt. Mains operated stabilised supply.

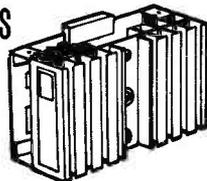Slim design. Size 12" x 5½" x 1½". Price £16.10.0



## NO SOLDERING—JUST PLUG CONNECTORS

## YOU CAN SAVE 25% brand new GARRARD

(Post 7/6)

SP25mkII £11-9-6, AP75 £16-19-6, SL65B £14-19-6, SL72B £25 A70mkII £11-19-6

**SPECIAL** Above with Sonotone 9tahr diam. Add £2, with magnetic add 70/-, with **OFFER** Goldring G800 add £8-10-0


Also Fitted with 9tahr diamond model 50

£8-10-0, 3000LM £9-15-0

Plinths/Covers: Standard 99/6, p.p. 4/6. De luxe

£8-10-0, p.p. 6/-, SL72B type £8-10-0, p.p. 6/-, Not for A70

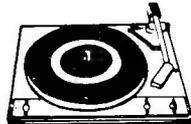
● Goldring GL69 with plinth and cover and G800 cartridge (usually £51) £39.10.0, p.p. 12/6.



## SCOOP New ¼" TRACK TAPE DECKS

British made 3 speed mains operated tape machine. Fitted Marriott XRF517 and XES11 ¼ track heads. Piano key operation. Designed for the home constructor. Operates with up to 7" spools vertically or horizontally. Size 13" x 10" x 5".

PRICE £13-19-6, p.p. 10/6

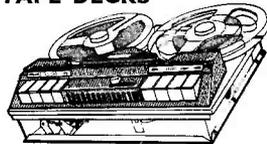

## ELECTRONIC ORGANS

★ MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT

★ TEAK VENEERED CABINETS FOR ALL MODELS


★ 49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE

★ KITS AVAILABLE IN SECTIONS AS REQUIRED

★ HP and CREDIT SALE FACILITIES

★ **FREE 16-PAGE BROCHURE**

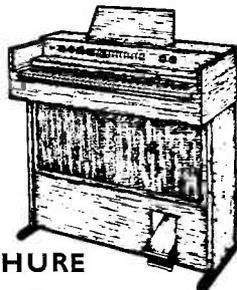Covering organs in kit form and ready built—write or phone to ORGAN DEPT. Ask for Peter Elvins.



# HENRY'S RADIO LTD.

Mail Order Dept, Electronic Components and Equipment, and Electronic Organ Dept.  
303 EDGWARE ROAD, LONDON W2.  
Telephone: 01-723 1008/9  
Open Mon-Sat 9am-6pm, Thurs 9am-1pm

High Fidelity and Audio Centre  
309 EDGWARE ROAD, LONDON W2.  
Telephone: 01-723 6963  
Open all day Saturday.