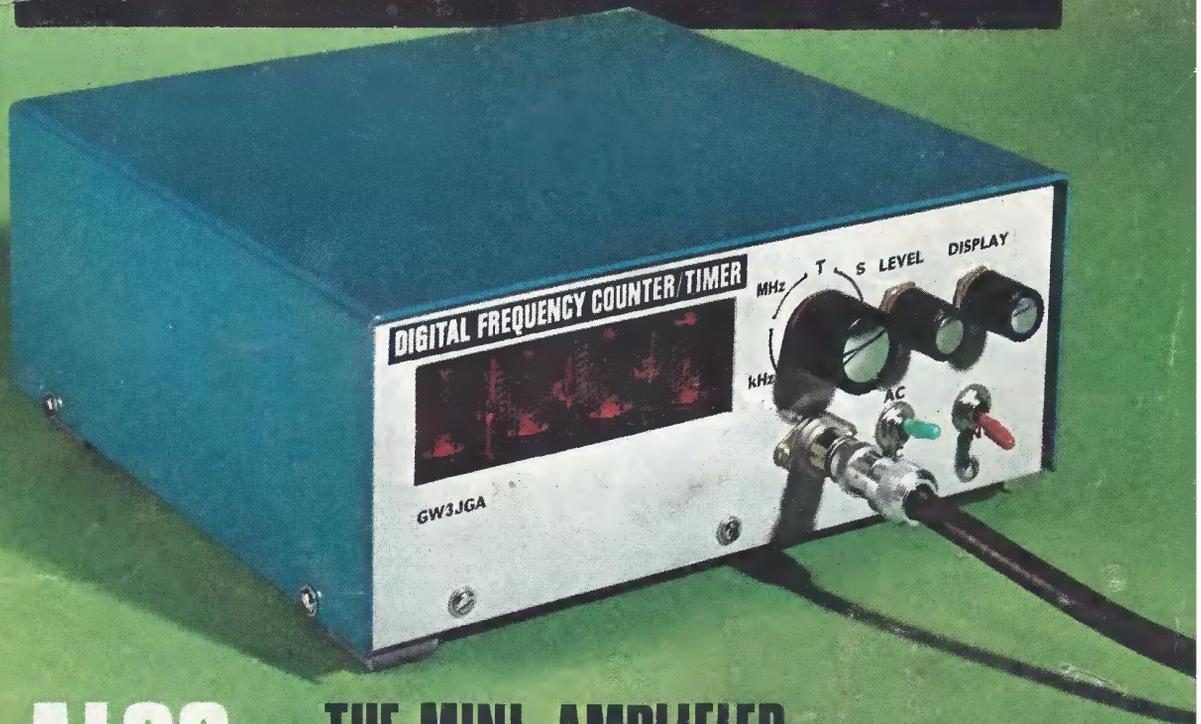


PRACTICAL WIRELESS

SEPTEMBER
1971

20p

DIGITAL FREQUENCY COUNTER/TIMER



ALSO... THE MINI-AMPLIFIER
THE 'HARMONIC SIX' RECEIVER

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{4}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{3}{16}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

PRICE
£1.85



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



* Write for price list and catalogue.

ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-822 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

WICKS FOR BARGAINS

E.A. STEREO AMPLIFIER:

5 watts per channel; In attractive afromosia veneered sleeve. Controls: On-off volume: Bass: Treble: Balance; Selector; Headphone Jack. Ceramic or Magnetic P.U. Radio and Tape Inputs: Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14½"W x 9½"D x 45"H approx. £16.50 inc. post.

3 WAY SPEAKER SYSTEM:

8" twin cone Bass speaker and 3" tweeter, fitted in extremely elegant teak veneered cabinet. Size: 18½"H x 11½"W x 10"D. 8 ohms handle 10 watts. £7.50 inc. Carr.

GARRARD OFFERS

Garrard SP25 Mk III (Rec. Price (£16.44) **Our Price £11.25.** Carr. & Ins. 50p.

Garrard SP25 Mk III ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23.79). **Our Price £16.** Carr. & Ins. 75p.

Or with choice of fitted cartridges.

SP25 Mk III/Sonotone 9TAHC (Rec. Price £27.89) **Our Price £18.** Carr. & Ins. 75p.

SP25 Mk III/Shure M3DM (Rec. Price £31.62) **Our Price £20.** Carr. & Ins. 75p.

SP25 Mk III/Goldring G800 (Rec. Price £36.79) **Our Price £21.** Carr. & Ins. 75p.

SP25 Mk III/Shure M55E (Rec. Price £36.76) **Our Price £21.** Carr. & Ins. 75p.

Note! Garrard SL65B (Automatic Changer version of **SP25 Mk III**) alternatively supplied—please add £3 to above prices.

Garrard AP76 (Rec. Price £28.88)

Our Price £20.85. Carr. & Ins. 50p.

Garrard AP76 ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs).

Please state choice. (Rec. Price £40.88). **Our Price £27.** Carr. & Ins. 75p.

OR WITH CHOICE OF FITTED CARTRIDGES.

Garrard AP76/Shure M3D (Rec. Price £48.29) **Our Price £30.55.**

Carr. & Ins. 75p. **Garrard AP76/Shure M55E** (Rec. Price £53.85). **Our Price £33.35.** Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £53.85) **Our Price £33.35.** Carr. & Ins. 75p.

Garrard 2025TC fitted with stereo/mono cartridge. £8.99. Carr. Paid.

TEAK PLINTH & PERSPEX COVER

Ready cut to take 2025TC, SP25 III, SL65B available at £4.99. Carr. & Ins. 35p.

CARTRIDGES

Sonotone 9TAHC dia. Rec. Price £4.10. **Our Price £1.99**

Shure M3DM (Rec. Price £7.41) **Our Price £4.87.**

Shure M55E (Rec. Price £12.97) **Our Price £9.50.**

Goldring 800 (Rec. Price £13.00) **Our Price £7.50.**

Goldring 800 H (Rec. Price £10.69) **Our Price £6.99.**

P & P 18p any type

- Guaranteed all brand new best quality goods. No rubbish.
- Mail order only.
- By return Post service.
- All enquiries SAE please.

Special Offer!
Grundig GDM312 Dynamic Microphones. List £7.35 **OUR PRICE £3.** P & P 30p

Service Sheets
1,000's on all makes T.V.'s, Radios, Tape Recorders, Record Players. 13p incl. post. Please state model. Cheques & open P.O.'s returned if sheets not available.

Hi-Fi Stereo Headphones
(Value £5.00) Only £2.25 inc. post.

Speaker Cloth
Best quality. Width 36". Under half price at 55p per yd. Black with gold fleck, will blend with any room setting. End of stock line, yds and yds must go.

Plugs, Sockets and Leads.

Phono plugs; 3p each

30p per dozen.

2 pin Din spkr. plugs

10p each.

3 pin Din plugs.

15p each.

5 pin Din plugs.

13p each.

5 pin Din sockets

(chassis) 7p each.

Stereo Jack Sockets

c/cct. 13p each.

Phono sockets

(chassis) 2 way 3p; 3

way 4p; 4 way 5p.

6ft. stereo lead 5 pin

Din to open end. 45p

6ft. stereo lead 2

phono to open end. 37p

12ft. spkr. lead 2 pin

Din to open end. 40p.

Please add P & P 5p.

100 Mixed Resistors

½ watt 10% all best quality (no ex government) 40p.

Pots

100K x 100K lins & Logs.

stereo. 35p inc. post.

100K DP switch stereo,

log. 45p inc. post.

50K single Balance.

15p inc. post.

4 B.A. brass nuts

50 for 25p inc. post.

Speaker cabinets

Attractively veneered

in afromosia, black

front. Size approx.

7½"W x 9½"D x 4½"H.


Ready cut to take

8" x 5" speaker.

£1.99. P. & P. 12p.

D. T. WICKS & CO. 49 North Station Rd, Colchester, Essex.

Tel: (0206) 78807

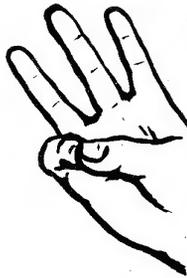

3 WAYS

HOME RADIO (Components) LTD.
 Dept. PW, 234-240 London Rd.,
 Mitcham, CR4 3HD. 01-648 8422

of obtaining components *quickly & easily*

1

**CALL AT No. 240
 London Rd., Mitcham**

If you live within easy reach of Mitcham or are in the area at any time do call on us. We are almost opposite Mitcham Baths. We open 9 a.m. every weekday. On Wednesdays we close 1 p.m. and all other days, including Saturdays, 5.30 p.m. On Saturdays we have extra staff to deal with queries. We carry a vast stock of components, and 999 times out of a 1,000 we can immediately lay our hands on the particular item required.

2

**JOIN OUR CREDIT
 ACCOUNT SERVICE**

We began our Credit Account Service about 18 months ago and it has proved extremely popular. Little wonder! Our customers find it a very simple and convenient way of purchasing all their radio and electronic needs. We supply pre-paid envelopes and order forms and no matter how many orders you send us you make only one payment per month. There are several other advantages with our Credit Account Service. Please write or phone for details.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

3

**and
 ORDER BY MAIL
 OR TELEPHONE**

Although we are kept busy selling "over the counter" we supply even more by Mail Order. You can telephone any time of day or night, Sundays included. If you ring out of office hours a recording machine takes your message for us to deal with as soon as we open shop again. Our number is 01-648 8422. If you wish to order by post our address is in the panel at the top of the page. We deal with all orders promptly.



**WHICHEVER WAY YOU
 CHOOSE** you need the
 Home Radio Catalogue

In its 315 pages are listed over 8,000 components, over 1,500 of them illustrated. Each copy contains 10 Vouchers, each worth 5p when used as instructed. Free Supplements are supplied regularly to keep you up-to-date. The Catalogue costs 50p over the counter, or 70p including postage and packing.

*Post this Coupon with
 Cheque or PO for 70p*

Please write Name and Address in block capitals.


Name

Address

.....

HOME RADIO (Components) LTD.
 Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD

SP25 MKIII SPECIAL!

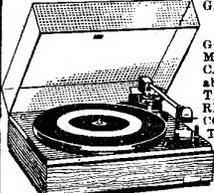

GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDING S90 or AT66 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.

Total list price over £29.
PREMIER PRICE
£19.90
 P. & P. 50p.

TAPE CASSETTES



C60 (60 min.)	37p	£1.05
C90 (90 min.)	62p	£1.80
C120 (120 min.)	87p	£2.55

P. & P. 5p.

All cassettes can be supplied with library cases at 3p. extra each



"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped - attractively boxed.

LP3 3" 250'	P.V.C.	28p	DT6 5 1/2" 1800'	POLYESTER	£1.18
TP3 3" 450'	POLYESTER	37p	TT8 5 1/2" 2400'	POLYESTER	£1.87
DT3 3 1/2" 600'	POLYESTER	57p	SP7 7" 1800'	P.V.C.	62p
SP5 5" 800'	P.V.C.	42p	LP7 7" 1800'	ACETATE	75p
LP5 5" 900'	P.V.C.	50p	DT7 7" 2400'	POLYESTER	£1.25
DT5 5" 1200'	POLYESTER	75p	TT7 7" 3600'	POLYESTER	£2.50

TAPE SPOOLS 8" 10p, 5", 5 1/2", 7" 8p.
 Post and Packing 3" 5p, 5", 5 1/2", 6p, 7" 10p. (3 reels and over Post Free).

PREMIER QUALITY MICROPHONES



Precision made, beautifully designed and offering reliability at reasonable price.

FANON MKO-47 MINIATURE DYNAMIC
 Frequency response 60-13,000 Hz. Impedance 60K ohms (-59 db). Can be used with stand, hand held or around neck. Diecast body with chrome finish. Features removable windscreen. Complete with 8ft. cable, stand adaptor and Lavalier cord.
PREMIER PRICE £5.97, P. & P. 20p.

FANON MKO-45 3-WAY DYNAMIC
 Frequency response 60-12,000 Hz. High impedance. Complete with 8ft. cable, table stand and Lavalier cord.
PREMIER PRICE £2.87, P. & P. 20p.

FANON MKC-54 DYNAMIC
 Frequency response 60-12,000 Hz. Impedance 50K ohms (-60 db) and 150 ohms (-71 db). On/Off switch. Complete with 20ft. cable and stand adaptor.
PREMIER PRICE £8.97, P. & P. 20p.

E.M.I. 13x8in. HI-FI SPEAKERS



Fitted two 2 1/2in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.

£3.47 P. & P. 40p

METER BARGAINS

MODEL GT-800 MULTIMETER

A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 10, 50, 250, 1,000V (1,000 opV). AC Voltage: 10, 50, 250, 1,000V (1,000 opV). DC Current: 1mA, 100mA. Resistance: 0-150K ohms. Decibel: -10 +23db (at AC 10V range) £2.47, P. & P. 17p.



MULTIMETER 20,000 O.P.V.

Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4 1/2" x 3 1/2" x 1". RANGES D.C. Voltages 0-5-25-50-250-500-2500V. A.C. Voltages 0-10-50-100-500-1000V. D.C. Current: 0-50µA-2.5mA-250mA. Resistance: 0-6000 ohms 0-6 megohms (300 ohms and 30 K ohms at centre scale). Capacity: 10 µF to +0.01µF, -0.01µF to -1µF. Decibels -20 to +25dB. £4.90. P. & P. 17p.



MODEL CT-62 MULTITESTER

RANGES—DC Voltages: 0, 5, 25, 100, 500/1,000V (20,000 ohms/V). AC Voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). DC Current: 0, 50µA, 0, 5, 50, 500mA. Resistance: 0, 6K, 600K, 6M, 60M ohms. Decibels: -20 db to +62 db in 5 ranges. £5.62, P. & P. 17p.



PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
 HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451




JACKSONS

Accelerator Spin Wheel

for that Extra Long Scale

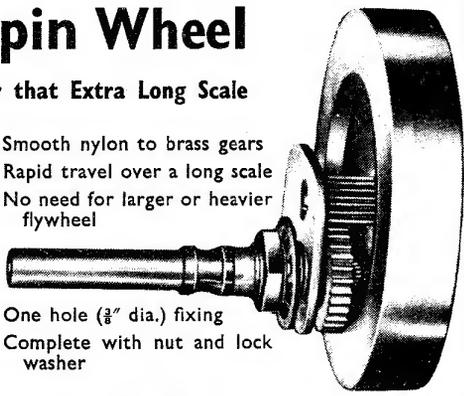- ★ Smooth nylon to brass gears
- ★ Rapid travel over a long scale
- ★ No need for larger or heavier flywheel



- ★ One hole (3/8" dia.) fixing
- ★ Complete with nut and lock washer

Write for literature:
JACKSON BROTHERS (London) LIMITED
 Dept. P.W. Kingsway, Waddon, Croydon CR9 4DG.
 Phone: (01)-688 2754/5 Grams: Walfilco, Croydon.
 U.S. Office: M. Swedgal,
 258 Broadway, New York, N.Y. 10007

AUDIO POWER AMPLIFIERS

TYPE S1-1010A
 MAX CONTINUOUS
 OUTPUT POWER
 10W
 SINGLE ENDED
 PUSH-PULL
 CIRCUIT

TYPE S1-1020B
 MAX CONTINUOUS
 OUTPUT POWER
 20W.
 CAN WITHSTAND
 5 SEC. SHORT
 CIRCUIT

PRICES FROM
 £2.75 to £11 ea
 ACCORDING TO
 TYPE & QUANTITY

TYPE S1-1020A
 MAX CONTINUOUS
 OUTPUT POWER
 25W.
 HARMONIC DISTORTION
 LESS THAN
 0.5%

TYPE S1-1050A
 MAX CONTINUOUS
 OUTPUT POWER
 50W.
 FREQUENCY RANGE
 20HZ to 100KHZ

FOR FULL INFORMATION WRITE TO
PHOTAIN CONTROLS LTD.
 RANDALLS ROAD, LEATHERHEAD. 2776-5517

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	4p	OC170	4p
AC126	0-15	OC171	0-23
AC127	0-13	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACV17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-80	2N1302-3	0-50
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171	0-13	2N1308-9	0-35
BC172	0-13	2N3819PBT	0-45
BF194	0-15		
BF274	0-15	Power Transistors	
BFY90	0-20	OC20	0-50
BSY25	0-87	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-13	OC36	0-37
OC41	0-13	AD149	0-30
OC44	0-13	ALY10	1-25
OC45	0-13	2B014	0-25
OC71	0-13	2N3055	0-63
OC72	0-13		
OC73	0-17	Diodes	
OC81	0-13	AA42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	CA81	0-09
OC140	0-17	IN9114	0-07

FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

CLEARANCE LINES

SL403D Audio Amp.	1.10	10.80	80+
IC 709C Linear Opp. Amp.	2.00	1.95	1.80
A.E.I. Fully marked & tested Gates	50p	40p	35p
A.E.I. Fully marked & tested Flipflops	25p	22p	20p
OC71/78 Fully tested, unmarked	50p	40p	30p
Matched Sets 1-OC44, 2-OC45 Per set	5p	3p	4p
Matched Sets, OC45, 1st & 2nd I.F. Per set	25p	20p	15p
TIG45 Thyristors, 6A, 50V Texas	15p	15p	12p
DA457 Gold bonded Diodes, marked & tested	3p	3p	2p
1W Zener Diodes 6.8V, 7.5V, 24V, 27V, 30V & 43V	5p	4p	3p
10W Zener Diodes 7.5V, 11V, 13V, 20V & 100V	20p	17p	15p
Micro Switches, S/P, C/O Popular size	25p	20p	15p
1 Amp Bridge Rectifiers 25V, RMS	25p	22p	20p

1 Amp Plastic Rectifiers. These are voltage, reverse Polarity and other rejects from the BY 127 range. Ideal for low voltage Power Units etc. Price £1 per 100.

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each post and packing 25p.

BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1

Post and packing 25p.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	1N4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV, 1 amp, plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	20	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

F.E.T. PRICEBREAKTHROUGH!!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

Make a Rev. Counter for your Car. The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

FREE CATALOGUE AND LISTS for:-

ZENER DIODES
TRANSISTORS, RECTIFIERS
FULL PRE-PAK LISTS
& SUBSTITUTION CHART

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS **8 FOR £1**
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, metal TO-5 can. 25300 type, direct replacement for the OC200/203 range.

TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.

TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.

TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

BULK BUYING CORNER

NPN PNP Silicon Planar Transistors TO-18 mixed untested similar to 2N706-6A-8, BSY26-7A9-95A and BCY70 etc. £4.25 per 500. £8 per 1000.

NPN Silicon Planar transistors plastic encapsulation untested similar to 2N3707 to 3711. £4.25 per 500. £8 per 1000.

Silicon planar diodes do-7 glass similar to OA200-202, BAY31-36. £4.50 per 1000.

NPN PNP Silicon planar transistors plastic TO-18 similar to BC113-4, BC153-4, BF153-160, etc. £4.25 per 500. £8 per 1000.

NPN Silicon planar transistors TO-5 can similar to BC142 3, BFY50-2-3. £5.25 per 500, £10 per 1000.

OC44, OC45 transistors fully marked and tested 500 to 999, 8p each, 1000+ 6p each.

OC71 transistors fully marked and tested, 500 to 999, 6p each, 1000+ 5p each.

A amp miniature plastic diodes 1N4001 at 500 to 999, 4p each, 1000+ 3p each. 1N4004 at 500 to 999, 5p each, 1000+ 4p each. 1N4006 at 500 to 999, 6p each, 1000+ 5p each. 1N4007 at 500 to 999, 8p each, 1000+ 7p each.

NEW UNMARKED UNTESTED PAKS


B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW, Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1½ watt Zeners. Top hat type	50p
H11	30	MAT Series "alloy" pnp Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts.	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

FREE! A WRITTEN GUARANTEE WITH ALL OUR SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

28watts, r.m.s. 40Hz to 40kHz ± 3 dB

There are two stereo amplifiers — the RT100 for ceramic cartridges, the RT101 for magnetic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

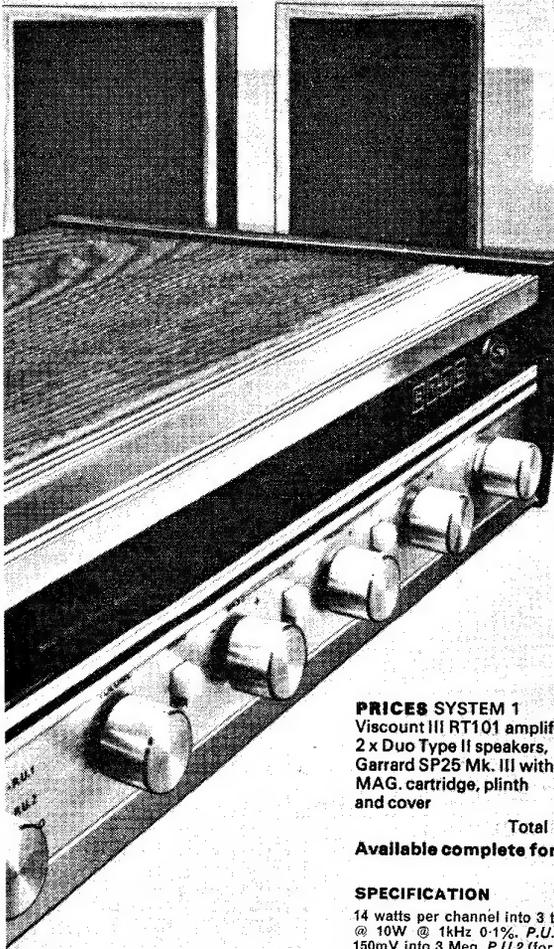

Viscount III Audio Suite complete £49

PRICES SYSTEM 1

Viscount III RT101 amplifier £22.00 + 90p p&p
2 x Duo Type II speakers, £14.00 + £2 p&p
Garrard SP25 Mk. III with
MAG. cartridge, plinth
and cover

Total £23.00 + £1 p&p
£59.00

Available complete for only £52.00 + £2.50 p&p

SPECIFICATION

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within ± 1 dB R.I.A.A. Radio 150mV into 220K (Sensitivities given at full power.) Tape out facilities; headphone socket, power out 250 mV per channel. Tone controls and filter characteristics: Bass: ± 12 dB to -17 dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control; treble $+ 12$ dB to -12 dB @ 15kHz. Treble filter: 12 dB per octave. Signal to noise ratio: (all controls at max.) RT101 — P.U.1. & radio — 65dB. P.U.2 — 58 dB. RT100 same as RT101 but P.U.2. for crystal cartridges 450 mV into 3 Meg. Cross talk better than -35 dB on all inputs. Overload characteristics 26dB on all inputs. Size $13\frac{1}{2}'' \times 9'' \times 3\frac{1}{2}''$

Goods cannot be despatched outside the U.K.

SYSTEM 2

As System 1, but with 2 x Duo Type III speakers at pair £32.00 + £3 p&p
Available complete for £69 + £4 p&p

SYSTEM 3

Viscount III Amplifier RT100 £17.00 + 90p p&p
2 x Duo Type II speakers, pair £14.00 + £2 p&p
Garrard SP25 Mk. III with CER. diamond
cartridge, plinth and cover £21.00 + £1 p&p

Total £52.00

Available complete for only £49.00 + £2.50 p&p

SPEAKERS Duo Type II


Size $17'' \times 10\frac{3}{4}'' \times 6\frac{3}{4}''$. Drive unit $13'' \times 8''$ with parasitic tweeter. Max. power 10 watts, 3 ohms. Teak veneer cabinet. £14 pair + £2 p&p.
Duo Type III Size $23\frac{1}{2}'' \times 11\frac{1}{2}'' \times 9\frac{1}{2}''$. Drive unit $13\frac{1}{2}'' \times 8\frac{1}{2}''$ with H.F. speaker. Max. power 20 watts at 3 ohms. Frequency range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

Radio and TV Components (Acton) Ltd, 21c High Street, Acton, London W3 6NG
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.

R+TV

SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

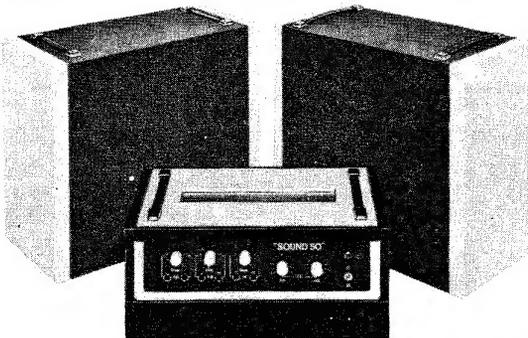

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). **Frequency response:** -3dB points 30Hz at 18KHz. **Total distortion:** less than 2% at rated output. **Signal to noise ratio:** better than 60dB.

Speaker Impedance: 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

SPEAKERS! Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

COMPLETE SYSTEM £50 Plus £4 P. & P.


Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.50 plus £1.50 P. & P.
Speakers £12.50 each plus £1.75 P. & P.

THE ELEGANT SEVEN Mk. III

(350m W Output)

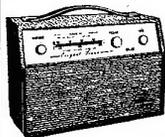


7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 75p extra.

Price £5.25 plus 50p. P. & P.

Circuit 13p FREE WITH PARTS.

THE DORSET (600m W Output)

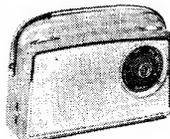


7-transistor fully tunable M.W.—L.W. superhet portable. Set of parts. The latest modularised and pre-alignment techniques make this simple to build. **Sizes:** 12 x 8 x 3in.

Price £5.25 plus 50p P. & P.

Circuit 13p FREE WITH PARTS

CONTINENTAL 4 TRACK, 3 SPEED TAPE DECK

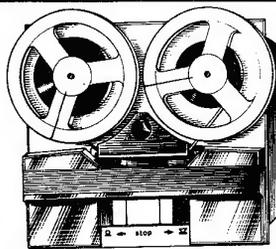

R.C. 74 tape deck. Three speeds—7½, 3½ and 1½ ips.

4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7". The R.C. 74 is driven by a powerful 200/250V 50-cycle A.C. motor. A heavy, accurately balanced, flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7½ ips. Fast rewind in both directions.

Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6 inches. Every single deck fully tested before dispatch. Spools not supplied.

Price complete £15.00. Plus 75p P. & P.

TOURIST


MARK 3

CAR RADIO

ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

See previous page for address

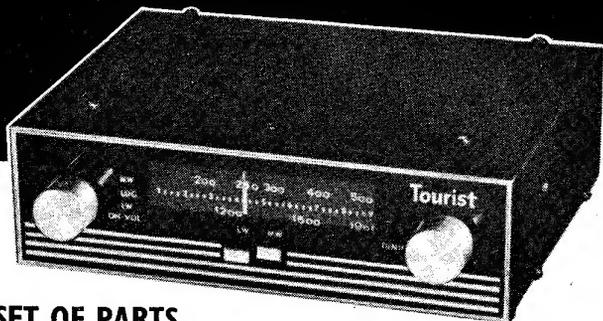

SET OF PARTS

£6.30

plus P. & P. 50p.

Circuit diagram 13p. Free with parts

Speaker, baffle and fixing kit

£1.25 extra plus 25p. p. & p.

Postage free when ordered with parts.

RADIO & TV COMPONENTS
R+TV
(ACTON) LIMITED

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- Radio Operator Certificates
- General Certificate of Education, etc.

Now available Colour T.V. Servicing Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewarts Road, London, S.W.8 4UJ
Please send me the ICS prospectus—free and without obligation.
(state Subject or Exam).....

NAME
(BLOCK CAPITALS PLEASE)

ADDRESS

AGE.....OCCUPATION..... 9/71

INTERNATIONAL CORRESPONDENCE SCHOOLS

AT HOME SOLDERING ?

Our miniature irons are used all over the world in that most exacting market—the modern electronics industry, the rapidly developing technology of which has made possible the enormous growth of activities available to the technical hobbyist.

He now also requires equipment to the highest commercial standards. Like our soldering irons, for example.

Look at the ADAMIN Model 15. If there is a smaller iron for mains use, we haven't seen it. It weighs a mere ½ oz (less flex) and is about 7 inches long.

But it has a big performance. Used with interchangeable bits from $\frac{3}{16}$ " to $\frac{1}{16}$ " it is suitable for all work, from Hearing Aids to Colour Television.

Use the mains version at home or clip the 12 volt model to the car battery or 12 volt power unit (consumption only 1.25A).

Send for HOBBY PACK 10 consisting of Model 15 iron with four bits, $\frac{3}{16}$ ", $\frac{1}{8}$ ", $\frac{1}{16}$ " and tube of Bit Lubricant. State voltage required—12v or 220/240v.

PRICE: HOBBY PACK £2.30
p & p FREE

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL
Telephone 01-688 8589 and 4559



TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1. WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. 4 section 24" retractable chrome plated Telescopic aerial for Short Waves for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Parts Price List and Easy Build Plans 25p (FREE with parts).


Total building costs £6.98 Post, packing and insurance 41p.

Overseas P. & P. 90p



roamer seven mk IV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

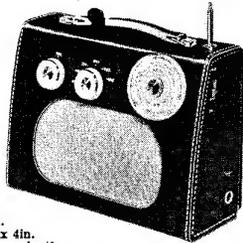


Total building costs £5.98 Post, packing and insurance 41p.

Overseas P. & P. 90p

NEW! trans eight

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra

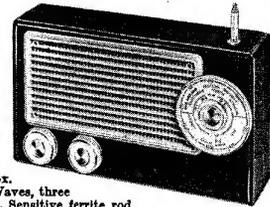


Total building costs £4.48 Post, packing and insurance 31p.

Overseas P. & P. 70p

pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

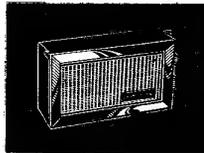Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.



Total building costs £2.23 Overseas P. & P. 55p Post, packing and insurance 21p.

transona five

NOW WITH 3" SPEAKER

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE

Attractive case with red speaker grille. Size 9½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra




Total building costs £2.50 Overseas P. & P. 55p Post, packing and insurance 22p.

IMPROVED MODEL!

roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra

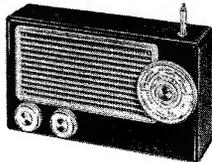

Total building costs £3.98 Overseas P. & P. 70p Post, packing and insurance 26p.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT ROAMER SEVEN
TRANSONA FIVE TRANS EIGHT
POCKET FIVE ROAMER SIX

Parts price list and plans for

Name

Address

PW.30

★ Callers side entrance Barratts Shoe Shop

★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

IMPORTANT. THIS LATEST 1971 MODEL INCORPORATES ALL THE LATEST TECHNOLOGICAL IMPROVEMENTS AND SUPERSEDES ALL EARLIER MODELS! YES, THIS SENSATIONAL BRAND NEW VEF 204 RUSSIAN 8 WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION will probably make your present radio seem like a "crystal set"! It's far better than any other 8 wave radio that even they have produced before! It even incorporates a special MARINE WAVEBAND to receive spoken communications from ship-to-shore! Complete with optional battery eliminator for both battery and mains use! It represents the finest value we have ever offered! We're almost giving them away at only £13.97—a mere fraction of even today's Russian miracle price! In fact we challenge you to compare the performance and value with that of £42.00 radios! *You just can't lose, we'll refund your money instantly if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto, for absolute "pin-point" station selection! Yes, the Russians have really surpassed themselves this time, proving once again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO ITS TRUE VALUE! Yes, 8 separate wavebands, including Standard Long, Medium and Short Waves to cover the world. PLUS special "ship-to-shore" MARINE BAND! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions, and stations at your fingertips 24 hours a day, including ships at sea, etc. and messages from all over the world—truly nothing is secret! The radio enthusiast can have the world in the palm of his hand! You must hear it to believe it! Super-sweet tone—controlled from a whisper to a roar that will fill a hall! Genuine push-pull output! Separate ON/OFF volume and Treble/Bass-tone controls! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v. AC mains supply. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 31ins length. It's also a fabulous CAR RADIO—any speed, requires no additional aerial, UNIQUE! Elegant Black & Chrome finish case. SIZE 11ins. x 9ins. x 3 1/2ins. overall approx. Magnificently designed & superbly made to give years of perfect service. Complete with WRITTEN GUARANTEE, manual with simple operating instructions & circuit diagram. ONLY £13.97 (with mains/battery eliminator £13.98 extra). BOX, POST ETC. 50p. Standard batteries 38p extra. Can also be used through extension amplifier, tape recorder or public address system. Send today or call at either store, but HURRY! It's the chance of a lifetime. (Sorry—We cannot change these new radios for any earlier model already purchased). Send quickly or call at either store. Refund guaranteed.

RUSSIAN WORLD BEATER!

JUST ARRIVED!

The Fabulous BRAND NEW 1971

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

VEF 204 8 WAVEBAND

10 TRANSISTOR PLUS 2 DIODES PORTABLE RADIO

AND NOW WITH SHIP-TO-SHORE MARINE BAND

BATTERY MODEL £13.97p
BOX POST ETC. 50p

MAINS/BATTERY ELIMINATOR £1.38p extra



WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!

***COMPARE IT'S PERFORMANCE with £42 RADIOS!**

SHOPERTUNITIES LTD. SL

HOLBORN, LONDON, W.C.1 (opposite Chancery Lane). (Wednesday 1, Thursday 7). Both stores open MONDAY-SATURDAY 9-6.

Dept. WP/9 164 UXBRIDGE RD., LONDON, W.12 8AQ (facing Shepherd's Bush Green). (Thursday 1 pm, Friday 7 pm) ALSO 37/39 HIGH

4-STATION INTERCOM



£6.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. £0.40.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price **£13.95** P. & P. £0.55

INTERCOM/BABY ALARM



OUR PRICE ONLY £3.15

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 13p. P. & P. £0.25.



£2.98

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 13p. extra. P. & P. 20p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.S.)
169 KENSINGTON HIGH STREET, LONDON, W.8.

PIEZO DYNAMIC MICROPHONE

50k Ω £1.00 pp 8p

MULLARD SCREW TERMINAL CAP

4,500uf 64v 50p pp 13p.

BELLING LEE 1.5 amp in-line rubber covered interference suppressor 25p pp 8p.

SOLENOIDS 12 VOLT FULL ACTION

2" x 1" x 3" 40p pp 8p.

SPC SEALED RELAYS DOUBLE POLE CHANGEOVER

48v 2500 Ex-equip. 15p pp 5p. Miniature 12v 2500 New 2 changeover 40p pp 5p new.

SIEMENS MINIATURE RELAY. Double pole changeover dust cover/base 48v 2500 60p pp 5p new.

TELESCOPIC AERIALS

Chromed 7" closed 28" extended 6 section ball jointed base 23p pp 8p new.

MULLARD 4 DM 160 INDICATORS in plastic holder/cover ex-equip. size approx. 1 1/2" x 1 1/2" x 3/4" 38p pp 8p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200

Diodes: 1 reed relay: 10 AZ 228 zenner ass. capacitor/resistors. Power supply 22v 250 mA DC. Output 240v. AC £1 pp 20p ex-equip.

TOGGLE SWITCHES. Single pole Double Throw

ex-equip. new condition. 50p doz. pp 13p.

FIBRE GLASS TAPE. 100 yd. roll: 3" 3/4" wide

£1 per roll pp 20p.

PAINTON PLUG SOCKETS Type 169 series working voltage 350v AC/DC current max. 3 amp AC/DC


7 pin plug & socket 50p pp 10p. 15 pin plug & socket £1 pp 10p.

CASH WITH ORDER PLEASE

FIELD ELECTRIC LIMITED

3 SHENLEY ROAD, BOREHAMWOOD, HERTS.
Adjacent Elnetree Mainline Station
Tel: 01-953 6009.

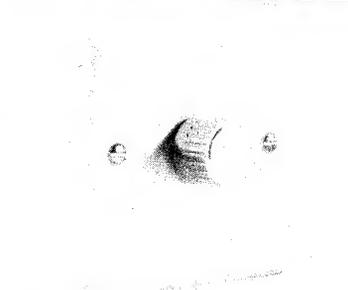Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300w or 600w of all lights except fluorescent at mains voltages from 200-250v, 50Hz. The DIMMASWITCH has built-in radio: 600—£3.20 Kit from £2.70 300—£2.70 Kit from £2.20 All plus 10p. post and packing. Please send C.W.C. to:—

DEXTER & COMPANY
2 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH Tel: 0244-25883,
As supplied to H.M. Government Departments.

DISCOUNTS UP TO 60% ON BRANDED GOODS

ALL BRAND NEW
in manufacturer's sealed cartons.
GUARANTEED 12 MONTHS.

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG · THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

SPECIAL OFFER

Garrard SP25 Mk.III.
Goldring G800H

Teak plinth and tinted cover
Ready wired for immediate use.
Please add £1.15 for post & packing

£19.50

TURNTABLES

Please add 50p for post and packing

*Garrard SP25 Mk.III	£10.75
*Garrard 2025TC with stereo cart.	£8.00
*Garrard 2025TC with Sonotone 9TAHC	£8.95
*Garrard 3000 with Sonotone 9TAHC	£12.25
*Garrard SL65B	£13.25
*Garrard AP76	£18.75
*Garrard SL72B	£24.00
*Garrard SL75B	£26.00
*Garrard SL95B	£35.50
Garrard 401	£27.00
*B.S.R. MP60	£11.50
Pioneer PL12AC	£39.00
Thorens TD 125	£24.50
Thorens TD 125AB	£26.50
Thorens 150 AB11	£42.50
Goldring GL69/2	£21.50
Goldring GL69 P2	£29.50

* Items marked can be mounted in plinth and cover, ready wired for £4.50 extra plus 25p for post & packing.

AMPLIFIERS

Please add 50p for post and packing

Armstrong 521 (cased)	£41.95
Armstrad 8000	£17.70
Euromphon 10+10	£14.50
Leak 30 Chassis	£42.95
Leak 70 chassis	£51.50
Leak 30 Cased	£49.00
Leak 70 Cased	£59.00
Metrosound ST20	£25.25
Philips R580	£20.50
Pioneer SA500	£41.50
Pioneer SA700	£68.00
Pioneer SA900	£94.50
Rogers Ravensbrook Chassis	£36.00
Rogers Ravensbrook Cased	£41.00
Rogers Ravensbourne Chassis	£45.00
Rogers Ravensbourne Cased	£49.50
Sinclair 2000 Mk1	£21.00
Sinclair 2000 MkII	£24.50
Sinclair 3000	£32.50
Sinclair PRO 60/2 x Z30/P25	£18.00
Sinclair PRO 60/2 x Z30/P26	£18.00
Sinclair PRO 60/2 x Z50/P28/Tran	£28.95
Teleton SAQ206	£18.00

TUNERS

Please add 50p for post and packing

Armstrong 523 AM/FM	£41.00
Armstrong 524 FM	£32.00
Dulci FMTT	£20.00
Dulci FMTT Stereo	£27.50
Teleton GT101 MPLX	£31.50
Rogers Ravensbourne FET 2 Chassis	£47.00
Rogers Ravensbourne FET 2 Cased	£51.00
Rogers Ravensbrook FET 4 Chassis	£34.00
Rogers Ravensbrook FET 4 cased	£39.00

PICK-UP ARMS

Please add 35p for post and packing

SME 3009/S2	£26.00
SME 3012/S2	£27.50

TUNER AMPLIFIERS

Please add 75p for post and packing

Armstrong 525 FM	£70.75
Armstrong 526 AM/FM	£80.75
Teleton CR10T with speakers	£28.25
Teleton CR200 (new product)	£30.75
Teleton CR55	£87.00
Teleton TSF50	£55.00
Teleton F2000	£31.50
Wharfedale 100-1	£114.00

SPEAKERS

Please add £1.25 for post and packing

(PRICE PER PAIR)

Wharfedale Denton	£31.25
Wharfedale Melton	£49.90
Wharfedale Triton	£45.75
Wharfedale S/Linton	£16.50
Keletron KN500	£19.50
Keletron KN700	£31.50
Keletron KN123/3	£27.50
Keletron KN1000	£37.00
Keletron KN1500	£41.50
Keletron KN2000	£35.50
K.E.F.	£35.50
Celestion Dittion 120	£26.50
Celestion Dittion 15	£24.50
Celestion Dittion 25	£101.00
Celestion Dittion 10	£67.50
Ste-Ma 400	£34.00
Ste-Ma 300	£45.50
Hi-Fi 4	£78.00
Hi-Fi 115	£17.50
Hi-Fi 3	£83.50

GLOBAL CONTRACT SERIES

Contract 8 3-way 7 watts R.M.S.	£16.00
Contract 6 3-way 5 watts R.M.S.	£10.75

SPEAKER KITS

Wharfedale Unit 3	£20.50
Wharfedale Unit 4	£27.00
Wharfedale Unit 5	£39.00

CARTRIDGES

Please add 10p for post and packing

Goldring G850	£4.15
Goldring G800H	£5.75
Goldring G800	£6.95
Goldring G800E	£10.95
Goldring G800SE	£15.95
Sonotone 9TAHC Diamond	£1.75
Shure M3DM	£4.95
Shure M445/7/C	£7.20
Shure M55	£9.20
Shure M75E	£14.50
Shure V15 Type 2	£28.00
Shure M44E	£3.25
Shure M31E	£8.75
Shure M32E	£9.15
Audio-Technica AT66	£4.95
Audio-Technica AT35	£14.95
SMC 101	£3.15
VC15	£5.75

TAPE DECKS & RECORDERS

Please add 75p for post and packing

Teleton FXB 5100	£46.50
Teleton TCR130	£28.75

PERSONAL CALLERS VERY WELCOME!

Come and browse through our multi 1,000 foot warehouse/showroom.

NO PARKING PROBLEM


The following branded names are not allowed to be advertised at Discount Rates—**SONY, SANYO, BANG & OLUFSEN, TRIO, RADFORD, SONAB, NIKKO, CHILTON, FERROGRAPH, LUXOR, CELESTION, AKAI, TANNOY, TANDBERG, TEAC, CAMBRIDGE, ARENA, ROTEL.**

Send a stamped addressed envelope for a **GUARANTEED DISCOUNT PRICE.**

PLINTHS & COVERS

(as illustrated)

£3-25

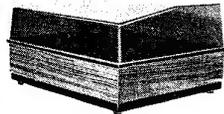

plus 35p post and packing

Finished in real teak veneer with tinted dustcover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B.

ALSO FOR B.S.R. McDONALD MP60 AND OTHERS

Plinths and Covers for AP76; AP75; SL72B; SL75B; SL95B. £4.25 plus 35p post and packing. Also finished in walnut to match Japanese equipment—no extra charge.

GLOBAL TRANSEUROPEAN COMBO

Made by world famous European manufacturer

COMPLETE HI-FI STEREO SYSTEM

VHF/MEDIUM/LONG WAVE Tuner Amplifier 4 watt per channel, separate tone and balance controls. Two neat speakers with wooden slatted front. Single play deck in plinth and cover. Finished in teak. Fully guaranteed 12 months. On constant demonstration.

£38.50

plus £1.25 carriage




GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept.(P.W.1.)174 Pentonville Road, London, N1. Telephone 01-278 1769

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

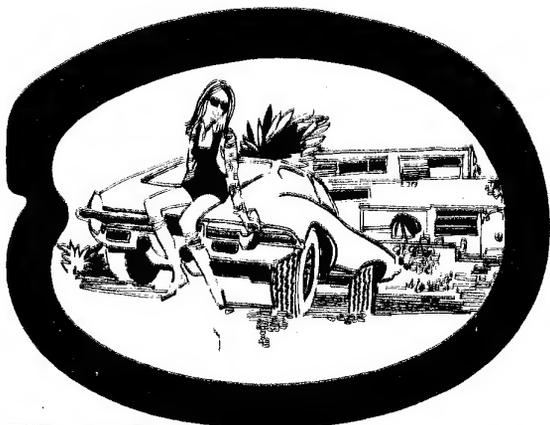MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).




**High Salary
A Dream House
A New Car
And A Secure Future**

Get into the Computer Industry the fast and easy way.

Now for the first time, anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a **computer operator in only 4 weeks** — and can earn £2,000 + + p.a.

How? We are the only commercial training organisation in the U.K. permitted to use the famous 'Eduputer'. **JOBS GALORE!** 144,000 new operators will be needed over the next five years alone. And the moment you qualify our exclusive computer appointments bureau introduces you to computer users everywhere. This is your big opportunity to get out of a rut and into the world's fastest growing industry. Find out more **FREE** and without obligation by posting this coupon **TO-DAY.**

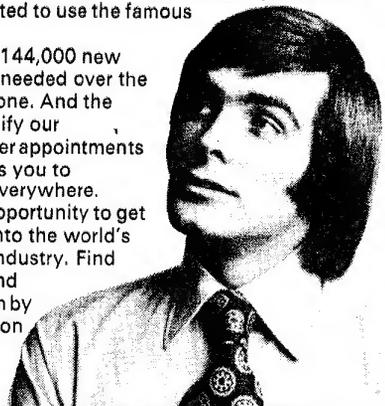

London Computer Operators Training Centre

C18 Oxford House, 9/15, Oxford Street, London, W1. Telephone: 01-734 2874
127/131 The Piazza, Dept. **C18** Piccadilly Plaza, Manchester 1. Telephone: 061-236 2935.

Please send me your **FREE** illustrated brochure on exclusive Eduputer 'hands on' training for computer operating.

Name _____

Address _____

Tel. _____



**M. & B. COMPONENTS
(LEEDS) LIMITED**

(INCORPORATING M. & B. RADIO)

PO BOX 125, 38 BRIDGE END, LEEDS LS1 4EW. Tel: 0532-38649

AD108D MARCONI COMMUNICATION RECEIVER. 9 miniature valves plus Xtal filter and tunable BFO covering 260 to 310 Kc/s and 2 to 14.5 Mc/s in 4 switched bands. Slow motion drive with logging scale. Originally intended for 24v DC operation but supplied with details for converting to mains operation. In very clean tested condition. **£15.50**

BC 221 FREQUENCY METER. Complete with chart. In clean condition. Limited number only. **£14.75**

MB2/20A TWO METRE TRANSCEIVER. Rx tuneable over 2 metre band. 20 watts RF output AM modulated. Ideal for mobile or fixed station, only requires connection to speaker, aerial and 12v DC supply to become fully operational. Fuller details on our lists. **£50.00**

6 TO 12 VOLTS DC TRANSISTOR CONVERTOR. Brand new. 6v DC input, 12v DC output at 4 amps conservatively rated. Ideal VW owners. **£5.40**

TRANSISTOR BOARDS. 10 assorted boards containing approx. 100 transistors and diodes for **£1.00**


12V INVERTER TRANSFORMERS. Complete with circuit to build inverter to give 350v output at 300 m/a. **£2.20**

GEIGER COUNTERS. Well-known contamination meter comprised of main unit fitted with meter marked in Milli Rontgens/Hours probe lead and carrying case. Audio output available from socket on front panel. Supplied new or as-new condition. Model 1 fitted with vibrator PSU using 4 pen cell batteries. **£4.85**

Send SAE for full lists with many bargains of general interest
All prices include carriage and packing

INTER-LOCKING PLASTIC STORAGE DRAWERS

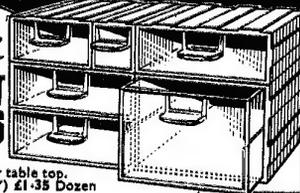Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.



DISCOUNT PRICES
SINGLE UNITS: (5" x 2 1/2" x 2 1/2") £1.35 Dozen
DOUBLE UNITS £2.25 Dozen
TREBLE (3D) £2.35 for 8
DOUBLE TREBLE 2 draws in one outer case (6D2) £3.65 for 8 extra large size (6D1) £3.30 for 8.

PLUS QUANTITY DISCOUNTS! Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £. Pack./Post./Carr.: Add 35p to all orders under £5. Orders over £5 P/P free. (Dept PW9) 124 CRICKLEWOOD BROADWAY, LONDON N.W.2

IVORYET LIMITED

ELECTRONIC IGNITION **pwjune**

Type P1/6 transformer, £1.50 including p&p. Complete kit including ready drilled case, screws, terminals, wire, etc. 12v only, state whether positive or negative earth system. **£8.75** including p&p.

MAGTOR LTD., 68, DALE STREET, MANCHESTER 1

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK • OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS
 TYPES WX.100
 100 x 80 mm.



20V. D.C.	23-97	50V. D.C.	23-97
50-0-50μA	23-87	300V. D.C.	23-97
100μA	23-87	1 amp. D.C.	23-97
100-0-100μA	23-87	5 amp. D.C.	23-97
500μA	23-121	300V. A.C.	23-97
1mA	23-97	VU Meter.	23-75


BAKELITE PANEL METERS
 TYPE S-80
 80 mm.
 square fronts



50μA	23-121	50V. D.C.	23-47
50-0-50μA	23-87	300V. D.C.	23-47
100-0-100μA	23-87	1 amp. D.C.	23-47
500μA	23-62	5 amp. D.C.	23-47
1mA	23-47	300V. A.C.	23-62
20V. D.C.	23-47	VU Meter.	23-75

"SEW" CLEAR PLASTIC METERS

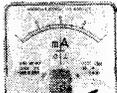Type MR.85P. 4 1/4 in. x 4 1/4 in. fronts.



50μA	23-60	500mA	23-60
50-0-50μA	23-10	1000mA	23-60
100μA	23-10	5 amp. D.C.	23-60
100-0-100μA	23-10	15 amp. D.C.	23-60
200μA	23-87	30 amp. D.C.	23-60
500μA	23-75	20V. D.C.	23-60
1mA	23-60	50V. D.C.	23-60
1-0-1mA	23-60	15V. A.C.	23-60
5mA	23-60	30V. A.C.	23-60
10mA	23-60	S Meter 1mA	23-60
		VU Meter.	23-60

Type MR.38P. 1 1/2 x 3 1/2 in. square fronts.



50μA	23-60	200mA	23-37
50-0-50μA	23-87	300mA	23-37
100μA	23-87	500mA	23-37
100-0-100μA	23-87	750mA	23-37
200μA	23-75	1 amp. D.C.	23-37
500μA	23-60	2 amp. D.C.	23-37
500-0-500μA	23-37	5 amp. D.C.	23-37
1mA	23-37	10V. D.C.	23-37
1-0-1mA	23-37	15V. D.C.	23-37
2mA	23-37	100V. D.C.	23-37
5mA	23-37	150V. D.C.	23-37
10mA	23-37	300V. D.C.	23-37
20mA	23-37	500V. A.C.	23-37
50mA	23-37	500V. A.C.	23-37
100mA	23-37	S Meter 1mA	23-60
150mA	23-37	VU Meter.	23-10

Type MR.45P. 2 in. square fronts.

50μA	23-25	5 amp.	23-50
50-0-50μA	23-10	10V. D.C.	23-50
100μA	23-10	20V. D.C.	23-50
100-0-100μA	23-10	50V. D.C.	23-50
200μA	23-10	300V. D.C.	23-50
500μA	23-10	15V. A.C.	23-50
500-0-500μA	23-10	30V. A.C.	23-50
1mA	23-10	5 amp. A.C.	23-50
5mA	23-10	10 amp. A.C.	23-50
10mA	23-10	20 amp. A.C.	23-50
1 amp.	23-10	30 amp. A.C.	23-50

Type MR.52P. 2 1/2 in. square fronts.

50μA	23-10	10V. D.C.	23-10
50-0-50μA	23-60	20V. D.C.	23-10
100μA	23-60	50V. D.C.	23-10
100-0-100μA	23-87	300V. D.C.	23-10
500μA	23-25	15V. A.C.	23-10
1mA	23-10	30V. A.C.	23-10
5mA	23-10	S Meter 1mA	23-10
10mA	23-10	VU Meter.	23-10
50mA	23-10	1 amp. A.C.	23-10
100mA	23-10	5 amp. A.C.	23-10
500mA	23-10	10 amp. A.C.	23-10
1 amp.	23-10	20 amp. A.C.	23-10
5 amp.	23-10	30 amp. A.C.	23-10

Type MR.65P. 3 1/4 in. x 3 1/4 in. fronts.

50μA	23-75	10V. D.C.	23-10
50-0-50μA	23-75	50V. D.C.	23-10
100μA	23-75	15V. A.C.	23-10
100-0-100μA	23-60	30V. A.C.	23-10
500μA	23-60	300V. D.C.	23-10
500-0-500μA	23-10	50V. A.C.	23-10
1mA	23-10	150V. A.C.	23-10
5mA	23-10	300V. A.C.	23-10
10mA	23-10	5 amp. A.C.	23-10
50mA	23-10	10 amp. A.C.	23-10
100mA	23-10	20 amp. A.C.	23-10
500mA	23-10	30 amp. A.C.	23-10
1 amp.	23-10	500mA A.C.*	23-10
5 amp.	23-10	1 amp. A.C.*	23-10
10 amp.	23-10	5 amp. A.C.*	23-10
50 amp.	23-10	10 amp. A.C.*	23-10
5V. D.C.	23-10	20 amp. A.C.*	23-10

***MOVING IRON—ALLOTTHERS MOVING COIL**
 Please add postage

SEW EDUCATIONAL METERS



meter movement is demonstrate internal working. Available in the following ranges:

50μA	24-50	20V. d.c.	23-97
100μA	24-25	80V. d.c.	23-97
1mA	23-97	300V. d.c.	23-97
50-0-50μA	24-25		
1-0-1mA	23-97	Dual range	
1A d.c.	23-97	600mA/5A d.c.	24-25
5A d.c.	23-97	6V/50V d.c.	24-25
10V d.c.	23-97		

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/4 in. square fronts.

500mA	23-75	1 amp.	23-75
5 amp.	23-75	5 amp.	23-75
15 amp.	23-75	15 amp.	23-75
30 amp.	23-75	30 amp.	23-75
50 amp.	23-75	5V. D.C.	23-75
5V. D.C.	23-75	20V. D.C.	23-75
20V. D.C.	23-75	50V. D.C.	23-75
50V. D.C.	23-75	300V. D.C.	23-75
300V. D.C.	23-75	50V. A.C.*	23-75
50V. A.C.*	23-75	150V. A.C.*	23-75
150V. A.C.*	23-75	300V. A.C.*	23-75
300V. A.C.*	23-75	500mA A.C.*	23-75
500mA A.C.*	23-75	1 amp. A.C.*	23-75
1 amp. A.C.*	23-75	5 amp. A.C.*	23-75
5 amp. A.C.*	23-75	10 amp. A.C.*	23-75
10 amp. A.C.*	23-75	20 amp. A.C.*	23-75
20 amp. A.C.*	23-75	30 amp. A.C.*	23-75
30 amp. A.C.*	23-75	VU Meter.	23-10

25μA	23-50	50μA	23-37
50-0-50μA	23-25	100-0-100μA	23-25
100μA	23-25	500μA	23-10
100-0-100μA	23-25	1mA	23-10
500μA	23-10	1-0-1mA	23-10
1mA	23-10	5mA	23-10
1-0-1mA	23-10	10mA	23-10
5mA	23-10	50mA	23-10
10mA	23-10	100mA	23-10

EDGWISE METERS

Type PE.70. 3 1/8 in. x 1 1/8 in. x 1 1/8 in. deep.

50μA	23-60	500μA	23-60
50-0-50μA	23-87	1mA	23-87
100μA	23-87	300V. A.C.	23-87
100-0-100μA	23-75	VU Meter.	23-25
200μA	23-75		

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

MULTIMETERS for EVERY purpose!




TECH PT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500mA. D.C. 0/100K. \$19.75. P. & P. 124p.

HONOR TE.10A. 20k Ω/Volt 5/25/50/250/500/2,500 v. D.C. 10/50/100/500/1,000 v. A.C. 0/50mA/2.5mA/250mA D.C. 0/6K/6 meg. ohm. -20 to +22 db. 10-0, 100 mfd. 0.100-0.1 mtd. \$3-47. P. & P. 15p.



MODEL TE-200 30,000 O.P.V. Mirror scale, overload protection. 0/5/15/60/300/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30mA/300/300mA. 0/16K/160K/1.6M/16M Ω. -20 to +62 db. \$3-75. P. & P. 15p.

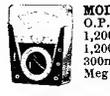MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection. 0/5/15/60/300/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30mA/300/300mA. 0/16K/160K/1.6M/16M Ω. -20 to +62 db. \$5-97. P. & P. 15p.



MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30mA/300/300mA. 0/16K/160K/1.6M/16M Ω. \$5-60. P. & P. 15p.

TMK MODEL MD.120 Mirror scale. 20k Ω/Volt D.C. 10k Ω/Volt A.C. 30/60/300/600/3,000 V. D.C. 6/12/120 V. A.C. 0-60mA/0 - 12/300mA. 0-60K/0-6 Mohms -20 to +63 db. \$4-52. P. & P. 15p.




MODEL TE-12 20,000 O.P.V. 0/0.5/6/30/120/1,200/5,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/6K/600K/6Meg./60 Meg. Ω 50pF. 0.2mFd. \$2-97. P. & P. 174p.

MODEL TE-90 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 v. D.C. 0/6/30/120/300/1,200 v. A.C. 0/3K/60/600/600mA. D.C. 10K/100K/1.6M/16M Ω. -20 to +63 db. \$7-50. P. & P. 15p.



MODEL PL436 20k Ω/Volt D.C. 8k Ω/Volt A.C. Mirror scale. 0/3/12/30/120/600V. D.C. 0/30/120/600V. A.C. 50/600mA/600/600 mA. 10/100K/1 Meg/10 Meg/10 Meg. Ω P & P 174p.

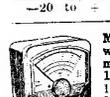SKYWOOD SW-500 50k Ω/Volt. Mirror scale DC Volt 0/3/12/30/100/600. DC Current 50mA/600. 600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +57 db. \$7-50. P. & P. 15p.




MODEL 500 30,000 O.P.V. with overload protection. mirror scale 0/5/25/100/250/500/1,000/5,000/6,000V. D.C. 1/2.5/10/25/100/250/500/1,000V. A.C. 0/30mA/300/300mA. 12 amp. D.C. 0/60K/6 Meg./60 Meg. Ω. \$2-87. Post paid.

MODEL AS-100D. 100K Ω/Volt. 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 v. D.C. 0/6/30/120/300/600 v. A.C. 0/10mA/60/300mA/12 amp. 0/2K/200K/2M/2000K Ω. -20 to +17 db. \$12-50. P. & P. 174p.



TMK MODEL TW-20CB FEATURES RESETTABLE OVERLOAD BUTTON. Scale 0/5k Ω/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 3, 10, 50, 100, 500, 1,000V. D.C. Currents: 1-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K. 5 MEGΩ. Decibels: -20 to +52 db. \$11-60. P. & P. 174p.

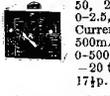TE-900 20,000 Ω/VOLT GIANT MULTIMETER. Mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/25/100/500/1,000 v. A.C. 0/25/12.5/10/50/250/1,000 5,000 v. D.C. 0/50mA/110/100/500mA/10 amp. D.C. 0/2K/200K/20 MEG. OHM. \$15. P. & P. 25p.




TMK LAB TESTER. 100,000 O.P.V. 6in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. 5K Ω/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 10, 50, 100, 500, 1,000V. D.C. Current: 10, 100mA, 10, 100, 500mA, 2.5, 10 100 MEQΩ. Decibels: -10 to 49 db. Plastic Case with Carrying Handle. Size 7 1/4 in. x 6 1/4 in. x 3 1/4 in. \$18-95. P. & P. 25p.

FTC-401 TRANSISTOR TESTER Full capabilities for measuring A-B and IGO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$2-97. P. & P. 15p.



270° WIDE ANGLE mA METER MW1-6 60mm square \$3-97 MW1-8 80mm square \$4-97 P. & P. extra

HONEYWELL DIGITAL VOLT METER VT.100 Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug-in cards. Specification: Accuracy: ± 0.2 ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999) Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Full floating (3 poles). Input power: 110-250V. A.C. 83/16in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE \$49-97 1/2 Carr. 50p.

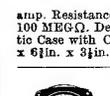

TE-40 HIGH SENSITIVITY A.C. VOLTMETER 10 meg. input 10 ranges: 0/1/000-1/3/1/30/130/300V. R.M.S. 4cps-1.2 Mc/s. Decibels -40 to +60db. Supplied brand new complete with leads and instructions. Operation 230V. A.C. \$17-50. Carr. 25p.

HONEYWELL DIGITAL VOLT METER VT.100 Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug-in cards.

HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE

SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



RECORD DECKS

- B.S.R.**
Mini Mono† \$4-97
CI29* \$8-97
MP60 \$11-75
610 \$12-75
610 \$12-95
310 \$10-95
MP60 T.P.D.I. \$19-50
- GARRARD**
A40 II* \$8-40
2025 T/C* \$9-87
3500* \$9-75
SE25 III \$11-75
A70 II \$11-97
SL65B \$14-97
AP76 \$20-97
SL72B \$28-00
SL75B \$28-50
SL90B \$38-50
401 \$29-50
- GOLDRING**
GI.69/2 \$21-95
GL.69/2 \$28-50
GL75 \$29-97
GL75P \$28-50
LID69/75 \$21-40
G99 \$28-97
PIONEER
PL12AC \$37-95




TELETON SAQ-206 STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag, xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List \$29.50 OUR PRICE \$19-50 Carr. 37p.

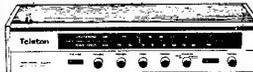TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/ Amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/ Car phono inputs. APC/Built-in MPX List \$51. OUR PRICE \$30-50. Carr. 50p.

SUGGESTED SYSTEM

F.2000, Garrard 2025/T/C Changer fitted stereo cartridge, with plinth and cover and pair of G.W.S. 3 way Speakers. Total Rec. Price \$97-79. OUR PRICE \$56-95 Carr. \$1.


TRANSISTORISED FM TUNER

TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6x4x2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. \$59.75. P. & P. 12p. Stereo multiplex adaptor \$4-97.



TE-1035 STEREO HEADPHONES
Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedances. 25-18,000 Hz. With lead and stereo jack plug. ONLY \$1-97. P. & P. 12p

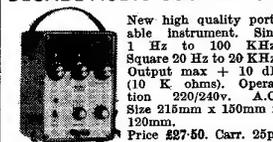BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR




New high quality portable instrument. Size 1 1/2 x 1 1/2 x 1 1/2 in. Square 20 Hz to 20 KHz. Output max + 10 dB (10 K ohms). Operation 200/240V A.C. Size 215mm x 150mm x 120mm. Price \$27-50. Carr. 25p.

B.C. 221 FREQUENCY METERS

latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. \$27-50 each. Carr. 50p.

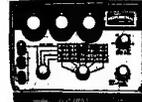TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. 6 Ranges ± 1% L.L. μ H - 111 HENRY'S 6 Ranges ± 2% C. 10pF - 1110nF. 6 Ranges ± 2%. TURNS RATIO 1:1/100. 1:1/100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2 1/2 in. \$20. P. & P. 25p



TE-16A Transistorised Signal Generator. Ranges 400Hz-30MHz. 100Hz modulation. Operates on 9v battery. Wide easy to read scale. 5 1/2 x 8 1/2 x 3 1/2 in. Complete with instructions and leads. \$7-97. P. & P. 20p.

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mFd 2 ohms 200 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New \$17-50. Carr. 37p.



RUSSIAN 22 RANGE MULTIMETER

Model U487 20,000 o.p.v. First class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 mA/1/10/100mA/A. Resistance 300 ohms/3/30/300K/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$5-97 P. & P. 25p.



RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 2 sec to 100 milli sec/cm. Supplied complete with all accessories and instructions \$87. Carr. paid.

TEI I. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz (-3dB). Accuracy: ± 0.05dB. Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new. \$27-50. P. & P. 25p.




ROUND SCALE TYPE PENCIL TESTER MODEL TS 68

Completely portable, simple to use pocket sized tester. Ranges 0/5/30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY \$1-97 P. & P. 15p.



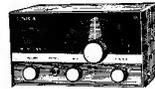UR-1A SOLID STATE COMMUNICATION RECEIVER
4 Bands covering 550kc/s-30mc/s. FET, 8 Meter, Variable BFO for 8SB, Built-in Speaker, Bandspread, Sensitivity Control. 220/240V, A.C. or 12V. D.C. 12 1/2 x 4 1/2 x 7 1/2 in. Brand new with instructions. \$25. Carr. 37p.



UMR-30 RECEIVER
4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240V. A.C. or 12V. Brand new with instructions. \$15-75. Carr. 37p.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-450kc/s, 550 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., phase inverter, S. Meter, Bandspread, RF Gain. 15" x 9 1/2" x 8 1/2". 13 lbs. 220/240V. A.C. or 12V. D.C. Brand new with instructions. \$45. Carr. 50p.

CRYSTAL CALIBRATORS NO. 10

Small portable crystal controlled wavemeter. Size 7 x 7 x 4 in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V D.C. 0.8A. Excellent condition. \$4-47. Carr. 37p.



SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 30V-230V. Model MR 2306 5 amp 68 x 48 x 43mm \$8-97. Model MR 2310 10 amp 90 x 68 x 60mm \$11-97. Postage 12p.



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.
150 W. \$2-37 1/2 P. & P. 17p
300 W. \$3-25 P. & P. 23p
500 W. \$4-97 1/2 P. & P. 32p
1000 W. \$7-25 P. & P. 37p
1500 W. \$8-97 1/2 P. & P. 42p
5000 W. \$20-00 P. & P. \$1

VOLTAGE STABILISERS TRANSFORMERS

150-230V. Input. Output 230V. Available 150w or 225w. \$12-50. Carr. 25p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots \$40) Quantities available.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range stock. Single hole fixing. 1/2 in. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 72p. P. & P. 7p.
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. \$1-05 P. & P. 7p.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. \$1-37 P. & P. 7p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery
8-260 General Purpose Bench Mounting
1 Amp \$5-50
2.5 Amp \$6-75
5 Amp \$9-75
8 Amp \$14-50
10 Amp \$19-50
12 Amp \$21-00
20 Amp \$27-00

8-260B Panel Mounting
1 Amp \$5-50
2.5 Amp \$6-82
Please add postage
ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS.
Special discounts for quantity

RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge.
Garrard 2025 T/C with Sonotone 9TAHCD \$14-50
Garrard SP2511 Goldring G800... \$19-50
Garrard AP76 Goldring G800... \$20-95
BSR MP60 Audio Technica AT.55... \$21-00
Goldring GL68/2 Goldring G800... \$27-50
Goldring GL75 Goldring G800... \$27-50
Goldring GL75 Goldring G800... \$32-50
Carriage 50p extra any model.



SINCLAIR EQUIPMENT

Project 60. Package offers.
2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. \$18-75 Carr. 37p. Or with PZ6 power supply \$18-85 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ5 power supply. \$20-25. Carr. 37p.
Transformer for PZ5. \$28-97 extra.
Add to any of the above \$4-87 1/2 for active filter unit and \$16 for a pair of Q16 speakers.
Project 60 FM Tuner \$20-97. Carr. 37p.
All other Sinclair products in stock.
2000 Amp \$24-50 Carr. 37p.; 3000 Amp \$31-50 Carr. 37p.; Neoteric Amp \$45-97 Carr. 37p IC10/IC23 \$2-50



LATEST CATALOGUE



SEND NOW!
STILL ONLY 37 1/2 P
P & P 10p

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

Note! ALL SHOPS AND OFFICES CLOSED FOR ANNUAL HOLIDAYS AUGUST 2nd to AUGUST 14th. No goods will be despatched during this period—please order early.

G.W. SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1
3 LISLE STREET, LONDON, W.C.2
34 LISLE STREET, LONDON, W.C.2
311 EDGWARE ROAD, LONDON, W.2

Tel: 01-636 3715
Tel: 01-437 8204
Tel: 01-437 9155
Tel: 01-262 0387

OPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to—
11-12, Paddington Green,
London, W.2
Tel: 01-262 3562
(Trade supplied)

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	33p
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	36p
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	36p
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	36p
Rod Aerial	RA2W		72p
Driver Transformer	LFDT4/1		58p
Output Transformer	OPT1		58p
Printed Circuit	PCA1		58p

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS


Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	39p
T41/2E	2nd I.F. Transformer	39p
T41/3T	3rd I.F. Transformer	57p
T41/3T	B.F.O. Coil	57p

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

WEYRAD (ELECTRONICS) LIMITED
SCHOOL STREET, WEYMOUTH, DORSET

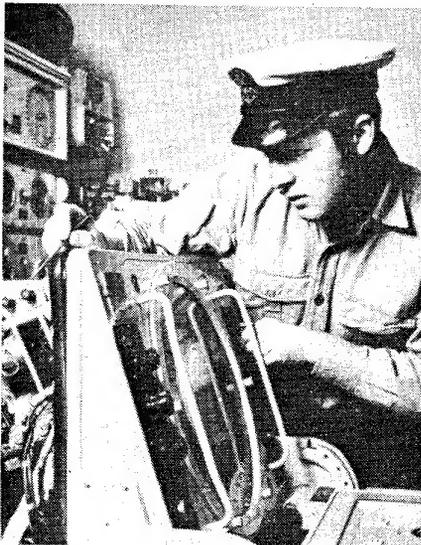Be a technician on radar, radio and electronics.



As an Artificer Apprentice, you train to be one of the Navy's top technicians: at 24 you'll be a £2,000 a year man responsible for ultra modern radar, radio and electronic equipment. If you're 15½-17½, with 'O' level standard in Maths, and Science or English, send for details.

APPRENTICESHIPS

Name _____

Address _____

Date of birth _____

(Enquiries from U.K. residents only)

Royal Naval Careers Service (830QED),
Old Admiralty Bldg., Whitehall,
London S.W.1. Please send me,
without obligation, your free booklet,
"Royal Navy Technician Apprenticeships".

RN
ROYAL NAVY

AUDIO SUPPLIES

SLASH PRICES! UP TO 60%

SUPERB Plinths & Covers



ONLY
£3.25 P. & P. 50p

for GARRARD and B.S.R. SP25, SL65B, 3500, 3000 2025TC, 2000, 1025, 5100, AT6, AT60, 40B, B.S.R. McDonald range. All decks are finished in teak polish and will blend in any modern home. The covers are of tinted Perspex (please state deck when ordering).

SUPERIOR PLINTHS AND COVERS FOR GARRARD AP75, AP76, SL72B, SL75B and SL95B.
£4.99. P.P. 60p (R.R.P. £9.50)

STEREO AMPLIFIERS p.p. £1-00

ARMSTRONG 521	£42.99
AMSTRAD 8000	£17.99
H.L. SA707	£19.90
TELETON SAC208	£18.95
VICEROY AS70	£42.00
VICEROY 55	£18.00
SANSUI In stock	
METROSOUND ST20	£25.00
SINCLAIR 8000	£23.50
SINCLAIR 8000	£35.00
SINCLAIR NEOTERIC	£46.00
SINCLAIR A.F.U.	£4.75
SINCLAIR 980 + 2 Z30/PZ5	£40.00
SINCLAIR 960 + 2 Z30/PZ8	£19.00
SINCLAIR 960 + 2 Z50 + PZ8 and Mains trans.	£25.00

TUNER AMPLIFIERS p.p. £1-00

ARMSTRONG 528	£82.00
ARMSTRONG 528	£72.00
TELETON TFS50	£54.00
TELETON CRT10T with speakers	£29.00
TELETON F2000	£32.00
WHARFEDALE 100-1	£15.00
PHILIPS RH781	£53.00
GOODMANS MODULE 80	£74.00
TELETON TAT1	£80.00
TELETON CR55	£85.00
TELETON R8000 with speakers	£35.00

TUNERS p.p. 75p

ARMSTRONG M8	£7.75
ARMSTRONG 523	£42.00
ARMSTRONG 524	£33.00
TELETON GT101	£34.00
TELETON STQ204X	£40.00
SINCLAIR Pro. 80	£21.50
RODGERS RAVENSBORNE FET2 Chassis	£48.00

Easy to find—50 yards from (B.R.)
Stoke Newington Stn.
67, 149, 247, 73, 76, 243 Buses Pass our door.

A VICEROY VA4 COMPLETE STEREO SYSTEM

For ONLY £38.50. P. & P. £1.25

ITS PERFORMANCE CAN BE COMPARED WITH EQUIPMENT COSTING £130.00.

Fully guaranteed for 12 months

WHY PAY MORE?

APOLLO 3-WAY SPEAKER SYSTEMS.
The systems are housed in handsome Slim-Line Cabinets of Modern Design, finished in Polished Teak with Padded Front Panel covered in I.C.I. Vynair Grille.

The **APOLLO 3-WAY SPEAKERS SYSTEMS** are designed and built on the Infinite Baffle Principle and are completely Airtight and fully padded to damp out any Panel Resonance. Polished on all sides they can be used either vertically or horizontally and are ideal for Shelf or Wall Mounting.

Below are just a few from the **APOLLO** comprehensive range starting with:

APOLLO-15 3-WAY SPEAKER SYSTEM.
Impedance 8 ohms. Power Handling 15 watts. RMS (30 watts peak). Frequency Range: 35 to 18,000Hz. Colour: Teak. Size 21 + 15 + 7 1/2 in.
PRICE £18.50 each (p. & p. £1.00).

THE APOLLO-10 3-WAY SPEAKER SYSTEM employs a specially designed 10in. Bass Unit which has a high efficiency Anisotropic Ferrite Magnet and two 4in. Treble Units and LC Crossover Network. Specification: Impedance 4-8 ohms (15-16 ohms to order). Power Handling 10 watts RMS (20 watts peak). Frequency Range 50Hz to 18,000Hz. Size: 21 + 11 1/2 + 9 1/2 in. Finish Polished Teak.

OUR PRICE £13.47 each (85p p. & p.).

APOLLO-8 3-WAY SPEAKER SYSTEM.
As above but 7 watts RMS (14 watts peak). F.R. 5 to 18,000Hz. Size 20 + 12 + 8 in. £10.12 each (50p p. & p.).

APOLLO-6 3-WAY SPEAKER SYSTEM.
As above but 5 watts RMS (10 watts peak). F.R. 75 to 18,000Hz. Size 14 1/2 + 8 + 8 in.
PRICE £6.97 each (37 1/2p p. & p.).

PICK-UP ARMS

SME 3009/S2	£26.50
SME 301/S2	£28.00
GOLDRING L75	£10.00
GOLDRING L69	£8.00
AUDIO TECHNICA AT1005	£18.25

VISIT OUR 3-STORY WAREHOUSE PACKED WITH HI-FI & STEREO EQUIPMENT. 1000's OF ITEMS ALWAYS AVAILABLE TO SELECT FROM.

FOR ALL YOUR NEEDS IN HI-FI EQUIPMENT SEND A LARGE S.A.E. or PAY A VISIT

2 SHOWROOMS DEVOTED TO DEMONSTRATING SPECIALLY SELECTED SYSTEMS

SPECIAL OFFERS

**GARRARD SP25 Mk. III
GOLDRING G800H Superb Plinth and Cover.**

SINCLAIR Project 60—Stereo 60 Pre-Amplifier and Control Unit. 2 Z30's and PZ5. 2 WHARFEDALE Unit 3. List Price £82.31. OUR PRICE £55. P. & P. £1.75.

**GARRARD SP25 Mk III
GOLDRING G800 H**

**Plinth and Cover complete
OUR PRICE £19.00. P. & P. 75p.**

**ARMSTRONG 526
GARRARD AP76
SHURE M55E**

**Plinth & Cover complete
STE-MA 400 speakers
OUR PRICE £148.00. P. & P. £1.25**

CARTRIDGES

GOLDRING G850	£4.20
GOLDRING G800H	£5.00
GOLDRING G800	£7.00
GOLDRING G800E	£11.00
GOLDRING G800/SE	£16.00
SHURE M30	£3.00
SHURE M44/57/C	£7.25
SHURE M55E	£9.25
SHURE M75E	£15.00
SHURE V15 type 2	£39.75
SHURE 44E	£8.50
SHURE 31E	£9.00
SHURE 32E	£8.25
SONATONE 9TAHCD	£1.75
AUDIO TECHNICA AT66	£4.50

SCOOP BUY

MC1-5 HIGH FIDELITY STEREO MOVING MAGNET CARTRIDGE. PRICE: £6.00.

TURNTABLES

GARRARD SP25/Mk. III	£10.97
GARRARD 2025TC with Sonotone 9TAHC Cartridge	£8.75
GARRARD A70 Mk. II	£10.97
GARRARD SL65B	£12.75
GARRARD AP76	£18.75
GARRARD SL72B	£25
GARRARD SL75B	£27.75
GARRARD 401	£27.50
GARRARD SL95B	£34
GOLDRING GL75P	£35
GOLDRING GL75	£28.50
GOLDRING GL59	£21
THORENS TD125	£62
THORENS TD150AB/2	£35
PIONEER PL11AC complete	£49
Dual 1219	£34
DUAL 1208	£34
PHILIPS 202A	£54

OPEN

Monday - Wednesday 9.30 a.m.-7 p.m.
Half day Thursday until 1 p.m.
Late night Friday until 8 p.m.
SATURDAY 9.30 a.m.-6 p.m.

SEND CHEQUES, P.O., MONEY ORDER, etc. to—

AUDIO SUPPLIES

PW. 50 STAMFORD HILL, LONDON, N.16.

Telephone: 01-806 3611

PERSONAL CALLERS PLEASE NOTE: Cheques are only accepted when accompanied by a Bank Cheque Card (not Barclay Card).

All prices subject to change without notice

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it’s as fascinating as a hobby

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of “OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO”. This brand new booklet—just out—tells you all about TECHNATRON and B.I.E.T.’s full range of courses.

FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF



POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF
Please send books and full information — FREE and without obligation.




NAME..... AGE.....

ADDRESS.....

OCCUPATION.....

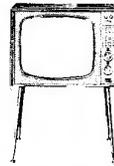BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



EX RENTAL TV's

19" — £29.95

23" — £39.95

All Channels 405/625
2 Years Guarantee.
Free List by return.

17" Slim line TV's £11.95, 19" Slim line TV's £15.95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1.95. Daily demonstrations to personal shoppers.

TEAK HI-FI STEREO CABINETS £14.95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1.00.

TRANSISTOR GANG CONDENSERS 30p. Miniature AM precision Tape Motors £1.95 famous German manufacturer. 200/250V. Post 20p.

Transistor Radio Cases: 25p each.
Size 9½" x 6½" x 3½". P. & P. 15p.
SPEAKERS 50p 2½" 8Ω BRAND NEW. P. & P. 5p.

TV TUBES REBUILT GUARANTEED 2 YEARS

TRANSISTORS Post Free

AC 126 AF 179 OC 81
AC 128 OC 44 OC 81D
AF 114 OC 45
AF 117 OC 71 15p each

POTENTIOMETERS 23p each

Double & Switched	500 KΩ/500 KΩ	3½" shaft
Double & Switched	500 KΩ/100 KΩ	2" shaft
Double & Switched	1 MEG/100 KΩ	1½" shaft

Post. & Pack. 5p.—4 for 10p

KNOBS 100,000 to clear (Brand New)

100 assorted Radio & T.V. knobs 50p.
Postage 10p. (If you require sets 2 to 6 just ask)

14"—£3.95, 17" & 19"—£5.95,

21" & 23"—£6.45.

Exchanged Bowls. Carr. 83p.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3

Stamp for Free List

FANTASTIC BARGAIN OFFER!

TRANSEUROPEAN

Transistorised Stereophonic High Fidelity AM/FM Tuner Amplifier System.



This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, Medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in. matching elliptical speakers. A complete Hi-Fi Stere Radiogram at less than half normal price.

Easily fitted no technical knowledge necessary.

SPECIAL OFFER £44

P. & P. 88p

Credit Terms available. First monthly payment of £5.83 followed by 9 monthly payments of £4.95. Total Credit Sale Price £49.50. Send £5.83 today.

FABULOUS VALUE


Hi-Fi stereo at a new low. 4 speed BSR autochanger with cue and pause control plus solid state amplifier, 20 watt total output. Frequency response 20-20,000 Hz. Two elliptical speakers in book shelf enclosures—100% complete.

ONLY £4.93 CREDIT SALE TERMS: Send £4.93 (being the first of TEN monthly payments of £4.05 plus 88p Carriage and Packing). To be followed by NINE monthly payments of £4.05 (Total Credit Sale Price £40.50)
DOWN (Total Credit Sale Price £40.50)
EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.

CALLERS WELCOME
PLEASE SEND ME FREE DETAILS OF YOUR RANGE
Name
Address P871


FREE leaflets
LEWIS radio 100, Chase Side London N.14
Tel: 01-886 3733/9666

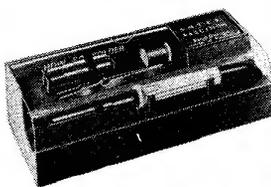cut out this coupon and answer your soldering problems



**SK1
SOLDERING
KIT**
In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted $\frac{3}{16}$ " bit. Spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder".

Send me
kit(s) **£2.75**

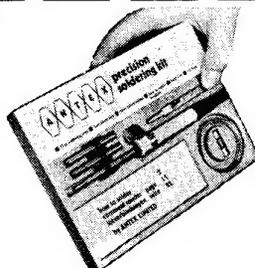

**SK2
SOLDERING
KIT**
In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with $\frac{3}{16}$ " bit, 2 spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".


Send me
kit(s) **£2.40**



Model CN 240/2
- 15 watts
- 240 volts

Fitted with nickel plated $\frac{3}{32}$ " bit and packed in handy transparent box.


Send me
pack(s) **£1.70**

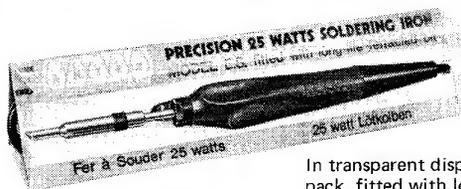

**ES240 D 25 watt
soldering iron**

In transparent display pack, fitted with long life iron-coated bit $\frac{1}{8}$ " diam. Interchangeable spare bits $\frac{3}{32}$ ", $\frac{1}{16}$ ", $\frac{1}{4}$ " (extra) available. Improved design to ensure strong and reliable high speed iron. Heats up in 2 minutes.

Send me
pack(s) **£1.83**

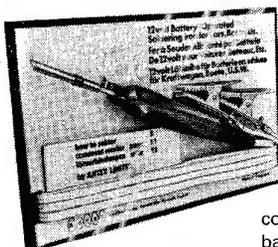

**M.E.S.
Battery-operated
12 volt
soldering iron**

Complete with 15 ft (4.50m) lead, 2 heavy gauge clips for instant

connection to car battery and a guide 'How to Solder'. Packed in strong plastic wallet.

Send me
kit(s) **£1.95**



from electrical and radio shops or by Free Post (No stamp required) from ANTEX Ltd. FREE POST. PLYMOUTH, PL1 1BR Tel: (0752) 67377/8

● Please send the ANTEX colour catalogue.

● Please send the following:

I enclose cheque / P.O. / Cash (Giro No. 2581001)

NAME

ADDRESS

PW9

MAIL ORDER DEPARTMENT
No. 11 Mayes Rd., London, N22 6TL

RADIO LTD

BARGAIN COMPUTER BUMPER BOARDS



Many Resistors, Condensers, Diodes and Transistors (minimum of 4 resistors on each board).
5 BOARDS FOR 120p. Post Free.



BLACK TERMINALS

Length as indicated 1 inch
10p per pair P. & P. 3p.

BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator, 2 1/2" x 2 1/2" x 3 1/2" approx. 4V £1.50, 6V £1.50, 9V £1.50, 7.2V complete with cable and plug for Philips Cassette. £2 plus 3p P. & P. each.




SEND S.A.E. FOR GREAT BARGAINS IN MICROPHONES, AMPS, DECKS, COMPLETE DISCOTHEQUE CONSOLS, SPEAKERS AND MANY OTHER ITEMS

LIGHT DIMMER


The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from off to full brightness. Power—up to 300 watts interference suppressed.

£2.75 P. & P. 3p

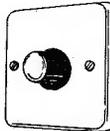

SOLID STATE BLOCK MODULES

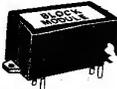Phono pre-amp E1311 input 100k; gain 28dB max out 3 volt; max input 50mV. Tape pre-amp as above E1313. Power amp E1314 input 1,000 ohms gain 20dB 300mW. Organ tone osc E1315 tone freq. 200-1k, Hz output 80mW. All above modules 9 volt. Dual flasher E1318 flash time 1-4 secs power 6 volt. Lamp 6v 150mA. All at £1.25 P. & P. 10p



D.P.D.T. SLIDE SWITCH



SIZE 1 1/2 ins long & wide each 13p 3p Postage

Transformer Scoop

Primary 220, 250 v. fused. Secondary 220 v. at 50mA, 6.3v. at 1 amp. Overall size 2 1/2" x 2" x 2 1/2" high. 63p P. & P. 15p.



COMPONENT CENTRE

8 x 6 Printed circuit board	10p each
By100 Type rectifier 800 Piv 750 mA	16p
4 Pin transistor holders	3p
21 8 ohm speaker	38p
U2 Battery holders	5p
100HM W/W Pots	13p
OC81 Heat clips (double)	3p
Page rev counters	25p
1.500mF 150v Dc 4" x 2" dia approx	40p
Flex connector 2amp approx non-reversible	5p
Ideal for loudspeaker connections	8p
21 80 ohm Speaker	35p

Please include Post & Packing
Send S.A.E. for return of post quote of your electronic project.

CHROMOSOMIC SOUND OPERATED LIGHT DISPLAY


This compact unit (size 8 1/2" x 5 1/2" x 3" high) is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour light display (500 watts light output each colour). Send S.A.E. for further details or call in at any branch for demonstration. £18-50 P. & P. 33p



100 WATT

HIGH POWER AMPLIFIER

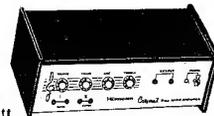- In excess of 100 watt peak output
- Open and short circuit proof
- Sensitivity 10mV for full output
- Frequency Response 10-25,000Hz
- Safe with all loudspeaker systems 4 to 16 ohms
- Silicon transistors used throughout
- F.E.T. Front end



Send S.A.E. for further details.
▲ £42.00 if purchased with light unit above £40.00
Post and Insurance £1.00.

GUARANTEED 12 MONTHS

DWELL TIME UNIT

These small units contain the following components: 700 ohm DPDT relay with base, 1µF 220v. paper, 0.01µF 400v. paper, 50µF 35v. electrolytic, 3 diodes OC200 transistor, a 2N2926 type transistor unmarked, a skeleton pre-set pot, 4 pin din plug & skt., 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many timing devices. 43p P. & P. 8p




BRANCHES 11e 40 MAYES RD LONDON N22-888-3206
13 SOUTH MALL EDMONTON GREEN LONDON N9 803 1685

PRINTED CIRCUIT KIT

BUILD 50 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet Printed Circuits for Amateurs (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 50 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

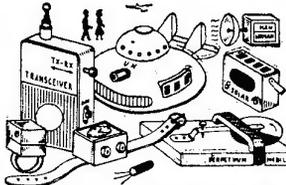

EXPERIMENTERS PRINTED CIRCUIT KIT

50p
Postage & Pack. 10p. (U.K.)
Commonwealth:
SURFACE MAIL 15p
AIR MAIL 50p
Australia, New Zealand,
South Africa, Canada

- (1) Crystal Set with biased Detector.
- (2) Crystal Set with voltage-quadrupler detector.
- (3) Crystal Set with Dynamic Loudspeaker.
- (4) Crystal Tuner with Audio Amplifier.
- (5) arrier Power Conversion Receiver.
- (6) Split-Load Neutralised Double Reflex.
- (7) Matchbox or Photo-cell Radio.
- (8) "TRI-FLEXON" Triple Reflex with Self-adjusting regeneration (Patent Pending).
- (9) Solar Battery Loud-speaker Radio.
- (10) The smallest 3 designs yet offered to the Home Constructor anywhere in the World.
- (11) 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere.
- (12) Postage Stamp Radio. Size only 1-62" x .95" x .26".
- (13) Wristwatch Radio 1-15" x .80" x .55".
- (14) Ring Radio .70" x .70" x .55".
- (15) Bacteria-powered Radio. Runs on sugar or bread.
- (16) Radio Control Tone Receiver.
- (17) Transistor P/P Amplifier.
- (18) Intercom. (17) 1-valve Amplifier.
- (19) Reliable Burglar Alarm.
- (20) Light-Seeking Animal. (21) Perpetual Motion Machine.
- (22) Metal Detector.
- (23) Transistor Tester.
- (24) Human Body Radiation Detector.
- (25) Man/Woman Discriminator.
- (26) Signal Injector.
- (27) Pocket Transceiver (Licence required).
- (28) Constant Volume Intercom.
- (29) Remote Control of Models by Induction.
- (30) Inductive-Loop Transmitter.
- (31) Pocket Triple Reflex Radio.
- (32) Wristwatch Transmitter/Wireless Microphone.
- (33) Alarm Alarm.
- (34) Ultrasonic Switch/Alarm.
- (35) Stereo Preamplifier.
- (36) Quality Stereo Push-Pull Amplifier.
- (37) Light-Beam Telephone "Photophone".
- (38) Light-Beam Transmitter.
- (39) Silent TV Sound Adaptor.
- (40) Ultrasonic Transmitter.
- (41) Thyristor Drill Speed Controller. . . plus 10 Photo-electric Circuits, Alarms, Modulators, Stabilisers. . .

YORK ELECTRICS, Mail Order Dept.
335 Battersea Park Road, London, S.W.11


Send a S.A.E. for full details, and a brief description of all Kits and Projects.

BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

- Maximum Power 15 watts
- Bass Resonance 45 c.p.s.
- Flux Density 12,000 gauss
- Voice Coil impedance 3 or 8 or 15 ohm models
- Useful response 45-13,000 c.p.s.
- Nett weight 5 lbs.
- GUITAR MODEL "GROUP 25" £7
- 25 watt rating
- Latest catalogue 5p with enclosure plans.

£7

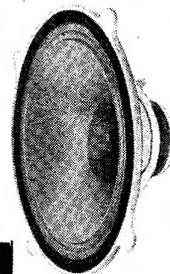

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

When in LUTON, BEDS, you must visit the . . . SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.
Closed all day Wednesday.

SURPLECTRONICS
216 LEAGRAVE ROAD, LUTON, BEDS

**BRAND NEW
GUARANTEED**

SEMICONDUCTORS & COMPONENTS

**RETURN OF POST
SERVICE**

SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA). IN U.K.

TRANSISTORS

2G301	20p	2N3404	321p	40310	46p	BC212L	121p	BSX28	321p	NKT281	271p
2G302	20p	2N3405	45p	40311	35p	BCY30	271p	BSX60	621p	NKT401	871p
2G303	20p	2N3414	221p	40312	471p	BCY31	30p	BSX61	821p	NKT402	80p
2G306	45p	2N3415	221p	40314	50p	BCY32	30p	BSX62	30p	NKT403	75p
2G308	30p	2N3416	371p	40320	471p	BCY33	25p	BSX77	271p	NKT404	621p
2G309	30p	2N3417	371p	40323	321p	BCY34	30p	BSX78	271p	NKT405	75p
2G371	15p	2N3570	21-25	40324	471p	BCY38	40p	BSY10	271p	NKT406	621p
2G374	15p	2N3572	971p	40326	371p	BCY39	60p	BSY11	271p	NKT451	621p
2G381	20p	2N3605	271p	40329	30p	BCY40	30p	BSY22	15p	NKT452	621p
2N404	221p	2N3606	271p	40344	271p	BCY42	15p	BSY25	15p	NKT453	471p
2N696	20p	2N3607	221p	40347	571p	BCY43	15p	BSY26	171p	NKT603F	321p
2N697	20p	2N3702	121p	40348	521p	BCY44	521p	BSY27	171p	NKT613F	321p
2N698	25p	2N3703	121p	40350	421p	BCY58	221p	BSY28	171p	NKT674F	30p
2N706	121p	2N3704	171p	40361	471p	BCY59	221p	BSY29	171p	NKT677E	30p
2N705A	121p	2N3705	15p	40362	571p	BCY60	971p	BSY32	25p	NKT713	25p
2N708	15p	2N3706	121p	40370	321p	BCY70	20p	BSY36	25p	NKT781	30p
2N709	621p	2N3707	15p	40406	571p	BCY71	421p	BSY37	25p	NKT10419	30p
2N716	25p	2N3708	0p	40407	40p	BCY72	171p	BSY38	25p	NKT10439	30p
2N726	20p	2N3709	10p	40408	521p	BCZ10	271p	BSY39	221p		
2N727	30p	2N3710	11p	40410	621p	BCZ11	421p	BSY40	321p	NKT10519	
2N914	171p	2N3711	12p	40467A	571p	BD116	11-12p	BSY61	321p		
2N916	171p	2N3715	22-22p	40468A	35p	BD121	65p	BSY62	321p	NKT20329	
2N918	15p	2N3716	22-22p	40469	571p	BD124	321p	BSY64	371p		
2N929	221p	2N3791	221p	AC107	30p	BD124	321p	BSY64	371p	NKT20339	
2N930	271p	2N3819	35p	AC126	20p	BD131	75p	BSY66	80p		
2N1090	221p	2N3823	971p	AC127	25p	BD132	85p	BSY78	471p	NKT80111	
2N1091	221p	2N3854	271p	AC128	20p	BDY10	11-37p	BSY79	45p		
2N1131	25p	2N3854	271p	AC129	25p	BDY11	11-37p	BSY80	45p	NKT80112	
2N1192	25p	2N3855	271p	AC176	25p	BDY17	11-37p	BSY90	571p		
2N1202	171p	2N3855A	30p	AC187	621p	BDY18	11-37p	BSY95A	121p	NKT80113	
2N1303	171p	2N3856	30p	AC188	371p	BDY19	11-37p	BSW41	421p		
2N1304	221p	2N3856A	35p	AD127	271p	BDY20	11-37p	BEW70	271p	NKT80211	
2N1305	25p	2N3856A	35p	ACV11	25p	BDY38	20p	C111	25p		
2N1306	25p	2N3858A	30p	ACV19	25p	BDY60	11-25	C424	271p	NKT80212	
2N1307	25p	2N3859	271p	ACV20	25p	BDY61	11-25	C425	55p		
2N1308	30p	2N3859A	321p	ACV21	25p	BDY62	11-25	C426	55p	NKT80213	
2N1509	30p	2N3904	271p	AF117	75p	BF125	35p	BF422	921p		
2N1507	171p	2N3866	11-50	ACV28	20p	BF117	471p	C744	30p	NKT80214	
2N1613	25p	2N3877	40p	ACV40	20p	BF163	371p	D16P1	371p		
2N1631	35p	2N3877A	40p	ACV41	25p	BF167	371p	D16P2	371p	NKT80215	
2N1632	30p	2N3900	971p	AD144	40p	BF173	321p	D16P3	371p		
2N1633	271p	2N3904	40p	AD147	50p	BF175	30p	D16P4	371p	NKT80216	
2N1639	271p	2N3901	971p	AD149	571p	BF178	30p	GET102	30p		
2N1678	11-00	2N3903	35p	AD160	621p	BF179	30p	GET113	20p	OC20	75p
2N1711	25p	2N3904	35p	AD161	371p	BF180	35p	GET114	20p	OC22	50p
2N1781	35p	2N3917	371p	AF112	521p	BF181	321p	GET115	20p	OC23	50p
2N1893	371p	2N3906	371p	AF106	521p	BF184	221p	GET119	20p	OC24	60p
2N2147	621p	2N4056	171p	AF114	25p	BF185	421p	GET120	521p	OC25	50p
2N2148	571p	2N4059	10p	AF115	25p	BF194	171p	GET873	121p	OC26	25p
2N2160	571p	2N4060	121p	AF116	25p	BF195	20p	GET880	30p	OC28	821p
2N2193	45p	2N4061	121p	AF117	25p	BF196	421p	GET881	20p	OC29	821p
2N2193A	45p	2N4093	121p	AF118	621p	BF197	421p	GET889	221p	OC85	50p
2N2194A	30p	2N4244	471p	AF119	20p	BF198	421p	GET890	221p	OC86	621p
2N2217	271p	2N4286	171p	AF124	221p	BF200	521p	GET896	221p	OC41	221p
2N2218	321p	2N4286	171p	AF126	20p	BF224	20p	GET897	221p	OC42	25p
2N2219	321p	2N4287	171p	AF129	20p	BF235	30p	GET898	221p	OC44	25p
2N2220	25p	2N4288	171p	AF127	271p	BF237	221p	MJ400	11-07p	OC45	181p
2N2221	25p	2N4289	171p	AF139	371p	BF238	221p	MJ420	11-12p	OC46	16p
2N2222	30p	2N4290	171p	AF178	421p	BF244	321p	MJ421	11-12p	OC70	10p
2N2270	471p	2N4291	171p	AF179	75p	BF261	471p	MJ430	11-12p	OC71	121p
2N2297	171p	2N4292	171p	AF180	521p	BFX12	221p	MJ440	95p	OC72	121p
2N2368	171p	2N4303	471p	AF181	221p	BFX13	221p	MJ480	971p	OC74	821p
2N2369	171p	2N6027	621p	AF239	471p	BFX29	30p	MJ481	11-25	OC76	821p
2N2369A	171p	2N6028	571p	AF279	471p	BFX30	30p	MJ482	11-25	OC77	821p
2N2440	421p	2N6175	421p	AF280	421p	BFX42	371p	NJ1481	11-37p	OC81	20p
2N2443	271p	2N5030	421p	AF211	321p	BFX44	371p	MJ1800	22-17p	OC81	20p
2N2484	321p	2N5172	121p	ASX26	25p	BFX68	671p	MEJ340	621p	OC81D	20p
2N2539	221p	2N5174	521p	ASX27	371p	BFX84	25p	MEJ520	971p	OC83	25p
2N2540	221p	2N5175	521p	ASX28	271p	BFX85	25p	MEJ521	971p	OC84	25p
2N2613	35p	2N5176	45p	ASX29	271p	BFX86	25p	MPP102	421p	OC139	321p
2N2614	30p	2N5282A	30p	ASX36	25p	BFX87	271p	MPP103	371p	OC140	321p
2N2646	521p	2N5245	45p	ASX50	25p	BFX88	25p	MPP104	371p	OC170	30p
2N2696	821p	2N5246	421p	ASX51	321p	BFX89	25p	MPP105	371p	OC171	30p
2N2712	25p	2N5249	671p	ASX54	25p	BFX93A	621p	MPS838	321p	OC200	40p
2N2712	25p	2N5265	23-25	ASX85	321p	BFY10	321p	NKT0013	471p	OC201	60p
2N2713	271p	2N5266	22-75	AU103	11-25	BFY11	421p	NKT124	421p	OC202	75p
2N2714	30p	2N5267	22-22p	ASZ21	421p	BFY17	221p	NKT125	271p	OC203	421p
2N2825	621p	2N5268	371p	BC107	421p	BFY18	321p	NKT126	271p	OC204	421p
2N2904	30p	2N5306	40p	BC108	121p	BFY19	321p	NKT128	271p	OC205	90p
2N2904A	321p	2N5307	371p	BC109	121p	BFY20	421p	NKT135	271p	OC207	75p
2N2906	371p	2N5308	371p	BC113	30p	BFY21	421p	NKT137	321p	OCPT1	421p
2N2906A	40p	2N5309	621p	BC115	271p	BFY24	45p	NKT130	30p	ORP12	621p
2N2906	25p	2N5310	421p	BC116A	271p	BFY25	25p	NKT211	30p	ORP61	50p
2N2906A	271p	2N5354	271p	BC118	35p	BFY26	20p	NKT212	30p	P346A	221p
2N2907	30p	2N5355	271p	BC121	20p	BFY29	50p	NKT213	30p	T1834	40p
2N2923	15p	2N5356	321p	BC122	20p	BFY30	50p	NKT214	221p	T1843	40p
2N2924	15p	2N5357	471p	BC125	35p	BFY41	50p	NKT215	11-00	T1844	121p
2N2925	15p	2N5366	321p	BC126	35p	BFY43	821p	NKT216	371p	T1845	121p
2N2926	15p	2N5367	571p	BC140	371p	BFY50	221p	NKT217	421p	T1846	121p
Green	14p	2N5457	371p	BC147	171p	BFY51	221p	NKT219	30p	T1847	121p
Yellow	121p	2N505	75p	BC148	121p	BFY52	221p	NKT223	271p	T1848	121p
Orange	121p	2N5200	22-00	BC149	171p	BFY53	171p	NKT224	25p	T1849	121p
2N3011	30p	2N5102	50p	BC152	171p	BFY56A	571p	NKT225	221p	T1850	171p
2N3014	321p	2N5103	25p	BC157	20p	BFY75	30p	NKT229	30p	T1851	121p
2N3053	25p	2N5104	25p	BC158	171p	BFY76	421p	NKT237	35p	T1852	121p
2N3054	50p	2N5101	321p	BC159	20p	BFY77	571p	NKT238	25p	T1853	221p
2N3055	50p	2N5202	85p	BC160	621p	BFY90	671p	NKT240	271p	T1850	221p
2N3133	30p	2N5803	371p	BC167	15p	BFW58	271p	NKT241	271p	T1861	25p
2N3134	30p	2N383	40p	BC168B	14p	BFW69	25p	NKT242	20p	T1862	271p
2N3135	25p	2N3128	70p	BC198C	15p	BFW60	25p	NKT243	621p	T1863	60p
2N3136	25p	2N3129	71p	BC142B	14p	BFX05	11-35	NKT414	171p	T1864	60p
2N3390	25p	2N141	721p	BC169C	15p	BFX29	21-80	NKT245	20p	T1P31A	621p
2N3391	30p	2N142	55p	BC170	121p	BFY10	11-45	NKT261	20p	T1P32A	75p
2N3391A	30p	2N143	671p	BC171	15p	BFY39	471p	NKT262	30p	T1P33A	621p

All prices in pounds and new pence

VALVES		25		30		35		40		45		50		55		60		65		70		75		80		85		90		95		100	
1A7GT	40	6B46	25	6J6	20	7C5	11-13	12R7	35	57	40	DAF91	25	EBL31	11-38	EL41	55	N75	11-00	PL504	80	UA44	40										
1C931	20-00	6BE6	30	6J7M	45	7C6	45	7C7	50	42	50	DAF96	42	EC80	33	EL42	58	N108	11-50	PL508	90	U801	11-18										
1H5	42	6BH6	45	6J7G	30	7D5	55	19A Q5	40	50B55	45	DCC90	11-00	ECC81	33	EL84	25	OA2	38	PL509	11-45	UAB C80	35										
IN5GT	48	6BJ6	45	6J7GT	45	7H7	55	20D1	50	50C5	40	DF33	48	ECC82	30	EL95	35	OC8	38	PL502	83	UAF42	55										
IR5	35	6BQ7A	40	6K6GT	55	7R7	70	30P2	70	50C D6G	11-05	DF70	45	ECC83	30	ELL80	11-00	OZ4	40	FX4	23-00	UBC41	50										
3Q4	40	6BZ7	35	6K7M	35	787	29-25	30L1	11-10	50L6GT	50	DF91	25	ECC84	30	EM34	30	PC86	60	FX25	23-00	UCR31	45										
384	45	6BR8	65	6K7G	20	7Y4	80	20P4	11-10	75	50	DF92	20	ECC85	25	EM80	40	PC88	60	FX33	63	UBF80	40										
3A4	35	6C8	25	6L6G	45	10F18	45	10F18	45	25Z5GT	55	801	50	DK92	30	ECH83	43	EZ40	45	PC822	35	Y801	50	UCH81	35								
3Q4	40	6CD6G	11-20	6L18	45	10LD11	60	25Z6	65	807	55	807	55	DK96	42	ECL80	40	EZ41	48	PCF84	60	R2	60	UCL82	38								
3Q5	45	6CH6	55	6Q7G	30	10P13	65	30C13	33	318USA	23-75	DL66	11-25	ECL82	35	EZ80	25	PCF86	60	R19	40	UCL83	60										
3V4	45	6D6	25	6S7A7M	43	11E3	24-00	30C15	30	30C17	85	954	60	DL93	35	ECL83	65	EZ81	28	PCF801	50	S130	11-75	60	80								
5R4Y	60	6E5	38	6SC7M	70	12A7T	33	30C18	75	1625	40	DL94	45	ECL800	11-00	GZ30	50	PCF805	75	SP41	45	UL41	65										
3U4G	38	6F1	70	6S7M	35	12A7U7	30	30P11	75	5783	70	DL96	42	EP9	11-50	GZ32	50	PCF806	70	SP61	55	UL84	35										
5Y3GT	32	6F6G	60	6S7GT	30	12AX7	30	30P12	95	7193	20	DM70	40	EP37A	60	HN309	11-60	PC82	38	SVT380/80	UM80	23											
5Z4G	40	6F8G	35	6K7GT	30	12BA6	35	30P14	75	7475	40	DY86	33	EP39	40	KT36	11-00	PC83	58	SU25	11-00	U07	11-05										
6/30L2	75	6P11	38	6SL7GT	35	12BB6	35	30L15	85	A61	48	DY87	35	EP41	65	KT81	11-25	PC84	43	SU2150	75	U78	11-05										
6A7	75	6P13	38	6SN7GT	35	12CGT	35	30L17	85	ATP4	35	EP80C	65	EP60	25	KT66	11-70	PC85	40	T41	11-00	U79	45										
6A8G	63	6P14	65	6SQ7GT	40	12E1	21-15	30P4	11-15	ATP5	60	EAB9	20	EP80	25	KT81	11-75	PC86	45	TDD4	60	UY21	50										
6AK5	30	6P24	75	6U6G	60	12J7GT	35	30P19	80	AU2	24-00	EAF42	55	EP86	35	KT81(7C5)	PD500	11-50	TH41	11-75	UY41	45											
6AM6	32	6P25	75	6V6M	60	12K7GT	35	30P11	80	AU5	60	EB91	20	EP89	28	KT85	11-13	PEN44	11-00	U14	60	VMP4G	85										
6AQ5	35	6P32	25	6V6GT	70	6V6G	30	30P13	93	AZ1	48	EP83	50	EP91	35	KTW61	11-00	PEN45	40	U19	23-50	VP4E	11-25										
6ASTG	80	6G6	25	6X4	30	12SA7GT	40	35A5	75	CBL31	90	EB90	30	EP98	75	ML4	88	PL36	55	U26	78	VR100/30	35										
6AT6	30	6H6	23	6X6G	35	12S67	35	35L6	50	CCH35	75	EBF80	40	EP183	33	ML6	40	PL81	50	U78	60	VU111	60										
6AU6	25	6J5M	50	6X5GT	85	12SH7	30	35W4	30	CL33	11-00	EBF83	45	EP184	35	MSP4	50	PL82	45	U191	75	VU120	80										
6B4G	11-00	6J5G	20	7B6	70	12S7	30	35Z4GT	50	CY31	60	EB93	33	EP93	40	KT41	45	EP94	60	PL84	40	U191	80	VU108	23-50								
6BSG	20	6J5GT	30	7B7	45	12SK7	45	35Z5	40	DAC32	42	EBL21	60	EL34	58	MX40	63	PL500	80	U463	50	Y63	50										

Transistors		2N2918		2N2919		2N2920		2N2921		2N2922		2N2923		2N2924		2N2925		2N2926		2N2927		2N2928		2N2929		2N2930		2N2931		2N2932	
IN914	08	2N2987	18	2N2946	15	AC127	25	AF117	25	AF117	25	BF351	20	MJE2959	88	OA70	10	OA2210	40	OC58	80	OC170	25	ZTX300	15						
18113	25	2N706	10	2N2904	80	AC128	25	AS726	25	BY100	18	MJE2955	18	11-75	OA81	10	OA2224	38	OC59	65	OC171	30	ZTX304	28							
19202	23	2N1132	30	2N2926	13	ACY90	55	BC109	13	CR81-40	48	MJE2055	93	OA85	13	OA2241	23	OC71	15	OC200	40	ZTX500	20								
2Q302	23	2N1305	25	2N2055	75	ACY39	55	BC109	13	DD003	18	NK7212	27	OA91	08	OA2342	23	OC72	25	OC71	98	ZTX503	20								
2Q371	23	2N1247	75	2N3702	13	AD140	50	BC109	13	GET102	30	NK7214	15	OA211	35	OA2346	23	OC81	25	ORP12	50	ZTX531	30								
2N404	23	2N3169	65	2N3819	35	AD149	50	BC169C	18	GF7882	25	NKT223	33	OA2900	55	OC35	60	OC81D	20	ZS170	10										
						AAZ126	20	AD161	38	BF898	28	GJ7M	38	NKT251	24	OA2201	50	OC44	18	OC82	25	ZS271	18								
						AF115	25	AF117	25	BFY50	20	KS100A	23	NKT713	25	OA2207	48	OC45	15	OC82D	15	ZTX107	15								
						AF117	25	AF117	25	BFY51	20	MJE2959	88	OA70	10	OA2210	40	OC57	60	OC74	60	ZTX108	15								
						AS726	25	BY100	18	MJE2955	18	MJE2955	18	11-75	OA81	10	OA2224	38	OC58	80	OC170	25	ZTX300	15							
						BC107	23	BC107	23	BY100	18	MJE2955	18	11-75	OA81	10	OA2224	38	OC59	65	OC171	30	ZTX304	28							
						ACY39	55	BC109	13	CR81-40	48	MJE2055	93	OA85	13	OA2241	23	OC71	15	OC200	40	ZTX500	20								
						AD140	50	BC109	13	DD003	18	NK7212	27	OA91	08	OA2342	23	OC72	25	OC71	98	ZTX503	20								
						35Z5	40	DAC32	42	EBL21	60	EL34	58	MX40	63	PL500	80	U463	50	Y63	50										


TRANSISTOR POSTAGE 1p EACH, OVER 10 POST FREE

Express Postage & Insurance 5p one valve plus 1p each additional valve. ORDERS over £5 Post free. 6,000 types in stock send for lists, 5p.

R.S.T

"Renowned for Service"

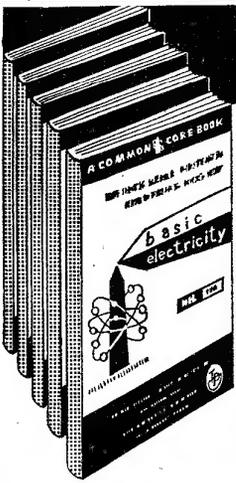BLACKWOOD HALL, WELLFIELD RD., STREATHAM, SW16 2BF
 Tel. 01-769-0199/1649. Open to callers Mon-Sat 9 a.m.—5 p.m. Closed Saturday 1.00—2.30 p.m.



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 vols.) BASIC ELECTRONICS (6 vols.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.


WHAT READERS SAY

- "HOW UNDERSTANDABLE"**
Pleased to say how understandable your books are, I now have a sound knowledge of the subject. *A.K., Hull.*
- "INVALUABLE"**
Invaluable for my training as a Technician. *W.J., Stockport.*
- "A MATHEMATICAL IDIOT"**
They have an easy approach to learning that a mathematical idiot like myself can easily understand. *K.L.Y., Ashton-u-Lyne.*

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP
 Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY £4.50** Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. **BASIC ELECTRONICS £5.40** Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.
 Tick Set required (Only one set allowed on free trial)
 BASIC ELECTRICITY **BASIC ELECTRONICS**
 Prices include Postage and Packing.
 Signature _____
 (If under 21 signature required of parent or guardian)
 NAME _____
 BLOCK LETTERS
 FULL POSTAL ADDRESS _____

POST NOW FOR THIS OFFER!!

PHILIPS PORTABLE PLAYER CABINET

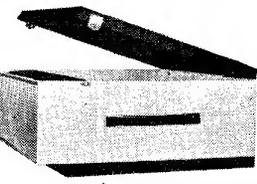

Size 18 x 15 1/2 x 7 1/2 in. Cut for B.S.R. UA12/14/15/16/25 deck. Amplifier space 14 x 5 x 3 1/2 in. Satin aluminium front grille. Really smart appearance. £4 Post 25p

BSR C.109 SUPERSLIM STEREO AND MONO CHANGER



Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL £7.75 Post 25p

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond and Mono Sapphire. SP25 MK II £15 Model 3500 Stereo and Mono Autochanger £14. Post 25p.

RECORD PLAYER PORTABLE CABINET. Space for amplifier and autochanger. Post 25p. £3.75

ACE DE-LUXE 3 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL32, E230. £4

Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £3

R.S.2 2 WATT AMPLIFIER with loudspeaker. Post 25p. £3

R.O.S. TEAKWOOD BASE. Ready out for mounting (State player make and model) £2.75

R.O.S. PLASTIC COVERS FOR ABOVE BASE. £2.75

Durable tinted plastic, attractive appearance.

EMI PICK-UP ARM with mono xtal and stylus £1.25

HI-FI PICK-UP CARTRIDGES. Diamond Stereo/Mono/TA 22-90; GP94 £2.75; GP93 £2.25; Mono GP91 £1.50; GC8 £1.25; AOS L.P. only 50p.

All standard fixing complete with stylus.

PHILIPS TRANSISTOR FM STEREO MULTIPLEX DECODER

As used in LEAK Touchline Tuner. Brand New. Pre-aligned with 9 semi conductors. 24v. D.C. at 6mA. Complete with circuit and connection details. £4 Post Size 3 1/2 x 2 in. Free

WEYRAD P50—TRANSISTOR COILS

RA2W Ferrite Aerial..	65p	Spare Cores	3p
Osc. P50/LAC	30p	Driver Trans. LPD74 ..	50p
I.F. P50/200 470 kΩs.	35p	Printed Circuit, PCA1 ..	50p
3rd I.F. P50/300	35p	J.B. Tuning Gang	65p
P51/I or P51/2	35p	Weyrad Booklet	10p
P50/3V	35p	OPTI	55p

Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 25p.

VOLUME CONTROLS

Low spindles. Metric Size 5 K. ohms to 2 meg. LOG or LIN. 1/8, 1/5, D.P. 25p. STEREO L/R S.E.P. 75p. EDGE 5K S.E.P. Transistor 25p

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 Ω to 30 K. £25p

WIRE-WOUNDS-WATT STANDARD SIZE POTS. LONG SPINDLE 10 OHMS to 100 K. £40p

VEROBOARD 0-15 MATRIX

2 1/2 x 5 in. 19p. 2 1/2 x 3 1/2 in. 16p. 3 1/2 x 5 in. 26p. EDGE CONNECTORS 4 way 25p; 24 way 58p. PINS 96 per packet 17p. FACE CUTTERS 38p.

S.R.B.P. Board 0-15 MATRIX 2 1/2 in. wide 3p per 1 in., 3 1/2 in. wide 4p per 1 in.; 5 in. size 5p per 1 in. (up to 1 7/8 in.). S.R.B.P. undrilled 1/2 in. Board 10 x 8 in. 15p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides. 6 x 4 in. 45p; 8 x 6 in. 50p; 10 x 7 in. 70p; 14 x 6 in. 90p; 16 x 6 in. 90p; 12 x 3 in. 50p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 8p; 8 x 6 in. 15p; 10 x 7 in. 17p; 12 x 8 in. 22p; 14 x 8 in. 27p; 12 x 12 in. 32p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2 p. 2-way, or 2 p. 4-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.

1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 wafer 60p, 2 wafer 90p. Extra wafers up to six 30p each.

TOGGLE SWITCHES, 9p. 14p; 6p. 18p; 4p. 25p.

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms Super Sensitive £1.75
 LOW RESISTANCE HEADPHONES 8-5 ohms .. £2.00
 DE-LUXE STEREO HEADPHONES 8 ohms .. £3.25

"THE INSTANT" 200/250 v. A.C. 20-15,000 cps. Full instructions. S.A.E. £2.35 Post 15p

BULK TAP ERASER AND RECORDING HEAD DEMAGNETISER £2.35 Post 15p

Minimum Post and Packing 15p RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass road. S.R. Stn. Selhurst. Tel. 01-684-1665

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

for Mike, Tape, P.U., Guitar, etc.
 Battery 9-12v or H.T. line 200-300v. D.C. operation. Size 1 1/2 x 1 1/2 x 2 1/2 in. Response 25 cps to 25 Kc/s. 26db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. Guaranteed. Details S.A.E. 90p Post 10p

NEW TUBULAR ELECTROLYTICS

2/850V ..	14p	100/25V ..	10p	18+16/500V ..	55p
4/850V ..	14p	250/25V ..	14p	50+50/350V ..	35p
8/450V ..	14p	500/25V ..	20p	60+100/250V ..	55p
16/450V ..	14p	8+5/450V ..	15p	32+32/250V ..	18p
32/450V ..	20p	8+18/450V ..	20p	32+32/450V ..	33p
25/25V ..	10p	16+16/450V ..	25p	32+32+32/850V ..	43p
50/50V ..	10p	32+32/350V ..	25p	100+50+50/850V ..	48p

SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 12V 15p; 2000mF 25V 35p.

CERAMIC 1pF to 0.01 mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. 1,000V-0.001, 0.0022, 0.0047, 3p; 0.01, 0.02, 12p; 0.047, 0.1, 16p.

SILVER MICA. Close tolerance 1% 2-2-500pF 5p; 500-3-200 pF 10p; 2,700-5,600pF 20p; 6,800F-0.01, mfd 30p; each.

TWIN GANG. "0-0" 208pF + 179pF. 65p; Slow motion drive 365+365 with 25+25pF. 50p 500pF. 200/250V. 55p

48 equal 13-gang SHORT WAVE. Single 25pF 55p

CHROME TELESCOPIC AERIAL. swivel base, 23in. 20p.

TUNING. Solid dielectric. 100pF. 500pF. 35p each.

TRIMMERS. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 5p; 250pF, 10p; 600pF, 10p; 1000pF, 10p; 120pF, 10p.

RECTIFIERS CONTACT COOLED wave 60mA 38p; 85mA 48p. SILICON BYZL3 30p; BY100 30p; BY127 30p.

EX-GOVERNMENT RECTIFIERS 250V, 200mA, 30p.

NEON PANEL INDICATORS 250V AG/UD Red or Amber 20p.

RESISTORS. 1 w. 1/2 w. 20p. 1p. 2 w. 5p.

HIGH STABILITY. 1 w. 2% 10 ohms to 1 meg. 10p. Ditto 5%. Preferred values 10 ohms to 10 meg. 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K, 10p each; 2 watt, 1 ohm to 8.2 ohms 10p.

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key

3 in. 88p	3 in. 88p	1 1/2 in. 22p	1 1/2 in. 22p	2 1/2 in. 22p	2 1/2 in. 22p
3 in. 88p	3 in. 88p	1 1/2 in. 22p	1 1/2 in. 22p	2 1/2 in. 22p	2 1/2 in. 22p
3 in. 88p	3 in. 88p	1 1/2 in. 22p	1 1/2 in. 22p	2 1/2 in. 22p	2 1/2 in. 22p

AM-FM/VHF TUNING GANG

Super quality small size 1 1/2 x 1 1/2 x 1 1/2 in., plus spindle 1 1/2 x 1/2 in. 365 + 365 pF with 25 + 25 pF. British made. Gearing slow motion drive. Front plastic dust cover. 3BA tapped trim. Fixing. Cast aluminium frame

50p Post Free

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 50 mA. 6-8 v. 2 amps. centre tapped ..	£1.10
250-0-250 80 mA. 6-8 v. 4 amp.	£1.40
250-0-250 100 mA. 6-8 v. 3.3 v. 1.8 or 5 v. 2.2 ..	£2.00
350-0-350 80 mA. 6-8 v. 3.5 v. 6.3 v. 1.8 or 5 v. 2.2 ..	£2.00
300-0-300 v. 120 mA. 6-3 v. 4 a. C.T. 6.3 v. 2 a.	£2.50
MINIATURE 200 v. 20 mA. 6-3 v. 1 a. 2 1/2 x 2 1/2 in.	75p
MIDGET 200 v. 45 mA. 6-3 v. 2 a. 2 1/2 x 2 1/2 in.	90p
P.P. AUTORA TRANS. 12 v. 12v. 500mA.	£1.50
MINI-MAINS 20v. 100mA. 1 1/2 x 1 1/2 x 1 1/2 in.	50p
HEATER TRANS. 60v. 3 a.	60p

Ditto tapped sec. 1.4 v. 2.5, 4, 6, 8, 3 v. 1 1/2 amp. 50p

GENERAL PURPOSE 0-15 VOLTA. Tapped Outputs at 2 amp. 5, 4, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2.00

1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2.00

2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.00

3 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.00

Input/Output 150w. £2.00; 500w. 25; 1000w. 12.

CHARGE TRANSFORMERS. Input 200/250v. for 6 or 12v. 1 1/2 amp. £1.20; 2 amp. £1.50; 4 amp. £2.00.

FULL WAVE BRIDGE CHARGER TRANSFORMERS: 6 or 12 v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.

All transformers Postage 25p extra.

E.M.I. 1 1/2 x 8 in. LOUSPEAKERS

With fared tweeter cone and ceramic magnet. 10 watt. £2.25

Bass res. 45-60 cps. Post 15p

Size 3 or 8 or 15 ohm. Post 15p

Also with twin tweeters and crossover, 10 watt. Post 15p

Size 3 or 8 or 15 ohm. Post 15p

(As illustrated)

Recommended Teak Cabinet Size 16 x 10 x 8 in. Post 25p £5

10W MINI-MODULE LOUSPEAKER KIT

Post 25p

Triple speaker system combining on ready cut baffle. 1/2 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 100-15,000 cps. Full instructions for 3 or 15 ohm.

TEAK VENEERED BOOKSHELF ENCLOSURE. 18 1/2 x 10 1/2 x 6 in. Modern Design, dark grey Tegan covered baffle £5 Post 25p

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in. MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free

Module Kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch £7	12 inch £9	15 inch £19
25 watt 3 or 8 or 15 ohm	35 watt 3 or 8 or 15 ohm	50 watt 5 or 10 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front for 12in. Loudspeaker £9. Post 25p

For 13 x 8in. Loudspeaker £5. Post 25p

For 10 x 6in. Loudspeaker £4. Post 25p

LOUSPEAKER CABINET WADDING 13in. wide, 15p 1/2

THIS ELAC CONE TWEETER IS OF THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF PERFORMANCE THAN MORE EXPENSIVE UNITS.

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 15,000 cps. Size 8 1/2 x 3 1/2 x 2 1/2 in. deep. Rating 10 watt, 3 ohm or 15 ohm models. £1.90 Post 10p

TWO-WAY XOVER NETWORK 3000 c/s.

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5 1/2 in. x 4 in. with control knob, tweeter and woofer leads and input terminals. Suitable for 3 to 8 ohm imp. £1.90 Post 10p

GOODMANS HEAVY DUTY 10in. WOOFER 15 OHM

10w. Large ceramic magnet. 30-12,000 cps. Ideal F.A. Systems, Columns, Hi-Fi Enclosures etc. £4

Horn Tweeters 2-18k/4, 10W 8 ohm or 15 ohm £1.50

De Luxe Horn Tweeters 2-18 Kc/s, 15 W, 8 ohm £3.

Two-Way 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p.

SPECIAL OFFER: 80 ohm, 2 1/2 in. dia.; 35 ohm, 3 in. dia. 25 ohm, 3 in. dia.; 15 ohm, 3 1/2 in. dia. £1 EACH

15 ohm 3 1/2 in. dia.; 7 x 4 in.; 8 x 5 in. TYPE 3 ohm, 2 1/2 in. dia.; 5 x 3 in. 7 x 4 in. LOUSPEAKERS P.M. 3 OHMS. 9 1/2 in. £1.10; 8 x 5 in. £1.25; 8 x 2 1/2 in. 90p; 8 in. £1.75; 10 x 6 in. £1.90.

6in. WOOFER 5 watt max. 20-10,000 cps. 3 or 15 ohm £1.90.

EM-LAC 8 in. De Luxe Ceramic 8 ohm or 15 ohm £2.60.

RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8 in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £1.95 each. Post 15p.

OUTPUT TRANS. EL84 etc. 25p. MIKE TRANS. 50-1 25p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

GOODMANS OUTPUT TRANSFORMER 5 watt push-pull for valves EL84 etc. 3, 8 and 15 ohms 85p. Post 25p.

100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250v. 50p. Post 15p

Treble and Bass Controls Details: S.A.E. £36 Post Free

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES

ILLUSTRATED EAGLE CATALOGUE 20p. Post Free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £10

BARGAIN FM TUNER as above less cabinet £7.50

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTPUT BOXES. SURFACE OR FLUSH 25p.

BALANCED TWIN FEEDERS 5p. 30 ohms or 300 ohms.

FACE SOCKET 5p. open-circuit 14p. closed circuit 23p.

Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p.

JACK PLUGS 5p. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 15p; 5-pin 25p. DIN PLUGS 4-pin 15p; 5-pin 25p.

VALVE HOLDERS, 5p; CERAMIC 8p; CANS 5p.


E.M.I. TAPE MOTORS 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.37 x 0.75in. Size 8 1/2 x 2 1/2 x 2 1/2 in. (Illustrated). Post 15p. £1.25

BALFOUR GRAM MOTORS 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 1 x 3/32. Size 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p. 85p

DENSHI BOARD KITS

EXPERIMENTAL AND EDUCATIONAL ELECTRONIC CIRCUIT SYSTEMS

The **DENSHI BOARD** system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all! Basically the system comprises of a slotted circuit board into which plug-in components and bridge pieces are set to produce up to 30 different circuits. The components are encapsulated in transparent plastic blocks bearing the appropriate circuit symbol and value. Thus enabling even the complete novice to visually grasp the fundamentals of circuitry after only a few moments study.

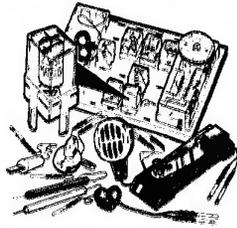

DENSHI BOARD KITS comes complete with an 80 page manual of circuits and data. Manuals are available separate at 23p. Post 3p refundable if you purchase kit.

LASKY'S PRICE £3.35 Post 13p

DENSHI BOARD KIT SR 1A

Comprises: Base board, tuner block, 4 resistors, choke coil, transformer, 2 8A transistor for RF, 2 diodes, 3 capacitors, battery block, morse key, antenna, lead, crystal earphones, various bridge and connecting pieces. This kit permits the building of 16 basic circuits.

DENSHI KIT SR 2A as **SR 1A** with these additional parts: 25B transistor for AF, 2 resistors, capacitor, crystal microphone, test probes, electrode, additional connecting pieces, 9V battery. This kit permits the building of 30 circuits.

LASKY'S PRICE £5.25 Post 13p

BSR McDONALD MP60

High precision low-mass counterbalanced pick-up arm heavily balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.

LASKY'S PRICE £12.50 Post 35p



BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

MODEL	A	B	C	D	E
610	£15.45	£18.75	£22.50	£24.50	£28.50
510	£13.45	£16.95	£20.75	£22.00	£26.00
310	£9.95	£13.45	£17.25	£21.00	£23.50
MP60	£12.50	£15.75	£19.50	£21.50	£25.50

GARRARD UNITS AND PACKAGES

GARRARD SL 55B

Four speed autochanger
LASKY'S PRICE £10.50 Post 35p



Garrard SP25 Mk. III ... £11.50
Garrard SP25, Mk. III wired ... £12.00
Garrard SP25 Mk. III with 9TA cart. ... £13.95

Garrard SL40B ... £9.95
Garrard AP76 without cart. ... £20.95
Garrard 3000 with 9TA cart. ... £10.50
Garrard 2025TC with 9TA cart. ... £9.85

GARRARD PACKAGES

Garrard AP76 with AD76K cart. and Lasky's plinth and cover ... £35
Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover ... £40
Garrard SP25 Mk. III, AD76K cart. and Lasky's plinth and cover ... £20
Garrard SP25 Mk. III, Micro M2100 e cart. and Lasky's plinth and cover ... £25


LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Singles	5	10	20
C-60	41p	£1.82	£3.41	£6.55
C-90	63p	£3.04	£5.78	£10.89
C-120	96p	£4.13	£7.43	£13.41

Post Each 5p. 5-20p. 10-25 20-50p.

SONY 8FC 59W SCOOP

DIGITAL AM/FM CLOCK RADIO

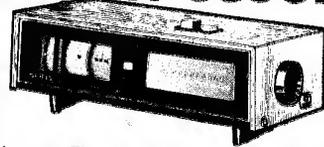


Digital Alarm Clock Radio. The digital clock shows you the time minute by minute with matchless accuracy and once set the Digimatic will wake you up at the same time every morning without having to be re-set. The radio section features Sony's unique sleep button, you fall gently to sleep lulled by the sweet tone of the radio, which switches itself off at a predetermined time. Available in either black, white or red (8FC-59W). Frequency range 530-1,605KHz (AM); 87-108MHz (FM). Uses 8 transistors and 8 semi-conductors, built-in ferrite aerial and 3 1/2in loudspeaker. Power requirements: 230V AC 50Hz. Dimensions: 12 1/2in x 3 1/2in x 5 1/2in.

LIST PRICE £30.00

LASKY'S PRICE £22.50 Post free in U.K.

KATONE AM/AIRCRAFT PORTABLE RADIO


BATTERY/MAINS

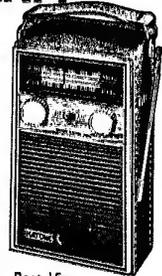

A combined battery and mains portable of exceptionally attractive design. Housed in a leatherette covered case, size 8 1/2in. x 5 1/2in. x 3 1/2in., fitted with an 8-section external telescopic aerial for FM and internal ferrite rod for MWV wave bands, and clear easy-to-read dial with logarithmic scale. Wave band coverage is FM 88-108MHz, AM 535-1,605KHz. A highly selective circuit using 9 transistors and 9 semi-conductors operating from either 4 x 1.5 volt torch batteries or direct from 230 volts 50Hz AC house mains, from a built-in mains unit. A socket is fitted for a personal earphone. Easy-to-use silver colour knobs, with "woodgrain" panel enhances the appearance of this fine radio.

LASKY'S PRICE £9.95 Post 15p

DIGITAL CLOCK SCOOP

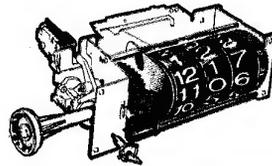

EXCLUSIVELY FROM LASKY'S

for you to mount into any housing. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V 3A. Complete with instructions, HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

LASKY'S PRICE £6.95 Post 18p

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12-HOUR ALARM
- AUTO "SLEEP"
- SWITCH HOURS MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR
- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

SPECIAL QUOTES FOR QUANTITIES

TRIO HS.1 & HS.2 STEREO HEADPHONE BARGAINS



Models HS-1 and HS-2. Both these sets by TRIO offer really superb stereo reproduction in a lightweight, fully adjustable headset designed for optimum comfort. Listening fatigue is unknown with TRIO headphones. Brief spec. both models: Input imp. 8Ω nominal (matching 4 to 8Ω); max. input 0.5W; frequency response 20-19 kHz; output sensitivity at 1mW input; HS-1 118 dB, HS-2 111 dB; weight 0.66lbs. identical in appearance—both models are finished in ivory with contrasting foam filled ear pads and head band.

LIST PRICE £8.40 LIST PRICE £6.75
HS.1 £5.20p HS.2 £4.15p Post 18p

Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821



PRACTICAL WIRELESS

VOL 47 NO 5

Issue 775

SEPTEMBER 1971

TOPIC OF THE MONTH

Electronic Vandals

A NEW generation of vandals is infesting the countryside. The scale of the menace can be judged by a report in *The Times* which says that more than 50 archaeological sites in Britain have been robbed by vandals using metal locators in the "last three months". These looters are urged on by irresponsible promptings such as contained in the book *A Fortune Under Your Feet*, which would not have been publicised in the article last month had the editor been aware of passages which recommend amateurs to operate metal locators on established Roman and pre-historic sites. We also condemn remarks made recently in *Coin Monthly* which, in slightly hysterical rhetoric, suggest that "an insignificant group of professional archaeologists" want to stop "those rights and pleasures" (of operating metal detectors). This technique of twisting the facts is as familiar as it is sickening.

This type of rabble-rousing emotionalism, coupled with the stimulation of the greed motive, is a ready incitement to gullible and unprincipled people to abandon whatever vestiges of conscience they may have had. It has led to a situation where our dwindling number of archaeological sites are being systematically ravaged. Archaeologists are seriously considering the possibility of not releasing information of newly discovered sites—a sad reflection of the times we live in, since the main objective of such exploration is the dissemination of knowledge.

It is galling also that having developed the skill of scientific and methodical excavation to its modern level, yielding a degree of information hitherto impossible, a process made possible largely by generations of voluntary research, skilled field workers are now confronted by sites irrevocably ruined by zombies whose motivating objectives are simply personal gain. A sad, sordid picture.

There are laws to protect important sites and moves are afoot for heavily increased penalties for despoiling archaeological sites. Welcome as this might be, we feel that the problem is more a case of civil conscience than Acts of Parliament. Readers of P.W. can help. Avoid areas where invaluable evidence may be disturbed or destroyed. If a "casual" find looks important, contact your county archaeological society at once—and don't spread the word around; if you have discovered a site of potential importance it will require highly specialised workers and scientific treatment to interpret the findings and to extract the maximum information. This may be impossible for all time if a site is heedlessly disturbed. Moreover, if you are genuinely interested in the advancement of knowledge, coupled with the excitement of glimpses into the past,

—continued on page 418

NEWS AND COMMENT

Leader	383
News . . . News . . . News	384
Electronotes by S. Ginsberg	390
On the Short Waves	
by Malcolm Connah and	
David Gibson G3JDG	413
Practically Wireless by Henry	415
MW Column by Charles Molloy	421
CQ! CQ! CQ! CQ! CQ!	430

CONSTRUCTIONAL

Linear Ohmmeter by J. N. Watt	386
Harmonic Six Receiver	
by F. G. Rayer, G3OGR	393
Digital Frequency Counter/Timer	
by John Thornton Lawrence	
GW3JGA	404
Variable Stabilised Power Supply	
by B. T. English	412
Take 20, No. 29, Slave Flash Trigger,	
by Julian Anderson	416
Variable Frequency Audio Oscillator	
by J. B. Willmott, A.I.P.R.E.	417
Novel Door Alarm by David Cross	420
Mini-Amplifier by R. A. Penfold	422

OTHER FEATURES


SERVICING—Part 5	
by H. W. Hellyer	399
I.C. of the Month (RCA CA3062)	
by L. A. J. Ireland	425
Going Back by Colin Riches and	
Arthur Dow	429

**OCTOBER ISSUE WILL BE
PUBLISHED ON SEPTEMBER 10th**

©IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

NEWS... NEWS... NEWS...

Impex instrument cases

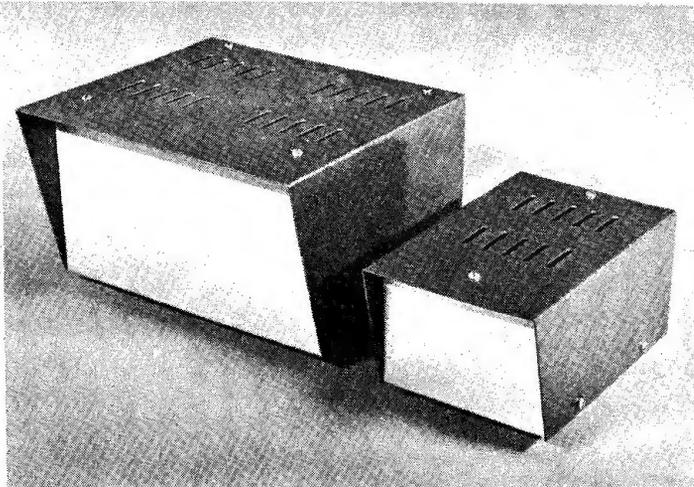

The cases shown come in a standard range of 36 sizes and are of 20 s.w.g. steel with a stove enamelled green hammer finish. The passivated zinc-plated steel base is 18 s.w.g.

Detachable front and back panels are of 18 s.w.g. satin anodised aluminium and are designed to lie flat for easy piercing. Phillips screws are used throughout and each case is provided with four rubber feet.

At no additional cost, Impex cases can be supplied with all or some of these specifications: alternative colours of blue or bronze; no hood; no ventilating slots or back/front anodised front/rear panels.

Examples of prices are: 2½in. height, 3⅜in. width and depth of 5in.: £1.13 plus 15p post and packing. A case measuring 5in.×13½in.×5in. costs £3.19 plus 25p p.&p. and one measuring 5in.×13½in.×11in. costs £6.40 with p.&p. charge of 28p.


Further details of prices of these cases, one-off jobs and rack-mounting units may be obtained from "Impex" McArdle and Brainsby (Import & Export) Ltd., P.O. Box 2BB, Newcastle-upon-Tyne, NE99 2BB.

Precision hand press


The "Innovcom" precision hand press can be used for the assembly and dis-assembly of small components and the application of precise pressure to a very small surface area.

Construction is light alloy body with hollow open base, drilled for two screw attachment to bench and drilled beneath chuck to hollow cavity. Link and plunger are of mild steel. Sintered bronze Oilite bushes are oiled for life. Handle length is 7½in. and full handle traverse of 2½in. gives chuck movement of 0.6in. Daylight (clearance) from chuck to platform is 1in. Chuck takes 40 thou wire, nail shaft or rod.

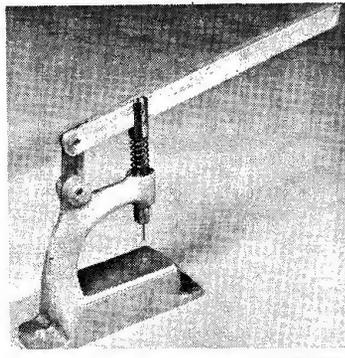The price is £3.45 postage and packing included and the unit is for UK distribution only. *Innovcom Ltd., Southbank, Daveylands, Wilmslow, Cheshire, SK9 2AG.*



The Mini Iron is here!

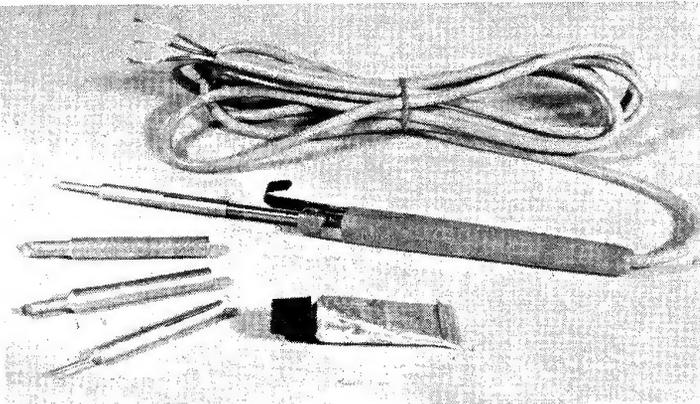

The Adamin Model 15 is a miniature soldering iron which comes complete with a set of interchangeable bits and a tube of lubricant. This iron weighs half an ounce less flex but its versatility is by no means "light weight." Used with the interchangeable bits from 0.047in. to ⅜in. it is suitable for all jobs from minute hearing aid soldering to heavy "chassis bashing."

A 12V version of the iron is also available and the complete hobby pack as shown and priced at £2.30 (p.&p. free) is available from *Light Soldering Developments at 28 Sydenham Road, Croydon CR9 2LL.*

NEWS... NEWS... NEWS...

Transensor kit

In the February 1971 issue we mentioned the Transensor slide synchroniser, which enables a cassette recorder to be used with an automatic slide projector.


The unit is now available in kit form, enabling it to be fitted by the purchaser to his own cassette tape recorder. The makers claim that some twenty or thirty improved versions of the mono cassette recorder appear on the market every year and as the Transensor S/2 kit is adaptable, it can be transferred from one machine to another as new models are introduced. The price is £18.

One other feature of the Transensor S/2 is that it allows pulses to be introduced and erased independently of the master sound track.


Further information may be obtained by writing to *Audio Visual Picture Enterprises, 17 Abercorn Place, London, N.W.8.* or telephoning 01-328-1461.

Bib auto record cleaner

The Bib Division of Multicore Solders Ltd., Hemel Hempstead, Herts has introduced an automatic record cleaner under the brand name Bib Groov-Kleen Model 40. Resembling a high quality miniature cartridge arm, it is finished mainly in anodised aluminium. The base is supplied with a self-adhesive disc so that it is easily fixed to the player deck. The base has a chromium-plated pivot pillar which can be raised or lowered so that the arm can be adjusted to be parallel with the turntable. The arm, which is cranked to provide better tracking, has a brush at one end and a counterweight at the other. A small roller mounted behind

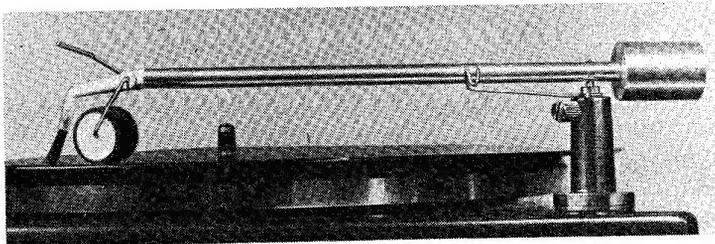

Return of the Maka Switch

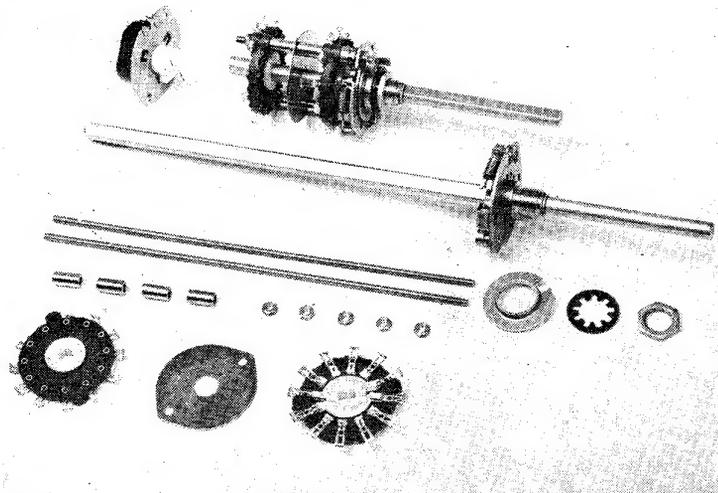

Constructors who have mourned the loss of the MAKAswitch will be delighted to learn that A. B. Electronic Components Limited manufacture a similar, but more versatile switch, which is available from stockists, in kit form. The size is approximately the same as the MAKAswitch, and as can be seen from the illustration consists of a shafting unit with a six inch length shaft, wafers, screens, spacers, studding and a mains switch.

The six inch shaft length will accommodate several wafers, or it may be cut down if only one or two wafers are required. The wafers are available as follows:—"Break before Make"—one pole twelve way; two pole six way; three pole four way; four pole three way; six pole two way. "Make before Break"—one pole ten way; two pole five way.

The metal screens are a feature which have been added. These switch kits are available from these suppliers:—Crescent Radio, 40 Mayes Road, London, N.22; Home Radio (Components) Ltd., 240 London Road, Mitcham, Surrey; Servio Radio, 156-158 Merton Road, Wimbledon, London, S.W.19; Garland Bros., Chesham House, Deptford Broadway, London, S.E.8; Radioparts, 5 Market Way, Plymouth, Devon.

the brush automatically sets its own level. A swivelling arm-rest is provided to hold the arm when a record is being placed on the turntable.

The recommended Retail Price is £2.08 plus P.T. of 51p. *Bib Division, Multicore Solders Ltd., Hemel Hempstead, Herts.*

Derby Rally

The fourteenth annual Derby Mobile Radio Rally will be held on Sunday August 15th, 1971, at Rykneld School, Bedford St., Derby. There will be a band concert, junk sale, prize draw, children's events, trade stands, competitions, demonstrations, ice cream, refreshments, etc. in addition to G3ERD/A on 160 metres and G8DBY on v.h.f.

Admission and parking are free and further details may be obtained from Tom Darn G3FGY, Hon. Organiser, "Sandham Lodge," 1 Sandham Lane, Ripley, Derbys. DE5-3HE. Phone Ripley 2972.

LINEAR Ω METER

J.N.WATT

THE first item of test equipment obtained by most home experimenters is a multi-range testmeter, capable of reading voltage and, probably, current and resistance as well. One large drawback of the ohms ranges is that they are very non-linear, being open at the low end and extremely cramped at the high end, see Fig. 1.

Besides being inconvenient to read, accuracy suffers when measuring values of resistance more than, say, 100kΩ on most instruments. Moreover, increasing resistance is read at the left-hand end, the opposite to the voltage and current ranges.

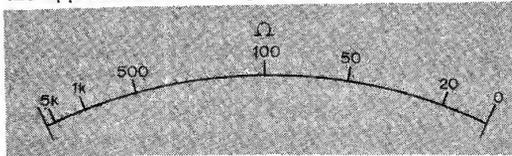


Fig. 1. Illustrating the cramped scale of a normal ohm-meter.


The ohm-meter described here has a linear calibration, with increasing resistance towards the right-hand end of the scale and uses five switched ranges to cover 10MΩ; the lowest value of resistance that can be measured is set by the accuracy with which the meter can be read but is about 100Ω. The possibility of extending this lower end downwards by a factor of 10 is discussed later. The ohm-meter is self-contained, although external batteries and an external moving-coil meter could be employed.

As a bonus, the form of circuitry used lends itself to adapting the instrument to test capacitors as well. Their value can be read and an indication is given of their insulation resistance i.e. leakage. The range of capacitors that can be tested in this way is about 0.1μF to 10,000μF, including electrolytics, but excluding those of less than about 8 volt rating, unless precautions are taken (see later for further details on this point.)

PRINCIPLE OF OPERATION

The principle of operation of the linear scale ohm-meter is illustrated in Fig. 2. A constant current is sent through the unknown resistance, R_x . Now, by Ohm's Law:—

$$R_x = \frac{E}{I}$$

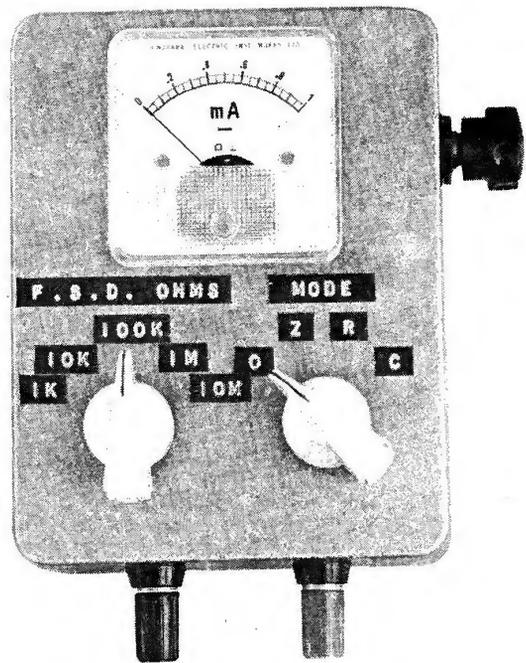

so that if I is constant:—

$$R_x \propto E$$

and a measure of E is a measure of R_x . Thus if a linear scale voltmeter can be arranged to read R_x , this also will be read on a linear scale.

To measure capacitance, use is made of the relationship

$$Q = VC$$

Charge Q is current x time, so

$$VC = It$$

$$\text{or } C = \frac{It}{V}$$

Remembering that C is in farads and I is in amperes, a current of 1μA flowing into a capacitor C for 10 seconds and producing a rise in potential of 10 volts means that C has a value:—

$$C = \frac{10^{-6} \times 10}{10} = 1\mu\text{F}$$


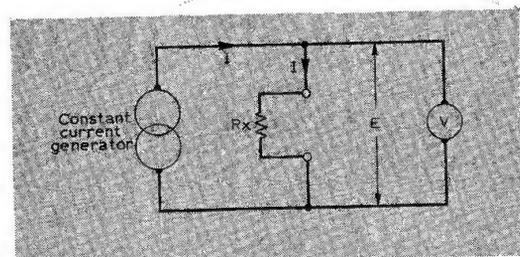


Fig. 2. Circuit to demonstrate the principle of the linear scale ohm-meter.

Similarly, $10\mu\text{A}$ for 10 seconds and a rise of 10 volts means that a capacitor of $10\mu\text{F}$ was connected, and so on.


Actual values of current used and voltage monitored are different from these examples but the principle is exactly the same.

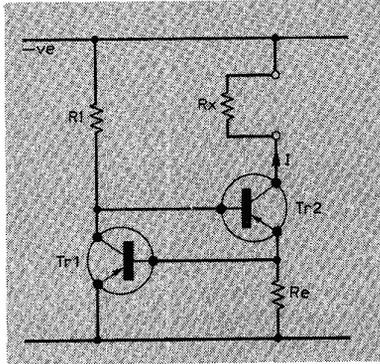Two difficulties now present themselves. How can we generate a constant current? How can we measure E on the voltmeter without upsetting the circuit? Remember that simple voltmeters, based on a moving coil meter and series resistors must draw some current to function at all. This latter point is best illustrated by example.



◀ Fig. 3. Circuit of a constant-current generator.

Fig. 4. Basic circuit of a very high impedance input voltmeter using an FET. ▶

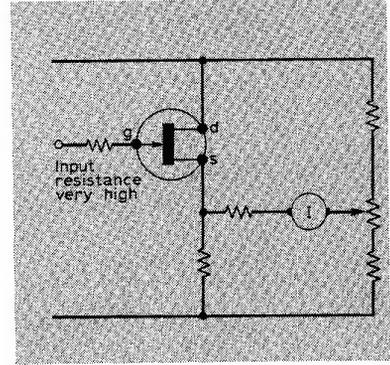

Suppose R_X is $1\text{M}\Omega$ and we have a $100\mu\text{A}$ meter, which requires $100\text{k}\Omega$ in series to read as a 10 volt f.s.d. voltmeter; if this were placed in parallel with R_X , as in Fig. 2 then obviously it would shunt the $1\text{M}\Omega$ to a considerable extent, and give a false reading.

To deal with the point first raised, that of generating a constant current, consider the circuit of Fig. 3. The base-emitter voltage of Tr1 is virtually constant at about 0.7 volt for a silicon transistor; hence the voltage drop across R_e is similarly constant. With a constant voltage across R_e , a constant current must flow to the emitter of Tr2 and hence,

if Tr2 has a high enough current gain for base current to be ignored, a constant current will flow at Tr2 collector. This will remain so, no matter if the value of R_X varies, due to the negative feed-back loop between Tr2 base and Tr1 collector, which functions as follows.

Suppose, for any reason, I increases. Then the voltage developed across R_e will increase, and so therefore will the base current of Tr1. The resultant voltage drop at Tr1 collector will tend to reduce the base current of Tr2 and hence also reduce its emitter current, so counter-acting the original increase.

The actual value of constant current is set to


that required by adjusting the value of R_e , and also by making some broad adjustment to R_1 . A value for R_1 suitable for $1\mu\text{A}$ is no longer so when, say, 10mA is required, and so some changes in R_1 are called for.

While any desired current can, in theory, be derived, obviously there are practical limitations. At the upper end dissipation in the transistors will be the deciding factor; note that maximum transistor dissipation occurs when R_X is at its lowest value, for then, for a given (constant) current, the voltage across the transistor Tr2 is greatest.

The lowest current that can be set up is limited in two ways. Adequate current gain must be available and the desired current must be large compared to the leakage current.

In the practical circuit, a lowest current of about $0.7\mu\text{A}$ is used; a BCY71 has a current gain of about 40 at this level, while leakage current is quoted as $0.05\mu\text{A}$ maximum. Should a substitute transistor be used, constructors must ensure that it is suitable from these points of view. No germanium device is likely to be a practicable substitute; BC179, BCY70 and BC157 should prove to be reasonable alternatives.

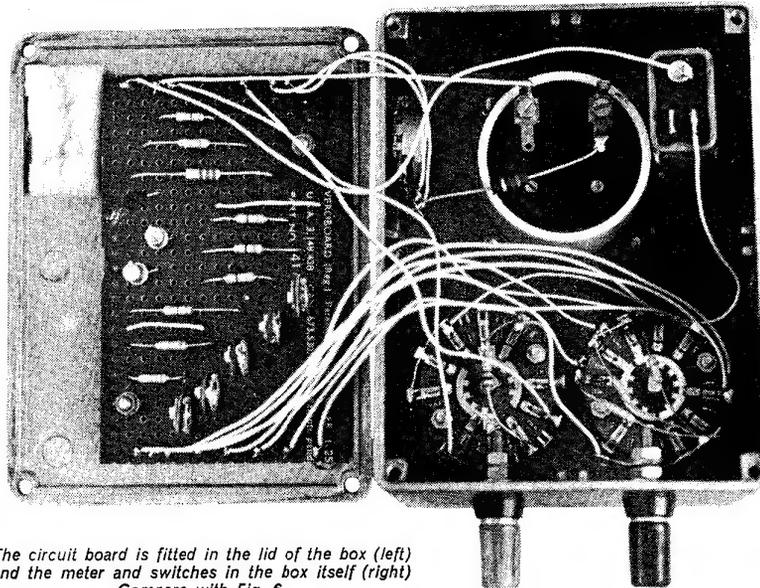With a constant current flowing through R_X we now require a high impedance voltmeter to measure the voltage



The circuit board is fitted in the lid of the box (left) and the meter and switches in the box itself (right) Compare with Fig. 6.

drop across R_x , so giving its resistance value. An FET seems to be called for and the ready availability of these devices at reasonable prices makes one the obvious choice.

Many circuits of high impedance voltmeters using FETs have appeared in the technical press but the one used here is based on a simple configuration published by Mullard Ltd., see Fig. 4.

The FET is arranged as a source follower; its source voltage is compared with a voltage derived from a potential divider. The series resistor in the gate circuit gives some protection against unwanted transients, which could damage the gate-source junction, by limiting the gate current. The input resistance of the circuit of Fig. 4 is many tens of megohms; in point of fact, the author was unable to measure it, it was so high—just what we require.

PRACTICAL CIRCUIT

The full circuit diagram now becomes as in Fig. 5, which includes the necessary switching.

One pole of S1 selects different emitter resistors for Tr2, consisting of a fixed and small variable in series, and this is the range switching. The other pole of S1 switches in one of three different resistors, to cover the five decades, for Tr1 collector load.

With S2 in the "Z" position, R9 is connected from the FET gate to supply negative, so permitting zero setting of the meter to be done by means of VR6. This done, and with the test resistor connected, when S2 is moved to position "R", the value of the resistor is displayed on a linear scale. This means that, for example, on the 10k Ω range, a reading of 0.7mA is to be taken as indicating 7k Ω , a reading of 0.35mA, 3.5k Ω and so on.

★ components list

Resistors:

R1 68 Ω	R6 6.8k Ω	R11 4.7k Ω
R2 680 Ω	R7 68k Ω	R12 2.7k Ω
R3 6.8k Ω	R8 680k Ω	R13 680 Ω
R4 68k Ω	R9 1k Ω	R14 2.2k Ω
R5 680k Ω	R10 68k Ω	

All $\pm W 10\%$.

VR1 100 Ω miniature pre-set

VR2 1k Ω " " "

VR3 10k Ω " " "

VR4 100k Ω " " "

VR5 1M Ω " " "

VR6 4.7k Ω (or 5k Ω) carbon potentiometer

Semiconductors:

Tr1 BCY71

Tr2 BCY71

Tr3 2N3819

Miscellaneous:

S1, 2 pole 5-way wafer switch. S2 2 pole 4-way wafer switch. M1, 0.1mA moving coil meter. Diecast box 4 $\frac{1}{2}$ x 3 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in. Veroboard 0.15in matrix. Terminals, red and black. Knobs, PP3 battery, etc.

For testing capacitors, the capacitor is connected with S2 at "Z", whence R9 removes any charge on the capacitor, and, after setting of zero as before. S2 rotated to "R" for either 10 seconds or until the meter reads f.s.d. Further rotation of S2 to "C" holds the reading and enables an assessment of capacitor quality to be made; see later under 'Capacitor evaluation'.

The second pole of S2 is the supply on/off switch.

Note that S2b **must** be a make-before-break switch, otherwise the instrument will be switched off between

positions of S2 and this would invalidate any capacitor measurements. Should such a switch not be available, then S2b should be replaced by a small toggle or slide switch mounted conveniently; S2a can be the more usual break-before-make type.

CONSTRUCTION

Having dealt with the basic theory and circuit of the linear scale ohmmeter, we can turn to constructional details.

The photographs and drawing show the layout of the prototype, which was housed in a die-cast box.

Most of the components are mounted on a piece of 0.15" pitch veroboard which is in turn mounted

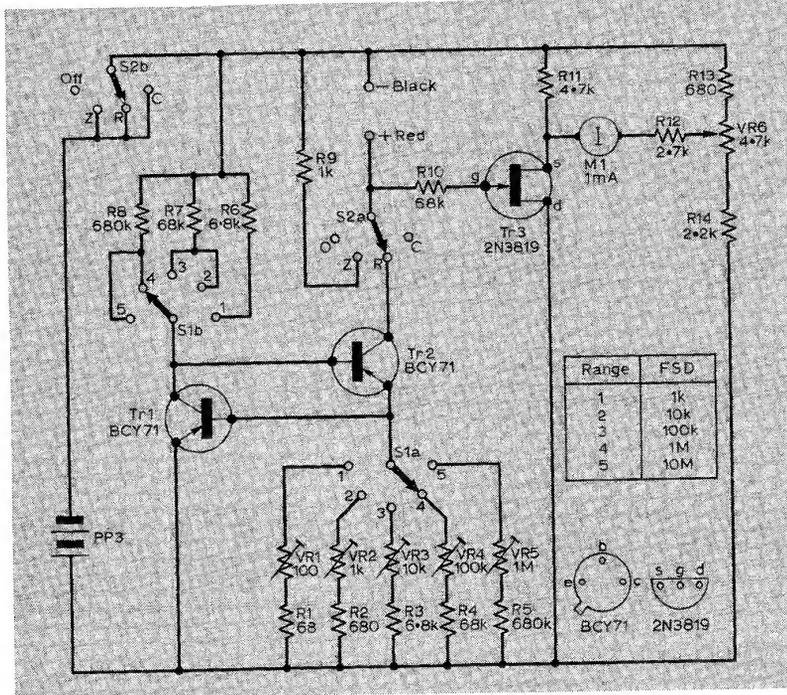


Fig. 5. Complete circuit of the linear ohm-meter, with transistor lead-out connections.

Fig. 6. Suggested layout of components with the circuit board in the lid of the die-cast box.

on the inside of the box cover, using nylon nuts as insulated spacers. Connections to the switches, meter, battery and terminals are made via veropins. The small pre-set variable resistors, VR1 to VR5 are 0.1 watt components intended for 0.1" pitch veroboard, but, by a slight bending of the terminal tags can be made to fit the board used.

A suggested layout is given, Fig. 6, but if for any reason the constructor wishes to alter this in any way, then this is in order.

The dimensions of the box used will depend on a number of factors. The meter is the most important of these; in the prototype the meter was one 2in. square. Although this may seem rather small, it is still capable of being read to about 2%, which is better than the accuracy with which the instrument can be set up by most constructors; it is also about the limit of accuracy of the meter movement itself.

A meter of such a size enables a box of 4 $\frac{3}{4}$ x 3 $\frac{3}{4}$ x 2 $\frac{1}{4}$ in. to be used, provided reasonable care is taken in the choice of components.

The rotary switches shown are of 1 $\frac{1}{2}$ in. diameter and so can be accommodated comfortably, while a PP3 9 volt battery is simply fitted by clamping it, in a vertical position, between the box and its cover. Two scraps of foam plastic, one at each end of the battery, prevent it from moving and at the same time provide insulation for its terminals. Connection to these is by soldering wires directly to them, there being no room for the usual snap connector. Since the whole instrument draws only 3 mA, plus any test current, a PP3 should last a very long time if the unit is switched off when not actually in use, and thus solder connections to the battery are no great disadvantage.

With wiring up completed, check that the voltmeter section is functioning correctly by switching S2 to "Z" and seeing that VR6 enables the meter to be brought to zero.


Actual setting up of the emitter resistors of Tr2 by means of VR1 to VR5 can only be done by making use of known values of resistance. However, even just the loan of resistors of 2% accuracy will suffice, while 5% resistors can be bought quite cheaply. Values required are 10M Ω , 1M Ω , 100k Ω , 10k Ω and 1k Ω .

Start with range 1 and fit the 1k Ω to the terminals; with S2 at "R" adjust VR1 to give a reading of 1mA on the meter. Repeat on the other ranges, using the appropriate resistors, and remembering to put S2 to "Z" before removing resistors.

CAPACITOR EVALUATION

Measurement of the value of medium to large capacitors and an indication of their leakage resistance can be considered as a bonus with the ohmmeter but can be omitted if desired.

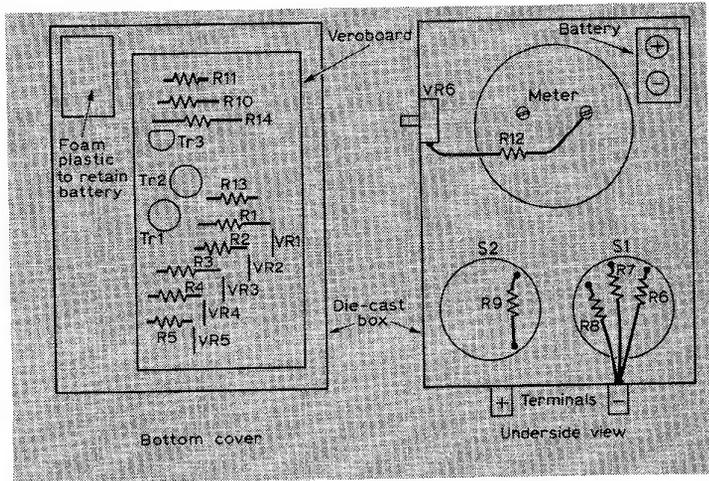Demonstration of this mode of use can best be carried out using a 1 μ F paper capacitor. With S1 on range 5 and S2 at "Z", connect the capacitor and then put S2 to "R". Note that the meter reading



slowly increases at a constant rate. When the meter reads 0.8mA or so, switch to "C"; the unit is now reading the voltmeter that was developed across the 1 μ F by the constant current which flowed into it on "R", and if the meter reading stays constant, or almost so, then the 1 μ F capacitor is a good one. The implication is that the voltmeter input resistance is very many megohms and hence is extremely difficult to measure.

With this confirmation that the 1 μ F capacitor is a good, low leakage specimen, it is now an easy matter to measure its actual value.

First, put S2 back to "Z", so discharging the capacitor by means of R9. Then, switch S2 to "R" and commence timing, either by stop watch or a sweep second hand on a watch or clock. When 10 seconds have elapsed, or the meter reads f.s.d. which ever is the sooner, switch S2 to "C", noting the elapsed time if less than 10 seconds.

If, after 10 seconds, the meter reads 1mA, then the capacitor was exactly 1 μ F. A meter reading of, say, 0.8mA after 10 seconds indicates a value of

$$\frac{1}{0.8} \times 1 \text{ or } 1.25\mu\text{F and so on.}$$


On the other hand, if 1mA was reached after only 7 seconds, then the capacitor was

$$\frac{7}{10} \times 1 \text{ or } 0.7\mu\text{F}$$

Whether the capacitor is actually larger or smaller than the 1 μ F corresponding to f.s.d. on range 5 is easily remembered by recalling that a large value capacitor will take longer to reach a given voltage at a given constant current than will a small value capacitor.

The values of capacitance corresponding to each position of S1 and 10 seconds for meter f.s.d. are as follows:—

RANGE	RESISTANCE	CAPACITANCE
1	1k Ω	10,000 μ F
2	10k Ω	1,000 μ F
3	100k Ω	100 μ F
4	1M Ω	10 μ F
5	10M Ω	1 μ F

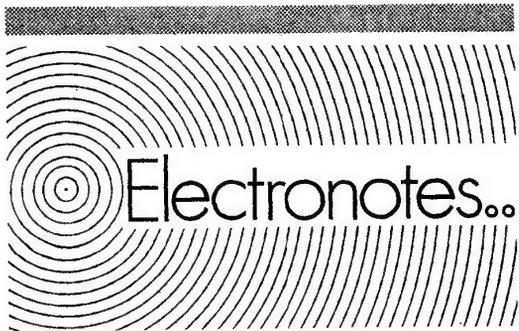

Electronotes..

S. GINSBERG

WHEN someone takes an accepted practice and does exactly the opposite the results are often astounding. This has been the case in the Siemens Laboratories in Berlin. Ever since the electron microscope has been invented, everyone has employed it to peer at the most minute items, relying on the microscope, with its tremendous magnification, to give a clear and detailed image. Siemens decided it was time to try things in reverse, rather like looking through the other end of a telescope. The result is that just as the items could be magnified by very large amounts they can also be reduced. This means that it is possible to put the whole of the contents of the Bible on an area of some 0.25×0.25mm. Think of the idea as a means of storage. Around 1,000 Bible-length volumes could be stored, ready to be read by looking at them through the electron microscope the "right way", in an area of 25 square millimeters. Scotland Yard might well be interested since it is possible to store one million photographs on a piece of foil 5×5mm. They'll be fingerprinting fleas next.

Valve enthusiasts, certainly those interested in generating r.f., have wagged their wise old heads for years at the transistor lovers and pointed out that when it comes to generating lots of power, the solid state devices available just aren't in the same class as their glass-encapsulated brothers. It now looks as though this is no longer true. One company has announced an h.f. amplifier which is broadband from 1.5—30MHz and thus requires no tuning. It is solid state—not a valve in sight—and will supply 1kW on all modes of radiotelegraph and radiotelephone transmissions. For the 1,000W output, which, by the way, is the continuous rating, it requires only 100mW input. The amplifier is not a delicate device. A patented level control will prevent any damage which might be caused by an antenna mismatch which can range from an open circuit to a short circuit.

Hats off to the Allen Company in America. They are making an electronic organ which uses a computer to provide tones and voices. The 22 circuits on chips half-an-inch square contain some 48,000 transistors. The various waveforms and tones are simply stored in the musical computer's memory and called out or "read" at will. The number of voices available are almost unlimited, running into millions. The electronics for the computer have been worked out in association with another American company—North American Rockwell who have done a great deal of work on aerospace digital computers.

It is essential to observe polarity when testing electrolytic capacitors.

Should these be of a very low voltage rating i.e. less than, say, 8 volts, then do not allow the meter reading to rise above about half scale. This will restrict the voltage on the capacitor to a low level. Using a charge time of 5 seconds in lieu of 10 seconds, then a meter reading of 0.4mA indicates a capacitance of

$$\frac{1}{0.4} \times 5 \text{ or } 1.25\mu\text{F}$$

To sum up, the value of capacitance is, in general:

$$C_x = \frac{1}{I} \times \frac{t}{10} \times C$$

where I is meter reading in mA

t is time to reach that reading

C is capacitance given in the table.

A little practice with capacitors of known value will soon make this method clear.

It is always as well to carry out a quick check first on doubtful capacitors to test for leakage. If leakage is taking place, as indicated by a falling meter reading on "C", then any capacitance values read off will of course be in error, for some of the current fed to the capacitor will have gone towards providing the leakage current and the voltage reached will thereby be less.

Whether the amount of any leakage so detected can be tolerated will depend on the application intended and no general rules can be laid down.

NOTES

If a multi-range current meter is available, it is quite instructive to use it to measure the test current on each range. No matter whether, say, on range 3, 100kΩ or a short circuit is connected, then about 60μA should flow, and, similarly, with other currents on other ranges as appropriate. The actual value of the current depends on the particular setting of the appropriate emitter resistor.

In the introduction, mention was made of the possibility of extending the lowest range of resistance measurement downwards by a factor of 10. If carried out, this would make the lowest range indicate up to 100Ω with a good indication down to 10Ω. This is not possible, however, without some alteration of transistor type.

A range of 100Ω f.s.d. requires a constant current of about 60mA and so a possible dissipation in Tr2 of about 600mW, which is too great for the BCY71 specified.


A glance at some manufacturers' data shows that a number of suitable transistors are available, such as BFX88, 2N1132 and 2N4036 and no doubt others. Not all of these have a low enough leakage current however, to enable them to give good results on the 10MΩ range and it would be as well to omit this latter if the 100Ω range is incorporated.

The author regrets that he can give no further practical details, not having tried a low resistance range; what is obvious is that a larger battery, or a small mains supply, will be needed to provide the extra current required. The care that will be called for in use should not be overlooked, for up to 600mW might be dissipated in the test resistor, and consequently testing will have to be restricted to resistors of that wattage rating or greater. ■

Discosound

P. A. AND DISCOTHEQUE EQUIPMENT

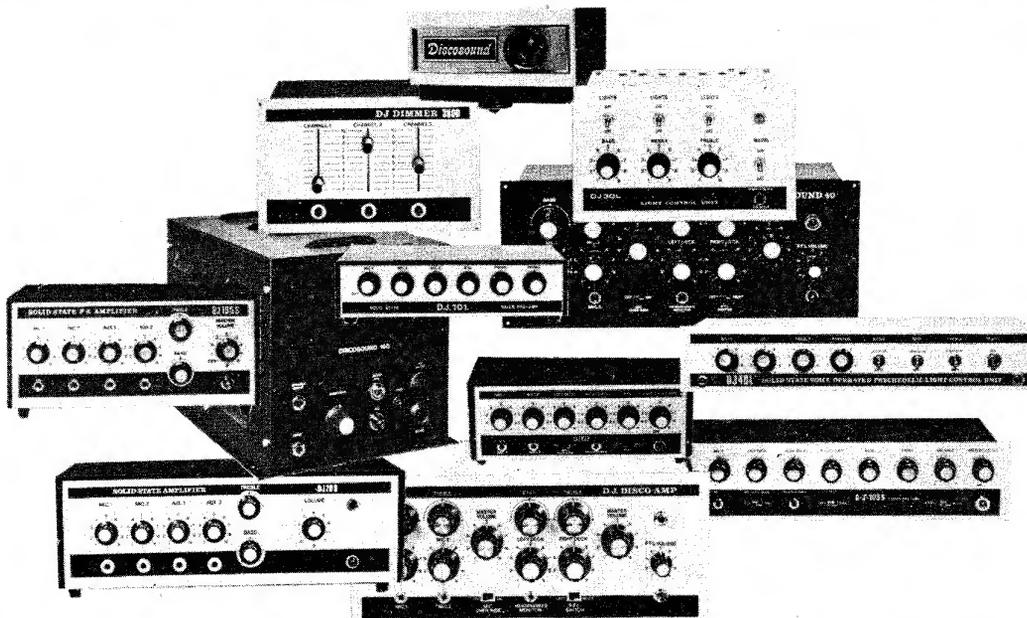— A COMPREHENSIVE RANGE COVERING EVERY REQUIREMENT
AMPLIFIERS, MIXERS, LIGHT CONTROL UNITS.



D.J. 102 Discotheque Mixer Pre-Amplifier

4 inputs each with its own volume control plus master volume control, PFL monitoring and mic override switches.
Size 10½" x 4" x 4".

Suggested Retail Price £25-00

D.J. 105S P.A. Amplifier

4 channel mixing facilities each with separate inputs and volume controls 30 watts r.m.s. power output A.C. Mains 200/250v A.C. Size 11½" x 5" x 6".

Suggested Retail Price £41-00

D.J. 70S Integrated Mixer Amplifier

Power output 70 watts r.m.s. 4 channel mixer with separate inputs and volume controls, plus master volume and separate bass and treble controls.
Size 15¼" x 5" x 6".

Suggested Retail Price £68-00

D.J. Disco-Amp

Designed specifically for use with discotheques. Power output 100 watts r.m.s. Two mike inputs and two gram inputs, with independent volume controls plus bass and treble controls. Incorporates many exclusive features.
Front panel size 16¼" x 7".

Suggested Retail Price £85-00

D.J. 101 Mixer Pre-Amplifier

Six inputs allow full mixing facilities for all types of equipment. 9v battery operation. Size 10½" x 2½" x 4½".

Suggested Retail Price £14-00

Discosound 40 Discotheque Pre-Amplifier

Features independent inputs and volume controls for two microphones and two turntables plus separate bass, treble and master volume controls. Self powered and ideal for use with Discosound 100 Power Amplifier (is capable of running 10 of these power amplifiers—total 1000 watts)

Front panel size 16¼" x 7".

Suggested Retail Price £40-00

Discosound 100 Power Amplifier

100 watts r.m.s. power amplifier (at 8 ohms) utilising all silicon transistors and features full automatic overload against short or open circuits. Frequency response 20-20,000 Hz ± 3db. Distortion less than 1% at 70 watts r.m.s. ± 1db.

Size 10½" x 8" x 7".

Suggested Retail Price £49-50

D.J. 103S Stereo Pre-Amplifier

A high quality stereo discotheque pre-amp unit. Incorporating two microphones and two turntable inputs each with independent volume control, plus bass, treble, balance and master volume control. Offers full mixing and monitoring facilities.
Front panel size 16¼" x 3¼".

Suggested Retail Price £49-50

D.J. 30L Psychedelic Light Control Unit

3 channel light unit enabling bass, middle and treble frequencies from the amplifier to be operated individually. Handles 1000 watts per channel.

Front panel size 10" x 6".

Suggested Retail Price £37-50

D.J. 40L Sound Operated 3 Channel Light Unit

Features built-in microphone which eliminates the need for connections to any amplifier or sound source.

Handles 1000 watts per channel.

Suggested Retail Price £56-25

D.J. DIMMER 3000

3 channel light dimmer unit offered in two versions: Dimmer 3000—a straight three channel dimmer unit with mains input and three light outputs.

Dimmer 3000S—for use in conjunction with D.J. 30L Light Control unit only and has three mains inputs and three light outputs. Front Panel size 10" x 6".

Suggested Retail Price £32-50

Discosound Disco-Wheel

A projector designed to project a range of liquid wheels and colour change wheels for special lighting effects, adding colour and variety to any form of entertainment.

Size 7½" x 10½" x 5½".

Suggested Retail Price £50-00

A range of complete Discotheques with matching Speakers also available.

DISCOSOUND PRODUCTS ARE GUARANTEED FOR 12 MONTHS

For full details of the Discosound range of products call at or write to your nearest Discotheque Centre — Demonstrations given at any time.

DISCOSOUND

122 Balls Pond Road, London N.1. Tel: 01- 254 5779

HENRY'S RADIO LTD.,

309 Edgware Road, London W.2. Tel: 01-723 6963

STROBE! - STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. **EXPERIMENTERS' ECONOMY KIT** Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.30 plus 25p P. & P.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50, P. & P. 50p.

HY-LIGHT STROBE MK III

This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £12.00, P. & P. 50p.

AND NOW!

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

- Incorporating:
- Heavy duty power supply.
 - Variable speed from 1-23 flash per sec.
 - Fantastic Octal based tube with massive electrodes.
 - Reactor control circuit producing an intense white light.

The brilliant light output of the 'SUPER' HY-LIGHT gives fabulous effects with colour filters.

Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.

7-1/2" POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.

RECHARGEABLE BUTTON CELLS

2 x 1.2V, 250 MA HR Nickel Cad. Cells, connected to give 2.4V @ 25 milliamp. 10 hr. rate, complete with 200/250V a.c. charger. Fully tested and unused Price 48p each plus 8p P. & P. or 2 units for £1.00 post paid.



VENNER ELECTRIC TIME SWITCH

200/250V Ex. G.P.O. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk. OFF dawn. Price as above.



200-250V A.C. NEON INDICATOR

Available in red or amber at 20p each. Or in green at 32p each. Minimum order 3 units. P. & P. 5p.



ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2V batteries. Complete set of parts including speaker etc., together with full instructions and 10 tunes. Price £3.00, P. & P. 22p.

50 IN 1 ELECTRONIC PROJECT KIT
50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75, P. & P. 30p.

CRYSTAL RADIO KIT
Complete set of parts, including Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instructions. £1.75 inc. post.

12 VOLT DC MOTOR


Powerful 1 amp. REVERSIBLE motor, Speed 3750 RPM complete with external gear train (removable) giving final speed of 125 RPM. Size: 4 1/2" x 2 1/2" dia. Price 95p inc. post.



SERVICE TRADING CO

All Mail Orders, Also Callers, Parking Space. Dept. PW9 57 BRIDGMAN ROAD, LONDON, W4 5BB. Phone 01-995 1560. Showrooms now open, Mon.-Fri. Personal Callers only. Open SAT. 9 LITTLE NEWPORT ST. LONDON. WC2H 7JJ 01-437 0576.

BETTER GET 'SET'

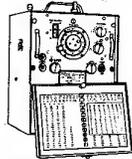

BEST OFFER YET!
FAMOUS BC.221
FREQUENCY METER
125 KHz-20 MHz. Complete with valves, crystal and charts. ONLY £18.50. Carr. £1.50. LIMITED NUMBER - ORDER NOW!

CRYSTAL CALIBRATOR

No. 10 Crystal controlled heterodyne wave-meter covering 500 KHz-10 MHz (Harmonics up to 30 MHz). Power required 300V. D.C. 15mA. 12v. 0.8A. D.C. Test equipment for 62TM/RC. ONLY £4.25. P. & P. 50p. NEW ONLY - No. 62TM/RC 1.5-10 MHz £17.50. Carr. £2.





MARCONI 801A SIGNAL GENERATOR

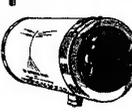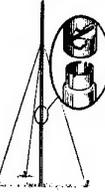10-310 MHz. In original transit case. £45. Carr. £2.50.

AERIAL MAST EQUIPMENT

20' TELESCOPIC MASTS £3.75. Carr. £1.
5' 2" Extension Sections to fit bottom of above mast to increase height. £1.25 each (any number supplied).
35' MAST (7-5' 2" interlocking sections) with base plate and 12 nylon guys with semi-auto tensioner. £22.50. Carr. £2.50.
70' MAST Ditto. 16 guys, block and tackle. £45. Carr. £2.75.



R.F. ANTENNA TUNER (A.T.U.)


Cylinder design 10" x 4 1/2". Precision calibrated scale. Suitable for tuning most aerials for increased signal strength. A must for serious operators for RC or TM. Full instructions. ONLY £11.75. P. & P. 25p.

R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE

Mounted on ceramic former and feet. "Roller Coaster" design 18 G silver or silver plated wheel traversing on wire on ceramic former. Will handle considerable R.F. In original packing. As used with No. 53 Transmitter. ONLY £2.50. P. & P. 50p.

VHF COMMUNICATION RECEIVER 1392

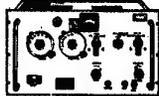Frequency range 95-100 MHz. Normally crystal controlled. (Modes supplied for tuneable operation.) Power requirements 240V AC 80mA 6.3v-4A. ONLY £8.50. Carr. £1.



No. 19 TM/RC

Rebuilt. Complete station with PSU, Cables, Mic, Aerial etc. £22.50. Carr. £3.

No. 19 SET 500uA METERS

Scaled 0-600 and 0-15V. Brand new, boxed £1.25 Post Paid. (Quantity prices on request.)



ALL No. 19 SPARES IN STOCK

Complete instruction book with circuits for No. 19 Equipment. 87p Post Paid.

R.F. AMPLIFIER

To increase output of No. 19 Set. ONLY £3.75. Carr. £1.25. Instruction Book for RF Amp. 37p Post Paid.




HEAVY DUTY BATTERIES

New in metal cases with carrying handles.

6v. 40 AH 10 1/2" x 9 1/2" x 5" £3.25. Carr. £1
6v. 85 AH 13" x 9 1/2" x 7" £3.25. Carr. £1.25

FAMOUS TELE 'F' FIELD TELEPHONES

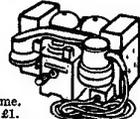Suitable for Farms, Building Sites etc. Communication up to 8 miles or more. Rugged construction, will last a lifetime. ONLY £5.75 PAIR. Carr. £1. (Twin telephone wire for above available—ask for price.) Many other Ex-Govt. Surplus Equipment items in stock. Receivers etc. in small quantities too numerous to mention. Enquiries invited. L.S. £25 Post Paid. (Refundable against purchases over £3.)



NEW 3in. SPEAKERS 15 ohms 75p, p. & p. 10p.

BARGAIN PARCELS 14lb at £1.45 plus 32p p.p.; 28lb at £2.75 plus 52p p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £2s. Lucky Dip Service.

NEW 6 ft. VHF AERIALS. Freq. 75-78 Mc/s, 70 ohms. £2.50p, p. & p. 50p.

VHF Receiver, Type 715, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tuneable 12 volt input, not tested; complete with valves and speaker. £3 plus 41 p.p.

VHF AERIAL TUNING UNITS consisting of the following: 1-1 1/2" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 50/50 watts R.F. input. Size only 5 1/2" x 4 1/2" x 3" Sealed. Price £1-37p p.p. 25p

CRYSTALS AS NEW: Hc 6u, 5,345; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,560; 4,520; 4,510; 2,800; 2,255 Kc/s and 10 x 3465 Kc/s. 50p each plus 8p. p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS: 10% tolerance 1/2 & 1/4 watt. Preferred values in packets of 10. Our price 50p per 100, 50p per 200, £1-35 per 300, 500 at £2-12. Our selection, p.p. 8p per 100 and 2p per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice. Trimmers without Xtal—60p per doz. plus 17p p.p. Trimmers with Xtal—75p per doz. plus 17p p.p. Also 20 PF min. brand new air spaced. 50p per doz. plus 17p p.p.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1" dia x 3 ft. long. Brass screw in type, copper coated and painted. New 20p each, p.p. 5p. each. Minimum order 6.

BRAND NEW HARTLEY OSCILLOSCOPES CT316 in original packing. Band width up to 5 Mc/s. Mains supply. Price £40, p. & p. £1-50p.

AERIALS NEW CONDITION. Whip type 4ft 25p, 14ft. 77p. Used condition 4ft. 20p, 14ft. 62p. All collapsible type p. and p. 4ft. 10p, rest at 17p. Bases for above 25p, p.p. 12p. New matching unit coax connection for above 80p, p.p. 6p.

Huge release of valves for the 62 set TX/RX. In original rubber packing consisting of VQ04/7 x 61M, ARP12 etc. 10 valves in all at the bargain price as seen 87p plus 17p p.p.

New Headphone and Mike rubber muff type. Low impedance. 97p, p. & p. 17p.

NEW AERIAL WIRE ON BOARDS 7/82 UNCOVERED. 75ft, 40p, 90ft, 47p, 100ft 55p, 150ft, 75p, 180ft, 95p, 250ft, £1-80p, p. & p. 12p.

Headphones, ex Gov. DLR No. 5 high impedance. New 87p 17p p.p. Used condition 62p 17p p.p.

MUIRHEAD DECADE A.F. SIGNAL GENERATOR.

This precision instrument can be used:

1. To Measure Gain up to 50 db.
2. To Measure Loss up to 45 db.
3. To compare Power levels (A.F.).
4. As an Audio Frequency Generator covering 100 Hz to 41 kHz. With a dial setting accuracy of ±0.5 Hz. Output —1 M/W into 800 Ω. Complete with mains power unit. Tested. Good Condition. £12, p. & p. 75p.

Heavy New Coax Cable 760HM will handle at least 1KW 50ft lengths, Plug on end, £1.70p + 30p.p.

Also 1/2" 75 ohm Coax in 50ft coils with BNC plugs good condition. price £1 + 30p, p.p.

2 BNC plugs on short length coax cable large size low loss plugs 80p + 5p, p.p.

Block Type capacitor TCC 8UF + 15% 350 VDC WKG 60°C. 250 VDC WK9 70°C Type 62 CIM Price 40p + 13p p.p. New.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

A. H. THACKER,


Radio Dept., HIGH STREET, CHESLYN HAY, Nr. Walsall, Staffs.

Surplus Electronic Trading

DRIVERS END LANE, CODICOTE, HITCHIN, HERTS, SG4 8TP

HARMONIC SIX RECEIVER

E.G. RAYER
G30GR

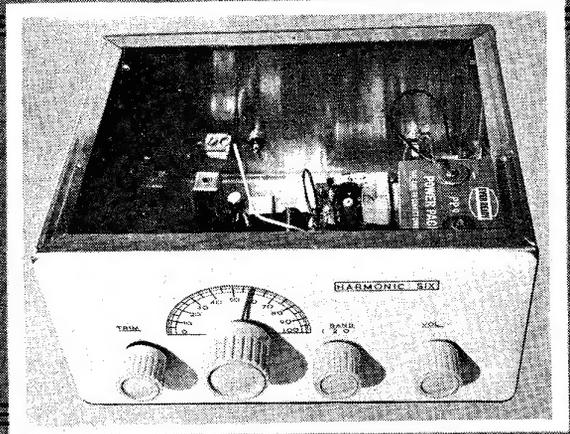

THIS is a short wave receiver covering the most active short wave bands of about 5.5-22MHz, or 55-14 metres, where very many short wave broadcasts are to be found. The range is divided into two bands, so related that harmonic mixing makes it unnecessary to have oscillator coil switching. This will be found to give excellent results with a minimum of constructional difficulty, and band-change switch wiring is extremely simple.

The receiver is constructed in three sections, mixer, i.f. amplifier and audio amplifier, accommodated in a neat aluminium case which also takes the battery. A separate speaker is used, because headphones may sometimes be preferred, allowing personal short wave reception without disturbance to others.

CIRCUIT DETAILS

Mixer. Fig. 1 is the circuit which also shows the division into three parts. The mixer assembly is complete with tuning capacitor, band-switch, coils and other items, having a small sub-panel for the controls.

L1 is the aerial coil for the higher frequency range of about 11-22MHz, while L2 is for about 5.5-11MHz. S1 selects the wanted coil. Base coupling windings for Tr1 are in series, and thus require no switching.

L3 is the oscillator coil, the values of C6 across the coil and C7 in series with the oscillator tuning capacitor VC2 allowing this circuit to tune from approximately 6MHz to 11.5MHz. When L2 is in

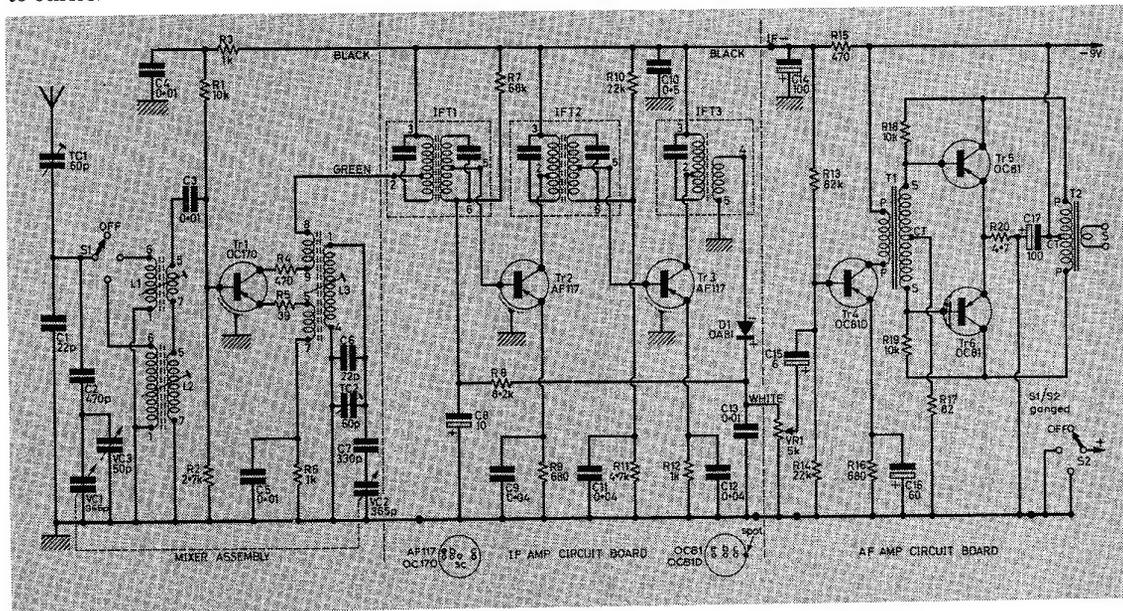


Fig. 1: Circuit diagram of the Harmonic Six with transistor lead-out connections.

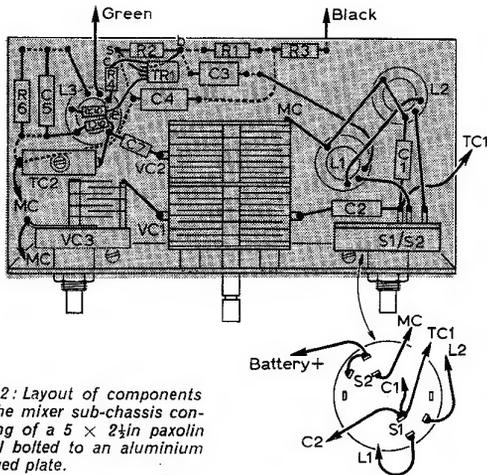


Fig. 2: Layout of components on the mixer sub-chassis consisting of a $5 \times 2\frac{1}{2}$ in paxolin panel bolted to an aluminium flanged plate.

circuit, VC1, in conjunction with C1 and C2, allows the aerial section to tune from approximately 5.5-11MHz. In terms of actual frequencies, the oscillator is 465kHz h.f. of the aerial circuit, in the usual way.

To reduce oscillator pulling, some transistor receivers have the oscillator working at half frequency, for the highest frequency range. This is purposely done in this receiver, so that no switching, or further coil or trimmer will be needed instead of L3. Instead, the second harmonic of the oscillator frequency is used, and the range of this harmonic is approximately 12-23MHz. L1 is in circuit for this band, and tunes 465kHz lower in frequency than the second harmonic, or about 11.5-22.5MHz. There is

actually a little overlap between bands, giving continuous coverage from about 5.5-22MHz.

The receiver can bring in many transmissions with a short indoor aerial, either wire, or self-supporting rod, and the aerial trimmer VC3 is a panel control, so that L1 or L2 can be peaked for maximum results, despite changes to the aerial.

Resistors R4 and R5 are to avoid excess oscillation, which sometimes causes whistles and other troubles on the higher frequencies. In some cases it may be worth while modifying the values of R4 or R5, as mentioned later.

The mixer assembly is secured in the case by the bushes of VC3 and S1, this completing the positive or earth return. Two leads run from the mixer assembly—black for the negative supply circuit, and green for the i.f. amplifier.

IF Circuit. This board carries i.f.t.1, i.f.t.2, i.f.t.3, Tr2, Tr3, and the associated components. It is wired separately, and may be checked or tested alone. Two double-tuned i.f.t.'s with AF117's give very good gain and selectivity. Automatic gain control bias is obtained from the diode D1 in the usual way.

The positive circuit of the i.f. board is completed by its two mounting bolts, through the metal case. Audio output is from D1, the white lead running to the volume control VR1.

VR1 is fixed to the case front and so is not present on either i.f. or a.f. boards.

AF Amplifier. Audio signals are taken to the audio amplifier and driver Tr4, which is followed by the push-pull output pair Tr5/6. This is a straight-forward arrangement capable of giving a good output, and it is wired complete on its own circuit board. Positive returns are made through the fixing bolts and metal case, as before.

S2 is the second pole of the switch S1, which is 3-way. The third position interrupts the positive circuit for "OFF." Should an on-off switch be preferred on VR1, it is necessary to fit a compact potentiometer with switch, or there will not be enough space for a PP9 battery in the receiver.

A connecting point is provided at the junction of C14 and R15 for the black lead from the i.f. board.

CONSTRUCTION

Mixer Assembly. Components are placed as in Fig. 2. Holes are made in the 5 x 2in. flanged plate for the variable capacitors and switch. Washers or other means of spacing, about $\frac{3}{8}$ in. thick, are put between the plate and ganged capacitor, on each of the three fixing screws. It is essential that these screws are not too long.

Two bolts hold the insulated board to the flanged plate. Wire

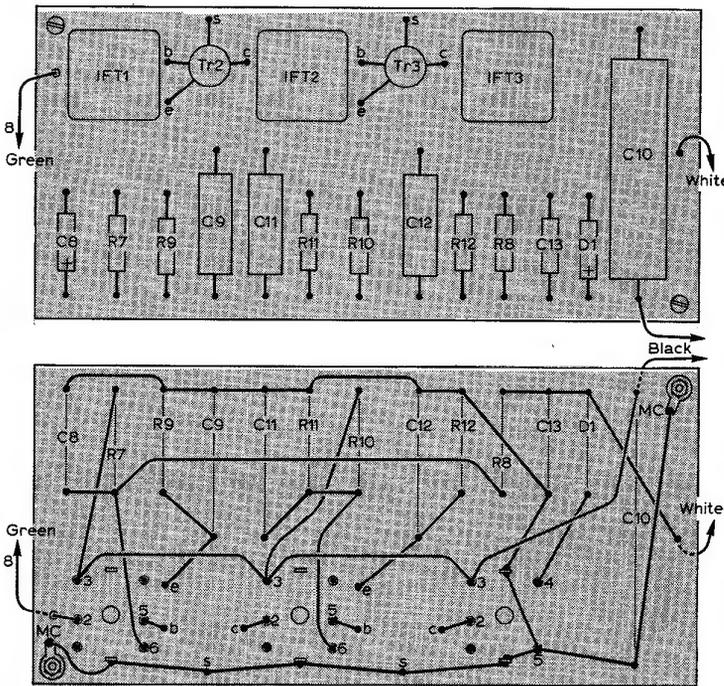


Fig. 3: Component layout and wiring details of the i.f. circuit board $3\frac{1}{2} \times 1\frac{1}{2}$ in.

TRANSISTORS

NEW LIST - NEW PRICES
SEND FOR FREE COPY TODAY
Brand New Fully Guaranteed

2N404	20p	BC107	12p	BYZ13	25p
2N696	15p	BC108	12p	BYZ16L1-00	
2N697	15p	BC109	12p	GET880	37p
2N705	10p	BC113	15p	MAT100	25p
2N706A	12p	BC114	25p	MAT101	30p
2N930	25p	BC115	20p	MAT120	25p
2N1131	25p	BC116	25p	MAT121	30p
2N1182	25p	BC116A	30p	MJ280121-37	
2N1302	20p	BC118	25p	MJ290122-25	
2N1303	20p	BC119	35p	MJ290123-25	
2N1304	25p	BC124	25p	MJ290124-25	
2N1305	25p	BC125	20p	MJ290125-25	
2N1306	25p	BC136	22p	MJ290126-25	
2N1307	25p	BC137	25p	MJ290127-25	
2N1308	25p	BC138	25p	MJ290128-25	
2N1309	25p	BC147	17p	MJ290129-25	
2N1613	22p	BC148	12p	MJ290130-25	
2N1711	25p	BC149	20p	MJ290131-25	
2N2147	75p	BC154	37p	NK2717 40p	
2N2160	60p	BC155	20p	NK2717 40p	
2N2218	20p	BC158	17p	NK1408 75p	
2N2219	20p	BC159	20p	NK1408 75p	
2N2922	20p	BC160C	15p	OA5	20p
2N2922A	25p	BC177	25p	OA5	10p
2N2965	20p	BC179	25p	OA7	10p
2N2966	50p	BC179	27p	OA7	10p
2N2964	50p	BC182L	12p	OA70	10p
2N2964A	50p	BC183L	12p	OA73	10p
2N2964B	50p	BC184L	15p	OA81	10p
2N2965	50p	BC219	25p	OA81	10p
2N2966	20p	BCY30	25p	OA85	12p
2N2966A	25p	BCY31	30p	OA90	10p
2N2967	20p	BCY32	50p	OA91	7p
2N2926	10p	BCY11	25p	OA95	7p
2N3011	25p	BCY34	70p	OA200	70p
2N3055	20p	BCY38	40p	OA200	10p
2N3054	50p	BCY39	85p	OC16	50p
2N3055	75p	BCY40	50p	OC20	97p
2N3055	75p	BCY41	50p	OC20	97p
2N3055	75p	BCY59	25p	OC23	60p
2N3702	10p	BCY70	15p	OC24	60p
2N3703	10p	BCY71	20p	OC25	37p
2N3704	15p	BCY72	15p	OC26	25p
2N3705	15p	BCY73	15p	OC27	25p
2N3707	15p	BCY79	10p	OC29	60p
2N3709	10p	BCZ10	35p	OC35	50p
2N3710	10p	BCZ11	45p	OC36	60p
2N3819	85p	BD112	50p	OC41	25p
2N3820	60p	BD121	60p	OC42	30p
2N4055	15p	BD123	60p	OC43	40p
2N4061	15p	BD124	75p	OC44	17p
2N4497	37p	BD125	50p	OC45	15p
2N4548	37p	BD131	75p	OC70	12p
2N4549	50p	BD132	75p	OC72	25p
2S301	50p	BD153	62p	OC72	25p
2S302	50p	BD156	57p	OC73	30p
2S303	60p	BDY104L-25	OC74	30p	
2S304	75p	BDY104L-25	OC75	30p	
40250	50p	BDY121-50	OC76	25p	
40361	50p	BDY121-50	OC77	40p	
40362	55p	BDY121-50	OC81	25p	
AA30	10p	BDV621-25	OC82	25p	
AA42	15p	BDV621-25	OC83	25p	
AAZ13	12p	BF116	25p	OC84	25p
AAZ17	10p	BF152	30p	OC139	25p
AC107	37p	BF154	40p	OC140	37p
AC126	25p	BF158	30p	OC141	62p
AC127	25p	BF167	25p	OC170	25p
AC128	25p	BF167	25p	OC171	30p
AC176	25p	BF170	35p	OC200	40p
AC187	30p	BF173	30p	OC201	70p
AC188	30p	BF174	40p	OC202	30p
ACY17	30p	BF175	40p	OC203	40p
ACY18	25p	BF179	40p	OC204	40p
ACY19	25p	BF180	35p	OC205	75p
ACY20	20p	BF181	25p	OC206	30p
ACY21	20p	BF182	30p	OC207	80p
ACY22	10p	BF184	20p	OC217	97p
ACY29	50p	BF185	20p	ORP19	50p
ACY40	15p	BF194	17p	ORP40	40p
AD149	50p	BF195	15p	ORP40	40p
AD149	50p	BF196	15p	TIP29A	50p
AD161	37p	BF197	15p	TIP30A	60p
AD162	37p	BF200	37p	TP31A	62p
AF114	25p	BF274	37p	TP32A	75p
AF115	25p	BFX13	25p	TP33A	75p
AF116	25p	BFX29	25p	TP33A	75p
AF117	25p	BFX30	25p	TP33A	75p
AF118	25p	BFX37	32p	TP33A	75p
AF124	25p	BFX84	25p	TP33A	75p
AF125	20p	BFX85	35p	TP33A	75p
AF126	17p	BFX86	25p	TP33A	75p
AF127	17p	BFX87	25p	TP33A	75p
AF139	30p	BFX88	20p	ZTX107	15p
AF178	47p	BFX18	30p	ZTX108	15p
AF179	65p	BFX20	22p	ZTX300	12p
AF180	52p	BFY51	20p	ZTX301	15p
AF181	42p	BFY52	22p	ZTX302	20p
AF182	40p	BFY53	17p	ZTX303	20p
AF239	40p	BFY90	65p	ZTX304	25p
ASY26	25p	BXS20	17p	ZTX500	20p
ASY27	32p	BXS21	20p	ZTX501	25p
ASY28	26p	BXS76	15p	ZTX502	25p
ASY29	30p	BXS76	15p	ZTX503	25p
ASY67	47p	BY195A	15p	ZTX504	40p
ASZ21	42p	BY100	15p	ZTX531	30p
BA116	7p	BY126	15p		
BA164	10p	BY127	20p		
BAX13	6p	BAX12	35p		
BAX16	6p	BAX12	35p		
BAY31	7p	BYZ11	35p		
BAY38	17p	BYZ12	30p		

HENRY'S LOW COST INTEGRATED CIRCUITS

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS

Part No	Ceramic	Description	1-24	25-99	100	250+
7400		Quadruple 2-input NAND Gate	23p	20p	15p	13p
7401		Quadruple 2-input Positive NAND Gate (with open collector output)	23p	20p	15p	13p
7402		Quadruple 2-input Positive NOR Gates	23p	20p	15p	13p
7403		Quadruple 2-input Positive NAND Gates (with open collector output)	23p	20p	15p	13p
7404		Hex Inverters	23p	20p	15p	13p
7405		Hex Inverter with open collector	23p	20p	15p	13p
7410		Triple 3-input Positive NAND Gates	23p	20p	15p	13p
7413		Dual 4-input Schmitt Trigger	35p	32p	22p	25p
7430		Dual 4-input Positive NAND Gates	23p	20p	15p	13p
7430		8-input Positive NAND Gates	23p	20p	15p	13p
7440		Dual 4-input Positive NAND Buffers	23p	20p	15p	13p
7441		BOD to decimal nixie driver	87p	77p	60p	60p
7442		BOD to decimal decoder (4-10 lines, 1 of 10)	87p	77p	60p	60p
7447		BCD-Seven-Segment Decoder/Drivers (15-V Output)	£1.40	£1.30	£1.20	£1.05
7450		Expandable dual 2-input AND-OR-INVERT	23p	20p	15p	13p
7451		Dual 3-wide 2-input AND-OR-INVERT GATES	23p	20p	15p	13p
7452		Quad 2-input Expandable AND-OR-INVERT	23p	20p	15p	13p
7454		4-wide 2-input AND-OR-INVERT GATES	23p	20p	15p	13p
7460		Dual 4-input Expander	23p	20p	15p	13p
7470		Single-phase J-K Flip-Flop	35p	32p	22p	25p
7472		Master-slave J-K Flip-Flop	35p	32p	22p	25p
7473		Dual Master-slave J-K Flip-Flop	43p	40p	37p	35p
7474		Dual 0 type Flip-Flop	43p	40p	37p	35p
7475		Quad latch	47p	45p	43p	40p
7476		Dual J-K with pre-set and clear	47p	45p	43p	40p
7480		Gated Full Adders	87p	77p	67p	60p
7481		16-bit read/write memory	£1.90	£1.25	£1.15	£1.00
7482		2-bit Binary Full Adders	87p	77p	67p	60p
7483		Quad Full Adder	87p	77p	67p	60p
7486		Quad 2 input Exclusive OR Gates	80p	70p	60p	60p
7490		BCD decade counter	87p	77p	67p	60p
7491		8-bit Shift Registers	£1.21	£1.00	£0.90	£0.75
7492		Divide-by-Twelve Counters	87p	77p	67p	60p
7493		4-bit Binary Counters	87p	77p	67p	60p
7494		Dual entry 4-bit shift register	87p	77p	67p	60p
7495		4-bit up-down shift register	87p	77p	67p	60p
7496		8-bit Parallel in parallel out Shift Register	87p	77p	67p	60p
74100		8-bit Bistable Latches	£1.75	£1.65	£1.55	£1.35
74118		Hex Set-Reset Latches	£1.30	£1.20	£1.00	85p
74121		Monostable Multivibrators	87p	77p	67p	60p
74141		BCD-to-Decimal Decoder/Driver	87p	77p	67p	60p
74145		BCD-to-Decimal Decoder/Drivers	£1.60	£1.70	£1.80	£1.15
74151		8-bit Data Selectors (with Strobes)	£1.40	£1.30	£1.20	£1.05
74153		Dual 4-Line-to-2-Line Data Selectors/Multiplexers	£1.40	£1.30	£1.20	£1.05
74191		Binary Counter reversible	£3.80	£3.25	£3.00	£2.50

Devices may be mixed to qualify for quantity price.
Data available for above prices in booklet form, price 10p. (Ref. No. 30).
Larger quantity prices Extn. 4. Dual Inline 14 Pin Socket 30p each 16 Pin 35p each.

SEMI-CONDUCTORS

LOOK AT THESE PRICES FOR QUANTITIES FROM STOCK

AF114 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	AF115 Mullard 25p 25 + 20p 100 + 17p 500 + 15p
AF116 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	AF117 Mullard 25p 25 + 20p 100 + 17p 500 + 15p
2N3055 75p Mullard 115Watt Silicon Power 100 + 25p 500 + 20p 1000 + 19p	2N3819 Texas 35p 25 + 30p 100 + 25p 500 + 20p 1000 + 19p
BFY90 65p 100 MC/S 25 + 60p 100 + 55p 500 + 50p	2N2646 40p Motorola Unijunction 25 + 35p 100 + 30p 500 + 25p
AF139 30p Siemens V.H.F. 100 + 25p 200 + 22p 500 + 19p	AF186 40p Mullard V.H.F. 25 + 35p 100 + 30p 500 + 25p
OC170 Mullard 25p 25 + 21p 100 + 17p 500 + 15p	BYZ13 25p Mullard 6a 200V 25 + 20p 100 + 17p 500 + 15p
OC171 Mullard 30p 25 + 21p 100 + 22p	BC107, BC108, BC109 12p each I.T.T. Planars 25 + 11p 100 + 10p 500 + 8p
BY127 Mullard 20p 1000V amp Plastic 25 + 17p 100 + 15p 500 + 13p	OC71 97p Mullard Photo 25 + 85p 100 + 80p 500 + 75p
BC113 SGS 15p 25 + 13p 100 + 11p 500 + 9p	OC28 62p Mullard Power 25 + 55p 100 + 50p 500 + 42p
OA202 10p SILICON Diodes 25 + 8p 100 + 6p 500 + 5p 1000 + 4p	OC42 Mullard 30p 25 + 25p 100 + 23p 500 + 21p 1000 + 18p
OC45 Mullard 15p 25 + 13p 100 + 12p 500 + 10p 1000 + 8p	OC71 Mullard 15p 25 + 12p 100 + 10p 500 + 8p
OC75 Mullard 25p 25 + 21p 100 + 17p 500 + 15p 1000 + 13p	ORP12 Mullard 50p 25 + 45p 100 + 42p 500 + 40p
OC20 97p Mullard 100V 25 + 85p 100 + 80p 500 + 75p	2N930 25p 25 + 23p 100 + 20p 500 + 17p 1000 + 15p
OC44 Mullard 17p 25 + 15p 100 + 13p 500 + 11p 1000 + 10p	OC72 Mullard 25p 25 + 20p 100 + 17p 500 + 15p 1000 + 13p
OC139 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	OC83 25p 25 + 20p 100 + 17p 500 + 15p
OC81 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	OC84 25p 25 + 20p 100 + 17p 500 + 15p
	AF239 42p 25 + 35p 100 + 30p 500 + 25p

SILICON RECTIFIERS

1 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS

Type P.I.V. 1-49 50+ 100+ 500+ 1000+

IN4001	50	8p	5p	4p
IN4002	100	9p	7p	5p
IN4003	200	10p	7p	5p
IN4004	400	10p	8p	7p
IN4005	600	12p	10p	7p
IN4006	800	15p	14p	12p
IN4007	1000	20p	16p	12p

1.5 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS

Type P.I.V. 1-49 50+ 100+ 500+ 1000+

PL4001	50	10p	9p	7p
PL4002	100	11p	9p	7p
PL4003	200	12p	11p	9p
PL4004	400	12p	11p	9p
PL4005	600	15p	13p	11p
PL4006	800	17p	15p	12p
PL4007	1000	20p	17p	15p

3 AMP PLASTIC WIRE ENDED RECTIFIERS

Type P.I.V. 1-49 50+ 100+ 500+ 1000+

Fig. 4: Wiring and layout of the audio amplifier board, $3\frac{1}{2} \times 2$ in.

up as in Fig. 2, keeping all leads in this section short and direct. The metal flanged plate is the positive or chassis return, a tag being put under one fixing nut. Solder a black flexible lead to R3.


Tr1 is suspended by its wire ends about level with the top of L3 while trimmer TC2 is mounted on the paxolin by its tags.

IF Board Wiring. Fig. 3 shows both top and bottom of this panel. Holes are drilled so that the pins and can fixings tags on the i.f.t.'s are placed as shown. A central hole is required under the i.f.t.'s for trimming.

Two $\frac{1}{2}$ in. 6BA bolts secure the tags MC. Later, extra nuts are put on these bolts, which pass through the metal case, forming the positive or chassis return.

Guide lines are scribed on the paxolin and holes for resistors and other leads made with a $\frac{1}{16}$ in. or $\frac{5}{64}$ in. drill. The i.f.t.'s, resistors and capacitors are then inserted. Note the polarity of C8 and D1. The board is then turned over, and wired as shown. Use insulated sleeving on all leads which cross. Joints are kept against the board so that they will not touch the metal of the case.

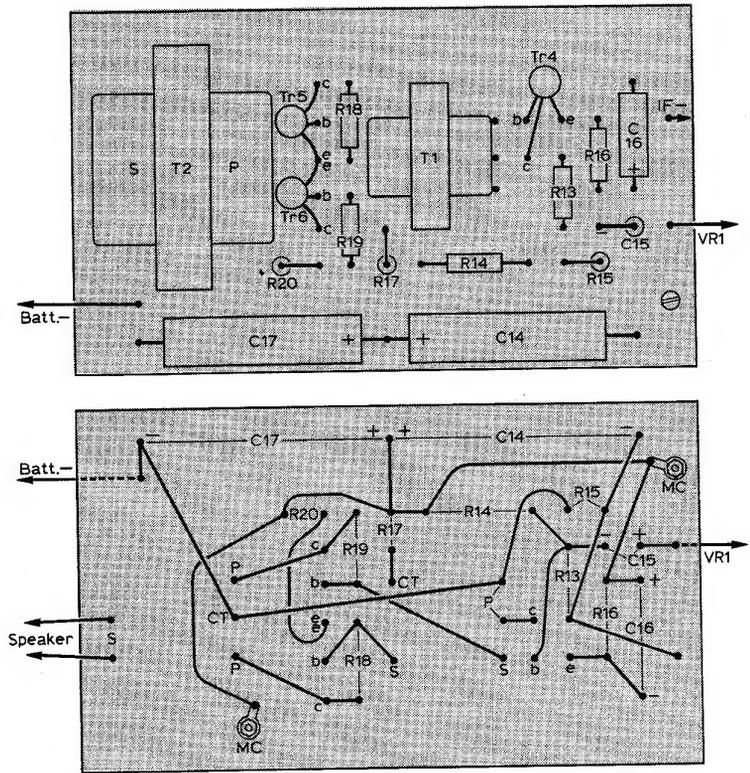Before inserting the transistors, it is helpful to put pieces of 1mm coloured sleeving about $\frac{3}{8}$ in. to



$\frac{1}{2}$ in. long on the leads—blue for emitter, green for base, and orange for collector, leaving the shield wires bare. Then position the leads as shown in Fig. 3, solder them and snip off excess.


For easy identification of external connections, solder on a green lead for pin 2 of i.f.t.1, a black lead for the negative line, and a white lead from D1 positive.

Audio Amplifier Wiring. Fig. 4 shows both sides of the a.f. amplifier. Tags MC are tightly bolted as before, for chassis return points. All the capacitors are electrolytic, so have to be placed as shown.

T1 is the driver transformer but note that various makers place the tags in different positions. In Figs. 1 and 4, P-P are the primary, S-S the secondary, and CT the secondary centre tap. These connections must be correct for the actual transformer used.

T2 is the output transformer, with primary connections P-P and primary centre tap CT. Two thin flexible leads are soldered to the secondary tags S which run to the speaker (or phones) jack.

Fig. 5: Disposition of the three boards inside the cabinet.

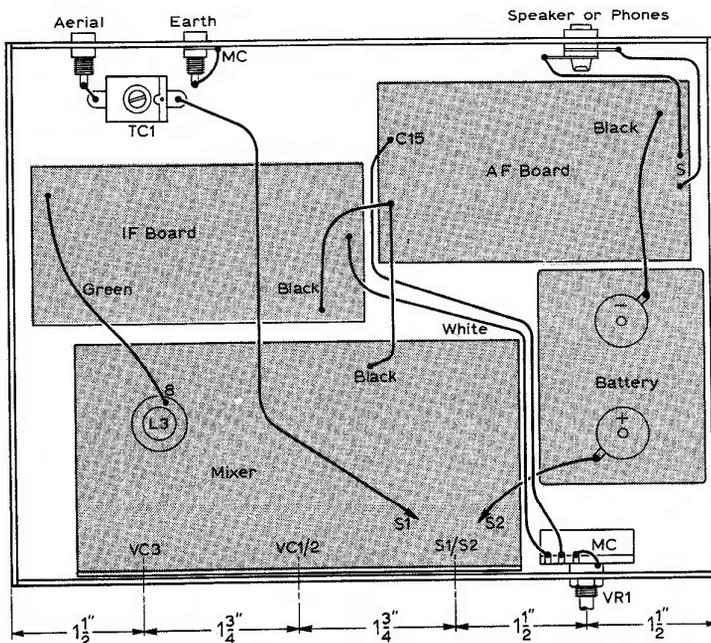

★ components list

Resistors:

R1 10kΩ	R6 1kΩ	R11 4.7kΩ	R16 680Ω
R2 2.7kΩ	R7 68kΩ	R12 1kΩ	R17 82Ω*
R3 1kΩ	R8 8.2kΩ	R13 82kΩ	R18 10kΩ*
R4 470Ω	R9 680Ω	R14 22kΩ	R19 10kΩ*
R5 39Ω	R10 22kΩ	R15 470Ω	R20 4.7Ω

All ½W 10% except those marked * 5%
VR1 5kΩ potentiometer, log.

Capacitors:

C1 22pF SM	C7 330pF SM	C13 0.01μF tub.
C2 470pF SM	C8 10μF 6V	C14 100μF 12V
C3 0.01μF tub	C9 0.04μF tub.	C15 6μF 6V
C4 0.01μF tub	C10 0.5μF tub.	C16 60μF 6V
C5 0.01μF tub	C11 0.04μF tub.	C17 100μF 12V
C6 22pF SM	C12 0.04μF tub.	

VC1/2 365 + 365pF 2-gang Type OO slow motion
(Jackson)
VC3 50pF miniature airspaced variable (Jackson)
TC1 60pF trimmer TC2 60pF trimmer

Inductors:

L1 Range 5 'Blue'	} Denco miniature type for transistors.
L2 Range 4 'Blue'	
L3 Range 4 'Red'	
IFT1 Type 18/465	} Denco
IFT2 Type 18/465	
IFT3 Type 14/465	

Semiconductors:

Tr1 OC170	Tr4 OC81D
Tr2 AF117	Tr5 OC81
Tr3 AF117	Tr6 OC81
D1 OA81	

Chassis:

Universal Chassis side 5 × 2in.
Universal Chassis members:—
2 off 8 × 4in. CU56A
2 off 6 × 4in. CU41B
2 off 8 × 6in. plates CU178
All from Home Radio

Miscellaneous:

T1, OC81D/2 × OC81 driver transformer
T2, 2 × OC81/3Ω speaker transformer
S1/2, 2 pole, 3-way, wafer switch.
Paxolin or 'eyelet' boards, 5 × 2½in, 3½ × 2in,
3½ × 1½in. Knobs, 1-off type KN84F and 3-off type
KN84D (Home Radio). Feet 4-off type Z146 (Home
Radio).

Transistor leads can be identified as mentioned, or sleeving put on the wires to avoid possible short circuits.

Solder on a black flexible lead, fitted with a battery negative clip. Leave a short wire projecting at the point IF negative, and connect an insulated wire from C15 positive.

FINAL ASSEMBLY

If preferred, the mixer, i.f. and a.f. sections can be wired together and tested before fitting them in the case. The positive circuits must then be temporarily joined with wire.

The case front is a 4 x 8in. flanged member and three holes, for VR1, switch and VC3 are made 1½in. from the bottom edge. The hole for VC1/2 is 2in. from this edge.

The fixing nuts of the switch and VC3 are then removed, so that the bushes can pass through the case front. If necessary, put a washer or two on each bush, then fit the mixer assembly to the case front, and lock it in position with the nuts of VC3 and the switch.

The bottom is then fixed. It was placed inside the flanges, but could be outside. Take a piece of paper of the same size, and mark the positions of L1, L2 and L3. Also the fixing bolts of i.f. and a.f. boards, and the central holes under the i.f.t.'s. Drill or punch these holes, which are to allow alignment when all boards are in position.

The bottom is then bolted to the bottom flange of the front, the sides and back of the case being added later.

The i.f. and a.f. panels are fixed as in Fig. 5 by using extra nuts and lock nuts on the ½in. bolts. There should be plenty of clearance, but if any joints are too near the metal, cut pieces of card to match the panels, and fit these under the i.f. and a.f. boards.

The green lead from i.f.t.1 is then cut and soldered to pin 8 of L3. VR1 is fitted to the front, and connected to positive line, D1 and C15, and other connections are made as shown.


When the case is to be completed, this is done by adding the two sides, then the back. All are bolted together with the flanges provided.

IF ALIGNMENT

The i.f.t.'s listed are supplied pre-aligned. This means that signals should be obtained through the i.f. amplifier at good strength. If no signals are obtained, it is better to look for a wiring error or other fault, rather than move the cores of the i.f.t.'s.

When a signal is present, carefully adjust each core for best results. A screwdriver blade can easily break this type of core, and should not be used. If a proper tool is not available, it is recommended that one be obtained from the i.f.t. maker—the "Denco" TT5 tool is suitable.

Signals for i.f. alignment may be from a signal generator, input being to the base of Tr1, or from a transmission, correctly tuned in. If adjustment is by ear, use a signal which is quite weak even with VR1 near maximum. Alternatively, set a 10kΩ/V or other high-resistance meter at its 10V range, and clip it across VR1, negative to chassis. Alignment is then for maximum voltage reading. Only slight re-adjustment

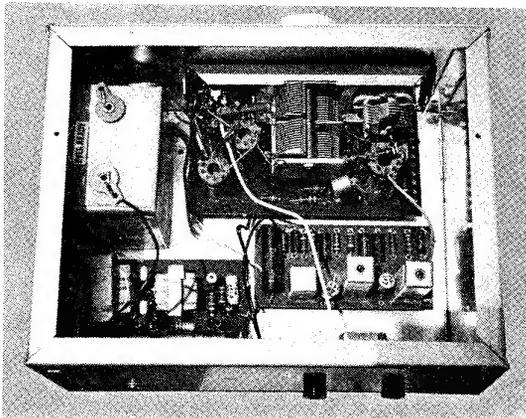

—continued on page 418

SERVICING

AN INTRODUCTION TO FAULT-FINDING

PART 5

H. W. HELLYER

A KNOWLEDGE OF JUST HOW STEREO SIGNALS ARE GENERATED AT THE TRANSMITTER AND DECODED AT THE RECEIVER IS ESSENTIAL TO AN UNDERSTANDING OF THE STEPS INVOLVED IN THE ALIGNMENT OF STEREO RECEIVERS

WHETHER or not you live in an area of the country served by a stereo transmitter, your interest in this series of articles must also encompass stereo broadcasting. Quite apart from the hideous interference that spoils a.m. radio on the "broadcast" bands, especially during peak hours, the restricted frequency response that results from a necessarily narrow bandwidth takes away any pretension to quality reception. With f.m. broadcasting, we can achieve a wider bandwidth and more nearly approach hi-fi—whatever that may mean.

FM MULTIPLEX— THEORY AND PRACTICE

Nowadays, very few mono tape recorders and hardly any mono record players are to be found in the shops. Stereo is the order of the day, even in a cheap radiogram where the loudspeaker placement quite obliterates any good effect channel separation

may have given! Stereo radio is the only way onwards.

Here is where that ugly word "compatibility" takes the stage. So that users of the existing mono system could continue to listen; so that stereo broadcasts could be "slotted in" to the current framework of programmes without robbing some poor listener of his entertainment, a system had to be devised whereby the stereo signals were combined in some way with the mono signals and some form of switched selector devised to differentiate between them.

Fig. 1 shows how this is done in the system employed in this country. Here, we have the encoder at the transmitter which takes the stereo signal, applies it to an electronic adder and subtractor, and produces a left+right and a left-right signal. The difference signal, L-R is the vital stereo information. The L+R signal gives the mono listener all he needs (with, it must be admitted, a slight degradation of the signal-to-noise ratio... but this is seldom mentioned).

The L-R signal modulates a sub carrier, the frequency of which is 38kHz. This is obtained by doubling the 19 kHz pilot tone output of a high stability oscillator. The trick here is to amplitude modulate the 38kHz sub-carrier at the transmitter. The modulator suppresses the sub-carrier so all that comes out, for application to the adder, is the upper and lower sidebands of the signal.

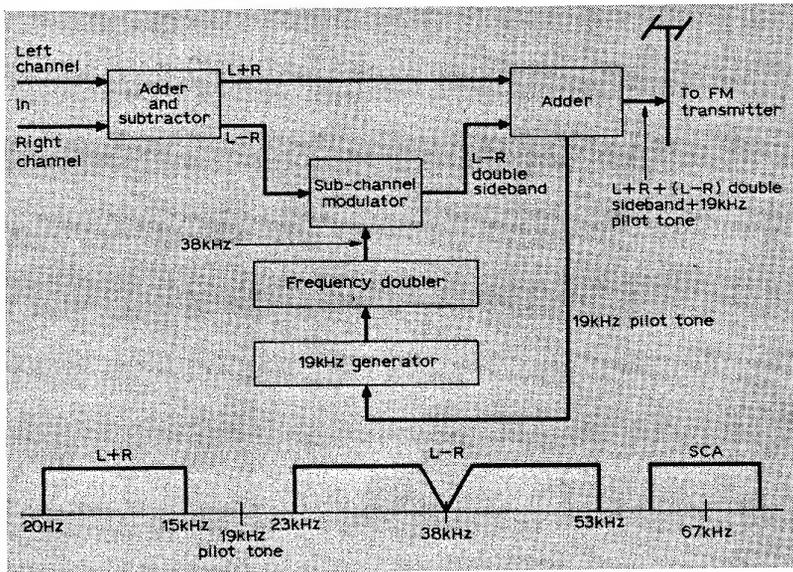


Fig. 1. (top) illustrates the number of stages involved in the formation of a stereo signal at the transmitter while Fig. 2 (below) shows the frequency spectrum of a multiplex signal.

Also applied to the adder is the untreated L+R signal, and a 19kHz pilot tone, which is to be used as a reference at the receiver. The signal spectrum at the transmitter, Fig. 2, helps to make this plain. This is the true multiplex signal. Suppression of the sub-carrier has given the two signals, L+R and L-R, 90% of the 100% modulation, the remaining ten per cent being taken up by the pilot tone.

It should be remembered that when L+R is maximum L-R is minimum and vice versa; in this way, the best use is made of the modulation "space". If the sub-carrier had been left in, the available "space" would have been reduced to 50%.

COMPATABILITY

Fig. 2 shows that the ordinary mono information is still available up to quite a high frequency, around 15kHz. The useful sidebands of the 38kHz sub-carrier extend to well over 50kHz. So a flat frequency response is needed throughout the propagation chain. One aspect not always considered is the need for good phase relationship. As the L+R and L-R signals depend on cancellation (in effect, the +L and -L components must cancel in the right-hand channel and the R components in the left-hand channel) the phase relationships of the various signals must stay correct. One reason, you may argue, for a good aerial, and not just any old piece of wet string that happens to receive a signal. As we shall see, there are other reasons, too.

From the adder, this composite signal is fed to the transmitter and is used to frequency modulate it. It is this f.m. signal we receive, in the 88-97MHz section of the f.m. band.

Without going too deeply into this matter, we can state that there are two completely different ways of achieving this stereo signal and more than

two ways of decoding it. Referring again to Fig. 1, we note that an electronic "mixing" system has been used to encode the stereo signal. A "switching" system could have been used as easily. Similarly, the decoder, in the receiver, can be the matrix type or the simpler switching decoder which is more often used.

SERVICING PROBLEMS

Tuners are undergoing some revolutionary changes just at present. Gordon King has said, and will be saying, a few things about varicaps, and tuning devices. From the servicing point of view, the

problems that arise are the same as in other tuners: component failures, displaced components, causing changes in inductance/capacity, where leads and supports are significant at the frequencies in use; plus the inevitable bogey of mistuning. Plus—it must be said—aerial mismatching, inadequate aeriels and troubles with the feeder and its connections.

Through the i.f. channel, the main consideration is to achieve the necessary bandwidth and broad tuning is the order of the day. Attempts to "peak up" the i.f. channel of an f.m. receiver will inevitably result in an impaired response. IC's are being widely used in modern i.f. strips, giving very high gain. Tuning problems remain much the same, but are practically lessened by there being, in general, less tuned circuits to align. Ceramic filters, too, have made our life a little easier in the service department, refusing to go off tune, except when externally abused.

THE DECODER

So let us get on to the decoder. This can either be the sum-and-difference type of Fig. 3a or the switching type of Fig. 3b. In the first, a mirror image of the encoder at the transmitter, three filters split the signal into its components. The first selects the 19kHz pilot tone, which is passed on to the frequency doubler stage. The second selects the mono L+R signal and presents it to the matrix. The L-R signal is selected by the third filter and passed to the balanced demodulator. To the same point the regenerated 38kHz sub-carrier is also fed. Addition and subtraction in the matrix now produces replicas of the original left and right signals.

The switched type of decoder is more common (less complicated!) and so will concern us more. Fig. 3b shows its block diagram. Multiplexed signals from

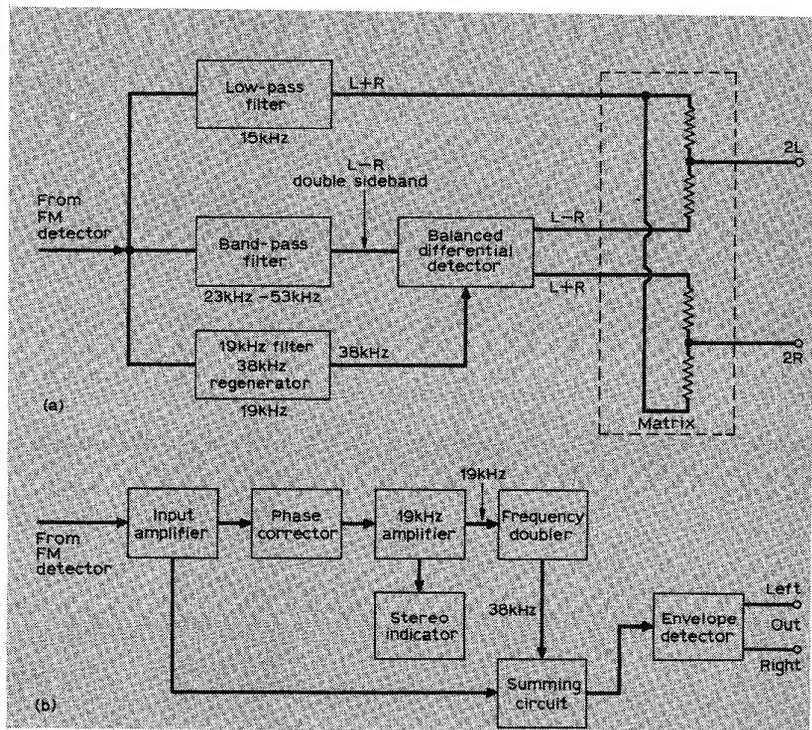


Fig. 3 (a) gives the requirements of a matrix decoder, the more common switching decoder being depicted in Fig. 3 (b).

the f.m. detector are fed to an input amplifier. From the output is selected the 19kHz pilot tone and the stereo information. No filters are necessary at the input to this amplifier, revealing at least one reason why the matrix decoder is out of favour in this country.

From the input amplifier, the pilot tone is phase corrected and amplified, then doubled in frequency to produce the 38kHz sub-carrier. An envelope detector is used, as with this method the left channel information is amplitude modulated on one side of the 38kHz carrier and the right channel information modulated on the other side. Alternate demodulation at a repetition rate of 38kHz gives a resultant audio output to each channel.

After demodulation, de-emphasis is applied. That bald statement is the reason why so many attempts at adding a decoder to a mono f.m. receiver to convert it to stereo failed dismally. Quite apart from the impaired S/N ratio—a factor which makes it vital to first obtain as good a mono signal as possible—the de-emphasis network which is fitted to counteract the high-frequency boost given to the signal at the transmitter has its effect as soon as we attempt to convert. De-emphasis is usually incorporated in the decoder design. The idea of this system is to obtain the best possible audio signal and also to attenuate residual sub-carrier components.

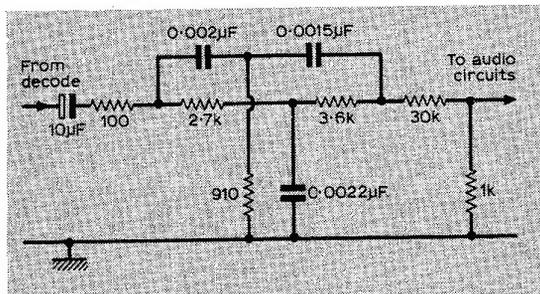


Fig. 4. Practical circuit of a 38kHz notch filter.

Despite this attenuation, some additional filtering may be needed if the stereo broadcast signals are to be applied to a tape recorder. Fig. 4 shows a notch filter suitable for removing all trace of the 38kHz signal from a tape recorder input. Many tape recorder manufacturers, particularly Continental ones, well used to f.m. reception, have already fitted filters, usually LC types in screened compartments near the input sockets. The circuit of Fig. 4 is easily constructed for experimental purposes by the person who adds his own decoder. It can give a fair measure of de-emphasis as well, and should be fitted between the decoder output and the amplifier input.

DECODER CARE

Whenever any work is done at or around the decoder, connecting wires must be kept as short as possible. High frequency attenuation is easily caused by careless wiring, and instability by shoddy component placing. If a stereo socket is to be fitted, it should be mounted for efficiency rather than for convenience. There is always a temptation to cut corners—sometimes with costly results.

An example is the omission or removal of the

“cross-diodes” in a decoder circuit. Good stereo separation is still obtained; the signal is received clearly; there is no obvious interference. But more than once damage to output transistors has been caused, and it is possible that tweeters could be impaired in a hi-fi system, simply because the removal or failure of this circuit allows the 38kHz sub-carrier to break through at full strength. We cannot hear it, but we shall certainly hear its effect!

One item noted on the block diagram of our decoder is the stereo beacon light. This is latched to the 19kHz amplifier and should light only when a pilot tone is present. Unfortunately, as any user of stereo receivers will know, it more often lights with every blip of noise.

OTHER FACTORS

Other factors that are special to the f.m. receiver, and to stereo receivers particularly, are the automatic frequency control circuits, the muting circuits, and various devices to aid “capture.” Some examples of these can be seen in Fig. 9 of Part 2 by Gordon King. (Page 136, PW, June 1971). See also the description of the a.f.c. circuits, on page 153 of the same issue.

Reference must also be made to my last part, where we began by treating the stereo receiver as we would a normal mono receiver, aligning for the correct response and checking the i.f. with a marker. The basic method is to connect the instruments as shown in my Fig. 6 of the last part, for normal f.m. alignment.

For more detailed work, a specially designed stereo generator is employed.

TEST EQUIPMENT

An example of such an instrument is the Heathkit IG-37, costing £47.35 as a kit. This instrument provides a composite stereo signal plus a pilot tone and gives a phase test signal (i.e. channels added) for sub-carrier transformer adjustment. A variable r.f. oscillator signal is available, having an adjustable sweep width around a nominal 100MHz frequency. A mono f.m. signal can be obtained and this is modulated by any one of three modulation frequencies—giving a rapid “spot check facility.”

In addition to this, four marker frequencies are supplied for r.f. alignment checks and two s.c.a. (subsidiary communications authorisation) frequencies for adjustment of filters. To the workshop that has to undertake regular checks of f.m. receivers, such an instrument can be invaluable.

MULTIPLEX ALIGNMENT

With the proviso that the service manual for the receiver being aligned should be consulted initially, we now go on to detailed general steps of the alignment procedure of a typical stereo receiver, using the IG-37.

IF alignment: connect output of the generator, “RF Out,” to the aerial terminals of the receiver. Connect the input of the last limiter circuit of the receiver to the vertical input of an oscilloscope, using a demodulator probe. Loosely couple the “IF Marker” of the generator to the first i.f. stage of the receiver.

This produces a 10.7MHz marker signal. Adjust the oscilloscope for a 60Hz line sweep. Use the "Mono/FM" facility with audio modulation and tune the generator to approximately 100MHz. Then switch to "RF Sweep" input, with "IF marker." Produce a response curve (Fig. 5a) and adjust the successive i.f. stages for best response.

The next step entails comparison of curves and to do this we first need to view the generator output as applied to the oscilloscope and then beat in the signal from the receiver. To do this, first "kill" the tuner section, remove the vertical input of the oscilloscope from the receiver limiter circuit and connect it to the output of the detector stage.

Disconnect the i.f. marker. Connect the composite signal from the generator to the horizontal input of the oscilloscope, now set for external sweep, i.e. trigger the scope with the generator. With the tuner in action again, a curve as in Fig. 5b should appear. The detector coil can now be adjusted to approach this. Always refer to the maker's manual, if this is available.

Recheck the front end alignment using the r.f. marker signals at 90.95, 96.3, 101.65 and 107MHz adjusting the r.f. and oscillator coils for good response, and accurate tuning.

Stereo alignment: this needs a step-by-step operation, according to the type of circuit in use. In the IG-37 manual, these basic circuits are divided into four types (1) several 19kHz amplifier stages followed by a doubler; (2) a 19kHz oscillator circuit and doubler; (3) 19kHz amplifier, doubler and 38kHz oscillator, and (4) 19kHz amplifier and 38kHz oscillator. It is necessary to identify the circuit before proceeding, but some tests are common to all.

First set "Pilot Level" to minimum and function level fully clockwise, switch frequency to SCA and filter switch to 65 or 67kHz to suit the filter of the receiver, set function switch to "Audio" and "Mono/FM," adjust the r.f. frequency adjustment to get a signal in a clear spot of the tuner band somewhere

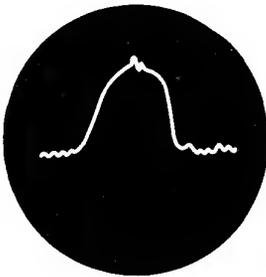


Fig. 5 (a) Response curve of i.f. channel of stereo receiver with superimposed 10.7MHz marker signal.

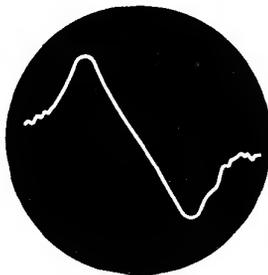


Fig. 5 (b) Response curve required at the output of the detector stage.

near 100MHz. Make sure the phase control is central. If a separation control is provided on the generator, centralise this. Switch the a.f.c. off, and also, if available, the squelch circuit. Connect generator to aerial terminals. Switch on both generator and receiver and allow to warm up for 10 minutes.

If the set has an oscillator type of circuit, this should be "killed" for the SCA filter adjustment. If the filter is a complex or stagger-tuned one, the tuning will have to be done according to the maker's instructions. When feeding in the signal to the receiver keep the level such that the scope gives a clear trace—i.e., do not overdrive.

After this, proceed according to the type of circuit; the differences being the positioning of the oscilloscope, setting of the pilot level control and synchronisation of signals (19kHz and 38kHz) as against peaking.

Taking the example of our Fig 3, i.e., 19kHz amplifier and doubler, we first peak both 19kHz and 38kHz circuits. The oscilloscope is connected to the output of the 38kHz doubler, pilot level turned to maximum (with regard to overloading), function switch set to Left channel, frequency switch to 1000Hz and the relative coils, including any stereo indicator coils, peaked for maximum indication.

Next, an operation common to all types, to adjust the phase of the reinserted carrier to the same phase as the sub-carrier. The oscilloscope is now connected to the left channel output, other settings are the same, and the phase is adjusted for maximum audio output. Normally, this operation requires the alteration of a 19kHz or 38kHz coil, and will be special to the particular circuit. Again, we need to refer to the maker's instructions, or trust our experience. No general guidance can be given without being misleading.

If a separation control is fitted, now is the time to adjust it. With the input to the left channel, we now read off the output from the right channel and adjust the control for minimum. (This operation can be done with the aid of the B.B.C.'s late night test signals.)

Last step is adjustment of the 19kHz and 38kHz traps. Here, the pilot level control is turned to minimum, the function switch is again set to "Mono" and the generator frequency to the appropriate 19 to 38kHz. The oscilloscope reads off the appropriate channel output and adjustments are made for a minimum. Any automatic switching circuit that is fitted must here be locked according to the maker's instructions.

Now and again we come across circuitry that does not allow for easy adjustment. In these cases, always follow the maker's instructions explicitly. It is unfortunate that this has to be said so often, but circuits vary widely, as Gordon King has shown and which I hope my previous notes may have underlined. Something of the same conditions has to be met with audio equipment generally and with tape recorder circuits in particular, as we shall show in succeeding articles.

END OF PART FIVE.

NEXT MONTH WE RETURN TO CO-AUTHOR GORDON KING WHO WILL DISCUSS THE DESIGN, CHARACTERISTICS AND PROBLEMS OF THE AUDIO SIDE OF EQUIPMENT BOTH VALVED AND SOLID-STATE



IN NEXT MONTH'S

PRACTICAL WIRELESS

EXTRA INSIDE

**8 PAGE SUPPLEMENT
SMALL
WORKSHOP
TOOLS**

We have seen some 'bird's-nests' in our time, purporting to be copies of our various projects! While ingenuity in using a kitchen knife as a screwdriver-cum-wire-stripper might be commendable in an emergency we feel that the serious constructor would prefer to buy the proper tools for the job. This supplement provides plenty of information on all kinds of small tools and accessories thus enabling readers to assess their requirements before spending their money.

plus

**Wall Chart
CIRCUIT
BUILDING
BRICKS**

The free wall chart is complementary to a new series of articles especially written for the beginner that starts in next month's issue of Practical Wireless.

This series takes the beginner step-by-step through the theory and practice of transistor circuitry. Transistor parameters, operating conditions, transistor symbols, r.f., i.f. and a.f. circuits are covered together with output stage protection and power supply stabilisation.

Start reading this comprehensive series next month!

**ALL IN THE OCTOBER ISSUE
ON SALE SEPTEMBER 10th**

MODULAR AUDIO MIXING SYSTEM

Consists of matching pre-amplifiers, tone control unit and line amplifier, etc., from which to build almost any audio signal mixing system from a simple three or four channel mono mixer for tape recording to a multi-input stereo signal mixer for discotheque or public address and music amplifiers.


The pre-amplifiers, seven in all, cater for: Microphones with built-in transformers, high and low impedance microphones, magnetic, ceramic and crystal pick-up cartridges and guitar pre-amplifier (medium to high Z).

Each signal pre-amp has a built-in gain control and provides a 100mV output signal to match the bass and treble unit or the line amplifier unit.

The line amplifier provides up to 1 volt r.m.s. signal output suitable for driving power output modules direct, or any large external amplifier or a tape recorder.

The system allows for the inclusion of line signal level inputs, from about 200mV to over 1 volt, which do not require pre-amplifiers and provision has been made for built-in VU meters and a suitable mains power supply. The system can be run from batteries for portable use.

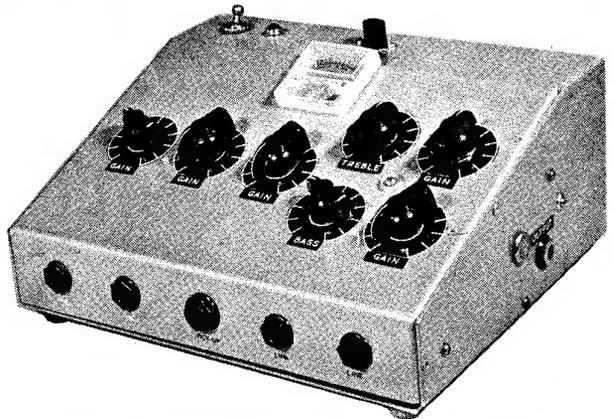The performance of the pre-amplifiers, tone control unit and line amplifier are to high fidelity standards. The various pre-amps, the tone control unit and line amplifier are simple to construct and can be panel mounted with one hole fixing. Full constructional details start in the October issue.



Plus many other constructional articles and all the regular features. Be certain not to miss the next issue, price 20p.

IN the past, as far as the amateur or experimenter was concerned, there have been two main instruments for measuring frequency, the absorption wavemeter and the heterodyne frequency meter.

The absorption wavemeter has the advantage of being simple and responding to the fundamental frequency, but having a measurement accuracy limited to about 1%. It consists of an LC tuned circuit where the variable capacitor has a calibrated dial. It must be coupled to the circuit containing the frequency to be measured and when tuned to this frequency the absorption of power from the circuit may be noticed either by an effect produced in the circuit itself, or by an indicator attached to the wavemeter as shown in Fig. 1.

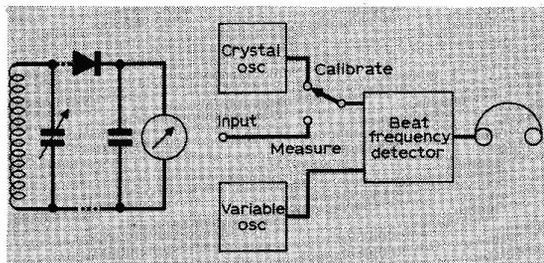


Fig. 1 (above left) Absorption wavemeter.

Fig. 2 : (above right) Heterodyne frequency meter.

The heterodyne frequency meter is a much more sophisticated instrument which is capable of accurate frequency measurement. This is limited mainly by the accuracy of its internal standard oscillator and tuning dial. It consists of an accurate crystal oscillator, a stable variable frequency oscillator, with a finely divided dial and a beat frequency detector feeding headphones, as shown in Fig. 2. The variable oscillator is calibrated against the crystal oscillator by observing the zero-beat points where the fundamental or harmonics of the crystal and variable oscillators coincide. The input signal is measured by zero-beating the variable oscillator with it and then reading off and calculating the frequency from the crystal check points nearest to that of the input signal frequency.

Because the heterodyne frequency meter will also respond to harmonics of the input frequency, reasonable care has to be taken to identify and exclude these and other spurious responses.

Frequency Measurement by Counting

An example of this method is in measuring the frequency of a heart beat. To do this, the doctor feels the patient's pulse and counts the number of pulses that occur in a fixed period of time.

The frequency of the heart beats can be stated in pulses per minute, no matter whether he counts for half a minute, one minute or ten minutes, simply by multiplying by a suitable factor.

Although electronic frequency counters have been in use professionally for many years, their construction has remained outside the range of home constructors, because of their complexity and high cost. However, the present availability of quite complex integrated circuits at extremely low prices has now made the construction of a frequency counter with digital read-out not only within the price range of

the home constructor but, in some aspects, its performance and price compares favourably with the cost of a heterodyne frequency meter available on the surplus market, such as the BC221.

Principle of Operation

An electronic frequency counter consists of a switch, to define the counting period, in series with the input to an electronic counter and associated display, as shown in Fig. 3.

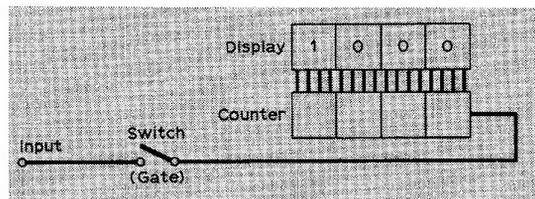


Fig. 3 : Frequency counter and display.

Assume for a moment that the input signal is a square wave of frequency 1000 Hz. If we close the switch for exactly 1 second, then in that time 1000 cycles of the input signal will have passed through the switch to the counter. If the counter has 4 decades, comprising of thousands, hundreds, tens and units, then this will have completed a count of 1000 and as the counter is connected to a numeral display, the number displayed will be 1000.

It follows then that the frequency of any input signal will be indicated directly on the display, in cycles per second (Hz), providing that it is not greater than 9999Hz, which is of course the maximum reading for 4 digits.

DIGITAL FRE

The digital frequency counter/timer offers reliability, stability and read-out convenience, which can not be achieved using alternative techniques.

Wide use is made in this design of integrated circuits. Their use considerably simplifies the design, construction and adjustment. In its present form, this instrument is capable of operating in excess of 15MHz.

JOHN THORNTON-LAWRENCE

Should we wish to make the same sort of measurement at 1MHz (1,000,000Hz) then we must arrange for the switch to be closed for exactly 1mS (1/1000 of a second). In that time 1000 cycles of the input signal will have passed through to the counter and the display will again show 1000, but this now represents 1000kHz, not Hz, (1000kHz=1MHz).

In a practical frequency counter, the switch is in the form of an electronic switch or "gate" and we call the time the switch is closed, the "gate time."

The accuracy of the frequency measurement made by counting depends mainly on the accuracy of the gate time. For instance when counting an input signal of 1MHz for a gate time of 1mS, an inaccuracy of 1μS will cause an error of one count, which in the displayed answer represents 1kHz. (There is also a counting error of one least significant digit, and this is discussed later.)

Below is a list of maximum frequency readings displayed by a 4 decade counter for different gate times.

Gate time	Maximum Reading
100μS	99·99MHz
1mS	9·999MHz
10mS	999·9kHz
100mS	99·99kHz
1 Second	9·999kHz or 9999 Hz.


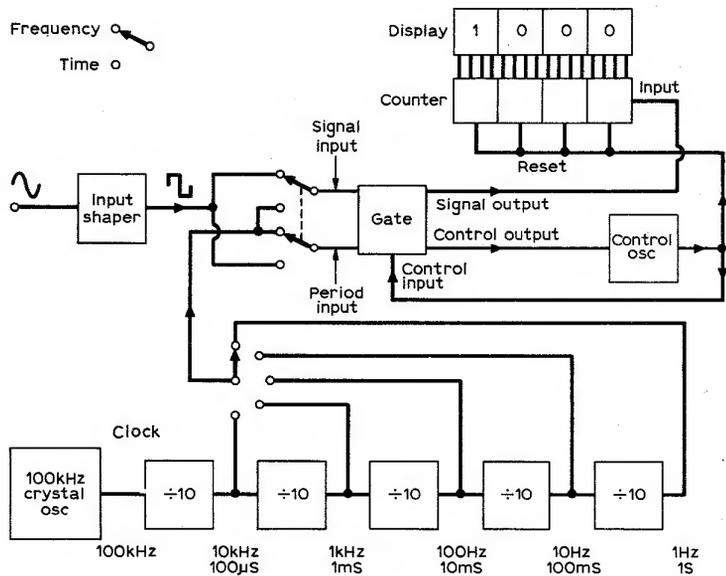


Fig. 4 : Digital frequency counter timer.

To obtain the required order of accuracy it is necessary for the gate time to be derived from a very accurate and stable oscillator. A crystal oscillator operating at 100kHz and at normal room temperature 18°C-22°C, can be expected to have a frequency stability of about 1 part in 100,000, which is equivalent to 0·01% and is more than adequate for a 4 digit read out.

FREQUENCY COUNTER/TIMER

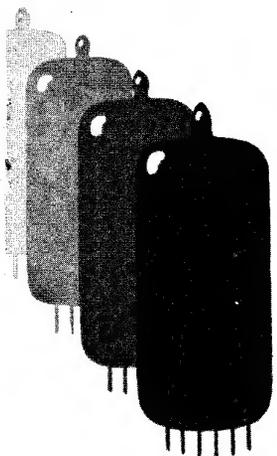

GW3JGA



The block diagram in Fig. 4 shows how various gate times may be generated and connected to the gate. In this arrangement the crystal oscillator operates at 100kHz and this frequency is divided or counted down in stages of ten giving the frequencies and gate times shown in the diagram. As this section determines the exact gate time we call it the "clock".

For example, with the clock switch in the 1 second position, the start of a 1 second square wave will open the gate (equivalent to closing the switch in Fig. 3) and the start of the next 1 second square wave will close the gate (equivalent to opening the switch), producing a 1 second gate time during which the input signal will pass through to the counter to be counted and displayed. It is assumed that prior to the gate opening, the counter is reading 0000; if this were not so then each successive reading would add to the previous one and defeat the object of the measurement.

The Control Oscillator

To ensure that the counter is set to zero, a control oscillator is used. This oscillator has several functions; first it resets the counter to 0000, then instructs the gate to operate on the next clock signal and after the measurement has been made disables the gate for a few seconds, long enough to allow the displayed reading to be read before resetting to 0000 and repeating the operation. The sequence of operation is shown in Fig. 5 and will be discussed in more detail later.


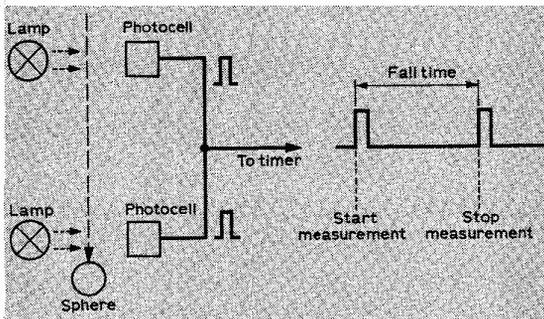


Fig. 5: Measurement of time between two events

Counter and Display

The counter and digital display for a 4 digit read-out consists of 4 identical counter and display units. Each digit has a decade counter which counts from 0 to 9, returning to 0 on the tenth count and providing a "carry" signal to the next higher decade. The counters count in binary form and the actual count figure is presented in binary coded decimal at 4 outputs, these having a weighting of 1, 2, 4 and 8 respectively.

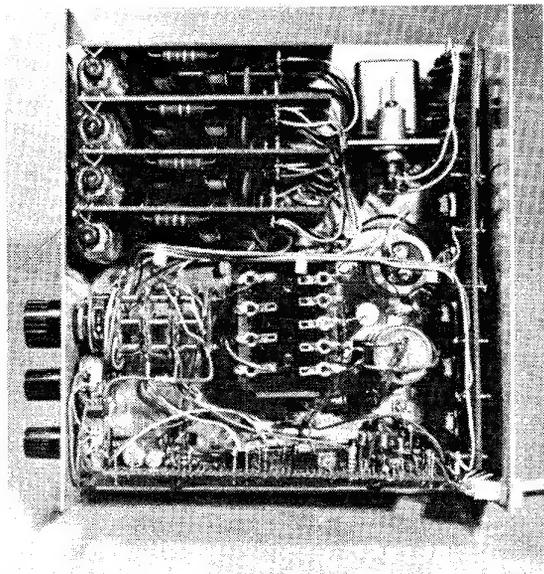The outputs are connected directly to a "decoder-driver" which converts the binary coded decimal input to a decimal output. The 10 outputs are connected directly to a numerical indicator tube which displays the figure existing in the counter. A separate input connection to the counter enables it to be reset to zero at any time.



Photograph showing general layout of the digital frequency counter timer.

In the block diagram the input stage is shown connected between the input terminal and the gate. The purpose of this stage is firstly to shape the input signal to provide a square wave output suitable for driving the counter stages and secondly to provide a high input impedance.

Time and Period Measurement

The basic component parts of a frequency counter can be rearranged very simply to provide the measurement of the period of one cycle of a low frequency signal or the time between two events. This is done by crossing over the clock and signal inputs by means of a change-over switch as shown in Fig. 4.

For example, suppose that we need to measure the frequency of a signal of 0.5Hz by the period method, (0.5Hz=2 seconds per cycle). With the change-over switch in the time position, the input signal now controls the gate and the counter counts the clock output.

If the clock output is 1kHz, that is 1 pulse per millisecond, and the period of one cycle of the input signal is exactly 2 seconds, then there will be a total count of 2000. We can convert this reading to frequency.

$$f = \frac{1}{t} = \frac{1}{2000\text{mS}} = 0.5000\text{Hz}$$

This means that we can now measure a low frequency with good accuracy.

The period measurement can also be used as an electronic stop watch for measuring the time between two events. For example, to determine the time taken for a sphere to fall a known distance, a set-up as shown in Fig. 5 may be used. Many other applications of this feature come to mind including race timing, camera shutter speed measurement, etc.

★ components list

Resistors:

R1	47k Ω	R18	150k Ω
R2	1M Ω	R19	1k Ω
R3	2.2k Ω	R20	150k Ω
R4	1k Ω	R21	1k Ω
R5	470 Ω	R22	3.3k Ω
R6	680 Ω	R23	2.2k Ω
R7	2.2k Ω	R24	1k Ω
R8	2.2k Ω	R25	470k Ω
R9	680 Ω	R26	82 Ω 1W
R10	10 Ω	R27	82k Ω 1W
R11	220 Ω	R28	82k Ω 1W
R12	1k Ω	R29	82k Ω 1W
R13	10k Ω	R30	82k Ω 1W
R14	10k Ω	R31	220k Ω
R15	4.7k Ω	VR1	50k Ω pot. carbon, linear
R16	1k Ω	VR2	50k Ω pot. carbon, linear.
R17	1.5k Ω		

all resistors 10% $\frac{1}{2}$ watt unless otherwise specified.

Capacitors:

C1	200pF	S.M.	500V
C2	0.47 μ F	Polyester	400V
C3	200pF	S.M.	500V
C4	0.01 μ F	Disc cer	15V
C5	50 μ F	Elec	15V
C6	10 μ F	"	"
C7	0.47 μ F	Polyester	125V
C8	470pF	S.M.	500V
C9	60pF	Concentric trimmer	
C10	50pF	S.M.	500V
C11	1000pF	Polyester	125V
C12	32 μ F	Elec	450V (or 16 + 16 μ F in parallel)
C13	100 μ F	Elec	25V
C14	2000 μ F	" can	" 1in. dia.
C15	0.01 μ F	Disc cer	15V
C16	0.01 μ F	"	"
C17	0.01 μ F	"	"
C18	0.01 μ F	"	"
C19	0.01 μ F	"	"

Integrated Circuits:

IC1	SN7473N	Texas Instruments
IC2	SN7400N	" "
IC3	SN7490N	" "
IC4	SN7490N	" "
IC5	SN7490N	" "
IC6	SN7490N	" "
IC7	SN7490N	" "
IC8	SN74141N	" "
IC9	SN7490N	" "
IC10	SN74141N	" "
IC11	SN7490N	" "
IC12	SN74141N	" "
IC13	SN7490N	" "
IC14	SN74141N	" "
IC15	SN7490N	" "

I.C. Sockets:

14 pin—dual in-line-11 off
16 pin—dual in-line-4 off
Barnes or Texas Supply Co.

Semiconductors:

Tr1	2N3823	Texas Instruments
Tr2	2N3702	" "
Tr3	BSX20	" "
Tr4	BSX20	" "
Tr5	2N3704	" "
Tr6	2N3704	" "
Tr7	2N3704	" "
Tr8	2N3704	" "
Tr9	2N3704	" "
Tr10	2N3704	" "
Tr11	MJE521	Motorola
D1	1S44	Texas Instruments
D2	1S44	" "
D3	1S44	" "
D4	1S44	" "
D5	1S44	" "
D6	VR525 (CV7172)	A.E.I. (5.25V 1.5W 5% zener)
D7	1N4007	Texas Instruments
D8	BS1100 p.i.v. 1A	bridge rectifier
D9	1S2051	International Rectifier Texas Instruments

Indicator Tubes:

V1	XN13	Hivac
V2	XN13	" alternatively the XN3 may be used
V3	XN13	"
V4	XN13	"
V5	Min. wire end neon.	Radiospares
V6	" " " "	"
V7	" " " "	"

Transformer:

T1 Midget mains trans. Radiospares.
sec. 250V 25mA and 6.3V 1.2A

Switches:

S1 SPST miniature toggle
S2 4 pole 11 way, built from—
1—miniature 'Maka-Switch' shafting assy.
4—M-B wafers, 1 pole, 12 way
2—packets miniature spacers—Radiospares.
S3 DPDT Miniature Toggle

Crystal:

X1 100kHz STC 4044 Type A
Senator Crystals or Henry's Radio Ltd.

Metalwork:

Complete metalwork (undrilled) in plain 16 s.w.g. aluminium is available from H. L. Smith & Co., 289 Edgware Rd., London W.2., at £1.40 (inc. p & p).

Miscellaneous:

Veroboard 17.9 × 4.7in., 0.1 × 0.1in. matrix (part no. VB126) cut to make 4 panels 2.325 × 4.1in., 1 panel 2.325 × 5.5in., 1 panel 2.325 × 7.1in. Crystal socket 10XJ. Brackets 12-LK2331 Lektrokitt (Home Radio). Knobs with pointers. Filter, red 1½ × 4½in. Coax socket, 3-3mm. Insulated sockets, wire, nuts, screws, etc., 4 plastic stick-on feet, cable cleat, grommets, capacitor clips.

The instrument to be described operates according to the principles already outlined. Integrated circuits are used as far as is possible and these are of the Texas Transistor-Transistor Logic (TTL) 74 Series, which require a +5 volt supply and are capable of operating at frequencies in excess of 15MHz.

For this type of Logic the 'High' or logic '1' level is a voltage of greater than +2 volts and the low or logic '0' level is a voltage of less than 0.8 volts.

The numeral display employs Hivac neon numeral indicator tubes which operate from a 300 volt supply and give a clear bright display.


The clock crystal oscillator uses a 100kHz quartz crystal and this frequency and two of the divided frequencies are brought out to sockets for calibrating receivers, etc.

The complete circuit is shown in Fig. 6.


The input stage consists of an f.e.t. source follower directly coupled through a transistor emitter fol-

DIGITAL FREQUENCY COUNTER TIMER


Fig. 6: The complete circuit of the digital frequency counter timer. The diagram shown on the lower page contains the input stage, gate, control oscillator, crystal clock, clock dividers and power supply. The diagram on this page shows the counter and display section.

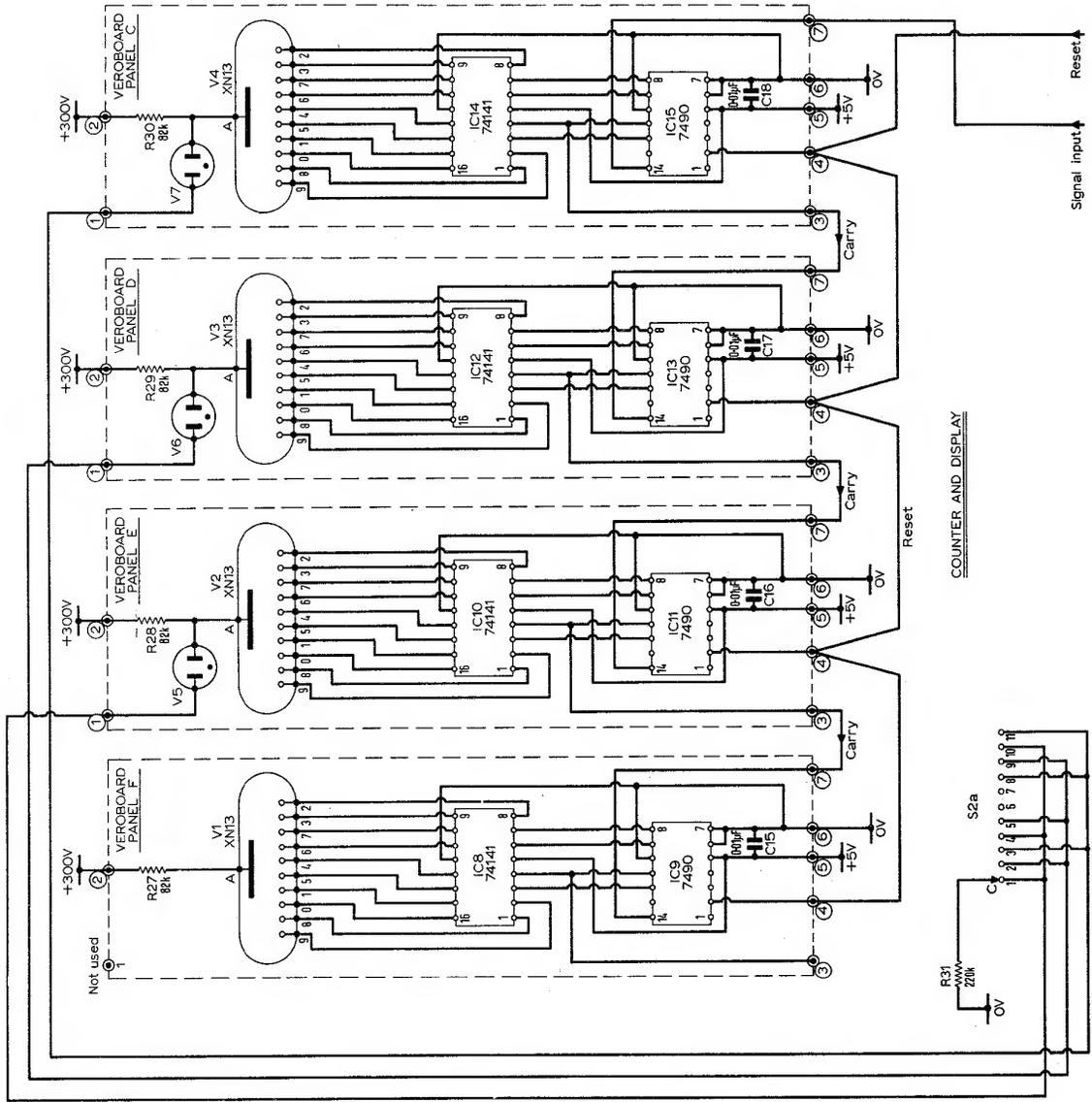


Direction of viewing →

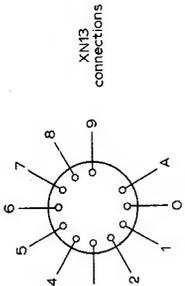

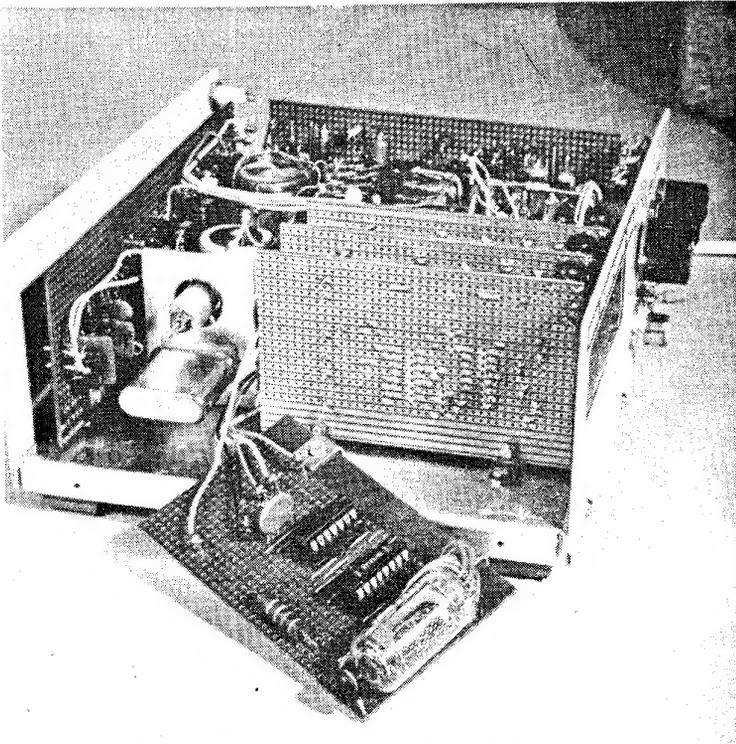7 — Indicates connecting pin on veroboard panel



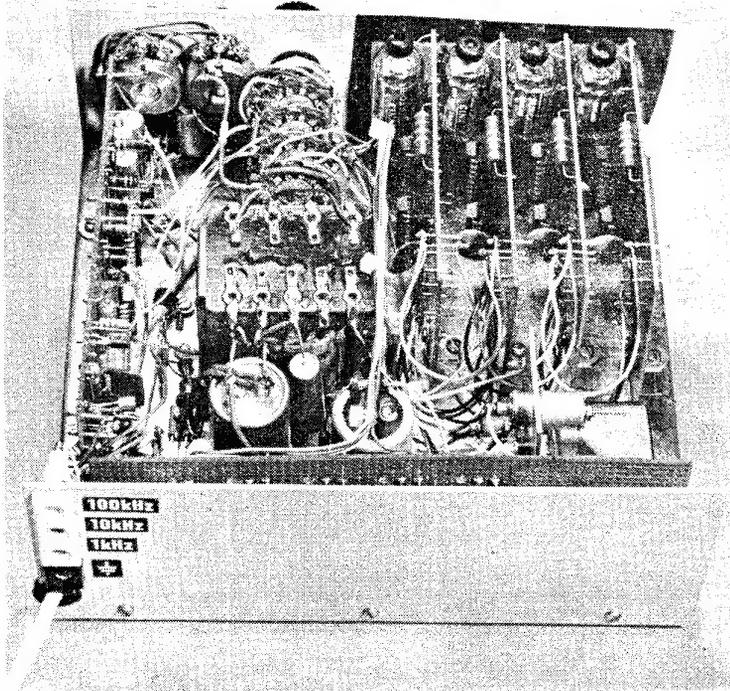Counter and display panel removed, showing the integrated circuits and numeral indicator tube. The position of the oscillator crystal and concentric trimmer can be clearly seen at the rear of the counter and display panels.



Rear view of the instrument. The crystal oscillator and divider outputs can be seen on the rear metal panel.

lower to a Schmitt trigger circuit, which drives the TTL circuits through a further emitter follower.

Working backwards, the output from Tr5 must be sufficient to drive the TTL at frequencies up to about 20 MHz. This means that the output voltage must swing from greater than +2 volts to less than +0.8 volts at this frequency.

An input at the base of Tr3 of greater than +0.8 volts causes Tr3 to conduct, Tr4 to cut off and the output from Tr5 emitter to be +4.0 volts, representing a logic '1'. An input to the base of Tr3 of less than 0.7 volts causes Tr3 to cut off, Tr4 to conduct and the output from Tr5 emitter to be +0.1 volts, representing a logic '0'.

For small input signals Tr1 and Tr2 have a gain of less than unity and an input of about 100 mV r.m.s. is sufficient to drive the Schmitt trigger circuit. To ensure that the output voltage at Tr2 emitter is at the correct level for switching Tr3, the gate of Tr1 is connected through R2 to a variable voltage provided by the 'LEVEL' control VR1. The LEVEL control is set at the position which gives reliable operation on small input signals. It will also allow the point of operation to be set to a particular level on a larger input signal.

For an input signal of a few volts peak-to-peak, Tr1 and Tr2 form an input clipping circuit having a high input impedance. At this signal level, Tr1 is cut off during the negative half cycles and Tr2 is cut off during the positive half cycles. This results in a square wave signal at the base of Tr3 having an amplitude which is more than sufficient to drive the Schmitt trigger reliably.

Input Protection

The input to Tr1 gate is protected against excessive voltage by the clamping diodes D1 and D2. These diodes conduct at +5.6 volts and -5.6 volts respectively. R1 is included in the input circuit to limit the current that might be passed through the diodes, and C1 bypasses R1 for the higher frequencies. C2 is a direct voltage blocking capacitor which is in circuit in the 'AC' position of S1 and blocks off any direct voltage which may be present on the input signal.

In the 'DC' position of S1, C2 is shorted out and a direct input is available for very low frequency signals and for use in the timer or period mode of operation.

Clock Crystal Oscillator and Divider

The clock consists of a crystal oscillator running at 100kHz followed by five +10 stages giving output frequencies and equivalent gate times as shown below:—

Frequency	Gate time
10kHz	100 μ S
1kHz	1mS
100Hz	10mS
10Hz	100mS
1Hz	1 Second

Crystal Oscillator

The crystal oscillator contains a 100kHz quartz crystal connected in the feedback loop of a two-stage amplifier formed by Tr8 and Tr9. Simple biasing is provided by R16 and R18. C8 is connected between the base and collector of Tr8 to provide the correct gain and frequency response for reliable oscillation of the crystal.

(N.B. A surplus 100kHz crystal was tried in the prototype and due to its lower activity it required C8 to be reduced to 200pF.)

The crystal operates in series resonance and C9 enables a fine adjustment of frequency to be made. The output from the oscillator is coupled by C11 and R22 to the clipping stage Tr10. The square wave output at Tr10 collector has a suitable voltage swing for driving the first decade divider IC3.

Each decade divider consists of an integrated circuit decade counter connected to give a division of ten and a square wave output of unity mark space ratio. The outputs are fed to S2d and to the output sockets as shown in the circuit diagram.

Control Oscillator and Gate

The gate actually carrying the signal through to the counter is IC2a. This gate is controlled by the Q output of the JK flip-flop IC1b which in turn is controlled by the JK flip-flop IC1a and the control oscillator.

The simplified sequence of events is shown in Fig. 7 and is as follows:—

The leading edge of a positive pulse from IC2d resets the coun-

ter to zero and the negative going edge sets IC1a with Q high and \bar{Q} low. This causes the output of IC2b to be high and the output of IC2c to be low, causing the clamping diode D4 to conduct. The control oscillator multivibrator is rendered inoperative by the conduction of D4.

The output condition of IC1a presets IC1b so that at the next negative going edge of the clock period input waveform Q of IC1b will go high. This is the commencement of the gate period.

—continued on page 430


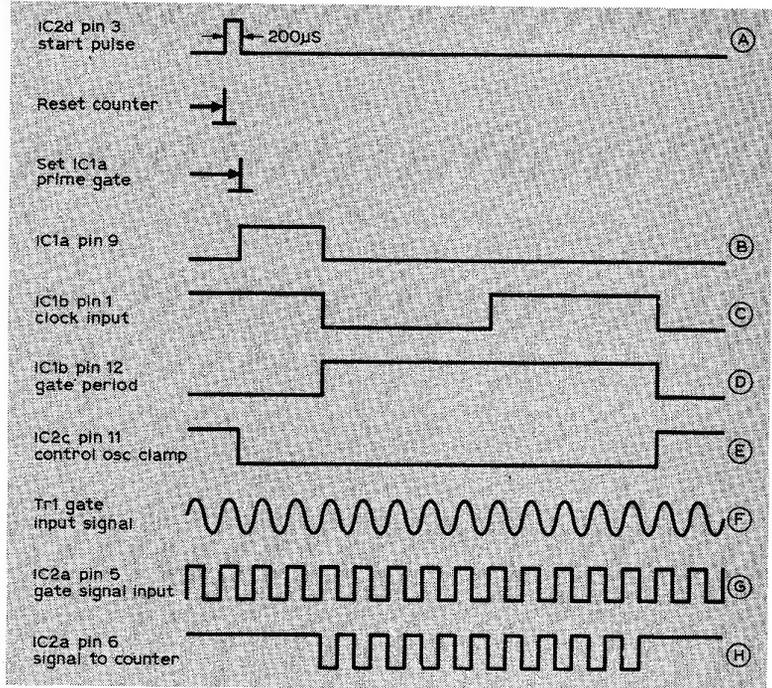


Fig. 7: Frequency counter gate waveforms

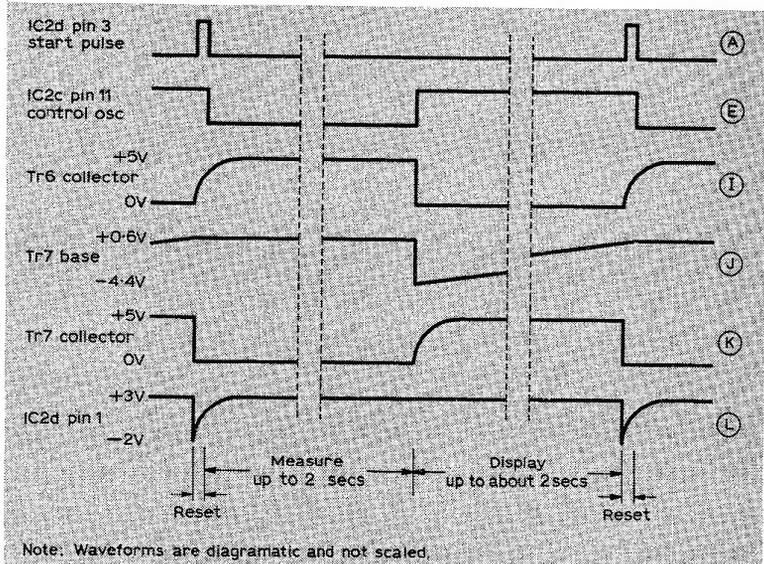

Note: Waveforms are diagrammatic and not scaled.

Fig. 8: Frequency counter control oscillator waveforms

VARIABLE STABILISED power supply

B.T. ENGLISH

A very popular piece of equipment in any experimenters workshop is a variable low voltage d.c. supply. Most transistorised equipment operates from supplies of from 3-30V and the unit described here was designed to give this output with a maximum current rating of 500mA which should satisfy the needs of most experimenters. An added advantage is that the unit is cheap to construct and rugged in use. Virtually any PNP transistors capable of withstanding 30V can be used in the unit and surplus transistors were found to give very satisfactory results. Tr4, of course, must be a power transistor capable of dissipating up to 10W, but no difficulty should be experienced if it is mounted properly on the aluminium chassis.

The theoretical circuit diagram is shown in Fig. 1. Full wave rectification is achieved by the diodes D1-D4 in the form of a silicon bridge rectifier type BY164 giving a d.c. voltage on C1 of about 22V. Two zener diodes in series provide the reference voltage on the base of Tr1. The voltage across these diodes remains constant at 20V over a wide range of current through the diodes. Consequently Tr1 will act as a constant current transistor with the potential developed across VR1 remaining fixed. Voltage control is achieved by varying the current through Tr4 connected in series with the load, this is done by VR1. Tr2 and Tr3 connected in the *super-alpha* configuration offer a high input impedance and prevent loading of VR1.

The prototype was constructed on a small tag board with flying leads to the transformer, power transistor, and output circuit. Details of the mounting and general layout are given in Fig. 2.

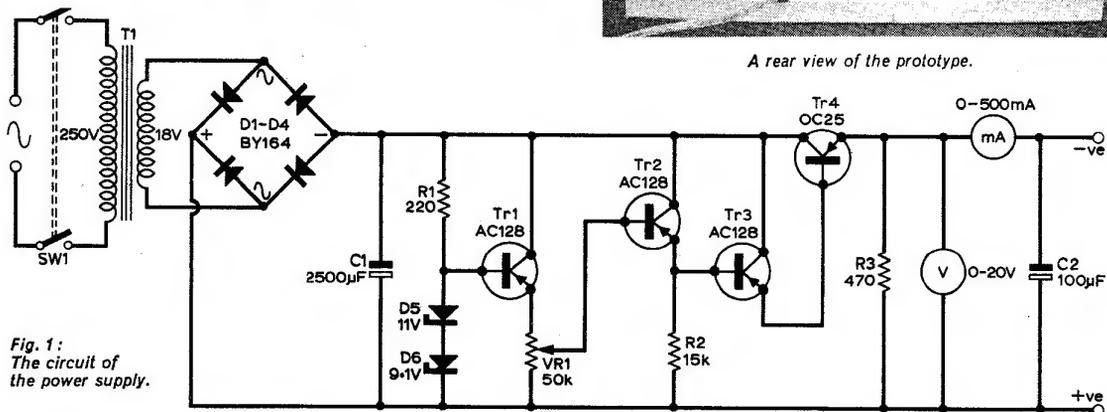


Fig. 1:
The circuit of
the power supply.


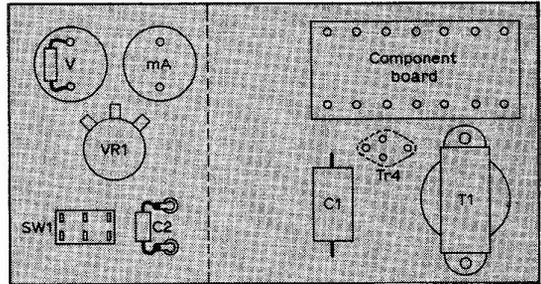
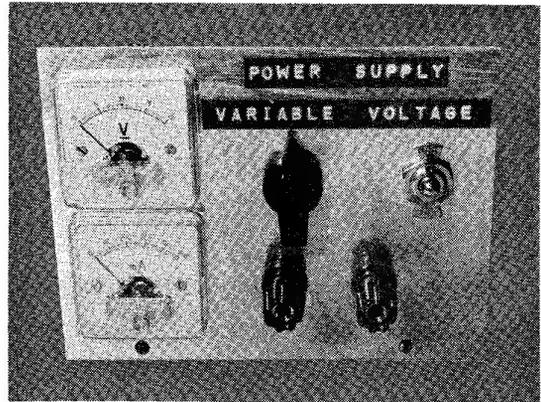


Fig. 2: A suggested component layout.

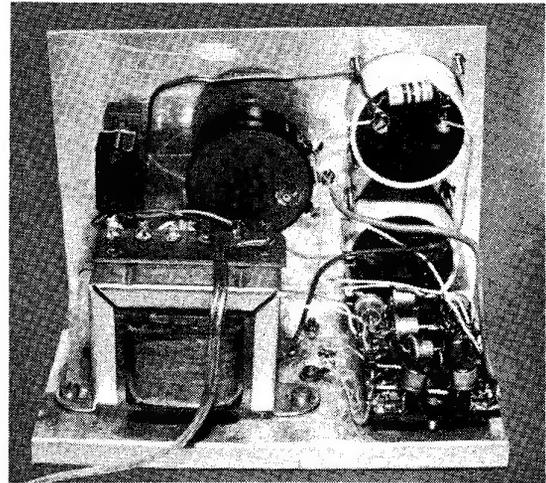

A rear view of the prototype.

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

THE recent bad weather has probably been the cause of the large number of reports received this month. The first report this times comes from **Martin Ward** in Portchester. Martin's equipment consists of a Mullard 5-valve domestic receiver and a 75-foot end-fed antenna, his log included: —

- 7285 R. *Warsaw*, Poland with music at 1200.
- 9620 R. *Yugoslavia* in English at 1530.
- 9750 R. *Pakistan*, Karachi in English at 1945.
- 11920 R. *Kuwait* with music at 2000.
- 15105 WIBS, Grenada with music at 2000.
- 15250 R.S.A., South Africa in English at 1800.
- 17845 R. WNYW, U.S.A. at 1700.

The next report is from **Alan G. Crookes** of Sheffield who has a Veritone CR-150 and a 200-foot long-wire at 20 feet, these enabled him to hear: —

- 6115 R. *Berlin Int.* in English at 2035.
- 6135 R. *Free Europe* in English at 2315.
- 9600 R. *Baghdad*, Iraq in English at 2030.
- 11860 R. *Vilnius*, Lithuania at 2335.
- 15160 R. *Ankara*, Turkey noted in English at 2205.
- 15345 R. *Kuwait* in English at 1800.
- 21520 SBC, Switzerland from Berne at 1530.
- 21535 R.S.A., South Africa at 1600.

Stephen John Mathews of Hull has used a Bush 4-valve domestic receiver and a 90-foot wire in his loft. This simple equipment brought in many interesting stations including: —

- 11672 *Radio Pakistan* in English at 0030.
- 11730 *Radio Kiev* in English at 0030.
- 11790 *Radio Australia* in English at 1710.
- 11760 R. *Havana*, Cuba in English at 0355.
- 11795 R. *Nacional de Rio de Janeiro* in Portuguese at 0210.
- 11805 R. *Globo*, Brazil in Portuguese at 0145.
- 11825 R. *Jornal de Comercio*, Brazil at 0040.
- 11914 *Radio Nacional Lima*, Peru at 2150.
- 11935 R. *Clube Paranaense*, Brazil at 2025.
- 15265 R. *Afghanistan* in English at 1810.
- 15290 *Damascus Radio*, Syria in English at 2040.
- 17765 VOA *Tinang* in English at 1700.
- 17855 NHK, Japan in English at 1020.

Hugh Cocks of Mayfield used his Unica UNR-30, 50-foot long-wire and outdoor TV aerial to compile an extremely long log which included: —

- 6135 HCJB, Ecuador at 0845.
- 6540 *Pyongyang*, N. Korea at 1900.
- 7235 R. *Australia*, signing off at 1730.
- 7270 R.S.A., South Africa at 2000.
- 9525 R.S.A., South Africa at 2100.
- 9550 R. *Australia* at 1700.
- 9580 BBC, Ascension Island at 0715.
- 9745 HCJB, Ecuador at 0930.
- 9912 *All India Radio* at 2000.
- 10040 Hanoi, N. Vietnam at 2000.

- 11675 *Radio Pakistan* at 2000.
- 11775 TWR, Bonaire, signing on at 0730.
- 11795 WINB, U.S.A. at 2100.
- 11835 *Algeria* in French at 1200.
- 11860 BBC, Ascension Island at 0700.
- 11910 ETLF, Ethiopia with news at 1930.
- 11955 BBC, Malaysia at 1645.
- 11960 VOA *Thessaloniki*, Greece at 1630.
- 15018 Hanoi, N. Vietnam at 2000.
- 15110 WIBS, Grenada at 2000.
- 15125 R. *Australia* at 0700.
- 15155 ELWA, Liberia in Arabic at 1615.
- 15185 Lagos, Nigeria at 0700.
- 15200 Lagos, Nigeria with news at 1530.
- 15295 TWR, Bonaire in English at 2145.
- 15325 Rwanda relay of Deutsche Welle at 0630.

Jeffrey Malina, London N.4, has a Skyrover Mk. II receiver and a 110-foot long-wire which enabled him to hear: —

- 7245 BBC, East Med. relay at 2115.
- 9009 *Israel*, Jerusalem, English at 2115.
- 9480 *Radio Kiev*, Ukraine in English at 1930.
- 9545 BBC, Ascension Island at 2100.
- 9625 *Israel*, Jerusalem at 2045.
- 15250 R. *Bucharest*, Rumania at 1300.
- 17775 R. *Afghanistan* in English at 1815.
- 17875 VOA, Monrovia, Liberia in Russian at 2115.
- 21535 NHK, Japan in English at 0800.
- 21545 R. *Accra*, Ghana at 1445.

Colin Beesley of Bristol is another reporter with a Unica UNR-30 receiver which he uses in conjunction with a 75-foot aerial to hear stations which include: —

- 9725 R. *Sweden* in German at 1200.
- 9805 R. *Cairo*, Egypt with news at 2340.
- 11875 RAI, Italy in French at 1530.
- 11930 *Radio Australia* at 2230.
- 15160 R. *Ankara*, Turkey, news in English, 2300.
- 21545 R. *Accra*, Ghana, news in English at 1630.
- 25790 R.S.A., South Africa in English at 1625.

Christopher Gibbs in Camberley has a Trio 9R-59DS receiver, a 20-foot long-wire and a Joystick antenna which enabled him to hear: —

- 5035 R. *Clube de Cabinda*, Angola with music at 2000.
- 6025 R. *Portugal* with DX programme at 2100.
- 6090 R. *Luxembourg* at 2109.
- 7210 R. *Norway* noted at 1805.
- 7220 R. *Budapest*, Hungary at 2132.
- 9525 R. *Warsaw*, Poland with news at 2030.
- 11755 R. *Finland* with news at 1815.
- 11940 R. *Bucharest*, Rumania in French at 1900.

Reports should arrive by the 15th of the month, and be addressed to the author at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

THE short skip conditions of the last month seemed to suggest that two metres should be showing some interesting results. However, logs from listeners did not bear this out. The skip was particularly noticeable on twenty where locals and near Europeans were coming in at colossal signal strength despite many of them using verticals, including some ground planes, which are often described in the antenna textbooks as just the thing for cutting down the local signals and picking up the DX.

Conditions have been about average for the time of year with most of the DX packing into 14 and 21MHz. The lower frequency bands have not seemed to be too keen to part with any DX, at least, at this scribe's QTH. Ten metres has been up and down with the "down" being the more dominant of the two. Trouble is with ten, the moment you switch to another band the 28MHz sector can quite easily jump to life and permit the keen listener to log five continents in about the same number of minutes.

Topband has been lively as far as G stations are concerned with the usual crop of mobiles (including G3JDG) putting up quite a bit of r.f. Apart from the odd OK this band appears to have become a G-band unless someone has been hearing things I haven't?

John Moore (Leicester) says that his c.w. is quite good and claims that not only does he now find c.w. DXing as easy as phone, but he has the extra pleasure of knowing that fewer listeners are hearing his best c.w. DX stations. Just goes to show what can be done with a bit of persistence and determination. John bagged a couple of OK's on Topband and even managed to log s.s.b. squeaks from: MP4MBC, UF6FAX (c.w.) ZC4MU, ZS4RO, ZS6AYW, 5H3LV, 9J2RA, 9J2TF on ten metres.

"There's no 'H' in Witney," says **Stefan Kaye** (Witney with no 'H'). A peep at 80 metres with an AR88D and a 250ft. long wire at ground level revealed: CT1UEG, EA4ITU, EP2BQ, PY1AJ, VE1AGH, ZL4JF/A, ZL3LE, ZS1MH, all s.s.b.

T. Wright (High Wycombe) seems to bear out my remarks about 160 by saying that there have been "hoards of G stations about this month". Tim's log for 14MHz received on an R107 and 120ft. end fed includes: JA3EP, JX8IL and KP4GM plus a long list of EU stations. Looks like the short skip was quite prominent for best part of the month.

D. Palmer (Bishopbriggs) observes that I do not appear to receive many logs for forty metres. Receiver is a modified 19 set with a 7MHz dipole and a.t.u. which raised thirteen PY stations plus: CX1AA, CX1BBR, JW7UH, JW9QH, K1GZL, LU8AJG, VP2AA, ZB2A, 4Z4DX.

M. Bradford (Edmonton, N.9.) says that the 1f. bands have failed to produce anything interesting and that ten metres has been disappointing. This was not the case with 14MHz which obliged with s.s.b. from: CN8MC, CT2BB, EA8DJ, K4RON, KG4AL,

KG4EQ, LU4ECO, PY4AEB, VK2NN, VK5AZ, VP2BGL, W3UBM/MM, 4X4AE, 4Z4JW, 9K2YG. A listen on 21MHz produced: CE4ME, EA8GZ, JA4JBP, JA7EA, KZ5AA, LU2ECS, VS9MB, VS9MT, 9Q50A.

Les took his homebrew v.h.f. Rx and it didn't work (hard luck Les), this is only part of the story. Three conspirators pooled their gear to form a combined assault on the amateur bands. The results on 20 were: FG7TD, HK1CDK, HK3AUE, HR1SO, HR5JDC, MP4BIN, TI2AAC, UL7NW, VE1AVM, VE2DVV, VE3DLC, VK3BM, W5DRW, XE1WA, YV5BPG, and on 15 metres: CR6GA, W2AMM, W9IYY, YV1AVU, 4X4AE, 4Z4HF. Will the real **D. Lawley, A. Wade and L. Allen** please stand up? Incidentally, D. Lawley also sent in an individual log which included 27 VK stations received on his CR70A and 64ft. end fed at about 18ft.

S. Lamprey (Cardiff) has a 9R59DE which has had a few unspecified mods done to it. The aerial is 30ft. of wire with a Joystick on the end. Signals received from: EP2SW, HV3SJ, JW5NM, JW7UH, JY1, MIACH, MP4BJG, OD5FI, ST2SA, DJ3DH/TA, TU2AZ, 5Z4MI, 7Z2OM, 7Z3AB, 9K2AM, 9M2CP, 9Q5IA. No mode mentioned.

DX letter this month comes from **Tony Curtis** (Canberra, Australia). Tony is 17 and has been an s.w.l. for about four months. His s.s.b. log, using domestic receiver (Circa 1950), is fitted with a homebrew b.f.o. which has a bad attack of the drifts. However, the log for 20 metres reads: G6IA, G7LB, JA1EPJ, VK1EP, VK2ACD, VK3AJ, VK4AZ, VK5EB, VK6RU, VK8JS, VK9XI, countless W stations, ZL1ALW, ZL2ON, ZL3FM.

Happiness is JR-500S-shaped to **J. Iredale** (Llandudno). His pet is fed regularly with a dipole or 132ft. end fed (nothing like a varied diet) and in return for this loving care produced 20 metre evidence of: CT2AK, CT2BB, DUIDBT, JA3AAW, JA6AV, JA9YBA, JW5NM, K2LQQ/TF, KV4AM, KZ5JF, LU1FKF, LU8DFB, OX3BD, PY2CSV, PY3BXW, PY7YS, TI2JO, TI2WA, TG9LM, WA1NGK /TF, W6REH, ZB2A, ZL1PY, ZL2ABY, 4Z4HF.

A new CR70A at the Coulsdon QTH of **J. Iggleden** is fed from a 215ft. network of wire (knit yourself an antenna kit?). Since installation it has produced 21MHz s.s.b. from: EA7DJ, JA8NJO, K5HYB, K6HTM, PY2ERS, TR2AA, W6ATW/M, W6TUQ, ZM6UP, 4X4AE.

Busy month for keen types. August 7-8, WAE c.w.; 8, Woburn mobile rally; 9, 2 metre s.s.b. contest; 15, 70MHz c.w. contest; 15, Derby mobile rally; 15, Torbay mobile rally; 22, Swindon mobile rally; 28-29, All Asia c.w. contest; 29, Stratford-upon-Avon mobile rally. September 4-5, v.h.f. n.f.d.; September 4-5, Region 1 IARU v.h.f./u.h.f. contest.

Logs, in alphabetical order please, to arrive by the 15th of the month to:

12, Cross Way, Harpenden, Herts.

practically wireless commentary by HENRY

No. 83

Odd
Audio
—again

THE more we get embroiled in that fringe area of wireless—what is now known as the hi-fi world—the less scrupulous salesmen seem to be. Trade Descriptions Act notwithstanding, some purveyors of audio equipment beg a great many questions when they prepare their sales brochures.

We are familiar with the 'what's a Watt?' argument, aware that output power can depend on all sorts of different measuring conditions, from the way you supply your amplifier voltage to the way you cock your head. By judicious juggling, one can make a humble ten-watter sound—on paper—like one of those monstrosities that pump P.A. around the local disotheque.

What we are not always ready, or able, to dispute, even if willing, is the more subtle business of distortion percentage, signal-to-noise ratio and overload. Even where these are stated, the trusting soul can be caught out.

Just lately, our illustrious contributor, Gordon J. King, has been insisting on applying more stringent tests. He would like makers to quote a true 'power bandwidth' and he requires more comprehensive distortion limits than a manufacturer is usually prepared to give. And what

Gordon wants, Gordon usually gets.

One of the things he wants is a statement of the output power over the rated frequency range of the equipment relative to the test frequency setting. The frequency limits where output falls by half then become the 'power bandwidth,' much more revealing than a single figure at a single frequency.


Moreover, he demands rms watts—none of your cheap and nasty Music Power for him. No use the amplifier designer arguing that real-life conditions do not encompass sinewave signals at full whack. Gordon and others argue that unless the rms test can be applied—continuous sinewave power—meaningful measurements cannot be taken and true comparisons can never be made.

Distortion is another matter for argument. A lovely low percentage at full power at 1kHz may make a Class B amplifier seem impressive. Check it again at 'normal' listening level, and see what you have got.

Then do a 'distortion bandwidth' test the way you did the power bandwidth test, i.e., over the specified frequency range. Oh boy! You should see the curves obtained from some quite well-regarded amplifiers when we make them suffer that indignity.

Some of the high-falutin' chatter that is going on about low-noise tape recording and the superiority of cassettes conveniently overlooks the fact that the distortion figure for a run-of-the-mill machine may be a couple of per cent—against the 0.1% we nowadays expect from a good amplifier and the 0.5% we usually get from a mid-price version. All right then—don't jump on me, Joe. I know that you cannot compute percentages like that.

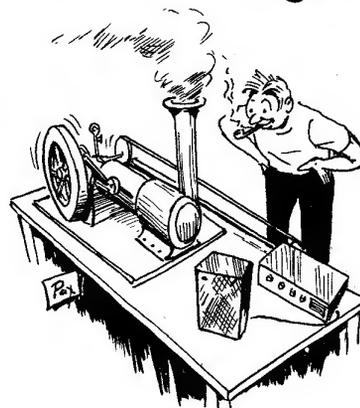But Henry would also like to see a regular set of standards applied. Even now, there is a committee advising another sub-committee, who are passing on their



Driving our amplifiers by steam

findings to the British Standards Institution, who may—eventually—stir their sluggish feet and complete BSS 3860; 1968 and 1568 and Part 1 1970.

Mind you, there is some very odd audio around. Take the Bose system. At 250-quid for a couple of speakers and an equaliser—you take it. Henry sticks his neck out in merely mentioning it for Dr. Aram Bose is currently suing the American Consumer Association for more than they have got because they said his speakers needed tons of power to drive them and were not very effective when you did!

There is a review of the Bose 901 in the July 1971 issue of *Hi-Fi News*, where Ralph West keeps on about the 'smoothness' of the sound. He theorises about violins and Rolls-Royces being 'run-in' and the good sound of paper-cone speakers because the bugs are worn away.

Then the Editor chips in with a dry footnote to the effect that the original 4 inch drive units (Bose has nine of these per speaker) were taken from a Fisher FM table radio. You see? Odd audio or not, we come back to wireless in the end. Just think, if Benjamin Franklin hadn't earthed his key, we would have been driving our amplifiers by steam.



Don't jump on me, Joe

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

ELECTRONICS has brought about the introduction of excellent, inexpensive electronic flash guns. They are so cheap in fact that there is little demand for circuits to build one's own (though this is perfectly possible) but a number of ancillaries can be made for use with a flash gun.

One of the disadvantages with flash pictures is that the subjects often look harsh as narrow bands of dark shadow usually outline one edge of the subject. This, of course, is due to the flash point not being at exactly the point of the lens on the camera.

Bounce flash overcomes this but has the serious drawback that it is extremely difficult to calculate the exposure.

Another solution is to use two flash guns, one conventionally but a second one pointing from a very different angle whose job it is to soften the hard shadows and we can call this one a "slave flash". It would be possible to arrange some form of direct switching to trigger both from the shutter contacts but the one described here is completely unconnected electrically and is thus far more versatile.

The light from the master flash is arranged to trigger our little circuit, which in turn makes the contacts for the slave flash.

The reduction of components prices in recent years has made it possible for us to use some components that would not have been possible before in our series as the total cost would have exceeded the £1 limit. In this circuit we are using two such components: a light dependent resistor (LDR) and a thyristor or silicon controlled rectifier (SCR).

Light dependent resistors are exactly what their name implies. In bright light—such as produced by a flash gun—their resistance is very low. The actual value varies considerably with the actual specimen but ranges between 10Ω and 200Ω. On the other hand in complete darkness a good sample will have a resistance of several megohms and even poorer ones at least 10kΩ.

This LDR is connected between the positive line and the base of Tr1. In the ordinary way, even in complete darkness, this would be sufficient to bias the transistor into conduction, but VR1 is connected between the base and the emitter, forming a potential divider.

Being a silicon transistor, Tr1 will be off (i.e. no current will flow from emitter to collector) until the base is at about 0.6V above that of the emitter. It will thus be seen that, by correct setting of VR1, Tr1 can be arranged to be off in ambient light but as soon as extra light falls on the LDR, the potential at the base rises and the transistor is switched on.

The SCR in the collector circuit of Tr1 operates in much the same way as a relay. In normal conditions there is a very high resistance between anode

No. 29

SLAVE FLASH TRIGGER

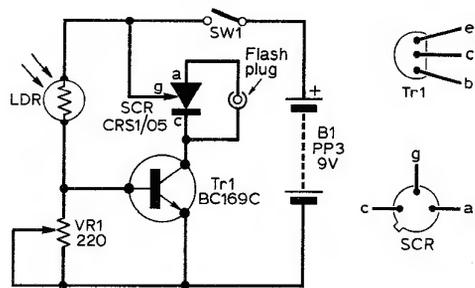


Fig. 1: The circuit of the slave flash trigger with the semiconductor connections shown on the right.

★ components list

Tr1	BC169C	11p†
SCR	CRS1/05 Thyristor, 50V, 1A	25p*
LDR	Light dependant resistor	43p‡
VR1	220Ω linear potentiometer	12p†
SW1	On-off toggle switch	7½p‡
		98½p

† Electrovalue Ltd.

* G. W. Smith Ltd. or A. Marshall and Son.

‡ J. Bull (Electrical) Ltd.

Prices are those advertised in Practical Wireless July 1971 and may have changed. No allowance is made for minimum order costs or for postage and packing and these should be checked carefully before ordering.

and cathode but when triggered with a pulse at the gate, the resistance falls to practically nothing. In this circuit, for convenience, the gate is constantly at supply potential and it is arranged for the cathode to be made more negative, but it comes to the same thing as pulsing the gate.

If the electronic flash switch contacts are connected across the SCR, these will thus be shorted out when the light level on the LDR reaches a certain level. This operation takes place at electronic speeds and although there will be a delay between the main flash and the slave flash, it can be measured as a few millionths of a second.

Flash guns are usually fitted with 3mm coax plugs and the corresponding sockets can be obtained from most photographic shops, though the cost of this item takes us outside our £1 limit.

Note that the flash contacts *must* be connected the right way round, positive to anode, negative to cathode, and the potentials at the flash gun's plug should be checked.

As far as the camera aperture is concerned, this will depend on the film used and the direction in which the slave flash is pointed. Black and white film is not so critical as colour as far as exposure is concerned and no adjustment is necessary. ■

VARIABLE FREQUENCY AUDIO OSCILLATOR

J.B.WILLMOTT A.I.P.R.E.

MANY constructors will have in their spares box a selection of 1.4V filament battery valves taken from discarded "All Dry Portable" receivers. It occurred to the author that, when only intermittent operation over short periods is required, battery type valves of the B7G based miniature range form an excellent basis for the construction of simple test equipment. The one which forms the subject of this article was a wide range variable frequency audio oscillator, an extremely useful piece of equipment for testing audio amplifiers or the audio section of radio receivers. The majority of the old type battery portable receivers used a standard line up of four "DK" type valves, typically DK96, DF96, DAF96 and DL96. The requirements of the instrument described here are for two general purpose triode valves, and it was found that using the DF96 and DAF96 (or the older 1T4 and 1S5) connected as triodes, gave very satisfactory results.

The completed instrument will give a generous output (somewhere in the range of 2V peak) over a wide range of frequencies, from approximately 40Hz to 20kHz, the latter of course beyond the range of human hearing, but desirable when testing audio equipment. The coverage is given in three switched ranges (a fourth position of the range switch is the "Off" position), each of which slightly overlaps its predecessor. The waveform produced is good, and if an oscilloscope is available, the response of the amplifier under test can be accurately displayed and tendency to distortion at certain frequencies becomes readily apparent.

Circuit Description

The circuit composes two triode connected valves, linked together by conventional RC coupling by the components R3, C7 and R4. The output from the anode of V2 is applied in the form of negative


feedback via the capacitor C9, and the potential divider network provided by VR2 and VR3 to the cathode (filament) of V1. Simultaneously, positive feedback is applied to the grid of V1 through the potential divider network comprising C1, C2 or C3 (as selected by the section "A" of the range switch) and VR1a, together with C4, C5 or C6 (selected by section "B" of the range switch) and VR1b.

Provided that the amount of positive feedback at the grid of V1 exceeds that of the negative feedback applied to its cathode, oscillation will take place and be maintained, the frequency depending on the setting of the range switch and the ganged potentiometer VR1. Both VR2 and VR3 are adjustable, and the circuit can be so "balanced" that steady a.f. oscillation is maintained throughout the range. The values specified for C1 to C6 are such that each "sweep" of VR1 provides the desired range of audio frequencies. It is important that VR1 is a dual ganged potentiometer of the linear type, otherwise a steady increase in frequency as the control is rotated clockwise will not be obtained. The third "pole" ("C") of the range switch is utilised to provide on/off switching, in the maximum anti-clockwise position, the LT supply to the valve filaments is broken, and hence the instrument is "off", as no HT current can flow unless the valve filaments are heated by the passage of the LT supply through them.

The audio output of the instrument is picked off from the anode of V2 via C8, and taken to the coaxial output socket. In order to minimise the effect of connecting external apparatus of widely varying output impedance, a 27kΩ resistor is connected permanently across the output socket (R6).

—continued overleaf

Fig. 1: The complete circuit of the variable frequency audio oscillator.

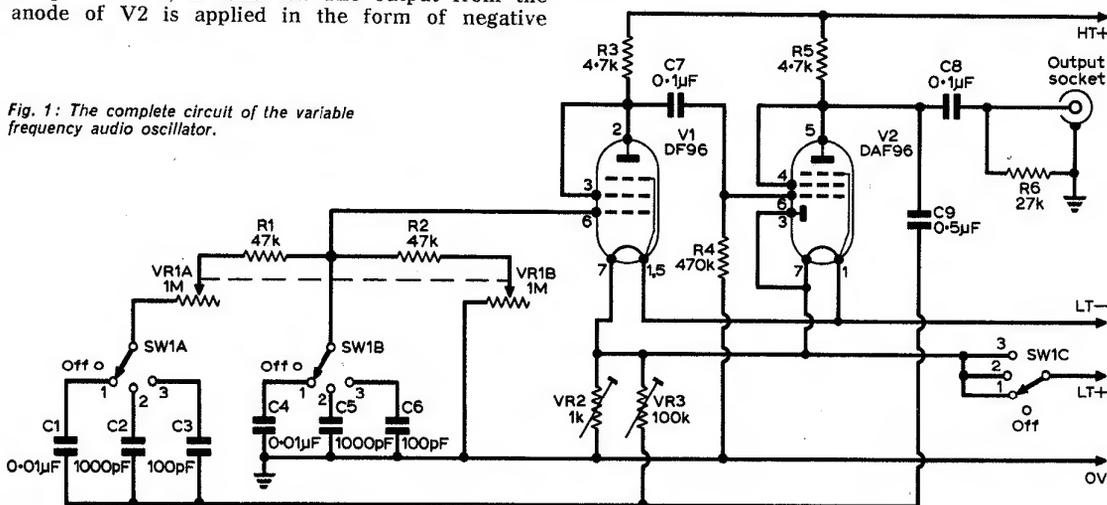

Testing the Instrument

Connect the output of the instrument to the input sockets of any available audio amplifier (valve or transistor) known to be in good working order, or to the pick-up sockets of a radio receiver. Set the fine frequency control to the mid-point of its range, and also set VR2 and VR3 to approximately midway setting. Switch on the amplifier (or radio receiver) and in the case of valve equipment, allow time to warm up. The volume control should be set approximately at the level required for normal radio (or record) reproduction. Now, having first made sure that the HT and LT batteries have been connected, turn the range switch to position 3, i.e., the middle range of frequencies. A note of approximately 400Hz should be heard in the loudspeaker. Adjust VR2 for maximum output, then reduce the setting of VR3 (by turning it anticlockwise) until oscillation ceases. Now re-advance VR3 until the oscillation just recommences. Next vary the setting of the fine frequency control VR1 and ensure that oscillation is maintained at all settings. VR3 should be set at the "minimum" consistent with maintained oscillation. Now set the switch to Range 1 (lowest), and finally to Range 3 (highest) frequency settings, and make sure that all positions of VR1 oscillation is maintained. Adjust VR3, and VR2 if necessary, to ensure that this is the case. The instrument is now completed and ready for use. ■

TOPIC OF THE MONTH

"Electronic Vandals" continued from page 383.

why not join the society and take part in properly conducted explorations!

How does all this square up with the publication last month of the P.W. *Treasure Tracer*? In the first place let it be said that your editor is not only professionally involved in the making and using of electronic devices but is also an active archaeologist, a foot in both camps as it were. Basically it is felt that there is no reason why people should not enjoy innocent amusement with metal locators. It is generally thought that some site looters are unaware of the irreparable damage they can do so quickly, but a little thought will show that the robbing of archaeological sites is as indefensible as looting the showcases in a local museum. These sites are not only part of our heritage but also of future generations. So, don't get carried away with ideas of a vast fortune just waiting to be dug up—try the pools for that! And don't go tramping about on farmland without having first obtained permission from the owner.

W. N. STEVENS—*Editor.*

BACK NUMBERS

We regret that the back numbers department of P.W. has now closed and consequently we are unable to supply these.

Requests for specific back issues can usually be included in our 'CQ' section; there is no charge for this but it is a service between readers and P.W. are unable to meet any of these requests.

HARMONIC SIX—*continued from page 398*

of the cores should be needed.

Once the i.f. amplifier is aligned it should not be touched further as it is pointless to alter these cores again while aligning the mixer stage.

MIXER ALIGNMENT

All the cores are adjusted so that about $\frac{3}{8}$ in. of brass rod projects. Screw TC2 about half down. Switch to the lower frequency range and tune in a signal with VC1/2 nearly fully open. Peak up the signal by rotating VC3. If VC3 is nearly fully open, screw down TC2 a little. With a signal peaked with VC3, tune towards the l.f. end of the band. When signals are tuned in, adjust the core of L2 for best volume. Continue until VC1/2 is nearly fully closed. If much adjustment of L2 core is needed, repeat from the h.f. end of the band. The purpose is to adjust TC2 so that signals peak with VC3 near the h.f. end of the band, with VC3 about half closed, then to set the core of L2 so that the minimum re-adjustment of VC3 is necessary, while tuning to the l.f. end of the band.

When this is done, switch to the h.f. range and repeat, adjusting the core of L1 near the l.f. end of this range.

If necessary, actual band coverage can be altered by moving the core of L3 near the l.f. end of the bands, and adjusting the trimmer TC2 near the h.f. ends of the bands. After any such change to coverage, adjust L1 and L2 to match, as mentioned.

AERIALS

For a short rod or wire aerial, TC1 can be about half closed but for a longer aerial it should be unscrewed somewhat.

The aerial in use will influence the setting of VC3. Provided VC3 can be peaked for best results, at any frequency, and is not fully open or fully closed, there is no loss of efficiency due to wrong alignment. However, when alignment is correct, little or no adjustment of VC3 will be wanted while tuning, except perhaps to peak up very weak signals.

NOTES

Resistors R4 and R5 are to prevent squegging and violent oscillation near the h.f. end of the oscillator range. With the coils and values shown, good results should be obtained without experiment.

In some cases a change in one or both values will be more suitable for the actual transistor fitted for Tr1. It may be found that R5 can be omitted, Tr1 emitter being wired directly to pin 5. With some transistors, R4 could also be omitted, or could be of lower value. R4 and R5 should be of the lowest values which do not result in numerous whistles and oscillation accompanying all signals tuned in near the higher frequency ends of the wavebands.

A 3-ohm speaker is suitable and should be in a cabinet, or fixed to a baffle board. A headset with headband is more convenient than a miniature or single earpiece for this type of reception. Medium or low impedance phones will generally be satisfactory.


The tuning dial may consist of a numbered dial, or two scales can be drawn on thin card, and marked with frequencies. The card can extend over the whole panel, and may be covered with thin transparent material. ■

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

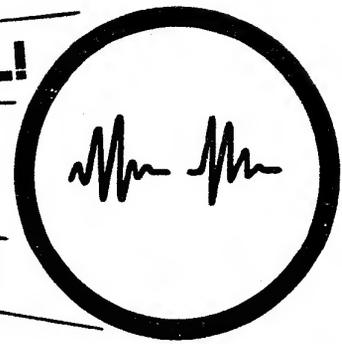


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing ...


1 ▶ OWN and HANDLE a

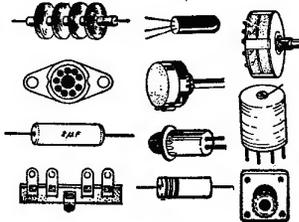complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

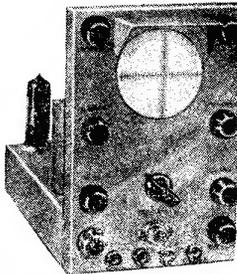a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND **CIRCUIT DIAGRAMS**

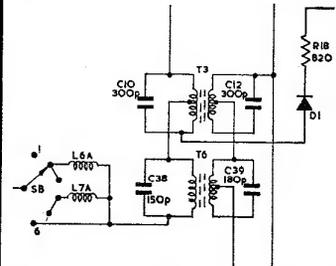

4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK ... INCLUDING ...

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.


FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW9

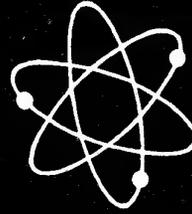

NOVEL DOOR ALARM

DAVID CROSS

As the author's doorbell needed replacing, it was decided that an electronic replacement would be a good idea. It would be simple, but rather dull, to replace this by a simple audio oscillator feeding an amplifier and for this reason a two-tone version was designed, that is one that would provide two notes in rapid succession. Readily available components were used in the construction and on the prototype many of the components were found on discarded computer board panels.

The sound produced by this circuit has many uses other than for a door alarm and works equally well as a burglar alarm. This is especially useful as the sound produced can be made to sound almost exactly like that of a police siren—enough to worry any potential burglar!

When Tr1 is switched on, diode D1 conducts, this provides an additional conducting path for C2, thus shortening the time taken for the capacitor to discharge and trigger Tr2, which does exactly the same for C3 in the next half cycle. As it can be seen, if the resistance is high in VR2, VR3, the frequency is hardly altered, but as the resistance is decreased, C2, C3 alternately discharge through it, shortening their discharge times and therefore the frequency. The two pots used were actually salvaged from ex-equipment computer circuit boards, as were the transistors and some of the resistors.

The output from this multivibrator is picked up from the collector of Tr1 and is fed via C1 to the volume control of the amplifier.

The amplifier used by the author was taken from

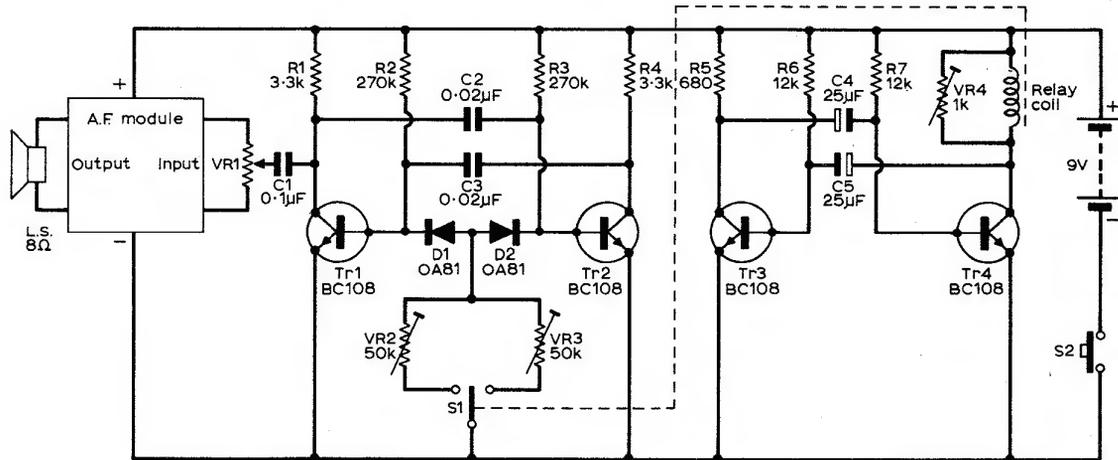


Fig. 1: The circuit of the two tone door alarm.

THE CIRCUIT

The circuit comprises three main parts; two multivibrators and an audio amplifier. One of the multivibrators controls the rate of switching of the two notes, Tr3 and Tr4 provide this function and C4 and C5 control the rate of change. Tr4 has a reed switching coil in the collector circuit and a 1kΩ preset potentiometer is wired across this. VR4 controls the division between the two notes; it can be set for equal division or for any other spacing.

The second multivibrator is designed to operate at audio frequencies, the actual notes generated depend on the settings of VR2 and VR3.

an old battery tape recorder but any of the commercial amplifiers are suitable such as the Eagle EG 2004 250mW model. Many simple audio amplifier circuits have been published in Practical Wireless and these are also suitable.

Construction is a matter of personal choice but all the components can be mounted on plain Veroboard, the main wiring being provided using Cir-Kit strip. The existing bell wiring can be used and the bell push is represented by S2.

Once completed VR2 and VR3 can be adjusted for a pleasant couple of notes and VR4 adjusted for the balance between them. ■

THE Medium Wave Column

CHARLES MOLLOY

THE new station at Kinshasa in the Congo has been widely heard in the U.K. with African style music and announcements in French. Listen before 0300hrs GMT while the channel is clear of QRM. On weekdays Deutschlandsender is off the air from 0130 to 0300hrs but on Sunday there is only a 15 minute break from 0245hrs. The north/south path is usually good during the summer. Gerry Wood from a QTH near Cape Town reports regular reception of the more powerful Europeans using a modified car radio.

Medium Wave stations in Newfoundland are often conspicuous in summer from 0200hrs GMT until sunrise. The strongest signal is from CBN 640kHz in St. John's which is the outlet of the Canadian Broadcasting Corporation. Satellites CBNA 610kHz in St. Anthony and CBNM 740kHz in Marystown usually carry the same programme which is announced as the CBC Radio Network. VOXM 590kHz in St. John's is the key station of a commercial network which is also represented by CKCM 620kHz in Grand Falls and CHCM 560kHz in Marystown. All three carry the same programme and have a common identification. CJOX 710kHz in Grand Bank and CJCN 680kHz Grand Falls relay the CJON Radio Service which has its chief station CJON 930kHz in St John's. Newfoundlanders are logged regularly in this country and are often noted

before sunrise as a cluster at the bottom of the band.

Broadcasting Stations of the World Part 2 is published at intervals of approximately 18 months by the Foreign Broadcasting Information Service of the United States Government. All known broadcasting stations in the long, medium and shortwave bands in the range 150kHz to 26MHz, in order of frequency, with some data on location, power and station identification, are listed except for MW stations in the U.S.A. The latest edition of the FBIS list, correct to January 1971, is now available. It can be obtained from the Superintendent of Documents, Government Printing Office, Washington DC20402, U.S.A., by quoting catalogue number PX EX 7.9.971 part 2, and sending a money order for \$2 in U.S. currency.

Leslie Smith of Witham, Essex, R. T. Johnston of Christchurch, Hants, and Frank Jeniker of Spur Tree Jamaica have written asking for information on MW loops. Anyone who would like to see an illustration of a loop should write to Radio Nederland and ask for the Frame Aerial Data Sheet. It can be obtained free of charge from Postbus 222, Hilversum, Holland.

Arthur Cushen of Invercargill, New Zealand, has recently verified his 2000th medium wave station. He sends the following details which will surprise many DXers. His QSLs are from stations in 132 different countries and 114 of them are from Europe and include every country. Arthur, who is blind, was awarded the MBE for his services to broadcasting. DXers, including the writer, who met him during his visit to this country in 1969 will be happy to congratulate him on his latest achievement. All reports and information concerning Medium Wave DXing may be sent to me at the following address:

Practical Wireless Editorial Department, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD.


Charles Molloy



WHAT A BIND!

Well, it is a bit of a bind if your issues of P.W. get all dog-eared and grubby just because you have not lashed out 85p for a special Practical Wireless binder!

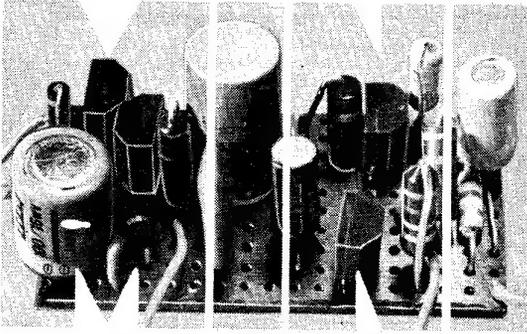Binders are sent post free and when ordering, please state the volume number required (if at all) and send your order to: Binding Department, Practical Wireless, Carlton House, 66-69 Great Queen Street, London, WC2B 5DD



amplifier

R.A.PENFOLD

ALTHOUGH integrated circuits have largely taken over in the field of miniature electronics, it is still possible to construct a miniature audio amplifier which is economically competitive with an i.c. and which will give far more satisfaction to build.

The amplifier which is the subject of this article measures approximately 2 x 1 x 1 inches, and will deliver about 250mW to a 25Ω impedance loudspeaker. Its most obvious use is in the role of the audio stages of a small transistor radio, but it may be used for many other purposes. It is possible to buy all the components (excluding the various miscellaneous items) for under £1.

THE CIRCUIT

The circuit is given in Fig. 1. Four transistors are used, and these are all silicon types. Tr1 is an NPN, low noise type, which is used as the input stage. The input signal is coupled to the base of this transistor by C1, after having first passed the volume control. It is biased by the potential divider formed by R1 and R2, R3 being the load resistor.

C2 is a frequency correcting capacitor which is used to give negative feedback at high frequencies, where it has a lower reactance, and thus attenuating the higher frequencies.

Tr2 is a PNP type, and is used as the driver transistor. Biasing is performed by R4 and R5. As R5 is connected to the junction of the emitters of the two output transistors, as the voltage at this junction goes positive and negative with the input signal, the biasing of Tr2 will alter, and thus negative feedback is applied. R6 and R7 allow a small current to flow through the output transistors under quiescent conditions. This prevents crossover distortion which would otherwise occur as the input pulses change from one polarity to another. R6 and R7 also form the load for the driver stage.

OUTPUT STAGE OPERATION

A complementary output pair are used, the BC159 being a PNP transistor, and the BC147 being the NPN type. These transistors are used as emitter

followers and so have a very low output impedance, and thus require no output transformer. The bases of these transistors are directly coupled to the driver transistor.

When a negative pulse is applied at the bases, the NPN transistor will shut off, and the PNP one will amplify, and its resistance will fall accordingly. This will cause the voltage at the junction of the two emitters to swing down to a very low level.

If a positive pulse is applied to the transistors, the PNP one will shut off, and the resistance of the

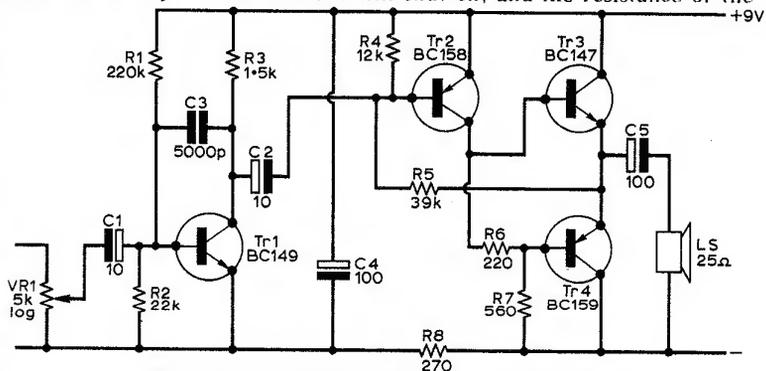


Fig. 1: The circuit of the Mini Amplifier. Note that Tr3 and Tr4 should preferably be matched transistors.

★ components list

Resistors

R1	220kΩ	R5	39kΩ
R2	22kΩ	R6	220Ω
R3	1.5kΩ	R7	560Ω
R4	12kΩ	R8	270Ω

All resistors ½W, 10% types.

VR1 5kΩ log. pot. with switch

Capacitors

C1	10μF 6V	C4	100μF 10V
C2	10μF 6V	C5	100μF 10V
C3	5000pF		

Semiconductors

Tr1	BC149	Tr3	BC147
Tr2	BC158	Tr4	BC159

Miscellaneous

Veroboard, 2 x 1", 0.1" matrix.
15-30Ω impedance loudspeaker.
9V battery with battery clips.

—continued on page 425

STEPHENS

**ELECTRONICS,
P.O. BOX 26,
AYLESBURY, BUCKS.**

**SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded.**

NOW INTRODUCE COMPONENTS

TELEVISIONS ELIZABETHAN TW12LZ PORTABLE TV

12 in. screen model complete with loop aerial system. Operates on 230/240v. AC or 12v. DC battery or 12v. DC car battery. All transistor covering UHF BBC1, BBC2 and ITA Channels 21-70. Size 15 in. x 12 1/2 in. x 12 in. Weight 16 1/2 lbs. List Price £75. OUR PRICE ONLY **£52.97**, Carr. £1.

Also the 14 in. Elizabethan Television Model No. F.14 (L2). OUR PRICE **£56.50**, Carr. £1.

MULTIMETERS AND OSCILLOSCOPES TWO NEW OSCILLOSCOPES FROM RUSSIA CI-5 SINGLE BEAM OSCILLOSCOPE

10 mc/s passband, triggered sweep from 1 µsec. to 3 millise. Free running time base from 20 c/s to 200 kc/s. Built-in time marker and amplitude calibrator, 3-in. cathode ray tube with telescopic viewing hood. **£39.00**

CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mc/s passband. Separate Y1 and Y2 amplifiers, rectangular 5 in. x 4 in. cathode ray tube. Calibrated triggered sweep from 0.2 µsec. to 100 milli-sec. per cm. Free running time base 50 c/s to 1 mc/s. Built-in time base calibration and amplitude calibrator. **£87.50**
Full details on request. Full servicing facilities and spares available.

TWO NEW AC/DC MULTIMETERS FROM RUSSIA

TYPE 4313—High sensitivity for general electronic and TV-radio repair applications. Sensitivity: 20,000 o.p.v. DC and 2,000 o.p.v. AC.

DC ranges: 75mV-1.5-3-7.5-15-30-60-150-300-600V. 60-120-600µA-3-15-60-300mA-1.5 Amp.

AC ranges: 1.5-3-7.5-15-30-60-150-300-600V. 600µA-3-15-60-300mA-1.5A.

Resistance: 0.5-5-50-500kΩ.

Capacity and Transmission level scales.

Accuracy: 1.5% DC; 2% AC.

PRICE, with carrying case and leads, **£10.50**.

Both instruments have knife-edge pointers and mirror scales.

TYPE 4312—Low sensitivity (667 o.p.v.) extremely sturdy instrument for general electrical use.

DC ranges: 0.3-1.5-7.5-30-60-150-300-600-900V and 75mV; 300µA-1.5-6-15-60-150-600mA-1.5-6A.

AC ranges: 0.3-1.5-7.5-30-60-150-300-600-900V. 1.5-6-15-60-150-600mA. 1.5-6A.

Resistance: 0.2-3-30kΩ.

Accuracy: DC 1%; AC 1.5%.

PRICE, with carrying case and leads, **£9.75**.

BEST QUALITY CAPACITORS WIMA DUROLIT

Capacitance	Working Voltage	Tolerance ±20% Net
1000 pF	630	25p pack of 5
1500 pF	630	25p pack of 5
2200 pF	630	25p pack of 5
3300 pF	630	25p pack of 5
4700 pF	630	25p pack of 5
6800 pF	630	27p pack of 5
0.01 µF	630	29p pack of 5
0.015 µF	630	29p pack of 5
0.022 µF	630	29p pack of 5
0.033 µF	630	33p pack of 5
0.047 µF	630	40p pack of 5
0.068 µF	630	42p pack of 5
0.1 µF	630	50p pack of 5
0.15 µF	630	56p pack of 5
0.22 µF	630	67p pack of 5
470 pF	1000	29p pack of 5
680 pF	1000	29p pack of 5
1000 pF	1000	25p pack of 5
1500 pF	1000	25p pack of 5
2200 pF	1000	27p pack of 5

WIMA TROPYFOL

Capacitance	Working Voltage	Tolerance ±20% Net
47 pF	400	21p pack of 5
68 pF	400	21p pack of 5
100 pF	400	21p pack of 5
150 pF	400	21p pack of 5
220 pF	400	21p pack of 5
330 pF	400	21p pack of 5
470 pF	400	21p pack of 5
680 pF	400	21p pack of 5
1000 pF	400	17p pack of 5
1500 pF	400	17p pack of 5
2200 pF	400	17p pack of 5
3300 pF	400	19p pack of 5
4700 pF	400	19p pack of 5
6800 pF	400	19p pack of 5
0.01 µF	400	21p pack of 5
0.015 µF	400	21p pack of 5
0.022 µF	400	23p pack of 5
0.033 µF	400	23p pack of 5
0.047 µF	400	25p pack of 5
0.068 µF	400	27p pack of 5
0.1 µF	400	33p pack of 5
0.15 µF	400	44p pack of 5
0.22 µF	400	46p pack of 5
1500 pF	630	21p pack of 5
2200 pF	630	21p pack of 5
3300 pF	630	21p pack of 5
4700 pF	630	21p pack of 5
6800 pF	630	23p pack of 5
0.01 µF	630	25p pack of 5
0.015 µF	630	25p pack of 5
0.022 µF	630	27p pack of 5
0.033 µF	630	31p pack of 5
0.047 µF	630	36p pack of 5
0.068 µF	1000	21p pack of 5
0.1 µF	1000	21p pack of 5
0.15 µF	1000	23p pack of 5
0.22 µF	1000	23p pack of 5
4700 pF	1000	25p pack of 5
6800 pF	1000	27p pack of 5
0.01 µF	1000	27p pack of 5
0.015 µF	1000	31p pack of 5

+ 5p PER PACK OF 5

TOP-QUALITY CARBON FILM RESISTORS

Type	Watt	Tolerance	Ohmic Range From To	Net
WP0131	1/8W	±5%	5-1 330 K	6p per 10 24p per 25 80p per 100
WP051	1/2W	±5%	10 10 M	6p per 10 24p per 25 80p per 100 P. & P. 5p P. & P. 5p P. & P. 4p

**ALL ITEMS ADVERTISED IN LAST
MONTH'S ISSUE ALWAYS IN
STOCK FOR SAME DAY DISPATCH**

**TERMS, CASH WITH ORDER ONLY. POST AND
PACKING PAYABLE ON ORDERS UP TO £6, AFTER
THAT, FREE EXCEPT C.R.T.'s.**

SPECIAL PURCHASE!

BRAND NEW FM MULTIPLEX STEREO DECODER UNITS.

Manufactured by PHILIPS. Size 9" x 3 1/4" x 1 1/2". All transistors 25v. at 6 mA. Supplied prealigned with full circuit diagram and connection details. \$24 each Post Free

FEW ONLY—LEAK MK I TRANSCRIPTION PICK-UP ARMS

Using the world famous gimbal pivot system. Complete unit less pick up head £2.60 P. & P. 20p


INPUT MATCHING TRANSFORMER

Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/2" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick up from low to high impedance or vice versa. 75p each Post Free

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS

For TO3, complete with mica's & bushes. Size 2 1/2" x 3/8" approx. 25p pair P. & P. 5p.

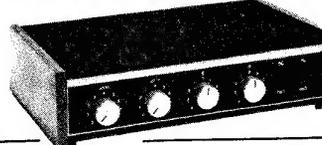HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY REPLY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for use with speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 6 ohms. Frequency response ±3dB 12-20,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth: ±3dB 12-15,000 Hz. Bass boost approx. to ±12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25v. at 1.9 amp. Overall Size 19" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.B.

PRICES
AMPLIFIER KIT . . . £10-50 P. & P. 15p
POWER PAIR KIT . . . £3-00 P. & P. 30p
CABINET . . . £3-00 P. & P. 30p
(Post Free if all units purchased at same time)

Full after sales service.
Also available ready built and tested £20-50. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium power Hi-Fi Discosque use, etc.

SPECIAL PURCHASE OF MANUFACTURERS SURPLUS!

All transistor F.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. FM RF Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s) output with optional AFC connection. Built on printed circuit panel and fully screened. Extremely stable over range 88-108Mc/s. Brand new and pre-aligned. Size 2 1/2" h x 1 1/2" w x 2 1/4" d. For 6v. D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER. Only £2.25 post free. Connection details supplied.

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/8 in. FIVE for 50p. P. & P. 13p.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 25 1/2 in. approx. Maximum diameter 3/8 in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 6in. long x 3 1/2 in. wide x 3 in. deep. Price £1-75 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1-38. P. & P. 30p. Tapped Primary 900-220-240v. Sec. 21.5v. at 500mA. 65p. P. & P. 15p.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tigran/Uynal front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitter with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £8.40 Carr. 65p

Cabinet Available Separately £4-50 Carr 60p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £6-50 Carr. 65p

LOUDSPEAKER BARGAINS

3" 4 ohm 50p. P. & P. 5p. 5in. 3 ohm 80p. P. & P. 15p. 7 x 4in. 3 ohm £1-05. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1-62. P. & P. 20p. E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet £2-10 (13 ohm £2-25). P. & P. 30p. E.M.I. 13 x 8in. 3 or 15 ohm with two built in tweeters and crossover network £4-20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2-25 P. & P. 30p.

BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well known British maker. Now with Hifix ceramic ferrobar magnet assembly £5-50. Guitar models: 25w. £6-50, 35w. £8-50. P. & P. 38p. E.M.I. 3in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 98p each. P. & P. 13p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm £2-20. P. & P. 30p.

35 ohm SPEAKERS 3in. only 65p. P. & P. 13p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1-75 yd., our price 75p yd. length. P. & P. 15p (min 1 yd.) S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE £2-95. P. & P. 15p.

SINGLE HEADPHONE. With aluminium headband. Approx. 200 ohm, 25p. P. & P. 8p.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 98p. P. & P. 8p

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1-05. P. & P. 8p

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 24dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price 88p. P. & P. 13p.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST. Fitted mono T/O stylus and cartridge for LP/78. ONLY £1. P. & P. 13p.

QUALITY RECORD PLAYER AMPLIFIER MK II. A top quality record amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £3-75 P. & P. 40p.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4-88 P. & P. 50p.

DELUXE QUALITY PORTABLE R/P CABINET MK II. Unmet non-board size 14 x 12 in. clearance 2in. below 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8 in. PRICE £3-98. P. & P. 50p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF85 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7-97 P. & P. 65p. Also available ready built and tested complete with std. input sockets, £9-97. P. & P. 65p.


BRAND NEW TRANSISTOR BARGAINS. GET 15 (Match pair, 75p; V14 50p; OC71 25p; OC76 30p; AF117 15p; 90339 (NPN) 15p. Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 £1-25; ORP12 Cadmium Sulphide Cells 53p. All post free.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Match pair, 75p; V14 50p; OC71 25p; OC76 30p; AF117 15p; 90339 (NPN) 15p. Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 £1-25; ORP12 Cadmium Sulphide Cells 53p. All post free.

SPECIAL PURCHASE! SPEAKER CABINET FROM FAMOUS MAKER!

Beautifully made all wooden construction cabinet with medium walnut finish front, gold anodised expanded aluminium grille and dark sides. Approx. size overall 11 1/2" high x 5" deep x 13 1/2" wide at base. Easily removable handle cut out for 8" speaker. Fibre board back. Could accommodate amplifier or radio together with speaker. An expensively made cabinet at a give away price. LIMITED NUMBER ONLY £1-38 Post Free.

DE LUXE STEREO AMPLIFIER

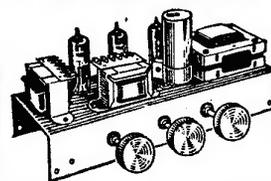

Valve line up: 2 x ECL86 Triode Pentode, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11 1/2" x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £8-92 P. & P. 45p

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £6-97 Carr. 60p. With stereo cartridge £7-97 Carr. 50p.

SUITABLE PLINTH UNIT FOR ABOVE with rigid plastic cover. £5-75 complete P. & P. 60p.

LATEST GARRARD MODELS. All types available 1025-3025, 3025, 3000, AT60 etc. S.A.E. for latest PRICES! PLINTH UNITS cut out for Garrard Models, 1025, 2025, 2000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5-75 complete. P. & P. 50p.

LATEST ACOS GP91/18C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

SONOTONE STAEC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST BONNETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78. £1-65 P. & P. 10p.

LATEST BONNETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

LATEST ACOS GP91/18C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

SONOTONE STAEC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST BONNETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78. £1-65 P. & P. 10p.

LATEST BONNETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

LATEST ACOS GP91/18C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

SONOTONE STAEC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST BONNETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78. £1-65 P. & P. 10p.

LATEST BONNETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

LATEST ACOS GP91/18C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.


SONOTONE STAEC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST BONNETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78. £1-65 P. & P. 10p.

LATEST BONNETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

LATEST ACOS GP91/18C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

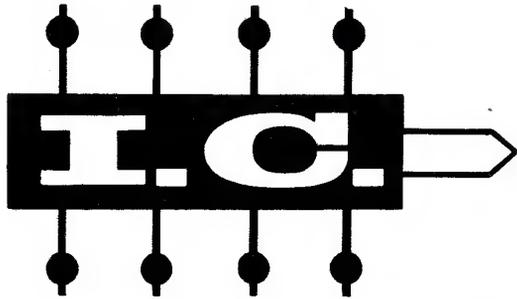SONOTONE STAEC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.



OF THE MONTH

L.A.J. IRELAND

Number 23

RCA CA3062 Photo-detector/amplifier


At the outset of the present series of articles it was pointed out that full constructional details could not be given in each article due both to the flood of new devices released on the market and the complexity of some of the i.c.'s reviewed. As a result some inexperienced constructors may have found themselves uncatereed for as it would be too much to expect of them to draw up their own printed circuit and layout designs. This month, however, a very useful i.c. is reviewed and a layout pattern illustrated so that a relatively inexperienced constructor may approach it with confidence. Few external components are needed so that success is virtually guaranteed.

Circuit

Photocell devices have always fascinated constructors as their uses are so varied and diverse from such things as counters and position sensors to the more familiar burglar alarm units. Considered in this month's article is the RCA type CA3062, described as a photo-detector and power amplifier and which is particularly suited for operations from either visible light sources or the newer infra-red Gallium Arsenide emitters.

Simple light dependent resistor control circuits suffer from two major drawbacks. First of all their response time is slow and secondly small variations in light intensity are not registered unless amplification follows. The photo-transistor is a much more

sensitive device especially when a pair of them are connected in a super-alpha configuration as in the present design. In fact the photo transistors themselves give a variation in current from a mere 4 microamps in the absence of light to 2 mA with a light intensity of 100 lumens per sq. ft. This current variation is usually used to develop a corresponding variable voltage across a 22kΩ load resistor which in turn controls the biasing on either Tr2 or Tr3.

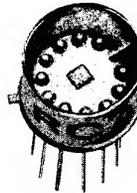

This photograph of the CA3062 is 2½ times its actual size. The i.c. itself can be seen in the centre of the package which is a modified 12-lead TO-5 style.

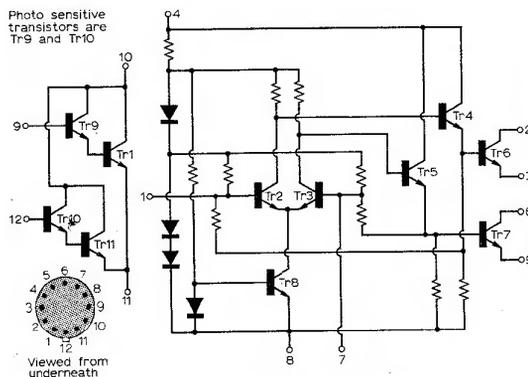


Fig. 1. Circuit of the photo-detector amplifier.

In Fig. 1 a complete circuit diagram of the unit is shown and it can be seen that Tr2 and Tr3 form a differential pair with Tr8 acting as a constant current source. From this configuration it follows that phase inversion occurs between the collectors of Tr2 and Tr3 which in turn control the current in the output pair Tr6 and Tr7 via Tr4 and Tr5 which prevent loading of the differential pair. Some constructors may notice the great similarity in circuit design between this i.c. and an earlier one manufactured by the same company, type CA3020, and featured in the May 1968 issue of P.W. The main amplifier in both are almost identical except for the inclusion of a constant current sink Tr8 in the CA3062 replacing a simple resistor in the earlier i.c. to provide better stability and greater amplification. The same type of specially fabricated output transistors are used in each to enable them to carry the higher currents they draw as output transistors. In fact, up to 100 mA can be taken from the output stage and this is more than adequate to directly drive a relay or thyristor.

Operation

For proper on-off operation the voltage on either pin 1 or pin 7 (either may be connected to the photo transistors) should not exceed 3 volts. This can be achieved by limiting the current through the photo transistors or on the other hand by inserting a

clamping diode between whichever pin is used and earth.

It should also be noted that the device can also respond linearly to light variations by connecting a potential divider network between pin 6 and earth with the tap joined to pins 9 and 12 (two 20M Ω). However, in this mode of operation the output current is limited considerably as greater heat dissipation takes place in the silicon chip.

Practical Circuit

A suitable layout pattern for the photo-detector is shown in Fig. 2 and use could profitably be made of a TO-5 12 lead i.c. holder to prevent damaging the i.c. during the soldering process.

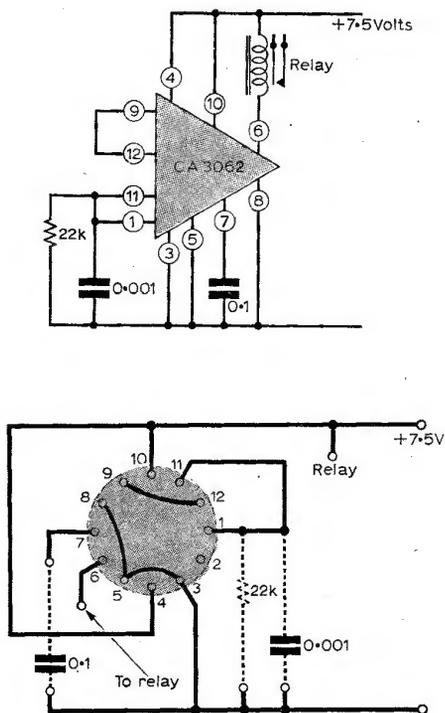


Fig. 2. The top circuit shows the two capacitors, one resistor and the relay needed to provide a practical circuit around the CA3062. The bottom diagram is a suggested layout for a circuit board using a TO5 12-lead i.c. holder.

In conclusion it may be pointed out that this device can provide light beam detection of up to 100 yards when used in conjunction with the new Helium-Neon lasers and which in the past year or so have appeared on the American market and no doubt will eventually filter over to this side of the Atlantic. The prohibitive prices of these devices severely limited their uses to industry and research centres but now one of these laser tubes sells for £20 and a suitable power supply to operate it can be built for under £5. No doubt this offers intriguing possibilities especially in the field of intrusion alarms and we can continue to expect in the future further developments along these lines.

MINI-AMP—continued from page 422

NPN one will fall. This will cause the voltage at the junction of the two emitters to swing to a very high level.

In this way the emitter voltage will swing up and down with the input signal. This voltage swing is coupled to the speaker via C5.

Under quiescent conditions the voltage at the emitter junction should be approximately half the supply voltage. This voltage is set by the values of resistors R4 and R5.

If the amplifier is to work properly, the output transistors should be fairly evenly matched. These transistors are not generally available in matched pairs, but some semiconductor suppliers will match transistors, although there may be a small surcharge for this.

Current limiting resistors are often connected between the emitters of the output transistors and the output capacitor, to prevent thermal runaway. Silicon transistors, however, do not suffer from runaway to anything like the extent that germanium types more usually found in this type of circuit do, and these resistors were found to be completely unnecessary.

Although the amplifier will operate using speaker impedances outside the range 15 Ω to 30 Ω , this is not recommended as it will mean either a loss in available output power, or an increase in the level of distortion.

CONSTRUCTION

The amplifier is built on a 2 x 1 inch piece of 0.1 inch matrix Veroboard, with the copper strip running lengthwise. This has to be cut from a larger piece of Veroboard using a small hacksaw. A wiring diagram of the panel is given in Fig. 2.

Great care will have to be taken with the connections to the Veroboard, and this project should not be attempted by the complete beginner. A soldering iron with a very fine bit is required, and some sort of stand to hold the board steady will be found to be extremely helpful.

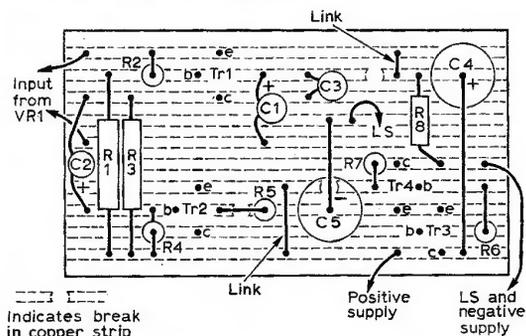


Fig. 2: The component layout on Veroboard.

All transistors are fitted with special leadouts which plug into the Veroboard. These leadouts are very short, and although silicon transistors are very hardy, these should be soldered quickly into place, and should be left until last.

The capacitors will have to be subminiature types, and like many of the components may have to be mounted vertically so as to fit into the available space.

INCREASE YOUR KNOWLEDGE



Established 1891


MANY COURSES TO CHOOSE FROM incl.
 RADIO & TV ENGINEERING & SERVICING,
 TRANSISTOR & PRINTED CIRCUIT SERVICING,
 COLOUR TV SERVICING, ELECTRONICS,
 NUMERICAL CONTROL ELECTRONICS,
 TELEMETRY TECHNIQUES, CONTROL SYSTEMS,
 ELECTRONICS FOR AUTOMATION,
 COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

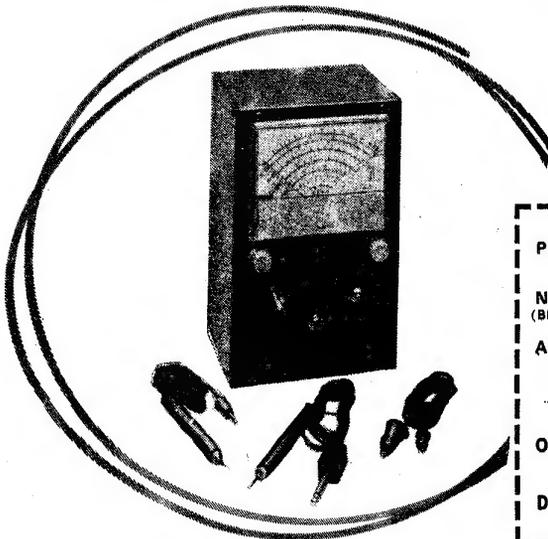C. & G. Telecommunication Technicians' Certificates
 C. & G. Electronic Servicing
 R.T.E.B. Radio/TV Servicing Certificate
 Radio Operator Certificates
 Radio Amateurs' Examination
 General Certificate of Education, etc.

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN **ICS** COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio, television and electronics **PLUS** details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME
 (BLOCK CAPITALS PLEASE)

ADDRESS

.....

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS
 Dept. 170, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8

9/71

BI-PAK SEMICONDUCTORS

SILICON RECTIFIERS—TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	4p	5p	5p	7p	14p	21p	47p
100	4p	5p	5p	7p	14p	21p	75p
200	5p	5p	5p	14p	20p	24p	21p
400	6p	13p	7p	20p	27p	37p	£1.25
600	7p	10p	23p	34p	45p	£1.85	
800	10p	17p	13p	25p	37p	55p	£2
1000	11p	25p	15p	33p	46p	65p	£2.50
1200	—	33p	—	33p	57p	75p	—

NEW LOW PRICED TESTED S.C.R.'s

PIV	1A	3A	7A	10A	16A	30A
	TO5	TO66	TO66	TO48	TO48	
50	23p	25p	47p	50p	53p	£1.15
100	25p	33p	53p	58p	63p	£1.40
200	35p	37p	57p	61p	75p	£1.60
400	43p	47p	67p	75p	93p	£1.75
600	53p	57p	77p	97p	£1.25	—
800	63p	70p	90p	£1.20	£1.50	£4

2A POTTED BRIDGE RECTIFIERS. 200V. 50p

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 75p each.

UNIUNCTIONS
 UT48. Eqt. 2N2646 Eqt. TI543. BEN3000
 27p each. 25-99 25p. 100 20p

NPN SILICON PLANAR
 BC107/8/9 10p 50-99 9p. 100 up 8p each.
 1,000 off. 7p each. Fully tested and coded TO-18 case.

ADI161 NPN ADI162 PNP
 MATCHED COMPLEMENTARY PAIRS OF
 GERM. POWER TRANSISTORS
 OUR LOWEST PRICE OF 63p PER PAIR

Sil. trans. suitable for P.E. Organ. Metal TO-18 Evt. ZTX300 5p each. Any Qty.

TRIACS.

	2A	6A	10A
VBOM TO5	TO66	TO48	
100	50p	63p	£1
200	70p	80p	£1.25
400	90p	£1	£1.60

VBOM—Blocking voltage in either direction.

SILICON DIAC
 For use with Triacs
 BR100 37p each

BRAND NEW TEXAS GERM. TRANSISTORS
 Coded and Guaranteed

Pak No.	EQVT.
T1	8 2G371A OC71
T2	8 2G374 OC72
T3	8 2G374A OC81D
T4	8 2G381A OC81
T5	8 2G382T OC82
T6	8 2G344A OC44
T7	8 2G345A OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G347 AF17

All 50p each pack.

CADMIUM CELLS
 ORP60, ORP61 40p each

PHOTO TRANS.
 OCP71 Type 43p


FREE
 One 50p Pack of your own choice free with orders valued £4 or over.

SIL. G.P. DIODES
 300mV 30 50p
 40PIV (Min.) 100 £1.50
 Sub-Min. 500 25
 Full Tested 1000 £3
 Ideal for Organ Builders

ANOTHER BI-PAK FIRST!

THE NEW SGS EA 1000 AUDIO AMPLIFIER MODULE

★ **GUARANTEED NOT LESS THAN 3 WATTS RMS**
 Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TAA621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, answering applications and phone answering machines. OTHER USES—portable applications where supply rails as low as 9V are of prime importance.

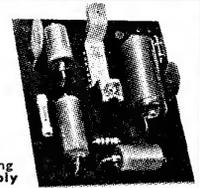

- Sensitivity 40 mV for 1 watt VOLTAGE GAIN 40 dB but can be varied up to 73 dB for some applications.
- Signal to Noise Ratio 86 dB.
- Frequency response better than 50 Hz to 25 KHz for —3 dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.
- Overall Size 2" x 3" x 1".

● Typical Total Harmonic distortion at 1 watt less than 1%.
 ★ Supply Voltage (Vs)—24V 15 ohm load.
MODUL TESTED AND GUARANTEED.
 Qty. 1-9 10-25 Larger quantities
 Price each £2.63 £2.28 quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

"Q" PAKS QUALITY TESTED SEMICONDUCTORS

Pack Qty. per No. pack	Description	Price
Q 1 20	Red spot trans. P.N.P.	50p
Q 2 16	White spot R.F. trans. P.N.P.	50p
Q 3 4	OC 77 type trans.	50p
Q 4 6	Matched trans. OC44/45/81/81D	50p
Q 5 4	OC 75 transistors	50p
Q 6 4	OC 72 transistors	50p
Q 7 4	AC 128 trans. P.N.P. high gain	50p
Q 8 4	OC 268 trans. P.N.P.	50p
Q 9 7	OC 81 type trans.	50p
Q 10 7	OC 71 type trans.	50p
Q 11 2	OC 127/128 Comp. pairs PNP	50p
Q 12 3	AF 116 type trans.	50p
Q 13 3	AF 117 type trans.	50p
Q 14 3	OC 171 H.F. type trans.	50p
Q 15 5	2N2926 Sil. Epoxy trans.	50p
Q 16 2	OC 160 low noise Gern. trans.	50p
Q 17 3	NPN 1 ST141 & 2 ST140	50p
Q 18 4	Madt's 2 MAT 100 & 2 MAT 120	50p
Q 19 3	Madt's 2 MAT 101 & 1 MAT 121	50p
Q 20 4	OC 44 Gern. trans. A.F.	50p
Q 21 3	AC 127 NPN Gern. trans.	50p
Q 22 20	NKT trans. A.F. R.F. coded	50p
Q 23 10	OA202 Sil. diodes sub-min.	50p
Q 24 8	UA 81 diodes	50p
Q 25 6	IN914 Sil. diodes 75PIV 75mA	50p
Q 26 8	OA95 Gern. diodes sub-min. IN 69	50p
Q 27 2	16A 600PIV Sil. Rects. 1S425R	50p
Q 28 2	Sil. power rect. BYZ 15	50p
Q 29 4	Sil. trans. 2x2N696, 1x2N697, 1x2N698	50p
Q 30 7	Sil. switch trans. 2N706 NPN	50p
Q 31 6	Sil. switch trans. 2N708 NPN	50p
Q 32 3	PNP Sil. trans. 2x2N1131, 1x2N1132	50p
Q 33 3	Sil. NPN trans. 2N1171	50p
Q 34 7	Sil. NPN trans. 2N2369, 500MHZ	50p
Q 35 3	Sil. NPN TO-5 2x2N2904	50p
Q 36 7	2N3646 TO-18 plastic 300MHZ NPN	50p
Q 37 3	2N3053 NPN Sil. trans.	50p
Q 38 7	PNP trans. 4x2N3703, 3x2N3702	50p
Q 39 7	NPN trans. 4x2N3704, 3x2N3705	50p
Q 40 7	NPN amp. 4x2N3707, 3x2N3708	50p
Q 41 3	Plastic NPN TO-18 2N3604	50p
Q 42 6	NPN trans. 2N6172	50p
Q 43 7	BO 107 NPN trans.	50p
Q 44 7	NPN trans. 4xBC108, 3xBC109	50p

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at the **EXCLUSIVE LOW PRICES**. T.T.L. Digital SN74N Series fully coded, brand new to Manufacturers' Specifications. Dual In-Line plastic 14 & 16 pin packages.

BI-PAL Order No.	Description	Price and Qty. Prices 1-24 25-99 100 up
BP 00=7400	Quadruple 2-input NAND Gate	23p 20p 15p
BP 01=7401	Quadruple 2-input Positive NAND Gate (with open collector output)	23p 20p 15p
BP 02=7402	Quadruple 2-input Positive NOR Gates	23p 20p 15p
BP 03=7403	Quadruple 2-input Positive NAND Gates (with Open-Collector Output)	23p 20p 15p
BP 04=7404	Hex Inverters	23p 20p 15p
BP 10=7410	Triple 3-input Positive NAND Gates	23p 20p 15p
BP 13=7413	Dual 4-input Schmitt Trigger	24p 20p 15p
BP 20=7420	Dual 4-input Positive NAND Gates	23p 20p 15p
BP 30=7430	8-input Positive NAND Gates	23p 20p 15p
BP 40=7440	Dual 4-input Positive NAND Buffers	23p 20p 15p
BP 41=7441	BCD to decimal nixie driver	87p 77p 67p
BP 42=7442	BCD to decimal decoder (4-10 lines, 1 of 10)	87p 77p 67p
BP 47=7447	BCD-Seven-Segment Decoder/Drivers (15-V Outputs)	£1.40 £1.30 £1.20
BP 50=7450	Expandable dual 2-input AND-OR-INVERT	23p 20p 15p
BP 51=7451	Dual 2-wide 2-input AND-OR-INVERT GATES	23p 20p 15p
BP 53=7453	Quad 2-input Expandable AND-OR-INVERT	23p 20p 15p
BP 54=7454	4-wide 2-input AND-OR-INVERT GATES	23p 20p 15p
BP 60=7460	Dual 4-input Expander	23p 20p 15p
BP 70=7470	Single-phase J-K Flip-Flop	35p 32p 28p
BP 72=7472	Master-slave J-K Flip-Flop	35p 32p 28p
BP 73=7473	Dual Master-slave J-K Flip-Flop	43p 40p 37p
BP 74=7474	Dual 0 type Flip-Flop	43p 40p 37p
BP 75=7475	Quad latch	47p 45p 43p
BP 76=7476	Dual J-K with pre-set and clear	47p 45p 43p
BP 80=7480	Gated Full Adders	47p 45p 43p
BP 81=7481	16-bit read/write memory	£1.35 £1.25 £1.15
BP 82=7482	2-bit Binary Full Adders	£1.30 £1.20 £1.00
BP 83=7483	Quad Full Adder	87p 77p 67p
BP 86=7486	Quad 2 input Exclusive OR Gates	30p 27p 60p
BP 90=7490	BCD decade counter	87p 77p 67p
BP 91=7491	8-bit Shift Registers	£1.21 £1.00 87p
BP 92=7492	Divide-by-Twelve Counters	87p 77p 67p
BP 93=7493	4-bit Binary Counters	87p 77p 67p
BP 94=7494	Dual entry 4-bit shift register	57p 57p 67p
BP 95=7495	4-bit up-down shift register	87p 77p 67p
BP 96=7496	5-bit Parallel in parallel out Shift-Register	£1.10 £1.00 80p
BP100=74100	8-bit Bistable Latches	£1.75 £1.65 £1.55
BP118=74118	Hex Set-Reset Latches	£1.30 £1.20 £1.00
BP121=74121	Monostable Multivibrators	87p 77p 67p
BP141=74141	BCD-to-Decimal Decoder/Driver	87p 77p 67p
BP145=74145	BCD-to-Decimal Decoder/Drivers	£1.80 £1.70 £1.60
BP151=74151	8-bit Data Selectors (with Strobes)	£1.40 £1.30 £1.20
BP153=74153	Dual 4-Line-to-Line Data Selectors/Multiplexers	£1.40 £1.30 £1.20
BP191=74191	Binary Counter reversible	£3.50 £3.25 £3.00

Devices may be mixed to qualify for quantity price. Larger quantities—prices on application. (TTL 74 series only).

Data is available for the above series of I.C.'s in booklet form. PRICE 13p.

LINEAR I.C.'s

Type No.	Case	Leads	Description	Price 1-24 25-99 100
BP201C—SL201C	TO-5	8	G.P. Amp	63p 50p 45p
BP701C—SL701C	TO-5	8	OP Amp	63p 50p 45p
BP702C—SL702C	TO-5	8	OP Amp Direct O/P	63p 50p 45p
BP702—72702	D.I.L.	14	G.P. O.P. Amp (Wide Band)	53p 45p 40p
BP709—72709	D.I.L.	14	High Gain OP Amp.	53p 45p 40p
BP709C—74709C	TO-5	8	High Gain OP Amp.	53p 45p 40p
BP741—72741	D.I.L.	14	High Gain OP. Amp (Protected)	75p 60p 50p
µA708C—µA708C	TP-5	6	P.R.—IF Amp	48p 35p 27p
TAA263	TO-72	4	A.F. Amp	70p 60p 50p
TAA263	TO-74	10	G.P. Amp	70p 75p 70p

TTL INTEGRATED CIRCUITS

Manufacturers' "Full outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00=12x7400N 50p	UIC02= 5x7450N 50p	UIC80= 5x7480N 50p
UIC01=12x7401N 50p	UIC05=12x7450N 50p	UIC82= 5x7482N 50p
UIC02=12x7402N 50p	UIC08=12x7451N 50p	UIC83= 5x7483N 50p
UIC03=12x7403N 50p	UIC09=12x7450N 50p	UIC86= 5x7486N 50p
UIC04=12x7404N 50p	UIC70= 8x7470N 50p	UIC90= 8x7490N 50p
UIC05=12x7405N 50p	UIC72= 8x7472N 50p	UIC92= 8x7492N 50p
UIC10=12x7410N 50p	UIC73= 8x7473N 50p	UIC93= 5x7493N 50p
UIC20=12x7420N 50p	UIC74= 8x7474N 50p	UIC94= 5x7494N 50p
UIC40=12x7440N 50p	UIC75= 8x7475N 50p	UIC96= 5x7496N 50p
UIC41= 5x7441AN 50p	UIC76= 8x7476N 50p	UIC96= 5x7496N 50p

UICX1=25x Ass'd 74's £1.50

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

DTL (Diode Transistor Logic) INTEGRATED CIRCUITS

Manufacturers' "Full outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.
UIC930=12xµA930	UIC948= 8xµA948
UIC938=12xµA938	UIC951= 8xµA951
UIC938=12xµA938	UIC961=12xµA961
UIC935=12xµA935	UIC903= 5xµA903
UIC936=12xµA936	UIC904= 5xµA904
UIC94=12xµA944	UIC907= 5xµA907
UIC945= 8xµA945	UIC909= 5xµA909
UIC946=12xµA946	UIC925 Assorted 930 Series


UIC925 Assorted 930 Series £1.50

Packs cannot be split but 25 Assorted Pieces (our mix) is available as PAK UICX9. Every PAK carries our BI-PAK Satisfaction or money back guarantee. Data Booklet available for the BP930 Series. PRICE 13p


ALL PRICES IN NEW PENCE.
 Please send all orders direct to our warehouse and despatch department.
BI-PAK SEMICONDUCTORS
P.O. BOX 6, WARE, HERTS.
 Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please. *GIRO No. 388-7006

ALL OUR UNTESTED SUPER PAKS ARE STILL AVAILABLE. See previous issue for details or send S.A.E. for LISTS

GOING BACK...

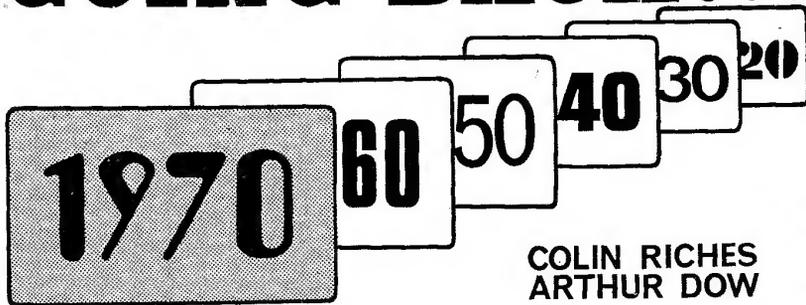

COLIN RICHES
ARTHUR DOW

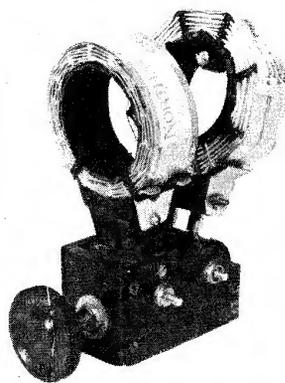

FOLLOWING our brief mention of the type LS3 valve in 'Going Back' for June we were pleased to hear from George Jessop, G6JP, who has been with one of the leading valve manufacturers of this country for many years. George points out that the LS family of valves was introduced to make available larger output powers than were currently available with the 'R' type valve which had first appeared around 1915 (see 'Going Back' July 1971).

'LS' indicated a loudspeaker valve and applied to the earlier series LS1-6 and to several later types such as the LS7, 8, 8A and 9 although these had little in common with the earlier series, having oxide coated filaments and being specially manufactured for the Post Office.

The most famous valve of the early range was undoubtedly the LS5 which was for general purposes while the LS5A was meant for use as an output valve. The higher impedance LS5B completed the range and was intended for use in resistance-capacity coupled stages.

Both the Post Office and the BBC used these valves in their high quality audio amplifiers while, with the radio amateurs, the LS5B reigned supreme in frequency multiplier stages and the LS5 did duty in the power amplifier output stage. G6JP mentions that in 1936 his first 10-metre transmitter used these valves and that a very early 2-metre oscillator, illustrated in "Short Wave Communication" by Ladnor and Stoner (1932), used two 'de-based' LS5's. Since the circular base of the standard LS5 was of metal a considerable reduction in self-capacity was possible by removing the base thus enabling an output of some 5 watts to be obtained from this particular oscillator.

Readers may like to know that this famous range of valves has been graced with CV numbers:


LS5	Metal 4-pin UX base	VT24—CV1636
LS5	Standard British base	VT25—CV1637
LS5A	" " "	VT66—CV1650
LS5B	" " "	VT40—CV1647

All these valves had an anode dissipation of 10 watts but the later LS6A had this figure increased to 25 watts.

Our thanks to George Jessop for all this interesting information and we are sure that if he cared to put his reminiscences on paper they would prove very absorbing reading.

Vintage Equipment

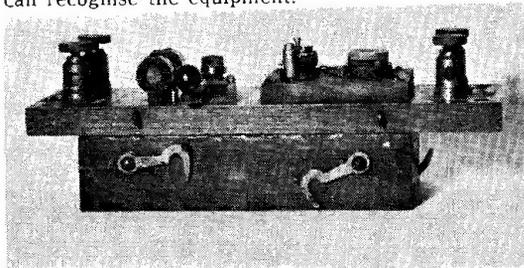One of our correspondents has sent this photograph of an ancient piece of gear and asked us to assist in identifying it. Unfortunately we can't help so we are passing the buck to our older but nevertheless revered readers in the hope that someone can recognise the equipment.



Two of the terminals are marked 'aerial' and 'earth' and the other two 'cell'. A couple of coils, a buzzer and a kniveswitch complete the 'thing'. The switch looks rather like a Morse key and no doubt could be used as such with a bit of ingenuity.

Our correspondent did connect a 1.5 volt 'cell' as instructed and reports "it did no good to our TV set". We can imagine! We think it is a crude transmitter for test purposes which could be left running while a receiver was adjusted. Any other ideas?

Devices

Assuming that one or two readers of 'Going Back' have been coerced into using solid state devices, they have probably endeavoured to follow the advice of their betters by using a heat-sink when soldering the leads of transistors and keeping the metal clips on certain FET's until they are safely tucked in. (The FET's, not the readers!)

However the early users of valves also suffered a barrage of injunctions on how to handle their new toys. The following directions, taken from the wireless press of 50 years ago, should raise a smile or two!

BREVITIES FOR VALVE USERS

1. Remember that your receiving apparatus is not a crude collection of switches, but that the operation of every switch should receive due consideration.

2. Turn on your valves slowly.
3. Do not burn them too brightly.
4. Signals are not necessarily stronger the brighter the valves are lighted.
5. Do not let your valves 'howl'. Your neighbour may report you and you risk having your licence cancelled.
6. Having roughly tuned in on your inductance and accomplished finer tuning with your variable condenser, bear in mind para. 5.
7. Remember there is a proper arrangement for the valves. Interchange them from left to right, having tuned in a station, such as FL, until you find the best position for each.

We are sure that reading these 'instructions' will bring back many memories to those who fiddled about in those pioneering days. At least one could see when a valve had failed which is more than one can do with today's 'devices'!




This year we are sponsoring another Project Autumn competition. The rules have been amended so that the PW "Designer's Trophy 1971" will be awarded to the author of the best constructional article published in PW issues dated July 71 to March 72 inc. This allows submitted articles to be published as soon as possible and for authors to be paid without delay.


SUBMIT YOUR ARTICLES NOW

MAXWELL

by G8DSH

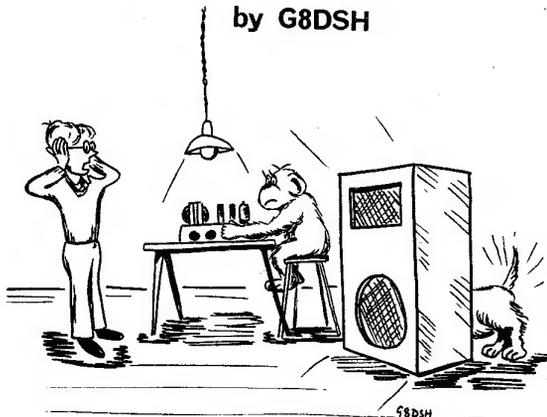

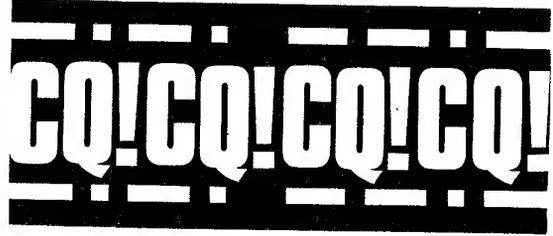"Your bass response is dreadful . . . whatever are you using for a Woofer?"



Items in this section are carried free of charge as a service to readers. We only ask that those making use of the service answer all correspondence resulting and reimburse postage and all reasonable expenses. We cannot guarantee inclusion and requests for inclusion will not be acknowledged. Material for inclusion should be sent to Practical Wireless Editorial, Fleetway House, Farringdon Street, London, E.C.4.

INFORMATION WANTED

- ...circuit diagram for the BCC 715. All costs refunded.—Eskil Persson, Frotunagrand 1, 19400 Upplands Vasby Sweden.
- ...handbook for Admiralty B40 (Murphy) receiver.—M. Johnson, 5 Barons Court, Haverhill, Suffolk.
- ...Eagle RX-80N circuit diagram and handbook—buy or borrow.—Lloyd, 70 Heath Drive, Ware, Herts.
- ...information on the fitting of a magic eye tuning indicator or S-meter to a mains operated superhet 5-valve domestic receiver and any information on issues of P.W. which contain gen on this subject.—J. Towers, 107 Hatfield Galleries, 1068 Burnett Street, Hatfield, Pretoria, Transvaal, South Africa.
- ...any mods. to the B40C receiver.—B. Eames, 58 Fairway Crescent, Allestree, Derby, DE3, 2PE.
- ...circuit or info. required for Tx/Rx type CR1—43044 (TBY8)—borrow or buy —D. Byrne, Kylemore, Endsleigh, Douglas Road, Cork, Eire.
- ...titles of books on electronics for beginners. All correspondence to C. S. Powell, 30 St. Michaels Way, Brundall, Norwich, Norfolk, NR9, 8BZ.
- ...instructions or valve line-up for U.S. war surplus Valve Tester I-177.—Roger Decamps, P.O. Box 24, 2800 Malines, Belgium.
- ...manual or information on Eagle RX80 receiver....R. Williams, 204 Dysart Road, Grantham, Lincs.
- ...address of place where I may get ferrite rod aerial for Bush mains radio AM62 or any gen on how to make same.—S. C. Moodley, 5 Dale Close, Addlestone, Surrey.
- ...information on adding a second manual to the Polyphonic Organ published by P.W. some years ago.—R. Wendrick, 22 Longcliffe Gardens, Nanpanton, Loughborough, Lincs.
- ...instruction manual or any gen on Cossor 1039M oscilloscope.—G. J. Banner, Johnson's Radio, St. Martins Gate, Worcester.
- ...technical information required regarding ex-Army (Mazda) AT20, CV1361 transmitting valve.—P. A. G. Price, 56/57 The Mall, Meerut, Cantonment, U.P., India.
- ...any information at all on the surplus W/S 31 especially the valve line-up, supply connections and handbook.—J. H. McGee, 6 Ripon Road, Newton Hall, Durham, Co. Durham.
- ...any info. on converting the 19 set Rx/Tx.—T. Izard, 41 Clumber Drive, Radcliffe-on-Trent, Notts.
- ...a fault-finding chart No. 2 which was issued with the May 1968 issue of P.W.—Norman Quinn, E.B.E. Limited, Postbus 6275, Rotterdam, Holland.

ISSUES WANTED

- ...issues of P.W. (about 1955) dealing with mods to the R1155.—D. Sager, 92 Marnham Crescent, Greenford, Middx.
- ...P.W. for Jan. and Feb. 1971 and P.E. for Jan. to Oct. 1970 inclusive and P.E. for Jan. and Feb. 1969.—J. R. Rourke, 12 Daisy Grove, Edge Hill, Liverpool, L7, 1QR.
- ...buy or loan the June 1965 issue of P.W. containing the article on PCR Mods.—T. Roche, Arno, Florence Road, Bray, Co. Wicklow, Ireland.

DIGITAL FREQUENCY COUNTER TIMER

continued from page 411

With Q of IC1b high, the signal gate IC2a allows the input signal to produce an output which passes to the counter.

The Q output from IC1b is now low and this clears or resets IC1a directly so that the Q output of IC1a now becomes low and the Q becomes high.

As the Q of IC1b is low, IC2b and IC2c maintain the clamping action of D4.


The condition of IC1a with Q low presets IC1b so that on the next negative going edge of the clock period signal, IC1b will set to Q low, thus producing a continuous high output from the signal gate IC2a and terminating the gate period by isolating the input signal from the counter.

The Q of IC1a and the Q of IC1b are now both high causing IC2b output to be low and IC2c output to be high and rendering the clamping diode D4 non-conducting. The waveforms of the control oscillator are shown in Fig. 8. The state of the control oscillator whilst in the clamped condition is with Tr6 non-conducting and Tr7 conducting. When D4 is made non-conducting, the current through R13 and D3 causes Tr6 to conduct producing a negative-going step at Tr6 collector from +5V to 0V.

TO BE CONTINUED

new

Super IC-12

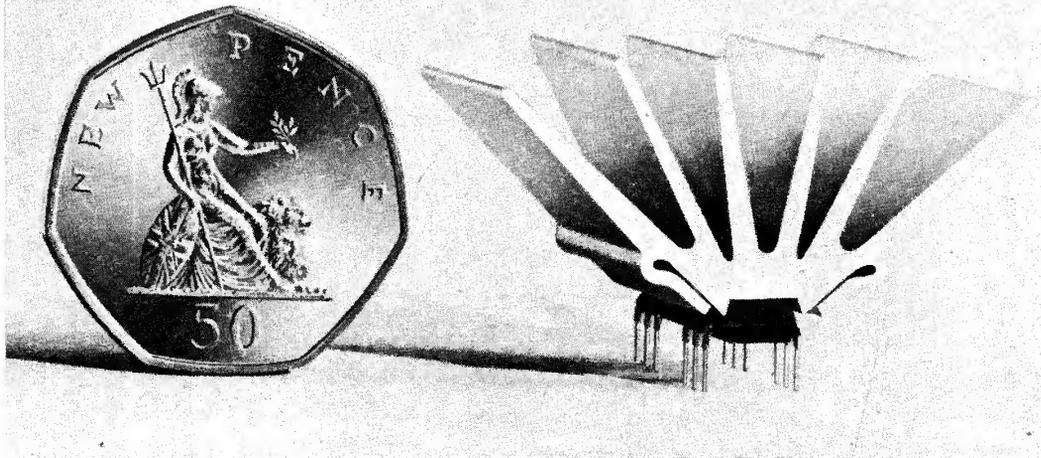

High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

Output power 6 watts RMS continuous (12 watts peak).

Frequency Response 5 Hz to 100KHz \pm 1 dB.

Total Harmonic Distortion Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

Load Impedance 3 to 15 ohms.

Power Gain 90dB (1,000,000,000 times) after feedback.

Supply Voltage 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

Size 22 x 45 x 28 mm including pins and heatsink.

Input Impedance 250 Kohms nominal.

Quiescent current 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.



Price, inc. FREE printed circuit board for mounting.

£2.98 Post free


SINCLAIR GENERAL GUARANTEE
Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

Sinclair Radionics Ltd, London Rd, St. Ives
Huntingdonshire PE17 4HJ
Telephone St Ives (048 06) 4311

sinclair


Sinclair Project 60

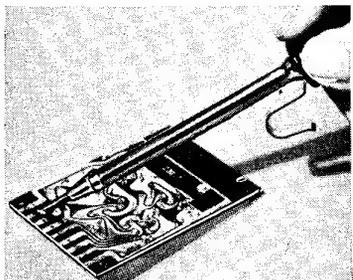The World's leading range of high fidelity modules



Sinclair Radionics Limited, London Road,
St. Ives, Huntingdonshire PE17 4HJ.
Tel: St. Ives (048 06) 4311

sinclair

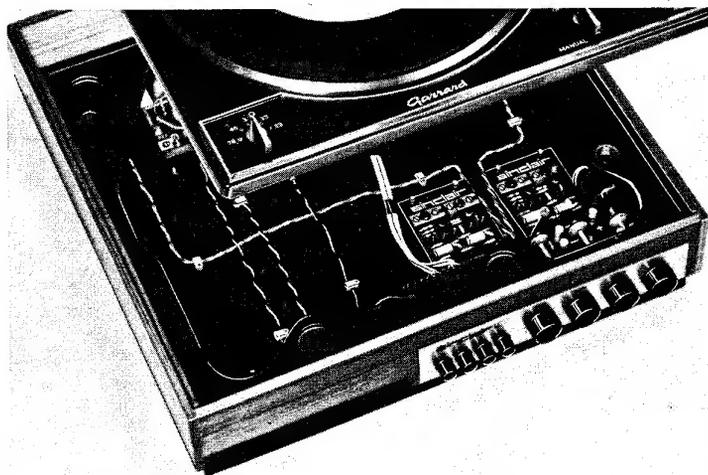

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile—using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all—price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.


Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
20 + 20 W. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
20 + 20 W. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
40 + 40 W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. Filter Unit (£5.98) may be added as required.

from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

Z.30 & Z.50 power amplifiers

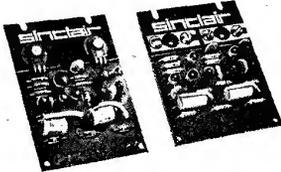

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

Frequency response: 30 to 300,000Hz ± 1 dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size: 14 x 80 x 57 mm.

Z.30

Built, tested and guaranteed with circuits and instructions manual.

£4.48

Z.50

Built, tested and guaranteed with circuits and instructions manual.

£5.48

Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ.5 30 volts unstabilised **£4.98**

PZ.6 35 volts stabilised **£7.98**

PZ.8 45 volts stabilised

(less mains transformer) **£7.98**

PZ.8 mains transformer **£5.98**



The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

Project 60 Stereo F.M. Tuner



First in the world to use the phase lock loop principle

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2 μ V for 30dB quieting; 7 μ V for full limiting. **Squelch level:** 20 μ V. **A.F.C. range:** ± 200 KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz (± 1 dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Mains on; Stereo on; tuning. **Size:** 93 x 40 x 207 mm.

Built and tested. Post free.

£25

Stereo 60 Pre-amp/control unit



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS—Input sensitivities: Radio – up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A curve ± 1 dB; 20 to 25,000 Hz. Ceramic p.u. – up to 3mV; Atx – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE ± 15 to -15 dB at 10 KHz; BASS ± 15 to -15 dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207 mm.

Built tested and guaranteed.

£9.98

A.F.U. High & Low Pass Filter Unit



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less

loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages – rumble (high pass) and scratch (low pass). Supply voltage – 15 to 35V. Current – 3mA. H.F. cut-off (-3 dB) variable from 28KHz to 5KHz. L.F. cut-off (-3 dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm.

Built tested and guaranteed.

£5.98

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

PW.971

THIS MONTH'S NEW BARGAINS

TO 3 Heat Sink. Suitable for most power transistors OC 26 etc. This is aluminium, anodised black for maximum heat dissipation. Supplied complete with mica disc and insulation bushes. Price 10p each or 10 for 80p. Size approx. 2 1/2" x 2 1/2".

18 Volt 600 M.A. Mains Transformers. Miniature type now available, price 56p each or 10 for £5.

3 Core Flex, New Colours. Brown or Ivory blue for neutral, yellow/green for earth. This is completely P.V.C. covered and ribbed, virtually non-kinkable. Suitable for washing machines (without heaters) and all portable tools, lawn mowers etc. Conductor size 23/36. £1 per dozen yards or £10 per 100 yards coil.

Valve Holders at remarkably low prices—moulded construction—made by most famous company.

Price per each

	1-9	10-99	100-999	1,000 up
B7G Flanged	2p	1-5p	1-25p	1p
B7G Skirted	3p	2p	1-75p	1-5p
B7G Printed				
Circuit	2p	1-8p	1-4p	1-6p
B9A Flanged	2p	1-6p	1-3p	1-1p
B9A Skirted	3p	2-5p	2-25p	2p
B9A Printed				
Circuit	2p	1-9p	1-6p	1-3p

MOTOR by A.E.I. 1/20 hp, 1275 rpm self starting for normal A.C. Mains, a well made enclosed motor with standard 3/4" dia. shaft 1" long. Suitable for light power operation. Continuous rating. £1-80 plus 20p post.

Instrument Motor by Eveready Hysterex motor—makers type No. PEV35-0630. This is a capacitor start motor for 110v AC working double ended shaft—£3-50 plus 20p post and insurance. Cut and Prepared 3 Core Leads, 2 yds. long, P.V.C. covered and ribbed virtually non-kinkable 23/36 conductors. Old colour scheme, 8p each, 10 for 70p. New colour scheme 15p each or 10 for £1-35.

Hearing Aid Amplifiers. (Ex behind ear deal aids). 3 transistors on tiny P.C. board with volume control—whole thing only about half as big as Oxo cube. £1-75 or with sub-miniature microphone and L.S. attached £3-50.

Totally Enclosed Mains Transformers with Primary for normal 230/240 Hz mains and secondary rated at 4 amp 50v tapped at 75v and 70v. This is a very well made transformer totally enclosed in metal case. Size 4 1/2" x 5 1/2" x 6 1/2" high. Made to be mounted above or below with terminations all on bottom. £3-50 each plus 65p post.

3 AMP Varises. 0-260v—panel mounting type—ex unused equipment, fully guaranteed, £10 each. Carriage—England £1. Wales and Scotland, £1-50.

Wafer Switches. Standard Size (1 1/2 wafers) built to Post Office spec, good contacts and generally very reliable. 9 pole 3 way on 3 wafers 45p—10 for £4. Ditto 2 pole 3 way. 20p—10 for £1-80.

F.C. Edge Connector. 18 contact switch with 2 mounting/switching lugs—30p each 10 for £2-70.

Pointer Knobs. Bulgin brass insert type, ref. no. K.357. Black with white line down pointer, grub screw fixing. 5p each—10 for 45p.

Jack-socket Bulgin. Catalogue no. J14. This is a standard size panel mounting jack, with leaf contact switches incorporated. Makers recommended price 41p. Our price 30p or 10 for £2-70.

Miniature Wafer Switch. 1 Pole 5 Way. This has a short spindle and is therefore suitable only for mounting through a metal panel. Price 12p or 10 for £1-05.

24 Way Rotary Switch. Single pole £1-25—double pole £1-95.

Double Pole, Double Throw Toggle Switch. Suitable for mains voltage and up to 10 amps. 16p or 10 for £1-55.

BREAK GLASS FIRE ALARM

PUSH

Made by A.F.A. and used all over the country. Made from heavy cast steel. Drop front. Open with Allen key for test. Switch normally closed, opens when glass is broken. Diameter approx. 1 1/2" £1-25 or with cast metal mounting box £1-75. Post 20p.



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 38p each or 10 for £3-42.

ROCKER SWITCH

18 amp self-fixing into an oblong hole, size approximately 1 1/2" x 1 1/2" 6p each, 10 for 54p.

MAINS RELAY BARGAIN

Special this month are some single, double and triple pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. (Good British Make. Unused. Size approx. 1 1/2" x 1 1/2" x 1 1/2")

Open construction

Single pole	25p each	10 for £2-25
Double pole	32p each	10 for £2-80
Treble pole	40p each	10 for £3-60

PUSH BUTTON CHANGE OVER SWITCHES

This is a Honeywell micro switch mounted on a metal frame with spring loaded plunger to operate. Panel fixing by single 1/8" hole. Single Changeover switch 25p each or ten for £2-25. 2-changeover switch operated by single plunger 35p each or ten for £3-15. 3-changeover switches 45p each or ten for £4-05.



HORSTMANN "TIME AND SET" SWITCH

(A 15 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1-50, p. & ins. 25p.



OUT OF SEASON BARGAIN

TANGENTIAL HEATERS

Once again we are able to make a special bargain offer of these very popular heating units. Tangential heaters although brought out a few years ago are still the latest and best type as nothing has yet been made which could be called an improvement on them. The Tangential unit is still the only one used in good quality heaters made by Hoover, G.E.C. and all the famous names. The unit comprises quiet running AC induction motor with special bearings, the tangential impeller and a 2 section heater element which allows switching half and full heat in the case of the 2 k.w. and one third—two thirds and full heat in the case of the 3 k.w. These heaters are also fitted with a safety cutout to cut the heaters should the impeller stop or the air flow be impeded. They are free standing and need only the simplest of cases, even a wooden cabinet is suitable or the plinth of the kitchen cabinet. Lots of customers missed our special Summer offer of these heaters last year so order early. 200/240 2 k.w. model £2-50. 200/240 3 k.w. model £3-50. Control switch heaters only 25p or two-heat, cold-blow and off 85p. Postage and insurance 35p on heaters.



AMPLIFIER MAINS TRANSFORMERS

50v 1/2 amp. Upright mounting with fixing brackets and metal shrouds to contain magnetic field, 50 c/s primary, tapped 110v, 117v, 210v, 230v and 250v. 2 secondaries, one 60v 1 1/2 amp, other 6v 1 amp for pilot light etc. £1-85, postage 30p.



THIS MONTH'S SNIP

LIGHT DIMMER

For any lamp up to 200 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price £1-99 plus 20p post & insurance.



CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for improved and even more efficient version, price £4-95. When ordering please state whether for positive or negative systems. Plus 30p post.



ELECTRONIC IGNITION

Standard 1 1/2 wafers—silver-plated 5-amp contact, standard 1/2" spindle 2 1/2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	7 way	8 way	9 way	10 way	12 way
1 pole	40p	40p								
2 poles	40p	40p								
3 poles	40p	40p	40p	40p	40p	70p	70p	70p	85p	85p
4 poles	40p	40p	40p	40p	70p	70p	70p	70p	£1-20	£1-20
5 poles	40p	40p	70p	70p	85p	85p	85p	85p	£1-45	£1-45
6 poles	40p	70p	70p	70p	85p	85p	85p	85p	£1-70	£1-70
7 poles	70p	70p	70p	85p	£1-20	£1-20	£1-20	£1-85	£1-95	
8 poles	70p	70p	70p	85p	£1-50	£1-50	£1-50	£2-00	£2-30	
9 poles	70p	70p	85p	£1-45	£1-45	£1-45	£1-45	£2-45	£2-45	
10 poles	70p	70p	85p	£1-20	£1-45	£1-45	£1-45	£2-70	£2-70	
11 poles	70p	85p	85p	£1-20	£1-70	£1-70	£1-70	£2-85	£2-85	
13 poles	70p	85p	85p	£1-20	£1-70	£1-70	£1-70	£3-20	£3-20	


INSTRUMENT SWITCHES

Precision made with finest indexing mechanism. Full length 1 1/2" spindle 5 amp and silver plated contacts. Range except for 3 way standard water switches. Prices obviously higher. For 40p read 60p, for 70p read £1, for 90p read £1-40, for £1-20 read £1-80, for £1-45 read £2-20. Note also 2 way types available up to 36 pole, 3 way 30 pole, 4 way 34 pole, 5 way 19 pole, but 10 and 12 way only available up to 6 pole.



3 STAGE PERMEABILITY TUNER

This Tuner is a precision instrument made for the famous Radiomobile Car Radio. It is a medium wave tuner (but set of longwave coils available as an extra (if required) with a frequency coverage 1920 Kc/s-525 Kc/s and intended to operate with an I.F. value of 470 Kc/s. Extremely compact (size only 2 1/2" x 2 1/2" x 1 1/2" thick) with reduction gear for fine tuning. 85p, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier.

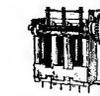

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small disks enable switching on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only £2-50, less than the value of the clock alone—post and insurance 15p.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2 less plug £2-25 with fitted 13 amp plug; £2-40 with fitted 15 amp plug, plus 23p P. & I.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1 1/2" pull—approx size 1 1/2" x 1 1/2" 80p.
Model 400/1 1/2" pull. Size 2 1/2" x 2" x 1 1/2" 75p.
Model TT10 1 1/2" pull Size 3" x 2 1/2" x 2 1/2"—£1-80 plus 20p post and insurance.




TREASURE TRACER

Complete Kit (except wood battens) to make the metal detector as described in last month's issue. £2-50 plus 20p



Mains Connector

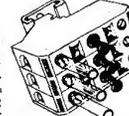A quick way to connect equipment to the mains safely and firmly—L, N, and E, coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection cable inlets firmly hold one hair wire on up to four 7/029 cables. 85p each



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 5 way—1 pole, 12 way. All at 18p each, £1-80 dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70v. Self-regulating temperature control. 50p post free.

COMPUTER TAPES

2,400' of the Best Magnetic Tape money can buy—users claim good result with Video and sound. 1 1/2" wide £1-45 plus 33p post and insurance. 1 1/4" wide £1-25 plus 30p post and insurance with cassette. 1 1/8" wide £1 plus 25p post and insurance with cassette. Spare spools and cassettes—1 1/2" £1, 1 1/4" 85p, 1 1/8" 75p each plus 25p post and insurance.



BALANCED ARMATURE UNITS

These Capsules are 1 1/2" in diameter and 1 1/2" thick. They will operate as a microphone or loud speaker so can be used in intercom and similar circuits. 33p ten for £3.

MULTI-SPEED MOTOR

Replacement in many well-known food mixers. Six speeds are available 600, 850 and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 & 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. This drive shaft is 1/2" diameter and approximately 1 1/2" long. A further point about this motor is that being 230/240v. A.C.-D.C. series wound its speed may be further controlled with the use of our Thyristor controller. This is a very powerful and useful motor size approx. 2 in. dia. x 5 in. long, mains 230/240v. Price 85p plus 25p postage and insurance. 12 or more post free.



MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Class 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2 1/2". £1 each.



QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have anti-basis bulb for tea, baby's food, etc. £1-25, post and insurance 14p. 12v. car model also available same price. Jug heater £1-50 plus p. & p. 14p.



DIGITAL COUNTER TIMER

as described in this issue. Send today for price list of parts.


J. BULL (ELECTRICAL) LTD.

Dept. P.W. 7, Park Street, Croydon CRO 1YD

COMET

HI-FI DISCOUNT WAREHOUSES

DRIVE-IN CAR PARK

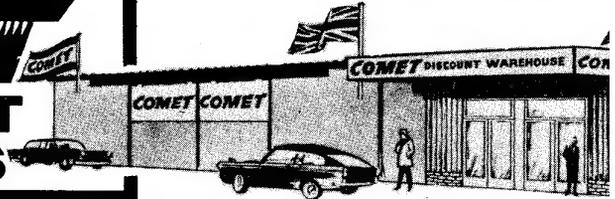

STEREO AMPLIFIERS

	Rec. Retail Price	Comet Price
ALBA JA 700	34.50	26.00
ARMSTRONG 521	55.00	42.50
*DULCI 207	26.00	17.50
DULCI 207M	32.00	21.95
FERROGRAPH F307	62.00	44.00
GOODMANS Maxamp	54.00	38.00
LEAK Stereo 30 Plus	55.50	43.00
LEAK Stereo 30 Plus, in teak case	82.50	47.95
LEAK Stereo 70	69.00	52.00
LEAK Stereo 70, in teak case	75.00	56.95
*LINEAR LT 65	21.00	17.00
METRO SOUND	36.00	24.95
METRO SOUND ST20E	39.50	29.50
PHILIPS RH 591	79.00	61.50
PHILIPS RH 590	52.00	39.50
PHILIPS RH 580	29.00	23.00
PIONEER SA500	62.00	41.95
PIONEER SA700	98.00	68.95
PIONEER SA900	134.10	95.95
PIONEER Reverberation	45.50	31.95
ROGERS Ravensbourne	59.50	45.95
ROGERS Ravensbourne (cased)	36.00	24.95
ROGERS Ravensbrook Mk. II	47.50	36.50
ROGERS Ravensbrook (cased) Mk. II	52.50	41.50
SINCLAIR 2000	35.00	27.00
SINCLAIR Project 6012 x Z30/PZ5	23.90	16.50
SINCLAIR PROJECT 6012 x Z50/PZ8/trans.	34.86	23.25
SINCLAIR AFU	5.95	4.95
SINCLAIR Neoteric	61.95	46.00
SINCLAIR 3000	45.00	34.95
TELETON SAQ 208 (new release)	29.00	18.50
TELETON SA101	37.50	28.50
VOLTEX 100w. Stereo Discotheque, 8 electronically mixed inputs	185.00	139.00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

TUNERS

*ARMSTRONG 523 AM/FM	53.76	42.00
*ARMSTRONG 524 FM	41.89	33.00
ARMSTRONG M8 Decoder	9.50	8.00
*DULCI FMT.7 FM	26.00	22.00
DULCI FMT.7S Stereo	35.00	29.50
GOODMANS Stereobrook (cased)	82.52	49.95
LEAK Stereofetic Chassis	66.50	52.00
LEAK Stereofetic in teak case	72.50	59.00
PHILIPS RH 690	47.00	38.00
PHILIPS RH 691	39.00	29.50
PIONEER TX500 AM/FM	77.94	63.50
PIONEER TX900 AM/FM	153.69	123.00
ROGERS Ravensbourne chassis	61.89	47.95
ROGERS Ravensbrook (cased)	45.01	38.00
ROGERS Ravensbrook (cased)	51.26	41.00
TELETON 201 FM	36.00	27.50
TELETON GTX 101	45.50	34.95

All above Tuners are complete with MPX Stereo Decoder except where starred.

TUNER/AMPLIFIERS

AKAI AA 8500	229.00	181.00
AKAI 6000	142.53	112.00
ARENA R500	82.00	67.00
ARENA 2400	90.30	72.00
ARENA 2700	105.00	85.00
ARENA T9000	303.45	258.00
ARMSTRONG M8 Decoder	9.50	8.00
ARMSTRONG 525	91.89	74.50
ARMSTRONG 526	104.71	84.50
GOODMANS Mod. 80, 35w. R.M.S.	95.00	72.00
MIDLAND 19/542	48.56	37.50
PHILIPS RH 790	139.00	112.00
PIONEER SX770 AM/FM	180.43	126.00
PIONEER SX900 AM/FM	194.74	150.00
PIONEER 440	111.10	89.00
TANDBERG 1171 comp. with decoder	110.00	94.00
*TELETON F2000	51.50	30.50
TELETON 7AT20	105.00	77.95
TELETON 10AT1 150w. RMS	160.00	103.00
TELETON TFS90	82.50	59.00
TELETON TFS 50LA MWLW/VHF	87.50	63.50
*TELETON R.8000 with Speakers	63.25	37.50
TELETON CR55	120.00	87.00
WHARFEDALE 100.1	149.00	119.00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

All the above Tuners and Tuner/Amplifiers include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.

PICKUP ARMS

GOLDRING Lenco L75	12.33	10.50
GOLDRING Lenco L69	9.29	7.00
SME 3009 with S2 Shell	34.47	27.00
SME 3012 with S2 Shell	36.71	30.50



COMET for after-sales service THROUGHOUT THE U.K.

Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, and Bridlington

CARTRIDGES

	Rec. Retail Price	Comet Price
GOLDRING 800	13.00	6.95
GOLDRING 800E	18.96	10.95
GOLDRING 800 Super E.	28.01	19.50
*GOLDRING CS90 Stereo	5.20	4.25
*GOLDRING CS91/E.	7.81	6.25
GOLDRING G850	6.50	5.25
EMPIRE 1000Z/X	63.00	52.50
EMPIRE 999VEX	44.50	36.00
EMPIRE 999TE/X	27.60	22.50
EMPIRE 999SE/X	21.00	17.50
EMPIRE 999E/X	16.50	13.00
EMPIRE 999EX	45.00	11.50
EMPIRE 908E/X	12.85	10.25
EMPIRE 908/X	9.00	7.50
EMPIRE 90EE/X	9.75	8.00
ORBIT Magnetic NM 22	Special Price	2.90
PICKERING V15 AC2	8.40	7.00
ORTOFON SL15E	29.65	23.75
ORTOFON 2X15K Transformer	7.00	5.25
SHURE M3DM	7.41	4.95
SHURE M31E	12.05	8.95
SHURE M32E	11.10	8.25
SHURE M32-3	10.20	8.00
SHURE M44-5	11.10	7.95
SHURE M44-7	10.20	8.00
SHURE M44C	10.20	8.00
SHURE M44E	12.05	9.25
SHURE M55E	12.95	9.50
SHURE M75G	17.60	14.00
SHURE M75-6	16.70	13.00
SHURE M75EJ	19.45	16.00
SHURE M9V95G	23.15	18.00
SHURE M75E	21.30	14.50
SHURE V15-11	40.76	28.95
SHURE V15-11-7	38.90	29.00

Starred cartridges above are ceramic. All others are magnetic.

TURNABLES

GARRARD AP76 turntable, fully wired complete with Goldring G.800 Cartridge, base and cover. Special Price 30.95		
GARRARD SP25, Mk III fully wired with Goldring G.800 Magnetic Cartridge. Complete with base, plinth and cover—Special Price 21.98		
GARRARD 2025 fully wired with Sonotone 9TAHC Cartridge complete with base and cover. Special Price 15.90		
GOLDRING 705/P turntable, fully wired complete with Goldring G.850 Cartridge, base and cover. List Price £25.00 Special Price £15.95		

DUAL 1219 transcription	60.40	50.00
DUAL 1209 transcription	42.62	35.00
GARRARD SP25 Mk III	16.45	11.90
GARRARD SL65 B	21.25	15.50
GARRARD SL75 B	39.20	26.50
GARRARD SL95 B	50.01	35.50
GARRARD 401	38.07	29.25
GARRARD SL72 B	33.11	25.50
GARRARD 3500, with GKS Cartridge. Base and cover to fit GARRARD SP25, SL55, SL65B and 3500. Special Price 4.00		
GARRARD 40B	13.84	10.97
GARRARD AP76	28.88	21.50
GOLDRING GL69 Mk. II	26.63	21.25
GOLDRING GL69P Mk. II	35.14	29.50
GOLDRING GL75	36.41	31.50
GOLDRING GL75P	46.94	38.50
GOLDRING Covers for 69P and 75P for G99	4.21	3.50
GOLDRING G99	11.45	9.90
GOODMANS 3025	26.00	22.90
GOODMANS 3025	37.74	26.90
McDONALD MP 60	15.75	11.75
McDONALD 610	20.00	15.75

Base and Cover for McDONALD

	Rec. Retail Price	Comet Price
MP 60 and 610	Special Price	4.50
PHILIPS 228	20.00	17.00
PHILIPS CA146	31.50	25.00
PHILIPS 202 Electronic	69.00	54.00
PIONEER PL12A with base & cover	49.93	37.95
THORENS TX 25 cover	8.85	7.00
THORENS TD125	79.04	61.95
THORENS TD125AB	120.00	98.00
THORENS TD150A Mk. II	46.16	35.95
THORENS TD150AB Mk. II	49.96	42.95
THORENS TX11 Cover	4.43	3.95


SPEAKERS

B & W Model 70	159.50	121.95
B & W DM5	63.00	49.95
B & W DM1	32.00	25.50
CELESTION Ditton 120	24.00	18.00
CELESTION Ditton 15	32.00	25.50
CELESTION Ditton 25	65.00	50.95
GOODMANS Minister	25.00	20.50
GOODMANS Magister	62.50	47.95
GOODMANS Maxim	20.39	16.50
GOODMANS Mezzo 3	34.00	25.95
GOODMANS Magnum K2	44.00	33.00
KEF Cresta	22.17	18.00
KELETRON KN500 4 speaker system (pair)	23.00	15.50
KELETRON KN700 4 speaker system (pair)	27.50	18.25
KELETRON KN1000 4 speaker system	19.25	13.95
KELETRON KN1500 4 speaker system	24.75	18.95
KELETRON KN2000 4 speaker system	28.75	20.95
LEAK 200	24.95	18.90
LEAK 300	32.50	23.95
LEAK 400	49.50	38.90
LOWTHER Acousta (with PM6)	45.50	38.50
LOWTHER Acousta (with PM7)	53.00	46.00
LOWTHER Ideal Baffle	35.50	30.00
METRO SOUND HFS103 (pair)	25.00	17.95
METRO SOUND 202	21.50	15.95
METRO SOUND HFS20 (pair)	39.00	27.95
METRO SOUND HFS10 (pair)	27.44	22.95
PHILIPS RH481	11.00	8.95
PHILIPS RH482	18.50	14.95
SINCLAIR Q16	8.88	6.95
STE-MA Model 400	24.00	16.95
TANDBERG TAN 7	28.80	24.50
TANDBERG TAN 11	19.30	16.50
TANDBERG TAN 15	45.00	35.95
WHARFEDALE Speakers		
Airedale	69.50	54.95
Denton	19.95	15.50
Super Lion	24.95	20.50
Melton	32.50	24.95
Dovedale 3	42.50	31.95
Rosedale	65.00	50.95
Triton (pair)	59.90	45.95
Unit 3 Speaker Kit	19.00	13.95
Unit 5 Speaker Kit	26.00	19.95

CHASSIS SPEAKERS

GOODMANS Axiette 8	8.10	6.50
GOODMANS Twinaxiette 8	9.17	7.50
GOODMANS Axiom 10	4.16	7.75
GOODMANS Axiom 20	28.31	23.75
GOODMANS Axiom 201	14.45	10.95
GOODMANS Axiom 301	20.70	15.75
GOODMANS Axiom 401	17.86	14.95
GOODMANS Audiom 8P	5.55	4.45
GOODMANS Audiom 10P	6.05	3.58
GOODMANS Audiom 51	13.05	9.75
GOODMANS Audiom 61	18.95	14.00
GOODMANS 12P	12.37	10.00
GOODMANS 15P	20.00	16.97

(OVER 1,520 sq. yds.)

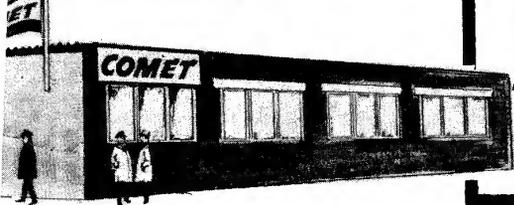

OVER 1000 ITEMS ALWAYS IN STOCK

ALL FULLY GUARANTEED - WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

	Rec. Price	Retail Price	Comet Price
GOODMANS Audiom 18P	34-00	28-97	
GOODMANS Twin Axium 10	10-23	8-25	
GOODMANS ARU172	4-50	3-50	
GOODMANS Trebox 100	8-60	6-00	
GOODMANS Trebox 5K/20XL	9-70	7-50	
GOODMANS Midex	12-95	9-00	
GOODMANS Attenuator	3-55	2-50	
GOODMANS Crossover Networks			
XO1950/5000	9-75	7-25	
GOODMANS Crossover Networks			
XO950	7-40	5-75	
GOODMANS Crossover Networks			
XO5000	2-65	2-00	
WHARFEDALE 8in. Bronze/RS/DD	8-40	8-00	
WHARFEDALE Super 8/RS/DD	8-50	7-00	
WHARFEDALE Super 10/RS/DD	14-00	11-50	
WHARFEDALE WMT 1 Matching Transformer	0-84	0-75	

HI-FI STEREO SYSTEMS (complete)			
ARENA MR15	145-00	115-95	
ALBA UA852	47-50	35-95	
ALBA UA662	82-97	47-95	
DECCA Sound 603	72-50	72-95	
DECCA Sound 604	72-50	60-95	
DECCA Sound 1204	97-50	78-95	
DECCALIAN 5, complete with stand.	69-50	52-95	
DECCA Compact 3	135-00	112-95	
EKCO SRC 608	68-50	69-95	
EKCO ZUS	165-00	135-00	
FERGUSON 3422	87-85	69-95	
FERGUSON 3423	118-25	94-95	
FERGUSON 3424	123-15	99-95	
FERGUSON 3425	145-10	111-95	
FERGUSON 3450 with radio	75-00	62-95	
FIDELITY Music Master UA2	46-00	33-95	
FIDELITY Music Master UA1	98-00	82-95	
H.M.V. 2416	129-70	103-00	
H.M.V. 204/5/6	202-85	165-00	
H.M.V. 2452	63-00	56-95	
H.M.V. 2450 with Stereo radio	139-00	115-00	
K.B. KA1250, complete with two 653 speakers	72-00	59-50	
K.B. KA1250, complete with two 651 speakers	83-00	65-95	
K.B. 2010 with Stereo radio	76-00	62-95	
LEAK30/GOLDRING/WHARFEDALE	182-65	142-95	
LEAK 70/THORENS/WHARFEDALE	228-97	175-00	
MARCONI Unit 4	77-45	66-95	
MARCONI Unit 3	88-00	69-95	
METROSOUND Stereo 1010	92-30	65-95	
PHILIPS 6501/81/105	71-00	55-95	
PHILIPS GF823	51-50	41-50	
PHILIPS GF824	69-50	56-95	
PHILIPS GF833	67-50	55-95	
PHILIPS GF834	85-00	73-95	
PHILIPS 682 (less L/S)	99-00	78-50	
PHILIPS GF417	99-50	82-75	
TELETON 2500F, with Radio	75-00	65-95	
TELETON 8TK stereo system	54-75	48-00	
TOSHIBA SP8507	248-00	175-00	
ULTRA 6405	79-95	66-95	

TAPE RECORDERS AND TAPE DECKS			
AKAI M101	245-00	185-95	
AKAI X200D	190-00	125-00	
AKAI X5000 W/L	177-98	135-95	
AKAI X330	342-57	265-95	
AKAI X-380	312-50	243-95	
AKAI X-360 D-deck	318-92	243-00	
AKAI 1800SD	199-42	129-00	
AKAI 1710L 4-track stereo	97-85	65-95	
AKAI 1720L	97-85	77-50	
AKAI CR80 8-track stereo recorder	115-03	99-95	
AKAI CR80D 8-track stereo tape deck	95-00	79-95	
AKAI 4000 4-track Stereo	124-90	97-95	

	Rec. Price	Retail Price	Comet Price
AKAI 4000 D 4-track Stereo deck	89-95	69-50	
BUSH TP 60 Cassette Tape Rec.	29-40	24-95	
BUSH TP 70 Cassette Battery/ Mains Tape Recorder	29-95	23-95	
BUSH Discassette DC70	21-85	16-95	
FERGUSON 3228 4-track	104-30	83-95	
FERGUSON 3245 Twin track	38-00	29-95	
FERGUSON 3246 4-track	44-10	34-95	
FERGUSON 3247 4-track	43-15	34-95	
FERGUSON 3248 4-track	55-65	43-95	
FERROGRAPH 722	266-41	198-00	
FERROGRAPH 784	266-41	198-00	
FERROGRAPH 702 2-track tape deck	228-71	193-00	
FERROGRAPH 704/W 4 track tape deck	228-71	193-00	
GRUNDIG C200 deluxe Cassette	39-90	29-95	
GRUNDIG TK 141 (4-track)	61-85	49-95	
GRUNDIG TK 121 (Twin-track)	49-85	43-95	
GRUNDIG TK 146 (4-track Auto)	68-14	53-95	
GRUNDIG TK 149 (4-track)	57-63	47-95	
GRUNDIG 222 stereo cassette	59-85	48-95	
GRUNDIG TK 147 (4-track Auto.)	96-85	79-95	
MIDLAND TC 144 cassette	18-00	11-95	
PHILIPS 2202 Cassette	29-90	21-95	
PHILIPS 2204 Cassette bat./main.	33-50	25-95	
PHILIPS 2205 Cassette Tape Rec.	43-15	34-95	
PHILIPS 3302 Cassette	23-90	18-25	
PHILIPS 4307 4-track	49-50	38-95	
PHILIPS 4404 2-track stereo recorder	95-00	73-95	
PHILIPS 4407 4-track stereo	120-00	93-95	
PHILIPS 4303 new release	42-00	34-95	
PHILIPS 4302 Twin Track Auto	39-00	32-00	
PHILIPS 4500 4-Track Stereo Tape Deck	128-00	98-95	
PHILIPS 4408 4-Track Stereo	139-00	109-00	
PHILIPS 4308 4-Track	60-50	44-95	
PHILIPS Cassette Stereo Tape Deck	54-00	44-95	
PHILIPS 2400 Stereo Cassette (less L/S)	68-00	59-95	
PYE Cassette Recorder/Radio (Batt. /Mains)	45-50	36-95	
TANDBERG 1841 4-track Stereo Tape Deck	69-75	59-95	
TANDBERG 3021X twin track stereo	109-80	93-00	
TANDBERG 3041X 4-track stereo	109-80	93-00	
TANDBERG 4021X twin track stereo	180-00	150-00	
TANDBERG 401X 4-track stereo	180-00	150-00	
TANDBERG 6021X twin track stereo	195-00	165-00	
TANDBERG 6041X 4-track stereo	195-00	165-00	
TELETON 511 Batt./mains cassette	29-50	17-50	
TELETON 8110 cassette	22-00	14-95	
TELETON FXB 510 4-track Stereo	67-50	47-50	
TELETON TRC 130 cassette, with VHF/AM radio. Battery/mains, twin motors	41-75	31-90	
TELETON TC10 cassette, bat/mains	27-75	20-00	
TOSHIBA GT 840 S	110-00	55-95	
TOSHIBA GT 601V Twin Track	45-15	29-95	
TOSHIBA 830 SA	94-00	59-95	
WHARFEDALE Dolby DC9 Cassette Stereo Tape Deck	115-00	97-00	

BASES AND COVERS			
GARRARD WB1 Base	3-88	3-25	
GARRARD WB4 Base	5-69	4-75	
GARRARD SPC 1 Cover	3-74	3-00	
GARRARD SPC 4 Cover	4-44	3-75	
Special offer of Base and Cover to fit GARRARD SP25, SL35, SL65B and 3500			
GOLDRING Plinth 75	8-52	7-00	
GOLDRING Plinth 69	8-52	7-00	
GOLDRING Covers for 69P and 75P	4-21	3-50	
THORENS TX25 (for TD125AB)	3-22	6-50	
THORENS TX11 Cover	4-11	3-75	
Base and Cover for TD 125	15-18	12-50	
SME Plinth System 2000	39-20	31-25	
MOTORBOARDS only	4-95	3-00	

COMPLETE HI-FI SYSTEMS

Completely wired, mounted and ready for use.

	Rec. Price	Retail Price	Comet Price
GOODMANS AUDIO SUITE, Goodmans Maxamp stereo amplifier, Goodmans stereomax AM/FM Tuner with decoder, Pair of Goodmans Magnum K2 speakers, Garrard AP76 turntable in base, complete with cover and Goldring G800 Cartridge. Beautifully finished in walnut	257-13	169-95	
GOLDRING 705P turntable complete with G800 Cartridge, Midland Tuner/Amp., pair of Metrosound 103 Speakers	99-56	69-95	

GOODMANS Module 90 Tuner/Amplifier Garrard AP76 Turntable with Goldring G800 Cartridge and 2 Goodmans Minister Speakers			
	199-00	139-00	

METROSOUND 448 8-track stereo playback unit complete with 2 HFS 10 Speakers			
	83-56	70-95	

GOLDRING 705P turntable complete with G800 Cartridge, Teleton 206 Amplifier, pair of Keleton KN500 Speakers			
	77-00	49-95	

TELETON Stereo 8 track tape Audio system complete with speakers			
	54-75	48-00	

GARRARD SP 25, Mk. III mounted in base, plinth and cover with GOLDRING G800 Cartridge, Teleton 206 Stereo Amplifier 12 watts RMS, and 2 KELETON KN500 Speakers, each speaker is a 4 speaker system			
	88-33	58-95	

PIONEER PL 12 turntable, Goodmans Maxamp, Shure M55E Cartridge, 2 Keleton KN 700 speakers (each speaker cabinet contains 4 speakers)			
	144-38	105-00	

GARRARD AP76 turntable complete with Goldring G800 Cartridge, base and cover, Rogers Ravensbrook Amplifier in teak case and 2 Goodmans Minister Speakers			
	142-51	108-50	

LEAK 30/THORENS/WHARFEDALE			
	182-65	142-95	

GOLDRING GL 75P mounted in teak base with hinged perspex cover complete with GOLDRING G800E Cartridge, Leak Stereo 30 Plus Amplifier in Teak case, 2 GOODMANS Mezzo 3 Speakers			
	200-50	154-20	

THORENS TD 150AB Mk. II with TX11 dust cover, SHURE M55E Cartridge, LEAK Stereo 70 Amplifier in Teak case, 2 Wharfedale Dovedale 3 Speakers			
	226-87	175-00	

THORENS TD 125AB Electronic Turntable complete with cover, SHURE V15-11 Cartridge, GOODMANS Maxamp, GOODMANS Stereomax AM/FM Tuner, 2 GOODMANS Magister Speakers			
	422-48	309-00	

Open daily to the public from 9-0 A.M. until—

5-30 P.M. MON.
1-0 P.M. TUES.
8-0 P.M. WED.
8-0 P.M. THUR.
8-0 P.M. FRI.
5-30 P.M. SAT.

Customers are welcome to call. Ample car parking facilities

Complete Price List FREE on request!

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

- (Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407806 and 407677
- (Dept. P.W.) 68A Armley Rd. (Artist St.), Leeds LS12 2EE Tel. 32055 (3 lines)
- (Dept. P.W.) Teesway, Portrack Lane, North Teesside Industrial Estate, Teesside, TS18 2RH Tel. 66132/65215
- (Dept. P.W.) Heeley Road, Selly Oak, Birmingham

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or, if Securicor delivery required, add £1.50 only. Make cheques, Money Orders payable to "COMET".



All in-stock items delivered by **SECURICOR** WITHIN 72 HOURS (Add £1.50 only for Securicor delivery) ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 7/8 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.

We still do the well known Shelley and Caxton column speaker systems




STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output, has 2 position switch to give headphones only—speakers only.
Only £1.37 each P & P 12½.

CARTRIDGES

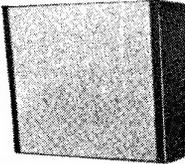Stereo: Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output. £1.40. S106 High Output. £1.40. Acos GP93 1 Sapphire. £1.90. GP94 1 Sapphire. £2. TA709 equivalent to B.S.R. SX1M. £1.75. Japanese equivalent to B.S.R. TC8s. £1.75. P. & P. 7np on each.



DUDLEY

11" x 9½" x 5" deep, tapering to 3½" deep covered in Black resine and Mottled fawn Vynair £2-10 P & P 25p.

SPEAKERS

E.M.I. 13½ x 8in. 3 ohm £2.50, 15 ohm. P. & P. 30np. E.M.I. 13½ x 8in. fitted two 2½in. tweeters, 15 ohm £4.50. P. & P. 30np. E.M.I. 13½ x 8in. (15 ohm) Hi-Fi quality £6.25. P. & P. 30np. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30np. Eagle Crossover 86np. P. & P. 5np.

BROADWAY ELECTRONICS


(Nr. Tooting Broadway Underground Station) 92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984 (Closed all day Wednesday)

SPEAKER MATCHING TRANSFORMERS

3, 7, 15 ohms, 8 watt, 70np. P. & P. 17np.


FARRADAY

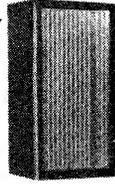5½" x 11" x 4½" covered in White, Green or Black rexine or Teak cloth with Silver coloured metal front
£2-90 P & P 25p.



VYNAIR

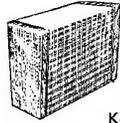Widths from 50 to 54 in., 75np. yd. off roll. P. & P. 10np. ½ yard 40np. P. & P. 10np. Send 5np stamps for samples.



IMP

Wedge shaped extension speaker 7½ x 6½ x 4in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1.25. P. & P. 36np each


MONO

PG.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. T.T.C. Crystal High Gain, 75np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.

CLARENCE

11" wide x 8½" x 4½" deep with volume control covered in Black rexine and Mottled Vynair. £2-25 P & P 25p.

NOCTURNE 73 STEREO SYSTEM

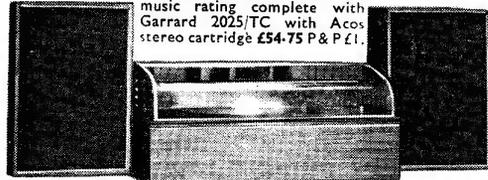

6w. per channel speech and music rating complete with Garrard 2025/TC with Acos stereo cartridge £54-75 P & P £1.

Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Education Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name _____

Address _____

Age _____

Phone _____

5H1

**CONTROL DATA
INSTITUTE**

**CONTROL DATA
LIMITED**

The Education Division of one of the world's largest Computer manufacturers.

Ring

01-637 2171

between 9 a.m. and 9 p.m. and ask for Mr Payne

NEW 1971 CATALOGUE

NOW READY — OUR BEST YET

64 pages and cover, thousands of well classified items — pages of valuable information, post free 10p.

ELECTROVALUE

Electronic Component Specialists

EVERYTHING BRAND NEW & TO SPEC • LARGE STOCKS • NO SURPLUS

BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES • ALL POWER TYPES WITH FREE INSULATING SETS

40801	85p	2N3906	44p	2N4391	15p	BC144	9p	BFX87	80p
40869	88p	2N3906A	47p	2N4392	15p	BC149	10p	BFX88	80p
2N606	15p	2N3924	85p	AC107	48p	BC158	10p	BFX90	80p
2N706	18p	2N3928	88p	AC126	80p	BC164	90p	BFX91	80p
2N930	80p	2N3933	11p	AC127	80p	BC167	12p	BFX92	80p
2N1181	80p	2N3953	87p	AC128	80p	BC168	11p	BKX30	15p
2N132	80p	2N3955	40p	AC153K	80p	BC169	12p	C407	17p
2N1302	19p	2N3708	18p	AC176	16p	BC167	11p	MC140	80p
2N1303	19p	2N3704	18p	ACY30	80p	BC168	10p	MPB0591	80p
2N1304	20p	2N3706	18p	AD140	68p	BC169	11p	MPB0584	80p
2N1305	20p	2N3706	18p	AD140	68p	BC177	14p	NKT211	80p
2N1306	20p	2N3707	18p	AD149	68p	BC178	13p	NKT212	80p
2N1307	20p	2N3708	18p	AD149	68p	BC179	14p	NKT214	80p
2N1308	20p	2N3709	18p	AD162	86p	BC182L	11p	NKT274	18p
2N1309	20p	2N3710	18p	AF114	84p	BC183L	10p	NKT408	65p
2N1613	20p	2N3711	18p	AF115	84p	BC184L	11p	NKT409	65p
2N1711	20p	2N3810	28p	AF117	82p	BC218L	15p	OC71	80p
2N1889	54p	2N3804	80p	AF124	84p	BC214L	15p	OC81	80p
2N2147	95p	2N3806	85p	AF127	82p	BCY70	18p	ZTX300	14p
2N2218	94p	2N4058	18p	AF139	86p	BCY71	80p	ZTX301	15p
2N2218A	80p	2N4059	19p	AF289	86p	BF173	18p	ZTX302	80p
2N2219	80p	2N4060	11p	ASV26	87p	BF115	80p	ZTX303	80p
2N2219A	80p	2N4061	11p	ASV28	87p	BF147	18p	ZTX304	80p
2N2370	80p	2N4062	12p	BC107	19p	BF178	11p	ZTX305	19p
2N2369A	15p	2N4124	80p	BC108	19p	BF194	14p	ZTX501	81p
2N2458	44p	2N4126	80p	BC109	18p	BF195	18p	ZTX502	80p
2N2484	45p	2N4284	15p	BC126	16p	BFX29	81p	ZTX503	80p
2N2646	47p	2N4286	15p	BC126	80p	BFX84	80p	ZTX604	58p
2N2904A	48p	2N4289	15p	BC147	10p	BFX85	80p		

Appointed distributors for
SIEMENS (U.K.) LTD.

Appointed stockists for
**NEWMARKET TRANSISTORS
RADIOHM POTENTIOMETERS**

SAVE £6.25 ON THE NEW ENGLEFIELD 840 AMPLIFIER

This latest Peak Sound high fidelity amplifier incorporates many strikingly original features including facility for adding in stereo FM tuner, superb performance characteristics and luxurious styling. Electrovalue's choice of simulated soft leather covering in black, blue, red or dark green. As advertised at £45. Our price . . .

£38.75 nett

MAINLINE AMPLIFIER KITS

70W. £18.00 nett. (main amplifier module).

30 WATT BAILEY AMPLIFIER PARTS

Transistors and PCB for one channel 25-45 Capacitors, resistors (metal oxide), and transistors, one channel. 25-41. Complete unregulated power supply pack, 24.75. Suitable heatsink 10DN 400C. 85p.

INTEGRATED CIRCUITS SIEMENS' TTL INTEGRATED

CIRCUITS. Full range of all types in stock for very wide range of applications. For full details, see our latest components list. Please send S.A.E.

PLESSEY SL408A 7.5 ohms. 22-10 nett. Applications data 10p.

S-DeCs put an end to birds nesting

Components just plug in—saves time—allows reuse of components. S-Dec (70 points), £1.00. S-Dec, may be temperature-cycled (208 points), 22-50. Also µ-DeCs and IC carriers.

INDICATOR LAMPS

NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C, 24p. Neon, square red type L85C/P, 18p; amber type L85C/A, 18p; clear type L85C/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type L85C/R-6V, 80p, 6V 0.04A amber type L85C/A-6V, 80p; 6V 0.04A clear type L85C/C-6V, 80p; 6V 0.04A green type L85C/G-6V, 80p; 12V 0.04A L85C/R-12V, 84p; 34V 0.04A L85C/R-28V, 45p.

SIEMENS' POLYCARBONATE CAPACITORS

5% tolerance
250V up to 0.1mF. 100V 0.1mF and above.
0-01, 0-015, 0-018, 0-018, 0-022, 0-027 . . . 5p
0-038, 0-038, 0-047, 0-056, 0-068, 0-082, 0-1, 0-12, 0-15, 0-18, 0-22 . . . 8p
0-27 . . . 7p . . . 0-33 . . . 8p

DIN CONNECTORS

Loudspeaker	2-pole	plug	socket
Audio	3-pole	12p	10p
Audio	4-pole	14p	12p
Audio	5-pole 180 deg.	15p	12p
Audio	5-pole 240 deg.	15p	12p
Audio	6-pole	15p	12p

CORED SOLDER—64/40 alloy, 20 s.w.g. 8oz reel, 65p, 1 lb reel, £1.50.

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

RESISTORS 10%—5%—2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω—220K Ω	E12	9	8	7
C	1/8W	5%	4.7 Ω—470K Ω	E24	1	0.8	0.7
C	1/4W	10%	4.7 Ω—10M Ω	E12	1	0.8	0.7
C	1/2W	5%	4.7 Ω—10M Ω	E24	1-2	1	0.9
C	1W	10%	4.7 Ω—10M Ω	E12	2-3	2	1.8
MO	1/2W	2%	10 Ω—1M Ω	E24	4	3-5	3
WW	1W	10% ± 1/20 Ω	0.22 Ω—3.9 Ω	E12	7	7	6
WW	3W	5%	12 Ω—10K Ω	E12	7	7	6
WW	7W	5%	12 Ω—10K Ω	E12	9	9	8

Codes: C = carbon film high stability low noise
MO = metal oxide Electrosl TR5 ultra low noise
WW = wire wound Plessey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

MULLARD polyester C280 series

200V 20% 0-01; 0-022; 0-033; 0-047 3p ea. 0-068; 0-1, 0.15 4p, 0.22 5p, 0.33 7p, 0.47 8p, 0.68 11p, 1µF 14p, 1.5µF 15p, 2.2µF 14p.

MULLARD SUB-MIN ELECTROLYTIC

C495 range axial lead
Values (µF/V): 0-04/64; 1/40; 1-6/25; 2-5/16; 2-5/16; 4/10; 4/10; 5/84; 6-4/6; 6-4/6; 8/4; 8/4; 10/2-6; 10/18; 10/64; 12-5/25; 16/40; 20/16; 20/64; 25/6-4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2-6; 50/6-4; 50/25; 50/40; 64/4; 64/10; 80/2-5; 80/16; 80/25; 100/6-4; 125/4; 125/10; 125/16; 100/2-5; 200/6-4; 200/10; 200/4; 320/2-5; 320/6-4; 400/4; 500/2-5.

LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 82p; 2000/25 37p; 2000/50 57p; 2000/100 81-44; 2500/64 77p; 2500/70 88p; 5000/25 62p; 5000/50 81-10; 5000/100 82-81; 10000/50 82-40.

COMPONENT DISCOUNTS

10% on orders for components for 25 or more, 15% on orders for components for 115 or more (No discount on nett items).

POSTAGE AND PACKING

Free on orders over 22. Please add 10p if orders under 22. Overseas orders welcome: carriage and insurance charged at cost.
Send S.A.E. for latest list. Prices subject to alteration without notice.

ZENER DIODES

5% full range E24 values; 400mW; 2.7V to 30V 15p each
1W: 0.6V to 92V 27p each 1.5W: 4.7V to 75V 80p each
Clip to increase 1.5W rating to 3 watts (type 286F) 4p.

CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.
Single gang linear 220 Ω to 2.2M Ω 12p
Single gang log 4.7K Ω to 2.2M Ω 12p
Dual gang linear 4.7K Ω to 2.2M Ω 42p
Dual gang log 4.7K Ω to 2.2M Ω 42p
Log/antilog 10K, 47K, 1M Ω only 42p
Any type with JA D.P. mains switch, extra 12p

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω 470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω Vertical or horizontal mounting 5p each.

ENAMELLED COPPER WIRE even No S.W.G. only.
20c reels 16.22 S.W.G. 25p; 24-30 S.W.G. 30p; 32-34 S.W.G. 33p; 36-40 S.W.G. 35p; 42c reels 16.22 S.W.G. only 41p.

ELECTROVALUE

(Dept. PW.971) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475

DISCOTHEQUE EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MKII AMPLIFIER PR. FANE POP 25/2 25W L/SPKERS	£33.50 £13.50	PACKAGE PRICE	
Terms: Deposit £5.50 and 9 monthly payments of £4.72 (Total £47.98)	£44	£1	
F.A.L. PHASE 50 MK.II AMPLIFIER PR. FANE POP 50 L/SPKERS	£33.50 £21	PACKAGE PRICE	
Terms: Deposit £10.50 and 9 monthly payments of £5 (Total £55.50)	£49.50	£1	
F.A.L. PHASE 100 AMPLIFIER PR. L125 50W 1/2 in cabinets	£61.95 £59.80	PACKAGE PRICE	
Terms: Deposit £22 and 9 monthly payments of £11 (Total £121)	£110	£1.50	
F.A.L. PHASE 100 AMPLIFIER 4 FANE POP 50 L/SPKERS	£61.95 £42	PACKAGE PRICE	
Terms: Deposit £14 and 9 monthly payments of £10 (Total £104)	£94	£1.50	

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.75**

OR SENIOR 15 WATT INC. £6.75 Carr. 30p
HI126 15,000 LINE SPEAKER carr. 35p

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated cone surround. "D" indicates Tweeter cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

HF801D 8" 8W	£2.71	HF120D 12" 15W	£4.75
HF102D 10" 10W	£3.40	HF128 12" 15W	£5.50
HF120 12" 15W	£4.25	HF128D 12" 15W	£5.90

FANE 807 HIGH FIDELITY LOUDSPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis R11 P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is tilted to extend high note response. Frequency range 25 Hz to 15 KHz. Impedance 3 or 8-15 Ω. Gauss 10,000. Remarkable value. **£3.50**

HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 30p per enclosure

JES Size 16 x 11 in. Pressurised. Gives pleasing results with any 8in. HI-FI speaker. £5.35

SES For optimum performance with any 8in. HI-FI speaker. Size 22 x 13 x 9in. Ported SE10 For outstanding results with any 8in. HI-FI speaker and Tweeter. £6.47

SE10 For excellent performance with 12in with 10in. HI-FI 'spkr HI-FI speaker and Tweeter. £7.87
Size 24x15x10in. P'd. Size 25 x 16 x 10in.

R.S.C. PLINTHS

Superior Solid Natural Wood Construction for Record Playing units, for Garrard 1025, 2025, 3000, AT50, SP25 etc. **£3.15**

WITH TRANSPARENT PLASTIC COVER **£6.30**

LEADING MAKES HI-FI EQUIPMENT AT CLEARANCE PRICES AVAILABLE AT BRANCHES ONLY

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BMI An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 60c/s is available. Complete kit with diagram 23 or assembled ready for use £3.50



R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3%. at 1,000 c.p.s. Separate Bass and Treble. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching diagrams and instructions. **£7.50** Carr. 40p

OR FACTORY BUILT WITH 12 MONTHS GUARANTEE **£9.75**

R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER

PUSH-PULL OUTPUT. Two input sockets with sep. vol. controls for mixing. High sensitivity. 5 valves. Bass and treble controls. Response ± 3dB 30-20,000 c/s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc.

Std. A.C. mains. For 3 & 15 ohm spkrs. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 50p S.A.E. for leaflet. Twin handled metal cover **£1.75**

Factory built £14.75 or Dep. £2 and 9 monthly payments of £1.60 (Total £17.40). **£10.50**

R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS



All types 15 Ohms covered in Rexine Vynair

TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C485 25-30 WATTS
Fitted four 8" high flux 8 watt speakers. Overall size approx 48 x 10 x 5 in. Carr 50p
Terms: Dep £3 and 9 monthly payments £2 (Total £21) **£17.75**

TYPE C4125 50 WATTS
Fitted four 12" 11,000 line 15 watt speakers: Overall size approx 58 x 14 x 5 in. Carr 75p
payments £3 (Total £21) **£27.50**

TYPE C4100 100 WATTS inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £7.50 and 9 monthly. pyts. £5.45 (Total £56.55). Carr. £1 **£50.50**

30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.

A 2 or 4 input, 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. **£19.95** Carr. 65p



HIGH QUALITY LOUDSPEAKER UNITS

IN TEAK VENEERED CABINETS

L125 12" x 8" 10 Watt L12 12" Also supplied
10,000 lines 3 or 15 25 WATT 10,000 lines
ohms. State impedance 15 ohms. covered

£5.25 carr. 40p **£10.50** carr. 45p


L125 50 WATT
Two tone Rexine and Vynair finish. Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Or deposit £4 and 9 monthly payments of £3.35. Total £34.15 **£31** Carr. 75p

R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit optional horizontal or vertical mounting. **£60**

★ Two extra heavy duty 12in. Loudspeakers.
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes"
Bass and Treble controls. Send S.A.E. for leaflet. Carr. £1.50

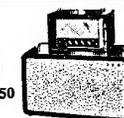Credit Terms Deposit £16 and 9 monthly payments of £5.75 (Total £67.75)



FAL PHASE 50 MKII AMPLIFIER 50W

Solid state 4 Separately controlled inputs. Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for speaker's 8-30 ohms. Size 17" x 7" x 7" 200-250v. A.C. mains. Output 60 watts music rating Or deposit £6 & 9 monthly payments £3.50. Total £37.50. Carr. 65p

FAL PHASE 100 AMPLIFIER 100W

Solid State. 4 Separately controlled inputs Plus master volume control. Ind. Bass and Treble Controls. Output for speaker's 8-30 ohms. Protective circuit to guard against damage from accidental shorts. I.H.F.M. Output rating. Or deposit £12 & 9 monthly payments £8.25. Total £68.25. Carr. 75p Send S.A.E. for leaflets.

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE

'POP' 100 18" 100Watt 14,000 gauss 8/15Ω	'POP' 60 15" 60 Watt 14,000 gauss 8/15Ω	'POP' 50 12" 50 Watt 13,000 gauss 15Ω
£22.05	£12.90	£10.50

Dep. £2 and 9 monthly payments £2.10 (Total £24.90)

Dep. £2.30 and 9 monthly payments. £1.15 (Total £12.35) - Pair suitable all purposes

FOR BASS GUITAR, ELECT. ORGAN, ETC.

FANE

'POP' 25/2
12in. 25 WATT
Dual Cone 15Ω (for use other than Bass Guitar or Electronic Organ). **£6.75** Carr. free or Dep. £1 and 9 monthly payments 75p (Total £7.75)

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level -70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones, etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes, 200-250 v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with wiring diagram and instructions. Twin-handled perforated cover **£15.75** Or factory built with EL34 output valves and 12 months' guarantee for £18.75 Carr. 65p

TERMS: Deposit £4 and 9 monthly payments of £2.10 (Total £22.90). Send S.A.E. for leaflet.

RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary

PRIMARIES 200-250v. 50c/s. Screened

MIDGE CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in. 90p

250v. 60mA. 6.3v. 2a. 95p

250-0-250v. 60mA. 6.3v. 2a. 95p

FULLY REVERSED UPRIGHT MOUNTING

250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a. £1.25

300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £1.28

300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £1.98

300-0-300v. 130mA. 6.3v. 4a. c.t., 6.3v. 1a. £2.40

For Mullard 510 Amplifier

350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £1.98

350-0-350v. 130mA. 6.3v. 4a. 0-5-6.3v. 3a. £2.40

425-0-425v. 200mA. 6.3v. 4a. c.t., 5v. 3a. £2.49

425-0-425v. 200mA. 6.3v. 4a. 6.3v. 3a., 5v. 3a. £4.89

TOP SHEETED DROP-THERO TYPE

250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a. £1.20

250-0-250v. 100mA. 6.3v. 3.5a. £1.40

250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. £1.45

300-0-300v. 130mA. 6.3v. 4a. 0-5-6.3v. 2a. £1.50

250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £1.98

300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £1.98

300-0-300v. 130mA. 6.3v. 4a. 0-5-6.3v. 1a. £2.35

Suitable for Mullard 510 Amplifier

350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £2.35

350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a. £2.35

FLAMMENT OR TRANSISTOR POWER PACK

Types 6.3v. 1.5a. 45p; 6.3v. 2a. 48p; 6.3v. 3a. 65p; 6.3v. 6a. £1.15; 12v. 1a. 50p; 3a. or 24v. 1.5a. £1.20; 0.9-18v. 12a. 98p; -12-25-42v. 2a. £1.60

CHARGER TRANSFORMERS 0-9-15v. 13a. 95p
24v. 95p; 5a. £1.10; 1a. £1.30; 6a. £1.40; 8a. £1.55

AUTO (STEP UP/STEP DOWN) TRANSFORMERS
0-110/120v. 200-220-250v., 50-80 watts 98p;
150 watts, £1.70 250 watts £2.40; 500 watts £5.25.

OUTPUT TRANSFORMERS
Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 45p
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 75p
Push-Pull 10 watts 6V6, ECL86 to 3 Ω, 5 Ω or 15 Ω 150p
Push-Pull EL84 to 3 Ω or 15 Ω 10-12 watts £1.25
Push-Pull Ultra Linear for Mullard 510, etc. £1.90
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω £1.80
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 8 or 15 Ω £2.40

SMOOTHING CHOKES 150mA. 7-10H. 25Ω
65p; 100mA. 10H, 200 Ω 55p; 80mA. 10H, 350 Ω 45p; 60mA. 10H, 400 Ω 25p.

SELENIUM RECTIFIERS F.W. (Bridged)
All 6/12v. D.C. output. Max. A.C. input 18v.
1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 6a. 80p.

Introducing R.S.C. MkIII SUPER 30 HI-FI STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE, REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

Only high grade components by leading manufacturers. **£25 Carr. 65p**
COMPLETE KIT OF PARTS



- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

Or FACTORY BUILT with 12 months guarantee Dep. £3-75 and 9 monthly payments £3-50 (Total £37-25)
Or FACTORY BUILT in cabinet as illustrated Dep. £6 and 9 monthly payments £3-86 (Total £40-74)

PRINTED CIRCUITRY, TWENTY SILICON TRANSISTORS, FOUR DIODES, FOUR RECTIFIERS.
TECHNICAL DETAILS (Applying to each channel where appropriate)
CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble, and Balance. Plus Ceramic Mag P.U. Switch.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. Price 10 watts R.M.S. (Continuous) into 15 ohms.
HUM & NOISE - 75dB Min. Vol. - 65dB Full Vol. HARMONIC DISTORTION
FREQUENCY RESPONSE: -3dB 7Hz to 70KHz 0-1% at 1000 Hz 10 Watts
TREBLE CONTROL: +16dB to -16dB at 14KHz
BASS CONTROL: +17dB to -16dB at 40Hz
CROSS TALK - 58dB
SENSITIVITIES: Disc Mag. 2.5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.
REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

R-S-C HIGH FIDELITY STEREO PACKAGE OFFERS

Four fully wired units ready to 'plug in.' SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
★ GARRARD SP25 MKIII Turntable on Plinth with cover
★ GOLDRING CS90 Ceramic Pick up Cartridge with diamond stylus
★ PAIR OF STANWAY II Speaker Units **£79-80**
Total Price Carr. £1-50

Matching as recommended for optimum performance. Send S.A.E for coloured brochure showing other money-saving offers.



Starway II ATTRACTIVE TEAK or AFROFORMIA VENEERED CABINETS and PLINTHS

★ TA12 AMPLIFIER 6.5+6.5 watt in veneered housing
★ GARRARD SP25 MK III Player unit on Plinth
★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus
★ PAIR OF DORCHESTER Loudspeaker Units
Special Total Price Carr. £1-25 **£58**

★ Super 30 Amplifier (15 + 15 watt) in veneered housing
★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
★ Goldring Magnetic P.U. Cartridge.
★ Pair of Stanway II speaker units
Special Total Price **£96-75** Carr. £1-50

Or Deposit £7-15 and 9 monthly payments £6-35 (Total £64-30). Trans. Plastic Cover £3-15 extra.
Package as above but with Garrard 3000 Auto-changer and Sonolone 87A Ceramic Cartridge in lieu of SP25 **£51-75** Carr. and £800.
Or Deposit £6 and 9 monthly payments £5-70 (Total £57-30). Trans. Plastic cover £3-15 extra.

TERMS AVAILABLE ON ALL PACKAGE OFFERS

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. COMPLETE KIT **£22**
★ Response 30-20,000 c.p.s. Carr. 63p
Impedance 15 ohms
★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-50 and 9 monthly payments £2-25 (Total £24-75).

DEMONSTRATIONS AT ALL BRANCHES

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.
DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 5in. **£9-45** Carr. 40p.
Dual Cone speaker. Imp. 3 or 15 ohms.
STANWAY II Size 20 x 10 1/2 x 9 1/2in. approx. Rating 10 watts. Inc. 13 x 5in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives **£17-85** smooth realistic sound output. See 'package offers' for illustration


RSC G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Suitable for Crystal Pick-ups, etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200-250V A.C. mains operation. Attractive silver finished metal face plate & matching control knobs.
COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring **£9-99** carr. 40p.
Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated or dep £2-50 and 9 mthly pymnts. £1-45 (Total £15-55).



R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION
HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL
Designed for optimum performance with any crystal or ceramic (trans. F.V. cartridge, Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 8-15 ohms ★ For 200-250V A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 24dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs.
COMPLETE KIT OF PARTS WITH FULLY WIRED DIAGRAMS & INSTRUCTIONS. Factory built with 12 months guarantee **£19-50** or Deposit £3 and **£15-50** Carr. 9 mthly pymnts £2-15 (Total £22-85). Or in Teak veneer housing **£23** Dep. £3 & 9 mthly payments £2-55 (Total £25-85). Send R.A.E. for leaflet

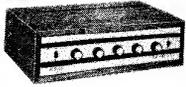

AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

5 + 5 WATT OUTPUT
GARRARD 5200 CHANGER WITH LOW MASS PICK-UP ARM AND STEREO CARTRIDGE.
CONTROLS: TREBLE, BASS, VOLUME, STEREO, BALANCE.
Operation on 200-250v. A.C. mains.
Output rating. I.H.F.M



PAIR OF LOUDSPEAKER UNITS incorporating high flux 8 x 5 ins. speaker. Size approx. 13 x 7 1/2 x 8 1/2 ins.
Price complete **£42** Carr. £1-25
ONLY
Terms: Deposit £5-50 and 9 monthly payments £4-50 (Total £46.)

A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINABLE FROM THIS COMPACT LOW PRICED SYSTEM

LOW DEPOSIT CREDIT TERMS

AVAILABLE ON PURCHASES OVER £8 (KITS OF PARTS EXCEPTED)
INTEREST CHARGES REFUNDED
ON CREDIT SALES SETTLED IN 3 MONTHS

- BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gt. Western Arcade (Half-day Wed.) 021-236-1279
- DERBY** 26 Osbaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. 556 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Hancroft Lane, Leeds 13. Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 25p extra under £2. 30p extra over £2 or as quoted. Trade supplied, S.A.E. please with enquiries. Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County(Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252 **LEEDS**
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**
- 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2779 **MANCHESTER**
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**
- 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 8½p per word (minimum 12 words), box number 7½p extra. Semi-displayed setting £6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Miscellaneous

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5-20 NOW

TO: 'BOFFIN PROJECTS'

DEPT. KW2010
4 CUNCLIFFE ROAD
STONELEIGH, EWELL, SURREY

JOHN SAYS...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module £7. Unit £8-90. **WAA-WAA** Pedal kit of all parts, incl. all mechanics & instr. Only £2-45. **AUTO RHYTHM** from Dewtron is a simple design with quite an AMAZING RANGE—etc. costs £16-55 in modules. **ORGAN PERCUSSION** and other fascinating effects. Send 15p for illust. list. D.E.W. Ltd., 25A Ringwood Road, Ferndown, Dorset.

AE 396

PICK-UP CONVERSION KIT

To replace E.M.I. Double 'C' cartridge, comprising pick up head shell, turn-over holder and dual sapphire cartridge. Mono only. Full D.I.Y. instructions supplied.

£3-72

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.,
Chilton Works, Garden Road,
Richmond, Surrey.

ENGINEERING SERVICE for constructors. Lathe work, milling, sheet metal, castings, etc. S.A.E. for details. Chelmsford Machine Tool Company, P.O. Box 55, Chelmsford CM1 2AU.

DAILY UFO Flight Patterns, 37½p. UFO Map, S. England, 37½p. TV Notes UFO Detection, 2 Optical Circuits, 50p. UFO Wave pattern and prediction, 45p. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

IRISH READERS. Eagle products available, send 10p in stamps for latest illustrated catalogue to Toner Electronics, Lismore Park, Waterford.

Miscellaneous

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 12 transistors for only £1

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (K)

17 Buckridge, Portpool Lane, London, E.C.1

THE NEW

ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2½p stamp.

17. BBC/ITV

TELEVISIONS £5

Working Perfectly
plus P&P £1 C.W.O.

SUITABLE FOR ANY AREA

3 Channel 19in D/S TVs. ITV, BBC 1, BBC 2, £25 inc. carriage. 17in 13 Channel, complete but untested £1-50 each, plus £1 P&P. C.W.O.

SPEAKERS

6in x 4in, 7in x 4in 3OHM
20p plus 8p P&P each. C.W.O.

Regular deliveries throughout England and N. Ireland.

TRADE TV'S

407 Thornton Road, Gillington, Bradford 8, Yorks.

MAINS KEYNECTOR

The safe quick way to connect electrical equipment without a plug!



SIMPLY PRESS KEY AND INSERT LEAD!

SEND ONLY
£2-75
+20p P&P

Revolutionary new Keynector connects electrical equipment to mains supply in seconds. Ideal for high-speed bench testing, shop demonstrations or do-it-yourself experts. Keynector can take multi-parallel connections up to 13 amp. maximum loading off one mains point, is easy to operate, and pays for itself by saving time. Safety features include wall or bench fixing built-in safety switch with 13 amp fuse, no protruding parts eliminates accidental shocks, special neon safety light shows Keynector is working. As selected for the Design Centre.

DEPT. P.W.1.
72 WILLESDEN LANE,
LONDON, N.W.8
01-824 4683


MARKTYME
(MAIL ORDER) LTD.

Miscellaneous

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond Surrey.

12 VOLT FLUORESCENT LIGHTS

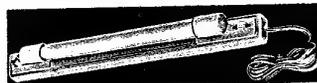

Beat Power Cuts, 12 ins 8 watt Tube, Ideal for Caravan, Tent, Emergency Lighting etc, Fully Transistorised, Low Battery Drain, With ON/OFF Switch and 12v Socket to Run other Lights or 12V Equipment.

Unbeatable at **£3-30** post paid
or in kit form **£2-90**

SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire S.A.E. for lists

CHEMICALS. Wide range. Send S.A.E. for list. Kemco, 22 Kemerton Road, London S.E.5. Mail Order only.

CONSTRUCTORS. Stop Marking Out Heat Sinks. Use my non-wear drill jig for all (TO3) Transistor Bases, e.g. OC25, OC28, OC20, etc. Price 40p plus 5p p&p. Enquiries: R. Camps, 115 St. Anthony's Drive, Chelmsford, Essex.

MARKEM ELECTRONIC AIDS

SIGNAL INJECTORS 1K/c output can be heard well above 40 M/Hz. £2-30 each.

SIGNAL TRACERS complete with earpiece: R.F. and A.F. input at the flick of a switch. £3-00 each, fully tested.

Both units use P.P.S. battery (not supplied) Post free in U.K. C.W.O. only.

KENWORTHY TOOLS LIMITED
LYON ROAD,
MERTON. SW19 2RT

Ladders

VARNISHED TIMBER LADDERS from manufacturer. Lowest prices anywhere. 15½ ft. extd. £6-20, 17ft. ext. £6-50, 20ft. ext. £7, 21½ ft. ext. £7-75, 24½ ft. ext. £8-90, 29ft. ext. £10-25, 31½ ft. triple ext. £12-25, 36ft. triple ext. £16. Carr. 80p. Free lists. Also Aluminium Ext. & Loft Ladders. Callers welcome.—(Dept. W.L.S.) Home Sales, Baldwin Road, Stourport, Worcs. Phone 02-993 2574/5222. Placing order on C.O.D.

Wanted

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

WE BUY New Valves and Transistors. State price: **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

TOP PRICES PAID for NEW VALVES popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

CASH PAID for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

WANTED: Murphy A40c. Condition immaterial, but must be complete. Box No. 96.

WANTED: PRACTICAL WIRELESS, March 1965. Electronic, December 1968. Borrow or buy. Top price paid. Write: G. Watts, 236 Dill Hall Lane, Church, Nr. Accrington, Lancs.

HIGHEST POSSIBLE CASH PRICES for Revox, Ferrograph, Brenell, Vortexion, Tandberg. 9.30-5.00. 01-837 8200.

Educational

YOUNG MEN (AND WOMEN) trained as Radio Officers on liners and other ships. Salaries rising to £2,500 per year (all found). Immediate vacancies. Grants available for Day full-time course. For details of training write to:

THE RADIO COLLEGE,
91 Lancaster Road, Preston, Lancs.
stating if interested in Day or Postal Course.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON, SW8 4UJ

MEN! You can earn £50 p.w. Learn Computer Operating. Send for **FREE** brochure—London Computer Operators Training Centre, C94 Oxford House, 9-15 Oxford Street, London, W.1.

GO TO SEA as a Radio Officer. Write: Principal, National College, Broadwater, Fleetwood FY7 8JZ.

Educational

RTEB CERTS., City & Guilds, Colour TV, Radio, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—**FREE**: **BIET**, (Dept. H.7), Aldermaston Court, Reading, RG7 4PF.

CIE, AMSE, City & Guilds, etc., on 'Satisfaction or Refund' terms. Thousands of exam. successes. Postal Courses for all branches of Engineering. Illustrated prospectus **FREE**. Please state subject of interest: **BIET**, (Dept. H.8), Aldermaston Court, Reading, RG7 4PF.

Situations Vacant

EAGLE INTERNATIONAL require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-636 0361.

RADIO OPERATORS

DO YOU HOLD PMG II OR PMG I OR NEW GENERAL CERTIFICATE OR HAD TWO YEARS' RADIO OPERATING EXPERIENCE?

Looking for a secure job with good pay and conditions

Then apply for a post with the Composite Signals Organisation—these are Civil Service posts, with opportunities for service abroad, and of becoming established i.e. non-contributory pension scheme.

Specialist training courses (free accommodation) starting January, April and September 1972.

If you are British born and resident in the United Kingdom write **NOW** for full details and application form from:

**RECRUITMENT OFFICER
GOVERNMENT COMMUNICATIONS
HEADQUARTERS
OAKLEY, PRIOR ROAD, CHELTENHAM,
GLOS. GL52 5AJ**

Telephone: Cheltenham 21491 Ext. 2270

Aerials

**BAKER AND BAINES
UHF AERIALS—BBC, ITA, BBC II**
all from one aerial.

All aerials come complete with tilt clamp and will fit up to a 2-inch mast. **POSTAGE PAID INLAND.**

8 element 1-90; 10 element £2-10; 14 element £2-35; 18 element £3-25; 22 element £3-75.

UHF Pre-Amps, high gain, low noise, completely self-contained with 9 volt battery. Group A, B and C available. Battery model £3-75, Mains £581, Postage 124p.

Low loss co-ax 625 type 11p per yard. Aerial lashing kits—poles—diplexers etc., SAE will bring full lists.

11 DALE CRES., TUPTON, CHESTERFIELD

For Sale

MORSE MADE !! EASY !!

FACT NOT FICTION If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:

G3HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL MAY...

Get these **air drying GREY HAMMER** NOW! OR **BLACK WRINKLE (CRACKLE) Finishes**

Yukan Aerosol spraykit contains 483g fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, Modern Eggshell Black Wrinkle (Crackle) all at 45p at our counter or 50p, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (399g self-spray cans only) 70c carriage paid.

Other Yukan Air Drying Aerosols: 450g of 90p carb-poid; Zinc Chromate Clear Lacquer; Metallic Grey, Blue.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 25p/60p 99c, carriage paid). Choice of 13 self-spray plain colours and primer (floor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

Dept. M-YUKAN, 307A, EDGWARE ROAD, LONDON, W2 1BN

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday, Closed Thursday afternoons.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. **S.A.E. K. R. WHISTON**, Dept. PW, NEW MILLS, Stockport.

AUSTRALIAN READERS! SEND **S.A.E. FOR ELECTRONICS CATALOGUE**. **HOBIPAK**, P.O. Box 224, Carlton South, 3053, Victoria, Australia.

Metal Work

METAL WORK: All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

Service Sheets

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 10p. **S.A.E. enquires**. **TELRAY**, 11 Maudland Bank, Preston.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each, Manuals from 50p. **"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"** Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

**C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11**

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

Service Sheets

Service Sheets & Manuals

LARGE RANGE OF MODELS AVAILABLE FOR RADIO, TELEVISION, TAPE RECORDERS, R/PLAYERS, ETC.
FROM 25p EACH — S.A.E. WITH ENQUIRIES PLEASE — 1971 LISTS ARE AVAILABLE 13p.

MULLARD TRANSISTOR AUDIO AND RADIO CIRCUITS	PRICE £1-65p	
T.V. FAULT FINDING BOOK BY DATA PUBLICATIONS LTD.	55p	
MULLARD VALVE & SEMI CONDUCTOR DATA BOOK	25p	Post free
MAZDA VALVE & PICTURE TUBE DATA BOOKLET	25p	
BRIMAR VALVES & TELE TUBE DATA LIST	20p	
RESISTOR COLOUR CODE INDICATOR DISC	13p	

Sets of Brand New Valves supplied for most makes of Radio / T.V. etc. Prices on request.

BELLS TELEVISION SERVICES
Albert Place Harrogate Yorkshire Tel 0423-86844

RADIO, TELEVISION over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone Bexhill 7097.

SERVICE SHEETS. TV, Radio, etc., 25p. Large stocks. S.A.E. with enquiries please, callers welcome. K. L. Bower, 35 Briarwood Drive, Wibsey, Bradford.

TRADER SERVICE SHEETS

40p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES

LIMITED

29 CHURCH ROAD,
TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1971 List now available at 10p. plus postage

If list is required indicate with X

From

Address

enclose remittance of

(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (February PW)

Receivers and Components

BRAND NEW COMPONENTS by return. Electrolytics 15 or 25 volts, 1, 2, 5, 10 mfd. 3.5p 25, 50 4p, 100 5p. Mylar film 100V .001, .002, .005, .01, .02 2p, .04, .05, .1 2-5p. Mullard miniature Carbon Film Resistors 1/2 W E.12 series 10-10MΩ for 5p. Postage 5p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

Receivers and Components

TRANSFORMERS, Chokes, Solenoids rewound. Modern, obsolete or unusual types, any size or voltages. Guaranteed as new. SAE enquiries. Ratcliffe, 18 Beech Avenue, Thongsbridge, Huddersfield.

PRINTED CIRCUITS

PW 10 Watt Amplifier (May 1971) Price 55p inc. p/p.

PW Hi-Fi Signal Generator (May 1971) with separate Stabilised Power Supply. Total price £1.15 inc. p/p.

All boards are drilled and tin plated with the reverse side screen printed for easy component and connection identification.

Send S.A.E. for List of other P.C. Projects.

SERVITRON ELECTRONICS

18 Beckdean Ave, Poulton-le-Fylde, Blackpool, Lancs. FY6 8BG.

CIRCUITS CIRCUITS CIRCUITS

Ten exciting circuits per month with instructions to build. Every month a completely new set. This month's circuits cover

RECEIVERS OF ALL KINDS

Only 50p per set of ten p & p free
Free Data and Technical A-Z cards (build up the complete set month by month).
Cheques and PO to Dept FWC, Phonotronics, 3 Whitehall Gardens, London, E4.

See for details.

SINCLAIR SUPER IC-12

12 W integrated circuit amplifier and pre-amplifier. Frequency response 5Hz-100kHz ±1dB. Harmonic distortion less than 1% (Typically 0.1%). Supply voltage 6-28V (PZ5 or PZ6 power units ideal—see below for our low prices). Supplied complete with comprehensive instruction and application manual.

ONLY £2-65

SINCLAIR BARGAINS

Power supply PZ5 £3-80. PZ6 £6-80. PZ8 £8-80. Transformer for PZ8 £2-25. Micro-matic receivers—Assembled £2-70. Kits £2-20. Batteries 27p extra.

EMI PROFESSIONAL RECORDING TAPE

First grade, brand-new, unused, 1/2 inch, standard play magnetic tape with leaders. Supplied in manufacturer's attractive sealed boxes. A superb bargain at £1 for 1200ft or 65p for 600ft.

SINCLAIR PROJECT 60 OFFERS

Stereo 60/2 Z30/PZ5	£16-40
Stereo 60/2 Z30/PZ6	£19-00
Stereo 60/2 Z50/PZ8	£21-25
Transformer for PZ8	£2-25
Project 60 FM tuner (in stock at last)	£20-50
Active Filter Unit	£4-75
Q16 Loudspeaker	£7-70
Kit of extra capacitors, plugs, cables, fuse to complete Project 60	£2-20

S-DECS AND T-DECS

Buy at our new low prices. Solderless, plugin, breadboard panels allowing rapid construction of lashups and unending re-use of components.

S-DeC (70 points)	£9-95
T-DeC (208 points)	£2-10

THE 0-7P TRANSISTOR

Surplus PNP silicon transistors supplied complete with data. From 2S300 series. Typical Vcb = 25 V, hfe = 35, ft = 1 Mcs, Pmax = 300 mW. Untested and unmarked, but we guarantee at least 80% are good. 50 for 40p. 100 for 70p.

SWANLEY ELECTRONICS

32 GOLDSSEL RD., SWANLEY, KENT

Mail order only. Postage 37p on Project 60 orders, 10p on others. All goods are brand new. Money back if not satisfied.

Receivers and Components

EX-GOVT. COMMUNICATIONS RECEIVERS, calibrators, signal generators, components, etc., with money back guarantee. SAE list. Callers welcome, please phone first.—P. R. Golledge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only £3-40. P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12pp. P. & P. Free.

Cheques, Postal Orders to:

Dept. P.W.,

Galleon Trading Co., 25 Avelon Road, Romford, Essex

COMPLETE RANGE of receivers by Trio, Lafayette, Hallicrafters, etc. Chassis, panels, cabinets. S.A.E. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263 7829.

Stella Nine Range Cases

LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7 1/2" Height
6 1/2"	3 1/2"	90p	£1-05	£1-23
6 1/2"	4 1/2"	96p	£1-23	£1-40
8 1/2"	3 1/2"	£1-05	£1-40	£1-40
8 1/2"	6 1/2"	£1-40	£1-74	£2-00
10 1/2"	7 1/2"	£1-88	£2-28	£2-45
12 1/2"	3 1/2"	£1-40	£1-74	£2-03
12 1/2"	5 1/2"	£1-85	£2-25	£2-43
12 1/2"	8 1/2"	£2-30	£2-74	£2-93
14 1/2"	3 1/2"	£1-65	£2-03	£2-25
14 1/2"	9 1/2"	£2-73	£3-50	£3-65
16 1/2"	6 1/2"	£2-45	£2-93	£3-24
16 1/2"	10 1/2"	£3-15	£4-05	£4-45

Cases—Post 25p. per order.

Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/2" Walls

6" x 3"	33p	10" x 7"	51p	14" x 3"	44p
6" x 4"	34p	12" x 3"	40p	14" x 9"	84p
8" x 3"	39p	12" x 5"	45p	16" x 6"	64p
8" x 6"	46p	12" x 8"	64p	16" x 10"	95p

Chassis—Post 15p. per order.

Discounts available on quantities.

Electro magnetic counters. New Boxed. 500 ohm 4 digit 30p post free.

Copper Laminate Board 1/8" single sided. 12" x 12" 30p. post free.

P.O. relays (600 Type) 500 ohm + 500 ohm. 1 make 1 break 2 change over New boxed 30p post free.

Heavy duty sliding reostat. 1 ohm 12 amp New boxed £1-25p. post free.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD
STOCKPORT - CHESHIRE

Tel: 061-480 2179

COMMUNICATION RECEIVERS

Checked and tested HRO, CR100, etc. Many other types available, also power supplies, amateurs' testgear, etc. SAE details, stating requirements.

Precision Stabilised Power Supply Compact unit in grey hammer case.

Mains input. Fully metered outputs 220-400 V stabilised, 150 mA. 550 V 150 mA. Also 6.3 V 4 A, 6.3 V 2 A (twice). Excellent condition £5-70, carriage £1.

Richard Sellers, Eastington, Goole, Yorkshire. 04-305 254.

Receivers and Components

MICROCIRCUITS:

700	40p	BL402A	£1.75	7420	31p
741	75p	MEL11	30p	7473	42p
PA230	97p	D40C1	55p	7474	42p
PA234	87p	7400	31p	7488	62p
PA237	£1.63	7410	21p	DIL conn.	25p

TRANSISTORS:

2N3055	60p	ME402	21p	ME4102	12p
2N6172	7p	ME412	20p	ME6001	13p
BOY70	18p	ME413	18p	ME8101	15p
BD124	80p	ME1002	12p	MEP104	45p
BFX80	15p	ME4101	11p	MEP811	35p

1 AMP RECTIFIERS

80V	7p	400V	10p	600V	14p	1000V	19p
Bridges	—	80V	37p	100V	40p	200V	40p

Printed Circuit Resist Fen . . . 80p

JEF ELECTRONICS (P.W.)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only, C.W.O.
P.&P. 5p per order. Overseas 40p.
Money back if not satisfied.
List free on application.

CHROMASONIC ELECTRONICS

supply only brand new guaranteed goods

LOW NOISE HI-STABS

4 watt 5% all E24 values 3 for 2p plus p. & p. 6p up to 50 resistors + 1p for each additional 50.

CAPACITORS

Multifar C280-.01 mf., .015 mf., .022 mf., .033 mf., .047 mf. 2p each.

.068 mf. 81p., .1 mf., .15 mf. 4p., .22 mf. 6p., .33 mf. 81p., .47 mf. 8p., .68 mf. 11p., 1 mf. 13p., 1.5 mf. 20p., 2.2 mf. 24p.

C450 series now all 6p. Also in stock C388, C431 and C487 series, plus polystyrene and S. mica's.

SN7400N, 1, 2, 4, 6, 10, 20, 30, 40, 50, 51, 64

SN7480N all 28p ea.

SN7414N, 42, 51, 62, 66, 92, 93, 94, 95 all 87p ea.

MC1301L £1.85 PA234 87p TAA320 65p

MC1304P 28.50 PA237 11.67 TAD100 11.95

MC1305P 28.50 PA246 11.60 µ7080 80p

MPC4000P 70p TAA288 70p 4710 50p

MPC4510P 75p TAA300 11.50 UA7410 75p

BC107 15p BF187 25p

BC108 11p BF173 25p

BC109 12p BB104 87p

BC147 15p BB105G 20p

BC148 12p BZY88 series

BC149 15p Zeners 15p each

2N3058 25p 2N3819 35p

2N3054 50p T1843 35p

2N3005 70p 1N4004 10p

FREE CATALOGUE p. & p. 3p.

p. & p. on all orders other than resistors 6p.

56, Fortie Green Road, London, N10, 3HN

EX RENTAL TV's

17" Semi 81mm (90 degree tube)	£23
17"/21" 81mm (110 degree tube)	£25
10" 81mm	£28
10" 3 channel sets	£16

All TV's sold complete but unserviced, 12 channel tuners, good cabinets, plus carriage £1.

PERFECT SPEAKERS EX TV

PM 3 ohm (minimum order two) 5" round, 8" by 4" rectangular—121p each. Add 74p per speaker postage and packaging.

VALVES EX EQUIPMENT

8E01	15p	86L16	18p	PCL82	171p	6Y82	171p
8EFA9	121p	80P4	18p	PL46	801p	80P18	80p
8CC82	121p	PC97	171p	PL41	171p	80F5	10p
8F90	121p	PCF90	171p	PV81	15p	80L17	171p
8F96	121p	PC84	71p	PV80	15p	80PL1	181p
8F180	121p	PCF80	71p	PV82	71p	80P16	80p
8F184	121p	PC89	161p	PV83	801p		
8Y80	171p	PCL85	881p	U191	171p		

ADD 21p PER VALVE P. & P. ORDERS OVER £1 P. & P. FREE

UHF TUNERS

To suit Ferguson 860 900 Chassis £2.50p P. & P. 50p

SLOT METERS

Smiths 6d/2p switchmaster Mk II £1 including P. & P. £2 for 10 delivered.

Dept. T.S.

THORNBURY TRADE DISPOSALS

Thornbury Roundabout, Leeds Rd., Bradford
Telephone 66670

RADIO SPARES EQUIPMENT

Now available for enthusiasts and amateurs. Callers by appointment. S.A.E. must accompany all enquiries.

SONAR GROUP (Dept. P.W.),
24 Fordway Avenue, Blackpool, Lancs.
Telephone 0253 (Blackpool) 32819

RESISTORS BRAND NEW, 1p each
1/2 W, 100 1K 10K. Discount 100+10%;
500+15%; 1000+20%. Minimum order
10 mixed or single value. Post 4p, over
100 post free. C.U. Resistors, 10 Auckland Avenue, South Shields, Co. Durham.

SAVE MONEY build your own speakers

And save even more with Cava's Big Discounts

	Unit	Price	Cash
LEAK 800	pair	£49.90	£34.90
LEAK 800	pair	£59.00	£44.95
W/GALE TRITON	pair	£39.95	£29.95
Kof Kit 3		£39.00	£29.80
T17 Tweeter		£3.00	£2.75
T19 Tweeter		£8.00	£5.10
B110 LF MED unit		£8.07	£7.10
8000 LF unit		£9.31	£8.00
B139 LF unit		£10.60	£10.00
DNE Xover		£1.75	£1.50
DNE Xover		£2.00	£1.45
EMI 450 Kit (10 watts)		£5.16	£3.50
W/ale unit 3		£13.00	£11.00
W/ale unit 4		£17.00	£14.75
W/ale unit 5		£20.00	£17.50
Taney 1112Z		£31.00	£27.95
Taney 12 Gold		£36.90	£31.95
Taney 15 Gold		£45.95	£37.95
Telefunken G410		£32.00	£28.50
Telefunken G400		£24.00	£21.50
Armations 821		£28.00	£24.50
Armations 800		£24.00	£21.00
Meltracord ST20E		£39.90	£33.50
Sinclair Z		£25.00	£22.25
Sinclair Z		£24.00	£21.50
Sinclair Z		£20.95	£18.95
Sinclair Z		£27.22	£23.00
Sinclair Z		£24.47	£21.50
Sinclair Z		£4.07	£4.10
Sinclair PZ-3		£7.97	£6.50
Sinclair PZ-3		£7.97	£6.50
Sinclair A.F.U.		£5.97	£2.10
Sinclair Control 80		£3.97	£2.50

SEND 5p STAMP FOR TREMENDOUS MONEY SAVING CATALOGUE—COMPARE OUR PRICES AND START SAVING MONEY RIGHT AWAY

F. CAVE TOP DISCOUNTS

Dep. PW, 5 BRIDGE ST., RICHMOND, SY.
Tel. 01-948 1441.

Dep. PW, 27 EDEN ST., KINGSTON, SY.
Tel. 01-546 7845.

Dep. PW, 86 SOUTH ST., ROMFORD, ESSEX.
MAIL ORDERS TO RICHMOND

JOHNSONS (RADIO)

ST. MARTINS GATE, WORCESTER
Est. 1943 Tel. 24884

NEW! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Converter, Receiver and tuner-feeder. Fantastic transistorised performance! Complete kit of high grade parts with coils covering 80-178MHz, 9v battery, etc., plus easy/build diagrams and instructions, 24-19p direct from makers. S.A.E. for free literature


FAMOUS TELETON—AM/FM

Stereo Tuner Amplifier R8000

Supplied complete with 2 speakers. Total 12 watts RMS. Specification MPX Beacon, AFC Connections for Tape Recorder, Stereo Headphone Socket, etc. Mfgs. Rec. Price £63.50

P.S.P. FANTASTIC OFFER **only £39.95**

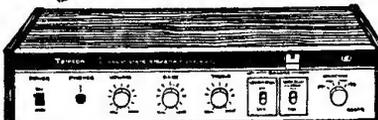Plus GARRARD DECK 2025 Complete with plinth and perspex cover. Fitted with superb Sonotone 9TAHCO cartridge. P.S.P. offer **ONLY IF YOU BUY THE ABOVE only £15.40**



PERSONAL SHOPPERS PLAN LTD.
The Centre
36-38 West Green Road, Tottenham, N.15
Tel. No. 01-800 5533

SAVE ££s
ANOTHER PSP SUPER SCOOP



All orders C.W.O. Special Securicor fast delivery £3.

STOP PRESS!
FREE FREE! Pair Teleton Stereo Headphones, value £5, if you order the above before September 30

TELETON SAQ 206 STEREO AMPLIFIER
Latest release, beautifully styled in walnut case, 6+6 watts r.m.s. Switched inputs for magnetic X tal, aux, Tape. Incorporates volume, bass, treble and, slide balance control, scratch filter and loudness control. Rec. £32.50. Our price £19.95.

Suggested System.
SAQ 206 Amplifier, SP25 III Plinth and Cover, G800 cartridge, pair large 3-way speaker system size 18" x 10" x 7" Would normally cost £85 complete. Our price £59.95

Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)
 Transistors etc. AC126 12½p. AF115 20p. AF116 15p. AF117 20p. OA5 7½p. OA10 7½p. OA81 7½p. OA85 7½p. OC25 32½p. OC25 30p. OC28 37½p. OC28 42½p. OC35 42½p. OC44 14p. OC45 12½p. OC7 12½p. OC7 12½p. OC75 18½p. OC81 12½p. OC81D 12½p. OC82D 12½p. OC170 20p. OC171 12½p. Many more in list. S.D.R. BY100 800piv 14p. 8 amp series: BYZ13 300piv 20p. BYZ12 600piv 25p. BYZ11 900piv 30p. BYZ10 1200piv 35p. (Charges 6½p up to 11, paid for 12 and over). Sub-Min Transformers: OUTPUT 2.0 for OC72 etc.) 14p (up to 9, 9½p). **MULTIMETER**. Our famous 20000 Ω per V £4.62 (10p). All parts replaceable, highest quality, full guarantee: £1.07 (10p). **DIAMOND SYLLI** Replacements for BSE TC8/LP, TC8/S, TC8LP/STEREO; COLLARO 'O'; RONETTE BP 40LP; Garrard GC2/LP and GC8/LP; ACOS GP65/67, all at 40p. (5p). **CDOS**: PHILLIPS AG3306, 3060 (3065, 3066, 3301, 3302, 3304); Garrard GKS25, GCM21, GC823, and many more 'Garrard' etc. types. All at 75p. (6p). All are of the very highest quality. **DOUBLE DIAMOND**: ST4 (ST3, ST5); ST10 (ST9, ST8); STA, STAHC, 3306, GP91 (For GP92, GP93, GP94 cartridges); GP91-80 for all GP91-80 Cartridges. All at £1.50 each (6p). **PICK-UP CARTRIDGES**. All Standard fittings and stylus. Mono GP67/2 50p. STEREO-COMPATIBLE (MONO) GP91/SC £1.10 STEREO GP93 £1.30 STEREO CERAMIC GP94 £1.95 SONOTONE STEREO STAHC (DIA.) £2.40. **GOLDRING** G850 £4.87p. G800 £2.50. G800E £13.50. G800 SUPER E £19.50 (6½p all types or Reg. Post, 22½p). **SYLLI FOR ALL ABOVE TYPES**, including **GOLDRING** available. **RECORDING TAPE**. Still the finest quality British Mylar available. Standard 5" 600ft. 36p. 5" 900ft. 50p. 7" 1200ft. 56p. **LONG PLAY** 5" 900ft. 50p. 5" 1200ft. 56p. 7" 1800ft. 80p. (7½p on 5" and 5½", 9p on 7"). **MICROPHONES** Crystal Mic 91, hand/desk 81p. MIC45. Curved metal hand-grip £1.00. CM21 Grey hand desk 62½p. Stick '60' £1.02. CM70 "Planet" unsheathed metal tapered stick type with neck cord, adaptor for floor stands £1.47 (5½p). LAPEL (or hand) with clip 32½p (6p). All are fitted with leads. **Dynamic MS10 50K Ω** for desk, tapered with base and slide-out adaptor £1.97. **MS11**. Similar, but fixed on swivel swan neck to switch-fitted base, £2.22 (Either 15p). **Type 209 Cardioid** ball, 50K/800 Ω, omnidirectional, built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £2.30. **UD130 Uni-Dir.** Ball, mesh, 50K/600 Ω. Adap. cable, jack plug 24.80. (20p). **DM160**, omnidirectional. Ball 50K. Cable adaptor £3.87 (all at 27½p). **MICROPHONE INSERTS**, Dia., 1.75" OR 0.9" either size 27½p (6p). **EARPIECES** with lead and min. jack plug (2.5 or 3.5 mm., state which). **Magnetic 9p Crystal (3.5 only) 24p** (Up to 3 for 6p on any). **HEADPHONES** De-luxe STEREO 8-16 Ohms £2.47. Same, fitted vol. control each earpiece £4.20. Both have lead and stereo jack plug (17½p) High Res. 2000 ohm. Adjustable 92½p (7½p). **SPEAKERS** 12" ROUND fitted tweeter, 3 or 15 Ω (state which) £1.87 (27½p) for Stereo £4.25 pair, carr. paid 2½" 3 OR 8 Ω (state which) 87½p (6p). **EMI 13" x 8", 3, 8 or 15 Ω** (state which) £2.12 (25p); with two tweeters and ec. pins. 27½p. 12.7" pin 8ydc. (28.7) 62½p. (28.7) 62½p. (Both types 6½p per vibrator). **CONNECTING WIRE**. Packs of 5 coils assd. cols. ea. coil 5yds. Solid core 14p (6p). Flexible 16p (7½p). Super thin for transistor wiring 16p (6p). **PICK-UP WIRE**. Super thin twin flex, screened and sheathed 6p yd. (6p up to 6yds., over free). **RETRACTABLE Flex. Leads**. (Curlies) Phonoplug each end 12ft. 30p. 6ft. phono plug/phono socket other end 25p. 12ft 42½p (6p per lead all types). **SEND S.A.E.** for full free lists—Small 3W and 7½W trans. amplifiers, Electrolytics, Vol. Controls, all types of radio switches, car and portable expanding aerials, Meters, Test prods, all types of Brit. and Cont. standard and min. plugs and sockets SDR's, Thyristors, cros. clips (various) terminals, etc. etc. and "Special Offer" lines at lowest possible prices.

FELSTEAD ELECTRONICS (PW 48)
 LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE
 Cash with order only. No COD or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage, unacceptable. SAE please for enquiries or cannot be replied to. Charges apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: **British National Radio School, Reading, Berks.**

Please send **FREE BROCHURE** to

NAME Block
 ADDRESS Caps.
 Please

9/71

BRITISH NATIONAL RADIO SCHOOL

INDEX TO ADVERTISERS

Adcola Products Ltd.	Cov. 2	Galleon Trading Co....	445	Photronics	445
Antex	377	Global Audio Discount		Premier Radio	362
Audio Supplies	375	Warehouses	369	Radio College, The	444
Baker & Baines	444	Government Communications		Radio Components Specialist	381
Baker Reproducers Ltd.	378	Headquarters	444	Radio Exchange Co.	367
Bells Television Services	445	'HAC' Shortwave Products	442	Radio & T.V. Components (Acton)	
Bentley Acoustic Corporation Ltd.	442	Harverson Supplies Co. Ltd.	424	Ltd.	364, 365
B.I.E.T.	376, Cov. 3	Henry's Radio Ltd.	Cov. 4	R.D.I. Ltd.	443
Bi-Pak Semiconductors	428	Home Radio (Components) Ltd.	361	RSC Hi Fi Centres Ltd.	440, 441
Bi-Pre-Pak Ltd.	363	International Correspondence		R.S.T.	380
Boffin Projects	443	Schools	444, 366, 427	Salop Electronics	443
British National Radio School	419, 447	Ivoryet	370	SEBA Electronic Photography	434
Broadway Electronics	438	Jackson Brothers (London) Ltd.	362	Service Trading Co.	392
Bull, J., Electrical Ltd.	435	J.E.F. Electronics	446	Servitron Electronics...	445
Caranna, C.	444	Johnsons (Radio) Ltd.	446	Sellers	445
Cave, F., Ltd.	446	Kemworthy Tools Ltd.	443	Sefray Book Co., The	380
Chromasonics	446	Kensington Supplies...	444	Sinclair Radionics Ltd.	431, 432, 433
Circuits & Supplies	443	King, J. M.	443	Shopertunities Ltd.	368
C.O.I. (Royal Navy)	374	KVA Electronics	442	Smith G. W. & Co. (Radio) Ltd.	371, 372, 373
Colomar (Electronics) Ltd.	434	Lasky's Radio Ltd.	382	Sonar Group	446
Comet High Fidelity Discount		Light Soldering Developments Ltd.	366	Stephens Electronics	423
Warehouse	436, 437	Lewis Radio	376	Surplronics...	378
Concord Electronics Ltd.	395	London Computer Operators Training		Surplus Electronic Trading	392
Control Data Institute Ltd.	438	Centre	370	Swanley Elec	445
Crescent Radio	378	M & B Components (Leeds) Ltd.	370	Technical Trading	434
Dexter & Co.	368	Magtor Ltd.	370	Thacker, A. H....	392
D.E.W. Ltd.	443	Marktyme	433	Thornbury Trade Disposals	446
Discosound	391	Marshall, A., Son	379	Trade TVs	443
Duke & Co. (London) Ltd.	376	Multicore Solders Ltd.	434	West London Direct Supplies	368
Electro Value	439	Nicholls, E.R.	445	Weyrad (Electronics) Ltd.	374
Felstead Electronics	447	Oakfield Enterprises	445	Wicks, D. T. & Co.	Cov. 2
Field Electric Ltd.	368	Personal Shoppers Plan Ltd.	446	York Electronics	378
Francis, George	442	Photain Controls Ltd.	362	Yukan (Cesar Prod)	454
				Z & I Aero Services Ltd.	448

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical
A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesl Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship
A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic
A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomm.
C. & G. Telecomm.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero
A.M.I.M.E.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production
Computer Programming
Inst. of Marketing
A.C.W.A.

Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional
A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General
C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education
Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T., and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.
WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT— SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B2, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



BIET

POST THIS COUPON TODAY

To: B.I.E.T., Dept B2, Aldermaston Court, Reading RG7 4PF.
Please send me book and details of your Courses in

Name..... Age.....

Address.....

Occupation.....

453A

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2-65. PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.


HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI - COMPONENTS - TEST - PA - DISCOTHEQUE - ELECTRONIC ORGANS - MAIL ORDER

COMPLETELY NEW
10th EDITION
CATALOGUE

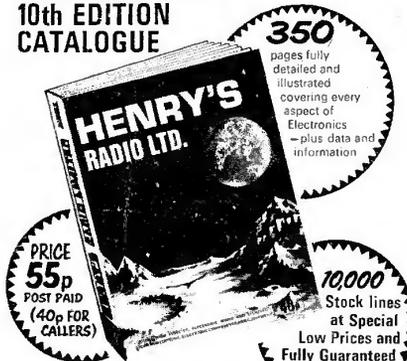

PRICE
55p
POST PAID
(40p FOR
CALLERS)

350

pages fully
detailed and
illustrated
covering every
aspect of
Electronics
— plus data and
information

10,000
Stock lines
at Special
Low Prices and
Fully Guaranteed.

**PLUS! FIVE 10p VOUCHERS
FOR USE WITH PURCHASES**

FREE to Industry, Educational or any Organisation,
including Schools and Colleges etc.
Apply on Official heading to our "303" address.

**A NEW HENRY'S CATALOGUE IS
A MUST FOR ELECTRONICS TODAY!**

To Henry's Radio Ltd. (Dept. P.W.)
3, Albemarle Way, London, E.C.1.

Please send copies at 55p each Post Paid

I enclose Cheque/PO for

(Use BLOCK CAPITALS—cut out and send with
Cheque or Postal Order (No cash please) Use only
for ordering catalogue)

Name

Address

..... P.W.

Allow 7-10 days from date of posting.

**MORE OF EVERYTHING AT LOW
PRICES ALWAYS FROM HENRY'S**

*Components from stock for
almost all published designs.




TRANSISTOR AMPLIFIERS

NEW RANGES NOW IN STOCK
(Leaflets Ref. No. 6 and 8)
Post etc. 20p

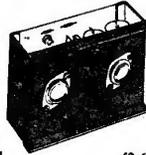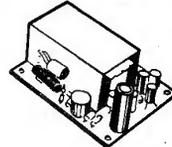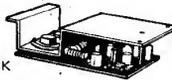- 4-300 4 TR 9V 300mW £1-75
- 104 4 TR 9V 1W £2-12
- 304 4 TR 9V 3W £2-47
- 555 6 TR 12V 3W £2-75
- PA7 6 TR 16V 7W £3-62
- 608 6 TR 24V 10W £4-12
- 410 4 TR 28V 10W £4-97
- MPA12/3 6 TR 18V 12W £4-50
- MPA12/156TR36V12W £5-25
- Z30 9 TR 30V 20W £3-75
- PA25 10 TR (Sp) 25W £7-50
- Z50 30V 40W £5-47
- PA50 12TR (Sp) 50W £9-50
- 100 100W with Power Supply £45-00
Post 45p

OPTIONAL POWER SUPPLIES

- Post etc. 20p.
- PS00 (One or Two) for 104, 304 £2-62
- PS20 (One or Two) for PA7 £3-47
- MU24/40 (One or Two) for MPA12/3 or MPA12/15 £4-50
- P75 for Z30 £3-97 or PZ6 for Z30 £6-97
- PZ8 for Z50 £3-97 Transformer £2-25
- P11 for 608 £2-87 P15 for 410 £2-62
- MU442 for 1 or 2 PA25 or 1 only PA50 £6-50



HI-FI TO SUIT
EVERY
POCKET




CHOOSE 100 STEREO
FROM SYSTEMS

and a complete range of
individual units in stock—
Demos 1st class all day—
visit our new HI FI Store.
LOW CASH OR CREDIT/
HP TERMS (Credit terms
from £20 purchase—callers
only).
FREE—Stock list No.
16, 17 on request—
BEST VALUE IN U.K.

NEW MINIATURE LOW COST AMPLIFIER

MODEL 4-300

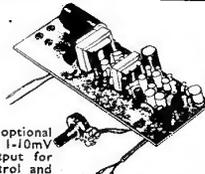7 volt operated or mains unit optional
transformer (MT98 70p), 1-10mV
adjustable sensitivity. P/P output for
3-8 ohms. Fitted volume control and
leads. Size 5 1/2" x 1 1/2" x 1/2". Thousands
of uses—takes magnetic, dynamic and
crystal inputs direct. Output 300mW—
very high gain—built in rectifier circuit.
Complete with FREE leaflet No. 8.




PRICE £1-75
p.p. 15p

GARRARD TAPE DECK



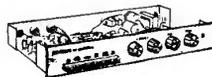9 volt operated 2-speed
tape deck fitted Record/
Replay 1 track and Erase/
Bias Osc. Head. Complete
with Oscillator/Record
head circuit. Unit size
9" x 6 1/2" x 1 1/2" and 2 1/2"
below motor board. Takes
up to 4" spools. Supplied
Brand New.
Price £9.97 P. & P. 33p
3 1/2" Tape 300" and spool 40p



HENELEC EQUIPMENT (as previously advertised)

SELF-POWERED SILICON
PRE-AMPLIFIERS
FET.154 Stereo £16-50 Post 25p
FET.9/4 Mono with mike mixer £12-50
Post 20p

SILICON POWER AMPLIFIERS
FOR USE WITH ABOVE
PA25 25 watts into 8 ohms £7-50
Post 20p
PA50 50 watts into 4 ohms £9-50
Post 20p

MU442 Power Supply for 1 or 2
PA25's or 1 only PA50 £6-00 Post 20p

PACKAGE DEALS
FET.9/4 plus PA25 plus MU442 £25
Post 40p
FET.9/4 plus PA50 plus MU442 £27
Post 40p
FET.154 plus 2xPA25 plus MU442 £36
Post 50p
FET.154 plus 2xPA50 plus 2xMU442
£40 Post 50p

NO SOLDERING—JUST EDGE
CONNECTORS AND
DIN PLUGS SOCKETS
FREE BROCHURE No. 25

BUILD YOURSELF A QUALITY RADIO

Excellent printed circuit
design with full power
output. Fully tuneable on
both MW/LW bands. 7
Mullard transistors. Fitted
5in. speaker. Room filling
power. Easy to build with
terrific results. Two colour
leather-cloth cabinet with
silvered front. All local
and continental stations.
Complete detailed instruc-
tions.



Total cost £6-98 p.p. 35p. All parts sold separately.
Ask for leaflet No. 1.

SINCLAIR PROJECT 60 PACKAGE DEALS
2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply,
£18-75. Carr. 40p. Or with PZ6 power supply £18-25.
Carr. 40p. 2xZ50 amplifier, stereo 60 pre-amp, PZ6 power
supply, £20-25 Carr. 40p. Transformer for PZ5 £2-25
extra. Any of the above with Active Filter unit add £4-75
or with pair Q16 speakers add £15. Also new FM Tuner
£21.

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS
300 kc/s BAND-WIDTH,
PRINTED CIRCUIT, HIGH
FIDELITY REPRODUCTION,
MONO AND STEREO.
A popular VHF FM Tuner for
quality and reception of mono
and stereo. There is no doubt
about it—VHF FM gives the
REAL sound. All parts sold
separately.



Free Leaflet No. 3 & 7.
TOTAL £6-97 p.p. 20p. Cabinet 100p. Decoder Kit £5-97
Tuning meter £1-75
Mains unit (optional) Model PS900 £2-47
Mains unit for Tuner and Decoder PS1200 £2-62

Electronic Components,
Audio and Test Gear Centre
356 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales &
Demonstrations Centre
354 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 5854

Electronic Organs,
P.A. & Discotheque Centre
309 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 6963

Mail Orders, Special Bargain
Shop, Industrial Sales
303 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY