


# PRACTICAL WIRELESS

MARCH  
1972

20p

FREE INSIDE  
**DX DATA**  
WALL CHART

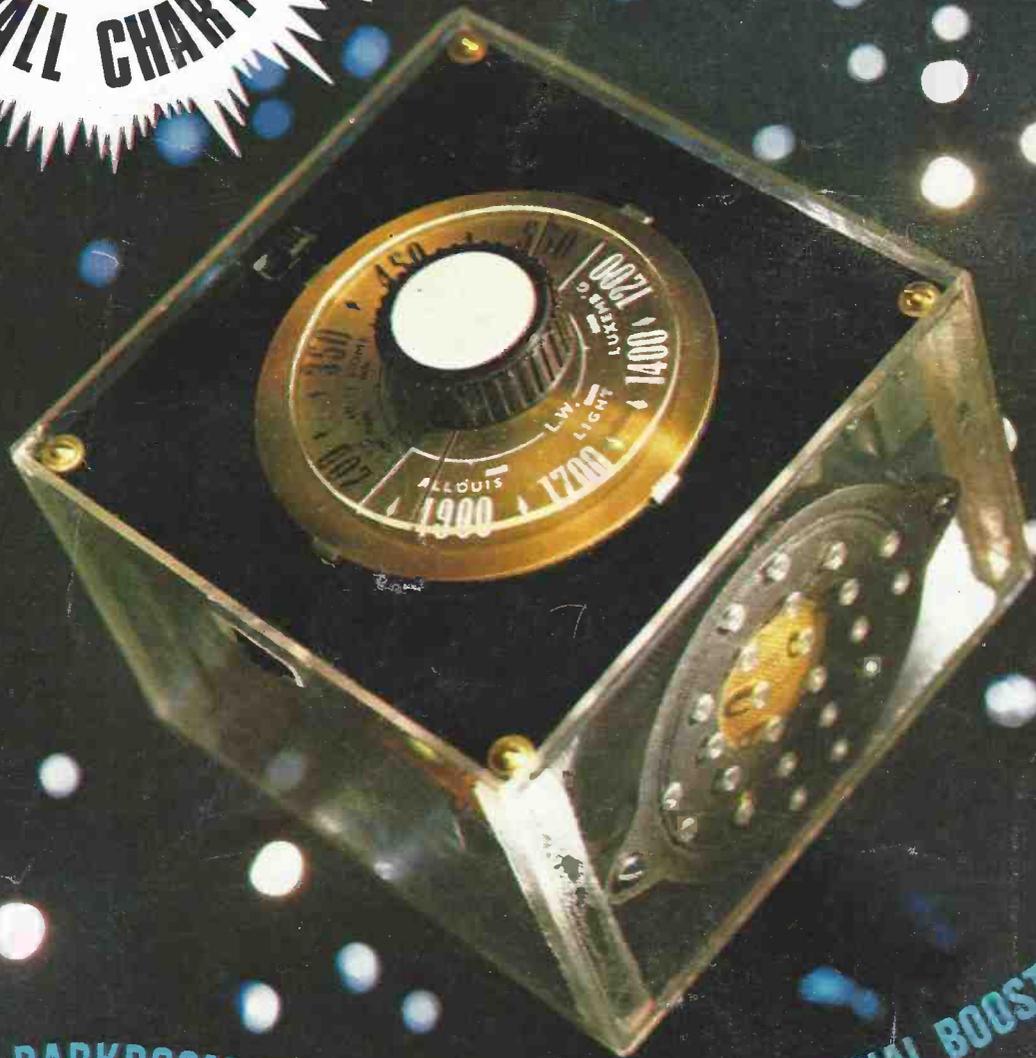build the PW  
**CUBE RADIO**  
7 transistor superhet



ALSO: DARKROOM THERMOMETER · CAR RADIO SIGNAL BOOSTER



# HIGH-FIDELITY STEREO

## PACKAGE OFFERS

Four fully wired units ready to 'plug in'

- ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
- ★ GARRARD SP25 MK III Turntable on Plinth with cover
- ★ GOLDRING CS90 Ceramic Pick-up Cartridge with diamond stylus
- ★ PAIR OF STANWAY II Speaker Units

Special Total Price **£79.80**  
Carr. £1.50

Terms: Deposit £12 and 9 monthly payments £8.55 (Total £88.95).



ATTRACTIVE TEAK OR AFRORMOSIA VENEERED CABINETS AND PLINTHS

Send S.A.E. for coloured brochure showing other money saving offers.

- ★ TA12 AMPLIFIER 6.5 + 6.5 watt in veneered housing
- ★ GARRARD SP25 MK III Player unit on Plinth
- ★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus
- ★ PAIR OF DORCHESTER Loudspeaker Units

Special Total Price **£58**

Or Deposit £7.15 and 9 monthly payments £6.35 (Total £64.30). Carr. £1.25  
Trans. Plastic Cover £3.15 extra.

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
- ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
- ★ Goldring Magnetic P.U. Cartridge.
- ★ Pair of Stanway II Speaker Units.

Special Total Price **£97.75**  
Carr. £1.50

Terms: Deposit £15 and 9 monthly payments £10.53 (Total £114.55).

Matching as recommended for optimum performance. Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.

PACKAGE AS ABOVE but with Garrard 3000 Autochanger and Sonotone 9TA Ceramic Cartridge in lieu of SP25 and CS90 Carr. £1.25

**£51.75**

Or Deposit £6 and 9 monthly payments £5.70 (Total £57.30)  
Trans. Plastic cover £3.15 extra.

### 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

Moderate size only 25 x 14 x 10in. COMPLETE KIT Carr. 65p **£23**

- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more.

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quality acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4.60 and 9 monthly payments £2.47 (Total £26.83).

### HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.

DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High Flux 13 x 8in. **£9.45** Carr. 40p.

STANWAY II Size 20 x 10 1/2 x 9 1/2 in. approx. Rating 10 watts, Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. See 'package offers' for **£17.85** Illustration

### RSC G66 MkII 6.5 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs.

COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£11.50** Carr. 40p

Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated **£15.99** or dep. **£3.20** and 9 monthly payments **£1.70** (Total **£18.50**).

### R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic beam P.U. cartridge. Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs.

COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS. **£15.50** Carr. 40p. Factory built with **£19.50** Dep. **£3** and 9 mthly pymts **£2.15** (Total **£22.35**). Or in Teak veneer housing Dep. **£3** & 9 mthly payments **£2.55** (Total **£25.95**). Send S.A.E. for leaflet. **£23**

### AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction.

OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£6.75** Carr. 35p

### HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. All sizes approx. Carr. 30p. per enclosure.

JES Size 16 x 11 x 9in. Pressurised. **£5.35** Carr. 30p. For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. **£6.47**

SE10 For outstanding results with 10in. Hi-Fi spkr. **£6.74** Carr. 40p. Size 24 x 15 x 10in. P.t'd.

SE12 For excelnt prfmece with 12in Hi-Fi speaker and Tweeter. **£7.87** Carr. 40p. Size 28 x 16 x 10 1/2 in.

### AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE. Exceptional performance at low cost.

HF808T	8"	10W	£2.88	HF120D	12"	15W	£4.75
HF102D	10"	10W	£3.40	HF126	12"	15W	£5.50
HF120	12"	15W	£4.25	HF126D	12"	15W	£5.90

### R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v and 90v to battery radio where A.C. mains 200/250v. 50c/s is available.

COMPACT KIT WITH DIAGRAM **£3.25** FOR USE

ASSEMBLED READY **£3.75**

### FANE 807 HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. STATE **£3.50** WHEN ORDERING


### R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. - 2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 9 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.50** Carr. 40p.

OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£9.75**
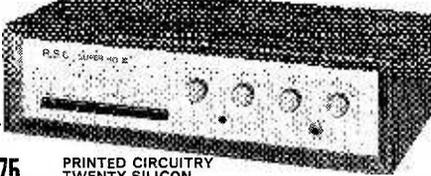
# R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.



Only high grade components by leading manufacturers

COMPLETE KIT OF PARTS Or FACTORY BUILT with 12 months guarantee. Dep. **£5.75** and 9 monthly payments **£3.50** (Total **£27.25**).

Or FACTORY BUILT in cabinet as illustrated. Dep. **£8** and 9 monthly payments **£3.88** (Total **£40.74**)

TECHNICAL DETAILS (Applying to each channel where appropriate)

CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble and Balance. Plus Ceramic Mag P.U. Switch.

PRINTED CIRCUITRY TWENTY SILICON TRANSISTORS. FOUR DIODES. FOUR RECTIFIERS

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms.

HUM & NOISE - 75dB Min. Vol. - 65dB Full Vol. HARMONIC DISTORTION

FREQUENCY RESPONSE: -3dB 7Hz to 70kHz 0-1% at 1000 Hz 10 Watts

TREBLE CONTROL: +16dB to -12dB at 14kHz

BASS CONTROL: +17dB to -16dB at 40Hz

CROSS TALK - 58dB

SENSITIVITIES: Mag. 2-5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.

REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETTED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ALL MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE. WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

**50 WATT SPEAKER** **RSC DISCOTHEQUE EQUIPMENT** **FAL**

**SAVINGS ON PACKAGE OFFER**

(1) FAL FGI/2 Console  
 (2) 100W Power Amplifier  
 (3) Pair High Quality Headphones  
 (4) Matching Microphone fitted to Headphones  
 (5) Pair 50W Speakers black rexine covered Size approx. 18" x 18" x 8"

**TOTAL COST OF ALL ILLUSTRATED UNITS Carr. £22.50** **£136**

Terms: Deposit £30 and 9 monthly payments of £13.25 (Total £149.25)

**50 WATT SPEAKER**  
**100 WATT AMPLIFIER**  
**TWIN TURNTABLE WITH PRE-AMP**

**HEADPHONES MICROPHONES**

**SEND S.A.E. FOR LEAFLET**

**F.G. 1/2 DISCO CONSOLE**  
 Incorporating twin Garrard SP25 Mk.III turntables and Goldring C850 Ceramic Cartridges with diamond stylus. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate Input for 'mike' with vol. control switch. Black Rexine covered Cabinet with lid. Carr. £1.25 **£69**

Terms: Deposit £15 and 9 monthly payments of £8.75 (Total £75)

**R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS**

All types 15 Ohms covered in Rexine and Vynair

**TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN**

**TYPE C48S 25-30 WATTS**  
 Fitted four 8" high flux 8 watt speakers  
 Overall size approx. 48x10x6in  
 Terms: Dep. £3 and 9 monthly payments £2 (Total £31) Carr. 50p.

**TYPE C412S 50 WATTS**  
 Fitted four 12" 11,000 gauss 15 watt speakers. Overall size approx. 56x14x8in  
 Terms: Dep. £4 and 9 monthly payments £3 (Total £31) Carr. 75p. **£27.50**

**TYPE C4100 100 WATTS** inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 58x16x10" Acoustically filled and pressurised. Terms: Dep. £7.50 and 9 mthly. pmts. £5.45 (Total £68.55). Carr. £1

**FAL ULTRA HIGH POWER LOUDSPEAKERS**

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE  
 High flux ceramic magnets. All carr. free

**'POP' 100**  
 18" 100Watt  
 14,000 gauss  
 8/15Ω  
**£22.50**  
 Dep. £6 and 9 mthly payments £2.15 (Total £25.35)

**'POP' 60**  
 15" 60 Watt  
 14,000 gauss  
 8/15Ω  
**£12.90**  
 Dep. £3.30 and 9 mthly payments £1.80 (Total £12.15)

**'POP' 50**  
 12" 50 Watt  
 13,000 gauss  
 15Ω  
**£10.50**  
 Dep. £2 and 9 mthly payments £1.15 (Total £12.85)

FOR BASS GUITAR, ELECT. ORGAN, ETC.

**R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER** Highly sensitive. Push-Pull high output, Hum level—70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF88, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, Strings Bass, etc. Gram. Radio

or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes. 200-250v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete Kit of parts with wiring diagram and instructions. Twin-handled perforated cover **£19.90**. Or factory built with EL34 output valves and 12 months' guarantee for £19.75 Carr. 65p

**TERMS: Deposit £4 and 9 monthly payments of £2.10 (Total £22.90). Send S.A.E. for leaflet.**

**FAL LOUDSPEAKERS 'POP' 25/2 12" 25 WATT**

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). **£6.75** Carr. or Dep. £1 and 9 mthly payments 75p (Total £7.75).

**R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS**

FULLY GUARANTEED. Impregnated and interleaved where necessary.

Primaries 200-250v. 50c/s. Screened

**MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.**

250v. 60mA. 5-3v. 2a. 99p  
 250-0-250v. 60mA. 6-3v. 2a. £1.05

**FULLY SHROUDED UPRIGHT MOUNTING**

250-0-250v. 60mA. 6-3v. 2a., 0-5-6-3v. 2a. £1.40  
 250-0-250v. 100mA. 6-3v. 4a., 0-5-6-3v. 2a. £2.20  
 300-0-300v. 100mA. 6-3v. 4a., 0-5-6-3v. 3a. £2.20  
 For Mullard 610 Amplifier £2.45

350-0-350v. 100mA. 6-3v. 4a., 0-5-6-3v. 2a. £2.20  
 350-0-350v. 150mA. 6-3v. 4a., 0-5-6-3v. 3a. £2.65  
 425-0-425v. 200mA. 6-3v. 4a., c.t., 5v. 3a. £2.95  
 425-0-425v. 200mA. 6-3v. 4a., 6-3v. 3a., 5v. 3a. £5.10  
 450-0-450v. 200mA. 6-3v. 4a., c.t., 5v. 3a. £5.50

**TOP SHROUDED DROP-TYPE TYPE**

250-0-250v. 70mA. 6-3v. 2a., 0-5-6-3v. 2a. £1.95  
 250-0-250v. 100mA. 6-3v. 3-5a. £1.65  
 250-0-250v. 100mA. 6-3v. 2a., 6-3v. 1a. £1.60  
 350-0-350v. 80mA. 6-3v. 2a., 0-5-6-3v. 2a. £1.65  
 250-0-250v. 100mA. 6-3v. 4a., 0-5-6-3v. 3a. £2.20  
 300-0-300v. 100mA. 6-3v. 4a., 0-5-6-3v. 3a. £2.20  
 300-0-300v. 130mA. 6-3v. 4a., c.t., 6-3v. 1a. £2.40  
 Suitable for Mullard 510 Amplifier. £2.60  
 350-0-350v. 100mA. 6-3v. 4a., 0-5-6-3v. 3a. £2.20  
 350-0-350v. 150mA. 6-3v. 4a., 0-5-6-3v. 3a. £2.60

**PILAMENT OR TRANSISTOR POWER PACK**  
 Types 8-3v. 1-5a. 49p; 6-3v. 2a. 54p; 6-3v. 3a. 76p;  
 6-3v. 6a. £1.00; 12v. 1a. 55p; 12v. 3a. or 24v. 1.5a. £1.35; 0-9-18v 1 1/2a. £1.10; 0-12-25-42v 2A117L.  
**CHARGE TRANSFORMERS 0-9-15v. 1 1/2a. 99p;**  
 2 1/2a. £1.10; 3a. £1.25; 5a. £1.45; 6a. £1.65; 8a. £2.00  
**AUTO (STEP UP/STEP DOWN) TRANSFORMERS**  
 0-110/220v. 200-230-250v. 50-80 watts £1.10,  
 150 watts, £1.90 250 watts £2.75; 500 watts £5.75

**OUTPUT TRANSFORMERS**  
 Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 50p  
 Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 88p  
 Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15 Ω £1.37  
 Push-Pull EL84 to 3 or 15 Ω 10-12 watts £1.85  
 Push-Pull Ultra Linear for Mullard 510, etc. £2.20  
 Push-Pull 15-18 watts, sectionally wound 6L6, K T66, etc. for 3 or 15 Ω £1.99  
 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, K T66 etc. to 3 or 15 Ω £3.80

**SMOOTHING CHOKES 150mA, 7-10H, 250 Ω**  
 70p; 100mA, 10H, 200 Ω 90p; 80mA, 10H, 350 Ω 50p; 60mA, 10H, 400 Ω 25p.

**SELENIUM RECTIFIERS F. W. (Bridged)**  
 All 6/12v. D.C. output. Max. A.C. Input 18v.  
 1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 6a. 80p.

**GROUP/DISCO EQUIPMENT PACKAGE OFFERS**

**F.A.L. PHASE 50 Mk.III AMPLIFIER** £34.75  
**PR. FAL POP 25/2 25W L/SPEAKERS** £18.50  
 Terms: Deposit £5.50 and 9 monthly payments of £4.75 (Total £48.95) **£45** carr. £1.25

**F.A.L. PHASE 50 Mk.III AMPLIFIER** £34.75  
**PR. FAL POP 50 L/SPEAKERS** £21  
 Terms: Deposit £12 and 9 monthly payments of £5 (Total £57.00) **£51** carr. £1

**F.A.L. PHASE 100 AMPLIFIER** £55.75  
**PR. L125 50W L/S in cabinets** £59.80  
 Terms: Deposit £22 and 9 monthly payments of £11.82 (Total £129.58) **£118** carr. £2.50

**F.A.L. PHASE 100 AMPLIFIER** £61.95  
**4 FAL POP 50 L/SPEAKERS** £42  
 Terms: Deposit £12.52 (Total £109.50) **£99** carr. £2

**HIGH QUALITY LOUSPEAKER UNITS**

**TWO TONE REXINE AND VYNAIR FINISH**

**L125 50 WATT**  
 Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Or deposit £4 and 9 monthly payments of £3.85. Total £34.15

**L12 12" 25 WATT**  
 10,000 lines 15 ohms. Also supplied with Rexine covered Carr 45p

**L18 12" x 8" 10 Watt**  
 10,000 lines 3 or 15 ohms. State impedance required. **£5.25** carr. 40p

**FAL PHASE 50 Mk.III AMPLIFIER 50W**

Solid state 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3-30 ohms. Size 17" x 7" x 7 1/2"

200-250v. A.C. mains. Output 50 watts music rating. Or deposit £7.25 and 9 monthly payments £3.50. Total £38.75. **£34.75** Carr. 75p.

**LOW DEPOSIT CREDIT TERMS INTEREST CHARGES REFUNDED**

Available on purchases over £8 (Kits of parts excepted) on credit sales settled in 3 months.

**R.S.C. Branches listed below open all day Sats.**

**BRADFORD** 10 North Parade (Half-day Wed.). Tel. 25349

**BLACKPOOL** (Asent) O & C Electronics 227 Church Street

**BIRMINGHAM** 30/31 Great Western Arcade, Tel. 021-236 1279 (Half-day Wed.)

**DERBY** 26 Osaston Rd. The Spot (Half-day Wed.). Tel. 41361

**DARLINGTON** 18 Priestgate (Half-day Wed.). Tel. 68043

**EDINBURGH** 133 Leith St. (Half-day Wed.). Tel. 556 5766

**GLASGOW** 326 Argyle St. (Half-day Tues.). Tel. 248 4158

**HULL** 91 Paragon Street (Half-day Thurs.). Tel. 20505

**LEICESTER** 32 High Street (Half-day Thurs.). Tel. 56420

**LEEDS** 5-7 County (Mecca) Arcade, Brigate (Half-day Wed.). Tel. 28252

**LIVERPOOL** 73 Dale Street (Half-day Wed.). Tel. 236 3573

**LONDON** 238 Edgware Road, W.2 (Half-day Thurs.). Tel. 723 1629

**MANCHESTER** 60A Oldham Street (Half-day Wed.). Tel. 236 2778

**MIDDLESBROUGH** 106 Newport Rd. (Half-day Wed.). Tel. 47096

**NEWCASTLE UPON TYNE** 41 Blakett Street (opp Fenwicks Store) (Half-day Wed.). Tel. 21469

**NOTTINGHAM** 19/19A Market Street (Half-day Thurs.). Tel: 48068

**SHEFFIELD** 13 Exchange Street (Castle Market Bldg.) (Half-day Thurs.). Tel. 20716

**Another New Branch!**

**NOW OPEN AT—**  
**19/19A MARKET STREET**  
**NOTTINGHAM**  
 (Half Day Thursday) Tel: 48068

**RSC HI-FI CENTRES LTD.**

**MAIL ORDERS & EXPORT ENQUIRIES TO:—**  
 AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: Pudsey (09785) 7781.

**TERMS C.W.O. or C.O.D. No C.O.D. under £1.**  
 Postage 25p extra under £2. 30p extra over £2 or as quoted.  
 Trade supplied. S.A.E. please with enquiries.  
 Suppliers to Govt. Depts, Education Authorities, Schools, Hospitals, H.M. Forces etc.

**MAIL ORDERS MUST NOT BE SENT TO SHOPS**

**R.S.C. BASS REGENT 50 WATT AMPLIFIER**

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating Loudspeaker unit optional horizontal or vertical mounting.

★ Two extra heavy duty 12in. Loudspeakers.  
 ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes".  
 Bass and Treble controls. Send S.A.E. for leaflet.

Credit Terms: Deposit £18 and 9 monthly payments of £5.75 (Total £67.75) **£60** Carr. £1.50

**30 WATT HI-FI AMPLIFIER**

**For Guitar, Vocal or Instrumental Group.**

A 4 input, 2 vol. control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. facia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £3.70 and 9 monthly payments of £2.10 (Total £22.60). **£19.95** Carr. 85p

# AT HOME SOLDERING ?

Our miniature irons are used all over the world in that most exacting market—the modern electronics industry, the rapidly developing technology of which has made possible the enormous growth of activities available to the technical hobbyist.

He now also requires equipment to the highest commercial standards. Like our soldering irons, for example.

Look at the ADAMIN Model 15. If there is a smaller iron for mains use, we haven't seen it. It weighs a mere  $\frac{1}{2}$  oz (less flex) and is about 7 inches long.

But it has a big performance. Used with interchangeable bits from  $\frac{3}{8}$ " to  $\frac{3}{16}$ " it is suitable for all work, from Hearing Aids to Colour Television.

Use the mains version at home or clip the 12 volt model to the car battery or 12 volt power unit (consumption only 1.25A).

Send for HOBBY PACK 10 consisting of Model 15 iron with four bits,  $\frac{3}{8}$ ",  $\frac{3}{16}$ ",  $\frac{3}{32}$ ",  $\frac{1}{8}$ ",  $\frac{1}{16}$ " and tube of Bit Lubricant. State voltage required—12v or 220/240v.

**PRICE: HOBBY PACK £2.30**  
p & p FREE

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL  
Telephone 01-688 8589 and 4559



# JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

1N4148	Signal Diode	18 for 50p
(= 1N914)		
1N5060	1 Amp Rectifier 400V	
(= A14D)	avalanche protected	7 for 50p
2N2923	NPN Silicon Transistor	
	hfe 90-180 (25v)	7 for 50p
2N2926	NPN Silicon Transistor	
(Red)	hfe 55-110	8 for 50p
2N3391A	Si NPN Hi Gain (250-500)	
	low noise transistor	3 for 50p
2N3402	Medium power (driver)	
	900mw 25v Hfe 75-225	6 for 50p
C6U	1.6 amp general purpose	
	25v SCR in T05 case	3 for 50p

Post and packing 10p for 1 or 2 packs; 3 packs or more post free.

Order any quantity, till sold (but we regret packs cannot be subdivided).



P.O. or Cheque payable,  
Jermyn Industries,  
Vestry Estate,  
Sevenoaks, Kent.

Star Bargain  
Sprague (Pirgo) Triacs  
PT406S (6 amp 400v)  
48p each

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.

**INTER-LOCKING PLASTIC STORAGE DRAWERS**

NEAT! HANDY! TIDY!

**DISCOUNT PRICES**

**SINGLE UNITS** (5" x 2 1/2" x 2 1/2") £1.35 Dozen  
**DOUBLE UNITS** £2.25 Dozen  
**TREBLE (3D)** £2.35 for 8  
**DOUBLE TREBLE** 2 draws in one outer case (6D2) £3.65 for 8 extra large size (6D1) £3.30 for 8.

**PLUS QUANTITY DISCOUNTS!** Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £. Pack./Post./Carr. Add 35p to all orders under £5. Orders over £5 P/P/C free.

**IVORYET LIMITED** (Dept. P.W.3 124 CRICKLEWOOD BROADWAY, LONDON N.W.2)

**5 SIZES ALL INTERLOCK**

**AMAZING MINI-DRILL**

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.50, p.p. 13p. De Luxe Professional Kit with 17 tools £7.00 p.p. 23p. Money ref. g'tee.

**FOR PRECISION MODEL WORK**

**+ 6 TOOLS**

**£2** P.&P. 10p

PW3/72


**MERLIN SUPPLY CO.**

Dept. PW372 Nailsea, Bristol BS19 2LP

# FANTASTIC! WHARFEDALE
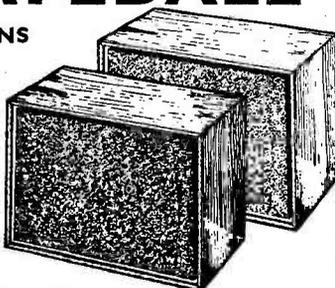
## SPEAKER BARGAINS DENTON 2 SAVE £8.40

Sold in matched pairs for a perfectly balanced stereo system. Each Denton contains an 8in.-bass unit with 3in. pressure unit, coupled by a Wharfedale crossover network. Rated input: 18 watts maximum. Frequency response: 65-17,000 Hz. Impedance: 4/8 ohms. Cabinet 9½in. x 14in. x 8½in.



All speakers available in Teak or Walnut

List Price **LASKY'S** **£31.50** C & P  
£39.90 PRICE Per Pair £2.00

	List Price	Lasky's Price	C & P		List Price	Lasky's Price	C & P
LINTON 2 p.p.	£49.90	£39.95	£2	ROSEDALE ea.	£65.00	£50.00	£1
TRITON 3 p.p.	£65.00	£53.50	£2	UNIT 3 each	£12.50	£9.70	50p
MELTON 2 p.p.	£35.00	£25.50	£1	UNIT 4 each	£18.00	£12.50	50p
DOVEDALE 3 ea.	£45.00	£33.00	£1	UNIT 5 each	£26.00	£18.50	50p

## BSR McDONALD MP60

High precision low-mass counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.

LASKY'S PRICE £10.95 C & P 50p

### BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

MODEL	A	B	C	D	E
MP.60	10.95	15.50	18.50	18.75	22.00
HT.70	15.90	19.90	23.50	23.75	27.00
610	14.50	18.75	23.00	22.25	25.50
510	12.10	16.50	18.85	20.00	22.85
310	9.75	14.00	16.50	17.25	20.25
210					9.95
MP.60 TPD2 Styrene base				17.50	21.00



## GARRARD UNITS AND PACKAGES

### GARRARD SL 55B

Four speed autochanger

LASKY'S PRICE £10.25 C & P 50p

Now available ZERO 100S

£43.50, C & P £1.50

Garrard SP25 Mk. III. ... £11.50

Garrard SL40B	£9.95
Garrard AP76 without cart.	£20.95
Garrard 3000 with 9TA cart.	£10.50
Garrard 2025TC with KS40A cart.	£8.50



## GARRARD PACKAGES

Garrard AP76 with Micro M2100/e cart. and Lasky's plinth and cover	£31.50
Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover	£33.75
Garrard SP25 Mk. III, AD76K cart. and Lasky's plinth and cover...	£18.50
Garrard SP25 Mk. III with Shure M3 cart. and Lasky's plinth and cover	£27.95

## LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Singles	5	10	20
C-60	32p	£1.52	£2.96	£5.60
C-90	50p	£2.37	£4.62	£8.75
C-120	69p	£3.28	£6.38	£10.85

Carriage and packing: each-7p, 5-25p, 10-40p, 20-68p.

# Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

## INTERNATIONAL

MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. RT.20 Message Tape 225ft.	19p	5½in. RT.25 Triple play, 2,400ft.	£1.31
3½in. RT.21 Triple play, 600ft.	50p	7in. RT.22 Standard play, 1,200ft.	63p
5in. RT.23 Double play, 1,200ft.	75p	Acetate	
5in. RT.18 Long play, 900ft.	43p	Mylar	63p
Acetate	50p	7in. RT.10 Standard play, 1,200ft.	63p
5in. RT.17 Standard play 600ft.	43p	Mylar	63p
5½in. RT.15 Double play, 1,800ft.	£1.13	7in. RT.12 Long play, 1,800ft.	95p
Mylar		Mylar	95p
5½in. RT.16 Long play 1,200ft.	75p	7in. RT.13 Double play, 2,400ft.	£1.25
Acetate	75p	Mylar	£1.25
5½in. RT.24 Standard play 900ft.	60p	7in. RT.11 Long play, 1,800ft.	75p
P.V.C.	60p	Acetate	75p
5½in. RT.14 Long play 1,200ft.	75p	7in. RT.19 Triple play, 3,600ft.	£2.50
Mylar	75p	Mylar	£2.50
		3½in. RT.22 Quad play, 1,100ft.	£1.02


P. & P. 5p extra per reel, 4 reels & over Post Free. Special quotes for quantities

## OUT NOW! 1972 AUDIO TRONICS

The great new 1972 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1,000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Man. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories and don't miss LASKY'S AUDIO TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

ALSO the fantastic £1,000 plus SONY COLOUR TV Audio Tronics '72 Competition

## DIGITAL CLOCK SCOOP

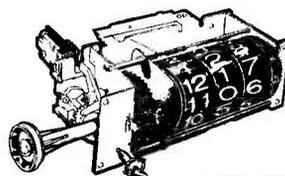

EXCLUSIVELY FROM LASKY'S

For you to mount into any housing. The clock measures 4½ W x 1½ H x 3½ D (overall from front of drum to back of switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V, 3A. Complete with instructions, HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

LASKY'S PRICE £6.50

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
  - MAINS OPERATION
  - 12-HOUR ALARM
  - AUTO "SLEEP" SWITCH
  - HOURS, MINUTES AND SECONDS READ-OFF
  - FORWARD AND BACKWARD TIME ADJUSTMENT
  - SILENT OPERATION
  - SYNCHRONOUS MOTOR
  - SHOCK AND VIBRATION PROOF
  - BUILT IN ALARM BUZZER
- SPECIAL QUOTES FOR QUANTITIES

C & P

52p

## BARGAIN SCOOP!

### PYE S.W. CAR RADIO CONVERTER MODEL 2649

High quality transistorised and ultra compact Shortwave Converter for use with any suitable MW (AM) Car Radio. Self powered for use on 12V positive or negative earth systems. The model 2649 is simply connected to the radio via the aerial socket and provides shortwave covering in 9 push button selected band spread ranges (13, 16, 19, 25, 31, 41, 49, 60 & 90 M) combined with the normal radio tuning to give full cover from 3.2MHz-21.75MHz. On/off switch and by-pass switch for normal M.V. radio use. Complete with mounting bracket fitting and alignment instructions. Black hammer crackle finished case—size: 6(W) x 1½(H) x 3½(D) in. C & P 20p.

Made to sell LASKY'S PRICE £8.75

approx. £20



# COMET

## HI-FI DISCOUNT WAREHOUSES

DRIVE-IN CAR PARK



	Rec. Price	Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>			
ALBA UA 700	34-50	24-95	
ALPHA 212 By Highgate	36-75	27-95	
AMSTRAD Stereo 8000 Mk 2	27-95	17-95	
AMSTRAD I.C. 2000	42-95	27-95	
ARMSTRONG 521	59-00	44-95	
DULCI 207	26-00	16-95	
DULCI 207M	32-00	19-95	
FERROGRAPH F307 Mk. II (cased)	64-00	43-95	
FERROGRAPH F307 Mk. II (Metal case)	60-00	43-95	
GOODMANS Maxamp	54-00	37-95	
LEAK Delta 30 (cased)	65-00	51-95	
LEAK Delta 70 (cased)	79-50	63-95	
METROSOUND ST20E	39-50	27-95	
METROSOUND ST60	70-00	49-95	
PHILIPS RH 581	79-00	54-95	
PHILIPS RH 580	52-00	36-95	
PHILIPS RH 580	29-00	19-95	
PIONEER SA500A	53-62	38-95	
PIONEER SA600	83-75	59-95	
PIONEER SA700	97-97	66-95	
PIONEER SA800	109-21	75-95	
PIONEER SA900	59-50	42-95	
PIONEER SA1000	137-56	95-95	
PIONEER Reverbation 202W	46-35	33-95	
RANK Rotel 310	47-50	35-95	
RANK Rotel 610	74-50	53-95	
RANK ROTEL 210	34-90	24-95	
ROGERS Ravensbourne	59-50	42-95	
ROGERS Ravensbourne (cased)	44-00	47-95	
ROGERS Ravensbrook Mk. II	47-50	36-95	
ROGERS Ravensbrook (cased) Mk. II	52-50	39-95	
SINCLAIR 2000	35-00	23-75	
SINCLAIR Project 60/2 x Z30/PZ5	23-90	15-95	
SINCLAIR PROJECT 60/2 x Z50/PZ8trans	34-86	23-25	
SINCLAIR PROJECT 60S	29-95	21-95	
SINCLAIR AFU	5-95	4-45	
SINCLAIR Neoteric	61-95	43-95	
SINCLAIR 3000	45-00	31-50	
TELETON SAQ 206	32-50	18-25	
TELETON 307	30-00	19-95	
VOLTEX 100W Stereo Disothetue	185-00	139-00	
8 electronically mixed inputs			
WHARFEDALE Linton Amplifier	60-00	47-95	
All take both ceramic and magnetic cartridges.			
<b>TUNERS</b>			
*ARMSTRONG 523 AM/FM	54-22	42-95	
*ARMSTRONG 524 FM	42-17	33-95	
ARMSTRONG M8 Decoder	9-50	7-70	
*DULCI FMT.7 FM	25-10	17-95	
DULCI FMT.7S Stereo	33-79	27-25	
GOODMANS Stereomax	80-07	47-95	
LEAK Delta FM	75-00	55-95	
LEAK Delta AM/FM	89-50	69-50	
PHILIPS RH 690	45-30	36-50	
PHILIPS RH 691	85-80	69-95	
PIONEER TX500 AM/FM	86-09	57-95	
PIONEER TX500 AM/FM	147-15	116-00	
RANK ROTEL 320	54-94	43-95	
ROGERS Ravensbourne chassis	59-63	46-95	
ROGERS Ravensbourne In teak case	64-45	48-95	
ROGERS Ravensbrook chassis	43-37	34-95	
ROGERS Ravensbrook (cased)	49-39	38-95	
SINCLAIR 2000	45-00	34-95	
SINCLAIR (S) 60 tuner (stereo)	25-00	19-95	
TELETON GT 101	43-93	30-95	
All above Tuners are complete with MPX Stereo Decoder except where starred.			
<b>TUNER/AMPLIFIERS</b>			
AKAI AA 8500	221-85	175-00	
AKAI 6600	137-34	108-00	
AKAI 6300	128-85	99-95	
AKAI 6200	91-56	79-95	
ARENA 2600	111-30	89-95	
ARENA T8000	303-45	285-00	
ARMSTRONG M8 Decoder	9-50	7-70	
ARMSTRONG 526	92-77	71-95	
ARMSTRONG 526	105-72	84-95	
GOODMANS Module 80, 35w. RMS	91-59	71-95	
GOODMANS Module 80 Compact	165-00	129-00	
GOODMANS Model 110 FM/MW/LW/SW 100W RMS	135-00	108-00	
LEAK Delta 75	165-00	139-95	
MIDLAND 19/542	49-58	37-50	
PHILIPS RH 790	134-00	79-95	
PIONEER SX770 AM/FM	139-23	109-95	
PIONEER SX900 AM/FM	187-83	129-95	
PIONEER 440	104-18	82-95	
ROGERS Ravensbrook Chassis	99-39	81-95	
ROGERS Ravensbrook (cased)	108-43	89-95	
ROTEL RX150	69-90	54-95	
TANDBERG 1171	110-00	91-95	
TANDBERG TR200	99-00	82-95	
TELETON F2000	51-50	28-95	
TELETON 10AT1 150w. RMS	160-00	94-00	
TELETON TFS50	79-65	52-95	
TELETON TFS50 LA MW/LW/FM	86-64	60-95	
TELETON CR55	125-26	67-95	
WHARFEDALE 100-1	139-00	89-95	
All the above Tuners and Tuner/Amplifiers take			



### COMET for after-sales service

THROUGHOUT THE U.K.  
 Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, Bridlington, Birmingham, Edinburgh, Leicester and Rochdale

both ceramic and magnetic cartridges except Teleton F2000 which takes ceramic only. All include MPX Stereo Decoder with the exception of Armstrongs where decoder is extra as listed.

	Rec. Price	Retail Price	Comet Price
<b>CARTRIDGES</b>			
AUDIO TECHNICA LT66	6-47	4-50	
GOLDRING G800	12-55	6-75	
GOLDRING G800E	18-16	10-50	
GOLDRING G800 Super E	25-10	19-95	
*GOLDRING CS90 Stereo	5-02	4-10	
*GOLDRING CS91/E	7-53	6-00	
GOLDRING G850	6-27	3-95	
EMPIRE 1000ZE/X	60-34	51-25	
EMPIRE 999TE/X	43-00	34-95	
EMPIRE 999SE/X	25-09	21-00	
EMPIRE 999E/X	20-31	16-95	
EMPIRE 999E/X	15-89	12-50	
EMPIRE 999E/X	12-55	10-25	
EMPIRE 905E/X	11-87	9-95	
EMPIRE 905E/X	8-26	7-75	
EMPIRE 905E/X	9-56	7-95	
ORBIT Magnetic NM 22	Special Price	2-95	
ORTOFON SL15E	28-62	22-95	
ORTOFON 2 X 15K Transformer	7-00	4-95	
ORTOFON M15E	29-08	23-50	
SHURE M3DM	7-16	4-75	
SHURE M31E	11-63	8-70	
SHURE M32E	10-73	8-05	
SHURE M32-3	9-84	7-80	
SHURE M44-5	10-73	7-19	
SHURE M44-7	9-84	7-15	
SHURE M-44C	9-84	7-15	
SHURE M44E	11-83	7-95	
SHURE M55E	12-52	8-95	
SHURE M75G	16-99	13-75	
SHURE M75-6	16-10	12-45	
SHURE M75EJ	18-78	14-95	
SHURE M75E	20-57	13-50	
SHURE V15-11	39-35	27-95	
Starred cartridges above are ceramic. All others are magnetic.			
<b>PICKUP ARMS</b>			
GOLDRING Lenco 75	13-98	9-50	
GOLDRING Lenco L69	17-04	6-50	
SME 3009 with S2 Shell	33-26	24-95	
SME 3012 with S2 Shell	35-42	26-45	
<b>TURNTABLES</b>			
The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.			
GARRARD SP25 Mk III with Goldring G.800	Special Price £18-95		
GARRARD SP25 Mk III with Shure M.44/7	Special Price £22-95		
GARRARD SP25 Mk III with Shure M.55E	Special Price £23-95		
GARRARD AP76 with Goldring G800	Special Price £32-95		
GARRARD AP76 with Shure M55E	Special Price £35-95		
GARRARD AP76 with Shure M75EJ	Special Price £39-95		
GARRARD 2025 with Sonotone 9TAHC	Special Price £14-50		
GARRARD SP25 Mk III	15-85	8-95	
GARRARD SL65 B	20-48	13-45	
GARRARD SL95 B	49-23	32-95	
GARRARD 401	39-26	27-45	
GARRARD SL72 B	31-83	23-95	
GARRARD Zero 100	56-25	42-95	
GARRARD Zero 100S	91-75	41-95	
GARRARD WB4 base Mk I/2 to fit Zero 100 & Zero 100S	6-40	4-95	
Base and Cover to fit GARRARD SP25, SL55, SL65B	Special Price 3-95		
GARRARD 40B	13-34	10-49	
GARRARD AP76	27-65	18-90	
GOLDRING 705/P with G850	26-00	16-95	

	Rec. Price	Retail Price	Comet Price
<b>SPEAKERS</b>			
ARENA HT 227 (pair)	42-00	26-95	
AKAI SW 155	58-48	39-95	
B & W Model 70	159-00	119-95	
B & W DM3	63-00	48-40	
B & W DM1 (per pair)	76-94	62-95	
CELESTION Dilton 120 (per pair)	57-70	45-95	
CELESTION Dilton 150	38-47	31-95	
CELESTION Dilton 25	65-00	46-95	
CELESTION Dilton 44	54-00	42-95	
GOODMANS Minister (per pair)	48-20	37-95	
GOODMANS Havant (per pair)	56-00	43-95	
GOODMANS Magister	62-50	41-95	
GOODMANS Double Maxim	33-00	25-95	
GOODMANS Mezzo 3	34-00	24-95	
GOODMANS Magnum K2	44-00	30-95	
GOODMANS Dimension 8	69-00	49-95	
GOODMANS DIN 20NT kit	12-54	9-95	
KELETRON KN400 2-speaker System (pair)	16-10	12-95	
KN600 3-speaker System (pair)	26-86	18-95	
KN800 3-speaker System	15-90	10-95	
KN1100 4-speaker System	20-40	14-20	
KN1600 3-speaker System	25-20	16-95	
KN2100 3-speaker System	30-60	20-95	
LEAK 150 (per pair)	49-90	37-95	
LEAK 250 (per pair)	65-00	49-95	
LEAK 600	49-50	35-95	
LOWTHER Ideal Baffle	37-50	32-95	
METROSOUND HFS 103 (pair)	48-00	32-95	
METROSOUND 202	21-50	15-95	
PHILIPS RH 411 (pair)	21-20	16-95	
PHILIPS RH 481 (pair)	21-20	16-95	
PHILIPS RH 482 (per pair)	34-70	28-95	
PHILIPS 496	38-00	30-95	
SINCLAIR Q16	24-00	16-95	
STE-MA 400	28-00	23-95	
TANDBERG TAN 7	38-00	31-95	
TANDBERG Tan 11 (per pair)	28-00	23-95	
VOLTEX (Teak) pair	20-50	14-95	
<b>WHARFEDALE Speakers</b>			
Denton Mark II (per pair)	39-90	31-95	
Linton Mark II (per pair)	49-90	39-95	
Melton Mark II	35-00	27-95	
Doveclad 3 (new model)	45-00	31-95	

(OVER 1,520 sq. yds.)

# OVER 1000 ITEMS ALWAYS IN STOCK

## ALL FULLY GUARANTEED— WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

	Rec. Price	Retail Price	Comet Price
Rosedale	85-04	48-50	
Trilon (pair)	72-16	37-95	
Unit 3 Speaker Kit	12-53	9-70	
Unit 4 Speaker Kit	18-00	12-50	
Unit 5 Speaker Kit	26-00	18-50	
<b>CHASSIS SPEAKERS</b>			
GOODMANS Twin-taxette 8	8-84	6-95	
GOODMANS Axiom 201	14-45	10-45	
GOODMANS Axiom 401	17-86	13-95	
GOODMANS Twin Axiom 10	9-86	7-50	
GOODMANS Audiom 8P	5-35	4-09	
GOODMANS Audiom 10P	5-83	4-50	
GOODMANS Audiom 12P	12-37	9-50	
GOODMANS Audiom 15P	20-00	16-50	
GOODMANS Audiom 18P	34-00	25-95	
GOODMANS ARU172	4-50	3-25	
GOODMANS Trebas 100	8-60	5-50	
GOODMANS Axiom 100	6-90	4-95	
GOODMANS Midax 650	12-95	8-50	
GOODMANS Attenuator	3-95	2-25	
GOODMANS Crossover Networks			
XO/950/5000	9-75	7-15	
GOODMANS Crossover Networks			
XO/950	7-40	5-50	
GOODMANS Crossover Networks			
XO/5000	2-65	1-85	
WHARFEDALE 8in. Bronze/RS/DD	4-82	3-50	
WHARFEDALE Super 8/RS/DD	8-19	6-75	
WHARFEDALE Super 10/RS/DD	11-20	9-50	
WHARFEDALE WMT1 Matching Transformer	0-84	0-70	
<b>HI-FI STEREO SYSTEMS COMPLETE</b>			
ALBA UA552	45-86	35-50	
DANSETTE Concert Stereo	33-74	29-95	
AMSTRAD Stereo 1000	48-00	36-95	
DECCA Sound 813	70-14	37-95	
DECCA Sound 814	86-55	54-95	
DECCA Sound 1204	89-44	72-95	
DECCA Compact 3	119-56	103-95	
DECCA 403	59-50	48-95	
ELIZABETHIAN L2101	59-95	42-95	
FERGUSON 3450 with radio	72-40	61-95	
FERGUSON 3451	59-50	79-95	
FIDELITY UA2 Music Master	44-50	34-95	
FIDELITY UA1 Music Master with radio	103-00	79-97	
GOODMANS Module 80 Compact System FM/35W, R.M.S. (less L/S)	165-00	129-00	
<b>SPECIAL OFFER</b>			
GOODMANS Max-amp Stereo Amplifier, Goodmans Stereo-max AM/FM Tuner with Decoder, Pair of Goodmans Magnum K2 Speakers, Garrard A.P.76 Turntable in base, complete with cover and Goldring G.800 Cartridge. Beautifully finished in Walnut	257-13	165-00	
H.M.V. 2404/5/6 with radio	198-00	153-00	
HMV 2452	65-65	54-95	
HMV 2450 with stereo radio	134-20	109-00	
MARCONI 4452	76-00	57-95	
PHILCO Ford M1500	99-93	68-50	
PHILIPS 808	96-05	79-95	
PHILIPS 580/481/105	71-00	55-95	
PHILIPS GF 823	47-80	37-95	
PHILIPS GF 824	67-10	35-95	
PHILIPS RF 833	67-10	52-95	
PHILIPS GF 834	66-40	66-95	
PYE Black Box Unit Stereo 1022	93-45	69-95	
STEEPLETONE Stereo system	41-75	33-95	
TELETON STP 8-track Stereo System	54-75	47-00	
ULTRA 6405	77-00	64-95	
<b>TAPE RECORDERS AND TAPE DECKS</b>			
AKAI 1720L 4-track Stereo	83-73	59-95	
AKAI 4000D 4-track stereo deck	89-95	64-95	
AKAI CR80D 8-track stereo tape deck	79-95	55-95	
AKAI CR80 8-track stereo recorder	99-95	69-95	

	Rec. Price	Retail Price	Comet Price
AKAI X200D	145-95	105-00	
AKAI 1800SD	153-00	109-00	
AKAI 2000SD	289-00	216-00	
AKAI GXC 400 Cassette Tape Deck	87-50	67-95	
AKAI GXC 40 Cassette recorder	105-00	79-95	
BUSH Discassette DC70	21-19	16-95	
BUSH T70 Cassette, battery/mains tape recorder	28-91	23-50	
DANSETTE DCT 105 Cassette	21-40	14-95	
FERGUSON 3245 Twin track	36-70	26-95	
FERGUSON 3248 4-track	42-55	31-95	
FERGUSON 3247 4-track	47-95	35-95	
FERGUSON 3249 4-track	53-75	41-95	
FERGUSON 3252 4-track	100-52	80-95	
FERGUSON 3255 4-track	72-40	55-95	
FERROGRAPH 7022-2-track tape deck	220-22	185-00	
FERROGRAPH 704/W 4-track tape deck	220-22	185-00	
FERROGRAPH 702 Dolby	258-52	209-00	
FERROGRAPH 702	272-25	220-00	
FERROGRAPH 724	256-52	209-00	
FERROGRAPH 722 Dolby	308-55	262-00	
GRUNDIG C200 De Luxe Cassette	38-45	28-95	
GRUNDIG TK 121 twin track	57-90	42-95	
GRUNDIG TK 141 4-track	63-90	47-95	
GRUNDIG TK 146 4-track Auto	68-90	53-95	
GRUNDIG TK 147 4-track Auto	95-75	79-95	
GRUNDIG C410 Cassette recorder	43-70	33-95	
PHILIPS 2202 cassette	26-90	21-95	
PHILIPS 2204 cassette, battery/mains	32-30	25-95	
PHILIPS 3302 cassette	23-05	17-50	
PHILIPS 4307 4-track	40-55	32-50	
PHILIPS 4308 De Luxe 4-track	47-80	36-95	
PHILIPS 4308 De Luxe 4-track	58-40	44-95	
PHILIPS 4404 4-track stereo recorder	91-70	69-95	
PHILIPS 4407 4-track stereo recorder	106-20	86-95	
PHILIPS 4500 4-track stereo tape deck	121-65	95-95	
PHILIPS 4608 4-track stereo	134-20	105-95	
PHILIPS 2503 Cassette Stereo tape deck	52-05	45-95	
PHILIPS 2400 stereo cassette less L/S	65-55	58-45	
PYE 9109 cassette	20-95	18-95	
PYE 9116 Stereo cassette	68-00	52-95	
TANDBERG 1641 4-track stereo tape deck	68-00	54-95	
TANDBERG 3021X twin track stereo	107-00	91-00	
TANDBERG 3041X 4-track stereo	107-00	85-95	
TANDBERG 4021X twin track stereo	174-00	145-00	
TANDBERG 4041X 4-track stereo	174-00	143-95	
TANDBERG 5041X 4-track stereo	188-00	158-95	
TANDBERG 6021X twin track stereo	188-00	158-00	
TELETON TC110 cassette battery/mains	26-79	18-95	
TELETON TRC130 cassette with VHF/AM Radio, bat./mains, twin	40-31	27-95	
WHARFEDALE Dolby DC9 cassette stereo tape deck	110-00	94-50	
<b>BASES AND COVERS</b>			
GARRARD WB1 Base	3-71	3-25	
GARRARD WB4 Base	5-49	4-75	
GARRARD SPC1 Cover	3-60	2-95	
GARRARD SPC4 Cover	4-27	2-75	
Special offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500			
<b>Special Price 3 95</b>			
GARRARD WB4 base Mk I/II to fit Zero 100 & Zero 100S	6-40	4-95	
GOLDRING W84 Base	8-60	7-00	
GOLDRING Plinth 69	8-60	7-00	
GOLDRING Covers for 69P and 72P	4-48	3-75	
Cover for 75p	5-02	3-95	
THORENS TX25 (for TD125AB)	8-92	6-95	
THORENS TX11 Cover	4-26	3-75	
Base and Cover for TD 125	15-04	12-45	
SME Plinth System 2000	41-36	33-50	
MOTORBOARDS only	5-22	3-25	

## COMPLETE HI-FI SYSTEMS

Completely wired mounted and ready for use

	Rec. Price	Retail Price	Comet Price
<b>GOODMANS AUDIO SUITE</b>			
Goodmans Maxamp stereo amplifier, Goodmans stereomax AM/FM Tuner with decoder, Pair of Goodmans Magnum K2 speakers, Garrard AP76 turntable in base, complete with cover and Goldring G800 Cartridge. Beautifully finished in walnut	257-13	165-95	
<b>THORENS TD 150AB Mk. II with TX11 dust cover, SHURE M55E Cartridge, LEAK Delta 70 Amplifier, 2 Wharfedale Dovedale 3 Speakers</b>			
	234-33	175-95	
<b>TELETON STP 801 Stereo 8 track tape Audio system complete with speakers</b>			
	54-75	47-00	
<b>GARRARD AP76 with base and cover with Shure M55E cartridge Arena AM/FM and SW Tuner/amp and 2 Goodmans Mezzo III speakers</b>			
	229-43	149-00	
<b>GOLDRING GL75 complete with base and cover, G800 Cartridge, Wharfedale 100-1 Tuner/Amp and 2 Wharfedale Dovedale III speakers</b>			
	294-79	198-95	
<b>GOODMANS Module 80 Tuner/Amplifier, Garrard AP78 Turntable with Goldring G800 Cartridge and 2 Goodmans Minister Speakers</b>			
	189-95	137-95	
<b>GOLDRING 705P Turntable fully wired, complete with Goldring 800 Cartridge, Amstrad stereo 8500 amplifier and 2 Metrosound 103 speakers</b>			
	81-00	49-95	
<b>METROSOUND 448 8-track stereo play-back unit complete with 2 HFS 103 Speakers</b>			
	83-56	70-95	
<b>LINTON Systems with Wharfedale Linton Amplifier, Linton Turntable with Shure M47 Cartridge and pair of Linton Mk II Speakers</b>			
	144-90	109-95	
<b>ALBA UA 700, Garrard SP25 with G800 cartridge including base, plinth and cover and pair of Arena speakers</b>			
	110-85	65-95	
<b>AMSTRAD 8000 Mk. II Amplifier, Garrard SP25 with G800 cartridge including base, plinth and cover and pair of Voltex speakers</b>			
	82-45	51-95	
<b>PHILIPS 308 Transcription Turntable, complete with plinth, base and cover and fitted with Empire 909EJ cartridge, Rank Rotel 310 Amplifier and pair of Wharfedale Triton Speakers</b>			
	169-63	112-00	

Open daily to the public from 9-0 A.M. until—

5-30 P.M. MON.  
1-0 P.M. TUES.  
8-0 P.M. WED.  
8-0 P.M. THUR.  
8-0 P.M. FRI.  
5-30 P.M. SAT.

Customers are welcome to call  
Ample car parking facilities

## Complete Price List FREE on request!

# COMET HIGH FIDELITY DISCOUNT WAREHOUSES

(Dept. P.W.) 78 Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407906 and 407877

(Dept. P.W.) 68A Armley Rd., Leeds LS12 2EF Tel. 40551 (10 lines)

(Dept. P.W.) Teesway, Portrack Lane, North Teesside Industrial Estate, Teesside, TS18 2RH Tel. 66132 and 65215

(Dept. P.W.) Heeley Road, Selby Oak, Birmingham Tel. 021-472 6181

(Dept. P.W.) 7, Newhaven Road, Edinburgh EH6 5QX Tel. 554 8501

(Dept. P.W.) Syston Street, Leicester Tel. 52236

(Dept. P.W.) Corner of Well 't' Lane and Queensway, Rochdale Tel. 50606

Free Technical Advisory Service. If in doubt, ask us!

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or if Securicor delivery required add £1.75 only. Make cheques, Money Orders payable to "COMET"



All in-stock items delivered by  
**SECURICOR**  
WITHIN 72 HOURS  
(Add £1.75 only for Securicor delivery)

ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

**THIS FANTASTIC OFFER ONLY FROM US!**

**SAVE £20.25 NOW!**

**SOLID STATE BATTERY/MAINS AC**

This equipment's got EVERYTHING!

**Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**

WITH REMOTE CONTROL MICROPHONE



RECOMMENDED RETAIL PRICE £44

**OUR PRICE £23.75** CARR. 35p

Latest sensation in the world of sound! First-class makers. Fabulous V.H.F. AM/FM Radio AND Cassette Tape Recorder and Player combined, AND runs off standard batteries or mains (plug in the 220/240v. AC line cord). Record, play back anything, anywhere! Even tape direct from Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44, WE OFFER AT ALMOST HALF PRICE!** Wonderful features: \* Press-button Keyboard Control Panel! \* New "pop-up" Cassette ejection system! \* "MAGIC EYE!" Visual Battery check/recording level indicator or built-in automatic leveller! \* Separate ON/OFF, HI-LO volume controls! \* Heavy duty built-in speaker! \* Earphone (for personal listening or "monitoring") and extension speaker sockets! \* Remote control microphone! \* Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case, size 11 1/2in. x 9in. x 3 1/2in. overall approx., with carry handle. Designs vary slightly. Takes standard 30, 50, 90 or 120-minute Philips Cassette Tapes obtainable everywhere. The amazing built-in full circuit V.H.F. AM/FM Radio gives you superb clarity of tone, incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus BBC, National, V.H.F. Picks up dozens of foreign stations. Also fabulous in car! You could pay £££'s more for a Car Radio or Car Cassette player ALONE £23.75, CARR. 35p. Simple instructions, remote control microphone with on/off switch and microphone stand. **BONUS—Standard Batteries WITH WRITTEN GUARANTEE** and Cassette Tape 25p extra, if required.

Order by post to Uxbridge Road or call at either store. **COMMERCIAL TRAVELLERS** please note: Merchandising office at our Holborn Store

**SHOPERTUNITIES LTD. SIL**

**ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!**

**BRAND NEW RUSSIAN WORLD BEATER!**

**6 WAVEBAND 10 TRANSISTOR PORTABLE RADIO**

**WORLD WIDE RECEPTION** THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

**£9.97** (EX POST ETC. 43p)

**NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!**

**\*COMPARE ITS PERFORMANCE with £34 RADIOS!**

**THE VERY LATEST MODEL SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION.** Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! \* Instant refund if you are not astounded! \* Purer and sweeter tone than ever! \* Much wider band spread than hitherto for "pin-point" station selection! \* Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. **YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE** Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover the world! \* Unique side control waveband selection unit gives incredible ease of station tuning! \* Thousands of different transmissions and stations at your fingertips 24 hours a day, even messages from all over the world! \* Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! \* Separate ON/OFF volume and Treble/Bass tone controls! \* Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2in. length. It's also a fabulous CAR RADIO—any speed requires no additional aerial. **UNIQUE!** Elegant Black, White and Chrome finish case. SIZE 10 1/2in. x 8in. x 3 1/2in. overall approx. Magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST ETC. 43p.** Standard batteries 25p extra, if required. Can also be used through extension amplifier, tape recorder or public address system. Refund guarantee.

Dept. WP/15, 164 UXBIDGE ROAD, LONDON W12 8AG (facing Shepherds Bush Green) (THURSDAY 1, FRIDAY 7). Also at 37/39 High Holborn, LONDON, W.C.1, (Wed. 1, Thurs. 7). Both stores open MON. to SAT. 9 a.m. to 6 p.m.

**VEROSTRIP**

LENGTH 8'5"



WIDTH 1'5"

Available from your Local Retailer

0.1 and 0.15 pitch Veru Strip is suitable for all applications where Tag Boards can be used.

**VERO**

VERO ELECTRONICS LTD. INDUSTRIAL ESTATE CHANDLERS FORD HANTS.

**PRACTICAL WIRELESS ELECTRONIC IGNITION SYSTEM**



This Capacitor-discharge Electronic Ignition system was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the Standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the De-luxe version containing a ready-dressed roller-trimmed printed circuit board and fully machined die-cast case with electrical connection block. Each kit is supplied with a custom wound transformer, first-grade components and full construction details. Suitable for 12V. systems only, pos. or neg. earth. All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, refundable on purchase of kit.

Price: Standard kit .. £7.25 post free  
De-luxe .. £8.75 post free  
Trade enquiries invited. Mail order only.

State pos. or neg. earth when ordering.

**DABAR ELECTRONIC PRODUCTS**

98a, LICHFIELD STREET, WALSALL, STAFFS. WS1 1UZ  
Tel. Walsall 34385

**4-STATION INTERCOM**



**£7.25**

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. £0.40.

**MAINS INTERCOM**

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £12.40 P. & P. £0.55

**INTERCOM/BABY ALARM**



**OUR PRICE ONLY £3.35**

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 14p. P. & P. £0.25.

**TELEPHONE AMPLIFIER**



**£2.99**

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p. extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (PWS)**  
169 KENSINGTON HIGH STREET, LONDON, W.8.

# ANTEX

## your soldering appliance specialists.



**E.240** 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price **£1.80**.

**ES.240** 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit and packed in a transparent display box. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price **£1.83**



**CN.240/2** Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price **£1.70**

**CN.240** Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price **£1.70**

**G.240** Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price **£1.83**.



**CCN.240** New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety; fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. Price **£1.80**


**CCN.240/7** The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price **£1.95**



### SK. 2 SOLDERING KIT


This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price **£2.40**.

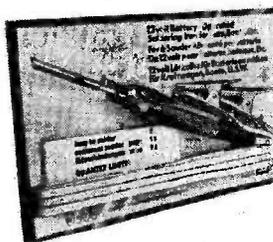
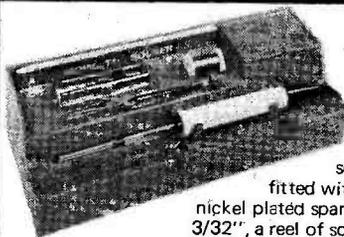
### MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price **£1.95**.




### SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price **£2.75**
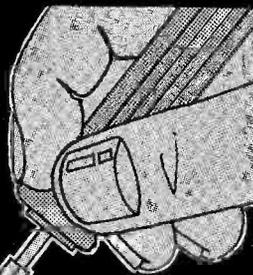
## sign here to answer all your soldering problems.



# ANTEX

from electrical, radio or car accessory shops or from **Antex Ltd., Freepost** (no stamp required) **Plymouth**

**PL1 1BR** Telephone 0752 67377/8

Please send the Antex colour catalogue.

Please send the following:

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I enclose cheque/P.O./Cash (Giro No. 2581000)

Name \_\_\_\_\_  
Address \_\_\_\_\_

P.W.3

# THE BEST OF BOTH WORLDS

THE ANTENNA SYSTEM WHICH ACHIEVED A WORLD RECORD!

**FOR THE OPERATOR:**  
EQUIPMENT TO SATISFY  
THE MOST VERSATILE &  
EXACTING REQUIREMENTS!

Size: 6" x 2½" x 4½"  
Weight: 2lb

Finish: Gold stove enamel with  
fascia off-white on maroon.



YOU HAVE EARTHING PROBLEMS?—  
DO PLEASE CONTACT US!

**FOR THE XYL:**  
A DELIGHT TO THE EYE!!

★ AND  
SPECIAL BARGAIN OFFERS!

Protected by World Patents  
and Trade Marks

7' 6" (2.28m) long. Wt. 1½lb. The new improved "JOYSTICK" V.F.A.

In matching gold stove enamel, black and red finish.

The "JOYMATCH" 111 A.T.U. for RECEIVING ONLY tunes the "JOYSTICK" V.F.A. and many other antennae from 500 kHz through 30 MHz plus.

The new "JOYSTICK" V.F.A. is extremely lightweight, exceptionally strong, rigid, tough and weather proofed when assembled by screwing three sections together in seconds.

The new "JOYSTICK" V.F.A. OUTPERFORMS many beam antennae in practice BECAUSE of its low reflected power factor and absence of harmonics.

On RECEPTION—High Selectivity & Sensitivity on both Amateur & Broadcast Bands.

★ GENUINE BARGAINS — MAIL ORDER ONLY — WHILE STOCKS LAST!

1. Superb A.T.U. in kit form with step by step assembly and operating instructions £4.50; or £5.50 assembled. Tunes Receiver (communications or solid state) 1.2 MHz to 32 MHz. On Transmit Handles 300w PEP (PA input) 160 thru 10m—with "JOYSTICK" V.F.A.
2. Lo-z "JOYMATCH" A.T.U. (the world famous one!) £9.50.
3. New "JOYSTICK" V.F.A. in white stove enamel plus FREE external mounting insulators £8.00. Add 40p p/p or 45p if two items ordered together.

Details 3p stamp (not S.A.E.)

Phone: (Thanet) 0843 62535

**PARTRIDGE**  
BROADCASTERS WENT ENGLAND  
**ELECTRONIC LTD**

## The low-down on hi-fi

Hi-fi News & Record Review is the magazine for people who care about sound. We pack each issue with information on how to get the best from your equipment. We look closely at all new equipment as it comes onto the market and then give an honest appraisal of it. We give pages of reviews on the latest records, covering the full spectrum from classical to pop. You'll find stories on recent sound happenings. Features on sounds from the past plus a constant look at the future. And the pages of ads let you shop around for bargains without leaving your armchair.

Hi-fi News & Record Review is published monthly. So call in at your newsagent and get a copy now. 20p.

**hi-fi  
news  
& record review**

A Link House  
Group Publication.

## PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL: HECKMONDWIKE 4285

**Amplifier Unit Type A413.** Complete with 5Z4 & 6V6GT valves. 250.230 Volt Transformer. Clean condition untested. £1.25. Carriage 75p.

**Air Position Indicator.** Contains Gears. Ball Races. Dimmer Unit. Lamps. Four numbered Counters. 24 Volt Motor etc. Great interest to the model makers. Good condition 75p. Carriage 50p.

**Ground Position Indicator.** Contains 24 Volt Lamp. Prisms Mirror and Gears. Could interest schools and model makers. 75p. Carriage 75p.

**Latest Air Ministry Release Radio Receiver. Type R4187.** 2.8 to 18 MHz In Three Bands. Complete with 17 miniature valves. 26 Volt Motor. Power supply motor and manually tuned. Very clean, but not tested. £5. Carriage and Insurance 75p.

**Control Unit.** Type 4190. Complete with three miniature valves. 1½ 500 µA Meter. Six Relays. Model makers Motor with Gears. 24 Press Buttons. Lots of spares. Clean condition. £1.50. Carriage and Insurance 75p.

**Autostabiliser Amplifier Unit.** Complete with Carpenter Relay and Base. Many spares. 50p. P/P 33p.

**Special Offer. Aircraft Sighting Head.** Comprising flexible drive, lens prism unit, Giro. Useful for model constructors, schools, etc. Condition fair. 75p. Carr. 75p.

**Reclaimed T.V. Tubes. All with 12 months guarantee.** AW43/88. £2. AW43/80. £1.50. MW43/69 £1. Special offer Brand New Brimar Tubes C17P.M. £1. Many older types in stock. Carriage and insurance on any tube £1.10.

**Breaking-up. Ferguson Model 506T.** Tested L.O.P.T. £1.45. Post paid. Fireball Tuner Unit with Valves less Knobs. 75p. Post paid. S.A.E. for Price List of other spares for this set and other types.

**Valve List Ex Equipment All Valves Tested on a Mullard Valve Tester before despatched. 3 Months Guarantee on all Valves Single Valves P/P 3p. Over three Valves P/P Paid.**

ARP12	5p	PCC84	5p	U191	20p
EB91	4p	PCF80	5p	U251	12½p
EF65	12½p	PCL82	12½p	6BW7	10p
EF80	12½p	PCL83	12½p	6U4	10p
EF89	12½p	PCF92	12½p	6F23	20p
ECC81	10p	PL36	20p	20P1	20p
ECC82	12½p	PL81	17½p	20P3	10p
ECL80	7½p	PY81	7½p	20D1	10p
EF80	7½p	PY33	17½p	30P4	20p
EF91	4p	PY82	7½p	30P12	20p
EY85	20p	PL82	7½p	30FL1	20p
EF50	60p per dozen	PL83	7½p	6/30L2	20p
		PCL84	12½p	30F5	10p





# "Where can I get exclusive ROC ELECTRONICS!"

## ACADEMY STEREO CASSETTE TAPE DECK, MODEL CS-20000

No hi-fi system is complete without one - hook it up to any ROC or other good quality amplifier, and the results are fantastic! The CS-20000 records and plays back. A big feature is its easy-to-use piano-key controls. Easy-to-get-at mic inputs are on top; line inputs and outputs at the rear. Dual-channel recording level meter. Pop-up cassette ejection. Stereo/Mono button. Tape counter. Pause control. Tape speed 1 7/8 ips (4-7.5 cms). Frequency response 100-10,000 Hz. Wow and flutter better than 0-3%. Rewind time better than 60 sec with C60 cassette. Engineered throughout to the highest electrical and mechanical standards. Size 16" wide, 4 1/2" high and 8" deep. Walnut cabinet with satin aluminium trims.

ROC PRICE  
**£54.95**

Including two pencil microphones and all connecting leads  
Normal Price £65.00

## REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls - magnetic phono (high/low) tuner, aux, mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz  $\pm$  1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono - 50db; tuner/aux - 65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.

ROC PRICE  
**£43.75**

Normal Price £55.50



## OLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as it's good looking design! But of course it's also the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands: FM: 87-108 MHz; AM: 525-1605 kHz. FM Sensitivities: FM, 3 $\mu$ V; AM, 250 $\mu$ V. Stereo separation 30dB at 1kHz. Image rejection 60dB. Size: 11 1/2" wide, 4" high, 7 1/2" deep.

ROC PRICE  
**£39.95**

Normal Price £50.00



## REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide  $\times$  3" high  $\times$  5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/tuner and power on/off slide switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 10 to 10,000 Hz  $\pm$  3db. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.

ROC PRICE  
**£14.50**

Normal Price £21.00

## REALISTIC TM-100 AM/FM/MPX STEREO TUNER

Here's another unit that gives you fabulous value in miniature! Designed specifically to match the Realistic SA-100B in both appearance, size and performance, the TM-100 is superb value-for-money. It gives you the full FM and AM ranges - FM, 88-108 MHz; AM, 535-1605 kHz. Sensitivities: FM 5 $\mu$ V; AM 250 $\mu$ V. Image rejection 50dB.



## OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate systems. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for tapping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz  $\pm$  3db. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3-0mV RIAA, crystal phono 100mV; tape 160mV; tuner 160mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well - sounds even better!

ROC PRICE  
**£23.25**

Normal Price £28.80



ROC PRICE  
**£29.00**

Normal Price £39.80

Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz  $\pm$  3dB. Output 6 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.



ROC PRICE  
**£98.50**

Including connecting leads  
Normal Price £115.00

## REALISTIC HI-FI 36-WATT STEREO CONCERTMASTER FM-AM RECEIVER SYSTEM, MODEL 12-694

Brilliantly designed tuner/amplifier with two matching speakers. All three units in beautifully finished walnut cabinets with smart aluminium vertical trims. The tuning dial is franted by unique black glass. Figures light up in green when the unit is on. Separate easy-to-operate Left and Right volume controls. Headphones socket on front panel for easy access. Single tuning knob for FM and AM. Microswitch for on/off. Programme selector. Separate bass and treble control. Built-in aerials, facilities for external FM aerial. Illuminated dial. Stereo broadcast indicator light. Each speaker has 6 1/2" bass and 3" treble units. Output: 9 watts r.m.s. per channel into 8 ohms. Frequency response: 30 to 20,000 Hz. FM: frequency range 80-108 MHz, sensitivity 2.5 $\mu$ V, stereo separation 30dB, image rejection 40db. AM: frequency range 530-1605 kHz, sensitivity 100 $\mu$ V. Sizes: speakers 8" wide, 12" high and 9 1/2" deep; receiver 6" wide, 12" high and 9 1/2" deep. And their sophisticated appearance matches the excellence of the specification.

ROC PRICE  
**£76.50**

Normal Price £95.00



## REALISTIC 8-TRACK STEREO CARTRIDGE TAPE DECK, MODEL RP-1000ST

The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual override. Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in pre-amp. Tape speed 3 1/2 ips (9.5 cms). Frequency response: playback 30-10,000 Hz; recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect in a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 9" deep. Cabinet in walnut. Including connecting leads.

ROC PRICE  
**£39.95**

Normal Price £49.00

## 8-TRACK HOME STEREO CARTRIDGE PLAYER MODEL E1

With this unit, you can play any standard 8-track cartridge on the market - at a fraction of the normal retail value! It gives you a total of 5 watts of power, to feed into two 8-ohm speakers. The frequency response is 50 to 10,000 Hz, giving you a fine tonal quality that can't be bettered at anything near this price. The E1 has separate tone, balance and volume controls, giving you complete freedom to select the sound you want to hear. Tape speed is 3 1/2 ips, and wow and flutter are both less than 0-3%. Size: 11 1/2" wide, 5" high, 11" deep.

ROC PRICE  
**£16.40**

Normal Price £22.50 per pair.

## R.446 3-WAY MATCHED SPEAKERS

These will do justice to your amplifier - and to your pocket. At only £16.40 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.

## OLSON AM-357 4-WATT STEREO AMPLIFIER

Here's a marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz  $\pm$  3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.

## 25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-5b

This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units an 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2"  $\times$  7 1/2"  $\times$  8 1/2". Exactly right for matching the most modern decor.

ROC PRICE  
**£27.25**

Normal Price £39.95 each.

ROC PRICE  
**£33.20**

Normal Price £42.00

## PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16

This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to 'Stereo'! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz; AM 535-1605 kHz. Frequency response: 50-10,000 Hz  $\pm$  3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.

## ROC-WATT STEREO AMPLIFIER CHASSIS SK-317

This exclusive ROC Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 6 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz  $\pm$  3dB; output 3.5 watts music power per channel into 8 ohms; input, phono, 800mV; signal-to-noise ratio better than 45dB.

ROC PRICE  
**£5.50**

Normal Price £7.75

ROC PRICE  
**£18.25**

Normal Price £25.20

## OLSON AM-372 16-WATT STEREO AMPLIFIER

Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz  $\pm$  3dB. Output 6 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

ROC PRICE  
**£10.50**

Normal Price £14.70

# units at lowest prices?..."

Compare our prices with any other unit on the hi-fi market, and you'll find you won't beat ROC unit prices. No matter where you live, London or Land's End!

Take a good look at all these super audio equipment bargains. They're all on demonstration at our Shop from 9 to 6 p.m. Monday to Saturday, late night Thursday until 7 p.m. But don't worry if you can't get there yourself. Our Mail Order service is at your disposal. With the same exclusive ROC equipment - and at the same super value-for-money prices!

When you invest in ROC equipment you're getting much more than an exclusive product. You're getting value for money that is literally unbeatable. ROC units are bought direct from the manufacturer, and ALL the savings ROC derive from this are passed on to you!

At ROC Electronics, we take extra care to select only the best buys. We check everything before you do - and it's fully guaranteed whether you buy at the shop or by Mail Order.



exclusive unit

## TOP VALUE • TOP QUALITY ACCESSORIES THAT EVERY HI-FI ENTHUSIAST NEEDS TO COMPLETE HIS SYSTEM

Every item shown here is the best of its kind within its price range. Buy them separately or at the same time as the other top-value audio products listed.



**R.328 STEREO HEADPHONE**  
If you're starting in hi-fi, and you discover the need for a pair of really good stereo headphones. The R.328 is ideal, at a price you can afford. They have padded ear cushions, a 6-foot cord and jack plug. Frequency range 30-15,000 Hz. Impedance 8 ohms per channel.  
**ROC PRICE £2.95**



**EAGLE SE-80 STEREO HEADPHONE**  
Here's the ultimate in headphone design! Apart from its fantastic ability to reproduce all the frequencies from 20 to 20,000 Hz, the SE-80 has eliminated the discomfort and strain associated with traditional headphone design. Eagle have designed and produced a pair of headphones which breaks with all previous concepts. You hear all the sounds crisp and clear. In fact, the reproduction is so good, that it compares favourably with the most expensive hi-fi speaker systems. Separate slider volume control on each earpiece. Impedance: 8 ohm per channel.  
**ROC PRICE £14.90**




**EAGLE SE-30 STEREO HEADPHONE**  
This model is for the more discriminating listener. For a start the frequency range extends from 30 to 16,000 Hz. And you can adjust the volume of each earpiece independently. There's also a mono/stereo switch. For maximum comfort, the ear cushions are covered in soft leathers.  
**ROC PRICE £7.05**



**TEC HR-007 HEADPHONE RADIO**  
When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW.  
**Normal Price £9.45 ROC PRICE £7.65**



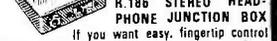**THORENS TD150AB/II Transcription Turntable**  
Complete with pick up arm, plinth and cover. **£52.31**




**R.186 STEREO HEADPHONE JUNCTION BOX**  
If you want easy, fingertip control of headphones and loudspeakers, here's the ideal solution to the problem. All you do is connect it to your speakers and amplifier, plug in your headphones - and you're ready to take over! At the flick of a slide switch, you can have headphones alone, or speakers alone, or both together. Input: suitable for use with amplifiers rated up to 20 watts. Size: 2 3/4" x 3 3/4" x 1 1/2".  
**ROC PRICE £1.50**




**R.151 STEREO CAR SPEAKERS**  
Smart black, tough, plastic cases, each containing a high flux 110mm diameter speaker unit. Just what you need to go with the CS.5 Cartridge Player or any other car stereo system. Fitted with over three yards of connecting cable. Dimensions: 6 1/2" x 5 1/2" x 3 1/2". Impedance: 8 ohms per speaker. Rating: 5 watts max per speaker. **ROC PRICE £3.72**
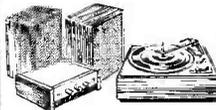
### HERE'S A RANGE OF AUDIO SYSTEMS BUILT AROUND EXCLUSIVE ROC AMPLIFIERS AND TUNERS


Now run your eye over the prices, select the System nearest to your budget - and you've hit on the best value that your money can buy! Supplied with all necessary leads and plugs, ready to use.



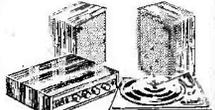**OLSON AM-357 SYSTEM**  
Olson AM-357 Stereo Amplifier, Garrard 2025 T/C Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.088 4 watt Speakers.  
**Normal Price £45.28 ROC PRICE £36.70**



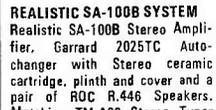**OLSON AM-372 SYSTEM**  
Olson AM-372 Stereo Amplifier, Garrard 2025 T/C Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers.  
**Normal Price £68.18 ROC PRICE £51.53**



**REALISTIC SA-100B SYSTEM**  
Realistic SA-100B Stereo Amplifier, Garrard 2025TC Autochanger with Stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers. Matching TM-100 Stereo Tuner £23.25 extra if required.  
**Normal Price £63.98 ROC PRICE £47.60**



**PALACE SYSTEM**  
Palace SSA-16 Stereo Tuner Amplifier, Garrard 2025 T/C autochanger with stereo ceramic cartridge, plinth and cover and a pair of ROC R.446 Speakers.  
**Normal Price £84.98 ROC PRICE £66.30**



**REALISTIC 12-694 SYSTEM**  
Realistic 12-694 Stereo Tuner Amplifier with matching speakers and Garrard SP25 Mk III with Eagle LC.07 Stereo Magnetic Cartridge and plinth and cover.  
**Normal Price £144.05 ROC PRICE £124.50**



**OLSON AM-395 SYSTEM**  
Olson AM-395 Stereo Amplifier, Garrard SP25 Mk III Record Player with Eagle LC07 Stereo Magnetic Cartridge, plinth and cover and a pair of Eagle DL.67 Speakers. Matching RA.310 Stereo Tuner £39.95 extra if required.  
**Normal Price £106.65 ROC PRICE £92.60**




**REALISTIC SA-500 SYSTEM**  
Realistic SA-500 Stereo Amplifier, Garrard SP25 Mk III Single Record Player with Eagle LC.07 Stereo Magnetic Cartridge, plinth and cover and a pair of Chrysler CE-5b Speakers. **Normal Price £157.95 ROC PRICE £124.00**




**ROC E1 SYSTEM**  
ROC E1 8 track Stereo Cartridge Player complete with a pair of ROC R.088 4 watt Speakers.  
**Normal Price £59.10 ROC PRICE £49.45**



**EAGLE 8-TRACK CAR STEREO PLAYER, CS.8**  
Drive to the sound of music - with this fabulous 8-Track Cartridge Player. It gives you superb tone and power to fill the car with stereo sound. Ideal for use with R.151 or R.152 speakers. Complete with all mounting accessories. For negative earth electrical systems only. Output: 2.5 watts per channel. Frequency range: 70-10,000 Hz. Wow and flutter: less than 0.3%. Tape speed: 3.5 cm/sec. Channel selector: automatic with manual override. Mounting dimensions: 5 3/4" x 5 1/2" x 2 1/4". **ROC PRICE £27.20**

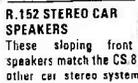

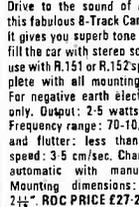**R.152 STEREO CAR SPEAKERS**  
These sloping front speakers match the CS.8 Cartridge Player or any other car stereo system. Fitted with high flux 110mm diameter speaker unit, and over three yards of connecting cable. Dimensions: 6 1/2" x 6 1/2" x 3 1/2". Impedance: 8 ohms per speaker. Rating: 5 watts max per speaker. **ROC PRICE £4.96**



**EAGLE LC.05 STEREO MAGNETIC CARTRIDGE**  
For fabulous reproduction at a very low price, you'll find it hard to beat. 0.7 mil diamond stylus. Output: 6mV per channel. Frequency range: 30-18,000 Hz. Channel balance: ±1.5dB. Channel separation: 20dB. Recommended stylus pressure: 2.4 grams. Compliance: 9 x 10<sup>-6</sup> cm/dyne. **ROC PRICE £4.75**




**EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE**  
Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-li amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: ±1dB. Channel separation: 28dB. Compliance: 12. 10-6 cm/dyne. **ROC PRICE £6.37**




**RECORD CLEANERS**  
The original "Dust Bug" Automatic Record Cleaner keeps your records clean as they play. £1.20 Watts Disc Preener. Keeps new records like new - for perfect record reproduction. 35p



**R.307 TRANSISTORIZED STEREO PRE-AMPLIFIER**  
Now your amplifier that could only reproduce ceramic or crystal pick-up cartridges, can accept signals from moving-magnet cartridges! The R.307 steps up signals from between 5-20mV to 200-800 mV. Input: 5-20mV. Equalisation: RIAA. Output: 200-800mV flat. Frequency range: 20-22,000 Hz. Dimensions: 3 1/2" x 1 1/2" x 2 1/4". Supply: 240 VAC. **ROC PRICE £4.92**

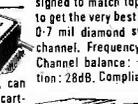

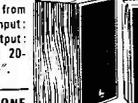**15-FOOT STEREO HEADPHONE EXTENSION CORD R.362**  
Fitted with heavy duty 3-circuit stereo plug at one end and a matching stereo socket at the other. **ROC PRICE £1.30**  
**R.361 STEREO HEADPHONE ADAPTOR**  
R.361 Enables you to use two sets of stereo headphones from a single socket. Fitted with male plug and two female sockets. **ROC PRICE £1.30**



**R.088 MATCHED STEREO LOUD-SPEAKERS**  
Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. **ROC PRICE £9.50 pair**

**EAGLE DL.67 HIGH COMPLIANCE 3-WAY TACK SPEAKER SYSTEM**  
From a rich, deep, 35 Hz bass to above the limit of human hearing - this fantastic response comes from such a small size - only 10" x 8" x 6 1/2"! The DL.67 is the end product of several years effort into the problems of full frequency response from small cabinets. The DL.67 has a dual cone high compliance bass mid range unit, and a horn tweeter. The speaker has a variable brilliance control to suit individual rooms - a feature normally only found on very expensive speaker systems. Power handling capacity: 10 watts rms, 20 watts peak. Frequency range: 35-20,000 Hz. Flux density: 11,000 gauss. Impedance: 8 ohms. Dimensions: 11 1/2" high x 8" wide x 6 1/2" deep. Finish: oiled teak. **ROC PRICE £18.80 each**

Return-of-post mail order service. Over £10 post free (UK only). Add 25p for p & to orders under £10. HP terms available for callers

## ROCELECTRONICS LTD

M. JORY, Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211

CALLERS WELCOME AT THE SHOP

9-6 MON TO SAT,

LATE NIGHT THURSDAY 7 PM



# WEYRAD

## COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil .....	P50/1AC (For OC45)	P50/1AC (For AF117)	33p
1st I.F. Transformer .....	P50/2CC (For OC45)	P51/1 (For AF117)	36p
2nd I.F. Transformer .....	P50/2CC (For OC45)	P51/2 (For AF117)	36p
3rd I.F. Transformer .....	P50/3CC (For OC45)	P50/3V (For AF117)	36p
Rod Aerial .....	RA2W		72p
Driver Transformer .....	LFDT4/1		58p
Output Transformer .....	OPT1		58p
Printed Circuit .....	PCA1		58p

## I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer .....	39p
T41/2E	2nd I.F. Transformer .....	39p
T41/3T	3rd I.F. Transformer .....	57p
T41/3T	B.F.O. Coil .....	57p

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

**WEYRAD (ELECTRONICS) LIMITED**  
SCHOOL STREET, WEYMOUTH, DORSET


**FANTASTIC BARGAIN OFFER!**  
**TRANSEUROPEAN**

Transistorised Stereophonic High Fidelity AM/FM Tuner Amplifier System.



This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM. Short, medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in. matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price. **SPECIAL OFFER £44**  
Easily fitted no technical knowledge necessary. P. & P. 88p

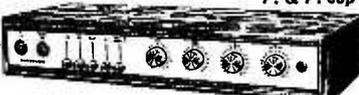Credit Terms available First monthly payment of £5.83 followed by 9 monthly payments of £4.95. Total Credit Sale Price £49.50. Send £5.83 today.



**FABULOUS VALUE**  
Hi-Fi stereo at a new low. System Ten-Ten; 4 speed BSR autochanger with cue and pause control plus solid state amplifier, 20 watt total output. Frequency response 20-20,000 Hz.

**ONLY £4.93 DOWN**

**CREDIT SALE TERMS:** Send £4.93 (being the first of TEN monthly payments of £4.05 plus 88p. Carriage and Packing). To be followed by NINE monthly payments of £4.05 (Total Credit Sale Price £40.50).

**EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.**

CALLERS WELCOME  
PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name .....

Address .....

PW272

**LEWIS Radio** 100, Chase Side London N.14  
Tel: 01-886 3733/9666

Post coupon NOW for...  
**FREE** leaflets

When in LUTON, BEDS, you must visit the . . .

**SELF-SERVICE RADIO COMPONENTS SHOP**

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.  
Closed all day Wednesday.

**SURPLECTRONICS**  
216 LEAGRAVE ROAD, LUTON, BEDS

**AERIAL BOOSTERS**  
We make four types of Aerial Boosters. L45 625 U.H.F., L12 V.H.F. TV. L11 V.H.F. Radio, L10 M/W & S/W. Price L45, L12 & L11 £2.95, L10 £2.45.

**19" TV £6.50**  
19" 405 Slimline Televisions in good working order, with complete set of spare valves. Price £6.50. Carriage £1.50.

**VALVE BARGAINS**  
Any 5-45p, 10-70p:  
ECC82, ECL80, EF80, EF85, EF183, EF184, EBF89, EB91, EY86, FCC84, FCC89, PC97, PCF80, PCF86, PCL82, PCL83, PCL84, PCL86, PL86, PY83, PY82, PY800, FY801, 30L15, 30C15, 6-30L2.

**PRINTED CIRCUIT BOARD**  
2-8 ins by 4 ins boards complete with etching compound and instructions-40p.

**500MFD CAPACITORS**  
500mf-25v/w Brand New Electrolytic with long leads. 11p each.

POST & PACKING under £1.5p Over £1.10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

**VELCO ELECTRONICS**  
62A Bridge Street, Ramsbottom, Bury, Lancs.

**BRAND NEW  
GUARANTEED**

**SEMICONDUCTORS & COMPONENTS**

SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

**RETURN OF POST  
SERVICE**

**TRANSISTORS**

2G301	20p	2N3404	32p	40310	45p	BC212L	18p	BSX28	32p	NKT281	27p
2G302	20p	2N3405	45p	40311	45p	BCY30	27p	BSX30	32p	NKT401	27p
2G303	20p	2N3414	23p	40312	47p	BCY31	30p	BSX61	62p	NKT402	75p
2G306	42p	2N3415	23p	40313	47p	BCY32	50p	BSX76	25p	NKT403	75p
2G308	20p	2N3416	37p	40320	47p	BCY33	25p	BSX77	27p	NKT404	62p
2G309	30p	2N3417	37p	40323	32p	BCY34	30p	BSX78	27p	NKT405	75p
2G371	15p	2N3570	11.25p	40324	47p	BCY38	40p	BSY10	27p	NKT406	62p
2G374	20p	2N3572	97p	40326	37p	BCY39	60p	BSY11	27p	NKT451	62p
2G381	22p	2N3605	27p	40329	30p	BCY40	50p	BSY25	15p	NKT453	47p
2N404	22p	2N3606	27p	40344	27p	BCY42	15p	BSY26	17p	NKT603F	32p
2N496	20p	2N3607	22p	40347	57p	BCY43	15p	BSY27	17p	NKT613F	32p
2N497	17p	2N3702	11p	40348	52p	BCY54	32p	BSY28	17p	NKT674F	30p
2N498	25p	2N3703	10p	40360	42p	BCY58	22p	BSY29	17p	NKT677F	30p
2N706	12p	2N3704	11p	40361	47p	BCY59	22p	BSY32	25p	NKT713	30p
2N705A	12p	2N3705	10p	40362	57p	BCY60	97p	BCY70	20p	NKT781	30p
2N708	15p	2N3706	09p	40363	11p	BCY71	25p	BCY72	25p	NKT10439	37p
2N709	62p	2N3707	11p	40406	32p	BCY73	25p	BCY74	25p	NKT10519	32p
2N718	25p	2N3708	97p	40407	40p	BCY75	17p	BCY76	25p	NKT20329	47p
2N726	30p	2N3709	09p	40408	52p	BCZ10	27p	BCY77	25p	NKT20339	37p
2N727	30p	2N3710	09p	40410	62p	BCZ11	42p	BCY78	25p	NKT80111	77p
2N914	17p	2N3711	12p	40467A	57p	BD116	11.12p	BCY79	47p	NKT80112	77p
2N916	17p	2N3715	11.25p	40468A	85p	BD121	35p	BCY80	47p	NKT80113	97p
2N918	30p	2N3716	11.25p	40469	80p	BD123	82p	BCY81	57p	NKT80114	11.12p
2N920	22p	2N3717	22.06p	AC107	80p	BD124	60p	BCY82	40p	NKT80211	92p
2N930	27p	2N3819	35p	AC126	20p	BD131	75p	BCY83	30p	NKT80212	92p
2N1090	22p	2N3823	97p	AC127	25p	BD132	85p	BCY84	40p	NKT80213	92p
2N1091	22p	2N3824	27p	AC128	20p	BDY10	11.87p	BCY85	47p	NKT80214	92p
2N1131	25p	2N3854A	27p	AC154	22p	BDY11	11.87p	BCY86	47p	NKT80215	92p
2N1132	25p	2N3855	27p	AC176	25p	BDY12	11.87p	BCY87	47p	NKT80216	92p
2N1302	17p	2N3856A	30p	AC187	62p	BDY18	11.75p	BCY88	52p	NKT80217	92p
2N1303	17p	2N3856	30p	AC188	37p	BDY19	11.97p	BCY89	42p	NKT80218	92p
2N1304	22p	2N3866A	35p	ACY17	27p	BDY20	11.12p	BCY90	42p	NKT80219	92p
2N1305	22p	2N3858	25p	ACY18	25p	BDY38	97p	BCY91	75p	NKT80220	92p
2N1306	25p	2N3868A	30p	ACY19	25p	BDY60	11.25p	BCY92	35p	NKT80221	92p
2N1307	32p	2N3869	27p	ACY20	25p	CA24	42p	BCY93	35p	NKT80222	92p
2N1308	30p	2N3869A	32p	ACY21	25p	CA25	40p	BCY94	35p	NKT80223	92p
2N1309	30p	2N3860	30p	ACY22	20p	BF115	25p	BCY95	35p	NKT80224	92p
2N1607	17p	2N3866	11.50p	ACY28	20p	BF117	47p	BCY96	35p	NKT80225	92p
2N1613	25p	2N3877	40p	ACY40	20p	BF163	37p	BCY97	35p	NKT80226	92p
2N1631	35p	2N3877A	40p	ACY41	20p	BF167	18p	BCY98	35p	NKT80227	92p
2N1632	30p	2N3900	37p	ACY44	40p	BF175	18p	BCY99	35p	NKT80228	92p
2N1638	27p	2N3901	37p	AD140	52p	BF177	40p	BCY00	35p	NKT80229	92p
2N1639	27p	2N3901	37p	AD149	57p	BF178	30p	BCY01	35p	NKT80230	92p
2N1671B	11.00p	2N3903	35p	AD150	62p	BF178	30p	BCY02	35p	NKT80231	92p
2N1711	25p	2N3904	35p	AD161	37p	BF180	35p	BCY03	35p	NKT80232	92p
2N1889	32p	2N3905	37p	AD162	37p	BF181	35p	BCY04	35p	NKT80233	92p
2N1893	37p	2N3906	37p	AF106	42p	BF184	25p	BCY05	35p	NKT80234	92p
2N1947	32p	2N4058	17p	AF114	25p	BF185	42p	BCY06	35p	NKT80235	92p
2N1948	37p	2N4059	10p	AF115	25p	BF194	17p	BCY07	35p	NKT80236	92p
2N1980	37p	2N4060	12p	AF116	25p	BF195	15p	BCY08	35p	NKT80237	92p
2N1984	37p	2N4061	12p	AF117	25p	BF196	42p	BCY09	35p	NKT80238	92p
2N1985	37p	2N4062	12p	AF118	25p	BF197	42p	BCY10	35p	NKT80239	92p
2N1986	37p	2N4063	12p	AF119	25p	BF198	42p	BCY11	35p	NKT80240	92p
2N1987	37p	2N4064	12p	AF120	25p	BF199	42p	BCY12	35p	NKT80241	92p
2N1988	37p	2N4065	12p	AF121	25p	BF200	42p	BCY13	35p	NKT80242	92p
2N1989	37p	2N4066	12p	AF122	25p	BF204	14p	BCY14	35p	NKT80243	92p
2N1990	37p	2N4067	12p	AF123	25p	BF205	15p	BCY15	35p	NKT80244	92p
2N1991	37p	2N4068	12p	AF124	25p	BF206	15p	BCY16	35p	NKT80245	92p
2N1992	37p	2N4069	12p	AF125	25p	BF207	15p	BCY17	35p	NKT80246	92p
2N1993	37p	2N4070	12p	AF126	25p	BF208	15p	BCY18	35p	NKT80247	92p
2N1994	37p	2N4071	12p	AF127	25p	BF209	15p	BCY19	35p	NKT80248	92p
2N1995	37p	2N4072	12p	AF128	25p	BF210	15p	BCY20	35p	NKT80249	92p
2N1996	37p	2N4073	12p	AF129	25p	BF211	15p	BCY21	35p	NKT80250	92p
2N1997	37p	2N4074	12p	AF130	25p	BF212	15p	BCY22	35p	NKT80251	92p
2N1998	37p	2N4075	12p	AF131	25p	BF213	15p	BCY23	35p	NKT80252	92p
2N1999	37p	2N4076	12p	AF132	25p	BF214	15p	BCY24	35p	NKT80253	92p
2N2000	37p	2N4077	12p	AF133	25p	BF215	15p	BCY25	35p	NKT80254	92p
2N2001	37p	2N4078	12p	AF134	25p	BF216	15p	BCY26	35p	NKT80255	92p
2N2002	37p	2N4079	12p	AF135	25p	BF217	15p	BCY27	35p	NKT80256	92p
2N2003	37p	2N4080	12p	AF136	25p	BF218	15p	BCY28	35p	NKT80257	92p
2N2004	37p	2N4081	12p	AF137	25p	BF219	15p	BCY29	35p	NKT80258	92p
2N2005	37p	2N4082	12p	AF138	25p	BF220	15p	BCY30	35p	NKT80259	92p
2N2006	37p	2N4083	12p	AF139	25p	BF221	15p	BCY31	35p	NKT80260	92p
2N2007	37p	2N4084	12p	AF140	25p	BF222	15p	BCY32	35p	NKT80261	92p
2N2008	37p	2N4085	12p	AF141	25p	BF223	15p	BCY33	35p	NKT80262	92p
2N2009	37p	2N4086	12p	AF142	25p	BF224	15p	BCY34	35p	NKT80263	92p
2N2010	37p	2N4087	12p	AF143	25p	BF225	15p	BCY35	35p	NKT80264	92p
2N2011	37p	2N4088	12p	AF144	25p	BF226	15p	BCY36	35p	NKT80265	92p
2N2012	37p	2N4089	12p	AF145	25p	BF227	15p	BCY37	35p	NKT80266	92p
2N2013	37p	2N4090	12p	AF146	25p	BF228	15p	BCY38	35p	NKT80267	92p
2N2014	37p	2N4091	12p	AF147	25p	BF229	15p	BCY39	35p	NKT80268	92p
2N2015	37p	2N4092	12p	AF148	25p	BF230	15p	BCY40	35p	NKT80269	92p
2N2016	37p	2N4093	12p	AF149	25p	BF231	15p	BCY41	35p	NKT80270	92p
2N2017	37p	2N4094	12p	AF150	25p	BF232	15p	BCY42	35p	NKT80271	92p
2N2018	37p	2N4095	12p	AF151	25p	BF233	15p	BCY43	35p	NKT80272	92p
2N2019	37p	2N4096	12p	AF152	25p	BF234	15p	BCY44	35p	NKT80273	92p
2N2020	37p	2N4097	12p	AF153	25p	BF235	15p	BCY45	35p	NKT80274	92p
2N2021	37p	2N4098	12p	AF154	25p	BF236	15p	BCY46	35p	NKT80275	92p
2N2022	37p	2N4099	12p	AF155	25p	BF237	15p	BCY47	35p	NKT80276	92p
2N2023	37p	2N4100	12p	AF156	25p	BF238	15p	BCY48	35p	NKT80277	92p
2N2024	37p	2N4101	12p	AF157	25p	BF239	15p	BCY49	35p	NKT80278	92p
2N2025	37p	2N4102	12p	AF158	25p	BF240	15p	BCY50	35p	NKT80279	92p
2N2026	37p	2N4103	12p	AF159	25p	BF241	15p	BCY51	35p	NKT80280	92p
2N2027	37p	2N4104	12p	AF160	25p	BF242	15p	BCY52	35p	NKT80281	92p
2N2028	37p	2N4105	12p	AF161	25p	BF243	15p	BCY53	35p	NKT80282	92p
2N2029	37p	2N4106	12p	AF162	25p	BF244	15p	BCY54	35p	NKT80283	92p
2N2030	37p	2N4107	12p	AF163	25p	BF245	15p	BCY55	35p	NKT80284	92p
2N2031	37p	2N4108	12p	AF164	25p	BF246	15p	BCY56	35p	NKT80285	92p
2N2032	37p	2N4109	12p	AF165	25p	BF247	15p	BCY57	35p	NKT80286	92p
2N2033	37p	2N4110	12p	AF166	25p	BF248	15p	BCY58	35p	NKT80287	92p
2N2034	37p	2N4111	12p	AF167	25p	BF249	15p	BCY59	35p	NKT80288	92p
2N2035	37p	2N4112	12p	AF168	25p	BF250	15p	BCY60	35p	NKT80289	92p
2N2036	37p	2N4113	12p	AF169	25p	BF251	15p	BCY61	35p	NKT80290	92p
2N2037	37p	2N4114	12p	AF170	25p	BF252	15p	BCY62	35p	NKT80291	92p
2N2038	37p	2N4115	12p	AF171	25p	BF253	15p	BCY63	35p	NKT80292	92p
2N2039	37p	2N4116	12p	AF172	25p	BF254	15p	BCY64	35p	NKT80293	9

# TECHNICAL TRAINING

## *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunications Techns'. Certs.
  - Radio Amateurs' Examination
  - General Radiocommunications Certificate
  - C. & G. Radio Servicing Theory
  - General Certificate of Education, etc.
- Now available Colour T.V. Servicing

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

Accredited by the CACC.

Member of the ABCC.



EST. 1891

### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. FA28, Intertext House, Stewarts Road, London, S.W.8 4UJ  
Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam).....

NAME (BLOCK CAPITALS PLEASE).....

ADDRESS.....

AGE.....OCCUPATION.....

INTERNATIONAL CORRESPONDENCE SCHOOLS



## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 75p



Size 12

### THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 75p



Size 10

### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF.	ALLOY	SWG	Length	Price
19A	60/40	18	18p*	
Size 5 (Ultra-thin)	Savbit	18	18p*	
15	60/40	22	22p*	

\*Recommended Price



### INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER.

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 50p



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

## SAVE UP TO £10\* on the Boots Audio System now!



The amplifier is fitted with controls for treble, bass and stereo balance and a special contour control. Power output 4 watts.  
The deck made by Philips has autochange and single-play facility, with a manually operated pick-up lift, ceramic cartridge, diamond stylus and transparent dust cover.  
The Loudspeakers are 6 1/2" dual cone high flux units.  
The Mono Radio Tuner covers VHF, Medium and Long Wavebands. Mono but stereo convertible if required. Mains powered. (can be purchased separately).

This Unit Stereo and Mono Radio Tuner are the components of the popular Boots Audio System. • Now you can buy them both for only £67.90 instead of £77.90. • Or separately – The Unit Stereo normally £52.90 is now £47.90 a saving of £5. • The Radio Tuner, normally £25 is now £20, a saving of £5.

And you can be sure you're getting good value for money. This superb Audio System is normally great value at £77.90. It has up-to-the-minute styling, using electronically matched components to provide outstanding performance.

Such an excellent bargain can be yours for just £67.90. And once you've come along to a Boots Audio and Record Department you'll find lots of interesting things to delight the music lover. But don't delay because the offer ends on March 11th.

\*These special offers are available from Boots Audio and Record Departments, while stocks last from Jan 31st to March 11th.



# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS!

### CLEAR PLASTIC METERS

TYPE SW.100  
100 x 80 mm.

50μA	...	\$2-60
50-0-50μA	...	\$2-45
100μA	...	\$2-30
100-0-100μA	...	\$2-45
500μA	...	\$2-35
1mA	...	\$2-10
20V D.C.	...	\$2-10
50V D.C.	...	\$2-10
300V D.C.	...	\$2-10
1 amp. D.C.	...	\$2-10
5 amp. D.C.	...	\$2-10
300V. A.C.	...	\$2-10
VU Meter	...	\$2-75

### BAKELITE PANEL METERS

TYPE S-80  
80 mm.

square fronts

50μA	...	\$2-80
50-0-50μA	...	\$2-10
100μA	...	\$2-75
100-0-100μA	...	\$2-10
500μA	...	\$2-80
1mA	...	\$2-60
20V D.C.	...	\$2-80
50V D.C.	...	\$2-80
300V D.C.	...	\$2-80
1 amp. D.C.	...	\$2-80
5 amp. D.C.	...	\$2-80
300V. A.C.	...	\$2-80
VU Meter	...	\$2-37

## "SEW" CLEAR PLASTIC METERS

Type MR.52P. 1 2 1/2" x 4 1/2" fronts.

50μA	...	\$2-80
100μA	...	\$2-80
500μA	...	\$2-80
1 amp.	...	\$2-80
5 amp.	...	\$2-80
30 amp.	...	\$2-80
20V D.C.	...	\$2-80
50V D.C.	...	\$2-80
150V D.C.	...	\$2-80
300V D.C.	...	\$2-80
15V A.C.	...	\$2-80
300V A.C.	...	\$2-80
S Meter 1mA	...	\$2-87
VU Meter	...	\$2-60
1 amp. A.C.*	...	\$2-80
5 amp. A.C.*	...	\$2-80
10 amp. A.C.*	...	\$2-80
20 amp. A.C.*	...	\$2-80
30 amp. A.C.*	...	\$2-80

Type MR.52P. 1 2 1/2" x 3 1/2" square fronts.

50μA	...	\$2-10
50-0-50μA	...	\$2-10
100μA	...	\$2-10
100-0-100μA	...	\$2-10
500μA	...	\$2-10
1mA	...	\$2-10
1-0-1mA	...	\$2-10
5mA	...	\$2-10
10mA	...	\$2-10
10V D.C.	...	\$2-80
20V D.C.	...	\$2-80
50V D.C.	...	\$2-80
300V D.C.	...	\$2-80
15V A.C.	...	\$2-10
300V A.C.	...	\$2-10
S Meter 1mA	...	\$2-10
VU Meter	...	\$2-10
1 amp. A.C.*	...	\$2-10
5 amp. A.C.*	...	\$2-10
10 amp. A.C.*	...	\$2-10
20 amp. A.C.*	...	\$2-10
30 amp. A.C.*	...	\$2-10

Type MR.52P. 2 1/2" x 3 1/2" square fronts.

50μA	...	\$2-10
50-0-50μA	...	\$2-60
100μA	...	\$2-60
100-0-100μA	...	\$2-60
500μA	...	\$2-60
1mA	...	\$2-60
5mA	...	\$2-60
10mA	...	\$2-60
50μA	...	\$2-60
100μA	...	\$2-60
500μA	...	\$2-60
1 amp.	...	\$2-60
5 amp.	...	\$2-60

Type MR.52P. 2 1/2" x 3 1/2" square fronts.

50μA	...	\$2-10
50-0-50μA	...	\$2-60
100μA	...	\$2-60
100-0-100μA	...	\$2-60
500μA	...	\$2-60
1mA	...	\$2-60
5mA	...	\$2-60
10mA	...	\$2-60
50μA	...	\$2-60
100μA	...	\$2-60
500μA	...	\$2-60
1 amp.	...	\$2-60
5 amp.	...	\$2-60

## "SEW" BAKELITE PANEL METERS

Type MR.55. 3 1/2" square fronts.

500μA	...	\$1-90
1 amp.	...	\$1-90
5 amp.	...	\$1-90
15 amp.	...	\$1-90
30 amp.	...	\$1-90
50 amp.	...	\$1-90
5V D.C.	...	\$1-90
10V D.C.	...	\$1-90
20V D.C.	...	\$1-90
50V D.C.	...	\$1-90
150V D.C.	...	\$1-90
300V D.C.	...	\$1-90
15V A.C.	...	\$1-90
300V A.C.	...	\$1-90
S Meter 1mA	...	\$2-37
VU Meter	...	\$2-30
50mA A.C.*	...	\$2-20
100mA A.C.*	...	\$2-20
200mA A.C.*	...	\$2-20
500mA A.C.*	...	\$2-20
1 amp. A.C.*	...	\$2-20
5 amp. A.C.*	...	\$2-20
10 amp. A.C.*	...	\$2-20
20 amp. A.C.*	...	\$2-20
30 amp. A.C.*	...	\$2-20

**\*MOVING IRON—**  
**ALL OTHERS MOVING COIL**  
 Please add postage

## SEW EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	...	\$2-00
100μA	...	\$2-45
1mA	...	\$2-40
50-0-50μA	...	\$2-45
1A d.c.	...	\$2-40
5A d.c.	...	\$2-40
10V d.c.	...	\$2-40
20V d.c.	...	\$2-40
50V d.c.	...	\$2-40
300V d.c.	...	\$2-40
Dual range	...	\$2-45
500mA/5A d.c.	...	\$2-45
5V/50V d.c.	...	\$2-45

## EDGWISSE METERS

Type PE.70. 3 1/2" x 1 1/2" x 1 1/2" deep.

50μA	...	\$2-10
50-0-50μA	...	\$2-10
100μA	...	\$2-10
100-0-100μA	...	\$2-10
500μA	...	\$2-10
1mA	...	\$2-10
500μA	...	\$2-75
1mA	...	\$2-45
300V A.C.	...	\$2-45
VU Meter	...	\$2-40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

# MULTIMETERS for EVERY purpose!

MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection 0/5/15/60/300/1,200V. D.C. 0/5/30/120/600/1,200V. A.C. 0/300μA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm—20 to +63 db. \$2-97. P. & P. 15p.

MODEL PL436 20kΩ/Volt D.C. 8kΩ/Volt A.C. Mirror scale. 6/3/12/30/120/600V D.C. 3/30/120/600V A.C. 50/600μA/60/600 mA. 10/100K/1 Meg/10 MegΩ. -20 to +46db. \$2-97 P & P 12p.

MODEL 5025 57 Ranges. Giant 5 1/2" Meter. Polarity Reverse Switch. Sensitivity: 50K/Volt D.C. 5K/Volt A.C. D.C. Volts: -125, -25, 1-25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50IA, 2-5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 2K, 10K, 100K, 1MEG, 10 MEG. Decibels: -20 to +80 db. \$12-50. P. & P. 17p.

TKM MODEL TW-20CB FEATURES RE-SETTABLE OVERLOAD BUT-TON Sensitivity: 20K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 0-0.5, 2-5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0-5, 5, 50, 500mA, 10 amp. Resistance: 0-5K, 50K, 0-500K. 5 MEG. Decibels: -20 to +52dB. \$11-50. P. & P. 17p.

ROUND SCALE TYPE PENCIL TESTER MODEL TS 68. Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V A.C. and DC at 1000 ohm p.v. Resistance 0-20K ohms. ONLY \$1-97 P. & P. 13p.

TKM MODEL 117 F.E.T. ELECTRONIC VOLTMETER. Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3-1200V. AC VOLTS 3-300V RMS. 8-0-800V P-P. DC CURRENT 15-150mA. Resistance up to 20000 ohm. Decibels -20 to +51 db Complete with leads/instructions. \$17-50. P. & P. 20p.

TE-40 HIGH SENSITIVITY A.C. VOLTMETER. 10 meg input 10 ranges: 0/100mV/1/3/1/3/10/30/100/300V. R.M.S. decs.-1.2 Mc/s. Decibels -40 to +50db. Supplied brand new complete with leads and instructions. Operation 230V. A.C. \$17-50. Carr. 25p.

TE22 SINE SQUARE WAVE AUDIO GENERATORS. Sine: 20cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 5,000 ohms, 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. \$17-50. Carr. 37p.

TE-20RF SIGNAL GENERATOR. Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V A.C. Brand new with instruction. \$18. P. & P. 37p. S.A.E. for details.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE. A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11-1 megΩ. 6 Ranges ± 1% 50 μA H. 11 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Overload to 100V. Meter indication. Attractive 2 tone metal case. Size 7 1/4" x 5" x 2 1/2". \$20. P. & P. 25p.

MODEL LT.101 1000 O.P.V. 0/10/50/250/1000 V. D.C. 0/10/50/250/1000 V. A.C. 0/1/100 M.A. 0/100 K ohms. \$1-97. P. & P. 15p.

TKM MODEL MD.120 Mirror scale. 20kV/Volt D.C. 10kΩ Volt A.C. 30/60/300/600/3,000 V. D.C. 6/12/20/1,200 V. A.C. Current 0-60mA/0-12/0/300mA. 0-60K/0-6 MegΩ. -20 to +63 db. \$2-82. P & P 15p

MODEL 500 30,000 O.P.V. with overload protection mirror scale 0/5/2-5/10/25 100/250/500/1,000V. D.C. 0/2-5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg/60 MegΩ. \$2-87. Post paid.

TKM LAB TESTER. 100,000 O.P.V. 5 1/2" Sosis Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: -5, -2.5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 10, 50, 100, 250, 500, 1,000V. D.C. Current: 10, 100μA, 10, 100, 500mA, 2-5, 10 amp. Resistance: 1K, 10K, 100K, 1MEG, 100 MEG. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size 7 1/2" x 6 1/2" x 3 1/2". \$18-90. P. & P. 25p.

RUSSIAN 22 RANGE MULTIMETER. Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 μA/1/10/100mA. Resistance 300 ohms/3/30/300K/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$22-97 P. & P. 25p.

TO-2 PORTABLE OSCILLOSCOPE. A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPS-1 MHz. Input imp. 2 meg Ω 25 P.F. Illuminated scale. 2" tube. 115 x 180 x 230mm. Weight 81b. 220/240 V a.c. Supplied brand new with hand-book. \$22-50. Carr. 50p.

FTC-401 TRANSISTOR TESTER. Full capabilities for measuring A, B and ICQ. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$2-97. P. & P. 15p.

NEWELL DIGITAL VOLTMETER VT.100. Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1-999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2" x 2 1/2" x 3 1/2". AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. \$28-97. Carr. 50p.

G. W. SMITH & CO (RADIO) LTD. Also see next two pages

# SEMI-CONDUCTORS/VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors		2N3415 25p		2N5458 35p		BC114 15p		BFW90 30p		NK7219 30p	
2G301	20p	2N3416	27p	2N5459	40p	BC115	15p	BFW91	20p	NK7223	20p
2G302	20p	2N3417	37p	2N5460	25p	BC116	15p	BFX12	22p	NK7224	22p
2G303	20p	2N3418	37p	2N5461	25p	BC117	15p	BFX13	22p	NK7225	22p
2G304	20p	2N3419	37p	2N5462	25p	BC118	15p	BFX14	22p	NK7226	22p
2G400	20p	2N3515	37p	2N5558	25p	BC214	15p	BFX110	22p	NK7322	22p

||
||
||

# HI-FI EQUIPMENT

SAVE UP TO  
**33 1/3% OR MORE**  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!



## RECORD DECKS

B.S.R. Mini Mono†	24-97	SP25 III	210-50
C129†	26-70	SL65B	218-45
MP60	10-75	AP76	218-90
810	214-85	SL72B	228-95
510	211-85	SL75B	228-50
310	49-85	SL95B	232-95
810	234-47	401	229-95
MP60 TPD1	217-85	ZERO 100A	245-95
MP60 TPD2	215-85	ZERO 100S	242-75
610 T.P.D.I	220-97	GOLDRING	
210 Package*	49-85	GL69/2	218-97
H.T.70	215-55	GL69P	225-95
H.T.70 Pack	222-50	GL72	223-25
THOBENS		GL72P	230-25
TD125	259-85	GL75	229-97
TD126AB	294-25	GL75P	238-50
TX325	23-70	LID 72	23-75
TD150AII	234-50	LID 75	23-95
TD150ABII	240-25	GL85	249-50
TX11	23-77	GL101	226-60
GARRARD		G99	219-95
2025 T/C*	28-50	PIONEER	
3500*	29-75	238-50	

† Mono. \* Stereo Cartridge  
All other models less Cartridge  
Carriage 50p extra any model.

## RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cart. ridge. Garrard

2025 T/C with Sonotone 9TAHCD	218-95
Garrard SP25 Sonotone 9TAHCD	215-95
Garrard SP25III Goldring 8300	218-95
Garrard AP76 Goldring 8300	228-95
Garrard SP25III/Shure M75-6	219-95
Garrard AP76/Shure M75-6	230-95
BSB MP60 Audio Technica AT.85	221-00
Goldring GL72 Goldring 8300	237-50
Goldring GL75 Goldring 8300	242-50
Goldring GL75 Goldring 8300E	248-65

Carriage 50p extra any model.

## ★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6x4x2 1/2 in. 3 I.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 V battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. **26-37p.** P. & P. 12p. Stereo multiplex adaptors **24-87p.**

## SINCLAIR EQUIPMENT

Project 60. Package offers.

2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. **214-75** Carr. 37p. Or with PZ6 power supply **218-85** Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. **220-25** Carr. 37p. Transformer for PZ8. **22-97p.** extra. Add to any of the above **24-87p.** for active filter unit and **218-90** for pair of Q15 speakers. Project 60 FM Tuner **220-25** Carr. 37p. All other Sinclair products in stock. 2000 Amp **223-75** Carr. 37p.; 3000 Amp **231-50** Carr. 37p.; Neoteric Amp **248-95** Carr. 37p. IC10/IC12 **22-50** Carr. 37p. NEW PROJECT 605 — **220-97p.** Carr. 37p.

## LATEST CATALOGUE

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 272 pages, fully illustrated and detailing thousands of bargains.

SEND NOW  
**ONLY 37 1/2 p**  
P & P 10p

## TELETON SAQ-206B STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag, xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List **232-50** OUR PRICE **219-95** Carr. 37p.

## TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/Amp. and now offered at a ridiculous low price. 5 watts rms. per channel. Tape/Cer phono inputs. AFC/Built-in M.P.X. List **251.00** OUR PRICE **238-75** Carr. 50p.

## ● SUGGESTED SYSTEM ●

F.2000, Garrard 2025T/C Changer fitted stereo cartridge, with plinth and cover and pair of G.W.S. 3 way Speakers. Total Rec. Price **297-73p.** OUR PRICE **254-65** Carr. 41p.

## MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mics: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono neg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. **28-97p.** P. & P. 20p.

## HA-10 STEREO HEADPHONE AMPLIFIER




All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5MU/100MU. Output 50MW. **25-97p.** P. & P. 15p.

## NS-1600W STEREO AMPLIFIER



Excellent on a budget price amplifier. All silicon transistor. Handsome Walnut case. Switched input selector, separate balance, volume, treble, bass controls. Output 2x6W RMS. Inputs Mag. Tape. Xtal. Tuner. Tape Out. **214-75** Carr. 37p.

## EA.41 REVERBERATION AMPLIFIER

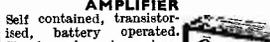


Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverb control. Beautiful walnut cabinet. 7 1/2 x 3 x 4 1/2 in. **25-97p.** P. & P. 15p.

## BH.001 HEAD-SET AND BOOM MICROPHONE



Moving coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. **24-62p.** P. & P. 15p.
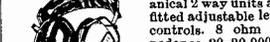
## HOSIDEN DH-085 DE-LUXE STEREO HEADPHONES



Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack plug. **27-97p.** P. & P. 12p.

## Model S-100TR MULTIMETER TRANSISTOR TESTER

100,000 o.p.v. MIRROR SCALE OVERLOAD PROTECTION  
0/12/6/3/12/30/120/600 V D.C. 0/6/30/120/600 V A.C. 0/12/600/1/12/300MA 1/12 AMP D.C. 0/10K/1 MEG/100 MEG. -20 to +50 db. 0-01 -2 MFD. Transistor tester measures Alpha, Beta and Ico. Complete with batteries, instructions and leads. **213-50** P. & P. 25p.

## MCA.220 AUTOMATIC VOLTAGE STABILISER

Input 88-125 V AC or 176-250 V AC. Output 120 V AC or 240 V AC. 200 VA rating. **211-97** Carr. 50p.

## BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000 Hz; Square 18-50,000 Hz  
Output max. +10 dB (10 K ohms)  
Operation internal batteries  
Attractive 2-tone case 7 1/2" x 5" x 2". Price **217-50** Carr. 17p.

## TE-16A Transistorised Signal Generator

Stranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. **27-97p.** P. & P. 20p.

## CRYSTAL CALIBRATORS NO. 10

Small portable crystal controlled wavemeter. Size 7 x 7 1/2 x 4 in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated to read scale. Power requirements 300V. D.C. 15mA and 12V D.C. 0.3A. Excellent condition. **24-47p.** Carr. 37p.

## TEI II. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ohm range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.05dB. +Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ohm load resistance with internal/external switch. Brand new. **227-50** P. & P. 20p.

## SDH 8V HI-FI PHONES

Input 8-16 Ohm. Frequency 20-18,000Hz stereo or mono switch, separate volume controls each ear. padded headband. **23-97p.** P. & P. 20p.

## HELICAL POTENTIOMETERS

ITT MCFM15 10 TURN 2 1/2 WATTS Available 500 ohm, 1K, 5K ohm. **21-25** each P. & P. 15p.

## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1/2 in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, **72p.** P. & P. 7p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, **21-05** P. & P. 7p. 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms, **21-87p.** P. & P. 7p.

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

S-280 General Purpose Bench Mountings	1 Amp	27-00
	2.5 Amp	28-00
	5 Amp	21-75
	8 Amp	21-50
	10 Amp	22-50
	12 Amp	22-60
	20 Amp	22-00

S-280B Panel Mounting  
1 Amp 27-00  
2.5 Amp 28-05

Please add postage ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS. Special discounts for quantity

## RF214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V A.C. Size 185 x 85 x 105mm. **23-97** P. & P. 25p.

## PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 Volt DC up to 3 amps. Meter to monitor current. Input 220/240V A.C. Size 4" x 3 1/2" x 6 1/2". **211-97** P. & P. 25p.

## UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s-30mc/s. FET, 8 Meter, Variable BFO for SSB, Built-in Speaker, Bandspread, Sensitivity Control. 220/240V. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. **225** Carr. 37p.

## LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, 3 Meter, Bandspread, RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12v. D.C. Brand new with instructions. **245** Carr. 50p.

## UNR-30 RECEIVER

4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. **215-75** Carr. 37p.

## B.C. 221 FREQUENCY METERS

latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. **227-50** each. Carr. 50p.

## SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electric appliances etc. Input 230/240V. A.C. Output continuously variable from 20V-230V. Model MR 2305 5 amp 68 x 46 x 43mm **28-87p.** Model MR 2310 10 amp 90 x 65 x 60mm **211-97p.** Postage 12p.

## AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

150 W.	22-87p	P. & P. 17p
300 W.	23-25	P. & P. 22p
600 W.	24-97p	P. & P. 32p
1000 W.	27-25	P. & P. 37p
1500 W.	28-97p	P. & P. 42p
5000 W.	236-00	P. & P. 21


# G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9.5 MONDAY TO SATURDAY
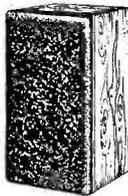
# LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 1/2 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.



## ELF

An extension speaker of quality; 9 x 5 1/2 x 3 1/2 in. veneered in natural teak with smart gold and mottled Vynair front 3 ohm speaker. The baffle is half inch thick. A real bargain at £1-85 P. & P. 37 1/2 p.

## THE SHELLEY


Size 21 x 11 x 6 1/2 in.

An extremely elegant speaker system made of 12mm. chipboard covered with black leathercloth with mottled Vynair front. This unique system uses three ex-TV speakers. Carefully matched and tested. Will handle 10 watts and will match 8 ohms impedance, if preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4-95 plus 70p P. & P. MATCHING TRANSFORMER for 15 ohms 85p post free.


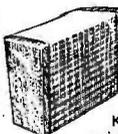
## VYNAIR

Widths from 50 to 54 in., 75p yd. off roll. P. & P. 10p, 1/2 yard 40p. P. & P. 10p. Send 5p stamps for samples.



## IMP

Wedge shaped extension speaker 7 1/2 x 6 1/2 x 4 in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1-25. P. & P. 36p each

## CARTRIDGES-Mono

GP.91 Stereo Compatible £1-25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95p. T.T.C. Crystal High Gain, 75p. B.S.R. TC8H Jap. equivalent £1-25. P. & P. 7p.

## HI-FI STEREO HEADPHONES

Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms, frequency range 30-15,000 Hz 6ft. cord and standard stereo plug. Only £2-57 1/2. P. & P. 27p.

## Stereo Headphone Junction Box

Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 2 position switch to give headphones only, speakers only. Only £1-50. P. & P. 12 1/2 p.

# BOOST THE SOUND

OF TAPE RECORDERS, RECORD PLAYERS, EXTENSION SPEAKERS

P. & P. 57p  
Makes all the difference to volume and quality. Contains 3 speakers in series—ex-TV with hi-fi flux magnet recon., tested for Mono or Stereo. Output 8 watts. Impedance 9 ohms. Available in black leathercloth. Size 23 1/2" x 5 1/2" x 5 1/2". Keyhole slot for wall mounting. Twin connecting cable 12yds., 35p min. Matching transformers if required for other output impedance 85p post free.

## CLARENCE

11" wide x 8 1/2" x 4 1/2" deep with volume control covered in Black rexine and Mottled Vynair. £2-25 P & P 25p.

## CARTRIDGES-Stereo

Sonotone 9TA H/C Diamond £2-40. Ronette S105 Medium Output, £1-40. S106 High Output £1-40. Acos GP93/1 Sapphire, £1-90. GP94 1 Sapphire, £2. TA700 equivalent to B.S.R. SX111, £1-75. Japanese equivalent to B.S.R. TC8s, £1-75. P. & P. 7p on each.

## SPEAKERS

E.M.I. 13 1/2 x 8in, 3 ohm £2-50, 15 ohm. P. & P. 30p. E.M.I. 13 1/2 x 8in, fitted two 2 1/2 in. tweeters, 15 ohm £4-50. P. & P. 30p. E.M.I. 13 1/2 x 8in. (15 ohm) Hi-Fi quality £6-25. P. & P. 35p. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30p. Eagle Crossover £1-02p. P. & P. 5p.

# BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984 (Nr. Tooting Broadway Underground Station)

(Closed all Wednesday)



**AMPEX 7-5v. D.C. MOTOR.** This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500 ma. Draws 60 ma on run. 600 rpm + 5% speed adjustment. Internal AF/RF suppression 1/2" dia. 1" spindle, motor 3/4" dia. 1 1/2". Original cost £16-50. Our price £4-25. P. & P. 25p. Mu-metal enclosure available 75p each.

### SYNCHRONOUS MOTORS

**SMITHS, 250v. 50 Hz.** Available in the following R.P.M. 2-3-6-10-30-60. Price 75p each. Carr. paid.

**CROUZET, 220/380v. 50/60 Hz. 250-300 rpm.** 75p. Carr. paid.

**MAINS INDUCTION MOTOR.** Open frame, 1/2" spindle, weight 1/2 lb. Powerful. 88p each. P. & P. 12p.

**GEARED MOTORS**  
**ELECTRO CONTROL (CHICAGO).** Shaded pole 240v. 50Hz. 200rpm. 10lb. in. £2-50. P. & P. 25p.  
**MYCALEX.** Open frame, shaded pole motors, 240v. 50 Hz 7 rpm. 28 lb. in. 80 rpm. 12 lb. in. £2-25 each. P. & P. 25p.

**"CROUZET" TYPE 965. 115/240v. 50 Hz. 47/68 watts. 50 rpm.** Stoutly constructed. Size: 2 1/4" dia. x 3 1/4" long plus spindle, 1" x 1/2" dia. Anticlock. £2-75. P. & P. 25p.

**TYPE 955.** Same as above, but 3 rpm. £3-00 P. & P. 25p.

**"MALLORY" LONG LIFE BATTERIES.** Type A. RM12 cell 1-35v. 3,600 ma/H. CAP. 250/300 ma cont. current. Size: 2" x 3". 5 for £1-00 or £2-00 per doz. Carr. Paid. Type B. Comprises 8 x RM12 cells. Nom. volts. 1-35 each 10-5v. Overall, 350 ma/H. CAP. 20/25 ma cont. current. Size: 2 1/4" x 1 1/2" x 3". 3 for £1-00 or £3-00 per doz. Carr. Paid.

**A.C./D.C. M/IRON AMMETERS.** 0-5 amps or 0-8 amps (suitable battery chargers, etc.). Perspex front. Size: 1 1/2" x 1 1/2". Any 2 for £1-10. Carr. Paid.

**ERNEST TURNER 800µA METER.** 1600 movement, 2" case elliptic, plastic front. Green - Red - Green uncalibrated scale. £1-50 each. Carriage paid.

## PROGRAMME TIMER BY HONEYWELL.

A bank of 15 micro-switches, are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 rpm) Originally cost £15-00 plus. Many applications such as lighting effects, etc. New in original makers precision. First class value at £5-75 plus 25p P. & P.

## PRECISION FAN CO (SMITHS INDUSTRIES) DOUBLE ENTRY CENTRIFUGAL FAN / BLOWER.

This is a beautifully balanced particularly quiet running unit giving approx. 90 cubic ft./min. The motor is a 2 pole shaded pole Mycalex, drawing only 240 ma on run. Weight 2 1/2 lbs. Sizes: case dia. 3-1 ins., width (case only) 3-125 ins. Width overall (inc.) 5-25 ins. Aperture 3-125 ins. x 1-85 ins. Offered well below makers price at £2-95. P. & P. 25p.

## RELAYS

Perspex enclosed, plug in, with base. Size: 1 1/2" x 1 1/2" x 2" MQ 308 6000 24v. 4 c/o. 60p each.

**SANGAMO WESTON.** Moving coil relay 3150 310µa, complete with base, 75p each.

**S.T.C. Midget Sealed Relay type 4109EC.** 12v. 40 ma 170Ω, single H.D. make. 53p each.

**"B. & R."** 3 c/o. 10 amp contacts (silver) operates on 2 volts D.C. Draws approx. 1 amp. Size: 2" x 1 1/2" x 1 1/2". £1-00.

**"ENGLE & GIBBS"** 240v. A.C. Plug-in relay 3 c/o perspex enclosed £1-00.

**NEW "F.I.R.E." PLUG-IN RELAY.** -115v. Coil 50/60 c.p.s. 3 heavy duty silver change-over contacts. Very robust. 63p.

**NEW "ISKRA" 240v. A.C. RELAY.** 3 x 6 amp. Changeover contacts. 63p.

**SIEMENS HIGH SPEED RELAY.** Type 89L, 1,700Ω + 1,700Ω coil. New 63p each.

**6 DIGIT NON-RESET COUNTER** by E.N.M. Ltd. 240v. A.C. Size: 2 1/2" high x 1 1/2" x 1 1/2". £1-75

**"SORENG" MAINS SOLENOID.** 1" travel, 18lb. pull (approx.). Size: 2 1/2" long x 2 1/2" x 2 1/2" high. Powerful. £1-75. P. & P. 25p.

**"DAVENSET" MAINS SOLENOID.** 1" travel. 8lb. pull (approx.). Size: 2 1/2" long x 2 1/2" x 2" high. Similar in appearance as above. £1-25. P. & P. 25p.

**"MAGNETIC DEVICES"** Mains Solenoid. 2" x 1 1/2" x 1 1/2" approx. 2lb. pull. Plunger Travel 1 1/2". New in makers boxes; offered at half original cost. 75p. P. & P. 25p.

**SLIDER SWITCHES.** 3 amp. type D.P.D.T. 1" x 1/2" x 1/2" deep. 1 amp. type 3 P.D.T. 1" x 1/2" x 1/2" deep £1-25 per doz. Either type or mixed as required. Carr. Paid.

**BONNELLA "CHERRY" ROLLER LEVER OPERATED MICRO-SWITCH TYPE B23-30K.** 5 amp. c/o. 502 operating pressure. Length of Lever. 1/2". Pre-travel .062". £2-25 per doz.

**"HONEYWELL" V3 Series.** Flush micro-switch 10 amp. c/o. The side panel is insulated. End plate size: 2" x 8". £1-50 per. doz. Carriage paid.

**VINKOR POT CORE ASS. TYPE LA.2103.** Normal price £1-48. Our price 75p.

**L.T. TRANSFORMERS.** Prim. 0-110-240v. Sec. 4-5-0-4-5v. at 1 amp. Size: 1 1/2" x 1 1/2" x 1 1/2". 60p. P. & P. 15p.

Prim. 220/240v. Sec. 0-5-10-15-20v. at 2 amps. £1-25. P. & P. 15p.

Prim. 200/240v. Sec. 0-1-56-58-60 at 3-5 amps plus 0-90 at 100 ma. Wax impregnated with screw term. blocks. Weight 10 lbs. £3-60, plus 40p P. & P.

**"WODEN."** Prim. 10-0-200-240v. Sec. two separate windings 6v. at 4 amps each. £2-50, plus 30p P. & P.

**"WODEN."** Prim. 0-110-200-220-240v. Sec. 34-36-38v. at 60va. £7-50, plus 50p P. & P.

**H.T. TRANSFORMER Prim. 240v. Sec. 0-380-400-420-440v. at 40va. £3. Carr. paid.**

**CURRENT FLOW INDICATOR.** Ideal for all types of battery operated equipment (portable machines, tape recorders, etc.). Four white segments appear when current flows. Coil is 600Ω 6/12v. Drawing only 8 ma on function. Neat in appearance. Size: dia. 1 1/2" x 1 1/2" deep. Fixing centres 1 1/2". £1-25 each. Carr. Paid.

# ELECTRO-TECH SALES

BUSINESS HOURS 301 EDGWARE ROAD, LONDON W2 1BN

9a.m.—6p.m. MON. TO SAT. (PW1) Tel. 01-262 2251/2



# 28watts, r.m.s. 40Hz to 40kHz $\pm$ 3dB



## Viscount III Audio Suite complete **£49**

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic and ceramic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

### PRICES SYSTEM 1

Viscount III R101 amplifier	£22.00+90p p&p
2 x Duo Type II speakers,	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG.	
cartridge plinth and cover	£23.00+£1.50
	p&p
<b>Total</b>	<b>£59.00</b>

Available complete for only **£52.00+£3.50 p&p**

### SYSTEM 2

Viscount R101 amplifier	£22.00+90p p&p
2 x Duo Type III speakers	£32.00+£3 p&p
Garrard SP25 Mk. III with MAG.	
cartridge, plinth and cover	£23.00+£1.50
	p&p
<b>Total</b>	<b>£77.00</b>

Available complete for **£69+£4 p&p**

### SYSTEM 3

Viscount III Amplifier R100	£17.00+90p p&p
2 x Duo Type II speakers, pair	£14.00+£2 p&p
Garrard SP25 Mk. III with CER. diamond	
cartridge, plinth and cover	£21.00+£1.50
	p&p
<b>Total</b>	<b>£52.00</b>

Available complete for only **£49.00+£3.50 p&p**

### SPEAKERS Duo Type II

Size approx 17" x 10 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ ". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts. 3 ohms. Simulated Teak cabinet. **£14 pair+£2 p&p.**

Duo Type III. Size approx 23 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ ". Drive unit 13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. **£32 pair+£3 p&p.**

### SPECIFICATION R101


14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges). 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within  $\pm$  1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities; headphone socket, power out 250mV per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio—65dB. P.U.2. -58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx 13 $\frac{3}{4}$ " x 9" x 3 $\frac{3}{4}$ ".

# R+TV

Radio and TV Components (Acton) Ltd. 21C High Street, Acton, London W3 6NG  
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.  
Goods not despatched outside U.K.

# SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

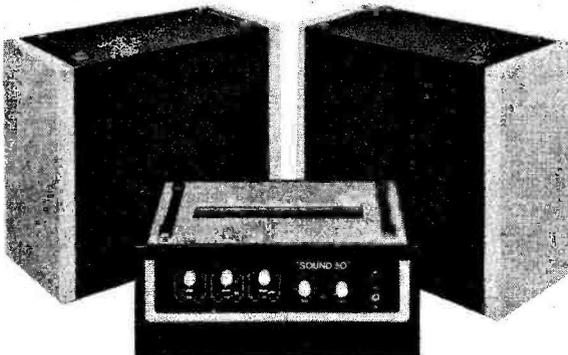

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

**Output Power:** 45 watts R.M.S. (Sine wave drive). **Frequency response:** -3dB points 30Hz at 18KHz. **Total distortion:** less than 2% at rated output. **Signal to noise ratio:** better than 60dB.

**Speaker Impedance:** 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

**SPEAKERS!** Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM £50** Plus £6 P. & P.

Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.50 plus £1.50 P. & P.  
Speakers £12.50 each plus £2.25 P. & P.

## THE ELEGANT SEVEN Mk. III

(350m W Output)




7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

**MAINS POWER PACK KIT:** 75p extra.

Price **£5.25** plus 50p. P. & P.  
Circuit 13p **FREE WITH PARTS.**

## THE DORSET (600m W Output)

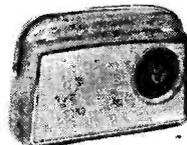

7-transistor fully tunable M.W.—L.W. superhet portable. Set of parts. The latest modularised and pre-alignment techniques make this simple to build. Sizes: 12 x 8 x 3in.

Price **£5.25** plus 50p P. & P.  
Circuit 13p **FREE WITH PARTS**

## CONTINENTAL 4 TRACK, 3 SPEED TAPE DECK



with high impedance heads

R.C. 74 tape deck. Three speeds—7½, 3½ and 1½ ips.

4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7". The R.C. 74 is driven by a powerful 200/250V 50-cycle A.C. motor. A heavy, accurately balanced, flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7½ ips. Fast rewind in both directions.

Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6 inches. Every single deck fully tested before dispatch. Spools not supplied.

Price complete **£15.00**. Plus 75p P. & P.

## RELIANT mk. IV



Provides a high standard of sound reproduction, with full mixing facilities. It's versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- ★ Five Electronically Mixed Inputs
- ★ Three Individual Mixing Controls
- ★ Separate base and treble controls common to all five inputs
- ★ Mixer employing F.E.T. (Field Effect Transistor)
- ★ Solid State Circuitry ★ Attractive Styling

**£9.50** plus P. & P. 60p.

**INPUTS:**—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity.

**CONTROLS:**—3 Volume controls. Base control range: 13db @ 60 Hz. Treble control range ± 12db @ 15KHz. Separate ON/OFF Switch. Neon Indicator.


**POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker

**SIGNAL/NOISE:**—Better than -80db on inputs 3, 4 and 5 & -50db on 1 & 2

**SUPPLY:**—220 - 250 AC Mains. **SIZE:**—12½" x 6" x 3½"

## TOURIST CAR RADIO

MARK 3

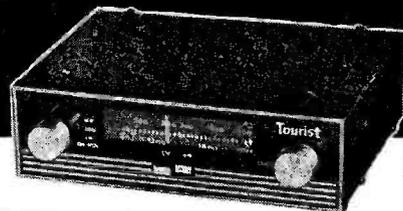

### ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

SET OF PARTS

**£6.30**

plus P. & P. 50p.

Circuit diagram 13p. Free with parts  
Speaker, baffle and fixing kit £1.25  
extra plus 25p. p. & p. Postage free  
when ordered with parts.



See previous page  
for address

RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED
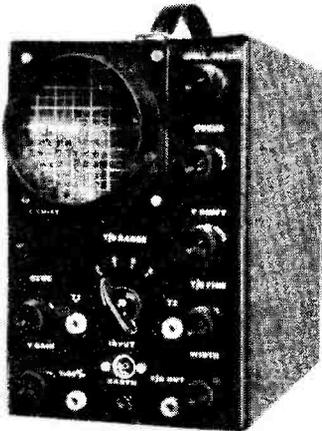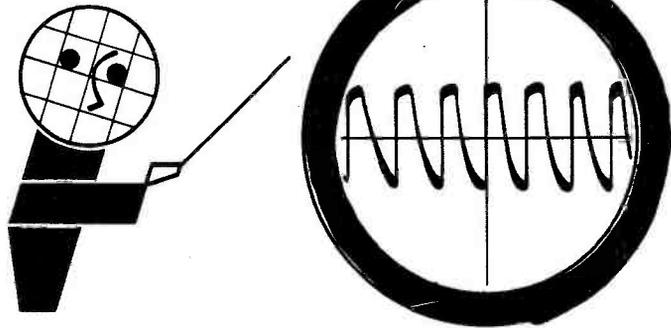
# look! electronics really mastered

**... practical  
... visual  
... exciting!**

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
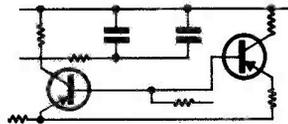
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME

BLOCK CAPS

ADDRESS

PLEASE P.W.6

**special free gift also to all our students**

# PRACTICAL WIRELESS

VOL 47 NO 11

Issue 781

MARCH 1972

## DX JUBILEE

ACCORDING to reliable eye (or ear?)-witnesses, such as our venerable columnist Henry and the antedeluvian researchers Colin Riches and Arthur Dow, founders of *Going Back* (official organ of the P.W. Darby and Joan Club), one of the major impacts at the dawn of broadcasting was not so much the material transmitted as the fascination of hearing something—anything—from a point far removed from the listener's ear.

Although they would have been horrified at the thought, these ancient radio listeners were, in fact, the first DX'ers. It is, of course, a far cry from pulling in 2LO with an adroit twiddle of the catswhisker in 1922 to phasing in an exotic Pacific station with the crystal filter in 1972. Nevertheless the motivation and reactions are similar.

Since the pioneer London broadcasting station 2LO officially opened in November 1922, this year we can celebrate (or mourn, according to taste) 50 years of broadcasting. More apposite to P.W. readers, we can hang out the bunting for 50 years of DXing. In that time, of course, many changes have taken place, not only in equipment but in the art and style of DX listening.

In the early stages of the hobby, the main criterion was actual distance—first the local stations, then Europe, then North America (all on medium waves), followed by the development of the short wave bands which permitted reception of the USA during daylight hours and extended the listening ear to all parts of the world. But then, as useable frequencies became higher, the old aim of maximum distance took a back seat, for on v.h.f., and later on u.h.f., a DX catch could be judged in hundreds instead of thousands of miles. One of the latest activities is DX television.

The style of transmissions has changed dramatically over the years; the early short wave programmes were of the pure entertainment type and they could be picked up on relatively simple receivers on bands that were blissfully uncluttered; amateurs had a wonderful time operating on low power—and getting through. The 30's, however, saw a change of direction. The Spanish Civil War brought with it jamming for the first time, together with the first invasion of amateur territory by propaganda broadcasting. The process has continued to the present day with its multitude of high powered political broadcasters, many disregarding international agreements, and the further erosion of amateur bands and consequent congestion.

Despite all these changes (many of them obviously for the worst), the DX bug still exerts its fascination.

We hope that the wall chart contained in this issue will be helpful to some of the newer recruits to the ranks of long distance listeners.

W. N. STEVENS—*Editor*.

## NEWS AND COMMENT

Leader	975
News . . . News . . . News . . .	976
New Books	989
Electronotes by <i>S. Ginsberg</i>	999
MW Column by <i>Charles Molloy</i>	1010
On the Short Waves by <i>Malcolm Connah</i> and <i>David Gibson, G3JDG</i>	1012
Letters	1017
CQ! CQ! CQ! CQ! CQ!	1022

## CONSTRUCTIONAL

Car Radio Signal Booster by <i>Caleb R. Bradley</i>	978
A Darkroom Thermometer by <i>R. A. Bottomley</i>	980
Take 20, No. 34, Magic Candle by <i>Julian Anderson</i>	986
Quality Hi-Fi System, Part 2 by <i>C. R. Bradley</i>	990
The P.W. Cube Radio 7 Transistor Superhet by <i>R. F. Graham</i>	996
Transistorised Oscilloscope, Part 2 by <i>J. Ransome</i>	1000
Comprehensive Multi-Band Receiver (Further Notes) by <i>F. G. Rayer, G3OGR</i>	1005

## OTHER FEATURES

DX Reception of VHF "Local" Radio by <i>Keith Pitt</i>	982
Transistor Circuitry for Beginners, Part 6 by <i>H. W. Hellyer</i> and <i>Michael Hollier</i>	1006
Going Back by <i>Colin Riches</i> and <i>Arthur Dow</i>	1018
IC of the Month, Toshiba TH9013P 20W Audio Amplifier by <i>L. A. J. Ireland</i>	1021

APRIL ISSUE WILL BE  
PUBLISHED ON MARCH 3rd

©IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

# NEWS... NEWS... NEWS...

## The BBC Stereo Service

The BBC is planning to expand its stereo service considerably during the next few years. The extension beyond the present Radio 3 service will take place in three phases.

(1.) *The installation of stereo origination facilities for Radio 2 (with Radio 1) and Radio 4.* This has called for a major re-equipment programme involving modifications to the continuity suites and central control equipment in London as well as a considerable increase throughout the United Kingdom in the number of tape machines, gramophone desks, studios and outside broadcast units equipped for stereo. This phase is already in progress, and it is expected that it will be possible to originate a major proportion of stereo programmes on Radio 2 by the end of 1972, and also to make possible the transmission of some stereo programmes on Radio 4. Further increases in stereo capability will continue during the succeeding years.

(2.) *The extension of Radio 2 and Radio 4 stereo to those transmitters already radiating Radio 3 in stereo.* For this a new system of s.h.f. radio links is planned, using pulse code modulation (PCM) (see below). It is expected that the three-network service, which involves the construction of several new radio link sites on the main route, will be available in the London area and the Midlands by the end of 1972 and in the North of England during 1973. Rowridge, serving central southern England, will be included in this phase and a full stereo service from Belmont, serving Lincolnshire, will follow the extension to the North of England.

(3.) *The extension of the three network stereo service northwards to Central Scotland and westwards to the Bristol Channel area.* The Post Office Corporation and the BBC are working towards this phase which it is expected will start in 1974. The transmitters expected to be included are Kirk o'Shotts (Lanarkshire), Pontop Pike (Durham), Sandale (Cumberland), and Wenvoe (Glamorgan). It is hoped also to include North Hessary Tor (Devonshire) in this phase, as well as certain of the relay stations associated with the main transmitters mentioned.


The PCM system to be used on the s.h.f. radio links has been developed by the BBC. It will carry 10 audio circuits. Each stereo programme will use two circuits, for the A and B channels, and the stereo coding will be carried out at each main transmitting station. The PCM system will provide improved quality in respect of both audio bandwidth and signal to noise ratio, from which mono as well as stereo listeners will benefit. It thus forms part of the BBC's plan to improve still further the quality of its v.h.f. transmissions throughout the country.

## Golden Silence



Picture shows Gloria Connell, actress daughter of the chairman of the Noise Abatement Society enjoying peace and quiet against a background of noise which would be intolerable without the Ear Defenders which reduce the noise of the road drills to a mere whisper. The Survey Meter's red lamp lights up when noise reaches danger levels. Ideal for "pop" fans who can't stand classical music and "classics" fans who can't stand pop music, the meter costs £10 and the Ear Defenders cost £5 from local stores or carriage paid from *Noise Abatement Society, 6 Old Bond Street, London W.1.*


## Jackson's Drive

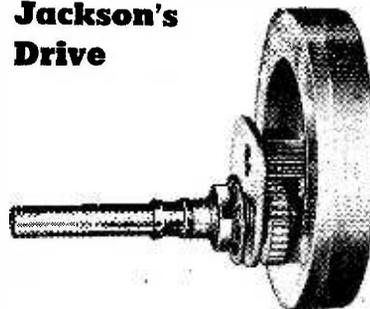

The *Accelerator Spinwheel Drive* is a cord drive unit intended for modern radio receivers with extra-long scales. It incorporates a 2 $\frac{1}{4}$ -inch-diameter (57mm) zinc-alloy flywheel driven through nylon-to-brass step-up gears at more than twice the speed of the drive-shaft. The complete unit weighs only 6oz (170g) but provides an inertial effect equivalent to a much larger flywheel, permitting rapid traverse of the scale. *Jackson Brothers (London) Ltd., Croydon CR9 4DG, England.*

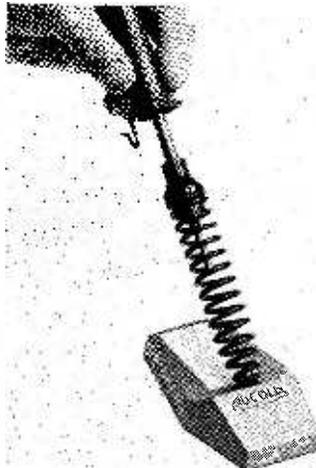
## Adcola Soldering Station

To complement the Invader range of soldering irons, Adcola Products Ltd has introduced the "Invader Soldering Station." It consists of a cast aluminium base, finished in hammered silver grey, containing an integral wiping sponge to facilitate the removal of solder from the tip of an instrument.



# NEWS... NEWS... NEWS...

## EMI Speaker Kits

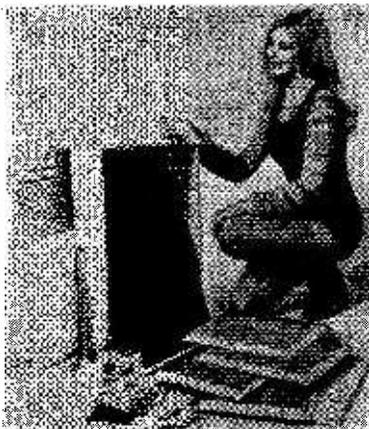


EMI has entered the loudspeaker enclosure market with a range of high quality enclosures in kit form. Available in polished wood veneers, the enclosures have been introduced by EMI Sound Products Limited, of Hayes, Middlesex, for use with its range of matched loudspeaker systems.

The enclosures are priced from £5.80, for a 12in. x 6in. x 8in. bookshelf model, to £29.50 for a large floor-standing enclosure measuring 33in. x 20in. x 15in. They have been designed to incorporate each of the eight different EMI loudspeaker systems which cover the 6 to 35 watts r.m.s. output range.
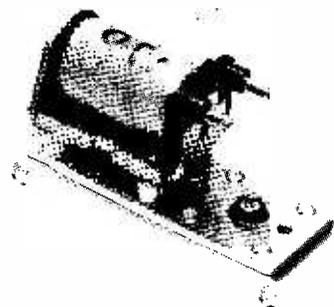
## Coax Relay

This is the Series 951 Co-axial Relay from Magnetic Devices for aerial switching at frequencies in the order of 450 megacycles.

For further information please contact *Magnetic Devices Limited, Newmarket, Suffolk. Telephone Newmarket 3451.*



## BBC Scholarship

*Mr I. G. Phillipps graduated with an upper second class honours degree in the Electrical Sciences Tripos at the University of Cambridge in 1971, and has been awarded a three-year BBC Research Scholarship to undertake research in the Department of Engineering at the University of Cambridge, under the supervision of Professor P. S. Brandon, MA. The subject of Mr Phillipps' research will be "ways of reducing the channel capacity required by a television signal or improving the quality of a television image within a given channel capacity, by the use of digital electronic techniques."*


## Radio Amateur Invalid & Bedfast Club

The address to which all correspondence concerning the Radio Amateur Invalid & Bedfast Club should now be sent is: Mrs. Frances Woolley, G3LWY, Woodclose, Penselwood, Wincanton, Somerset.

Bedfast Club membership is almost at the 400 mark and covers 13 countries. Any handicapped licensed amateur or short-wave listener, wherever he or she may live, who does not already belong to the Club is invited to apply to the Hon. Secretary at the address above for full details of membership, enclosing a stamped, addressed envelope.

Readers will be interested to know that Mr. Cecil Lewis, of Bude, received three letters telling him of the R.A.I.B.C. following his appeal for help which we printed in *Practical Wireless* last year.

## Criterion Mk. X

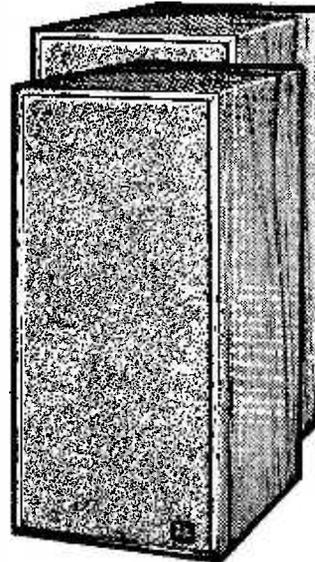


We recently had the opportunity to try the Lasky's Criterion Mk X speakers. They are bookshelf types employing the sealed infinite baffle enclosure principle and they are well worthy of consideration by the budget-conscious Hi-Fi enthusiast. An 8in. woofer, 5in. mid-range and 2½in. tweeter are used and the cabinets are oiled walnut with black woven speaker grilles. Frequency response is 40Hz-20kHz and maximum power handling capacity is 20W. The impedance is 8Ω. A useful feature of these speakers is that two types of speaker lead connection are supplied—phono or screw terminals. Cabinet size is 18¾ x 9⅞ x 9⅞in. and the very reasonable price is £25 the pair. Postage is 50p and the speakers are available singly for £13.50. *Lasky's Radio Limited, 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel. 01-790-4821.*
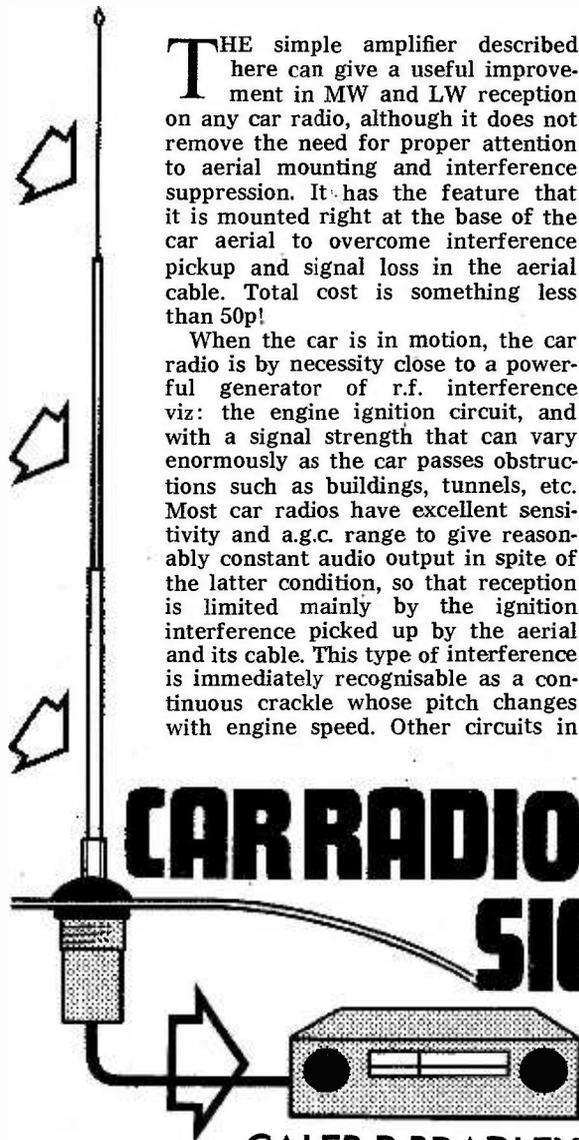
## The Practical Wireless CQ! Column

Items in the CQ! Column are carried free of charge as a service to readers. We only ask that those making use of the service answer all correspondence resulting and reimburse postage and all reasonable expenses. We cannot guarantee inclusion and requests for inclusion will not be acknowledged and will be dealt with in strict rotation. It would also help if readers could write out their "CQ!" in the style used in P.W. as this would help to speed things up.

Material for inclusion should be sent to Practical Wireless Editorial, Fleetway House, Farringdon Street, London, EC4A 4AD.



**T**HE simple amplifier described here can give a useful improvement in MW and LW reception on any car radio, although it does not remove the need for proper attention to aerial mounting and interference suppression. It has the feature that it is mounted right at the base of the car aerial to overcome interference pickup and signal loss in the aerial cable. Total cost is something less than 50p!

When the car is in motion, the car radio is by necessity close to a powerful generator of r.f. interference viz: the engine ignition circuit, and with a signal strength that can vary enormously as the car passes obstructions such as buildings, tunnels, etc. Most car radios have excellent sensitivity and a.g.c. range to give reasonably constant audio output in spite of the latter condition, so that reception is limited mainly by the ignition interference picked up by the aerial and its cable. This type of interference is immediately recognisable as a continuous crackle whose pitch changes with engine speed. Other circuits in

h.t. cable. Add-on suppressor resistors, typically 50k $\Omega$ , are sold for older cars or addition to others, and can be screwed into the middle of the h.t. lead from coil to distributor (e.g. Belling-Lee Sparkmaster L.1274/S). In conjunction with stray capacitance, such resistors form a top-cut filter which bypasses the r.f. component of the fast-rising spark voltage but has negligible effect on the strength of the spark.

The metalwork of the engine compartment helps screen ignition interference from the aerial, but poor bonding between the body, the bonnet and the engine block can reduce its effectiveness. The engine compartments of fibreglass bodied cars have to be lined with metal foil to obtain this screening. For ultimate interference suppression it is possible to replace all the h.t. wiring with coaxial cable. Use solid-dielectric TV co-ax as low-loss cellular dielectric type will not withstand the ignition voltage (perhaps 30kV peak), and earth all the screens to the coil mounting bracket. Such measures though are hardly necessary for domestic reception.

Another type of interference is a whine which also changes with engine speed and is caused by the generator. This is cured by connecting a standard car suppressor capacitor (still called *condenser* in the motor trade) between chassis and the brush (larger) terminal. Switches, both manual and automatic such as the brake pressure switch, and the motors of the wipers and heater can similarly be silenced by capacitors across their terminals. Car suppressor capacitors are usually about 0.5 $\mu$ F and are built much more ruggedly than corresponding electronics components.

Other circuits, such as the lights, should not cause

the car can also contribute interference and in the author's experience capacitor-discharge transistor ignition systems can be especially troublesome.

## INTERFERENCE REDUCTION

The car aerial should be mounted as far from the engine as possible. With front-engined vehicles this means on a rear wing, or at least on the roof. If the existing aerial cable needs to be extended, a 10ft. coaxial cable already fitted with appropriate plug and socket can be purchased (Norman type SL11).

The cable screen must make a good electrical connection to the car body at the aerial end. Paint must be scraped off to permit this and the underside of the aerial mounting should be sealed against road filth as rust can ruin the connection.

All modern cars are fitted by law with ignition suppression in the form of resistance in the high voltage paths, possibly in the form of spark plug connectors incorporating resistors, or special resistive

# SIGNAL BOOSTER

interference unless there is an intermittent connection somewhere. Indicator flashers normally contain their own suppressor capacitors.

## HEAD AMPLIFIER

The circuit of the unit is shown in Fig. 1 (negative earth cars) and Fig. 2 (positive earth cars). The difference lies only in the way the h.t. supply is derived, and the voltage readings with respect to chassis are different of course.

Two silicon planar transistors are used with d.c. feedback to stabilise the circuit against wide changes of temperature and supply voltage. Common-emitter stage Tr1 operates at low collector current (100 $\mu$ A) and provides the voltage gain of the circuit. Tuned circuits and chokes could have been used to give more amplification and less noise but in practice a small amount of untuned amplification is quite adequate and avoids overloading the aerial circuit of the car radio. Emitter resistor R2 gives Tr1 a high input impedance to minimise loading of the aerial. The amplified signal across R1 is direct-coupled to emitter follower Tr2 which provides no voltage amplification but acts as an impedance converter, giving a low impedance output to the aerial cable. Bias for Tr1 base is taken from the divider R4/R5 in Tr2 emitter to give negative feedback; R3 has a high value to preserve the high input impedance.

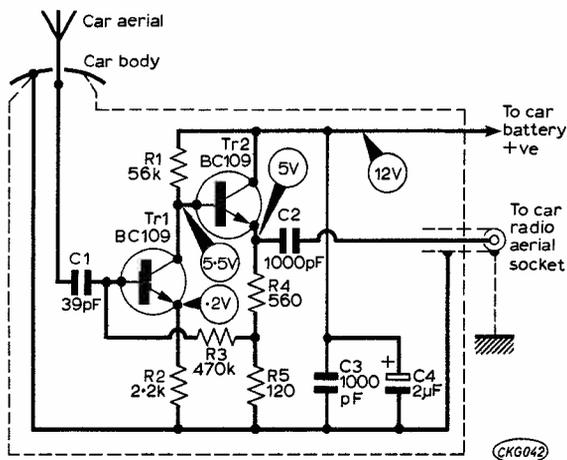


Fig. 1: Circuit suitable for negative chassis cars. All resistors are  $\frac{1}{4}W$ , 5% and the capacitors should be at least 20V working.

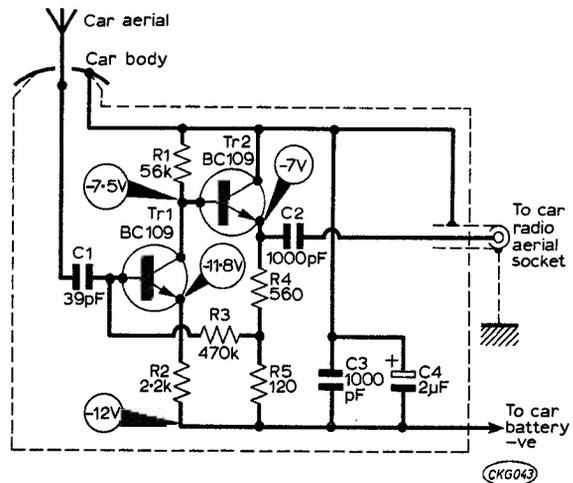


Fig. 2: The modified circuit designed for use with cars having a positive chassis.

The output isolating capacitor C2 is not essential since the radio will probably have an aerial isolating capacitor, but it does protect Tr2 against shorts in the cable or plug. It may seem curious that the h.t. supply is decoupled by both a large value electrolytic capacitor C4 and a small value ceramic C3. This is because the electrolytic may not be as effective at r.f. due to its own stray inductance; C3 ensures effective decoupling at r.f.

## CONSTRUCTION

While conventional wiring on, say, a piece of Veroboard can be employed, the method used by the author is simplicity itself. The components are simply wired together and encapsulated in candle wax inside a 35mm film cassette tin which serves as a screen. The arrangement is shown in Fig. 3. If you have a choice of cans use an Ilford tin as it has

slightly more room than the Kodak one. The tin cap is held under the aerial mounting nut (with insulating washer between) so it makes good contact with the car chassis. The body of the tin is then screwed onto the cap from underneath. The aerial cable and power wire leave through holes in the base of the tin. The input end of C1 is anchored under the aerial nut with sufficient lead to allow the tin to be screwed through about  $\frac{3}{4}$  turn, all that is required. The chassis connection to the circuit is by a short length of wire that can conveniently be trapped between the body and the cap threads. Note that if this connection is not made the circuit will still amplify, due to the chassis return via the aerial cable screen, but interference will be at a high level.

There is no need to switch the amplifier with the radio since the drain on the battery is negligible; the power lead can therefore be connected to the same point from which the radio gets its supply, often the ignition or light switch. Plug the aerial cable into the radio and unscrew fully the aerial trimmer if the radio has one. Since there is now plenty of signal, this can be done to minimise the loading on the first tuned circuit to improve selectivity.

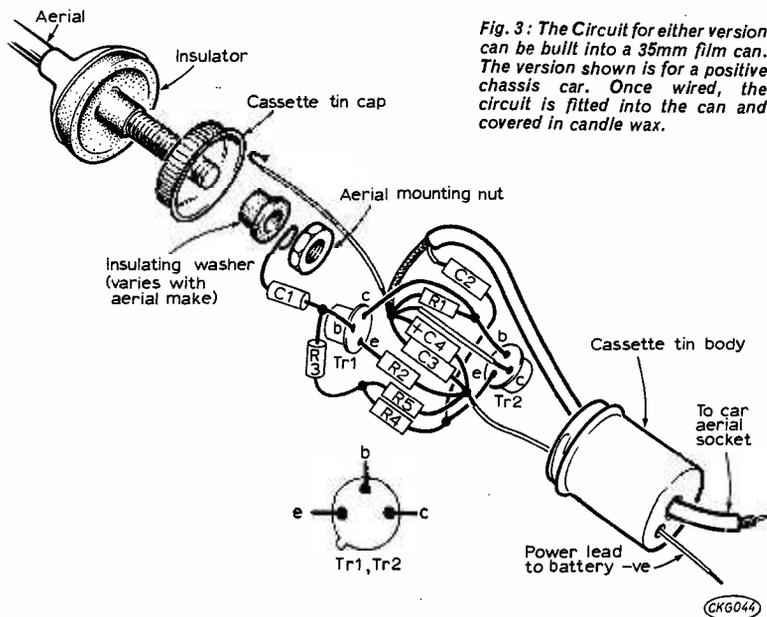


Fig. 3: The Circuit for either version can be built into a 35mm film can. The version shown is for a positive chassis car. Once wired, the circuit is fitted into the can and covered in candle wax.

## PERFORMANCE

The design of the amplifier was prompted by the author's difficulty in receiving news bulletins while driving through London, where tall steel-framed buildings prove effective Faraday screens, and in receiving British broadcasts on the continent. While the amplifier cannot cure completely non-existent signals or interference from other vehicles, the improvement is remarkable; it is now just possible to hear uninterrupted Radio 1 while driving under the Holborn Viaduct outside the PW offices (should one ever feel this to be necessary!). ■



# A DARKROOM THERMOMETER

R.A. BOTTOMLEY

THE conventional mercury or spirit filled thermometer is a thoroughly reliable instrument but, especially from the photographic worker's point of view, it is less than ideal on two counts. In the first instance the scale can be difficult to read in daylight let alone in the subdued light of the darkroom. Again, even those which incorporate a magnifying lens have to be viewed from a fairly critical angle and this can be exasperating. Secondly, the slow response time of the conventional thermometer can be an inconvenience. It was with these two points in mind that it was decided to build a thermometer incorporating a thermistor. The thermistor has an almost immediate response time and by use of the appropriate circuitry its measurement of temperature can be presented on the scale of a panel meter which is very much more easily read.

## Principle of operation

The thermistor is a resistor with a very pronounced negative temperature co-efficient. In other words its resistance decreases with increasing temperature. By measuring the value of its resistance, one can arrive at the temperature of the medium in which the thermistor is immersed. One might, as with an ordinary resistor, apply a known voltage and measure the resultant current which flows . . . the principle of the simple ohmmeter. A more precise way to measure resistance, however, is to incorporate the unknown in one arm of a Wheatstone bridge and this is the principle which has been adopted in the instrument to be described. By a suitable choice of component values an expanded scale has been achieved and this scale, as far as can be determined, is linear. The scale can be read to an accuracy of  $\pm 0.1^{\circ}\text{C}$  and, with  $20^{\circ}\text{C}$  at mid scale and plus and minus  $6^{\circ}\text{C}$  spread over the rest of the scale, it should meet most of the darkroom workers' needs.

SPECIFICATION	
Temperature range	$33^{\circ}\text{C}$ to $29^{\circ}\text{C}$
Mid-scale	$30^{\circ}\text{C}$
Reading accuracy	$\pm 1^{\circ}\text{C}$ (Hand cal. scale)
"	$\pm 0.1^{\circ}\text{C}$ (From graph)
"	(Straight line graph, microamps v. temp)
Inherent accuracy	As good as standard thermometer used for calibration
Battery consumption	12mA
Stability	Readings unaffected until battery drops below 8V
Life of battery	Very extended with average use

## Circuit description

A 9V battery (type PP6) powers the instrument. This is preferable to a mains unit since the instrument is going to be handled in proximity to a water supply. This voltage is reduced by way of two zener diodes, ZD1, ZD2, to approximately 3.3V. There are two reasons for this. By adopting a relatively low voltage to energise the bridge, self-heating effects


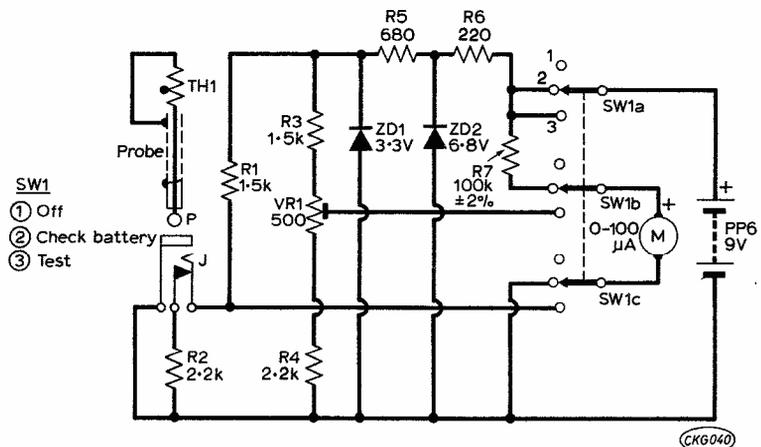


Fig. 1: The circuit of the thermometer.

of the thermistor are minimised. Additionally, the cascaded zener diodes stabilise the bridge voltage effectively so that there is no variation of the instrument's indications over the useful life of the battery. The bridge itself is formed by the components TH1, R1, R3, R4 and VR1, and it is in balance at approximately 14°C as indicated by zero deflection of the meter at this temperature. As the temperature rises, so the resistance of the thermistor falls and the pointer of the meter moves up scale accordingly. At this point it might be as well to describe the function of R2. It is only brought into circuit when the probe is disconnected. Were it not for its presence, an excessive current would pass through the meter under this condition. However, it also serves the dual purpose of reference standard whose resistance approximately equals the resistance of the thermistor at 20°C. If all is well, the pointer of the meter will always take up the same position on the scale when the probe is disconnected. A note can be kept of this reading or a "calibration" mark can be inscribed on the scale. The switch SW1 has three positions. In position "1" the instrument is off. In position "2" the meter, in conjunction with R7, is converted to a voltmeter so that one can have an indication of the state of the battery. In position "3" the meter is connected across the detector points of the bridge for temperature measurement.

### ★ components list


<b>Resistors</b>	
R1 1.5kΩ 5%	R6 500Ω 5%
R2 2.2kΩ 5%	R8 220Ω 5%
R3 1.5kΩ 5%	R7 100kΩ 2%
R4 3.3kΩ 5%	
All resistors 1/4W, high stability carbon film.	
VR1 500Ω potentiometer preset	
<b>Zener diodes</b>	
ZD1 3.3V at 5mA	ZD2 6.8V at 5mA
<b>Thermistor</b>	
TH1 Type 125 (RTT) (Available direct from I.T.T. Electronic Services, Edinburgh Way, Harlow, Essex. Price £1.30 plus 50p postage. Quote Cambridge No. 159X1132D)	
<b>Miscellaneous</b>	
Meter 5-100 μA (resistance 1,050Ω) Eagle KM65.	
Switch 2-pole, 3-way, jack plug and socket, 3.5mm.	

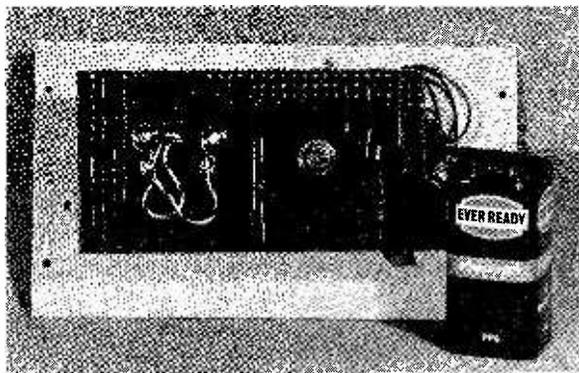

An internal view showing the Veroboard mounted on the meter terminals.
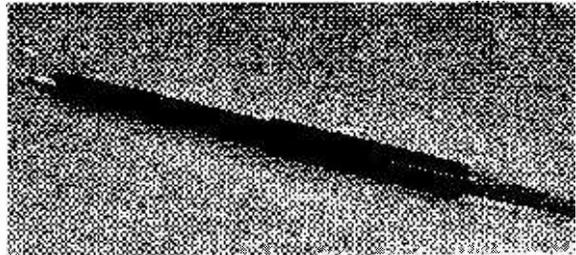
### Construction

The circuit is so simple that there is no need to elaborate upon its construction. There is absolutely nothing critical about its layout and tag strip, tag board or Veroboard (as in the prototype) can be employed. If a Veroboard layout is adopted there should scarcely be any need to stress that the copper strip should be cleared away around the meter terminals. All the components, with the exception of the switch and the jack, are mounted on the Veroboard panel which is supported by the meter terminals. The meter, switch and jack are mounted on a small aluminium panel and this panel is mounted in a small plywood box covered with leatherette. The thermistor itself is mounted into a suitable housing with the aid of Araldite. In the



The thermistor can be mounted into a test probe or a ballpoint pen case.

case of the prototype, this housing took the form of a redundant test-meter probe, turned to a smaller diameter at one end. The case of a spent ballpoint pen suggests itself as another suitable container and in this instance the thermistor tip would be protected, when not in use, by the cap of the pen.

There is nothing difficult about calibration but it should be borne in mind that the final accuracy of the instrument depends both on the care with which this is done and upon the accuracy of the thermometer which is used as standard. It is also worth noting that hot and cold water, like most dissimilar liquids, do not mix immediately. It is for this reason that it is recommended that a fairly large basin be used when calibrating and that the water be stirred thoroughly before making a reading. First the water bath should be adjusted to 20°C exactly and, when this is stabilised, VR1 should be adjusted so that the meter indicates exactly 50 μA or mid scale. Once again adjust the temperature of the water bath, this time to 15°C and when this is stable note the reading on the meter. Increase the temperature of the water bath to 25°C and, once again, note the reading. When plotted on a graph these three points will be found to lie on a straight line and the intermediate points on the scale can be determined from this graph. In the case of the prototype an increase of 1°C was represented by an increase of 8 μA, which is four divisions on the meter scale. Thus it can be seen that it is not difficult to read to 0.1°C.

One final note. If the water is not thoroughly mixed during the calibration procedure, the pointer of the meter will be seen to oscillate. This is because the thermistor is so sensitive and has such a fast response time that it indicates the variation in temperature of the water bath due to convection currents.

The instrument is so sensitive that it can even determine the slight temperature gradient between the bottom and top of a 35mm developing tank. ■

# DX reception of VHF 'LOCAL' radio

KEITH PITT

THE extension of the BBC local radio network to 20 stations has made available an additional service to about 74% of the population of England. Inevitably, in addition to many areas with no official coverage from any of the locals, there are other areas with signals available from a number of transmitters. The promised new IBA network of 60 commercial stations will add to the choice of programmes in many areas.

The BBC local radio stations are, at present, on v.h.f. mainly in the band 94.6 to 97.0MHz. The main BBC networks, Radios 2, 3 and 4, transmit almost exclusively between 88.1 and 94.5MHz.

The powers used for the local radio transmitters range from 9W for the Rotherham relay to 16.5kW for Radio London. The complete list of stations is given in Table 1. All except Blackburn, Derby and Manchester, use horizontal polarisation. These three use slant polarisation. Very little loss of quality will be observed, except in the weakest signal strength areas, if horizontal aerials are used to receive slant polarisation.

## COVERAGE

The coverage of a v.h.f. station in Band 2 is controlled by a number of factors. Like the other v.h.f. bands its signals behave rather like light waves and are obstructed by objects such as hills where the signal strength on the side away from the transmitter is much reduced. However, unlike Band 3 and u.h.f. which are used for television, a significant amount of signal is diffracted over a hill or the horizon. This then gives considerably greater coverage than might be expected from simple predictions.

One of the most important factors in determining signal strength at any point is the distance from the transmitter, since the field strength is inversely proportional to the square of the distance. Transmitter power, however, has less effect than might be expected, as the signal is proportional to the square root of the power. The height of both aerials is also of prime importance since these will determine whether or not the receiver is within the radio horizon. Signal strength diminishes quite rapidly beyond it because only diffracted waves bend over it. To a close approximation the distance of the horizon in miles is given by 1.3 times the square root of the height in feet. To approximate still further, the sum of the distances for the receiving and transmitting aerials gives the radio line of sight between them, assuming there are no major obstacles in the way.

To determine whether worthwhile results may be obtained from any given station, the following actions are necessary. First, the approximate receiving and transmitting aerial heights should be found. Secondly, using an Ordnance Survey map, measure their distance apart and determine whether any large hills get in the way. Thirdly, determine the transmitter

power. In practice, a low power station, under half a kilowatt will not be effective for more than 25-30 miles, except under very favourable conditions. Medium power, up to 10-20 kW, will often give reasonable results up to 40-50 miles. A high power station may often be receivable regularly at distances of up to 100 miles.

As a general rule, for long distance reception, the higher the receiving aerial above sea level, the greater the chance of good reception. The author lives in North London at about 350ft. above sea level and regularly has reliable reception from both Rowridge and Tacolnaston at about 80-90 miles. Of the 'local' stations, both London and Medway, which

TABLE 1 BBC LOCAL RADIO STATIONS

Station	Frequency (MHz)	Max. ERP (kW)	Aerial height (ft.) (a.s.l.)
Sheffield	95.6	0.03*	200
Durham	94.5	2.0	1400
Stoke-on-Trent	94.6	2.5	700
Leeds	94.6	0.14*	
Notttingham	94.6	0.14*	
Oxford	95.0	4.5	800
Rotherham	95.05	0.005	
Manchester	95.1	4.05	2210
Liverpool	95.2	0.185*	
London	95.3	16.5	
Humberside	95.3	4.0	
Bristol	95.4	5.0	1000
Newcastle	95.4	3.5	1400
Birmingham	95.6	3.5	1250
Brighton	95.8	0.5	550
Merseyway	95.9	5.0	
Solent	96.7	5.0†	300
Blackburn	96.4	1.55	
Derby	96.5	5.85	
Teeside	96.6	5.0	
Medway	97.0	5.5	

All transmitters except those marked \* have directional aerials. Stations marked S have slant polarisation.

are transmitted from Wrotham, are received well. (It should be noted that quoted powers are usually the maximum, but that the power radiated may be very low in some directions to avoid interference with other stations or to reduce wastage where coverage is not required.) For this reason, Medway is relatively weak, despite being within line of sight, because its power in a NW direction is very low, while London is beamed strongly in that direction.

Consistent signals are also obtained from Solent at about 85 miles, while Oxford with the same power and half the distance, is very weak. This is because nearby hills obstruct the latter but the former is quite clear for nearly 40 miles.

## AERIALS

Most BBC local radio stations radiate horizontally polarised signals. This means that a single dipole

# BI-PRE-PAK



## TELEPHONE DIALS

Standard Post Office type.  
Guaranteed in working order.

**ONLY 50p**

**8 RELAYS FOR £1**  
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

### NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V. 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

### NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mV. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts. 1½ watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

### MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



### OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.

### FULLY TESTED AND MARKED SEMICONDUCTORS

4p		6p	
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACV17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC107	0-13	2N1308-9	0-35
BC108	0-13	2N3819FET	0-45
BC109	0-14		
BF194	0-15	<b>Power Transistors</b>	
BF274	0-15	OC20	0-50
BFY50	0-20	OC23	0-30
BSY25	0-87	OC25	0-25
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-15	OC36	0-30
OC41	0-13	AD149	0-30
OC44	0-13	AU710	1-25
OC45	0-13	25034	0-25
OC71	0-13	2N3055	0-50
OC72	0-13	<b>Diodes</b>	
OC81	0-13	AAY42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9114	0-07

### F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



### BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/B, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 5p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:  
IN4001, 500+ at 4p each; 1,000+ at 3p each.  
IN4004, 500+ at 5p each; 1,000+ at 5p each.  
IN4006, 500+ at 6p each; 1,000+ at 5p each.  
IN4007, 500+ at 8p each; 1,000+ at 7p each.

### FREE CATALOGUE AND LISTS FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS & SUBSTITUTION CHARTS



### CLEARANCE LINES

#### COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

**NOW ONLY 50p each**  
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

#### INTEGRATED CIRCUITS

SL403D Audio Amp. 3-Watts	2-00	1-95	1-80
709C Linear Op. Amp.	50p	40p	35p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
PA234 1-watt Audio Amp.	1-60	90p	80p
UL914 Dual 2 I/P Gate	40p	35p	30p

#### LOW COST DUAL IN-LINE I.C. SOCKETS

14 pin type at 15p each  
16 pin type at 16p each.

#### BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:  
**B.P.I. Transistor Equivalents and Substitutes;** 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.  
**The Iliffe Radio Valve & Transistor Data Book 9th Edition;** 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.  
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....


ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

# BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344 SSO 9DF

## BETTER GET 'SET'

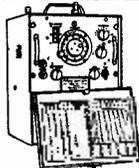

**BEST OFFER YET!**  
**FAMOUS BC.221**  
**FREQUENCY METER**  
 125 KHz-20 MHz. Complete with valves, crystal and charts. ONLY £13.50. Carr. £1.50  
 Less charts £8, carriage £1.5. Less charts & crystal £5, carriage £1.50.

**CRYSTAL CALIBRATOR**  
**No. 10** Crystal controlled heterodyne wave-meter covering 500KHz-10 MHz (Harmonics up to 30 MHz). Power required 300V. D.C. 15mA. 12V. 0-3A D.C. Test equipment for 62TM/RC. ONLY £4.25. P. & p. 50p.  
**FEW ONLY—No. 62 TM/RC** 1.5-10 MHz £17.50. Carr. £2.




**R.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12V D.C. Internal Power Supply. As New. Tested. £18.50. Carr. £1.50.

**MARCONI 801A SIGNAL GENERATOR**  
 10-310 MHz. In original transit case. £45. Carr. £2.50.
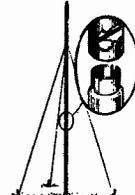
### AERIAL MAST EQUIPMENT

**20' TELESCOPIC MASTS** £37.75. Carr. £1.  
 5' 2" Extension Sections to fit bottom of above mast to increase height. £1.25 each (any number supplied).  
**35' MAST** (7-5' 2" interlocking sections) with base plate and 12 nylon guys with semi-auto tensioner. £29.50. Carr. £2.50.  
**70' MAST.** Ditto. 16 guys, block and tackle. £45. Carr. £2.75.



**AERIAL RODS** 3ft. Screw-in 1" dia. sections. Brand New, green finish. Suitable for many other uses. 10 for £2. Carr. 50p. 25 for £5. Carr. Paid.

### R.F. ANTENNA TUNER (A.T.U.)

Cylinder design 10" x 4 1/2". Precision calibrated scale. Suitable for tuning most aerials for increased signal strength. A must for serious operators for RC or TM. Full instructions. ONLY £1.75. P. & p. 25p.

### R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE

Mounted on ceramic former and feet. "Roller Coaster" design 16 G silver or silver plated wheel traversing on wire on ceramic former. Will handle considerable R.F. In original packing. As used with No. 53 Transmitter. ONLY £2.50. P. & p. 50p.

**No. 19 SET TRANSMITTER RECEIVER** Rebuilt. Complete station with PSU, Cables, Mic, Aerial, etc. £22.50. Carr. £3.

**No. 19 SET 500uA METERS** Scaled 0-600 and 0-15V. Brand new, boxed £1.25 Post Paid. (Quantity prices on request.)

**R.F. AMPLIFIER.** To increase output of No. 19 Set. ONLY £3.75. Carr. £1.25. Instruction Book for RF Amp. 37p Post Paid.

### ALL NO. 19 SPARES IN STOCK

Complete instruction book with circuits for No. 19 Equipment. 87p Post Paid.

### HEAVY DUTY BATTERIES

New in metal cases with carrying handles.  
 6V. 100/125AH. 15" x 11" x 7" £5.25. Carr. £1.25.  
 6V. 170AH. 15 1/2" x 12" x 7" £6.25. Carr. £1.25.

### LIQUID PRISMATIC COMPASSES

2" diameter £7.50. p. & p. 25p

### FAMOUS TELE 'F' FIELD TELEPHONES

Suitable for Farms, Building Sites etc. Communication up to 5 miles or more. Rugged construction, will last a lifetime. ONLY £6.25 PAIR. Carr. £1.25 (Twin telephone wire for above available—ask for price.) Many other Ex-Govt. Surplus Equipment items in stock. Receivers etc. in small quantities too numerous to mention. Enquiries invited. LIST 25p Post Paid. (Refundable against purchases over £3.) C.W.O. Carriage charges apply to Mainland only. Minimum Export Order £50.

## Surplus Electronic Trading

**DRIVERS END LANE, CODICOTE, HITCHIN, HERTS, SG4 8TP**

Hours of business: 8-5 Mon-Fri., 8-12 Sat. Telephone: Codicote 242 for appointment

## MAINS UNITS for all types of TRANSISTOR EQUIPMENT



### RUN YOUR TAPE RECORDER OFF A.C. MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.)  
**£2.50** P. & P. 15p

### 12 VOLT CAR BATTERY UNIT

Enables you to run your cassette recorder off 12V. car battery. (State 6v or 7 1/2v output, model and plug required.)  
**£2.00** P. & P. 15p

### PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v, 7 1/2v, and 9v. DC. attractive case with indicator light, mains lead output socket, plug and lead. Size 4 1/2 x 3 1/2 x 2 1/2 in.  
**£3.00** P. & P. 15p.



Extra lead with plug to fit your cassette recorder 50p. (State model and plug required.)

**MAINS UNIT FOR ALL TRANSISTOR RADIOS, ETC. USING PP3 TYPE BATTERY. (ALSO AVAILABLE FOR 6V.)**  
**£1.15** P. & P. 10p.

### MAIN UNITS

For single outputs, 6v, 9v, 12v, 18v, £2.00. For two separate outputs, 4 1/2v + 4 1/2v, 6v + 6v., 9v + 9v, £2.50. P. & P. 15p. per unit. (Please state outputs reqd.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

**R.C.S. PRODUCTS (RADIO) LTD.**  
 (Dept. P.W.), 31 Oliver Road, London, E17

## U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

**LOFT MOUNTING ARRAYS**  
 7 element 2.25. 11 element 2.75.  
 14 element 3.25. 18 element 3.75.  
**WALL MOUNTING c/w WALL ARM & BRACKET**  
 7 element 3.25. 11 element 3.75. 14 element 4.25. 18 element 4.75. **CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT.** 7 element 4.00. 11 element 4.50. 14 element 4.75. 18 element 5.25. **MAST MOUNTING arrays only.** 7 element 2.25. 11 element 2.75. 14 element 3.25. 18 element 3.75. Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 90p yd. **KING TELEBOOSTERS** from 3.75. **LABGEAR** all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7.50. State clearly channel number required on all orders. P.D. on all aerials 50p. Accs. 15p C.W.O. Min. C.O.D. charge 25p.

**BBC—ITV—FM AERIALS**  
**BBC** (band 1) Wall S/D 2.00. **LOFT** inverted 'T' 1.25. **EXTERNAL 'H'** array only 3.00. **ITV** (band 3) 5 element loft array 2.50. 7 element 3.00. **COMBINED BBC—ITV.** loft 1+5 2.75. 1+7 3.50. **WALL & CHIMNEY UNITS ALSO AVAILABLE.** Pre-amps from 3.75. **COMBINED U.H.F.—V.H.F.** aerials 1+5+9 4.00. 1+5+14 4.50. 1+7+14 5.00. **F.M. RADIO** loft S/D 1.00 3 element 3.25. 4 element 3.50. Standard coaxial pluss 90p. Coaxial cable 50p yd. Outlet box 30p. P.p. all aerials 50p. Accs. 30p. C.W.O. Min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

**CALLERS WELCOMED OPEN ALL DAY SATURDAY**

**K.V.A. ELECTRONICS**  
 40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY  
 Telephone 01-648 4884

**BELLING LEE INSULATED TERMINALS.** Red or Black, 5 amp. max. 10p pair. pp 2 1/2

**BERECOSTAT WIREWOUND RHEOSTAT.** 50 volt, 800 Ω 25 watts, 2" dia. 25p. pp 7 1/2

**FINNED ALUMINIUM HEATSINK** 9" x 1 1/2", Ready Drilled. 20p. pp 5p

**SMITHS CIRCULAR TAPE POSITION INDICATORS** Resectable, 50p. pp 5p

**G.E.C. 5 AMP 240 VOLT A.C. CIRCUIT BREAKER.** 75p. pp 10p.

**SUB MIN CROC CLIPS.** Red or Black, insulated 4p. Min. quantity, 6 pp 3p.

**GAREARD MAG TAPE DECKS:** 1 1/2ips. 50v solenoid operated brakes etc. Mains voltage motors £7.50 each, pp £1.25.

**4 1/2" PLAINAIR FANS.** Complete, capacitor, ex-equip. 2,800 r.p.m. £3.50, pp 40p.

**ELECTRIC MOTORS, HOOVER OR CROMPTON PARKINSON.** 250v. Single Phase

1 h.p. 1,440 r.p.m. £3.75 pp £1.00

1 h.p. 1,425 r.p.m. or 2,800 r.p.m. £6.75 pp £1.25

1 h.p. 1,440 r.p.m. £2.25 pp 75p

### AUDIO CONNECTORS

3 pin Din Plug . . . . . 13p each  
 5 pin Din Plug A type, B type . . . 13p "  
 2 pin Din Speaker Plug/socket . . . 10p "  
 3 pin Din Line Socket . . . . . 13p "  
 3.5mm Jack Plug Screened . . . . . 10p "  
 Standard Jack Plug . . . . . 10p "  
 Screened Standard Jack Plugs . . . 15p "  
 Stereo Jack Plug . . . . . 13p "  
 Screened Stereo Jack Plug . . . . . 15p "

**PHONO PLUGS:** Red or Black 3p each. pp on above items 3p.

**B.S.R. MINI AUTO-CHANGER.** Mono Cartridge £4.75 pp 30p.

**MAINS NEONS.** Red or Green. Size: 1" x 1 1/2" 15p, pp 3p.

**LEVER ACTION P.O.1000 TYPE SWITCHES.** Lock 4-pole changeover 15p, pp 3p.

**LOCK 2 POLE CHANGEOVER** 10p pp 3p. (ex-equip.)

### AUDIO LEADS

**SCREENED PHONO LEADS** 46" long, 15p  
 3.5 mm JACK/3.5mm JACK 7' 6" long 40p  
**5-PIN DIN A TYPE.** Approx 5' long 70p. pp above items 5p.

**PIEZO DYNAMIC MICROPHONE** 50k Ω £1.00 pp 5p.

**MULLARD SCREW TERMINAL CAPACITORS.** 4,500 Ω 64v. 7100 Ω 40v. 50p each pp 10p.

**BELLING LEE** 1.5 amp in-line rubber covered interference suppressor 25p pp 5p.

**RUBBER 3 PIN 5 AMP NON REVERSIBLE CABLE CONNECTORS** 20p pp 5p.

**FIBRE GLASS TAPE** 3" wide 50 yd. roll. 50p pp 15p.

**SOLENOIDS 12 VOLT PULL ACTION** 2" x 1" x 1" 40p pp 8p.

**STC SEALED RELAYS DOUBLE POLE CHANGEOVER** 48v 2500 Ex-equip. 15p pp 5p.

**SIEMENS MINIATURE RELAY.** Double pole changeover dust cover/base 48v 2500 50p pp 5p new.

**STC MINIATURE RELAY** 280 Ω Perspex Cover 6-15v new, 35p pp 5p.

**GARDNER'S POTTED TRANSFORMER** 0-250v Input: 18v 500m/150v 50v 150m/50p 250m/50p. Size 3" x 2 1/2" x 2 1/2", £1.00, pp 20p. Ex-equip. tested.

**TELESCOPIC AERIALS** Chromed 7" closed 35" extended 6 section ball jointed base 85p pp 3p new.

**MULLARD 4 DM 160 INDICATORS** in plastic holder/cover ex-equip. size approx. 1 1/2" x 1 1/2" x 1 1/2" 80p pp 8p.

**PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200** Diodes: 1 red relay: 10 AZ 229 zener aa, capacitor/resistors. Power supply 22v 250 mA DC. Output 240v. AC £1 pp 20p ex-equip.

**TOGGLE SWITCHES.** Single pole Double Throw ex-equip. new condition. 50p doz. pp 13p.

**PAINTON PLUG SOCKETS** Type 159 series working voltage 350v AC/DC current max. 3 amp AC/DC 7 pin plug & socket 50p pp 6p. 15 pin plug & socket £1 pp 6p. 31 WAX PLUG & SOCKET. £1.50. pp 10p.

**CASH WITH ORDER PLEASE**

## FIELD ELECTRIC LIMITED

**3 Shenley Road, Borehamwood, Herts.**  
 Adjacent Elstree Mainline Station  
 Tel: 01-953 6009.

has some directional properties and thus does not receive equally well from all directions. The maximum signal strength is obtained with the aerial at right angles to a line joining the transmitter and the receiver. An improvement in directivity and gain can be obtained by the addition of a reflector and, perhaps, one or more directors.

Figure 1 shows the dimensions of a simple Band 2 aerial. No attempt has been made to allow for mismatch at the dipole caused by the addition of two directors and a reflector. If need be, the dipole can be folded when the input impedance will then afford a reasonable match to 72Ω coaxial feeder. If the object of the exercise is to obtain as many stations as possible, then, while the additional gain is very useful, the aerial will need re-alignment towards each one. A rotary system would then be worthwhile, but a simple expedient is to use two simple dipoles at right angles with two feeder cables and to switch over to the more effective one when tuning in a station.

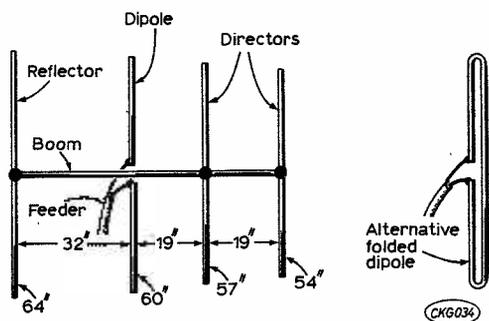


Fig. 1: A four element Yagi beam. If the dipole is folded it will provide a better match to 70Ω feeder. If constructed of metal tubing the centres of the directors and reflector may be clamped directly to the boom.

In practice, if only one aerial is possible, whether indoors or outside, it should be mounted as high as possible. Its direction should be chosen so that it gives the maximum possible pickup of the weakest of the available stations consistent with minimum loss on any of the others. The author uses two separate aerials, a four element for Solent, which still gives acceptable results on Medway and London, and a single dipole for Oxford. The latter is insufficient to reduce the interference from the adjacent Radio London. This raises the other critical point in reception of v.h.f. stations; receiver properties.

## RECEIVERS

Most commercial v.l.f. receivers can resolve clearly two adjacent stations 0.5MHz apart, but, in some cases, the spread of a local may be so great that it can cover almost a whole MHz of the spectrum, rendering adjacent stations very difficult to find and resolve. On one portable the author could just separate Oxford on 95MHz from London on 95.3MHz and listen to the former, and yet the same set produced some traces of London on Solent on 96.1MHz. Similarly, other sets spread Wrotham Radio 4 on 93.5MHz from just over 93 to 94MHz. BBC 4 Oxford on 93.9MHz cannot be separated from Wrotham on any of the four sets the author has tried. This

spread rather limits the usefulness of some of the weaker stations.

Reception is also made worse by "spurious signals" which sometimes appear at places on the dial where there is no true signal, although this is more a function of the quality of the receiver. Quite often portables give better results using their own aerial, carefully positioned for maximum signal than when using a high outside aerial. This is because spurious signals appear to be produced in many sets much more strongly when an external aerial is used.

In conclusion, there will be many areas where satisfactory results will be obtained from two or more "local" radio stations. Unless they are very strong, a good aerial system will probably be required to give the best results. It will, however, happen that in some cases spread within the set may spoil the reception of weaker signals close to a local.

# TELEVISION

## MARCH ISSUE

### RENOVATING THE RENTALS

A large number of ex-rental sets are now appearing on the second-hand market and with judicious renovation can be made to give useful service for some time—particularly for the booming market in second sets. Many of these sets exhibit common stock faults and in this new series we shall be passing on tips and advice to help get—and keep—these sets going.

### LINE TIMEBASES OF THE FUTURE

One of the developments that is likely to be with us before long is the slimline colour set, i.e. one fitted with a 110° shadowmask tube. The main technical difficulty concerns the line scanning and this month we shall be examining an interesting development—a thyristor line output stage—that has been evolved for this application.

### COLOUR RECEIVER INSIGHT

A great deal of uncommon circuitry is to be found in colour chassis—the sort of thing you've not come across before and can spend hours puzzling over. So we've decided to take the lid off, so to speak, and explain in detail just what those apparent circuit mazes do. Starting with the ITT-KB CVC5 chassis.

### SERVICING TELEVISION RECEIVERS

The next chassis to be covered in this popular feature is the Bush TV103/TV105 series.

### PLUS ALL THE REGULAR FEATURES

**Advance News:** Starting in the April issue, the TELEVISION Colour Receiver for the Constructor.

**ON SALE FEBRUARY 21**

# TAKE 20

JULIAN ANDERSON

**P**ART of the fun of electronics is in being able to 'amaze and mystify' members of the family and friends with little tricks. Those unfamiliar with the mysteries of electronics invariably assume that anyone who has tackled even the simplest crystal set is a true genius and, even when they see how few parts are employed, refuse to believe that 'that's all there is to it'. When they can't see the components that make an item tick they are even more impressed—let us not shatter their illusions, let us allow the uninitiated to marvel at our unquestionable brilliance!

Our project this month is purely for fun; to my knowledge it has no practical use whatsoever but it should amuse and it does fall within our budget of £1.

Using the constructional layout shown none of the component leads need be cut short and this will allow the components to be employed later for some more practical purpose.

The title of magic candle is self explanatory: the wick and flame are replaced by a small light bulb; when a lighted match or cigarette lighter is moved near it the bulb lights up and remains alight until "snuffed" by turning it off.

Apart from the battery, only four components are used: a light dependent resistor (LDR), a thyristor (SCR), a potentiometer (VR1) and the bulb itself. At normal light levels the resistance of the LDR will be several hundred ohms (though this varies enormously with the specimen and the actual light level) and with VR1 at maximum setting there will not be sufficient current flowing in the gate circuit to trigger the SCR. However, if VR1 is reduced in value and the light level on the LDR increases there will be an increase in current, the SCR will turn on and apply the battery volts across the bulb. Because of the action of an SCR, even when the triggering current falls away completely, current will still be passed in the anode-cathode circuit.

VR1 acts as the sensitivity control; when it is set to minimum resistance and with a sensitive LDR, even quite low light levels will trigger the circuit. At maximum resistance the bulb will probably not light at all.

Ideally one would use both a battery and a bulb of the same voltage but SCRs don't seem to work well at voltages much below 9V and 9V bulbs with low current consumption are not widely available. If one can be obtained (note that the current should be no higher than 60mA) the circuit is exactly as shown. However 6V, 40mA bulbs are available and cheap but to avoid blowing it a 68Ω resistor should be wired in series with the bulb at the point marked both in the circuit and the constructional layout.

The circuit is best built to look something like a wax candle. A cardboard tube, such as aluminium foil is supplied on, is suitable. The battery sits on the bottom to give stability with VR1 just above this. For ease of wiring it is best to wire up VR1 first with three long leads, two to come out of the top and one that goes down to the battery and then to fit it into a hole cut out of the side.

## No. 34 MAGIC CANDLE

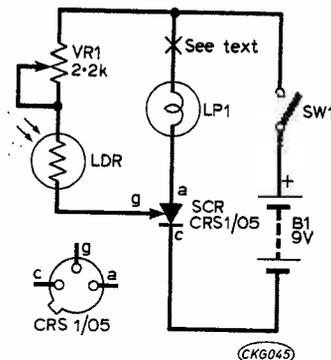


Fig. 1: Circuit of the 'Magic Candle'.

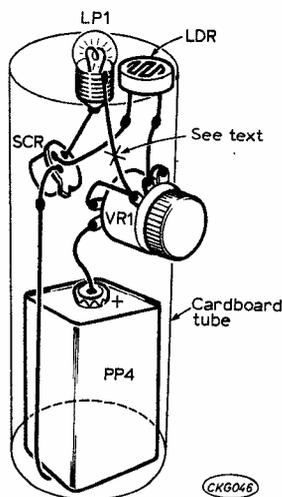


Fig. 2: The components can all be mounted inside a cardboard tube.

### ★ components list

VR1 2.2kΩ lin. pot with switch .. ..	24p
LDR Light dependent resistor .. ..	43p
SCR CRS1/05 Thyristor, 50V, 1A .. ..	23p
LP1 6V, 40mA bulb, see text .. ..	5p
	<hr/>
	95p

Prices are those recently advertised in *Practical Wireless* and may have changed. No allowance is made for minimum order costs or for postage and packing; these points should be checked carefully before ordering.


A stout card disc, cut to go over the top, can then be fitted with the bulb and the LDR which should be lightly glued under a small hole about ¼in. in diameter. This should be as near to the bulb as possible. The SCR can be either left floating as shown or it can be glued to the top cardboard disc. A long wire should be fitted to the cathode which is fed down the tube to the battery negative terminal. Once working the tube and top may be painted white to give the appearance of a candle. ■

## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £10.50. P. & P. 25p.

## DE LUXE STEREO AMPLIFIER

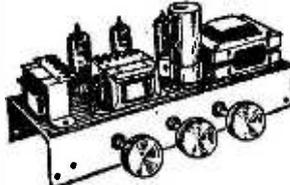

A.C. mains 200-240 v. U a 1 n g heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (3 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £8.92 P. & P. 45p.

**SPECIAL PURCHASE OF MANUFACTURERS SURPLUS!** All Transistor F.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. FM RF Transistor oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional AFC connection. Built on printed circuit panel and fully screened. Extremely stable over range 88-108Mc/s. Brand new and pre-aligned. Size 2 1/2" x 1 1/2" x 2 1/4". For 6v D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER. Only £2.95 post free. Connection details supplied.

## SPECIAL PURCHASE!

**BRAND NEW FM MULTIPLEK STEREO DECODERS.** Manufactured by PHILIPS. Size 2" x 3 1/2" x 1". All transistor 24v. at 6mA. Supplied pre-aligned with full circuit diagram and connection details. £4 each. Post Free.

**INPUT MATCHING TRANSFORMER.** Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/2" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes of pick up from low to high impedance or vice versa. 75p each. Post Free.

**BLACK ANODISED 16g. ALUMINIUM HEAT SINKS.** For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 85p each. P. & P. 5p.

**HIGH GRADE COPPER LAMINATE BOARDS.** 8 x 6 x 1/16 in. FIVE for 50p. P. & P. 13p.

**TELESCOPIC AERIALS WITH SWIVEL JOINT.** Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 22 1/2in. approx. Maximum diameter 1/4in. 25p each. P. & P. 5p.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. Half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £1.75 P. & P. 30p.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240v. Sec. 0-9-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.33. P. & P. 30p. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 65p. P. & P. 13p.

**4 AMP BATTERY CHARGER TRANSFORMER.** Brand new. For 6 or 12v. 240v. Primary. Secondary volts r.m.s. off load 10v and 16.5v. Overall size approx. 2 1/2" x 2 1/2" x 3". Weight 3lbs. Limited number at £1.35. P. & P. 35p.

**4-SPEED RECORD PLAYER BARGAINS**  
Mains models. All brand new in maker's packing.  
**LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £6.97 Carr. 50p. With stereo cartridge £7.97 Carr. 50p.

**LATEST GARRARD MODEL 8. S.A.E. for latest Prices!**  
**PRECISION ENGINEERED PLINTHS**  
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Reasonably free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Choice of Black leatherette or Teak grain finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). PRICE £45.50. P. & P. 60p.

**LATEST ACOS GP81/180** mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.50 P. & P. 8p.

**SONOTONE STEREO COMPATIBLE STEREO CARTRIDGE** T/O stylus Diamond Stereo LP and Sapphire 78 ONLY £2.50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

**LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. £1.68 P. & P. 10p.

**LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.50 P. & P. 10p.

**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 2 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £8.75 P. & P. 40p.

**DELUXE QUALITY PORTABLE R/P CABINET MK II.** Uncut motor board size 14 1/2 x 12in. clearance 2in. below. High above. Will take any amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE £4.75. P. & P. 50p.

## SPECIAL OFFER!

### HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Uynair front. Size 16 1/2" high x 10 1/2" wide x 3 1/2" deep. Fitter with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

**OUR PRICE £8.40 Carr. 65p**  
Cabinet Available Separately £4.50 Carr. 60p  
Also available with EM.I. 13" x 8" bass speaker with parastic tweeter £8.50 Carr. 65p

### LOUDSPEAKER BARGAINS

5in. 3 ohm 80p. P. & P. 15p. 7 x 4in. 3 ohm £1.05. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.68. P. & P. 20p. E.M.I. 13" x 8in. 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 30p. E.M.I. 12 x 8in. 3, 8 or 15 ohm with two built in tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13 x 8in. twin cone (parastic tweeter) 8 ohm £2.25. P. & P. 30p.

**BRAND NEW.** 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by a well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly £5.50. Guitar magnet. 25w. £6.50, 35w. £8.50. P. & P. 35p. E.M.I. 3 1/2in. 8-16 ohms. H.F. TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 95p each. P. & P. 13p.

12in. "EA" TWIN CONE LOUSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm £2.20. P. & P. 30p.

85 ohm SPEAKERS 3in. only 65p P. & P. 15p.

**"POLY PLANAR" WAFER TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKERS.** Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

**VYNAIR & BEXINE SPEAKERS & CABINET FABRICS** ap. 64 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min 1 yd.). S.A.E. for samples.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoon earmuffs. Wired and fitted with standard stereo 1/4in jack plug. Frequency response 30-16,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £2.95. P. & P. 15p.


**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE £1.05. P. & P. 8p

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 85p. P. & P. 15p.

**CENTRE ZERO MINIATURE MOVING COIL METER.** 100uA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.
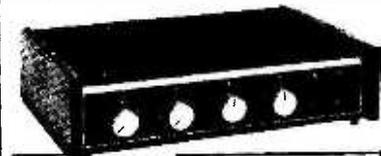
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




**NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for use speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. 10  $\pm$  12dB. Treble cut approx. 10  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

**PRICES**  
AMPLIFIER KIT . . . . . £10.50 P. & P. 15p  
POWER PACK KIT . . . . . £3.00 P. & P. 30p  
CABINET . . . . . £3.00 P. & P. 30p  
(Post Free if all units purchased at same time)

Full after sales service  
Also available ready built and tested £20.50. Post Free.  
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, turn record etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

### 3-VALVE AUDIO AMPLIFIER HA34 MK II

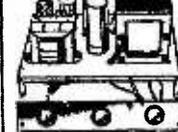


Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

**ESL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.88. P. & P. 40p.

**HARVERSON'S SUPER MONO AMPLIFIER**  
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.  
FEW ONLY. BARGAIN PRICE £2.75 P. & P.

**10/14 WATT HI-FI AMPLIFIER KIT**  
A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.

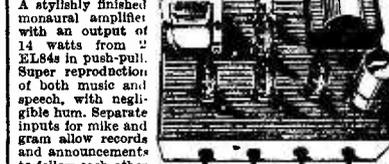Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-out 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7.97 P. & P. 55p.



**HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES**  
A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

Open 9-5.30 Monday to Saturday  
Early closing Wed. 1 p.m.  
A few minutes from South Wimbledon Tube Station.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985


SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

# NEW FROM LINEAR TWO STEREO AMPLIFIERS

Representing really exceptional value IN ELEGANT TEAK FINISH CASES!

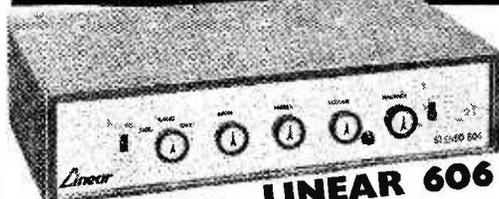

**LINEAR 606**  
6+6 WATTS  
Recommended Retail Price  
**£22.50**

0-200-230-250v. 50 Hz A.C. mains operation. Inputs for magnetic or Ceramic Pickup, Tape or Radio Tuner.

**TECHNICAL DETAILS**  
Bass Control  $\pm 12$  dB at 40 Hz.  
Treble Control  $\pm 12$  dB at 14 KHz.  
Sensitivities Mag. P.U. 3.5 m.v. into 47K ohm R.I.A.A. Ceramic P.U. 35 m.v. into 100K ohm. Tape Amp. 100 m.v. into 100K. Radio Tuner 400 m.v. into 400K ohm. Crosstalk 53 dB.  
Hum and Noise -75 dB min. vol. -85 dB max. vol.  
Total Harmonic Distortion 0.1% at 1 watt into 15 ohms.  
Output (per channel) 6.5 watts I.H.F.M.

- ★ Individual Bass and Treble Controls.
- ★ Frequency Response  $\pm 1\frac{1}{2}$  dB 20 Hz to 65 KHz.
- ★ Outputs for Speaker impedances between 3 and 15 ohms.
- ★ Stereo/Mono Switch.
- ★ Input Selector Switch.
- ★ Solid State Circuitry.
- ★ Attractive silver finished metal facia and matching control knobs.

- ★ A modestly priced solid state unit.
- ★ The Silver Facia with black lettering enhanced by matching control knobs, provides a high standard of appearance.
- ★ Suitable for crystal or ceramic Gram. Pick-up cartridges, and Radio input.
- ★ A wide range of tone variation is provided by the separate Bass and Treble 'lift' and 'cut' controls.
- ★ A selector switch permits instantaneous selection of Gram. or Radio.
- ★ Speaker impedances between 3 and 15 ohms are suitable.

**TECHNICAL DETAILS**  
Frequency Range 20 Hz to 20 KHz  
Output (per channel) 5 watts I.H.F.M.  
Bass Control  $\pm 12$  dB at 60 Hz.  
Treble Control  $\pm 14$  dB. at 14 KHz.



**LINEAR 505** 5+5 WATTS  
Recommended Retail Price  
**£17.50**

0-200-250v. 50 Hz A.C. mains operation

PRINTED CIRCUIT CONSTRUCTION EMPLOYING 10 TRANSISTORS

ALL LINEAR AMPLIFIERS GUARANTEED FOR 12 MONTHS

Wholesale and Retail enquiries to the Manufacturers  
**LINEAR PRODUCTS LTD.,** Electron Works, Armley, Leeds LS12 3SA Tel. 630126

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for £1-02. DAF96, DF96, DK96, DL96, 4 for £1-48.

1R5	28	30C1	28	LY802	28	EL000	62	PCL82	82	UABC80	82
1S5	22	30C15	58	EABC80	32	EM80	38	PCL83	57	UAF42	50
1T4	18	30C17	76	EAF42	50	EM81	38	PCL84	84	UBC41	52
3S4	28	30C18	81	EB41	40	EM84	82	PCL85	38	UBP89	34
3V4	37	30C3	64	EB91	10	EM87	34	PCL86	38	UBR89	38
5U4G	31	30FL1	61	EBC33	40	EY31	33	PCL88	65	UCC84	32
5Y4G	35	30FL12	69	EBC41	54	EY36	39	PCL800	75	UCC85	32
5Y3GT	38	30FL14	68	EBC90	32	EZ40	48	PEN A4	77	UCF80	38
5Z4G	35	30L1	29	EBF80	32	EZ41	43	PEN36C	70	UCI42	58
6Y80L2	54	30L15	57	EBF89	32	EZ50	39	PFL200	82	UCH81	32
6AL5	11	30L17	87	ECC81	17	EZ81	23	PL36	49	UCL82	32
6AM6	13	30P4	57	ECC82	20	GZ30	34	PL81	44	UCL83	55
6AQ5	22	30P12	72	ECC83	35	GZ32	40	PL81A	47	UF41	56
6AT6	20	30P19	57	ECC85	34	GZ34	48	PL82	81	UF89	30
6AU6	20	30PL1	60	ECC804	54	KT41	77	PL83	38	UL41	57
6BA6	20	30PL13	80	ECP80	31	KT81	55	PL84	30	UL44	£1-00
6BE6	21	30PL14	85	ECP82	28	KT86	78	PL500	85	UL84	30
6BJ6	41	35L6GT	45	ECH35	55	LN319	63	PL604	63	UM84	22
6BW7	52	35W4	25	EOH42	50	LN329	78	PM84	33	UY41	42
6FL4	40	35Z4GT	26	ECH81	38	LN336	63	PX25	25	UY85	25
6F23	68	50T	45	ECH83	40	N75	87	PY22	55	VP4B	77
6F25	58	60G3	62	ECH84	35	P81	40	PY33	55	W77	43
6J7G	24	AC/VP3	77	ECL80	30	PABC30	34	PY81	25	Z77	22
6K7G	12	B349	65	ECL82	31	PC86	47	PY82	25	Transistors	
6K8G	17	B729	62	ECL86	35	PC88	47	PY83	28	AC107	17
6Q7G	35	COH35	67	EP39	38	PC86	42	PY88	38	AC127	18
6SN7GT	30	CY31	36	EF41	40	PC87	59	PY800	34	AD149	37
6V6G	23	DAF91	22	EF50	28	PC800	31	PY801	34	AF115	20
6V8GT	28	DAF96	28	EF85	28	PCC84	39	R19	30	AF116	20
6X4	23	DF33	38	EF86	30	PCC85	25	R20	56	AF117	20
6X5GT	28	DF91	18	EP89	28	PCC88	40	U25	64	AF118	28
10P13	58	DF96	36	EF91	13	PCC89	45	U26	56	AF125	17
12AT7	17	DH77	20	EF92	30	PC189	46	U47	64	AF127	17
12AU6	20	DK32	33	EF98	35	PCC805	58	U49	55	OC28	25
12AU7	20	DK91	28	EF183	28	PCF80	28	U50	36	OC44	18
12AX7	22	DK92	38	EF184	31	PCF82	31	U52	31	OC45	18
19BG6G	80	DL35	40	EL33	55	PCF800	68	U191	59	OC72	18
20F3	67	DL92	26	EL34	45	PCF801	28	U193	42	OC75	18
20P3	77	DL94	37	EL41	54	PCF803	40	U251	64	OC81	18
20P4	92	DL96	38	EL84	28	PCF805	61	U301	38	OC82	18
25L6GT	19	DY88	24	EL90	26	PCF806	58	U329	66	OC82D	18
25U4GT	57	DY87	24	EL95	33	PCF808	68	U801	30	OC170	28

### READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.  
Post and packing on 1 valve 6p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 5p extra.

### MW/LW TRANSISTOR RADIO

Complete set of parts for this MW/LW Transistor Radio. Originally sold by world-famous company as a set for more than £17. Coverage 192-555m-4-1070-1870m. 9 volt 6 transistor superhet using 3 AF117 in RF and IF stages powered by a two stage AF amplifier using 3 x AC128. Output approx. 500mW. Also works off car-aerial. Full instruction book 12pp free with parts. Red only, ply case, rexine covered. Requires PP7 battery, price 22p extra. 3 1/2 in high-quality speaker. Price £8 plus 40p P. & P. Size 8 1/2" x 6" x 8".

### STEREO AMPLIFIER Type SHV—2 x 3 watts

Fully built. Separate vol., base and treble controls each channel; 12 x 4 1/2 x 6 1/2 in high. EZ40, ECP89, 2 x ECL86 valves. O.P. trans. for 3-ohm speakers. Double wound mains trans. Suitable for crystal, magn. cartridge, tuner, etc. Fitted mono-stereo switch. 200-250V a.c. mains. £7.25, 50p P. & P.

### MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short. Gram., 200-250V A.C. Ferrite aerial. Chassis 13 x 7 x 1 1/2 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81, EF99, EBC81, EL84, EZ30. Price £10-52. (37p p. & p.) Output trans. for 3-ohm speaker

### MAINS TRANSFORMERS (240-250V input)

Postage in brackets  
6.3V at 2 1/2A, 40p (15p).  
250V at 50mA and 6.3V at 1 1/2A, 50p (20p).  
22V at 1A, 6.3V at 2A and 250V at 50mA, 75p (25p).  
90V at 20mA and 1.4V at 250mA, 50p (15p).  
Deduct 10 per cent from total bill for more than one transformer.

Miniature A.M. transistor tuning gang. 250 + 250pf; 2 x 60a. fixings, size 1 1/2 x 1 1/2 x 1 1/2 in.; gearing 3:1 to 1/4 in dia. moulded bush. Plastic dust cover; Plessey.  
25p post pd., less 10% for 6.

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants  
(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240  
CLOSED WEDNESDAY. S.A.E. for enquiries please.



Books reviewed on this page are normally obtainable through any retail bookshop. In this instance, the information printed in heavy type should be quoted.

### **HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES**

Published by Babani Press  
78 pages, 7 × 4in. Price: 40p.

ONE hardly needs to review a book of this type—the title itself (and the modest price) is enough to make the mouth water. Such a book has long been needed and congratulations to the publishers for introducing it.

Personally I have never met anyone who has known more than a handful of the transistor types available and as far as substitutes are concerned no one has worked out the perfect way of presenting these. This handbook has, however, made a brave attempt (and largely successful one) to give equivalents of transistors in a thoroughly practical way. Equivalents, by the way, only refers to parameters and ignores encapsulation, a sensible thing to do as it opens the field considerably.

About 3,000 types have their equivalents given and in most cases several alternatives are shown; take for instance the OC71, an old fashioned but very well known transistor, here 15 equivalents are shown and this is not untypical.

One of the best points (and if all the other virtues were missing this only would make the book a good buy) is the inclusion of a mass of Japanese types. There must be hundreds of thousands of small transistor radios imported from the Far East which have been written off because a dud transistor is unidentifiable. I have never come across a better list of these types.

Altogether an excellent handbook and, for those who need to find equivalents, indispensable. **H.W.M.**

### **PUBLIC ADDRESS HANDBOOK**

By Vivian Capel  
Published by Fountain Press,  
46 Chancery Lane, London. WC2.  
208 pages, 8 × 5in. Price: £3.00.

VIVA Vivian! This contribution to the literature of audio is like a light in darkness. With the growing world of discos, clubs and semi-pro 'do's' at the local Church Hall, some guidance is necessary for the well-meaning PA operator. Until now, his only recourse was to very specialist works that told him a lot about the acoustics of the City Hall in Walamazoo but little about hooking up an ailing 10W amplifier to the vicar's home-made loudspeakers.

Public Address Handbook is very soundly based on the author's practical experience. Anyone who has attempted PA will know that the most unexpected problems can crop up. Mr. Capel has worked in small halls and large, on private jamborees and public demonstrations and passes on to us the benefit of his know-how.

There is little theoretical depth. The author argues that you would not be reading the handbook if you

had not at least a glimmering of the background and the acumen to seek out more in the appropriate places. But he takes full cognisance of our probable ignorance where public address is concerned and guides us through the mysteries of microphones and mixers, amplifiers and loudspeakers—always from a practical point of view.

The author is a practising musician and this becomes apparent when one reads his Chapter 10, 'Live Music.' His advice is firsthand and authentic. Practical systems are described in another chapter; nine working hookups based on requirements that vary between the small hall and the football stadium, taking in a factory canteen on the way.

Still more practical, the final two chapters deal with fault-finding and setting-up. I was tickled pink by Mr. Capel's advice on page 80: 'Never panic, even though the programme may be held up while you try to rectify matters!' There speaks the voice of experience as it does, indeed, throughout this excellent and rare book on a little-known and infrequently explored subject. For amateur and professional both, this public address handbook is to be recommended. **H.W.H.**

### **GUIDE TO PRINTED CIRCUITS**


By Gordon J. King  
Published by Fountain Press  
148 pages, 8½ × 5½in. Price: £2.50

AN excellent and timely book, written, as the author says, "with the enthusiastic amateur, experimenter and the radio service apprentice and technician in mind."

The six chapters begin with the reasons for the introduction of the printed circuit board and the early problems involved and continues with the design methods and manufacture of boards in the electronic industry. For the reviewer the chapter on "rolling one's own" printed circuit boards was the most interesting with its detailed advice and guidance. Interest was maintained at a high level in the following chapter which covers the alternative systems to the pcb, such as Veroboard, Cir-Kit and S-DeC. Many readers will find the information on converting a circuit diagram into a finished circuit board of the greatest use.

A book such as this would not be complete without detailed information on the methods of servicing pcb's. The author, who has accumulated many years of servicing expertise, has been able to incorporate some of that experience into Chapter Five. Other useful guidance covers the field of soldering irons and guns, solders and soldering aids and the few other accessories which will enable the amateur to turn out a professional pcb.

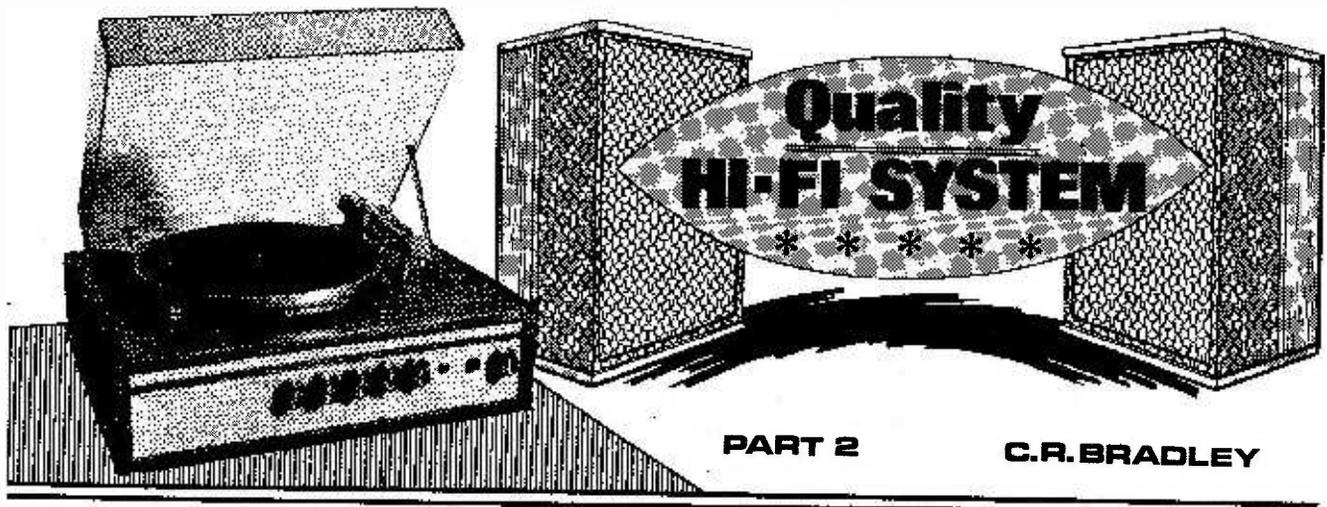The book is well written with many photographs and line drawings. £2.50 is little enough to pay for such a mine of information. **A.E.D.**



*Continued from the February issue*

The circuit of the plinth is shown in Fig. 6. This comprises the power supply, the left and right power amplifier modules and the left and right preamplifiers. The preamplifiers are separately constructed on pieces of Veroboard which plug into two 24-way edge connectors on the back of the control panel. In return for their small extra cost, the use of edge connectors has some important advantages.

First, construction is simplified since construction of each preamplifier and the fairly complicated wiring around the controls can be separately completed and checked, with improved accessibility in both cases. Secondly, either preamplifier board can be removed in seconds for fault finding; it is very helpful when tracing a fault to be able to swap the preamplifiers and observe whether the fault changes channel. Thirdly, all the small-signal carrying wires are kept as short as possible and run close to the aluminium front panel so that fewer wires have to be screened to avoid instability, hum pickup and crosstalk problems. The latter is especially important since the equipment uses silicon transistors throughout which individually have responses extending far beyond audio into radio frequencies.

### Preamplifier Circuit

This will be fully described as it contains some unusual features. The BC109 transistor was an obvious choice for all stages since it has a very low noise factor and is commendably cheap. Non-branded BC109's may not be as good.

The low level signal is received by the equalisation stage Tr1 and Tr2. These are connected as a d.c. coupled pair in which Tr1 runs at a low collector current of  $75\mu\text{A}$  to minimise the electrical noise introduced at this vital point. D.C. stabilisation is performed by R8 since if Tr1 collector current should rise, Tr2 base voltage drops, Tr2 emitter voltage follows and Tr1 base bias is therefore reduced. R8 also provides some signal feedback but the main signal feedback path is from Tr2 collector through C3 and the components selected by S1b to Tr1 emit-

ter. For radio tuner input the feedback through R11 provides flat frequency response and 150mV sensitivity at the input. For magnetic cartridge input R13/C5/C6 provide frequency conscious feedback to obtain the standard RIAA disc playback response—see Fig. 8. Almost any desired input sensitivity and impedance can be made available at the AUXILIARY position of S1 by choosing component values from Table 1. Clearly there is scope for arranging any desired selection of inputs by S1 from the values given, although if planning to introduce more complex switching it is important to bear in mind that this area of circuit is where hum pickup and crosstalk are most likely to occur. For the purpose of the components list it is assumed that the AUXILIARY position is fitted with components for 300mV input sensitivity, useful for, say, the low level outputs from a stereo tape recorder.

TABLE 1  
Component values for different AUXILIARY input characteristics

R1	Rx	Sensitivity	Input Impedance	Suitable for:
470k $\Omega$	0	300mV	500k $\Omega$	Tape recorder
0	62k $\Omega$	3.5mV	22k $\Omega$	Dynamic mic.
1M $\Omega$	62k $\Omega$	300mV	1M $\Omega$	Crystal mic. or pickup

Virtually all of the preamplifier gain is provided by Tr1 and Tr2 which are followed by the stereo volume control VR1. For this a linear track component is chosen rather than the logarithmic type usually used in this position. This has the advantage that the two ganged sections will be better matched than in a cheap logarithmic control so channel balance will be maintained at different volume settings. The preset gain controls VR2 in each channel are a means of overcoming the usual disadvantage of linear volume controls i.e. most of the subjective volume range being compressed into the first few degrees of rotation. The preset controls are intended to be set to give the maximum likely listening

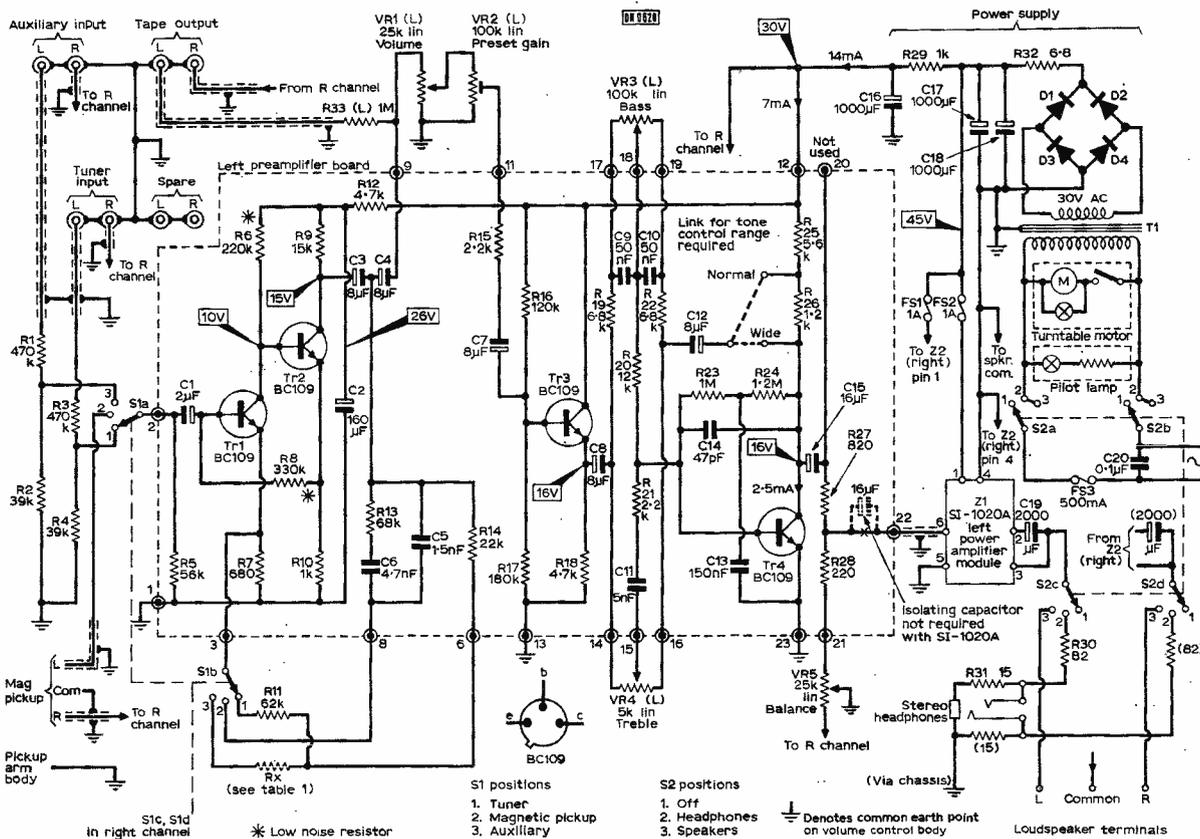


Fig. 6: Circuit of plinth unit. Preamplifier and power amplifier for left channel only are shown, plus balance control VR5. Some components in right channel speaker output shown for clarity. Right channel is identical. All voltages are positive with respect to chassis.

volume with the manual control at maximum, so that its whole range can be utilised. They also allow any difference in the gains of the left and right channels, due to component tolerances, to be compensated so that the manual balance control normally rests midway.

### Emitter Follower Buffer

In most preamplifier designs a Baxandall tone control stage follows immediately after the equalisation stage. Here however an extra emitter follower stage Tr3 is used as a buffer between the equalisation stage Tr1/Tr2 and the tone control stage Tr4. This reduces distortion since the high input impedance of the emitter follower minimises the loading (via the volume controls) on Tr2, and the low output impedance ensures a constant-voltage drive to the varying load presented by the tone controls.

### Tone Controls

Although the Baxandall tone control circuit, with its familiar bass and treble boost and cut characteristic shown in Fig. 9, is used with minor variation in almost all modern high fidelity equipment, its operation is seldom explained and is not obvious. It is best

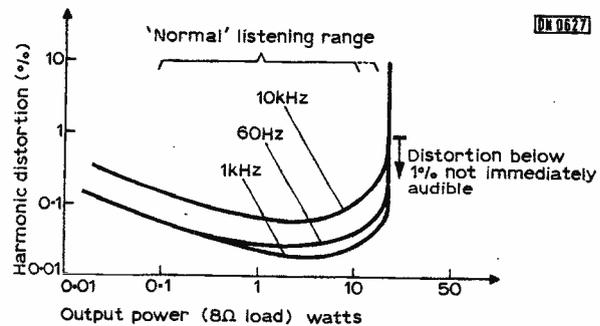


Fig. 7: Distortion curves for Sanken SI-1020A amplifier module, taken from manufacturer's data sheet

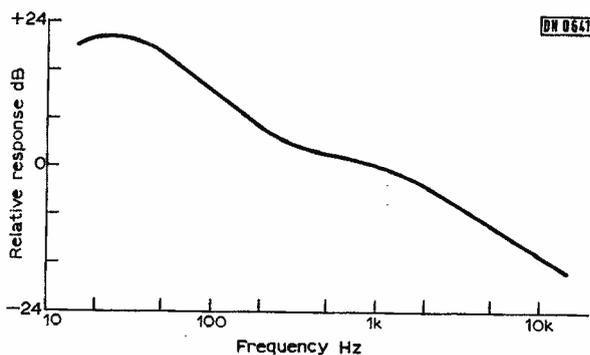


Fig. 8: On modern L.P. recordings high frequencies are boosted to a standard (RIAA) specification to overcome surface noise. The output of a magnetic pickup must be passed through a preamplifier whose response shown above is a mirror image of the recording response i.e. boost at low frequencies, to regain the original sound.

understood by separately considering how the circuit appears at high and low frequencies.

Resistors present the same impedance to signals of all frequencies whereas the impedance of capacitors decreases with rising frequency. Hence at very high frequencies C9/C10/C11 are virtually short circuits and the circuit reduces to Fig. 10a. Conversely at very low frequencies the same capacitors are virtually open circuits and the circuit reduces to Fig. 10b. In both these simplified circuits the components which are ineffective are dotted.

Now both the simplified circuits are just elaborations of Fig. 10c in which a transistor base is fed from the slider of a potentiometer connected between input and output. Assuming the transistor itself has sufficiently high gain, the stage gain is  $R_b$  (which

simple relation is the root of all operational amplifier theory). This confirms what is fairly obvious, that the gain is high when the slider is at the input

DN 0643

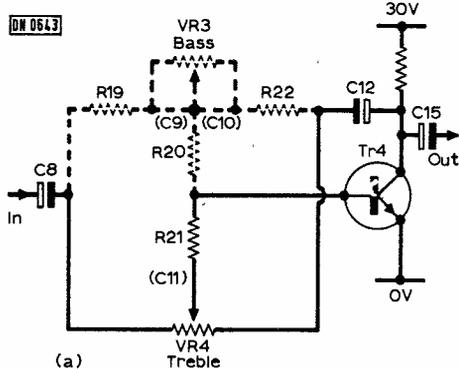


Fig. 10a: Active parts of tone control circuit at very high audio frequencies

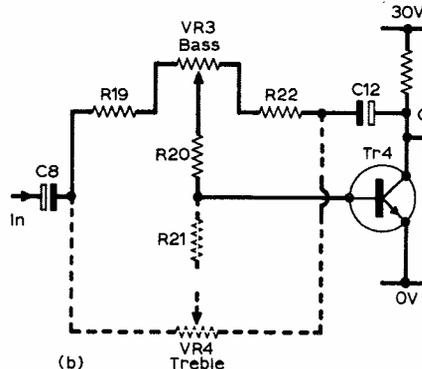


Fig. 10b: Active parts of tone control at very low audio frequencies

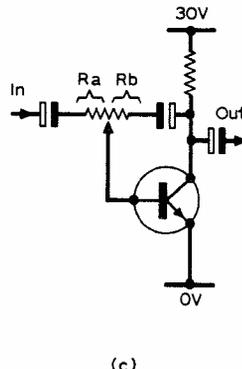


Fig. 10c: Simplified operation of both Figs 10a and 10b.

end of the track and drops as it moves to the right due to increasing negative feedback from the output. Thus in Figs. 10a and 10b the active potentiometer simply acts as a gain control at the frequency concerned while the dotted control has no effect. The arrows across the sliders indicate the direction of clockwise rotation and boost. At other than very high or low frequencies the assumptions made about the action of the capacitors become less true and it is only a matter of choosing component values to make the controls progressively effective over desired frequency ranges.

Figs. 10 do not show the base bias arrangement for Tr4 which is a bleed via R23/R24 from its collector with decoupling by C13 to prevent signal feedback by this route. Stability at all tone control settings is ensured by top-cut capacitor C14.

C12 prevents d.c. flowing in the tone controls and is large enough for its impedance to be negligible at all audio frequencies. It is normally connected to the junction of R25 and R26. It can alternatively be connected directly to Tr4 collector whereupon the range of the tone controls becomes wider than the specification since they have more negative feedback to "play" with. For normal listening however there is no need for great extremes of tone control.

The signal at Tr4 collector is taken to a spare pin on the edge connector in case a mono-stereo switch is required. This would just link pin 20 on the left and right preamplifiers for mono operation. But for

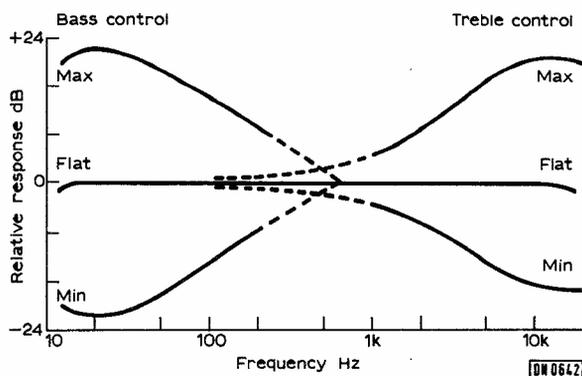


Fig. 9: Tone control response with C12 linked to NORMAL. Curves are dotted over mid-frequency range where both Bass and Treble controls have some effect.

record playing at least, where a mono record reproduces through both channels anyway, such a switch seems superfluous. If occasionally one wishes to feed an external mono signal (e.g. from an a.m. radio tuner) into both channels, this can be done by making up a suitable linking adaptor to plug into the auxiliary input sockets.

The left and right preamplifier outputs are taken from a resistor divider whose mid-point is the earthed slider of the Balance control. In anticipation that this preamplifier may be used with other power amplifiers there is provision in the board layout for an isolating capacitor at the output. This is not needed (though does no harm) with the Sanken amplifiers specified which contain their own input blocking capacitors.

## Power Amplifiers Z1, Z2

The Sanken SI-1020A monolithic power amplifier has already been described in "IC of the Month" and its internal (and inaccessible) circuit is the conventional quasi-complementary Class AB push-pull arrangement. The convenience of its packaging is far more remarkable since its metal case can be bolted directly to a heatsink without any electrical isolation. This i.c. was possibly overshadowed at its introduction by its 50 watt sister (SI-1050) but its excellent distortion claims are the reason for choosing it for the system.

Fig. 6 shows an unusual arrangement at the loudspeaker outputs which solves two problems common to high power push-pull amplifiers. Firstly one may inadvertently overload stereo headphones with resulting distress to ears and/or headphones. Secondly there is the familiar thump from each speaker when the amplifier is switched on, caused by the output capacitor (C19) charging through the speaker. This may or may not be damaging to the speakers but one is certainly better off without it. Accordingly the on/off switch S2 is arranged to pass through a HEADPHONES position between OFF and SPEAKERS. If it is switched through this intermediate position not too fast, C19 will have charged up via R30 and R31 before being connected to its speaker, so there will be no thump. These resistors also attenuate the headphone signal level to give a reasonable range of volume.

### Power Supply


The simple unstabilised power supply in Fig. 6 delivers 45V via separate fuses FS1/FS2 to the power amplifiers, and a well smoothed common 30V supply to the preamplifier boards. The mains input is also fused. A reservoir capacity of 2000 $\mu$ F is required and can be made up from two 1000 $\mu$ F capacitors in parallel as shown (C17, C18) or a single component used if available. In either case the capacitor(s) should be good quality components intended for power supply use since there is a hefty 100Hz ripple current from the bridge rectifier D1-4. The current surge as the capacitors charge up at switch-on is limited to a safe value by R32 which should not be omitted.

The mains input is switched by S2a/b to the power supply transformer T1, the turntable (which has its own switch and pilot lamp) and to a neon pilot lamp on the front panel. C20 may be of some use in suppressing r.f. interference from the mains; it is most important that no suppressor capacitor is connected between mains live and the chassis since this would make exposed metal parts live if ever the mains earth connection were broken.
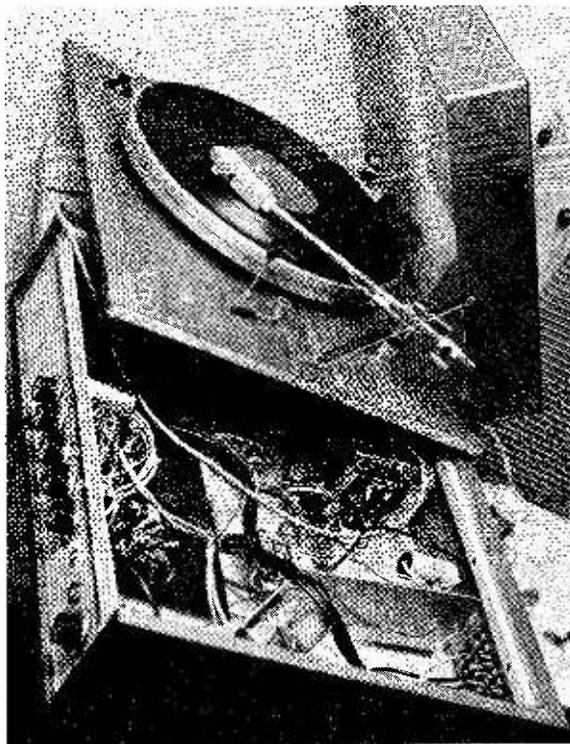
### Turntable, Arm and Pickup

The choice of these three can be left to the constructor since any good quality equipment can be used. Comparative judgments on magnetic cartridges especially are rather subjective.

The author's equipment illustrated uses a Connoisseur Craftsman turntable (very simply but soundly made), Goldring L75 pickup arm and Eagle LC07 moving magnet cartridge. The latter is a fairly recent Japanese product which the author regards as a "best buy" at about £7 since its performance on a test record is comparable to, say, a Goldring G800E at several pounds more. Tracking is at 1 $\frac{1}{2}$ gm, which can be set accurately on the Goldring arm without a gauge. Readers might well find the Connoisseur BD1 "do-it-yourself" turntable kit a good buy for the system. For economy one of the better BSR or Garrard players would give fair results but a cheap autochanger should certainly not be used since



Photograph shows inside of assembled plinth

the amount of wow and flutter would be unacceptable.

### Plinth Construction

The carpentry is straightforward, the cabinet being made up from five pieces of  $\frac{1}{2}$ in. chipboard fixed by countersunk screws to  $\frac{1}{2}$ in. square corner battens—see Fig. 11. A rectangular aperture is cut in the rear board for the rear panel. The turntable mounting board is cut out to suit the unit and arm chosen after having made sure everything will fit under the Goldring perspex lid. The space available here is about 17 $\frac{1}{4}$ in. wide  $\times$  13 $\frac{1}{2}$ in. deep  $\times$  2 $\frac{3}{4}$ in. high and it was only barely possible to fit in the author's units, the Craftsman turntable having to be positioned with the motor at rear left. It is not essential for the turntable board to be screwed down to the battens on which it rests, so there need be no screw heads visible after all exposed wood surfaces have been veneered. For access to the electronics the turntable board is simply lifted clear.

Two eyelet screws can be bent to serve as hinges for the rear of the perspex cover and screwed to the turntable board as shown in Fig. 11. A small wood wedge is glued to the board to support the prop-up arm which is part of the lid.

The front panel is an aluminium sheet cut as shown in Fig. 12a. A length of L-shaped aluminium girder is used to hold the two preamplifier edge connectors behind the front panel (or some other support can be arranged) and has tabs ready for

# ★ components list

**PLINTH**

**Resistors:**  
 All 10% 1W carbon unless otherwise specified

†R1 470kΩ	†R17 180kΩ
†R2 39kΩ	†R18 4.7kΩ
†R3 470kΩ	†R19 6.8kΩ
†R4 39kΩ	†R20 12kΩ
†R5 56kΩ	†R21 2.2kΩ
†R6 220kΩ 1W 5% high stability	†R22 6.8kΩ
†R7 680Ω	†R23 1MΩ
†R8 390kΩ 1W 5% high stability	†R24 1.2MΩ
†R9 15kΩ	†R25 5.0kΩ
†R10 1kΩ	†R26 1.2kΩ
†R11 62kΩ	†R27 820Ω
†R12 4.7kΩ	†R28 220Ω
†R13 68kΩ	†R29 1kΩ
†R14 22kΩ	†R30 82Ω 1W carbon
†R15 2.2kΩ	†R31 15Ω
†R16 129kΩ	R32 6.8Ω 5W wirewound
VR1 25kΩ + 25kΩ linear double-ganged carbon potentiometer	†R33 1MΩ
†VR2 100kΩ linear miniature skeleton preset potentiometer	
VR3 100kΩ + 100kΩ linear double-ganged carbon potentiometer	
VR4 5kΩ + 5kΩ linear double-ganged carbon potentiometer	
VR5 25kΩ linear carbon potentiometer	

**Capacitors:**

†C1 2μF 8V electrolytic
†C2 100μF 25V electrolytic
†C3 8μF 15V electrolytic
†C4 8μF 15V electrolytic
†C5 1.5nF ceramic or polyester
†C6 4.7nF ceramic or polyester
†C7 8μF 15V electrolytic
†C8 8μF 15V electrolytic
†C9 50 (or 47) nF ceramic
†C10 50 (or 47) nF ceramic
†C11 5 (or 4.7) nF ceramic or polyester
†C12 8μF 15V electrolytic
†C13 350nF ceramic or metallised film
†C14 47nF ceramic
†C15 12.5 (or 10) μF 25V electrolytic
C16 1000μF 30V electrolytic
C17 1000μF 50V electrolytic
C18 1000μF 50V electrolytic
†C19 2000μF 25V electrolytic
C20 0.1μF 500V paper tubular

**Semiconductors:**  
 1Tr1, 1Tr2, 1Tr3, 1Tr4 BC109  
 D1, D2, D3, D4 100 PIV 2A silicon diodes  
 Z1, Z2 Sanken SL1020A  
 (Photo Controls Ltd.,  
 Randalls Road,  
 Leatherhead, Surrey)  
 † indicates one needed for each channel.

**Switches:**  
 S1 4P 3W rotary S2 4P 3W rotary

**Fuses:**  
 FS1, FS2 1/4in. 1A (or 500MA—see text)  
 FS3 1/4in. 500MA  
 † fuseholders to suit

**Sockets:**  
 Stereo jack socket (Eagle SS34)  
 8 phono sockets (or 4 stereo pairs)

**Transformer:**  
 T1 Mains primary 200/250V a.c., secondary 30V-2A  
 e.g. Douglas MT3AT

**Miscellaneous:** Veroboard, 2 24-way Veroboard edge connectors (0.1in. pitch), knobs, mains pilot neon, screened cable, wood, aluminium, etc.

**ENCLOSURE (components for each channel)**

**Resistors:**  
 R1, R2, R3, R4 10kΩ 1W carbon (not wirewound)

**Switch:**  
 S1 2P 5W rotary

**Crossover:**  
 Eagle CN28 B12

**Woofer:**  
 Baker Major 30

**Tweeter:**  
 Eagle MHT10 B1

**Miscellaneous:** Hardboard, wood, sand, fret, fibre eggbox, carpet felt, knobs, screw terminals (2) aluminium panel, etc.

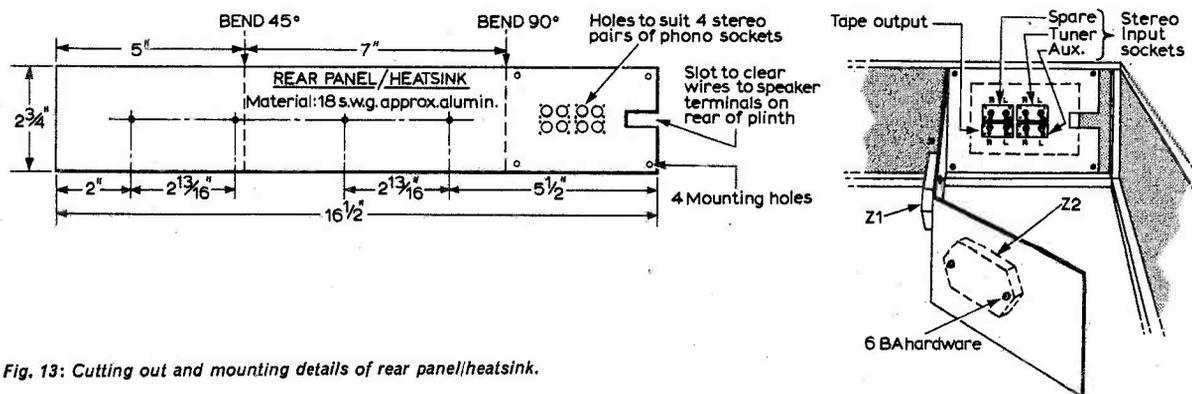


Fig. 13: Cutting out and mounting details of rear panel/heatsink.

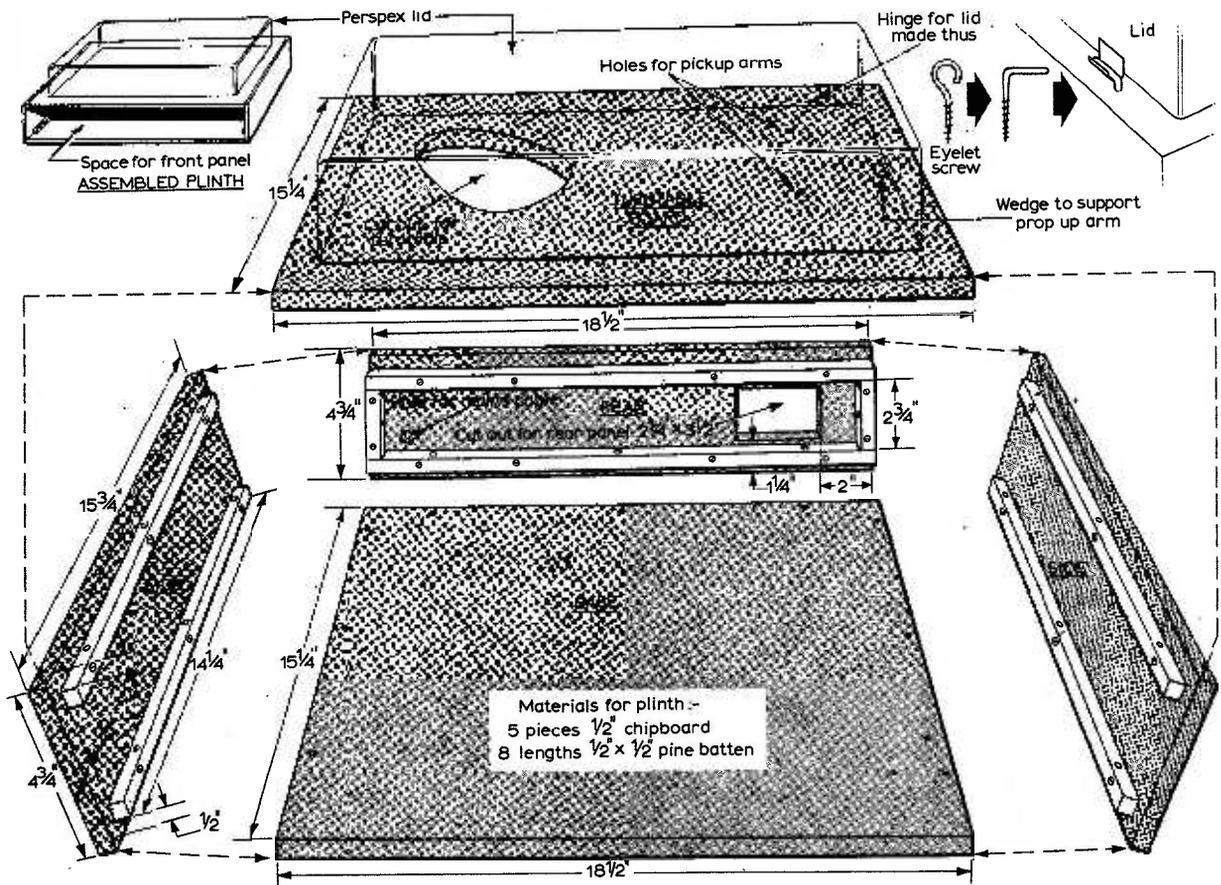


Fig. 11: Construction of plinth

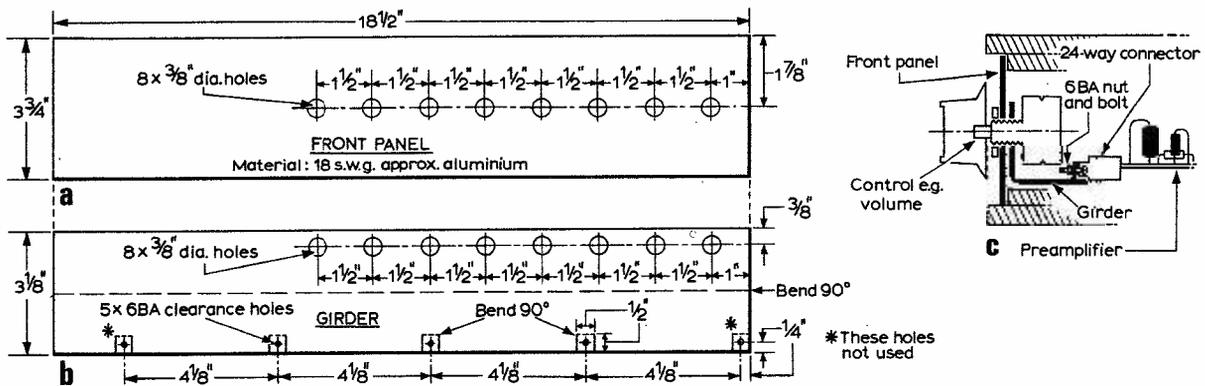


Fig. 12(a): Front panel (front view). Fig. 12(b): Girder. Fig. 12(c): Cross section of front panel and girder showing method of fixing connectors.

mounting two more edge connectors in case of future needs—see Fig. 12b and c. The girder is held to the front panel by the controls so no screw heads need show at the front. The front panel assembly should fit snugly enough in its slightly recessed position to need no fixing to the cabinet.

A second aluminium sheet forms the heatsink for Z1 and Z2 and also the rear panel carrying four stereo pairs of phono sockets—see Fig. 13. It is fixed to the cabinet by four screws from the inside. The amplifiers should be bolted tightly to the aluminium making sure they make contact over the whole of their bases. A thermally conductive grease can be used to improve the heat transfer but this is not essential for normal listening use.


#### NOTE

On page 905 of the February issue, reference is made to strip "S in Fig. 1." This should have referred to Fig. 2.

To the materials list on page 907, the following should be added to the FRAME: 4 off 16 in.  $\times$   $\frac{7}{8}$  in.  $\times$   $\frac{7}{8}$  in. pine.

The construction details of the inner sheets on page 907 show screw holes in the vertical corner edges of the hardboard—these should be ignored. It would be impossible to use wood screws in this position and they are in fact unnecessary.

**TO BE CONTINUED**

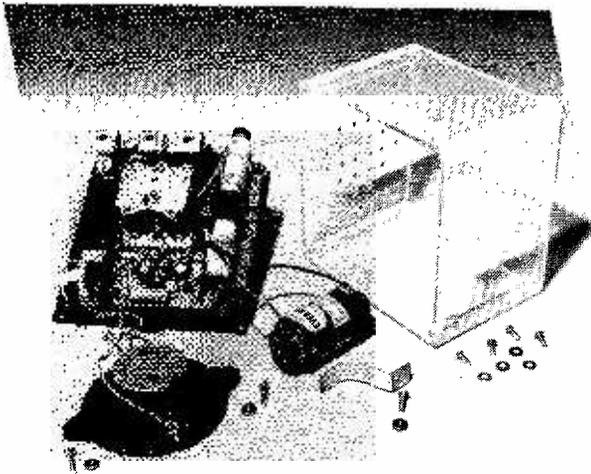

# The **pw** Cube Radio

## 7 Transistor Superheterodyne

R.F. GR

**T**HIS is an attractive 7-transistor receiver of straightforward construction, tuning long and medium waves. The receiver is assembled as a complete working unit on a single piece of Vero-board (except for the loudspeaker) and actual building is simplified by using a small, ready-made audio amplifier module. Thus only the mixer and i.f. amplifier are built from separate components.

### CIRCUIT

Fig. 1 is the circuit, and a brief description should be helpful to beginners.

**Ferrite Aerial.** The ferrite rod has medium wave section L1 and long wave section L2. Switch S1 shorts out the l.w. section for m.w. reception. VC1 tunes the aerial together with trimmer TC1. Trimmer TC3 is for l.w. trimming. A coupling winding on L1 and tapping on L2 applies the signal to Tr1 base via C1. Tr1 is an OC44 mixer/oscillator.

**Oscillator Coil L3.** This is tuned by VC2, with

trimmer TC2. Capacitor C4 provides "tracking" so that the oscillator circuit always tunes 470kHz higher in frequency than the aerial circuit. With S1 in the l.w. position C3 and TC4 are across the oscillator winding for long wave reception.

**Intermediate Frequency Amplifier.** The 470kHz output of Tr1 passes to the first intermediate frequency transformer IFT1. Signals pass to the first i.f. amplifier Tr2 an AF117, then from IFT2 to Tr3, another AF117. The three IFTs are tuned to 470kHz by means of adjustable cores.

**Emitter Detector.** The OC71 Tr4 demodulates the output of IFT3 and amplified audio signals appear at the collector and are taken via C11 to the volume control VR1.

**Automatic Gain Control.** Strong signals increase Tr4 collector current causing an increased voltage drop across R10. The base potential of Tr2 thus becomes more positive, the change in voltage being applied via R6. As a result, amplification provided by Tr2 is reduced when strong signals are present,


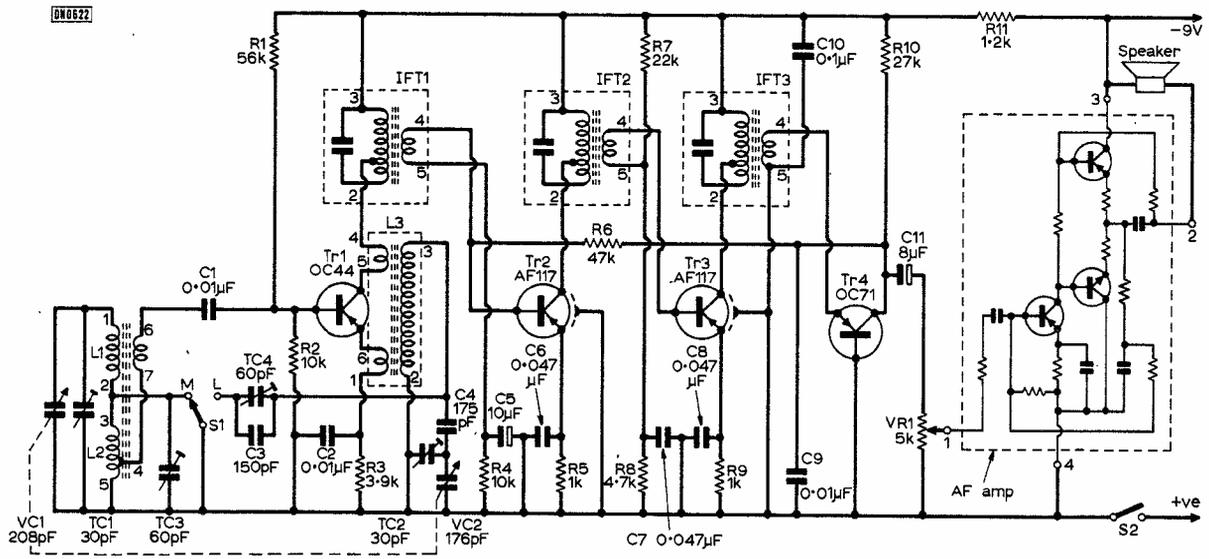


Fig. 1: Circuit of the Cube Radio. The audio amplifier is obtained as a module, the circuit being given here for reference purposes only.

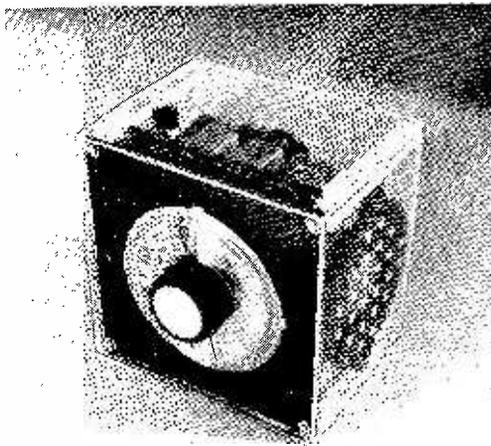

and the output of the i.f. amplifier is relatively constant, despite changes in signal level.

**Audio Section.** The slider of VR1 is taken to pin 1 of the a.f. module which is a small separate unit, mounted on the receiver board, and having only four external connections. The module contains a driver/amplifier, followed by a pair of transistors in a complementary single-ended push-pull circuit. This drives a 40 ohm or similar miniature speaker, 2<sup>1</sup>/<sub>2</sub>in in diameter.

### CIRCUIT BOARD

The plain Veroboard is 3<sup>7</sup>/<sub>8</sub> × 3<sup>3</sup>/<sub>8</sub>in. to fit inside the 4 × 4in. case. It is cut to clear the corner strips and speaker as in Fig. 2.

Holes are drilled or enlarged to match the pins and screening can tags of L3 and the IFT's, noting that L3 will be fitted in the way which results in pins located as in Fig. 2.

Holes are also drilled for TC3 and TC4, the rod

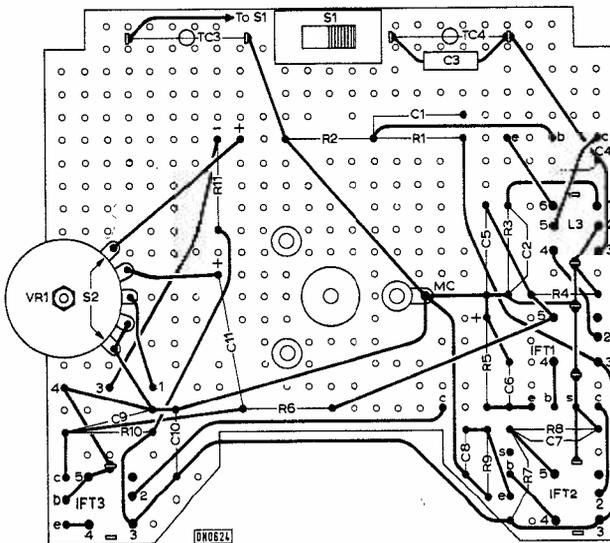


Fig. 2 : Wiring details of the underside of the Veroboard panel on which the receiver is constructed.

mounting and 6BA bolts holding the a.f. amplifier. A clearance hole is needed for VC1/2, and three holes which match up with the tapped holes in the front of the capacitor frame.

In many places resistor ends and other leads are soldered to Vero pins inserted in the board. These are most easily inserted with the correct tool, which resembles a small screwdriver with a hole, so that when a pin is pushed in it projects equally each side of the board. With Tr2, Tr3 and Tr4 it is more convenient to put the wire ends through the holes, anchoring only the collector of Tr3 at a pin.

When wiring is complete, the Veroboard is secured to a 4 × 4in. panel of 1/16in. black polished paxolin with about 7/16in. space between the two, to clear wiring, pins and VR1. VC1/2 is secured with 4BA bolts or studding which can project about 1/16in. on the capacitor side of the board. Longer bolts will damage the capacitor plates. Another way is to secure the capacitor with short bolts, with washers under their heads, if required. Panel and board are then drilled with matching holes to take three 6BA bolts. These are countersunk at the panel, and have extra lock nuts, so that panel and board will be held about 7/16in. apart. The positions of the bolts does not matter, provided they clear resistors, etc., since their heads will be covered by the metal dial.

### FERRITE AERIAL

As the ferrite rod normally supplied is too long for the case, it was snapped off at about 3<sup>1</sup>/<sub>2</sub>in. by securing it in a vice and giving the rod a sharp tap.

L1 is placed so that the base winding 6-7 is towards the middle of the rod. Thin sleeving was put on all leads. Lead 1, Fig. 3, goes to the larger section (front) of the capacitor, VC1/2. Lead 2 runs to the wavechange switch S1.

L2 is put on the rod so that its turns are in the same direction as those of L1, which can be seen by looking at the windings. If L2 is reversed, i.v. alignment is impossible, and the winding should be taken off the rod, turned round, and replaced. The

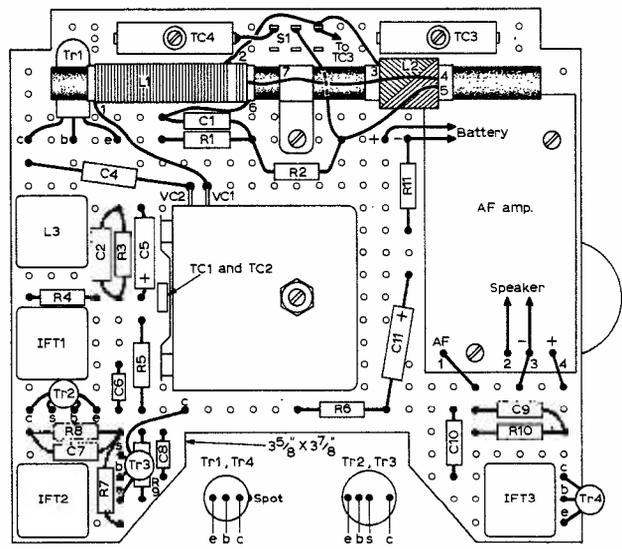


Fig. 3 : Topside of board showing location of the major components. Ensure that IFT's and L3 are correctly orientated to give pin positions shown in Fig. 2.

outer lead 3 of L2 joins lead 2 at the switch. The lead 5 taken to positive line must be that which is adjacent to tap 4, which is not at the centre of the winding.

Those lead ends which are single strand wire can be cut, if necessary, carefully scraped, and soldered. But the finely stranded (Litz) wire is difficult to deal with, so the ready tinned ends should be left. Excess length can be taken round the rod in the same direction as the winding.

The rod is mounted by means of a strip of plastic material clamped round it, with a 3/4 in. 6BA bolt and spacer, or extra nuts, so that it easily clears TC3, TC4, etc. It is as well to leave fitting of the rod until last.

## WIRING


Switch S1 is mounted by passing its tags through holes in the board. The tag MC is securely held at one of the fixing screws of VC1/2.

Place transistors so that their leads come as in Fig. 3, with sleeving on the wires. Put suitable lengths of sleeving on the wires which project, bend these over, and solder to the IFT's etc. as in Fig. 2.

The screening can tags of the IFT's and L3 must be connected to the positive line, as in Fig. 2. It proves helpful to use red sleeving on this circuit, black on negative circuits, and some other colour on other wiring; 26s.w.g. or similar tinned copper wire and small sleeving will be convenient.

## ★ components list

<b>Resistors:</b>		
R1 56kΩ	R5 1kΩ	R9 1kΩ
R2 10kΩ	R6 47kΩ	R10 27kΩ
R3 3.9kΩ	R7 22kΩ	R11 1.2kΩ
R4 10kΩ	R8 4.7kΩ	
All 1/2W 10%		
VR1 5kΩ miniature pot. with switch (S2)		
<b>Capacitors</b>		
C1 0.01μF	C7 0.047μF	
C2 0.01μF	C8 0.047μF	
C3 150pF 2% SM	C9 0.01μF	
C4 175pF 2% SM	C10 0.1μF	
C5 10μF	C11 8μF	
C6 0.047μF		
Minimum working voltage, 9V		
TC1/2 part of VC1/2		
TC3 50pF compression trimmer		
TC4 50pF compression trimmer		
VC1/2 208 + 175pF, slow motion, with trimmers (Jackson)		
<b>Semiconductors</b>		
Tr1 OC44	Tr3 AF117	
Tr2 AF117	Tr4 OC71	
<b>Inductors</b>		
L1/2 Ferrite rod aerial (Denco MW/LW5FR)		
L3 Oscillator coil (Denco TOC1)		
IFT1 IF Transformer (Denco IFT13)		
IFT2 IF Transformer (Denco IFT13)		
IFT3 IF Transformer (Denco IFT14)		
<b>Miscellaneous</b>		
Switch S1, two-way slide switch. Audio amplifier 125mW (Newmarket PC1). Dial and knob (Home Radio DL64 and KN64). Plain veroboard 0.15in. matrix, 3 1/2 × 3 1/2 in. Speaker, 2 1/2 in. diameter, 30 to 80 ohms.		

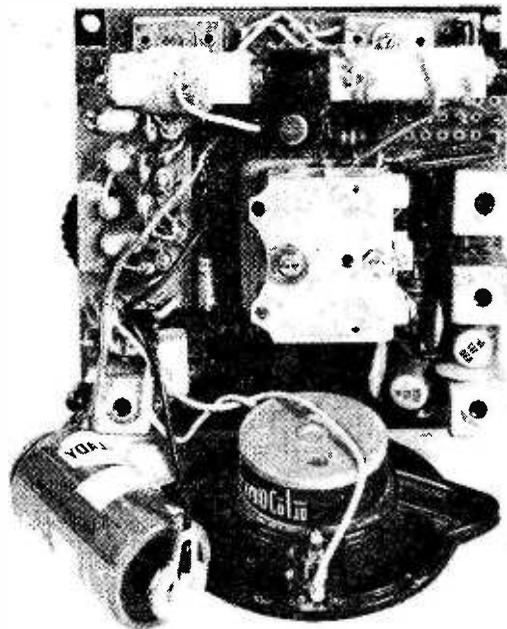

A general view of the completed receiver. It may be tested and aligned in this form before finally fitting it into its case.

Volume control VR1 is fixed with a small bolt and connected as in Fig. 2. Solder the correct clips to red and black flex for the battery.

## AF AMPLIFIER

Connections shown in Fig. 3 are when looking at the amplifier from the components side. Thread thin wires down through the small holes, and solder to the foil below.

Mount the amplifier with bolts, using a few washers to avoid contact with the bolt holding VR1. Take lead 1 through the board to VR1 slider (centre tag). Twist leads 2 and 3 together, leaving these long enough to reach the speaker. Take a second lead 3 through the board to battery negative, Fig. 2. Lead 4 goes to the positive line.

Leads 2 and 3 should be soldered to the speaker so that the receiver can be tested before adding the panel.

## IF ALIGNMENT

Use a Denco TT5 or other correct tool for adjusting the IFT's and L3 since a screwdriver or wedge-shaped blade may easily break the cores.

If a signal generator is to hand, set it to 470kHz, connect it to C1, and adjust the IFT cores for best volume, keeping this low by reducing generator input.

If no generator is available, alignment may be made with any signal tuned in, following by more careful adjustment with a weak signal, if necessary. Do not use strong signals, with VR1 turned towards minimum volume, because the a.g.c. action tends to make adjustment of the cores seem flat with no sharp peak.

When IF alignment is finished, these cores need not be touched again.

## MW ALIGNMENT

The core of L3 has a considerable influence on band coverage. With S1 at m.w., tune in a station with VC1/2 near maximum capacity and move L1 on the rod for maximum. If dial readings are badly in error, rotate the core of L3, following the signal with VC1/2, to correct this and re-adjust L1 on the rod.

Move to the h.f. end of the band (VC1/2 nearly fully open) and set TC2 for a suitable dial indication, peaking TC1 for maximum volume.

These adjustments should be repeated a few times until no further improvement is obtained. If a generator is available use it at suitable frequencies instead of selecting actual stations.

## LW ALIGNMENT

With S1 at l.w., tune in any transmission, and move L2 on the rod for best volume. Subsequently, it will be found that oscillator coverage can be adjusted with TC4, so that the setting of TC4 and core position of L3 governs band coverage. Then TC3 is peaked for best results towards the h.f. end of the band, and L2 is moved on the rod at the l.f. end of the band.

If any slight adjustment is made to the core of L3, m.w. alignment will have to be repeated. Otherwise merely touch up m.w. adjustments, after completing l.w. alignment.

## CABINET

The cabinet is made of clear Perspex for its novelty effect. The bottom is 4×4in. and  $\frac{1}{8}$ in. thick while the sides are 4×3in. and  $\frac{1}{8}$ in. thick. Front and back are also  $\frac{1}{8}$ in. thick, but are  $4\frac{1}{8}$ ×3in. to overlap the sides. The front is drilled to take the speaker with a grid of holes over the cone area.


The pieces should be accurately cut and the edges smoothed with a file. After cementing together a strip  $\frac{1}{4}$ × $\frac{1}{4}$ in. and 2 $\frac{3}{4}$ in. long is cemented in each corner to strengthen the box. The strips were tapped 6BA at the top, to take four bolts which pass through the receiver panel, which is slightly inset in the case top. The Perspex could be drilled for self-tapping screws.

A clip is made and fixed to the case bottom with a countersunk bolt, to hold the battery. The speaker leads are long enough to allow the receiver to be lifted out leaving the speaker in the case. A slot is filed to clear the knob of the volume control. Another slot is required for the wave-change switch.
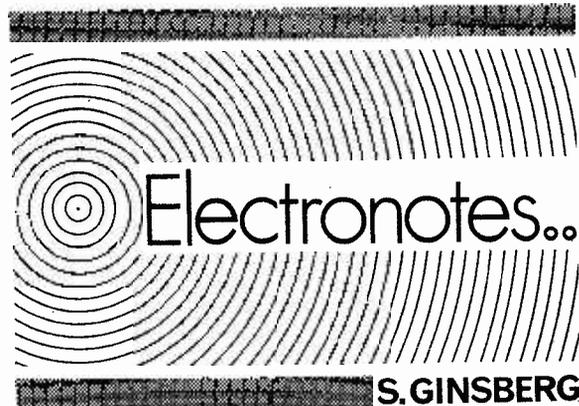
## DIAL

The dial listed has four metal lugs, which pass through slots in the panel. The slots can be made by drilling two or three small holes very closely together and finishing with a very small flat file.

The panel is fixed in the manner described earlier and the dial then put on the lugs being turned over behind the panel. The tuning indicator fitted was a disc of  $\frac{1}{8}$ in. Perspex, with a black line each side to travel over the m.w. and l.w. scales, and fixed to a brass bush which is locked on the capacitor spindle with a set-screw. A Perspex disc is readily cut with an adjustable tank cutter and the bush made by sawing through a  $\frac{1}{4}$ in. brass shaft coupling. An alternative is to use a stout wire pointer. ■



**H**AVE you ever thought just how those complex integrated circuits are made? These innocent looking little slabs of plastic with some 16 pins sticking out of the side are now common to most shops selling components for the constructor.

One of the most difficult parts of the whole process is aligning masks. A slice of silicon is taken and coated with a photoresist. A photographic mask is then laid carefully over the slice and an exposure made. The resultant image is transferred to the slice which, in turn is then taken for processing.

After this first processing, the slice is given the same treatment again; another coating and exposure, then further processing. There may be several printing exposures made during the manufacture of the slice which can quite easily contain thousands of individual tiny semiconductors.

As can be appreciated, because individual devices on the chip are so very very tiny, it is absolutely imperative that during the printing of the individual masks, these must be aligned very, very precisely.

A normal method is to have an operative peering at the chip and the relevant mask through a high powered microscope and the mask guided into position by the operative. While this is successful it does take time since, if the mask is not aligned accurately, several hundred integrated circuits on the slice may be ruined.

A British company has now developed a machine which will align the mask and chip automatically. The secret is the printing of two minute crosses between the pattern for the circuit required. These crosses have their members made up of shaded lines. The machine uses these to align subsequent masks to within 10 micro-inches. Circuit patterns down to 0.0001in. can be printed. The entire printing process from when the operative puts the new slice into the holder to the time it is ejected is only 25 seconds.

A further advantage of this British invention is that the masks are not in direct contact with the slice. Thus there is no abrasion on either slice or mask and the life of the masks, which are very expensive indeed to produce, is considerably prolonged.


Once set up, the machine needs no further attention during the run. The slices are lifted automatically in and out of the photo-electric system by precision mechanical arms. The machine is also self-checking and will stop and/or throw up warning lights if anything goes wrong. For example, if there were no slice in the input receptacle the machine would stop. If a slice were to be damaged the machine would stop and flash a light.

Last month the first part of this article described the case, power supply, display units and initial testing. This second part concludes the article.
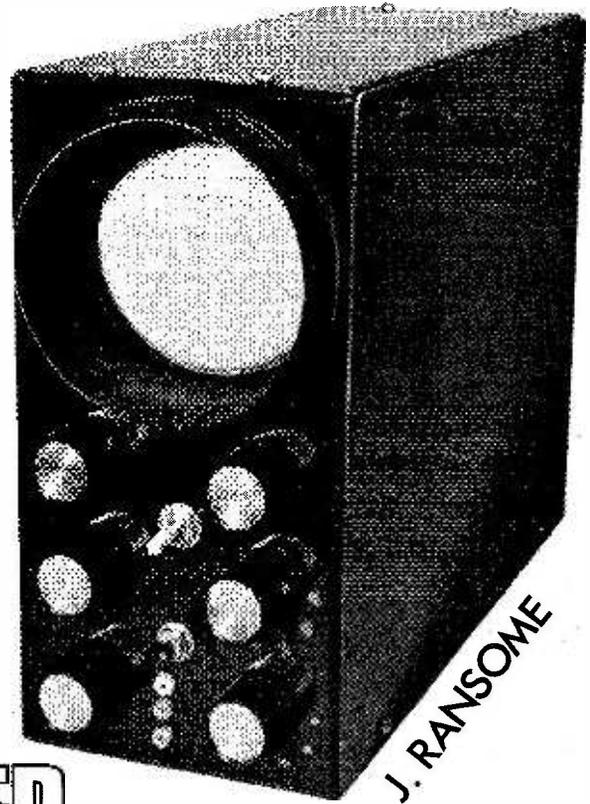
## DEFLECTION AMPLIFIERS

The next phase of the construction is concerned with the deflection amplifiers. Two of these are required, one each for the X and Y plates. The deflection sensitivity of the CRT used is such that about 100V peak-to-peak is required to give a full scan on the tube. Most cathode ray tubes require push-pull deflection to give a scan which is free from trapezium distortion. In order to give something extra in hand on scanning ability the push-pull deflection amplifiers have been designed to give 140V peak-to-peak scan.

The theoretical circuit of the deflection amplifiers is shown in Fig. 10. Tr3a acts as a phase splitter and low gain amplifier. Counterphase signals of equal amplitude appear across R15a and R16a. The only disadvantage of this type of phase splitter is that the two signals have differing source impedances. We therefore push the outputs from the phase splitters into the emitter followers of Tr4a and Tr6a which have a high impedance and are not fussy about signal source impedance. The emitter followers serve a further purpose of controlling the working points



# TRANSISTORISED

## PART 2

# OSCILLOSCOPE

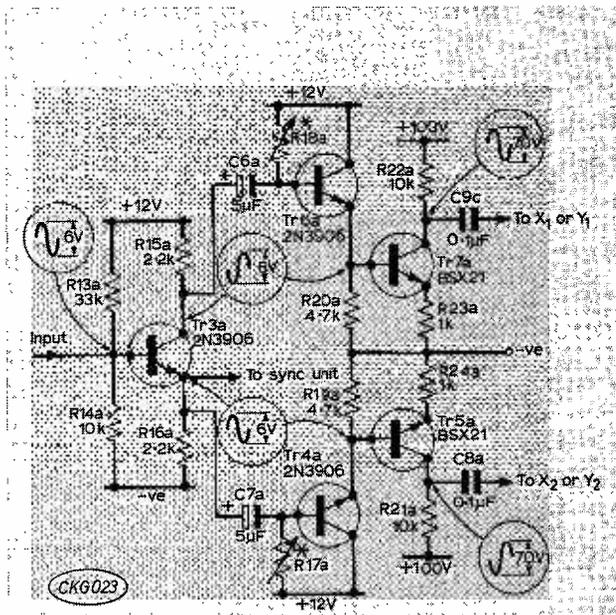


Fig. 10: Circuit of the deflection amplifiers—two are required, one for the X and one for the Y amp. See text regarding R17 and R18.

of the output transistors Tr5a and Tr7a by means of the standing currents in R19a and R20a. Tr5a and Tr7a are directly coupled to these emitter followers. The voltage gain of the complete amplifier is 12 when referred to a single ended output or 24 when referred to the push-pull output. As the transistors Tr4a and Tr6a control the working points of the output transistors they must be low leakage types. Suspect transistors must be avoided at all costs.

## CONSTRUCTION

The remaining units are built up on a 0.1in matrix Veroboard panel. The board used in the prototype was 6 $\frac{1}{2}$ in  $\times$  4in. It is recommended that at this stage all the breaks in the copper strip should be milled out before construction commences. This prevents disasters due to cross wiring as a result of forgetting a hole (here again the voice of experience speaks). The Veroboard layout, also including the Timebase and Y preamplifier, is shown in Fig. 13.

When using 0.1in matrix Veroboard, some care is necessary to avoid shorting out between conductor strips and when the wiring is complete, run a pen-knife along between the strips to make sure that no solder overlaps the conductors and that no small blobs of solder are shorting out any of the copper

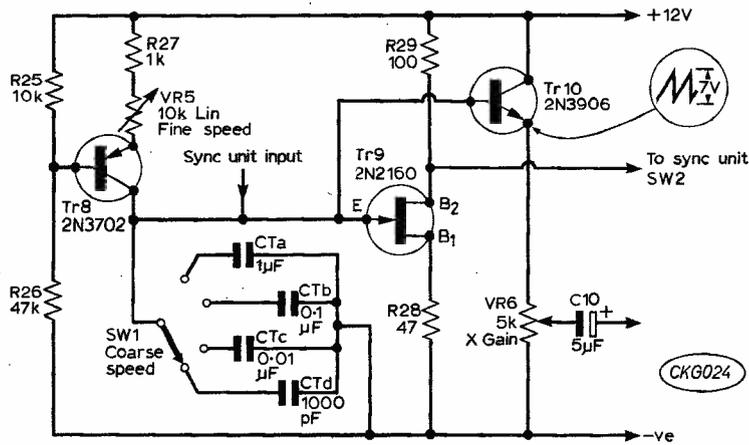


Fig. 11: The Timebase unit circuit.


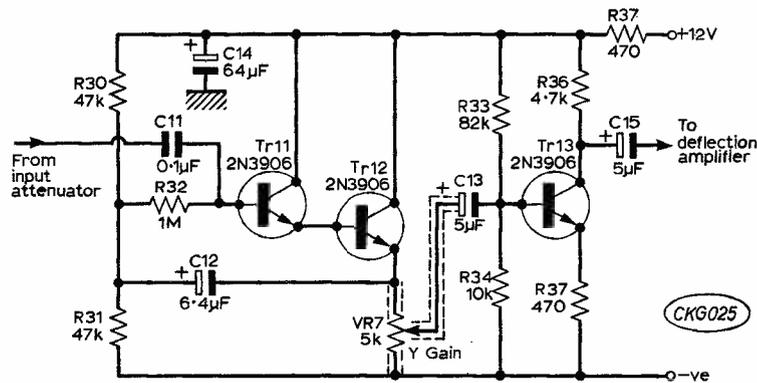


Fig. 12: The Y-preamp circuit. Note that the emitter resistor of Tr13 should be shown as R35, not as R37; the value shown is correct.

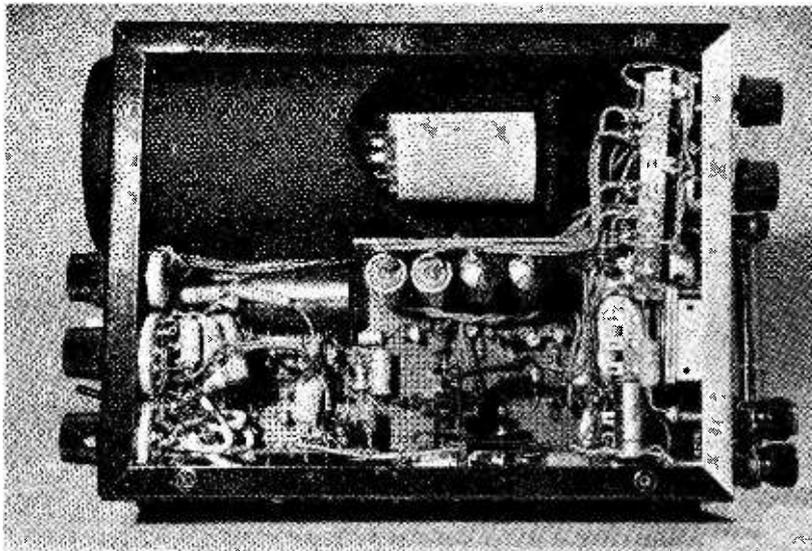

An internal view of the completed prototype. The main circuit board can be seen face on while C8 and C9 (a and b) can be seen mounted below the c.r.t. The sync unit is mounted on the base and cannot be seen.

strips. Wire in all the components with the exception of R17a and b and R18a and b when fixed resistors are preferred as their value must be determined empirically. Do not connect in the h.t. ends of the resistors R21a and b and R22a and b.

VR5 and R27. The output from the constant current source is used to charge the timing capacitor CT selected by SW1. The charge on the capacitor rises until the voltage on the capacitor is sufficient to cause the unijunction transistor Tr9 to fire. When

Connect the meter between R21a and the h.t. line and switch on. Only a very small leakage current should be indicated on the meter ( $250\mu\text{A}$  maximum). If the current is more than this, switch off and check the wiring. If the wiring looks satisfactory, check Tr4a for leakage. If all is well R17a may be wired in place and adjusted to give a standing current of  $4\text{mA}$  in the collector of Tr5a. For those wishing to use a fixed resistor for R17a the following procedure should be followed. Take a  $330\text{k}\Omega$  resistor and bridge between the base of Tr4(a) and the  $12\text{V}$  line. Note the current taken. If the current taken by Tr5a is more than  $4\text{mA}$ , increase the value of the bridging resistor until there is a standing current of  $4\text{mA}$  through the collector of Tr5a if the current is less than this figure—decrease the value of this resistor. Repeat the above procedure for R18a and Tr7a.

The construction and testing of the second deflection amplifier (b components) follows exactly that outlined above.


When all is satisfactory connect the output capacitors to the relevant input terminations on the display unit.

## TESTING

Switch on the complete unit and connect the low level signal to the X amplifier input. A horizontal line of approximately  $4\text{cm}$  long should be shown on the tube face. Next apply the signal to the Y amplifier input when a similar line in the vertical plane should be displayed. Next couple the X and Y inputs to the test unit via two  $0.1\mu\text{F}$  capacitors when a circle or ellipse similar in shape to that shown when testing the display unit should be seen. Whatever shape is displayed it should be regular with no flats, ripples or waves in it. Any distortions which do occur will almost certainly be due to incorrect selection of the bias resistors R17a and b and R18a and b.
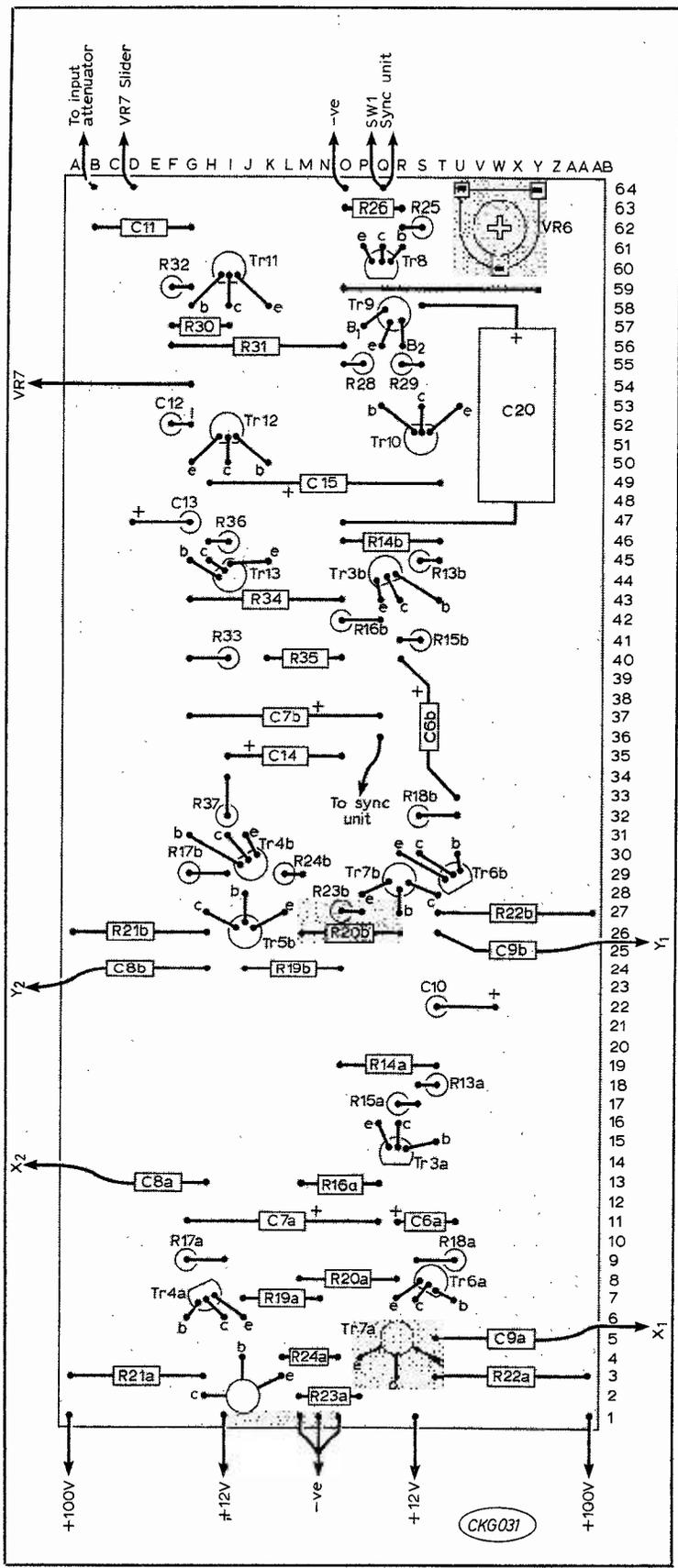
## TIMEBASE UNIT

The theoretical diagram of the ramp generator is shown in Fig. 11. Tr8 acts as a constant current source—the current being determined by the variable resistor



Tr9 fires it discharges the capacitor and the cycle repeats. The voltage across the capacitor takes the form of an almost pure saw-tooth waveform. Tr10 is employed as an emitter follower—serving to isolate the timing capacitor from the loading effects of the deflection amplifier. VR6 varies the voltage output and, therefore, the scan width. The main advantage of the circuit is that the amplitude of the output waveform is independent of operating frequency for all practical purposes.

Fig. 13 (left): The main component board. The deflection amplifiers are in the middle and at the bottom; the Y-preamp is top left and the Timebase top right.

### CONSTRUCTION

The scan generator is built on the same piece of Veroboard as the main deflection amplifiers and comprises the components on the top right-hand side of Fig. 13. SW1 and the frequency control resistor VR5 are mounted on the front chassis and flying leads taken back to the Veroboard. The timing capacitors CT are mounted around the course frequency control SW1. Note that Tr8 is a PNP type and is, therefore, connected upside-down in the circuit.

The timing capacitors CTa to CTd are the subject of individual choice but for general purpose audio work the values shown in Fig. 11 should suffice.

Having connected the timebase unit to the X amplifier switch the coarse speed control switch SW1 to select the 1 $\mu$ F capacitor. Connect the power supply and set VR6 to the top end (emitter end) of its travel. A horizontal line should now be traced across the screen. Adjust VR6 until the ends of the trace are just visible at each end of the tube. Some adjustment of the X shift control may be required. Apply a signal from the low level output of the test generator to the input of the Y amplifier. A sine-wave should now be displayed on the tube face. The number of waves seen will depend on the setting of the fine speed control VR5. It may be that the peaks of the sine-waves may disappear over the top and bottom of the tube—this is quite in order—the tops of the sine-waves should, however, not be flat. Any flattening of the trace is due to incorrect adjustment of the standing current in the Y amplifier output transistors.

The performance of the X amplifier may also be checked for correct biasing by applying the timebase output to the Y amplifier and the test signal to the X amplifier and following the above procedure.

## Y PREAMPLIFIER

The theoretical circuit of the Y pre-amplifier is shown in Fig. 12. Tr11 and Tr12 are employed as a bootstrapped amplifier. This configuration offers a very high input impedance (most desirable for an oscilloscope) but gives very little gain, as a consequence the bootstrapped amplifier is followed by the voltage amplifier of Tr13. The gain of the pre-amplifier is controlled by VR7 which is placed in the low impedance part of the circuit to minimise stray current pick-up in the connecting leads.

The input impedance of the original unit was measured as  $1.8M\Omega$  and the voltage gain 7.

## CONSTRUCTION

The pre-amplifier is built on the main Veroboard panel shown in Fig. 13. The components around Tr11 and Tr12 must have leads which are as short as possible as a precaution against pick-up of stray signals. Screened leads must be used for the connection to VR7 earthing the outer braid to the chassis line at one point only. If the leads of the input capacitor are longer than 10mm each these too should be screened.

## TESTING

This is probably the easiest circuit to test! Switch on the whole unit and apply a finger to the input capacitor C11. With a  $1\mu F$  capacitor switched in on the time base unit, a series of sine-waves will be displayed on the tube face (the amplitude of which may be varied by VR7). The input capacitor C11 should now be shorted to chassis—no vertical trace should be seen on the CRT face. If a trace can be seen then more attention must be paid to input screening. The area to concentrate on is the circuitry around Tr11 and Tr12.

## INPUT ATTENUATOR

The circuit of the input attenuator is shown in Fig. 14. The attenuation provides two decades of attenuation—10 and 100. As is the convention, the 100 stage is assigned the level 1 and the two other switch positions are referred to this and represent  $\times 10$  and  $\times 100$  gain. In the  $\times 1$  position the sensitivity is 20V/cm, 2V/cm in the  $\times 10$  and 200mV/cm in  $\times 100$  position.

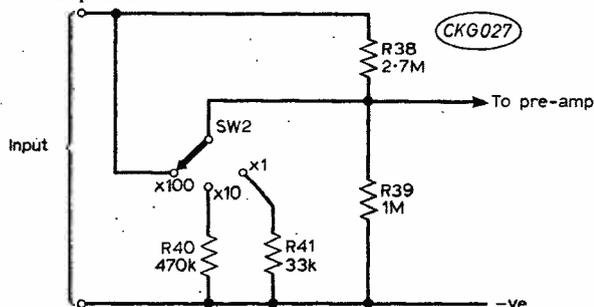


Fig. 14: The input attenuator circuit.


## CONSTRUCTION

All components are mounted on the switch. As the layout is absolutely straight forward and depends to a large extent on the components used, no wiring diagram is shown.
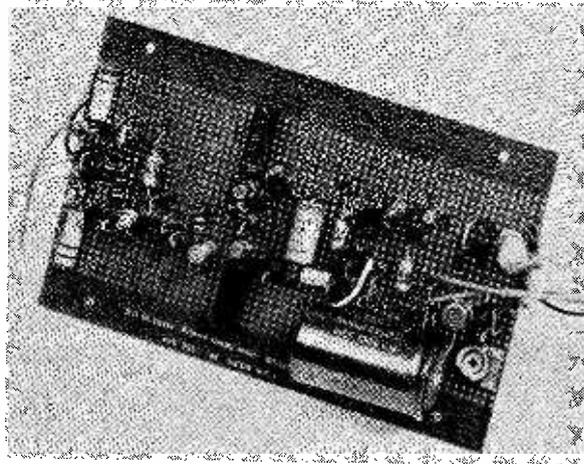
## SYNC CIRCUIT

The theoretical circuit of the sync unit is shown in Fig. 15. The function of the sync unit is to present a stable trace on the CRT screen. While this can be achieved by careful adjustment of the fine frequency control, the sync unit enables traces of waveforms of varying frequency to be displayed.

Tr17 acts as a switch and is effectively wired across



The main component board; compare this with Fig. 13.

the timing capacitor CT. When Tr17 is switched on, CT is shorted and cannot charge from the constant current source. As soon as the base of Tr17 is open circuited Tr17 then becomes effectively a high resistance across CT allowing CT to charge in the normal way. The resistance of Tr17 in the open circuit mode is sufficiently high not to affect the charge in CT.

Tr17 is switched by the bistable built around Tr15 and Tr16. Negative pulses applied to the base of Tr16 switch off Tr17. Negative pulses applied to Tr15 base switch Tr17 on.


The operational sequence is as follows: as the unijunction Tr9 fires and discharges the timing capacitor CT, a negative pulse is developed across R29. This pulse is fed to the base of Tr15 and this switches Tr17 on—shorting out the timing capacitor CT. The timebase is now switched off and will not start again until a negative pulse is applied to the base of Tr16, thereby "opening the gate". These negative opening pulses are effectively the sync pulses and are derived from the Y amplifier circuit.

The sync pulses are derived from the Y amplifier by means of the squarer circuit around Tr14. Tr14 is an over-driven amplifier producing square waves from any sine-wave or square wave input. The square-wave produced across R42 is put into the differentiator circuit of C16 and R43. From the differentiator circuit two sets of pulses are produced—one set positive going and the other negative going. The positive pulses are rejected by D7 and only negative going pulses are applied to Tr15. It must be noted that the resistor R43 does not repre-



speed of the timebase on the higher ranges.

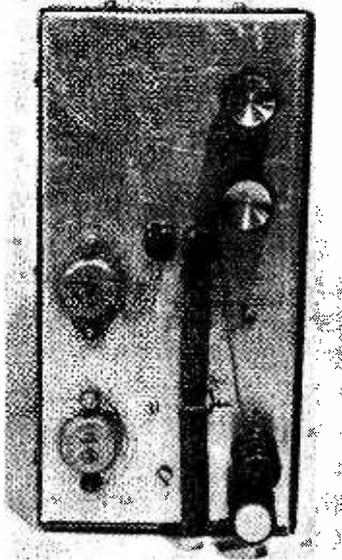Using the calibrated Y input set the output of the multivibrator to 1V peak-to-peak and seal the output potentiometer VR301 and the timing resistor VR300. The calibrator may then be built into the oscilloscope unit if required. No constructional details are given of this simple circuit.



A rear view of the completed unit showing the resistors making up R12.

## GENERAL

As stated in the introduction, a wide range of transistors may be used in the circuit. With the exception of the deflection output transistors all the NPN transistors can be almost any type satisfying the following criteria:

- a Silicon construction (or low leakage germanium)
- b  $V_{\infty}$  greater than 15V
- c Dissipation greater than 250mW
- d Gain greater than 40

The PNP transistors must be of silicon construction as the circuits in which they are employed rely on the transistors having low leakage. Within this limit any silicon PNP working at a low voltage greater than 15V will be satisfactory.

The output transistors can be any type having a  $V_{\infty}$  greater than 120V and a gain greater than 20. ■

## Back Numbers

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of *Practical Wireless* and *Television*.

To ensure obtaining regular copies of these magazines readers are strongly urged to place a regular order with their local newsagent, or to take out an annual postal subscription.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

# COMPREHENSIVE MULTIBAND RECEIVER

(PW Nov-Dec. 1971)

## FURTHER NOTES

By  
**F. G. RAYER**

On the short wave ranges, coverage is approximately 1.7-5.0MHz, 5-15MHz and 11-31MHz, similar to that provided with many receivers. As plug-in coils are used, it is easy to split up coverage to include one extra range. This opens out tuning a little, but its main advantage arises if a v.h.f. convertor requiring continuous tuning from 4-6MHz is added, as this then falls in a single range, avoiding coil-changing.

To add this range, adjust the coil cores for ranges of 1.6-3.8MHz, 7-14.5MHz and 13-31MHz. The new or additional range is 2.5-6.0MHz. The coils for this coverage are as follows:

**Aerial.** "Blue" Range 3. Remove 12 turns from the tuned section, and re-solder.

**Mixer.** "Yellow" Range 3. Modify as for aerial coil.

**Oscillator.** Use a "White" Range 3 oscillator coil, instead of the "Red" Range 3 oscillator coil, padder values and connections remaining unchanged.

Proper ganging will be obtained, after adjusting the aerial and mixer coil cores in the way described.

## TUNING METER

Space is available to the left of the tuning scales for a 42mm square S-Meter (1mA f.s.d.), and a suitable circuit is shown in Fig. 1. With aerial shorted to earth, VR1 is rotated until the S-Meter reads zero. When a signal is tuned in, the a.g.c. voltage reduces the i.f. stage cathode current through R1. Less voltage is dropped across R1, causing the negative terminal of the meter to become negative, so that a reading is produced. Sensitivity can be modified by changing the value of R2.


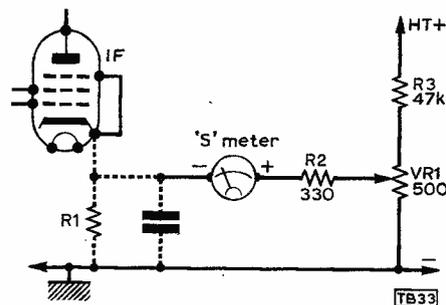


Fig. 1: Additional circuitry required for installing the S-meter

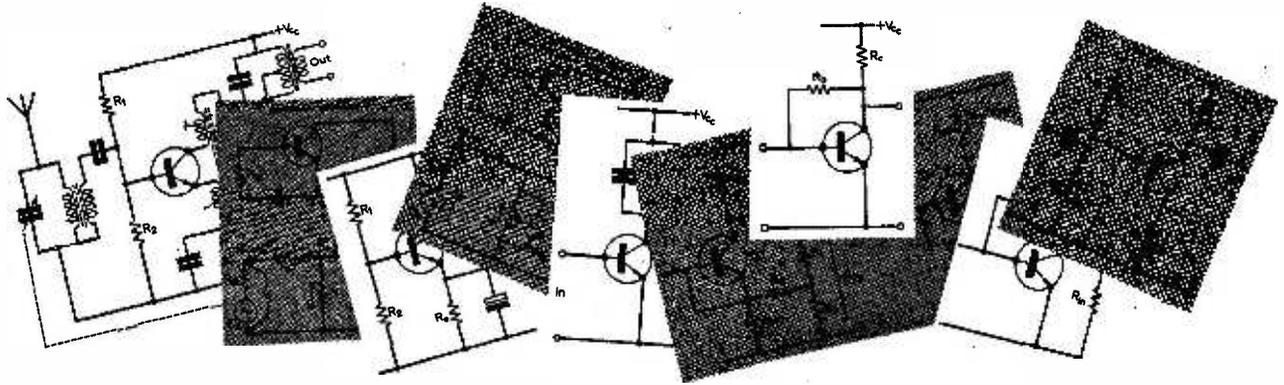All trimming or other receiver adjustments are directed towards obtaining the highest meter reading. External improvements, as to the aerial-earth system, will also increase meter readings. ■



# TRANSISTOR CIRCUITRY for beginners

## PART 6

H.W. HELLYER & MICHAEL HOLLIER

### Upper and Lower-case

Those of you who are still with us, and old hands at transistor circuit building, may not need reminding; newcomers may wonder what the heck I am talking about; but recent correspondence reveals that it is necessary to recap on one vital point—the use of upper-case (capital) and lower-case (small) letters when we are discussing transistor parameters.

More than ever necessary when we ourselves are guilty of the cardinal error of using them wrongly. My excuse could easily be that I could not read Michael's scribble that accompanied the little module that we made the subject of Part 5. But I should have spotted that in the section headed "input Impedance", the second sentence of the second paragraph began . . . "H parameters again, but  $h_{ie}$  simply means. . . ."

That capital H should have been a small one, of course, and I should have rewritten the sentence so that it did not kick off with "H".

Later on, talking about the base bias, I committed a similar crime. "The base current  $I_B$  is found from

the formula  $I_B = \frac{I_C}{H_{FE}}$  where  $H_{FE}$  is the d.c. current gain of the transistor.

Our capitals are quite right on the suffix—FE refers to the d.c. current gain, certainly, while fe is the forward current gain with output shorted and in the common emitter mode. But the capital H is wrong. As you will have noted from the December 1971 issue, page 711, hybrid parameters have their own strict code of symbolism, and we use h, as in  $h_{ie}$  or  $h_{te}$  or  $h_{FE}$ , and so on. On another page, friend Henry, who is probably poking gentle fun at our floundering, would be quick to tell you that capital H means something quite different!

### Super Alpha

Back then to our subject, the Darlington Pair of transistors, or, to give them their alternative title, the Super Alpha circuit. Their purpose, to recap to the end of Part 5, to increase the input impedance of our buffer amplifier circuit, without despoiling any other of its good points. Remember, we pointed

out that good matching was more easily achieved if the impedance of the device into which the signal was being fed was ten times or more that of the output which was feeding it.

There is no cast-iron rule about this, but the generalisation needs stating, for, so often, manufacturers fail to agree with any known standard in stating their specifications, and 100k $\Omega$  might mean the input "wants to see" 100k $\Omega$ , and is actually considerably higher if measured, or might mean that it actually is 100k $\Omega$ .

Then, you see, if you try to match some circuits with 100k $\Omega$  output into this "specified" input, you simply would not get the conditions that the specifications might have led you to expect.

This is a practical problem, and I make no apology for introducing it at this point, for the Darlington circuit, on the face of it, looks like a complicated way of achieving what could be done much more simply. Not so, as we shall demonstrate by a step-by-step design exercise.

### Why high?

Accept, first of all, that we need a high impedance input. Harking back to the prototype that Mike built, we were able to measure 105k $\Omega$  input impedance on the built-up model, and could probably have improved somewhat on this with a bit of fiddling. But did you notice the underlined remark that followed? To summarise, frequency limits are affected by the source impedance.

There are occasions when we want to match something whose source impedance is (a) much higher than a tenth, or even a fifth, of our input impedance, or (b) alters drastically with frequency, i.e., is reactive. A perfect case in point is the crystal microphone. There are a lot of these about, and they are often capable of giving much better results than they do when matched into the tape recorders or "Disco" mixers with which they are sold. Don't always blame the microphone: if you don't believe me, ask Cosmocord Ltd., who market a wide range of these devices under the Acos label and get very hot under the collar when they think of some of the ways in which their products are used—or mis-used!

So, what are the limiting factors that prevent us achieving a higher input impedance, or, to be technical  $Z_{in}$ ? First, the forward current gain,  $h_{fe}$ . The larger this is, the greater the input resistance will be,  $h_{ie}$ . Check back with part 5 to see the significance of this and go on to  $r_e$ . This (often overlooked) internal resistance of the transistor itself matters a lot. Because it doesn't show up on circuit diagrams, the clever dicks who simply alter calculated circuits, like the well-engineered Mullard, Ferranti or Motorola published circuits, find their finished construction behaving in unpredictable ways. It is a fixed value. It cannot be altered, but, though small in relation to  $R_E$ , it has to be allowed for.

$R_E$ , the external resistance, seems to give us scope for manoeuvre. Increase this and, as we have seen, we increase the input impedance. Lovely—except that an increase in resistance here will mean an increase in the voltage dropped across the resistor, so we now need a higher supply. Even if this can be made available, it is not always desirable for input stages, where, in general, the higher the operating voltages, the more the noise problem rears its ugly head.

Base bias resistors also have to be considered. Remember, in Part 5, we were very concerned with their effect on the overall circuit. To put it into plain language, if you calculate them to get the best d.c. conditions, you may very well find your circuit unable to cope with the a.c. conditions or the matching—which, after all, is why the darned thing is being built!

If the values of base bias resistors are increased, we can reduce their shunting effect on the transistor input d.c. resistance ( $h_{ie}$ ). But under a.c. conditions, we may very well find the stability of the circuit seriously affected.

So, accepting that there are limits to what we can do in the way of altering components and voltages of a common emitter amplifier circuit in order to achieve a high input impedance, let's turn immediately to the solution, and see what, in fact, it does.

## Darlington Pair

There is nothing magical about the term Darlington. Without delving into the historical context, we are simply referring to a method of combining two transistors in such a way that they effectively form one, but with different characteristics.

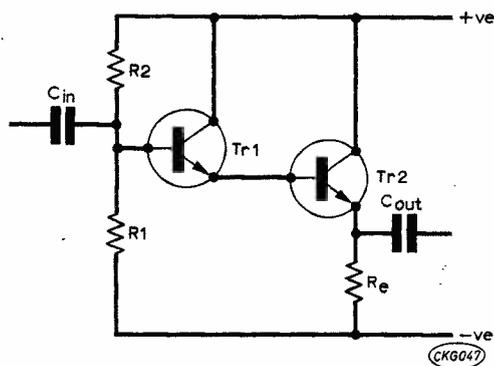


Fig. 26: The rudiments of the Darlington Pair circuit.

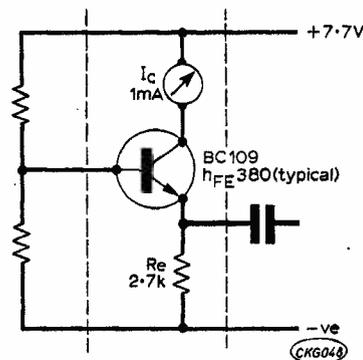


Fig. 27: Consider only Tr2, isolated from the rest of the circuit, with imaginary bias.

Take a look at Fig. 26, and you will see this done in the emitter follower mode. As I hope to show later, this is not the only configuration in which it applies, but it suits our purpose at the moment to rip it to bits and discuss the design.

If you want to make a buffer circuit yourself, with a high impedance output, then the following notes may help you adapt your own bits and pieces rather than have to mourn about "those lucky blokes at PW who can lay their hands on anything they want" as a recent correspondent said.

Fig. 26 shows two n.p.n. transistors, connected so that both collectors are taken to the positive rail, the input to the base of the first, Tr1, is biased in the way we have already seen, but whose emitter is taken to the base of Tr2. Looked at one way Tr2 forms the emitter load of Tr1; another way, Tr1 and its operating conditions, determine the base input conditions of Tr2.

Looking first at Tr2, and referring to Part 5, we see that the output is taken across  $R_E$ , the emitter resistor, via  $C_{out}$ , but the base bias, instead of being derived from two resistors (as with Tr1) depends on Tr1 and its operation. So let's pretend for a moment that Tr1 doesn't exist, and that Tr2 has conventional biasing, repeating last month's circuit, but with dotted lines to show that the BC109 between them is really the Tr2 of our present Fig. 26. We now have Fig. 27, where some values are inserted and a few more details are given.

## Calculations

Recapping again, we chose a typical transistor and typical operating conditions, so in Fig. 27 we state an  $I_c$  of 1mA, an  $h_{FE}$  of 380 and as the base current  $I_b$  is the former divided by the latter,

$$I_b = \frac{I_c}{h_{FE}} \text{ or } \frac{1\text{mA}}{380}$$

which is  $2.6\mu\text{A}$ .

If now we refer back to Fig. 26, and connect Tr1 in the base circuit of Tr2, making them similar transistors, as it happens, though they don't necessarily have to be, we shall see that base current of Tr2 will flow through Tr1 emitter, so we can immediately say that the emitter current of Tr1 is  $2.6\mu\text{A}$ .

Unfortunately—there's always a catch, isn't there?—at such a low current, almost all forms of transistor likely to be used in our buffer circuits

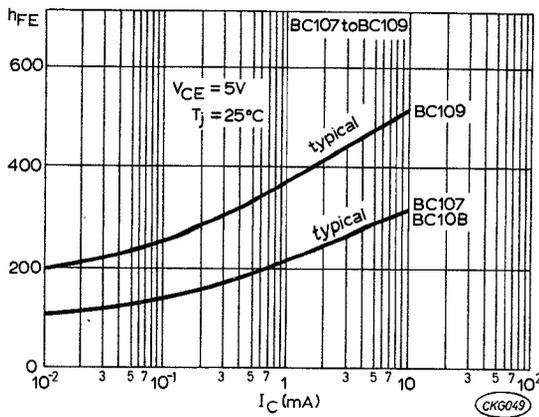


Fig. 28: Typical variations of forward current transfer ratio  $h_{FE}$  with collector current  $I_C$ . Note that curve is for specific collector voltage  $V_{CE}$ .

would have a very small a.c. current gain  $h_{fe}$  in these circumstances. Now do you see why I began with that upper-case and lower-case argument.

We must do something about this. Increasing the current in Tr1 is the obvious first thought, so we refer to the  $h_{FE}/I_C$  graph for the transistor in question.

Messrs Mullard, as ever, are immensely helpful, and can provide graphs that tell us practically everything except the Sign of the Zodiac when the transistor was born, so our Fig. 28. is a reproduction of their "typical variation of forward current transfer ratio with collector current". Please note, this is at a particular collector-emitter voltage, in this case  $V_{CE}=5V$ . But from this we can get some idea of what we want, and this is the sort of collector current it would be desirable to use. Here, we see the lowest usable value is down around  $10\mu A$ . We shall use a collector current of around  $50\mu A$ , and from the graph we can see that this will give us a d.c. current gain,  $h_{FE}$ , of somewhere around 260.

### Increasing $I_E$

We have  $2.6\mu A$  of emitter current so far, and we need  $50\mu A$ . Let's just revert to previous theory and stick in another resistor  $R_{e1}$  from the emitter of Tr1 to the negative line, as in Fig. 29. Now, this circuit is not for construction: it is deliberately

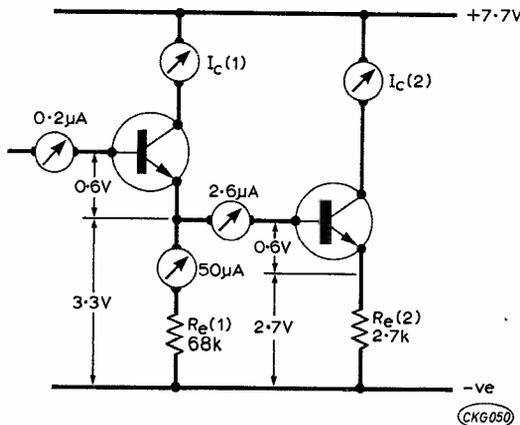


Fig. 29: The voltage and current plan of the simple circuit from which the final working model will evolve.

drawn to illustrate the design theory; please bear with me!

We have included the known voltages and currents, that is the collector current of Tr2, which is  $1mA$ , and the base current of Tr2, which is  $2.6\mu A$ . So the emitter current is effectively the same as the collector current, as the effect of the very small base current, which also flows through  $R_{e2}$ , can be ignored.  $1mA$  flowing through  $2.7k\Omega$  gives a voltage drop of  $2,700/1,000$  or  $2.7V$ . That's our emitter voltage of Tr2 fixed.

The base to emitter voltage of a silicon transistor is around  $0.6V$ , so we come up with a base voltage for Tr2 of  $2.7 + 0.6 = 3.3V$ . Take another look at Fig. 29. This is now the emitter voltage of Tr1, which was one of the missing factors. Again add  $0.6V$  and we get a figure for the base voltage of Tr1, i.e.,  $3.3 + 0.6 = 3.9V$ .

$R_{e1}$  is the mystery component. The emitter current of Tr1 will be the sum of that base current previously considered and the current flowing through  $R_{e1}$ . But we have already said that the required emitter current is to be  $50\mu A$ . So that leaves us with  $50 + 2.6$  or  $52.6\mu A$  as the actual emitter current.

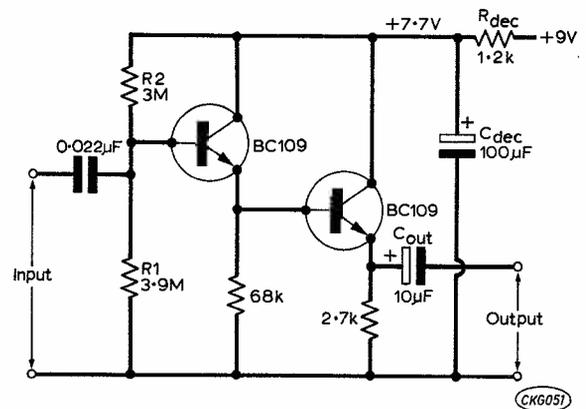


Fig. 30: The end result, a Darlington Pair input circuit with reasonably high impedance, good stability and the gain required.

The collector current  $I_C$  of Tr1 flows through  $R_{e1}$  and we know the emitter voltage. So  $R_{e1}$  the emitter resistor

$$= \frac{3.3V}{50\mu A} \quad \text{or} \quad \frac{3.3}{50 \times 10^{-6}} \quad \text{or} \quad \frac{3.3 \times 1,000,000}{50} = 66,000\Omega$$

Choosing components within a 5% tolerance range, we can settle for a preferred value of  $68k\Omega$ , and this is now marked in on Fig. 29.

### Base current Tr1

We now have the correct base current in Tr2 and the correct emitter current in Tr1 so can go on to calculate the values of bias resistor we shall need.

The base current of Tr1 will be its collector current (which we know) divided by  $h_{FE}$ , the d.c. current gain. But this base current is only a very small fraction of the emitter current, and can be ignored for the next calculation.

Taking the collector current  $I_C$  of Tr1 to be the same as its emitter current,  $52.6\mu A$ , we prove this point by saying:

$$I_{b(1)} = \frac{I_{c(1)}}{h_{FE(1)}} = \frac{52.6\mu A}{260}$$

somewhere near  $0.2\mu A$ .

Developing our final circuit, Fig. 30., and ignoring for the moment that I've already marked in the values of R1 and R2, let's calculate their ohmic values from what we already have. First, a proviso: for good stability, we want about five times as much current flowing in the bias chain as we have base current. So,  $0.2 \times 5 = 1\mu A$  as a guiding value.

We know the base voltage of Tr1 is 3.9V. The lower resistor, R1, has our desired figure of  $1\mu A$  through it, so the value is

$$R1 = \frac{3.9}{1 \times 10^{-6}} \text{ or } 3.9 \times 1,000,000 = 3.9M\Omega$$

This is a standard value, and a 5% tolerance component would be used.

R2 has a voltage dropped across it which is the difference between the collector voltage (in this case, the positive rail after decoupling) and the base voltage,  $= 7.7 - 3.9 = 3.8V$ . So

$$R2 = \frac{3.8}{1.2 \times 10^{-6}}$$

where the denominator in this case is the  $1\mu A$  flowing through R1 plus the  $0.2\mu A$  of base current.

$$R2 = \frac{38,000,000}{12} = 3,166k\Omega$$

A  $3M\Omega$  resistor, 5%, is near enough, and two  $1.5M\Omega$  resistors in series may be a more practical solution.

If you are in doubt about this tolerance business and having to make up values with series or parallel resistor combinations, bear in mind the simple rule: in series, variations in the biggest resistor have most effect—in parallel, variations in the smallest resistor have most effect.

## Input resistance

Looking into the base of Tr1, ignoring R1 and R2 for the moment, the input resistance is calculated from  $R_{in} = h_{fe(1)} \times h_{fe(2)} \times RE(2)$ . Approximately—because we now ignore those tricky hidden resistors,  $r_e$  of each transistor, which are now very small in comparison with the values of external  $R_e$  we have calculated.

Provided  $R_{e1}$  is many times larger than  $R_{e2}$ , its shunting effect on the input of Tr2 will be negligible. Make it between 5 and 30 times the value of  $R_{e2}$  and we shall not have many worries, so our  $R_{e1}$  is  $68k\Omega$ .

Harking back to the formula for  $R_{in}$ , we get the  $h_{fe}$  figures from the published data sheets ( $h_{fe}$  rising as collector current rises, remember), see Fig. 31.  $R_{in} = 240 \times 440 \times 2,700 = 285.12M\Omega$  to be exact.

The Stage Resistance is the parallel combination of this with R1 and R2, which is—work this one out from the formula

$$\frac{1}{R_{IN}} = \frac{1}{R1} + \frac{1}{R2} + \frac{1}{R_{in}} = \frac{1}{3.9M\Omega} + \frac{1}{3M\Omega} + \frac{1}{285M\Omega}$$

approximately  $1.6M\Omega$

## Decoupling

Theory and practice never coincide, and the desired rail voltage may be quite a lot less than a convenient battery size. So we drop the residual voltage and decouple the line to prevent alternating signals modulating the battery resistance and causing the supply voltage to vary.

The components used are shown in Fig. 30. and are calculated from the voltage difference  $9V - 7.7V = 1.3V$  divided by the total current. This is the collector current of Tr1,  $0.05mA$ , of Tr2,  $1mA$  and in R2,  $0.0012mA$ , total  $1.0512mA$ .

We can take this as  $1mA$  through  $R_{dec}$ , giving  $1.3$

$1 \times 10^{-3}$  or  $1.3k\Omega$ . Again, using the nearest preferred value, within tolerance, we'll settle for  $1.2k\Omega$  at 5%.

The decoupling capacitor needs to be quite large, as we have already discussed, and a practical value is  $100\mu F$ . Similarly, a practical value of the output coupling capacitor,  $C_{out}$ , would be around  $10\mu F$ .

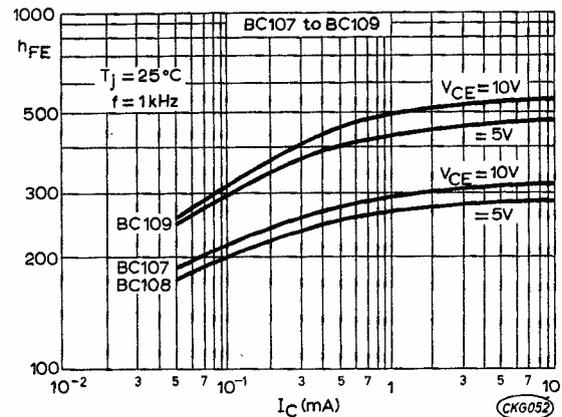


Fig. 31: Graph of variation of input impedance with collector current.

But  $C_{in}$  need not now be so large as we previously needed. The a.c. resistance (impedance) into which it is feeding is so much higher than before that a value such as  $0.022\mu F$  could be used. To check this, take the value that gives the same reactance to your desired lower frequency limit as does the input impedance of the circuit—i.e., the  $-6dB$  point (voltage). This works out to around  $4Hz$  for  $0.022\mu F$  which is plenty good enough for our purpose.

Before leaving the subject, I revert to that designation "Super Alpha". The term alpha, symbol  $\alpha$ , you will remember from previous notes is in our case the same as  $h_{fe}$ . As we obtained our  $R_{in}$  by multiplying the two  $h_{fe}$  figures, the effective  $h_{fe}$  of the Darlington Pair is called Super Alpha.

## Other uses

We have only been talking about input circuitry, and an impression may have been given that the Darlington pair is explicitly an input device. Not so, and just to prove it, but without any calculations, Fig. 32 shows four possible configurations of complementary push-pull output stages of audio amplifiers. These are stripped to their essentials, and have all been used in some form or another.

The use of the Darlington pair in power amplifiers

# THE Medium Wave Column

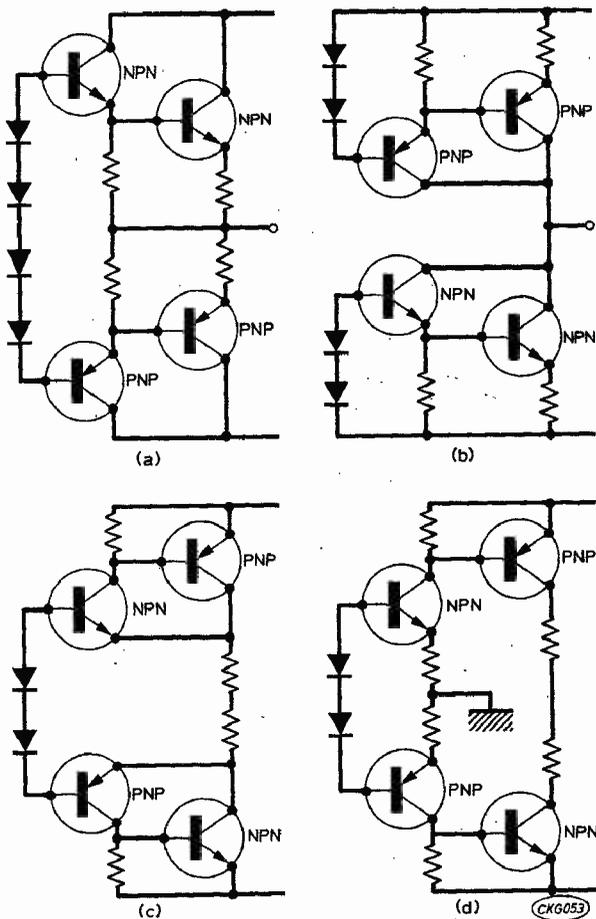


Fig. 32: Four variations of the Darlington Pair as used in push-pull output circuits of commercial power amplifiers.

overcomes (to some extent) a disadvantage of complementary symmetry, which is high current dissipation of a Class A driver transistor. Some other solutions exist, of course, such as quasi-complementary circuits, where the driving pair are "opposites" and the driven pair a matched and similar pair of transistors. This is not the place to talk about power amplifiers—a fascinating subject—but to illustrate the Darlington pair, so first to Fig. 32(a), where the two "halves" of the complementary circuit are formed from two pairs, much the same as we have already dealt with.

The drawback here is a biasing problem: base/emitter voltage at the point of conduction differs widely between driver and output transistor. Some bias adjustments are needed to supplement the work of the diodes.

Fig. 32(b) is an alternative, solving some problems, but really doing no more than turning the Darlington pairs upside down.

If we try, instead, the pair "inside out", we produce the cascaded complementary configuration of Fig. 32(c) where each set operates as an emitter follower. It is easier to provide bias because the diodes are more easily matched, but Fig. 32(d) shows the more usual solution, where we get the power gain of the two cascaded common emitters and a better bias system. But it has a drawback not always taken care of in eventual construction, and that is a more touchy thermal stability.

TO BE CONTINUED

F. E. WILDMAN of Southall, Middlesex has been busy with his Practical Wireless medium wave loop antenna. North American stations logged include WOR New York on 710kHz; CBM Montreal on 940kHz; WINS New York 1010kHz; CBA Moncton on 1070kHz; WBAL Baltimore 1090kHz; WNEW New York 1130kHz. He asks if medium wave DX is best during periods of anti-cyclonic weather. Although high pressure systems affect v.h.f. reception they appear to have no effect on the medium waves. Propagation on the lower frequencies is through the ionosphere which lies far above the thin shell of weather that surrounds the earth.

P. J. Kay who lives in Magull near Liverpool, reports reception of WNEW 1130kHz at 0030hrs on November 15th using a Perdio transistor portable. Very occasionally, high power North American medium wave stations such as WNEW, which is 50kW, are received in this country at considerable strength and can be heard from a favourable location on simple equipment. More reliable reception will be obtained by using a sensitive and selective receiver of communications standard along with an outdoor aerial or an indoor medium wave loop. Search before midnight for the following stations, all of which have been logged frequently during recent months. CBN St John's, Newfoundland on 640kHz; CJOX Grand Bank, Nfld and WOR New York, both on 710kHz; WDHN Boston on 850kHz; CJON St. John's 930kHz; CHER Sydney 950kHz; WINS New York 1010kHz; CBA Moncton 1070kHz; WNEW 1130kHz. These broadcasters are easy to identify as they use their callsigns frequently. After midnight look for Godhavn in Greenland on 650kHz. It can usually be heard with programmes in Danish or "Greenlandic", when reception from North America is favourable.

Harold Emblem of Mirfield, Yorkshire, reports reception of the new EAK5, Radio Popular Las Palmas in the Canary Islands on 836kHz. Michael Barraclough of Whitby mentions that this newcomer to the band is anxious for reception reports which should go to AP744, Las Palmas de Gran Canaria-1, Canary Islands. Harold has also logged the new outlet at Abu Dhabi in the Persian Gulf on 809kHz at 0230 hrs. Radio Pakistan has been heard testing on 1010kHz and has been logged by the writer at 2320hrs. This station is believed to be in West Pakistan.

Gordon Darling of South Harrow draws attention to a recent supplement to the Post Office Guide which says that Commonwealth Reply Coupons are no longer accepted in Canada, Australia, Ceylon, Trinidad and Tobago. In future, MW DXers sending reports to Canada will have to enclose an International Reply Coupon.

Please send reports and information about the medium waves to the author at 132 Segars Lane, Southport, PR8 3JG.

# INCREASE YOUR KNOWLEDGE



Established 1891

**MANY COURSES TO CHOOSE FROM incl.**


RADIO & TV ENGINEERING & SERVICING,  
TRANSISTOR & PRINTED CIRCUIT SERVICING,  
COLOUR TV SERVICING, ELECTRONICS,  
NUMERICAL CONTROL ELECTRONICS,  
TELEMETRY TECHNIQUES, CONTROL SYSTEMS,  
ELECTRONICS FOR AUTOMATION,  
COMPUTERS, ETC.

**ALSO EXAMINATION COURSES FOR**

C. & G. Telecommunication Technicians' Certificates  
General Radio Communications Certificate  
Radio Amateurs' Examination  
General Certificate of Education, etc.

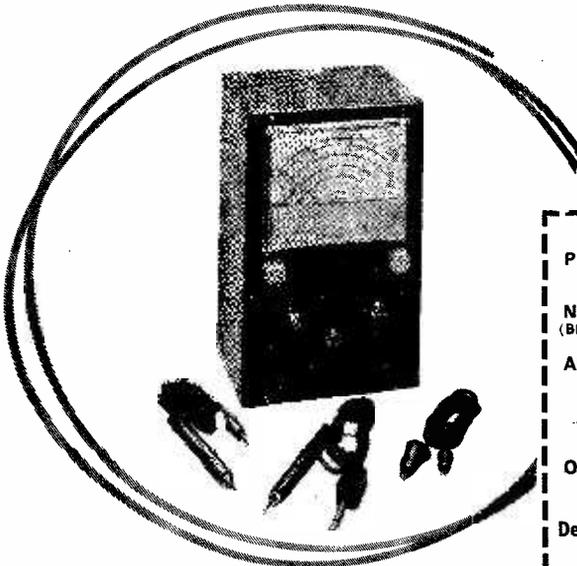**BUILD YOUR OWN RADIO AND INSTRUMENTS**

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



## RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

C & G Radio Servicing Theory

### THERE IS AN **ICS** COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

**FILL IN AND POST THIS COUPON TODAY**

You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio, television and electronics **PLUS** details of over 150 specialized subjects.

Accredited by the CACC.

PLEASE SEND FREE BOOK ON.....

NAME .....  
(BLOCK CAPITALS PLEASE)

ADDRESS .....

.....

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS  
Dept. FB28, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8 4UJ.

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**N**OW that we have all recovered from the Festive Season we can get back to our shacks and start logging some DX. Many of you will have received new equipment as presents so how about putting it to good use and sending in a report.

### Logs

The first report this time comes from **Bryan Ewing** in Seven Kings, Ilford. Bryan's equipment consists of a Codar CR70A, an ATU and a 50 foot long-wire, his log included:—

6025 *Radio Portugal* at 2112.  
 6075 *R.A.I., Rome, Italy* at 0436.  
 6120 *S.B.C., Berne, Switzerland* at 0152.  
 6170 *Radio Sofia, Bulgaria* at 1900.  
 7105 *R.N.E., Spain* at 2030.  
 7230 *Radio Monte Carlo* at 1125.  
 7290 *Trans World Radio, Monaco* at 1525.  
 9460 *Radio Pakistan* at 2005.  
 9525 *All India Radio* at 2015.  
 9615 *H.C.J.B., Quito, Ecuador* at 0402.  
 9625 *Radio Sweden* at 1115.  
 9645 *Vatican Radio* at 2030.  
 9680 *Trans World Radio, Monaco* at 0925.  
 9710 *H.C.J.B., Quito, Ecuador* at 0146.  
 9912 *All India Radio* at 2015.  
 11710 *R.A.E., Argentina* at 2345.  
 11730 *R. Nederland, Bonaire* at 0200.  
 11750 *Finnish B.S.* at 1000.  
 11815 *Trans World Radio, Bonaire* at 0110.  
 11830 *Radio Havana, Cuba* at 0109.  
 11835 *R.T.V. Algerienne* in French at 2100.  
 11875 *R.S.A., South Africa* at 2347.  
 11895 *All India Radio* at 2330.  
 11955 *Voice of the Lebanon* at 0230.  
 15200 *Vatican Radio* at 1500.  
 15200 *Voice of Nigeria* at 0648.  
 15325 *Radio Canada* at 1520.  
 15410 *United Nations Radio* at 1700.  
 17820 *Radio Canada* at 0743.  
 17945 *Radio Pakistan* at 1345.  
 21545 *Radio Accra, Ghana* at 1445.  
 21590 *Radio Pakistan* at 0806.  
 (All these transmissions were in English except where otherwise stated.)

**Robin Yates** of Deganwy, Caernarvonshire heard the following stations on his Alba stereogram:—

5960 *H.C.J.B. Quito, Ecuador* at 0800.  
 5990 *Radio Canada* at 0715.  
 7310 *Radio Vilnius, Lithuania* at 2230.  
 9530 *All India Radio* at 1930.  
 9690 *WNYW, U.S.A.* at 2100.

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

9805 *Radio Cairo* at 2145.  
 11935 *FEBA, Seychelles* noted at 1730.  
 15130 *WNYW, U.S.A.* at 2000.  
 15155 *Radio Havana, Cuba* at 2010.  
 17720 *WINB, Red Lion* noted at 1930.  
 17855 *NHK, Japan* at 0800.

**Clive Jones** of Colliers Hatch near Epping describes his equipment as "a four valve domestic receiver with a looped, coiled and bent, untuned dipole!" This equipment enabled him to hear:—

6025 *Radio Portugal* in English at 2100.  
 9009 *Kol Israel* in English at 2120.  
 9480 *Radio Kiev, Ukraine* at 1950.  
 9545 *R. Accra, Ghana* in English at 2115.  
 9630 *R. Sweden, Saturday Show* at 1100.  
 9695 *R.S.A., South Africa* at 0040.  
 11720 *Radio Canada* in English at 2120.  
 11765 *Radio Australia* at 0900.  
 17880 *H.C.J.B., Quito, Ecuador* at 1915.

**Julian Moss** of Rayleigh has a Meridian 10 transistor superhet and a 60 foot long-wire enabling him to hear:—

5960 *H.C.J.B., Quito, Ecuador* at 0815.  
 6025 *R. Portugal, Voice of the West* at 2130.  
 7235 *R. Australia* in English at 1530.  
 9460 *R. Pakistan* with news at 2100.  
 9525 *R.S.A., South Africa, English* at 2245.  
 9530 *A.I.R., Delhi* in English at 1915.  
 9530 *V.O.A., Monrovia, sign-off* at 2230.  
 9545 *R. Accra, Ghana* in English at 2045.  
 9550 *Finnish B.S.* in English at 1830.  
 9570 *R. Australia* with DX News at 0735.  
 9575 *R.A.I., Rome* in Italian at 2130.  
 9620 *R. Belgrade, Yugoslavia* at 1550.  
 9625 *R. Sweden* in English at 1255.  
 9625 *Radio Canada* at 0720.  
 9670 *Damascus, Syria, news* in English at 2030.  
 9690 *WNYW, U.S.A.* at 2000.  
 9695 *R.S.A., South Africa* in English at 2215.  
 9745 *R. Baghdad, Iraq* in German at 2045.  
 11720 *Radio Canada* in English at 2120.  
 11765 *Radio Australia* in English at 0735.  
 11770 *A.F.R.T.S., football match* at 1950.  
 11790 *A.I.R., Delhi, news* in English at 2200.  
 11805 *VOA, Greenville, N. Carolina* at 1930.  
 11970 *R.S.A., South Africa news* in English at 2238.

Reports should arrive by the 15th of the month and be addressed to me at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.




**IN NEXT MONTH'S**

**PRACTICAL  
WIRELESS**

*Changing Times...*
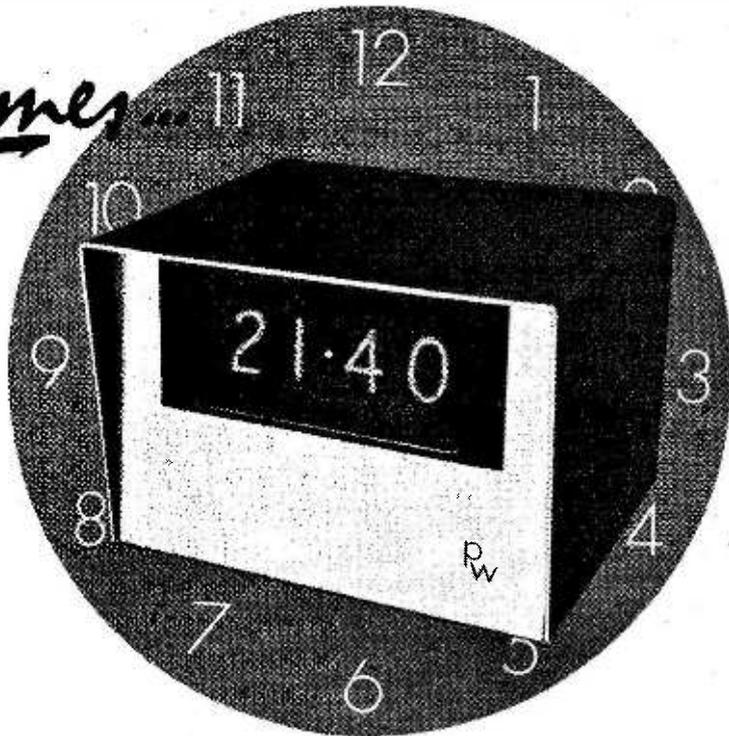
# Digital Clock

Times certainly are changing. Eighteen months ago you would have been lucky to afford the components for a digital clock even if you could have found a supplier—but 1972 sees the dawning of a new age. While digital techniques become better known, prices continue to fall (about 50% last year). This digital clock is mains frequency operated and although it uses 12 i.c.'s (price at the time of writing 67p each) there is practically nothing else apart from the readout tubes. For the serious constructor now is the time to enter the digital field and how better than with a really practical project such as our digital clock.



## WIPER DELAY UNIT

"It never rains but it pours" is a saying that many car makers seem to take literally, forgetting that grizzle (not exactly an unknown phenomena in the British Isles!) causes poor visibility and is difficult to deal with using fixed speed wipers. This simple unit gives full speed control over the wipers using a few, inexpensive components.

**PLUS MANY OTHER CONSTRUCTIONAL ARTICLES AND ALL THE REGULAR FEATURES. BE CERTAIN NOT TO MISS THE NEXT ISSUE. PRICE 20p**

## TRANSISTOR TESTER

Although surplus transistors are excellent value, a small percentage are usually duds. The transistor tester to be described in the April issue has been specifically designed to sort these out. Both NPN and PNP devices can be tested and an unusual feature is that gain is directly read off, even though the meter used is of the cheapest type available. This is a thoroughly ingenious project for its simplicity—be sure not to miss it.



**ALL IN THE APRIL ISSUE  
ON SALE 3rd. MARCH**

# SHORT WAVES

## THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz ● Times in GMT

**Q**UITE an easy month on the Amateur bands with not too many scribes sending in logs. I expect you're all still getting over the excitement of Christmas plus the novelty of the presents. Hands up all those who got a nice new receiver?

Some reporters have bemoaned the difficulties of learning to read c.w. signals and have asked if there is any "easy" way to pick up the morse code. If you own a tape recorder then you're half way there. All you need is some sort of morse key and buzzer (or better still an oscillator) and you can record your own morse. This will give you practice at sending and you can then play the tape back and practice reading also. Advantage is that you can send at just the right speed for your particular ability at receiving. Hint; use groups of mixed letters which don't make any sense, i.e., AMSZX, ATHQP, etc. This stops you anticipating the next character and makes sure that you really do "read" every symbol.

Another aid is the many slow morse transmissions which members of the R.S.G.B. put out specifically for those wishing to learn to read c.w. Topband is a favourite and since these stations are located all over the country there is almost certain to be a local station near you. In any case, you can see how many of the slow c.w. members you can log. There is some very good d.x. to be heard on c.w. On topband, for example, down very close to 1.8MHz you can often hear W stations. So get a copy of the code, learn it and start using your receiver to the full. Incidentally, you need a b.f.o. for c.w. reception and if you are one of the many who are just getting your feet wet on the amateur bands with a commercial broadcast-type receiver which happens to cover short waves but which doesn't have a b.f.o., then take a peep at the January 1972 issue of Practical Wireless. On page iii of the Experimenters Circuits Supplement you will find a very simple circuit for a b.f.o. which can be used in conjunction with most receivers. Check that your receiver has an i.f. of 465kHz or 1.6MHz otherwise you will need to change the i.f. transformer shown in the circuit. Incidentally, this external b.f.o. will also enable you resolve single sideband too.

If you kid yourself that you are already well proficient in the gentle art of reading c.w., try tuning in at 1900g.m.t. on the first Tuesday of each month. Listen on 3.520MHz for the G3BZU morse proficiency transmissions. These rattle merrily away at 20, 25, 30, 35, and 40 words per minute. If you get it all down 100 per cent correct and send it with 10p to the QRQ Manager, RNARS, H.M.S. Mercury, Leydene, Petersfield, Hants, you get a nice certificate which tells all and sundry what a super dot and dash sorter-outer you really are.

Another query which keeps cropping up in the mail is the one involving some poor s.w.l. who, while reading about beams and long wires, is stuck in a

room on the umpteenth floor of a "no aerials allowed" block of flats.

One idea is to build an a.t.u. (antenna tuning unit) and put a length of wire around the picture rail. Another sneaky (but effective) aerial is made by getting a length of enamelled copper wire, about 24 s.w.g., boring a hole in a small sorbo ball and pushing the end of the wire through and anchoring or tying it. You can now lower the ball out of the window and play out the wire. You've virtually got a vertical antenna and the good thing is that even with A1 vision, 24 s.w.g. enam. is invisible at more than a few feet. Idea of the rubber ball is to weight the wire and hold it down and also, if it's windy, the ball doesn't stove in someone's window 22 floors down. The idea of using some form of metal rod clipped to the window ledge will work but there is always the hazard that it will fall off and skewer some poor soul to the sidewalk—definitely not recommended!

Gibby's been chattering again and not getting on with the logs, but some questions in the mail come up again and again, so periodically it seems a good idea to answer these.

**Chris Kitchener** (Haverhill) has been swotting for O-levels and the R.A.E. (gd 1k OM). Time between "swots" brought signals from SV0WII, SM4DIT/MM, VK2YU, ZD3D, ZL3RB, 4X4SM, 8R1J, 9H1CU and 9J2JY all on a TR500SE receiver and PR30 pre-selector plus a tank whip at 36ft.

Interesting letter from **John Stevenson** (Woking) who has been playing with a solid state direct conversion receiver. This has two BC108's as a product detector fed from the aerial, BC108 b.f.o. and another three BC108's as an a.f. amplifier. Aerial is 50ft. end fed "wrapped round an oak tree." (Bet it brings in the signals a "Treet"). Preliminary peeps on 14MHz raised visions of CT1BT, IS1LID, IT9CLB, PY7EXY, UA3IQO, UB5AD, ZE1BP, 5Z4GK, 9H1GK.

**Howard Dearing** has dropped the s.w.l. prefix and now talks back signing G3XVX. Rig is a homebrew running 25W p.e.p. and 10W c.w. Receiver is a Hammerlund Super Pro with a homebrew topband converter using 3.1-3.3MHz as an i.f. Howard's log for 1.8MHz stations worked (I'm green already) reads: K2GNC, K8RNE, VE3EK, W1WQC, W2FD, W2IU, W2UEZ, W3GM, W4WFL/1, W4QCW, ZD8AY (Ascension Island) all on c.w. On s.s.b. the log reads: W1WQC, W1HGT, W2HCW. Antenna is an inverted L Marconi with 55ft. vertical section some 10ft. longer than an electrical quarter wave and tuned with a series capacitor. Earth system is a radial affair plus 12 buried copper pipes.

*Logs, in alphabetical order please, to arrive by the 15th of the month to:*

**12 Cross Way, Harpenden, Herts.**

**HENRY'S** FOR **FIRST GRADE** BRAND **NEW** **BRANDED** GERMANIUM and SILICON TRANSISTORS, DIODES, RECTIFIERS, TRIACS, FETS, ZENERS, BRIDGES and INTEGRATED CIRCUITS  
 BY ATES · EMIHUS · FAIRCHILD · FERRANTI · I.T.T. · MULLARD · NEWMARKET · PHILIPS · R.C.A. · TEXAS

**TRANSISTORS**

**A SELECTION FROM OUR LIST**

AA130	10p	BD115	75p	OC16	50p	2N1803	18p
AA132	15p	BD123	85p	OC20	35p	2N1804	22p
AA213	10p	BD124	80p	OC22	50p	2N1805	22p
AA215	10p	BD131	75p	OC23	60p	2N1806	25p
AA217	10p	BD132	80p	OC24	60p	2N1807	25p
AC107	35p	BDY11	OC25	40p	2N1807	25p	
AC126	30p		OC26	25p	2N1808	25p	
AC127	25p	BDY17	OC28	60p	2N1809	25p	
AC128	20p		OC29	60p	2N1813	20p	
AC178	20p	BDY38	OC35	50p	2N2147	75p	
AC187	25p	BDY60	OC36	80p	2N2160	80p	
AC188	25p		OC42	40p	2N2217	25p	
AC188	25p		OC43	50p	2N2218	25p	
AC197	30p	BF116	OC44	15p	2N2218A		
AC198	25p	BF154	OC45	12p			
AC198	25p	BF158	OC70	12p	2N2219	20p	
AC199	20p	BF159	OC71	12p	2N2219A		
AC230	20p	BF180	OC72	20p			
AC232	10p	BF194	OC75	25p	2N2220	25p	
AC239	55p	BF195	OC76	25p	2N2221	20p	
AC240	55p	BF196	OC77	40p	2N2221A		
AF115	18p	BF197	OC81	20p			
AC244	25p	BFX13	OC81D	20p	2N2222	20p	
AD140	50p	BFX29	OC81Z	40p	2N2222A		
AD149	50p	BFX30	OC83	25p			
AD161	35p	BFX34	OC84	25p	2N2369	15p	
AD162	35p	BFX35	OC139	25p	2N2369A		
AF114	25p	BFX36	OC140	40p			
AF115	25p	BFX37	OC141	60p	2N2646	40p	
AF116	25p	BFX38	OC170	25p	2N2904	20p	
AF117	20p	BFY18	OC171	12p	2N2904A		
AF118	20p	BFY50	OC200	40p			
AF124	25p	BFY61	OC201	75p	2N2905	25p	
AF125	20p	BFY62	OC202	20p	2N2905A		
AF126	20p	BFY63	OC206	25p			
AF127	20p	BFY90	OC271	97p	2N2906	20p	
AF139	30p	B8X20	ORP12	50p	2N2906A		
AF180	50p	B8X21	ORP60	40p			
AF181	45p	B8Y27	ST140	15p	2N2907	25p	
AF186	50p	B8Y34	ST141	20p	2N2907A		
AF186	40p	B8Y35	TIP29A	50p			
AF239	40p	BU105	TIP30A	60p	2N2925	15p	
AS296	25p	BY100	TIP31A	60p	2N2920	10p	
AS297	30p	BY126	TIP32A	70p	2N3011	20p	
AS298	25p	BY124	TIP33A	20p	2N3053	20p	
AS299	30p	BY122	TIP33A	10p	2N3054	50p	
AS291	35p	BYZ10	TIP34A	10p	2N3055	75p	
BA100	15p	BYZ11		1.50			
BA102	30p	BYZ12	TS143	40p			
BA110	20p	BYZ13	TS160	12p	2N3614	55p	
BA115	7p	BZ778L	TS161	10p	2N3702	10p	
BA133	5p	GE1102	TS162	10p	2N3703	10p	
BA136	7p	GE1103	TS166	12p	2N3704	12p	
BA137	7p	GE1111	TS169	20p	2N3705	10p	
BA138	15p	GE1113	TS182	25p	2N3707	12p	
BC107	10p	GE1114	V405A	25p	2N3708	10p	
BC108	10p	GE1115	VR525	35p	2N3714		
BC109	10p	GE1116	W01	30p			
BC109C	12p	GE1117	W06	45p	2N3715	22p	
BC113	10p	GE1118	ZTX107	15p			
BC114	20p	GE1119	ZTX108	15p	2N3716	22-25	
BC115	20p	GM378A	ZTX109	15p			
BC116	20p	MAT101	ZTX300	12p	2N3771	22-25	
BC116A	25p	MAT101	ZTX301	15p			
BC117	20p	MAT121	ZTX302	20p	2N3772	22-25	
BC118	20p	MAT224	ZTX303	25p			
BC119	30p	MJ420	ZTX304	25p	2N3773	22-25	
BC134	20p	MJ421	ZTX500	15p			
BC135	15p	MJ2801	ZTX501	15p	2N3791	22-25	
BC136	20p		ZTX502	20p			
BC137	20p	MJ2901	ZTX503	17p	2N3818	35p	
BC138	20p		ZTX504	40p	2N3820	55p	
BC147	12p	MJE340	ZTX531	25p	2N3823	50p	
BC148	12p	MJE370	IN914	7p	2N3824	95p	
BC149	12p	MJE371	IN916	10p	2N3903	20p	
BC153	20p	MJE520	IN4148	7p	2N3906	25p	
BC154	20p	MJE521	IS44	7p	2N4088	12p	
BC167	15p	MJE525	IS221	7p	2N4081	12p	
BC169	12p		IS222	9p	2N4092	12p	
BC169C	15p	MJE3065	2G301	25p	2N4289	12p	
BC177	20p		2G302	30p	2N4280	12p	
BC178	20p		2G303	35p	2N4871	35p	
BC179	20p	MPSA56	2N404	20p	2N5457	30p	
BC1821	10p	MPSA101	2N696	15p	2N5458	35p	
BC1831	10p	MPSA106	2N697	15p	2N5459	40p	
BC1841	12p	MPSA107	2N698	30p	40250	50p	
BC212L	12p	NKT214	2N706	10p	40360	40p	
BC213L	12p	NKT216	2N708A	12p	40361	40p	
BC214L	15p	NKT403	2N708	15p	40362	50p	
BCY30	35p	NKT404	2N830	20p	40430	1.00	
BCY31	40p	OA15	2N987	40p	40543	65p	
BCY32	60p	OA10	2N1131	25p	40594	1.05	
BCY33	60p	OA47	2N1132	25p	40595	1.05	
BCY34	35p	OA70	2N1802	18p	40636	1.10	
BCY38	45p	OA79					
BCY39		OA81					
BCY40	1.00	OA90					
BCY40	1.00	OA91					
BCY70	15p	OA95					
BCY71	20p	OA200					
BCY72	15p	OA202					

Full transistor list available—send for your free copy today!

**HENRY'S** LOW COST **INTEGRATED CIRCUITS**

**BRAND NEW FULL SPECIFICATION TTL74 SERIES**  
**BRANDED FAIRCHILD, I.T.T. AND TEXAS**  
 DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICES

No.	Description	1-11	12-24	25-99	100+	250+
7400	Quadruple 2-input NAND gates	20p	18p	14p	14p	12p
7401	Quad 2-input open collector NAND gates	20p	18p	16p	14p	12p
7402	Quad 2-input NOR gates	20p	18p	16p	14p	12p
7403	Quad 2-input open collector NAND gates	20p	18p	16p	14p	12p
7404	Hex inverter	20p	18p	16p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	16p	14p	12p
7410	Triple 3-input NAND gates	20p	18p	16p	14p	12p
7413	Dual 4-input Schmitt triggers	20p	18p	16p	14p	12p
7420	Dual 4-input NAND gates	20p	18p	16p	14p	12p
7430	Single 8-input NAND gates	20p	18p	16p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	16p	14p	12p
7441	BCD-Decimal decoder/Hex driver	75p	72p	70p	60p	55p
7442	BCD-Decimal decoder (4-10-line) TTL O/P	75p	72p	70p	60p	55p
7443	Excess 3-Decimal decoder TTL outputs	1.00	95p	90p	80p	70p
7447	BCD-Decimal 7 seg. decoder/indicator driver	1.10	1.00	1.45	1.30	1.15
7448	BCD-Decimal 7 seg. decoder/indicator driver TTL O/P	1.10	1.00	1.45	1.30	1.15
7450	Expand dual 2-input AND-OR-INVERT gates	20p	18p	16p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	16p	14p	12p
7452	Quad 2-input expand AND-OR-INVERT gates	20p	18p	16p	14p	12p
7454	4-wide 2-input AND-OR-INVERT gates	20p	18p	16p	14p	12p
7480	Dual 4-input expanders	20p	18p	16p	14p	12p
7470	Single J-K flip-flop (gated inputs)	30p	27p	25p	20p	18p
7472	Single J-K flip-flop (gated inputs)	30p	27p	25p	20p	18p
7473	Dual J-K flip-flop	40p	37p	35p	30p	28p
7474	Dual J-K flip-flop	40p	37p	35p	30p	28p
7475	Quadruple bistable latch	45p	42p	40p	35p	30p
7476	Dual J-K flip-flops with Preset and Clear	40p	37p	35p	30p	28p
7480	Gated Full Adder	80p	75p	70p	55p	50p
7481	16-bit read/write memory	1.25	1.15	1.10	1.00	90p
7482	2-bit binary Full Adder	1.00	90p	85p	80p	75p
7483	4-bit binary Full Adder	1.00	90p	85p	80p	75p
7484	16-bit RAM with gated write inputs	1.00	85p	80p	75p	71p
7486	Quadruple 2-input Exclusive OR gates	45p	41p	38p	35p	32p
7490	BCD decade counter	75p	70p	65p	60p	55p
7491	8-bit shift register	1.00	95p	90p	80p	75p
7492	Divide twelve counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	80p	75p	70p	65p	60p
7494	Dual entry 4-bit shift register	80p	75p	70p	65p	60p
7495	4-bit up-down shift register	80p	75p	70p	65p	60p
7496	5-bit parallel/serial in/out shift register	1.00	90p	85p	80p	75p
74100	8-bit bistable latch	2.00	1.80	1.75	1.50	1.40
74118	Hexuple Set-Reset latches	1.00	95p	90p	80p	75p
74121	Monostable multivibrators	80p	75p	70p	60p	55p
74141	BCD-Decimal decoder/Hex driver	1.00	95p	90p	80p	75p
74145	BCD-Decimal decoder (1-4-line) TTL O/P	1.00	95p	90p	80p	75p
74160	16-bit data selector/multiplexer	2.25	2.20	2.25	2.15	2.05
75151	8-bit data selector/multiplexer	1.10	95p	90p	80p	75p
74163	Dual 4-line to 1-line data selector/multiplexer	1.35	1.27	1.20	1.15	1.10
74154	16-bit decoder/demultiplexer	2.00	1.75	1.65	1.50	1.45
74155	Dual 2-line to 4-line decoder/demultiplexer	1.55	1.47	1.35	1.30	1.25
74156	Dual 2-line to 4-line decoder/demultiplexer	1.55	1.47	1.35	1.30	1.25
74190	Sync decade up-down counter, 1-line mode	1.95	1.85	1.75	1.60	1.50
74191	Sync 4-bit up-down counter, 1-line mode	1.95	1.85	1.75	1.60	1.50
74192	Sync decade up-down counter, 2-line mode	2.00	1.90	1.80	1.65	1.55
74193	Sync 4-bit up-down counter, 2-line mode	2.00	1.90	1.80	1.60	1.50
74196	Asynchronous presetable 4-bit binary counter	1.50	1.40	1.30	1.10	1.00
74197	Asynchronous presetable 4-bit binary counter	1.50	1.40	1.30	1.10	1.00

Complete data on the above in booklet 20 pages, Ref. 29, Issue 2 at 15p post paid.  
 Texas I.C. Handbook. Complete information on 100 types. 40p. Post 10p.  
 Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 25p.

**INTEGRATED CIRCUITS**

MFC4000P	55p
MFC4010P	60p
ICL2	22.50
FA246	21.50
TAD100	21.50
TAD110	21.50
MC724P	50p
709C(T05)	75p
709C(T05)	45p
709C(D.I.L.)	45p
723C(T05)	1.00
741C(T05)	2.00
MC1303P	22.25
MC1304P	21.50
741C(D.I.L.)	75p
914(T05)	40p
923(T05)	40p
TOSHIBA	
20 wait amp.	24.47
TOSHIBA	
Pre amp	1.50

**PLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier**  
 \$14.00  
 Complete with 8-page booklet, circuits and data.  
**£1-50 ea.**

**ZENER DIODES**

1-25	100	500	1000
24	+	+	+
400m/w			
BZY 88 series*	12p	10p	8p
14 watt			
ZL series	25p	25p	20p
3 watt			
3TZ series	30p	27p	25p
10 watt			
ZS series + 40p	37p	35p	30p

All types are 5%. Wire ended - these stand in voltages 3-300 volt in all standard voltages. \*3-33 volt.

**TRIACS**

Stud with accessories

P.I. Current	1-11
Type volts	
SC35A	100 3 amps 80p
SC35B	200 3 amps 85p
SC35D	400 3 amps 90p
SC40A	100 6 amps 90p
SC40B	200 6 amps 1.05
SC40D	400 6 amps 1.00
SC45A	100 10 amps 1.05
SC45B	200 10 amps 1.15

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



**Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the practical way.**

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable TECHNATRON Self-Built Outfit take the mystery out of the subject, making learning easy and interesting.

**Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!**

... and what’s more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN—but it’s as fascinating as a hobby**

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

### New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of “OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO”. This brand new booklet—just out—tells you all about TECHNATRON and B.I.E.T.’s full range of courses.



## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF

### POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF  
Please send book and full information — FREE and without obligation.



NAME ..... AGE .....  
BLOCK CAPITALS PLEASE  
ADDRESS .....

OCCUPATION .....

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Accredited by the C.A.C.C.

1016

# WICKS FOR BARGAINS

### E.A. STEREO AMPLIFIER:

5 watts per channel; In attractive afrormosia veneered sleeve. Controls: On-off volume; Bass: Treble: Balance: Selector: Headphone Jack. Ceramic or Magnetic PU. Radio and Tape Inputs: Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14½”W x 9½”D x 45”H approx. £16.50 inc. post.

- Guaranteed all brand new best quality goods. No rubbish.
- Mail order only.
- All enquiries SAE please.

### 3 WAY SPEAKER SYSTEM:

8” twin cone Bass speaker and 3” tweeter, fitted in extremely elegant teak veneered cabinet. Size : 18½”H x 11½”W x 10”D. 8 ohms handle 10 watts. £7.50 inc. Carr.

### GARRAD OFFERS

**Garrad SP25 Mk III** (Rec. Price (£15.85) **Our Price £11.25.** Carr. & Ins. 50p.

**Garrad SP25 Mk III** ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23.19). **Our Price £16.** Carr. & Ins. 75p.

Or with choice of fitted cartridges. **SP25 Mk III/Sonotone 9TAHC** (Rec. Price £27.29) **Our Price £18.** Carr. & Ins. 75p.

**SP25 Mk III/Shure M3DM** (Rec. Price £31.02) **Our Price £20.** Carr. & Ins. 75p.

**SP25 Mk III/Goldring G800** (Rec. Price £36.19) **Our Price £21.** Carr. & Ins. 75p.

**SP25 Mk III/Shure M55E** (Rec. Price £36.16) **Our Price £21.** Carr. & Ins. 75p.

**Note! Garrad SL65B** (Automatic Changer version of **SP25 Mk III**) alternatively supplied—please add £3 to above prices.

**Garrad AP76** (Rec. Price £27.85) **Our Price £18.85.** Carr. & Ins. 50p.

**Garrad AP76** ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs). Please state choice. (Rec. Price £39.85). **Our Price £24.94** Carr. & Ins. 75p.

### OR WITH CHOICE OF FITTED CARTRIDGES.

**Garrad AP76/Shure M3D** (Rec. Price £47.26) **Our Price £28.94.**

Carr. & Ins. 75p. **Garrad AP76/Shure M55E** (Rec. Price £52.82). **Our Price £31.35.** Carr. & Ins. 75p.

**Garrad AP76/Goldring G800** (Rec. Price £52.82) **Our Price £31.35.** Carr. & Ins. 75p.

**Garrad 2025TC** fitted with stereo/mono cartridge. £8.99. Carr. Paid.

**TEAK PLINTH & PERSPEX COVER** Ready cut to take 2025TC, SP25 III, SL65B available at £4.99. Carr. & Ins. 35p.

### CARTRIDGES (All with diamond stylus)

**Sonotone 9TAHC** dia. Rec. Price £4.10. **Our Price £1.99**

**Shure M3DM** (Rec. Price £7.41) **Our Price £4.87.**

**Shure M55E** (Rec. Price £12.97) **Our Price £9.00.**

**Goldring 800** (Rec. Price £13.00) **Our Price £7.50.**

**Goldring 800 H** (Rec. Price £10.69) **Our Price £6.99.**

P & P 18p any type

**Special Offer!**  
Grundig GDM312  
Dynamic Microphones. List £7.35  
**OUR PRICE £3.**  
P & P 30p

**Hi-Fi Stereo Headphones**  
(Value £5.00)  
Only £2.25 inc. post.

**Speaker Cloth**  
Best quality. Width 36”. Under half price at 55p per yd. Black with gold fleck, will blend with any room setting. End of stock line. Yds and yds must do.

**Plugs, Sockets and Leads.**

Phono plugs: 3p each  
30p per dozen.  
2 pin Din spkr. plugs 10p each.  
3 pin Din plugs. 15p each.  
5 pin Din plugs. 13p each.  
5 pin Din sockets (chassis) 7p each.  
Stereo Jack Sockets c/cct. 13p each.  
Phono sockets (chassis) 2 way 3p; 3 way 4p; 4 way 5p.  
6ft. stereo lead 5 pin Din to open end. 45p  
6ft. stereo lead 2 phono to open end. 37p  
12ft. spkr. lead 2 pin Din to open end. 40p.  
Please add P & P 5p.

**100 Mixed Resistors**  
½ watt 10% all best quality (no ex government) 40p.

**Pots**  
100K x 100K lns & Logs. stereo. 35p inc. post.  
100K DP switch stereo. log. 45p inc. post.  
50K single Balance. 15p inc. post.

**4 B.A. brass nuts**  
50 for 25p inc. post.

**Speaker cabinets**  
Attractively veneered in afrormosia, black front. Size approx. 7½”W x 9½”D x 4½”H. Ready cut to take 8” x 5” speaker. £1.99. P. & P. 12p.

**D. T. WICKS & CO. 49 North Station Rd, Colchester, Essex.**  
Tel: (0206) 78807

# LETTERS... The Editor does not necessarily endorse the views expressed by correspondents

## Bottled-up

With regard to Mr. D. Smith's letter (January 1972 issue), I would like to point out to him that he most certainly is not the last of a "dying breed." Speaking as an ardent valve lover, I personally believe that the transistor will never completely overcome the valve, as if it does it would bring about the downfall of amateur radio as we know it. As for integrated circuits, they are beneath contempt and unworthy of further comment. So Mr. Smith is definitely not alone and does most decidedly have "relatives somewhere" as far as valve lovers are concerned—807's in particular.—**P. I. Martin** (*Sussex*).

\* \* \*

Having worked on several transistor radios which almost fall to pieces when you try to service them I can appreciate D. H. O. Smith's preference for valves.

However I am wondering if valve enthusiasts can take hope, for I notice that quite a number of instruments are using a device which in effect is a miniature valve and called a nuvistor. Is this the valve making a comeback? Having unsuccessfully tried to obtain some literature on these nuvistors I am wishing some day the editor will commission an article on these to lighten our darkness.

Until the happy day when valves return may we not lift any printed circuits with soldering irons or blow up half a dozen transistors when searching for one faulty one.—**K. Freeby** (*Plymouth*).

\* \* \*

I too suffer from being one of that dying breed. Mr. Smith has my complete sympathy. 99.9% of my equipment is fully "bottleized," including a 50 watt r.m.s. (sine wave drive) amplifier which has given no trouble for about 3 years. Everything I build with valves works first time and goes on working. Few people realize how easy and cheap valve

equipment is to make, and in my opinion valves are best for starting people off on electronics, because, electrically, they are infinitely more robust than transistors. To any other valve enthusiasts—please, please write to this column and make your existence known. Incidentally the 50 watt amplifier can be made for £30 complete.—**T. Watton** (*Hull*).

\* \* \*

I agree with D. H. O. Smith (Herts) "Dying Breed"—January '72. He is not alone in his support for the radio valve.

I do a fair amount of servicing of valve sets and I would support the valve against the transistor for tone and quality (except for the larger transistor sets which have larger loudspeakers, etc.—**J. F. Wade**, (*Leyland, Lancs*)).

## Cassette deck

With the advent of the tape cassette isn't it about time some manufacturers put onto the market a cassette deck.

By this I don't mean a recorder with pre-amps and record amps to be used with an external amplifier such as a Hi-Fi system. But strictly speaking a tape transport. Where the individual can build his own tape recorder as he would with a reel to reel machine. It is pleasing to see in *Practical Wireless* the building of recorders but there is an increasing lack of tape transporters, only one being advertised at the present time in this magazine.

For a variation one has to go to the upper price brackets such as Brenell and TRD decks. So come on manufacturers how about a tape transport for cassette tape-recorders.—**V. C. Watts** (*Bath, Somerset*).

## Join the club

I should be most grateful if some publicity could be given to our club through the medium of *Practical Wireless*. The club was formed early in 1970 and today,

with over a hundred members, has its own club rooms at 81 Virginia Street, Glasgow, Cl.

Meetings are held each Friday at 8 p.m., at which slow morse is given by GM3HLQ. Lectures by club members and the occasional film form the main subject material of our meetings.

On the premises we have our own club station, with call sign GM4AGG, which is active on the HF bands with a KW2000, 70MHz with a Pye Ranger, and 144MHz with an IC2F.

On December 10th we held our first annual dinner at which GM3AEL (Zonal Rep.) presented our club with the Scottish N.F.D. Trophy for 1971.—**Victor T. Budas**, GM3VTB, (*Hon. Sec. 28 Kelvin-side Gardens, Glasgow, N.W.*)

## Transformed!

May I reply to Mr. R. Wibberley's letter in the December issue in which he condemns modern methods of transformer winding.


He states, "Enamelled wires are clearly inferior and unreliable. More so when wax impregnated." Correctly used, with the layers of wire separated with suitable insulation, enamelled windings are extremely hardy. Why else would they have become practically the standard material in low to medium power transformers? As a bonus, enamelled wire is cheaper and much less bulky than Mr. Wibberley's preferred silk-covered winding.

Mr. Wibberley also says, "Oil insulated windings are inferior, especially when mains voltages are used in primary windings." May I point out that National Grid transformers are completely immersed in oil for cooling purposes and these devices operate reliably at voltages between 11kV and 400kV.—**C. Wright** (*Northants*).


### DIARY DATE:

Paris Audio Festival  
March 9-14

# GOING BACK...

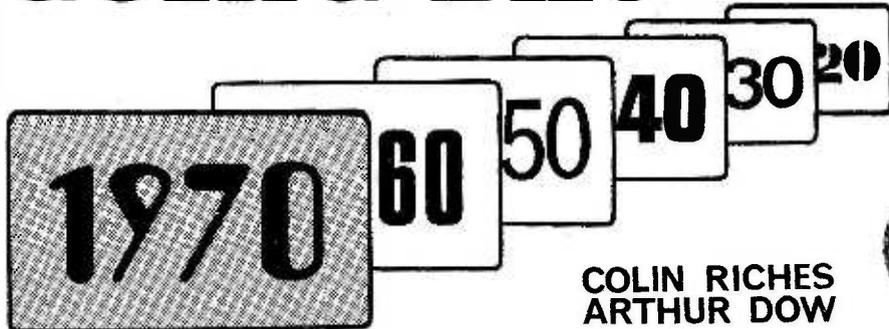

COLIN RICHES  
ARTHUR DOW

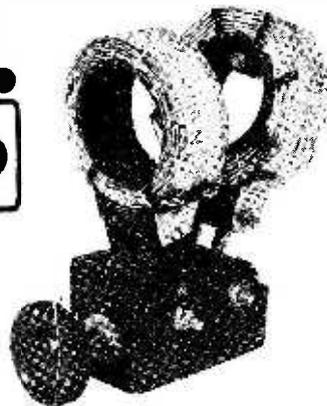

**V** P. MILLS, writing from 9 Fryars Bay, Beaumaris, Anglesey, Wales, says, "I possess a piece of ancient equipment owned by my father. It is a Sterling 2-valve upright cabinet receiver type BR2, instrument number 198 manufactured by Sterling Telephone and Electric Co. Ltd., London. Manufactured circa 1926 and using Marconi-Osram bright emitter valves types R5, red spot and green spot or alternatively type DER. The set is complete with Sterling headphones.

Unfortunately at some time the set was dismantled and whilst I have rescued the components concerned, I am devoid of the all important circuit diagram.

Recently I have been lucky enough to purchase another set found in an old workshop perched on a Welsh hillside. It is an exceptionally small receiver with valve holders and reaction coils located externally on top of the metal case. The set is titled "Polar Twin Receiving Set" (no Model No. or Serial No. given) and bearing a notice stating "Use with Mullard-Polar Valves".

Valves actually used are believed to be PM1 and PM1A. This set is also believed to date from 1925-6.

A very small S. G. Brown Hornspeaker was available, this has been restored and is now operational. There are a few loose ends within the receiver however which I think I can unravel.

I am particularly anxious to get these receivers

operational and Hamilton Radio who offer service sheets back to 1925 have not been able to help so I am writing in the hope that as a focal point of Veteran Radio you may be able to help or alternatively suggest a possible source of supply of relevant circuits.

I would also be very pleased to hear of any known source of supply of R5 or DER valves. Meanwhile keep the good work going, I hope to be able to join in shortly."

Mr. D. J. Lord, of 61 Empingham Road, Stamford, Lincs. tells us that although he was not around during the 20's and 30's, he has found the "Going Back" articles on the early days of radio most interesting.

On reading the article in last April's issue, he saw that Mr. F. C. Burgess has an old Marconiphone 2 valve set, which from his description must be very similar to the one that he has himself.


Mr. Lord enclosed a photograph of his set, the details of which are:—

Marconiphone V2A Long Range Model Type RB1B, Long Range Model M19, Inst. No. S/E 3926, G.P.O. Reg. No. 0175. Approved by the Postmaster Gen.

The set is still in working order, and is complete with a Marconi Distributor Unit for up to four pairs of headphones, and plug in coils and regenerator units covering the range 340-440m, 390-530m and 1300-1700m Long Wave.

The date of manufacture, or the original cost are not known, but he has always assumed that it was about 1923, and would be interested to learn the exact year if any reader can advise him. (We at P.W. would have said about 1924-1926)

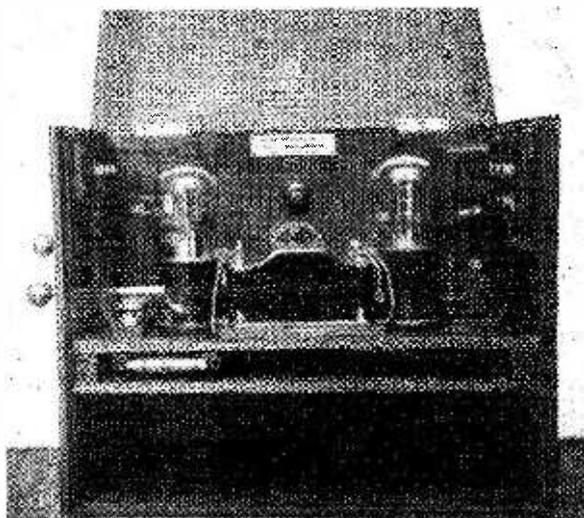He also has a copy of the BBC Hand Book for 1928, which contains an interesting selection of photographs and descriptions of the range of wireless sets available at that time, all of which appear to be of a considerably later design than his Marconiphone model.



Mr. D. J. Lord's receiver.

## Vintage CC

### BOOKS FOR DISPOSAL

...to sell: "More Practical Valve Circuits" by John Scott-Taggart, published in 1923. The first circuit is No. 68 and they go on to No. 151. Offers invited.—J. H. Greer, North Lodge, Great Ponton, Grantham, Lincolnshire.

...a three-volume copy of the Harmsworth's Wireless Encyclopedia and a bound copy of Wireless World for October 1923 to March 1924. I will sell to the highest bidder.—J. C. Porter, 15 Millais Gardens, Edgware, Middlesex.

...Harmsworth's Wireless Encyclopedia: three volumes with illustrations in good clean condition. Offers please.—C. Lesser, 7 Clippesby Close, Chessington, Surrey.

...a three-volume set of Harmsworth's Wireless Encyclopedia (1923).—Peter Thornhill, 5 Fourth Avenue, Scampton, Lincolnshire.

# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

**10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND**


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 8" x 2 1/2" Speaker. Air Spaced ganged Tuning Condenser with VLF section. Volume on/off. Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

**£8-50**

P. P. & Ins. 50p

(Overseas P. & P. £1)

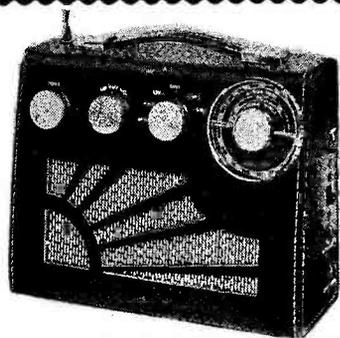

## ROAMER EIGHT Mk I

**NOW WITH VARIABLE TONE CONTROL**

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 9 transistors plus 3 diodes. 8" x 2 1/2" Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)



## ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.


Total building costs **£5-98** P. P. & Ins. 41p. (Overseas P. & P. £1)


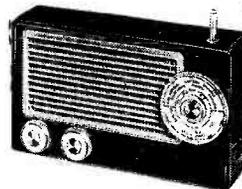
## ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


Total building costs **£3-98** P. P. & Ins. 26p. (Overseas P. & P. £1)


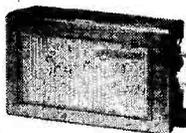
## POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 6 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 21p. (Overseas P. & P. 63p)




## TRANSONA FIVE

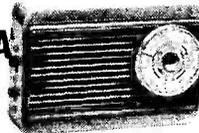**NOW WITH 3in SPEAKER**

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stages—6 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone 3in. moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts Price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 22p. (Overseas P. & P. 63p)




## TRANS EIGHT

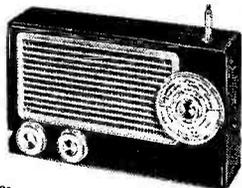**8 TRANSISTORS and 3 DIODES**

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P. P. & Ins. 31p. (Overseas P. & P. £1)



## NEW! "EDU-KIT"

**BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.**

**COMPONENTS INCLUDE:**  
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4x2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs.  
Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction

All parts including **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)

**FULL AFTER SALES SERVICE**

\* Callers side entrance Barratts Shoe Shop  
\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

PW.39

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722-9090

0A2	.30	6BZ6	.31	6SA7M	.35	12S77	.33	50L6GT	.45	EB34	.20	EL34	.44	KTW61	.33	PL38	.90	UCH42	.60	AC107	.15	BCY33	.30	OA390	.96	
0B2	.30	6CB6A	.38	6SC7GT	.33	12SK7	.24	85A2	.43	EB91	.10	EL35	1.00	KTW62	.33	PL81	.44	UCH81	.30	AC118	.25	BCY38	.23	OA292	.10	
0Z4	.25	6C4	.28	6SC7GT	.33	12SQ7GT		90C1	.59	EB41	.48	EL37	.74	KTW63	.50	PL81A	.48	UCH82	.33	AC127	.17	BCY39	.23	OA293	.10	
1A7GT	.33	6C9	.73	88H7	.33			50	150B2	.68	EB81	.29	EL41	.53	MHL66	.75	PL82	.30	UCH83	.43	AC128	.43	BF158	.29	OC23	.38
1B3GT	.35	6CD6G	1.06	68J7	.35	14H7	.48	807	.59	EB91	.28	EL42	.63	N78	2.05	PL83	.32	UF41	.50	AC154	.25	BF159	.25	OC24	.38	
1H5GT	.33	6CQ8A	.50	68K7GT	.23	14S7	.75	6702	.80	EBF80	.30	EL81	.50	N308	.95	PL84	.30	UF42	.60	AC156	.20	BF163	.20	OC25	.38	
1L4	.18	6CH6	.43	68Q7GT	.38	19A95	.24	3763	.50	EBF83	.38	EL83	.38	N329	.44	PL504/500		UF80	.35	AC157	.25	BF173	.38	OC26	.24	
1N5GT	.37	6CL6	.43	6V6G	.17	19B6G	.85	AC2/PEN		EBF89	.27	EL84	.22	P61	.44			UF85	.34	AC155	.25	BF181	.40	OC29	.68	
1R5	.26	6CM7	.50	6V6GT	.30	19G6	.50			EBL21	.60	EL85	.40	PAB60	.33	PL505	1.30	UF86	.65	AC166	.25	BF185	.40	OC35	.32	
1B4	.38	6CU6	.30	6X4	.50	20D4	1.05	AC2/PEN		EBL22	.60	EL86	.40	PAB60	.33	PL506	1.30	UF86	.65	AC168	.25	BF185	.40	OC35	.32	
1U4	.29	6CW4	.33	6X5GT	.25	20P2	.65	DD	.88	EB88	.59	EL91	.23	PC88	.47	PL509	1.30	UL41	.54	AC176	.55	BF194	.15	OC36	.43	
1U5	.48	6DE7	.50	7A7	.88	20L1	.98	AC6/PEN	.38	EC92	.34	EL93	.32	PC95	.53	PL802	.75	UL84	.31	AC177	.25	BFY50	.23	OC42	.63	
2D21	.85	6DT6A	.50	7B6	.68	20P1	.50	AC/PEN(7)		ECC32	1.50	EL96	.75	PC97	.36	PM84	.34	UM80	.38	AC177	.25	BFY51	.19	OC44	.10	
2CK5	.50	6EW6	.55	7B7	.32	20P3	.79			ECC33	1.50	EL96	.49	PC900	.32	PX4	1.16	UY41	.38	ACY18	.20	BFY52	.20	OC45	.11	
2A4	.25	6F1	.59	7C6	.30	20P4	.89	AC/TH1	.50	ECC40	.60	EM80	.38	PC984	.29	PX25	.96	UY85	.25	ACY19	.19	BY106	.18	OC70	.13	
3D6	.19	6F8	.68	7H7	.38	20P5	1.00	AC/TP	.98	ECC81	.18	EM81	.39	PC986	.26	PY33/2	.50	U10	.45	ACY20	.18	BY114	.18	OC71	.11	
3D4	.35	6F6G	.35	7R7	.45	25A9G	.29	AL80	.78	ECC82	.19	EM83	.75	PC988	.41	PY80	.33	U12/14	.38	ACY21	.19	BY126	.15	OC72	.11	
3Q5GT	.35	6F13	.38	7Z4	.50	25L6G	.20	ATP4	.13	ECC83	.22	EM84	.31	PC989	.45	PY81	.24	U13/20	.75	ACY22	.15	BY144	.18	OC73	.11	
3S4	.25	6F14	.42	9D7	.78	25Y3	.38	AZ1	.40	ECC84	.28	EM85	1.00	PC189	.48	PY82	.24	U19	1.73	ACY23	.18	BY127	.18	OC74	.23	
3V4	.32	6F18	.45	10C2	.49	25Y3G	.43	AZ31	.46	ECC85	.24	EM87	.35	PC189	.48	PY83	.26	U22	.39	AD140	.36	BYZ10	.25	OC75	.11	
4CB6	.50	6F23	.68	10D7	.50	25Z4G	.28	AZ41	.58	ECC86	.40	EY61	.38	PC182	.30	PY86	.32	U25	.64	AD149	.50	BYZ11	.25	OC76	.15	
5CG8	.50	6F24	.68	10F1	.75	25Z5	.40	CL38	.90	ECC88	.35	EY61	.35	PC184	.40	PY800	.95	U26	.56	AD161	.45	BYZ12	.25	OC77	.27	
5V4G	.84	6F25	.54	10F9	.45	25Z6G	.43	CV68	.53	ECC189	.49	EY63	.64	PC186	.44	PY806	.44	U32	.78	AD193	.45	BYZ13	.25	OC78	.15	
5Y3GT	.26	6F28	.60	10F13	.35	30A5	.44	CV1C	.53	ECC80A	.55	EY84	.50	PCF200	.67	PY801	.33	U47	.64	ADT140	.63	CG12E	.20	OC78D	.15	
5Z4G	.84	6F29	.15	10L11	.63	30C1	.28	CY31	.81	ECC8071	.70	EY87/6	.30	PCF801	.29	PZ30	.48	U191	.58	AF106	.50	FSY41A	.23	OC81	.11	
6/30L2	.55	6GH8A	.50	10P13	.64	30C15	.60	DAM91	.20	ECCF80	.27	EY88	.40	PCF802	.40	QV03/10		U251	.65	AF114	.25	FSY41A	.23	OC81D	.11	
6A8G	.33	6GK5	.50	10P14	1.08	30C17	.77	DAF96	.33	ECCF82	.26	EY91	.53	PCF805	.60			U281	.40	AF115	.15	GD9	.20	OC82	.11	
6AC7	.15	6GU7	.50	12A8	.63	30C18	.60	DF91	.14	ECCF86	.64	EZ40	.40	PCF806	.57	Q805/10	.49	U282	.40	AF117	.19	GET113	.20	OC82D	.11	
6AG9	.25	6H6GT	.15	12AC6	.49	30F5	.65	D986	.53	ECCF89	.42	EZ41	.43	PCF808	.63	QV04/7	.63	U301	.40	AF121	.30	GET116	.40	OC83	.20	
6AK9	.30	6I6	.19	12AD6	.40	30FL1	.60	DH76	.28	ECH21	.63	EZ80	.21	POH200	.62	R10	.75	U403	.33	AF124	.25	GET118	.20	OC84	.24	
6AM8A	.50	6J5GT	.29	12AE6	.48	30FL2	.60	DK40	.55	ECH42	.60	EZ81	.22	PC183	.32	R11	.98	U404	.33	AF126	.13	GET119	.20	OC123	.23	
6AN8	.49	6J6	.18	12AT6	.23	30FL12	.69	DK92	.35	ECH81	.27	EZ90	.20	PC183	.32	R16	1.75	U801	.98	AF129	.65	GET123	.38	OC139	.23	
6AQ5	.22	6J7G	.24	12AT7	.16	30FL14	.68	DK96	.36	ECH83	.39	FW4/900	.75	PC184	.34	R17	.88	U4020	.38	AF178	.68	GET187	.45	OC140	.25	
6AR5	.30	6J7GT	.28	12AU6	.21	30L1	.29	DL96	.35	ECH84	.34	FW4/900	.75	PC185/85		R19	.30	U28	.40	AF180	.48	GET187S	.15	OC169	.23	
6AT8	.19	6J9A	.50	12AU7	.19	30L15	.55	DH70	.30	ECL50	.30	GZ30	.34	GZ30	.34	SP42	.75	VP41	.33	AF186	.55	GET187	.25	OC172	.35	
6AV8	.28	6K7GT	.23	12AV6	.28	30L17	.67	DM71	.38	ECL82	.80	GZ32	.41	PC186	.38	SP61	.33	VT61A	.35	AF209	.38	GET189	.23	OC200	.22	
6AV6	.28	6K7GT	.23	12AV7	.22	30P4MR	.95	DY87/6	.24	ECL83	.92	GZ33	.70	PC188	.65	TH4B	.50	VU111	.44	BA123	.45	GET189S	.23	OC201	.33	
6AW8A	.54	6K8G	.18	12BA6	.30	30P12	.69	DY802	.35	ECL84	.54	GZ34	.48	PD500	1.44	TH233	.93	VU120	.60	BA115	.14	M1	.15	OC202	.43	
6AX4	.39	6L1	.98	12BE6	.30	30P19/		E80F	1.20	ECL85	.54	GZ37	.67	PEN4DD		TP2620	.98	VU120A	.60	BA116	.25	M2	.15	OC203	.30	
6B8G	.13	6L6GT	.39	12BH7	.27	30P4	.58	E833	1.20	ECL86	.35	GZ44	.48	HA8C80	.44			VU133	.35	BA129	.13	OA9	.13	OC205	.43	
6BA8	.20	6L7GT	.38	12BL1	.35	30P11	.59	E89CC	.80	EP23	.43	HL23D	.60	PEN36C	.75	UAF42	.49	W76	.34	BA129	.13	OA9	.13	OC205	.43	
6BC8	.50	6L15	.44	12C3GT	.39	30P13	.75	E92CC	.40	EF40	.49	HL41DD	.98	PEN48	.40	UBC41	.45	W107	.50	BA130	.10	OA10	.43	ORP12	.53	
6BE6	.21	6L19	1.38	12C7GT	.33	30P14	.65	E180F	.90	EF41	.58															
6BB6	.48	6LD20	.48	12K3	.50	30P15	.87	E182CC1	.00	EF42	.33															
6B36	.39	6N7GT	.40	12K7GT	.24	35A3	.48	E1148	.53	EF94	.98															
6BQ7A	.38	6O7	.43	12SA7GT		35L6GT	.42	E150	.18	EF73	.75															
6BR7	.79	6Q7G	.27		.40	35W4	.23	E176	.88	EF80	.22															
6BR8	.63	6R7	.55	12SC7	.33	35Z4GT	.24	E18C90	.30	EF83	.43															
6BW6	.79	6R7G	.45	12SG7	.23	35Z5GT	.30	E18C91	.38	EF85	.28															
6BW7	.54	6SA7GT	.35	12SH7	.15	50EH5	.55	E1AF42	.48	EF86	.29															


All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business - Cash or cheque with order only. Post/packing 3p. per item, subject to a minimum of 9p. per order. Orders over £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p. extra per order. Complete catalogue with conditions of sale free of charge. Price by post only. Business hours Mon.-Fri. 9-5.30 p.m. Sat. 9-1 p.m. We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

## TOP QUALITY — LOW COST



## AMATEUR RADIO EQUIPMENT

★  
**NEW!**

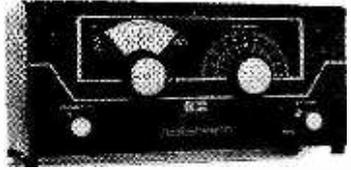


### MULTIBAND-6 TRF SHORT WAVE RECEIVER KIT

This new all transistor T.R.F. Receiver tunes 550 Khz-30 Mhz (540-10 metres) complete coverage, no gaps. Trawlers, Ship to Shore telephone, Six Amateur Bands, 160-10 metres, International Broadcast, Australia, Far East, Russia, USA, etc., using miniature plug in coils. Hi-Gain FET Regen. Det./Pre-Amp A.F./A.F. Module giving full loud speaker output to any external 2/3 ohm speaker. Two separate Tuning Dials, Calibrated Mhz and Degrees. Electrical Bandspread on all bands. Regen. det. receives CW/SSB signals also. Handsome styling with Black Perspex Panel, Steel Cabinet in Charcoal finish with Chrome Trim. This is a quality CODAR-KIT with full 12 months guarantee. No technical knowledge required, printed circuit construction. Instruction Manual with pictorial drawings backed by friendly Help-U After Sales Service if you have any queries.

Complete Kit (even to the resin-cored solder) with 3 Coils. £11.50 Carriage 50p. Available NOW. NEW AT5 MK 2, 12 WATT. Transmitter 160-80 metres. Also NEW PR40 FET Pre-Selector. Stamp brings illustrated leaflets.

★  
**GR 70A**

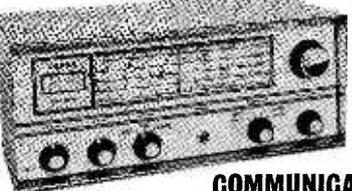

### COMMUNICATION RECEIVER

The CODAR GR 70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.

It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated "S" Meter and Slide Rule Scale, Two speed vernier tuning, Switched B.F.O. for CW/SSB signals, 5 valves inc. two twin triodes giving 7 valve line-up, separate output for Tape recorder.

Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.


Complete ready built £24.50, Carriage 50p.

Ask the chap who's got one, there's lots of them!

ON THE DESIGN STAFF—  
G3SZM G3IRE G8BBI
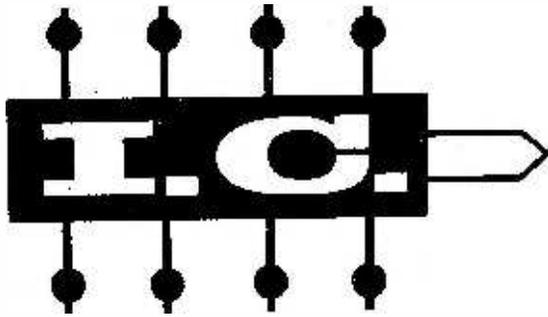
# CODAR RADIO COMPANY

Unit 1, Meadow Road Industrial Estate, East Worthing, Sussex.



# OF THE MONTH

L.A.J. IRELAND

Number 27 Toshiba TH9013P 20W Audio Amplifier

SOME time ago this column featured its first hybrid i.c., a 50 watt audio amplifier from Sanken of Japan. The hybrid approach, in which no attempt is made to fabricate the complete circuit of the unit on a single silicon chip (the "monolithic" approach), is particularly suited to high power or ultra high frequency applications.

Operation in these conditions poses requirements, such as component separation for minimum thermal or capacitive interaction, which are difficult to achieve within a single semiconductor slice. In audio circuits in particular it is advantageous to separate the output transistors, with their high current and thermal dissipation problems, from the driver stage which may usefully be monolithic.

Together with "chip" capacitors, which are also difficult to fabricate monolithically, these elements may be assembled into a single module or hybrid integrated circuit. This month's unit is an imported hybrid audio amplifier whose 20 watt rating fills the gap between the Sanken device already mentioned and the increasingly popular monolithics, whose power dissipation is of the order of 5 watts (G.E. type PA246, etc.).

The device is available from Erie Distribution Division, Erie Electronics Ltd., Gt. Yarmouth, Norfolk, and is quoted in the latest available price list at £4.31 for small numbers.

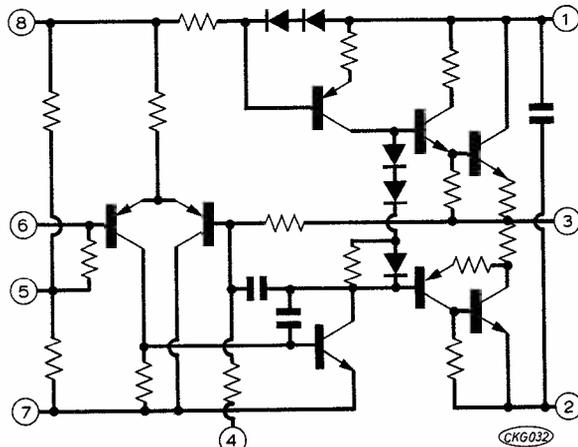


Fig. 1: Circuit of the hybrid audio amplifier.

## Circuit

Now for a detailed consideration of the capabilities of the unit. The high intercomponent leakage resistance possible with hybrid construction permits the use of supply voltages higher than is usual in i.c. work, with consequent lower currents for the same output, and the TH9013P therefore has a maximum supply rating of 50 volts at a current of 1.2 amps. The device should be attached to a heat sink of 300 sq.cms., giving a thermal resistance of 4°C/W or lower. This should retain the operating temperature of the device at 50°C or lower, but allowable case temperatures range from 0 to 90°C during operation, giving considerable latitude.

The circuit in Fig. 1 indicates that the device follows fairly conventional Class B lines, with identical n.p.n. silicon power transistors in push-pull, preceded by a complementary pair phase-splitter driving stage. A considerable advantage is the self-regulating character of the circuit, which does not require an external preset resistor to obtain symmetry of operation. Crossover distortion is therefore minimised, and ease of operation assured. In fact, the overall distortion figure quoted for the unit, at a signal frequency of 1kHz, is 0.3% at the full rated output of 20 watts, while the frequency response is flat to within 2dB from 10Hz to 40kHz. So it follows that if a pair of these devices is incorporated in a stereo outfit, departures from hi-fi standards should be sought in the record deck, the speakers or the preamps. Anywhere, in fact, except the power output stages!

## Power supplies

It is recommended that operation of the unit should be from twin power supplies rated at  $\pm 22.5$  volts. Such supplies are easily constructed using four silicon diodes of appropriate rating to make up a dual full wave rectifier set, working from a transformer with centre-tapped 45 volt secondary followed by suitable smoothing capacitors (at least 500 $\mu$ F, 50V).

Fig. 2 indicates the connections necessary for operation in a standard audio system, with the dual power supply mentioned; it also puts forward a method of operation from a single 45 volt supply should that prove necessary, using a 2000 $\mu$ F d.c.

blocking capacitor between the output of the amplifier and the 8ohm loudspeaker load. It is important to include the fuse link in the circuit; operation into an inadequate load can permanently damage the output transistors and some form of protection is vital. It should be noted that in the single supply case, the fuse link is in the power supply line, since otherwise the charging surge of the blocking capacitor could well blow the fuse.

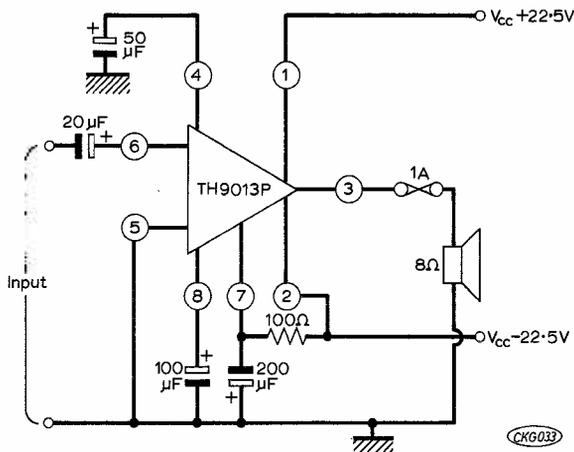


Fig. 2a: Connections to the TH9013P when using a dual power supply.

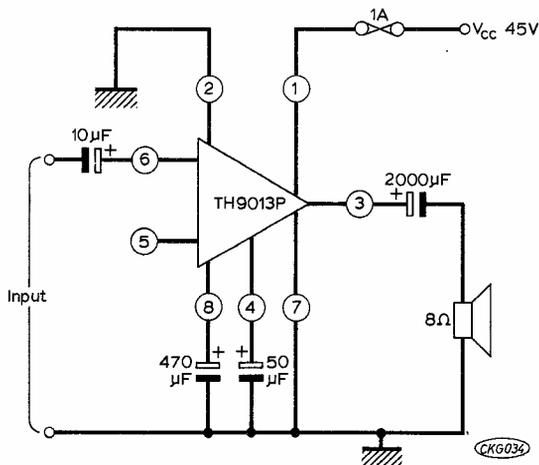


Fig. 2b: A single 45 volt power supply simplifies the external circuitry.

## Notes

Several i.c.'s suitable as preamps for the Toshiba unit have appeared from time to time in these columns, with associated tone and volume controls, so details of these accessories will not be pursued here.

The unit is presented in a sealed package 3×2×5/8in. with a machined face and mounting holes for heat sink attachment. Connections are via eight pins on the side of the package; the numbering in Fig. 1 is from left, when facing the pins with the heat sinking face downwards. For a convenient, economical and effective power amplifier for domestic applications, the TH9013P is certainly worth consideration. ■



## ISSUES WANTED

- ...Practical Electronics Feb. 1971.—P. Arden, Hallam Grange, Hallam Grange Rise, Fulwood, Sheffield, S10 4BE.
- ...Practical Wireless for June 1969 (final part of "Double 12" article).—W. Piddock, 128 Lodge Hill, Welling, Kent.
- ...Practical Wireless December 1963.—D. Hillman, 46 Spenser Street, Bootle, Lancashire, L20 4LW.
- ...Practical Wireless for May and June 1969. M. Jones, 44 Sturge Street, Sheffield, S2 3DP, Yorkshire.
- ...Practical Wireless December 1964, January 1969 to July 1970, September 1970, December 1970 and Practical Electronics for June and July 1970.—I. Moor, 6 Dykelands Road, Sunderland, Co. Durham, SR6 8EP.
- ...Practical Wireless Data Rule.—C. Jolliffe, 43 Holmea Road, Goring-on-Thames, Reading, Berkshire, RG8 9EX.
- ...blueprint for the P.W. 35W Guitar Amplifier (May 1964 issue).—R. Cross, 38 Priory Road, Fishtoft, Boston, Lincs.
- ...Feb. 1971 issue of P.W. and April, May and June 1971 issues of P.E. and any other issues of P.E.—B. Body, 27 Gimble Way, Penbury, Kent.
- ...May 1969 issue of P.W. and Jan to Feb. 1968 issues. T. McKernan, 55 Maryland, Hatfield, Herts.
- ...P.E. for Jan., Feb., Mar. and Oct. 1965, Feb., Apr., Aug. and Sept. 1966. "Television" for Oct. 1967, Apr., Jun. to Dec. 1968, Jan., Feb., Mar. and May 1969 and Feb., Dec. 1970. P. Mohan, 28 Hyde Park Terrace, Leeds, 6.
- ...P.W. for Jan. 1969 to Feb. 1969 and P.E. Jan. 1968 to Dec. 1970.—M. F. Green, 12A West Road, Weaverham, Northwich, Cheshire, CW8 3HQ.
- ...July 1960 P.W. with article on mods to the R1392 Rx.—G. W. Kilbee, 10 Woodlands Road, Ilford, Essex.
- ...Jan., Feb., Mar. and May P.W. for 1971.—C. Jennings, 13 Stonefield Street, Islington, London, N1 0HW.
- ...May and Jun. 1969 P.W.—G. A. Brooks, 227 St. Andrews Road, Coudson, Surrey.
- ...P.W. back numbers in exchange for Indian magazines.—N. Mohanty, M.Sc., Townhall Road, Cuttack-9, Orissa, India.
- ...P.W. for Apr. 1970 (General Coverage Receiver).—J. L. Littler, 61 Kent Road, Orpington, Kent, BR5 4AB.
- ...the issue of P.W. containing Mr. Cameron's decoder (May 1970).—G. R. Hunt, 53 Hand Lane, Leigh, Lancs.
- ...P.W. 1952-1955 and Radio Constructor 1952-1959.—Luxtun, 12 The Vale, Acton, London, W3 7SB.
- ...P.W. for Aug. 1967, Oct. 1969 and Jan. 1971. P.E. for Mar. 1971 and Radio Constructor for Feb. 1970.—A. D. Tuppen, "Greyholm" Geldeston, Beccles, Suffolk.
- ...Apr. 1965 issue of P.W. containing PC tuner article.—W. Pleass, 12 Farmadine Grove, Saffron Walden, Essex.
- ...P.W. for Jan. and June 1970 and P.E. for Jul 1967, Jan. 1968, May 1968, Sept. 1968, Oct. 1968, Feb. 1969, April 1969 and Mar. 1969.—C. Zammit Mangion, 59 St. Mary Street, Sliema, Malta.
- ...P.W. previous to Jan. 1969. Preferably complete sets. State details and price.—M. Tracey, 2 Maneway Way, Newquay, Cornwall.
- ...P.W. for June 1969.—M. J. Burrows, 7 Lyndhurst Road, Keynsham, Bristol.
- ...May 1971 issue of P.W.—A. Vermaak, 82 Kruger Avenue, Discovery, Transvaal, South Africa.

## ISSUES FOR DISPOSAL

- ...Three years P.W. 1967-1971. Hi Fi News and Sound 1967-1971. ?£2.—W. Pearce, 32 Wathen Road, Dorking, Surrey.
- ...most issues from 1966 of P.W., P.E., and R.C.—J. Partington, 30 Ings Way, Bradford, Yorkshire, BD5 0LJ.

## EQUIPMENT FOR DISPOSAL

- ...Beeson & Co. "Prototype" trombone, perfect condition and is silver, it is complete with mute and music clips.—Mrs. M. G. Brundrett, 8 Merlin Street, Carmarthen, South Wales.
- ...Willesden "Blenheim" series oil-cooled mains transformer, ex-oscilloscope. Solatron spares dept. quote is £30-75. Any offers?—R. Knight, "Lincoln's Imp", Roedowns Road, Medstead, Alton, Hants.
- ...S. H. Electronic equipment for sale. Transistors, Valves, all types of capacitors, resistors, tagboards, transformers, variable resistors, tuning capacitors, diodes etc. All at ridiculously low prices. Send for list.—A. Harman, 27 Norby Estate, Thirsk, Yorkshire.

## CORRESPONDENTS AND TAPESPENDENTS WANTED

- ...girl of my own age (16). I have a Bush cassette recorder.—S. Martin, 77 Meadow Rise Road, Norwich, Norfolk, NOR 97F.
- ...girl near my own age (16). I have Marconiphone 4-track machine with speeds 1½ and 3½ips. I am interested in all forms of music.—S. Gibbs, 382 Dereham Road, Norwich, Norfolk, NOR 42J.
- ...anyone who is interested in short wave and radio listening and LP records to correspond. Aged 18-23.—Geoff Dickinson, 5 Quarry Brow, Hawcoat, Barrow-in-Furness, Lancashire.
- ...Club secretaries of radio clubs near my home, as I am interested in joining to learn wireless as a hobby.—J. Tyson, 3 Friars Rise, Scaws Estate, Penrith, Cumberland.
- ...anyone to correspond. I am 13 and interested in electronics and simple circuits.—M. Wigglesworth, 4 Ellabridge Close, Keynsham, Bristol.
- ...boy or girl of my own age (15) interested in electronics.—Sidney Biria, 3/1 Raja Santosh Road, Calcutta-27, India.

## APPARATUS REQUIRED

- ...a direct Disc Recorder and information about this piece of apparatus.—F. Le grande, 81 Bangaree Road, Wilson, W. Australia 6107.
- ...spares for HMV transistor set model 28063. Push button or will buy complete set. Also anywhere where I can get Danette spares.—James Wood, 76a Arncliffe Road, Liverpool, 2C.
- ...Philips Novosonic loudspeaker system type AD5010.—J. C. Wilson, 59 Meadway, Harpenden, Herts.
- ...Radivet type 211 by Airmec Ltd. New or in working condition. Details and price to—G. A. Gray, 4 Bengal Road, Ilford, Essex.
- ...Grundig TK8 motor.—A. Pantou, 49 Peaksfield Avenue, Grimsby, Lincs.
- ...Denco blue coils range 4, white range 4 (one of each). Two 2N2626 transistors, one OCP71 and data of 2N2926 against stamps, view cards and International Reply Coupons.—P. S. Chalokia, 2192, Sector 27C Chandigarh, India.

## EXCHANGE

- ...sale or exchange quantity of electrical/electronic "junk" including valves, transformers, capacitors and 1W audio amp, for small quantity of LP and single records (POP only). Send s.a.e. for lists.—Mike Barnett, 17 Randall Avenue, London, NW2 7RL.
- ...100 small and 30 big valves which are all marked clearly. All these I will exchange for a second-hand general purpose audio amplifier of about 10W or a second-hand multimeter.—A. Harman, 27 Norby Estate, Thirsk, Yorkshire, Y07 1BN.

# EVERYTHING BRAND NEW AND TO SPECIFICATION

No surplus, clearance lines or manufacturers' seconds.

# ELECTROVALUE

## Electronic Component Specialists

### SEMI-CONDUCTORS

All power types with free insulating sets

1N914	5p	AC142H	25p	BD131	79p
1N916	10p	AC142HK	29p	BD132	86p
1N1768A	24p	AC153K	22p	BD135	35p
1N3754	20p	AC176	19p	BD136	44p
1N3999	21p	AC178K	17p	BDY20	92p
1N5402	28p	AC187K	31p	BF115	23p
1S44	9p	ACY17	31p	BF167	18p
1S940	5p	ACY18	19p	BF173	19p
2N696	17p	ACY19	23p	BF177	25p
2N697	18p	ACY20	20p	BF194	14p
2N706	12p	ACY21	21p	BF195	15p
2N930	99p	ACY22	21p	BF254	14p
2N1132	29p	ACY29	63p	BF255	15p
2N1302	19p	ACY40	17p	BFX29	31p
2N1303	19p	ACY41	18p	BFX84	25p
2N1304	26p	ACY44	31p	BFX85	32p
2N1305	26p	AD142	50p	BFX87	29p
2N1306	33p	AD149	58p	BFX88	26p
2N1307	33p	AD150	50p	BFY50	23p
2N1309	36p	AD151	35p	BFY51	20p
2N1613	29p	AD162	36p	BFY52	23p
2N1711	26p	AF114	24p	BSX20	16p
2N1893	54p	AF115	24p	BY164	45p
2N2147	95p	AF116	22p	BY288	18p
2N2218	34p	AF117	22p	BYX38-300	35p
2N2218A	44p	AF118	22p	BYX38-300Z	25p
2N2219	24p	CA07	24p	CA07	17p
2N2270	62p	AF125	24p	C782	19p
2N2369A	19p	AF126	22p	EA403	10p
2N2483	35p	AF127	22p	EB383	10p
2N2484	42p	AF139	33p	EC401	18p
2N2646	47p	AFY39	36p	EC402	17p
2N2904	28p	ASV26	27p	NKT211	25p
2N2905	28p	ASV27	26p	NKT212	25p
2N2905A	47p	ASV28	27p	NKT213	25p
2N2924	20p	ASV29	36p	NKT214	23p
2N2925	22p	AU111	97p	NKT217	50p
2N2926	11p	B30C250	24p	NKT251	21p
2N3053	27p	BW124	66p	NKT271	18p
2N3084	60p	B5041	72p	NKT274	18p
2N3702	13p	BA102	25p	NKT403	65p
2N3703	13p	BA130	22p	NKT405	79p
2N3704	13p	BA145	27p	NKT7813F	30p
2N3705	13p	BA158	13p	NKT674F	24p
2N3706	13p	BB103/B	16p	OA47	5p
2N3708	10p	BB103/G	16p	OA90	6p
2N3709	11p	BC108	11p	OA91	5p
2N3710	13p	BC109	12p	OA95	6p
2N3711	13p	BC122	21p	OA200	9p
2N3794	15p	BC125	15p	OA202	10p
2N3819	23p	BC126	22p	OC19	50p
2N3820	89p	BC149	30p	OC25	42p
2N3904	35p	BC147	10p	OC29	76p
2N3906	35p	BC148	9p	OC35	60p
2N4036	55p	BC149	10p	OC36	65p
2N4058	13p	BC153	19p	OC41	42p
2N4059	10p	BC159	11p	OC44	42p
2N4060	11p	BC177	14p	OC70	21p
2N4061	11p	BC178	13p	OC71	38p
2N4124	18p	BC179	14p	OC75	40p
2N4126	27p	BC182L	11p	OC81	25p
2N4284	15p	BC183L	10p	OC81D	25p
2N4286	13p	BC184L	11p	OC82	25p
2N4289	15p	BC186	42p	OC84	25p
2N4291	15p	BC212L	16p	P346A	26p
2N4410	24p	BC213L	16p	82CN1	10p
2N4991	62p	BC214L	16p	SD1	10p
2N5082	61p	BC257	9p	SD4	12p
2N5467	48p	BC259	9p	V703	25p
2N5459	49p	BC267	17p	W103B1	45p
40250	71p	BC268	15p	W02	40p
40251	89p	BC269	17p	W02	95p
40361	55p	BC300	49p	ZTX300	14p
40362	89p	BC301	37p	ZTX301	16p
40602	52p	BC303	80p	ZTX302	22p
AC107	40p	BCY30	80p	ZTX303	22p
AC126	20p	BCY31	75p	ZTX304	27p
AC127	20p	BCY70	15p	ZTX330	23p
AC128	20p	BCY71	33p	ZTX331	27p
AC141H	34p	BCY72	15p	ZTX500	15p
AC141HK	37p	BD130	50p		

### ES.10-15 BAXENDALL SPEAKER

As designed by P. J. Baxendall and originally described in "Wireless World". Complete kit including speaker unit, equalising network and special cabinet (18" x 12" x 10" when assembled) supplied out to size. 10 watts/15 ohms. Carr. free in U.K.

**£13.90**

Add good appearance to your building

### SIEMENS CAPACITORS



These electrolytic capacitors are all in the same style and colour and greatly enhance the appearance of the finished article when built. With axial leads and clearly marked polarity.  
0.47µF/100V., 2.2/100V., 4.7/100V. — 7p., 10/100V., 8p.: 22/100V., 9p.: 470µF/100V., 47µF/100V., 220/35V., 100/35V., 100/35V., 470/25V., 12p.: 220/30V., 1000/16V., 470/35V., 220/63V., 100/100V., 18p.: 1000/25V., 470/50V., 22p.: 2200/16V., 1000/35V., 220/100V., 27p.: 4700/16V., 89p. (Page 34 of catalogue for full list of more than 60 values.)

SIEMENS TTL I. Cs — wide range in stock at an all time low in prices.

### RESISTORS 10% — 5% — 2%

Code	Power	Tolerance	Range in ohms	Values 1 to 9	10 to 99	100 up (see note below)
C	1/20W	5%	22-220K	E12	9	8
C	1/8W	5%	4.7-470K	E24	1	0-8
C	1/4W	10%	4.7-10M	E12	1	0-8
C	1/2W	5%	4.7-10M	E24	1-2	1
C	1W	5%	4.7-10M	E12	2-5	2
MO	1/2W	2%	10-1M	E24	4	3-5
WW	1W	10% ± 1/20 Ω	0.22-3.0	E12	7	7
WW	3W	5%	12-10K	E12	9	9
WW	7W	5%	12-10K	E12	7	8

Codes: C — carbon film high stability low noise  
MO — metal oxide Electrofilm TR5 ultra low noise  
WW — wire wound Plessey

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades  
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 72, 91 and their decades.  
Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1p on total value of resistor order).

VEROBOARD. All popular sizes; INDICATOR LIGHTS; DIN CONNECTORS, etc.

### MULLARD polyester C280 series

250V 20% 0.01; 0.022; 0.033; 0.047 3p ea. 0.068; 0.1, 0.15 4p, 0.22 5p, 10%; 0.33 7p, 0.47 8p, 0.68 11p, 1µF 14p, 1.5µF 21p, 2.2µF 24p.

### MULLARD SUB-MIN ELECTROLYTIC

0428 range axial lead 8p each  
Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/25; 10/16; 10/64; 12.5/25; 15/40; 20/16; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/25; 50/64; 50/25; 60/40; 64/4; 64/10; 80/25; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 160/25; 200/64; 200/10; 250/4; 320/25; 320/64; 400/4; 500/25.

### LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 82p; 2000/25 37p; 2000/50 87p; 2000/100 144p; 2500/64 77p; 2500/70 98p; 5000/25 82p; 5000/50 110p; 5000/100 128p.

### 'SIEMENS' 5% TOLERANCE POLYCARBONATE CAPACITORS

50V up to 0.1mF, 100V 0.1mF and above.  
0.01, 0.12, 0.015, 0.018, 0.022, 0.027 5p  
0.033, 0.047, 0.056, 0.068, 0.081, 0.01, 0.1 to 0.22 6p.  
0.33, 0.39, 0p, 0.47, 10p, 0.56, 13p, 0.68, 15p.

### DUAL CONCENTRIC POTS.

Carbon track. Sections in same values as single gang (next column). Available in any combination of values, less switch 80p. With switch 72p.

### S-DeCs

Manufacturer's prices increase roughly by 20% on these on pages 51, 52 and 53 since printing our catalogue. S-DeC £1.44, Four pack £5.10, DeCATOR pack £2.88. T-DeC, may be temperature-cycled (208 pots), £2.68. µDeCa, £3.18. µDeCb, £5.84. Also I.C. carriers.

### DISCOUNTS

10% discount is allowed on orders for £5 to £15 in value.

15% discount allowed on orders over £15. No discount on items marked *Nett*. Prices subject to alteration without notice.

### CATALOGUE

The latest Electrovalue catalogue (1971-2nd edition) contains 64 pages packed with hundreds of items and valuable illustrated information. Post free 10p.

### AMPLIFIERS

#### 30 WATT BAILEY PARTS

Transistors and PCB for one channel **£6.40**

Capacitors, resistors (metal Oxide), and transistors, one channel. **£8.41**

Complete unregulated power supply pack. **£4.75**

Suitable heatsink 10DN400C. **55p**

**MAINLINE**  
70W main amplifier module **£12.80 nett.**

Power supply kit **£6.00 nett**  
Suitable pre-amp kit **£6.25 nett**  
(less chassis & panel)

Above for mono only.

**STEREO PACK OF UNITS** for building into your own cabinet — 2 power amps, pre-amp control unit, power supply unit and matched controls, **nett £38.40.**

### ZENER DIODES

5% full range E24 values; 400mW: 2.7V to 30V 15p each  
1W: 6.8V to 82V 27p each 1.5W: 4.7V to 75V 60p each  
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

### CARBON TRACK

#### POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.  
Single gang linear 100 Ω to 2.2M Ω **12p**  
Single gang log 4.7K Ω to 2.2M Ω **12p**  
Dual gang linear 4.7K Ω to 2.2M Ω **42p**  
Dual gang log 4.7K Ω to 2.2M Ω **42p**  
Log/anti-log 10K, 47K, 1M Ω only **42p**  
Any type with 1/4 D.P. mains switch, extra **12p**

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

### CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω, 470 Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M Ω Vertical or horizontal mounting 5p each.

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

### POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2. Overseas orders welcome; carriage and insurance are charged at cost.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081 for special prices

# ELECTROVALUE

(Dept. P.W. 372) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB  
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475

## FIND BURIED TREASURE!

### Transistorised Treasure Locator

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2.37 + 27p p. & p.** (Sectional handle as illustrated. 75p extra). Parts available separately. Made up looks worth £15!

### Eavesdrop on the exciting world of Aircraft Communications

#### V.H.F. AIRCRAFT BAND CONVERTOR

**ONLY £2.37**  
Listen in to AIRLINES, PRIVATE PLANES, TROUBLEMAKERS. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including **HEATHROW, GATWICK, LUTON, KINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL.** This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close tiny portables. **NO CONNECTIONS WHATSOEVER NEEDED. SEND ONLY £2.37 + 28p p. & p.** for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

## SHORTWAVE TRANSISTOR RADIO

**ONLY £2.25**  
Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on rot aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2" **ONLY £2.25 + 17p p. & p.** Kit includes cabinet, screws, instructions, etc. (Parts available separately).

### INGENIOUS ELECTRONIC SLEEP INDUCER

**ONLY £2.75**  
**CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT?** Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. **No soldering necessary.** Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. **SEND £2.75 + 25p p. & p.** (parts available separately).

## ELECTRONIC ORGAN

**ONLY £2.75**  
Don't confuse with ordinary electronic organs that simply blow air over mouth—organ type reads etc. Fully transistorised. **SELF CONTAINED LOUDSPEAKER.** Fifteen separate keys span two full octaves—play the "Yellow Sea of Tezoo", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering necessary. Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated step-by-step, simple instructions. **ONLY £2.75 + 23p p. & p.** for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

### Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

**ONLY £4.95**  
**FULLY TRANSAIS-TOIRISED PRINTED CIRCUIT METAL DETECTOR MODULE.** Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and **YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £80!** Extremely sensitive—penetrates through earth, sand, rock, water, etc. **EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC.** Signals exact location by "beep" pitch increasing as you near buried metallic objects. **So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN!** £4.95 + 30p carr. etc. (High quality Danish Stethoscope headphones £2.75 extra if required.) **EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.**

## BUILD 3 RADIO AND ELECTRONIC PROJECTS

**only £1.97**  
Amazing Radio Construction set! Become a radio expert for £1.97. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 37p extra as illus. (if required) (parts available separately) no soldering necessary. **Send £1.97 + 23p p. & p.**

### SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

**ONLY £2.25**  
**CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES!** Don't underestimate the uses of this fantastic new design the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. **IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron.** Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost self-life). **CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE** using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, components, nuts, screws, wire, etc. etc. (parts available separately) **£2.25 + 25p p. & p.**

**CONCORD ELECTRONICS LTD. (PW7) 8 Westbourne Grove, London, W.2. Callers welcome 9 a.m.-6 p.m. inc. Saturday**

## M. & B. COMPONENTS (LEEDS) LTD. (INCORPORATING M. & B. RADIO)

PO Box 125, 38 BRIDGE END, LEEDS 1 Telephone 0532-35649

**PYE AM25B VANGUARDS.** 12v boot mounting radio-telephones. 20 watts RF output from QQV03/20A. High band and low band in stock. Ideal for 2 or 4 metre mobile operation. Less mike and control Box and Speaker **£20 each plus 90p carr. UK.**

**MARCONI DIVERSITY TELEGRAPH RECEIVER TYPE R217.** As new in 7' rack. **ONLY £150 delivery arranged UK.**

**BRAND NEW SIFA M 2 1/2 sq 25-0-25 uA meters** **ONLY 95p each plus 10p carr. UK.**

**WALKIE TALKIES TYPE 88.** 4 crystal controlled channels. Un-tested. Less handset. In clean condition with circuit. **ONLY £4.75 or £8 for 2 inc. carr. UK.**

**RCA POWER TRANSISTORS TYPE 2N3773** on hefty heat sink. Ideal for high power Amps. **60p each or £1 a pair plus 10p carr. UK.**

**9 TRANSISTOR 455 Kc/s IF STRIPS.** Ideal basis for Receiver. **ONLY £1.20 inc. carr. UK.**

**TRANSISTOR TRANSMITTER PANELS.** 1/2 watt output on 68-88 MHZ. FM modulated. Needs external 2 transistor mike pre amp. Brand New. Ex-Pye. with circuit. **ONLY £4.75 inc. carr. UK.**

**EX-GPO DESK TELEPHONES.** Used but in working condition ideal for intercoms. **TWO for £2 inc. carr. UK.**


**QQV03-10 Ex equipment** **THREE for £1 plus 10p carr. UK.**

Send SAE for full list with many bargains of general interest.

## PRINTED CIRCUIT KIT

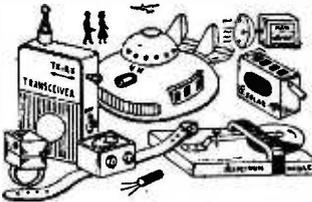**BUILD 50 INTERESTING PROJECTS ON A PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX**

**CONTENTS:** (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs* (9) 2 Miniature Radio Kits (10) 200p/W/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 50 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



### EXPERIMENTERS PRINTED CIRCUIT KIT 60p


Postage & Pack. 10p. (U.K.)  
Commonwealth:  
SURFACE MAIL 20p  
AIR MAIL 60p  
Australia, New Zealand, South Africa, Canada

- Crystal Set with biased Detector.
- Crystal Set with voltage-quadrupler detector.
- Crystal Set with Dynamic Loudspeaker.
- Crystal Tuner with Audio Amplifier.
- arrier Power Conversion Receiver.
- Split-Loud Neutralised Double Reflex.
- Matchbox or Photocell Radio.
- "TRI-FLEXON" Triple Reflex with Self-adjusting regeneration (Patent Pending).
- Solar Battery Loud-speaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World.
- 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere.
- Postage Stamp Radio. Size only 1.92" x .95" x .25".
- Wristwatch Radio 1.15" x .80" x .55".
- Ring Radio .70" x .70" x .55".
- Bacteria-powered Radio. Runs on sugar or bread.
- Radio Control Tone Receiver.
- Transistor P/P Amplifier.
- Intercom.
- 17-valve Amplifier.
- Reliable Burglar Alarm.
- Light-Seeking Animal, Tester.
- Human Body Radiation Detector.
- Man/Woman Discriminator.
- Signal Injector.
- Pocket Transceiver (Licence required).
- Constant Volume Intercom.
- Remote Control of Models by Induction.
- Inductive-Loop Transmitter.
- Pocket Triple Reflex Radio.
- Wristwatch Transmitter/Wireless Microphone.
- Rain Alarm.
- Ultrasonic Switch/Alarm.
- Stereo Pre-amplifier.
- Quality Stereo Fusi-Pull Amplifier.
- Light-Beam Telephone "Photophone".
- Light-Beam Transmitter.
- Silent TV Sound Adaptor.
- Ultrasonic Transmitter.
- Thyristor Drill Speed Controller. . . plus 10 Photo-electric Circuits, Alarms, Modulators, Stabilisers. . .

**YORK ELECTRICS, Mail Order Dept.**  
**335 Battersea Park Road, London, S.W.11**  
Send a S.A.E. for full details, and a brief description of all Kits and Projects.

# new

## Super IC-12

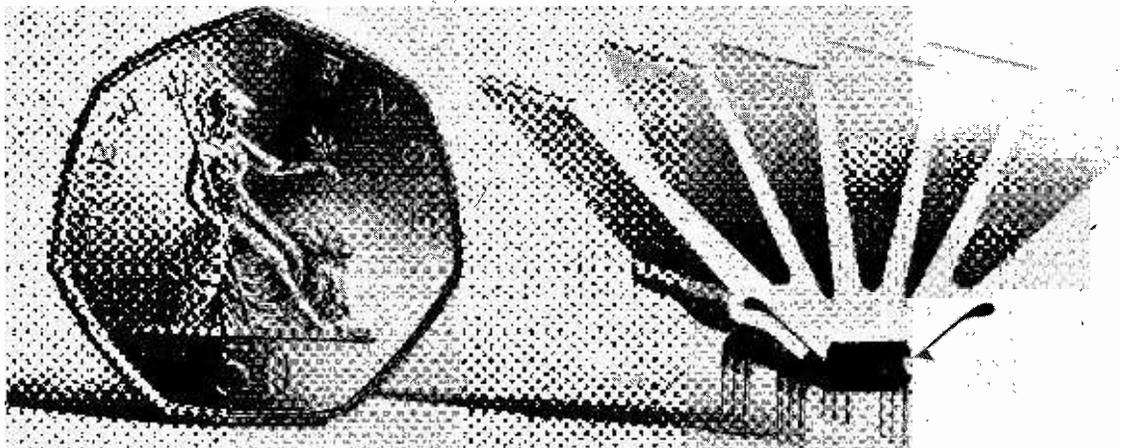

### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1 dB.

**Total Harmonic Distortion** Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Input Impedance** 250 Kohms nominal.

**Power Gain** 90dB (1,000,000,000 times) after feedback.

**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Quiescent current** 8mA at 28 volts; low enough to make the IC.12 ideal also for battery operation.

**Size** 22 x 45 x 28 mm including pins and heat sink.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added.



**FREE** 44 page instruction manual now included with all units. Available free on request to present IC.12 users. Gives full circuit and wiring diagrams for many applications including car-radios, oscillators, etc.



Price, inc. **FREE** printed circuit board for mounting and manual.

**£2.98** Post free

#### SINCLAIR GENERAL GUARANTEE



Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

Sinclair Radionics Ltd, London Rd, St. Ives Huntingdonshire PE17 4HJ  
Telephone St. Ives (048 06) 4311

# sinclair
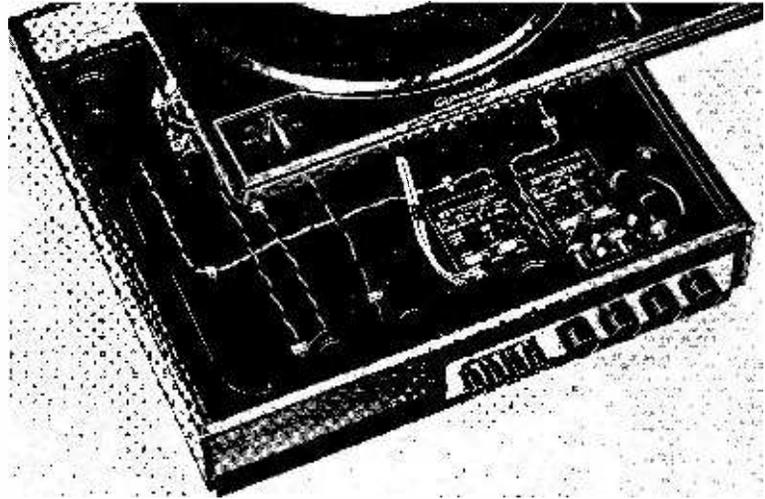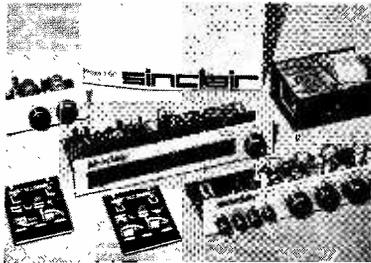
# Sinclair Project 60

The World's leading range of high fidelity modules



## New!

### Project 605

The easy way to buy and build Project 60



Project 605 is one pack containing: one PZ.5, two Z.30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**  
All you need for a superb 30 watt high fidelity stereo amplifier.

Sinclair Radionics Limited, London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

# sinclair

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world. Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.


#### Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	<b>£4.48</b>
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	<b>£9.45</b>
20 + 20 W. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	<b>£23.90</b>
20 + 20 W. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
40 + 40 W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains transformer	As above	<b>£34.88</b>
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	<b>£19.43</b>

F.M. Stereo Tuner (£25) & A.F.U. Filter Unit (£5.98) may be added as required.

# from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

## Z.30 & Z.50 power amplifiers

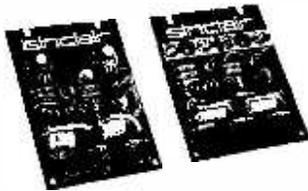

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).**

### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

**Frequency response:** 30 to 300,000Hz  $\pm 1$  dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB unweighted.

**Input sensitivity:** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

**Size:** 14 x 80 x 57 mm.

### Z.30

Built, tested and guaranteed with circuits and instructions manual. **£4.48**

### Z.50

Built, tested and guaranteed with circuits and instructions manual. **£5.48**

## Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

**PZ.5** 30 volts un stabilised **£4.98**

**PZ.6** 35 volts stabilised **£7.98**

**PZ.8** 45 volts stabilised

(less mains transformer) **£7.98**

**PZ.8** mains transformer **£5.98**



## Project 60 Stereo F.M. Tuner



*First in the world to use the phase lock loop principle*

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2 $\mu$ V for 30dB quieting; 7 $\mu$ V for lock-in over full deviation. **Squelch level:** 20 $\mu$ V. **A.F.C. range:**  $\pm 200$  KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz ( $\pm 1$ dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Power on/tuning/stereo. **Size:** 93 x 40 x 207 mm.

Built and tested. Post free.

**£25**

## Stereo 60 Pre-amp/control unit



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

**SPECIFICATIONS—Input sensitivities:** Radio—up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A curve  $\pm 1$ dB: 20 to 25,000 Hz. Ceramic p.u.—up to 3mV: Aux—up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 15 to -15dB at 10 KHz; BASS + 15 to -15dB at 100Hz.

**Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm. **£9.98**

Built tested and guaranteed.

## A.F.U. High & Low Pass Filter Unit



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less

loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm. **£5.98**

Built tested and guaranteed.

## The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

PW372

# DISCOUNTS UP TO

# 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

AKAI · LEAK · SINCLAIR · TELETON · ARMSTRONG · ROTEL  
THORENS · PHILIPS · GOLDRING · ROGERS · PIONEER

## SPECIAL OFFER £18

Garrard SP25 Mk. III  
Goldring G800H  
Teak plinth and tinted cover.  
Ready wired for immediate use.  
Please add £1.25 for post and packing.

## TURNTABLES

Please add 50p for P. & P.  
Garrard SP25 Mk. III £10.25  
Garrard 1025T with cartridge\* £5.95  
Garrard 2025TC with Sonotone 9TAHC £8.95  
Garrard Zero 100-Auto (New Product) £40.95  
Garrard Zero 100-Single Play (New Product) £37.95  
Garrard SL65B £19.50  
Garrard AP76 £27.00  
Garrard 401 £10.00  
BSR MP60 £36.00  
Pioneer PL12AC £62.50  
Thorens TD125 £42.50  
Thorens 150AB11 £20.00  
Goldring GL69J2 £26.95  
Goldring GL69 P2 £27.95  
Goldring GL75 £35.95  
Goldring GL75 P

## AMPLIFIERS

Please add 50p for P. & P.  
Alpha Highgate FA400 £33.00  
Armstrong 521 (cased) £44.95  
Amstrad 8000 Mk. II £16.95  
Amstrad IC2000 18 watts RMS £29.95  
Dulci 207 £15.95  
Dulci 207m £21.00  
Leak 30 Delta Range (New Prod.) £51.00  
Leak 70 Delta Range (New Prod.) £61.00  
Metrosound ST20E £26.00  
Philips R500 £18.00  
Pioneer SA600 New Prod £65.00  
Pioneer SA700 £92.00  
Pioneer SA900 £35.50  
Rogers R/brook Cased £39.50  
Rogers R/bourne Chassis £44.00  
Rogers R/bourne Cased £48.50  
Sansui AU101 £39.95  
Sansui 555A £75.00  
Sansui AU666 £28.50  
Tripletone 800 amp series 3 £16.95  
Euphron 10+10

All prices correct at time of going to press

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PW7) 174 Pentonville Road, London, N1. Telephone 01-278 1769  
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. GALLERIES: Please note that cheques can only be accepted together with Liquor Cards (not Bargain Cards).

2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

Goldring Lenco 15 watts RMS £32.95  
Rotel RA 301 £32.75  
Rotel RA 601 £49.80  
Sinclair 2000 Mk. II £22.50  
Sinclair 3000 £32.50  
Sinclair PRO 60/2 + Z30 PZ5 £15.75  
Sinclair PRO 60/2 + Z30 PZ6 £17.75  
Sinclair PRO 60/2 + Z50 £22.95  
PZ8/Trans £4.70  
Sinclair AFU £20.50  
Sinclair 605 (New Product) £37.95  
Goodmans Max. Amp. £17.95  
Teleton SAQ206B (New Prod.) £49.75  
Wharfedale  
Sinclair IC12 integrated circuit amplifier £1.85  
Eagle TSA 149 7w RMS £24.95  
Eagle TSA 151 15w RMS £34.90

## CARTRIDGES

Please add 10p for P. & P.  
GCS 36 95p  
Goldring G850 £3.65  
Goldring G800 £5.25  
Goldring G800E £10.30  
Goldring G800SE £15.90  
Sonotone 9TAHC Diamond £1.75  
Shure M3DM £4.50  
Shure M445/7/C £7.00  
Shure M55E £8.75  
Shure M75E £12.95  
Shure V15 Type 2 £27.75  
Shure M44E £7.25  
Shure M31E £8.50  
Shure M32E £8.00  
Austin Technics A335 £4.95

## PLINTHS & COVERS



£3.20\*  
(As illustrated)  
Plus 35p post and packing.  
Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 3000; AT50; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR McDonald MP60 and others.  
\*For AP76; AP75; SL72B; SL75; SL95B; £4.20 plus 55p P. & P.  
Also finished in walnut to match Japanese equipment—at no extra charge.

# TV's 19" NOW £11.95

TWO YEARS' GUARANTEE ALL MODELS


405/625: 19" £25.95

23" £35.95

CARR £1.95

FREE CATALOGUE

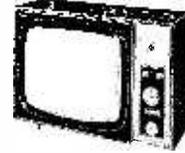
DAILY DEMONSTRATIONS FOR PERSONAL SHOPPERS



## TV TUBES REBUILT GUARANTEED 2 YEARS

14" £3.95; 17" and 18" £5.95; 21" and 23" £6.45

Exchange Bowls carr. 55p

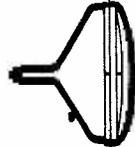

## COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 15p.  
Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p.  
VHF/FM Tuners: 95p. 88-108 megs. takes ECC85 valve (extra). Post 15p.  
Radio: £3.95 8 transistor LW/MV. Free case, battery. Post 15p.  
Precision Tape Motors: £1.95. 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free.  
Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p.  
Transistors 15p each. Post free. AC126, AC128, AF114, AF117, OC45, OC71, OC81, OC81D.  
Valve ELL80 50p. Only stock in the country.  
Pots: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg/100 KΩ. SJSW 500/500 KΩ. SJSW 500/1 meg.

## DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12. Phone 01-478 6001-2-3

# REEDS REEDS REEDS

We offer a comprehensive range of reed switch devices. These are not "seconds" or "job lots", but genuine manufacturers stock lines. Send S.A.E. for full data and prices.

## INTRODUCTORY OFFERS

Reed Relay type 2/E 3V .. 25p each  
Miniature Reed Switches type A JA 200V .. 20p each  
Reed Push Button Switches 1 contact .. 85p each

## REED COILS

3, 6, 9, 12, 24V Miniature .. 27p  
Small .. 27p  
Standard .. 34p

## REED SWITCHES

Large range of many sizes, types and manufactures  
Popular types: E Small normally open .. 10 for 50p  
A Miniature normally open .. 24p each  
B Standard change over .. 40p each

## REED RELAYS

Many versions available, popular types:  
3, 6, 9, 12, 24V  
Miniature 1/A normally open .. 56p  
Small 2/E 1 contact .. 36p  
2/EE 2 contacts .. 44p  
2/EEE 3 contacts .. 52p  
STD 3/B change over .. 87p

## REED PUSH BUTTON SWITCHES

Momentary Action  
1 contact .. £1.00  
2 contacts .. £1.25  
Illuminated 1 contact .. £1.30  
Illuminated 2 contacts .. £1.55 } Inc. P. Tax

## REELS of ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g.  
250 grams and 500 grams. Send for prices  
Packing and postage 7p on all orders.

C.B.M. ELECTRONIC COMPONENTS LTD.  
26 Avon Trading Estate, Avonmore Road, London, W.14

**FELSTEAD ELECTRONICS (PW 54)**

**LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE**

Selection from our List, sent free for stamped addressed envelope. (Free overseas). Cash with Order only—No C.O.D. or Caller service. Charges (Min. 6p) in brackets after all items apply to G.B. & Eire only. Regret Orders under 25p plus charges unacceptable. S.A.E., please, for enquiries or cannot be replied to. Overseas Orders welcomed.

**RECORDING TAPE:** Finest quality/value British Master available: **STANDARD** 5" 600ft. 35p; 5 1/2" 900ft. 50p; 7" 1200ft. 56p; **LONG PLAY** 5" 900ft. 50p; 5 1/2" 1200ft. 56p; 7" 1800ft. 90p. (7 1/2p on 5" and 5 1/2", 9p on 7"). Other sizes, Cassettes and accessories in List.

**CARTRIDGES.** All with standard fittings and stylus. Stereo-compatible Mono GP91/SC £1.10; STEREO GP93 £1.40; Stereo Ceramic GP94 £1.95. (All at 6p each.) Comparatives shown in List, with more types incl. Sonotone 9TAHC, Goldring etc. at lowest price.

**DIAMOND STYLUS:** Single tip types: ACOS GP37, GP59, GP65/67, GP71, BSR TCS/LP/ST; COLLARO O, P and DC284, GARRARD G62, G65, GCS/10, GCE/12, RONETTE RF40, O, P and T, PHILIPS 3501 (3050, 3066, 3302, 3304), 3010/12/13/16. SONOTONE 19T/20T ALL AT 40p each (6p). **SAPPHIRE** 17 1/2p (6p). Double-tip turn-over types (78 sap. on other side). For ACOS GP73, GP91 (for cartridges GP93, GP94 etc.). GP918C (for stereo-compat. types) GP104, BSR ST4 (ST3, ST5), ST9 (ST8), ST12/14/15. SONOTONE 3TA, 9TA, 9TAHC, PHILIPS 3309 (3310, 3324, 3228/22, GP280). GARRARD GCM21, 22, GCS28, GKS35 and 26, GCM21T and 22T, GKM34T, GCS23+ GKS23T, & 23T, GCM31, GCS3, GCS35, GCS38, KS40A, KS41B ETC. ALL AT 75p (6p). **SAPPHIRE** 35p (6p). **DOUBLE DIAMOND STYLUS:** (Same dia. tip each side: no 78) All types £1.50 (6p). **SAPPHIRE DOUBLE STYLUS, TIPPED** 40p (6p). **PICK-UP WIRE:** Super thin twin flex screened, sheathed, 6p per yard (Up to 6 yds. 6p over charges paid).

**MICROPHONES:** **CRYSTAL:** LAPEL 1 1/2", clip/hand, lead 3.5mm jack plug 32p (6p). CM20 Cream Plastic hand 52p; CM21 Grey Plastic Hand/Desk 62p; both have 3.5mm jack plug and lead (9p either). "STICK" 60 £1.02; CM70 "PLANET" Metal, tapered, with neck cord, adaptor for stand £1.47; "MIC 91" hand/desk 81p; "MIC 45" Curved metal hand grip £1.00. ALL with leads (all 9p). **MICROPHONE INSERTS:** 0.9" 27 1/2p (Up to 6 for 6p). **DYNAMIC:** 209 Cardioid Ball, 50K/600Ω built-in volume control, on/off switch, special 20ft. lead, the best value anywhere at 28.30; UD130, uni-dir. mesh ball 50K/600Ω jack plug, cable, adaptor, 24-80; DM160, omni-dir. Ball mesh, 50K cable adaptor jack plug 23-87 1/2 (27p each). **SPEAKERS:** Still very popular 12" ROUND, 8Ω, all parts replaceable, highest quality fully guaranteed £1.17 1/2 (10p). **TRANSFORMERS:** Sub-min 11x11x12mm. OUTPUT (3Ω for OC72, etc.) 14p or DRIVER 15p (Up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds. asstd. cols. **SOLID CORE** 14p. **FLEXIBLE or SUPER THIN** for transistor wiring, etc. either 16p (Any pack 6p). **RETRACTABLE FLEXIBLE LEADS (CURLIES):** With phono plug, each end, 6ft 23p. 12ft 38p. With phono plug/socket other end 6ft. 25p. 12ft. 42p (6p lead any type).

**VIBRATORS.** 12v/4 pin non-synch 121HD4, 24" ex. pins, 27p. SAME but 34" ex. pins, 1.8A, 20p. 12v/7 pin, synch. (125R7) 27" ex. pins, 22p (6p any type). **TRANSISTORS,** etc. AC125 12p, AF115 20p, AF116 15p, AF117 20p, OAS 10p, OA10 10p, OA81 10p, OC44 14p, OC45, OC71, OC72, OC75, OCS1D, OCS2D, all at 12p each, OC81 15p, OC170 20p, OC171 12p. BY100/800 pwr 14p. Many more incl. power types, thyristors, etc. in List.

**MAINS NEONS,** by leads 10p. **NEON SCREWDRIVER** (pocket tester) 17p (6p either) **MAINS BATTERY ELIMINATOR.** Input 240v-AC. Output 3, 6, 7 1/2 and 9v-DC by switch selector, On/off switch, pilot lamp, leads, plug, adaptor to suit most transistor sets and cassette recorders. Suitable for model use: £3.15 (24p).

**OUR CURRENT LIST** (see heading) includes more details of all above plus cartridge replacement table, many unrepeatable Special Offers, and cable, croc. clips, Volume controls Din plugs, Co-Ax, standard, miniature, phono plugs, sockets and adaptors, Tape Recording and Record Player accessories, panel and Test meters and equipment, Multimeters, min. motors, test prods, switches-rotary, toggle, slide, cabinet, lamp, etc., electrolytics, terminals, Veroboard, valve holders, extending aerials for cars and portable sets, ind. lamps and bulbs, diode, mikes, telephone amplifiers and pick-ups, drive cord, inter-coms, condenser and resistance testers, Stereo Headphones etc. etc.

**LIST SENT FREE WITH ALL ORDERS IF REQUESTED.**



**become a RADIO-AMATEUR!**

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!** Brochure, without obligation to:  
**BRITISH NATIONAL RADIO SCHOOL**  
READING, BERKS

NAME : \_\_\_\_\_  
ADDRESS : \_\_\_\_\_

BLOCK CAPS please

**ADCOLA Soldering Instruments add to your efficiency**

**THE NEW 'INVADER'**

**ADCOLA L.646**




for Factory Bench Line Assembly

**PRICE £1.85**


A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

\*Additional Stock Bits (illustrated) available

**COPPER**

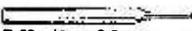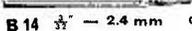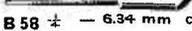-  **B 38** 3/8" — 3.2 mm CHISEL FACE
-  **B 14** 1/4" — 2.4 mm CHISEL FACE
-  **B 24** 3/8" — 4.75 mm SCREWDRIVER FACE
-  **B 12** 1/4" — 4.75 mm EYELET BIT
-  **B 58** ± — 6.34 mm CHISEL FACE

**LONG LIFE**

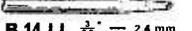-  **B 42 LL** 3/8" — 4.75 mm CHISEL FACE
-  **B 38 LL** 1/2" — 3.2 mm CHISEL FACE
-  **B 14 LL** 3/8" — 2.4 mm CHISEL FACE
-  **B 44 LL** 3/16" — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



\* Write for price list and catalogue

**ADCOLA PRODUCTS LTD.,**  
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.

Telephone: 01-622 0281/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

**Train for tomorrow's world in  
Radio and Television at The  
Pembridge College of Electronics  
Your first day on Television:  
6th September, 1972**



This is your opportunity to train as a television and radio engineer on our full-time 2 year College Diploma Course. That is the way to get into a rapidly growing industry with a tremendous demand for skilled technicians. You will be given theoretical and practical instruction on colour television receivers, following a syllabus specially designed to cover the new City and Guilds Radio, Television and Electronic Technicians' Course.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Complete the coupon below and we will send you the details about training for an exciting, new career.

**To: The Pembridge College of  
Electronics, (Dept. PW7.),  
34a Hereford Road, London,  
W2 5AJ.**

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME .....

ADDRESS .....

Setting up home?

**FREE 16-page  
Home Improvement  
Supplement**

Exciting, modern designs . . . easy-to-follow instructional articles . . . handy hints and ideas — all you need to make your house the home of your dreams!

Also in this issue . . .  
**FREE Plan Sheet for a 9ft Crest Car-top  
Sailing Dinghy.**

**PRACTICAL  
WOODWORKING  
Out 14th February only 20p**


**BAKER 12in. REGENT**

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

Maximum Power 15 watts  
Base Resonance 45 c.p.s.  
Flux Density 12,000 gauss  
Voice Coil impedance 3 or 8 or 15 ohm models  
Useful response 45-13,000 c.p.s.

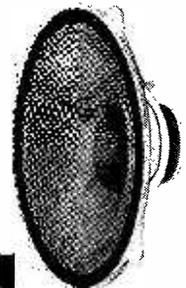**£7**

Nett weight 5 lbs. POST FREE  
GUITAR MODEL "GROUP 25" £7  
25 watt rating  
Latest catalogue 5p with enclosure plans.



**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

**C. T. ELECTRONICS**

FOR REAL SERVICE WITH THE LARGEST  
SELECTION OF ELECTRONIC COMPONENTS  
AND TEST EQUIPMENT YOU MUST VISIT—

**C. T. ELECTRONICS**

267 ACTON LANE, CHISWICK, LONDON W.4

9.30 a.m.—6.00 p.m. Mon.—Sat.

## BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 3 1/2 in. with STEREO and MONO XTAL



£7.75 Post 25p.

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL82, EZ80/81. Response 60-12,000 cps. Sensitivity 200mV. Post 25p. £4

## R.C.S. PORTABLE PLAYER CABINET



Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18 x 15 x 8 in. Metal fittings. Carrying handle. Two-tone £4 Post 25p.

GARRARD SINGLE PLAY TA MK II Ideal Discotheque or Hi-Fi Stereo/Mono £10

GARRARD PLAYERS with Sonotone 9TA Cartridges Stereo Diamond and Mono Sapphire. SP25 Mk III £16. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

R.C.S. TEAKWOOD BASE. Ready cut out for mounting (State player make and model) £2.75

R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. £2.25

EMI PICK-UP ARM with mono xtal and stylus £1.25. HI-FI PICK-UP CARTRIDGES. Diamond Stereo/Mono. STA £2.50; GP94 £2.50; GP93 £2.00; Mono GP91 £1.50; ACOS Standard fitting with LP Stylus only. 50p.

## E.M.I. WOOFER AND TWEETER KIT

£5.75 Post 25p

Comprising a fine example of a Woofer 10 1/2 x 8 1/2 in. with 4 Ohm Ceramic Magnet, 44oz. Gauss 13,000 lines. Aluminium cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Impedance Standard 8 Ohms. Maximum Power 12 watts. Useful Response 35 to 18,000 cps. Base Resistance 45 cps.



## WEYRAD P50-TRANSISTOR COILS

RA2W Ferrite Aerial... 85p Spare Cores... 3p  
Osc. P50/LAC... 30p Driver Trans. LPD74... 50p  
P.F. P50/CC 470 kc/s... 30p Printed Circuit, PCA1... 60p  
3rd L.F. P50/SCC... 35p J.B. Tuning Gang... 65p  
P51/L or P51/2... 85p Weyrad Booklet... 10p  
P50/3V... 35p OPTI... 55p  
Mullard Ferrite Rod 8 x 1/2 in. 20p, 6 x 1/2 in. 25p.

## VOLUME CONTROLS

Long spindles. Midset Size 5 K. Ohms to 2 Meg. L 00 or L1N. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p. WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 Ohm to 25 K. Carbon 80 K to 2 meg. 25p. WIRE-WOUNDS-3-WATT STANDARD SIZE POTS. LONG SPINDLE 10 OHMS to 100 K. 40p. VERBOARD 0-15 MATRIX 2 1/2 x 5 in. 25p. 2 1/2 x 3 1/2 in. 25p. 3 1/2 x 5 in. 30p. EDGE CONNECTORS 16 way 25p; 24 way 35p. PINS 36 per packet 21p. FACE CUTTERS 38p. S.R.B.F. Board 0-15 MATRIX 2 1/2 in. wide 3p per lin., 3 1/2 in. wide 4p per 1 in.; 5 in. wide 5p per lin. (up to 17 in.). S.R.B.F. undrilled 1/2 in. Board 10 x 8 in. 15p. BLANK ALUMINIUM CHASSIS 18 s.w.g. 2 in. sides. 7 x 4 in. 45p; 9 x 7 in. 60p; 11 x 7 in. 70p; 13 x 8 in. 80p; 14 x 11 in. 95p; 15 x 14 in. 99p; 11 x 3 in. 60p. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 9p; 8 x 6 in. 15p; 14 x 3 in. 16p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 3 in. 23p; 16 x 6 in. 28p; 14 x 9 in. 34p; 12 x 12 in. 40p. 1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2 p. 2-way, or 2 p. 6-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p. SILICON REC. 40-LUCAS 2DS500 Bridge 70V 5 amp 11. RECTIFIERS CONTACT COOLED 1/2 wave 60mA 38p; 80mA 48p. SILICON BY214 30p; BY100 30p; BY127 30p. TOGGLE SWITCHES, sp. 14p; dp. 15p; dp. ct. 25p.

"THE INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER 200/250v. A.C. £2.35 Post Leaflet S.A.E. 15p. HI-FI STOCKISTS RETURN OF POST DESPATCH

RADIO COMPONENT SPECIALISTS List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.)

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240v. A.C. Output voltages available 6 or 9 or 12 or 15 or 18 or 20v. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2 in. FREE

## GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U. Guitar. Can be used with Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 x 3/4". Response 25 c.p.s. to 25 Kc/s. 28db gain. For use with valve or transistor equipment. 90p Post Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V... 14p	250/25V... 14p	18-16/500V... 55p	
4/350V... 14p	500/25V... 20p	50-50/350V... 35p	
8/450V... 14p	1000/25V... 35p	60-100/350V... 55p	
16/450V... 15p	1000/50V... 47p	32-32/350V... 35p	
32/450V... 20p	8-8/450V... 18p	32-32/450V... 33p	
25/25V... 10p	8-16/450V... 20p	350-50/325V... 50p	
50/50V... 10p	16-16/450V... 25p	32-32-32/350V... 45p	
100/25V... 10p	32-32/350V... 25p	100-50-50/350V... 45p	

## LOW VOLTAGE ELECTROLYTICS

L. 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p. 500mF. 12V. 15p; 25V. 20p; 50V. 30p. 1000mF. 12V. 15p; 25V. 20p; 50V. 47p; 100V. 70p. 2000mF. 6V. 25p; 25V. 42p; 50V. 57p. 2500mF. 50V. 62p; 3000mF. 25V. 47p; 50V. 65p. 6000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 85p. CERAMIC 1pF to 0.01 mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p, 0-5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%, 2.2-500pF 8p; 500-2-200 pF 10p; 2,700-5,800pF 20p; 6,800pF-0.01, mid 30p; each. TWIN GANG. "0.0" 208pF+178pF, 65p; Slow motion drive 365+365 with 25+25pF, 50p 500pF slow motion, standard 45p; small 3-gang 500pF £1.60. SHORT WAVE, SINGLE, 10pF 30p; 25pF 55p; 50pF 55p. CHROME TELESCOPIIC AERIAL, swivel base, 23in. 20p. NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS. 1/2 w. 1/2 w. 20%, 1p; 2 w. 5p 10 ohms to 10 meg HIGH STABILITY. 1/2 w. 2%, 10 ohms to 1 meg., 10p. DITO 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 1/2 w. 10 watt, 15 watt, 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 8.2 ohms 10p.

## SCOOP! METAL PLINTH AND PLASTIC COVER

Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 1/2 x 14 1/2 x 1 1/2 in. £5.50 Post 25p

## MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6-3 v. 4 amp. £1.50  
250-0-250 60 mA. 6-3 v. 3.5 a. 6-3 v. 1 a. or 5 v. 2 a. £2.60  
350-0-350 80 mA. 6-3 v. 3.5 a. 6-3 v. 1 a. or 5 v. 2 a. £3.00  
800-0-800 v. 120 mA. 6-3 v. 4 a. C.T. 6-3 v. 2 a. £3.25  
MINIATURE 200 v. 20mA. 6-3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA. 6-3 v. 2 a. 2 1/2 x 2 1/2 in. 80p  
MINI-MAINS 20v, 100mA, 1 1/2 x 1 1/2 x 1 1/2 in. 50p  
HEATER TRANS. 6 v. 3 a. 5 watt. 10 watt. 60p  
DITO tapped sec. 1.4 v. 2, 3.4, 4.5, 6.3 v. 1 1/2 amp. 80p  
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2.25  
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60, £2.25  
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60, £2.25  
5 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60, £2.75  
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 150w. £2.25; 500w. £2.25; 750w. £1.0; 1000w. £1.4. CHARGER TRANSFORMERS. Input 200/250v. for 6 or 12v. 1 1/2 amp., 1.5-6.0; 2 amp. 1.5-6.0; 4 amp. £2.00. FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. output, 1 1/2 amp. 1.5-6.0; 2 amp. 1.5-6.0; 4 amp. £2.25. All transformers Postage 25p extra.

## E.M.I. 13 1/2 x 8 in. LOUSPEAKERS

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 15p £4. With sared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. Post 15p £2.25. State 3 or 8 or 15 ohm. Recommended Teak Cabinet Size 16 x 10 x 8 in. Post 25p £5

## 10W MINI-MODULE £3.25 LOUSPEAKER KIT

Triple speaker system combining on ready cut baffle, 1 in. chipboard 16 in. x 8 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 x 10 x 8 in. Modern design with sited wood front. Highly recommended. £5 Post 25p

## ALL MODELS "BAKER SPEAKERS" IN STOCK

## BAKER 12in. MAJOR £9

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free £11.50. Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50

## BAKER "BIG-SOUND" SPEAKERS

'Group 25' 12 inch 25 watt 3 or 8 or 15 ohm £7  
'Group 35' 12 inch 35 watt 3 or 8 or 15 ohm £9  
'Group 50' 15 inch 50 watt 8 or 15 ohm £19

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. or 10in. dia. speaker 20 x 15 x 8 in. £3. Post 25p For 13 x 8 in. or 8in. speaker 16 x 10 x 9 in. £5. Post 25p For 10 x 6 in. or 6in. speaker 16 x 6 x 6 in. £4. Post 25p LOUSPEAKER CABINET WADDING 18in. wide, 15p ft.

## GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambridge cone surround. Frequency response 30-12,000 cps. Ideal F.A. Columns, Hi-Fi Enclosures Systems, etc. £4

## ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1.90 Post 10p.

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1.50. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £3. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm, 2 1/2 in. dia.; 35 ohm, 2in.; 3in 25 ohm, 2 1/2 in. dia.; 3in dia.; 8 x 4in.; 8 x 5in. £1 EACH 15 ohm, 3 1/2 in. dia.; 7 x 4in.; 8 x 5in. TYPE 8 ohm, 6 x 4in. 3 ohm, 2 1/2 in. 3in. 5in. 5 x 3in. 7 x 4in. LOUSPEAKERS P.M. 3 OHMS. 6 1/2 in. £1.10; 8 x 3in. £1.25; 8 x 2 1/2 in. 90p; 8in. £1.75; 10 x 6in. £1.90. 5in. WOOFER 8 watts max. 20-10,000 cps. 8 or 15 ohm. £1.80. ELAC 10in. 10W. De Luxe Ceramic. 8 ohm. £4. RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £1.95 each. Post 15p. OUTPUT TRANS. EL34 etc. 25p; MIKE TRANS. 50L 25p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. GOODMANS' OUTPUT TRANSFORMER 5 watt push-pull for valves EL84 etc., 3, 8 and 15 ohms 85p. Post 20p.

## BAKER 100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250v. Separate Treble and Bass controls. £39 POST FREE. Guaranteed Details S.A.E.

## ALL EAGLE PRODUCTS

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4  
BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and turner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4.25  
BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £12  
BARGAIN FM TUNER as above less cabinet £7.50  
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Rectifier built, with volume control. 9v. £3.50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p. 9d. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 14p, closed circuit 23p; Chrome Lead Socket 45p; Phone Plugs 5p; Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 5 mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 6p; CERAMIC 6p; CANS 5p.

E.M.I. TAPE MOTORS Post 15p. 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. £1.25 Size 3 1/2 x 2 1/2 x 2 1/2 in. (illustrated). BALFOUR GRAM MOTORS 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 x 3/20. Size 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p 85p

CUSTOMERS FREE CAR PARK CALLERS WELCOME 337 WHITEHORSE ROAD, CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) Buses 50, 68, 159 pass door. Rail Selhurst Tel. 01-684-1665

# The largest selection

## NEW LOW PRICE TESTED S.C.R.'s

PIV	1A	3A	7A	10A	16A	30A
	TO-5	TO-66	TO-66	TO-48	TO-48	TO-48
50	0.23	0.25	0.47	0.50	0.53	1.15
100	0.25	0.33	0.53	0.58	0.68	1.40
200	0.35	0.47	0.87	0.81	0.75	1.60
400	0.43	0.47	0.87	0.75	0.83	1.75
600	0.53	0.57	0.77	0.97	1.25	
800	0.63	0.70	0.90	1.20	1.50	4.00

## SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
	\$p	\$p	\$p	\$p	\$p	\$p	\$p
50	0.40	0.05	0.05	0.07	0.14	0.21	0.47
100	0.04	0.06	0.05	0.13	0.16	0.23	0.75
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.27	1.25
600	0.07	0.16	0.10	0.22	0.34	0.45	1.35
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.15	0.30	0.46	0.83	2.50
1200		0.33		0.38	0.57	0.75	

## TRIACS

VBOM	2A	6A	10A
	TO-1	TO-66	TO-88
	\$p	\$p	\$p
100	30	50	76
200	50	60	80
400	70	75	1-10

## LUCAS SILICON RECTIFIERS

35 amp, 400 p.i.v. stud type. **\$1.10p** each.

**DIACS**  
FOR USE WITH TRIACS  
BR100 (D32) 37p each

## 2A POTTED BRIDGE RECTIFIERS 200V 50p

**UNIJUNCTION**  
UT46. Eqt. 2N2646, Eqt. T1843, BEN3000 27p each, 25-99 25p 100UP 20p.

**NPN SILICON PLANAR**  
BC107/8/8, 100p each; BC-99 \$p; 100 up. \$p each; Fully tested and coded TO-18 case.

**FREE**  
One 50p Pak of your own choice free with orders valued \$4 or over.

AP239 PNP GERM. SIEMENS VHF TRANSISTORS, RF MIXER & OSC. UP TO 900 MHZ. USE AS REPLACEMENT FOR AF139-AF186 & 100's OF OTHER TYPES IN VHE. OUR SPECIAL LOW PRICE:—1-24 37p each, 25-99 34p each 100+ 30p each.

**SPECIAL OFFER**  
2N2926 (Y) (O) 10 for 50p, 25 for \$1 20.00 TO CLEAR

**CADMIUM CELLS**  
ORP12 43p  
ORP60, ORP61 40p each

**PHOTO TRANS.**  
OCP71 Type. 43p

**SIL. G.P. DIODES \$p**  
300mW 30. .50  
40PIV(Min.) 100. 1.50  
Sub-Min. 500. .50  
Full Tested 1,000. 9.00  
Ideal for Organ Builders.

**D13D1 Silicon Unilateral switch 50p each.**  
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

**JUMBO COMPONENT PAKS**  
MIXED ELECTRONIC COMPONENTS  
Especially good value

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 38bs in weight. Price incl. P. & P. \$1.50 only  
Plus our satisfaction or money back guarantee.

**FULL RANGE OF ZENER DIODES**  
2-33V 400mV (D0-7 Case) 18p ea. 1W (Top-Hat) 18p ea. 10W (SO-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed  
Pak No. EQVT  
T1 8 2G3713 OC71  
T2 8 D1374 OC75  
T3 8 D1216 OC81D  
T4 8 2G381T OC81  
T5 8 2G382T OC82  
T6 8 2G344B OC44  
T7 8 2G345B OC45  
T8 8 2G378 OC78  
T9 8 2G389A 2N1302  
T10 8 2G417 AF117  
All 50p each pak

**2N2060 NPN SIL. DUAL TRANS. CODE D1699**  
TEXAS. Our price 25p each.

**100 VCB MIXIE DRIVER TRANSISTOR.** Sim. BX21 & C407, 2N1893 FULLY TESTED AND CODED ND 120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqt. ZTX300 \$p each. Any Qty.

**EX-EQUIPMENT MULLARD**  
AF117 transistors. Large can 4 leads type. Leads cut short but still usable, real value at 15 for 50p.

## KING OF THE PAKS Unequaled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED In Every Pak, or money back.

Pak No.	Description	\$p
U1	120 Glass sub-min. general purpose germanium diodes	0.50
U2	60 Mixed germanium transistors AF/RF	0.50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0.50
U4	40 Germanium transistors like OC81, AC128	0.50
U5	60 200mA sub-min. Sil. diodes	0.50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706	0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0.50
U8	50 Sil. planar diodes 250mA, OA200/202	0.50
U9	20 Mixed volts 1 watt Zener diodes	0.50
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132	0.50
U13	30 PNP-NPN sil. transistors OC200 & 28104	0.50
U14	180 Mixed silicon and germanium diodes	0.50
U15	25 NPN silicon planar transistors TO-5 sim. 2N697	0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0.50
U18	8 6-Amp silicon rectifiers BY213 type up to 600 PIV	0.50
U19	25 Silicon NPN transistors like BC108	0.50
U20	12 1-5 Amp silicon rectifiers Top-Hat up to 1,000 PIV	0.50
U21	39 A.F. germanium alloy transistors 2G300 series & OC71	0.50
U23	30 Madu's like MAT series PNP transistors	0.50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0.50
U25	25 300 Mc/s NPN silicon transistors 2N705, BSY27	0.50
U26	30 Fast switching silicon diodes like 1N914 micro-min	0.50
U29	10 1-Amp SCR's TO-5 can up to 600 PIV C8B1/25-600	1.00
U31	20 Sil. Planar NPN trans. low noise amp SN3707	0.50
U32	25 Zener diodes 400mW D07 case mixed volts, 3-18	0.50
U33	51 Plastic case 1 amp silicon rectifiers IN4000 series	0.50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	0.50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0.50
U36	35 Sil. planar PNP trans. TO-5 BFY50/51/52	0.50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 28322	0.50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0.50
U39	30 RF germ. PNP trans. 2N1303 5 TO-5	0.50
U40	10 Dual trans. 6 lead TO-5 2N2060	0.50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0.50
U42	10 VHF germ. PNP trans. TO-1 NKT667, AF117	0.50
U43	25 Sil. trans. plastic TO-18 A.F. BC113/114	0.50
U44	20 Sil. trans. plastic TO-5 BC115/116	0.50
U45	7 SA SCR's TO-66 up to 600 Piv.	1.00

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

## NEW QUALITY TESTED PAKS

Pak Description	Price \$p
Q1 20 Red spot trans. PNP AF	0.50
Q2 16 White spot R.F. trans. PNP	0.50
Q3 4 OC77 type trans.	0.50
Q4 8 Matched trans. OC44/45/81/81D	0.50
Q5 4 OC73 transistors	0.50
Q6 4 OC72 transistors	0.50
Q7 4 AC128 trans. PNP high gain	0.50
Q8 4 AC126 trans. PNP	0.50
Q9 7 OC81 type trans.	0.50
Q10 7 OC71 type trans.	0.50
Q11 2 AC127/128 comp. pair PNP/NPN	0.50
Q12 3 AF116 type trans.	0.50
Q13 3 AF117 type trans.	0.50
Q14 3 OC171 H.F. type trans.	0.50
Q15 5 2N2926 sil. epoxy trans.	0.50
Q16 2 GET880 low noise germ. trans.	0.50
Q17 3 NPN 1 SET41 & 2 SET40	0.50
Q18 4 Madu's 2 MAT 100 & 2 MAT 120	0.50
Q19 3 Madu's 2 MAT 101 & 1 MAT 121	0.50
Q20 4 OC44 germ. trans. A.F.	0.50
Q21 3 AC127 NPN germ. trans.	0.50
Q22 20 NKT trans. A.F. R.F. coded	0.50
Q23 10 OA205 sil. diodes sub-min.	0.50
Q24 8 OA81 diodes	0.50
Q25 6 1N914 sil. diodes 76PIV 75mA	0.50
Q26 8 OA85 germ. diodes sub-min. 1N69	0.50
Q27 2 10A 600PIV sil. rect. 1845E	0.50
Q28 8 Sil. power rect. BY213	0.50
Q29 4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	0.50
Q30 7 Sil. switch trans. 2N705 PNP	0.50
Q31 6 Sil. switch trans. 2N706 NPN	0.50
Q32 3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0.50
Q33 3 Sil. NPN trans. 2N1711	0.50
Q34 7 Sil. NPN trans. 2N2060, 500MHZ	0.50
Q35 3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0.50
Q36 7 2N3646 TO-18 plastic 300MHZ NPN	0.50
Q37 5 2N3053 NPN sil. trans.	0.50
Q38 7 PNP trans. 4 x 2N3703, 3 x 2N3702	0.50
Q40 7 NPN amp. 4 x 2N3707, 3 x 2N3708	0.50
Q41 3 Plastic NPN TO-18 2N3904	0.50
Q42 6 NPN trans. 2N5172	0.50
Q43 7 BC107 NPN trans.	0.50
Q44 7 NPN trans. 4 x BC108, 3 x BC109	0.50
Q45 3 BC113 NPN TO-18 trans.	0.50
Q46 3 BC115 NPN TO-5 trans.	0.50
Q47 6 NPN high gain 3 x BC167, 3 x BC168	0.50
Q48 4 BCY70 NPN trans. TO-18	0.50
Q49 4 NPN trans. 2 x BFY51, 2 x BFY52	0.50
Q50 7 BSY28 NPN switch TO-18	0.50
Q51 7 BSY35A NPN trans. 300MHZ	1.00
Q52 8 BY104 type sil. rect.	0.50
Q53 25 Sil. & germ. trans. mixed all marked new	1.50

## PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components. 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p Plus 10p P. & P. 100 Boards \$23. P. & P. 30p.

**NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

**F.E.T.'S**

2N3819	35p
2N3820	50p
2N3821	35p
2N3823	30p
2N3848	30p
2N3459	40p
BFW 10	40p
MPP105	40p

**PHOTO TRANS.**  
OCP71 Type. 43p

**SILICON PHOTO TRANSISTOR.** TO-18 Lens and NPN sim. to BP x25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

**Dual-in-Line Low Profile Sockets**  
14 and 16 Lead Sockets for use with Dual-in-Line Integrated Circuits

Order No.	Price each
1-24 25-99	100 up
TSO 14 pin type	30p 27p 25p
TSO 16 pin type	35p 32p 30p

## POWER TRANSISTOR BONANZA!

**GENERAL PURPOSE GERM. PNP**  
Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE.—OC25-29-30-35-36. NKT 401-403-404-405-406-430-451-452-453. T13027-3028, 2N250A. 2N456A-457A-458A. 2N611 A & B. 2G220-222, ETC. VCBO 80V VCEO 50V IC 10A PT. 30 WATTS Hie

**AD161** PNP  
**AD162** PNP  
M/P COMP GERM TRANS. OUR LOWEST PRICE OF 68p PER PAIR

**2N3055**  
115 WATT SIL POWER NPN 63p EACH

**SILICON 50 WATTS MATCHED NPN/PPN**  
Plastic. BIP 20 PNP. Brand new. VCBO 100V VCEO 50V IC 10A. HFE type 100/14 3mHZ. OUR PRICE PER PAIR: 1-24 26-99 100 prs. prs. prs. 60p 55p 50p

**EX-STOCK TYPE EACH AS PRICED**  
OC20 50p OC28 40p AD149 48p BD131 70p BD139 75p OC22 30p OC29 40p AL102 85p BD139 80p BD140 85p OC23 33p OC26 38p AL103 85p BD138 70p BD155 75p OC24 45p OC36 40p BD121 60p BD136 80p BU105 23 OC25 25p AD140 40p BD123 75p BD137 70p 2N3054 45p OC28 25p AD142 40p BD124 70p BD138 80p

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/S.** BSY27/28/29A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	\$p	100	For	1.75
50	For	500	For	7.50
50	For	1000	For	13.00

**OUR STOCKS** of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

**RTL MICROLEGIC CIRCUITS**

	Price each
Epoxy TO-5 case	1-24 26-99 100 up
uL900 Buffer	35p 33p 27p
uL914 Dual 2/p gate	35p 33p 27p
uL923 J-K flip-flop	50p 47p 45p

Date and Circuits Booklet for IC's Price 7p.

# -the lowest prices!

## 74 Series T.T.L. I.C'S DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C's. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed

BI-PAK Order No.	Price and qty. prices			BI-PAK Order No.	Price and qty. prices		
	1-24	25-99	100 up		1-24	25-99	100 up
BP00=SN7400	0.15	0.14	0.12	BP86=SN7486	0.82	0.30	0.88
BP01=SN7401	0.15	0.14	0.12	BP90=SN7490	0.87	0.84	0.88
BP02=SN7402	0.15	0.14	0.12	BP91=SN7491AN	0.87	0.84	0.88
BP03=SN7403	0.15	0.14	0.12	BP92=SN7492	0.87	0.84	0.88
BP04=SN7404	0.15	0.14	0.12	BP93=SN7493	0.87	0.84	0.88
BP05=SN7405	0.15	0.14	0.12	BP94=SN7494	0.77	0.74	0.88
BP07=SN7407	0.18	0.17	0.16	BP95=SN7495	0.77	0.74	0.88
BP08=SN7408	0.18	0.17	0.16	BP96=SN7496	0.77	0.74	0.88
BP09=SN7409	0.18	0.17	0.16	BP100=SN74100	1.75	1.85	1.55
BP10=SN7410	0.15	0.14	0.12	BP104=SN74104	0.97	0.94	0.88
BP13=SN7413	0.28	0.26	0.24	BP105=SN74105	0.97	0.94	0.88
BP16=SN7416	0.43	0.40	0.38	BP107=SN74107	1.40	0.93	0.98
BP17=SN7417	0.43	0.40	0.38	BP110=SN74110	0.85	0.88	0.80
BP20=SN7420	0.15	0.14	0.12	BP111=SN74111	1.25	1.15	1.00
BP30=SN7430	0.15	0.14	0.12	BP115=SN74118	1.00	0.95	0.90
BP40=SN7440	0.15	0.14	0.12	BP119=SN74119	1.35	1.25	1.10
BP41=SN7441	0.87	0.84	0.88	BP121=SN74121	0.87	0.84	0.88
BP42=SN7442	0.87	0.84	0.88	BP145=SN74145	1.50	1.40	1.30
BP43=SN7443	1.95	1.85	1.75	BP150=SN74150	1.80	1.70	1.60
BP44=SN7444	1.95	1.85	1.75	BP151=SN74151	1.00	0.95	0.90
BP45=SN7445	1.95	1.85	1.75	BP153=SN74153	1.20	1.10	0.95
BP46=SN7446	0.97	0.94	0.88	BP154=SN74154	1.80	1.70	1.60
BP47=SN7447	0.97	0.94	0.88	BP155=SN74155	1.40	1.30	1.20
BP48=SN7448	0.97	0.94	0.88	BP157=SN74157	1.40	1.30	1.20
BP49=SN7449	0.15	0.14	0.12	BP160=SN74160	1.80	1.70	1.60
BP51=SN7451	0.15	0.14	0.12	BP161=SN74161	1.80	1.70	1.60
BP53=SN7453	0.15	0.14	0.12	BP164=SN74164	2.00	1.90	1.80
BP54=SN7454	0.15	0.14	0.12	BP165=SN74165	2.00	1.90	1.80
BP60=SN7460	0.15	0.14	0.12	BP181=SN74181	2.75	2.60	2.40
BP70=SN7470	0.28	0.26	0.24	BP182=SN74182	0.97	0.94	0.88
BP72=SN7472	1.95	1.85	1.75	BP190=SN74190	3.50	3.25	3.00
BP73=SN7473	0.37	0.35	0.32	BP191=SN74191	3.50	3.25	3.00
BP74=SN7474	0.37	0.35	0.32	BP192=SN74192	2.10	1.95	1.75
BP75=SN7475	0.47	0.45	0.42	BP193=SN74193	2.10	1.95	1.75
BP76=SN7476	0.43	0.40	0.38	BP195=SN74195	1.10	1.05	0.95
BP80=SN7480	0.87	0.84	0.88	BP196=SN74196	1.50	1.40	1.30
BP81=SN7481	0.97	0.94	0.88	BP197=SN74197	1.80	1.70	1.60
BP82=SN7482	0.97	0.94	0.88	BP198=SN74198	5.50	5.00	4.00
BP83=SN7483	1.10	1.05	0.95	BP199=SN74199	5.50	5.00	4.00

PRICE-MIX. Devices may be mixed to qualify for quantity prices. PRICES for quantities in excess of 500 pieces mixed, on application. Owing to the ever increasing range of TTL 74 Series, please check with us for supplies of any devices not listed above, as it is probably now in stock. WARE 3442.

## NUMERICAL INDICATOR TUBE Type MG-17G

Cold Cathode gas-filled side-viewing numerals (0-9) and Decimal Point.

COLOUR: Neon Red.

DATA: Anode supply voltage 180 min Vdc.  
Cathode current: 0.35 Nom mA dc.

Ideal for use in constructing Digital Clocks, Desk Calculators etc., and many products described in this magazine. We recommend use of BP41 or BP141 to drive this tube.

Full data available on request.

PRICE 1-5 £1.55. 6-25 £1.40

ACTUAL SIZE

### BRAND NEW LINEAR I.C'S-FULL SPEC.

Type No.	Case	Leads	Description	Price
				1-24 25-99 100 up
BP 201C-SL201C	TO-5	8	G.P. Amp	83p 53p 45p
BP 701C-SL701C	TO-5	8	OP Amp	83p 50p 45p
BP 709C-SL709C	TO-5	8	OP Amp Direct OP	83p 50p 45p
BP 702-72702	D.I.L.	14	(G.P. OP Amp Wide Band)	53p 45p 40p
BP 709-72709	D.I.L.	14	High OP Amp	53p 45p 40p
BP 709F-7A709C	TO-5	8	High Gain OP Amp	53p 45p 40p
BP 710-72710	D.I.L.	14	Differential comparator	53p 45p 40p
BP 711-7A711	TO-5	10	Dual comparator	53p 50p 45p
BP 741-72741	D.I.L.	14	High Gain OP Amp (Protected)	75p 60p 50p
7A 709C-7A709C	TO-5	6	R.F.-I.F. Amp	43p 35p 27p
TAA 263-	TO-72	4	A.F. Amp	70p 60p 55p
TAA 293-	TO-74	10	G.P. Amp	90p 75p 70p
TAA 360	TO5	8	Wide Band limiting amplifier	170p 158p 150p

## STOP PRESS! NOW OPEN BI-PACKS NEW COMPONENT SHOP

A wide range of all types of electronic components and equipment available at competitive prices. Expert technical advice freely given.

18, BALDOCK ST. (A10), WARE, HERTS. Tel.: 61593  
OPEN 9.15-6 TUES. to SATS. FRIDAYS UNTIL 8 p.m.

## ANOTHER BI-PAK FIRST!

THE NEW S.G.S. EA 1000 AUDIO AMPLIFIER MODULE \*GUARANTEED NOT LESS THAN 3 WATTS RMS



Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/621 providing unrivalled applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines.

OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt. VOLTAGE GAIN 40dB but can be varied up to 78dB for some applications.
- Signal to Noise Ratio 86dB.
- Frequency response better than 50 Hz to 25 KHz for -8dB.
- Normal supply Voltage 9-24V.
- Suitable for 3-16 OHM Loads.
- Overall Size 2" x 3" x 1".
- Typical Total Harmonic distortion at 1 watt less than 1%.
- Supply voltage (V<sub>s</sub>) = 24V 15ohm load. Module Tested and Guaranteed.

Quantity Price each 1-9 10-85 22-83 42-28  
Larger quantities quoted on request.

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

### NOTE THESE PRICES!

#### I.C's DTL 930 SERIES LOGIC

Type No.	Function	Price
		1-24 25-99 100 up
BP830	Expandable dual 4-input NAND	13p 11p 10p
BP832	Expandable dual 4-input NAND buffer	13p 12p 11p
BP833	Dual 4-input expander	13p 12p 11p
BP835	Expandable Hex Inverter	13p 12p 11p
BP836	Hex Inverter	13p 12p 11p
BP944	Dual 4-input NAND expandable buffer without pull-up	13p 12p 11p
BP945	Master-slave JK or RS	25p 24p 22p
BP946	Quad, 2 input NAND	12p 11p 10p
BP948	Master-slave JK or RS	25p 24p 22p
BP991	Monostable	85p 60p 55p
BP982	Triple 3 input NAND	12p 11p 10p
BP9093	Dual Master-slave JK with separate clock	40p 38p 35p
BP9094	Dual Master-slave JK with separate clock	40p 38p 35p
BP9097	Dual Master-slave JK with Common Clock	40p 38p 35p
BP9099	Dual Master-slave JK Common Clock	40p 38p 35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

### DTL & TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"-out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C's and experimental work.

Pak No.	Part No.	Price	
UIC930 = 12 x $\mu$ A 930	50p	UIC948 = 8 x $\mu$ A 948	50p
UIC932 = 12 x $\mu$ A 932	50p	UIC951 = 5 x $\mu$ A 951	50p
UIC933 = 12 x $\mu$ A 933	50p	UIC961 = 12 x $\mu$ A 961	50p
UIC935 = 12 x $\mu$ A 935	50p	UIC9093 = 5 x $\mu$ A 9093	50p
UIC936 = 12 x $\mu$ A 936	50p	UIC9094 = 5 x $\mu$ A 9094	50p
UIC944 = 12 x $\mu$ A 944	50p	UIC9097 = 5 x $\mu$ A 9097	50p
UIC945 = 8 x $\mu$ A 945	50p	UIC9099 = 5 x $\mu$ A 9099	50p
UIC946 = 12 x $\mu$ A 946	50p	UIC x 925 Assorted 930 Series	£15 50

Packs cannot be split but 25 Assorted Pieces (our mix) is available as Pack UICX0 Data Booklet available for the BP930 Series, PRICE 13p

UIC00 = 12 x 7400N	50p	UIC46 = 5 x 7446N	50p	UIC81 = 5 x 7481N	50p
UIC01 = 12 x 7401N	50p	UIC47 = 5 x 7447N	50p	UIC82 = 5 x 7482N	50p
UIC02 = 12 x 7402N	50p	UIC48 = 5 x 7448N	50p	UIC83 = 5 x 7483N	50p
UIC03 = 12 x 73093N	50p	UIC60 = 12 x 7450N	50p	UIC86 = 5 x 7486N	50p
UIC04 = 12 x 7404N	50p	UIC51 = 12 x 7451N	50p	UIC89 = 5 x 7490N	50p
UIC05 = 12 x 7405N	50p	UIC53 = 12 x 7453N	50p	UIC91 = 5 x 7491N	50p
UIC10 = 12 x 7410N	50p	UIC54 = 12 x 7454N	50p	UIC92 = 5 x 7492N	50p
UIC13 = 8 x 7413N	50p	UIC60 = 12 x 7460N	50p	UIC93 = 5 x 7493N	50p
UIC20 = 12 x 7420N	50p	UIC70 = 8 x 7470N	50p	UIC94 = 5 x 7494N	50p
UIC40 = 12 x 7440N	50p	UIC72 = 8 x 7472N	50p	UIC96 = 5 x 7496N	50p
UIC41 = 5 x 7441AN	50p	UIC73 = 8 x 7473N	50p	UIC98 = 5 x 7498N	50p
UIC42 = 5 x 7442N	50p	UIC74 = 8 x 7474N	50p	UIC121 = 5 x 74121N	50p
UIC43 = 5 x 7443N	50p	UIC75 = 8 x 7475N	50p	UICX1 = 26 x Ass'd	74c £150
UIC44 = 5 x 7444N	50p	UIC78 = 8 x 7478N	50p		
UIC45 = 5 x 7445N	50p	UIC80 = 5 x 7480N	50p		

All prices quoted in new penny Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 9p per word (minimum 12 words), box number 10p extra. Semi-displayed setting £6.50 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

## Miscellaneous

### NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW  
(S.A.E. for details)

TO: 'BOFFIN PROJECTS'  
DEPT. KW210  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

### 12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, Ideal for Caravan, Tent, Emergency Lighting etc, Fully Transistorised, Low Battery Drain, With ON/OFF Switch and 12v Socket to Run other Lights or 12v Equipment.

Unbeatable at **£3.30** post paid  
or in kit form **£2.90**

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists

### JOHN SAYS...

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module £7. Unit £8.90. **WAA-WAA** Pedal kit of all parts, incl. all mechanics & instr. Only £2.95. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrots etc. costs under £20 in modules. **SYNTHESISER MODULES** and other miracles. Send 15p for illust. list.  
**D.E.W. Ltd.**, 254 Ringwood Road, Ferndown, Dorset.

### THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swings. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2½p stamp.

**RADIO AM** selling up quantity of equipment. SAE for list. 18 Knowles Place, Fairfield, Buxton.

## TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (X)

17 Buckridge, Portpool Lane, London, E.C.1

DO-IT-YOURSELF . . . . we stock a large range of audio and electronic components at very competitive prices, e.g.: chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale & Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for FREE list (2 x 3p stamps for fabric samples). Mail order ONLY. No callers please.

**AUDIOSCAN** Dept. PW3.72  
4, PRINCES SQUARE  
HARROGATE, YORKS.

## TAPE HEADS PICK-UP CARTRIDGES

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required.

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.,  
Chilton Works, Garden Road,  
Richmond, Surrey.

**WORLD RADIO TV Handbook 1972**, post free £2.25. World Radio Bulletin, fortnightly from Denmark, £2.55 surface mail, £3.17 airmail. S.A.E. for sample. Ordered together 35p off. McGarva, Chambers Street Union, Edinburgh 1.

**COMPLETE TX/RX** plus power pack; "Wireless Set Canadian No. 9 Mk. 2" 1943. Made by Marconi for use in vehicles; also complete RX Type R.G.39, frequency 100 kHz—25 MHz. Perfect working order. Tel. (Guernsey) 0481 38675, 6-7 p.m.

## . . . LOTS OF

suppliers forget to tell you that their metal locators won't function until you've first got a transistor radio with which to beat the locators signal. The **BOFFIN TREASURE PROBE**, however, comes to your doorstep with **PRINTED-CIRCUIT BOARD**, all **ELECTRONIC COMPONENTS**, a ready-drilled box to put it in plus search-coil and earphone. Think of the fun you'll have **BEACH-COMBING** with the sensitive **TREASURE-PROBE**, and the expectancy of hearing its **LOUD 'BEEP'** tell you "YOU'RE ON TO SOMETHING". **GET YOUR TREASURE-PROBE, SEND £6.95 NOW!** (S.A.E. for details)

**BOFFIN PROJECTS**

4, CUNLIFFE RD.  
STONELEIGH EWELL  
SURREY

Designed by GERRY BROWN & JOHN SALMON and presented on TV

## SYNTHESISER MODULES

Send SAE for details of voltage-controlled modules for synthesiser construction to D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

## NEW BATTERY/MAINS PORTABLES



E.D.S. LTD. offer big reductions on not only the three makes illustrated but also 29 other leading makes. Write or telephone for their leaflets and price list or call at

**EDS Ltd** 149, ESSEX ROAD  
LONDON N.1.

Telephone 01-837-2919 now!

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**RECORD TV SOUND** using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. CROWBOROUGH ELECTRONICS (P.W.), Eridge Road, Crowborough, Sussex.

**Miscellaneous**

**CHROMASONIC electronics**  
**1972 CATALOGUE**  
 10p post free  
 58 FORTIS GREEN ROAD, LONDON N10 3HN

**Situations Vacant**

**RADIO OPERATORS**  
**DO YOU HAVE PMG I, PMG II, MPT 2 YEARS OPERATING EXPERIENCE?**  
 Possession of one of these qualifies you for consideration for a Radio Operator post with the Composite Signals Organisation.  
 On satisfactory completion of a 7-month specialist training course, successful applicants are paid on scale rising to £2200 pa; commencing salary according to age—25 years and over £1548 pa. During training salary also by age, 25 and over £1152 pa with free accommodation.  
 The future holds good opportunities for established (i.e. pensionable) status, service overseas and promotion.  
 Training courses commence every January, April and September. Earliest possible application advised.  
 Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered. Full details from:  
**RECRUITMENT OFFICER, GOVERNMENT COMMUNICATIONS HEADQUARTERS, Room A/1105, Oakley Priors Road, CHELTENHAM, Glos. GL52 5AJ (Telephone: Cheltenham 21491, Ext. 2270)**

**Educational**

**TRAIN FOR SUCCESS WITH ICS**  
 Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs') RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.  
**ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS RD., LONDON, SW8 4UJ 'ACCREDITED BY THE CACC'**

**Educational**

**CIE, AMSE, City & Guilds, etc.** Thousands of exam successes. Postal Courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept H.8), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

**GO TO SEA as a Radio Officer.** Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

**RADIO, TV, RTEB CERTS.,** City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book FREE: BIET (Dept. H.7), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

**MEN!** You can earn £50 p.w. Learn computer operating. Send for FREE brochure—London Computer Operators Training Centre, E46 Oxford House, 9-15 Oxford Street, London, W1.

**For Sale**

**AMATEUR'S EQUIPMENT** and Junk for sale. Cheap. Room needed. S.A.E. list. Box No. 100.

**CRYSTAL CALIBRATED Oscillator,** complete as P.W. Oct. 67, £10. Calibrated DX Receiver, 10 valve, 13mc/s 150Kc/s, £30. Telephone Castle Hill 2842 (Dorset).

**YUKAN SELF-SPRAY** 500 ml. AEROSOL SPRAY  
 Get these NOW! in drying GREY HAMMER OR BLACK WRINKLE (CRACKLE) finishes  
 Yukan Aerosol spray contains 4000 Free quality durable easy + stain spray. No stove baking required. Hammer, available in grey, blue Modern Eggshell Black Wrinkle (Crackle) all at 85p at our counter or 90p airtight pack, per push button self-spray can. Also Durable, heat and water resistant Black Finishes for all (200p self-spray cans only) 75p carriage paid.  
 SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 25p for stop carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:  
**YUKAN 307A, EDGBWARE ROAD, LONDON W2 1BN**  
 We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations. We can supply you too.  
 Open all day Saturday, Closed Thursday afternoons.

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**TELEPHONE ANSWERING Machines.** New and Reconditioned, £55/£160. S.T.A.M.Co., 182A New North Road, N.1. 01-286 6119.

**MORSE MADE !! EASY !!**  
**FACT NOT FICTION** if you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed. Complete Course £4.50 (Overseas £1.00 Extra) Details only 4p stamp. 01-660 2895 or 01-668 3255. **G&HC (Box 19), 45 GREEN LANE, PURLEY, SURREY**

**RECEIVER A.R.88.D.** As New. Used four times. Complete Manual Spares. Phone: Stanington 386.

**Wanted**

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

**TOP PRICES PAID for NEW VALVES** popular T.V. and Radio types.  
**KENSINGTON SUPPLIES (C)**, 367 Kensington Street, Bradford 8, Yorkshire.

**HIGHEST POSSIBLE cash prices** for Akai, B. & O., Brenell, Ferrograph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

**CASH PAID** for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

**Aerials**

Direct from the Manufacturers  
**U.H.F. AERIALS**  
 EASY ASSEMBLY KITS  
**SAVE 40%**  
 10 Element £125.00 on normal retail price.  
 14 Element £150.00  
 18 Element £175.00  
 (Ready assembly kit only. 30p allow 12.0p carriage and packing. Please state office, branch or group.)  
**APEX AERIALS (P.W.)**  
 ALBION ROAD, WALSLEY ST. JOHNSSTONE, GLENSHIRE

**BAINES for High Frequency Aerials and Fittings**  
**POSTAGE PAID ON ALL AERIALS INLAND**  
 UHF Aerials: Multibeams, MEM 10 £1-90; MEM 18 £2-65; MEM 30 £3-50; MEM 38 £5-10; MEM 46 £5-50.  
 VHF Aerials: BBC Dipole £1-75; BBC H £2-50; BBC X £2-40; ITA 5 element £2; 8 element £2-70; Dipole and 5 £2; H and 5 £4-10; FM Dipole £1-40; FM 2 element £2.  
 Accessories: SAE for full list.  
 Pre-Amps: Masthead £2; Colourbooster £3-88. Please state channels on all aerials/Pre-amps orders.  
**R. BAINES**  
 11 Dale Cres, Tupton, Chesterfield

**GENUINE FULL SIZE 18 element TV aerial** as used by leading rental companies  
**FOR ONLY £1.99** + 34p p.&p.  
 A fantastic buy—save money and do-it-yourself. Receives BBC1, BBC2 and ITV on UHF 625 channels, colour and black/white. 18 element aerial with grid reflector for better reception. A proper aerial, usually supplied only by riggers. Buy now and cut out the middle man. An ideal aerial for the person who likes to do it himself. Complete with fixing clamp and instructions. Money back guarantee. Use inside or out.  
**IMPERIAL TRADING**  
 Dept. PW10, 45 ARKWRIGHT ST., NOTTINGHAM

## Service Sheets

### ★ Service Sheets and Manuals ★

COVERING RADIOS, TELEVISIONS, TAPE RECORDERS, RECORD PLAYERS, ETC. FROM 1933 UP-TO-DATE FROM 40p. EACH - 1971 SERVICE SHEET INDEX LIST 20p. - S.A.E. WITH ENQUIRIES PLEASE

#### NEW BOOKS & PUBLICATIONS ▶

	Price	Post
BEGINNER'S GUIDE TO RADIO by Gordon J. King, 7th Edition, 204 pages . . . . .	£1.00	10p
BEGINNER'S GUIDE TO TELEVISION by Gordon J. King, 208 pages . . . . .	£1.00	10p
RADIO VALVE AND TRANSISTOR DATA by A.M. Ball, 9th Edition, 232 pages . . . . .	£0.75	15p
UNDERSTANDING THE SEMICONDUCTOR by C.N.G. Matthews, 128 pages . . . . .	£1.00	10p
UNDERSTANDING TELEVISION by J.R. Davies, 512 pages . . . . .	£1.88	20p
THE PRACTICAL AERIAL HANDBOOK by Gordon J. King, 232 pages . . . . .	£2.70	15p
COLOR TELEVISION PICTURE FAULTS by K.J. Bahman, A.M.I.N.S.T.E. Illustrated in Colour . . . . .	£2.50	15p
T.V. FAULT FINDING BOOK by Data Publications Ltd, 405/425 Edition, 124 pages . . . . .	£0.50	7p
1971-1972 MULLARD DATA BOOK, Data on Valves & Semiconductors . . . . .	£0.30	5p
1970-1971 MULLARD DATA BOOK, Data on Valves & Semiconductors . . . . .	£0.20	5p
TRANSISTOR EQUIVALENTS & SUBSTITUTES HANDBOOK by B.B. Babani . . . . .	£0.40	5p
RESISTOR COLOUR CODE INDICATOR DISC . . . . .	£0.10	3p

Send S.A.E. for 'FREE' List of Practical and Technical Books on Radio & Television now available to-

## BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorkshire. Telephone 0423-86844

## TRADER SERVICE SHEETS

40p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES

LIMITED

29 CHURCH ROAD,  
TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1972 List now available at 10p plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....

(and a stamped addressed envelope)  
s.a.e. with enquiries please

**MAIL ORDER ONLY**

**SERVICE SHEETS** (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone Bexhill 7097.

**RADIO, TELEVISION** and Tape Recorders, 50 mixed odd sheets 50p. Also large stock of Obsolete/Current Valves. John Gilbert TV, 1B Shepherds Bush Road, London W6. 01-743 8441. SAE enquiries.

**SERVICE SHEETS.** Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each.

**"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"**  
Otherwise cannot be attended to  
(Uncrossed P.O.'s please, original returned if service sheets not available.)

### C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

## Ladders

**LADDERS**, timber, 20ft. £7, 29ft. £10-25. Carr. 80p. Brochure. Order C.O.D. Phone 02-993 5222 (Dept WLS) Home Sales, Baldwin Road, Stourport, Worcs. Callers welcome.

## Receivers and Components

### COMMUNICATION RECEIVERS

Checked, tested B40, R209, etc., and many others. SAE requirements.

**R1155 RX**  
Latest release, with super S/M drive in fine condition. 75kHz-1.5 MHz, 3-18.5 MHz in 5 bands. BFO, tuning ind. etc. Tested with CCT £10, carriage £1.

**VHF RX 67907**  
Compact double conversion RX with 20 min valves, AM/FM 10 ch. XTAL controlled, 250MHz approx. 500uA check/tuning meter etc., suitable for conversion to 2M. £4-50, carriage £1. Some for callers at £4.  
**RICHARD SELLERS EASTRINGTON** (254), Goole, Yorkshire.

**BRAND NEW COMPONENTS** by return. Electrolytics 15 or 25V 1, 2, 5, 10 mfd. 3-5p; 25, 50-4p; 100-5p. Mylar Film 100V .001, .002, .005 .01, .02-2p; .04, .05-2.5p; .068, .1-3p. Mullard miniature Carbon Film resistors E.12 series 1/2W 10-10MΩ 8 for 5p. Insured postage 8p. The C.R. Supply Co., 127, Chesterfield Rd., Sheffield S8.

## Receivers and Components

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 60p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875, All long leaded on panels 13in x 4in. 4 for £1, P. & P. 25p.

**708C OPERATIONAL AMPLIFIER**  
705 3 lead I.C. 1 off 50p; 50 off 35p; 100 off 20p.

**250 MIXED RESISTORS** 62p  
1/2 & 1 watt.

**150 MIXED HI STABS** 62p  
1/2, 1 & 1 watt 5% & better

### QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

### GPO EXTENSION TELEPHONES

with dial but without bell.  
85p each, P. & P. 30p.  
£1-75 for 2, P. & P. 60p.

### BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2-5kΩ coil. 8 for 50p. P. & P. 5p.

### KEYTRONICS mail order only

44 EARLS COURT ROAD,  
LONDON W.8 01-478 8499

## WITWORTH TRANSFORMERS

TV LINE OUT-PUT TRANSFORMERS

Manufacturers of the largest range in the country. All makes supplied.

Free catalogue

Modern **BAIRD, BUSH, GEC, PHILIPS**  
Replacement types ex-stock.

For "By-return" service, contact:

London: 01-948 3702  
Tidman Mail Order Ltd., Dept. PW,  
236 Sandycroft Rd., Richmond, Surrey

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-put Transformers also stocked. (182)

CALLERS WELCOME

### SOUND SUPPLIES (LOUGHTON) CO. LTD.

for Eagle International and International Rectifier Products. TOA P.A. Equipment and Mikes. Capacitors, Resistors, Plugs, Sockets, Cables, Audio Leads, Semiconductors, Valves, Vero Board, etc., for the constructor.

**ELECTRONICS DEPARTMENT,**  
12 Smart's Lane, Loughton, Essex.  
Tel. 01-508 2715.

Hours: 9.30 a.m.-1 p.m. 2-6 p.m. Mon., Tues., Wed. & Fri. 9.30 a.m.-1 p.m. 2-5.30 p.m. Sat. Closed all day Thurs.

**SHARPEN YOUR RESPONSES** with Vernitron ceramic i.f. resonators. Set of four TF-04 442, 455kHz, with associated capacitors for bandwidth 2, 4, 5-7, 7-5, 10 or 12kHz (state which), £1-85, U.K. post 5p. Mail order only. **AMATRONIX LTD.**, 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

## LOW PRICED semiconductors

All our stocks are brand new, no seconds. All guaranteed. P. & P. 5p.

### TRANSISTORS

2N 1132	25	BC 108	8	BCY 58	17
2N 1305	22	BC 109	8	BCY 59	18
2N 1613	22	BC 113	14	BCY 70	15
2N 1711	24	BC 114	15	BCY 71	20
2N 2369	17	BC 115	15	BCY 72	15
2N 2904	30	BC 116	15	BF 177	25
2N 2905	30	BC 117	19	BFX 86	25
2N 2906	25	BC 118	12	BFX 87	25
2N 3053	20	BC 125	15	BFX 88	24
2N 3054	48	BC 132	14	BFY 50	24
2N 3055	49	BC 134	14	BFY 51	10
2N 3823	75	BC 135	14	BFY 52	10
2N 3866	35	BC 137	14	BFY 90	65
AC 141K	20	BC 138	24	C 426	30
AC 142K	18	BC 148	11	C 428	20
AC 187K	20	BC 149	12	C 450	15
AC 188K	25	BC 182L	10	ME 0412	19
AC 19	22	BC 183L	10	ME 4101	10
AFY 239	37	BC 184L	12		
BC 107	8	BC 212L	12		

### DIODES

400 mWatt  $\pm 5\%$  3.3v to 30v. 10p each. 1 Watt  $\pm 5\%$  following valves only 25p 10v, 12v, 15v, 18v, 24v, 33v, 39v, 47v, 100v, 180v.  
IN 4148 6p OA 90 7p OA 91 7p

### RESISTORS

Carbon film  $\pm 10\%$  1p each Range 2-2 ohms to 10 meg ohms. Type TR5 triple rated  $\frac{1}{2}$  watt. Tin oxide resistor  $\pm 2\%$  3p each Range 10 ohms to 1 meg ohms.

Send for FREE Price List, includes hundreds of transistors, CAP'S, TTL'S, neon, etc.

FREE EQUIVALENT CHART

**G. HADLEY (PW)**  
24 WOODHILL,  
HARLOW, ESSEX.

NEW

**12 Watt Hi-Fi**  
plus 25p postage packing  
**£3.75** **AMPLIFIERS**

A great new 12 watt Hi-Fi amplifier is now available at the low cost of £3.75. Just look at the specification—Power 15 Watts R.M.S., frequency response 15 cs. Signal to noise ratio better than 70 db, Harmonic Distortion 0.1%. Input sensitivity 750mv into 2k. These factors make the H Electronics Hi-Fi amplifier the best at its price—order now.

**H ELECTRONICS.**  
105, Grange Road, London, S.E. 25

200 Mixed Resistors— $\frac{1}{2}$ , 1, 1 watt types	50p
5 x 700ohm Relays 2p 2co (very small)	50p
5 x 350ohm Moving Coil small sealed type	50p
10 x 2k Wire Wound small pots	50p
3 Transistors and circuit for 750mv amp	50p
1 watt, 5 transistor Amplifiers 9v 3ohm output	£1 each

MAIL ORDER ONLY. P. & P. 10p.

**A. J. MANLEY, 13 Randisbourne Gardens,  
Bromley Road, London S.E.6**

**EX-GOVT. COMMUNICATIONS RECEIVERS,** calibrators, signal generators, components, etc., with money back guarantee. S.A.E. list. Callers welcome, please phone first. P. R. Gollidge, G3EDW, Glen Tor, Tarrington, Devon. (STD 08-052) 2411.

### SINCLAIR IC-12

£2.45

Integrated circuit amplifier and pre-amp with 6W rms output. Frequency response 5Hz-100kHz. Harmonic distortion less than 1%, and typically 0.1%. Supplied complete with instructions and free printed circuit. Also available kits of parts including simple volume and tone controls to complete mono version £4.00. Similar for stereo version £2.45. Loudspeakers 8" (3 ohm) 50p, 8" x 5" (8 ohm) £1.35. Ideal power supply for the IC-12 is the Sinclair PZ5 £4.00.

### SINCLAIR PROJECT 605

The easy new way to buy and build project 60. Comes in one handy pack containing PZ5, two Z30 amplifiers, Stereo 60 and the new master-link module, which has all the input sockets and output components needed. Special cut to length leads make all soldering unnecessary.  
ONLY £20.95

### TRANSISTOR SENSATION

Thanks to bulk buying we have been able to smash the price of our well known surplus PNP Silicon transistors from the 2S300 series. These are untested and unmarked but we guarantee that at least 80% are good usable transistors. 100 for 55p, 200 for £1.00, 1000 for £3.60.

### S-DECS AND T-DECS

S-DeCs £1.25. T-DeCs £2.50.  $\mu$ -DeC A £2.00. Carriers with sockets to mount 14 and 16 pin in line ICs on T-DeC and  $\mu$ -DeC A £1.10.

### AUDIO CABLES AND PLUGS

DIN audio line plugs: 2 way 12p, 3 way 13p, 5 way 15p.  
DIN chassis mounting sockets: 2 way 10p, 3 way 12p, 5 way 12p.  
Screened cable with grey PVC outer sheath: Standard single 6p per yd., twin screened 9p per yd.  
3 core standard mains cable 8p per yd.  
Flat twin PVC loudspeaker cable 3p per yd.

### PROJECT 60 OFFERS

Stereo 60/2 Z30/PZ5	£16.75
Stereo 60/2 Z30/PZ5	£18.95
Stereo 60/2 Z50/PZ8	£20.25
Transformer for PZ8	£2.45
Completion kit (see below)	£2.40
Project 60 FM Tuner	£19.50
Active Filter Unit	£4.50
PZ5 Power unit, 30V unstabilized	£4.00
PZ6 Power unit, 35V stabilized	£6.40
PZ8 Power unit, 45V stabilized	£6.40
Z30 Amplifier, 15W rms into 8 ohms	£3.60
Z50 Amplifier, 30W rms into 8 ohms	£4.15
Stereo 60 Preamp/Control unit	£7.80
Q16 Loudspeaker	£7.40

### PROJECT 60 KIT

Our extremely popular completion kit contains the extra capacitors, DIN plugs and sockets, cables and fuse holder needed to complete Project 60 at the attractive price of £2.40.

### MULLARD UNILEX

EP9000 Amp £2.40. EP9001 Pre-amp £2.60. EP9002 Power unit £3.90. Control unit £2.80. Unilex booklet £0.22.

## SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent

Mail order only. Postage 37p on Project 60 orders 10p on others.

### NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateur, Mobile, Radio 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only £3.40. P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12p. P. & P. Free.

Cheques, Postal Orders to:

Dept. P.W.,  
Galleon Trading Co., 25 Avelon Road,  
Romford, Essex

NEW 8in. SPEAKERS 16 ohms 75p. p. & p. 10p.

**BARGAIN PARCELS** 14lb at £1.45 plus 22p p.p.; 25lb at £2.75 plus 22p p.p.; 50lb at £4.50 plus £1.25 p.p. Contains pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

**FANTASTIC BARGAIN.** New 6 inch tubes. E450 4/8/16 4V1, medium Persistence, green. Ideal scope tube. List price £5. Our price £1.40 carriage paid.

**500  $\mu$  AMP METERS.** Approx. 1" on panel with plug and switch ex new equip. 75p. p. & p. paid.

**NEW HEAVY COAX CABLE** dia.  $\frac{1}{2}$ " 70 ohms approx. 50ft. lengths £1.40, p. & p. 30p. 100 ft. lengths £2.70, p. & p. 50p.

**VHF AERIAL TUNING UNITS** consisting of the following: 1-1 $\frac{1}{2}$ " 500 micro/ampmeter. 1 small 2-gang 75 P $\mu$  capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 25/30 watts R.F. input. Size only 5 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ " x 5" sealed. Price £1.37 $\frac{1}{2}$  p.p. 25p.

**CRYSTALS AS NEW:** He 6u, 5,945; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,800; 2,295 Kc/s. 50p each plus 8p. p.p.

**SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS.** 10% tolerance  $\frac{1}{2}$  &  $\frac{1}{4}$  watt. Preferred values in packets of 10. Our price 50p per 100, 95p per 200, £1.35 per 300, 500 at £2.12 $\frac{1}{2}$ . Our selection. p.p. 8p per 100 and 8 $\frac{1}{2}$ p per extra 100.

**TRIMMER BARGAINS.** These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice.

Trimmers without Xtal—60p per doz. plus 17 $\frac{1}{2}$ p p.p. Trimmers with Xtal—75p per doz. plus 17 $\frac{1}{2}$ p p.p. Also 20 PF min. brand new air spaced. 50p per doz. plus 17 $\frac{1}{2}$ p p.p.

**ANY HEIGHT AERIAL TUBULAR SECTIONS**  $\frac{3}{4}$ " dia x 3 ft. long. Brass screw in ends, copper coated and painted. Good condition. 20p, p. & p. 5p each. Minimum order 10.

**BRAND NEW HARTLEY OSCILLOSCOPES** CT316 in original packing. Band width up to 5 Mc/s. Mains supply. Price £40, p. & p. £1.50p.

**AERIALS NEW CONDITION.** Whip type 4ft. 25p. 11ft. 75p. 14ft. 87p. Used condition 4ft. 20p. 14ft. 75p. All collapsible type. P. & p. 4ft. 10p, rest at 17 $\frac{1}{2}$ p. New bases on adjustable clamp for above 82p p. & p. 25p. New matching unit coax connection for above 30p p. & p.

Huge release of valves for the 62 set TX/RX. In original rubber packing consisting of QV047 x 61M. ARP13 etc. 10 valves in all at the bargain price as seen 87 $\frac{1}{2}$ p plus 17 $\frac{1}{2}$ p p.p.

R209. Set of valves 62p. p.p. 25p.

**NEW AERIAL WIRE ON BOARDS 7/23 UNCOVERED** 75ft. 40p, 90ft. 47 $\frac{1}{2}$ p, 100ft. 55p, 180ft. 95p, 250ft. £1.80p, p. & p. 20p.

### MURHEAD DECADE A.F. SIGNAL GENERATOR.

This precision instrument can be used:  
1. To Measure Gain up to 50 dbs.  
2. To Measure Loss up to 45 dbs.  
3. To compare Power levels (A.F.).  
4. As an Audio Frequency Generator covering 100 Hz to 41 kHz. With a dial setting accuracy of  $\pm 0.5$  Hz. Output:—1 M/V into 600  $\Omega$ L. Complete with mains power unit. Tested. Good Condition. £12, p. & p. 75p.

**ENCLOSED AERIAL RELAY COIL.** Res. 700 ohms approx. 25 watts RF BNC outlet, working voltage 12v. 75p, p. & p. 10p. £1 with BNC plugs.

Also 1" 75 ohm Coax in 50ft coils with BNC plugs good condition. price £1 + 30p. p.p.

**NEW BOXED AMP METERS** 1 $\frac{1}{2}$ " 20-0-20 dc. 65p. P. & p. 5p.

**AS NEW UNUSED REJECTOR UNITS** for rejecting unwanted signals. Four ranges 1-2-10 Mo/s. £1.50 p. & p. 20p each.

**AS NEW UNUSED AERIAL AVRIOMETER.** Cylinder design 10" x 4 $\frac{1}{2}$ ", suitable for tuning most aerials for signal strength. £1.50 p. & p. 25p.

**NEW HEADPHONES AND MIKE RUBBER** muff type low impedance 97 $\frac{1}{2}$ p. p. & p. 17 $\frac{1}{2}$ p. Also DLE number 5, low impedance used condition 62p p. & p. 17 $\frac{1}{2}$ p.

**TF1449 SIGNAL GENERATORS.** Good condition £12 p. & p. £1.50

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

**WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.**

**A. H. THACKER,**  
Radio Dept.,  
HIGH STREET, CHESLYN HAY.  
Nr. Walsall, Staffs.

## Receivers and Components

### EX-RENTAL TV's (UNTESTED)

Complete with 13 channel tuners. Good cabinets.  
Carriage £1-50 extra.

17" Semi Slim (30" Tube) ..	£2-50
17 1/2" Slim (110" Tube) ..	£4-50
19" Slimline ..	£6-50
23" Slimline ..	£8-50
19" BBC2 Sets ..	£14-50

### TUBES EX EQUIPMENT (Tested)

**SINGLE PANEL**

17" any type ..	£3-00
19"/21" any type ..	£3-00
23" any type ..	£4-00

**TWIN PANEL (BONDED)**

19" bonded ..	£5-00
23" bonded ..	£8-00

**PANORAMA TUBES (METAL RIM)**

19" Panorama ..	£5-00
23" Panorama ..	£8-00

All tubes add £1 carriage.

### PERFECT SPEAKERS EX T.V.

Pm 3 ohm (minimum order two) 5 in. round, 8 in. by 2 in. rectangular—12p each. Add 7 1/2p per speaker p. & p.  
Special offer:—100 Speakers delivered for £15-00.

### VALVES EX EQUIPMENT

EB91	5p	30L15	12 1/2p	PL36	22 1/2p
EB98	12 1/2p	30P4	12 1/2p	PL31	17 1/2p
EC92	12 1/2p	PC97	17 1/2p	PY31	15p
EC180	7 1/2p	PCF86	17 1/2p	PY800	15p
EF80	12 1/2p	PC84	7 1/2p	PY82	7 1/2p
EF85	12 1/2p	PCF80	7 1/2p	PY33	22 1/2p
EF183	12 1/2p	PCC89	12 1/2p	U191	17 1/2p
EF184	12 1/2p	PCL85	22 1/2p	8P23	17 1/2p
EY86	17 1/2p	PCL92	17 1/2p	30PL1	22 1/2p
30PL13	20p	PCL86	17 1/2p	30P12	30p
630LZ	12 1/2p	PCL83	12 1/2p	30F5	10p

Add 2 1/2p per valve p. & p., orders over £1 p. & p. free

### UHF TUNERS

For Ferguson 850 900 chassis. Adaptable for most UHF Chassis £2-50, p. & p. 30p.

## TRADE DISPOSALS (Dept. PW/TS)

Thornbury Roundabout, Leeds Rd., Bradford.  
Telephone 0274/665070

2N2926, GUARANTEED, 8p. OC23 Power Transistor, ex-equipment tested, 18p, p&p 8p. Mr. R. Tustin, 45 Brockhurst Street, Walsall.

**BEST QUALITY WIRE, PVC covering 1/036in.—50m 60p; 100m £1. 25/0.19mm—50m 80p; 100m £1.50, 37/006in. Silver plated copper—50m £1; 100m £1.75. New PO 3000 Relays 1,000, 4 H.O. contacts—35p; p&p 10p per item. Similar used repairable relays 10 for £1.25 incl. postage. Poole Electronics, 68 Danecourt Road, Poole, Dorset.**

### Build your P.W. Projects on new

## NIPPIBOARDS

PRINTED WIRING BOARD FOR TRANSISTORS

- Take Twenty Series SRBP Nippiboard Type 1A
- Experimenters Circuits Supplement-Nippiboard Type 1A (except Nos. 5, 8, 12, 13, 15, 19, 20, 21, 22)
- Transistor Circuitry for Beginners — Type 1A
- Stereo Decoder Unit — Type GAS
- AF/RM Mini Probe — Type 1A
- Sound Operated Flash — Type 1A
- Hypnoscope — Type 2A
- Car Rev Counter — Type 2A

Ask for NIPPIBOARD Types for other P.W. P.E. EE projects SRBP types or equivalent in FIBREGLASS

1A 15p	2AS 23p	1B 18p	2BS 34p
2A 28p	4AS 44p	2B 34p	4BS 52p
3A 36p	6AS 64p	3B 43p	6BS 72p
5A 52p	8AS 75p	5B 67p	8BS 91p

We can still supply IC 3L403D NOW DOWN TO £1.88

**NIP ELECTRONICS**  
Dept. NB/W, P.O. Box 11, St Albans, Herts.

**Assorted Wire-Wound Resistors.** A very good selection. 50 for 60p. P.P. 10p.

**Assorted Tag Strips.** Many different types. 100 for 50p. P.P. 10p.

**Mullard BY127 Silicon Diodes.** 800 P.I.V. 1 Amp. 15p post paid. Carbon Film Resistors. 1/2 watt 5%. Complete range stocked. 1 1/2 p each or £1 per 100 your selection.

**Assorted Potentiometers.** Includes ganged types etc. 10 for 50p. P.P. 10p.

**Plessey 1 Meg. Inv. Log. + 1 Meg. Inv. Log., D/P switched.** 50p.

**Toggle Switches. S.P.S.T.** 12p each.

Mail Order only.

**XEROZA RADIO**

1 East Street, Bishops-Tawton,  
DEVON

## TRIO

Thinking of buying a TRIO?

TS. 510, JR. 310, 9R-59-DS, etc. on demonstration. Send large SAE for "RSG" test report on JR.310 with Top Band, 144MHz Con. use, Cal. unit, etc. Borrow a manual for seven days. Deposit £2.

Hire purchase—Part exchange—Photo/Hi-fi equipment, etc.

### HOLDINGS

39-41 Mincing Lane, Blackburn BB2 2AF  
Tel: 59595/6



## LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8/15 ohm ..	£19-50
Fane Pop 60 watt 15" 8/15 ohm ..	£11-15
Fane Pop 50 watt 12" 8/15 ohm ..	£9-25
Top 20 12" 25 watt 8 or 15 ohm ..	£6-75
Top 10 10" 10 watt 8 or 15 ohm ..	£3-25
Baker Group 25" 25 watt 3, 8 or 15 ohm	£6-55
EMI 13 x 8, 3, 8 or 15 ohm ..	£2-25
EMI 13 x 8 with tweeter 3, 8 or 15 ohm ..	£2-95
EMI 13 x 8 twin tweeter 3, 8 or 15 ohm ..	£3-90
Handsome teak finish cabinet 17" x 10" x 6" for above 13 x 8 units (p. & p. 35p) ..	£5-00
Celestion 8" Round 15 ohm ..	£2-05
Celestion PS8 for Unitek ..	£2-35
Richard Allan 8" Round 8 ohm ..	£2-75
Fane 8" dual cone 8 ohm ..	£2-85
Handsome teak finish cabinet 17" x 10" x 6" to suit all above 8" units (p. & p. 35p) ..	£5-00
Elac or Goodmans 8" x 5" 3, 8 or 15 ohm	£2-15
Handsome teak finish cabinet 12" x 8" x 6" for above 8 x 5 units (p. & p. 25p) ..	£3-45
Goodmans 6 1/2" twin cone 8 ohm ..	£2-45
E.M.I. 10 x 6, 3, 8 or 15 ohm ..	£2-15
Fane 7 x 4, 3 or 8 ohm ..	£1-50
Richard Allan 12" round 3 or 15 ohm ..	£2-50
EMI 2 1/2" tweeter 3 ohm ..	65
Plessey 3" 80 ohm ..	65
Eagle CT10 tweeter ..	£1-50

All units guaranteed new and perfect.  
Prompt despatch p. & p. 25p per speaker.

Send 9p stamps for our fabulous discount catalogue of radios, tape recorders, HiFi, etc. (Illustrated).

**WILMSLOW**  
**AUDIO, M. O. Dept.**  
10 Swan St., Wilmslow,  
Cheshire

### TRAMPUS ELECTRONIC

Brand New to spec. Money Back Guaranteed. BC107 8p. BC108 8p. BC109 8p. 2N3055 53p. Op Amps 709 34p. 741 35p. TAA203 55p. PA257 £1-49. TAD100/110 Rx £1-67. Zeners 400mW 12p. LIGHT EMITTING DIODES. Visible red 2v 67p. 1a. 50v. bridge 30p. IC Photo Detector & amp 55p. Numerical Indicator. 0-9, Dec Pt. 5v 8mo bar 7 segment type 3015P £1-93. FITs DIL Sockets. 16 Pin 14p. 14 Pin 12p. 7447 driver £1-23. FREE CATA-LIST, SAE. Data Sheets 6p. C.W.O. P.P. U.K. 7p. DISCOUNT 10+10%. P.O. BOX 29, BRACKNELL, BERKS.

**RADIO SPARES COMPONENTS** specified for projects in this, and other magazines supplied on request. SAE with all enquiries. The Hobbies Shop, 32 The Parade, Cwmbran Town Centre, Cwmbran, Mon.

## INCOMPARABLE V.H.F. KIT


Johnsons CV2—unique triple-purpose (Converter, Receiver, Tuner-Feeder) kit for the Amateur enthusiast. Fantastic transistorized performance, World Wide Sales. Complete kit of top grade parts with coils covering 80-180 MHz, plus easy/build diagrams and instructions. £4 direct from makers or S.A.E. for free literature.

### JOHNSONS (RADIO) ST. MARTINS GATE WORCESTER WRI 2DT

Est. 1943      Tel. 24864  
(A division of the G-BAN Organization)  
SHORT WAVE & CRYSTAL SET KITS  
AVAILABLE SOON

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

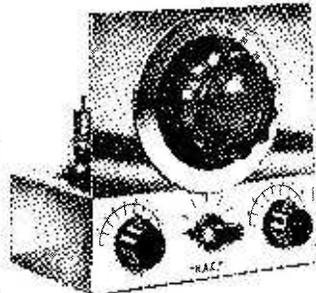

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

#### NEW "DX" RECEIVER

Improved over valve model "DX" mark 2. Complete kit—price £2.90 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.). Send now for free descriptive catalogue & order form.

**"H.A.C." SHORT-WAVE PRODUCTS**  
29 Old Bond Street, London W.1

# Discosound

Manufacturers of a comprehensive range of High Quality Equipment

**DISCOTHEQUES · PA AMPLIFIERS  
MIXERS · LIGHT CONTROL UNITS  
SPEAKERS ETC.**

Send for full details of the Discosound range

**Discosound** 122 Balls Pond Rd, London N.1 Tel: 01-254 5779



## ELEKON SPECIAL OFFER

**Twin Power Supply Panels**, contains 2 x Texas 1810J10 Silicon Bridge Rectifiers, 100 P.I.V. at 1A; 1 x Mullard OAZ225 Zener Diode, 7.5V, 10W; 1 x I.T.T. Zener Diode, 5.1V, 1W; 5 x Texas IS121 Silicon Diodes, 150 P.I.V. at 200mA. Electrolytic Capacitors, 2 x Plessey 1,000µF, 25V; 2 x 50µF, 50V; 2 x Mullard 250µF, 25V; 2 x Mullard 640µF, 25V; Circuit details supplied. A very definite bargain £4, post 10p.

**Metal Panels** with 2 McMurdo B11A Nylon Relay or Valve Bases; 1 McMurdo 8-way; 1 x 10-way Edge Plugs and Sockets. 2 Panels for 50p, post 10p.

**Transformers**, Primary 10-0-100-125-200-220-240V; Secondary 10-0-10V at 15mA, 1.25V at 1A, 50p, post 10p.

**Bargain Component Parcels**. Includes Resistors, Plugs, Sockets, etc., etc. 4lb net weight, £1, post 30p.

**Mixed Wire-Wound Potentiometers**, 10 for 50p, post 10p.

Mullard Zener Diodes, OA2224, 6.8V at 10W, 3 for 50p.

Fantastic range of Electrolytic Capacitors. Write for details.

### ELEKON ENTERPRISES

12A TOTTENHAM STREET, LONDON W1P 9PQ  
Telephone 01-580 7391

## NEW VALVES! GUARANTEED AND TESTED

### 24-HOUR SERVICE

1R5	25	30FL14	67	DY86	28	EF85	26	PC089	48	PY81	28
1R5	21	30L15	56	DY87	28	EF86	28	PC0189	47	PY82	24
1R4	14	30L17	66	DY89	30	EF89	24	PC080	27	PY80	32
3S4	24	30P4	56	EABC80	30	EF91	12	PCF86	43	PY801	33
3V4	37	30P19	56	EB91	9	EF183	26	PCF801	27	R19	29
5Y3GT	25	30PL1	58	EBC33	38	EF184	28	PCF802	38	U25	68
6/30L3	58	30PL13	87	EBF89	27	EL33	54	PCF805	59	U26	55
6AQ5	21	30PL14	63	ECC81	15	EL84	22	PCF82	30	U191	57
6BW7	50	DAF91	21	ECC82	18	EY51	30	PCL83	55	U251	68
6E1	57	DAF96	35	ECC83	21	EY86	28	PCL84	33	U329	65
6EP3	87	DC200	80	ECC82	26	EZ80	20	PCL85	37	U801	78
6P25	51	DF91	14	ECH35	53	EZ81	21	PCL86	37	UBF89	29
6SN7GT	28	DF96	35	ECH42	58	KT61	54	PFL200	51	UCC85	84
25L6GT	18	DK91	25	ECH81	26	KT66	75	PL36	47	UCH81	80
30C15	56	DK92	35	ECL80	29	N78	85	PL81	48	UCL82	81
30C17	75	DK96	86	ECL82	29	PC86	45	PL83	31	UL84	89
30C18	58	DL92	24	ECL86	34	PC88	45	PL84	29	UY85	84
30F5	88	DL94	37	EF39	36	PC900	30	PL500	61	W77	42
30FL1	58	DL96	38	EF80	22	PCC84	28	PL504	61	Z77	18

Post/Packing on 1 valve 6p, on 2 or more valves 3p, per valve extra. Any parcel insured against damage in transit 3p, extra. Office address, no callers.

**GERALD BERNARD** 83 Osbaldeston Road, Stoke Newington, London N.16

## INDEX TO ADVERTISERS

Adcola Products Ltd.	1029	Felstead Electronics	1028	R.D.I.	1034
Antex	959	Field Electrics Ltd.	984	Radio Component Specialists	1031
Apex Aerials	1035	Gladstone Radio	988	Radio Exchange Ltd.	1019
Audioscan	1034	Global Audio Discount Warehouse	1028	Radio & T.V. Components (Acton) Ltd.	972, 973
Baker Reproducers Ltd.	1030	Government Communication Headquarters	1035	Readers Radio	988
Bell's Television	1036	H-Electronics	1037	ROC Electronics Ltd.	962, 963
Bentley Acoustic Corporation Ltd.	1020	HAC Shortwave Products	1038	RCS Products (Radio) Ltd.	984
Bernard, Gerald	1039	Harverson Supplies Co. Ltd.	987	RSC Hi-Fi Centres Ltd.	cov. ii 953
B.I.E.T.	1016 cov. iii	Henry's Radio Ltd.	1015, cov. iv	R.S.T.	971
Bi-Pak Semiconductors	1032, 1033	Hi-Fi News and record review	960	Salop Electronics	1034
Bi-Pre-Pak Ltd.	983	Home Radio (Components) Ltd.	971	Sinclair Radionics Ltd.	1025, 1026, 1027
Boffin Projects	1034	Ivoryet Ltd.	954	Shopertunities Ltd.	958
Boots Co. Ltd.	966	Imperial Trading	1035	Sound Supplies	1036
British National Radio School	974, 1029	International Correspondence Schools	966, 1011-1035	Smith, G. W. & Co. (Radio) Ltd.	967, 968, 969
Broadway Electronics	970	Jermyn Industries	954	Surpletronics	964
Bull, J. (Electrical) Ltd.	961	Johnsons (Radio) Ltd.	1038	Surplus Electronic Trading	884
CBM Electronics Co.	1028	KVA Electronics	984	Swanley Electronics	1034
C.T. Electronics Ltd.	1030	Keytronics	1036	Thacker, A. H.	1037
Carrana, C.	1036	King, J. M.	1034	Thornbury Trade Disposals	1038
Chromasonic Electronics	1035	Lasky's Radio	955	Tidman Mail Order	1036
Codar Radio Co.	1020	Lewis Radio	964	Velco Electronics	964
Comet High Fidelity Discount Warehouses	956, 957	Light Soldering Developments Co. Ltd.	954	Vero Electronics Ltd.	958
Concord Electronics Ltd.	1023	Linear Products Ltd.	988	West London Direct Supplies	958
Dabar Electronics	958	M & B Components (Leeds) Ltd.	1024	Weyrad (Electronics) Ltd.	964
DEW Wokingham	1034	Manley	1037	Wicks, D. T. & Co.	1016
Discosound	1039	Marshall, A. Son	965	Wilmslow Audio	1038
Duke & Co.	1028	Merlin Supplies Co.	954	York Electronics	1024
E.D.S.	1034	Multicore Solders Ltd.	966	Yukan Self Spray	1035
Elekon Enterprises	1039	NIP Electronics	1038	Z & I Aero Services Ltd.	1040
Electro Value	1023	Padgetts Radio Store	960		
Electro-Tech Sales Ltd.	970	Partridge Electronics Ltd.	960		
		Pembridge College	1030		

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 12½p in £ for postage and handling  
MINIMUM CHARGE 15np. No C.O.D. orders accepted  
Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 586 8403  
Open all day Saturday

0A2	0.38	6A05	0.88	6EW6	0.70	8Y6G	0.70
0A3	0.45	6AQ6	0.65	6F1	0.75	7Y4	0.65
0B2	0.35	6AR5	0.45	6F5	0.75	9B7W	0.60
0B3	0.70	6AR6	0.55	6F6	0.55	10C2	0.50
0C3	0.38	6AR11	1.25	6F11	0.40	10D1	0.55
0D3	0.35	6AS5	0.45	6F13	0.45	10D2	0.50
1B3GT	0.40	6AS7G	0.85	6F14	0.70	10F1	0.75
1L4	0.20	6AT6	0.35	6F15	0.85	10F9	0.80
1R4	0.45	6AU6	0.25	6F18	0.50	10F13	0.50
1R5	0.40	6AV6	0.30	6F22	0.85	10L1	0.50
1R8	0.30	6AW8A	0.60	6F24	0.75	10LD11	0.85
1R5	0.30	6BA6	0.25	6F25	1.00	10P13	0.60
1T4	0.30	6BE6	0.30	6F26	0.35	10P14	1.10
1U4	0.30	6B7E	1.00	6F28	0.85	12AB5	0.70
1V5	0.60	6B7E	0.55	6GK6	0.60	12AC6	0.50
1V7	0.50	6B7E	0.75	6J4	0.50	12AD6	0.55
1X2B	1.50	6B7E	0.50	6J5GT	0.75	12AE6	0.55
2A3	0.50	6BK7A	0.60	6J6	0.20	12AL5	0.50
2C4	0.70	6BN5	0.43	6J7	0.45	12AQ5	0.50
2D21	0.38	6BN6	0.45	6KGGT	0.60	12AT6	0.30
3A4	0.40	6BQ5	0.25	6K7	0.35	12AT7	0.35
3BP1	3.00	6BR8	0.70	6KR9	0.40	12AU6	0.35
3B25	2.50	6BR7	1.30	6J4	0.75	12AU7	0.30
3B5	0.35	6BW6	0.85	6LAGT	0.45	12AV6	0.40
3V4	0.48	6BW7	0.80	6L7	0.40	12AV7	0.65
5R4GY	0.75	6BX6	0.25	6L18	0.45	12AX7	0.30
5U4G	0.85	6BZ6	0.40	6LD20	0.50	12AY7	0.75
5V4G	0.45	6C4	0.33	6N7GT	0.45	12B4A	0.60
5Y3GT	0.40	6C8GT	0.40	6P1	0.60	12B4E	0.40
5Z3	0.40	6B7E	0.35	6P28	0.85	12AU7	0.30
5Z4G	0.40	6C8GAL	0.25	6Q7	0.40	12BE6	0.40
6/30L2	0.90	6CG7	0.55	6SA7	0.40	12BH7	0.45
6AB4	0.35	6CH6	0.60	6S7	0.40	12BY7	0.80
6AF4A	0.55	6CL6	0.55	6K7	0.40	12K5	0.70
6AG5	0.22	6CW4	0.65	6S17GT	0.35	12K7GT	0.40
6AG7	0.40	6CY5	0.45	6S7GT	0.35	12Q7GT	0.40
6AH6	0.50	6CY7	0.70	6S7	0.40	12R7	0.40
6AJ8	0.30	6D3	0.50	6S7	0.40	12R7	0.40
6AK5	0.35	6DC6	0.80	6T8	0.35	10L1	1.10
6AK6	0.60	6DK6	0.50	6U4GT	0.65	10P1	0.50
6AL3	0.43	6D8B	0.70	6U8A	0.40	10P14	1.10
6AL5	0.20	6EA8	0.65	6X4	0.35	25C5	1.50
6AM5	0.35	6EH7	0.30	6X5GT	0.40	55L6GT	0.50
6AM6	0.33	6EJ7	0.30	6X8	0.60	55Z4G	0.30

First Quality Fully Guaranteed



ELECTRONIC VALVES

25Z6GT	0.85	50CD6G1.20	DK92	0.55	ECC88	0.40	
30A5	0.50	50L6GT.55	DL96	0.45	ECC89	0.50	
30AB3	0.40	55A2	0.50	DM160	0.85	ECC91	0.50
30C1	0.30	90A1	2.40	DY88	0.32	ECC189	0.65
30C15	0.80	90AV	2.50	DY87	0.33	ECC807	1.25
30C17	0.90	90C1	0.65	DY802	0.35	ECCF80	0.35
30C18	0.80	90CV	2.40	E88CC	0.65	ECCF82	0.35
30F5	0.85	907	0.50	E180F	1.00	ECCF86	0.65
30FL1	0.75	813	3.75	E167F	2.50	ECCF84	0.55
30FL12	1.00	866A	0.75	EA-BC800.35	0.55	ECH35	1.00
30FL14	0.85	5642	0.70	BAF42	0.55	ECH42	0.75
30L1	0.40	5670	0.50	EBC33	0.50	ECH81	0.30
30L15	0.85	6080	1.80	EBC41	0.55	ECH83	0.45
30L17	0.80	6146	1.60	EBC81	0.30	ECH84	0.45
30P12	0.80	6148B	2.50	EBF80	0.40	ECL80	0.45
30P19	0.55	6360	1.25	EBF83	0.40	ECL81	0.50
30PL1	0.75	6939	2.25	EBF89	0.30	ECL82	0.35
30PL13	0.93	7199	0.80	EC33	0.50	ECL83	0.70
30PL14	0.90	7360	2.00	EC86	0.80	ECL84	0.55
35A3	0.55	7386	1.25	EC88	0.80	ECL85	0.55
35A5	0.75	7895	1.25	EC90	0.33	ECL86	0.40
35B5	0.65	9003	0.50	EC91	0.60	EF40	0.50
35C5	0.50	9003	0.50	EC92	0.35	EF41	0.65
35D5	0.75	AZ1	0.55	EC93	0.55	EF42	0.70
35L6GT	0.50	AZ31	0.55	EC8010	2.25	EF80	0.25
35W4	0.35	CBLL	0.90	ECC35	1.00	EP83	0.55
36Z3	0.70	CLB31	1.00	ECC40	0.65	EP85	0.35
35Z4G	0.35	CV31	0.35	ECC81	0.35	EP86	0.30
35Z6GT	0.60	DA796	0.45	ECC82	0.30	EP89	0.28
50A5	0.75	DF96	0.45	ECC83	0.30	EP91	0.33
50B5	0.50	DK96	0.50	ECC84	0.30	EP92	0.35
50C5	0.50	DK40	0.60	ECC85	0.40	EP95	0.35

EF97	0.65	GZ33	0.70	PL36	0.55	U281	0.40
EP98	0.65	GZ34	0.60	PL81	0.50	U282	0.40
EP183	0.30	HABCS00.45	0.45	PL82	0.45	U301	0.40
EP184	0.35	HK90	0.40	PL83	0.45	U403	0.60
EK90	0.30	K766	2.05	PL84	0.40	U404	0.60
EL34	0.50	KT88	2.00	PL302	0.85	U801	0.80
EL36	0.50	N78	1.50	PL504	0.80	UABC90	
EL37	1.60	PABC800.40	0.40	PL508	0.90	UABC90	0.40
EL41	0.60	PC86	0.60	PL509	1.10	UAF41	0.50
EL42	0.65	PC88	0.80	PL801	0.80	UAF42	0.55
EL81	0.55	PC97	0.50	PL802	0.95	UB41	0.60
EL83	0.42	PC900	0.48	PM84	0.60	UBC41	0.50
EL84	0.25	PABC800.40	0.40	PY31	0.30	UBC91	0.40
EL85	0.43	PC84	0.40	PY33	0.63	UBF80	0.40
EL86	0.40	PC85	0.40	PY80	0.40	UBF89	0.35
EL90	0.38	PC88	0.55	PY81	0.30	UBL1	0.60
EL95	0.85	PC89	0.55	PY82	0.85	UBL21	0.65
EL821	0.60	PC89	0.55	PY83	0.38	UC92	0.40
EL822	1.30	PC806	0.85	PY88	0.40	UC85	0.40
EL880	0.75	PC806	0.80	PY500	1.00	UCF90	0.55
EM34	1.00	PCF80	0.30	PY800	0.40	UCF91	0.60
EM35	0.35	PCF82	0.35	PY801	0.50	UCF92	0.70
EM80	0.45	PCF84	0.60	PZ30	0.85	UCF93	0.40
EM81	0.80	PCF86	0.60	QQV02-6	0.25	UCF94	0.60
EM84	0.35	PCF87	0.90	QQV03-10	2.25	UCF95	0.35
EM85	1.00	PCF801	0.50	QQV03-10	1.25	UCF96	0.60
EM87	0.70	PCF802	0.50	QQV03-20A	3.00	UF1	0.60
EM91	0.38	PCF803	0.50	QQV06-40A	5.50	UF42	0.60
EM91	0.60	PCF806	0.70	UF1	0.60	UF43	0.60
EM98	0.55	PCF808	0.85	UF43	0.60	UF44	0.60
EY81	0.40	PCF809	0.70	UF44	0.60	UF45	0.60
EY83	0.55	PCL81	0.50	UF45	0.60	UF80	0.35
EY86	0.40	PCL82	0.35	UF80	0.35	UF85	0.40
EY87	0.43	PCL83	0.65	TY22	3.20	UF89	0.40
EY88	0.43	PCL84	0.45	TY22-125	10.00	UL41	0.85
EZ40	0.50	PCL85	0.40	UL18/20	0.75	UL84	0.40
EZ41	0.50	PCL86	0.45	U25	0.80	UM84	0.55
EZ42	0.50	PCL88	0.90	U26	0.80	UY24	0.25
EZ80	0.27	PCL800	0.98	U31	0.60	UY11	1.00
EZ81	0.29	PCL801	0.75	U37	2.10	UY41	0.48
EZ82	0.30	PCL802	1.30	U32	0.35	UY92	0.50
EZ83	0.40	PF86	0.65	U76	0.35	UY85	0.40
EZ84	0.35	PF818	0.85	U78	0.35	W729	0.75
EZ85	0.35	PF1200	0.65	U91	0.75	Z759	2.00
EZ86	0.35	PL33	0.35	U91	0.35	Z803U	1.20

## TRANSISTORS

2N696	0.17	AC127	0.20	BD123	0.80
2N697	0.17	AC128	0.15	BD131	0.85
2N698	0.30	AC132	0.35	BD132	0.85
2N705	0.70	AC153	0.20	BF115	0.20
2N706	0.10	AC154	0.40	BF167	0.18
2N708	0.15	AC157	0.50	BF170	0.20
2N733	0.10	AC169	0.10	BF179	0.30
2N929	0.22	AC176	0.25	BF180	0.35
2N930	0.25	AC187	0.30	BF181	0.25
2N987	0.30	AC188	0.30	BF184	0.25
2N1131	0.25	ACY17	0.275	BF185	0.20
2N1132	0.25	ACY18	0.20	BF194	0.15
2N1184	1.50	ACY19	0.25	BF195	0.15
2N1301	0.40	ACY20	0.20	BF196	0.20
2N1302	0.75	ACY21	0.20	BF197	0.20
2N1304	0.25	ACY22	0.15	BF200	0.35
2N1305	0.25	AD140	0.50	BFW87	0.25
2N1306	0.25	AD148	0.50	BFW88	0.25
2N1307	0.30	AD161	0.35	BFW89	0.20
2N1308	0.25	AD162	0.35	BFW91	0.20
2N1309	0.30	ADZ11	1.25	BFX88	0.25
2N1613	0.22	ADZ12	1.25	BFY17	0.40
2N1711	0.25	AF114	0.20	BFY19	0.60
2N1756	0.75	AF115	0.20	BFY20	0.20
2N2147	0.75	AF116	0.20	BFY21	0.20
2N2160	0.65	AF117	0.20	BFY22	0.25
2N2217	0.30	AF118	0.45	BSY26	0.20
2N2218	0.30	AF125	0.25	BSY27	0.20
2N2219	0.35	AF127	0.20	BSY28	0.20
2N2369A	0.20	AF180	0.35	BSY55	0.20
2N2477	0.65	AF181	0.35	BSY95A	0.15
2N2646	0.80	AF186	0.40	OC16	0.50
2N2905	0.35	AF239	0.40	OC22	0.50
2N2923	0.15	AF271	0.45	OC23	0.60
2N2924	0.15	AS726	0.25	OC24	0.50
2N2926	0.155	AS727	0.30	OC25	0.35
2N3003	0.25	AS728	0.25	OC26	0.25
2N3054	0.60	AS729	0.30	OC28	0.60
2N3055	0.75	AS754	0.25	OC29	0.60
2N3133	0.30	ASZ15	0.70	OC30	0.75
2N3134	0.30	ASZ16	0.70	OC35	0.60
2N3381	0.20	ASZ17	0.75	OC36	0.60
2N3392	0.15	ASZ18	0.75	OC42	0.20
2N3393	0.15	ASZ20	0.25	OC44</	

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn.

If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecomms.**  
C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

**Constructional**  
A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**  
Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B2, Aldermaston Court, Reading RG7 4PF.

## POST THIS COUPON TODAY

To: B.I.E.T., Dept B2, Aldermaston Court, Reading RG7 4PF.  
Please send me book and details of your Courses in

Name \_\_\_\_\_  
BLOCK CAPITALS PLEASE  
Address \_\_\_\_\_

OCCUPATION \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by C.A.C.C.

(Write if you prefer not to cut this page)



**B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE**

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage); For one year to any part of the world £2-6s.  
PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.


# HENRY'S RADIO LIMITED

## ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · ELECTRONIC COMPONENTS · TEST · P.A. · DISCOTHEQUE · LIGHTING · MAIL ORDER

### 10th EDITION CATALOGUE

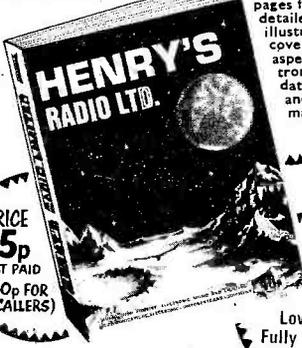

**350** pages fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

**10,000** Stock lines at Special Low Prices and Fully Guaranteed

**PRICE 55p** POST PAID (40p FOR CALLERS)

### PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. PW), 3 Albemarle Way, London, E.C.1—for catalogue by post only.

All other mail and callers to "303", see below  
**A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!**

### HOME EQUIPMENT



AF105 50k/V multimeter (illus.). Price £8.50, p.p. 20p. Leather case £1.42. 200H. 20k/V.  
 Price £3.87, p.p. 20p. Case 62p.  
 500 30k/V multimeter. Price £8.87, p.p. 20p. Leather case £1.50. TML33 2k/V.  
 Price £4.12, p.p. 15p. Leather case £1.15.  
 TE65 Valve voltmeter. Price £17.50, p.p. 40p.  
 SE250B Pocket pencil signal injector. Price £1.75, p.p. 15p.

SE500 Pocket pencil signal tracer. Price £1.50, p.p. 15p.  
 TE20D RF generator. Price £15, p.p. 40p.  
 TE22D Matching audio generator. Price £17, p.p. 40p.  
 TE15 Grid dip meter. Price £12.50, p.p. 40p.  
 TO3 Scope 3 in. tube. Price £37.50, p.p. 50p.  
 TE22 Audio Generator. Price £17, p.p. 40p.  
 CI-5 Pulse Scope. £39.00, p.p. 50p.  
 U4341 AC/DC Multitester and transistor tester. AC & DC Current. In steel case. Price £10.50, p.p. 15p.  
 TMK 500 30k/V Multitester. Price £8.87, p.p. 15p. Leather case £1.98.

**LARGEST RANGE of Panel Meters, Edge Meters and Test Equipment of every sort. Full details in latest catalogue—see above.**

### LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/4" x 8 1/4". Large Ceramic Magnet.  
**TYPE 150** 6 watt. 3, 8 or 15 ohms £2.20. Post 22p.  
**TYPE 150TC** Twin cone version £2.75. Post 22p.  
**TYPE 450** 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.85. Post 25p.  
**TYPE 350** 20 watt with tweeter and crossover. 8 and 15 ohms. £7.70. Post 28p.


**POLISHED CABINETS** For 150, 150TC and 450 £4.60. Post 30p.

**SPEAKER KITS**

WHARFEDALE 4-8 ohms. PEERLESS 8 ohm Systems.  
 Unit 3. 8" 15W £10.20. 20-2 8" 30W £11.25.  
 Unit 4. 12" 25W £13.50. 20-3 8" 40W £16.75.  
 Unit 5. 12" 35W. £19.50. 4-30/12 12" 40W £22.75.  
 GOODMAN'S DIN 20 KIT 20W 4ohm £10.75  
 Carriage etc. 50p each or 75p per pair for Kits.

**STEREO HEADPHONES**  
 With stereo jack. Post 15p.  
 Dulci SH650D £2.25  
 Rotel RH600 £4.67  
 Akai A5E95 £5.50  
 Eagle SE30 £5.97  
 Koss K711 £7.97  
 Pioneer SE30 £9.45  
 Koss PRO4A £15.50

### HI-FI TO SUIT EVERY POCKET

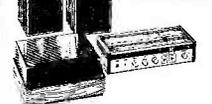

**SAVE 40% ON LIST UP TO 70c PRICES PLUS FREE 'BIB' Groov-Kleen Record Cleaner Value £1.99**

ROTA 1500. 5 + 5 watts. Garrard 2025TC with 9TAHC diamond ceramic. Plinth/Cover. Type 60 Compact Speakers. Size 16 x 9 1/2 x 6 1/4" SAVE £44.90 Carr. £29

TELETON '206' Garrard SP25 Mk. III. Goldring G800 Series Cart., Plinth/Cover. New 15 watt Quality SDLI Bookshelf Speaker Systems, all leads etc. SAVE £54.95 Carr. £29

TELETON F2000, Med. Wave, Stereo FM Tuner Amplifier, Garrard 2025TC, 9TAHC Diam., Plinth/Cover. Type 60 Speaker Systems as above, all leads, etc. SAVE £56.95 Carr. £36

or with 2 x SA125 Speakers £49.50 Carr. £22

ROTA 2200 10 + 10 Watt. Garrard SP25 III/G800H. Plinth/Cover. New 15 watt SDLI2 Twin Speaker Systems, all leads, etc. SAVE £65.50 Carr. £32

**LOW PRICES PLUS 12 MONTHS GUARANTEE & DEMONSTRATIONS FREE**

**LATEST SPECIAL PRICE STOCK LIST & STEREO SYSTEMS Ref. 16/17**

**FREE BROCHURES**  
 \* P.A., DISCO and LIGHTING No. 18  
 \* TRANSISTORS, I.C.'s No. 36

**20 WATT I.C. AMPLIFIER**  
 Toshiba 20 watt Power Amplifier, £4.57.  
 Toshiba Pre-Amplifier I.C., £1.50.  
 Data and suggested circuits No. 42. 10p.  
 SL403D 3 watt I.C. with 8 page data and circuits £1.50.  
 IC12 6 watt I.C. £2.50.

**TEXAS PRE-AMPLIFIERS & 1-100W AMPLIFIERS**  
 Circuits, layouts and data £1.25 post paid.

**NIXIE TUBES** (post 15p per order)  
 XN3 or XN13 0-9 side view with data sheet. 85p each.  
 GN4 end view 0-9 with socket and data. £1.75. All I.C.'s for Digital Clocks in stock. HENRY'S CLOCK CIRCUIT No. 29/2 15p.

**BUILD THIS VHF FM TUNER**  
 5 MULLARD TRANSISTORS 300 kc/s BAND-WIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO.  
 A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.  
**TOTAL £6.97**, p.p. 20p. Cabinet 100p. Decoder Kit £5.97.  
 Tuning meter £1.75.  
 Mains unit (optional) Model PS900 £2.47.  
 Mains unit for Tuner and Decoder PS1200 £2.62.



**HIGH QUALITY SILICON AMPLIFIER AND PRE-AMPLIFIERS**

Self powered Silicon—FET Pre Amplifier. Push button selectors, tape record/play, adjustable levels, drive up to 4 x PA25 or 2 x PA50  
 FET 9/4 Mono or single channel. All facilities plus microphone. Mixing.

**SPECIAL OFFER £10.50**

**SILICON POWER AMPLIFIERS RMS OUTPUT**  
 PA 25 25 watts into 8 ohms £7.50.  
 PA 50 50 watts into 4 ohms £9.50.  
 MU442 Power Supply for 1 or 2 PA25's or 1 only PA50, £6.00. p.p. 20p.  
**FREE BROCHURE No. 25 ON REQUEST. NO SOLDERING—ALL UNITS INTERCONNECTING. ON DEMONSTRATION AT "356".**

### TERRIFIC SAVINGS!

**GARRARD - BSR - THORENS GOLDRING PIONEER CONNOISSEUR**

CHASSIS (P)	ASSEMBLED (P)	ASSEMBLED
(less cartridge) (with cover)	MP60(TDIP) £17.75	2025TC/9TAHCD
*SP25 Mk III £11.30	HT70 PC £23.50	SP25/3-G800H £14.95
*AF76 £20.50	PL12AC £36.50	AP76-G800 £19.95
*MP60 £11.30	GL72 PC £30.95	AP76-G800 £29.95
*MP610 £15.15	GL75 PC £43.75	HT70PC/G800 £29.95
*HT70 £16.60	TD150AB/CL75 £38.97	
GL72 £28.50	TXII £45.50	
CL75 £38.97	BD2/SAUZ £33.50	
Dual 1215 £39.00		

**CHASSIS WITH CARTRIDGE (P) SPECIAL PRICE WITH CARTRIDGE—ADD**

*2025TC/9TAHCD £9.50	All magnetic—Recom-
*3000/9TAHCD £9.98	mended Y940 (=AD-
TEAK *P11T1 Std. £3.25	76K) £3.25; AT66 £4.95;
PLINTH *BN1 Deluxe £8.30	G850 £4.25; AT21 £9.60;
WITH *P4/T4 Std. £4.75	G800 £7.45 G800H £6.55;
COVER *BN4 Deluxe £8.30	M44.7 or C £7.45
(State *P6/T6 Std. £3.25	
deck) *BSR Deluxe £6.25	

Post etc.:—Chassis 50p, with plinth/cover 70p, Plinth/Cover 30p Carts. 15p.

**300mW TRANSISTOR AMPLIFIER MODEL 4-300**  
 Fully assembled 4TR Amplifier. Size 5 1/2 x 1 1/2 x 3 in. 1-10mV adjustable sensitivity. Output 3-8 ohms. Fitted Vol. control. 9 volt operated. Thousands of uses plus low cost.  
 Price £1.75, p.p. 15p (or 2 for £3.25, p.p. 15p).

**SINCLAIR PROJECT 60 PACKAGE DEALS —SAVE POUNDS!**

2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply £16.75. Carr. 40p. Or with PZ6 power supply £18.25. Carr. 40p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply £20.25. Carr. 40p. Transformer for PZ8 £2.45 extra. NEW! Project '60's stereo system £20.97. Any of the above with Active Filter unit add £4.75 or with pair Q16 speakers add £16. Also new FM Tuner £20.25. 2000 Amplifier £23.75, p.p. 50p. 3000 Amplifier £31.50. Also IC12 £2.50.

**"BANDSPREAD" PORTABLE TO BUILD**

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandsread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.  
**TOTAL COST TO BUILD £7.98**, p.p. 32p (Battery 22p). All parts sold separately—Leaflet No. 2.  
**77" PORTABLE** (as previously advertised) £6.98, p.p. 35p from stock—Leaflet No. 1.

**MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S** \* Components in stock for most published designs—send large S.A.E. with list for parts quote for your circuit.

<b>Electronic Components, Audio and Test Gear Centre</b> 356 EDGWARE ROAD, LONDON, W.2. Tel: 01-402 4736	<b>High Fidelity Sales &amp; Demonstrations Centre</b> 354 EDGWARE ROAD, LONDON, W.2. Tel: 01-402 5854	<b>P.A., Disco &amp; Lighting Centre</b> 309 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 6963	<b>Mail Orders, Special Bargain Shop, Industrial Sales</b> 303 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 1008/9
--	--	--	--

**"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY**