

M. Semmell

PRACTICAL WIRELESS

AUGUST 1973

20p

*IF 8
SWR
JES
76*

PW
'Student'
OSCILLOSCOPE



also:
**MINI-COMM
RECEIVER**

**VHF BAND
LOCATOR**

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

BUILD THE TEXAN

★ FREE TEAK CABINET with complete kits

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, seratch and rumble filters, mono/stereo switch, Input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).
Constructional details Ref. No. 21 30p

SPECIAL KIT PRICE **£28-50**

P & P 45p COMPLETE WITH FREE TEAK CABINET
Designer approved kits distributed by Henry's!

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



★ SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14 1/2" x 6" x 2" high

ELECTRONIC KITS
Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

IC RECEIVER
ZN414 Radio integrated circuit as featured in Practical Wireless, January 1973. Article Reprint Ref. No. 19 10p. Price £1-20.

BATTERY TAPE DECK
Garrard 9 volt Tape Deck with heads, etc. As previously advertised. Limited quantity. £9-50, post 30p.

LEARN A LANGUAGE
Recorded Cassettes with step by step phrase books. French, German, Spanish Italian. £1-36 per course. £5-00 per set of four.

DISCO SPOTBANK
3 channel Disco Spotbank for use with any psychedelic lighting display. £12-75, p. & p. 35p.

HI-FI EQUIPMENT
Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES. FREE detailed brochure (Ref. No. 17). You can see the savings!

HIGH QUALITY CASSETTES
The best UK low noise tapes but at a special price. 'Living Sound' cassettes meet the highest international standard (IEC 94A). Fantastic price savings.

	3 for	6 for	10 for
C60	1-00	1-80	2-80
C90	1-33	2-57	4-20
C120	1-62	3-15	5-00

Full guarantee. Post paid.
Made by EMI especially for Henry's.

ULTRASONIC TRANSDUCERS
Operate at 40kc/s up to 100 Ydrts. Ideal remote switching and signalling. Complete with data and new I.C. circuits. £5-90 per pair. Post 10p.

MARRIOT TAPE HEADS
4 TRACK MONO or 2 TRACK STEREO
'17' High Impedance £2-00
'18' Med. Impedance £2-00
'36' Med-Low Imp. £3-50
Erase Heads for above 75p
'63' 2 track mono—£1-75
Hi Imp. £1-75
'43' Erase Head for above 75p

7 SEG & NIXIE TUBES
(Post 15p per 1 to 6)
XN3, XN13, GN6 0-9 side view with data, 85p.
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
3015F 7 seg £2 each. £7 per 4 with data.
12 and 24 hour clock circuits Ref. No. 31 15p.

Miniature Amplifier
5 transistor, 300mV o/p. Fitted volume and sensitivity control, 9 volt operated. £1-75 each PIP 15p.

Quality Slider Controls
60mm stroke, singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K, 1 meg, Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged, 60p each.

P.W. Tricolour as per April/May June 1973. Parts list on request (52A).

TEST EQUIPMENT

- Just a selection!
- SE250B Pocket Pencil Signal Injector £1-90
 - SE500 Pocket Pencil Signal Tracer £1-50
 - THL33D Robust 2K/Volt £4-55 with case £4-95
 - TE15 Grid Dip Meter 440 KHz-280 mHz £13-45
 - 500 30 K/V Multimeter £9-25
 - With leather case £10-50
 - 200H 20K/V Multimeter £4-20. With case £4-95
 - AF105 50K/V Multimeter £8-50. With case £9-50
 - U4341 AC/DC Multimeter with transistor tester with steel case £10-50
 - TE20D RF Generator 120KHz-500MHz £16-50. Carr. 35p
 - TE22D Audio Generator 20Hz-200KHz £17-50. Carr. 35p
 - CI-5 3" Pulse Scope 10Hz-10mHz £39-00. Carr. 50p
 - TE65 Valve Voltmeter 28 ranges £17-50. Carr. 40p
- ALL NONBREM MODELS IN STOCK



LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2-20. Post 22p.
TYPE 150 TC Twin cone version £2-75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3-50. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7-50. Post 28p.



POLISHED CABINETS 150, 150TC 450 £4-60. Post 30p. ASSEMBLED IN POLISHED CABINETS (8 ohms) SERIES 6 (Assembled 150 TC) per pair £16-50. Post 70p SERIES 8 (Assembled 450) per pair £18-95. Post 70p

ML-3 MW/LW TUNER to BUILD



Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4-85. Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave Bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 MV push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7-98 p.p. 32p. (Battery 22p).

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed. Post PRICE 55p Paid (40p FOR CALLERS)

PLUS! FIVE 10p VOUCHERS

Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to "303" see below.

PA-Disco-Lighting

- UK's Largest Range—Write phone or call in. Details and demonstrations on request.
- DJ30L 3 Channel sound to light unit, 3KW, £29-50
 - DJ40L 3 channel Mic (built-in) to light, 3KW, £38-75
 - DJ70S 70 watt Disco amp/mixer, £49-75
 - DISCOAMP 100 watt amp/mixer, £68-85
 - DJ105S 30 watt Disco amp/mixer, £32-25
 - Anti-Feedback Quality Mic., £11-50
 - D1500 50 watt PA Amplifier £43-95
 - DJ700 70 watt £52-75
 - DJ1000 100 watt £63-00
 - GROUP 300 150 watt rms "Group" Valve Amplifier £86-00
- FIBRE OPTICS LIGHTING. — MIC'S. EFFECTS. PROJECTORS. SPOTS. DIMMERS — STANDS. MIXERS. SPEAKERS. Everything for PA — Disco — Lighting.
FREE Stock List Ref. No. 18
- PORTABLE DISCOS — DETAILS ON REQUEST
 - CREDIT TERMS FOR CALLERS



BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.
TOTAL £6-97, p.p. 20p. Mk. 1 Decoder Kit £5-97.
Built IC Decoder £6-50. Tuning meter unit £1-75.
Mains unit for Tuner and/or Decoder PS6/12 £3-25. Post 20p



SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!


Z30 £3-57; Z50 £4-37
STEREO 60 PZ5 £3-97 £7-97; PZ8 £4-77
PZ6 £6-37;



Transformer for PZ8 £2-95
Active Filter Unit £4-45
Stereo FM Tuner £16-95
IC12 £1-80; Q16 £1-18 pr.
Post etc. 20p per item

PACKAGE DEALS

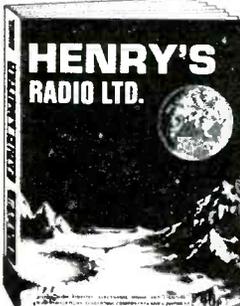Post 25p
2xZ30, Stereo 60, PZ5 £15-95
2xZ30, Stereo 60, PZ6 £18-00
2xZ50, Stereo 60, PZ8 £20-25
Transformer for PZ8 £2-95
PROJECT 60S KIT £19-95



VAT

All prices are exclusive of 10% VAT which must be added to all orders inc. carr/packing. (Note: Catalogue is not subject to VAT).

See earlier page of this magazine for transistors, I.C.'s and Semi Conductor prices—latest list Ref. no. 36 on request. E. & O.E.

Henry's RADIO LIMITED
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open: 9 am-6 pm
6 days a week
(309 closed Thursday)
All stores open all day Saturday

PRACTICAL WIRELESS

VOL. 49 NO. 4

ISSUE 798

AUGUST 1973

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Morris A. Colwell

ASSISTANT EDITOR

Lionel E. Howes, G3AYA

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Eric Dowdeswell, G4AR

PRODUCTION & NEWS EDITOR

Colin R. Riches

SECRETARIAL

Jenny Maunder
Jill Alflett

Telephone 01-634 4292

ADVT. MANAGER

Roy Smith

Telephone 01-634 4293

CLASSIFIED ADVTs.

Colin R. Brown

Telephone 01-634 4301

SUBSCRIPTIONS

Subscription Rates for one year to any part of the world £2.65 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477 Binders (£1.10) and Indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

● NEWS & COMMENT

- 312 THE SMALL PRINT—Leader article and September preview
- 313 NEWS . . . NEWS . . . NEWS
- 320 BOOK REVIEWS—New books reviewed
- 322 TELEVISION—This month's attractions
- 329 HOTLINES on recent developments—*Ginsberg*
- 330 Looking at the London ELECTRONIC COMPONENTS SHOW—a visit to Olympia
- 335 NEXT MONTH in *Practical Wireless*
- 342 ON THE AIR—Reports on Broadcast Bands
- 342 Short Wave—*Malcolm Connah*
- 345 Medium Wave—*Charles Molloy*
- 345 VHF/FM—*Simon David*
- 346 Amateur Bands, Short Wave/VHF—*David Gibson G3JDG*
- 366 PRODUCTION LINES—Products reviewed by *Colin Riches*

● CONSTRUCTIONAL

- 314 MINI COMM RECEIVER—*F. G. Rayer*
- 325 LOW POWER CLASS A AMPLIFIER—*R. A. Pen*
- 326 CASSETTE RECORDER IN THE CAR—*M. Vlietstra*
- 333 LIGHT OPERATED SWITCHES and alarms—*R. Penfold*
- 336 P.W. 'STUDENT' OSCILLOSCOPE, Part 1—*G. A. Cozens*
- 356 VHF BAND LOCATOR for 2 metres—*A. Sydenham*
- 357 TAKE 20 No. 51 Touch Sensitive Switch—*David Andrews*

● OTHER FEATURES

- 321 I.C. OF THE MONTH, LP1000 Stored Energy Regulator—*L. A. J. Ireland*
- 349 CALIBRATING SHORT WAVE RECEIVERS—*M. Connah*
- 353 GOING BACK Equipment of yesteryear—*Colin Riches and Arthur Dow*
- 361 MAGNETIC AMPLIFIERS, Part 2—*I. R. Sinclair*

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Telephone: 01-634 4444.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

PACKAGE PRICE R.S.C. STEREO PACKAGE OFFERS

FOR ILLUSTRATED UNITS

ONLY £39-99

Carr. £1-00
Or deposit £8-95
and 9 monthly
payments £4-22
(Total £44-98).




R.S.C. A55
LOUDSPEAKERS



GARRARD 2025

LINEAR 505 AMP

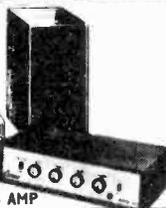

SAVE £30 approx.

MONARCH
SPEAKERS

GOLDRING
GL72



HIGH FIDELITY UNITS

PACKAGE PRICE **£108-25** Carr. £1-75

FOR ILLUSTRATED UNITS

Or deposit £15-00 and 12 monthly payments £8-78 (Total £120-36)
GOLDRING GL72 Transcription Turntable + P.L.I.
GOLDRING G800 Magnetic Cartridge
DE-LUXE PLINTH with Roll-over Cover
Pair R.S.C. MONARCH II LOUDSPEAKERS
R.S.C. SUPER 30 Mk III AMPLIFIER
Total value of individual items listed above £138-14.

Individual Rec. Retail Prices:
LINEAR 505 5 + 5 Watt Amplifier £18-25
GARRARD 2025 Autochanger + KR80A Cartridge £13-44
Teak Veneer Plinth with Transparent Plastic Cover £5-80
Pair A55 LOUDSPEAKERS (Inc 8" x 5" 10,000 Gauss) £10-82
TOTAL £49-41

SEND S.A.E. FOR
FREE COLOUR
BROCHURE

FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams, Frequency **£9-96** post free
Response 25 Hz-20 kHz.
Impedance 8-15 ohms.
Or Dep. £2 & 9 monthly payments £1-07 (Tot. £11-63)

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. **COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT** and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS **£12-65** Carr. 40p
OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £18-50 or dep. £2 and 9 monthly payments £1-88 (Total £18-92).

AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticized cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.
Exceptional performance at low cost.

HF808T	8" 10W	£2-98	HF120D	12" 15W	£5-50
HF102D	10" 10W	£3-30	HF128	12" 15W	£6-25
HF120	12" 15W	£4-98	HF128D	12" 15W	£6-85

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality. In suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω.
PLEASE STATE IMPEDANCE WHEN ORDERING
MODEL 803T 8" 15w. with parasitic Tweeter. **£3-70**
Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15. **£4-95**

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BM1. An all-dry battery eliminator. Size 5½ x 4½ x 2½ in. approx. Completely replaces batteries supplying 1-5v and 90v, to battery radio where A.C. mains 200/250v. 50c/s is available. **ASSEMBLED READY FOR USE £4-15**

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Screened and Interleaved where necessary. Primarys 200-250v. 50c/s. Screened

MIDGET CLAMPED TYPE 2½ x 2½ x 2½ in.	TOP SHROUDED DROP-THRO' TYPE
250v-60mA, 6-3v. 2a. £1-10	250-0-250v. 70mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-45
250-0-250v., 60mA 6-3v. 2a. £1-16	250-0-250v. 100mA, 6-3v. 3.5a. £1-71
FULLY SHROUDED UPRIGHT MOUNTING	250-0-250v. 100mA, 6-3v. 2a., 6-3v. 1a. £1-75
250-0-250v. 60mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-55	350-0-350v. 80mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-81
250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45	250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45	300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45
300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a. £2-95	300-0-300v. 130mA, 6-3v. 4a., c.t., 6-3v. 1a. £2-85
For Mullard 610 Amplifier £2-95	Suitable for Mullard 510 Amplifier. £2-85
350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-95	350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-85
350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-95	FLAMES or TRANSISTOR POWER PACK
425-0-425v. 200mA, 6-3v. 4a., c.t., 5v. 3a. £5-45	Type 6-3v. 1.5a. 55p; 6-3v. 2a. 60p; 6-3v. 3a. 85p;
425-0-425v. 200mA, 6-3v. 4a., 6-3v. 3a., 5v. 3a. £5-80	6-3v. 6a. £1-45; 12v. 1a. 81p; 12v. 3a. or 24v. 1.5a £1-50; 0-9-18v 1½a £1-25; 0-12-25-42v 2a £1-95.
450-0-450v. 250mA, 6-3v. 4a., c.t., 5v. 3a. £6-00	

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
Only high grade components by leading manufacturers

- Push Button Selector Switching
- Jack Socket for Headphones
- Neon Indicator
- Satin Silver Finish Metal Fascia
- Solid State Circuitry
- Twenty Silicon Transistors
- Four Diodes, Four Rectifiers

Send S.A.E. for full descriptive leaflet.

R.S.C. STEREO FM III TUNER. in cabinet
Visually matches Super 30 Mk. III **£37-50**

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8 Ω. Frequency Response 7 Hz to 70 KHz ± 1½ db.

COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £5 extra.

FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £4-54 (Total £47-86). **£27-50**
£42-50

SPIOI HIGH FIDELITY PLAYER UNIT

Comprising Goldring G101 hi-fi single player unit fitted high fidelity free field magnetic stereo cartridge with diamond stylus. Belt driven Attractive design super-slim plinth and 'roll-over' transparent tinted plastic cover. Or Deposit £4-95 and 9 Monthly Payments of £3-75 (Total £38-70) Excellent value. **£34-95** Post paid

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.

DORCHESTER (Illustrated) Size 16 x 11 x 9 in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High Flux 13 x 8 in. **£9-45** Carr. 40p.
Dual Cone speaker. Imp. 3 or 15 ohms.

MONARCH Size 19 x 10½ x 9 in. appr. Rating 10 watts. Inc. 13 x 8 in. speaker with highly flexible P.V.C. cone surround, long throw voice coil and 10,000 line magnet. High flux pressure tweeter. Handsome design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. See 'package offers' for illustration. Carr. 60p **£19-35**

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.

JEB Size 16" x 11" x 9". SE8 For optimum performance with any 8in. Hi-Fi speaker. **£6-50**
Size 19 x 10½ x 9 in.

SE10 For outstanding results with 10in. Hi-Fi speaker. Size 25½ x 16 x 9 in. P'td. **£6-75**

SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter. Size 25½ x 16 x 9 in. **£7-95**

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£6-50** Carr. 33p
OR SENIOR 15 WATT INCLUDING **£7-65** Carr. 39p
HF126 15,000 LINE SPEAKER

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. ±2db. Harmonic Distortion 0-3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm speakers. Max. sensitivity 6mV Output rating I.H.F.M. Fully enclosed enamelled case, 9½ x 2½ x 5½ in. Attractive brushed silver finish fascia plate 10½ x 3½ in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£8-50** Carr. 40p.
OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£12-05**

SELENIUM RECTIFIERS P.W. (Bridge) All 6½/2v. D.C. Output. Max. A.C. input 18v. 1a, 28p. 2a, 38p. 3a, 65p. 4a, 72p. 6a, 88p.


SMOOTHING CHOKES 150mA, 7-10H, 250 Ω 77p; 100mA, 10H, 20 Ω 66p; 80mA, 10H, 350 Ω 55p; 60mA, 10H, 400 Ω 28p.

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10 in. approx. **COMPLETE KIT £25-25**
★ Response 30-20,000 c.p.s. Impedance 15 ohms
★ Performance comparable with units costing considerably more Carr. 65p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5 in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-64 (Total £28-36).

RSC GROUP/DISCO UNITS

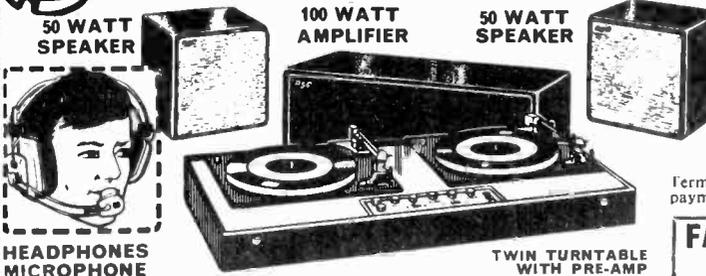

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C132 30-40 WATTS Fitted two exceptional efficient, low feedback havel characteristic high flux 13" x 8" 90 watt £21-95
 12thly payments £2-42 (Total £24-78) Carr. 65p

TYPE C313 50 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 64" x 14" x 11" Dep. £5 & 9 monthly pmts £3-54 (Total £36-86) Carr. 85p £32-72

TYPE C4100 100 WATTS Inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 88" x 16" x 10" Acoustically diled and pressurised. Termis: Dep. £11 and 12 nthly. pmts. £5-80 (Total £80-60). Carr. £1-50



R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level—70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86 EF88, 6CX8, EL34, EL84, 6Z84. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, Singing Bass, etc. Gram, Pick-up etc. for mixing purposes. 200-250V. 50 c/s A.C. mains. For 8 and 15 ohm speakers. Twin-handled perforated cover £20-10. 18 MONTHS' GUARANTEE. Carr. 72p
TERMS: Deposit £4 and 9 monthly payments of £2-27 (Total £24-48). Send S.A.E. for leaflet. £21-76

F.A.L. DISCO PRE-AMPLIFIER £18-97

Designed for use with a pair of Player Units and Amplifier with Bass and Treble Controls. Incorporates MONITORING FACILITIES and Mic. input. The 4 inputs are ind. controlled. Detector switch Gram (1), (2), and Tape. For operation on 200-250V A.C. Mains 50Hz. Size approx 16 1/2" x 3" x 4" deep. Brush Silver finished fascia. Fully enclosed but can be mounted in cabinet.

FANE "CRESCENDO" SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for speakers 8 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250V. A.C. mains. Output 50 watts music rating. Or deposit £7-95 & 9 monthly payments £2-98. Total £48-98. £37-95 Carr. 62p.



RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.

For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished. In black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Termis: Deposit £8-95 and 12 monthly payments £4-59 (Total £87-63). Carr. Free S.A.E. for leaflet. UK Mainland **ONLY £59-95**

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.
 * Two extra heavy duty 12in. 50w Loudspeakers.
 * Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet.
 Credit Termis: Deposit £15 & 9 monthly payments of £7-22. (Total £79-98.) Carr. £2 **£71-50**



RSC GP30 HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group

A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valve. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250V. A.C. mains. For 8 or 15 ohm speakers. Send S.A.E. for leaflet. Termis: Deposit £4-40 and 9 monthly payments of £2-85 (Total £49-15). £25-85 Carr. 72p

PACKAGE OFFER

- Units listed below
 (a) 100w POWER AMPLIFIER
 (b) PAIR OF HI-FI HEAD- PHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
 (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets. Size approx. 18" x 18" x 8"
 (e) RSC TDI DISCO CONSOLE
 (a) (b) (c) (d) & (e) Carr. £2-50 **£145**

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 Mk.III turntables and Sonotone or Acos Cartridges with diamond stylil. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mikes' with vol. control switch. Black Vynide covered Cabinet with lid. see illustration on left
 Or Dep. £10 and 9 nthly pmts £8-80 (Total £71-20) Carr. £1-50 **£63-26**

Terms Deposit £30 and 18 monthly payments of £8-00 (Total £174-00).

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
8" 100Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
£25-95	£14-75	£11-99
Dep. £2 and 9 nthly payments £2-49 (Total £28-41)	Dep. £3-80 and 9 monthly payments £1-50 (Total £16-80)	Dep. £2 and 9 monthly payments £1-33 (Total £13-97)

PAIR SUITABLE ALL PURPOSES
FOR BASS GUITAR, ELECT. ORGAN, ETC.

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£7-95** Or Dep. £1-25 and 9 nthly payments 89p (Total £20-26).

DISCO PACKAGE OFFER £45

Pair BSR MP60 T/tables GP91 PU Cartridges. FAL Disco Pre-amp. Total Rec. Ret. Price £50-11 Carr. £1

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.III AMPLIFIER	£87-95	PACKAGE PRICE	
PR. FANE POP 25/2 95W L/SPEAKERS	£15-90		
Termis: Deposit £7-50 and 9 monthly payments of £8-85 (Total £86-74)	£68-85	£49-50	£1-10 Carr.
F.A.L. PHASE 60 MK.III AMPLIFIER	£87-95	PACKAGE PRICE	
PR. FANE POP 50 L/SPEAKERS	£88-98		
Termis: Deposit £10 and 9 monthly payments of £8-07 (Total £94-65)	£101-98	£57-50	£1-10 Carr.
F.A.L. PHASE 90 MK.III AMPLIFIER	£87-95	PACKAGE PRICE	
PAIR L12/20 95W L/S in cabinet	£88-80		
Termis: Deposit £10 and 9 monthly payments of £8-58 (Total £98-65)	£94-95	£61	£1-35 Carr.
F.A.L. PHASE 100/5 AMPLIFIER	£89-85	PACKAGE PRICE	
4 FANE POP 60 L/SPEAKERS	£47-95		
Termis: Deposit £20 and 12 monthly payments of £8-58 (Total £128-58)	£117-81	£110	£2 Carr.

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH
L125 50 WATT Fitted pair of 12" 30 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50
 Or deposit £4-50 and 9 monthly pmts. of £4-97. Total £48-98
L12/20 12" 20-25 WATT 13,000 lines 15 ohms
 Dep. £2-80 & 9 nthly pmts. £1-48 (Total £16-28) Carr. 55p. **£13-15**
L12/10 10-15 Watt veneer finish cabinet 12" unit 8-15 ohm. Size approx. 14" x 14" x 9". Carr. 50p **£8-25**

CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

NOW FIVE NEW BRANCHES
BOLTON 23 DEANS GATE
NOTTINGHAM 19/19A MARKET STREET
SUNDERLAND 5 MARKET SQUARE
STOCKPORT 8 LITTLE UNDERBANK
COVENTRY 17 SHELTON SQUARE
NEW LARGER PREMISES AT HULL, DARLINGTON & NEWCASTLE See Addresses



HI-FI CENTRES LTD.
MAIL ORDERS & EXPORT ENQUIRIES TO:—
AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: Pudsey (09788) 77831.
TERMS C.W.O. or C.O.D. No C.O.D. under £1.
POSTAGE 88p EXTRA UNDER £8. 88p EXTRA OVER £8 OR AS QUOTED. TRADE SUPPLIED.
S.A.E. PLEASE WITH ENQUIRIES.
SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.
MAIL ORDERS MUST NOT BE SENT TO SHOPS

R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

- BRADFORD** 10 North Parade (Closed Wed.). Tel. 28349
- BOLTON** 23 Deansgate Tel: 33512. Opens Mid-July
- BIRMINGHAM** 30/31 Great Western Arcade. Tel. 28282
- COVENTRY** 17 Shelton Square, The Precinct. Tel. 021-236 1279 (Closed Wed.).
- DERBY** 28 Oameston Rd., The Spot (Closed Wed.). Tel. 41361
- DARLINGTON** 19 Northgate (Closed Wed) Tel 85043
- EDINBURGH** 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
- GLASGOW** 326 Argyle St. (Closed Tues.). Tel. 248 4158
- HULL** 7 Whitefriargate Tel. 20805
- LEICESTER** 32 High Street (Closed Thurs.). Tel. 56420
- LEEDS** 5-7 County (Mecca) Arcade, Bridge. Tel. 238 2778
- LIVERPOOL** 73 Dale St. (Closed Wed.). Tel. 236 3873
- LONDON** 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629
- MANCHESTER** 60A Oldham Street, (Closed Wed.). Tel. 238 2778
- MIDDLESBROUGH** 106 Newport Rd. (Closed Wed.). Tel. 47086
- NEWCASTLE UPON TYNE** 24 Newgate Shopping Centre (Closed Wed.). Tel. 21486
- NOTTINGHAM** 19/19A Market Street (Closed Thurs.). Tel: 48088
- SHEFFIELD** 13 Exchange Street (Castle Market Bldg.) (Closed Thurs.). Tel. 20716
- STOCKPORT** 8 Little Underbank. Tel: 480-0777.
- SUNDERLAND** 8 Market Sq. (Closed Wed.) Tel. 70573

Antex X25



て使用時に於
の内部は高質
材料を使用する
用になる事

・I/Cの使用
頻度が高く
との点
なる程、

ない半田ゴテ
層重要な
来ており、殆
事です。ん
テンレス鋼

The Japanese have a Yen for it.

*in case you are not familiar
with Japanese:*

Our distributors in Japan are telling
their customers about the importance
(when soldering I.C.'s and transistors)
of the low leakage of our Model X.25
soldering irons.

- Model X.25** - 25 watt sells at £1.75 + P & P 8p VAT 18p
- Model G** - 18 watt £1.95 + P & P 5p V.A.T. 20p
- Model CCN** - 15 watt miniature iron £1.95 + P & P 5p VAT 20p

Ask your usual wholesaler or retailer for Antex irons or
if you have any difficulty, send the coupon to us direct.



From radio or electrical dealers,
car accessory shops or in case of
difficulty direct from:
ANTEX LTD. FREEPOST
PLYMOUTH PL1 1BR
(no stamp required) Tel 0752 67377.

Please send the following:

Please send the ANTEX colour catalogue.

I enclose cheque/P.O./Cash (Giro No. 258 1000)

NAME

ADDRESS

PW 8

Reg. No. 393594

Another!
winner!

fane **MODE ONE**

**HIGH FIDELITY
LOUDSPEAKER KIT**



Recommended
retail price

£9-96

including V.A.T.

Please
send S.A.E
for fully
descriptive
leaflet.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

SPECIFICATION OF UNITS

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	3"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	10kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. **SIZE** 15½" x 10½" x 9".

*When used with above cabinet.

Distributors to the wholesale
and retail trade

LINEAR PRODUCTS LTD.

Electron Works, Armley, Leeds
LS12 3SA Tel. 630126

Manufactured by

FANE ACOUSTICS LTD.

Hick Lane, Batley, Yorkshire
Tel Batley 6431

**CAPACITOR
DISCHARGE
IGNITION KIT**



A comprehensive kit of parts with detailed constructional details, ready drilled diecast case, screws, leads, terminals etc.

Available in both 6 and 12v versions. State whether positive or negative earth. **£9-62** incl. p. & p. U.K. only.

De-coupling kit for impulse tachometer and interference suppression. **£1-10** incl. p. & p. U.K. only. All our kits use guaranteed quality components and have been approved by the Author.

MAGTOR LTD.

68 DALE ST., MANCHESTER
M1 2HS 061-236 3031

EX COMPUTER PC PANELS

2 x 4 in. packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (9p)

SPECIAL BARGAIN PACK

25 boards for £1 (25p).
Panels with 4 Power transistors sim OC28 50p (9p)

ELECTROLYTICS

68,000µ 16, 4½ x 2 in. dia., 25,000µ 25v, 20,000µ 30v, 5,000µ 90v, 35,000µ 15v, 8,000µ, 4½ x 3 dia. 50p (15p) 15,000µ (5v), 10,000µ 35v, 4½ x 2 in. dia. 30p (10p), 2,000µ 25v wire ends 15p (5p), 12 for £1/50 (15p)

20A DIODES 4 for £1 (7p)

3A DIODES 4 for 50p (5p)

8 BLACK TOGGLES dpst 50p (8p)

250 MIXED CAPACITORS 60p (8p)

250 MIXED RESISTORS 60p (8p)

150 HI-STAB RESISTORS 60p (8p)

200 SI PLANAR DIODES 50p (5p)

SUB. MIN. CO-AX PLUGS & SKTS. 4 pairs 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES 8 for 50p (8p)

ASSORTED RELAYS 8 for £1 (12p)

MIN. GLASS NEONS 12 for 50p (5p)

10 WAY TERMINAL BLOCKS 10 for 55p (5p)

PAPST EXTRACTOR/BLOWER FANS 100 cfm 4½ x 4½ x 2 in £3-50 (28p)

Q-H BULBS 12v 55w 50p (5p)

Postage and package shown in brackets.

Please add 10% VAT to prices

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD

LONDON W8. 01-478 8499

**GEIGER COUNTERS
(FOR MAINS OR PORTABLE BATTERY USE)**



Latest Home Office release and probably the last, of this well known Continuation Meter No. 1 this very useful instrument is used for the measurement of Radio-Activity. Indicated on an Internal Meter scaled 0-1 to 10 milli Röntgen/Hour, a socket is also provided for additional sound Monitoring on Headphones. This instrument is housed in a Strong Light Alloy Case, placed in a carrying Haversack with shoulder strap. Containing Cable and Hand held Probe. Instruction Card, plus the latest plug in Vibrator Power Unit, which uses current small Transistor Radio Batteries (4 Mallory Long Life RM12 or 4 Ever Ready H.P.7 or equivalent makes). For mobile use anywhere. (Cost Gov. approx. £70 each). Supplied Brand New in Carton only £25-50 carr. 50p. An additional plug in Power Unit for Laboratory use, operating from 100-120 volts or 200-250 volts A.C. Mains is available. Supplied Brand New in Carton at only £22-50 post 25p.

TRANSCEIVERS

Due to warehouse clearance we have for disposal, few only Transceivers No. 62 Mk. 2, made by Iye for the Navy and Army. Using a total of 11 valves, 1 RF and 2 I.F. stages, A.V.C., BFO, covering 1.5 Mc/s. to 10 Mc/s. (approx. 200 to 300 metres) in two switched bands. Can be used on RT or CW M.O. or Crystal. A very good internal ATU made of a rotating silver wire coil, tunable over the complete range, suitable for aerials 4ft. to 100ft., internal P.U. for 12 volt D.C. A meter is fitted for checking voltages. A.V.C. etc. Housed in a metal waterproof case, approx. size 18" x 10½" x 12½". Supplied in as new condition, being either rebuilt by Army Signals or store-soiled new set, in cartons two spare valves, circuit, price £17-50, carriage £2. Suitable hand telephone with spring coil plus transmitter switch in handle. Modern. £1-50.


JOHNS RADIO

424 BRADFORD ROAD, BATLEY, YORKS.
Phone: Batley 7732



I.L.P. (Electronics) Ltd

100 WATTS!

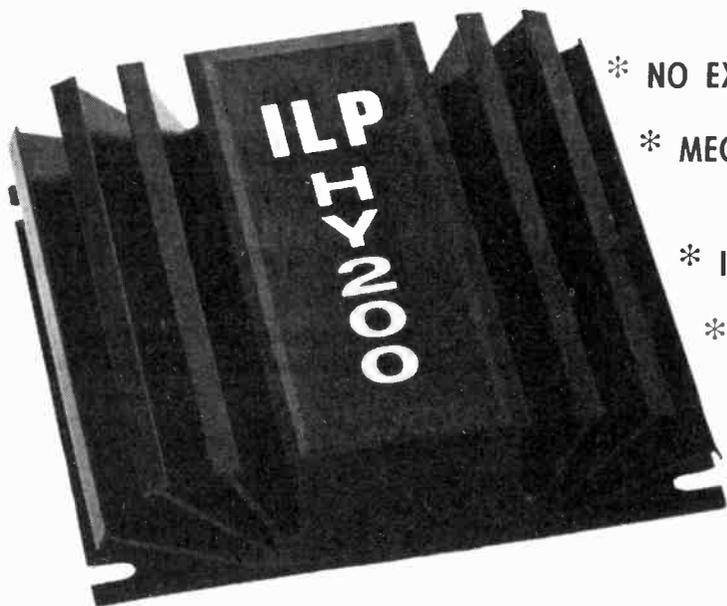

- * NO EXTERNAL COMPONENTS
- * MECHANICALLY & ELECTRICALLY ROBUST
- * INTEGRAL HEATSINK
- * HERMETICALLY SEALED UNIT
- * ATTRACTIVE APPEARANCE
- * LOW COST
- * BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

OUTPUT POWER: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10k Ω . **INPUT SENSITIVITY:** 0Dbm (0.775volt RMS). **LOAD IMPEDANCE:** 4-16 Ω . **TOTAL HARMONIC DISTORTION:** less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz-50KHz \pm 1Db. **SUPPLY VOLTAGE:** \pm 45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE:** £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

You'll hardly be able to believe your ears!

Can you really get
sound quality like
this **FOR LESS**
THAN £18?
YES, YOU CAN!
WITH THE NEW

STEREO
21

Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable **£17.95**, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!

And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience! Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for £17.95 (plus the cost of post and packing if you buy by mail), and—to round it all off—a money-back Guarantee if your pleasure in STEREO 21 is not complete!

Just think—in only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!

Personal shoppers and mail order price

£17.95 plus £1.50 p + p.

Diamond stylis, if required, £1.37 extra



**RADIO AND TV COMPONENTS (ACTON) LTD 21C HIGH STREET
ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2**

Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope
Goods not despatched outside U.K.

VISCOUNT III— a boost in the output,

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! And the teak finish will harmonise and enhance virtually any style of interior decor! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back.

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have never experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx. 17in × 10½in × 6½in. Drive unit 13in × 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Stimulated teak cabinet. £14.00 a pair + £2.20 p. & p. **Duo Type III** Size approx. 23½in × 11½in × 9½in. Drive unit approx 13½in × 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM 1

Viscount III R102 amplifier £24.20 + £1 p & p
2 Duo Type II speakers £14.00 + £2.20 p & p
Garrard SP25 Mk III with MAG cartridge /plinth & cover £18.00 + £1.75 p & p
total £56.20
Available complete for only **£49.00** + £3.50 p & p

STILL ONLY £49 COMPLETE

PRICES: SYSTEM 2

Viscount III R102 amplifier £24.20 + £1 p & p
2 Duo Type III speakers £32.00 + £3.30 p & p
Garrard SP25 Mk III with MAG cartridge /plinth & cover £18.00 + £1.75 p & p
total £74.20
Available complete for **£65.00** + £4 p & p




THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms. Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep. Circuit diagram and comprehensive instructions 55p free with parts. Fully retractable and lockable car aerial £1.37 post paid.

CAR RADIO KIT £6.60 p. & p. 55p. Speaker with baffle and fixing strips £1.65, + 23p p. & p. post free if bought with the kit. Send stamped addressed envelope for leaflet. If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

SOUND 50 45 WATT MONO AMPLIFIER. Ideal for Disco. Output Power: 45 watts R.M.S. (Sine Wave). Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19½ × 10½ × 8ins. Amplifier output for 3, 8 and 15 ohm speakers. **£31.35** + £1.65 p. & p.

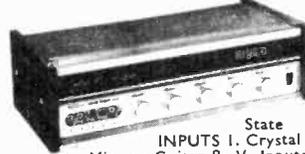


RELIANT MK IV

- *5 Electrically Mixed inputs.
- *3 Individual Mixing controls.
- *Separate bass and treble controls common to all 5 inputs.
- *Mixer employing F.E.T. (Field Effect Transistors).
- *Solid State Circuitry.
- *Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Output 20 watts into 8 Ω (suitable for 15 Ω.) Size approx. 12½ × 6 × 3½ ins. **£13.50** p. & p. 60p

UNISOUND MODULES

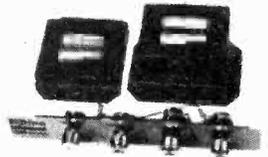ONLY £7.64 + 55p. p & p
For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lights indicate channel selected. The Viscount III, the fabulous Stereo 21 and the Unisound Modules **£9.90** plus p. & p. will accept this unit, simply connect up.



MAPLIN ELECTRONIC SUPPLIES

★ RETURN OF POST SERVICE



3RD EDITION NOW AVAILABLE

Send for your copy of this beautifully produced fully illustrated catalogue and we will forward it to you by return of post. Please send 9p in stamps.

Everything guaranteed brand new marked by manufacturer

MAPLIN: Projected site of London's third airport.

RESISTORS
Carbon film 5% from 1Ω to 1MΩ. 10% from 1MΩ. 1.2MΩ to 10MΩ. E12 series, $\frac{1}{2}$ W 1p; $\frac{1}{4}$ W 1.2p. Metal Oxide 2% 10Ω to 1MΩ. E24 series $\frac{1}{4}$ W 4p. Also 1W, 2 $\frac{1}{2}$ W, 5W, 10W types stocked.

POTENTIOMETERS

Miniature carbon track with $\frac{1}{2}$ in. spindles. 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ. Log or lin (and 1kΩ lin), 12p. Log or lin with switch 23p. Dual gang less switch 38p.

THE OTHER DAY WE RECEIVED A WIRE

It was too long + stop + so we cut it with a pair of our 5 inch diagonal nippers + stop + fully insulated handles + stop + they make a clean cut at only £1.40 a pair + stop + then we had to strip to the bare copper without a nick + stop + our fully adjustable strippers will strip cleanly any size wire from 12 S.W.G. to 26 S.W.G. with no nicked wires even if its stranded + stop + real value at only 54p a pair + stop + finally the wire had to come to an end so we terminated it with our 5 $\frac{1}{2}$ " long nosed wiring pliers + stop + their slender jaws are gap free and the fully insulated handles are gently tensioned apart by leaf springs + stop + irresistible at only £1.98 a pair + stop + so the next time you get a wire you'll know what to do, won't you?

8 pin DIL Op Amp 741C 36p.
14 pin 741C 45p.
70V r.m.s. 1.8A full wave bridge rectifier.
REC 41A £1.06
DIODES IN914 4p.
BAX13 5p, IN4001 6p, IN4002 6p
IN4003 7p, IN4004 7p, IN4005 8p, IN4006 8p, IN4007 9p.

SEMI-CONDUCTORS
We stock a large range of transistors and I.C.s. for details please see our catalogue. LOOK! These popular devices at amazingly low prices: BC107/8, 9 10p each. BC169C 12p. BFY51 16p. T1543 (S543) 28p. 2N706 10p, 2N2646 45p, 2N3055 49p, 2N3819 24p.

DIN PLUGS. 3 pin, 9p. 5 pin A (180°), 5 pin B (240°), 10p each.
DIN SOCKETS. 3 pin, 5 pin A, 5 pin B, 7p each.
DIN LOUDSPEAKER. 2 pin plug, 8p. Socket 6p.
JACK PLUGS standard $\frac{1}{2}$ in plastic barrel, 13p, Stereo, 25p. Bright metal barrel, 17p. Stereo, 29p. Jack sockets standard $\frac{1}{2}$ in open type 10p, Moulded 2 break 13p, Moulded stereo 3 break 18p

SPECIAL IC, for organ builders, 7 stage frequency divider in one 14 pin DIL package, £2.63 or special price for pack of 12, £25. Why not ask us to slip a data sheet in with your catalogue.

NUDES!

Clothe those naked projects with our superb instrument cases. We are sole distributors of the



range, designed for the professional market, now available to you at special low prices. S.A.E. please for free illustrated leaflet.

HARDWARE
Wide range of nuts and bolts, plated brass and nylon types plus solder tags, shakeproof washers, etc. SOLDER, 10 metres of 22 gauge multicore, 20p. Insulating sleeving 3 sizes, 6 colours.

MISCELLANEOUS
LT700 Eagle sub-miniature O/P transformer 1200/50 200mW max., 35p. Slide switch DPDT, 12p. Miniature Push to make non-locking switch 12p. Silicon grease in special dispenser, 20ml, 38p.

SEE OUR CATALOGUE for details of how you can obtain £1 worth of components.

V.A.T. Please add 10% V.A.T. to final total. Orders and enquiries for catalogues to **MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex SS6 8LR**

ABSOLUTELY FREE

Postage and packing FREE in U.K. But we have to ask you to send a 10p handling charge with order under 50p.

ROTARY SWITCHES
Adjustable stop, 1 pole 2-12 way, 2 pole 2-6 way, 3 pole 2-4 way, 4 pole 2-3 way. Only 24p each.



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

W883 BLOCK CAPS please

PLUGS & LEADS

Plugs
Pack 107 5 pin Din 22p
Pack 108 3 pin Din 20p
Pack 135 $\frac{1}{2}$ " Jack 27p
Pack 130 $\frac{1}{2}$ " Jack Stereo 50p
Pack 103 Loudspeaker Plug 17p
Pack 100 Phono Plug 7p
Pack 230 3 pin Socket 25p
Pack 236 5 pin Socket 33p
Pack 234 Loudspeaker Socket 33p
Ready-made Leads
3 pin to 3 pin Din 70p
3 pin to open end 55p
5 pin to 5 pin Din 90p
5 pin to open end 70p
5 pin to 4 phono plugs £1.00
Speaker lead Din to spade 12ft 40p
Extension lead Din plug to socket 12ft. 70p
All leads approx. 6ft. in length

DIAMOND STYLI

(Send SAE for complete list)
8T4; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8.All at 80p each.
Double Diamond £1.25
Diamond suitable for Orbit NM22; G800; M3D £2.25 each

CARTRIDGES

Goldring G800 £6.00
Orbit NM22 £4.00
Shure 75/6 £6.00
Sonotone 9TAHC (Dia) £2.00
Sonotone 8T4A (Dia) £1.50
Ronnette 105 (Dia) £1.25

All prices include VAT and postage

RECORD CARE

Cecil Watts Dust Bug £1.20
Parastatic Disc Preener 45p
Antistatic Fluid 20p
Dust Bug Spares (Brush & Roller) 15p

CASSETTE TAPES

Audio-Magnetic C60
Qty 3 6 10 20
Price £1.00 £1.90 £3.20 £6.30
Cassette Caddy £1.20
Cassette Head Cleaner 35p

ZONAL ILFORD TAPE

5" Standard 600ft 25p
5 $\frac{1}{2}$ " Standard 900ft 50p
7" (Plain boxed) 1200ft 60p
7" (Westminster Boxed) 1800ft £1.25
7" Reel of Leader Tape (Blue or green) 75p

HEADPHONES

Sennheisser HD414 £10.60
AKG K50 £6.50
Beyer DT485 £35.00

MICROPHONES

AKG D109 £11.50
AKG D202E1 £39.50
AKG D190C £17.00
AKG D190E £18.20
AKG D224 £50.00
Sennheisser MD211N £45.00
Sennheisser MD413N £27.00
Sennheisser MD421N £35.00
Audio RMS7F Radio Mike £210.00

SPEAKERS

E.M.I. 350 Kit Bohms £8.20
E.M.I. 450 Kit Bohms £4.50


J. J. Francis (Wood Green) Ltd

MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS Telephone: Matching 476

Cool lighting **for hot parties.**

Velvet dim to full brightness at a touch of the finger. Off/on and infinitely variable.

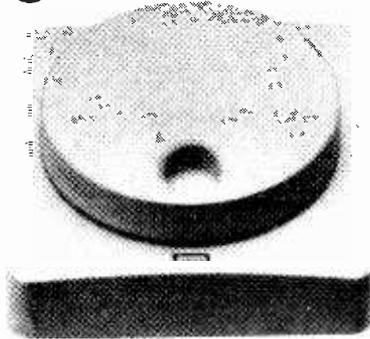Beta light glow makes switch easy to find in the dark and consumes no current.



Economical too!

As the light is progressively dimmed, so the current consumption drops – think of it as an electric tap. 300 watt capacity, straight replacement for standard light switch.

Complete kit of parts £2.80 or made up £2.90.



Hot Ignition for cold mornings.

The Jermyn capacitor discharge ignition system.

Instant starting in all weathers. Even with a near flat battery, the unit will produce a full sized spark.


Just one of the many advantages of an electronic ignition system, the others are:

High energy spark even at maximum revs.

Smoother running. Less strain on battery and starter. Lower petrol consumption. Long plug life with infrequent adjustment (typically 20,000 miles, gapped at .050").

No contact breaker arcing giving long life and less adjustment (typically 20,000 – 25,000 miles)

STATE + or – earth when ordering.

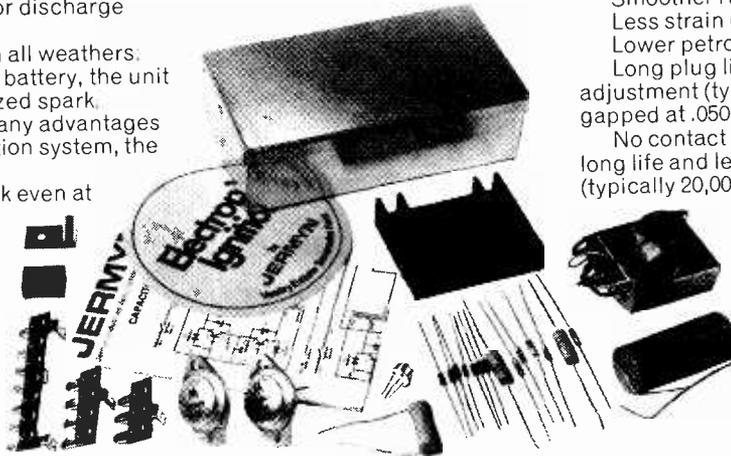

Complete set of parts to build it yourself for only £7.75, as described in Practical Wireless and fully approved by the author.

Save 55p
Buy both for £10.00

Reprints of the two part feature are available at 25p.

To Jermyn Industries, 93 Vestry Estate, Sevoyns, Kent.

Please despatch return of post light dimmer kit light dimmer
Ignition Kits + or – earth £10 pair. Enclose cheque or postal order.

BLOCK CAPITALS

NAME

ADDRESS

All Prices Exclusive of V.A.T.

JERMYN

NELSON-JONES FM TUNER KIT



as in 'W.W.' June '73

Now available for the first time to readers of 'Practical Wireless'. The Nelson-Jones tuner was originally made available by this company in May 1971, and consequently all 'bugs' have been 'ironed out' of this highly successful kit.

A recent design addition has used variable capacitance diodes and a Push Button Unit with 6 positions. AFC disable is incorporated as well as a pointer for each button showing tuning position in the range 87.5-108MHz.

Our complete metalwork system is supplied with nuts, bolts, board standoffs, push button mains on/off and stereo mute assembly, sockets, fuse and holder. Printed and Anodised Front Panel and Veneered Teak case. Power supply kits are supplied with complete kits of parts, or separately.

Prices for complete kits start at £23.75 + 45p pp. + VAT for mono tuners, (phase locked decoders are also available to fit in the cabinet). Please send large SAE for complete details of special offers and our complete lists.

TEXAN AMPLIFIER

The Cabinet of the Nelson-Jones Tuner is specially designed to match the Texan amplifier cabinet, see photographs, so that owners of Texan's are assured of compatibility, both in superb performance and appearance.

Texan amplifier kits are available at £28.50 + 45p pp. + Vat.
Worried about tuner alignment? then let our alignment service take over.



INTEGREX LIMITED, Dept. P.W., P.O. Box 45, Derby, DE1 1TW. Tel. Repton (028389) 3580



A special message to the Fumble Fingered Freds among us

NEW STEPHENSPEAKERS

A new range of loudspeaker kits and cabinets with a style and specification for every purpose. You'll be cheating a bit if you tell your friends "made it myself". We supply superb craftsmen built fully finished cabinets in beautiful stain and scuff resistant vinyl in white or teak.

Just fit the speaker cloth (supplied) and screw in your speaker.

HIGH QUALITY AT LOW COST

Send for our free booklet "Choosing a Speaker"



STEPHENSPEAKERS,
WILMSLOW AUDIO, Dept. 'PW', Swan Works, Bank Square, Wilmslow SK9 1HF

ALL PRICES INCLUDE VAT

BARGAIN PARCELS 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57½p p.p.; 56lb at £4.95 plus £1.37½ p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££s. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH. medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £1.55 post paid.

NEW HEAVY COAX CABLE dia. ¼" 70 ohms approx. 50ft. lengths £1.55, p. & p. 32½p. 100 ft. lengths £2.97, p. & p. 55p.

AERIALS. New Condition Whip Type, 4ft. 22p; 11ft. 82½p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 67½p. p. & p. 27½p.

CRYSTALS AS NEW. Hc 6u, 5,345; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,295 Kc/s. 55p each plus 8p p.p.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2½in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 27½p. minimum order of six.

ANY HEIGHT AERIAL TUBULAR SECTIONS ¾" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 22½p p. & p. 5p each. Minimum order 6.

AS NEW AERIAL TUNER UNIT No. 6 RF, consisting of 1½ inch 500 micro/ampmeter 3 gang tuner 75 PF geared BNC type socket size 5½" x 4½" x 5". Price £1.65, p. & p. 27½p.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft 50p, 100ft. 60p, p. & p. 22p.

AERIAL POLES 4ft high 2" in diameter push-in type as new 75p each p. & p. 25p each minimum four.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1.10 each section. Carriage 37½p each section. ¼" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1.10 + 32½p p.p.

AS NEW 500ua PENNY SIZE METERS complete with jack plug price £1.10 each, p. & p. 10p.

COMMUNICATION RECEIVER PCRS price £10. post paid.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.
Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

The largest selection

NEW LOW PRICED TESTED S.C.R.'s

P1V 1A	3A	5A	7A	10A	16A	30A
T05	T06	T066	T064	T048	T043	T048
50	0-28	0-39	0-39	0-52	0-55	0-59
100	0-28	0-37	0-52	0-52	0-64	0-70
200	0-39	0-41	0-54	0-54	0-63	0-67
400	0-48	0-52	0-62	0-62	0-74	0-83
600	0-59	0-63	0-75	0-75	0-85	1-07
800	0-70	0-77	0-88	0-88	0-99	1-32
						1-65
						4-40

SIL. RECTS. TESTED

P1V 300mA	750mA 1A	1.5A 3A	10A 30A
50	0-04	0-06	0-06
100	0-04	0-07	0-06
200	0-06	0-10	0-07
400	0-07	0-15	0-08
600	0-08	0-18	0-11
800	0-11	0-19	0-12
1000	0-12	0-28	0-16
1200	0-37	0-37	0-42

TRIACS		
VBO 2A	6A	10A
TO-5 TO-66 TO-48		
\$p	\$p	\$p
100	83	55
200	55	68
400	77	82

DIACS		
FOR USE WITH TRIACS		
BR100 (D32)	41p each	

FREE
One 50p Pak of your own choice free with orders valued \$4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed	EQVT
Pak No.	EQVT
T1	8 263713 OC71
T2	8 D1374 OC75
T3	8 D1216 OC75D
T4	8 26381T OC81
T5	8 26382T OC82
T6	8 26344B OC44
T7	8 26345B OC45
T8	8 26378 OC78
T9	8 26389A 2N1302
T10	8 26417 AF117

D1899 NPN SILICON DUAL TRANSISTOR
(Similar to 2N2906)
25 100+
0-28 0-28 0-23

ND 120 NIXIE DRIVER TRANSISTOR.
Suitable replacement for DSX 21, C 407, 2N 1893 120vcb.
1 25 100+
0-19 0-17 0-18

Sil. Trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 54p each. Any Qty.

GP 100 TO3 METAL CASE GERMANIUM
Vbeo=80V. Vceo=60V. I.C.=10 amps. Ptot=30W. hfe=30-170.

GP 300 TO3 METAL CASE SILICON
Vbeo=100V. Vceo=60V. I.C.=15 amps. Ptot=115W. hfe=20, 100Tf=1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.
1 25 100+
0-55 0-53 0-81

AD161/162 PNP M/P COMP GERM. TRANS. OUR LOWEST PRICE OF 60p PER PAIR

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 15p ea. 14W (Top-Hat) 20p ea. 10W (SO-10 Stud) 33p ea.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each

2 Amp. BRIDGE RECTS.
50 v RMS 35p each
100 v RMS 41p ..
400 v RMS 51p ..
Size 16 mm x 16 mm.

UT 46 UNIJUNCTION TRANSISTORS
Direct replacement for TIS 43rand BEN 3000 also electrically equivalent to 2N2646
1 25 100+
0-30 0-28 0-22

CADMIUM CELLS
ORP12 48p
ORP90, ORP61 44p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20 For	0-55
50 For	1-10
100 For	1-92
500 For	8-25
1000 For	14-30

SIL. G.P. DIODES 2p
30mW 30 55
40PIV(Min.) 100 1-85
Sub-Min. 600 5-80
Full Tested, 1,000 0-90
Ideal for Organ Bullers.

R 9400 TO3 NPN SILICON HIGH VOLTAGE
Vbeo=250V. Vceo=100V. I.C.=6 amps. Ptot=30W. hfe=typ.20
1 25 100+
0-55 0-50 0-44

2N3055
115 WATT SIL POWER NPN 55p EACH

B1P 19/20 TO3 NPN PLASTIC SILICON
Vbeo=100V. Vceo=50V. I.C.=10 amps. Ptot=50W. hfe=typ. 100 Tf=3MHz B1P 19/20 Matched Pair.
1 25 100+
0-37 0-35 0-32 0-66 0-61 0-55

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	60 Mixed Germanium Transistors AF/RP	0-55
U 3	75 Germanium Gold Bonded Sub-Min. like OA6, OA47	0-55
U 4	40 Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil. Planar Trans. NPN like BSY95A 2N706	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0-55
U 8	50 Sil. Planar Diodes DO-7 Class 250mA like OA200/202	0-55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-55
U10	20 BA750 charge storage Diodes DO-7 Glass	0-55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N112, 2N2904	0-55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-55
U13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0-55
U14	150 Mixed Silicon and Germanium Diodes	0-55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY61, 2N697	0-55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-55
U19	25 Silicon NPN Transistors like BC108	0-55
U20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-55
U23	30 MADT's like M1Z Series PNP Transistors	0-55
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-55
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0-55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-55
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0-55
U29	10 1 Amp BCR's TO-5 can. up to 600 PIV CR1/25-600	1-10
U30	16 Plastic Silicon Planar Trans. NPN 2N2926	0-55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-55
U32	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0-55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0-55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-55
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-55
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0-55
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-55
U39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0-55
U40	10 Dual Transistors 6 lead TO-5 2N2060	0-55
U41	25 RF Germanium Transistors TO-1, OC45, NKT2	0-55
U42	10 VHF Germanium PNP Transistors TO-1 NKT687, AF117	0-55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-55
U44	20 Sil. Trans. Plastic TO-5 BC115/116	0-55
U45	7 3A SCR. TO66 up to 600PIV	1-10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to HP x25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1 24 25-99 100 up Price each 49p 44p 38p

F.E.T.'S		
2N3819	81p	2N6458 35p
2N3820	55p	2N6459 44p
2N3821	39p	BFW10 66p
2N3823	81p	MPP105 41p

NEW 6th EDITION TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0-55
Q2	16 White spot R.F. transistors PNP	0-55
Q3	4 OC 77 type transistors	0-55
Q4	6 Matched transistors OC44/45/81/81D	0-55
Q5	4 OC 75 transistors	0-55
Q6	5 OC 72 transistors	0-55
Q7	4 AC 128 transistors PNP high gain	0-55
Q8	4 AC 126 transistors PNP	0-55
Q9	7 OC 81 type transistors	0-55
Q10	7 OC 71 type transistors	0-55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-55
Q12	3 AF 116 type transistors	0-55
Q13	3 AF 117 type transistors	0-55
Q14	3 OC 171 H.P. type transistors	0-55
Q15	7 2N2226 Sil. Epoxy transistors mixed colours	0-55
Q16	2 GE7880 low noise Germanium transistors	0-55
Q17	5 NPN 2 x ST.141 & 3 x ST.140	0-55
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 100	0-55
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-55
Q20	4 OC 44 Germanium transistors A.F.	0-55
Q21	4 AC 127 NPN Germanium transistors	0-55
Q22	20 NKT transistors A.F. R.F. coded	0-55
Q23	10 OA 202 Silicon diodes sub-min.	0-55
Q24	8 OA 81 diodes	0-55
Q25	15 IN914 Silicon diodes 75V 75mA	0-55
Q26	8 OA 85 Germanium diodes sub-min 1N69	0-55
Q27	2 10A PIV Silicon rectifiers IS425R	0-55
Q28	2 Silicon power rectifiers BYZ 13	0-55
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-55
Q30	7 Silicon switch transistors 2N706 NPN	0-55
Q31	6 Silicon switch transistors 2N708 NPN	0-55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0-55
Q33	3 Silicon NPN transistors 2N1711	0-55
Q34	7 Silicon NPN transistors 2N3269, 600MHz (code P397)	0-55
Q35	3 Silicon PNP TO-5 2 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3846 TO-18 plastic 300 MHz NPN	0-55
Q37	3 2N3053 NPN Silicon transistors	0-55
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0-55

ELECTRONIC SLIDE-RULE
The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and f of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and 'e' Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. Must for every electronic engineer and enthusiast. Size: 22 cm x 4cm. Complete with case and instructions. Price each: \$3 99

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UI000	12 x 7400	0-55	UI046	5 x 7446	0-55	UI086	5 x 7486	0-55
UI001	12 x 7401	0-55	UI047	5 x 7447	0-55	UI090	5 x 7490	0-55
UI002	12 x 7402	0-55	UI048	5 x 7448	0-55	UI091	5 x 7491	0-55
UI003	12 x 7403	0-55	UI050	12 x 7450	0-55	UI092	5 x 7492	0-55
UI004	12 x 7404	0-55	UI051	12 x 7451	0-55	UI093	5 x 7493	0-55
UI005	12 x 7405	0-55	UI053	12 x 7453	0-55	UI094	5 x 7494	0-55
UI006	8 x 7406	0-55	UI054	12 x 7454	0-55	UI095	5 x 7495	0-55
UI007	8 x 7407	0-55	UI060	12 x 7460	0-55	UI096	5 x 7496	0-55
UI010	12 x 7410	0-55	UI070	8 x 7470	0-55	UI100	5 x 74100	0-55
UI019	8 x 7413	0-55	UI072	8 x 7472	0-55	UI121	5 x 74121	0-55
UI020	12 x 7420	0-55	UI073	8 x 7473	0-55	UI141	5 x 74141	0-55
UI030	12 x 7430	0-55	UI074	8 x 7474	0-55	UI151	5 x 74151	0-55
UI040	12 x 7440	0-55	UI075	8 x 7475	0-55	UI154	5 x 74154	0-55
UI041	8 x 7441	0-55	UI076	8 x 7476	0-55	UI193	5 x 74193	0-55
UI042	5 x 7442	0-55	UI080	5 x 7480	0-55	UI199	5 x 74199	0-55
UI043	5 x 7443	0-55	UI081	5 x 7481	0-55			
UI044	5 x 7444	0-55	UI082	5 x 7482	0-55			
UI045	5 x 7445	0-55	UI083	5 x 7483	0-55			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES— 18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593.

OPEN MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.

Please add 10p postage and packing per order. Cash with order please. Orders to BI-PAK SEMICONDUCTORS, P.O. BOX 6, WARE, HERTS.

-the lowest prices!

74 Series T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS




	1	25	100+		1	25	100+		1	25	100+
SN7400	0-17	0-16	0-13	SN7450	0-17	0-16	0-13	SN74141	0-74	0-71	0-64
SN7401	0-17	0-16	0-13	SN7451	0-17	0-16	0-13	SN74145	0-65	0-61	0-54
SN7402	0-17	0-16	0-13	SN7453	0-17	0-16	0-13	SN74150	0-30	0-27	0-22
SN7403	0-17	0-16	0-13	SN7454	0-17	0-16	0-13	SN74151	0-10	0-10	0-09
SN7404	0-17	0-16	0-13	SN7460	0-17	0-16	0-13	SN74153	0-32	0-31	0-26
SN7405	0-17	0-16	0-13	SN7470	0-32	0-29	0-27	SN74154	0-98	0-87	0-76
SN7406	0-39	0-34	0-31	SN7472	0-32	0-29	0-27	SN74155	0-54	0-48	0-41
SN7407	0-39	0-34	0-31	SN7473	0-41	0-39	0-36	SN74156	0-54	0-48	0-41
SN7408	0-20	0-19	0-18	SN7474	0-41	0-39	0-36	SN74157	0-99	0-87	0-76
SN7409	0-20	0-19	0-18	SN7475	0-44	0-43	0-40	SN74160	0-98	0-87	0-76
SN7410	0-17	0-16	0-13	SN7476	0-44	0-43	0-40	SN74161	0-98	0-87	0-76
SN7411	0-28	0-27	0-26	SN7480	0-74	0-71	0-64	SN74162	0-40	0-43	0-35
SN7412	0-39	0-34	0-31	SN7481	0-32	0-29	0-27	SN74163	0-24	0-24	0-23
SN7413	0-32	0-29	0-27	SN7482	0-96	0-95	0-94	SN74164	0-23	0-27	0-23
SN7416	0-48	0-44	0-42	SN7483	0-21	0-18	0-16	SN74165	0-23	0-22	0-22
SN7417	0-48	0-44	0-42	SN7484	0-21	0-18	0-16	SN74166	0-23	0-22	0-22
SN7420	0-17	0-16	0-13	SN7485	0-35	0-32	0-29	SN74167	0-95	0-83	0-72
SN7422	0-55	0-53	0-50	SN7486	0-35	0-34	0-33	SN74174	0-23	0-22	0-22
SN7423	0-55	0-53	0-50	SN7489	0-65	0-57	0-50	SN74176	0-23	0-22	0-22
SN7425	0-55	0-53	0-50	SN7490	0-74	0-71	0-64	SN74177	0-23	0-22	0-22
SN7426	0-50	0-46	0-44	SN7491	0-10	0-10	0-09	SN74180	0-20	0-21	0-14
SN7427	0-50	0-46	0-44	SN7492	0-74	0-71	0-64	SN74181	0-05	0-05	0-05
SN7428	0-77	0-72	0-66	SN7493	0-74	0-71	0-64	SN74182	0-05	0-05	0-05
SN7430	0-17	0-16	0-13	SN7494	0-85	0-82	0-75	SN74184	0-23	0-22	0-22
SN7432	0-50	0-46	0-44	SN7495	0-85	0-82	0-75	SN74190	0-23	0-22	0-22
SN7433	0-88	0-83	0-77	SN7496	0-96	0-93	0-86	SN74191	0-22	0-22	0-22
SN7437	0-71	0-68	0-66	SN74100	0-82	0-78	0-71	SN74192	0-22	0-22	0-22
SN7438	0-71	0-68	0-66	SN74104	0-10	0-10	0-09	SN74193	0-22	0-22	0-22
SN7440	0-17	0-16	0-13	SN74105	0-07	0-04	0-04	SN74194	0-22	0-22	0-22
SN7441	0-74	0-71	0-64	SN74107	0-44	0-42	0-40	SN74195	0-22	0-22	0-22
SN7442	0-74	0-71	0-64	SN74110	0-61	0-59	0-55	SN74196	0-98	0-87	0-76
SN7443	0-14	0-13	0-12	SN74111	0-38	0-37	0-36	SN74197	0-98	0-87	0-76
SN7444	0-14	0-13	0-12	SN74118	0-10	0-10	0-09	SN74198	0-05	0-05	0-05
SN7445	0-19	0-18	0-17	SN74119	0-49	0-48	0-47	SN74199	0-05	0-05	0-05
SN7446	0-10	0-10	0-09	SN74121	0-44	0-41	0-38	3 Terminal Pos Volt Reg. T.O.3			
SN7447	0-10	0-10	0-09	SN74122	0-54	0-51	0-43	21 Pin Plastic O/P 1.5 Amps. μ A7805			
SN7448	0-10	0-10	0-09	SN74123	0-08	0-07	0-06	5V. & μ A7812 12V. μ A78			

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

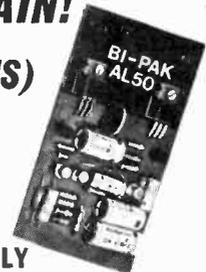


THE AL50

- ★ Frequency Response 15Hz to 100,000-1dB. **ONLY £3.58p each**
- ★ Load—3, 4, 8 or 16 ohms.
- ★ Supply voltage 10-35 Volts.
- ★ Distortion—better than .1% at 1KHz.
- ★ Overall size 63mm x 105mm x 13mm.
- ★ Signal to noise ratio 80dB.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.

STABILISED POWER MODULE SPM80

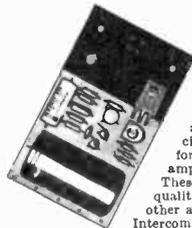

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Discos Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £3.25**

TRANSFORMER BMT80 £2-15 p. & p. 28p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

- Frequency Response 20Hz - 20KHz \pm 1dB
- Harmonic Distortion better than 0.1%
- Inputs : 1. Tape Head 1.25 mV into 50K Ω
- 2. Radio, Tuner 35 mV into 50K Ω
- 3. Magnetic P.U. 1.5 mV into 50K Ω
- All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within \pm 1dB. from 20Hz to 20KHz.
- Bass Control \pm 15dB at 20Hz
- Treble Control \pm 15dB at 20KHz
- Filters : Rumble (High Pass) 100Hz
- Scratch (Low Pass) 8KHz
- Signal/Noise Ratio better than - 65dB
- Input overload + 20dB
- Supply + 35 volts at 20mA
- Dimensions 292mm x 82mm x 35mm

ONLY £13.15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail.

Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

LINEAR I.C.'s—FULL SPEC.

Type No.	1-24	25-99	100 up
BP 201C—BL201C	70p	59p	50p
BP701C—BL701C	70p	59p	50p
BP 702C—BL702C	70p	59p	50p
BP 702—72702	50p	50p	45p
BP709—72709	40p	38p	33p
BP 709P— μ A709C	40p	38p	33p
BP 710—72710	50p	46p	44p
BP 711— μ A711	50p	48p	44p
BP 741—72741	55p	50p	45p
μ A703C	31p	29p	27p
TAA 263	77p	68p	61p
TAA 293	98p	88p	77p
TAA 350	£1.87p	£1.74p	£1.65p

S.G.S. EA1000 £2-90p

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	Price	1	25	100+
BP930	13p	12p	11p	
BP932	14p	13p	12p	
BP933	14p	13p	12p	
BP935	14p	13p	12p	
BP936	14p	13p	12p	
BP944	14p	13p	12p	
BP945	28p	27p	24p	
BP946	13p	12p	11p	
BP948	28p	27p	24p	
BP951	72p	66p	61p	
BP962	13p	12p	11p	
BP9693	44p	42p	39p	
BP9694	44p	42p	39p	
BP9697	44p	42p	39p	
BP9699	44p	42p	39p	

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series) only.

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.87	£1.70	£1.50

All indicators 0.9 + Decimal point. All side viewing. Full data for all types available on request.

RZL MICROLOGIC CIRCUITS

	Price each	1-24	25-99	100 up
Epoxy TO-5 case				
μ L900 Buffer	38p	36p	29p	
μ L914 Dual 2/p gate	38p	36p	29p	
μ L923 J-K flip-flop	55p	51p	49p	

Date and Circuits Booklet for IC's Price 8p.

DUAL-IN-LINE SOCKETS.

14 & 16 Lead Sockets for use with DUAL-IN-LINE I.C.'s. TWO RANGES PROFESSIONAL & NEW LOW COST.

PROF. TYPE No.	1-24	25-99	100up.
TSO 14 pin type	33p	30p	28p
TSO 16	39p	35p	33p

LOW COST No.

BPS 14	17p	15p	12p
BPS 16	18p	16p	13p



and it's
FREE
-The
Book
of
kits

See for yourself the range of wonderful new kits that Heath have presented in the latest catalogue. We now offer something for everyone, including stereo hi-fi equipment, radios, intercoms, calculators, automotive testers, shortwave and amateur radio, testers and instruments for technicians and hobbyists . . . all at money-saving prices. And payment is so easy—choose cash or our low deposit terms (starting at £2 per month for up to £40 credit).

You can build a Heathkit model using only a soldering iron and a few simple hand tools. Foolproof assembly is guaranteed using the step-by-step construction manual included with every kit.

Add to this a technical consultant service both before and after purchase and you will see why kit building the Heathkit way is so popular all over the world.

Send now for your free copy of the Heathkit electronic kit catalogue—and if your friend is likely to borrow it, fill his name and address in below and we'll send him a copy too!

Please send a **FREE** Heathkit Catalogue to my friend

NAME _____

ADDRESS _____

HEATH
Schlumberger HEATH (GLOUCESTER) LTD., DEPT. PW/08/73
BRISTOL ROAD, GLOUCESTER GL2 6EE

Please send me a **FREE** Heathkit Catalogue
 I want to know more about your Cash and Low Deposit Terms, without obligation.

NAME _____

ADDRESS _____

HEATH
Schlumberger HEATH (GLOUCESTER) LTD., DEPT. PW/08/73
BRISTOL ROAD, GLOUCESTER GL2 6EE


Multicore Solder Cream for high quality joints in the Electronics Industry

New Multicore Solder Cream was designed for jobs where second best will just not do. Like manufacturing diodes for instance. Or making a tuner chassis, or soldering thick-film circuits. Multicore Solder Cream, a finely graded solder alloy powder in a thixotropic organic vehicle, is easier, quicker, more economic and more reliable than conventional techniques.

Multicore Solder Cream is different. It doesn't spit or need stirring. It can be applied by syringe, automatic dispensers or screen printing—giving instant soldering with

good spread, strong joints with low contact angles. Suitable as a temporary adhesive during assembly, the clear colour flux residue—without solder globules—makes inspection easier. There are three types of Multicore Solder Cream—one of them may be just what you're looking for.

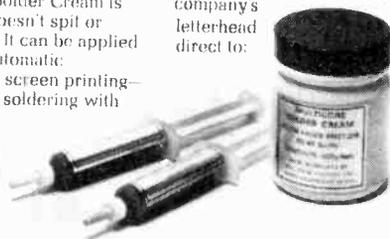For full information on this or any other Multicore products, please write on your company's letterhead direct to:



Multicore Solders Ltd., Maylands Avenue, Hemel Hempstead, Herts. HP2 7EP. Tel: Hemel Hempstead 3636. Telex: 82363.

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 4285

THE T.V. GRAVEYARD OF THE NORTH, AS SEEN ON T.V. CLOSE TO THE MOTORWAY. PLENTY OF FREE PARKING SPACE. EST. 1935.

SPECIAL OFFER

1000 PYE 19" 13 Channel T.V. Sets. Brilliant Picture, Extra Slim Bench Tested. Sold with Money Back Guarantee. Hurry, have a second set at the price of £5.50. Plus carr. and ins. £1.80. FAMOUS R. & A. 7x4" Speakers ex T.V. 3 Ohm 2½ Watt 50p. Post and Packing 12p.

COMPLETE UNTESTED T.V. SETS. With back and all valves. BBC 1 and ITV 17" 90° Tubes £1.10. 17" 110° Tube £2.20. 19" £3.30. Carr. and ins. on any set £1.75.

Reclaimed T.V. Tubes. All with 12 Months Guarantee, AW43/88 £1.65, MW43/69 £1.10, AW43/80, £1.65. Carr. and ins. on any tube £1.75.

¼ Cwt. of ex Government Scrap Resistors, Panels and Gears, etc. 30p. Carr. 80p.

SPEAKERS REMOVED FROM T.V. SETS, all 3 Ohm 2½ Watts. 7 x 4", 6 x 4", 8 x 2½". All at 27p. Post and packing 12p.

TOP QUALITY TAPE. Reel to Reel 5" ST. 44p 5" LP 55p, 5½ LP 60p, 7" ST 66p, 7" LP 80p. Cassette Types C60 35p, C90 45p, C120 55p. Post on any tape 12p.

Jap Earpiece 8 Ohm Magnetic 3-5 12p.
Ex Equipment Valves all tested on our Mullard Valve Tester before despatch. 3 months guarantee on all valves. Single Valves Post 3p, over Post Free.

ARP12	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	14p	U191	20p
EBF89	15p	PCL83	15p	6BV77	12p
ECC81	12p	PCL84	15p	6BW7	12p
ECC82	12p	PL82	10p	6U4	20p
EF91	5p	PL83	10p	6F23	15p
EY86	22p	PL36	17p	20P1	12p
EF183	20p	PY81	10p	20P3	12p
EF184	20p	PY801	17p	30F5	20p
		PY800	17p	30FL1	

ABOVE PRICES INCLUDE V.A.T.

ADVERTISEMENT



designed for the discerning mind

Everything you need in the way of Discotheque equipment. Our 4 Disco Studio Centres with full light and sound facilities offer a comprehensive range of DJ Electronics equipment – apart from being appointed stockists for AKG, Reslo Sound, Beyer, etc., etc.

Our equipment is designed to provide maximum flexibility of operation. We have a range of versatile component units suited for the enthusiast and professional alike.

In fact you decide the specification and we provide the system. Amplifiers – Speaker Systems – Microphones – Discotheques – Sound to Light Units – Effects Projectors – Strobes. All you need including a wide range of sliders with ready cut panels.

Send for our new catalogue – you can mail order with no-deposit credit terms.

Our Studio Centres are open Monday to Saturday.

DISCOScene
536 Sutton Road, Southend, Essex – (0702) 611577

DISCOSOUND
122 Balls Pond Road, London, N.1 – (01) 254 5779

HENRY'S DISCO
309 Edgware Road, London, W.2 – (01) 723 6963

DISCOSOUND
90-98 Shaftesbury Avenue, London, W.1. –
(01) 437 5832

WEYRAD

IMPORTANT ANNOUNCEMENT

IT IS WITH GREAT REGRET THAT WE HAVE TO STATE THAT OWING TO REVISED COMPANY POLICY WE SHALL NO LONGER BE PRODUCING COMPONENTS FOR AMATEUR CONSTRUCTORS OR SMALL QUANTITY USERS.

THIS CHANGE WILL COME INTO EFFECT IMMEDIATELY AND WE ARE UNABLE TO ACCEPT FURTHER ORDERS FROM THE TRADE OR INDIVIDUAL CUSTOMERS. EXISTING ORDERS WILL BE COMPLETED WITH A MINIMUM OF DELAY.

WE ARE SORRY TO HAVE TO TAKE THIS STEP WHICH HAS BEEN FORCED UPON US BY INCREASES IN THE COST OF LABOUR AND MATERIALS WHICH NOW MAKE ANY FORM OF SMALL SCALE PRODUCTION HOPELESSLY UNECONOMIC. IN CLOSING THIS PARTICULAR FACET OF OUR BUSINESS WE SHOULD LIKE TO THANK ALL OUR PAST AND PRESENT CUSTOMERS FOR THEIR VALUED SUPPORT OVER MANY YEARS.

WEYRAD (ELECTRONICS) LIMITED

New
VAT
EDITION



Lasky's Audio-Tronics Catalogue 1973

The new 1973 VAT edition of Lasky's famous Audio-Tronics catalogue will be available in early April—FREE on request. The 48 tabloid size pages—many in full colour—have been reprinted with VAT price changes for your convenience, together with many new items. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape Recording and Audio Accessories. Send for your copy now and see for yourself that VAT can mean a saving on many of the 1000's of items we offer.

FREE

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME

ADDRESS

PW14


LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

NOW CONVERT YOUR STEREO SYSTEM TO 4-CHANNEL

FOR
ONLY

£19
INC. CARR

The sound that envelops you from all-around—NOT just from two sides. Now you can have 4-channel sound using 4-channel quadraphonic records or surround sound from your existing stereo collection and enjoy this new, invigorating and exciting sound dimension! We've done the impossible—there's no need to spend a fortune on converting your existing 2-channel stereo system—just £19 buys you the famous PALM Stereo Master Converter and two CC500 Speaker Enclosures, teak finished, size 11" h. x 6 1/2" w. x 4" d. housing. E.M.I. Speakers with a power handling of 7 1/2 watts per channel. The PALM 4-channel Converter is also available separately for only £3.85 inc. p & p.

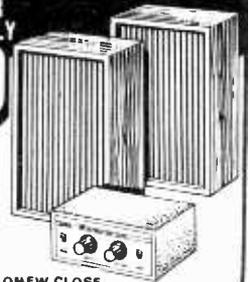

CCIE

(Dept. PW6) 43, BARTHOLOMEW CLOSE
LONDON, EC1A 7HP. Tel: 01-490 3211.

LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed—build as you learn with the exciting new 'Technatron' kit. No

Extras. Tools, transistors, meter etc. All supplied. You could build a radio in weeks.

SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV, ELECTRONICS, C & G, TELECOMMS ETC.

Dept. BPW18 Aldermaston Court, Reading RG7 4PF

Name

Address

Age CV BPW18



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

TRANNIES


£19.50 ELECTRONIC DIGITAL CLOCK

(For complete kit of parts including case.)

I DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)

ALL PRICES INCLUDE VAT

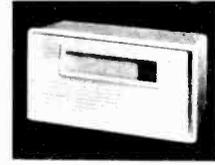

This 4 digit 24 hour clock is available to readers at this special price. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

74 Series TTL



1 25		1 25		1 25		1 25					
SN7400	16p	50p	723c	DIL	89p	SN7450	16p	15p	SN7489	6 05p	5 85p
SN7401	16p	15p	723c	T099	85p	SN7451	16p	15p	SN7490	74p	72p
SN7402	16p	15p	741c	8 PIN DIL	85p	SN7452	16p	15p	SN7491	1 10p	1 04p
SN7403	16p	15p	741c	14 PIN DIL	85p	SN7453	16p	15p	SN7492	74p	72p
SN7404	16p	15p	741c	T099	41p	SN7454	16p	15p	SN7493	74p	72p
SN7405	16p	15p	747c	DIL	46p	SN7455	16p	15p	SN7494	85p	78p
SN7406	35p	35p	748c	DIL	39p	SN7456	33p	29p	SN7495	85p	78p
SN7407	35p	35p	748c	DIL	39p	SN7457	33p	29p	SN7496	85p	78p
SN7408	20p	18p	748c	T099	41p	SN7458	33p	29p	SN7497	85p	78p
SN7409	20p	18p	748c	DIL	39p	SN7459	33p	29p	SN7498	85p	78p
SN7410	17p	15p	748c	DIL	39p	SN7460	33p	29p	SN7499	85p	78p
SN7411	27p	24p	748c	DIL	39p	SN7461	33p	29p	SN7500	85p	78p
SN7412	35p	35p	748c	DIL	39p	SN7462	33p	29p	SN7501	85p	78p
SN7413	35p	35p	748c	DIL	39p	SN7463	33p	29p	SN7502	85p	78p
SN7414	47p	43p	748c	DIL	39p	SN7464	33p	29p	SN7503	85p	78p
SN7415	47p	43p	748c	DIL	39p	SN7465	33p	29p	SN7504	85p	78p
SN7420	16p	15p	748c	DIL	39p	SN7466	33p	29p	SN7505	85p	78p
SN7422	55p	60p	748c	DIL	39p	SN7467	33p	29p	SN7506	85p	78p

* Devices may be mixed to qualify for Price Breaks
* 100 Plus less 10% off 25 plus break

Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	6 1/2p	15µF	6 1/2p	47µF	6 1/2p
100µF	6 1/2p	33µF	6 1/2p	100µF	9p
220µF	6 1/2p	68µF	6 1/2p	150µF	10p
330µF	6 1/2p	150µF	8p	220µF	11p
1000µF	13p	220µF	9p	470µF	19p
4700µF	29p	680µF	17p	680µF	25p
		1000µF	17p	1000µF	25p
		1500µF	25p	2200µF	44p
		2000µF	43p		

6 3 VOLT		25 VOLT	
33µF	6 1/2p	10µF	6 1/2p
68µF	6 1/2p	22µF	6 1/2p
150µF	6 1/2p	47µF	6 1/2p
470µF	11p	100µF	8p
680µF	13p	150µF	8p
1500µF	18p	220µF	10p
2200µF	18p	470µF	13p
3300µF	26p	680µF	20p
		1000µF	22p
		2200µF	39p
		5000µF	68p

10 VOLT		40 VOLT	
22µF	6 1/2p	6 8µF	6 1/2p
47µF	6 1/2p	15µF	6 1/2p
100µF	6 1/2p	47µF	6 1/2p
220µF	8p	100µF	8p
330µF	10p	150µF	13p
470µF	10p	220µF	19p
1000µF	11p	330µF	22p
1500µF	20p	470µF	26p
2200µF	24p	1000µF	44p

Linear Integrated Circuits

301	DIL	50p	723c	DIL	89p
301	T099	50p	723c	T099	85p
301	8 PIN DIL	46p	741c	8 PIN DIL	85p
301A	DIL	89p	741c	14 PIN DIL	85p
301A	T099	89p	741c	T099	41p
301A	8 PIN DIL	86p	747c	DIL	46p
307	DIL	89p	748c	DIL	39p
307	T099	89p	748c	T099	41p
307	8 PIN DIL	86p	1437	DIL	1 27p
308	T099	6 45p	1458	T099	1 27p
308A	T099	6 40p	1458	T099	1 27p
709c	DIL	35p	3046	DIL	84p
709c	T099	31p	7503	DIL	1 27p



Transistors

Diodes & Rectifiers		Diodes & Rectifiers	
AC107	16p	BC138	36p
AC126	14p	BC142	33p
AC127	13p	BC143	33p
AC128	13p	BC144	33p
AC142K	22p	BC145	28p
AC141K	20p	BC147	9p
AC176	15p	BC148	9p
AC187	13p	BC149	9p
AC187K	20p	BC153	18p
AC188	13p	BC154	17p
AC188K	20p	BC157	13p
ACY17	24p	BC158	12p
ACY18	21p	BC159	14p
ACY19	25p	BC167	13p
ACY20	22p	BC168	11p
ACY21	23p	BC169	11p
ACY22	18p	BC177	15p
ACY23	68p	BC179	15p
AD140	40p	BC182L	9p
AD142	44p	BC183L	9p
AD143	39p	BC184L	9p
AD149	35p	BC186	33p
AD150	60p	BC192L	11p
AD161	29p	BC213L	11p
AD162	28p	BC214L	11p
AD M 50p	50p	BC258	9p
AF114	14p	BC259	9p
AF115	14p	BC261	14p
AF116	14p	BC268	15p
AF117	14p	BC300	40p
AF118	82p	BC301	32p
AF124	27p	BC302	30p
AF139	39p	BC303	50p
AF239	41p	BC304	40p
AL100	77p	BC370	17p
AL102	66p	BC371	37p
AL103	55p	BC372	17p
ASY26	31p	BD123	86p
ASY27	40p	BD130	50p
AU103	99p	BD131	60p
AU110	41 10p	BD132	90p
AU111	77p	BD135	42p
BC107	9p	BD136	50p
BC108	9p	BD141	£1.87
BC109	9p	BD142	50p
BC113	15p	BF159	33p
BC116	16p	BF173	29p
BC126	16p	BF177	28p
BC126	25p	BF178	29p
BC132	16p	BF179	29p
BC134	16p	BF184	15p
BC135	16p	BF187	17p
BC137	16p	BF244	27p

MULLARD POLYESTER'S

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 33p, 0.33µF, 0.47µF, 0.068µF, 4p, 0.1µF, 41p, 0.15µF, 0.22µF, 51p, 0.33µF, 7p, 0.47µF, 81p, 0.68µF, 12p, 1.0µF, 14p, 1.5µF, 22p, 2.2µF, 27p

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 21p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 31p, 0.047µF, 0.068µF, 0.1µF, 41p, 0.15µF, 81p, 0.33µF, 12p, 0.47µF, 14p, 160V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 8p, 0.1µF 31p, 0.15µF, 41p, 0.22µF, 51p, 0.33µF, 61p, 0.47µF, 81p, 0.68µF, 12p, 1.0µF, 14p

VOLUME CONTROLS

Potentiometers
Carbon track 500 Ω to 2.2M Ω
Log or Linear
Single 13p, Dual gang (stereo) 44p
Single type with D.P. switch 13p extra.

SLIDE POTENTIOMETERS

56mm TRACK
SINGLE GANGED, LOG or LIN 1k to 1M, 45p each
TWIN GANGED, LOG or LIN 1k to 500k, 68p each.

CARBON SKELETON PRESETS

High quality type (linear only).
All values 100-5 meg ohms.
-1 watt 61p each
-2.5 watt 61p each

VEROBOARD

0-15 Matrix 0-1 Matrix
2 1/2in x 3 1/2in 15p
2 1/2in x 5in 28p
3 1/2in x 3 1/2in 28p
3 1/2in x 5in 38p
5in x 17in (plain) 94p
Vero Pins (bag of 36), 22p
Vero cutter, 50p; Pin insertion Tools (0-1 and 0-16 matrix) at 61p.

SLIDE SWITCH

SPST 11p each. D.P.D.T. 13p each.

MINIATURE NEON LAMPS

240V or 110V 1-4 5p, 5 plus 41p each

MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0-9 and decimals (Data Sheet on request)
ONLY £1.50
33p
16 DIL Socket 33p
Driven by 7447 £1.05

RECTIFIERS

P.I.V.	1 AMP	1.5 AMP
50	IN4001 44p	PL4001 8p
100	IN4002 44p	PL4002 9p
200	IN4003 51p	PL4003 10p
400	IN4004 61p	PL4004 10p
600	IN4005 8p	PL4005 13p
800	IN4006 9p	PL4006 15p
1000	IN4007 10p	PL4007 20p

BRIDGE RECTIFIERS

P.I.V.	1 AMP	2 AMP	5 AMP	10 AMP
50	33p	53p	£1.76p	£2.20p
100	35p	67p		
200	37p	80p	£1.98p	£2.31p
400	40p	64p	£2.15p	£2.42p
800	44p	68p	£2.42p	£2.75p

THYRISTORS

PIV	50	100	200	300	400
1 Amp	28	25	41	44	53
3 Amps	44	50	60	66	
7 Amps	98	1.01	1.11	1.24	

RESISTORS

1 watt 5% carbon 1p each
1 watt 10% carbon 1p each
1 watt 10% carbon 2 1/2p each
10 ohms to 4.7 meg.
1 watt m/o 25p 3p each
Range 10-1 meg ohms

BARGAIN PACKS

Unmarked Packs

Pack of 25 IN4148 55p

Pack of 10 BC108 55p
BC107 55p
(Plastic can)

Pack of 10 Plastic BC109 55p

Pack of 10 BC169 55p (unmarked) but tested

2N2646 (unmarked) 33p each

Pack of 10 2N2926G 55p unbranded but tested!

Unmarked but fully tested 2N3055 83p 10 plus 27p

FULLY MARKED TYPES

AD161, AD162 M/P 59p

1-9 10 plus 59p

BC107-BC108 BC109 9p 8p 61p

BC 182L-3-4-212-4 1-9 10 plus 8p 8p 10 plus 8p

AC127 or AC128 1-9 13p 10 plus 12p 100 plus 11p

ZENER DIODES

400 M/W 5% Miniature BZY 88 Range All voltages 3-3-33 Volt 8p each

1 watt 5% All voltages 6.8-200 Volt 14p each

10 watt 5% All Voltages 7.5-100 Volt 51p each

COMET HI-FI discount warehouses



NEW LOW PRICES

	Rec. Retail Price	Comet Price
STEREO AMPLIFIERS		
AKAI AA5200	87.45	80.95
AKAI AA5500	109.45	80.95
AKAI AA5800	164.45	121.95
AKAI SS1 Quadraphonic Decoder	54.45	42.95
ALBA UA 700	41.72	27.95
AMSTRAD 5000 Mk. II	30.75	16.95
AMSTRAD IC 2000	50.88	28.25
AMSTRAD Integra 4000	39.05	23.95
FERROGRAPH F307 Mk. II (cased)	74.80	49.95
GLIXOR MW3000, 15 watts RMS per channel	54.45	25.95
GODWIN RH 25 25	65.95	49.95
JVC Nivico VN 300	69.85	55.95
VN 700 SEA	140.25	112.95
MCA 104Z	169.40	135.95
4DD5 Demodulator for CD4	67.10	52.95
MCA V5E/VN550 Quadraphonic MCA V5E/VN890 Quadraphonic	104.50	83.95
VN 990 Quadraphonic	170.50	136.95
KELETRON KSA 700 Mk. II	34.10	21.95
KELETRON KSA 1500 Mk. II	45.10	29.50
LEAK Delta 30 (cased)	76.89	50.95
LEAK Delta 70 (cased)	94.49	63.20
METRO SOUND ST20 Mk. II	48.20	32.95
METRO SOUND ST40	59.40	42.95
METRO SOUND ST60	77.00	50.95
PHILIPS RH 520	85.00	66.95
RH 521	119.90	89.95
PIONEER SA500A	55.96	38.95
SA600	113.43	73.95
SA600	150.32	103.95
SA1000	185.12	121.95
SA6200	114.40	78.95
SA7100	144.10	99.95
SA8100	202.40	139.95
SA9100	248.60	171.95
Q4500A Quadraphonic Converter	141.32	96.95
QD210 Quadraphonic decoder	50.91	33.95
QA800A Quadraphonic QCS800A Pre-amp Quadraphonic	249.92	172.95
QMPow. amp.	178.31	122.95
QMPow. amp.	212.14	146.95
Reverberation 202w	65.25	44.95
RANK ROTEL 310	57.20	37.95
RANK ROTEL 610	86.35	56.75
RANK ROTEL RA 810	116.05	78.95
RANK ROTEL RA 1210	141.90	96.50
ROGERS Ravensbrook Mk. III (cased)	63.25	49.95
ROGERS Ravensbourne	77.00	59.50
Ravensbourne (cased)	82.50	64.95
SINCLAIR 2000	38.50	26.95
3000	49.50	34.95
SOLARVOX 20. 10 watts RMS per channel	43.95	26.95
SOLARVOX 30. 15 watts RMS per channel	51.65	35.95
SOLARVOX MA801 2 x 8 watts RMS plus MA TRIX 4 channel	42.30	29.75
SOLARVOX MA813 2 x 18 watts RMS plus MATRIX 4 channel	56.52	42.95
TANDBERG TA300 (Teak)	86.32	67.95
TANDBERG TA300M (Teak)	96.24	79.95
WHARFEDALE Linton amplifier	71.50	51.95
All take both ceramic and magnetic cartridges.		
TUNERS		
AKAI AT550 AM/FM/MPX/FET	84.10	64.95
AT580 AM/FM/MPX/MOS FET	131.09	102.95
AMSTRAD Multiplex 3000 FM	37.90	23.95
JVC Nivico MCT V5E/FT500 AM/FM	82.50	65.95
VT 700	126.50	101.50
MCT V7E AM/FM	115.25	94.95
LEAK Delta FM	74.43	52.95
Delta AM/FM	83.79	62.25
METRO SOUND FMS 20 MKK II	54.45	38.95
FMS 40	56.10	40.82
PHILIPS RH 620	45.68	33.50
RH 621	103.06	78.80
PIONEER TX 500A AM/FM	79.72	54.95
TX600 AM/FM	110.39	75.95
TX6200	94.60	65.50
TX7100	111.10	76.95
TX8100	150.70	103.95
TX9100	204.60	139.95
RANK ROTEL 320	55.91	36.20
620	87.86	59.95
ROGERS Ravensbourne Series II (cased)	61.05	47.50
Ravensbrook Series II (cased)	46.75	36.95
SINCLAIR 2000	42.44	28.95
3000	42.44	28.95
All the above Tuners are complete with MPX Stereo Decoder		
TUNER/AMPLIFIERS		
AKAI AA800	130.54	99.95
AKAI AA800S	178.07	128.50
AKAI AS100S Quadraphonic	243.85	189.95
AKAI 6300	129.21	69.95
AUTOMATIC RADIO CHX 9912 AM/FM: MPX stereo tuner/amplifier with built-in stereo cassette recorder	107.25	49.95

All prices quoted in this advertisement include VAT

	Rec. Retail Price	Comet Price
TUNER/AMPLIFIERS—continued		
GOODMANS Module 80, 35w. RMS	87.55	60.25
Module 80 Compact	158.16	112.50
Module 90	112.04	75.75
Module 110 FM/MW/LW/SW/100w. RMS	130.86	88.50
GOODMANS Module 110, Compact	230.65	169.95
JVC Nivico 4MM 1000 Quadraphonic 4VR 1006 Quadraphonic with CDA demodulator	161.15	128.95
VR 5501 AM/FM	229.35	183.50
VR 5521L AM/FM and SEA	172.70	138.95
4VR 5414 Quadraphonic SEA	229.35	183.50
4VR 5445 Quadraphonic SEA	308.00	246.50
KYOTO 1000 AM/FM Tuner/Amplifier with built-in Stereo Cassette Recorder. Complete with two speakers and two microphones	79.90	57.95
LEAK Delta 75 AM/FM MPX	163.83	112.95
PHILIPS RH 702	90.38	67.95
PHILIPS RH 720	202.41	152.95
PIONEER SX 424 AM/FM/MPX	118.70	78.50
PIONEER SX525 AM/FM/MPX	148.36	101.95
PIONEER SX626 AM/FM/MPX	203.21	138.95
PIONEER SX727 AM/FM/MPX	244.63	168.95
PIONEER SX828 AM/FM/MPX	313.74	216.95
PIONEER QX 4000 Quadraphonic AM/FM/MPX	238.50	164.95
PIONEER QX 8000A Quadraphonic AM/FM/MPX	339.23	233.95
PIONEER QX 9900 Quadraphonic AM/FM/MPX	473.26	327.50
ROTEL RX 150A	65.68	45.95
ROTEL RX 200A	84.10	60.95
ROTEL RX 400A	101.01	69.95
ROTEL RX 600A	140.91	95.95
ROTEL RX 800A	178.07	128.25
ROTEL RX 154A Quadraphonic	121.68	86.95
SOLARVOX TAM 1105 2 x 5 watts RMS AM/FM Multiplex comp. with 2 speakers and featuring Matrix 4 channel	37.06	29.75
TANDBERG TR200 MPX (Teak)	112.20	83.95
TANDBERG TR1000 FM MPX (Teak)	163.71	138.95
TANDBERG TR1010 AM/FM MPX (Teak)	177.33	148.95
TELETON CR55 LINTON W640 WHARFEDALE LINTON W640 AM/FM MPX	107.66	79.95
All the above take magnetic cartridges except Kyoto 1000 and Automatic Radio CHX 9912 which take ceramic only. All include MPX Stereo Decoder.		
TURNTABLES		
CONNOISSEUR BD1 Kit Chassis	12.65	10.50
CONNOISSEUR BD2 Chassis	31.02	24.95
CONNOISSEUR BD2 P/C/SAU2	39.16	32.25
GARRARD SP25 Mk. III Chassis	15.25	9.05
GARRARD 40B Chassis	12.95	9.50
GARRARD SL65B Chassis	18.78	12.95
GARRARD SL95B Chassis	46.40	30.60
GARRARD 401 Chassis	40.43	25.95
GARRARD SL72B Chassis	30.73	20.25
GARRARD AP76 Chassis	26.82	18.95
GARRARD Zero 100A Chassis	51.57	33.25
GARRARD Zero 100S Chassis	47.44	30.70
GOLDRING G101P/C	31.35	21.50
GOLDRING GL72 Chassis	34.65	23.95
GOLDRING GL72P	45.87	31.50

The following Turntables are complete with base, plinth, cover and cartridge. Fully wired and ready for use.

MCDONALD MP80 with G800	Sp. Price 15.95
MCDONALD HT70 with G800	Sp. Price 20.95
GARRARD 2025 TC with Sordolone 9714C ceramic Sp. Price 12.10	
GARRARD SP25 Mk. III with G800	Sp. Price 15.95
GARRARD AP76 with G800 Sp. Price 25.95	
GOLDRING GL72 with G800 Sp. Price 33.95	
GOLDRING GL75 with G800 Sp. Price 41.95	
GOODMANS TD100 with G800 cartridge	77.29 52.95
JVC Nivico SRP 473 with Nivico magnetic cartridge	71.50 56.95
LEAK Delta deck with Shure Cartridge	65.07 49.95
PHILIPS GA407 with GP400 mag. Cartridge	45.00 34.95
PHILIPS GA212 Electronic with GP400 cartridge	64.95 50.95
PIONEER PL335 with PC50 Magnetic Cart.	100.82 69.95
THORENS 160/C with Ortofon M15E Super cartridge	99.00 78.95
THORENS TD125 AB Mk. II with Ortofon M15E Super Cart.	154.00 122.50
WHARFEDALE Linton with Shure Cartridge	35.11 25.95

	Rec. Retail Price	Comet Price
TURNTABLES—continued		
GOLDRING GL75 Chassis	43.89	29.95
GOLDRING GL75P	56.76	38.95
GOLDRING GL75 Chassis with auto stop	53.46	36.95
GOLDRING GL78P/Cover with auto stop	76.89	52.95
GOLDRING GL85P/Cover with auto stop	98.34	65.95
MCDONALD MP80 Chassis	13.96	8.40
MCDONALD HT70 Chassis	19.49	12.50
MCDONALD 710 Chassis	33.44	21.50
MCDONALD 810 Chassis	41.80	27.50
PIONEER PL12D with base and cover	51.90	35.95
PIONEER PL12D with base and cover	180.33	124.95
THORENS TD125 Mk. II Chassis	83.60	66.50
THORENS TD125AB	109.04	72.50
THORENS TD 125AB Mk. II with TP 16 arm	126.50	99.95
THORENS TD 165/C including base and cover	60.50	48.50
THORENS TD 160/C including base and cover	71.50	56.95
SPEAKERS		
AMSTRAD ACOUSTA 1500 (Pair)	44.00	27.95
ACOUSTA 2500 (Pair)	55.00	31.95
138 (pair) Teak	28.60	19.95
B and W Model 70	175.45	125.95
B and W DM2	65.89	46.95
B and W DM4	46.75	35.95
B and W D5 (pair)	55.99	41.95
CELESTION HADLEIGH (pair)	43.34	30.95
Country (pair)	48.44	34.95
Dilton 15	36.95	26.50
Dilton 25	71.50	51.50
Dilton 44	59.40	40.50
Dilton 66	108.90	78.75
FERROGRAPH S1 Inc. stand	104.50	74.50
GOODMANS Minister (pair)	46.33	31.75
Havent (pair)	53.77	34.95
Magister	72.19	42.20
Double Maxim (pair)	63.45	42.25
Mezzo 3	39.27	25.60
Magnum K2	50.82	32.40
Goodwood	60.50	39.50
Dimension 8	78.68	58.50
PLANAX 2 Teak or White	46.20	32.95
DIN 20 NT Kit (pair)	22.95	16.50
KELETRON KS4 (pair)	22.66	13.95
KS6 (pair)	28.16	17.50
KS8 (pair)	36.30	22.75
KS10 (pair)	46.86	29.95
KS15 (pair)	69.85	43.50
KS20 (pair)	78.76	49.25
LEAK 150 (pair)	46.82	35.95
LEAK 250 (pair)	60.86	46.50
LEAK 600	54.45	38.50
MAGNETEN HALL		
NH110 (Pair)	35.20	23.95
NH150 (Pair)	42.90	28.95
NH200 (Pair)	53.90	35.95
NH300 (Pair)	99.00	64.95
METRO SOUND HFS 103 (pair)	27.50	19.25
202	23.65	16.95
202	35.20	26.95
Duplex 25	61.60	42.95
PIONEER CS53	56.52	38.95
ROGERS Ravensbourne Compact (pair)	61.60	49.95
SINCLAIR Q16	8.47	6.20
SOLARVOX TK19S twin speaker 20 watts Teak (pair)	40.65	29.95
TANDBERG TL 12 Teak (pair)	55.80	45.95
TL 25 Teak (pair)	75.16	60.95
TL 50 Teak	79.70	61.95
THORPE GRENVILLE TG100 (pair)	31.85	19.50
TG300 (pair)	46.15	28.50
WHARFEDALE Denton Mark II (pair)	61.95	34.50
Linton Mark II (pair)	39.33	27.95
Trilion III (pair)	48.89	33.95
Melton Mark II	60.85	41.95
Ovedale 3 Mark III	38.50	26.95
Unit 3 speaker kit (pair)	52.25	35.95
Unit 4 speaker kit (pair)	23.40	16.50
Unit 4 speaker kit (pair)	41.80	29.25
Unit 5 speaker kit (pair)	60.50	42.50
CHASSIS SPEAKERS		
GOODMANS Twin-Axiom 8	8.58	6.25
Twin Axiom 10	9.47	6.90
Axiom 401	19.45	13.95
Axiom 8P	5.17	3.75
Axiom 10P	5.62	4.10
Axiom 12P	14.30	10.49
Axiom 15P	23.16	16.50
Axiom 18P	39.27	27.95
Axiom 100 40 watts din.	13.20	9.50
ARU 172	4.95	3.60
Axent 100	7.59	5.40
Milax 650	14.95	9.60
Attenuator	4.10	2.95
Crossover network XO/950	8.55	5.95
WHARFEDALE 8 In. Bronze/RS/DD	4.44	3.20
Super 8/RS/DD	7.95	5.75
Super 10/RS/DD	13.11	9.45

OVER 1000 ITEMS ALWAYS IN STOCK
 All items brand new and fully Guaranteed
 and backed by after-sales service
 — latest models in manufacturers' sealed cartons



**COMET for
 after-Sales Service
 THROUGHOUT THE U.K.**

Service Departments at Hull, Birmingham, Biddisford, Dagenham, Doncaster, Edinburgh, Eastleigh, Gosport, Hockley, Hays, Jarrow, Leeds, Leicester, Nottingham, Renfrew, Rochdale, Rochester, Sheffield, Teesside, Wigan.

	Rec. Price	Retail Price	Comet Price
CARTRIDGES			
ADC 10E Mk. IV	Sp. Price	15 95	15 95
AUDIO TECHNICA AT 66	£ p	5 98	3 30
AUDIO TECHNICA UM35F for CD4	£ p	53 36	39 50
*CONNOISSEUR SCU1	£ p	5 78	4 75
GOLDRING G850	£ p	5 78	2 95
GOLDRING G800 Boxed	Sp. Price	4 20	4 20
GOLDRING G800E Boxed	Sp. Price	6 90	6 90
GOLDRING G800 Super E. Boxed	Sp. Price	10 95	10 95
GOLDRING G820	£ p	16 50	11 40
GOLDRING G820E	£ p	22 00	15 20
GOLDRING G820 Super E.	£ p	58 87	37 95
EMPIRE 1000ZE/X	£ p	42 05	26 95
EMPIRE 999VE/X	£ p	24 73	16 25
EMPIRE 999TE/X	£ p	19 98	12 70
EMPIRE 999E/X	£ p	15 49	9 95
EMPIRE 909E/X	£ p	12 10	7 95
EMPIRE 909E/X	£ p	9 41	6 20
EMPIRE 909E/X	£ p	5 81	3 30
SHURE M3D	£ p	7 91	4 40
SHURE M44-G	£ p	7 52	4 25
SHURE M44-7	£ p	7 52	4 25
SHURE M-44C	£ p	8 18	4 60
SHURE M44E	£ p	9 24	5 25
SHURE M35	£ p	14 00	7 90
SHURE M75G	£ p	8 18	4 95
SHURE M75-6 (S)	£ p	12 95	7 34
SHURE M75B	£ p	14 66	8 70
SHURE M75EJ	£ p	10 10	4 95
SHURE M75ED	£ p	18 10	10 95
SHURE M75ED	Sp. Price	12 15	12 15
SHURE M75EJ95G	£ p	18 10	9 20
SHURE M91D	£ p	37 52	24 95
SHURE V15-11	£ p	39 00	28 95
SHURE V15-Mk. III	£ p	3 58	1 30
*SONOTONE 9TAHC Diam/Saph	£ p	3 58	1 30
Starred cartridges above are ceramic—all others are magnetic.			
BASES AND COVERS			
CONNOISSEUR Plinth BD1	£ p	5 28	4 30
CONNOISSEUR Cover	£ p	3 95	3 20
CONNOISSEUR P.U. Mount Board	£ p	0 88	0 70
GARRARD WB1 Base	£ p	3 56	2 70
GARRARD WB4 Base	£ p	3 28	2 60
GARRARD SP C1 Cover	£ p	4 13	3 00
GARRARD SP C4 Cover	£ p	4 13	3 00
Special Offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500	Sp. Price	2 50	2 50
Special offer of base and cover to fit McDONALD MP60 and 610	Sp. Price	3 50	3 50
GOLDRING Plinth 75	£ p	12 87	8 90
GOLDRING Plinth 72	£ p	11 22	7 80
GOLDRING Covers for 72P	£ p	4 62	3 20
Cover for 75P De Luxe	£ p	5 28	3 64
Cover for 78P	£ p	7 26	5 00
Cover for 85P	£ p	9 35	6 50
McDONALD Plinth for 710/810	£ p	4 40	2 95
McDONALD Cover for 710/810	£ p	8 25	6 40
THORENS TX 25 (for TD125AB)	£ p	4 18	3 40
THORENS TX11 Cover	£ p	4 18	3 40
SME Plinth System 2000 with motor-board	£ p	43 56	34 95
SME P1 Spacer	£ p	5 51	4 00
MOTORBOARDS only	£ p	0 92	0 70
HEADPHONES			
AKG K180	£ p	30 80	18 50
AKG K60	£ p	16 50	9 75
AKG 100	£ p	8 80	5 40
AMSTRAD HPSSA	£ p	8 25	3 35
HPSSA with volume control	£ p	11 77	7 95
KOSS HVI	£ p	22 00	16 95
KOSS ESP-9 Electrostatic	£ p	75 90	58 25
KOSS ESP-6 Electrostatic	£ p	49 50	38 50
KOSS K2 plus 2 Quadrafone	£ p	49 50	38 95
KOSS PRO 5 L/C	£ p	33 00	26 50
KOSS PRO-4A	£ p	30 80	26 95
KOSS KO-727B	£ p	18 15	13 75
KOSS 747	£ p	22 00	16 50
KOSS K-711	£ p	11 00	7 95
KOSS K6	£ p	13 75	10 25
KOSS K6/LC (with volume control)	£ p	15 40	11 50
KOSS K6/LC Quadrafone	£ p	22 00	16 50
PIONEER SE 50	£ p	26 02	17 95

	Rec. Price	Retail Price	Comet Price
HEADPHONES—continued			
PIONEER SE 30A	£ p	15 02	10 25
PIONEER SE 20A	£ p	9 37	6 40
PIONEER SEL 20	£ p	12 52	8 50
PIONEER SEL 40	£ p	20 71	14 25
SOUND MD806	£ p	7 15	3 10
WHARFEDALE DDI	£ p	13 75	9 75
WHARFEDALE Isodynamic	£ p	21 95	16 50
HI-FI STEREO SYSTEMS—COMPLETE			
ALBA 852	£ p	37 87	27 95
BUSH A1005	£ p	66 25	47 95
BUSH 1006 with radio	£ p	89 06	64 95
DANSETTE 4010	£ p	58 25	39 95
DANSETTE 4005	£ p	67 73	44 95
DANSETTE 4020	£ p	45 50	32 95
DECCA SOUND 613	£ p	53 95	47 95
DECCA COMPACT 2 with radio	£ p	98 03	72 95
DECCA COMPACT 3 with radio	£ p	127 09	99 95
DECCA 403	£ p	54 45	42 95
FERGUSON 3450 B with Radio (new Model)	£ p	75 40	55 50
FERGUSON 3451 B with Radio (new Model)	£ p	101 50	79 95
FERGUSON 3454	£ p	39 36	28 50
FIDELITY UA1 Music Master with Radio	£ p	94 81	67 95
FIDELITY UA2 Music Master	£ p	41 23	27 95
FIDELITY UA3 incl. stereo radio	£ p	59 73	41 95
FIDELITY Stereo Nine	Sp. Price	22 95	22 95
G.E.C. 1810	£ p	74 89	56 95
GROSVENOR MPX 8400 AM/FM/MPX Tuner/Amplifier, magnetic input, built-in 8-track cartridge player with speakers	£ p	65 75	33 95
HMV 2451	£ p	115 70	89 95
HMV 2452	£ p	62 57	43 95
HMV 2453	£ p	165 90	119 00
I.T.T. KB1025 with 662 speakers	£ p	45 65	35 95
I.T.T. KB2250 with 659 speakers and radio	£ p	136 83	105 95
MURPHY 920	£ p	45 50	35 95
MURPHY 940	£ p	56 25	45 95
PHILIPS 808	£ p	99 53	71 95
PHILIPS 825	£ p	46 92	33 50
PHILIPS 826	£ p	71 09	45 95
PHILIPS 835 with radio	£ p	65 88	46 50
PHILIPS 836 with radio	£ p	90 05	62 95
ULTRA 6027	£ p	54 55	39 50
ULTRA 6028	£ p	56 85	41 50
ULTRA 6450 B (new model) with radio	£ p	75 40	58 95
ULTRA 6451	£ p	75 40	54 95
ULTRA 6454	£ p	36 80	25 95
ULTRA 6455	£ p	39 20	29 95
TAPE RECORDERS			
AKAI 1721L	£ p	93 87	66 95
AKAI 4000 DS	£ p	93 50	68 95
AKAI X201D	£ p	168 30	123 95
AKAI X1810	£ p	215 18	159 95
AKAI GX221D	£ p	215 18	159 95
AKAI GX1900D	£ p	224 57	166 95
AKAI GX370D	£ p	328 95	244 95
AKAI CR80D 8-track stereo tape deck	£ p	79 90	53 95
AKAI CR80 8-track stereo recorder	£ p	117 02	66 95
AKAI CR80DSS Quadrafonic	£ p	149 88	103 00
AKAI CR30T 8-track stereo recorder and tuner amplifier	£ p	140 78	84 95
AKAI CR81T 8-track cartridge stereo recorder and tuner/amplifier	£ p	145 65	102 00
AKAI CR81	£ p	102 89	71 95
AKAI CR81D	£ p	84 10	58 95
FERGUSON 3258 4-track	£ p	66 85	45 50
FERROGRAPH 702/704 Dolby	£ p	287 30	226 95
FERROGRAPH 702H Dolby	£ p	278 30	235 95
FERROGRAPH 722/724 Dolby	£ p	305 80	258 95
FERROGRAPH 722H Dolby	£ p	316 80	268 95

	Rec. Price	Retail Price	Comet Price
TAPE RECORDERS—continued			
FERROGRAPH 702/704	£ p	220 00	167 95
FERROGRAPH 722/724	£ p	258 50	194 95
FIDELITY Braemar 4-track	£ p	32 64	18 50
GROSVENOR 900 8-track recorder, play-back deck	£ p	51 15	36 95
GRUNDIG TK 121 (twin-track)	£ p	52 95	38 95
GRUNDIG TK 141 (4-track)	£ p	58 47	43 95
GRUNDIG TK 147 (4-track auto)	£ p	92 87	72 95
GRUNDIG TK 148 (4-track auto 2 speed)	£ p	69 76	53 95
GRUNDIG TK 246 4-track stereo deck	£ p	126 78	94 95
GRUNDIG TK 3200 Hi-Fi (Battery)	£ p	135 15	99 95
MARCONI 4248 4-track, 2 speed	£ p	49 66	35 95
PHILIPS 4416 4-track stereo recorder	£ p	137 45	99 95
PHILIPS 4418 4-track stereo	£ p	189 59	137 95
TANDBERG 3321X 2-track stereo deck (Teak)	£ p	137 38	114 95
TANDBERG 3341X 4-track stereo deck	£ p	137 38	114 95
TANDBERG 6041X 4-track stereo	£ p	187 62	153 95
TANDBERG 9021X 2-track stereo deck	£ p	236 00	198 95
TANDBERG 9041X 4-track stereo deck	£ p	236 00	198 95
TANDBERG GRENVILLE TD1458-track player deck	£ p	20 28	13 50
TAPE RECORDERS (CASSETTE)			
AKAI CS35D tape deck	£ p	75 13	48 95
AKAI CS35 Stereo incl. Speakers	£ p	105 71	77 95
AKAI GXC 40D tape deck	£ p	89 74	62 95
AKAI GXC 40	£ p	105 71	73 95
AKAI GXC 40T recorder, tuner/amplifier	£ p	157 40	109 00
AKAI GXC 45D tape deck	£ p	112 28	83 95
AKAI GXC 46 Dolby tape recorder	£ p	143 30	98 95
AKAI GXC 46D Dolby tape deck	£ p	131 09	91 95
AKAI GXC 65D Dolby auto-reverse deck	£ p	145 18	101 95
BUSH ARENA C440	£ p	58 11	46 95
BUSH Discassette DC70	£ p	19 55	11 95
BUSH TP 66 Battery/Mains	£ p	26 70	18 95
BUSH RTP 100 Radio/Cassette Recorder	£ p	41 66	29 50
DECCA 2000	£ p	27 29	21 50
FERGUSON 3253 (mains)	£ p	41 15	26 95
FERGUSON 3258 (mains)	£ p	36 61	23 95
FERGUSON 3257	£ p	53 45	37 95
FERGUSON 3257/7 speakers for above	£ p	15 20	10 95
GEC CR200 AM/FM Cassette/Radio, Battery/Mains with slide controls	Sp. Price	34 95	34 95
GRUNDIG C210 Battery/Mains	£ p	46 00	32 95
GRUNDIG C250	£ p	60 65	46 95
HANIMEX 3030 cassette batt/mains with AM/FM radio	£ p	43 65	19 95
HARVARD Elite Cassette/AM/FM Radio (battery/mains)	Sp. Price	22 95	22 95
I.T.T. KB SL53	£ p	31 00	23 95
I.T.T. KB SL75 with VHF/LW/MW radio	£ p	48 95	39 50
I.T.T. KB Studio 60	£ p	38 95	30 75
JVC Nivico 9420 LS with AM/FM radio, battery/mains	£ p	57 84	39 95
JVC Nivico 1710 Radio/Cassette, AM/FM	Sp. Price	37 95	37 95
PHILIPS RR 322 AM/FM Radio/Cassette Recorder Batt/Mains	£ p	43 36	32 95
PHILIPS 2202/2203	£ p	22 59	16 95
PHILIPS 2204 battery/mains	£ p	28 25	20 95
PHILIPS 2211, with built-in microphone	£ p	27 30	20 95
PHILIPS 2405 Stereo with 2 RH401L/S	£ p	67 78	50 95
PHILIPS 3302	£ p	20 24	13 95
PYE 9116 Stereo	£ p	65 80	47 95
PYE 9140	£ p	20 24	14 50
WHARFEDALE Dolby DC9 Mk. II	£ p	111 41	82 50

FREE Technical Advisory Service. If in doubt ask us! Price list on request.
 Comet guarantees that all prices quoted are genuine. All offers subject to availability. Make cheques, Money Orders payable to "COMET".
ORDERING INSTRUCTIONS: cartridges—add 22p for postage, packing and insurance, all other goods sent via Securicor Delivery—add £2.15 to each complete order for Securicor Delivery.

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

- BIRMINGHAM:** Heeley Road, Selly Oak, B29 6EY
- BIRMINGHAM:** Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley B26 1BJ
- EDINBURGH:** 1 Newhaven Road, EH6 5QZ
- GLASGOW:** Blythswood Trading Estate, Argyle Avenue, Renfrew, RA4 9EL
- GRIMSBY:** 389 Victoria Street, DN31 1ER
- HULL:** 56/64 Ellison Street, Jarrow NE32 3MT
- JARROW:** 78 Armitage Road, LS12 2FF
- LEEDS:** Syston Street
- LEICESTER:** Rainham Road South, Dagenham, RM10 8ST
- LONDON, Dagenham:** 190 London Road, Hackbridge, Wallington, Surrey
- LONDON, Hackbridge:** (Mr. Croxford)
- LONDON, Hayes:** Silverdale Road, Pump Lane, Hayes
- LONDON, Rochester:** Maidstone Road, Rochester
- NORWICH:** Roundtree Way, Norwich NR9 4P
- NOTTINGHAM:** 121, Town Street, Sandiacre, Nottingham NG10 5DW
- READING:** Monarch House, 75-81 Caversham Rd., Reading RG1 8AP
- ROCHDALE:** Corner of Well 1th Lane and Queensway
- SHEFFIELD:** The Mill, 1 Loxley Road, Malin Bridge, S6 4TN
- SOUTHAMPTON:** Chickenhall Lane, Eastleigh SO5 5ZQ
- STOCKTON:** Teesway, Portrack Lane, Teesside, TS18 2RH
- SUNDERLAND:** 4-7 St. Thomas Street, Sunderland, SR1 1HR
- WIGAN:** Wharf Mill, Princess Street, WN3 4EZ

- Tel: 021-472 6181
- Tel: 021-708 0684
- Tel: 031-554 4454 (9 lines)
- Tel: 041-886 5731
- Tel: 0472 59623
- Tel: 0482 46441 (6 lines)
- Tel: 0632 892211
- Tel: 0532 40551
- Tel: 0533 52236
- Tel: 01-595 5111
- Tel: 01-669 0271/0106
- Tel: 01-643 8989
- Tel: 01-573 1841
- Tel: 0532 40551
- Tel: 0603 411831
- Tel: Sandiacre 6116
- Tel: 0734 599911
- Tel: 50606
- Tel: 0742 341721/6
- Tel: 4722
- Tel: 66132/65215
- Tel: Sunderland 59993
- Tel: 0942 34741



TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88-108Mcs, with circuit diagram. £2.30p.

PINNACLE LOW NOISE CASSETTES C60-50p/C90-75p C120-£1.

P-C BOARDS (not computer panels)

1 off 6 transistors single wave band

1 off 4 transistor audio

1 off 3 transistor £1.60 the three.

Encapsulated bridge rectifier (itt usd 3 3mdh) 100 PIV 2 amps. 50p each, 3 for £1.35.

Transistor F.M. Stereo Multiplex Decoder. Size: $5\frac{1}{4} \times 2\frac{1}{4} \times 1\frac{1}{4}$. As used in well known British stereo units with circuit. £3.75.

GARRARD SP25 MK. II less Cartridge. £10.00.

10 VOLUME CONTROLS consisting of 2 off each.

100K log. ganged L/S-20K log. ganged L/S.

470K log. D/P Switch-10K lin. L/S-50K lin. L/S. £1.35.

4 PHONO SOCKETS ON PANEL. 10 panels for £1.25.

12 PLASTIC KNOBS. Chrome and Gold, 3 types-4 off each -spring clip £1.25.

10 COMPUTER PANELS packed with components including one panel with 2 Power Transistors. £1.00.

SLIDER CONTROLS (less knobs)

25K Log of Lin single 30p.

10K-100K Log ganged 50p.

100K-100K Log ganged 50p.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 30p each 4 for £1.00.

CRYSTAL CALIBRATOR No. 10 crystal controlled heterodyne wave-meter covering 500 KHz-10MHz (harmonics up to 30MHz) power required 300V. DC. 15mA. 12V. 0.3A DC. Test equipment for 62T M/R.C. £2.50 each.

ALL ITEMS INCLUDE VAT


All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

PHOTOELECTRIC KIT

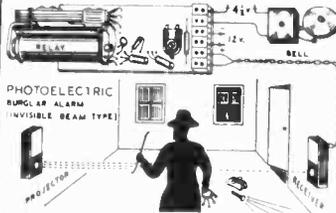CONTENTS. P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



PHOTOELECTRIC KIT
£2.85

Postage and Pack. 15p (U.K.)
Commonwealth

SURFACE MAIL 25p

AIR MAIL £1.40

Australia, New Zealand,
S. Africa, Canada and U.S.A.

Also Essential Data Circuits
and Plans for Building
10 advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms. Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-Red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1.45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Large Lenses, Filter, etc. Price £2.10. Postage 15p (U.K.) Commonwealth: Surface 20p, Air Mail £1.15.

BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.

CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4.75 postage and pack. 25p (U.K.). Commonwealth: Surface 30p, Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT


Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.

CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3.25, postage and pack. 16p (U.K.) Commonwealth: Surface 25p, Air Mail 75p.

YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

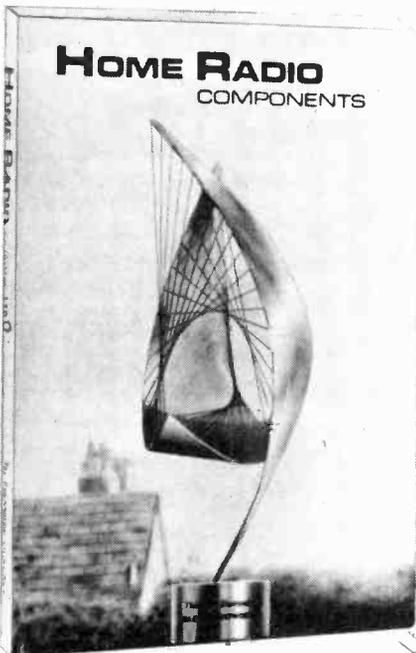Send S.A.E. for full details, a brief description of all Kits and Projects.



HOME RADIO
COMPONENTS

250 pages 11 $\frac{1}{4}$ " x 8 $\frac{3}{4}$ "

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

Only 55p.

plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Name _____

Address _____



HOME RADIO (Components) LTD. Regd. No. 912966 London Dept. PW, 234-240 London Road, Mitcham CR4 3HD

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS.
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors Now Available. To meet demand, we have included a more powerful module in our well-established and proven range. These power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



SA35 35 watts RMS. Uses 7 transistors and 7 diodes Carr. paid. **£4-45**

A NEW ADDITION IS THE SA50 at £5-65

Carr. paid. A rugged, well built unit, capable of 50 watts R.M.S. out, with all the advantages of Saxon Amplifier design and quality. Ready now.

SA100 makes an ideal unit in disco assemblies. A real glutton for work. **£10-90**

Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid.

BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA100.

Freq. response	15-40,000 Hz ± 1dB
Distortion	0-2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	SA35 25-45 volts SA50/SA100 40-70 volts
Size	4 1/2" x 4" x 1" (SA100) 4" x 3" x 1" (SA35/SA50)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilized supply for 2 SA25/35	£4-90
PU70	Unstabilized supply for one or two SA100	£7-75 carr. 40p
PS45	Stabilized module for 2 SA25's or two SA35's	£3-50 carr. free
MT45	Transformer for above, heavy duty	£2-85 carr. 20p
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3-50 carr. 20p
PS70	Stabilized supply module for one or two SA100's	£4-90 carr. free
MT70	Transformer for PS70	£4-90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

TWO NEW PA/MIXER CONTROL UNITS

Using grouped pairs of inputs and outputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master control. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos etc. Standard jack sockets. Compact design. In strong metal cases. All units guaranteed for 3 years.

●M.4H

4 high Z, 4 low Z inputs, 4 sets of controls. Case 14" x 8" x 2 1/2" Carr. pd.

£18-50 + V.A.T.

●M.6HL Case 18" x 8" x 2 1/2"

12 inputs (6 high Z, 6 low Z). Carr. pd.

£27-50 + V.A.T.

● Channel section modules, for building your own mixer. Gain—16 x (24dB). Tone controls—18dB swing. Carr. pd. £3-50 + V.A.T.

SAXON CONTROL UNITS

Mono (as shown)

Carr. 20p. **£6-50**

Stereo. Carr. 30p.

£15-80



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic Input.)



120 WATT HEAVY DUTY MODULE

Rugged class A driver stage, this module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors. These are the modules where extra power is demanded.

Power output 120 watts into 8 ohms Module only **£13-90**
Freq. response 20-20,000 Hz ± 2dB (Carr. 20p)

Input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply) Module & power supply **£18-95**

Low distortion parallel push-pull output stage. (Carr. 40p)

160 watt version with power supply (Carr. 50p) **£27-50**

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3KW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3KW lighting load. Smartly finished steel case. Carr. 30p. **£19-75**


SINGLE CHANNEL UNIT

Operates from 5 to 100 watt amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£8-90**

COMPLETE AMPLIFIERS

CSE 100. £34-90 carr. free

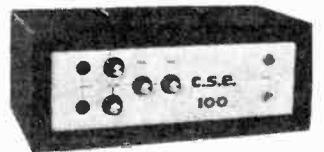This versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls.



SAXON 100 £48-50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5-95 carr. 30p. 15" 50 watt 8/15 ohm £14-50 carr. 50p. 12" 40 watt 15,000 gauss magnet system 8/15 ohm £11-50 carr. 40p.

600 Watt 3 colour Light Boxes Smart Rexine finish £15 carr. free.

A.K.G. MICROPHONES

D11 DHL IDEAL DISCO MIKE ONLY £9-45 (rrp £11-00).

Prices quoted do NOT include V.A.T. 10% must be added on to total value of order for V.A.T. S.A.E. for special price list.

Orders and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.

Telephone 01-684 6385

Hours 9.30 a.m.—5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED

TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by regd. letter, please

THE SMALL PRINT

AT some time or other, in hire purchase agreements, forms of guarantee, or simple purchases, most people encounter a moment of uncertainty and often wonder if the forms are really worth the paper they are printed on. What are the buyer's rights under signed guarantees or the Supply of Goods Act?

To go some way to tidying up the situation the "Supply of Goods (Implied Terms) Act 1973" has been introduced. The purpose is to make it a criminal offence to use misleading or invalid guarantees or exclusion clauses in any contract or guarantee, including hire purchase, credit sales and cash sales. Goods must compulsorily correspond with their descriptions, whether in advertisements or on the package, be of merchantable quality and "fit for the purpose intended". The phrase in quotes is often a disputable factor and does not sufficiently define how it is to be applied to technical products. If the magistrate is presumably the deciding authority in the event of such a case being brought to court, he will need authoritative technical advisors to sort this one out, but it is very common for suppliers to exercise their initiative in offering substitute components if the requested item is not currently available. These often serve to enable a project to be made operational but will not necessarily guarantee the optimum performance as achieved with quoted component types. It can be found that faulty conditions occur in a circuit which can cause chain reaction damage to other components. If standard or substitute components are used, one takes this risk, but the constructor has no redress on the supplier unless the supplier has stated that the substitute component is suitable for that project.

The act stipulates that where redress is justified, the onus is on the seller, usually the retailer. The manufacturer is only responsible for supplying the seller with products that correspond with their trade descriptions. If such a description is inadequate then it is the responsibility of the purchaser to satisfy himself that the goods are what he wants.

Exclusion clauses are made void but not illegal, so that customers should not be led to think that his rights are adversely influenced by such statements. Guarantees should now make clear to the consumer that *additional* rights are being given; no guarantee that offers less than the implied rights of the Supply of Goods Act will be valid.

M. A. COLWELL—*Editor.*

The September issue, on sale 3rd August, will be the first of our special series of Autumn issues. Special attractions include the very easy-to-make two-i.c. radio that uses a choice of popular speakers from 8 to 16 ohms, and only a handful of other components; no complicated alignment is needed. Also featured will be a multi-purpose low voltage power regulator and a short-wave converter for insertion between aerial and receiver to convert signals in the short-wave bands into one fixed frequency of 1600kHz or 190 metres on the MW band. Also in the September issue there will be a special announcement on Q4 and other extra attractions for Issue Number 800.

Further details on page 335.

NEWS...

Practical Wireless and Television in Berlin

FOR the first time *Practical Wireless* and *Television* will be taking part in an overseas exhibition at the end of August. The "International Radio and TV Exhibition," to be held in Berlin August 31 to September 9, is one of the largest commercial and public exhibitions of its kind. Of special significance is the celebration of 50 years since the first German radio station began transmitting officially in the former Reich capital.

This will be the 29th national and second international exhibition organised by the "Division Radio and Television" in the German Electrical and Electronic Manufacturer's Association (ZVEI).

There will be 88,000 sq metres of space in 23 halls and 4 pavilions, as well as 40,000 sq metres of open-air grounds. The truly international flavour is due to participation by 20 countries including Hong Kong, South Korea, China, Norway, U.S.A. and several European countries.

Displays will embrace all aspects of electronic home entertainment systems including associated equipment for servicing, studios and transmission installations. Programmes will also be transmitted from a 2,100 seat hall that will be converted into a television studio.

Practical Wireless and *Television* magazines will participate in the Technical Press section and visitors will be able to see much of the recent work that these two magazines have published as well as some new ideas for the autumn.

We cannot possibly tell you everything about this gigantic operation in just a few lines but we hope to be able to publish much of the exciting events that will take place in a future issue. So if you are around West Germany about that time we cordially recommend a visit to this show.

Texas Instruments Seminar

TEXAS Instruments Ltd. held their successful Interface 73 technical seminar at the Talk of the Town, London on June 12, 13 and 14.

Richard Mann of "Texan" amplifier fame introduced delegates to the programme. Bob Spoene-man, Marketing Manager (Northern European Semiconductor Div.) then gave a short talk entitled "Market Overview."

A lecture on the TTL system followed and Mick Mimmack and Bob Parsons reviewed new TTL products especially the range of low power Schottky devices.

The next talk was given by Roger Banks, Senior Product Marketing Engineer for military ICs, who spoke on Beam Lead ICs.

Adrian Tarr, Product Marketing Engineer for Metal Can Power Products and Bryan Norris, Applications and Contracts Manager lectured on Power Devices and discussed practical applications of Plastic Power, and High Voltage Transistors, SCRs and Triacs.

A lecture on Optoelectronics followed. This was presented by Millis Miller, a specialist in optoelectronics who also gave a demonstration of solid state targets for low light level TV applications.

Lunch followed at 13.05 and when delegates had finished their steak and tutti fruttii, the lectures continued.

All delegates were presented with a data pack which comprised:

Semiconductor Circuit Design vol. 2. over 200 pages hard bound.

A totally new TTL Data Book providing comprehensive coverage of Texas Instruments 5 families of 54/74 TTL ICs. 640 pages hard bound.

A Seminar Data wallet containing a selection of the very latest product information, together with a book reproducing all the Seminar Slides.



Delegates being presented with data packs, by Mrs Gina Penman.

BSR Award

BSR Limited of Warley, the manufacturer of record changers has received an award for the 810 transcription turntable.

The "Component Design Award" presentation was made recently at a conference held at the Excelsior Hotel, Birmingham Airport. Viscount Caldecote, Chairman of the Design Council presented the Design Award Certificate to Mr. G. R. Woolbridge, Director of BSR Limited.

BSR introduced the 810 transcription turntable into the range of Hi-Fi record changers in late 1971. Its pre-programmed sequential cam system introduces a new experience in featherlight push-button operation.

Logic design for Digital systems

A one week residential Vacation School intended for practising engineers scientists and teachers, who need have no previous knowledge of, but are interested in the fundamentals of logic circuit design is being organised by the Electronics Division of the Institution of Electrical Engineers. The School "Logic design—for digital systems" is intended to give an appreciation of both formal techniques and their application in practice and will be held at the University of Kent at Canterbury from 23-28 September 1973.

Lectures will cover the following subjects: historical and mathematical background; design of memoryless (combinational) circuits; design of circuits with memory (sequential); introduction to automata theory; microcircuit logic; array networks; complete design of a system; CAD techniques; testing and diagnostics; and recent advances in logic design.

Further details are available from *Senior Divisional Secretary (Electronics)*, IEE, Savoy Place, London, WC2R 0BL.

Northern Hi-Fi

THE Northern International Hi-Fi Festival, called "Audio 73" will be held at the Hotel Majestic, Harrogate, from August 31 to September 2.

Mobile rally diary

August 19—The Bristol "Mobile Picnic" will be held at Ashton Court, Bristol.

August 19—Preston Amateur Radio Society will be holding their rally at Kimberley Barracks, Deepdale Road, Preston, Lancs. There will be a free car park, trade stalls, bring-and-buy stalls and refreshments. Talk-in stations will be operating on Top Band and 2m. All the gen from G. W. Earnshaw, G3ZXC, 12 Withy Parade, Fulwood, Peston, Lancashire, PR2 4JN.

August 26—The Town and Country Festival Mobile Rally will be held at the National Agricultural Centre, Kenilworth, Warwickshire.

MINI-COMM

RECEIVER

F.G. RAYER

You do not have to leave this receiver behind when going camping, caravanning, or when pressed for space, as it is small in size, with internal battery and loudspeaker. Despite this, it has a very good performance for the reception of AM, CW and SSB on the short wave bands, in addition to normal medium wave reception.

CIRCUIT

Fig. 1 is the complete circuit, except for the BFO which is necessary for receiving CW and SSB. As this section is not required for general listening it is wired as a separate unit.

Sockets A1 and A2 are alternative aerial input points. A1 is most suitable for a reasonably long wire aerial, while A2 is better for a telescopic rod or short aerial. The "Blue" aerial coil is tuned by its own 365pF variable capacitor VC1, so that it can always be peaked up for best results with any aerial, no separate trimming being needed with this arrangement.

Tr1 is the OC170 RF amplifier, with the RF gain control VR1. The "Yellow" mixer coil is tuned by VC2, which is one section of a 2-gang tuning capacitor. The panel trimmer VC4 allows this circuit to be trimmed when coils are changed, or at any point of the band covered.

The "Red" oscillator coil is tuned by the second section of the ganged capacitor, VC3. VC5 is the bandspreading capacitor, which greatly simplifies

accurate tuning on the congested SW bands. A 3-gang component, giving simultaneous tuning of aerial, mixer and oscillator circuits could have been used, but was felt to be unnecessary because aerial and mixer circuits can be peaked up for any setting of VC5, by means of VC1 and VC4, if necessary. There is thus no loss of efficiency with this simplified arrangement—in fact, all circuits can be tuned for best results at any frequency.

Bands are covered by inserting a set of three coils for each waveband. Provision is made for four wavebands. The "Red" oscillator coils require series padders of 350pF, 1000pF (or 1100pF) and 3000pF for the lower frequency ranges, and a direct connection for the highest frequency range. These padders, CP1, CP2 and CP3 are wired to separate holder tags

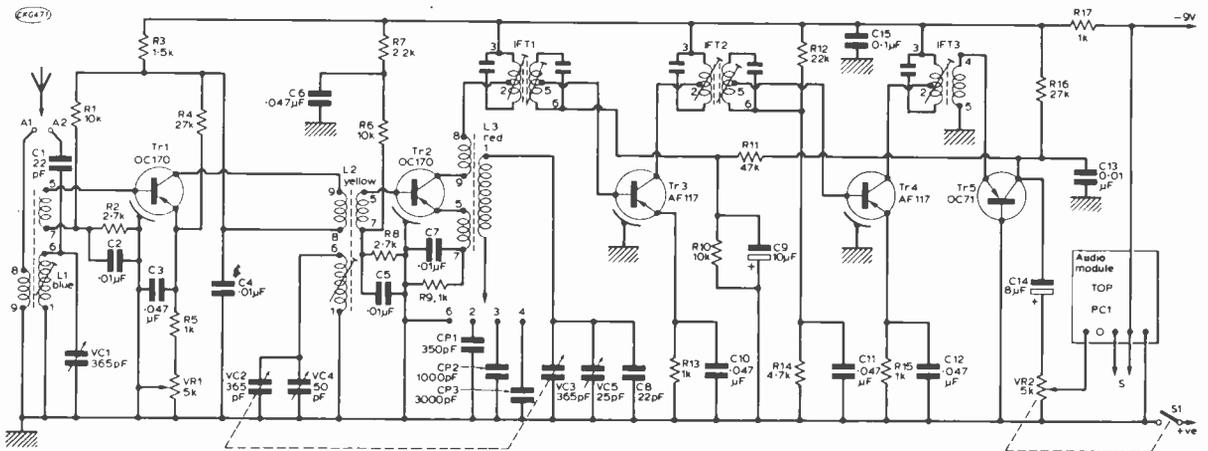


Fig. 1: Circuit of the Mini-Comm receiver. The circuit of the optional BFO is shown in Fig. 6. The photograph above shows the complete receiver, the speaker being mounted on the righthand side panel.

as in Fig. 1, so the correct padder is automatically included in circuit when the "Red" coils are changed.

The 2-stage IF amplifier has five tuned circuits in all, and although more complicated amplifiers were tried, this one was adopted on the grounds of easy construction, good gain and selectivity. Transistor Tr5 is a grounded base emitter detector with AGC fed from the collector through R11 to Tr3.

A 150mW packaged audio amplifier is fed from the volume control VR2 and gives sufficient output for most circumstances using the small internal speaker. A panel jack allows headphones to be plugged in when preferred.

Using the circuit in Fig. 1, the receiver gives AM reception over all usual short wave and medium wave bands. For the reception of CW and SSB signals on amateur or other frequencies a beat frequency oscillator has to be added, and this is covered later. Should CW/SSB reception be omitted, two panel holes for the BFO "pitch" capacitor and AM-CW/SSB switch will not be necessary.

Capacitor VC1 is mounted with three countersunk 4BA bolts, washers and spacers about $\frac{1}{8}$ in. thick being placed between the capacitor and panel, the spindle passing through a $\frac{3}{8}$ in. or $\frac{1}{2}$ in. dia. clearance hole. Take care that the bolts do not penetrate beyond the thickness of the capacitor front frame. Before mounting VC1, solder a lead to its rotor (chassis) tag, to go to a tag MC bolted at the "Blue" coil holder as in Fig. 2.

Gang VC2/3 is mounted in the same way and two leads are soldered to its central rotor tag. One runs directly to a tag at the "Yellow" coil holder and the other to a tag at the "Red" coil holder. The small drive used for VC5 is fixed to the panel with two 8BA bolts while VC5 itself is fixed to a bracket cut from scrap. Drive and capacitor should be lined up carefully.

The controls are positioned as in Fig. 3. As mentioned, S2 and VC6 will be required for the BFO only so if these items are not wanted VR1 can be moved to the VC6 position, for a symmetrical layout.

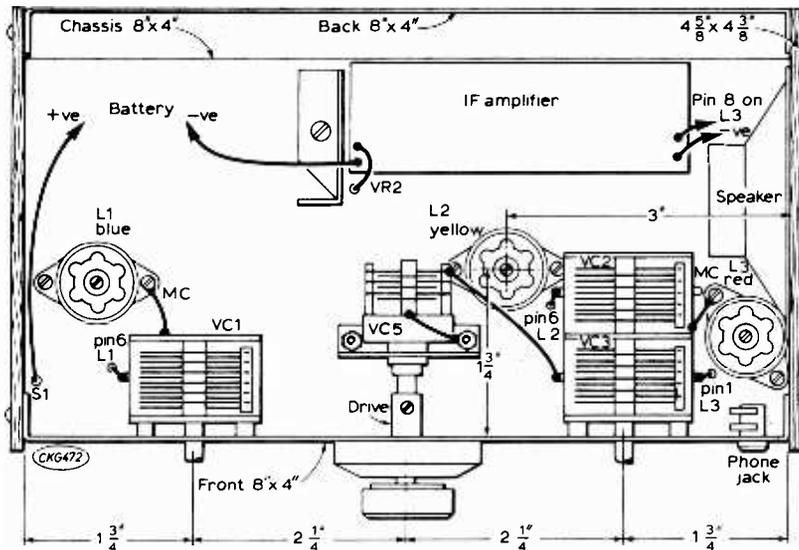


Fig. 2: Layout of the major components on top of the chassis.

GENERAL CONSTRUCTION

The receiver chassis is an 8 x 4in. "universal chassis" flanged member punched to take the coil-holders as in Fig. 2. A second 8 x 4in. flanged member forms the panel. The end flanges of the chassis member are cut so that they fit inside the flanges of the panel and bolts pass through the front flange to secure the chassis at a height of $1\frac{1}{4}$ in.

Both sides are $\frac{1}{8}$ in. or similar hardboard, $4\frac{5}{8}$ x $4\frac{5}{8}$ in. Bolts hold the sides to the chassis and panel flanges. The right side has an aperture for the speaker with perforated zinc or speaker material placed behind the opening. It is as well to leave the speaker off until construction is otherwise finished.

The case back is a third 8 x 4in. member. A bracket is cut from scrap or a spare member so that a PP9 battery can be placed as shown. Both top and bottom are 8 x $4\frac{1}{2}$ in. and can be metal or other material such as hardboard, paxolin sheet, or plywood. Self-tapping screws hold these parts to the front and back flanges.

As there is not much spare space under the chassis, the panel holes for these items come almost against the front flange of the chassis. In order that the controls are not tilted by this, it is necessary to fit one or more washers on each bush and to cut the flange to clear these. Alternatively, use five washers such as those punched out for the coil holders and cut a flat on each to clear the chassis flange.

Most of the wiring in Figs. 2 and 3 can then be done, mounting resistors and capacitors directly on the coil holder tags, as shown. Some 20 or 22swg tinned copper wire is suitable for other connections, with insulated sleeving.

The leads from Tr1 and Tr2 are left almost full length. It may be preferred to use coloured sleeving on the wires say green for emitter, blue for base, and orange for collector, with the shield wire bare or red.

The small circuit board in Fig. 3 carries the components shown in Fig. 4 and is wired separately. For external connections, insert Veropins or leave a projecting wire.

★ components list

Resistors

R1 10k Ω	RB 2.7k Ω	R15 1k Ω
R2 2.7k Ω	R9 1k Ω	R16 27k Ω
R3 1.5k Ω	R10 10k Ω	R17 1k Ω
R4 27k Ω	R11 47k Ω	R18 1k Ω
R5 1k Ω	R12 22k Ω	R19 22k Ω
R6 10k Ω	R13 1k Ω	R20 4.7k Ω
R7 2.2k Ω	R14 4.7k Ω	R21 390 Ω

All 10% $\frac{1}{4}$ watt

VR1 5k Ω linear VR2/S1 5k Ω log. with switch

Capacitors

C1 22pF SM	C12 0.047 μ F
C2 0.01 μ F	C13 0.01 μ F
C3 0.047 μ F	C14 8 μ F 6V W
C4 0.01 μ F	C15 0.1 μ F
C5 0.01 μ F	C16 0.1 μ F
C6 0.047 μ F	C17 0.01 μ F
C7 0.01 μ F	C18 0.01 μ F
C8 22pF SM	C19 5pF SM
C9 10 μ F 6V W	CP1 350pF SM
C10 0.047 μ F	CP2 1000pF SM
C11 0.047 μ F	CP3 3000pF SM

VC1 365pF variable (Jackson type O with slow motion drive)
 VC2/3 365 + 365pF variable (Jackson type O with slow motion drive)
 VC4 50pF variable (Jackson type C804)
 VC5 25pF variable (Jackson type C804)
 VC6 15pF variable (Jackson type C804)

Semiconductors

Tr1 OC170	Tr3 AF117	Tr5 OC71
Tr2 OC170	Tr4 AF117	Tr6 OC45

D1 Zener diode 6.8V

Miscellaneous

L1/2/3, Transistor miniature plug-in-coils, 'Blue', 'Yellow' and 'Red' for ranges required (Denco). L4, BFO coil (Denco IFT14). Valveholders B9A for coils (3). Audio module, PC1 (Newmarket). Slow motion dial $1\frac{1}{2}$ in. (Eagle). Output jack. AM-CW/SSB switch, 2 pole 2-way wafer. Speaker, $2\frac{1}{2}$ in. 30-60 Ω . Veroboard 0.15in. matrix. Universal flanged chassis members, 8 x 4in. (Home Radio). Hard-board, knobs, etc. IFT1/IFT2 (Denco IFT18/465). IFT3, (Denco IFT14/465).

A $1\frac{1}{2}$ in. 6BA bolt is fixed to the chassis in the position shown in Fig. 3 and an extra nut put on it, so that the board will be clear of the metal. The board is then placed as in Fig. 3, and fixed with a further nut.

The tag MC (Fig. 4) under the board is the chassis return.

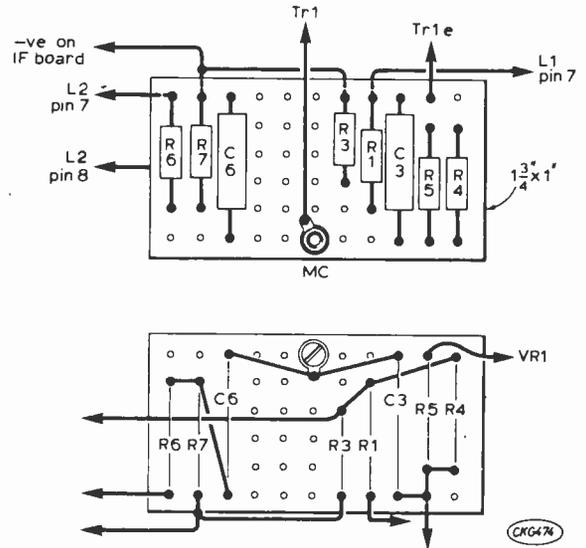



Fig. 4: Layout of the RF board.

IF AMPLIFIER

A piece of Veroboard is cut having 7 rows of holes one way, and 23 rows the other way, or $3\frac{1}{2}$ x $1\frac{1}{8}$ in. Components and leads can then be placed exactly as in Fig. 5 with the minimum of difficulty.

Drill holes for 6BA bolts to fix tags MC, place the board on the chassis as in Fig. 2, and drill matching holes in the chassis. Holes have to be drilled for the IFT's so that the pins are located as in Fig. 5. Probably the easiest method is to secure the board by one long edge in a vice and drill the holes, then if some do not match the pins with sufficient

Fig. 3: Arrangement of parts and wiring underneath the receiver. Top centre is seen the audio module and to its right the BFO board. The board at centre right carries some of the RF components and wiring.

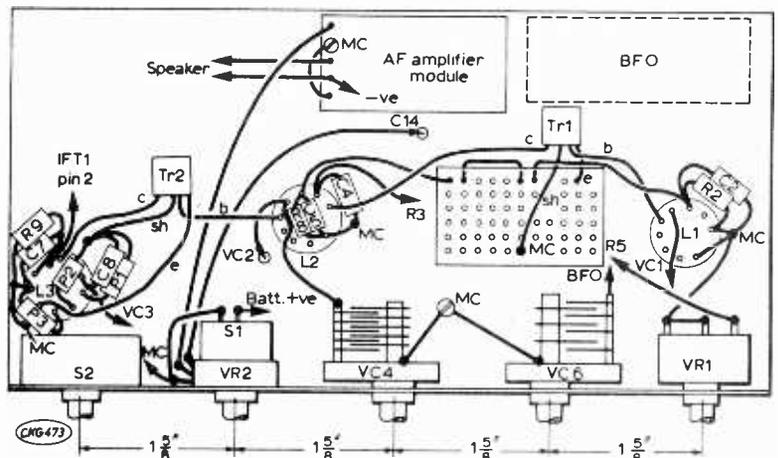

accuracy, to use a very small round file to enlarge the holes until the IFT's fit. A central hole is necessary under IFT1 and IFT2 to reach the lower cores.

Components can then be placed as in Fig. 5. In most places the wire ends of resistors and capacitors are long enough, so they are bent over, soldered and snipped off. Sleeving is put where needed to avoid shorts. The tags MC are secured tightly with $\frac{1}{2}$ in. 6BA bolts and nuts and one screening can tag of each IFT must also be wired to this earth circuit.

Fit four Veropins or wires as shown. At the right-hand end of the board "9V negative" has a black flexible lead and negative battery clip. A lead from C14 positive will run to VR2, as shown. At the other end of the board, IFT1 pin 2 will be connected to tag 8 of the "Red" coil holder. A wire from the

pin "negative for RF and mixer" will run to R3 and R7 on the under-chassis board.

Pieces of sleeving about $\frac{3}{8}$ in. long on the transistor wires will prevent shorts here and raise them a little above the board. Solder these wires directly to the points in Fig. 5 and snip off excess wire.

The IF amplifier can be tested by connecting a battery and phones (or AF amplifier) and injecting a signal at pin 2 of IFT1 from a signal generator. As the IFT's are pre-aligned by the maker, the cores should be left as they are until proper results are obtained, and only touched up as required afterwards.

The IF amplifier is mounted with lock nuts, making sure that there is no possibility that leads or joints will touch the chassis. Leads can then be connected as shown.



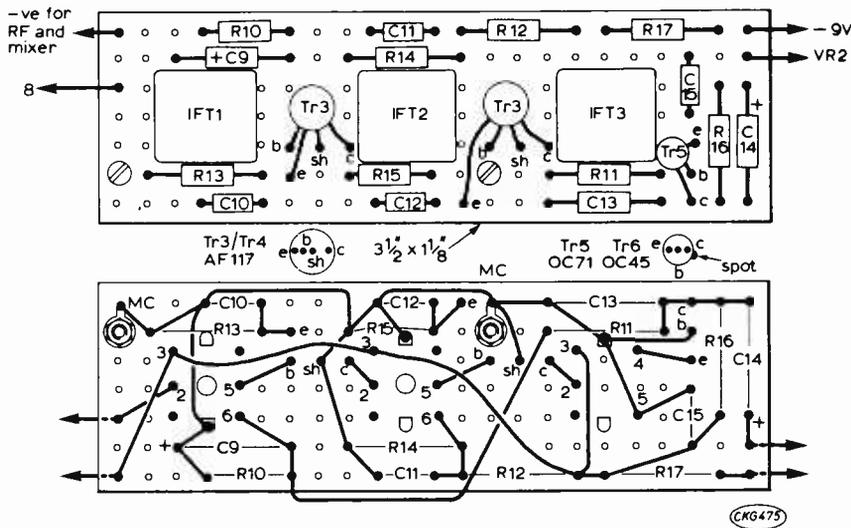


Fig. 5: Details of the wiring and construction of the IF strip. This can be tested and roughly aligned before being fitted into the chassis.

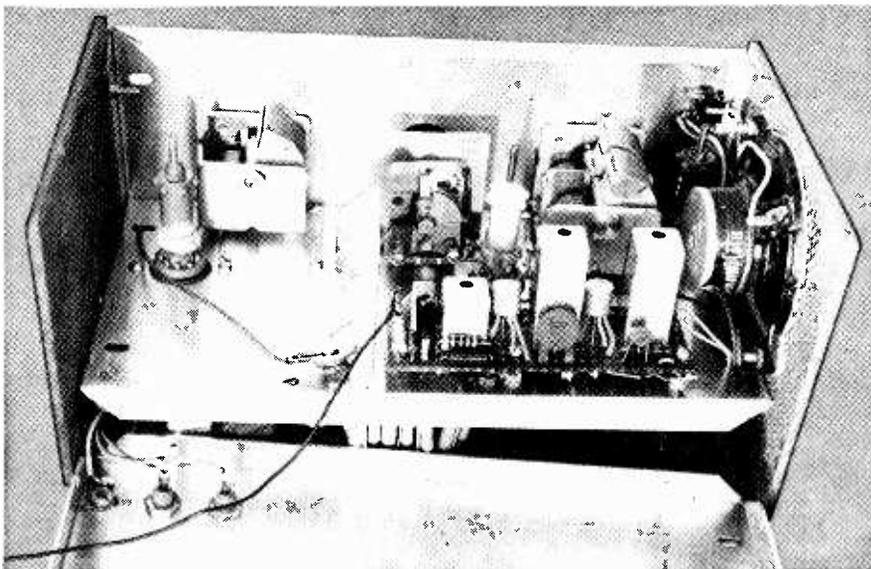

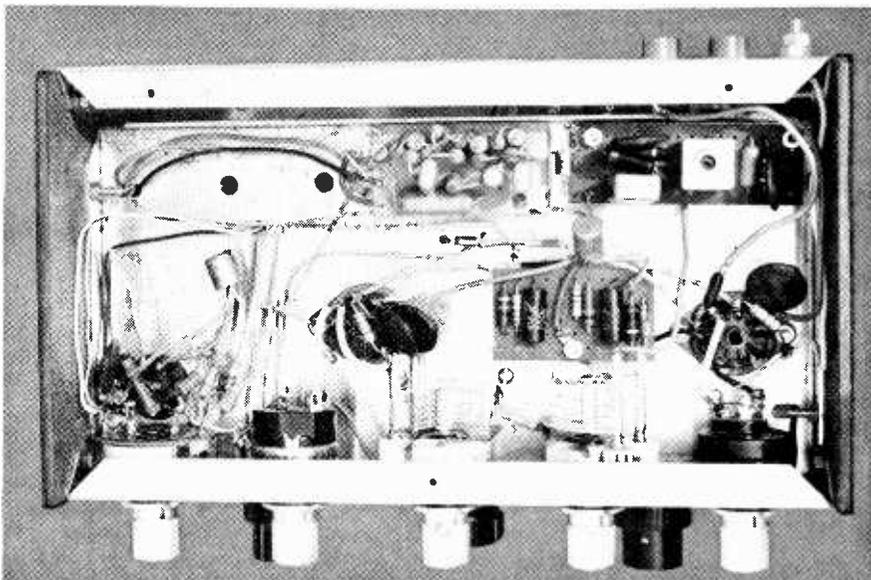A useful view of the receiver with the back removed to enable the IF strip to be seen.



Most components shown in Fig. 3 can be identified in this photograph of the underside of the receiver.

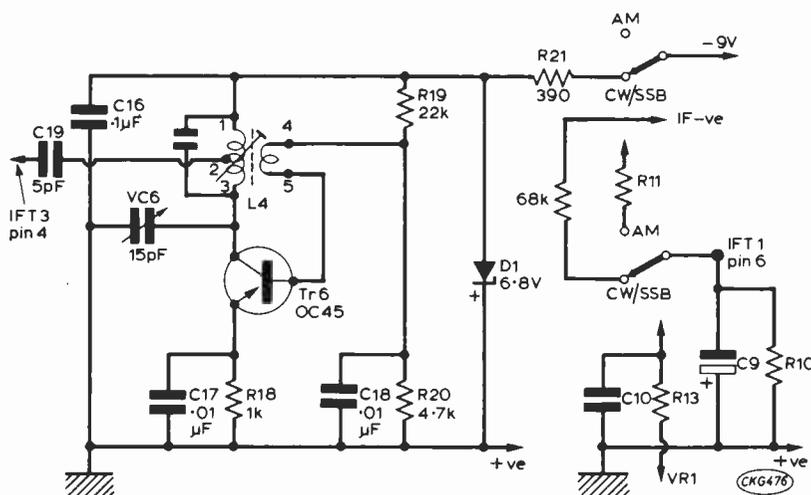


Fig. 6: The circuit of the optional BFO. The leadout connections for the OC45 can be found on Fig. 5.

AF AMPLIFIER

Figs. 1 and 3 show the packaged amplifier from the top. It is mounted clear of the chassis by a $\frac{1}{2}$ in. 6BA bolt with extra nuts, also securing a tag which forms the positive or chassis return connection as in Fig. 3.

Run the lead to VR2 slider (centre tag) against the chassis. Take two blue wires as shown for the speaker circuit. The one connecting point here also has a black lead, which passes to the 9V negative pin of the IF board, and thus to battery negative.

IF ALIGNMENT

This is carried out with a weak but stable signal, from a signal generator, or from a BBC MW station. VR2 should be at maximum, but signals can be reduced with VR1 so that the AGC action does not mask adjustments.

Adjust each core, if necessary, using a properly fitting tool (such as the Denco TT5 trimmer tool). Each core should have a quite sharp peak, but much adjustment ought not to be necessary.

Once this has been done, no further adjustment to the IF amplifier is necessary.

TUNING

As the coil cores are screwed right in for packing purposes they require adjusting so that some length of brass thread projects. Band coverage is set by means of the core of the "Red" coil. This adjustment is made at the low frequency end of the band.

Tune in a signal near the high frequency end of the band, and rotate VC4 for best volume. Now tune to a signal near the LF end of the band. Leave VC4 untouched and rotate the core of the "Yellow" coil for maximum volume. It should then be found that VC4 will require only a little adjustment, for best

volume, at any frequency in the band. To retain dial calibration, the core of the "Red" coil is locked with a 6BA nut.

In all cases VC1 should peak up signals when in a similar position to VC2/3. Adjust the core of the "Blue" coil at the LF end of the band so that this condition is obtained. It is then only necessary to keep VC1 approximately in step with VC2/3, while tuning, and to adjust VC1 for maximum signal strength with the wanted station, or for the narrow band of frequencies to be tuned by VC5.

The listed single capacitor VC1 and 2-gang capacitor VC2/3 have integral reduction drives and direct and slow-motion $\frac{1}{4}$ in. shafts. An "Electrovalue" type CK4 knob was fitted to the direct drive part of each spindle, by tapping out the metal insert or disc. A type JV18 knob was then fitted to the slow-motion part of the shaft. An alternative is to fit pointers to the direct drive part of each shaft, or to use direct drive (not slow motion) capacitors, with pointer knobs or scales.

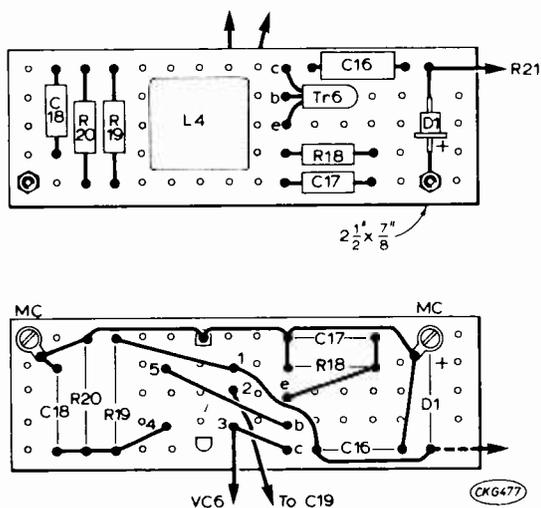


Fig. 7: The two sides of the board for the BFO components.

Coverage of the sets of "Blue", "Yellow" and "Red" coils is approximately as follows, and only those coils necessary for the frequencies wanted need be obtained.

- Range 2T 515—1545kHz (580-195m)
- Range 3T 1.67—5.3MHz (180-57m)
- Range 4T 5—15MHz (60-20m)
- Range 5T 10.5—31MHz (28.9-7m)



BEAT FREQUENCY OSCILLATOR

The circuit for this is shown in Fig. 6. When switched on, it produces an oscillation which can be tuned to approximately the receiver's intermediate frequency by the panel control VC6. This signal is coupled into the IF amplifier.

When CW is being received VC6 is adjusted so that the difference between the signal received and the BFO frequency will produce the wanted audio tone. With VC6 tuned to the receiver IF, no tone is produced. Moving VC6 either way produces a tone which rises in pitch. In some cases placing the BFO one side or the other of the IF may give greater freedom from interference.

When receiving SSB (single sideband) the BFO frequency is adjusted with VC6 so that it simulates the carrier which was removed before transmission. The speech will then be resolved. For this purpose, VC6 has to be adjusted carefully as required, for if the BFO (or carrier oscillator) is the wrong side the SSB signal, the latter cannot be resolved.

As the receiver has no separate product detector, it is essential to keep the level of the received signal down on SSB, as required, by means of the RF gain control VR1. For AM reception, VR1 will usually be at near maximum, while volume is controlled by VR2. But for SSB, VR2 will usually be at maximum (except when using phones) and gain will be reduced by VR1. (An exception is when strong AM signals cause cross-modulation of other AM signals, when VR1 should be turned back.)

The stabilising diode D1 is not absolutely necessary but as the current drawn by the AF amplifier varies considerably with audio level this can tend to cause modifications to the oscillator frequency due to fluctuations in oscillator voltage. A $100\mu\text{F}$ or $250\mu\text{F}$ capacitor from battery negative to chassis will help reduce this. For a similar reason, connections to Tr2 can be modified so that this stage is supplied from the regulated 6.8V line, though this again is not by any means essential.

BFO CONSTRUCTION

Fig. 6 shows wiring and components on the small BFO board. This is positioned as in Fig. 3, so that a short, stiff lead can run from pin 3 of the BFO coil to VC6. When first setting up the BFO, tune in a weak but stable AM signal. Put VC6 half closed, switch on the BFO, and rotate the VFO coil core until a strong audio heterodyne is produced, which is then adjusted to zero. Turning VC6 either way from this position should then cause an audio tone which rises in pitch.

When the BFO is in use, this produces some AGC voltage which reduces the IF gain. The second pole of the 2-way switch is wired as in Fig. 6 to avoid this. R11 is disconnected from the pin of IFT1 and colour coded leads are run from R11 and pin 6 through the chassis, connected to the IF board negative line. These circuits are connected as in Fig. 6 so that AGC is only applied to the first IF amplifier when the switch is in the AM position.

At the same time R13 can be disconnected from the positive line and a lead can be soldered on to run to VR1, as also in Fig. 6. This gives manual control of the gain of both the RF and the IF stages.



TELEVISION INTERFERENCE MANUAL

By B. Priestley G3JGO

Published by Radio Society of Great Britain

35 Doughty Street, London, WC1

92 pages, 8½ × 6in. spiral bound. Price: 80p

THE average transmitting amateur in this country is beset by two major problems—the complaints of neighbours who will persist in wanting to watch interference-free TV programmes and, having reluctantly agreed that the neighbours have a point, finding the relevant technical information to enable him to fix his transmitter and/or the TV set and live in peace ever more.

Unlike the United States, TV set manufacturers here are under no legal obligation to fit any kind of filter to their sets so the poor amateur is forced to do a PR job for them by visiting the complainant and, hopefully, finding a solution. The amateur soon finds out that every TV set has its own particular problems and that the filter that clears the X model set is useless on the Y model. So far, information on the subject for the amateur has only appeared in dribs and drabs, mainly in "Radio Communication" the monthly magazine for members of the RSGB and not on general sale. However, this new RSGB publication, long overdue, is a welcome collation of such information from many sources on just about every method of TV interference suppression that has ever been tried on transmitters and TV sets.

The eight chapters of the manual are packed with practical information ranging from an all-important explanation of the nature of TV signal through preliminary investigation of TVI to the design of transmitters. With the deluge of hi-fi gear that has now descended on the populace the amateur is often faced with the problem of audio breakthrough and this has been given a chapter to itself. The author makes much, and rightly so, of the great tact and diplomacy needed between the parties involved if there is to be a successful conclusion to TV breakthrough investigations. The Radio Interference Service of the Post Office usually comes into the act and their actions and responsibilities when investigating complaints are very clearly laid down in this manual.

So far, very little concerted effort has been made to form effective TVI investigation groups among the amateur fraternity and those that do exist are no doubt sitting on masses of useful information. For the amateur who must go-it-alone, this excellent manual will be his greatest ally. With some 18,000 licensed amateurs in the UK the RSGB should be able to sell at least that number of copies without any trouble at all. AED

STARTING IN THE OCTOBER ISSUE . . .

. . . a new series of articles devised specially for readers who want to experiment with simple circuits to find out how they work and how to alter their functions. This series is an entirely new approach to learning for P.W. readers: you actually make up simple projects that demonstrate circuit principles. It takes the tedium out of theory by getting you directly involved in practical work. For those readers who lack experience with delicate components, now is your chance to get started the easy way. This series will be fully illustrated and employs common components. No extra construction work before you start—you buy your components and dive straight in!

Since this is a continuing series, we strongly recommend students and teachers to order now—don't miss the first part. And don't forget the free P.W. Datacards to help you.

OCTOBER ISSUE ON SALE SEPTEMBER 7th.

BBC ENGINEERING 1922-1972

By Edward Pawley, OBE, M.Sc.Eng., C.Eng., CIEE

Published by the British Broadcasting Corporation,

35 Marylebone High Street, London, W1M 4AA.

569 pages 10 × 7½in. Price £7.00

THIS book is one of those "Bibles" that should be on the bookshelf of any man whose interest is in the earlier days of radio.

Chapter 1 explains what broadcasting is and takes the reader through the pioneering days of radio transmission. Chapter 2 tells of the period between 1922 and 1926 and is sub-divided into sections which include such things as transmitters and reception, studios, outside broadcasts, international relations and the Keston Receiving Station.


The years 1927 to 1939 are covered in chapter 3 and such items as the forming of the Corporation and short wave broadcasting are covered together with the story of the regional scheme of transmitters and the beginnings of television. There is also a section covering the BBC's preparation for the war.

The whole of chapter 4 is devoted to the war years and chapter 5 covers the post-war reconstruction of the BBC from 1946 to 1955.

The sixth and final chapter is entitled "The Years of Expansion" (1956-1972) and tells how the Corporation has progressed to the present day. A rather interesting section in this chapter deals with research and development.

Mr. Pawley has comprehensively covered the growth and progress of broadcasting throughout the six chapters of this book and traces the history from the experiments of Hertz, Marconi, Oliver Lodge and other great pioneers right through to the present day.

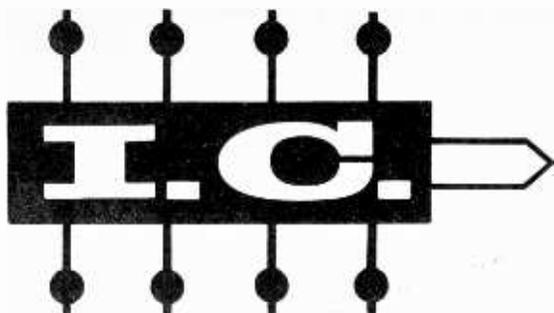This is a text that it is well worth putting on the "birthday present" or "Christmas present" list as it will, I am sure, provide many many hours of interesting reading to anyone who regards radio as his hobby. CRR



OF THE MONTH

L.A.J. IRELAND

Number 40

LP1000 STORED ENERGY REGULATOR

VISUAL power indication in battery operated equipment is usually absent so as to conserve power, except in the case of equipment incorporating high capacity or re-chargeable batteries. In some cases the power drain from a small filament incandescent bulb would be greater than the total consumption of the set. With the advent of the LED with its far greater light output efficiency it was possible in some cases to incorporate these as visual indicators but even here a 30mW or so power drain would be quite typical.

An alternative approach to reduce power drain even further to a mere 300 microwatts or so would be to pulse operate the LED every few seconds in addition to keeping it in operation only for a specified portion of the peak pulse thereby giving rise to maximum light output for minimum energy consumption.

A new monolithic integrated circuit type LP1000 manufactured by the Lithic Systems Inc. Co. of America performs just this function and is described as a 'Stored Energy Regulator' or 'Miser' for short, due to its extremely low power drain. This, however, is only one of a number of very interesting applications of this particular IC to be considered this month.

Circuit

A circuit diagram of the LP1000 IC together with a functional block diagram is illustrated in Fig. 1. Power for the device is usually obtained through a resistor capacitor network. The output power gate consisting of Tr4 is kept biased off as long as Tr1 is kept in a non-conducting state set by the voltage drop across D4 which is in series with the D1-D3 diode chain. As soon as Tr1 conducts the voltage drop produced across R2 saturates Tr2 which in turn forces the power gate Tr4 to change state.

The feedback signal to the base of Tr3 via R1, reduces further the voltage drop across D4 as it saturates Tr3 which is connected in parallel with D4 and this accentuates the turn-on time resulting in a sharply rising output pulse at the collector of Tr4.

As the LP1000 then discharges the capacitor C1 through the load, the voltage across C1 begins to drop but before it can reach zero level Tr3 will be biased off giving rise to an equally abrupt turn-off pulse. The peak and valley voltages for the LP1000

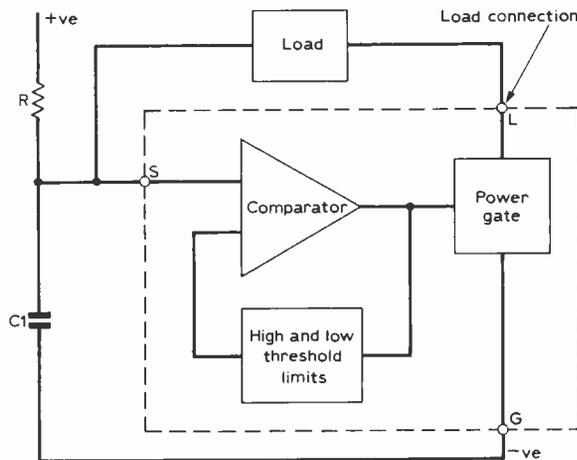
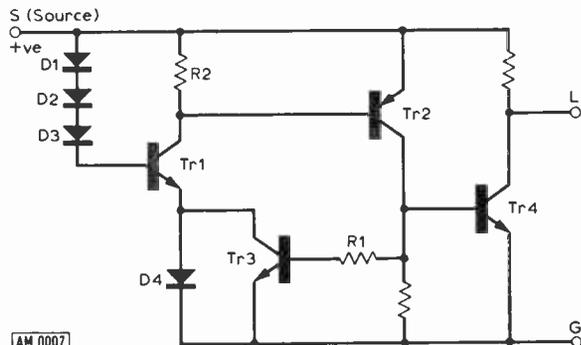


Fig. 1: Circuit diagram of the LP1000, together with a functional block diagram. The IC is produced in a TO-18 package.

lie between 2.4-1.9V so peak power is only consumed with the inherent advantage of maximum efficiency. This sequence of events continues so long as power is supplied to the device with the flashing rate set by the external RC time constant.

A high intensity light flash visible even in direct sunlight is possible using a 500 μ F capacitor. However, as the maximum voltage applied across this capacitor is in the region of 3 volts, the actual physical dimensions of the capacitor can be kept quite small. Less intense flashes are produced with

smaller value capacitors with a corresponding increase in the flashing rate provided the charging resistor remains constant.

Other uses

Due to the built in load resistor in the collector circuit of Tr4 the IC can also act as a free-running multivibrator with the frequency again controlled by the RC time constant. Frequency rates from as low as one cycle per minute to as high as 20kHz are possible using this simple arrangement with a typical power consumption of a mere 500 microwatts. Fig. 2 shows the LP1000 connected as a 1kHz oscillator.

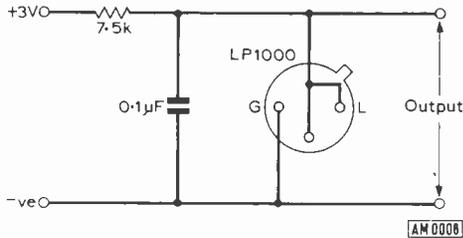


Fig. 2: LP1000 in a multivibrator circuit at 1kHz.

A further development from the oscillator application above is to power the IC from a solar cell giving rise to a self-contained unit which could find interesting applications as an aid to the blind. By replacing the load resistor with a miniature earphone an audible tone is available as a light indicator with the frequency of the note indicating the intensity of the light. Turning the cell towards brighter areas will be reflected by a corresponding increase in the pitch of the note. Solar cells capable of delivering 500 microwatts are relatively inexpensive and the light-to-sound indicator could prove to be an invaluable asset to any blind person, Fig. 3.

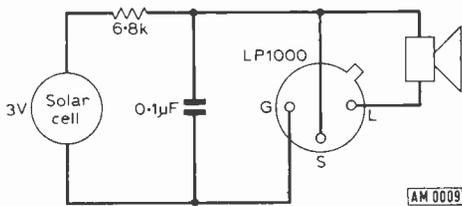


Fig. 3: Circuit using the LP1000 in a light-to-sound indicator.

Finally the last application to be considered is again a rather unusual one but the experimental possibilities it opens up are intriguing. If the load is replaced by a small step-up transformer voltages as high as 90 volts or so are obtainable. Naturally the available current from such a source is small but it does offer the possibility of trickle charging small capacity batteries from solar energy in a pretty efficient manner.

The Lithic Systems Inc. Co. have also recently released one of the first monolithic microtransmitters—a complete radio transmitter on a single chip with a 100 mW output. In the near future it is hoped that an article featuring this IC type LP2000, will be published in this column. ■

TELEVISION

AUGUST ISSUE

RECEIVER DEBUGGING

When you've built a TV receiver and tested it you will probably find all sorts of faults present. The aim of this new series is to run through the likely faults and to pinpoint the areas where action needs to be taken. The series will aid the understanding of fault-finding generally of course, and is a follow up to our series earlier this year on assessing receiver performance. In the first part the operation of the timebases is considered and the reasons for non-linear scanning outlined.

UHF FAULTS

When a dual-standard set is first switched over to 625-line operation all sorts of unsuspected faults are often encountered. George Wilding runs through the common ones and their causes, and the action necessary. Reception on u.h.f. has proved to be rather more troublesome generally than at v.h.f.

VALVE AND TRANSISTOR SUBSTITUTION GUIDE

It is not always necessary, and sometimes impossible, to fit exact valve and transistor replacements. This guide has been compiled to indicate generally what can and can't be done, list numerous helpful substitutes and lay down guidelines for the more difficult situations.

SERVICING TELEVISION RECEIVERS

This month Les Lawry-Johns deals with problems on the final GEC group dual-standard chassis, the GEC/Sobell 2032/1032 series.

SBF AERIAL FOR BAND V

Following the great interest shown in his short back-fire aerial for the lower u.h.f. channels Reg Roper presents a design suitable for the higher channels.

PLUS ALL THE REGULAR FEATURES

TO
(Name of Newsagent)

Please reserve/deliver the AUGUST issue of TELEVISION (20p), on sale JULY 16 and continue every month until further notice

NAME.....

ADDRESS

.....

LARGE STOCKS ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new & to makers specs.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power 80p
AC153K pnp germanium low power 32p
AC176K npn germanium low power 32p
AD161 npn germanium medium power 42p
AD162 pnp germanium medium power 40p
AF139 pnp germanium UHF 49p
BC 107 13p; BC108 12p; BC109 13p; } npn
BC187 11p; BC198 10p; BC169 11p
BC177 21p; BC178 19p; BC179 21p; } pnp
BC257 12p; BC258 11p; BC259 13p
Standard groupings available.
BD185 npn med power 37p
BD136 pnp med power 38p
DIODES
OA59, OA91, OA95 each 6p
OA200 8p; OA202 10p
Other semiconductors
AC128 17p; AF117 32p
BFY51 18p

Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

SIEMENS' THYRISTORS

0-8A 400V 56p, 600V 70p
3A 400V 60p, 600V 88p

ZENER DIODES full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 268F) 4p.

DIN PLUGS & SOCKETS

by Hirschmann, 4A rating




2 way LS—socket 10p; plug 12p. 3 way scr. socket 10p; plug 12p. 5 way scr. socket 12p; plug 15p.

TRANSISTOR ACCESSORIES

To3 cover 7p
Heat sinks 1°C/W, type 6W1, undrilled 60p

SWITCHES

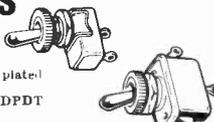101C SPST toggle 20p;
409 DPDT toggle 20p. (These are chrome plated 2.5A rating)
7201 Sub-miniature DPDT 250V a.c./2A 48p




ROTARY SWITCHES

Radloparcs Miniature Maka-switch (in assembly kit form) Shaft 45p.
Waters, MBB-2P5W, 1P11W: BBM-1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each, 6p.

WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, each 24p

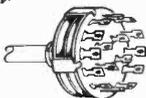

ELECTROLYTIC CAPACITORS

AXIAL LEAD Prices subject to amendment by the manufacturer.

Rated voltage: 3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity μ F							
0.47							
1.0					10p		7p
2.2				10p			7p
4.7					7p		8p
10			7p	7p	7p		8p
22			8p	7p	7p		8p
47	7p		8p	7p	7p		9p
100	8p	7p	7p	7p	7p		11p
220	7p	8p	8p	8p	8p		10p
470	8p	9p	9p	10p	12p		17p
1000	10p	12p	12p	17p	20p		24p
2200	14p	17p	22p	25p	38p		40p
4700	25p	25p	37p	41p	54p		
10,000	40p	43p					

Polycarbonate —5% Tolerance

250V up to 0.1 μ F: 100V/0.1 μ F and above.
0-01: 0-012: 0-015: 0-018: 0-022: 0-027: 0-033: 0-047: 0-058: each 4p.
0-068: 0-082: 0-1: 0-12: 0-15 each 4p.
0-18: 0-22: each 6p.
0-27: 0-33: 6p: 0-39 7p: 0.47 8p: 0.56 10p.
0.68 11p. 1 μ F 13p.
Prices subject to amendment by the manufacturer.

SILVERED MICA non-polarised capacitors in 34 values from 2.2 pF to 680 pF, each 8p

RESISTORS 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 μ p
C	1/20W	5%	82 Ω —220K Ω	E12	9	8	7.5
C	1/8W	5%	4.7 Ω —470K Ω	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 Ω —10M Ω	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 Ω —10M Ω	E24	1.2	1	0.9 nett
C	1W	5%	4.7 Ω —10M Ω	E12	2-6	2	1.8 nett
MO	1/2W	2%	10 Ω —1M Ω	E24	4	3	2 nett
WW	1W	10% \pm 1/20 Ω	0.22 Ω —38 Ω	E12	7	7	6
WW	3W	5%	1 Ω —10K Ω	E12	7	7	6
WW	7W	5%	1 Ω —10K Ω	E12	9	9	8

Codes: C—carbon film, high stability, low noise.
MO—metal oxide, Electrofil TR5, ultra low noise.
WW—wire wound, Pleesey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.


Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order).

★ Please remember to add V.A.T. to your order.

If you have already got your No. 6 catalogue and want to know latest additional items and price amendments, send S.A.E. for special supplementary list.

KNOBS

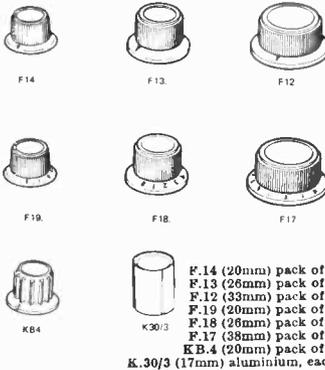All grub screw fitting for 1" shafts. Black. For other types—see Catalogue No. 6, P.94



F.14 (20mm) pack of 2 32p
F.13 (26mm) pack of 2 38p
F.12 (33mm) pack of 2 40p
F.19 (20mm) pack of 2 32p
F.18 (26mm) pack of 2 38p
F.17 (38mm) pack of 2 40p
K.B.4 (20mm) pack of 4 40p
K.30/3 (17mm) aluminium, each 24p


IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semi-conductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc. information and equivalent tables, etc. Well illustrated (96 pages 8 1/2" x 8 1/2") 25p. post free with refund voucher for 25p. allowable on orders over 25 or more.

with
25p
refund
voucher

POTENTIOMETERS

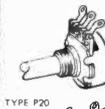
Rotary carbon track, double wiper
SINGLE P20 1in 100 Ω to 2.2M Ω
12P, P20 Log, 4.7K Ω to 2.2Meg. 12P
JP20 Log, 4.7K Ω to 2.2M Ω 12p.
Dual gang 1in 4.7K Ω to 2.2M Ω ,
42p; Dual log, 4.7K Ω to 2.2M Ω
42p; Log/anti-log, 10K, 22K,
47K, 1M Ω only 42p; Dual anti-
log, 10K only, 42p. Any type
with 2A D.P. mains switch,
12p extra.



TYPE P20



TYPE JP20

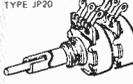


TYPE DP20

Only decades of 10, 22 & 47 available in ranges quoted.

DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.

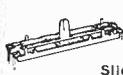SLIDER
Lin or log, 10K to 1Meg. in all popular values, each 26p.
Escutcheons—White, grey, black, 10p each.
Control knobs: blk/white/red/yel/gr./blue/blk. grey/lt. grey, each 5p.



Slider

All items offered for sale in accordance with our stated terms of business, copy of which available on request. Prices quoted DO NOT include V.A.T. Orders from U.K. customers must be accompanied by an additional 10% of nett value for V.A.T.

DISCOUNTS Not allowed on nett price items. 10% on orders for 25 or more, 15% on orders for 515 or more. Prices subject to alteration without prior notice.
PLEASE SEE LATEST AMENDMENT LIST. SEND S.A.E.

POSTAGE AND PACKING FREE
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

ELECTROVALUE

(Dept. P.W. 8) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB
Hours: 9—5.30; Sat. 1 p.m. Tel.: Egham 3603 Telex 264475
EGG. REG. NO. 1047788. R.O. 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB

SURPLUS BARGAINS

BLOWER MOTORS small double ended blower will work on 6 to 28v DC, outlet size 1½ sq. new boxed £1.79. **HEAD/MIKE SETS** for 19 set m.c. type new boxed £1.70. **PANEL METERS** 4 different for £1.25. **MULTICORE CABLE** 25 core coloured new in 5'9" lengths 2 for 86p. **YAXLEY SWTS** 4p 11w 4b with low value resistors and knob 76p. 4p 4w 2b with res. and knob 40p. **METER UNIT X** pointer type dual 115 Ua for use with 1155 Rx new £1.58. **TRIMMERS** 20pf air spaced ceramic type new 10 for 55p, £4.40 per 100. **JOY STICK CONTROL UNITS** operate 4x micro swts 1p c/o £1.35. **HEADPHONE MATCHING TRANS. & LEAD**, high to low impedance 5ft lead with standard plug new 60p. **LARGE TRANSISTOR PANELS** with 2N560 transistors Sil N.P.N. type also conds. res. metal fittings etc. panel size 13' x 12" new cond. two panels for £1.50 with min. of 40 transis. **PANEL LAMPS** aircraft type suitable car inst. panel with 24v m.e.s. bulb red or green two for 33p. **METERS** 500 Ua scale 0 to 5 1½" OSD on panel with 3p 3w swt. £1.25. **WAVEMETER & OSC. UNIT** covers range 150 to 230 Mc/s with charts, spares, instructions etc. new boxed £16.50. **MINIATURE FUSE HOLDERS** take ¼" fuse 4 for 33p. **PLUGS & SKS** Belling Lee type with cover 25 way 33p, 12 way 22p, 8 way 16p. **YAXLEY SWT UNIT** with 4p 12w 4b & 2p 12w 2b with shorting wafer part of xtal selector 64p. **POWER UNIT** 1/P 115v 50c/s O/P variable 0 to 26v D.C. at 3 amps smoothed with circ. tested £7.70. C.R.T. type 7BP7A 7" dia. flat face tube 6.3v heater 7Kv E.H.T. emag focus and Def as Blue/Yellow phosor suitable slow scan T.V. etc. new with base conn. £1.73. **SILICON DIODES** type ZR22 200 P.I.V. 8 amps 4 for 66p also 800 P.I.V. 750 Ma new 15 for £1.10. **INDICATOR UNIT** 266 with 6" tube green screen 18 valves, slow motion dial, tuning conds. etc. with outer cover £4.95. **POT CORES** miniature pot cores wax dipped ¼ x ⅜ new 10 for 33p. **RADIO TELEMETER UNITS** with 6 valves, tape unit, speaker, low speed motors, can be converted to Radio 2 for use on 200/250v mains in new cond. with circ. and mods. £4.18. **SELSYNS** for Ae position Ind. etc. for use on 115v 50C/S supplied in pairs with a 360 deg. compass Ind. scale & pointer new £4. **LAMPS** aircraft type double filament with silvered reflector dual 14 watt 28v new 5 for 65p. **NEONS** wire ended type 1/25th watt 470K res. for 240v new 10 for 55p. **PRESSURE GAUGE** thought to be oil press vehicle type elec. operated scaled 0 to 120 2½ dia. new boxed 44p. **CODER UNIT** part of IFF equip. American surplus contains 10 valves 12A7, 6X4, 12AU7 etc. 13 miniature relays plug in type coil 550 ohm 2p c/o will work on 12/24v also 12 miniature micro swts. complete in case good quality unit £2.70. **VIDICON CAMERA TUBES** standard 1" type with base conn. etc. graded according to scan marks A £9, B £6. **TAG STRIPS** solder type 24 way new 10 for 30p. **SPEAKER UNITS** P.A. type made by Truvox 8 ohm with line trans. in case 9" x 9" x 8" semi weather proof new cond. £3.13. **BATTERIES** 6 volt 40 A/Hr. type metal cased new with filling inst. £3.19. **XTAL OVENS** with 12 type Hc6/u xtal holders these can be removed and used separate 76p. **VALVES** 5U4, 6X5, 6SN7, 6SL7, 85A2, 12A7, 12AU7, 12AX7, 6AK5, 6BH6, 6H6, 6SK7M, 6SA7, 6N7M, 5Y3GT, 6J6, 6X4, VC173, EF50, 6BA6, 6SA6, CV2179 (Sim N78) any 3 for 55p. **BATTERY BOX** will take 4x U2 cells connected for 6 volts 48p. **POLARISED RELAYS** as 2 coils of 25 ohm each 1p c/l new 33p each.

THE ABOVE PRICES INC. POST/CARR. & V.A.T. CHARGES

Carr. charges apply to mainland only, all goods ex equip unless stated otherwise, S.A.E. with enquiry.

A. H. SUPPLIES


57 MAIN ROAD,
SHEFFIELD, S9 5HL

Phone 444278 (0742)

VISIT LONDON'S LIGHTHOUSE


*our lighthouse keeper
wants to meet you!*

Jim Roche has been Imhofs Eddystone lighthouse keeper for a good few years now - so who better than he to guide you into the right channel, for an Eddystone communications receiver:

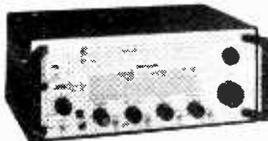

Model 1001 - general-purpose receiver with reception facilities for CW, MCW, AM and SSB. Provision for crystal control on 10 channels.

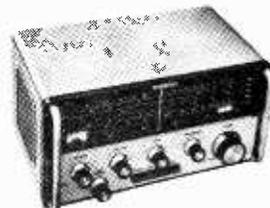EC10 Mk II still 'Top of the Pops' in the modest price range of communication receivers. Embodies features usually only found in the more expensive designs.



IMHOFS

112-116 New Oxford Street
London WC1A 1HJ
telephone 01-636 7878 R81

Train for television

Course commences 5th September, 1973


This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

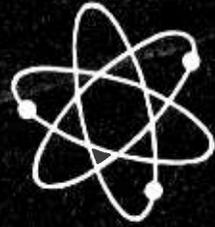THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept. PW5) 34a Hereford Rd., London W2 5AJ



LOW POWER CLASS A AMPLIFIER

R. A. Pen

IN some applications, such as in small pocket receivers, only comparatively small output powers are required, and small modern loudspeakers produce adequate volume for a small room from only a few milliwatts of power. In fact most miniature speakers have a maximum power handling capability of only 100-200mW.

While in the interests of battery economy class B amplification is usually used in the output stage of battery operated equipment, where only low output powers are involved, a simple class A circuit is quite suitable. Bearing these points in mind, the simple amplifier described below was constructed.

Circuit Explanation

A circuit diagram of the amplifier constructed by the author is shown in Fig. 1. This uses three inexpensive silicon n.p.n. transistors.


VR1 is the volume control, and C1 the input coupling capacitor. Tr1—Tr2—Tr3 are direct coupled. R2, and R5 bias the input transistor (Tr1) so that the voltage present at its collector (approximately 0.65V) is at the correct level to in turn bias Tr2. Likewise, Tr2 is biased to just the right level to produce a voltage at its collector which is suitable to bias the output transistor, Tr3. In effect Tr1—R1 form a potential divider which biases Tr2, and Tr2—R3 form a potential divider which biases Tr3.

As each transistor inverts the signal between its base, and collector terminals, the input and the output of the entire amplifier are 180° out of phase. The two biasing resistors, R2, and R5 being connected between the input and the output therefore introduce a considerable amount of d.c., and a.c. negative feedback. While the d.c. feedback is very

desirable as it gives stable biasing to a system which would otherwise be very critical, the a.c. negative feedback decreases the gain of the amplifier. This does however, give the amplifier improved quality (hi-fi).


The gain of the amplifier can be increased by connecting a capacitor of a suitable value between the junction of R2—R5, and earth. This decouples the a.c. signals through the biasing resistors, and virtually eliminates the a.c. feedback at audio frequencies.

A compromise between gain, and output quality can be achieved by placing a feedback limiting resistor in series with the decoupling capacitor. In Fig. 1, C3 is the decoupling capacitor, and R6 the feedback limiting resistor. The value of R6 is the highest one which gives adequate gain for the amplifiers intended purpose, a value of 22kΩ being used on the prototype. Its value can be varied to suit individual requirements, the required value being found by experimentation.

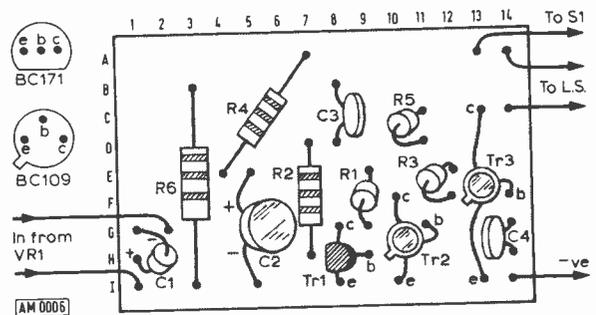

▲ Fig. 2: Component layout on the Veroboard.

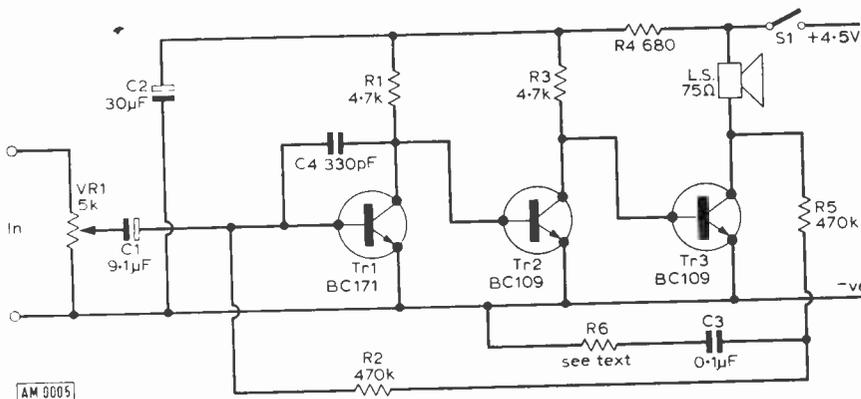◀ Fig. 1: The low power class A amplifier.



R4, and C2 are the supply decoupling components. The loudspeaker itself forms the collector load for Tr3. Speakers of other impedances can be used, but must have an impedance of at least 35Ω. Due to the large amount of d.c. negative feedback used in the circuit, altering the speaker impedance should not drastically change the operating parameters of the circuit.

The low value capacitor, C4, is required in order to reduce the upper frequency response of the circuit, and so maintain good stability. Without this component, direct pick-up of radio signals can become a problem.

S1 is the on-off switch, and can be ganged with VR1 if preferred.

The unit requires a 4.5V supply, an Ever Ready 1289 battery being a very economical source of power for the amplifier, although if small size is required, three U16 batteries connected in series can be used.

As the amplifier uses only a few components all

of which are of a small size, it is easily miniaturised. A diagram giving a suitable Veroboard layout for the unit is shown in Fig. 2. The prototype built to this layout measures only 1.4 x 0.9 x 0.75in. For obvious reasons miniature resistors, and components must be used. On the prototype a tantalum bead capacitor was used in the C1 position, but a miniature electrolytic of 8-10μF can be used providing it will fit into the available space.

There is only one break which has to be made in the copper backing strips, this being between the negative side of C1, and the collector of Tr1. A soldering iron with a fine bit is required when soldering the components to the board, and a continuity tester should be used to ensure that no excess solder is shorting two adjacent copper strips together.

One cannot expect too much in the way of output quality from the amplifier, mainly because such a small speaker is used, but the unit is economical to run, small, inexpensive to build, and sensitive, and is very useful for many purposes. ■

CASSETTE RECORDER IN THE CAR

ON a long trip it is often desirable that one can play one's cassette tape-recorder, but then it's battery life becomes very short. Since most cars use a 12 volt battery, the tape recorder cannot be run directly from the car's electrical system. One often used method is to connect a heavy resistor in series with the tape-recorder, but on a radio-cum-tape-recorder this method does not work since the tape recorder draws far more current than does a radio.

This problem can be overcome by using a very simple stabilising voltage supply consisting of only three components—a transistor, resistor and a zener diode. Before one selects any components, one must know exactly what one's requirements are—the figures given at the end of this article are for a typical cassette tape-recorder that draws a maximum of 350mA. It is however easy to modify one's design to cope with almost any portable tape-recorder.

Firstly, what is the voltage of the machine? This is easily determined by counting the batteries and multiplying by 1.5,—most recorders are either 6, 7.5 or 9 volts. Once the voltage has been determined, it is necessary to find the maximum current that the machine will draw. To do this, remove one battery and solder wires onto the ends of it. Connect an ammeter in series with the battery and by dabbing the wires where the battery was and by playing the tape recorder with it's volume fully turned up, the maximum current can be determined.

Our next job is to choose a transistor. The only specifications that need concern us are it's power and current rating and it's current gain (h_{fe}). For a tape recorder, a 2N3054 is normally sufficient, but for a large machine, a 2N3055 might be necessary, while for a small radio, a 2N1611 might suffice. To determine the power rating, we use the formula

$$\text{Power} = I \times V$$

$$= I(V_{in} - V_{out})$$

The zener diode is a low power device (250mW) and it's breakdown voltage is the required output voltage plus 0.6 volts, the latter being the emitter-

base voltage of a silicon transistor. The zener need not be specially selected, since a volt either way will have very little effect on the tape-recorder.

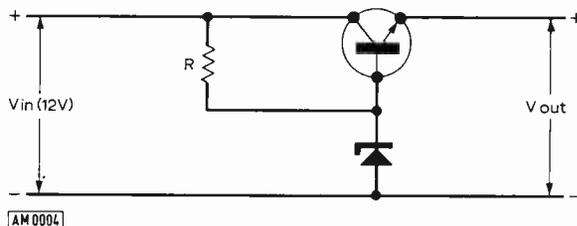


Fig. 1: Stabilising circuit for cassette recorders.

The resistor (R) is the most difficult to calculate. The current that passes through it performs two functions:

- i) A current of normally at least 5mA to maintain the voltage across the zener diode.
- ii) The base current of the transistor. As a rule of thumb, this should be twice the maximum required output current divided by the current gain of the device.

Adding these two we get that the current through the resistor is $(5 + 2 I_{out}/h_{fe})$ mA and assuming that the car uses a 12 volt battery, the value of the resistance, using Ohm's Law, is found to be:

$$R = \left(\frac{(12 - V_{out} + 0.6)}{(5 + 2 I_{out}/h_{fe})} \right) \text{ k}\Omega \quad \left(R = \frac{V}{I} \right)$$

The components given below are for a typical tape-recorder that draws 350mA. No list of prices is included as a person who can't build this for less than £1 just isn't trying!

Components.	6V	7.5V	9V
Resistor ($\frac{1}{2}$ W)	330Ω	270Ω	180Ω
Zener diode	6.6V	8.1V	10V
Transistor.		2N3054	

Build yourself a TRANSISTOR RADIO

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 2 diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

£9-35

P. P. & Ins. 52p

(Overseas P. & P. £1-05)

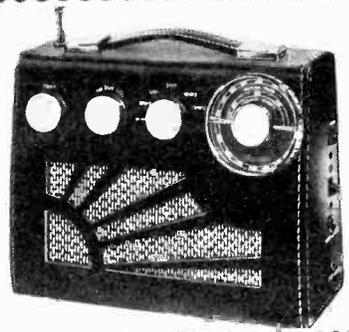

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£7-68** P. P. & Ins. 47p. (Overseas P. & P. £1-05)




ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler

Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes. fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

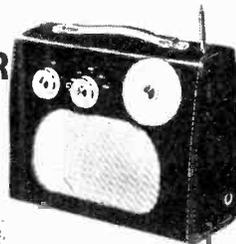
Total building cost **£6-58** P. P. & Ins. 47p. (Overseas P. & P. £1-05)



ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler, band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 25p (FREE with parts).

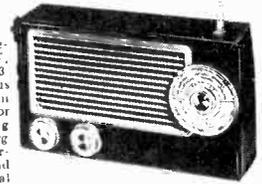
Total building costs **£4-38** P. P. & Ins. 31p. (Overseas P. & P. £1-05)



POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 6 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts).

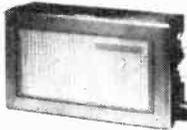Total building costs **£2-50** P. P. & Ins. 24p. (Overseas P. & P. 65p)



TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-75** P. P. & Ins. 25p. (Overseas P. & P. 65p)




TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

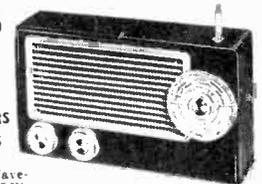Total building costs **£4-95** P. P. & Ins. 33p. (Overseas P. & P. £1-05)



"EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

All parts including Case and Plans **£6-05** P. P. & Ins. 33p. (Overseas P. & P. £1-05)

FULL AFTER SALES SERVICE

Callers side entrance "Lavells" Shop
Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.
PLEASE NOTE: ALL PRICES INCLUDE VAT

RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367
Reg. no. 788372

I enclose £..... please send items marked.

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Parts price list and plans for

Name

Address

PW55

SINCLAIR PROJECT 60

- Z30 £3-50
- Z50 £4-25
- P25 £3-97
- P26 £6-40
- Project 60
- tuner £16-80
- AFU £4-50
- PZ8 £6-60



Stereo 60 £7-80
2000 Amp £22-00
Transformer for PZ8 £2-95

EXECUTIVE CALCULATOR £50-00

PROJECT 60 KIT £2-50
Our extremely popular kit contains the extra capacitors, diode plugs and sockets, cable and fuseholder needed to complete Project 60.

IC RADIO CHIP TBA651 £2-10

The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2-10. Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1-75.


S-DECS AND T-DECS

- S-DECS £1-44
- T-DECS £2-88
- µ-DEC A £3-00
- 16 diode carriers £1-20



SINCLAIR SUPER IC12

ONLY £2 00

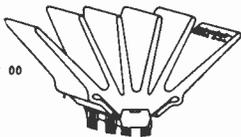

Max. supply volts 28. Power 6 Watts rms. Complete with free printed circuit board and 44 page instruction book.

SWANLEY IC TOMORROW £2-50

The World's most powerful IC amplifier. Similar to the above but operates at 35 volts max. supply and gives 12 Watts rms output. Manufactured for us by a leading semiconductor company. Supplied with our instructions and a 6 month guarantee, but no printed circuit.

KITS FOR IC12 AND IC TOMORROW

Except for the power kits and speakers, all items suit both integrated circuits.

DELUXE KIT

Includes all parts for the printed circuit and volume, base and treble controls needed to complete the mono version £1-45. Stereo version with balance control £3-30.

BASIC KIT

Contains components for the P.C. board and volume and simple tone controls. Mono version £1-25. Stereo version with balance control £2-90.

POWER UNITS FOR THE IC12

A set of components to construct a 28V 0.5 Amp power supply £2-27. Also suitable Sinclair PZ5 fully constructed £3-97.

POWER KIT FOR IC TOMORROW

A set of components to construct a 35V 1 Amp power supply £2-97.

LOUDSPEAKERS FOR THE IC12

Specially chosen for the IC12. 5" 8 ohm £1-00. 5" x 8" 8 ohm £1-45. 10" x 6" 15 ohm £2-27.

PREAMPLIFIER KITS

Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1-20. Stereo model £2-20. Type 2 for ceramic or crystal pickups. Mono 60p. Stereo £1-20. SEND S.A.E. FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAIN £3 40

Introducing the most versatile battery eliminator ever offered with a high current output that makes it suitable for operating most battery tape recorders, record players, cassette recorders and shavers. Input 200/240V. Output voltage selected by front panel switch may be set to 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500 ma. Housed in a very strong, attractive, plastic case and fully guaranteed for 12 months.




SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent

Post 10p per item. Please add 10% extra to total cost of order for VAT. Official credit orders welcome from schools etc. Full lists 10p post free. Mail order only. No callers please.

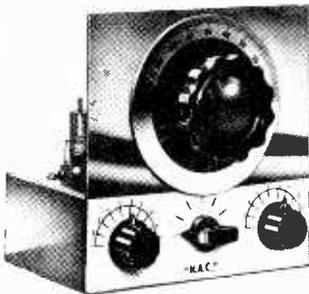H.A.C. SHORT-WAVE KITS
WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.


NEW "DX" RECEIVER

Complete kit—price £3-85 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume. I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world. This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. Kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

U.H.F. T.V. AERIALS

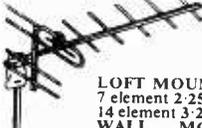SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS

7 element 2-25. 11 element 2-75.

14 element 3-25. 18 element 3-75

WALL MOUNTING c/w

WALL ARM & BRACKET

7 element 3-25. 11 element 3-75. 14 element 4-25. 18 element 4-75. CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT. 7 element 4-00. 11 element 4-50. 14 element 4-75. 18 element 5-25. MAST MOUNTING arrays only. 7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 99p yd. KING TELEBOOSTERS from 3-75. LABGAE PRE-AMPS 4-25.

BELLING LEE CONCORD BOOSTER

V.H.F., F.M., U.H.F., mains operated 8.20. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np. C.W.O. Min. C.O.D. charge 25np.

F.M. Radio Aerials

F.M. RADIO loft S/D 1-00 3 element 3-25. 4 element 3-50. Standard coaxial plugs 99p. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS

40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY
Telephone 01-648 4884

LOUDSPEAKER BARGAINS

- Fane Pop 100 watt 18" 8/15 ohm £21-45
- Fane Pop 60 watt 15" 8/15 ohm £12-26
- Fane Pop 50 watt 12" 8/15 ohm £10-17
- Fane Pop 25/2 25 watt 8/15 ohm £5-94
- Fane Pop 15 12" 15 watt 8/15 ohm £4-40
- Fane 122/10a or 122/12 ... £9-90
- Fane Crescendo 15" 8 or 15 ohm £27-50
- Fane Crescendo 12" 8 or 15 ohm £24-20
- Fane 8" d/cone 808T 8 or 15 ohm £2-64
- Fane 8" d/cone, rolt surr. 807T 8 or 15 ohm ... £3-16
- Baker Group 25 3, 8 or 15 ohm £6-00
- Baker Group 35, 3, 8 or 15 ohm £7-50
- Baker De Luxe 12" d/cone ... £9-62
- Baker Major ... £7-50
- EMI 13 x 8 3, 8 or 15 ohm ... £2-25
- EMI 13 x 8 type 150 d/cone 3, 8 or 15 ohm ... £2-58
- EMI 13 x 8 type 450 t/w 3, 8 or 15 ohm ... £3-85
- EMI 13 x 8 type 350 8 ohm ... £8-25
- EMI 6 1/2" 93850 4 or 8 ohm ... £2-80
- Elac 9 x 5 59RML09 15 ohm ... £2-53
- Elac 9 x 5 59RMLL4 8 ohm ... £2-53
- Elac 6 1/2" d/cone 6RM220 8 ohm ... £2-59
- Elac 6 1/2" d/cone, rolt surr. 6RM171 8 ohm ... £3-22
- Elac 4" tweeter TW4 8 or 15 ohm £1-21
- Celestion P58 for Unilux ... £2-16
- Celestion MFL000 25 watt horn 8 or 15 ohm ... £10-45
- Elac 5" 3 ohm ... £1-75
- Elac 7" x 4" 3 or 8 ohm ... £1-52
- Elac 8" x 5" 3 or 8 ohm ... £1-93
- Wharfedale Bronze 8 RS/DD ... £3-11
- Wharfedale Super 8 RS/DD ... £5-50
- Wharfedale Super 10 RS/DD ... £9-80
- Goodmans 8P 8 or 15 ohm ... £3-80
- Goodmans 10P 8 or 15 ohm ... £4-49
- Goodmans 12P 8 or 15 ohm ... £11-55
- Goodmans 15P 8 or 15 ohm ... £17-05
- Goodmans 18P 8 or 15 ohm ... £29-70
- Goodmans Twinaxiom 8 ... £6-79
- Goodmans Twinaxiom 10 ... £7-61
- Goodmans Axent 100 ... £6-60
- Eagle DT33 dome tweeter 8 ohm £5-45
- Eagle HT15 tweeter 8 ohm ... £3-66
- Eagle CT5 tweeter 8 ohm ... £1-25
- Eagle MHT10 tweeter ... £3-74
- Eagle CT10 tweeter ... £2-54
- Eagle FR4 ... £4-45
- Eagle Xovers CN23, 28, 216 ... £1-15
- Kef T27 ... £4-67
- Kef T15 ... £5-50
- Kef B110 ... £6-16
- Kef B200 ... £7-42
- Kef BL39 ... £10-72
- Kefkit 2 ... £24-75
- Richard Allan 12" d/cone 3 or 15 ohm ... £2-20
- Richard Allan 8" 3, 8 or 15 ohm £2-27
- 10" 6" 3, 8 or 15 ohm ... £1-92
- 8" x 5" 3 or 8 ohm ... £1-38
- 7" x 4" 3 or 8 ohm ... £1-38
- 3" 8 ohm or 80 ohm ... £65
- 2 1/2" 64 ohm ... £65
- Speaker matching transformer 3, 8 or 15 ohm ... £1-10
- Adastra Hiten 10" 10 watt 8 or 15 ohm ... £2-80
- Adastra Top 20 12" 25 watt 8 or 15 ohm ... £6-32
- Stephenspeaker kits and cabinets—send for illustrated brochure and list of recommended speakers.
- Car stereo speakers—ask for leaflet.
- PA/Disco amplifiers (carr. and ins. £1-00):
Baker 100 watt ... £46-00
Linear 30/40 ... £25-00
Linear 40/60 ... £30-00
Linear 80/100 ... £50-00
- FREE with speaker orders over £7 "Hi-Fi Loudspeaker Enclosures" book.
- All units guaranteed new and perfect. Prompt despatch.
- Carriage and insurance 25p per speaker. (Tweeters and Crossovers 15p each.)
- All prices quoted inclusive of V.A.T.

WILMSLOW AUDIO, Dept. PW

Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF

HOTLINES

ON RECENT DEVELOPMENTS

A COMMON circuit arrangement in the popular construction journals is that which allows temperature to control something—a sort of electronic thermostat.

Perhaps the most featured circuitry is that which has some form of temperature sensor (say, a thermistor) followed by a transistor or two which, in turn, drives a meter (for temperature to be read from a pre-calibrated dial) or a relay to actuate some form of control circuit.

Out on to the electronics market has come a new type of reed switch which can perform this kind of function—and without the need for any further electronic circuitry.

Basically, the reed switch has two contact blades which form a simple on-off switch. Around the glass tube which houses these contacts is a coil. Energising the coil causes the contacts to open (or close) while removal of the energising source causes the blades/contacts to return to their original state.

The new devices have the glass capsule and reed relay blades. Instead of a simple coil of wire, the capsule is surrounded by toroidal magnets which are separated by a ferrite material. Because the ferrite material separates the magnets, it also has the effect of separating their individual magnetic fields.

However, the particular make-up of the ferrite employed is such that there is a certain critical temperature point called the Curie point. Below this point, the ferrite no longer isolates the magnetic fields of the separate magnets and thus the switch can be caused to activate.

Once the temperature rises above the Curie point, the magnetic fields are again separated. Thus there is a complete switching action actuated only by temperature, and the reed blades themselves can be used to form a switch. There are many uses which will come to mind; standard units in the range extend from 0°C to 100°C in 5°C steps.

LIGHTS UP

Turning to the "lighter" side of smoking, solar cells are being used in electronic lighters to keep the batteries charged. One set of experiments shows that some 50 cigarettes

a day can be lit for a month before the batteries need recharging by exposing the light-cells to a light source. It seems reasonable to assume that one could leave such a lighter out in the open for various periods of time and thus the batteries would remain charged for far longer than a month.

Work is proceeding to improve the efficiency of solar cells as a means of supplying energy from ordinary daylight, i.e. without any sunshine at all. This should be a useful project for people living in or around Manchester on a rainy day.

ALL TOGETHER

Electronic calculators have become very real practicalities over the past few years. Progressing from the realms of theory they are now offered by the van load in a wide variety of shapes and sizes. Many things have contributed to the progress of electronic calculators not the least of which is the development of the i.c. which does all the calculating. The aim has been to be able to boast "A calculator on a chip".

Well, the dream gets closer every hour. A company has now brought out a chip which very, very nearly achieves this title. The low power calculator circuitry is on the same glass panel as the liquid crystal display. Thus the thing is literally a complete calculator on a single substrate.

But what of the buttons or keys which input the information? Well, the manufacturers have thought of that too—yes, and it's on the same panel. The inter-digitised contacts are shorted by a conductive rubber button whenever a key is depressed. Standby power is only 12mW and the calculator runs for about 100 hours from a single pen-sized cell. Sorry, they are not for sale in the U.K. as yet.

VERY HIGH-BROW

Capacitors are one type of component which seems to be getting ever smaller. The photograph on this page shows five tantalum chip capacitors from the range manufactured by Union Carbide. The T400 series has nine case sizes; values range from 0.1µF and can withstand temperatures of up to 300°C. Those



shown in our photograph are for a very "high-brow" application — at least, "eye" think they are.

Down in the forest something stirred, so we're told. In a certain Bavarian forest it is more than stirring. Laser equipment, supplied by Siemens, measures the trajectory of survey satellites. Power of this laser is 100MW (100 megawatts or one hundred million watts). One wonders if, in the decades to come, this type of equipment will be towed away from Lisle Street shops as surplus stock by delighted Amateurs who may have just given £1.75 for them. If this happens one must ask whatever will replace such equipment?

LITTLE THINGS

Little things please little minds so we're told, but sometimes it's not that cynically simple. Cramming a few thousand semiconductors into a dual in-line package is a common occurrence today, but what of the devices which are very difficult to integrate? Items such as tuned circuits are a problem. However, solutions are on the way, in the form of subminiature inductors or "coils".

Described as monolithic chip inductors, these minute devices are made by stacking U-shaped conductor patterns which have been screened onto a special ferrite tape. The U-shaped patterns are stacked such that when the individual ends of each U are connected to the U's above and below, a continuous "coil" pattern is achieved. When this has been done, the complete stack is "fired" resulting in a monolithic structure.

LOOKING AT THE

London ELECTRONIC COMPONENT SHOW

THE four-day London Electronic Components Show at Olympia, London opened on Tuesday 22nd May, the guest of honour at the inaugural luncheon being H.R.H. The Duke of Kent, who later made quite an extensive tour of the Show.

The Show's sponsors, the Radio and Electronic Components Manufacturers Federation, celebrating their 40th anniversary this year, managed to get no less than 480 companies to exhibit the very latest developments in electronic components and associated instruments, equipment and services.

Olympia's two main halls were utilised for this massive event and special preparations were made to receive and attend to the needs of the many visitors from abroad. Almost one-fifth of the stands belonged to exhibitors from overseas with representatives from more than sixteen countries including Australia, Austria, Belgium, Canada, Denmark, Hungary, Japan, West Germany, Spain, Sweden and the USA.

During the Show three discussion and question sessions were held outside at the Royal Westminster Hotel, being arranged jointly by the RECMF and the Institution of Electronic and Radio Engineers. The subject "European Component Survey" covered the aspects of component testing, evaluation and development.


Visitors to the Show were invited to try their luck in various competitions in which very attractive prizes such as an 8-track tape recorder, a £100 watch and even bottles of whisky could be won, not to mention a holiday for two in Rome!

All the components in the world would not be of much use if the many units into which they are fitted could not be connected together by means of efficient


connectors. In 1971 over £22 million of the electronic components market was accounted for by the sale of just such connectors.

About every possible variation of connector was on show with **Amphenol** making them their main theme on their stand together with switches, lamps, relays and indicators. **Ultra Electronic Components** featured a new range of connectors and accessories for use with printed circuit boards as well as an improved version of their 0.1in. pitch modular edge connector. Other products on their stand included plugs and sockets, terminal blocks, rotary wafer switches and water activated batteries.

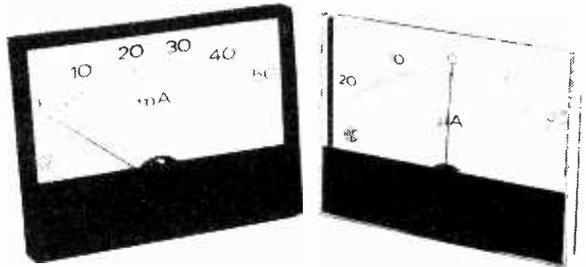AMP of Great Britain also had a wide range of low cost pin and socket and flat flexible cable connectors. They manufacture just about everything needed in solderless, crimped terminations and can supply everything from a single terminal to computer-plotted wiring system components.



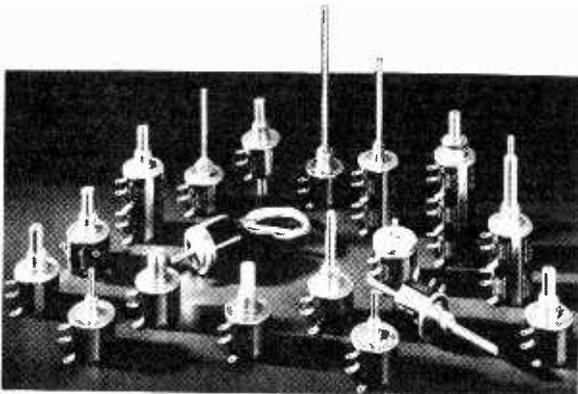In spite of their long and world wide reputation for testmeters, only now have AVO Ltd. started producing a line of panel mounting meters. Two of the new Dineline series are shown above.



Spectrol Reliance Ltd. were justifiably proud of this large number of permutations of their Model 534 'Universal' potentiometer.

AVO celebrated their Golden Jubilee with the introduction of their first-ever range of panel mounting meters. The new Dineline Fifty range marks, not only fifty years of Avo, but also their entry into Europe, with styling based on the rectangular DIN (IEC 51) specification. The matching series of eight models is available in two presentations, a moulded black finish and glass window or clear Macralon ensuring entirely shadow-free readings.

Selectro's stand had their complete range of products which includes RF connectors, multi-pin connectors, plugboards, insulated terminals, rotary switches and punched card readers. Centre piece of this display was the new series of punched card readers, the new 4mm grid plugboard system and the new FR/SR series of two-piece insulated terminals. New items in the RF range include a high isolation coaxial switch and a range of 75 ohm connectors to

DIN 47295. Sealectro's technical staff demonstrated a miniature RF connector assembly using flexible and semi-rigid cables.

Piher International Limited, were exhibiting in the United Kingdom for the first time. Piher are already among the world's leading suppliers of carbon film resistors with a daily output of some seven million resistors from their headquarters at Badalona near Barcelona. Over 90 per cent of their production goes to export markets, principally the United States, Germany and the United Kingdom. On Piher's stand could be seen many samples from their range of carbon film resistors, trimming potentiometers, small signal and medium power transistors and capacitors, and particular interest centred on a new range of preformed resistors.




One of the Series C16 Cermet potentiometers by AB Electronic Components Ltd. Standard models range from 100Ω to 2.5MΩ, linear, but special models down to 50Ω and up to 10MΩ are available, with soldering tags or printed circuit terminals.

Hungary was represented by **Elektromodul** who were showing components for telecommunication, engineering and electronics. Products on display included ferrites, electrolytic capacitors and ceramic capacitors.

Audax SA, from France, exhibited examples from a wide range of loudspeakers, while **Societe Francaise de l'Electro-Resistance** had on display metal film and hi-rel resistors, carbon and cermet track potentiometers and trimmers, plastics potentiometers and cermet film micro-circuits.

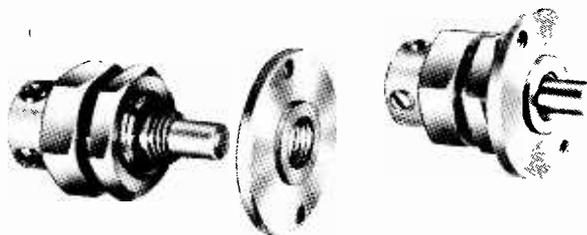Cosmocord-Stolec Limited were showing, for the first time in the United Kingdom, a range of low-cost multimeters and insulation testers, plastics mouldings and audio transcription transducer equipment.



One item from the vast range of drives, dials and tuning capacitors from Jackson Bros. Ltd., a miniature ball drive with a 10:1 reduction, Type 5870.

New ranges of DIN plugs and sockets and instrument components were featured by **Tape Recorder Spares Limited**. Audio and electronic components, switches, mains units, wire measuring and storing equipment and wire cutting and stripping equipment were among other products shown.

Watson Anodising Limited had a range of nameplates, labels, instrument panels, plain and printed chassis as well as examples of the general printing they undertake for the electronics industry.

Rectifiers, thyristors and triacs from **Raytheon-TAG Components Limited** included glassivated and planar plastics encapsulated thyristors and triacs, plastics encapsulated 10A rectifiers to 1300V, fast turn-off rectifiers and diffused SCRs up to 35A and triacs up to 25A RMS.

Radiatron Components Limited stand had a display of components and accessories ranging from collet knobs, instrument cases and housings to relays, connectors, switches and automation modules.

For visitors to the show interested in television, **AB Electronic Components Limited** makers of the only touch tuner made in the United Kingdom, which, when announced last year was the only one made anywhere in the world, is perhaps the best known of their products. Connectors, potentiometers, switches and thick film microcircuits are among others. Sharing AB's stand was **Wolsey Electronics**, a division of AB, showing various aerials and their range of radio and television master aerial and amplifier systems.



This 25-turn preset potentiometer by AB Electronic Components Ltd. is of carbon composition construction intended for use with varicap tuners. Resistance ranges up to 100kΩ in linear, logarithmic or diode characteristic law.

Solder, one of the most important materials used in electronics, was shown in all its forms by **Multicore Solders Limited**. Cored solder, solder creams, bar solders as well as liquid fluxes and chemicals for hand and wave soldering were included in their display. Some 50 per cent of Multicore products are exported to 107 countries throughout the world—one-quarter of the exports going into the competitive U.S.A. market.


Soft solder, fluxes, chemicals, solder preforms and samples from a wide range of solder products were to be seen on the stand of **Enthoven Solders Limited**.

A heavy duty aerial rotator was among communications, marine, television and radio aerial equipment featured by **J-Beam Engineering Limited**.

Communications cables, instrumentation cables, equipment and connecting wires, winding wires, mineral insulated heating cables and thermocouples, solder coated copper wire, silicone insulated fine wires and connectors were displayed by **BICC**.

The wire-wound component is one of the oldest devices used in electronics and remains an important adjunct in the industry. **Gardners Transformers Limited**, who specialise in this field, have orders currently valued at £450,000—a quarter of which come from overseas. They were displaying transformers, inductors, filters, delay lines, inverters, converters, power supplies and modules.

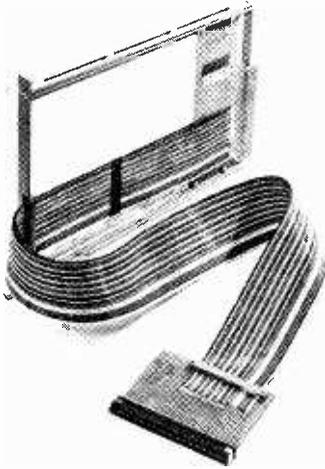Having recently merged with the Allen-Bradley Company of Wisconsin, USA, **Morganite Resistors Limited** had a wide range of resistors, potentiometers, switches, thin film and thick film networks, capacitors,



A Tekdata Ltd. flat flexible cable in FibaTEK p.v.c. material. This custom-made cable uses 7/0.193 and 14/0.193 wires.

filters and industrial controllers from both of their product lines. Not previously shown in the United Kingdom, the Morganite cermet single turn potentiometer, type 90, with a power rating of 0.5 watt and a resistance range of 10 ohms to 2 megohms, is designed for commercial and industrial applications. New from Allen-Bradley is the "Mod-Pot", a variable resistor available in single, dual, triple and quadruple construction plus potentiometers, line switches and vernier drive modules.

A. F. Bulgin & Company Limited commemorate 50 years as electrical and electronic component suppliers. During the last 12 months some 40 new products have been introduced, the complete range now containing over 15,000 items. Examples on show included fuses, fuseholders, knobs, switches, signal lamps, and plugs and sockets.

Custom-built specialists in MOS, bi-polar and hybrid thick film technologies, **GEC Semiconductors Limited** had a new phase control circuit for controlling triacs when driving small electric motors. One interesting device also on display was the MA1705, a MOS integrated circuit developed for use in electronic musical instruments and synthesizers. It generates four notes on an equally tempered scale by dividing successively by 1.0595




The Series 880 focus control has been specially designed by AB Electronic Components Ltd. for colour TV receivers and can be mounted on a metal chassis. The maximum continuous operating voltage is 10kV.

from a single master oscillator. Three packages can be cascaded to produce a complete octave of semi-tones, while further octaves can be generated by using compatible six-stage binary divider circuits.

Among new transistors by **Mullard** for use in high-power, high-quality audio amplifiers are families of complementary pairs that can give outputs of up to 100W. For example, in applications where an output of 6 to 15W is required, pairs from the transistor family BD433 to BD438 are suitable. (Odd numbers are n-p-n types, and even p-n-p.) These have a maximum V_{CEO} rating of 22 to 45V and a total dissipation of 36W.

Silicon power transistors type BD266 and BD267 form a complementary pair that can give a high-quality, audio output of 25W; they are also suitable for use in general purpose amplifiers and switching applications. Both are monolithic epitaxial-base Darlington transistors.

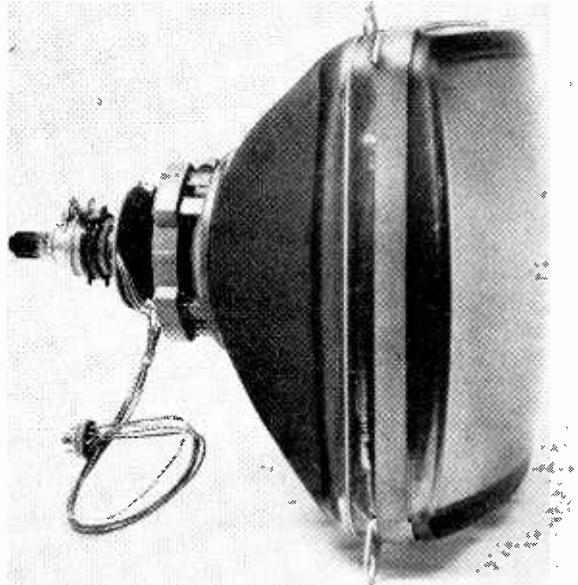Other new Darlington devices seen were types BDX62 to BDX67, which are power transistors with TO-3 encapsulations. Complementary pairs selected from these for use in audio amplifiers will give outputs of 25 to 100W.




Rather large, but a component never-the-less! The A51-160X Precision In-Line colour TV tube assembly features a slotted shadow mask, integral neck components and factory-set static/dynamic convergence and purity adjustments. The June issue of our companion magazine *Television* featured a technical article on the new Thorn tube.

The use of Mullard circuit modules and integrated circuits can reduce the design costs and assembly times of good radio receivers, a.m. and f.m. Different arrangements, demonstrating the ease with which a variety of receivers can be designed, were shown.

New to the United Kingdom and exhibited by **Bird Electronic Limited**, was the Bird model 4370 wide-band Thruline wattmeter and model 4342 combined power meter and VSWR monitor. Coaxial load resistors, attenuators, coaxial switches, filters and calorimeters were also shown.

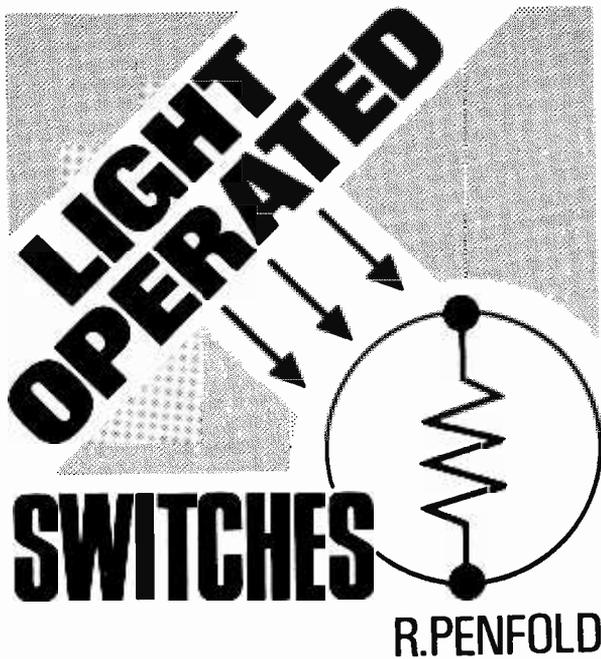Included in the **Spear Engineering Company Limited's** display were power transistor holders, connectors, valve and tube base mouldings and printed circuit assembly fixtures.



on. This causes the voltage at the collector of Tr1 to be at a very low level, and Tr2 receives only a very small amount of base current through R3. This means that Tr2 is turned off, and the relay will not operate.

When light falls on the ORP12, its resistance will decrease and it will have an earthing effect on the base of Tr1. This will cause a decrease in the current flowing through Tr1, and the voltage at the collector will swing to a high level. Tr2 can now obtain quite a heavy base current and will turn on, operating the relay. The voltage at the collector of Tr2 will now be at a low level, and it is Tr1 that is unable to obtain any appreciable base current, and will thus be turned off. Even if the light is now taken off the photocell, the circuit will still remain in the same state, as Tr1 will still be unable to draw sufficient base current due to the low voltage at the collector of Tr2.

The circuit may be reset by two methods. A push-button switch may be connected between Tr2 base and earth. When this is operated it will have the same effect as when light fell upon the photocell, except it will have the opposite result. Alternatively the unit may be turned off, and then turned on again.

A protective diode is connected across the relay in all the circuits shown. This is to prevent the high reverse voltage, which is induced into the relay coil by the collapsing magnetic field as the relay is turned off, from damaging the transistor. Almost any diode will work in this position.

LIGHT operated switches are extremely useful devices which have a number of uses in burglar alarms, automatic parking lights, etc. Most designs for these switches work along the lines of the circuit shown in Fig. 1. The ORP12 photo-resistor is a device which in total darkness has a very high resistance (usually a few megohms), but when light falls upon it, the resistance will fall to a very low level (usually a few hundred ohms).

It will be seen that in the circuit shown in Fig. 1, when there is no light falling on the ORP12, there will be very little base current flowing. In consequence very little collector current will flow and so the relay will not operate. However, when a small amount of light falls on the photocell, its resistance will drop, and a larger base current will flow, causing a larger flow in collector current, which will operate the relay.

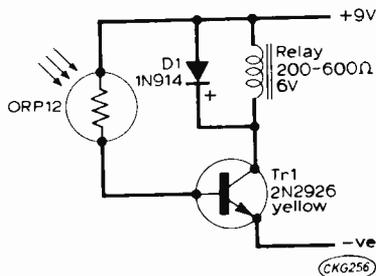


Fig. 1: Typical photoelectric switch.

Latch on circuit

The relay will only remain on for as long as light is falling on the photocell. This renders this type of circuit unsuitable for many applications. For example, if a burglar alarm which is meant to be triggered by the light from the torch of an intruder is required, if the circuit of Fig. 1 is used, the alarm will only sound for the period the torch is aimed at the photocell. This is of course of no use. A circuit which will remain operative once it is triggered is required.

A suitable circuit is shown in Fig. 2, based on a bistable multivibrator. When the circuit is turned on, as there is a far lower resistance to the base of Tr1 through the relay and R2 than there is through R1 and R3 to the base of Tr2, Tr1 is switched hard

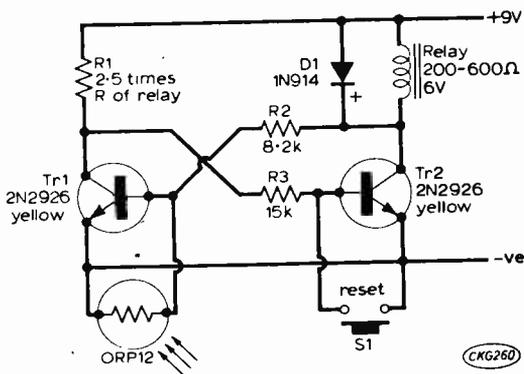


Fig. 2: Circuit suitable for applications where the relay must remain on once operated.

Higher sensitivity

The circuit of Fig. 2 does lack sensitivity and the ORP12 has to be almost fully illuminated before the relay is triggered. A more sensitive circuit is shown in Fig. 3. This circuit requires an extra transistor, and although BC183L is specified, the circuit should work equally well with any high gain, silicon, n.p.n. transistor.

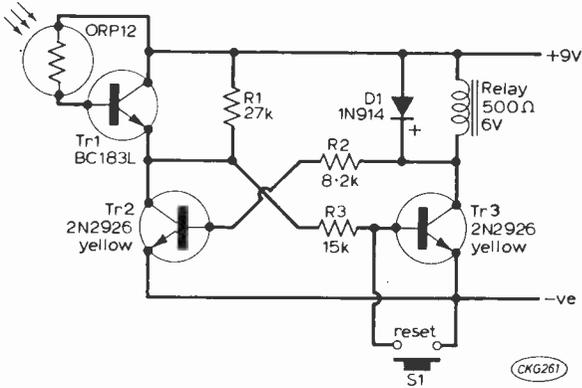


Fig. 3: Sensitive circuit using three transistors. A 25kΩ potentiometer may be placed in series with the ORP12 to control sensitivity.

With no light falling on the photocell it will have a high resistance. Tr1 will receive very little base current, and will have a high resistance between the collector and emitter. R1 also has a fairly high resistance and this will prevent much current flowing to the base of Tr3. This transistor will cut off while Tr2 is turned on, as occurred in the circuit of Fig. 2 when a small amount of light falls on the photocell, its resistance will fall, causing the resistance of Tr1 to fall by a far greater amount.

When this resistance reaches a low enough value, the voltage at the collector of Tr2 will be at a fairly high level. A large base current will now flow, turning on Tr3, and operating the relay. The voltage at the collector of Tr3 will drop, turning off Tr2. If the light is now taken away from the photocell, the resistance between the collector and the emitter of Tr1 will again be very high. The resistance of Tr1 and R1 will be just sufficient to give enough base current to Tr3 to hold the relay on.

Broken light beam alarm

Another type of alarm sometimes used is one in which a beam of light is aimed from one side of a room, or a doorway, to a photocell the opposite side. If anyone then passes between the two, breaking the beam, the alarm is sounded. A suitable circuit for an alarm such as this is shown in Fig. 4.

This works in very much the same way as the two previous circuits. When light is falling on the photocell it will have a resistance very similar to that of R2 in Fig. 2, and the circuit will behave in the same way initially. When the light to the photocell is

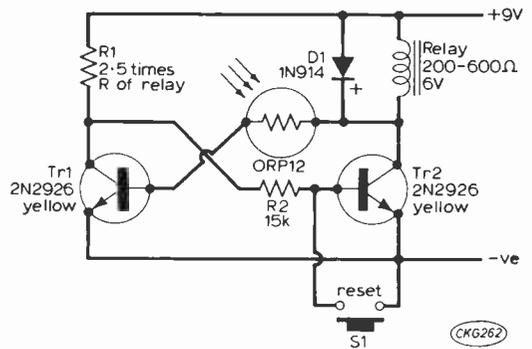


Fig. 4: Circuit for operating in a dark room.

interrupted, it will exhibit a high resistance. Tr1 will receive very little base current, the voltage at its collector will rise, Tr2 will be able to obtain a large base current, and will turn on. The voltage at the collector of Tr2 will drop and, even if light is now restored to the photocell, Tr1 will be unable to draw any appreciable base current. Thus Tr2 is able to draw a heavy base current and the relay remains on.

The circuit may be reset in the same way as the two previous circuits. For the circuit to function correctly, the room in which the photocell is situated has to be fairly dark, of course, or the light in the room will keep the relay off, regardless of the light beam.

These circuits are all fairly simple, and inexpensive, but should prove useful and interesting. With a little imagination a number of uses, other than those mentioned, may be found for the circuits. ■

OCTOBER IS ISSUE No.800

Will you be celebrating with us?

If so you will receive with your October copy of *Practical Wireless* the first pair of **PW Databards** absolutely free. A special "Going Back" feature with reproductions from early issues of *Practical Wireless*; the introductory article in our new series on Q4; "Experimental Workshop" and many other special and regular features will also appear. Further details next month.

The October issue is on sale September 7th.

IN NEXT MONTH'S

PRACTICAL WIRELESS

THE FIRST OF OUR SPECIAL AUTUMN ISSUES....

... will give full details of how to make our two-band, two-i.c. "pop" radio receiver,
... will give full details of the PW Datacard System announced elsewhere in this issue.
... will reveal the identity of Q4,
... will contain straightforward constructional projects designed around integrated circuits,

PW POP STAR ★

Specially designed to simplify construction, this smart looking radio uses two integrated circuits: a ZN414 for processing radio signals and an SL403D as the amplifier to drive an 8- or 15-ohm loudspeaker. Medium wave stations and Radio 2 (long wave) are covered with a very simple aerial coil; no alignment problems arise. The amplifier is designed to give 1 to 3 watts of output power and is ideally suited for a teenagers' room, kitchen, bathroom, in fact almost anywhere.



* SIMPLE 2-BAND RECEIVER

I.C.

ANALOGUE D.C. VOLTMETER



This very simple instrument is based on the popular 741 i.c. and with a minimum of other components is capable of voltage measurements up to 100 volts d.c. in five ranges. Accuracy on low voltage ranges is very good and the input sensitivity is much greater than in the conventional multimeter.

Also:


Short-Wave Converter for your MW receiver

&

I.C. POWER REGULATOR MODULE

*

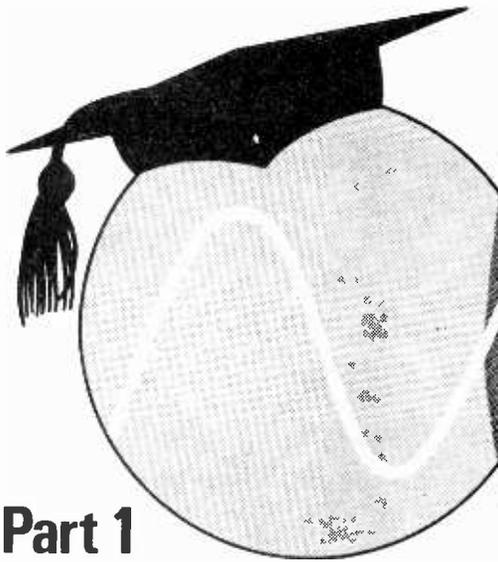DON'T MISS ANY ISSUE OF PRACTICAL WIRELESS • SEPTEMBER ISSUE ON SALE AUGUST 3rd



pw 'Student' OSCILLOSCOPE

Part 1

SIMPLE TO BUILD • INEXPENSIVE • ONE

IT occurred to the writer that many readers, being 'brought up' on transistors, would not have had the opportunity to learn about the oscilloscope from the 'bottom up' and that a basic transistorised design, with modern construction methods, would be welcomed.

An oscilloscope should be a substantial piece of equipment, and in view of the high voltages employed (700V for the e.h.t. and 300V for the deflection amplifiers) it must be emphasised that the rather solid nature of the model is deliberate.

Another feature is the simplification of the controls on the front panel, these being; brilliance, focus, Y attenuation (Y amp), Y shift, timebase coarse control in 6 ranges, timebase fine control (fine), timebase amplitude (X amp), and sync on/off.

There is a Y input socket and an external timebase input socket.

The writer has noticed that it is usually necessary to attenuate the input signal rather than amplify it, and with transistorised equipment the signal which is being examined can be dealt with quite effectively by an attenuator of the 'volume control' type. This makes it necessary to turn the Y attenuator down to zero before connecting a signal to the Y input socket but once this habit has been formed, the simplification of having just one continuously variable gain control with a d.c. amplifier is evident. The d.c. amplifier is necessary to maintain a good low frequency response, especially with square wave signals.

The Cathode Ray Tube

The cathode ray tube (c.r.t.) itself is a form of valve, having a heater and a cathode, a control grid and anode—which must be at a high positive potential (e.h.t.) with respect to the cathode.

For a 3in. c.r.t. the e.h.t. should be of the order of 900/1000V.

Between the control grid and the final anode are the first and focusing anodes. There are also two pairs of deflection plates, one pair—the Y plates—for vertical deflection, and the other pair—the X plates—for horizontal deflection. The deflection plates are usually operated in push-pull and with 1000 volts across the c.r.t. the push-pull voltage swing needs to be about 150V. This makes it necessary to have a 300V supply to the deflection amplifiers and the deflection transistors must be able to withstand this voltage.

The design utilises the 3BP1, c.r.t. which has a heater requirement of 6.3V at 0.6A. The c.r.t. has a 14 pin base with a locating spigot and the base connector should be obtained (if possible) when purchasing the c.r.t.


The tube gives a green trace of medium short persistence and a useful trace height is 5cms. The c.r.t. is approximately 10 inches in length including the base.

Cathode ray tubes are sensitive to stray magnetic fields, such as those produced by mains transformers, and even when a mu-metal shield is utilised to screen the c.r.t., transformers on the same chassis usually cause some interference to the spot. Mu-metal shields are quite expensive (when available).

In the present design, the mains transformers are fitted on a separate chassis, connected together by a multiway lead. By using this method, the problem of interference from the mains transformers was eliminated.

The Y (Vertical) Amplifier

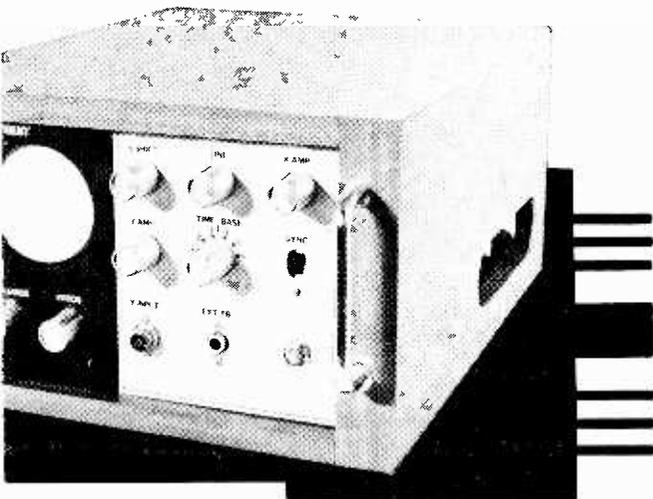The input to the Y amplifier is through a 'volume control' type attenuator VR1, and it is taken directly to the base of Tr1, which with Tr2 forms a boot-



G.A.COZENS ASSEMBLY BOARD

strapped amplifier with an input impedance of about $1\text{m}\Omega$. If the reader wishes, a $0.1\mu\text{F}$ capacitor (Cx) can be inserted in the lead from the slider of VR1 to the base of Tr1, with a shorting switch across it, to give a.c./d.c. facilities, but it must be pointed out that this is a sensitive part of the circuit, and all leads must be kept as short as possible to avoid stray pick up.

The output from the signal amplifier is passed through a resistor network to the long tailed pair which form the vertical deflection amplifier Tr3 and Tr4. This stage performs two functions:

1. To give two outputs which are 180° out of phase and supply the push-pull voltages to the vertical deflection plates.

2. To provide a voltage swing of 150V at each deflection plate.

When the base of Tr3 goes positive its collector goes negative. That is, the signal is inverted at Tr3 collector.

Also Tr3 emitter goes positive. This means that Tr4 emitter goes positive. The base bias of Tr4 is held at a fixed level by the bias network VR2 R15. As the potential difference between Tr4 base and emitter is decreasing the base of Tr4 is in effect going negative.

This causes the collector of Tr4 to move in a positive direction, which is the same as the original signal at Tr3 base. Thus Tr3 collector is the inverting output and Tr4 collector is the non inverting output.

The network R7, R8, R9 is designed to bias the base of Tr3 and prevent overloading, and the base bias of Tr4 is made variable to balance with Tr3 base and centre the trace on the screen. VR2 is therefore the Y shift. C2 by-passes any a.c. signals present at Tr4 base.

The collectors of Tr3 and Tr4 are connected directly to the Y plates. The values of the collector resistors were chosen by trial to balance the collector outputs, and the emitter resistors R11 and R14, and the coupling resistor R12, which controls the gain of

SPECIFICATION

Y Signal

Input via co-axial lead

Attenuator continuously variable

Input Impedance $1\text{M}\Omega$

Sensitivity on full gain 100mV r.m.s. gives trace height of 3cms p. to p.

Bandwidth d.c. to 1MHz .

Useful trace height 5cms.

X Deflection,

Sensitivity on external timebase 100mV r.m.s. gives trace width of 1cm p. to p.

Useful trace width 5 cms.

Timebase in 6 ranges.

Range;

1. 10—100Hz

2. 32—170Hz

3. 150—550Hz

4. 520Hz—3.5 kHz

5. 3.0—20kHz

6. 6.0—40kHz

Controls

Front Panel

Brilliance

Focus

Timebase fine frequency

Timebase range (course)

Timebase amplitude

Sync on/off

Side of Chassis

X linearity

X shift

Y gain

Y shift

X Signal

Astigmatism

the stage, may also be altered to match the transistors. When the trace is centred and no signal is present the collector voltages should be 180V. The maximum height of the Y trace when using a 100mV input signal (VR1 at maximum) is 3cms.

The Timebase Generator and X Amplifier

The timebase waveform generator Tr7 is a uni-junction transistor (TIS43) with Tr6 acting as a constant current device to regulate the charging of the timing capacitors (C5, C6, C7, C8, C9 and C10) and to give a linear rise time.

The fine frequency control (VR3) should be wire-wound and it should be possible to steady the trace at any part of the frequency range without using synchronisation. There is some loss of amplitude on the upper timebase range.

The sawtooth signal is taken from the emitter of Tr7 to the base of Tr8, via a closed circuit jack JK1 and a $0.1\mu\text{F}$ capacitor C12. The output signal from Tr8 collector is fed via capacitor C13 to the timebase amplitude control VR4.

The horizontal deflection amplifiers Tr9 and Tr10 are a long tailed pair with a common emitter resistor R31. Bias for Tr9 is by potentiometer network R28 R29 and as in the Y amplifier, the base bias of the second transistor Tr10 is made variable to act as a shift control to centre the trace on the c.r.t. screen. C17 by-passes any a.c. signals and stabilises the trace.

Synchronising

The purpose of synchronisation is to lock the time-base frequency to the Y signal and so hold a given number of complete waveforms steady on the screen.

The Y signal is taken from the emitter of Tr3 and is passed via C4 to the base of Tr5. Tr5 is driven hard by the Y signal and this produces a square wave at the collector of Tr5.

C3 and R16 form a pulse shaper and the diode D1 passes the positive going pulse to b2 of the uni-junction sawtooth generator Tr7.

The d.c. potential to b2 is stabilised by the zener diode D2. R24, C11 and the decoupling resistor R23 all contribute to improved synchronisation of the timebase.

The Power Supplies

Five a.c. supplies are required from the mains transformers, they are:

1. 6.3V at 0.6A for the c.r.t. heater (T2)
2. 250V at 2mA for the e.h.t. multiplier circuit (T2)
3. 15 to 22V at 500mA for the low voltage line (T3)
4. 250V at 50mA for the high voltage 300V d.c. line (T1)
5. 6.3V 0.6A for indicator lamps (T1)

The leads from the oscilloscope chassis are taken to the transformer subchassis and terminate in a multiway plug. It is suggested that constructors utilise a 10 way Jones plug and socket, for the inter-connection.

★ components list

Resistors

R1	4.7kΩ	R25	10MΩ
R2	2.2kΩ	R26	12kΩ
R3	47kΩ	R27	12kΩ
R4	100Ω	R28	3.3MΩ
R5	8.2kΩ	R29	18kΩ
R6	1kΩ	R30	47kΩ 1W
R7	8.2kΩ	R31	120Ω
R8	2.2kΩ	R32	47kΩ 1W
R9	1.8kΩ	R33	3.3MΩ
R10	68kΩ	R34	2.2MΩ
R11	390Ω	R35	2.2MΩ
R12	56Ω	R36	10kΩ 1W
R13	82kΩ	R37	10kΩ 1W
R14	470Ω	R38	1.2kΩ 1W
R15	5.6kΩ	R39	390Ω 1W
R16	1MΩ	R40	1.2kΩ 1W
R17	22kΩ	R41	1.2kΩ 1W
R18	1.5MΩ	R42	390kΩ 1W
R19	10kΩ	R43	8.2kΩ
R20	82kΩ	R44	1MΩ
R21	8.2kΩ	R45	680kΩ
R22	47Ω	R46	100kΩ
R23	470Ω	R47	100kΩ
R24	680Ω		

All ± 10% ½W carbon except where stated otherwise.

Transistors:

Tr1, Tr2, Tr5, Tr8	BC109
Tr3, Tr4, Tr9, Tr10	MJE340
Tr6	ASY26
Tr7	TIS43

Diodes:

D1	1N4148 or 1N914
D4, D5, D6	1N5054 or PL4007
D7, D8	400 p.i.v. 1A
D2	12V 1W
D3	18V 1W

Transformers:

T1, T2	Primary 200–250V 50Hz Sec. 250V 60mA, 6.3V 2A
T3	Primary 200–250 50Hz Sec. 18V 1.25A

Capacitors:

C1	100μF elect 25V
C2	0.47μF 250V
C3	0.1μF
C4	0.022μF
C5	0.68μF
C6	0.1μF
C7	0.02μF
C8	0.005μF
C9	0.001μF
C10	0.0005μF
C11	100μF elect 25V
C12	0.1μF
C13	100μF elect 25V
C14	100μF elect 25V
C15, C16, C17	0.47μF 250V
C18, C19, C24	50μF + 50μF + 50μF elect 350V
C20, C26	32μF + 32μF elect 350V
C21, C22	500μF elect 25V
C23, C25	250μF elect 50V
C27, C28, C29, C30	0.47μF 1000V
Cx	see text

Potentiometers:

VR1	2MΩ carbon
VR2	2.5kΩ w.w. linear
VR3	50kΩ w.w. linear
VR4	25kΩ w.w. linear
VR5	25kΩ w.w. linear
VR6	250kΩ carbon
VR7	250kΩ carbon
VR8	250kΩ carbon
VR9	50kΩ carbon

} good quality well insulated

CRT: 3BP1

Switches:

S1	2 pole c/o slide
S2	1 or 2 pole 6 way rotary. Only 1 pole used
S3	On/off mains toggle switch
JK1	Closed circuit p.o. type jack

Miscellaneous:

Veroboard, 0.15in matrix 3½ins. x 17ins. Veropins. 2, 4, 6BA screws, nuts, washers and spacers, panel lamps, coaxial sockets, systoflex, cleats, grommets, chipboard, laminated plastic sheet, 4 instrument handles, 8 rubber feet, aluminium for metalwork.


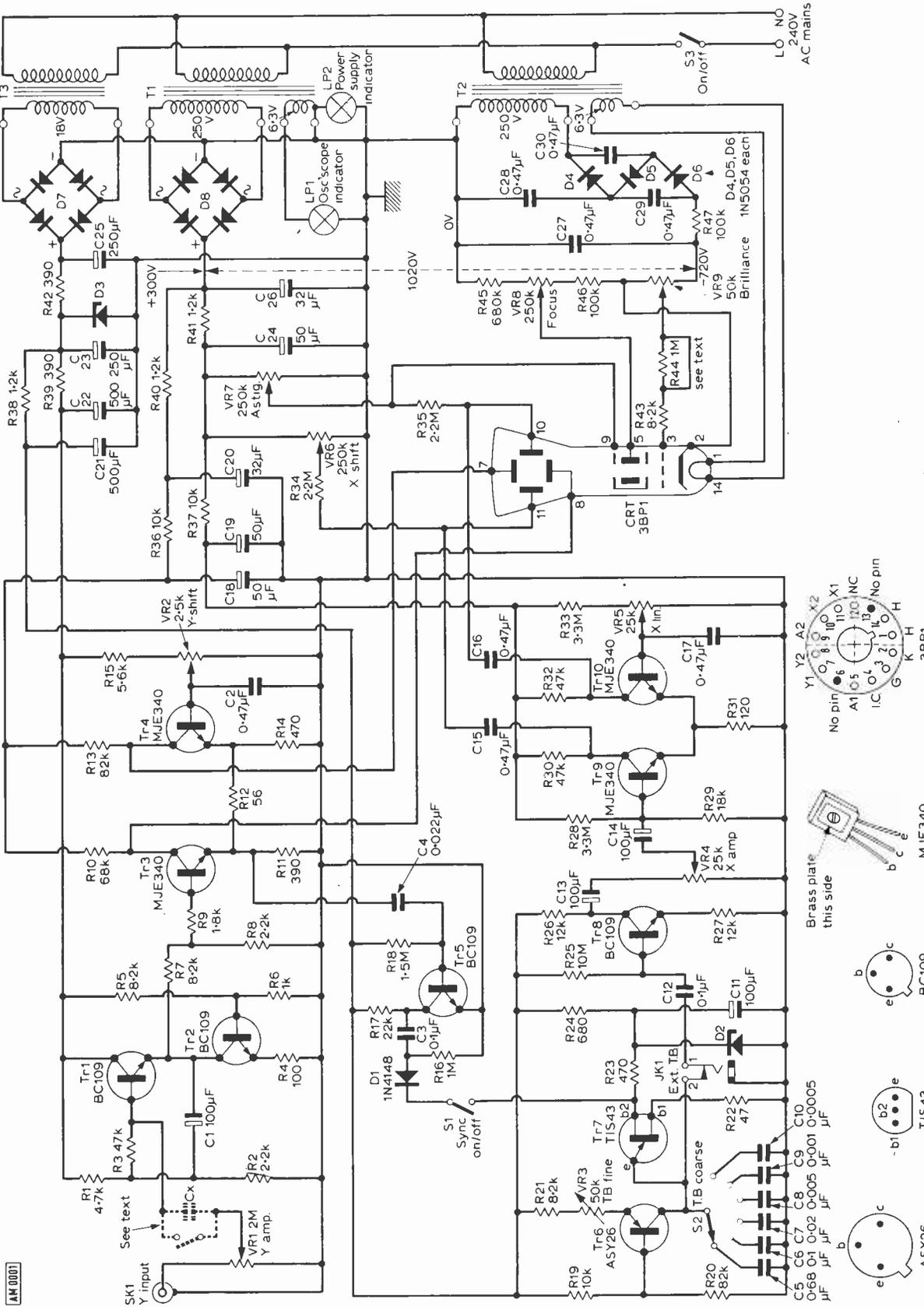
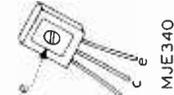


Fig. 1: Complete circuit of the P.W. Student Oscilloscope.

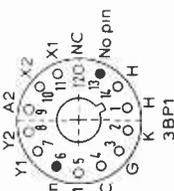

AK 0001

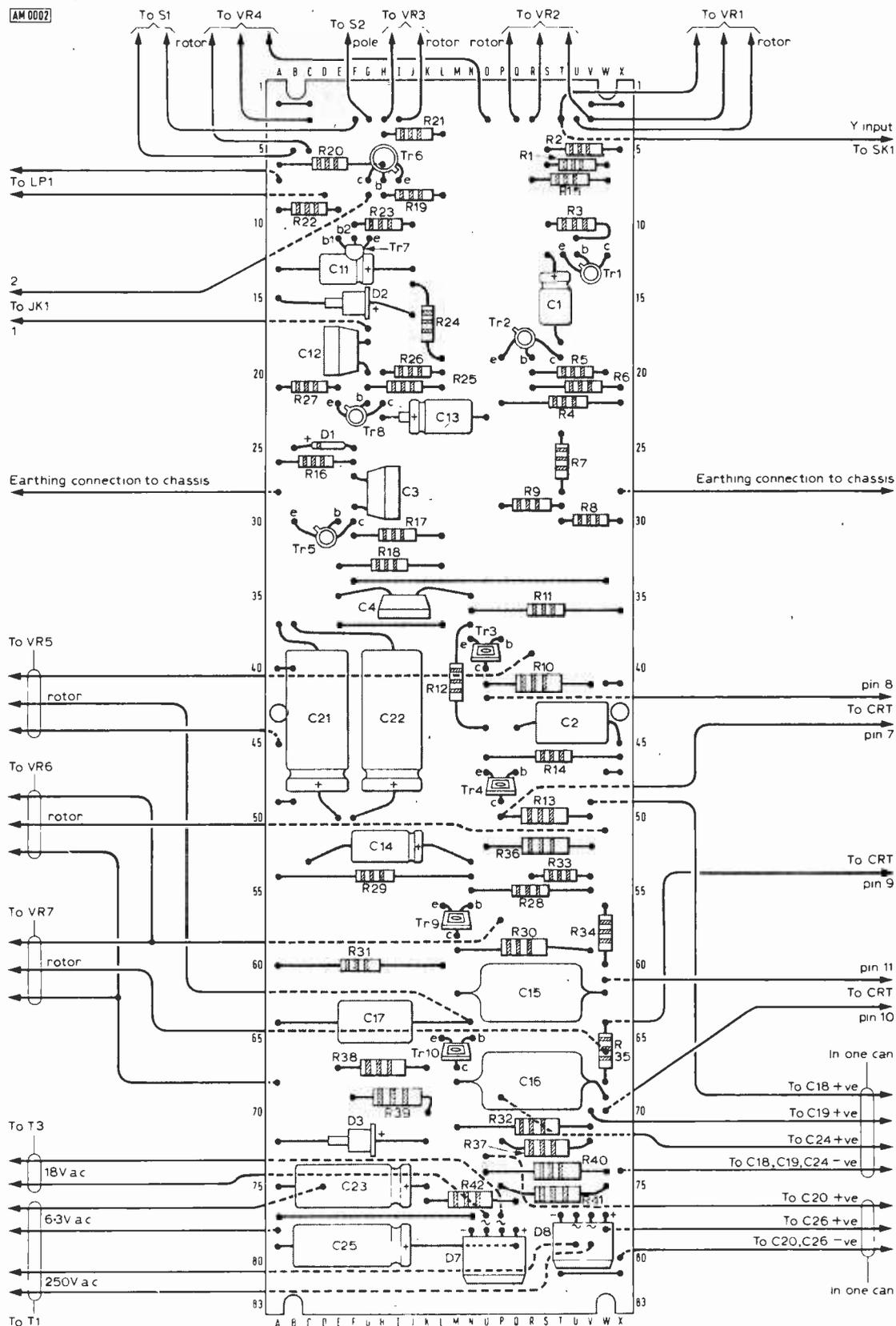


Fig. 2 The complete Veroboard layout for the oscilloscope.

The tube heater winding must withstand 1000V to the chassis. If the insulation breaks down it will put the whole e.h.t. voltage between heater and cathode of the c.r.t. The writer has not had this fault occur on any standard mains transformers that he has used. Well insulated twin flex of the type used for mains wiring is suitable for the c.r.t. heater leads.

Three rectifier diodes are used in the e.h.t. multiplier circuit. Although this type of circuit suffers from poor regulation, in this case, where the current required is only about 1mA it is quite stable.

The capacitors C28, C29 C30 help to maintain good regulation. The diodes are arranged to give a negative output, the positive end of the chain is at earth potential.

The circuit is so arranged that the 700V e.h.t. supply and the 300V line are in series. Therefore the voltage across the c.r.t. from the grid to the final anode, is equal to the sum of the two voltages.

The c.r.t. resistance network acts as a bleeder across the e.h.t. and the smoothing resistor R47 and the network should be fitted before the circuit is tested. It will limit the e.h.t. voltage and prevent possible damage to the smoothing capacitor C27.

The 1M Ω resistor R44 may be included in the circuit if flyback blanking is to be added later. Because of the unusual layout of the e.h.t. multiplier circuit extra care must be taken in layout and wiring.

The low voltage line is supplied from transformer T3 which gives an output of between 15 and 22 volts, the bridge rectifier being rated at 400V p.i.v. at 1A and the reservoir and smoothing capacitors at 50V. The smoothing resistor R42 has a value of 390 Ω and the zener diode D3 stabilises the line at 18V. The Y amplifier and the timebase circuit have separate smoothing components to reduce inter-action.


The high voltage 300V d.c. line is supplied by the bridge rectifier D8 which is rated at 400V 1A. The reservoir capacitor C26 is 32 μ F and is of the can variety. Each deflection amplifier has its own decoupling components to prevent crosstalk and the astigmatism and X shift potentiometers are in parallel across the 300V d.c. line and act as bleeders.

When the writer commenced his experiments with this oscilloscope, the method used for X and Y shift was similar to that employed in valved instruments, where the deflection plates were coupled to the valve anodes through capacitors and the shift voltages were determined by potentiometers across the positive end of the network. This method has been retained for the X deflection plates, the X amplifier being a.c. coupled throughout.

The Y amplifier is d.c. coupled and the Y shift is determined by the potential at the collectors of Tr3 and Tr4. This means that the signal level at Tr3 base must be matched by that at Tr4 base to keep the trace on the screen. The X shift can be set and needs no further attention, but the Y shift must be adjusted for positive or negative going signals and for changes in amplitude.

The Veroboard Panel

The Veroboard panel is 24 holes (or strips) wide and 83 holes long. This is cut from a standard 17in. x 3 $\frac{3}{4}$ in. Veroboard panel. The matrix is 0.15in. When working on the panel it is essential to make all joints with the minimum of solder. Where flexible leads are taken to components on the Veroboard, Veropins or the wire ends of components already attached to the copper strips should be used as anchoring points.

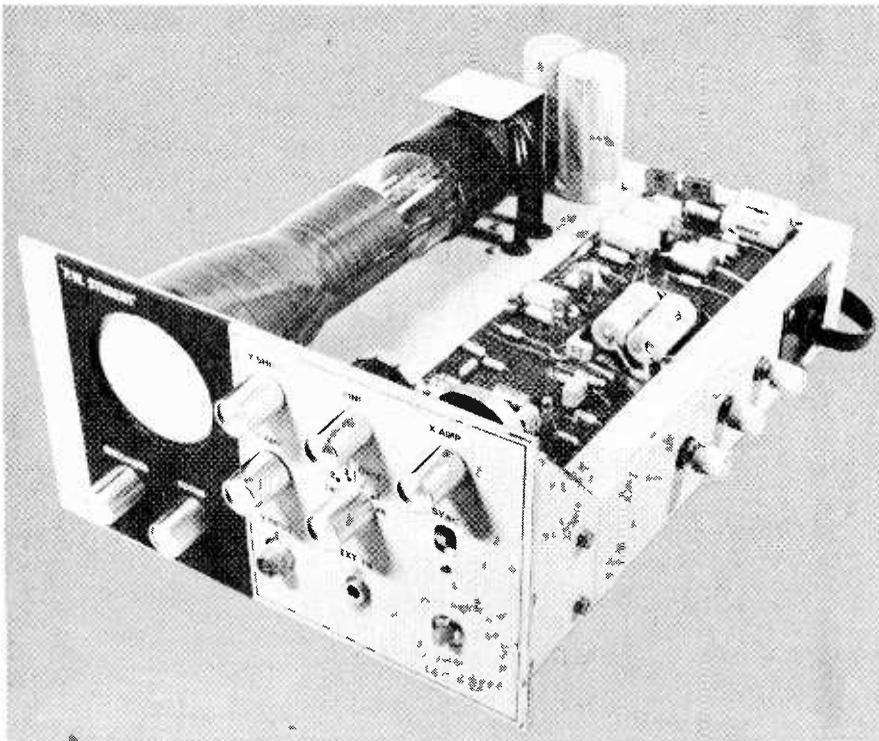

Photograph showing the completed oscilloscope. The three controls on the right hand side of the chassis are X linearity, X shift and astigmatism.

—to be continued—



Readers' Logs

The first log this month comes from **Roy Patrick** of Derby who returns to the page after a considerable absence. Welcome back OM. Roy's equipment consists of a Trio 9R59D receiver and an Eddystone 840. Stations logged included:

- 3240 R. *Baghdad, Iraq* in Arabic at 2000.
- 4945 R. *Colosal, Colombia* at 0700.
- 4980 *Ecos del Torbes, Venezuela* at 0605.
- 4995 R. *Brazil Central* at 2200.
- 11650 R. *Bangladesh* in English at 1700.
- 11710 RAE, *Argentina* noted at 2300.
- 11720 R. *Nacional, Brazil*, fair at 2100.
- 11725 R. *Ceylon* in English 1800-1830.
- 11790 R. *Australia* to SE Asia at 1800.
- 11800 R. *Ceylon* in Hindi, good at 1830.

Michael Johnson of Hockley in Essex describes his equipment as follows: "I use an ex-radiogram, 6 valve, Ferguson receiver; coupled with the dipole of an old 405 line TV aerial which works better than my 50 foot dipole on 31 metres!" This equipment enabled him to hear the following stations:

- 6050 RAI, *Italy* in English at 1935.
- 6070 R. *Sofia, Bulgaria* in English at 1930.
- 6185 R. *Norway* in English at 1700.
- 6580 R. *Pyongyang, N. Korea* at 1900.
- 7290 *Trans World Radio* in English at 1045.
- 9545 R. *Ghana, Accra* in English at 2145.
- 9670 R. *Trans-Europe* in English at 2000.
- 9840 *Voice of Vietnam* at 1915.
- 11880 *Voice of Turkey, Ankara* noted at 2200.
- 15185 R. *Finland* in English at 1800.
- 15415 R. *Kuwait* in English at 1645.

Messrs. **Wormleighton and Fletcher** of Rencomb College, Cirencester have sent in another excellent log using the following equipment: HRO with 8 metre folded dipole; Astrad-Altair with 150 foot long-wire, Bush PB63 with 35 foot long-wire.

- 5990 HCJB, *Quito, Ecuador* in English at 0825.
- 6050 RAI, *Italy* in English at 2030.
- 7235 R. *Australia* in English at 1500.
- 9525 RSA, *South Africa* noted at 2215.
- 9710 HCJB, *Quito, Ecuador* in English at 0715.
- 9715 R. *Nederland, Bonaire*, English at 0845.
- 9805 R. *Cairo, U.A.R.*, in English at 2200.
- 11745 HCJB, *Quito, Ecuador* in English at 0730.
- 11880 *Voice of Turkey, Ankara*. English at 2200.
- 11920 RNE, *Spain* in Spanish at 1300.
- 11945 R. *Voice of the Gospel, Ethiopia* at 1930.
- 11970 RSA, *South Africa* at 1900, News in English.
- 15415 R. *Kuwait* in English at 1730.
- 21545 R. *Ghana, Accra* in English at 1500.
- 21595 R. *Canada International* noted at 1640.

SHORT WAVE DX

by MALCOLM CONNAH

JUDGING from some of the letters and enquiries that I receive it would appear that many of you do not know of the existence of *The World Radio and TV Handbook*.

The book contains a list, by countries, of all the Broadcasting stations in the world. Each entry shows details of the station schedule including frequencies and language used; other details given are the station address and its QSL policy. The interval signal of the station is given along with the opening announcement which is the easiest way of identifying the station.

The first section of the book has various articles on Broadcasting subjects, which are useful to beginners and experienced DXers alike. The final pages of the book contain a listing, by frequency, of all the stations complete with call-sign and transmitter power.

The book is available through most good bookshops, the price is £3 which is a small price to pay for such a mine of information.

DX News

BANGLADESH: Radio Bangladesh now starts the English service at 1700 instead of 1715 on frequencies of 11650 and 15520kHz.

GABON: Plans are afoot for the installation of several 300kW shortwave transmitters to be used by both ORTF and Radiodiffusion TV Gabonaise. Libreville has been heard on the new frequency of 7130 from 1230 to 1430.

GRENADA: Radio Grenada, formerly Windward Islands Broadcasting Service, has moved from 11930 to 15105kHz for its transmissions to the U.K. at 1945-2130.


MONGOLIA: Radio Ulan Bator now also broadcasts programmes in English and French to Africa at 2000-2030 on 17780 and 17860kHz. The programmes in English are broadcast every Wednesday and Saturday, and in French every Tuesday and Friday. There are also programmes in English daily, except Sunday evening and Monday morning, at 1200-1250 on 17780 and 17860, and at 2200-2230 on 11810 and 11860kHz.

look!

electronics really mastered

... practical
... visual
... exciting!

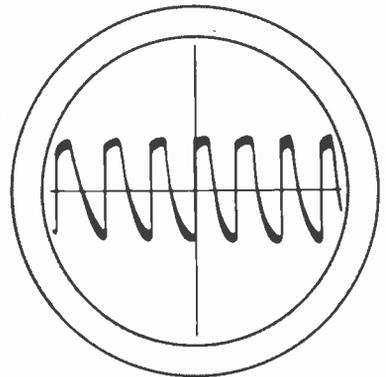no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

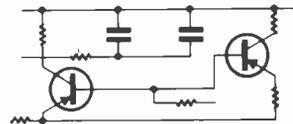2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a c experiments, d c experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required !: will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL83

special free gift also to all our students

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX

All prices include of V.A.T. Telephone 6743

OA2	.33	6B7G	.43	6N7GT	.40	12SH7	.15	50CD6G	2.17	EA50	.27	EF73	.75	HVR2	.58	PL36	.46	UL84	.28	AC128	-.92	BC118	-.95	OA70	-.17
OB2	.33	6B7G	.39	6Q7G	.35	12SH7	.28	50EH5	.55	EA76	.88	EF83	.21	HVR2A	.58	PL81	.42	UM80	.33	AC132	-.92	BC310	-.50	OA73	-.17
OZ4	.44	6B7G	.38	6Q7G	.35	12SH7	.28	50FGT	.45	EA080	.29	EF85	.25	KT2	.25	PL81A	.48	UY41	.38	AC154	-.28	BCY12	-.55	OA79	-.10
1A3	.49	5BR7	.79	6Q7(M)	.43	12SQ7	.48	85A2	.43	EA091	.38	EF86	.27	KT41	.98	PL82	.28	UY95	-.23	AC156	-.22	BCY33	-.22	OA81	-.10
1A7GT	.33	6BR8	.83	6R7G	.35	14H7	-.48	85A3	-.40	EA42	.48	EF89	.28	KT44	1.00	PL83	.30	U10	-.45	AC157	-.28	BCY34	-.25	OA85	-.09
1B3GT	.49	6BS7	1.25	6R7M	.55	14H7	-.48	90C1	.59	EA601	.50	EF91	.17	KT81	2.00	PL84	.80	U12/14	-.38	AC165	-.28	BCY38	-.25	OA90	-.14
1HG6T	.55	6BW6	.72	6SA7M	.35	19AQ5	.29	90CG	1.70	EB34	.20	EF92	.28	KT66	2.00	PL604/508	.50	U19	1.73	AC166	-.28	BCY39	-.28	OA91	-.10
1L4	.14	6BW7	.50	6SC7GT	.33	19CG6	.60	150B2	.58	EB41	.48	EF97	.55	KTW61	.63			U22	.89	AC168	-.42	BCY41	-.42	OA95	-.10
1NG6T	.60	6BZ6	.31	6SG7	.39	20D4	1.05	807	.59	EB091	.48	EF98	.65	KTW62	.63	PL508	.90	U25	.65	AC176	-.61	BCY48	-.32	OA200	-.08
1R6	.28	6CB6A	.28	6SH7	.35	20P2	.65	5763	.50	EBF80	.48	EF183	.25	KTW63	.60	PM84	.31	U26	.60	AC177	-.31	BF159	-.28	OA202	-.11
184	.33	6C4	.28	6MJ7	.35	20P1	.50	5765	.70	EBF83	.38	EF184	.27	MHL26	.75	PY33/2	.50	U191	.65	ACY17	-.28	BF163	-.22	OC22	-.42
1U4	.44	6C9	.73	6SK7GT	.25	20P3	.76	AC/PEN	.98	EBF89	.26	EF185	.25	P61	.40	PY80	.38	U251	.62	ACY18	-.22	BF173	-.42	OC23	-.42
1U5	.80	6CD6G	1.06	6SG7GT	.38	20P4	.89	AC2/PEN	.80	EBL21	.60	EF186	.27	PC86	.24	PY81	.34	U301	-.40	ACY19	-.21	BF180	-.33	OC24	-.42
2D21	.44	6CD8A	.50	6U4GT	.60	20P5	1.00	DD	.98	EC86	.59	EF187	.28	PC86	.24	PY82	.34	U403	1.73	ACY20	-.20	BF181	-.44	OC25	-.42
2GK5	.55	6CH6	.55	6V8GT	.17	20P6	1.00	DD	.98	EC86	.59	EF188	.28	PC86	.24	PY83	.34	U403	1.73	ACY21	-.20	BF182	-.44	OC26	-.42
3A4	.36	6CL6	.43	6V8GT	.27	20P7	1.00	DD	.98	EC86	.59	EF189	.28	PC86	.24	PY84	.34	U403	1.73	ACY22	-.20	BF183	-.44	OC27	-.42
3D6	.19	6CM7	.50	6X4	.20	25A6G	.29	AC/PEN	.98	EC88	.59	EF190	.28	PC86	.24	PY85	.34	U403	1.73	ACY23	-.20	BF184	-.44	OC28	-.42
3Q4	.49	6CU5	.30	6X5GT	.25	25L6G	.20	AC/TP	.98	EC88	1.50	EF191	.28	PC86	.24	PY86	.34	U403	1.73	ACY24	-.20	BF185	-.44	OC29	-.42
3Q6GT	.55	6CW4	.83	7B8	.58	25T2A	.28	AL60	.78	EC88	.55	EF192	.28	PC86	.24	PY87	.34	U403	1.73	ACY25	-.20	BF186	-.44	OC30	-.42
384	.26	6DE7	.50	7B7	.32	25Z5	.40	ATP4	.40	EC88	.68	EF193	.28	PC86	.24	PY88	.34	U403	1.73	ACY26	-.20	BF187	-.44	OC31	-.42
4CB6	.55	6DT6A	.50	7H7	.28	25Z6G	.43	AZ1	.40	ECC81	.18	EF194	.28	PC86	.24	PY89	.34	U403	1.73	ACY27	-.20	BF188	-.44	OC32	-.42
4CB6	.55	6DT6A	.50	7H7	.28	25Z6G	.43	AZ1	.40	ECC81	.18	EF195	.28	PC86	.24	PY90	.34	U403	1.73	ACY28	-.20	BF189	-.44	OC33	-.42
4T4	.36	6E5	.55	7Y4	.60	30C15	.55	CL33	.90	ECC82	.21	EF196	.28	PC86	.24	PY91	.34	U403	1.73	ACY29	-.20	BF190	-.44	OC34	-.42
5U4G	.30	6E1	.59	7Z4	.50	30C17	.74	CV63	.53	ECC82	.32	EF197	.28	PC86	.24	PY92	.34	U403	1.73	ACY30	-.20	BF191	-.44	OC35	-.42
5V4G	.35	6E6G	.35	9BW6	.50	30C17	.74	CV63	.53	ECC82	.32	EF198	.28	PC86	.24	PY93	.34	U403	1.73	ACY31	-.20	BF192	-.44	OC36	-.42
5Y3GT	.30	6F13	.33	9D7	.78	30F5	.69	CV16	.55	ECC86	.48	EF199	.28	PC86	.24	PY94	.34	U403	1.73	ACY32	-.20	BF193	-.44	OC37	-.42
5Z4G	.34	6F14	.40	10C2	.49	30F11	.58	CV31	.59	ECC88	.35	EF199	.28	PC86	.24	PY95	.34	U403	1.73	ACY33	-.20	BF194	-.44	OC38	-.42
5Z4GT	.38	6F18	.45	10D7	.50	30FL2	.60	DAF91	.22	ECC89	.48	EF200	.28	PC86	.24	PY96	.34	U403	1.73	ACY34	-.20	BF195	-.44	OC39	-.42
6C0L2	.55	6F23	.65	10P1	.75	30FL2	.67	DAF96	.36	ECC90	1.00	EF201	.28	PC86	.24	PY97	.34	U403	1.73	ACY35	-.20	BF196	-.44	OC40	-.42
6A8G	.44	6F24	.63	10P9	.45	30FL3	.47	DF91	.14	ECC92	.25	EF202	.28	PC86	.24	PY98	.34	U403	1.73	ACY36	-.20	BF197	-.44	OC41	-.42
6A07	.15	6F25	.51	10F18	.35	30FL3	.47	DF91	.14	ECC92	.25	EF203	.28	PC86	.24	PY99	.34	U403	1.73	ACY37	-.20	BF198	-.44	OC42	-.42
6A05	.27	6F28	.60	10LD11	.54	30FL4	.58	DF96	.34	ECC96	.64	EF204	.28	PC86	.24	PY100	.34	U403	1.73	ACY38	-.20	BF199	-.44	OC43	-.42
6A16	.50	6F32	.15	10P13	.54	30FL5	.65	DF96	.34	ECC96	.64	EF205	.28	PC86	.24	PY101	.34	U403	1.73	ACY39	-.20	BF200	-.44	OC44	-.42
6A15	.75	6F18A	.50	10P14	1.08	30P4MR	.95	DK40	.55	ECH21	.83	EF206	.28	PC86	.24	PY102	.34	U403	1.73	ACY40	-.20	BF201	-.44	OC45	-.42
6AK5	.25	6GK5	.50	12A6	.63	30P12	.69	DK92	.45	ECH35	.50	EF207	.28	PC86	.24	PY103	.34	U403	1.73	ACY41	-.20	BF202	-.44	OC46	-.42
6AK6	.30	6G17	.50	12AC6	.40	30P19	.69	DL92	.28	ECH42	.57	EF208	.28	PC86	.24	PY104	.34	U403	1.73	ACY42	-.20	BF203	-.44	OC47	-.42
6ANSA	.50	6H6GT	.15	12AD6	.40	30P19	.69	DL92	.28	ECH42	.57	EF209	.28	PC86	.24	PY105	.34	U403	1.73	ACY43	-.20	BF204	-.44	OC48	-.42
6AN8A	.49	6J5GT	.29	12AE6	.48	30P4	.65	DL96	.38	ECH81	.25	EF210	.28	PC86	.24	PY106	.34	U403	1.73	ACY44	-.20	BF205	-.44	OC49	-.42
6A06	.21	6J6	.18	12AT6	.23	30P11	.57	DM70	.30	ECH83	.38	EF211	.28	PC86	.24	PY107	.34	U403	1.73	ACY45	-.20	BF206	-.44	OC50	-.42
6A15	.30	6J7G	.24	12AUG	.21	30P13	.75	DM77	.50	ECH84	.34	EF212	.28	PC86	.24	PY108	.34	U403	1.73	ACY46	-.20	BF207	-.44	OC51	-.42
6A87	1.00	6J7M	.63	12AV6	.28	30P14	.75	DY87/7	.22	ECL80	.28	EF213	.28	PC86	.24	PY109	.34	U403	1.73	ACY47	-.20	BF208	-.44	OC52	-.42
6AT6	.13	6J8UA	.50	12BA6	.30	30P15	.87	DY82	.29	ECL82	.28	EF214	.28	PC86	.24	PY110	.34	U403	1.73	ACY48	-.20	BF209	-.44	OC53	-.42
6A06	.19	6K7G	.12	12BE6	.30	35A3	.48	ES00C	1.65	ECL83	.52	EF215	.28	PC86	.24	PY111	.34	U403	1.73	ACY49	-.20	BF210	-.44	OC54	-.42
6AV6	.28	6K8G	.33	12BH7	.27	35V5	.70	E80F	1.20	ECL84	.54	EF216	.28	PC86	.24	PY112	.34	U403	1.73	ACY50	-.20	BF211	-.44	OC55	-.42
6AW8A	.54	6L1	.98	12J7GT	.33	35L6GT	.42	E83F	1.20	ECL85	.54	EF217	.28	PC86	.24	PY113	.34	U403	1.73	ACY51	-.20	BF212	-.44	OC56	-.42
6AX4	.39	6L6GT	.50	12K5	.60	35W4	.23	E88CC	.60	ECL86	.58	EF218	.28	PC86	.24	PY114	.34	U403	1.73	ACY52	-.20	BF213	-.44	OC57	-.42
6B8G	.13	6L7	.38	12K7GT	.34	35Z4GT	.24	E92CC	.40	EFL22	.68	EF219	.28	PC86	.24	PY115	.34	U403	1.73	ACY53	-.20	BF214	-.44	OC58	-.42
6BA6	.19	6L8	.44	12K7GT	.28	35Z6GT	.30	E180F	.40	EF40	.58	EF220	.28	PC86	.24	PY116	.34	U403	1.73	ACY54	-.20	BF215	-.44	OC59	-.42
6BC8	.50	6L19	1.38	12SC7	.35	50B5	.35	E182CC1	.00	EF41	.58	EF221	.28	PC86	.24	PY117	.34	U403	1.73	ACY55	-.20	BF216	-.44	OC60	-.42
6BE6	.20	6L20	.48	12SG7	.23	50C5	.32	E1148	.53	EF42	.58	EF222	.28	PC86	.24	PY118	.34	U403	1.73	ACY56	-.20	BF217	-.44	OC61	-.42

TO SPARK YOUR IMAGINATION!

the **SPARKRITE** Electronic Ignition Kit only **£9.35**

Kit comprises EVERYTHING
Case, cables, coil connectors,
Silicon grease
8 page instruction leaflet

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready fitted to car in 15 minutes when built.

- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cys. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gulton ignition. Price **£9.35** inc V.A.T. and postage (12 volt only State Pos or Neg earth). Ready built unit also available **£11.55** inc V.A.T. and postage **GUARANTEED 5 YEARS**

ORDER NOW—send P.O./Cheque direct to:
ELECTRONICS DESIGN ASSOCIATES, Dept. PW8
82 Bath St., Walsall WS1 3DE. Phone: 33652

BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 0J-672 3984

CARTRIDGES—Stereo Sonotone 9TA H/C Diamond £2.47, Rockette S105 Medium Output £1.40, S106 High Output £1.40, Ac, G9931/1 Sapphire £1.95, GP94/1 Sapphire £1.95, Japanese equivalent to B.S.R. TC8s £1.80.

CARTRIDGES—Mono GP91 Stereo Compatible £1.29, B.S.R. TC8H Jap. equivalent £1.29.

HI-FI STEREO HEADPHONES Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms, frequency range 20-20,000 Hz 6ft. cord and standard stereo plug. Only **£5.75**.

STEREO HEADPHONE JUNCTION BOX Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only **£1.74**.

VYNAR Widths from 50 to 54in., 95p yd. off roll, ½ yd 5p. Send 5p stamps for samples. All prices include postage and post packing.

MASSIVE CLEARANCE BARGAINS

Bargain component parts contain Resistors, Capacitors, Switches, Potentiometers, Knobs, I.F.s, Tag Strips, Drive Drums, Transistor Panels etc. etc. Save yourself £s on these well selected parcels 6lbs net weight **£1.00**, p. p. 40p.

Assorted Electrolytic Capacitors. 6lbs net weight **£1.00**, p. p. 40p. Brand new Wire-wound Resistors. Good Selection. 100 for **£1** p. p. 15p.

Mullard Ferrite Bar Magnets ½" x ¾" x ¾". 100 for **£1.25**, p. p. 16p. Assorted Computer Panels. These panels are exceptionally good value and contain a minimum of 75 transistors, stacks of diodes plus Trim Pots. Polyester Capacitors, Resistors and include a few I.C.s. 10 panels for **£1.00**, p. p. 25p.

Mullard Ferrite Cores. LA3 up to 500kHz. 50p. LA4 up to 30kHz 75p. LA1200 up to 200kHz 50p.

Please include 10% V.A.T. to total cost of goods.

MAIL ORDER ONLY
XEROZA RADIO
1, EAST STREET,
BISHOPS TAWTON,
DEVON



MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

JOHN THORBURN (Glasgow) has used his Vasco Gold Star radio to hear CHER Sydney, Nova Scotia on 950kHz; WBT Charlotte, North Carolina on 1110kHz; Radio Bermuda 1340kHz; Voice of America Kavalla, Greece 791kHz; Radio Zagreb, Yugoslavia 1133kHz. John also logged the BBC local radio outlets at Blackburn on 850kHz, Sheffield 1034kHz; Leeds 1106kHz; Newcastle 1457kHz; Stoke 1502kHz; Bristol 1546kHz and Manx Radio, Isle of Man on 1594kHz.

Dominic Glynn (East Grinstead) has a Philips transistor receiver and a 100ft. longwire antenna. He reports hearing programmes in English from Radio Sweden 1178kHz at 2300hrs GMT; Trans World Radio Montecarlo 1466kHz at 2230hrs and Radio Berlin International 1511kHz at 1815hrs. Dominic has also logged Radio Tirana, Albania 1394kHz at 2230hrs and BBC Radio Stoke 1502kHz at 1045hrs.

From the BBC comes news that Radio Solent is now broadcasting on two frequencies, 998kHz and 1594kHz. The new outlet on 1594kHz brings the

VHF/FM by SIMON DAVID

HAVE you been suffering from "Sporadic—E" lately? If so we would like to hear from you. Sporadic—E is the name given to a disturbance in the "E" region of the ionosphere. It is most likely to occur in the summer months (U.K.) and gives rise to some odd goings-on on the v.h.f. bands up to about 100MHz.

Although almost impossible to predict accurately, such manifestations are in long distance reception, interference on television and radio and interaction between signals from one source and another, often several hundreds or even thousands of miles apart. Stations operating on close frequency allocations are susceptible and in particular those on v.h.f. mobile radio systems often fall victim.

Greetings in particular this month to listeners who can now pick up local radio on their portables and in cars in Leeds, Huddersfield, Barnsley, Dewsbury, Wakefield, Castleford, parts of Halifax, Bradford and Harrogate, Barnsley, Doncaster, Worksop, East Retford and Rotherham. In case you are not aware, you should now be able to *drive* to the lilt of BBC Radio Leeds (92.4MHz) or Radio Sheffield (97.4MHz).

The old Meanwood Park transmitter on 94.6MHz and Boston Park, Rotherham, transmitter on 95.05MHz have closed and all transmissions from these two stations now come from Holme Moss near Huddersfield. Sheffield listeners can still tune in on 88.6MHz, but all others tuning to 97.4MHz may need to turn their aerial round so that it is directed at Holme Moss (also home of BBC television). Aerials that are already rigged on the roof or chimney outside and directed at Holme Moss for Radios 2, 3 and 4 are likely to be suitable for the local radio stations also.

service to Bournemouth, Poole and Wimborne Minster while the existing service on 998kHz for the Southampton and Portsmouth areas is unaffected

Medium wave DXers who go abroad for their holidays have the opportunity to try the band from a new location. In Spain there are many low power local stations, some of which would be rarities if heard in this country and even a pocket sized transistor portable will pull them in. For those interested in keeping in touch with events at home there is the BBC Radio 2 transmission on 200kHz (1500m) on the long waves which can be heard over a large part of Europe after dark. Visitors to Majorca can hear Radio Mallorca (EAJ13) on 800kHz; Radio Popular de Mallorca (EAK18) on 1268kHz; Radio Juventud de Palma Mallorca (EFJ45) on 1385kHz. On the Costa Brava there are Radio Barcelona (EAJ1) on 827kHz; Radio Juventud Barcelona (EFJ15) on 1025kHz; Radio* Espana de Barcelona (EAJ15) on 1124kHz; Radio Sabadell (EAJ20) on 1475kHz; Radio Gerona (EAJ38) on 1520kHz. At Benidorm there are Radio Popular de Alicante (EAK31) on 1394kHz; Radio Gandia (EAJ23) on 1457kHz; Radio Alicante (EAJ31) on 1520kHz and La Voz de Alicante (EFE8) on 1570kHz. Those going to the Costa del Sol have the opportunity to hear Radio Gibraltar on 1484kHz which broadcasts in English and Spanish; Radio Ceuta (EAJ46) on 1106kHz which is located in a Spanish enclave in Morocco; Radio Juventud de Malaga (EFJ56) on 1133kHz; Radio Popular de Malaga (EAK11) on 1430kHz and Radio Costa del Sol (ECS15) on 1570kHz.


Some transmitters use slant polarisation to assist where vertical receiver aerials are used (such as on cars). One such is used for Radio Derby which is transmitted from Sutton Coldfield, Birmingham, on 96.5MHz. If you are not sure on the polarisation for your area you can ask at any local BBC radio offices or write to the Engineering Information Dept., BBC, Broadcasting House, London W1A 1AA; please enclose a stamped addressed envelope.

Now for some quick quotes from some of the letters received: **W. F. Kitching** in Shropshire has a Grundig "Yacht Boy" 210 with telescopic aerial and has picked up Radio Telefis Eirean 95.3MHz. He looks forward to police inactivity so that he can hear Radio Na Gaeltachta, Eire, on 97.0MHz.

On the other side of the Irish Sea, **Des Walsh** in Tipperary uses a Leak Troughline-3 and a BASF CC9300 Radio recorder and points a J-Beam FM6S and FM4S at South Wales and South West England. He has bagged Wenvoe, Haverfordwest, Blaen-plwyf, North Hessary Tor, Redruth and Radio Bristol. Turning north-east he can pick up Belfast and Radio Merseyside. Here's the crunch! With the help of tropospherics he can hear ORTF from N. W. France.

D.J. is a 14-year-old from Egham, Surrey, and is one of many who has heard the London Independent Radio transmissions on Radio Classic 94.4MHz. Hope his parents won't get annoyed when they find out that he was listening to "an extra programme" at 01.05 Easter Sunday morning. Was this a "Jolly Roger" operation?

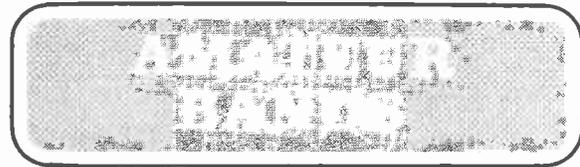Anybody heard broadcasts from the North Sea Radio Telephone Company? **Graham Wilson** has in Bordon Hampshire and wonders who was responsible. The transmission was heard on much of the 88-108MHz band (but was strongest at 91MHz) on March 5th.



SHORT WAVES

by DAVID GIBSON, G3JDG

IT'S getting hotter in more senses than one. The summer season brings great hotness with it and it is known in this scribe's shack as the Equinox of the molten ear'ole—a disease common to all wearers of headphones during periods of great warmth.

The other sense is a rumour to ban a.m. from the Amateur bands, notably the l.f. regions of 1.8 and 3.5MHz. What do readers think about this? Shall we settle for s.s.b. and c.w. only?

A staggering piece of news for professional call-sign changers. The latest act in the callsign circus is to change it just for a particular contest. The result is CR6 becoming CQ6 (a really clever choice—CQ) for the WPX contest. A little bird also tells me that MP4TEE is now A6XF.

Best piece of news on the callsign front, and one for some genuine rejoicing in Amateur circles, is that the People's Republic of China will probably be allowing/issuing callsigns in the not too distant future. It'll make the bands even more crowded but

a big welcome to the Chinese Amateurs as and when they appear on the bands.

In the April issue, mention was made of photographs showing readers' stations. First person to take up the gauntlet is **Graham Bleakley** who is 15 and lives in Cumbernauld New Town, Scotland. The gear shown is a "trusty old CR100". Graham is the one on the left with all the hair, and the CR100 is on the right, with all the knobs. No mention of what the tape recorder is for but Graham does say he reckons to become a G8 with a bit of help from the May 1974 RAE. No word of the antenna, but whatever it is, it pokes out of the windows of 82 Ash Road.

Info from G3RPJ that the Stratford on Avon Radio Club will have rigs working on 1.8MHz, 14MHz and 144MHz (a.m. f.m. and r.t.t.y.) at the Town and Country Festival on August 25/26/27. Place is the Royal Showground, Stoneleigh, Kenilworth, Warwickshire. The stations will stay on the air in the evenings after the show.

Karl Muller (Mbabane, Swaziland) has a JR-500SE 7MHz inverted V and a lot of patience. Rewards for same has given him 148 countries heard on 7MHz. On 7MHz c.w. Karl bagged; CE3ED, CE5HP, CX1BBL, CX9BT, FC9VN, FG7TG, FH8CY, KØALL, KH6AQ, KH6RS, SV1DO, TI2PZ, VP9GR, WN3TGR, WNØHYN, ZP5AL, 4K1A, 9F3USA, 9L1GC. On s.s.b., the latest log reads; CT2AJ, KC6SK, MP4BJP, OY7BD, WB6VGI/VQ9, ZC4EJ, ZD9GC, 4W1AF, 6W8DY.

Before going on with logs, I see that the May 1973 issue of Radio Communication, the journal of the RSGB, publishes a full list of intruder stations complete with all sorts of information; frequency, date, location, source etc. This seems a useful coincidence in view of previous remarks made in this column. Single copies of the journal are available to non-members at 30p plus postage.

J. Wright (Loughborough) homebrew converter, 960 receiver, 3-element beam at 30ft. sends in a log for 70MHz (Yippee). Stations bagged include: G3CDG/P, G3HCW/P, G3HVI, G3LVP/P, G3NQV/P, G3ONP, G3SFT/P, G3TOM/P, G3VER/P, G3VPF/P, G3VPK, G3WMR/P, G3ZVK, G4ALE/P, G4BEZ/P, G4BLQ, G4BPY, G4BZO, G5DF, GD2HDZ, GW3MHR, GW30BD/P, GW3WOS, GW4ABR/P, GW4BGG/P.

P. Newman (Thame) sends in a "Heard in the 144MHz and 70cm Contest" log. Pickings on 70cm; G8DOR/P, G88GHR/P, G3NNG/P, G5DF, G8FBG/P. Two meter goodies were; G8DWC/P, G2DRT/A, G8CIB/P, G8GSX/P, G8GTD, G8FBG/P, G8FTL, G8FZL/P, G3FZL/P, G3KIN/P; G3OSS, G3NNG/P, GW4ABR/P.

Contests for the month of July include: July 7/8, v.h.f./u.h.f. Jubilee contest (R.S.G.B.); 14/15, s.s.b. field day; 15, DF qualifying round at Coventry; 22, 432MHz portables contest; August 4/5, YO DX Phone and c.w. contest; August 5, DF qualifying round (Salde).



BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

Medium Waves Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

AMATEUR BANDS

Short Wave/VHF

Logs in alphabetical order please by 15th of the month to David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.

ZN414 £1.25 POST FREE
 The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets
 Dual in-line or Zig-Zag (Quil). 14 and 16 pin
Our Price 1p per pin

VDR's & Thermistors

A15B 75p	E298 ED/A258 10p	VA1005 15p
CZ1 15p	E298 ZZ/06 10p	VA1026 13p
CZ4 13p		VA1033 10p
CZ13A13p		VA1034 10p
CZ19 13p		VA1039 15p
GL16£1 00		VA1040 10p
GL23£1 00		VA1053 10p
R53 £1 32		VA1055S10p
R54 £1 46		VA1077 13p

Potentiometers



5KΩ	50KΩ	500KΩ	
10KΩ	100KΩ	1MΩ	
25KΩ	250KΩ	2MΩ	

log or lin less switch (& 1KΩ lin) 12p
 log or lin with switch 24p
 dual less switch 40p
 dual with switch 10K, 100K & 1M 52p
 10K log 10K antilog less switch 40p

Capacitors

disc ceramic	low voltage
0.1µF 18v 5p	0.1µF 30v 5p
0.22µF 18v 5p	0.22µF 6v 5p
0.47µF 12v 5p	0.47µF 3v 5p
ceramic plate	30V
1000pf 10p	4700pf 10p
2200pf 10p	10,000pf 10p

Slider Pots

Single	Dual	log or lin
10K	10 + 10K	
25K	25 + 25K	
50K	50 + 50K	
100K	100 + 100K	
30p	50p	Knobs 10p

Resistors

1/2 watt 5% Carbon Film - low noise 141 Stabs

All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value.

1W 10% Carbon Composition 3p each
 2W 10% Carbon Composition 6p each
 2.1W 5% Wire wound 9p each
 5W Wire wound 9p each
 10W Wire wound 10p each plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25

Eliminators



6 volt @ 50mA £1.50
 9 volt @ 50mA £1.50
 6 + 6 volt, 50mA £2.50
 9 + 9 volt, 50mA £2.50
 7 1/2 volt for cassette recorders £2.00
 6, 7 1/2 or 9 volt £3.00
 3, 4, 6, 7 1/2, 9, 12 @ 500mA (illus.) £3.99
 Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts £4.99 (p. & p. 15p on all types)

NEW LISTINGS
 LOUDSPEAKERS No. 4
 COILS AND INDUCTORS No. 5
 TRANSFORMERS No. 6
 (postage 5p)

Diodes & Rectifiers

AA119 9p	BA156 15p	BY176 £1 50
AA120 9p	BA243 56p	BY182 £1 50
AA129 9p	OA47 10p	BY250 23p
BA102 25p	OA79 9p	IN4001 6p
BA115 17p	OA90 7p	IN4002 7p
BA130 10p	OA91 7p	IN4003 8p
BA145 20p	OA200 10p	IN4004 8p
BA148 20p	BY100 15p	IN4005 10p
BA154 13p	BY126 15p	IN4006 12p
BA155 14p	BY127 15p	IN4007 15p

BYVM ZENER SERIES (see each)

SGS

EA1000



3 Watt Audio Amplifier
 Our Price inc. handbook £2 48

10+ less 15%
 25+ less 25%
 100+ less 35%

5 Watt Audio Amplifier
 Our Price £3 99
 Less quantity discount

Presets



Vertical or Horizontal
 0-1 watt 5p 0-25 watt 7p
 100 1KΩ 10KΩ 100KΩ 1MΩ
 250 2.5KΩ 25KΩ 250KΩ 2.5MΩ
 500 5KΩ 50KΩ 500KΩ 5MΩ

Ceramic - plate 33V (C333)

1000pf 2p	0.1µF 3p	068µF 4p
2000pf 2p	0.2µF 3p	1µF 5p
5000pf 2p	0.4µF 3p	2µF 4p
	0.5µF 3p	

polystyrene 160V
 10p to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallised polyester 250V (C280)

0.1µF 3p	068µF 3p	47µF 8p
0.15µF 3p	1µF 4p	68µF 11p
0.22µF 3p	1.5µF 4p	1µF 13p
0.33µF 3p	2.2µF 5p	1.5µF 20p
0.47µF 3p	3.3µF 6p	2.2µF 24p

metallised polyester 400V (C281)

0.1µF 4 1/2p	0.47µF 6p	22µF 10p
0.15µF 4 1/2p	0.68µF 6p	33µF 14p
0.22µF 4 1/2p	1µF 7p	47µF 15p
0.33µF 5 1/2p	1.5µF 8p	

silvered mica 1% (>50pf) 500V


2.2p—820p	4.7nF—5600pf	19p
1nF—2.2nF	9p	6800p—0.1µF
2.7nF—3.6nF	16p	

mixed dielectric 600V

0.1µF 7p	0.47µF 7p	22µF 16p
0.22µF 7p	0.68µF 8p	47µF 24p
0.33µF 7p	1µF 8p	1µF 33p

CHROMASONIC electronics PRICES DO NOT INCLUDE V.A.T.

Heat Sinks

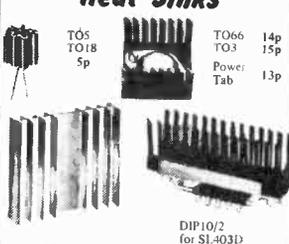

TO5 TO18 5p
 TO66 TO3 15p
 Power Tab 13p
 10D 50p
 DIP10/2 for SL403D 15p

Transistors & Integrated Circuits

AC107 25p	BC147 10p	BF196 15p	OC81 19p	2N1304 22p	2N5172 15p
AC126 17p	BC148 10p	BF197 15p	OC140 20p	2N1711 25p	LO05T1 £1 50
AC127 15p	BC149 10p	BF272 53p	OC170 23p	2N1993 30p	LO36T1 £1 50
AC128 15p	BC157 12p	BFY50 24p	OC171 30p	2N2926 23p	LO37T1 £1 50
AC176 15p	BC158 10p	BFY51 21p	ZTX107 15p	2N3053 40p	MC1303L £1 75
AC187 25p	BC159 12p	BRY39 36p	ZTX108 12p	2N3054 50p	MC1330 80p
AC187K 25p	BC169 15p	BSX21 26p	ZTX109 15p	2N3055 49p	MC1350 75p
AC188 25p	BC288 15p	BSY96A 14p	ZTX300 12p	2N3702 12p	MC1361 £1 00
AC188K 25p	BD115 81p	BUJE902 £1.75	ZTX301 15p	2N3703 12p	MC1362 £1 00
ACY20 20p	BD131 70p	MJE340 87p	ZTX302 20p	2N3704 10p	MFC4000B 49p
AD140 40p	BD132 70p	MPF192 40p	ZTX303 20p	2N3705 10p	MFC4001A 55p
AD149 40p	BD131/2M.P.	MPF103 37p	ZTX304 25p	2N3706 10p	LM380 11 1/2
AD181 60p	BF160 21p	MPF104 37p	ZTX341 20p	2N3707 15p	PA234 £1 90
AD182 60p	BF162 20p	MPF105 40p	ZTX500 15p	2N3708 12p	SL403D £1 50
AF114 18p	BF167 20p	MPF106 45p	ZTX501 15p	2N3709 12p	TAD100 £1 50
AF115 18p	BF173 20p	OC28 40p	ZTX502 20p	2N3710 12p	
AF116 18p	BF180 25p	OC35 40p	ZTX503 17p	2N3711 12p	
AF117 18p	BF181 30p	OC44 15p	ZTX504 50p	2N3819 15p	µA709C 34p
AF139 28p	BF184 25p	OC45 15p	ZTX531 25p	2N3903 15p	µA710 45p
BC107 10p	BF185 25p	OC71 11p	2N697 18p	2N3904 17p	µA725C 47p
BC108 10p	BF194 15p	OC72 17p	2N708 12p	2N3905 21p	µA748C 87p
BC109 10p	BF195 15p	OC78 15p	2N708 15p	2N3906 12p	

mixed dielectric 1000V

1000pf 6p	6800pf 9p	1µF 12p
2200pf 6p	0.1µF 9p	22µF 22p
3300pf 6p	0.22µF 9p	47µF 30p
4700pf 6p	0.47µF 12p	


Ceramic
 12KV d.c. 8KV d.c. HI-K 750V
 10µF 9p 200pf 9p 1000pf 5p
 15pf 9p 220p 9p 1500pf 5p
 22p 9p 250p 9p 2000pf 5p
 68p 9p 270p 9p 3000pf 5p
 82p 9p 300p 9p 5000pf 5p
 100p 9p 750V DISC 10,000pf 5p
 120p 9p 470p 5p feed-through
 140p 9p 1000pf 5p through
 150p 9p 5000pf 5p
 180p 9p 10,000pf 5p 1000pf 5p

Veroboard

Copperclad	Plain
0.1" 0.15"	0.15"
2 1/2" x 1" 6p	6p
2 1/2" x 3 1/2" 20p	16p (9) 10p
2 1/2" x 5" 24p	21p (7) 12p
3 1/2" x 3 1/2" 24p	21p (8) -
3 1/2" x 5" 27p	27p (10) 17p
17" x 2 1/2" 60p	50p 37p
17" x 3 1/2" 97p	70p 52p
17" x 5" 97p	70p 75p

Spot-face Cutter 36p
 Pin Insertion Tool 47p
 Terminal Pins 18p per pack of 36

THE TEXAN

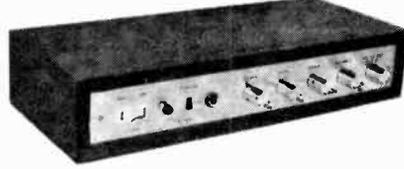

Complete Kit (inc. Test Case) **£28.50** PGP 45p

20 Watts per channel integrated stereo amplifier developed by engineers of Texas Instruments Ltd. This designer approved kit, has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 at -3db. The semiconductor complement of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistors, 4 rectifiers and 2 zeners. Controls include: bass; treble; volume; balance; on/off, on indicator; headphone sockets; scratch filter; rumble filter; inputs for magnetic phono, tuner; aux or tape; tape head etc, input; selector; mono/stereo switch.

The construction of this kit was featured in "Practical Wireless" May - Aug. 1972.

Mullard B Siemens Electrolytics

CAP µF	VOLTAGE							
	4	6.3	10	16	25	40	83	
1	-	-	-	-	-	-	-	6p
1.5	-	-	-	-	-	-	-	6p
2.2	-	-	-	-	-	-	-	6p
3.3	-	-	-	-	-	-	-	6p
4.7	-	-	-	-	-	-	-	6p
6.8	-	-	-	-	-	-	-	6p
10	-	-	-	-	-	-	-	6p
15	-	-	-	-	-	-	-	6p
22	-	-	-	-	-	-	-	6p
33	-	-	-	-	-	-	-	6p
47	-	-	-	-	-	-	-	6p
68	-	-	-	-	-	-	-	10p
100	-	-	-	-	-	-	-	12p
150	-	-	-	-	-	-	-	12p
220	-	-	-	-	-	-	-	12p
330	-	-	-	-	-	-	-	21p
470	-	-	-	-	-	-	-	21p
680	-	-	-	-	-	-	-	21p
1000	-	-	-	-	-	-	-	40p
1500	-	-	-	-	-	-	-	40p
2200	-	-	-	-	-	-	-	40p
3300	-	-	-	-	-	-	-	40p
4700	-	-	-	-	-	-	-	40p

Quantity Prices on application.

NEW LISTINGS
 BOXES, CHASSIS, etc. No. 7
 TRANSISTORS, I.C.'s, etc. (soon)
 (postage 5p)

Aluminium Boxes
 Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2 3/4"	5 1/4"	1 1/2"	35p	8p
(8)	4"	4"	1 1/2"	35p	8p
(9)	4"	2 3/4"	1 1/2"	35p	8p
(10)	4"	5 1/4"	1 1/2"	40p	8p
(11)	4"	2 1/2"	2"	35p	8p
(12)	3"	2"	1 1/2"	32p	9p
(13)	6"	4"	2"	50p	10p
(14)	7"	5"	2 1/2"	58p	12p
(15)	8"	6"	3"	75p	18p
(16)	10"	7"	3"	85p	20p

Hi-Volt Electrolytics

1 1/2, 4, 8µF 50V	14p 32V	450V 20p
15µF 450V	15p 50µF	350V 20p
8 1/2µF 450V W	18p 32µF	350V W 25p
8 1/2µF 450V V	20p 32µF	450V V 43p
16 1/2µF 450V V	25p 50µF	350V V 35p

Why pay more - look at our Fantastic Bargain Offer!

PENTHOUSE

A COMPLETE AUDIO SYSTEM

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorized tuner/amplifier with Stereo Multiplex Decoder. 4 wavebands Long/Medium-Short/VHF. 8 watts per channel (music power) output. The latest BSR C129 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.

OUR PRICE £35.00




Credit terms £5.00 deposit plus £2.00 p. & p. followed by 12 payments of £4.80. Total Credit Terms £62.60 SEND £7.00 TODAY.

BENSON


BENSON MW/FM/MPX STEREO 8 TRACK

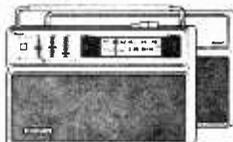AM/FM radio with decoder for stereo radio with integral 8 track cartridge player. Portable for operation from internal batteries or A.C. mains or 12V Car/Boat cigar lighter socket. Unit divides into two for stereo reproduction. Our price £39.95. Credit terms £5.00 deposit plus 12 monthly payments of £3.40 (Total £45.80), p. and p. £1.00. Send £6 Today!



UNIT DIVIDES TO GIVE 2 SEPARATE STEREO SPEAKERS

THE AVON AUDIO SYSTEM

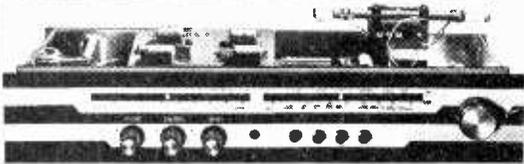

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

BSR 4 SPEED STEREO/MONO RECORD CHANGER plays all types or 7in., 10in., and 12in. Mono of Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £35.00. Credit Terms £3.50 deposit plus £2 Post & Packing

followed by 12 payments of £3.10 (Total Credit Terms £40.70). Don't miss this bargain. SEND £5.50 TODAY

ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

Please send me free details of your range

Post coupon NOW for **FREE** leaflets

Name

Address

LEWIS radio

100, Chase Side London N.14
Tel: 01-886 3733/9666

FIRST TIME EVER at £42.50

Solartron CD711S.2
Double Beam Oscilloscope d.c.—8MHz; 3mV-cm; trigger delay; crystal call/brator; 4in flat faced tube. In good working condition. Carriage £1.50.

SOLARTRON CT 316 (D300 range)

DC to 6 mcs. 3" tube. T_{up} to 0.75 micro secs per centimeter. Built in calibrator. Size 8 1/2" x 11" x 20". Price £22.50. Carr. £1.50.

MARCONI VALVE VOLTMETER type TF 958 (CT208)

DC to 100 mcs. 5" mirror backed meter complete with probe, leads etc. £12.50. Carr. £1.25.

GRATICULES. 12cm x 14cm in High Quality plastic. 30p ea. P. & P. 5p.
MODERN TELEPHONES type 706. Two tone grey, £3.75 ea. The same but black, £2.75 ea. P. & P. 25p ea. Also **TOPAZ YELLOW** £4.50 ea. P. & P. 25p.

STANDARD GPO DIAL TELEPHONE (black) with internal bell, 87p ea. P. & P. 50p. Two for £1.50. P. & P. 75p. All telephones complete with bell and dial.

20kHz to 200kHz: WB SINE AND SQUARE GENERATOR Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8.85 each. P. & P. 25p. (Not cased, not calibrated.)

MOTOR MIN SYNCHRONOUS Size 1 1/2" x 2" x 1/2" 240V operation 3.6 RPM 25p each. P. & P. 5p.

5 MOVING COIL METERS various £2 P. & P. 37p.

PLEASE ADD 10% V.A.T.
Open 9 a.m. to 7.30 p.m. any day.

CHILTMead LTD
7/9 ARTHUR ROAD, READING, BERKS.
(near Tech. College) Tel.: Reading 582605/65916

WOBBLEATOR

Sweeps 8 to 45MHz ready to use. 0.3V a.c. required. £9 each. P. & P. 25p. (Not cased, not calibrated.)

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 17p.
POTS—10 different values. Brand new—50p. P. & P. 17p.

COMPONENT PACK consisting of 2-2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors 1/2 and 1/4 watt, many high stabs, etc. Fine value at 50p per pack. P. & P. 17p.

P.C.B. PACK S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p. **FIBRE GLASS** as above £1 plus P. & P. 20p.

5 CRYSTALS to 90kHz. Our choice, 50p. P. & P. 15p. Matched pairs, 50p per pair. P. & P. 15p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

ELECTRONIC TIMER UNITS—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2.50 incl. carriage.

AMERICAN SCOPE type USM24. A 10 meg scope—all min valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore £29.00. With step-down transformer £22.50. Carr. £1.50.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand new 38p ea. Holder 1p ea. Information 5p. **PHOTO TUBE** equ OCP71—13p ea. **PHOTO-RESIST** type Clare 703. Two for 50p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 18S, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.20. DAP96, DF96, DK96, DL96, 4 for £1.65.

1R5	30	30FL12	60	EBC90	52	EY51	36	PCL85	37	UAF42	50	
18S	25	30FL14	65	EBF80	32	EY86	29	PCL86	37	UBC41	45	
1T4	20	30L1	29	EBF88	39	EY87	29	PCL88	80	UBF80	34	
384	20	30L15	70	EBF89	39	EZ40	39	PCL90	89	UBF89	38	
3V4	47	30L17	70	ECH81	35	EZ41	39	PCL905	37	UCC84	33	
5U4G	31	30P4	64	ECC82	21	EZ80	21	PEN4A	77	UCC85	35	
5V4G	35	30P12	69	ECC83	35	EZ81	22	PEN36C	70	UCF80	38	
5Y3GT	30	30P19	64	ECC85	34	EZ90	25	PFL200	48	UCH42	50	
5Z4G	35	30P11	66	ECC804	50	GZ30	34	PL36	48	UCH81	30	
6R80L2	50	30P113	80	ECP90	50	GZ32	40	PL81	48	UCL82	30	
6A36	18	30P114	50	ECH83	35	K741	77	PL81A	47	UCL83	35	
6AQ5	24	35W4	25	ECH42	59	K741	65	PL82	31	UF41	38	
6AT6	20	35Z4GT	25	ECH81	29	KT66	78	PL83	38	UF89	30	
6AU6	20	50CD6G	68	ECH83	38	LN319	56	PL84	30	UL41	38	
6BA6	20	807	55	ECH84	35	LN329	30	PL600	58	UL84	30	
6BE5	21	6063	21	00	ECL80	30	LN339	65	PL604	58	UM84	38
6B8	41	AC/VP2	77	ECL82	29	N78	21	05	PM84	30	UT41	37
6BW7	50	B349	70	ECL86	35	PABC80	31	PX25	55	UH85	35	
6F14	35	B729	64	EF37A	95	PC86	44	PY32	52	VP4B	77	
6F23	68	CCH35	67	EF39	46	PC88	44	PY33	52	W77	48	
6F25	50	CY31	28	EF41	67	PC96	43	PY81	28	Z77	38	
6J5GT	20	DAF91	25	EF80	33	PC97	35	PY82	26			
6J7G	24	DAF95	36	EF85	23	PC90	29	PY83	26	Transistors		
6V6GT	28	DF91	30	EF86	30	PC84	29	PY88	33	AC107	17	
6X4	30	DF96	36	EF89	26	PC85	29	PY800	31	AC127	18	
6X5GT	28	DH77	30	EF91	18	PC88	38	PY801	31	AD146	37	
10P13	58	DK91	30	EF92	18	PC89	43	R19	30	AF115	30	
12AT7	20	DK92	48	EF98	70	PCF189	48	R20	70	AF116	30	
12AU7	21	DK96	45	EF183	27	PCF805	70	U328	70	AF117	30	
12AX7	22	DL92	30	EF184	29	PCF80	28	U26	64	AF125	17	
19B6G	75	DL94	47	EH90	36	PCF82	38	U47	78	AF127	17	
20F2	67	DL96	38	EL33	35	PCF88	46	U49	70	OC44	18	
20P3	75	DY86	22	EL34	50	PCF800	58	U82	31	OC45	18	
26L6GT	18	DY87	22	EL41	52	PCF801	28	U78	80	OC71	18	
28U4GT	37	DY802	50	EL64	33	PCF802	39	U191	55	OC72	18	
30C1	26	EAC90	28	EL90	24	PCF805	57	U193	81	OC75	18	
30C15	53	EAP49	60	EL500	62	PCF806	56	U251	61	OC81	18	
30C17	78	EB91	12	EM80	38	PCF808	65	U301	38	OC81D	18	
30C18	57	EBC33	45	EM81	38	PCL82	30	U329	68	OC82	18	
30F5	64	EBC41	49	EM84	32	PCL83	55	U801	75	OC82D	18	
30FL1	65	EBC81	30	EM87	50	PCL84	33	UABC80	31	OC170	28	

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

PRICES ARE INCLUSIVE OF VAT, ONLY POSTAGE IS EXTRA

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per valve extra)

Any parcel insured against damage in transit 3p extra.



CALIBRATING SW RECEIVERS

M. CONNAH

WITH the Short Wave Bands becoming more crowded every year it becomes increasingly necessary for the listener to be able to determine the frequency to which his receiver is tuned. Conversely, if the receiver is accurately calibrated the listener is able to tune to a desired frequency to listen for a particular station.

spread control with a reasonable scale. The first part of the article, therefore, deals with adding a suitable bandspread control to a receiver which is lacking in this respect.

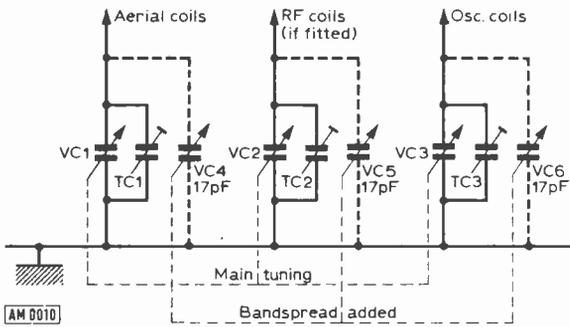


Fig. 1 Circuit showing the bandspread ganged capacitor added to the existing circuit.

ADDING BANDSPREAD

The addition of a bandspread control to a receiver which does not have this facility is probably the most effective, yet simple, method of improving the performance of the set. The total cost is little more than £1 so the project is well within the means of the average listener.

All superhet receivers have a main tuning control which is either a two or three gang variable capacitor. This is shown as VC1/VC2/VC3 in Fig. 1. The bandspread control required for the project is a two or three gang (depending upon the number of gangs of the main tuning) miniature variable capacitor each section having a capacitance of approximately 15 to 20pF. The most suitable type is that often used for the tuning of v.h.f. receivers, usually having a capacitance of 17pF per section.

The latter part of this article deals with a method of receiver calibration which costs less than a pound. The only requirement is that the receiver has a band-

The bandspread control is represented by VC4/VC5/VC6 in Fig 1. Each section of the bandspread

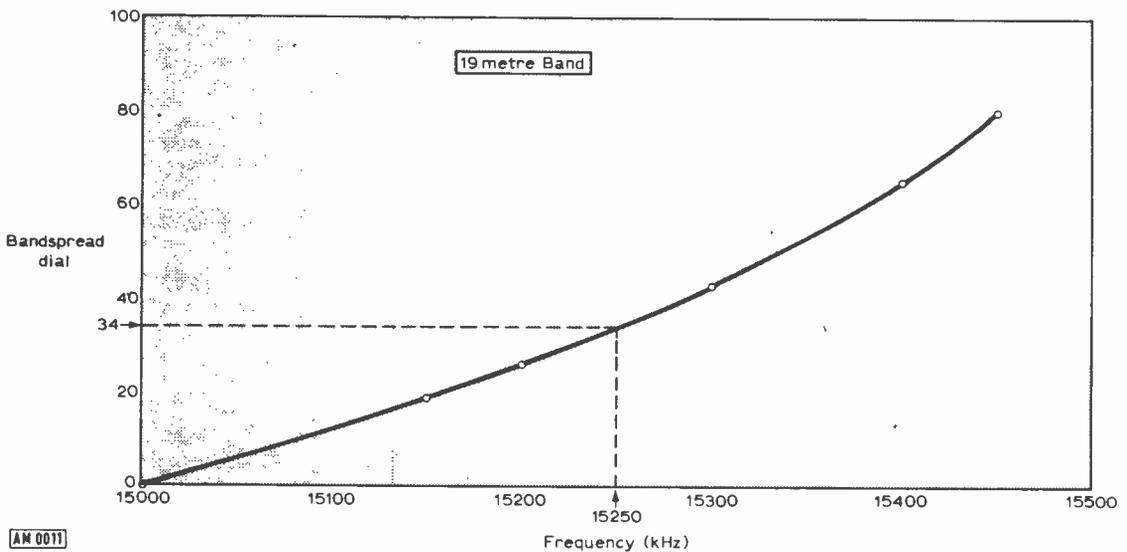


Fig. 2 A typical calibration chart produced by the method described in the article.

capacitor is wired in parallel with a section of the main tuning control. The new control should be mounted as near as possible to the existing variable capacitor with the wiring as short and straight as possible. In order to retain the previous calibration of the receiver, the bandsread control should be half closed and the trimmers TC1/TC2/TC3 unscrewed slightly to compensate for the additional capacitance of the bandsread control.

BANDSPREAD CONTROL

The bandsread control should be fitted with a knob which has a 0 to 100 scale; the larger the knob that can be accommodated on the receiver the better the tuning performance will be. A knob with integral slow motion is better still.

CALIBRATION

The lowest cost method of calibrating a receiver is by drawing calibration charts for the various frequency ranges of interest, using the bandsread control. The best graph paper to use is that which has each large division sub-divided into ten smaller divisions. A separate chart should be drawn for each band but some of the wider bands will require two charts as the bandsread control will not cover the entire band with one setting of the main tuning.

The main tuning is adjusted so that the bandsread will cover the band being calibrated. This position of the main tuning is noted by sticking a piece of tape on the dial or by reference to the receiver's logging scale if one is fitted. As an example, the author's receiver was calibrated on the 19 metre band, being fitted with a 0-100 logging scale, and with the main tuning set at 37 the bandsread control covered the whole band.

The next stage is to do some concentrated listening on the band, trying to hear those stations of which the frequency is known and plotting these on a graph similar to Fig. 2. The stations heard by the author were as follows:

Station	Frequency	Bandsread Setting
WWV	15000 kHz	0
Radio Cairo	15150 kHz	19
RSA, S. Africa	15200 kHz	26
VOA, Tangier	15300 kHz	43
RAI, Rome	15400 kHz	65
Radio Moscow	15450 kHz	80

When all these points have been plotted a smooth curve is drawn between them giving the result shown in Fig. 2. This procedure is repeated for all the bands required by the listener.

The method of calibration by plotting frequencies is tedious but, once done, the graph can be used again and again very simply. One of the basic ideas behind the article was that the minimum of expense was involved. The reader will have to spend some time drawing up the graphs but will have spent very little money.

The use of a crystal calibrator would, of course, speed up the process of drawing the charts. The The 3-range Crystal Marker by R. F. Graham was published in the February 1973 issue of PW and this is ideal for the job, being both simple and inexpensive.

USING THE CHARTS

It is possible to use the charts by simply returning the main tuning to the marked position from which the chart was drawn. This is not very accurate however, and the following method is recommended. When returning to a given band a search is made for one particular station the frequency of which is known, say 15250 kHz. Reference to the graph shows that this should appear at 34 on the bandsread scale. Both the main tuning and the bandsread are then adjusted until the station appears at this bandsread setting. The controls are now set for accurate listening on the band.

Having set up the receiver it is possible to use a chart in two ways. First, it is possible to determine the frequency of a station which has been tuned in by converting the bandsread reading to frequency, secondly, it is possible to tune to any particular frequency, to look for a station, by determining the correct bandsread setting for that frequency and adjusting the control accordingly. ■

PRACTICAL WIRELESS DATACARD SYSTEM 1973

Practical Wireless will be launching a new series of **PW Datacards** in the autumn. These will provide the radio, television, audio and electronics constructor with some of the background information he needs to understand his subject.

The first series of six cards will be printed in full colour and will be given away absolutely free of charge to purchasers of the autumn issues of *Practical Wireless*. To make sure that you do not miss this unique opportunity you should have an order placed with your newsagent at least for the October, November and December issues.

PW Datacards will be inserted in pairs in each of these issues; the first pair in October issue will help all newcomers and established constructors to see at a glance how to read resistor and capacitor values and will show how to determine combined values of two or more of these components quickly. The second pair of **PW Datacards** in the November issue will appeal to all audio enthusiasts.

PW Datacards are designed specially to fit into a jacket pocket, stand on the work bench, hang on the wall, use as a place mat, or even as a bookmark. **No other radio or electronics magazine has given such a comparable free service to its readers.**

Further details on all of these **PW Datacards** will be given in next month's issue of P.W. September issue on sale August 3rd; October issue on sale September 7th.

BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 month guarantee. AC £200/250v. Size 13½ x 11½ in. Above motor board 3½ in. Below motor board 2½ in. With STEREO and MONO XTAL **£8-25** Post 25p.

PORTABLE PLAYER CABINET £4-50

Modern design, black rexine covered, silver front grille. Suitable for above player. Post 25p. Motor board cut for BSR deck.



E.M.I. WOOFER AND TWEETER KIT £5-75

Available separately. Post 25p

Woofers £4-25, Tweeter £1-00

Comprising a fine example of a Woofer 10½ x 8½ in. with a massive Ceramic Magnet, 44oz. Gauss, 13,000 lines, Aluminium Cone centre to improve midrange and top response. Also the E.M.I. Tweeter 3½ in. speaker has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard..... 8 ohms
Maximum Power..... 12 watts
Useful Response..... 35 to 18,000 cps
Bass Resonance..... 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in. £9-90 POST 25p

MODERN GROOVED FRONT DESIGN, TEAK FINISH



SPECIAL OFFER SMITH'S CLOCKWORK 16 AMP TIME SWITCH

Single pole two-way. Maker's last list price £4-50. Brand new and fully guaranteed. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. TWO TYPES AVAILABLE 0 TO 60 MINUTES OR 0 TO 6 HOURS. OUR PRICE £1-86, P. & P. 15p OR £3 PAIR. (STATE TYPE A OR B WHEN ORDERING.)



WEYRAD P50—TRANSISTOR COILS

RA2W Ferrite Aerial..... 8p	Spare Cores..... 8p
Onc. P50/1AC..... 33p	Driver Trans. LFDT4..... 58p
I.F. P50/2CC 470 kc/s..... 38p	Printed Circuit, PCAL..... 58p
3rd I.F. P50/3CC..... 38p	J.B. Tuning Gang..... 65p
P51/I or P51/E..... 38p	Weyrad Booklet..... 10p
P50/3V..... 38p	OPTI..... 68p
Mullard Ferrite Rod 8 x ½ in. 20p, 6 x ½ in. 20p.	

VOLUME CONTROLS 80 Ohm Coax 4p. yd.

5 K. ohms to 2 Meg. LOG or LIN. L.P. 15p. D.P. 25p. STEREO L/S 65p. D.P. 75p. Edge 5K.S.P. Transistor 25p.

BRITISH AERIALITE AERAXIAL-AIR SPACED 40 yd. £1-40; 80 yd. 2£.

FRANGIS LOW LOSS IDEAL 825 & colour 10p yd.

8in & 10in ELAC HI-FI SPEAKERS

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm coil. 8in. 10 watt. **£3-75** Post 25p. 10in. 12 watt music power.



E.M.I. 13½ x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. **£4-50** (As illustrated) Post 25p.

With flared tweeter cone and ceramic magnet, 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. **£2-75** (State 3 or 8 or 15 ohm.) Post 25p.

BOOKSHELF CABINET £5-50 Post 25p. 16 x 10 x 9in.



BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 21 x 6½ x 1½ in. Pre-aligned. Complete with stereo beacon receiver, 12V d.c. operation. 400mV output for 100mV input. Full instructions for any FM Tuner. Some technical experience **£6-95** Post essential. 15p.



BLANK ALUMINIUM CHASSIS 18 s.w.g. 2in. sides, 6 x 4in 45p; 9 x 7in. 80p; 11 x 7in. 70p; 13 x 9in. 80p; 14 x 11in. 95p; 15 x 14in. 99p; 11 x 3in. 50p; 16 x 10in. 41.

ALUMINIUM BOX 6 x 4 x 4in. 80p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 9p; 8 x 6in. 15p; 14 x 8in. 10p; 10 x 7in. 19p; 12 x 8in. 20p; 12 x 8in. 29p; 16 x 8in. 29p; 14 x 9in. 34p; 12 x 12in. 40p; 16 x 10in. 50p

PAXOLIN PANEL 10 x 8in. 15p.

ANOTHER RGS BARGAIN!

4 Transistor Mono Amplifier

Powerful 3 watt output. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. Size 8in. wide x 4 in. deep x 3in. high.

Suitable 7" x 4" speaker, 21. **PRICE £5-95** Post 25p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Main Transformer input 200/240v. AC. Output voltages available 6 or 9 or 12 or 15 or 18 or 20v. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. **£2-20** POST Details S.A.E. Size 3½ x 1½ x 1½ in.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v. or H.T. line 200-300V D.C. operation. Size 1½ x 1½ x 1½". Response 25 c.p.s. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. **99p** Post Full instructions supplied. Details S.A.E.

NEW ELECTROLYTIC CONDENSERS

2/350V .. 14p	250/25V .. 14p	50+50/350V .. 35p
4/350V .. 14p	500/25V .. 20p	80+100/350V .. 58p
8/450V .. 14p	1000/25V .. 35p	32+32/250V .. 18p
18/450V 15p	1000/50V 47p	32+32/450V .. 38p
32/450V 20p	8+8/450V 18p	32+50/250V .. 50p
25/25V .. 10p	8+16/450V 20p	32+32+32/350V 45p
50/50V .. 10p	16+16/450V 25p	100+50+50/350V 45p
100/25V 10p	32+32/350V 25p	

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 15, 25, 30, 50, 100, 200mF. 15V. 10p. 500mF. 12V. 15p; 25V. 20p; 50V. 30p. 1000mF. 12V. 17p; 25V. 35p; 50V. 47p; 100V. 70p. 2000mF. 6V. 25p; 25V. 42p; 50V. 57p. 2500mF. 50V. 25p; 3000mF. 25V. 47p; 50V. 65p. 5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 95p; 50V. 95p.

CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%: 2-2500pF 5p; 500-2,200 pF 10p; 2,700-5,800pF 20p; 6,800pF-0.01m F 30p; each. TWIN GANG. "0-0" 208pF+178pF, 65p; 500pF standard 45p; 365+365 with 25+25pF Slow motion drive 50p. SHORT WAVE, SINGLE. 10pF 30p; 25pF 55p; 50pF 65p. NEON PANEL INDICATORS. 250V AC/DC Amber 20p. RESISTORS. 1 w. 1 w. 1 w. 1p; 2 w. 3 w. 10 ohms to 10 meg. HIGH STABILITY. 1 w. 2 w. 10 ohms to 8 meg. 10p. Ditto 5 w. Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each; 2½ watt, 1 ohm to 8.2 ohms 10p. TAPE OSCILLATOR Coil, Valve Type 35p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13½ x 10 x 3½ in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13½ x 10 x 8½ in. 3 watts per channel. Plays all records 33 rpm, 45 rpm. Separate volume and tone controls. 240v AC mains. Attractive Brown colour, weight 13½ lbs. **£25 + 85p carriage.**

BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned—requires 10.7 Mc/s IF. Complete with tuning gang. Connections supplied but some technical experience essential. **Our Price £3-95** Post 20p.

MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12 v. 50 mA. 25p

250-0-250 80 mA. 6.3 v. 3.5 a. 8.3 v. 1 a. or 5 v. 2 a. £2-50

350-0-350 80 mA. 6.3 v. 3.5 a. 8.3 v. 1 a. or 5 v. 2 a. £2-00

300-0-300 v. 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. £2-25

MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2½ x 2½ x 2in. 75p

MIDGET 220 v. 45 rpm. 45 rpm. 2.8 x 2½ x 2in. 80p

HEATER TRANS. 10p, 30p, 50p

GENERAL PURPOSE LOW VOLTAGE, Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2-25

1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2-25

2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2-75

3 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2-75

3 amp. 8, 5, 8, 10, 13 and 5-0-5 v. £1-80. Ditto 5 amp. 41-50

8-0-8 v. 500 mA. 90p. 9v. 1 amp. 95p. 12v. 300 mA. 75p. 12v. 500 mA. 85p. 12v. 750 mA. 95p.

AUTO TRANSFORMERS 11½v. to 230v. or 230v. to 11½v. 160w. £2-25; 500w. £2-25; 750w. 210v. 1000w. 110v. £2-25

CHARGER TRANSFORMERS. Input 200/250 v. for 6 or 12 v. 1 amp. £1-60; 2 amp. £1-80; 4 amp. £2-60.

BATTERY CHARGERS. 1½ A. 22; 8 A. 23; 4 A. 24. 5 A. 24-50

FACTORY ACT! MAINS ISOLATING TRANSFORMER

Primary 0-110-240 v. Secondary 0-240 v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make. Value £19. **OUR SPECIAL PRICE £10** Carriage 50p.

IDEAL FOR COLOUR TV 50p.

Can be used as 800 watt Auto Transformer 240-110V.

ALL MODELS "BAKER SPEAKERS" IN STOCK HI-FI Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free

BAKER 12in. MAJOR £10

80-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 80-17,000 c.p.s. with tweeter crossover, baffle and instructions. **£12-50** P. & P. 25p.



BAKER "BIG-SOUND" SPEAKERS P. & P. 25p

'Group 25'	'Group 35'	'Group 50'
12 inch £8-80	12 inch £9-90	15 inch £22
25 watt 3 or 8 or 15 ohm	35 watt 3 or 8 or 15 ohm	50 watt 3 or 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS

For 12in. or 10in. dia. speaker 20 x 13 x 9in. £2-90 Post 25p

For 13 x 9in. or 8in. speaker 16 x 10 x 9in. £2-50 Post 25p

For 8 x 5in. speaker 16 x 8 x 6in. £4-40 Post 25p

For 6in. and tweeter 12 x 8 x 6in. £4 Post 25p

LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft.

GOODMANS 6½in. HI-FI WOOFER £4

8 ohm, 10 watt. Large ceramic magnet. Special Cambic cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns, HI-FI Enclosures Systems, etc. Suitable Cabinet 12 x 8 x 6, £4-00. Suitable Tweeter, £2-00.



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 15,000 cps. Size 3½ x 3½ x 2in. deep. Rating 10 watts, 8 ohm or 15 ohm models. **£1-90** Post 10p

CROSSOVER, 95p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1-95.

De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm 23s.

TWO-WAY 8000cps CROSSOVERS 3 or 8 or 15 ohm 95p.

LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in. £1-25; 6½in. £1-50; 8 x 6in. £1-60; 10in. £2-00; 8in. £1-75; 10 x 6in. £1-90; 10in. £2-00. SPECIAL OFFER: 80 ohm, 2½in.; 2½in. 85 ohm, 2½in.; 2½in. 25 ohm, 2½in.; 3½in. dia.; 5in. dia.; 5in. dia. £1 EACH

15 ohm, 3½in. dia.; 6 x 4in.; 7 x 4in.; 8 x 5in.

3 ohm, 2½in.; 2½in.; 3½in.; 6 x 4in. 8 ohm £1-50

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4 watt; 10in. 5 watt; 12in. 6 watt 3 or 8 or 15 ohm models £2-20

VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO. 3, 8 and 15 ohms, 80p.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All transistorized. 4 inputs, speech and music. 4-way mixing. Output 8/15 ohm. A.C. 200/250v. Separate Treble and Bass controls. Guaranteed. Details S.A.E. **£49** Post. Free



BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4-95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphones, records, tape and tuner with separate controls into single output. 9 volt. **£3-95**

STEREO VERSION OF ABOVE £5-95

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tunings. Walnut Cabinet. Size 7 x 5 x 4 in. £14-85

BARGAIN FM TUNER as above less cabinet. £9-85

BARGAIN 8 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £4-50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTPUT BOXES. SURFACE OR FLUSH, 25p.

BALANCED TWIN RIBBON FEEDER 300 ohms 5p yard.

JACK SOCKET 8id. open-circuit 14p. closed-circuit 23p.

Chrome Lead Socket 45p. Phone Plug 5p. Phone Socket 12p.

JACK PLUGS 8id. Chrome 15p; 3-Imm. Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 8p; CANS 5p.

TWO RPM GEARED MOTOR 240v. A.C. mains. Ideal for displays/disco 95p post lightwheels. 25p.

E.M.I. GRAM MOTOR 120v. or 240v. A.C. 2.400 rpm. 2-pole 70mA. Spindle 3 x ¼ in. Size 2½ x 2½ x 2½ in. **£1-00** Post 25p.

DELUXE 4 POLE MOTOR 1400 rpm. 42W size 3½ x 3½, post 25p. £1-95.

Would you spend an hour a day to earn more money in Electronics- Television-Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and our wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics - in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments).

With ICS you study at home - at your own pace, when you choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

ICS your key to the door
of opportunity

Tick or state subject of interest and post to:
International Correspondence Schools, Dept. 232S,
Intertext House, Stewarts Road, London SW8 4UJ.

Subject of interest _____

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name _____

Address _____

Occupation _____ Age _____

■ Accredited by the Council for the Accreditation of Correspondence Colleges ■

GLADSTONE RADIO

66 ELMS ROAD, ALDRESHOT, Hants GU11 1LP

No export. Min. order 50p. Prices include VAT.


Closed Wednesdays



F.M. TUNER-AMPLIFIER for 88-102 MHz. Self-powered for 200-250v. a.c. double wound mains trans. Valves ECC85, EF89, EF80, rectx. Chassis 10" x 6" x 6". Audio module output stage giving 3W into 16-ohms. Price **£12** (p. & p. 65p).

MAINS TRANSFORMERS. 240-250v. input. Deduct 10% for more than two transformers. Trade enquiries invited.

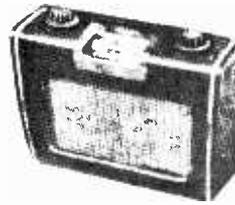- B. Charger 12v. at 1½A. **66p** (20p post)
- E. 250v. at 50 m.a., & 6-3v. at 1½A. **55p** (20p)
- H. 90v. at 100m.a., & 220v. at 50m.a. **88p** (20p)
- J. 37v. 2A, 24-0-24v. 150m.a. **£2-75** (70p)
- K. 250-0-250v. 150m.a. 20v. ½A. 15v. 1A. 6-3v. 5A. **£3-80** (70p)
- M. 110v. input; 200-0-200v. 50m.a. 6-3v. 1½A. **60p** (25p)
- P. Driver, 5 to 1 + 1 suitable 60W. amp. **42p** (20p)
- Q. 100v. 100ma, 25v. 250ma. 6-3v. A1. double shrouded **55p** (25p)
- R. 230v. 60ma. 6-3v. 2½A. **60p** (35p)
- S. 260-0-260v. 60ma. 6-3v. 2½A. **75p** (35p)
- 100 Resistors ½W. & ¼W. **27p** (10p)
- 100 Silvered Mica **40p** (10p)
- 100 Diodes AEI - CG82 = OA90 **£3** (10p)
- 100 Ceramics **60p** (10p)
- 100 High Stabs. **50p** (12p)
- ½ lb Tag Strips 2 to 10 way **£1** (10p).
- 100 Shakeproof washers ½" clear i.d. **25p** (5p)



MW/LW TRANSISTOR RADIO

Complete set of parts for this MW/LW Transistor Radio. Coverage 192-555m + 1070-1870m. 9 volt 6 transistor superhet using 3 AF117 in RF and IF stages powered by a two stage AF amplifier using 3 x AC128. Output approx. 500MW. Also works off car-serial. Ply case, rexine covered. Requires PF7 battery, price **£7p** extra. 3½in high-quality speaker. Price **£6-60** (40p).

P. C. BOARDS



FOR P.W. PROJECTS
REVERBERATION UNIT'
8 WATT AMPLIFIER & PRE-AMP
LOUDHAILER PRE-AMP & SIREN GENERATOR
VIBRASONIC GUITAR PRE-AMP
DIGITRONIC DIGITAL CLOCK

AND ALSO FOR MANY P.E. PROJECTS
SEND AN S.A.E. FOR OUR FREE LIST
(and with all enquiries please)

P.S. We also have components for most of the PCBs.

PHONOSONICS

DEPT PW8, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
MAIL ORDER ONLY

NEW VALVES!

GUARANTEED AND TESTED

24-HOUR SERVICE

PRICES INCLUDE VAT


1R5	28	30P19	53	ECC81	15	EL33	63	PCF86	44	PY801	80
1R5	23	30PL1	54	ECC82	17	EL41	47	PCF801	27	R19	27
1T4	18	DAF91	23	ECC83	21	EL84	20	PCF802	38	U26	68
354	28	DAF96	35	ECC85	31	EM80	35	PCF805	55	U26	64
3V4	46	DF91	18	ECH35	48	EM81	35	PCL82	28	U191	54
6/30L2	48	DF96	35	ECH42	56	EM84	30	PCL83	53	U251	60
6AT6	18	DH77	18	ECH61	28	EY85	27	PCL84	51	U329	65
6AQ5	23	DK91	28	ECL80	27	EZ80	19	PCL85	36	UABC80	29
6BW7	48	DK92	47	ECL82	27	EZ81	21	PCL86	35	UBF89	28
6F1	57	DK96	43	ECL86	32	KT61	63	PPL200	45	UCC85	32
6F23	64	DL92	28	EF39	43	KT66	75	PL36	45	UCH42	56
6F25	49	DL94	46	EF41	58	N78	£1.00	PL81	41	UCH81	28
12AU7	17	DL96	38	EF80	22	PC86	42	PL82	29	UCL52	30
25L6GT	18	DY86	21	EF85	28	PC88	42	PL83	31	UF41	49
30C15	56	DY87	21	EF86	27	PC97	34	PL84	28	UF89	28
30C17	78	DY802	28	EF89	24	PC900	28	PL500	56	UL41	58
30C18	55	EABC80	28	EF91	15	PXC84	27	PL504	56	UL84	27
30F5	60	EBC33	43	EF92	28	PXC89	41	PY81	28	UY41	35
30FL1	59	EBC41	47	EF183	25	PXC189	46	PY82	23	UY85	32
30FL14	63	EBF89	27	EF184	27	PCF89	25	PY900	30	W77	42

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no calls.


GERALD BERNARD

83 Osbaldeston Road,
Stoke Newington, London N16

GOING BACK...

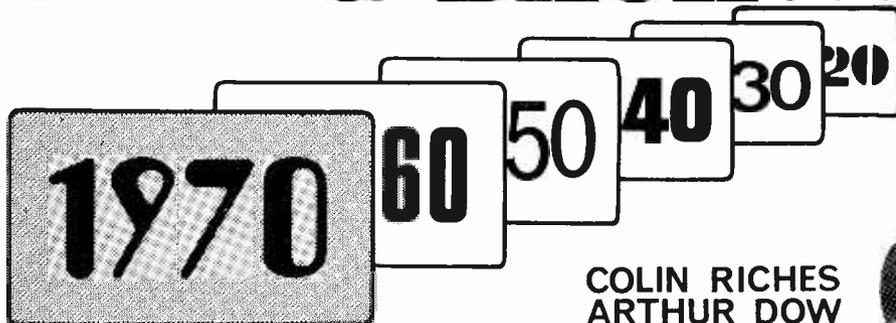

COLIN RICHES
ARTHUR DOW

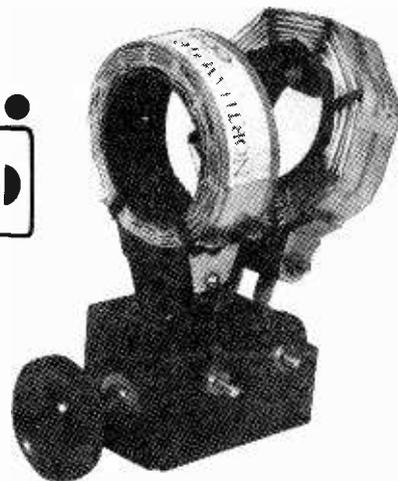

MR. J. TURNER tells us that he managed to purchase a Marconiphone model V2 receiver at a local auction. He has restored it to working order and it performs very well—especially on long waves. Tuning is accomplished by sliding in various ebonite slabs—each covering a different range. Each contains an “embedded” coil which is tuned by copper “spades.” There is a “regenerator unit” which does not seem to fulfil any useful purpose and Mr. Turner would like to hear from any readers who can comment on this. The valves are of the D.E.R. type (dull emitters). The h.t. supply is 90V and l.t. 3V. The set still bears its original transfers and is in very good condition throughout. Inside the lid there is an ivory plate giving the serial number of the set as “installation no. S/A 2535.

Mr. Turner would like any information on this set that readers could supply.

We found a reference to the V2 in a catalogue kindly lent to us by Dr. Brodribb—another vintage radio collector. It reads: “The Marconiphone V2 gives excellent results as a long-range instrument. By its reflex circuit, two valves do the work of three. It holds a remarkable record of results from overseas stations, including America. Cost of upkeep is comparatively negligible, and is perfectly simple to operate.”

In c1926 the V2 could be obtained from Upfield and Sons (Motors) at Hastings, for the sum of £10.5s.

The receiver complete with accessories, including two D.E.R. valves cost £14.11s.2d and a dry cell combination including two D.E.3. valves cost £14.13s.8d. There was also a Marconi royalty of £1.5s to pay.

Our old friend Chris Petsikopoulos from Greece tells us he has recently returned from holiday and writes:

“During that time I had the opportunity to make a great search which brought great finds, the most important of all was a French radio-set of the era 1917-1918, made by “DUCRETET”, Paris, providing a 100 watt spark Transmitter and crystal detector receiver connected in a common tuning circuit through a change-over switch.

The tuning circuit consists of an Oudine coil with a slider for the aerial and a variable capacitor used only for reception, this meaning that the transmitter works on a standard wave length (450m). The whole unit is housed in a compact wooden case 17 x 12 inches, and is in nice condition. In the case are housed the tuning coil, variable capacitor, send-receive switch, mica condenser, high tension coil with interrupter, and a 10 amp. meter. Also connectors for key and headphones. On top of the set are aerial-earth connectors, crystal detector, and spark-gap. Connectors for 12V d.c. are on the right side of the case.

Connecting a 12V battery, a 100 foot aerial and an earth, the set was able to work. The aerial was



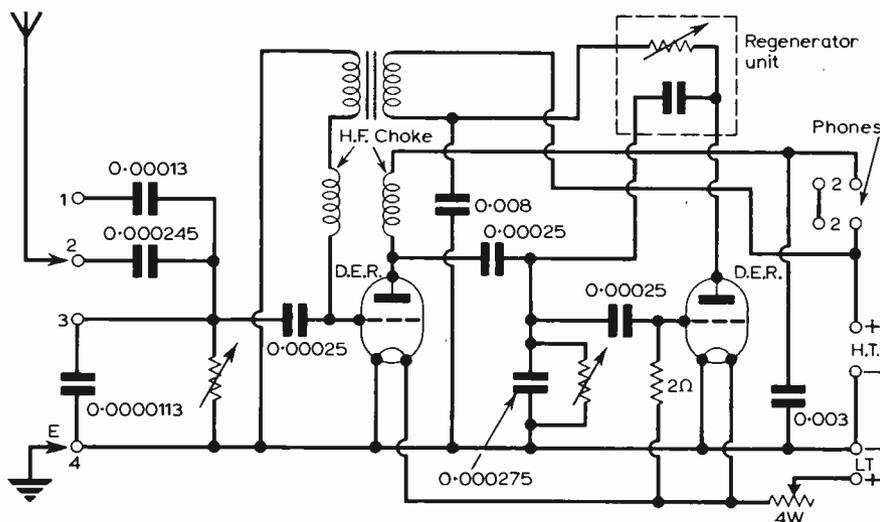


Fig. 1: The circuit of the Marconi V2 receiver re-drawn from the information supplied by Mr. J. Turner.

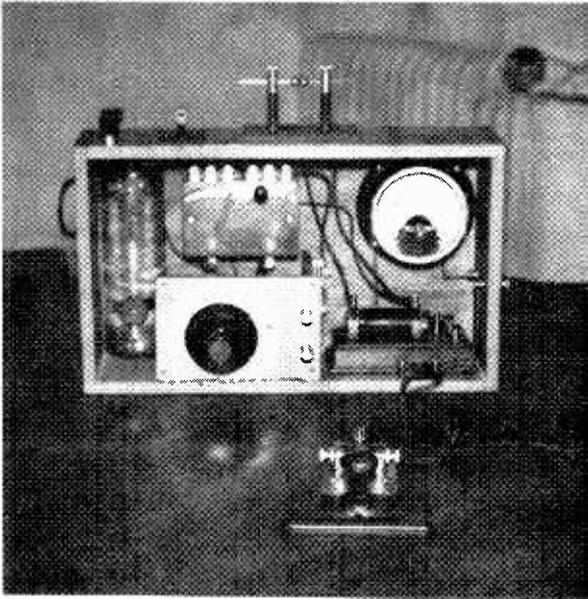

Chris Petsikopoulos' "Diuretel" Tx/Rx.

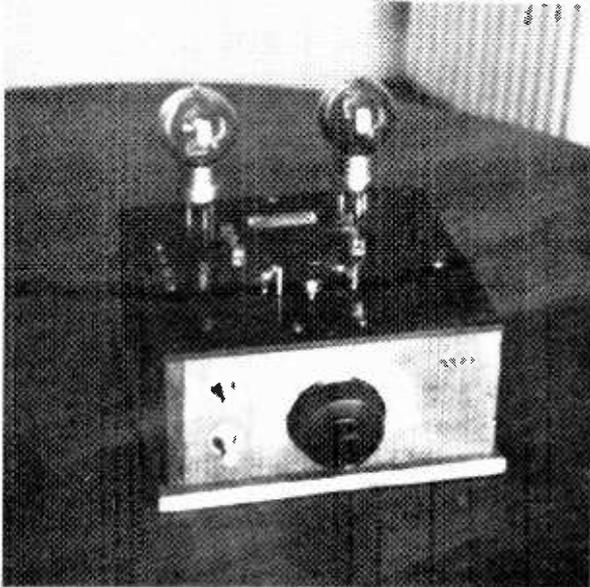

The "Thomson-Houston" receiver.

tuned with the slider for maximum current, 5-6 amp., giving a nice audible buzzing signal in a range of about 5-8 miles depending on the position of the car which was used for checking the range. The receiver has a range from 250-600m and the reception of several broadcasting stations was able with good volume, the only difficulty being in finding a sensitive position on the crystal although the change-over switch provides a third position where the tuning circuit is off and the buzzing of the interrupter is then used to adjust the detector.

Shown are pictures of the above set and of a 1922 two valve Heterodyne made by "Thomson-Houston", Paris, valves are type R-5 of "La Radio-technique" still working. The set is accompanied with a band switching frame aerial covering a wave length from 400m to 3,000m in three ranges "

Mr. H. E. Hunt, 68 Oundle Road, Thropston, Northants, quotes some prices he noticed for making one's own components.

"Your feature "Going Back" has caused me to reach for Vol. IV of "The Amateur Mechanic" whose mildewed covers contain the inspiration that set me building my first "Wireless Telegraph" set (1920-21).

There is no "Components List" because there were no components in those days but a "Specification of Materials" and I quote that portion for the variable condenser only:—

	s.	d.
1 sq. ft of 1/4 inch teak (to make box)	6	
1 sq. ft. of thin sheet zinc	2	
2 small nuts and bolts	2	
1 knob (off rubber stamp or screwdriver)	-	
2 small brass terminals	3	
8 ins. electric light flexible wire	2	
6 old quarter plate negatives	-	

Total cost 1 3

(The last item was for di-electric, not P.C.Bs.) These were the days of ebonite, teak, brass turning and 2lb. soldering irons (gas heated).

Such was the success of this "Long Distance Receiver"—Poldhu, Eiffel Tower and numerous spark transmitters were received—using a 6ft. twin spreader aerial, 50ft. long and 30ft. high, that I was able to obtain parental financial backing (30/-) to build a single valve receiver.

The valve was an ungettered one of Dutch manufacture (15/-) which not only furnished sufficient light to work to but formed the nucleus of a receiver that occupied one half of the work bench.

But what a new world it opened up, the Hague concerts on Sundays, and England's first and unsurpassed comper P. P. Eckersley from 2.MT. at Writtle, Essex on Tuesday evenings.

There were also at this time some excellent telephony transmissions from local Northampton amateurs (2.TV.-5XH-5XG).

I started using the d.c. mains for h.t. long before eliminators were on the market, except that one had to put up with a complete loss of signals every time a tram passed 200 yards away.

One could write a book on the early days of amateur "wireless" but for myself I must hurry off to change an under-rated thyristor in the speed control of my wheel chair (or something like that). Tempus fugit!!

FUTURE PLANS

Let us tell you why you should know about some of our future plans in *Practical Wireless*.

First, our autumn issues are being planned as the best yet; secondly, we will be doing what no other magazine has ever done before; thirdly, if you don't find out about these and order your copies in advance, your newsagent is very likely to sell out before you get there.

Naturally, we cannot tell you everything now, but we can tell you what to look for next month, and in the following issues. Want to know more? Then keep your eyes on our "Leader" page and turn to pages 320, 334, 335 and 350 for further details in this issue.

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIRCHILD



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
8N7400	P	P	P	8N7450	0	20	18	0	18	18	18
8N7401	0	20	18	8N7451	0	20	18	0	18	18	
8N7402	0	20	18	8N7452	0	20	18	0	18	18	
8N7403	0	20	18	8N7453	0	20	18	0	18	18	
8N7404	0	20	18	8N7454	0	20	18	0	18	18	
8N7405	0	20	18	8N7455	0	20	18	0	18	18	
8N7406	0	30	27	8N7456	0	30	27	0	25	25	
8N7407	0	30	27	8N7457	0	30	27	0	25	25	
8N7408	0	20	18	8N7458	0	20	18	0	18	18	
8N7409	0	45	42	8N7459	0	45	42	0	40	40	
8N7410	0	20	18	8N7460	0	20	18	0	18	18	
8N7411	0	23	22	8N7461	0	23	22	0	18	18	
8N7412	0	42	40	8N7462	0	42	40	0	35	35	
8N7413	0	30	27	8N7463	0	30	27	0	25	25	
8N7416	0	30	27	8N7464	0	30	27	0	25	25	
8N7417	0	30	27	8N7465	0	30	27	0	25	25	
8N7420	0	48	44	8N7466	0	48	44	0	40	40	
8N7422	0	48	44	8N7467	0	48	44	0	40	40	
8N7423	0	48	44	8N7468	0	48	44	0	40	40	
8N7425	0	48	44	8N7469	0	48	44	0	40	40	
8N7427	0	42	39	8N7470	0	42	39	0	35	35	
8N7428	0	50	45	8N7471	0	50	45	0	42	42	
8N7430	0	42	39	8N7472	0	42	39	0	35	35	
8N7432	0	42	39	8N7473	0	42	39	0	35	35	
8N7433	0	70	61	8N7474	0	70	61	0	50	50	
8N7437	0	85	80	8N7475	0	85	80	0	70	70	
8N7438	0	85	80	8N7476	0	85	80	0	70	70	
8N7440	0	20	18	8N7477	0	20	18	0	18	18	
8N7441AN	0	75	72	8N7478	0	75	72	0	60	60	
8N7442	0	75	72	8N7479	0	75	72	0	60	60	
8N7443	1	00	95	8N7480	0	80	75	0	67	67	
8N7445	2	00	175	8N7481	1	25	15	1	10	10	
8N7446	2	00	175	8N7482	0	87	80	0	70	70	
8N7447	1	75	160	8N7483	1	00	90	0	85	85	
8N7448	1	75	160	8N7484	0	80	75	0	80	80	
				8N7485	0	80	75	0	80	80	
				8N7486	0	45	42	0	38	38	
				8N7487	0	75	70	0	65	65	
				8N7488	0	80	75	0	80	80	
				8N7489	0	75	70	0	65	65	
				8N7490	0	80	75	0	80	80	
				8N7491	0	50	45	0	40	40	
				8N7492	0	75	70	0	65	65	
				8N7493	0	75	70	0	65	65	
				8N7494	0	80	75	0	80	80	
				8N7495	0	80	75	0	80	80	
				8N7496	1	00	97	0	95	95	
				8N7497	6	25	50	6	50	50	
				8N7498	2	00	30	2	20	20	
				8N7499	1	45	135	1	120	120	
				8N7500	1	45	135	1	120	120	
				8N7501	0	50	45	0	40	40	
				8N7502	0	70	60	0	50	50	
				8N7503	1	00	95	1	90	90	
				8N7504	1	00	95	1	90	90	
				8N7505	1	00	95	1	90	90	
				8N7506	1	00	95	1	90	90	
				8N7507	1	00	95	1	90	90	
				8N7508	1	00	95	1	90	90	
				8N7509	1	00	95	1	90	90	
				8N7510	1	00	95	1	90	90	
				8N7511	1	00	95	1	90	90	
				8N7512	1	00	95	1	90	90	
				8N7513	1	00	95	1	90	90	
				8N7514	1	00	95	1	90	90	
				8N7515	1	00	95	1	90	90	
				8N7516	1	00	95	1	90	90	
				8N7517	1	00	95	1	90	90	
				8N7518	1	00	95	1	90	90	
				8N7519	1	00	95	1	90	90	
				8N7520	1	00	95	1	90	90	
				8N7521	1	00	95	1	90	90	
				8N7522	1	00	95	1	90	90	
				8N7523	1	00	95	1	90	90	
				8N7524	1	00	95	1	90	90	
				8N7525	1	00	95	1	90	90	
				8N7526	1	00	95	1	90	90	
				8N7527	1	00	95	1	90	90	
				8N7528	1	00	95	1	90	90	
				8N7529	1	00	95	1	90	90	
				8N7530	1	00	95	1	90	90	
				8N7531	1	00	95	1	90	90	
				8N7532	1	00	95	1	90	90	
				8N7533	1	00	95	1	90	90	
				8N7534	1	00	95	1	90	90	
				8N7535	1	00	95	1	90	90	
				8N7536	1	00	95	1	90	90	
				8N7537	1	00	95	1	90	90	
				8N7538	1	00	95	1	90	90	
				8N7539	1	00	95	1	90	90	
				8N7540	1	00	95	1	90	90	
				8N7541	1	00	95	1	90	90	
				8N7542	1	00	95	1	90	90	
				8N7543	1	00	95	1	90	90	
				8N7544	1	00	95	1	90	90	
				8N7545	1	00	95	1	90	90	
				8N7546	1	00	95	1	90	90	
				8N7547	1	00	95	1	90	90	
				8N7548	1	00	95	1	90	90	

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SM 74 LOO } for list No. 36
LOW POWER SM 74 LOO }

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AAY30 10p	BC147 12p	RU105 2.25	OC44 15p	TR843 35p	2N3055 55p
AAY32 10p	BC169C 12p	RY100 15p	OC45 15p	V405A 25p	2N3440 75p
AZ13 10p	BE192 10p	BY126 15p	OC57 15p	ZTX108 15p	2N3442 1.25
AC707 85p	BC214 15p	BY127 15p	OC71 15p	ZTX300 12p	2N3625 25p
AC126 25p	BCY32 75p	BYZ13 35p	OC72 25p	ZTX301 15p	2N3614 55p
AC127 25p	BCY34 35p	CI06D 65p	OC77 45p	ZTX302 18p	2N3615 75p
AC128 25p	BCY39 1.00	GE111 55p	OC81 25p	ZTX341 20p	2N3702 10p
AC176 25p	BCY49 30p	GE115 55p	OC93 25p	ZTX500 15p	2N3704 10p
AC181 25p	BCY45 2.50	GE130 55p	OC140 55p	ZTX501 15p	2N3705 55p
AC188 25p	BCY55 2.50	LM309K	OC170 30p	ZG301 30p	2N3714 1.80
ACY17 30p	BCY70 15p	(T03) 1.87	OC200 45p	2N404 20p	2N3771 1.75
ACY20 20p	BCY71 20p	MAT121 25p	OC201 45p	2N527 35p	2N3773 2.00
ACY21 20p	BCY72 15p	MJF340 50p	OC202 75p	2N598 15p	2N3790 2.25
ACY39 55p	BCY87 2.95	MJF379 70p	OC203 50p	2N597 15p	2N3819 35p
AD140 80p	BCZ11 50p	MJE520 75p	OC204 45p	2N706 1.0p	2N3829 50p
AD149 50p	BD124 80p	MJE2855	OC271 1.25	2N930 20p	2N3866 85p
AD161 35p	BD131 75p	1.10	ORP12 50p	2N937 45p	2N3903 15p
AD162 35p	BD132 80p	MJE3055	ORP60 40p	2N1131 25p	2N3906 12p
AF117 20p	BF115 25p	75p	P346A 20p	2N1132 25p	2N4061 12p
AF118 50p	BF167 25p	MFP105 40p	RAS501AF	2N1302 15p	2N4062 12p
AF124 25p	BF172 25p	NKT214 20p	RAS502AF	2N1304 22p	2N4122 55p
AF139 30p	BF179 30p	NKT216 40p	TAA283 75p	2N1305 22p	2N4871 35p
AF186 40p	BF180 30p	NKT217 40p	TIL209 39p	2N1307 25p	2N5457 30p
AF239 40p	BF194 15p	NKT403 70p	TIP230A 80p	2N1308 25p	2N5777 55p
ASY27 30p	BF195 15p	NKT404 50p	TIP33A 1.00	2N1513 20p	28001 1.00
ASY28 25p	BF261 25p	OA10 35p	TIP34A 1.50	2N1671 1.00	28012 1.00
BA102 30p	BFX13 25p	OA200 7p	TIP35A 1.50	2N2147 75p	28018 6.25
BA115 7p	BFX13 25p	OA200 7p	TIP35A 1.50	2N2160 50p	28026 8.80
BA145 15p	BFX34 75p	OA209 10p	TIP36A 2.50		

TAKE 20

DAVID ANDREWS

No. 51 TOUCH-SENSITIVE SWITCH

A series of simple transistor projects, using not more than twenty components.

Nowadays there is a tendency to veer away from electro-mechanical switches to electronic versions which have no moving parts. The reason is twofold; first there is less likelihood of failure and secondly there is a strange fascination in setting something in motion or switching on something without any apparent mechanical intermediary. This is already happening in applications such as lift control buttons and desk calculator keying so why not in a few domestic situations, or as a replacement for the Morse operator's key?

This month's circuit is a very simple way of providing touch sensitive keying and is capable of several types of output including an output that illuminates a low voltage lamp but the circuit can be quite easily modified to provide a relay drive


(rather negating the original sentiment of avoiding mechanical components!) or, better still, a logic (TTL) compatible output.

Operation


Touch sensitivity is achieved by detecting the minute current that passes through the finger when a pair of contacts is bridged by the touch of the operator. The touch transducer in the prototype was made from a 1 in. square of 0.1 in. pitch Veroboard, with alternate copper strips paralleled together to form a contact pattern.

A more attractive touch plate could be made by printed circuit techniques and if this is done it is better to use a fibre-glass base. In either case the copper contacts need some protection from corrosion and this can be effected by lightly tinning the strips with solder.

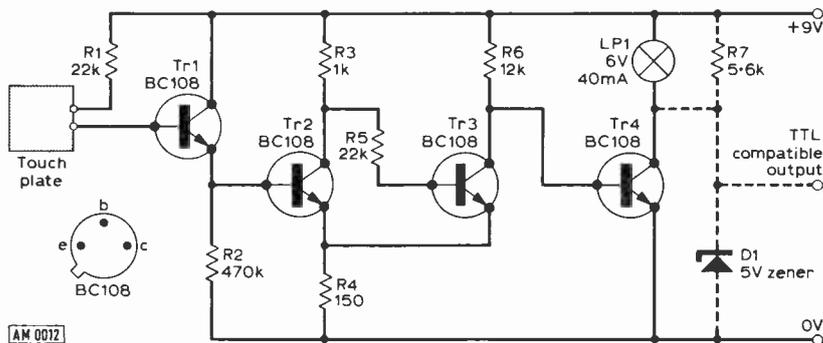The touch plate is connected between the supply



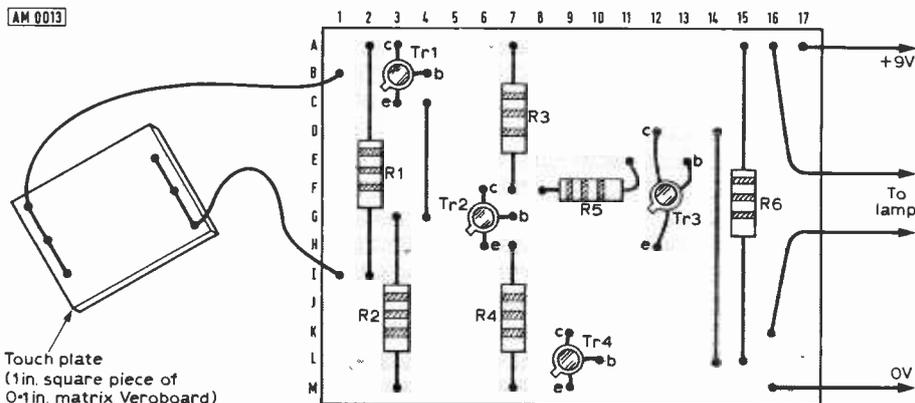Circuit of the touch-sensitive switch, with alternative TTL output circuit.



Layout of components on the Veroboard with details of the touch plate.

rail (through R1) and base of Tr1 which should have low leakage current (beware of cheap "reject" transistors). When the plate is touched a very small current flows in the base/emitter circuit of Tr1 and this in turn permits a much higher current to flow between collector and emitter. Tr2 and Tr3 are connected as a Schmitt Trigger circuit; the emitter current from Tr1 flows mainly into the base of Tr2 and turns it on; this causes Tr3 to turn off and the potential at its collector starts to rise until base current in Tr4 is established. When this occurs the lamp LP1 lights. Alternatively, considering the TTL version, the output level falls to "0".

★ components list

R1	22kΩ	1p
R2	470kΩ	1p
R3	1kΩ	1p
R4	150Ω	1p
R5	22kΩ	1p
R6	12kΩ	1p
Tr1	BC108	10p
Tr2	BC108	10p
Tr3	BC108	10p
Tr4	BC108	10p
LP1	6V 40mA,	10p
Veroboard		20p
		—
		76p
		—

No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

Removing the finger from the touch plate causes the base current to stop flowing in Tr1; current into the base of Tr2 thus stops and the latter starts to turn off. As this occurs Tr3 starts to draw base current through R3 and R5 and begins to turn on. As this happens the potential at Tr3's emitter starts to rise slightly and this (due to the feedback inherent in a Schmitt Trigger) causes Tr2 to turn off faster. At the same time the potential at Tr3's collector falls until sufficient base current into Tr4 can no longer be maintained. Tr4 thus turns off and the lamp goes out. Alternatively the TTL output goes to a logic level "1".

TTL Output

To obtain the TTL output version R7 and zener diode D1 should be in circuit and lamp LP1 omitted. For relay operation LP1 should be replaced by a 6 volt relay. The components list has not taken the alternative versions into account.

Note

A word of warning—the touch plate should not be used out of doors or with wet fingers because droplets of moisture bridging the conductors will provide sufficient current to make the circuit switch. Possibly this problem could be overcome by carefully painting in the gaps between the strips with a good quality water repellent paint having a high gloss finish.

VHF BAND

144

LOCATOR

145

A. SYDENHAM

146

MHz

THE easily built unit to be described is used to provide a signal in the 2 metre Amateur band (144-146MHz). When constructing or modifying apparatus for 2 metre use it can be very difficult indeed to locate the band or any part of it. Indeed in some areas, amateur activity is so low that many hours of experimenting may be wasted in tuning for non-existent transmissions. Experienced constructors will know to their cost that at v.h.f. finicky adjustments are often required and in the case of a tuning coil for example just one half turn too little or too much may result in the circuit being so far off frequency as to be useless for the purpose required. To overcome problems such as these this unit was quickly assembled—and at small cost.

The circuit of the device is shown in Fig. 1; it is by no means unique but rather the practical outcome of some earlier experiments. Basically a crystal-

controlled oscillator—Tr1 and associated items—provide harmonic output which is lightly audio modulated due to Tr2 circuitry. The modulating section is by no means essential but it does enable the user to aurally recognise the v.h.f. signal being generated which is, in the case of the 6025kHz crystal utilized, the twenty-fourth harmonic (6025 x 24 = 144.6MHz). Whether or not the final generated frequency is exactly at this figure is not too important provided it is in the 2-metre amateur band.

Inductor L1 is tuned by trimmer TC1 to the crystal harmonic frequency, L2 merely being a low impedance untuned output link closely coupled to L1. In the f.e.t. source circuit inductor L3 is tuned to the crystal frequency by capacitor C1, final fine tuning being accomplished by means of the dust core which when once set can be so left. The drain current taken by Tr1 when oscillating correctly is approximately 2mA from a 9V d.c. supply.



MULLARD AMP

Sensational "Once in a Lifetime Offer" Unrockable once stocks are cleared. The amplifier is made by Mullard. Carries maker's Guarantee. In neat case. May be used for Mono or

Stereo. Music or speech. Works off dry battery, car batt. or mains power pack. FREE—all who purchase we send copy of Mullard booklet DIY stereo. \$1.60.

DRILL CONTROLLER


NEW IKW MODEL

Electrically changes speed from approximately 10 revs to maximum. Full power at all speeds by fingertip control. Kit includes all parts, case, everything and full instructions. \$1.85. 13p post and p. Made up model also available. \$2.48.



MIGHTY MIDGET

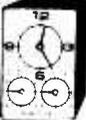Probably the finest possible radio, as described in *Practical Wireless*, January 73. All electronic parts \$2.20 post paid.



TIME SWITCH

Smith's mains driven clock with 16 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bill, etc. \$1.85.

I CHIP RADIO

Ferranti's latest device ZN414 gives results better than superhet. Supplied complete with technical notes and circuits. \$1.38 each. 10 for \$11.11.

HI-Q TUNER COMPONENTS

For experimenting with the ZN414. KIT NO. 1. Plessey Miniature Tuning Condenser with built-in LW switch and 3" Ferrite slab and litz wound MW coil, 72p. KIT NO. 2. Air spaced tuning condenser 6" ferrite rod litz wound MW and LW coils, 94p. KIT NO. 3. Air spaced TC with slow motion drive 8" ferrite rod, with litz wound LW and MW coils, \$1.10. KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coils, 45p.



12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 uF smoothing. Price \$2.20, plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps — maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply inter-change push on leads, silicon rectifiers and smoothing by 3,000uF. Price \$8.33 plus 50p post.

MICRO SWITCH

5 amp changeover contacts, 11p each 10 for 99p. 15 amp. 5p Model 15p Changeover 15p each.



MAINS RELAY BARGAIN

Special this month are some single, double and treble pole change-over relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Unused. Size approx. 1 1/2" x 1". Open construction. Single pole 25p each 10 for \$2.48. Treble pole 39p each 10 for \$3.57

MAINS OPERATED SOLENOIDS

Model 772 - small but powerful 1/2 in. pull approx size 1 1/2 x 1 1/2 in. 88p. Model 4001 - 3/4 in. pull. Size 2 1/2 x 2 x 1 1/4 in. 83p. Model 771 - 1 1/2 in. pull. Size 3 x 2 1/2 x 2 in. \$1.98 plus 20p post and insurance

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4; PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only \$1.10 plus 20p postage.

DESK TELEPHONES

Ex G.P.O. Black standard model with dialling dial but no internal bell. Supplied with connection diagram 94p each. Post, etc. 40p for single then 65p per pair. Ditto, with bell but without dialling dial 98p each plus 40p post for single then 65p per pair.



PAPST MOTORS

Est. 1/400th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. \$1.65 each. Postage one 25p, two 33p, 250V model \$3.80.



10 AMP DIMMER CONTROL

For the control of lighting on stage or in a studio or for control of portable equipment in workshops, etc. This has two 13 amp socket outlets each is controlled by a 5 amp solid state regulator. The overall length is 17in., width 3 1/2 in. and depth 1 1/2 in. In the end is fitted a master On/Off switch indicator, lamp and fuse. Price \$8.25.

STANDARD WAFER SWITCHES

Standard size 1 1/2" wafer—silver-plated 5 amp contact, standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2way	3way	4way	5way	6way	8way	9way	10way	12way
1 pole	44p	44p							
2 poles	44p	44p							
3 poles	44p	44p	44p	44p	77p	77p	77p	1.04	1.04
4 poles	44p	44p	44p	77p	77p	77p	77p	1.32	1.32
5 poles	44p	44p	77p	77p	1.04	1.04	1.04	1.80	1.80
6 poles	44p	77p	77p	1.04	1.04	1.04	1.87	1.87	1.87
7 poles	77p	77p	1.04	1.32	1.32	1.32	2.15	2.15	2.15
8 poles	77p	77p	1.04	1.32	1.32	1.32	2.42	2.42	2.42
9 poles	77p	77p	1.04	1.04	1.60	1.60	2.70	2.70	2.70
10 poles	77p	77p	1.04	1.32	1.60	1.60	3.00	3.00	3.00
11 poles	77p	1.04	1.04	1.32	1.87	1.87	3.25	3.25	3.25
12 poles	77p	1.04	1.04	1.32	1.87	1.87	3.52	3.52	3.52

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price \$6.55 plus 30p post. When ordering please state whether for positive or negative systems. Also available, ready made ignition systems for 6V. vehicles \$7.95 plus 20p.


ELECTRONIC IGNITION

MULLARD UNILEX

This D.I.Y. Stereo Amplifier is still available complete at £7.00 for the four Mullard Modules, or Modules can be bought separately as follows:— 4 watt amplifier module (2 required) Mullard Ref. No. E.P.9000—£1.80. Pre amp non ulx Mullard Ref. No. E.P.9001—£1.98 each. Power Module—Mullard Ref. No. E.P.9002—£2.53 each. In addition add made to Mullard specification we offer:— Standard Control Unit with escutcheon and knobs—£3.30. Knobs—Set of 4—50p. Special offer the complete Unilex with control panel at Pre VAT price £10.00 post paid.

ZPM MODULATION MOTOR

Could also be used to open ventilators, doors, valve, damper, etc. particularly suitable for remote control. Made by Satchwell. Essentially a reversible geared motor fitted with internal limit switches to stop it at the end of its travel. Size approx. 6in. x 6in. x 3 1/2 in. and weighing approx. 10 lb. This is extremely powerful and would lift a heavy door or open a long line of ventilators. To operate this motor you put the 50 cycle supply through a changeover switch. For instance a thermostat with changeover contacts could automatically regulate the temperature in a growing house, chicken hatchery, etc. An indicator on the motor graduated 0-10 shows the state of open or close. Also internally fitted is a variable resistor, wires from this to a volt meter would give a remote indication of the open or close position. A very expensive motor if both direct from Satchwell, our price complete with step down Transformer is £16.50.

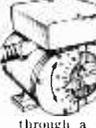

CENTRIFUGAL FAN

Mains operated, turbo blower type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p., giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2 in. wide x 12 in. dia. outlet into trunking 10 1/2 x 4 1/2 in. £8.55 plus £1 post and insurance.



THIS MONTH'S SNIP

TAPE PLAYBACK UNITS

Mains operated. Made by RealTime the famous "music in background" people. These are complete units ready to work and you understand that they are in good going order. We have not tested them but would exchange any that do not work properly. These have a superior motor from its wheel control the tap through the output and also an even equally useful valve amplifier with EL84 output. In a steel case with carrying handle. Two models offered, good as new £6.50 and somewhat used at £3.50. 75p carriage in. £2.00 miles then 50p per 100 miles extra.



24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 6A changeover contacts will switch circuit on or off during these periods. £2.75 post and ins. 25p. Additional time contacts 55p each.



MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags. Data supplied. Model 1153 600mW power output 72p. Model 1172 760mW power output 94p. Model EP9000 4 watt power output £1.60. EP9001 twin channel or stereo pre amp. £1.99 10% discount if 10 or more ordered.



TERMS: 10% discount if ten or an item ordered. send postage where quoted other items. post free if order for these items is £6.00 otherwise add 20p.

NEW ITEMS THIS MONTH

MINIATURE SEALED RELAY

American made. Our Ref.: REL A1. Measures only 1" wide x 1" thick and 1" high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 8-12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 28p including base.

SUB-MINIATURE MICROSWITCH

Made by Burgess, their ref. V476—our ref. MS. A1. These measure only 2" x 2" x 2" thick—have change over contacts and tag connection. Price 16p each or 10 for £1.44.

3 CORE MAINS FLEX

Metric size .5mm which is approx. equivalent to the old 1/16" rating. Suitable therefore for mowser or similar portable tools. Cores are colour coded to the new European standard. Brown—live. Blue—neutral. Yellow/Green—earth. Grey P.V.C. covering overall. 100m coils \$5. 50m coils \$3 and 25m coils \$1.75. Post 40p on 100m, 25p for 50m coils and 20p for 25m coils.

PANIC SWITCHES

Tough enough to be foot switches and elegant enough to be panel switches. Bakelite construction with white push rod. Price 40p less quantity discounts. Switch is rated 250v-2 amp.

20 WATT CAMPING LIGHT

Also makes good car emergency light. This uses a standard 2 ft. 20 watt tube and operates from a 12v car battery drawing approx. 1A. This gives illumination per amp/hour of battery life far in excess to filament lamps and in fact to the miniature 8-18 watt camping lights often offered. Complete unit ready to operate, in strong white enamelled metal frame. These would normally sell at £6 are unused but slightly soiled and we offer these at £3.50 plus 40p post and packing.

6 MAINS TRANSFORMERS

Our Ref.: MTM1 27 volt at 8 amp. Upright mounting fully shrouded—flying leads—fully tapped primary. Price \$3.80. Our Ref.: MTM2 12v at 1 amp. Upright mounting with fixing lugs, tag connection. 240v primary—12v 1 amp secondary. Price \$2p. Our Ref.: MTM3 6.3v 5 amp upright mounting with fixing lugs, tag connection. 240v primary 6.3v 2 amp secondary. Price 77p. Our Ref.: MTM4 18v 1/2 amp with thermal cut-out, upright mounting with fixing lugs & tag connections. Primary 240v—secondary 18v at 1/2 amp. Price 88p. Mains Isolation MTM5 350 watts earth shielded—flex leads—upright mounting lugs for fixing. Price \$4.40 each.

6 VOLT RELAYS

Our ref.: REL M1. Removable clear plastic enclosed two screw fixing. Have a 6 volt D.C. operated coil but two change-over contacts, each rated to make and break 240v A.C. at 15 amps. Price 66p each.

P.O. TYPE 3000 RELAY

Our ref.: REL M2—100 ohms coil and 2 pair normally open heavy duty contacts. Price 75p each.

6 DIGIT COUNTER

Resettable, 440 ohm coil up to 25 impulses per second. Ex-equipment but guaranteed perfect. \$2.20 each.



COMBINATION SWITCH

This comprises of 12 miniature change-over micro switches. Joined in banks of 3 and mounted on frame with four digital numbered thumb wheels and a removable lever for locking the thumb wheel — the thumb wheel operates 3 banks. Over 4,000 combinations are possible but by re-wiring the switch connections underneath then thousands more variations are possible. If you are making equipment which you don't want switched on accidentally or without authority then this is a switch to consider—this can also be used as a coding switch for many other operations. Very neat and compact and measuring approx. 4" x 1 1/2" x 1 1/2" deep. Priced at \$3.03.



PUSH BUTTON SWITCH

Type 14 D.M.G. A very fine switch made by Honeywell. The switch is intended for mounting on panel through opening hole. No screws required for fixing its spring clips secure it quite firmly. The operating button is approx. 1 1/2" dia. round and dished for ease of operation. Has 2 sets of 10 amp change-over contacts. Spring loaded, returns to normal when pressure is released. Ideal for instrument or quality gear. Price 50p each. 10 for \$4.50, 100 for \$40.

PHOTO-MULTIPLIER TUBE

American R.C.A. type No. 4553. These tubes have a gain of a million or more. Regular Price—over £15. We have a limited quantity and offer these at \$4.50.

J. BULL (ELECTRICAL) LTD.

(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

MAGNETIC AMPLIFIERS

PART 2

I. R. SINCLAIR

SELF-SATURATING MAGNETIC AMPLIFIERS

(continued)

If the control current is zero, the core is taken through a small magnetisation cycle and has an inductance determined by the average flux contributed by the secondary current. If the control current is in the *opposite* direction, the flux due to control current opposes it and the core can be made to change from negative to positive saturation when signal current flows. In this state, flux change is maximum and inductance is large so that the voltage drop across the secondary winding is large.

In a core operated in this way, the amplification obtained depends mainly on the shape of the magnetisation B—H curve, and a steep sloped curve with a very low value of saturation magnetic field strength is desirable. To obtain this shape of curve, cores are usually made by winding tapes of suitable material (permalloy etc.) round a former to form a toroid and winding the coils round these cores.

When such materials are used in such a core, the B—H curve is of the type shown in Fig. 6, where the scales of the graph are such that the values of B are large and those of H small. Saturation occurs at

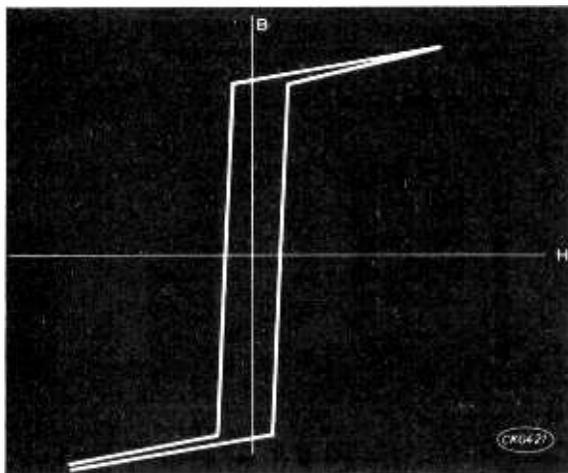


Fig. 6: B-H curve for material used for cores of magnetic amplifiers.

such a low value of flux (measured in milliamps of current X turns of coil) that the cores will saturate with the output current even with no control current applied, and so the control current must be applied so that its flux *always opposes* the output flux.

The circuit of a full-wave self-saturating magnetic amplifier is shown in Fig. 7. Since the secondary current in each core must be in one direction, a

rectifier is used in series with each secondary winding and two windings are used so that control can be exerted over the whole of one cycle. Note that the voltage across the load is alternating, despite the rectifiers. The output waveform of such an amplifier is also shown in Fig. 7; except for the value of voltage at minimum signal, the waveform is similar to that obtained from a thyristor circuit.

The transfer characteristic (voltage out plotted against *current* in control winding) is shown in Fig. 7. The precise form of this curve can be calculated if the B—H curve for the core in use is known, and it is one of the considerable achievements of core manufacturers that cores and core materials can now be made with reproducible values of B—H curve. The greatest sensitivity can be obtained if the control current is biased to the point O on this control curve, and for this purpose, if the bias signal cannot be obtained from the source, a separate bias winding may be used.

The self-saturating magnetic amplifier will give an a.c. voltage output across a load almost independent

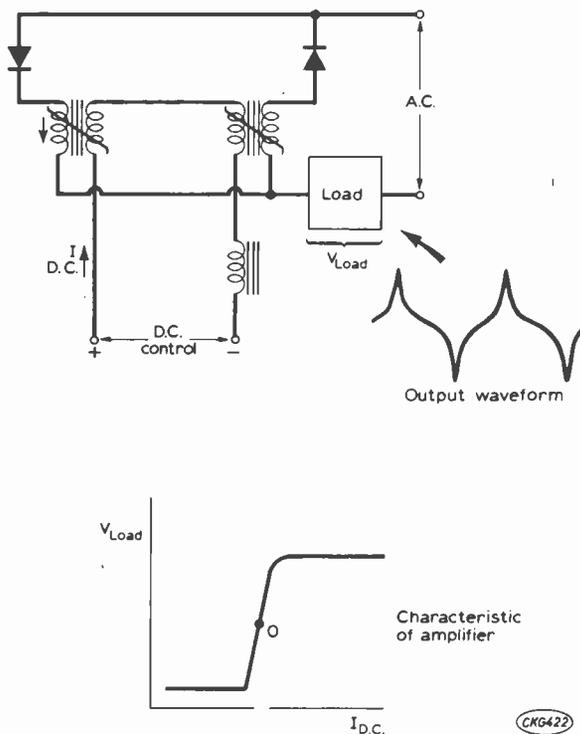


Fig. 7: Circuit of full-wave self-saturating magnetic amplifier with output waveform and amplifier characteristic curve.

of load impedance and determined only by the d.c. control current, so that a d.c. signal at the control winding produces an amplified a.c. output. The output power obtained depends on the size and type of core used.

DC OUTPUT FEEDBACK

The magnetic amplifiers described so far give an a.c. output for a d.c. input. Where the load of the amplifier must be supplied with d.c., or where one magnetic amplifier feeds a second (as when very large power amplification is required) the output of the magnetic amplifier must be rectified. This may be done by taking the output terminals to a bridge rectifier and connecting the load across the other two terminals of the rectifiers (Fig. 8a). A more economical method is to make use of the rectifiers which feed the cores, and add two more to form a bridge rectifier circuit (Fig. 8b) or to use a centre tapped transformer as power source and use the core rectifiers to provide the d.c. output (Fig. 8c).

When linearity of control is particularly important, this may be improved by feedback. To apply feedback to a magnetic amplifier a direct current must be obtained from the output and applied to a feedback winding in the direction opposite to the current in the control winding. The feedback ratio which by the usual feedback theory is approximately the new gain of the amplifier, is the ratio of control winding ampere-turns to the feedback ampere-turns.

DESIGN AND CONSTRUCTION OF PRACTICAL AMPLIFIERS

Because magnetic materials vary so much, it is not easy to give a "circuit" for a magnetic amplifier for home construction; it is rather like giving a circuit for a radio in which all the transistors had to be made at home as well! We can, however, outline the steps in design, so that the experimenter can construct reactors, determine their characteristics and make use of them in the circuits shown earlier. Since commercially obtainable reactors are £10 and upwards, there is a strong incentive for home construction!

CORES

The type of core material which can be used depends on the power available to drive the control winding. When large powers (about 1kW) are being controlled, and several watts can be used to drive the amplifier, an old transformer core can be rebuilt, provided that the transformer was rated to take such power loads. This requires some trial and error unless the core material is known and information on it is available. If this is not the case, the best cut-and-try method is to keep the original windings on the bobbin and reassemble the core with no gap, by replacing the **E** and **I** sections facing alternatively in opposite directions. The inductance of the main winding should then be checked for saturation point; this is easily done if an oscilloscope is available by feeding the winding from an a.c. supply through a large variable resistor and checking the voltage across the winding with an oscilloscope. As the current is increased, the voltage waveform becomes flat-topped when saturation point is reached, and the current flowing at this point is saturation current (the saturation current

here is peak current = $1.4 \times$ rms meter reading). Alternatively an a.c. voltmeter and ammeter can be used and voltage plotted against current on a graph, saturation being when the graph becomes flat-topped. Note that the a.c. current must be varied by a resistor, if a constant voltage source such as an auto-transformer is used, the current waveform will be the one which appears distorted.

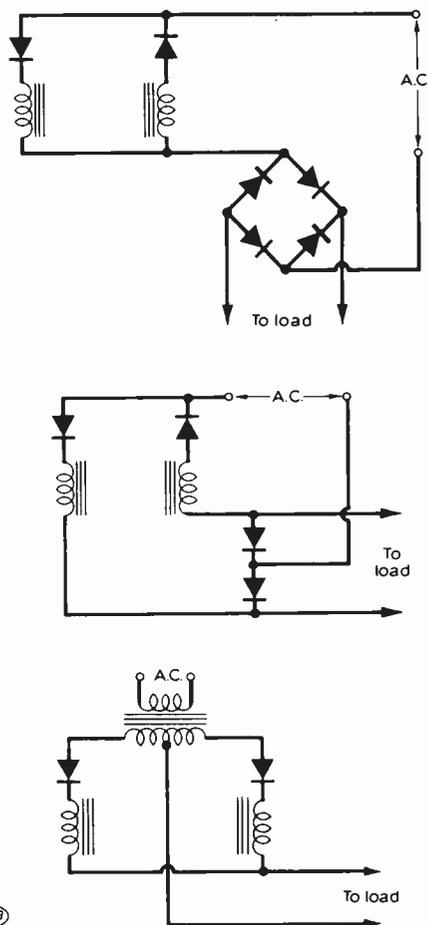


Fig. 8a, top, shows rectifiers needed to rectify AC output of amplifier when the load requires a DC supply. Fig. 8b, centre, and Fig. 8c, bottom, illustrate alternative methods of achieving DC output.

Once saturation current in the main winding is known, the saturation current in the other windings can be calculated, for it is inversely proportional to the voltage of the winding when used as a transformer. For example, if the saturation current in a 250V winding is 100mA the saturation in a 350-0-350

winding, total 700V is $100 \times \frac{250}{700} \text{ mA} = 36 \text{ mA}$

and this 700V winding can be used as the control winding. If the control winding has resistance of 100Ω, the voltage across it at saturation is 36V and this will be able to control currents of $\pm 100 \text{ mA}$ at 250V in the other winding. The voltage gain in this case is not impressive, but the power gain is fairly high and is achieved at less cost than many comparable devices.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE
ONLY £1-05

POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	55p
B81	10	Reed Switches, 1" long. Figure 1" dia. High Speed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	55p P+P 15p
H4	250	Mixed Resistors. Approx. quantity counted by weight	55p P+P 15p
H7	40	Wirewound Resistors. Mixed types and values.	55p
H9	2	OC771 Light Sensitive Photo Transistor	55p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	55p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8-43V.	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	55p
H38	30	Short lead Transistors, NPN Silicon Planar types.	55p
H39	10	Integrated Circuits, 6 Gates BMC 962, 4 Flip Flops BMC 945	55p
H40	20	BFY50/2, 2N696, 2N1613 NPN Silicon uncoded TO-5	55p
H41	2	Sil Power transistors comp pair. BD131/132	55p

UNMARKED UNTESTED PAKS

B44	150	Germanium Diodes Pin glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. 1N914 and 1N916 types	55p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1/ 2N706A, BSY95A, etc.	55p
B1	50	Germanium Transistors PNP, AF and RF	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H15	30	Top Hat Silicon Rectifiers, 750mA, Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied.	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volta.	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

MAKE A REV COUNTER FOR YOUR CAR

The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10 each



OVER

1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.
Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.
Please state Audio NPN or Audio PNP when ordering.
ALL AT 500 for £3-30, 1,000 for £5-50, 10,000 for £44 P. & P. 11p/1,000.

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon similar ZTX 300 range
TYPE "H" PNP Silicon similar ZTX 500 range

8 RELAYS FOR VARIOUS TYPES £1-10
P & P 2½

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors. Please ask for Pak P.I. Only 55p. 11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

This complete kit of parts costs £3.85, post paid.

A MUST for Colour T.V. Alignment.

STEREO DECODER £4-95

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner Unit. A tall-tale light can be connected to show the presence of a Stereo transmission and correct operation of the Unit.

The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us @ 16½p. Supplied with necessary instructions and written guarantee.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

100,000

Plastic Power Transistors in stock, more on way
NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design available in NPN or PNP at the most astonishingly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms. Range 1. VCE. Min 15. HFE Min 15.

40 Watt: 1-12 13-25 26-50
90 Watt: 26p 22p 18p
26p 24p 22p

Range 2. VCE. Min 40. HFE Min 40.
40 Watt: 1-12 13-25 26-50
90 Watt: 33p 31p 29p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available
This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16p each. Now new low profile 16 pin type at 18p each type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes; 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.

The Iliffe Radio Valve & Transistor Data Book 9th Edition; p. & o. 23½p 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications
N.B. Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% VAT
MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 11p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD
CO. REG. No. 820919

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF
TELEPHONE: SOUTHEND (0702) 46344

FROM SCRATCH

Much more efficient magnetic amplifiers can be obtained by designing from scratch. If the control power is more than about 200mW, transformer steel cores (such as Hypersil) can be used either in tape or C-core (with no gap) form, for lower powers a μ -metal or permalloy core is available. For any core, the power which can be controlled is approximately

equal to $\frac{D^2ABf}{200}$ where D is the diameter of the whole core (in cm), A the area of cross section of core

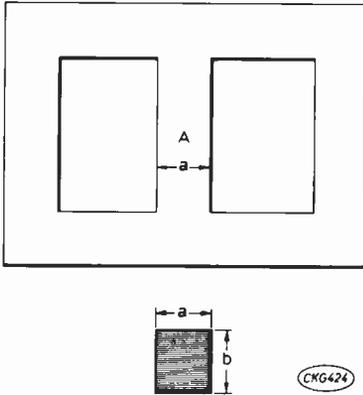


Fig. 9: The cross sectional area of the core can be obtained by multiplying 'a' and 'b' measured in cms.

(in sq.cm) in the bobbin, B is the saturation flux density of the core in Teslas (Weber per sq.m) and f is the frequency in Hertz (cycles per second).

The wire size may then be selected if the output current is known. Using a table of wire size which shows area in "circular mils" choose a wire size of about 1 circular mil for each milliamp of output current. The number of turns for the voltage required

at the output is then $\frac{25V}{A}$ where the area of

cross-section of the core (Fig. 9) in sq.cm and V is the voltage of the winding in volts.

After this, the design depends on the core material used, whose characteristic must be known. The ampere-turns for control should be obtained from the maker's information, and the control winding designed to suit amplification required and to fill the available bobbin shape.


In the case of a commercial design, considerably more would be done to calculate leakage flux, winding thickness, etc. but a cut-and-try approach is better for the amateur who is more interested in making a working device than in establishing a production line.

FINAL NOTES

Voltage gains are of the order of 8-40 with straight saturating circuits and up to 1200 with self-saturation. Feedback lines should include a choke to prevent a.c. feedback.

The frequency of the input signal should not be more than one-tenth of the frequency of the operating a.c.; for 50Hz operation, the input signal bandwidth is d.c. to 5Hz. ■

BUY YOURS NOW!

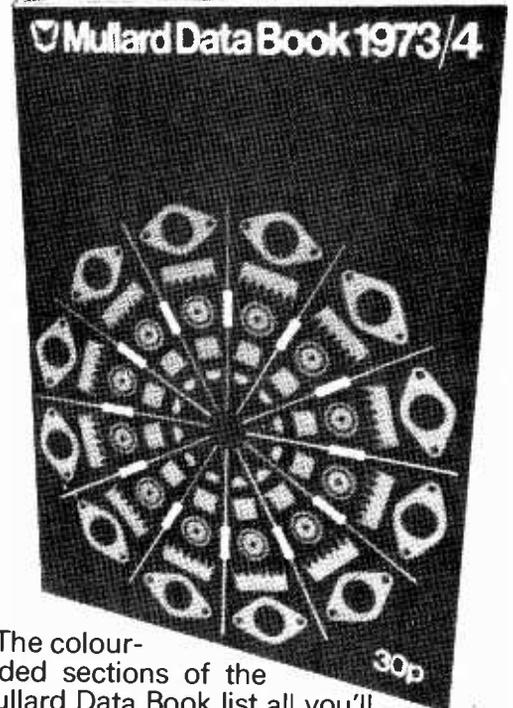

The colour-coded sections of the Mullard Data Book list all you'll want to know about valves, integrated circuits, semiconductors, picture tubes and other components. It also contains equivalents and comparables lists.

The Mullard Data Book 1973/74 is now available from your bookseller, or direct, cash with order, from the Selray Book Co Ltd, 60 Hayes Hill, Hayes, Bromley, Kent BR2 7HP.



RETAIL PRICE—30p (plus 5p postage)

PRODUCTION LINES

colin riches

STEREO 21

I didn't think it was possible, but, for the amazingly low price of £17.95, Radio and TV Components are marketing a stereo record playing outfit.

In kit form, it comprises a BSR C129R 3-speed record deck with cartridge, a pre-assembled amplifier module, giving 2.7W per channel, two 8in. x 5in. speakers, easy-to-assemble woodwork for the plinth, cover and speaker cabinets and all the wire, nuts and bolts, etc.

The "Stereo 21" is particularly suitable for beginners to home construction because no soldering is required. All electrical connections are made through push-on tags. The plinth and speaker enclosures employ pre-mitred, wood grain covered chip-board sections, the mitres being cut in such a manner that a hinge is formed. Glue is applied to the mitred sections which are then simply folded over to form a cabinet.

Another new item from the R & TV stable is an 8-track cartridge player retailing at £9.90. Housed in a smart wooden cabinet, the unit claims a frequency range better than 50-10kHz. Four track-indicator lights show which track is being played and the unit switches automatically from one channel to the next. This unit can easily be played through the Stereo 21 system, making it a comprehensive good-value-for-money stereo set-up.

Further information by sending s.a.e. to *Radio & TV Components (Acton) Ltd., 21 High Street, London, W3 6NG.*

ADVANCE TIMER/COUNTER



Mentioned last month, the TC17 measures frequencies from d.c. to 50MHz with resolution of 0.1Hz.

GL78/P/C


This is the latest addition to the range of Goldring/Lenco Turntable Units. The Model GL78/P/C incorporates an automatic shut-off switch which stops the motor at the end of the record and simultaneously raises the pick-up. A manual override control is built in, in case the shut-off facility is not required. *Goldring Ltd., 10 Bayford St., Hackney, London, E8 3SE.*



NEW 'TERRY' CLIPS

The picture shows the range of 'clipco' securing clips. 'Clipco' is versatile, easily fixed and no screwing is required. It is made of unbreakable, resilient rust-free nylon, which prevents damage to articles. 'Clipco' solves many fixing problems around the home and is a specially designed dual purpose plug which ensures efficient fixing to walls, tiles, wood and pegboard etc.

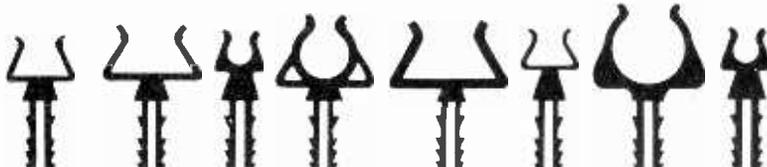The clips are available in three choices of visual blisters, containing 8, 9 or 10 clips dependent on size and shape. The recommended retail price of blisters is 21p to 23p. They are also available in bulk—100 at £2.18p. *Herbert Terry and Sons Ltd., Redditch, England.*



S.W. CRYSTAL SET

Partridge now market a short wave crystal set (see picture). Further information from: *Partridge Electronics, Broadstairs, Kent.*



VACUUM RECORD CLEANER

The manufacturers, R.I. Audio, claim that their new "Groovac" record cleaner is the only unit available which removes dust from records by vacuum cleaning.

A tracking force of only 0.7 gram has been achieved by using a lightweight design with lubricated-for-life bearings throughout. This is considerably below the 3 to 6 grams force of simple brush cleaners. Low tracking force allows fine hairs to be incorporated in the Groovac cleaning nozzle which ensure efficient removal of dust from the bottom of record grooves—most brush cleaners have hairs with a diameter which is larger than the width of the record grooves. Low tracking force also means an almost immeasurable reduction in turntable speed, a reduction which is at least 3 times less than that caused by brush cleaners.

The Groovac consists of a precision lightweight arm, and a suction



unit which is acoustically isolated in a special enclosure. The suction unit has been designed to be inaudible at a distance of 2 metres; it has a mains switch and indicator, and is attractively finished in teak. Price is £6.90p plus V.A.T. and it is available from hi-fi retailers or direct from *RI Audio, Kernick Road, Penryn Cornwall.*

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p	BCY38	30p	CA3035	£1.52	NKT405	62p	1N4004	10p	2N4491	46p
AC107	50p	BCY58	18p	CA3043	£1.73	NKT713	29p	1N4005	12p	2N5245	45p
AC126	20p	BCY70	15p	CA3044	£1.42	NKT773	25p	1N4006	15p	2N5457(MPF103)	1.0
AC127	25p	BCY71	30p	CA3046	86p	NKT781	29p	1N4007	19p	4D	1.0
AC128	24p	BCY72	15p	CA3048	£2.34	NTGD10	40p	1N4148	4p	42N5458(MPF10)	2.2
AC128/AC176		BD124	75p	CA3052	£1.80	OA47	8p	1N5400	14p	49	2.2
		BD131	75p	CA3065	£1.42	OA79	8p	1N5404	18p	2N5459(MPF105)	4.7
AC151	44p	BD132	75p	CA3088E	£1.38	OA81	8p	1N5408	25p	46	10
AC152	25p	BD131/132	£1.50	CA3089E	£1.19	OA80	8p	1S44	4p	2N5777	45p
AC153	26p	RDY20	92p	CD43090Q	£4.70	OA91	5p	1S920	7p	2N6027(D13T1)	22
AC176	20p	BF115	23p	CD4001AE	54p	OA95	5p	1S940	6p	45	22
AC153/176K	52p	BF163	35p	CD4009AE	£1.16	OA200	6p	1S5009	80p	3N84	£1.30
AC187K	17p	BF167	25p	CD4011AE	54p	OA202	7p	1S5012	7p	3N128	73p
AC188K	23p	BF173	29p	CD4012AE	54p	OC20	97p	1S5015	75p	3N140	92p
AC187/188K	40p	BF177	25p	CD4013AE	£1.11	OC25	37p	1S5018	75p	3N152	92p
AC177	40p	BF176	31p	CD4015AE	£2.92	OC28	70p	1S5024	75p	3015F	£2.00
AC178	20p	BF180	35p	CD4017AE	£2.92	OC29	76p	1S5047	23p	7400	£2.00
AC1918	20p	BF194	15p	CD4018AE	£2.92	OC35	60p	2N404	23p	7400	£2.00
AC1920	20p	BF195	15p	CD4020AE	£3.25	OC36	63p	2N696	15p	7401	20p
AC1921	19p	BF196	15p	CD4024AE	£2.09	OC41	40p	2N697	17p	7402	20p
AC1922	10p	BF200	35p	CR1/051C	50p	OC42	40p	2N698	30p	7403	20p
AD140	55p	BF254	74p	CR1/401C	65p	OC44	20p	2N706	10p	7404	20p
AD149	50p	BF255	75p	CRS3/05AF	£1.08	OC45	20p	2N708A	12p	7405	25p
AD161	37p	BFX13	25p	CRS3/40AF	£1.08	OC72	20p	2N911	16p	7408	25p
AD162	37p	BFX29	25p	CRS3/40AF	£1.08	OC72	20p	2N911	50p	7409	25p
AD161/162	74p	BFX84	25p	£1.53	OC75	25p	2N914	20p	7410	20p	
AF106	32p	BFX85	34p	£1.53	OC76	25p	2N918	42p	7413	30p	
AF114	25p	BFX86	30p	D10 (NTGD10)	OC77	20p	2N920	25p	7420	20p	
AF115	25p	BFX88	20p	£1.08	OC81	20p	2N929	28p	7425	20p	
AF116	25p	BFX89	24p	£1.08	OC81D	20p	2N1131	24p	7430	20p	
AF117	25p	BFY50	15p	IR2160	95p	OC84	23p	2N1132	24p	7440	20p
AF118	44p	BFY51	15p	IR220	48p	OC84	25p	2N1303	17p	7442	20p
AF124	25p	BFY52	17p	JAA24	£2.08	OC139	25p	2N1304	25p	7444	20p
AF125	24p	BFY53	15p	LIC709C/5	42p	OC170	20p	2N1303	24p	7445	20p
AF126	17p	BFY90	£1.05	LIC709C/8	42p	OC171	30p	2N1305	24p	7445	20p
AF139	47p	BFX01	£1.35	LIC723C/5	£1.02	OC171M	42p	2N1306	30p	7446	£1.45
AF186	40p	BFX66	40p	LIC741C/5	45p	ORP12	50p	2N1307	30p	7447	£1.25
AF239	50p	BRV39	40p	LIC741C/8	40p	ORP60	40p	2N1308	34p	7450	20p
AF279	55p	BSX19	16p	LIC741C/8	40p	ORP61	40p	2N1309	34p	7451	20p
AS226	25p	BSX20	16p	MC1303L	£1.75	ORP69	50p	2N1559	50p	401C	20p
AS227	30p	BSX21	20p	MC1307P	£1.65	PN71	9p	2N1613	15p	7450	20p
AS228	22p	BSY27	20p	MC1310P	£2.95	PN107	7p	2N1711	15p	7470	20p
AS229	35p	BSY29	25p	MC1310P	£2.95	PN107	7p	2N1711	15p	7470	20p
BA138	13p	BY95A	22p	MC1330P	£1.00	PN108	7p	2N1893	54p	7472	32p
BA138	8p	BY100	22p	MC1330P	£1.00	PN109	7p	2N2218	33p	7473	32p
BA138	16p	BY127	22p	MC1466L	£4.20	PN3819(2N3819)	22p	2N218A	44p	7474	46p
BB104	28p	BTY79/400R	92p	MC1468L	£2.88	2N2219	38p	7475	45p	7476	45p
BB105	32p	BT106	£1.20	MFC4000B	£2.20	ST2	28p	2N2368	17p	7480	67p
BC107	13p	BZ88C3V3	13p	MC4042P	£2.20	SL103A	50p	2N2369	17p	7480	67p
BC107/BC177	33p	BZ88C3V6	13p	MC4044P	£2.20	SL403A (Rect)	60p	2N2484	42p	7486	£1.32
BC108	12p	BZ88C4V3	13p	MFC6030	£1.63	SL403A (Rect)	60p	2N2484	42p	7486	£1.32
BC108/BC178	13p	BZ88C4V7	13p	MFC6035	£1.15	SL803A	80p	2N2646	44p	7491A	£1.28
BC109	28p	BZ88C5V1	13p	MFC8040	£1.24	SLC(Amp.)	£1.50	2N2904	49p	7492	45p
BC109/BC179	13p	BZ88C5V6	13p	MFC9020	£2.12	TA293	75p	2N2905	65p	7493	75p
		BZ88C6V2	13p	MJE371	68p	TA293	75p	2N2905	65p	7493	75p
BC109C	33p	BZ88C7V5	13p	MJE520	55p	TA293	75p	2N2905A	75p	7494	75p
BC117	15p	BZ88C8V2	13p	MJE521	62p	TA310	£1.25	2N2924	18p	7495	80p
BC140	30p	BZ88C9V1	13p	MJE3035	£1.06	TA320	75p	2N2925	20p	7496	£1.48
BC147	10p	BZ88C10V	13p	MJA80	97p	TA861	45p	2N2926	10p	74100	£1.64
BC148	9p	BZ88C11V	13p	MJ481	£1.25	TAD100	£1.97	2N3053	24p	74107	52p
BC149	10p	BZ88C12V	13p	MJ491	£1.25	TAD112	£2.00	2N3055	24p	74107	52p
BC157	12p	BZ88C13V	13p	MJ802	£4.12	TIL209	35p	2N3228	£1.10	74150	£1.00
BC158	11p	BZ88C15V	13p	MJ802/MJ4502	£1.50	TIP31A	60p	2N3321	29p	74151	£1.10
BC159	12p	BZ88C16V	13p	MJ900	£1.56	TIP32A	70p	2N3525	29p	74151	£1.10
BC147/157	22p	BZ88C18V	13p	MJ1000	£1.50	TIP41A	85p	2N3702	10p	74154	£2.00
BC148/158	22p	BZ88C20V	13p	MJ1050	£1.50	TIP42A	£1.00	2N3703	10p	74155	£1.55
BC149/159	22p	BZ88C22V	13p	MJ4502	£4.44	TIS43	30p	2N3704	10p	74156	£1.55
BC167	11p	BZ88C24V	13p	MPF102	37p	VA1066S	15p	2N3705	10p	74190	£1.80
BC168	10p	BZ88C27V	13p	MPF103(2N5457)	49p	VA1039	15p	2N3706	10p	74191	£1.80
BC169	11p	BZ88C30V	13p	VA1039	15p	2N3706	10p	74191	10p	74192	£1.74
BC169C	12p	BZ88C31V	13p	MPF104(2N5458)	VA1077	15p	2N3708	8p	74193	£1.74	
BC177	20p	BZ88C32V	23p	W005	30p	2N3709	10p	74196	10p	74197	£1.50
BC178	16p	BZ88C33V	23p	MPF105(2N5459)	46p	W02	31p	2N3710	10p	40250	66p
BC179	20p	BZ88C34V	23p	NKT0033	96p	W04	33p	2N3773	£2.50	40309	40p
BC182L	10p	BZ88C12V	23p	NKT211	25p	W06	35p	2N3819	28p	40310	60p
BC183	9p	BZ88C13V	23p	NKT212	25p	W08	44p	2N3820	60p	40311	42p
BC183L	10p	BZ88C14V	23p	NKT215	25p	ZTX107	12p	2N3822E	20p	40312	62p
BC184	13p	BZ88C16V	23p	NKT216	46p	ZTX108	11p	2N3826	30p	40320	52p
BC184L	12p	BZ88C18V	23p	NKT217	46p	ZTX109	13p	2N3866	£1.10	40360	56p
BC212	12p	BZ88C20V	23p	NKT218	25p	ZTX202	15p	2N3901	18p	40361	42p
BC212L	12p	BZ88C22V	23p	NKT219	25p	ZTX300	15p	2N3906	28p	40362	45p
BC238	10p	BZ88C24V	23p	NKT223	27p	ZTX303	23p	2N4008	30p	40406	52p
BC238/308	20p	BZ88C27V	23p	NKT271	18p	ZTX304	23p	2N4058	11p	40407	40p
BC257	9p	BZ88C30V	23p	NKT274	20p	ZTX314	11p	2N4060	11p	40408	54p
BC258	8p	CA3004	£2.25	NKT275	20p	ZTX320	30p	2N4061	11p	40409	62p
BC259	9p	CA3005	£1.50	NKT279A	12p	ZTX330	18p	2N4062	11p	40410	62p
BC307	12p	CA3011	22p	NKT281	15p	ZTX500	14p	2N441	70p	40410	62p
BC308	10p	CA3013	£1.30	NKT351	75p	ZX501	15p	1N4001	7p	40430	£1.13
BCY30	25p	CA3014	£1.52	NKT401	71p	ZX502	18p	1N4002	7p	40432	£1.13
BCY31	48p	CA3018	88p	NKT402	70p	ZX503	17p	1N4003	10p	40468A	£1.60
BCY32	50p	CA3018A	£1.19	NKT403	65p	ZX504	45p	2N4444	£2.20	40511	£1.92
BCY33	20p	CA3020	£1.55	NKT404	60p	1N914	4p	2N4871	40p	40512	£1.88
BCY34	25p	CA3028A	88p	NKT405	79p	1N3754	20p	2N4990	66p	40575	£1.54

ELECTROLYTIC AXIAL LEADS

Mfd.	Working Voltage	Price	Mfd.	Working Voltage	Price
1.0	40v	7p	100	16v	6p
1.0	100v	5p	100	25v	6p
2.2	25v	7p	100	40v	7p
2.2	63v	5p	100	63v	10p
4.7	40v	5p	220	25v	8p
10	25v	5p	220	40v	9p
15	25v	6p	470	10v	12p
22	25v	6p	1000	25v	16p
45	22	6p	2200	25v	16p
47	25v	6p	4700	16v	33p
73	47	6p			

CAPACITORS—METALLISED POLYESTER

Stock values: MFD 0.01, 0.015, 0.022, 0.033
0.047, 0.068, 0.10

Price each
3p
4p
5p
6p
7p
8p
9p
10p
12p
16p
25p
30p
40p
50p
60p
70p
80p
90p
100p
120p
150p
200p
250p
300p
400p
500p
600p
700p
800p
900p
1000p

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230V. 50/60 c/s. Variable output 0-260V.



MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

1 Amp	\$7-00
2.5 Amp	\$8-05
5 Amp	\$11-75
8 Amp	\$15-90
10 Amp	\$22-50
12 Amp	\$23-90
20 Amp	\$40-00
25 Amp	\$58-00
40 Amp	\$82-60



MODEL S-260B

Panel Mounting.	
1 Amp	\$7-00
2.5 Amp	\$8-05

Carriage and Packing Extra

AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.

80 W	\$2-10	P. & P. 18p
150 W	\$2-70	P. & P. 18p
300 W	\$3-60	P. & P. 23p
500 W	\$5-25	P. & P. 33p
1000 W	\$7-50	P. & P. 38p
1500 W	\$10-20	P. & P. 43p
2250 W	\$17-25	P. & P. 50p
5000 W	\$35-00	P. & P. \$1

MCA. 920 AUTOMATIC VOLTAGE STABILIZER

Input 88 125 VAC or 178, 250VAC. Output 120VAC or 240VAC. 200VA rating. \$11-97. Carr. 50p.



PS.200 REGULATED P.S.U.

Solid state. Variable output 20 volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240 V. A.C. Size 7 1/4" x 5 1/4" x 3 1/4". \$19-95. P. & P. 25p.



PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V A.C. Size 4" x 3 1/4" x 6 1/4". \$11-97. P. & P. 25p.



230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RPH CW; 50n each Post 12p.



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 1/2 in. dia. shafts. Bulk quantities available.



25 WATT. 10/25/50/100/250/500/1000 ohms. 85p. P. & P. 10p.

50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. \$1-85. P. & P. 10p.

100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. \$1-95. P. & P. 15p.



240° Wide Angle 1mA Meters

MW 1-6 60mm square \$3-97
MW 1-8 80mm square \$4-97

P. & P. extra

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots 240) Quantities available.



CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

Type SW.100 100 x 80 mm.

50μA	\$4-15
50-0-50μA	\$3-95
100μA	\$3-95
100-0-100μA	\$3-90
500μA	\$3-70
1mA	\$3-60
20V. D.C.	\$3-60
50V. D.C.	\$3-60
300V. D.C.	\$3-60
1 amp. D.C.	\$3-60



Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts

50mA	\$3-90
100mA	\$3-90
500mA	\$3-90
1 amp.	\$3-90
5 amp.	\$3-90
15 amp.	\$3-90
30 amp.	\$3-95
20V. D.C.	\$3-90
50V. D.C.	\$3-90
150V. D.C.	\$3-90
300V. D.C.	\$3-95
15V. A.C.	\$3-95
300V. A.C.	\$3-95
8 Meter 1mA	\$3-90
VU Meter	\$4-55
1 amp. A.C.*	\$3-90
10 amp. A.C.*	\$3-90
20 amp. A.C.*	\$3-90
30 amp. A.C.*	\$3-90



Type MR.38P. 1 1/2 | 3/2 in. square fronts

200mA	\$2-25
300mA	\$2-25
500mA	\$2-25
750mA	\$2-25
1 amp.	\$2-25
2 amp.	\$2-25
5 amp.	\$2-25
10 amp.	\$2-25
3V. D.C.	\$2-25
10V. D.C.	\$2-25
15V. D.C.	\$2-25
20V. D.C.	\$2-25
50V. D.C.	\$2-25
100V. D.C.	\$2-25
150V. D.C.	\$2-25
300V. D.C.	\$2-25
500V. D.C.	\$2-25
750V. D.C.	\$2-25
15V. A.C.	\$2-25
50V. A.C.	\$2-25
150V. A.C.	\$2-25
300V. A.C.	\$2-25
8 Meter 1mA	\$2-25
VU Meter	\$2-65




Type SD.830 82.5mm x 110mm Fronts

10mA	\$3-10
50mA	\$3-10
100mA	\$3-10
500mA	\$3-10
1 amp.	\$3-10
5 amp.	\$3-10
10 amp.	\$3-10
5V. D.C.	\$3-10
10V. D.C.	\$3-10
20V. D.C.	\$3-10
50V. D.C.	\$3-10
300V. D.C.	\$3-10
15V. A.C.	\$3-10
300V. A.C.	\$3-10
VU Meter	\$3-50




Type MR.52P. 2 1/2 in. square fronts

50μA	\$3-50
50-0-50μA	\$3-05
100μA	\$3-00
100-0-100μA	\$2-95
500μA	\$2-65
1mA	\$2-50
5mA	\$2-50
10mA	\$2-50
50mA	\$2-50
100mA	\$2-50
500mA	\$2-50
1 amp.	\$2-50
5 amp.	\$2-50

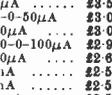


Type MR.45P. 2 in. square fronts

50μA	\$2-70
50-0-50μA	\$2-65
100μA	\$2-60
100-0-100μA	\$2-50
200μA	\$2-50
500μA	\$2-45
500-0-500μA	\$2-40
1mA	\$2-40
5mA	\$2-40
10mA	\$2-40
50mA	\$2-40
100mA	\$2-40
500mA	\$2-40
1 amp.	\$2-40
5 amp.	\$2-40
10V. D.C.	\$2-40
20V. D.C.	\$2-40
50V. D.C.	\$2-40
15V. A.C.	\$2-40
300V. A.C.	\$2-40
8 Meter 1mA	\$2-40
VU Meter	\$2-70

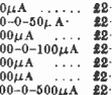


Type SD.640 63.5mm x 85mm Fronts

50μA	\$3-05
50-0-50μA	\$3-05
100μA	\$3-00
100-0-100μA	\$3-00
200μA	\$3-00
500μA	\$2-95
1mA	\$2-95
5mA	\$2-90
10mA	\$2-90
50mA	\$2-90
100mA	\$2-90

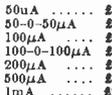

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts

50μA	\$3-70
50-0-50μA	\$3-15
100μA	\$3-10
100-0-100μA	\$3-10
200μA	\$3-05
500μA	\$2-75
500-0-500μA	\$2-60
1mA	\$2-60
5mA	\$2-60
10mA	\$2-60
50mA	\$2-60
100mA	\$2-60
500mA	\$2-60
1 amp.	\$2-60
5 amp.	\$2-60
10 amp.	\$2-60
20 amp.	\$2-60
30 amp.	\$2-60
50 amp.	\$2-60
5V. D.C.	\$2-60

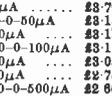

"SEW" BAKELITE PANEL METERS


Type MR.65. 3 1/2 in. square fronts

1 amp.	\$2-60
5 amp.	\$2-60
15 amp.	\$2-60
30 amp.	\$2-60
50 amp.	\$2-60
5V. D.C.	\$2-60
10V. D.C.	\$2-60
20V. D.C.	\$2-60
50V. D.C.	\$2-60
150V. D.C.	\$2-60
300V. D.C.	\$2-60
50μA	\$4-60
50μA	\$3-55
50-0-50μA	\$3-05
100μA	\$3-00
100-0-100μA	\$3-00
500μA	\$2-70
500-0-500μA	\$2-70
1mA	\$2-60
1-0-1mA	\$2-60
5mA	\$2-60
10mA	\$2-60
50mA	\$2-60
100mA	\$2-60
500mA	\$2-60



Type SD.460 46mm x 59.5mm Fronts

50μA	\$2-80
50-0-50μA	\$2-80
100μA	\$2-75
100-0-100μA	\$2-75
200μA	\$2-70
500μA	\$2-55
1mA	\$2-60
5mA	\$2-60
10mA	\$2-60
50mA	\$2-60
100mA	\$2-60
500mA	\$2-60

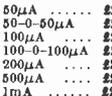

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is demonstrate internal working. Available in the following ranges:


50μA	\$2-90
100μA	\$2-40
1mA	\$2-95
50-0-50μA	\$2-40
1-0-1mA	\$2-95
1A d.c.	\$2-95
1V d.c.	\$2-95
10V d.c.	\$2-95
20V. d.c.	\$2-95
50V. d.c.	\$2-95
300V. d.c.	\$2-95
Dual range	
500mA/5A d.c.	\$7-00
5V/50V d.c.	\$7-00



"SEW" EDGWISSE METERS

Type PE.70. 3 1/2 | 3/2 in. x 1 1/2 | 3/2 in. x 2 1/2 in. deep

50μA	\$3-15
50-0-50μA	\$3-60
100μA	\$3-60
100-0-100μA	\$3-50
200μA	\$3-40
500μA	\$3-60
1mA	\$3-60
300V. A.C.	\$3-25
VU Meter	\$3-95

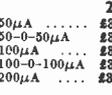

*MOVING IRON— ALL OTHERS MOVING COIL Please add postage

AF20 Mono Transistor Amplifier	\$4-80
AF20 Mon. Transistor Pre-Amplifier	\$2-61
AF310 Mono Amplifier (for Stereo use two)	\$5-91
AT6 Automatic Light Control	\$2-58
AT30 Photo Cell Switching Unit	\$5-70
AT60 400 Watt Triac Light Dimmer Speed Control	\$4-80
AT55 1,300 Watt Triac Light Dimmer Speed Control	\$5-70
AT68 2,200 Watt Triac Light Dimmer Speed Control	\$6-90
AT60 Psychedelic Light Control, Single Channel	\$7-80
AT65 Psychedelic Light Control, 3 Channel	\$14-55
HF61 Medium Wave Transistor Radio	\$3-38
HF66 F.M. Transistor Transmitter	\$2-70
HF75 F.M. Transistor Receiver	\$2-98
HF310 F.M. Tuner Unit	\$15-81
HF325 De Luxe F.M. Tuner Unit	\$24-12
HF330 Stereo Decoder for use with HF310 or HF325	\$9-98
HF395 Aerial Amplifier for AM/FM Bands I, II and III	\$1-77
GP310 Stereo Pre-Amp to use with 2, AF310	\$21-27
GU330 Tremolo Unit for guitars, etc.	\$7-50
NT10 Power Supply 100 mA 9 V Stab., 12 V Unstab.	\$6-15
NT300 Professional Stabilized Power Supply 2 x 30 Volt, 2.2 amp	\$12-51
NT305 Transistor Converter 12/15 V, AC/DC to 6 V, 7.5 V, or 9 V DC	\$4-50
NT310 Power Supply 240 V AC to 2 x 18 V DC at 2 amps	\$4-80
NT315 Power Supply 240 V AC to 4.5-15 V DC 500 mA	\$9-57

Post and Packing 15p per kit. Complete with comprehensive, easy to follow instructions and covered by full guarantee.

SEND SAE FOR NEW 8 PAGE LIST OF SEMI CONDUCTORS & VALVES

ALL PRICES ARE SUBJECT TO 10% VAT




G.W.S. SMITH & CO. (RADIO) LTD

UNR 30 RECEIVER



4 Bands covering 500 kc/s-30 mc/s
B.F.O. Built-in Speaker 220/240 v.
A.C. Brand new with instructions.
Our Price £15-75 Carr. 37p

UR-1A RECEIVER

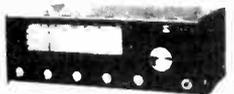

4 Bands covering 500 kc/s-30 mc/s
FET, 8 Meter. Variable BFO for
88B. Built-in Speaker, Band-
spread, Sensitivity Control, 220/
240 v. A.C. or 12 v. D.C. 12in. x
4 1/2in. x 7in. Brand new with
instructions.
Our Price £25-00 Carr. 37p

SKYWOOD CX203 RECEIVER



Solid state, 2 bands covering 200-
420 KHz and 55 to 30 MHz.
Illuminated slide rule dial. Band-
spread. Aerial tuning. BFO. AVC.
ANL, "S" meter, AM/CW/SS B.
Integrated speaker and phone
socket. 220/240 v. A.C. or 12 v.
D.C. Size 325 x 120 x 150 mm.
Complete with instructions and
circuit.
Our Price £32-50 Carr. 50p

LAFAYETTE HA-600 RECEIVER



General coverage, 150-400 kc/s, 500
kc/s-30 mc/s, FET front end, 2
mech. filters, product detector,
variable B.F.O., noise limiter,
8 Meter Bandspread, RF Gain,
15in. x 8 1/2in. x 8 1/2in. 18 lb.
220/240 v. A.C. or 12 v. D.C.
Brand new with instructions.
Our Price £50-00 Carr. 50p

TRIO 9R59DS RECEIVER



4 bands covering 500 kc/s to 30
mc/s continuous and electrical
bandspread on 10, 15, 20, 40 and
80 metres, 8 valve plus 7 diode
circuit, 4/8 ohm output and phone
jack, 88B-CW, ANL, Variable
BFO, 8 meter, Rep. bandspread
dial, IF frequency 445 kc/s, audio
output 1.5w. Variable RF and AF
gain controls 115/250 v. A.C.
Size: 7in. x 13in. x 10in. with
instruction manual.
Our Price £49-50 Carr. Paid.
FULL RANGE OF TRIO STOCKED

EMI LOUDSPEAKERS



Model 380, 13" x 8" with single tweeter/crossover, 20-20,000 Hz, 15 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 37p.
Model 450, 13" x 8" with twin tweeter/crossover, 55-13,000 Hz, 8 watt RMS. Available 8 or 15 ohms. £8-62 each. P. & P. 25p.



SPECIAL OFFER 1 STEREO SPEAKERS

Matched pair of stereo hook-shelf speakers, Deluxe (teak veneer) finish. Size 14 1/2" x 9" x 7 1/2". 8 ohms, 5 watt RMS.
In watt peak. Complete with DIN lead.
Our Price £12-95 Carr. 50p

HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic or ceramic or twin stereo
headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5M Ω /100M Ω . Output 50mW.
Our Price £5-97 P. & P. 15p

1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers with additional 100% all
facility for stereo switching, 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2".
Our Price £2-25 P. & P. 15p

MP7 MIXER PREAMPLIFIER



5 micro-phone inputs each with individual gain controls enabling complete mixing facilities. Battery operated, 9 1/2" x 5" x 3". Inputs Mic: 3 x 3mV 50K Ω ; 2 x 3mV 600 ohm. Phono neg: 12 x 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.
Our Price £8-97 P. & P. 20p

HAND HELD 2-WAY WALKIE TALKIES

Industrial quality in robust metal cases. Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases.
100mW £24-95 pair. Packing & Post 50p.
2 channel 500mW £52-50 pair. Post 50p.
3 channel £71-25 pair. Post 50p.
1 watt
Licence required for operation in U.K.

AUDIOTRONIC

RANGE OF HIGH QUALITY EQUIPMENT

Audiotronic Products are manufactured exclusively for the Audiotronic Group of Companies and as a member of the group we are pleased to offer you this fabulous range of high quality equipment. Made to our own specifications each item provides outstanding performance and reliability at a value for money price!

ACR.14 Battery Mains Cassette Recorder




Portable twin track mono recorder with automatic recording level control. Built-in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. AC 220/240v or 6v DC operation. Complete with remote control microphone, mains lead, earpiece and batteries.
Our Price £10-50 P. & P. 50p.

AR.1000 Sportsman AM/FM Portable Radio



5 waveband covering AM 635 1065KHz FM 88-108MHz AIR 108 135MHz PB 147 174MHz WB 162 5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for FM and built in ferrite bar for AM. AFC. 8in. speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 152 x 79 x 219mm. Battery/mains operation.
Our Price £11-50 P. & P. 35p.

AMR-9000 Global AM/FM Portable Radio

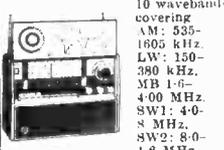

10 waveband covering AM: 635-1605 kHz LW: 150-390 kHz MB 162-400 MHz SW1: 4.0-8 MHz SW2: 8.0-14 MHz SW3: 16-30-60 MHz. PSB1: 148-174 MHz, FM 88-108 MHz. AIR: 108-136 MHz. Features time zone map and tuning dial. Large clear scale. Telescopic aerial and built in speaker. AFC or FM. 6" x 4" Battery/mains operation. Size: 345 x 133 x 305mm.
Our Price £36-00 P. & P. 50p

Stereo Headphones

LSH.20 Individual volume controls Stereo mono switch, 8 ohms, 40 19,000 Hz. £3-50 P & P 30p

LSH.30 Open back type. Individual tone and volume controls, 8 ohms, 30-20,000 Hz. £5-50 P & P 30p

LSH.40 Two way speaker system. Individual volume controls, 8 ohms, 20-20,000 Hz. £8-95 P & P 30p

ACD.660 Stereo Cassette Deck



A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter normal/chronome tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/DIN line input sockets, 3.5mm DIN input sockets etc., etc. Frequency response 100-8KHz (100-12KHz CrO2) S/N-45dB, Crosstalk 45dB, Separation-35dB, Noise limiter-6dB at 10KHz. Complete with phono connecting leads.
Our Price £39-50 Carr. 50p

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 162" x 8" x 3 1/2". AC 220/240v.

PROCESS TWO
For use with cassette and tape recorders. Freq. res. 30Hz-20KHz \pm 2dB. Off tape monitoring. Switchable multiplex filter. 20 Full source tape monitoring. Record/Play metering. Switchable multiplex filter. Supplied with test tape.
Our Price £34-50 P & P 50p

LOW NOISE TAPE CASSETTES

TYPE	5	10	25	Cassette
C80	£1 29	£2 53	£5 99	Tape Head
C90	£1 85	£3 62	£5 69	Cleaner 30p
C120	£2 29	£4 48	£10 68	

P. & P. 15p. post free



ACP-8 8 TRACK CAR PLAYER

Attractive black and silver finish. 12v neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.
ONLY £12-50 P & P 40p



ACR1 PUSH BUTTON CAR RADIO

Push button tuning of one LW and five MW stations of your choice. 12v pos. or neg. earth. Complete with speaker, mounting brackets and instructions.
Our Price £8-95 P & P 50p

AHP-8D 8 Track Stereo Tape Deck



Can be used with most hi fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. AC 220/240v.
Our Price £11-95 P. & P. 30p.

AHP-8A 8 Track Stereo Tape Player




Incorporates built-in amplifiers giving 4 1/2 + 4 1/2 watts rms output. Push button track selector, illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. AC 220/240v.
Our Price £17-25 P. & P. 50p.



PROCESS FOUR

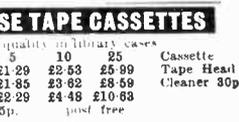For use with semi-professional tape recorders. Freq. res. 30Hz-20KHz \pm 2dB. S/N better than 70dB. Full source tape monitoring. Record/Play metering. Switchable multiplex filter. Supplied with test tape.
Our Price £50-00 P & P 50p



ACA 5SE ELECTRIC CAR AERIAL

Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker, mounting brackets and instructions.
Our Price £6-50 P & P 50p



3 section. Fully automatic. 12v DC. Extends to approx. 40". Complete with switch, all leads and instructions.
Our Price £5-95 P & P 50p

SAVE UP TO 33 1/3% OR MORE! GWS

RECORD DECK PACKAGES



Carriage and Packing 75p.
Complete units with Stereo cart-ridge ready wired in plinth cover.

GARRARD

2025 TC9/TAHCD	£10.85
SP25 111/G800	£15.95
SP25 111/M44E	£16.45
SP25 111/M44-7	£18.10
SP25 111/M35E	£18.90
SP25 111 Module/M75-6	£18.99
AP76/G800	£23.95
AP76/G800E	£25.95
AP76/M44E	£24.95
AP76/M55E	£25.65
AP76/M75ED	£31.70
AP76/M75EJ	£27.85
AP76 Module M75-6	£26.85
AP96 Module M75-6	£30.40
ZERO 1008 Module/M93E	£41.85

B.S.R. McDONALD

210/SC7M	£8.85
MP60/G800	£15.50
MP60/TPD1/G800	£15.20
MP60/M44-7	£16.60
HT70/TPD1/G800	£18.60

GOLDRING

GL72/G800	£30.90
GL75/G800	£33.80
GL75/G800E	£36.75

GOODMANS

TD100/G800 Teak	£46.85
TD100/G800 White	£48.60

LEAK

Delta/M75-6	£43.95
-------------	--------

PHILIPS

GA105/GP200	£13.80
GA160/GP200 Teak	£19.50
GA212/GP400	£24.25
GA308 (less cartridge)	£23.95
GA308 P.T.	£32.75

PIONEER

PL12D (Less cartridge)	£29.60
PL15C (Less cartridge)	£41.25
PL41D (Less cartridge)	£95.25
PL50 (Less cartridge)	£89.90
PL61 (Less cartridge)	£102.75
PLA35 (Less cartridge)	£98.60

THORENS

TD160/Oortofon M15ES	£66.95
TD125 AB11/Oortofon M15E Super	£104.25
TD165/Oortofon M15E Super	£59.60

WEARFEDALE

Linton/M44-7 Teak	£23.70
Linton/M44-7 White	£23.90

RECORD DECKS



Carriage and Packing 50p
B.S.R. McDONALD

C114 Mini	£3.95
C129 Mono	£5.50
C137	£7.00
610/TPD1	£13.85
610	£9.90
610/TPD1	£14.85
710	£19.20
810	£24.50
MP60	£7.65
MP60/G800	£10.25
MP60/TPD1	£12.60
MP60/TPD2	£11.25
HT70	£10.87
HT70/G800	£13.60
HT70/TPD1	£15.95

CONNOISSEUR

BD1 Chassis	£8.65
BD1/SAU2/Plinth/Cover	£21.75
BD2/SAU2/Chassis	£22.70
BD2/SAU2/Plinth/Cover	£28.20

GARRARD

2025 T/C Stereo	£8.40
SP25 III	£8.50
SP25 III Acos GP104C	£8.60
SP25111/G800	£10.95
SP25/M75-6	£13.90
AP76	£15.40
SL65B	£11.15
SL72B	£17.75
SL95B	£23.25
401	£23.50
ZERO 100A	£30.30
ZERO 100S	£27.95

GOLDRING

G95	£18.85
G101P/C	£19.55
GL69/2	£25.75
GL72	£17.85
GL72/P	£23.20
GL75	£23.75
GL75/P	£28.30
GL78/P	£46.55
GL85P/C	£49.50

SPECIAL GARRARD OFFERS!



4 speed autochanger unit fitted with stereo ceramic cartridge.
Our Price £4-95 Carr. 50p

SP25 III WITH ACOS GP 104

SP25 MK.III, 4 speed single record player fitted with Acos GP104 stereo ceramic cartridge.
Our Price £8-50 Carr. 50p

Audiotronic AMB.500 Multiband Radio

5 wavebands covering MW 535-1605KHz and FM 88-175MHz. All transistor. Complete with batteries, shoulder strap and earpiece.
OUR PRICE £6.95 P & P 50p

FANTASTIC OFFER!



AKAI CS35

CASSETTE RECORDER with a pair of OS88 Speakers. List £96.10.

OUR PRICE £56-50 P & P 50p

CASSETTE (P. & P. 50p)	
CS85D Deck	£44.45
CS85/CS88 Speakers	£67.95
GXC40D Deck	£57.20
GXC40D Recorder	£67.20
GXC40T Deck/Receiver	£99.05
GXC45 Deck	£78.25
GXC46D Dolby Deck	£89.95
GXC46D Recorder	£87.65
GXC65D Dolby Deck	£92.85

CARTRIDGE (P. & P. 50p)

CR41 Deck with amps.	£65.40
CR41D Deck	£53.60
CR41T Recorder/Receiver	£92.75
CR808S 4 channel Rechr.	£114.25
CR808DS 4 channel Rechr.	£93.65

TAPE (P. & P. 75p)

4000DS Deck	£59.95
4000DS Dust Cover	£3.95
1721L Recorder	£80.35
X5000 Recorder	£92.55
X201D Deck	£108.20
GX220D Deck	£123.95
GX221D	£138.40
GX280D Deck	£196.50
GX370 Deck	£211.50

TAPE/CASSETTE (P. & P. 75p)

GX1900D Deck	£144.50
--------------	---------

MICROPHONES (P. & P. 50p)

ADM.11 Dynamic (pair)	£7-50
-----------------------	-------

STEREO RECEIVERS (P. & P. 75p)

AA6300 20+20 watt	£81.85
AA8030 25+25 watt	£92.50
AA8080 40+40 watt	£117.50
AA8100S 2x36 or 4x18 W	£175.00
AA8500 65+65 watt	£150.50

STEREO AMPLIFIERS (P. & P. 50p)

AA5200 20+20 watt	£61.75
AA5500 30+30 watt	£78.50
AA8300 45+45 watt	£117.50

STEREO TUNERS (P. & P. 50p)

AT550 AM/FM	£60.50
AT580 AM/FM	£94.50

4-CHANNEL UNIT (P. & P. 50p)

SSI Synthesiser	£39.95
-----------------	--------

SPEAKERS

8W155 (each)	£51.00
--------------	--------

STEREO HEADPHONES

ASE11	£4.75
ASE20	£7.30
ASE22	£8.25

HOMER INTERCOMS



Ideal for home, office, stores, factories, etc. complete with batteries, cable and instructions.

2 Station £2-97, P. & P. 15p.
3 Station £5-25, P. & P. 15p.
4 Station £6-62, P. & P. 17p.

SH628 STEREO HEADPHONES



Outstanding value. Soft ear-pads, adjustable headband, 8-16 ohms, 20-20,000 Hz. Complete with lead and stereo plug.
Our Price £1-87 P. & P. 30p

LHO25 STEREO HEADPHONES



Lightweight headphones with padded earpieces, 4-16 ohms, 20-20,000 Hz. Complete with 6 ft. cord and plug.
Our Price £1-95 P. & P. 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.
Our Price £2-25 P. & P. 30p

BH.001 HEAD SET AND BOOM MICROPHONE



Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms.
Our Price £4-95 P. & P. 30p

FM TUNER CHASSIS



4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/a. Ready built ready for use. Fantastic value for money.
Our Price £5-95 P. & P. 12p

SPECIAL PURCHASE! FERGUSON EXPORT MODELS



FERGUSON 3408 STEREO TUNER AMPLIFIER. Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape etc. Separate bass treble, balance and volume controls.
Our Price £31-50 P. & P. 50p



3418 STEREO TAPE DECK. 4 track. 7 1/2, 3 1/2, 1 1/2 i.p.a. Stereo/mono recrd./play. 7" reels. Inputs for dynamic mikes, radio, gram. Complete with cover.
Our Price £41-95 P. & P. 75p

VAT

All prices are subject to 10% VAT (10p in the £)

10% VAT

Order with confidence by post - but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY.

SEND LARGE S.A.E. FOR FULL HI-FI DISCOUNT LIST

G.W.SMITH & CO (RADIO) LTD

ALL MAIL ORDERS TO UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JW

TELEPHONE 01-205 3735

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON	257, E. Tottenham Court Rd. W.1. Tel: 01-580 0670	311, Edgware Road, W.2. Tel: 01-282 0387
10, Tottenham Court Rd. W.1. Tel: 01-437 2232	382, Edgware Road, W.2. Tel: 01-723 4194	
27, Tottenham Court Rd. W.1. Tel: 01-436 3718	162/3, Fleet Street, E.C.4. Tel: 01-353 2833	
87, Tottenham Court Rd. W.1. Tel: 01-680 3728	378, Harrow Road, W.9. Tel: 01-288 9530	
21, Old Compton Street, W.1. Tel: 01-437 9388	86, South Street, Romford. Tel: Romford 20218	
3, Lisle Street, W.C.2. Tel: 01-437 8204	SURREY	
34, Lisle Street, W.C.2. Tel: 01-437 9155	1046, Whitgift Centre, Croydon. Tel: 01-681 3027	
118, Edgware Road, W.2. Tel: 01-723 9789	27 & 29, Eden Street, Kingston. Tel: 01-546 7845	
193, Edgware Road, W.2. Tel: 01-723 6211	32, Hill Street, Richmond. Tel: 01-948 1441	

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

Buy it with Access

BARCODE CARD

All items and prices are correct at

but subject to change without notice. E & O E

CREDIT TERMS FOR CALLERS (£50 and over)

ALL EQUIPMENT IS BRAND NEW FULLY GUARANTEED AND OFFERED WITH FULL AFTER SALES SERVICE

parts for PRACTICAL WIRELESS projects

After many requests, Electro Spares are now supplying lists of components for ALL the projects featured in "Practical Wireless", commencing this month. Just forward an S.A.E. (Preferably 9" x 4" minimum) stating which project is of interest to you—we will forward an individually priced list of components required. No need to buy a full kit—you need only purchase the parts you require at any one time.

All Electro Spares supplied components are new, branded products of reputable manufacturers and carry full makers guarantee.

We regret we cannot supply lists for projects published before this issue.

"ONE SOURCE" BUYING MAKES SENSE—IT CAN SAVE YOU TIME, MONEY AND POSTAGE.

"p.e." f.m. varicap stereo tuner

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics" May 1973.

Features include push button "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses NEW pre-set modules for R.F. and I.F. Circuits—no circuit alignment. High efficiency Integrated Circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator. Fibre Glass P.C. Board, neat slimline cabinet with brushed aluminium front panel, push buttons etc. etc.

IDEAL FOR USE WITH THE "TEXAN," "GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER

Please send large S.A.E. for full details.

"p.e. gemini" stereo amplifier

QUALITY HI-FI FOR THE HOME CONSTRUCTOR
30 Watts per channel into 8 ohms! Total Harmonic Distortion 0.02%! Frequency Response (-3 dB) 20Hz-100kHz!

We are still continuing to supply components for this fabulous Amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the Home Constructor—we can supply a Booklet containing full specification, complete constructional information wiring diagrams, fault finding guide, etc. etc. Price 55p, plus 4p postage.

Our New Low Price List is supplied with each booklet, or supplied separately on receipt of a large S.A.E.

FOR PEOPLE WHO REQUIRE THE BEST, IT HAS TO BE THE "p.e. gemini".

Note Our New Address—With New Mail Order Department For Quick, Efficient Service.

**PLEASE PAY US A CALL—VISITORS WELCOME.
NO PARKING PROBLEMS**

Electro-Spares

288, ECCLESALL ROAD,
SHEFFIELD, S11 8PE

"THE COMPONENT CENTRE OF THE NORTH"

D.I.Y. ELECTRONIC ORGAN KITS

*In use throughout
the world by
professionals*



★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2x5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55.


V.A.T. please add 10%—show separately on order.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT, ELECTRICAL HOUSEHOLD APPLIANCES AND MUSICAL INSTRUMENTS.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

**YOU ARE WELCOME TO VISIT THE ONLY D.I.Y. ELECTRONIC ORGAN CENTRE IN EUROPE
AT 12 BRETT RD., HACKNEY E8, TEL. 986 8455**

CASED AMPLIFIERS

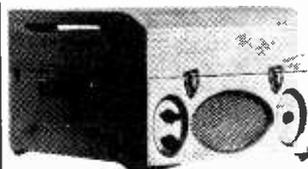

Polished wooden cabinet 14 x 13 x 9" with hinged lid containing a sensitive (20μV) 4-valve amplifier with tone and volume controls, giving about 3 watts output to the 7 x 4" 3Ω speaker. Also a non-standard single motor tape deck. Easily converted to record player, guitar practice amp, baby alarm, etc. Supplied in good working condition with circuit diagram. Mains operated. Only £3 (£1 up to 200 miles, £1.20 over). Special cassettes £1 (25p). Spare heads 40p. Damaged machines from £1.50 to callers only.

COMPUTER PANELS

Type A: 4 OC35, 4 GET103, etc. 50p; Type C: 2 OC35, 2 OC76, 6 OC42, etc. 30p; Type D: 4 OC36, 8 GET103, etc. 60p. (5p ea). Parcel of 12 top quality boards £2 (25p). 7lb of lower quality including some broken £2 (40p), 56lb £12 (c.p.). Boards from 5p to callers.

7lb BARGAIN PARCELS

Hundreds of new components—capacitors, resistors, switches, crystals, pots, PC boards, etc. Outstanding value £1.65 (35p).

500 assorted resistors, good selection £1 (15p); 40 asstd pots £1 (25p); 300 asstd capacitors, all types £1 (25p). Heavy duty heat sinks 6 x 5 x 3". Wt. 3lbs with 2 power transistors, OC36 or 2N1146A £1 (25p). Large selection of panel meters for callers. Audio oscillator 50Hz-20kHz, BFO No. 8 £10; RF Signal generator Marconi TF144G 85kHz-25MHz from £12. 741C TO99 28p; BC107-9 14 for £1; 2N3055 35p. Veroboard in stock. Post in brackets, small parts 3p. VAT NOT INCLUDED. SAE List, details.

GREENWELD ELECTRONICS (PW3)

24 Goodhart Way, West Wickham, Kent. SHOP AT 21 Deptford Broadway, SE8 (Next to old cinema). Callers most welcome. Tel: 01-692 2009.

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK. 9.00 a.m. - 6.00 p.m.



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD. 163 MITCHAM ROAD, LONDON SW17 9PG 01-672 3137/9080

PRE-AMPLIFIER £4.22



All Tuac audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with W.S. carbon film resistors are used throughout. Extensive research has gone into the various wide range tone control circuits, producing superb sound quality from any signal. Previous range still available. 40V d.c., 30mV o/p.

VA08 — Vol, Treb, Mid and Bass Controls. HI £4.22 IMP. FET I/P. Suitable Mic, Guitar, Radio, Illus. Crystal/Ceramic P.U. Sensitivity 4mV. P. & P. 20p

Treb +35dB at 16kHz, Mid +20-15dB at 1kHz, Bass +20-10dB at 40Hz.


VA06 — Vol, Treb and Bass Controls. 8mV sensitivity. Treb +28-15dB at 12kHz, £3.72 Bass ± 18dB at 40Hz.

MVA01 — Vol, Tone, Vol, Tone Controls. Ideal for Disco. Suitable for Mic I/P. Sensitivity £4.50 2mV. Tone range +25dB at 12kHz to +20dB at 40Hz.

AMF01 — Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade P. & P. 20p

O/P to main Amp. 30mV operating level. Depth and Vol Controls.

POWER AMPLIFIER £15.18

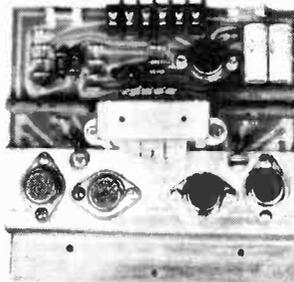


TPI00W with RCA output transformers—150w device 2N6254

TPI00W 100 Watts r.m.s. continuous sine wave into 8Ω. 30mV input into 3kΩ full power frequency response 10Hz-20kHz ± 2dB. Hum and noise better than —70dB. T.H.D. at 100 Watts 2%. This rugged circuit incorporates a special layer wound driver transformer to give increased reliability under all conditions. Short and open circuit proof. An external heatsink area is required. Just bolt on the module.

TP50W 50 Watts r.m.s. continuous sine wave into 8-15Ω. With 115 Watt RCA 2N3055 output transformers. Specification as TPI00W. £10.36

POWER SUPPLY £9.10

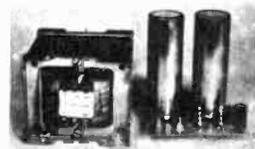

100 W. R.M.S. sine. 200 mV. R.M.S. square. £28.50 + p & p Trade & export enquiries welcome. Call for a demonstration

PS100— 100 Watt Power Supply for one TPI00W £9.10 Module. Complete as illus. above.

PS50 50 Watt Power Supply for one TP50W £6.86 Module. Similar to illus. above. Postage and Packing 50p each.

PSU2— 40V. 250mA. Pre-amp./Disco Mixer £2.95 Supply. P. & P. 25p.

ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS

DISCO-THEQUE MIXER FEATURING AUTO-FADE



Panel mounting Cut out 17 x 3 1/2 ins.

£22.00. P. & P. 50p. PSU £2.95 Designed for the discerning D.J. of professional standard. Auto Fade is fitted as standard. Controls: Mic Vol, Tone. Over-ride depth, Auto Manual Sw. Tape Vol, L & R Deck Faders. Deck Volume, Treb & Bass. H. Phon Vol, Selector. Master Vol, on/off sw.

HIGH POWER AMPLIFICATION



Suitable for Disco, P.A., Guitar etc. Rugged circuit, rugged case.

LIGHT MODULATORS

Triac controlled. Safety isolating input transformer. 0.5 Watt sensitivity with controls.

SILMB 3 1000 Watt outputs' £17.45 Bass, Mid & Treb.

S2LMB 1 1800 Watt output. £6.47 Operates on all fre- P. & P. quencies. 30p

ALL TUAC KITS ARE SUPPLIED COMPLETE WITH EASY TO FOLLOW WIRING INSTRUCTIONS AND CIRCUIT DIAGRAM. ALL PRICES INCLUDE VAT.

LARGE S.A.E. WITH ALL ENQUIRIES PLEASE.

ALL TUAC MODULES ARE READY ASSEMBLED ON GLASS FIBRE P.C. BOARD AND INDIVIDUALLY TESTED

SAVE TIME AND MONEY

LIST PRICE **£6.87** | OUR PRICE **£5.32** INCLUDING V.A.T.



As supplied by us to **SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY.** Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21" x 11" x 6 1/2". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available. Callers welcome Mon.-Sat. 9 a.m.-1 p.m. 2 p.m.-9 p.m. **NEW as illustrated OUR PRICE ONLY £5.32 plus 56p carriage on orders less than £10.** Money back guarantee. **SEND FOR FREE LISTS.**

TRADE AIDS
(DEPT. PW13), 111 CHILTERN DRIVE, BERRYLANDS, SURBITON, SURREY

01-399 4383
100 yds. Berrylands Railway Station.

TRANSFORMERS

DOUGLAS GUARANTEED
Prices include 10% VAT & p. & p.
12 or 24 volts

Output V. & Amps	Ref. No.	Price
12V x 1 250mA x 2	MT11C8**	£1.15
12V x 2 500mA x 2	MT213CT**	£1.86
12V x 2 1A x 2	MT71AT*	£1.97
12V x 2 2A x 2	MT18AT	£2.70
12V x 2 3A x 2	MT70AT	£3.34
12V x 2 4A x 2	MT105AT	£3.74
12V x 2 5A x 2	MT72AT	£4.30

Output Amps	Ref. No.	Price	
500mA MT112CT*	£1.47	4A MT21AT	£4.02
1A MT79AT*	£1.98	5A MT61AT	£5.73
2A MT8AT	£2.92		
3A MT20AT	£3.39		

Output Amps	Ref. No.	Price	
500mA MT102AT*	£1.92	3A MT105AT	£4.98
1A MT103AT	£2.87	4A MT106AT	£6.50
2A MT104AT	£3.83	5A MT107AT	£9.11

60 volts. All tapped at 0-12-15-20-30V.

60 volts. All tapped at 0-19-25-33-40-50V.

80 volts. All tapped at 0-24-30-40-48-60V.

AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price
20VA	0-115-210-240	XMT118CT	£1.28
75VA		XMT64AT	£2.85
150VA	0-115-200-220-240	XMT74AT	£2.85
200VA		XMT65AT	£3.84

400V Output at 50 HZ. Rel. IT3AT
C-D Ignition System by R. M. Marston, Esq., Wireless World. £2.98

EQUIPMENT RANGE

Sec. output (r.m.s.)	Ref. No.	Price
3-0-3 V. 200mA	MT238C8**	£1.59
9-0-9 100mA	MT138C8**	£1.24
12-0-12 50mA	MT238C8**	£1.24
20-0-20 30mA	MT241C8**	£1.24
0-20 x 2 300 x 2	MT230CT**	£1.89
0-8-3 x 2 500mA x 2	MT207CT**	£1.87
0-15-20 x 2 500mA x 2	MT205AT**	£2.86
0-15-27 x 2 500mA x 2	MT203AT*	£3.17
0-15-27 x 2 1A x 2	MT204AT*	£4.26
20-12-0-12-20 700mA (d.c.)	MT221AT*	£1.58

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. spalls; * with interwinding screen; † untapped 240V Primary; ** tapped at 210-240V; other Primaries tapped at 200-220-240V.

Over 200 types in stock through agents or direct. Please send for lists.

DOUGLAS ELECTRONIC INDUSTRIES LTD.
Direct Sales Dept. F.W., Thames Street, LOUPE, Lincs. LN11 7AD

4-STATION INTERCOM



£7.99

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. and other accessories. P. & P. 44p

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price **£16.95** P. & P. 60p

INTERCOM BABY ALARM



OUR PRICE ONLY £3.99

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Complete with Battery. P. & P. 29p

TELEPHONE AMPLIFIER

£3.46

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the hand-set. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 24p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.6)
169 KENSINGTON HIGH STREET, LONDON, W.8.

ESSENTIAL BOOKS FOR RADIO AMATEURS

A GUIDE TO AMATEUR RADIO
by Pat Hawker G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.
90p post paid

TELEVISION INTERFERENCE MANUAL
by B. Priestley G3JGO

The causes of interference to TV receivers are examined, and ways in which they can be overcome are suggested in this latest RSGB publication.
90p post paid

AMATEUR RADIO TECHNIQUES
by Pat Hawker G3VA

4th Edn. 256 pages. A source book for many useful circuits and aerials. An ideas book aimed at extending the reader's awareness of new devices and techniques.
£1.80 post paid

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's UK origin ensures easy availability of components. Complete coverage of technical and constructional fields.
£4.10 post paid

These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send S.a.e. for complete list

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688




All prices in pounds and new pence

VALVES		6BA6		28 6J8		30 7C5		1113 12SR7		50 37		60 DAF91		30 ERL31		£1.50 EL34		50 N78		£1.60 PL500		80 U403		70	
1A7GT	55	6B8E	32	6J7M	45	7C6	75	14H7	50	42	60 DAF96	50	EC90	35	EL41	75	N108	£1.50	PL510	50	U404	70	£1.18		
1D5	60	6BH6	75	6J7G	45	7D5	70	19AQ5	50	50B35	70	DC900	£1.35	ECC81	40	EL43	65	OA2	40	PL508	80	U401	£1.18		
1H5	50	6BR7	55	6J7GT	45	7H7	70	20D1	50	50C35	80	DF33	55	ECC82	33	EL84	25	OC3	40	PL509	£1.60	U402	40		
IN5GT	55	6BR8	70	6K7M	45	7R7	75	20P2	75	20P2	70	50CD60	£1.20	DF70	45	ECC83	33	OZ4	45	PL802	85	U4F42	60		
1R5	30	6BW6	80	6K8M	60	10C2	65	20P4	£1.10	501.6GT	55	DF91	30	ECC84	30	ELL80	£1.00	PC86	60	PX4	£3.00	U4C41	55		
1R5	30	6C4	35	6K8GT	50	10F1	75	20P5	£1.20	75	55	DF92	20	ECC85	40	EM90	45	PC88	60	PX25	£3.00	U4C81	45		
1T4	30	6W7	85	6K8GT	50	10F3	90	25A6	35	80	60	DI776	35	ECC86	40	EM81	60	PC97	50	PY33	65	U4B80	40		
3A4	45	6C5G	46	6K25	75	10F9	65	25L6GT	50	85A2	55	DK32	45	ECH35	£1.00	EM94	35	PC84	40	PY81	30	U4P89	40		
3Q4	60	6C8	40	6L25	50	10F18	60	25Y5	30	150C4	65	DK92	70	ECH42	75	EY86	40	PC99	50	PY92	35	U4C94	43		
8Q5	50	6CD6G	£1.30	6L18	50	10LD11	70	25Z4	30	50Z4GT	55	801	60	DK96	60	ECH83	45	EZ40	50	PCF82	35	PY800	47	U4C42	70
3V4	48	6CH6	40	6Q7G	45	10L13	75	30C15	£1.00	866A	85	DL92	40	ECL80	50	EZ41	75	PCF84	60	PY801	50	U4C81	60		
5R4GY	75	6D6	40	68A7M	85	11E3	£4.80	30C17	£1.10	954	60	DL94	48	ECL86	40	GY501	80	PCF80	50	PY90	50	U4F41	65		
5U4G	40	6E5	£1.00	68C7M	80	12A1E	40	30C18	90	10Z5	70	DL95	50	ECL88	40	GZ30	45	PCF85	80	BP4	70	U4F89	40		
5V4G	50	6F1	75	68G7M	45	12A17	40	30P15	£1.00	4022A2	£5.50	DL96	55	ECL90	60	EP9	90	PCF86	60	BP4	£3.00	U4F41	65		
5Y3GT	45	6F5G	60	68H7M	45	12A17	40	30P16	£1.20	7193	40	DM70	80	EP9	90	EP9	90	PCF87	85	SP61	75	U4L84	43		
5Z4G	45	6F8G	55	68K7GT	40	12A17	40	30P17	90	7475	60	DY87	36	EP39	60	EP37A	£1.20	PCF88	65	STY380/80	UM80	35			
6J30L2	90	6P11	50	68L7GT	45	12A17	40	30P18	90	ATP5	60	E88CC	70	EP41	65	KT61	£1.75	PCF89	45	SU25	£1.20	U4I9	50		
6A7	75	6P13	50	68N7GT	45	12B6G	50	30P19	95	AU2	£4.00	EBC80	38	EP42	60	KT81	£1.75	PCF90	45	SU2150	75	U4Y41	48		
6A8G	45	6P14	70	68Q7GT	40	12C8GT	35	30P20	95	AU5	75	EBC33	60	EP43	60	KT81(7C5)	PD500	£1.30	TD44	80	VMP34G	85			
6AK5	40	6P23	80	6U3GT	70	12E1	£3.90	30P21	£1.00	ATP7	75	EBC41	65	EP44	65	KT88	£2.25	PEN4	£1.00	U10	75	VP48	£1.25		
6AM5	40	6P24	80	6U8G	£1.00	12F5GT	35	30P22	95	AU2	£4.00	EBC41	65	EP45	65	KT88	£2.25	PEN4	£1.00	U14	75	VR105/30	38		
6AM6	37	6P28	70	6V6G	60	12G7GT	50	30P23	95	AU5	75	EBC30	60	EP46	60	KT88	£2.25	PEN4	£1.00	U19	£3.50	VR150/30	35		
6AQ5	42	6P32	80	6V6GT	45	12H8GT	50	30P24	£1.25	AZ31	55	EBC90	40	EP47	37	KT241	60	PEN46	50	U25	85	VU111	75		
6AS7G	85	6G6	35	6X4	40	12J7GT	45	35A5	75	CLB31	£1.00	EBF90	40	EP48	40	ML4	38	PL36	55	U26	85	VU120	£1.00		
6AT6	38	6H6	30	6X5G	40	12K7GT	45	35L6	50	COH35	75	EBF98	40	EP49	75	ML6	60	PL81	50	U78	35	VU508	£3.50		
6AU6	30	6J5M	60	6X3GT	45	12L7GT	45	35W4	40	CL33	£1.50	EBF89	32	EP183	30	ML8	50	PL82	45	U191	75	W81M	63		
6B4G	£1.00	6J5G	20	7B6	75	12M7	£1.37	35Z4	75	CY30	63	EBF89	32	EP184	35	MSP4	50	PL82	45	U191	75	W81M	63		
6B8G	30	6J6GT	40	7B7	70	12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31	50	EBL1	£1.00	EL32	50	MU14	75	PL83	45	U251	80	Y63	£1.25		
						12N8GT	50	35Z4GT	75	CY31															

PRICES NOW INCLUDE VAT


SUPERSOUND 13 HI-FI MONO AMPLIFIER

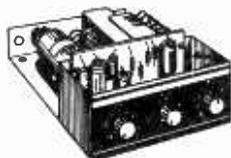

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts

r.m.s. into 8 ohm. Frequency response 12Hz - 30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, switchgear panel, input and output plugs. Overall size 3" high x 8" wide x 7 1/2" deep. PRICE 200/250V. AC 200/240V. P. & P. 25p.

DE LUXE STEREO AMPLIFIER

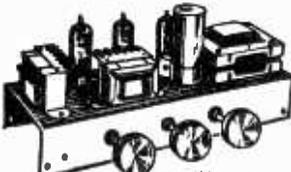

A.C. mains 200-240 V. 10 A 1 n g heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Valve line up:—2 x ECC85 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully isolated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, rings etc. size 11" x 4". Overall height including valves 6". Really built & tested to a high standard. PRICE 89-90 P. & P. 40p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7.5v, and 9v, and 12v, at 1 amp continuous (1 amp intermittent).

Wired insulated output terminals and pilot lamp indicator. Manner finish metal case overall size 9" x 3 1/2" x 2 1/2". Suitable for Transistor Radio, Tape Recorders, Amplifiers etc. etc. Really built and tested. PRICE 15-00 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T.O.S. complete with nuts and bushes. Size 2 1/2" x 3" approx. 85p pair. P. & P. 2p.

HIGH GRADE COPPER LAMINATE BOARDS 8" x 4" 5 for 55p P. and p. 13p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-10-10-20-20-30-35-40-60v. half wave at 1 amp, or 10-10-20-20-30-30-30v, at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price 88-10 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 0-0-0 at 500mA. 11-00 P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 11-10 P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 11-65 P. & P. 30p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100µA. For balance or tuning. Approx. size 1 1/2" x 1 1/2" deep. Limited number. 88p. P. & P. 10p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 8-15v. battery or from H.T. line 200-300v. Frequency response 15Hz - 20KHz. Gain 20dB. Molded encapsulation size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price. 11-00 P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents 80p
Transistor Equivalents 90p
Transistor Characteristics 11-15
POST FREE.
All three together 42-80

Open 9-5.30 Monday to Friday, 9-5 Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C129 AUTOCHANGER UNITS with latest stereo/mono compatible cartridge 27-60 + 50p P. & P.

GARRARD SP25 Mk III with heavy precision machined 4ie cast turntable 110-56, carr. 50p.

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, BL60B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including right angled acrylic cover).
NOW ONLY 44-95 P. & P. 35p.

LATEST ACOS GP91/18C mono compatible cartridge with 1/2" stylus for LP, EP, 78. Universal mounting bracket. 21-50 P. & P. 30p.

SOMOTONE STARCH COMPATIBLE STEREO CARTRIDGE
T/O stylus Diamond Stereo LP and 45rpm 78.
ONLY 22-30 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. 22-80 P. & P. 10p.
LATEST RONETTE TO STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. 11-63 P. & P. 10p.
LATEST RONETTE TO MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 11-50 P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Really built and tested. PRICE 84-00 P. & P. 40p.
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE 25-85 P. & P. 50p.

SPECIAL OFFER ! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Yuarin front. Size 10 1/2" high x 10 1/2" wide x 9" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.P. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohm impedance.

OUR PRICE 19-25 Carr. 70p
Cabinet Available Separately 24-95 (arr. 65p)
Also available in 8 ohm with EMI 13" x 8" bass speaker with parasitic tweeter 17-15 (arr. 70p)

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECC82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohm. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. At mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. 13-30 P. & P. 35p BARGAIN PRICE

LOUDSPEAKER BARGAINS

8in. 3 ohm 11-05 P. & P. 10p. 7 x 4in. 3 ohm 11-16 P. & P. 20p. 10 x 6in. 3 or 15 ohm 11-80 P. & P. 30p. E.M.I. 8" x 8in. 3 ohm with high flux magnet 11-65 P. & P. 20p. E.M.I. 13 1/2" x 8in. with high flux ceramic magnet with parasitic tweeter 17-15 (arr. 70p) 22-80 P. & P. 30p. H.M.I. 13 x 8in. 3, 8 or 15 ohm with 1/2" built tweeter and crossover network 24-85 P. & P. 30p. E.M.I. Ceramic magnet heavy duty tweeter. Approx 3 1/2". Available 3 or 8 or 15 ohm. 11-25 + 10p x 1 p.

BRAND NEW 12in. 16w. H/D Speaker, 3 or 15 ohm. Current production by well-known British maker. Now with Hillix ceramic ferrite magnet assembly 17-80. Guitar models: 25w. 17-80, 35w. 19-85 P. & P. 40p



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC TWIN CONE LOUDSPEAKERS

With large ceramic magnet and plasticised cone surround. 3 ohm impedance. 22-70 P. & P. 25p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm 22-45 P. & P. 30p. 35 ohm SPEAKERS 3in. only 70p P. & P. 13p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11" x 14 1/2" x 1 1/2" deep. Weight 10oz. Power handling 20W r.m.s. (40V peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only 26-85 each. P. & P. 25p.


YMAIR & BEXINS SPEAKERS & CABINET FABRICS
per yd. (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexible ear-muffs. Wired and fitted with standard stereo 1/4" jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE 23-80 P. & P. 10p.

HIGH IMPEDANCE CRYSTAL STICK MIKES.
OUR PRICE 11-15 P. & P. 10p

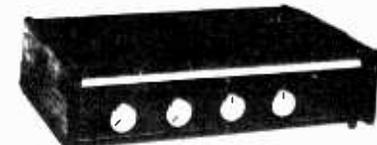HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A truly first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Fully simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohm. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Minute step by step instructions enable any constructor to build an amplifier to his usual or brief specifications. Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response ±3dB 12-20,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth: ±3dB 12-15,000 Hz. Bass boost approx. to ±12dB. Treble cut approx. to -10dB. Negative feedback 18dB over the amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" h. x 9 1/2" d.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. AMPLIFIER KIT 11-55 P. & P. 14p (Magnetic Input components 33p extra)
POWER PACK KIT 23-80 P. & P. 35p
CABINET 23-80 P. & P. 31p (Post Free if all units purchased at same time)

Also available ready built and tested 123-10. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, turn record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discographic use, etc.




12 VALVE AUDIO

AMPLIFIER HA84 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Really built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" x 4 1/2" h. Incorporates ECC83, EL84, K280 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and laid extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 42-50 P. & P. 30p.
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA84 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 44-50 P. & P. 40p.

British made 80w. size 11 silicon stereo amplifier. 11 watts rms per channel output. rev. 2011a to 20KHz. Suitable for magnetic or ceramic pickup type mics. Built in switchable scratch filter, rumble filter and loudness control, 80 m/m slider controls for bass, treble and volume. 10 way push button function, selector switch. This amplifier has specification and performance usually only found in amplifiers costing twice as much. Each amplifier supplied, tested and fully guaranteed. Finished in the most attractive contemporary style teak cabinet. Size 10 1/2" x 8 1/2" x 4 1/2". Makers recommended price 248-30 (inc. VAT) Our price (while stocks last) 138-75 (inc. VAT) + 75p. p. & p. Send SAE for full details of specification.

10 1/2 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Hi-Fi reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 2-15 Ω speaker and 2 ohm volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 B144s, ECC82, E280 and E280 rectifier. Simple instruction booklet 10p + MAF (Free with parts). All parts sold separately. ONLY 28-80 P. & P. 50p. Also available ready built and tested 123-10 P. & P. 60p.

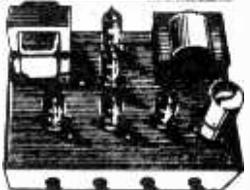

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Sinclair Project 60

Now—the Z.50 Mk.2

with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual
£5.48

Z.30 the power amplifier for quality and economy




with free manual
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/4 x 1/2). Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.

Brilliant new technical specifications

Input impedance 100 K Ω
Input (for 30w into 8 Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8 Ω . See curve
Frequency response 10Hz to more than 200 KHz \pm 1dB
Max. supply voltage 45v (4 Ω to 8 Ω speakers) (50v 15 Ω speakers only)
Min. supply voltage 9v
Load impedance — minimum : 4 Ω at 45v HT
Load impedance — maximum : safe on open circuit

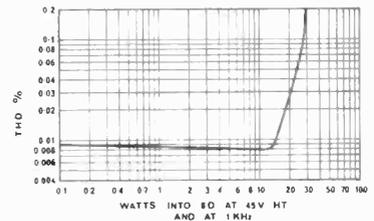

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave deluxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stocklists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

sinclair

SINCLAIR RADIONICS LTD., R.O. London Road, St. Ives, Huntingdonshire, PE17 4HJ (Phone St. Ives 4311) Reg. No. 699483 England

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit



Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—**Input sensitivities:** Radio — up to 3mV Mag p.u. 3mV: correct to R.I.A.A. curve —1dB 20 to 25,000 Hz. Ceramic p.u. — up to 3mV Aux — up to 3mV **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB **Tone controls:** TREBLE+12 to —12dB at 10KHz: BASS +12 to —12dB at 100Hz **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed **£9.98**

Project 60 Stereo F.M. Tuner



The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—**Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz **Sensitivity:** 7µV for lock-in over full deviation. **Squelch level:** Typically 2µV. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10Hz — 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2µV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC, make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak), 6–8Ω. **Frequency Response:** 5Hz to 100KHz ±1dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (20V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual **£2.98** Post free

Power Supply Units The new PZ.8 Mk.3



The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK 2 amplifiers are used. Nominal working voltage—45

PZ 8 Mk 3—£7.98

(Mains transformer, if required) £5.98

PZ 5 30v. un stabilised

(not suitable for Project 60 tuner) £4.98

PZ 6 35v. stabilised

(not suitable for IC. 12) £7.98

Project 605



the easy way to
buy and build
Project 60
without
soldering

Project 605 in one pack contains one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free
All you need for a superb 30 watt high fidelity stereo amplifier

£29.95

Order form

Please send

I enclose cash/cheque/money order.

Name _____

Address _____

PW7

SINCLAIR RADIONICS LTD., R.O. London Road,
St. Ives, Huntingdonshire, PE17 4HJ

sinclair

ADD 10% V.A.T. ON PRICES ON PAGE OPPOSITE AND ABOVE

Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Books and Publications

Radio BOOKS

Handbk of Transistor Equip and Substitutes	45p
Handbook of Tested Transistor Circuits	45p
Rad & Electr Colour Codes and Data Chart	20p
Hi Fi PA & Disco Amplifier Design Hbk	80p
Boys Bk of Crystal Sets and Simple Circuits	23p
How to make FM & TV Aerials, Bands 1,2,3	23p
Radio Servicing for Amateurs	25p
High Fidelity Loudspeaker Enclosures	25p
Practical Tape Recording Handbook	35p
Practical Stereo Handbook	35p
Practical Radio Inside Out	45p
Transistor Circuits Manual No. 1	20p
Transistor Circuits Manual No. 2	20p
Coil Design and Construction Manual	35p
Radio TV and Electronics Data Book	30p
Transis Circuits for Radio Controlled Models	45p
Pract Transistor Audio Amplifiers, Book 1	25p
Transistor Test Equip and Servicing Manual	30p
Handbook of Simple Transistor Circuits	40p
Modern Transistor Circuits for Beginners	45p
Sound and Loudspeaker Manual	55p
Resistor Colour Code Disc Calculator	15p
Manual Transistor Audio Amplifiers	45p
Practical Car Radio Handbook	35p
Radio TV and Industrial Tube & Valve Equip	45p
Practical Transistor Novelty Circuits	45p
Television Servicing Vol. 1	85p
Television Servicing Vol. 2	85p
Television Servicing Vol. 3	70p
Television Servicing Vol. 4	95p
Using an Oscilloscope	80p
Servicing Transistor Radio Receivers	85p
Television Timebase Circuits	£1.10p
Pal-D Colour Receiver Questions & Ans	78p

All prices include postage & packing
FREE lists of other titles avail on request. Send to

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

DENCO CLACTON LIMITED

355-7-9 Old Road

Clacton-on-Sea, Essex

Catalogue 20p post paid

S.A.E. all enquiries

TRANSISTOR DATA

THE INTERNATIONAL TRANSISTOR DATA MANUAL

1973 EDITION is now ready. Data on upwards of 18,000 transistors of international origin. £5-25 plus 35p post & packing in the UK. Brochure available. Order direct from

SEMICON INDEX LTD.

Freeport, Wokingham, Berks. RG11 2AY.

DIGITAL COMPUTER LOGIC and Electronics. Four volume self-instructional course. £2-95 including p & p. Money back assurance. Cambridge Learning (PW), 8a Rose Crescent, Cambridge.

Service Sheets

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS) Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"
Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

Aerials

BAINES FOR HIGH FREQUENCY AERIALS

VHF/UHF MULTIBEAMS BY 7 BEAM. Postage paid MBM 10 £2-20, MBM 18 £2-90, MBM 30 £3-90, MBM 46 £3-90, MBM 70 £11-00, SBM 4 £4-60, SBM 6 £6-95, 75 to 300 ohm Balun £1-00, Aerial Rotators £22-00. VHF/UHF Masthead Amplifiers—Gryphon complete with power units. Postage paid.

A/1053 Single Stage £5-75, A/1059 Twin Stage £7-75, A/1057 Wideband £7-75, A/1083 FM £5-75, FM2 Setback £4-75 complete.

Accessories: SAE for List. Co-ax 5p and 9p. Please add 10% for VAT.

11 DALE CRES., TUPTON, CHESTERFIELD S42 6DR
Telephone 863755

For Sale

MORSE MADE EASY!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only £3-30, Complete Course £4-50 (Overseas £1-00 extra) details only, 4p stamp. 01-660 2898
G9HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

TV LINE OUTPUT TRANSFORMERS

Tidman Mail Order Ltd., 236 Sandycombe Rd., Richmond, Surrey. TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

SPARES, new, for Philips and some other Cassette Recorders. SAE enquiries. Harvey, 94 Derby Lane, Liverpool L13 3DW.

BACK ISSUES Practical Wireless for sale May 1966-Oct. 1972. Complete £12 o.n.o. 01-223 1986 (London).

APPROXIMATELY Three Thousand new boxed valves as Lot For Sale. For details: write to Cosmo Television Services, 427 Shields Road, Glasgow S.1.

LARGE QUANTITY Test equipment, receivers, transceiver, meters, variacs, P.S.U.S. over 1,000 items for immediate disposal. S.A.E. Plus 25p refunded on purchase over £2-00. F. J. C. Colnemill, Alvington, Lydney, Glos.

Radiospares Components at Competitive Prices

3 W Audio Amp. IC £2-92 ea. (2 off for stereo).
Heat Sink for above 23p ea. (2 off for stereo).
Stereo P.C. Board for above 63p
14 Resistors for above 28p
6 Potentiometers for above £2-44
30 Capacitors for above £4-18
Rectifier type 41A for above £1-18
Hygrade Fil. Transformer for above £1-95
8 ohm Longthrow speaker £4-55 ea. (2 off for stereo).
Audible warning device, 2-6 KHz mod. tone, 10-18V £1-89

Stripboards—similar to Veroboard,
Type A 0-15 in. pitch 85p
Type B 0-10 in. pitch 96p
T05 Voltage Regulator, 2-37 V at 150 ma. £1-76
Numerical Indicator Tube, 7 seg. filament, 5V £2-64
Transistors BC117, BF594, BC109 23p ea.
BC107, BC108 22p ea.
BF597, BC478, BFY50, BFY51, BFY92 24p ea.
BU103, Vcc 1500v, 10W, 4-7.5 MHz £1-90 ea.
BU106/02 Vcc 1700v, 10W, ft 7-5 MHz £3-23 ea.
2N3054 (NPN Type) £1-06 ea.
2N3054 (PNP Type) £2-05 ea.
2N3055 (NPN Type) £1-18 ea.
2N3055 (PNP Type) £2-35 ea.

Prices include VAT. Add 20p post and packing for orders under £5. Terms: Cash With Order Only

All R.S. COMPONENTS Available from M. A. Austin & Co.

14A Grosvenor Square, South-hampton, Hampshire.

Wanted

TOP PRICES PAID FOR NEW VALVES

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),

367 Kensington Street, Bradford 8,

Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

P.W. October 1964 to October 1965 inclusive. Milne, 7 Healey Street, N.W.1.

CLASSIC MUSIC COMPOSER building a complicated electronic organ and synthesiser needs drawings and know-how for sustain, slew, formants, filters, other effects. Robert Lombardi, Rue Nagelmackers, 14 4000-Liege, Belgium.



TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commencing Sept. 10th. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. A8/, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**

RADIO, TV, RTEB Certs., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book—FREE. BIET (Dept ZL BPW 29), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

CIE, AMSE, City & Guilds, etc. Thousands of exam successes. Postal courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept ZL BPW 40), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Situations Vacant

HARROW COLLEGE OF TECHNOLOGY AND ART

TECHNICIAN: SCHOOL OF PHOTOGRAPHY

Up to £1,980

A Technician/Engineer in television and sound is required for a new post in the Film and Television Department. Duties will include the technical operation and routine maintenance of a C.C.T.V. Studio requiring electronic and mechanical skills and knowledge in the television field. Relevant City and Guilds or H.N.C. qualifications are desirable and further in-service training will be considered.

Unless otherwise stated all the above positions involve a 35-hour week (Monday to Friday).

Application forms from The Registrar, Harrow College of Technology and Art, Northwick Park, Harrow, Middx. HA1 3TP (864 4411 Ext. 31).

Receivers and Components

TAPE HEADS

For valve and transistorized recorders from £2 ea.

Send stamp for lists
R.D.I. Ltd.
Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

INTEGRATED CIRCUIT and FET modules for construction of low-cost receivers, converters, pre-selectors, etc. SAE details.—P. R. Gollidge, Glen Tor, Torrington, Devon.

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0.47µF:	±6%	80p:	±2%	40p:	±1%	50p
1.0µF:	±8%	40p:	±2%	80p:	±1%	80p
2.2µF:	±8%	50p:	±2%	80p:	±1%	70p
4.7µF:	±8%	70p:	±2%	80p:	±1%	11.1µ
5.6µF:	±6%	85p:	±2%	£1.15:	±1%	£1.50
10µF:	±6%	£1.10:	±2%	£1.40:	±1%	£1.60
15µF:	±8%	£1.60:	±2%	£2.10:	±1%	£2.70

TANTALUM BEAD CAPACITORS—Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (78 capacitors) £5.

NEW!—TRANSISTORS. BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178—35p each or 3 for 95p.

POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1. IN916—9p each, 6 for 50p, 14 for £1. IS44—5p each, 11 for 50p, 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5 mA. All new and marked. Price 8p each, 6 for 50p, 14 for £1.00. Special offer 6 off each voltage (66 zeners) £4.25

RESISTORS. Carbon film ½W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS. 0.1µF, size 1½in x ½in, 25p; 0.25µF, size 1½in x ½in, 30p; 0.47 and 0.5µF, size 1½in x ½in, 35p; 1.0µF, size 2in x ½in, 45p; 2.0µF, size 2in x ½in, 75p each.

SILICON PLASTIC RECTIFIERS 1.5 Amp Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

3p post and packing on all orders below £5.

Please add 10% VAT to all orders.

MARCO TRADING

Dept. W.8. The Maltings, Station Road, Wern, Salop

World-wide acclaim, the incomparable

GLOBE-KING

V.H.F. & S.W. KITS

Precision standard, inexpensive, low-cost valve and transistor Kits for Short-Wave 10-350 m. V.H.F. 80-180 Mc/s. Ideal for beginners with unique "Easy-Build" diagrams and simplified instructions. Send to-day for free literature price list and order form, kindly enclose stamped addressed envelope (Overseas: Int. Reply Coupon). Direct to the sole manufacturers:

JOHNSONS (RADIO)
SHAW ST., WORCESTER.
WR1 3QQ

Please note new address, city centre. Pioneers in DX radio—Established for over 30 years.

(A JOHN BANNER COMPANY)

TAPE-HEAD reconditioning service. Guaranteed satisfaction. Send worn head with £2 to: Sara Electronics, Fawkham Avenue, Longfield, Kent.

MINI MAINS TRANSFORMERS 30x30x37mm. Cool, quiet, British. Pri. 220/250V. Type MT3, 3-0-3V rms; 300mA, £1. MT7, 7-0-7V, 120mA, £1. VAT included. Use MT3 for 3V or 6V rectified d.c., MT7 for 9V or 18V. Circuits supplied. Mail order only, UK post 5p per order. Amatronics Ltd., 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

THE

TEXAN

NOW ON DEMONSTRATION



Designer approved Kit £28.50
Instructions only 35p

- Pack 1. RESISTORS 80p
- Pack 2. SMALL CAPS £1.50
- Pack 3. LARGE CAPS £1.40
- Pack 4. SUNDRIES £2.50
- Pack 5. SWITCHES £1.00
- Pack 6. CONTROLS £1.45
- Pack 7. SEMI COND. £8.25
- Pack 8. TRANSFORMER £4.95
- Pack 9. P.C. BOARD £2.50
- Pack 10. CHASSIS, etc. £4.20

Post extra—parts available separately
Send for list and technical spec.

Kits also available for

- ★ Radio Control Systems
- ★ Digital Clock Systems
- ★ Integrated Circuit Amplifiers (to 50W)
- ★ Hi-Fi Pre-amps
- ★ Stabilized Power Supply Units

TELERADIO HI FI, 325 Fore Street, Edmonton, London N.9 01-807 3719
CLOSED ALL DAY THURSDAY

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfds.—4p, 22, 47—4½p. (50V—5p.) 100—5½p. (50V—7p.) 220—6p. (50V—9p.). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p, 0.04, 0.05—3p, 0.068, 0.1—3½p. Polystyrene 63V, E12 series 10 pf.—1,000 pf.—2p, 1,200 pf.—10,000 pf.—3p. Miniature Highstab resistors, 5%, E.12 series—Carbon Film ½W 1Ω—10MΩ (10% over 1 Meg.) Metal Film ½W 10Ω—2.2MΩ and 1W, 27Ω—10MΩ all ¾p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 +p.&p. 10p U.K. only.

Illustrated catalogue of selected kits and components, 20p inc. VAT. P&P free.

ALL PRICES PLUS 10% VAT
Galleon Trading Co.
12, Burra Way,
Coringham,
Stanford-Le-Hope,
Essex. SS17 9DE

Trampus electronic

ALL BRAND NEW, no rejects. Money back warranty. **5V DIGITAL INDICATOR** 0-9D/P sockets and filter £1.45. **LED TYPE 1" 0-BDP DIL** £2.25 ea. **LIGHT EMITTING DIODES**. All with data and panel clip. **TIL 209 1" dia.** 24p. **Red LED type 38p.** **Green 75p.** **INFERA RED beam LED** £1.10. **TGS GAS detector** £1.60. **ULTRASONIC TRANSDUCERS** £2. **DALO PCB resist marking pen** 67p. **Copper board 12" x 6" SRBP** 40p. **FeC etch PAK** 19p. **INTEGRATED CIRCUITS**: with data if required. **IC LITE SWITCH**: Photo amp/trigger 40ma/11-20 relay or TTL 87p. **Dil relay** £1.10.



IC digital clock

MOS/LSI type 28 pin 4 or 6 digit 12/24 hr. Chip with socket **£13**. **PCB** £1.69. **KIT** £21.40. **741 DII** 8 pin 28p. **709 14P**, **DII 28p**, **748 28p**, **710 33p**, **555** **TIMER** mono/stable osc. clock 89p. **REGULATORS**: **1A** 5 to 20V £1.49. **723 57p**. **RECEIVER** ZN414 £1.09. **Mini Rx kit** £1.99. **1310 stereo decoder** for tuners £2.89. **Kit** £2.45. **748 TTL**: (Gates 7400 etc. 15p ea. 7413 27p. 7441 78p. 7447 £1.09. 7490 59p. 7492 67p. 74121 45p. **DIL SOCKETS**: New type 8/14/16 pin 13p. **SEMICONDUCTORS**: **1A** rects. 50V 31p. 400V 8p. **2N3055 32p**. **BC107 7p**. **BC108 7p**. **BC109 7p**. **BC147/8/9 10p**. **BC107/8/9 13p**. **BC177/8/9 15p**. **BC182/3/4 10p**. **BC212/3/4 11p**. **BCY70/72 13p**. **BD131/2 55p**. **BFY50/51/52 13p**. **TIS43 UJT 24p**. **2N706 11p**. **2N2869 12p**. **2N2926 OY 8p**. **2N2646 49p**. **2N3053 17p**. **2N3614 55p**. **2N3702/3/4/5/6/7/8/9/10/11** All 9p ea. **FETS**: **2N3819E 19p**. **2N3819 27p**. **2N3423E 19p**. **ZENERS**: **BZ788 8p**. **SCR** 400V: **1A 29p**. **TRANSFORMER 1A** 6/12V £1. **Resistors 11p**. **450 & 470 mini IF transformers**—Set 3 40p. **CAPACITORS**: Disc 22pf to 0.1 µf 3p. **Electrolytic 25V**: 10, 50, 100 µf. 1000 µf. Presets 5p. **CARBON POTS**: 11p ea. switch + 11p. **Dual 89p**.

FLUORESCENT LIGHTS 12VOLT £2.79

13" x 8 watt fully built with diffuser. 13W £3.79. **V.A.T.** You must add 10% (1/10) to all prices. **FREE CAT. S.A.E.** Data sheets. 8p ea. **P. & P.** 8p **CWO P.O. BOX 29, BRACKNELL, BERKS.**

BUILD THE TREASURE TRACER MK III Metal Locator

- Vancap tuning
 - Excellent sensitivity and stability
 - Weighs only 22oz
 - Speaker and earphone operation
 - Knocks down to only 17in
 - Prebuilt search coil assembly
 - Ministry approved design
 - Thoroughly professional finish
 - You only need soldering iron, screwdriver, pliers and a few nails
 - Completely new design
- Send s.a.e. for leaflet

Complete kit **£9-80** Built tested and guaranteed Post 35p **£13-75**
MINIKITS ELECTRONICS, 35a LANGLEY DRIVE, WAINSTEAD, LONDON EH 2LN. (Mail order only)

TRANSISTOR BARGAINS. High Quality, individually tested. Similar to BC107/8/9, BC168/3, 10 for 30p, 25 for 65p, 50 for £1.05. Package 5p. Mail Order Only. 305 Eccleshall Road, Stafford, Staffs.

BRAND NEW FULL SPEC. DEVICES SATISFACTION OR YOUR MONEY BACK
U.K. ORDERS—ADD 10% V.A.T. to total. **MICROCIRCUITS**: 709 24p; 710 36p; 723 51p; 741 27p; 748 37p; PA230 60p; **FET Op. Amp.** £1.62. **SOLDER CON. IC PIN SOCKETS** 53p per pin. **SOCKETS**: 14 pin DIL HI or LO 12p each. **RECTIFIERS 1A**: 50V 31p; 100V 4p; 200V 4p; 400V 5p; 800V 6p; 1000V 4p. **ZENERS**: BZY88C 2V7 to 33V 8p each. **DIODES**: IN1916 4p; OA90 6p; IN148 4p. **LED Panel Lamp** with Bush and Data 28p. **DALO PCB RESIST PEN** 68p. **TRANSISTORS**: 2N2926 BROWN 5p; 2N3053 15p; 2N3055 35p; 2N3702 10p; 2N3704 10p; 2N3819 26p; 2N4058 12p; BC107A 8p; BC108B 8p; BC109B 8p; BC109C 8p; BCY70 15p; BFY50/51/52 15p; OC44/45/71/72 12p; AF114/5/6/7 14p. (Above prices on May 16th. Check our list.)

JEF ELECTRONICS (P.W.8)
York House, 12 York Drive, Grappenhall, Warrington WA4 2EJ
Mail Order Only.
C.W.O. P. & P. at cost. 10p min. List free.

5-N-CHANNEL FETs 3819E-£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LIMITED
45 Station Road, Gerrards Cross, Bucks.
Mail Order only

TV'S COLOUR TV'S

Reserviced, perfect working order, repolished.
19in. DECCA £110
19in. GEC 2028 £115
19in. THORN 2000 £120
25in. DECCA £125
25in. RBM PHILIPS £130
25in. THORN 2000 £135
One month comprehensive written guarantee. These are cash and collect prices. Delivery quotations by phone

MONO UHF

Fabulous TVs. No rubbish, from good source. Repolished cabinets. Many working. Recent transistorised models. Incl.:
BUSH TV 148U, TV 164, TV 176
PHILIPS style 70 and 210
PYE & ECKO 868 chassis
THORN 950, 1400, GEC Concorde from £12 each
Valve UHF models inc.:
BUSH push button THORNE 850, SOBELL, 1000, etc. from £5

U.H.F. TUNERS

For FERGUSON 850, 900 chassis but adaptable for most D/ST chassis £2.50 each, cwo postage included. Send s.a.e. for lists of tubes, tvs, valves, etc. For England:
TRADE DISPOSALS, 1043 Leeds Road, Bradford, Tel. Bradford 665870
For Scotland:
TRADE DISPOSALS, Unit 5, Peacock Cross INDUSTRIAL ESTATE, 32 Burnbank Road, Hamilton. Tel. Hamilton 29511/2

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gas, pots, etc. Tremendous value. Send £1 + 10p P & P C.W.O. to Caledonian Components, Fosterton Firs, Strathore Road, Thornton, Fife.

TRANSISTOR AMPLIFIER 80p. Vol/Tone Control Panel 75p. 465 K/CS IF Panel 75p. Wavechange-OSC Panel 75p. LW-MW Rod Aerial 25p. Colour Television. Cromax Panels £3.50. IF Panels £3.00. EHT Tripler Panel £1.08. Control Panel ON/OFF + Vol/Brightness Controls £1.00. Archer, 9 Pine Grove, Maidstone, Kent.

VALVE LIST

ALL VALVES FULLY TESTED
One valve postage 3p. Over 5 valves postage paid.

DY86-87	12p	PCF80	5p	6F23	15p
EB91	15p	PCF86	15p	6/30L2	15p
ECC82	10p	PCF805	25p	30F5	10p
ECC85	20p	PCL82	12p	30FL1	20p
ECL80	75p	PCL83	12p	30PL1	20p
EF80	75p	PCL84	12p	30PL13	17p
EF183	10p	PCL85	20p	MANY MORE AVAILABLE	
EF184	10p	PCL86	17p	S & W ELECTRONICS	
EH90	15p	PFL200	25p	114 Burnley Road	
PC86	20p	PL36	20p	Rawtenstall	
PC88	20p	PL504	20p	Rossendale	
PC900	10p	PY800	12p	Lancs.	
PCC84	5p	Y901	25p		
PCC189	75p	U191	17p		
PCC805	15p	U26	10p		

ELEVEN BAND RADIO. SW1-4 (4.30 MHz). Marine. LW, MW, FM. PB (76-86). Aircraft (108-136). PB (148-174). Battery/Mains. BFO. AGC. Squelch Control. Output: 1-3W. 15in x 10in x 5 1/2 in, £66. Eight Band Model, with BFO, £42. Four Band, MW, FM. Aircraft. PB. £15. SAE. Full Lists. Langtons Radio, High Street, ROCESTER, Staffordshire, Tel. 388.

SPECIAL INTRODUCTORY OFFER OF BRAND NEW & MARKED COMPONENTS ALL PRICES INCLUDE V.A.T.

TRANSISTORS: BC107B, BC108A/B/C, BC109B/C all at 8p; BFY50/51 14p; 2N3055 38p. **DIODES**: IN4148 4p; IN914 4p. **CARBON FILM RESISTORS**: 1W 5% 3p each. 30p/50 any mix (220-2.2M) £12.
UNMARKED BARGAIN PAKS: These transistors have been properly tested and are guaranteed to have the specified hfe spreads. Pak of 5, Plastic BC108A hfe 125-240, 25p; Pak of 5, Plastic BC109B hfe 240-500, 25p; Pak of 5, Plastic BC179A hfe 124-240, 25p; Pak of 4, BFY51 20p; Pak of 4, 2N697 20p. **DIODES**: Pak of 5 OA200 20p; Pak of 12 IN4148 20p. **C.V.O. P. & P.** 10p. on orders below £4. Overseas at cost. S.A.E. for lists. Mail Order only. Money back if not satisfied.

ADFOINIC (Dedford PW), 18 YEW LANE ASHLEY, NEW MILTON, HANTS BH25 5BA

FIBREGLASS PRINTED CIRCUIT BOARD 1/2" SINGLE—5p per 12 sq. ins. 30p sq. ft. DOUBLE—8p per 12 sq. ins. 70p sq. ft. ANY SIZE CUT, NO EXTRA CHARGE NO VAT REQUIRED
P. and P. 10p up to 1 sq. ft. 25p up to 4 sq. ft. 57p up to 18 sq. ft.
BRB
17, SOUTHBRECK RISE WORKSHOP NOTTS S80 2UP

ROSLESS SERVICES

GUARANTEED SEMICONDUCTORS FAST SERVICE—LOW PRICES

AC126	13p	BFX84	27p	ZENER DIODES
AC127	13p	BFX85	34p	400mW 5%
AC128	13p	BSX20	16p	3 to 33 volts
BC107	8p	2N930	22p	12p each
BC108	8p	2N1132	27p	1 watt 5%
AF114	18p	2N1711	25p	all voltages
AF115	13p	2N2904	38p	6-8 to 200 volts
AF116	13p	2N2904A	42p	16p each.
AF117	8p	2N2905	44p	
BCY71	3p	2N3708	8p	

ALSO CAPACITORS RECTIFIERS, ETC.
PRICES INCLUDE VAT
CASH .W.O + P.P. 10p TO ROSLESS SERVICES
PARNOLD HALL - HAMSTED ROAD HARLOW - ESSEX

UNUSED RESISTORS and Capacitors 250 of each. Including high stabs and electrolytics. Only £1.50. Trade enquiries invited. 676 Foxhall Road, Ipswich, Suffolk.

COMPONENTS AND HARDWARE, new and used, for P.W. circuits. S.A.E. for list. David Coulam, Tathwell, Louth, Lincs.

TUNBRIDGE WELLS. Components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

Miscellaneous

"AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS"

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5-80 (inc. VAT) NOW (S.A.E. for details) 'MAIL ORDER ONLY'

TO: 'BOFFIN PROJECTS' DEPT. KW2010 4 CUNLIFFE ROAD STONELEIGH, EWELL, SURREY

Darned Electronic Wizardry

by Dewtron (VAT extra)

Famous kits, e.g. waa-waa complete kit £2.95; Puzzle kit £4.75, auto rhythm modules P & P 20p min. Ring Modulator modules £4 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 94 Ringwood Road, Ferndown, Dorset.

BEDFORD ELECTRONICS

2 Grove Place, Bedford
Bedford 51961
YOUR LOCAL
COMPONENTS SUPPLIER

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwick.

Remember the R & E "MEMORY"
Invented 1971

You can leave your Detector to get on with it
Now Modified using latest IC/Solid State
Technology (741C's or LSI Chip)

3 Circuits, details, numerous applications: Baby Alarm, Burglar Recorder/Alarm, UFO All-night Detection; Micrologic Multi-purpose System Circuits, 75p. Numerous other systems, (detection), Map, Predictions, re 1,000 UFOs at Banbury. Details and List send SAE - 5p (refundable with order).

R & E Publications
Highlands, Needham Market, Suffolk.

GLASS FIBRE P.C. BOARD. Large supplies available in single sided one ounce copper 2p per 3 sq. inches (under 1 foot), 75p per sq. ft. (over 1 foot). In double sided one ounce copper 1p per sq. inch (under 1 ft.) £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

CONSTRUCTION AIDS—Screws, nuts, spacers etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd., Stratford on Avon, Warwks.

EXPERIMENTERS! Hundreds of unusual items cheap. 1973 catalogue 5p. Grimsby Electronics, 64 Tennyson Road, Cleethorpes, Lincs. (Mail Order Only).

GM4AGG—The West of Scotland Amateur Radio Society, meets on Friday evenings at 8. Everyone welcome. 81 Virginia Street, Glasgow or Tel: Cumbernauld 26922.

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-UHF £25, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30:—
ECC82, ECL80, E891, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15.

19" UHF/VHF (BBC2) £6.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—65p

½ to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Capacitors up to 500MFD—£1.10 (our choice).

BARGAINS PARTS

Transistor UHF Tuners—£2.00, 500k-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2.25. Brand New Transistors BF115, BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order
Money back guarantee. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury,
Lancs. Tel. Rams 3036

SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER



WITH LIGHT DIMMER

Max. load 2kW. at 250V. A.C.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price £7.90 inc. VAT

EXTRA FACILITIES. Push-button for Manual Pulsing 25p extra. Photocell for turning on the lights as the ambient light decreases, 75p extra.

3 CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested. Price £3.50 inc. VAT

OIL WHEEL PROJECTOR

Build your own using our



MULTI-COLOURED OIL WHEEL AND MOTOR KIT

Suitable for mounting on virtually all Slide Projectors.

Kit contains:

- ★ 6" dia. or 4" dia. OIL WHEEL (please state size required when ordering).
- ★ Suitable Miniature mains motor.
- ★ Full instructions.
- For Professional Discotheque use or home enjoyment. Price £7.15 inc. VAT

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.
- 1 500 Carbon resistors, ½, 1, 1, 2 watt.
 - 2 100 Electrolytic Condensers.
 - 3 250 Ceramic, Polystyrene, Silver Mica etc. condensers.
 - 4 250 Polyester, Polycarbonate, Paper, etc. condensers.
 - 5 25 Potentiometers, assorted.
 - 6 250 High-stab, 1%, 2%, 5% resistors.
 - 7 50 Assorted Tagstrips.
 - 8 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
 - 9 25 Assorted switches, rotary, lever, micro, toggle, etc.
 - 10 50 Preset Potentiometers.

All components new and unused.
£1 + 25p p.p. per pack, £5 for 5 packs p/Free

C. T. ELECTRONICS

Mail Order, Retail Shop, Components—
287 Acton Lane, LONDON, W4 SDG 01-994-6275

Warehouse, Test Equipment, Surplus Goods—
20-24 Beaumont Road, LONDON, W4

Audio Accessory Shop, Components—
17 Turnham Green Terrace, LONDON, W4

D.I.Y. TECHNICAL BOOKS

RADIO RECEIVER SERVICING GUIDE	£1-90
101 EASY HAM RADIO PROJECTS	£1-50
101 EASY AUDIO PROJECTS	£1-40
RAPID T.V. REPAIR (224 pp)	£1-30
ELECTRONIC GAMES AND TOYS YOU CAN BUILD	£1-40
PAL RECEIVER SERVICING GUIDE (280 pp)	£3-50
BASIC ELECTRICITY (6 VOLUMES, 630 pp, 600 ILLUS.)	£5-10
ELECTRONIC DESIGNERS HANDBOOK	£3-40
BASIC ELECTRONICS (6 VOLUMES, 674 pp, 700 ILLUS.)	£5-10
ELECTRICITY, ELECTRONICS MADE SIMPLE	Each 95p
RADIO HANDBOOK (896 pp)	£6-50
1-2-3-4- SERVICING STEREO AMPLIFIERS (240 pp)	£2-50
MAKING & REPAIRING TRANSISTOR RADIOS, ADVANCED RADIO CONTROL, EASY WAYS TO SERVICE RADIO RECEIVERS, BEGINNERS GUIDE TO T.V. REPAIR, PRACTICAL HAM RADIO PROJECTS, HI-FI PROJECTS FOR THE HOBBYIST	Each £1-00
HOW TO BUILD SPEAKER ENCLOSURES	£1-50
HI-FI STEREO SERVICING GUIDE, 99 ELECTRONIC PROJECTS, 99 WAYS TO IMPROVE YOUR HI-FI	Each £1-50
ELECTRONICS FOR THE BEGINNER, T.V. SERVICING MADE EASY, 101 QUES. & ANSWERS ABOUT AM, FM & SSB	Each £1-75
HOW TO REPAIR SMALL APPLIANCES	£1-20
ADD 10% FOR POSTAGE AND PACKING	
WHEEL (PWJ), 41A ADELAIDE GROVE, LONDON, W12	

ELECTROLYTIC CAPACITORS $\mu\text{F}/\text{V}$ 2000/50, 2500/50, 5000/50, 10000/50, 12500/50
All at 50p each, post paid, 5000 μF , 70V 4½" x 2½" 85p.

SPECIAL OFFER ERIE DISC CERAMIC CAPACITORS. 0.1 μF 500V, 10 off 20p.
100 off £1, 500 off £4, 1000 off £6.

PAPER/BLOCK/MOTOR-START CAPACITORS:

	£		£
1 μF 350V AC	0-80	6 μF 440V R.M.S. Block	1-00
1-5 μF 300V R.M.S. Block	0-40	6 μF 440V R.M.S. 5½" x 1½"	1-50
2 μF 2500V D.C. Block	1-75	6 μF 250V Polyester	0-85
3 μF 100V A.C. Polyester	0-50	8 μF 300V A.C. Block	1-50
3-5 μF 250V A.C. 2½" x 1½"	0-35	10 μF 250V R.M.S. Block	1-50
4 μF 250V A.C. 2½" x 1½"	0-40	15 μF 2-5kV D.C. Block Photoflash 3-50	
		20 μF 275V R.M.S. 6½" x 2½"	£1-20

PLESSEY VIBRATORS, Type 1214 50p

SUBMINIATURE PLUG-IN CRYSTALS FOR RADIO CONTROL, 26.96MHz and 27-025MHz, 70p each.

Add 10% V.A.T.

ELEKON ENTERPRISES

224a St Paul's Road, Highbury Corner, London N1

<p>TRANSISTORS</p> <p>Output Transistors</p> <p>BD 112 25p OC 36 50p BD 145 25p</p> <p>Small Signal N.P.N.</p> <p>BC 108 10p BC 109 10p BF 194 10p</p> <p>Transmitting Types</p> <p>BFR 64 £1 BKY 89A £5 BLY 93A £9</p> <p>Microwave Varactor Diodes</p> <p>BXY 27/28/32/35/36/37/38/39/40/41 . . . £1</p> <p>Microwave Detector</p> <p>CAY 10 £5</p> <p>Microwave Mixer</p> <p>CL 7331 £20</p> <p>Microwave Gunn Effect Oscillator</p> <p>CL 8370 £10 CL 8380 £10 CL 8390 £10 CL 8470 £40</p> <p>Microwave Tunnel Diodes</p> <p>AEY 13 £5 AEY 16 £10</p> <p>R.F. Transistors</p> <p>BF 180 20p BF 194 10p AF 124 20p</p>		<p>Field Effect Transistors</p> <p>BFW 12/13/14 25p</p> <p>Micro-miniature N.P.N.</p> <p>BFS 18R 10p LDA 400/403/450/452 10p</p> <p>Infra-red Transmitters</p> <p>CQY 11A £4 CQY 12A £10</p> <p>Light-sensitive Trans.</p> <p>OCP 70 20p</p> <p>Complementary Drivers, 2 watts (per matched pair) 30p. a pair.</p> <p>INTEGRATED CIRCUITS</p> <p>TBA 500 Luminance I.C. £1 TBA 510 Chrominance I.C. £1 TEO 101 64bit Memory £1 7400 12p 7401 12p 7410 12p 7420 12p 7440 12p 7453 12p 7470 24p 7472 24p 7473 32p 7474 32p 7482 88p 7483 88p 7490 95p 7491 78p 7492 58p 7493 58p 7495 88p 5400 10p 6404 10p</p>		<p>NEW! NEW! NEW! NEW!</p> <p>An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly. Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner. Light sensitive aerosol spray £1.00 plus Developer and Etchant 50p postage</p> <p>NEWER THAN NEW!!!</p> <p>Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.</p> <p>75 mm x 100mm 33p 150mm x 100mm 66p 150mm x 200mm £1.32</p> <p>Epoxy-Resin</p> <p>75mm x 100mm 22p 100mm x 150mm 44p 150mm x 200mm 88p</p> <p>Copper-clad Fibre Board</p> <p>12in x 6in 45p</p> <p>Copper-clad Epoxy Resin Board</p> <p>12in x 6in 25p</p> <p>MULLARD POLYESTER CAPACITORS 500,000 in STOCK!!!</p> <p>.001µf .0018µf .0056µf .015µf .0012µf .0022µf .01µf .033µf .0015µf .0027µf .012µf .082µf</p> <p>20p dozen; 75p-100; £5-1,000; £40-10,000 .15µf .18µf .22µf .68µf 20p dozen; £1-100; £6-50-1,000; £50-10,000</p> <p>VEROBOARD</p> <p>2 1/2in x 1in x 0.15in 6p 3 1/2in x 2 1/2in x 0.15in 16p 3 1/2in x 3 1/2in x 0.15in 20p 5in x 2 1/2in x 0.15in 20p 5in x 3 1/2in x 0.15in 28p 17in x 2 1/2in x 0.15in 55p 17in x 3 1/2in x 0.15in 74p 3 1/2in x 2 1/2in x 0.1in 21p 3 1/2in x 3 1/2in x 0.1in 24p 5in x 2 1/2in x 0.1in 23p 5in x 3 1/2in x 0.1in 28p</p> <p>Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0.1 or 0.15) 36 for 18p. Special Offer Pack consisting of 5 2 1/2in x 1in boards and a Spot Face Cutter—50p. *ODDS & ENDS"—1p sq in.</p> <p>ERIE MONOLITHIC CERAMIC CAPACITORS</p> <p>3p each; 20p dozen; £1.75 per 100</p> <p>20pf 68pf 560pf 15pf 100pf 620pf 12pf 150pf 680pf 33pf 220pf 1,000pf 39pf 330pf 47pf 470pf</p>			
<p>£1 100 WATT RESISTORS 100 CERAMIC CAPACITORS 100 DIODES</p> <p>POSTAGE 15p PACK No. 1</p>		<p>£1 1 VERO-BOARD CUTTER 5 1/2 in. x 1 in. x .15 BOARDS 30 SQ. IN. "ODD PIECES" VERO</p> <p>POSTAGE 15p PACK No. 3</p>		<p>£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108 ETC.</p> <p>POSTAGE 15p PACK No. 5</p>		<p>£1 6 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS & CAPACITORS</p> <p>POSTAGE 25p PACK No. 7</p>	
<p>£1 100 RESISTORS 100 CERAMIC CAPACITORS 100 POLYSTYRENE CAPACITORS</p> <p>POSTAGE 15p PACK No. 2</p>		<p>£1 100 RESISTORS 100 CERAMIC CAPACITORS 80 MULLARD POLYESTER CAPACITORS</p> <p>POSTAGE 15p PACK No. 4</p>		<p>£1 1 TRANSISTORISED SIGNAL TRACER KIT 1 TRANSISTORISED SIGNAL INJECTOR KIT</p> <p>POSTAGE 15p PACK No. 6</p>		<p>£1 100 RESISTORS 100 CAPACITORS (ASSORTED TYPES)</p> <p>POSTAGE 15p PACK No. 8</p>	

POSTAGE (MINIMUM) 15P PER ORDER

ALL GOODS PLUS 10% V.A.T.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd. Stratford-on-Avon, Warwick.

LADDERS 24 1/2 ft £9.80. Carr 80p. (Please add 10% V.A.T. to total order). Leaflet. Home Sales Ladder Centre, (WLS) Haldane, Halesfield (1) North, Telford, Salop. Tel: 0952 586644.

CIRCUIT DIAGRAMS

R1155, B.F.L.N. R1392, R1475, B40, 52 Rx, R220, all 66p ea. R4187 Rx set of circuits, etc. £1.10. R107 Rx 88p. R209 Rx circ. & notes £1.21, R210 £1.10, R216 £1.10, CR100 £1.10, 19 set 88p, 31 set 88p, 88 set 88p, Wavemeter D No. 2 £1.10 CT38 66p, Sig Gens TF144G 66p, TF801a 88p, Scope 13A 66p. CT316 (CD518) 66p, Cossor 1035 Mk 1, 2 & 3 all 66p ea. 1049 Mk 3a 66p, Scope CT52/84 with notes £1.32. CD513-2 3 shts £1.65, CD1014-2 3 shts £1.65, Rx3673 66p, Ind CRT26 66p.

AMERICAN types ARR-2 55p, RxInd/APN-9 55p, AR88D & AR88LF £1.10 ea, Tx/Rx BC634/5 88p, USM-24 £1.65, TS-34 88p, OS-8 66p, Dumont 208 66p, TS-382 88p, TS-413 £1.65, RX36736 6p, Ind CRT26 66p.

The above prices inc. post and VAT charges, where available values are supplied. Full manuals available on some of above, SAE with enquiry.

A. H. SUPPLIES

57 Main Road Sheffield S9 5HL
 Telephone 444278 (0742)

GETTING BORED WITH ELECTRONICS

Some things are repetitive, once you have built an astable multivibrator; they tend to get boring—tried a 555 timer? It works in mono or astable modes for long or short pulses (95p). How about building a radio tuner for your simple player, the ZN414 chip makes this simple (£1.10). LEDs? We have a fantastic choice—LED lamps—TIL209 or HP4480, 4 for £1, 50 for £10; large lamps (HP4880), 35p each, 50 for £15, RED and GREEN LEDs £1 per pair. LED displays—TIL302 (or similar) £2.50 each, TIL312 (similar to MAN4) £2 each—limited quantity. TIL360 6 digit package £15, DL34 four digit package £10, DL62 (1/2") £6.50. Phosphor diode displays DG10 or DG12 £2 each.

CLOCKS CLOCKS CLOCKS
 Bywood is now foremost in the LSI clock chip market (who else has four different clock chips in stock with two more on order!). MM5311—the original—£11.50. MK5017AN with alarm and radio controls £15.50. MK5017AA with alarm or MK5017BB with calendar, either of these two is offered with a PCB, socket and suitable displays (4 DG12s) at £24.

Don't get bored, if none of the above fascinate you how about liquid crystal displays, DVM chips, etc! This technology, is here to stay, Bywood have got it or can get it—give us a try.

VAT. All prices above EXCLUDE VAT, add 10% P. & P. Please add 10p post and packing.

You can have clock data sheets for a S.A.E. or our 1973 catalogue (2nd issue) for 15p. (And we haven't even mentioned our calculators yet—but they are in the catalogue).

You may phone us for help on 0442-62757 and you can use your ACCESS card for phone, or personal purchase—Service from Bywood!

BYWOOD

ELECTRONICS
 181 EBBERNS ROAD, HEMEL
 HEMPSTEAD, HERTS. 0442 62757

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP
(as in 'W.W.' July '72)

MOTOROLA MC1310P EX STOCK DELIVERY
SPECIFICATION:-Separation: 40dB 50Hz-15kHz. Distortion: 0.3% I/P level: 560mV rms. O/P level: 485mV rms per channel. Input Impedance: 50kΩ. Power requirements: 8-12V at 16mA.
Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB (printed and fitted), Resistors, I.C.s, Capacitors, Preset Pcm, & Instructions.
ONLY 3£-40 WHY PAY MORE! post free.

LIGHT EMITTING DIODE (Red)
Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions.
ONLY 29p plus p.p.

MC1310P only £2-77 plus p.p. 6p
NOTE:-As the supplier of the first MC1310P decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.
V.A.T.:-From April 1st add V.A.T. at the standard rate to all prices.

Fi-Comp Electronics

BURTON ROAD, EGGINTON, DERBY, DE6 6GY

If you have difficulty in obtaining

PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£2.65) to:-

**Subscription Department,
Practical Wireless,
Tower House, Southampton Street,
London, WC2E 9QX**

FELSTEAD ELECTRONICS (PW 71) LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only—No C.O.D. or Caller service. Charges (Min. 7p) in brackets after all items apply to G.B. and Eire only. Regret orders under 30p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas, include Post and Channel Island. Orders less 10% off prices below, which include V.A.T. including Eire and Channel Island. British Mylar available: ST AND LD 45 600t, 40p. 51" 900H. 55p. 7" 1200t. 82p. LONG LEY 15" 900F. 55p. 51" 1200t. 82p. 7" 1800H. 1£. (Charges for 5" and 51", singles 9p, two to four 8p each; five and over 39p the lot. For 7", one or two 11p each reel, 3, 4 and 5 reels 33p the lot. 6 reels and over 39p the lot.) Other sizes and accessories in list. **CASSETTES**, Two types, Both in Library Cases, C60 33p, C90 48p, C120 72p. Deluxe Types: C50 55p, C90 72p, C120 88p. (Charges for both types, under 5, 9p. Above 5, 17p. Above 9, 25p. Above 17, 33p. Above 25, 41p. Above 33, 49p. Above 41, 57p.) **AMMETERS** with standard fittings and stylus. Stereo-compatible Mono GP91/8C 89p; STEREO GP93 1£.35, Stereo Ceramic GP94 1£.75. (All at 7p each.) Comparatives shown in List, with more types inc. Sonotone 9TAHC, Stereo Ceramic Diamond 1£.70 (7p). **DIAMOND STYLII**: single tip types: Acos GP37, GP69, GP65/67, GP71, BSR T8/LP/ST; COLLARO O.P. and DC284, GARRARD G2, G28, GCS10, GCE12, RONETTE BF40, O.P. and T. PHILIPS 3301 (3060, 3065, 3302, 3304), 3010/12/13/16, SONOTONE 191/207 ALL AT 35p each (7p). **SAPPHIRE 16p** (7p) DIAMOND DOUBLE TIP TURNOVER TYPES (78 sup. on other side). For Acos GP78 & GP79 for cartridges GP93, GP94 etc.) GP93C (for stereo compat. types) GP104 BSR 814 (873, 875, 879 (ST), 871/2/14/15, SONOTONE 8TA, 9TA, 9TAHC. PHILIPS 3306 3310, 3224, 3228/22 GP28, GARRARD GCM21, and 22, GCS23, GK825 and 26, GCM21T and 22T, GCM24T GCS23, GK825T and 26T, GCM31, GCS36, GC835, GCS38, K840A, K841B/ETC. ALL AT 88p (7p). **SAPPHIRE 32p** (7p). **DOUBLE DIAMOND STYLII**: same dia 814/LP tip each side: no 78) All types 1£.35 (7p). **SAPPHIRE DOUBLE ST/LP**, TIPPED 32p (7p). **DIAMOND STYLII GOLDRING REPLICEMENTS**: G800, G800H & G850, £2.25 each, G800E, £3.75 (8p each). **PICK-UP WIRE**: super thin flex screened, sheathed TWIN 7p per yard, 4-core 13p per yard (either up to 6 yds. 7p). Over, charges paid. **MICROPHONES**: CRYSTAL: LAPEL 15", clip/hand, lead 3.5mm jack plus 39p (9p). CM20 Cream Plasti hand 58p (9p). "MIC 45". Curved metal hand grip 1£.10 (11p) ALL with leads. **DYNAMIC**: Excellent Mike. 50K Ω, only 31" long, black/chrone, switched, lead with 2.5 and 3.5 mm jack plugs 1£.37 (9p). Cardoid Ball, 50K/600 Ω built in volume control, on/off switch, special 20' lead, the value at 200 (33p); Uni-dir mesh ball 50K/600 Ω jack plug cable, adaptor, £5.28 (33p); Omni-dir. Ball mesh, 50K, cable adaptor, £2.75 (25p) £4.89 (33p each). **SPEAKERS**: Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) £2.06 (33p) or pair for stereo £4.65, charges paid. **SMALL 21"**, 3 Ω, 8 Ω or 64 Ω (state which) 41p (9p). More speakers in List. **HEADPHONES**: High resistance 2000 Ω adjustable 1£.10 (11p). **EARPIECES**: with lead and min. 2.5mm or 3.5mm (state which) jack plug. **MAGNETIC 12p**. CRYSTAL (3.5mm plug only) 28p (up to 6 for 9p any size). **SCORING IRON**: Shim stock. (British high speed, 81", all parts replaceable, highest quality, fully guaranteed 1£.29 (11p). **TRANSFORMERS**: Built-in 11 x 11 x 12mm. OUTPUT (3 Ω for OCT2, etc.) 16p or DRIVER 17p (Up to 12 for 7p). **CONNECTING WIRE**: Packs of 5 coils, each coil 5yds. Asss. cols. **SOLID CORE 16p** (7p). **FLEXIBLE CORE 18p** (9p). **RETRACTABLE FLEXIBLE LEADS (CURLIES)** with phono plug each end, or phono plug one end, phono socket at the other (state which) 6ft. 30p, 12ft. 58p (each 7p). **VIBRATORS**: 12V/4 pin non-synch 12H/D4, 21" ex. pins, 38p. SAME but 31" ex. pins, 12V/4 pin synch. (12S/17) 21" ex. pins, 72p (9p any type). **MAINS BATTERY ELIMINATORS**: Two models, both 240v A.C. input. Suit most radios and cassette recorders/players with front switch, pilot lights, mains and output leads Model SC, 3, 6, 7 & 9v 400mA, stabilised with multi-output adaptor £5.50 (35p) Model N.R. has additional 12v output and is 500mA £6.00 (35p).

OUR LIST (see heading) has added to the above items Cartridge and Stylus Comparison Special Non-repeatable Offers, Aerials, Dials, Transistors, Multi-Leads, Plugs, Socket of many types, Speakers, Volt Controls, Multi-testers, Mike Inserts, Neon Indicators STEREO Headphones, Pocket Screwdriver Testers, Tel. Pick-ups, Wire, Cable, etc., etc.

INDEX TO ADVERTISERS

A.H. Supplies	324, 382
AdFonic	380
Antex Ltd.	293
Arrow Electronics	367
Audionic	380
B.R.B.	380
B.H. Component Factors Ltd.	292
Baines, R.	378
Baker Loudspeakers Ltd.	292
Bedford Electronics	381
Bentley Acoustic Corporation Ltd.	344
Bernard, Gerald	352
B.I.E.T.	306, Cover iii
Bi-Pak Semiconductors	301, 302, 303
Bi-Pre-Pak Ltd.	363
Boffin Projects	380
British National Radio and Electronic School	288, 343
Broadway Electronics	344
Bull, J. (Electrical) Ltd.	359
Bywood Electronics	382
C.C.I.L. Ltd.	306
C.T. Electronics	381
Caranna, C.	378
Childmead Ltd.	348
Chromasonic Electronics	347
Colomar Electronics Ltd.	360
Comet High-Fidelity Discount Warehouses	308, 309
Control Data Institute	360
D.E.W. Ltd.	381
Dabar Electronic Products	364
Denco (Clacton) Ltd.	378
Discosound	305
Douglas Electronic Industries Ltd.	373
Electrokit	292
Electronic Mail Order	381
Electronic Design Associates	344
Electrospares	372
Electrovalue	323
Elekon Enterprises	381
Elvins Electronic Musical Instruments	372

Felstead Electronics	383
Fi-Comp Electronics	383
Francis, J.J. Ltd.	298
Galleon Trading	379
Gladstone Radio	352
Greenweld Electronics	372
HAC Shortwave Products	328
Harrow College of Technology and Art	379
Harverson Surplus Co. Ltd.	375
Heath (Gloucester) Ltd.	304
Henry's Radio Ltd.	Cover ii, 355
Home Radio (Components) Ltd.	310
I.C.S.	352
I.L.P. (Electronics) Ltd.	295
Imhof	324
Integrex Ltd.	300
Jef Electronics	380
Jermyn Industries	299
Johns Radio	294
Johnson (Radio)	379
K.V.A. Electronics	328
Kensington Supplies	378
Keytronics	294
Lasky's Radio Ltd.	306
Lewis Radio	348
Linear Products Ltd.	294
London Computer Operators Training Centre	292
London Electronic College	379
Magtor Ltd.	294
Maplin Electronic Supplies	298
Marco Trading Ltd.	379
Milward, G.F.	382
Minikits Electronics	380
Morse	378
Multicore Solders Ltd.	304
Mullard Ltd.	304

Padgetts Radio Store	304
Partridge Electronics Ltd.	364
Piccadilly	Cover iv
Pembridge College	324
Phonosonics	352
R.D.I. Ltd.	379
R.E. Publications	381
R.S. Components	378
Radio Component Specialists	351
Radio Book Service	378
Radio Exchange Co. Ltd.	327
Radio & T.V. Components (Acton) Ltd.	296, 297
Radio Society of Great Britain	374
Readers Radio	348
Redhawk Sales	380
Riversdale Electronics Ltd.	364
Rossless Services	380
RSC (Hi-Fi Centres) Ltd.	290, 291
R.S.T. Valve Mail Order Co.	374
S. & W. Electronics	380
Saxon Entertainments	311
Semicon Index Ltd.	378
Sinclair Radionics Ltd.	376, 377
Smith, G.W. & Co. Ltd.	368, 369, 370, 371
Surplronics	310
Swanley Electronics	328
Teleradio Co. Ltd.	379
Thacker, A.H. & Sons Ltd.	300
Tidman Mail Order	378
Trade Aids	373
Trade Disposals	380
Trampus Electronix	380
Trannies	307
Tuac Ltd.	373
West London Direct Supplies	373
Weyrad (Electronics) Ltd.	306
Wheel	381
Wilmslow Audio	300, 328
Xeroza Radio	344
York Electronics	310
Z. & I. Aero Services	384

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 12p in £ for postage and handling
MINIMUM CHARGE 15np. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please note that the valves offered below are not necessarily of U.K. origin

0A2	0.40	6A87G	0.85	6F13	0.50	10D1	0.65
0A3	0.48	6AT6	0.38	6F14	0.70	10D2	0.55
0B2	0.40	6AU6	0.30	6F15	0.65	10F1	0.75
0C3	0.70	6AV6	0.40	6F18	0.50	10F9	0.65
0B3	0.40	6AW8A	0.65	6F24	0.90	10F18	0.60
0D3	0.40	6BA6	0.28	6F24	0.80	10L1	0.60
1B8GT	0.45	6BE8	0.22	6F25	1.00	10LD11	0.70
1L4	0.25	6BF6	0.55	6F26	0.35	10L13	0.75
1R4	0.80	6BH6	0.75	6F28	0.70	12A5	0.70
1R5	0.45	6BJ6	0.55	6GK6	0.60	12A6	0.60
1S4	0.40	6BK7A	0.75	6J4	0.80	12AE	0.55
1R6	0.80	6BN6	0.45	6K4	0.40	12A5	0.55
1U4	0.50	6B6A	0.80	6J6	0.80	12AQ5	0.50
1U4	0.40	6BQ5	0.25	6J7	0.45	12AT8	0.40
1U5	0.75	6BR8	0.75	6K47	0.60	12AT7	0.40
1V2	0.55	6BT7	1.85	6K6GT	0.75	12A0	0.45
1X2H	0.85	6BW6	0.90	6K7	0.43	12A07	0.33
2D21	0.40	6BW7	0.90	6K8A	0.45	12A07	0.33
8A4	0.45	6BX6	0.25	6K25	0.75	12AV7	0.70
8A5	0.75	6BZ6	0.45	6L6GT	0.55	12AX7	0.33
8S4	0.40	6C4	0.35	6L7	0.45	12AY7	0.75
3V4	0.70	6C5GT	0.55	6L18	0.50	12BA4	0.65
5R4GY	0.75	6CB6	0.40	6LD20	0.50	12BA5	0.45
5U4G	0.40	6CD4G	0.40	6N7GT	0.55	12B47	0.50
5V4GT	0.80	6C7	1.30	6P75	0.50	12BE5	0.50
6Y8GT	0.45	6C6T	0.80	6Q7	0.50	12BH7	0.50
6Z5	0.75	6CL6	0.80	6R7A	0.45	12BY7	0.55
5Z4G	0.45	6C8U	0.90	6R8T	0.45	12E1	1.00
6/30L2	0.90	6C94	0.70	6R8K7	0.50	12K5	3.00
6A4	0.45	6CY5	0.80	6R8K7	0.50	12K5	3.00
6AF4A	0.60	6CY7	0.75	6SL7GT	0.45	12K7GT	0.50
6A5	0.25	6D2	0.55	6S8GT	0.50	12R7	0.45
6A6T	0.45	6D8C	0.80	6R87	0.50	20D1	1.60
6A6H	0.60	6DK6	0.60	6T8	0.38	20L1	1.10
6A78	0.30	6DQ6B	0.75	6U4GT	0.70	20P1	0.50
6AK5	0.40	6D84	1.25	6U6G	0.75	20P2	0.50
6AK6	0.60	6E8	0.65	6V8GT	0.45	20P5	1.20
6AL3	0.48	6E8H	0.85	6X4	0.40	25L6GT	0.50
6AL6	0.22	6EJ7	0.35	6X4	0.40	25L6GT	0.50
6AM6	0.37	6EW6	0.70	6X5GT	0.45	25Z4G	0.35
6AQ5	0.42	6F1	0.75	6X8	0.65	25Z6GT	0.25
6AQ8	0.70	6F5	0.75	6Y6G	0.90	30A	0.50
6AR5	0.55	6F6	0.45	6Z1	0.75	30AE3	0.40
6AR8	0.65	6F6G	0.75	6W6G	0.70	30C1	0.30
6A85	0.50	6F11	0.50	10C2	0.60	30C15	1.00

First Quality Fully Guaranteed



ELECTRONIC VALVES

30C17	1.10	90A4	2.40	DY86	0.35	ECC80	0.40
30C18	0.90	90A5	2.50	DY87	0.38	ECC81	0.40
30C19	1.00	90C1	0.75	DY802	0.37	ECC189	0.50
30C21	0.90	90C2	0.40	E80F	1.35	ECC807	1.00
30FL12	1.10	607	0.50	E880C	0.70	ELL80	1.15
30FL14	0.90	813	4.00	E180F	1.00	EM71	0.85
30L1	0.40	866A	0.85	E810F	2.90	EM80	0.85
30L15	0.95	8642	0.70	EAPC80	2.85	EM83	0.60
30L17	0.95	6080	1.75	EAP47	0.60	EM84	0.85
30P12	1.00	6145	1.00	EBC33	0.80	EM85	1.00
30P19	0.95	6144B	2.50	EBC41	0.85	EM87	0.70
30P1L1	0.95	6360	1.25	EBC41	0.33	EN91	0.40
30P1L3	1.10	6939	2.25	EBF80	0.40	EN91	0.40
30P1L4	1.25	7199	0.85	EBF83	0.40	EY80	0.75
35A3	0.60	7856	1.50	EBF89	0.32	EY81	0.40
35A5	0.75	7895	1.50	EBS1	1.50	EY83	0.55
35B5	0.85	A2293	2.20	EC3	0.50	EY84	0.55
35C5	0.90	AZ1	0.60	ECS8	2.85	EY87	0.43
35D5	0.75	AZ3	0.55	ECS8	0.90	EY88	0.43
35L6GT	0.75	CB1	0.90	ECS8	0.90	EY88	0.43
35W4	0.40	CDL31	1.00	EC90	0.35	EZ40	0.50
35Z2G	0.40	CY1	0.50	EC92	0.45	EZ41	0.75
35Z4G	0.40	CY31	0.50	EC93	0.90	EZ80	0.28
35Z5GT	0.70	DAF95	0.50	ECC35	1.00	EZ81	0.28
50A5	0.80	DF95	0.50	ECC40	0.70	GTIC	3.00
50B5	0.75	DK92	0.70	ECC81	0.40	GTIC	3.00
50C5	0.60	DK96	0.80	ECC82	0.38	GTIC	3.00
50C8	0.60	DL96	0.55	ECC83	0.38	GTIC	3.00
50E5H	0.65	DM70	0.60	ECC84	0.30	GTIC	3.00
50L6GT	0.60	DM160	0.68	ECC84	0.30	GTIC	3.00
85A2	0.55	DY51	0.55	ECC84	0.30	GTIC	3.00

EP95	0.40	HK90	0.50	PL33	0.40	U404	0.70
EP97	0.55	KT66	2.35	PL36	0.55	U801	0.80
EP98	0.75	KT77	1.00	PL81	0.50	U801	0.80
EP183	0.30	KT88	2.25	PL82	0.45	U801	0.80
EP184	0.35	N78	1.60	PL83	0.45	UAF41	0.70
EP804	1.25	PAC800.40	PL84	0.40	UAF42	0.80	
EK90	0.32	PC86	0.60	PL302	0.55	UB41	0.85
EL34	0.50	PC88	0.80	PL504	0.75	UBC41	0.85
EL38	0.50	PC92	0.50	PL508	0.90	UBC81	0.45
EL41	0.75	PC97	0.50	PL509	1.10	UBF80	0.40
EL81	0.55	PC900	0.48	PL801	1.00	UBF89	0.40
EL83	0.50	PC884	0.40	PL802	0.95	UBL1	0.70
EL84	0.25	PC885	0.40	PM84	0.80	UBL21	0.70
EL85	0.43	PC888	0.55	PY31	0.85	UCL92	0.35
EL86	0.40	PC839	0.55	PY33	0.83	UC85	0.45
EL90	0.42	PC8189	0.90	PY80	0.40	UCF80	0.70
EL90	0.42	PC8805	0.95	PY81	0.30	UCH21	0.70
EL922	1.15	PC8806	0.95	PY82	0.35	UCH42	0.70
EL930	0.85	PCF80	0.30	PY83	0.38	UCH81	0.40
EM71	0.80	PCF83	0.35	PY88	0.40	UCL21	0.80
EM80	0.45	PCF84	0.60	PY800	1.00	UCL92	0.35
EM83	0.60	PCF86	0.60	PY800	1.00	UCL92	0.35
EM84	0.85	PCF87	1.10	PY801	0.47	UCL93	0.85
EM85	1.00	PCF801	0.50	PZ30	0.38	UF11	0.60
EM87	0.70	PCF802	0.50	QQV02-6	2.25	UF41	0.85
EN91	0.40	PCF805	0.90	QQV03-10	1.25	UF42	0.85
EY61	0.40	PCF806	0.75	QQV03-10	1.25	UF43	0.85
EY80	0.75	PCF808	0.90	TT21	3.80	UF85	0.45
EY81	0.40	PC82000.70	TT22	4.00	UF89	0.45	
EY83	0.55	PCL83	0.50	U18 ²⁰	0.75	U141	0.65
EY84	0.55	PCL82	0.35	U25	0.85	U184	0.45
EY87	0.43	PCL83	0.45	U26	0.85	U184	0.45
EY88	0.43	PCL84	0.45	U31	0.70	U184	0.45
EY88	0.43	PCL85	0.45	U37	0.50	U1Y1	1.00
EZ40	0.50	PCL88	1.25	U52	0.40	U41	0.45
EZ41	0.75	PCL200	0.75	U76	0.40	U782	0.50
EZ80	0.28	PCL800	1.10	U78	0.40	U785	0.40
EZ81	0.28	PCL801	0.95	U191	0.75	W709	0.75
GTIC	3.00	PCL805	0.60	U201	0.60	X12	0.60
GTIC	3.00	PCL806	0.60	U281	0.55	Y63	0.75
GTIC	3.00	PCL807	0.60	U282	0.55	Z5048	4.50
GTIC	3.00	PCL808	0.60	U301	0.55	Z5058	7.00
GTIC	3.00	PCL809	0.60	U403	0.70	Z803U	1.35

TRANSISTORS

2N695	0.15	AC128	0.15	BD121	0.65
2N697	0.15	AC132	0.85	BD123	0.80
2N698	0.80	AC153	0.20	BD124	0.70
2N705	0.70	AC184	0.15	BD132	0.80
2N706	0.10	AC157	0.17	BF115	0.20
2N708	0.15	AC159	0.10	BF187	0.18
2N758	0.25	AC176	0.17	BF173	0.20
2N929	0.20	AC187	0.25	BF179	0.30
2N930	0.20	AC188	0.25	BF180	0.30
2N987	0.30	AC17	0.25	BF181	0.30
2N1131	0.25	AC18	0.25	BF184	0.20
2N1132	0.25	AC19	0.25	BF185	0.20
2N1187	0.25	AC190	0.20	BF186	0.14
2N1302	0.17	AC191	0.20	BF195	0.14
2N1303	0.17	AC192	0.10	BF196	0.18
2N1304	0.20	AD140	0.50	BF197	0.12
2N1305	0.20	AD149	0.45	BF200	0.85
2N1306	0.25	AD161	0.85	BF207	0.25
2N1307	0.25	AD162	0.85	BF208	0.20
2N1308	0.25	AD211	1.25	BF209	0.20
2N1309	0.25	AD212	1.25	BF291	0.20
2N1613	0.17	AF114	0.17	BFX88	0.20
2N1711	0.20	AF115	0.17	BFY17	0.45
2N1786	0.75	AF116	0.17	BFY18	0.25
2N1814	0.75	AF117	0.17	BFY19	0.20
2N2180	0.80	AF118	0.80	BFY61	0.20
2N2217	0.25	AF125	0.20	BFY62	0.20
2N2218	0.20	AF127	0.20	BSY26	0.17
2N2219	0.20	AF180	0.85	BSY27	0.15
2N2369A	0.15	AF181	0.85	BSY28	0.17
2N2477	0.65	AF186	0.40	B8Y65	0.20
2N2646	0.40	AF239	0.38	B8Y95A	0.12
2N2905	0.25	AF211	0.45	OC16	0.50
2N2923	0.18	AF212	1.00	OC22	0.50
2N2924	0.18	ASV28	0.25	OC23	0.60
2N2926	0.10	ASV27	0.30	OC24	0.60
2N3053	0.20	ASV28	0.25	OC25	0.35
2N3054	0.50	ASV29	0.30	OC26	0.25
2N3055	0.80	ASV54	0.25	OC29	0.60
2N3133	0.25	ASZ15	0.70	OC35	0.50
2N3134	0.25	ASZ16	0.70	OC36	0.45
2N3391	0.17	ASZ17	0.75	OC42	0.20
2N3392	0.17	ASZ18	0.75	OC44	0.15
2N3393	0.15	ASZ20	0.25	OC45	0.12
2N3394	0.15	ASZ21	0.40	OC70	0.10
2N3395	0.20	AUY10	1.00	OC71</	

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold"—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW07 Aldermaston Court, Reading RG7 4PF.

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world \$2-65. PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

- | | | |
|--|--|---|
| <input type="checkbox"/> MECHANICAL | <input type="checkbox"/> Man. Prod.—cont. | <input type="checkbox"/> Constructional-cont. |
| <input type="checkbox"/> A.M.S.E. (Mech.) | <input type="checkbox"/> Quality Control | <input type="checkbox"/> Building |
| <input type="checkbox"/> Boiler Inspect. | <input type="checkbox"/> Salesmanship | <input type="checkbox"/> Building Drawing |
| <input type="checkbox"/> & Operation | <input type="checkbox"/> Storekeeping | <input type="checkbox"/> Build. Foreman |
| <input type="checkbox"/> C & G Eng. Crafts | <input type="checkbox"/> Work Study | <input type="checkbox"/> Carpentry & Join. |
| <input type="checkbox"/> C & G Fabricat. | <input type="checkbox"/> Works | <input type="checkbox"/> Civil & Municipal |
| <input type="checkbox"/> Diesel Eng. | <input type="checkbox"/> Management | <input type="checkbox"/> Eng.nering |
| <input type="checkbox"/> Eng. Inspection | <input type="checkbox"/> Draughtsmanship | <input type="checkbox"/> Constructional |
| <input type="checkbox"/> Eng. Metallurgy | <input type="checkbox"/> A.M.I.E.D. | <input type="checkbox"/> Eng.nering |
| <input type="checkbox"/> Inst. Eng. & Tech. | <input type="checkbox"/> Design of Elec. | <input type="checkbox"/> Construction |
| <input type="checkbox"/> Inst. Motor Ind. | <input type="checkbox"/> Machines | <input type="checkbox"/> Surveyors |
| <input type="checkbox"/> Mainten. Eng. | <input type="checkbox"/> Die & Press Tool | <input type="checkbox"/> Institute |
| <input type="checkbox"/> Mechanical Eng. | <input type="checkbox"/> Design | <input type="checkbox"/> Clerk of Works |
| <input type="checkbox"/> Sheet Metal Work | <input type="checkbox"/> Electrical | <input type="checkbox"/> Council Eng. |
| <input type="checkbox"/> Welding | <input type="checkbox"/> Draughtsmanship | <input type="checkbox"/> Geology |
| <input type="checkbox"/> ELECTRICAL & ELECTRONIC | <input type="checkbox"/> Gen. Draughtsmanship | <input type="checkbox"/> Health Eng. |
| <input type="checkbox"/> M.S.E. (Elec.) | <input type="checkbox"/> Jig & Tool Des. | <input type="checkbox"/> Hydraulics |
| <input type="checkbox"/> C & G Elec. Eng. | <input type="checkbox"/> Tech. Drawing | <input type="checkbox"/> Inst. Builders |
| <input type="checkbox"/> C & G Elec. Inst. | <input type="checkbox"/> RADIO & TELE-COMMUNICATIONS | <input type="checkbox"/> Inst. Works & |
| <input type="checkbox"/> C & G Elec. Tech. | <input type="checkbox"/> Colour TV | <input type="checkbox"/> Highway Sup. |
| <input type="checkbox"/> Computer Elect. | <input type="checkbox"/> C & G Radio/TV/ | <input type="checkbox"/> Painting & Dec. |
| <input type="checkbox"/> Elec. Maths | <input type="checkbox"/> Electronics | <input type="checkbox"/> Public Hygiene |
| <input type="checkbox"/> Elec. Science | <input type="checkbox"/> C & G Telecomm. | <input type="checkbox"/> Road Engineer. |
| <input type="checkbox"/> Electronic Eng. | <input type="checkbox"/> Tech. | <input type="checkbox"/> Structural Eng. |
| <input type="checkbox"/> Electrical Eng. | <input type="checkbox"/> Exam. | <input type="checkbox"/> Surveying |
| <input type="checkbox"/> Install. & Wiring | <input type="checkbox"/> Radio Amateurs | <input type="checkbox"/> GENERAL |
| <input type="checkbox"/> Meters | <input type="checkbox"/> Pract. Rad. Elec. | <input type="checkbox"/> Agricultural Eng. |
| <input type="checkbox"/> & Measuring | <input type="checkbox"/> (with kit) | <input type="checkbox"/> Council of Eng. |
| <input type="checkbox"/> Instruments | <input type="checkbox"/> Radio Servicing | <input type="checkbox"/> Inst. |
| <input type="checkbox"/> MANAGEMENT & PRODUCTION | <input type="checkbox"/> & Repairs | <input type="checkbox"/> Farm Science |
| <input type="checkbox"/> Auto. Control | <input type="checkbox"/> Radio & TV Eng. | <input type="checkbox"/> General Educat. |
| <input type="checkbox"/> Computer Prog. | <input type="checkbox"/> Trans. Course | <input type="checkbox"/> Gen. Plastics |
| <input type="checkbox"/> Electronic Data | <input type="checkbox"/> TV Main. & Serv. | <input type="checkbox"/> Pract. Maths |
| <input type="checkbox"/> Processing | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> Pract. Slide Rule |
| <input type="checkbox"/> Estimating | <input type="checkbox"/> Aero Eng. | <input type="checkbox"/> Pure & Applied |
| <input type="checkbox"/> Foremanship | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Maths |
| <input type="checkbox"/> Inst. Cost & Man | <input type="checkbox"/> A.E.C. Cert. | <input type="checkbox"/> Refrigeration |
| <input type="checkbox"/> Accountants | <input type="checkbox"/> Auto Engineer. | <input type="checkbox"/> Rubber Tech. |
| <input type="checkbox"/> Inst. Marketing | <input type="checkbox"/> Auto Repair | <input type="checkbox"/> Sales Engineers |
| <input type="checkbox"/> Management | <input type="checkbox"/> C & G Auto. Eng. | <input type="checkbox"/> Tech. Report |
| <input type="checkbox"/> Metrication | <input type="checkbox"/> Garage | <input type="checkbox"/> Writing |
| <input type="checkbox"/> Motor Trade Man. | <input type="checkbox"/> Management | <input type="checkbox"/> Timber Trade |
| <input type="checkbox"/> Network Plan. | <input type="checkbox"/> MAA/IMI Dipl. | <input type="checkbox"/> University Bnt. |
| <input type="checkbox"/> Numerical Cont. | <input type="checkbox"/> Motor Vehicle | |
| <input type="checkbox"/> Operational | <input type="checkbox"/> Mechanics | |
| <input type="checkbox"/> Research | <input type="checkbox"/> CONSTRUCTIONAL | |
| <input type="checkbox"/> Personnel Man. | <input type="checkbox"/> A.M.S.E. (Civil) | |
| <input type="checkbox"/> Planning Eng. | <input type="checkbox"/> Architecture | |
| <input type="checkbox"/> Production Eng. | | |

Coaching for many major exams. including O.N.C. C & G, etc.

G.C.E.

58 'O' & 'A' LEVELS SUBJECTS
Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW


To B.I.E.T., Dept. BPW07 Aldermaston Court, Reading RG7 4PF QN BPW07

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____

Accredited by C.A.C.C.

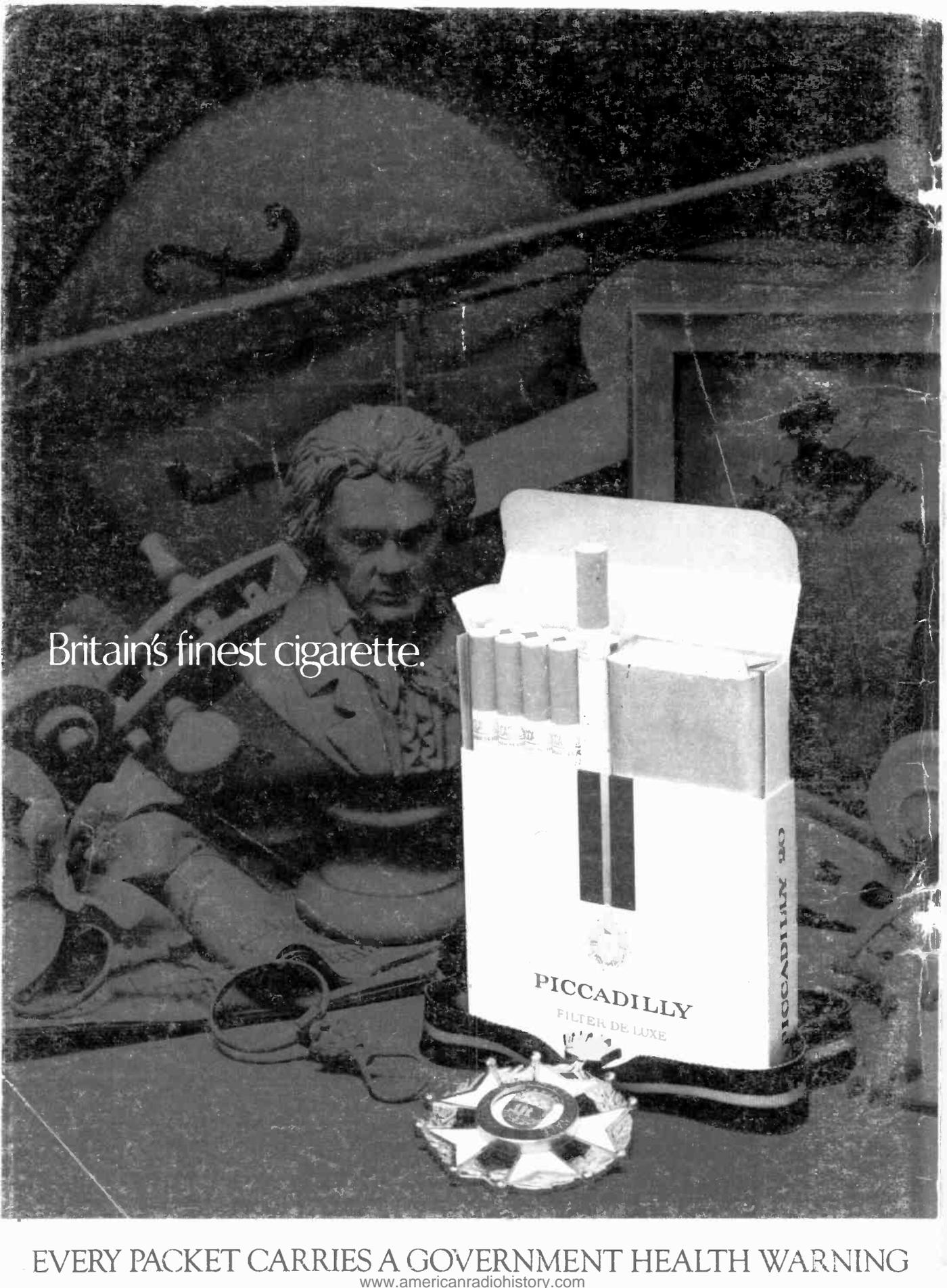BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



Britain's finest cigarette.

PICCADILLY
FILTER DE LUXE

EVERY PACKET CARRIES A GOVERNMENT HEALTH WARNING

www.americanradiohistory.com