

PRACTICAL WIRELESS

SEPTEMBER
1973

20p

P
W

*
POP
STAR



*
SIMPLE TWO I.C. RADIO




also: **I.C.** ANALOGUE D.C. VOLTMETER
POWER REGULATED MODULE

look!

electronics really mastered

... practical
... visual
... exciting!

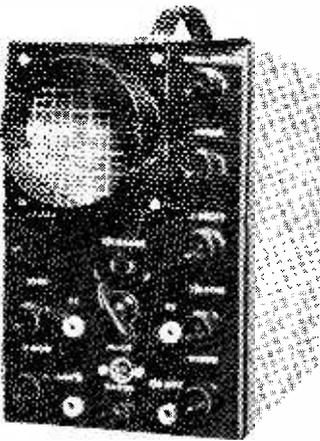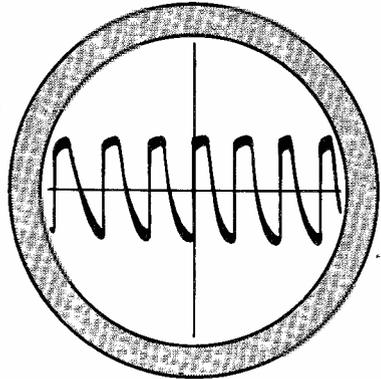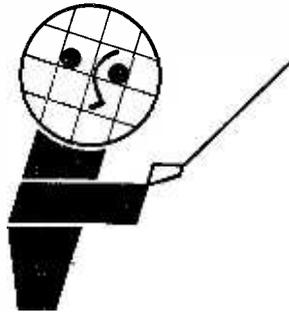no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

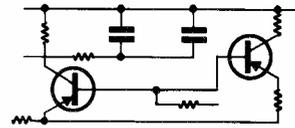2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL93

special free gift also to all our students

PRACTICAL WIRELESS

VOL. 49 NO. 5
ISSUE 799
SEPTEMBER 1973

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Morris A. Colwell

ASSISTANT EDITOR

Lionel E. Howes, G3AYA

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Eric Dowdeswell, G4AR

PRODUCTION & NEWS

EDITOR Colin R. Riches

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder

01-634 4292

Susan Corne

ADVERTS. MANAGER

01-634 4293

Roy Smith

CLASSIFIED ADVERTS.

01-634 4301

Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Subscription Rates for one year to any part of the world £2.65 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". Binders (£1.10) and indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 406 LISTENERS' CHOICE—Leader article and October preview
- 407 NEWS . . . NEWS . . . NEWS
- 417 TELEVISION—This month's attractions
- 418 PRODUCTION LINES—Products reviewed by *Colin Riches*
- 425 DEAR SIR—Readers' letters to the Editor
- 430 HOTLINES on recent developments
- 431 NEXT MONTH in *Practical Wireless*
- 437 CQ! CQ! Back numbers wanted
- 440 BOOK REVIEWS
- 448 ON THE AIR—Reports on Broadcast Bands
- 448 Short Wave—*Malcolm Connah*
- 451 Medium Wave—*Charles Molloy*
- 451 VHF/FM—*Simon David*
- 452 Amateur Bands, Short Wave/VHF—*David Gibson G3JDG*

● CONSTRUCTIONAL

- 408 SHORT WAVE CONVERTER for 190m on MW
- X 421 HIGH SENSITIVITY D.C. VOLTMETER—*D. Silvester*
- 432 'P.W. POP STAR' Two I.C. a.m. Radio—*F. G. Rayer*
- 441 'P.W.' STUDENT' OSCILLOSCOPE, Part 2—*G. A. Cozens*
- 446 TAKE 20 No. 52 Waa-Waa Unit—*David Andrews*
- 447 JOINING COAXIAL CABLES—*R. A. Butterworth*
- X 455 I.C. POWER SUPPLY MODULE (2 to 20V up to 150mA)—
J. Lewis, B.Sc.

● OTHER FEATURES

- 411 BROADCASTING IN BERLIN—P.W. tour of Berlin
- 414 I.C. OF THE MONTH, LP2000—*L. A. Ireland*
- 426 BETTER AERIALS FOR BETTER STEREO Part 1—
Gordon J. King
- 438 GOING BACK Visits Sweden—*Colin Riches and Arthur Dow*

PACKAGE PRICE R.S.C. STEREO PACKAGE OFFERS

FOR ILLUSTRATED UNITS

ONLY £39-99

Carr. £1-00
Or deposit £6-95
and 9 monthly
payments £4-22
(Total £44-98)



R.S.C. A55 LOUDSPEAKERS

GARRARD 2025

LINEAR 505 AMP

Individual Rec. Retail Prices:

LINEAR 505 5 + 5 Watt Amplifier	£19-95
GARRARD 2025 Autochanger + KS40 Cartridge	£13-44
Teak Veneer Plinth with Transparent Plastic Cover	£5-90
Pair A55 LOUDSPEAKERS (Inc 8" x 5" 10,000 Gauss)	£10-82
TOTAL	£49-41

SAVE £30 approx.

SEND S.A.E. FOR FREE COLOUR BROCHURE



MONARCH SPEAKERS

GOLDRING GL72

'SUPER 30' AMP

HIGH FIDELITY UNITS

PACKAGE PRICE

FOR ILLUSTRATED UNITS **£108-25**

Carr. £1-76

Or deposit £15-00 and 12 monthly payments £8-78 (Total £120-36)

GOLDBRING GL72 Transcription Turntable + P.T.
GOLDRING G800 Magnetic Cartridge
DE-LUXE PLINTH with Roll-over Cover
Pair R.S.C. MONARCH LOUDSPEAKERS
R.S.C. SUPER 30 Mk III AMPLIFIER

Total value of individual items listed above £138-14.

FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams, Frequency **£9-96** post free
Impedance 8-15 ohms. Or Dep. £2 & 9 monthly payments £1-07 (Tot. £11-63)

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating 1.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING

COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12-65 Carr. 40p
or FACTORY BUILT IN TEAK VENEERED CABINET £12-65 Carr. 40p
as illustrated £16-50 or dep. £2 and 9 monthly payments £1-88 (Total £18-92)



AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.

HF808T	8"	10W	£2-85	HF100D	12"	15W	£5-50
HF100D	10"	10W	£3-30	HF128	12"	15W	£6-85
HF120	12"	15W	£4-95	HF128D	12"	15W	£6-85

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality. In suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. PLEASE STATE IMPEDANCE WHEN ORDERING MODEL 803T 8" 15w. with parasitic Tweeter. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15 Ω. **£3-70**
£4-95

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BHI. An all-dry battery eliminator. Size 5½ x 4½ x 2in. approx. Completely replaces batteries supplying 1.5v and 90v. to battery radio where A.C. mains 200/250v. Post 30p
50c/s is available. ASSEMBLED READY FOR USE **£4-15**

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

MIDGET CLAMPED TYPE 5½ x 2½ x 2in.	
250v., 60mA, 6-3v. 2a	£1-10
250-0-250v., 60mA 6-3v. 2a	£1-16
FULLY SROUDED UPRIGHT MOUNTING	
250-0-250v. 60mA, 6-3v. 2a., 0-5-6-3v. 2a.	£1-55
250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-45
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-45
300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a.	£2-45
For Mullard 510 Amplifier	£2-95
350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-45
350-0-350v. 160mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-95
425-0-425v. 200mA, 6-3v. 4a., c.t., 5v. 3a.	£2-45
425-0-425v. 200mA, 6-3v. 4a., 6-3v. 3a., 5v. 3a.	£5-60
450-0-450v. 200mA, 6-3v. 4a., c.t., 5v. 3a.	£6-00
TOP SROUDED DROP-THRO' TYPE	
250-0-250v. 70mA, 6-3v. 2a., 0-5-6-3v. 2a.	£1-49
250-0-250v. 100mA, 6-3v. 2a., 0-5-6-3v. 2a.	£1-71
250-0-250v. 100mA, 6-3v. 2a., 6-3v. 1a.	£1-75
350-0-350v. 80mA, 6-3v. 2a., 0-5-6-3v. 2a.	£2-81
250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-45
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-45
300-0-300v. 130mA, 6-3v. 4a., c.t., 6-3v. 1a.	£2-85
Suitable for Mullard 510 Amplifier.	£2-85
350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-45
350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a.	£2-85
FLAMANT or TRANSISTOR POWER PACK	
Type 6-3v. 1.5a. 55p; 6-3v. 2a. 60p; 6-3v. 3a. 85p;	
6-3v. 6a. £1-45; 12v. 1a. 61p; 12v. 3a. or 24v. 1a.	
1-5a. £1-50; 9-18v 1½a. £1-25; 0-12-25-42v 2a. £1-95.	

SP101 HIGH FIDELITY PLAYER UNIT

Comprising Goldring G101 hi-fi single player unit fitted high fidelity free field magnetic stereo cartridge with diamond stylus. Belt driven Attractive design super-slim plinth and 'roll-over' transparent tinted plastic cover. Or Deposit £4-95 and 9 Monthly **£34-95** Post paid
Payments of £3-75 (Total £38-70) Excellent value.

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.
DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. **£9-45** Carr. 40p.
Dual Cone speaker. Imp. 3 or 15 ohms.
MONARCH Size 19 x 10½ x 9in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible P.V.C. cone surround, long throw voice coil and 10,000 line magnet. High flux pressure tweeter. Handsome design cabinet. Range 30-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. Carr. 50p
See 'package offers' for illustration. **£19-35**

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.
JES Size 16" x 11" x 9". SE8 For optimum performance with any 8in. Hi-Fi spkr. **£6-50**
Size 19 x 10½ x 9in. SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter **£7-95**
SE10 For outstanding results with 10in. Hi-Fi spkr. Size 25½ x 16 x 9in. Ported **£6-75**

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£7-65** Carr. 39p

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. -2db. Harmonic Distortion 0-3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm spkrs. Max. sensitivity 6mv Output rating 1.H.F.M. Fully enclosed enamelled case, 9½ x 2½ x 2in. Attractive brushed silver finish fascia plate 10 x 9in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. OR FACTORY BUILT WITH 18 MONTHS' GUARANTEE **£12-05** Carr. 40p.

R.S.C. MKIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
Only high grade components by leading manufacturers
* Push Button Selector Switching
* Jack Socket for Headphones
* Neon Indicator
* Satin Silver Finish Metal Fascia
* Solid State Circuitry
* Twenty Silicon Transistors
* Four Diodes, Four Rectifiers
Send S.A.E. for full descriptive leaflet.




For Magnetic or Ceramic Pick-Ups regardless of Price.
Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ± 1½ db.

R.S.C. STEREO FM III TUNER. in cabinet. Visually matches Super 30 Mk. III **£37-50**
FACTORY BUILT UNIT - INC. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £4-54 (Total £47-86) **£42-50**

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.
★ Response 30-20,000 c.p.s. Impedance 15 ohms
★ Performance comparable with units costing considerably more Carr. 65p
COMPLETE KIT **£25-25**
Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet.
(2) 3-way quarter section series cross-over system.
(3) 8 x 5in. high flux middle range speaker.
(4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet.
(7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-64 (Total £28-36).

RSC GROUP/DISCO UNITS

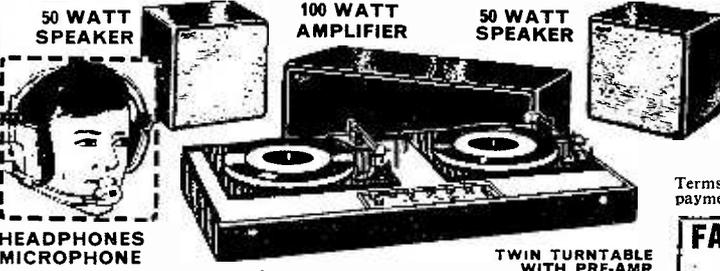

HEADPHONES
MICROPHONE

TWIN TURNTABLE
WITH PRE-AMP

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback howl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £8 and 9 mthly payments £2-42 (Total £24-78) Carr. 65p. **£21-95**

TYPE C818 50 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5 & 9 mthly pymts £3-54 **£32-72** (Total £38-88) Carr. 85p.

TYPE C4100 100 WATTS Inc. four 12" 60 watt speakers for conservative rating. Extra heavy construction. Size approx. 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £11 and 12 mthly. pmts. £5-80 (Total £60-80). **£71-50** Carr. 85p.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level -70dB. Response +3dB 30-20,000 c/s. All high grade components. Valves EP86 EP86, ECC83, EL84, EL84, 6Z84. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. for linkage from accidental shorts. Output for speakers. Twin-handled perforated cover £2-10. 12 MONTHS GUARANTEE. Carr. 72p. **£21-75**

TERMS: Deposit £4 and 9 monthly payments of £2-27 (Total £24-43). Send S.A.E. for leaflet.

F.A.L. DISCO PRE-AMPLIFIER £18-97

Designed for use with a pair of Player Units and Amplifier with Bass and Treble Controls. Incorporates MONITORING FACILITIES and Mic. input. The 4 inputs are ind. controlled. Detector switch Gram (1), (2), and Tape. For operation on 200-250v A.C. Mains 50Hz. Size approx 16 1/2" x 3" x 4" deep. Brush Silver finished fascia. Fully enclosed but can be mounted in cabinet.

FANE "CRESCENDO" SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speakers/3 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £7-25 & 9 monthly payments £2-82. Total £42-53. **£37-95** Carr. 82p.




RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker


For Lead (Guitar, Mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £8-95 and 12 monthly payments £4-80 (Total £67-63). Carr. Free SAE for leaflet. **ONLY £59-95** UK Mainland

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting. ★ Two extra heavy duty 12in. 50w Loudspeakers. ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £15 & 9 monthly payments of £7-22. (Total £79-88.) Carr. £2 **£71-50**

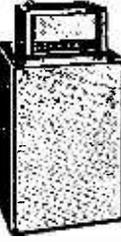

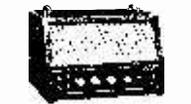RSC GP30 HI-FI AMPLIFIER For Guitar, Vocal or Instrumental Group



A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 9 monthly payments of £2-75 (Total £29-15). **£25-85** Carr. 72p

NOW SIX NEW BRANCHES

- BOLTON 23 DEANS GATE
- COVENTRY 17 SHELTON SQUARE
- DONCASTER 3 QUEENSGATE
- NOTTINGHAM Opening soon
- STOCKPORT 19/19A MARKET STREET
- SUNDERLAND 8 LITTLE UNDERBANK
- NEW LARGER PREMISES AT HULL, DARLINGTON & NEWCASTLE See Addresses



HI-FI CENTRES LTD.
MAIL ORDERS & EXPORT ENQUIRIES TO:—
AUDIO HOUSE, HENCONNER LANE, LEEDS, 13. Tel: Pudsey (99735) 77681.
TERMS C.W.O. or C.O.D. No G.O.D. under £1.
POSTAGE 25p EXTRA UNDER £2. 35p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED. S.A.E. PLEASE WITH ENQUIRIES.
SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.
MAIL ORDERS MUST NOT BE SENT TO SHOPS

PACKAGE OFFER

- Units listed below
 - (a) 100w POWER AMPLIFIER
 - (b) PAIR OF HI-FI HEAD- PHONES
 - (c) MATCHING DYNAMIC 'MIKE' (attached to h' phone)
 - (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 7"
 - (e) RSC TDI DISCO CONSOLE
- (a) (b) (c) (d) & (e) **£145** Carr. £2-50

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 Mk.II turntables and Sonecans or Acon Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid. see illustration on left
Or Dep. £10 and 9 mthly pymts £8-80 (Total £71-20) **£63-26** Carr. £1-50

Terms Deposit £30 and 18 monthly payments of £8-00 (Total £174-00).

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15"	15" 60 Watt 14,000 gauss 8/15"	12" 50 Watt 13,000 gauss 15"
£25-95	£14-75	£11-99
Dep. £8 and 9 mthly payments £2-49 (Total £28-41)	Dep. £3-30 and 9 monthly payments £1-50 (Total £18-80)	Dep. £2 and 9 monthly payments £1-83 (Total £13-97)

FOR BASS GUITAR, ELECT. ORGAN, ETC. PAIR SUITABLE ALL PURPOSES

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£7-95** or Dep. £1-25 and 9 mthly payments 89p (Total £9-26)

DISCO PACKAGE OFFER £45

Pair BSR MP60 T/tables GP91 PU Cartridges. FAL Disco Pre-amp. Total Rec. Ret. Price £50-11 Carr. £1

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

- F.A.L. PHASE 50 MK.III AMPLIFIER £37-95
- PR. FANE POP 25/2 25W L/SPEAKERS £15-90
- Terms: Deposit £7-50 and 9 monthly payments of £5-36 (Total £55-74) **£49-50** carr. £1-10
- F.A.L. PHASE 50 MK.III AMPLIFIER £37-95
- PR. FANE POP 50 L/SPEAKERS £23-98
- Terms: Deposit £10 and 9 monthly payments of £6-07 (Total £64-83) **£57-50** carr. £1-10
- F.A.L. PHASE 50 MK.III AMPLIFIER £37-95
- PAIR L12/20 25W L/S in cabinets £26-80
- Terms: Deposit £10 and 9 monthly payments of £6-52 (Total £68-68) **£61** carr. £1-35
- F.A.L. PHASE 100/8 AMPLIFIER £37-95
- 4 FANE POP 50 L/SPEAKERS £47-96
- Terms: Deposit £20 and 12 monthly payments of £8-68 (Total £128-56) **£110** carr. £2

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH
L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50
Or deposit £4-50 and 9 monthly pmts. of £4-27. Total £42-83


L12/20 12" 20-25 WATT 13,000 lines 15 ohms	L12/10 10-15 Watt veneer finish cabinet 12" unit 8-15 ohm. Size approx. 14" x 14" x 9".
Dep £2-50 & 9 mthly pymts £1-48 (Total £15-28) Carr. 65p.	£8-25

CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

- BRADFORD 10 North Parade (Closed Wed.). Tel. 28349
- BOLTON 23 Deansgate Tel: 33512
- BIRMINGHAM 30/31 Great Western Arcade, Tel. 021-236 1279 (Closed Wed.)
- COVENTRY 17 Shelton Square, The Precinct (Closed Wed.)
- DERBY 26 Osaston Rd., The Spot (Closed Wed.) Tel. 41361
- DARLINGTON 19 Northgate (Closed Wed) Tel 68043
- EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
- GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158
- HULL 7 Whitefriargate Tel. 20505
- LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
- LEEDS 5-7 County (Mecca) Arcade, Briggate Tel. 28852
- LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
- LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629
- MANCHESTER 60A Oldham Street, (Closed Wed.). Tel. 236 2778
- MIDDLESBROUGH 106 Newport Rd. (Closed Wed.). Tel. 47098
- NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469
- NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel: 48068
- SHEFFIELD 13 Exchange Street (Castle Market Bldgs.) (Closed Thurs.). Tel. 20716
- STOCKPORT 8 Little Underbank. Tel: 480-0777.
- SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 70573

240v AC FROM A CAR BATTERY.

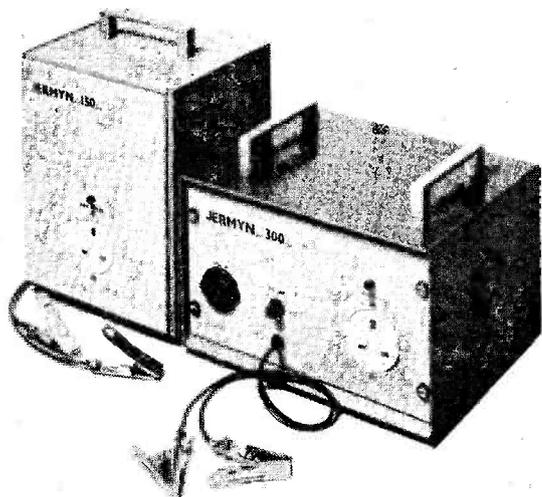

The Jermyn Inverter provides a completely portable source of 240v 50Hz power, working from an ordinary car battery.

No noise. No smell. No fuel oil. No maintenance.

And much cheaper than a 2-stroke generator — 150W version (needs 12v battery) £29.00 (+£2.90 VAT). 300W version (needs 24v battery) £39.00 (+£3.90 VAT).

The circuit includes electronic short-circuit prevention and wrong-connection protection.

And you can work it backwards; plug into the mains to recharge the battery.

Ideal for all kinds of field radio equipment, and as a stand-by for the house.


Please send me 150W 300W
Jermyn Inverter(s).
I enclose cheque/PO value £.....

Name
Address


Jermyn

Jermyn Industries 99 Vestry Estate Sevenoaks Kent

London's Lighthouse

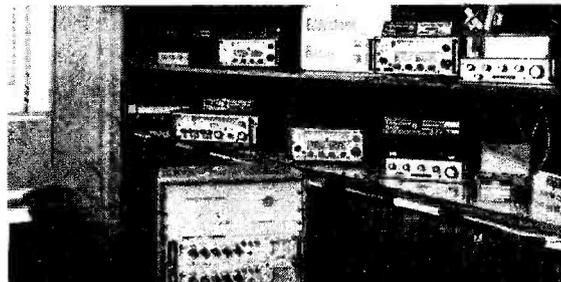

see the

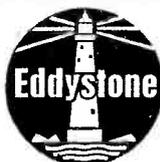

showroom
at

IMHOFS

Here at Imhofs we have a whole showroom entirely devoted to the Eddystone range of communication receivers. From the remarkable little EC10 MkII, the elegance of the Series 1000 range to the sophistication of the 830/7. Pop in and see us — or write for details to:—

112-116 New Oxford Street
London WC1A 1HJ
Telephone 01-636 7878

R83

PLUGS & LEADS

Plugs	
Pack 107 5 pin Din	22p
Pack 108 3 pin Din	20p
Pack 135 1/2" Jack	27p
Pack 130 1/2" Jack Stereo	50p
Pack 103 Loudspeaker Plug	17p
Pack 100 Phono Plug	7p
Pack 230 3 pin Socket	25p
Pack 236 5 pin Socket	33p
Pack 234 Loudspeaker Socket	33p

Ready-made Leads	
3 pin to 3 pin Din	70p
3 pin to open end	55p
5 pin to 5 pin Din	90p
5 pin to open end	70p
5 pin to 4 phono plugs	£1.00
Speaker lead Din to spade	40p
12ft	
Extension lead Din plug to socket	12ft. 70p
All leads approx. 6ft. in length	

DIAMOND STYLI	
(Send SAE for complete list)	
8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8. All at 80p each.	
Double Diamond	£1.25
Diamond suitable for Orbit	
NM22; G800; M3D	£2.25 each

CARTRIDGES	
Goldring G800	£6.00
Orbit NM22	£4.00
Shure 75/6	£6.00
Sonotone 9TAHC (Dia)	£2.00
Sonotone 8T4A (Dia)	£1.50
Ronnette 105 (Dia)	£1.25

All prices include VAT and postage

RECORD CARE

Cecil Watts Dust Bug	£1.20
Parastatic Disc Preener	45p
Antistatic Fluid	20p
Dust Bug Spares (Brush & Roller)	15p

CASSETTE TAPES	
Audio-Magnetic C60	
Qty 3 6 10 20	
Price	£1.00 £1.90 £3.20 £6.30
Cassette Caddy	£1.20
Cassette Head Cleaner	35p

ZONAL ILFORD TAPE	
5" Standard 600ft	25p
5 1/2" Standard 900ft	50p
7" (Plain boxed) 1200ft	60p
7" (Westminster Boxed) 1800ft	£1.25
7" Reel of Leader Tape (Blue or green)	75p

HEADPHONES	
Sennheisser MD414	£10.60
AKG K50	£6.50
Beyer DT48S	£35.00

MICROPHONES	
AKG D109	£11.50
AKG D202E1	£39.50
AKG D190C	£17.00
AKG D190E	£18.20
AKG D224	£50.00
Sennheisser MD211N	£45.00
Sennheisser MD413N	£27.00
Sennheisser MD421N	£35.00
Audio RMS7F Radio Mike	£210.00

SPEAKERS	
E.M.I. 350 Kit Bohms	£8.20
E.M.I. 450 Kit Bohms	£4.50


J. J. Francis (Wood Green) Ltd

MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS
Telephone; Matching 476


ADCOLA

ELECTRICAL SOLDERING EQUIPMENT OF THE FINEST QUALITY

Available from Stock

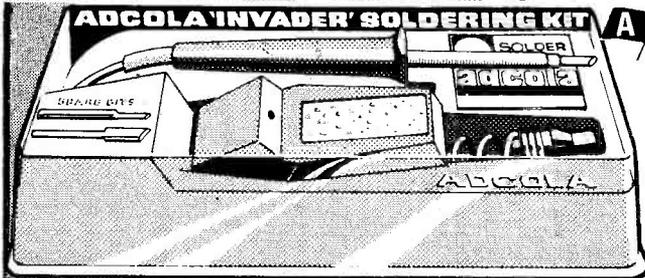


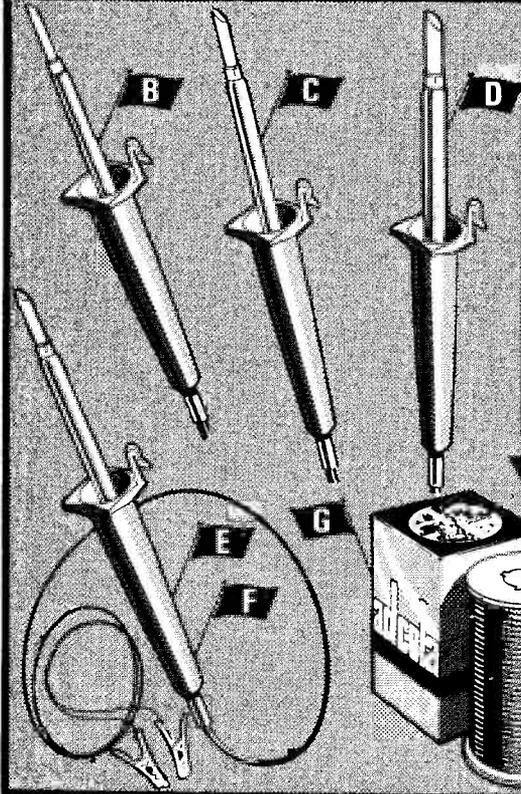We don't expect to hear from you for some time once you have purchased our Invader Soldering Kit containing a 3/16" bit soldering instrument, two spare bits, a soldering station and a pack of solder—everything you need.



The versatile Invader Range with a large selection of interchangeable bits

- B** L706 19 watt instrument 1/8" bit with cable
- C** L646 23 watt instrument 3/16" bit with cable
- D** L1076 27 watt instrument 1/4" bit with cable
- E F** BL646 and BL1076 12 volt battery models 3/16" & 1/4" bit size come complete with crocodile clips and 12ft PVC cable. Just clip on to a car battery.
- G H I** 18 swg top quality cored solder in 1/2 kilo, 3 oz and handy pack sizes.
- G** Non-corrosive de-soldering braid allows quick easy de-soldering (5 1/2 ft spool).
- K** For extra safety use an L686 soldering station.
- L** L68 protective shield for your Invader

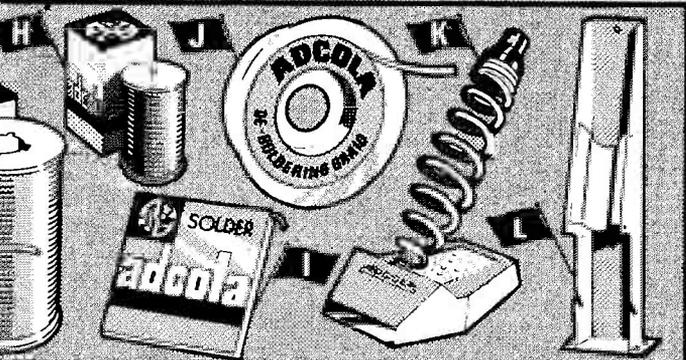

Please send me the following items

PRINT NAME

PRINT ADDRESS

A INVADER SOLDERING KIT	£4.39	<input type="checkbox"/>
B L706 INVADER	£2.15	<input type="checkbox"/>
C L646 INVADER	£2.33	<input type="checkbox"/>
D L1076 INVADER	£2.40	<input type="checkbox"/>
E BL646 BATTERY MODEL	£2.99	<input type="checkbox"/>
F BL1076 BATTERY MODEL	£3.12	<input type="checkbox"/>
G SOLDER REEL 1/2 KILO	£1.28	<input type="checkbox"/>
H SOLDER REEL 3 OZ	£0.45	<input type="checkbox"/>
I SOLDER PACK	£0.065	<input type="checkbox"/>
J DE-SOLDERING BRAID	£0.66	<input type="checkbox"/>
K L686 SOLDERING STATION	£1.88	<input type="checkbox"/>
L L68 PROTECTIVE SHIELD	£0.99	<input type="checkbox"/>

PW

New Catalogue.....



ADCOLA PRODUCTS LTD ADCOLA HOUSE GAUDEN ROAD LONDON, SW4 6LH
V.A.T. REGD. No. 235 6153 72 REGD. No. 442762

All prices include 10% V.A.T. Please tick items required.

**Fully guaranteed
Individually packed
VALVES**

H12H	£1.75	ECH84	40p	OA2	38p
CY31	40p	ECL80	40p	OA2	38p
DAF96	40p	ECL82	31p	PAB'80	35p
DF96	40p	ECL83	63p	PC97	41p
DK96	47p	ECL36	36p	PC900	42p
DL92	32p	EF36	50p	PC884	36p
DL94	45p	EF37A	35p	PC'89	49p
DL96	40p	EF40	50p	PC'89	49p
DM70	40p	EF41	65p	PC'89	49p
DY86	29p	EF80	25p	PCF80	25p
DY87	28p	EF83	60p	PCF82	27p
DY802	30p	EF85	31p	PCF84	54p
EB8CC/01	£1.08	EF86	27p	PCF86	50p
EF89	25p	PCF200	60p	OC26	25p
E180CC	37p	EF91	27p	PCF801	40p
E181CC	90p	EF92	31p	PCF801	40p
E182CC	£1.08	EF183	26p	PCF805	80p
EA50	18p	EF184	31p	PCF806	65p
EABC80	27p	ELF200	77p	PCF808	85p
EAB42	46p	ELF34	45p	PC'89	49p
EB81	20p	EL41	56p	PC'89	49p
EB83	45p	EL84	21p	PCL82	30p
EB84	50p	EL85	37p	PCL83	60p
EB81	50p	EL86	36p	PCL84	35p
EB81	31p	EL90	31p	PCL85	35p
EBF80	36p	EL95	31p	PCL86	48p
EBF83	36p	EL500	76p	PCL200	60p
EBF89	27p	EL504	78p	PL36	50p
EC81	27p	EM31	22p	PL81	40p
EC82	25p	EM84	36p	PL82	35p
EC83	27p	EM84	31p	PL83	36p
EC84	27p	EM87	62p	PL84	30p
EC85	36p	Y81	36p	PL600	62p
EC86	75p	Y82	36p	PL604	62p
EC88	40p	Y83	40p	PL608	70p
ECU89	55p	EZ41	45p	PL609	£1.05
ECF80	31p	EZ80	22p	PX4	£2.50
ECF82	31p	EZ81	24p	PY33	55p
ECF83	67p	EZ84	52p	PY80	35p
ECF81	56p	EZ87	68p	PY81	30p
ECH81	25p	KT66	£2.35	PY82	23p
ECH82	25p	KT88	£2.25	PY83	30p
ECH83	40p	N78	£1.60	PY88	32p

V.A.T.

Please add 10% to all orders

METERS

Full List of our very large stock of meters on request.

TRANSISTORS, ZENER DIODES etc.

OA9	30p	OC71	12p	IN823A	£1.30	3N154	95p	BC108	10p	GET115	45p
OA10	25p	OC72	20p	IN4785	50p	3N159	£1.45	BC113	10p	GET116	50p
OA70	10p	OC73	30p	IZMT5	35p	6PR5	45p	BC118	20p	GEX66	£1.00
OA73	7p	OC75	25p	IZMT10	37p	12FR60	75p	BCY72	15p	NKT222	20p
OA74	7p	OC76	25p	IZT5	67p	40R54	21p	BF115	25p	RAS304A	50p
OA74	7p	OC81	20p	IZT10	63p	40R55	21p	BF173	20p	6J4WA	65p
OA79 (61)	15p	OC81D	20p	2C385	51p	40R56	21p	BFY71	20p	GJ5	35p
		OC81DM	20p	2C408	51p	AD149	50p	BFY52	20p	GJ6GT	30p
		OC82	25p	2N918	37p	40R69	£1.40	BS	45p	SD195	23p
		OC82DM	30p	2N1304	22p	AC126	25p	BS	45p	SD938	31p
		OC83	25p	2N1306	25p	AC127	25p	BSY29	25p	SD94	21p
		OC83B	15p	2N1307	25p	AC128	20p	BU100	£1.30	SD988	46p
		OC84	25p	2N2147	64p	AC176	20p	BY213	25p	V405A	30p
		OC122	50p	2N3411	65p	ACV17	25p	BY216	65p	Z2A51CF	75p
		OC209	25p	2N4172	50p	ACV28	17p	CR8110	35p	ZR21	42p
		OC240	40p	2N2989	£4.00			CR8120	38p	ZR22	42p
		OC310	25p	2N3053	20p	AD161	35p	CR8130	40p		
		OC317	30p	2N3054	50p	AD162	35p	CR8135	43p		
		OC172	37p	2N3055	64p	AF118	20p	CR8140	48p		
		OC200	60p	2N3730	50p	AF127	20p	CR83/05	30p		
		OC201	75p	2N3731	£2.75	AF139	30p	CR83/20	35p		
		OC206	95p	2N4172	50p	AF178	45p	CR83/30	43p		
		OC219	30p	8203	50p	AF186	40p	CR825/025	7W		
		OC35	50p	IN25	60p	3F100	62p	ASV26	25p		
		OC38	42p	IN43	10p	3FR5	32p	ASX28	25p		
		OC44	17p	IN70	7p	3N128	87p	ASX67	48p		
		OC45	12p	IN677	12p	3N139	£1.75	BAW19	29p		
		OC70	12p	IN702-72580	3N140	87p	BC107	10p	GET103	23p	
		PY800	35p	UAF42	50p	UY85	35p	3Q4	55p	6AH6	50p
		PY801	48p	UBC41	48p	UR105/30	38p	384	35p	6AK5	35p
		QVQ03-10	URB80	38p	UR160/30	38p	3V4	48p	6AK8	30p	
		URB99	34p	UR801	£1.00	5B154H	£2.75	6AL5	13p	6BG6G	47p
		UR17	45p	UC85	35p	Z8011	£1.40	6R/25M	6AL5W	35p	
		UR19	35p	UCF80	60p	Z8031	£1.10	£3.10	6AM6	35p	
		STV280/40	UCH42	60p	Z800T	90p	5R4Y2	60p	6AN8	60p	
		STV280/80	UCH81	35p	IL4	13p	5U4G	30p	6AQ5	36p	
		UCL82	35p	IR5	35p	5V4G	45p	6AQ5W	45p		
		UCL83	55p	IR6	30p	5Y3GT	35p	6AS6	30p		
		UCL84	30p	IR6	30p	5Y4G	35p	6AT8	30p		
		UCL85	50p	IR7	30p	5Z3	70p	6AUG	20p		
		UCL86	50p	IR9	35p	IX2A	38p	5Z4	75p		
		UCL87	45p	IX2B	50p	5Z4GT	32p	6AX5GT	60p		
		UCL88	35p	2K25	£7.50	6B7	35p	6B7	35p		
		UCL89	65p	U3	65p	6A87	25p	6B8	£1.35		
		UCL90	65p	UABC80	30p	Y41	45p	6B87	60p		

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K.

Postage 1p to £1.25, £1-£2.17p, £2-£3.22p. Over £3 post free. C.O.D. 25p extra.

TEXAS INTEGRATED CIRCUIT SN 76131N Stereo

pre-amp £9.65. VACUUM CONDENSERS 12, 50, 55p each 20,000v. £1-50. P. & P. 20p. 4, 5 and 8 bank 25 way uniselectors, 24V, guaranteed perfect, £3.75; £4.50; £5.87 respectively. MODULATION TRANSFORMERS made to order. They resp. 200-5000 CPS; Pri. 6000ct 3000 TV Sec. 6000ct 3000 TV Audio power 20W. £1-25. Post and packing 25p.

GET115	45p	6J4WA	65p	6060	60p
GET116	50p	GJ5	35p	1487	70p
GEX66	£1.00	GJ6GT	30p	1495	40p
NKT222	20p	19A3	25p	19A3	£5.75
RAS304A	50p	19G6	30p	19G6	£5.75
6J4WA	65p	19H4	35p	19H4	£5.75
GJ5	35p	20P4	£1.00	9001	15p
GJ6GT	30p	25L6GT	45p	9002	40p
19A3	25p	30C15	70p	9003	45p
19G6	30p	30C17	85p	9004	15p
19H4	35p	30C18	75p	9006	12p
20P4	£1.00	30P5	80p		
25L6GT	45p	30P11	70p	CR. Tubes	
30C15	70p	30P12	85p	VCR97	
30C17	85p	30P14	80p		£4.00
30C18	75p	30P17	80p	VCR517B	
30P5	80p	30P12	75p		£5.00
30P11	70p	30P19	80p	VCR517C	
30P12	85p	30P11	70p		£7.00
30P14	80p	30P13	90p	881	£8.10
30P17	80p	30P14	85p	883	£8.10
30P12	75p	35L3GT	50p	881	£8.10
30P19	80p	6X4	33p	60C6	
30P11	70p	6X5GT	25p	60D6G	£1.10
30P13	90p	60EH5	55p	931A	£5.00
30P14	85p	60E7	75p	6097C	
30P17	80p	630L2	75p		£18.00
30P12	75p	6Z4	40p	78	50p
30P19	80p	7B7	50p	80	50p
30P11	70p	7Y4	60p	723A/B	£7.00
30P13	90p	80D6	30p	803	£5.50
30P14	85p	11P2	23p	805	£12.00
30P17	80p	12AT6	35p	807	50p
30P12	75p	12AT7	35p	813	£4.00
30P19	80p	12A7	24p	822A	£2.70
30P11	70p	12A6	40p	866A	£1.25
30P13	90p	12A7	25p	931A	£4.75
30P14	85p	12BA6	25p	964	35p
30P17	80p	12B26	35p	965	35p
30P12	75p	12BH7	25p	966	30p
30P19	80p	12C8	30p	957	35p
30P11	70p	12E1	£2.35	991	40p
30P13	90p	12K5	95p	2051	70p
30P14	85p	12K7GT	45p	5933	£1.00
30P17	80p	12RGT	40p	714A X	£8.00
30P12	75p	12RGT	40p	4057	55p

Colomer (Electronics) Ltd.
170 GOLDHAWK ROAD, LONDON W12.
RETAIL: 743 4946 TRADE: 743 0899
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.



VEROBOARD

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

VERO ELECTRONICS LTD.
Industrial Estate, Chesham Road,
200 399 Tel: Chesham 340 340

GETTING BORED WITH ELECTRONICS

Some things are repetitive, once you have built an astable multivibrator, they tend to get boring—need a 555 timer? It works in mono or astable modes for long or short pulses (95p). How about building a radio tuner for your record player, the ZN414 chip makes this choice—LED lamps—£1.10, LEDs? We have a fantastic choice—LED lamps—TIL209 or FRP480, 4 for £1.50 for £10; large lamps (HP4880) 35p each, 50 for £15, RED and GREEN LEDs £1 per pair. LED displays—TIL302 (or similar) £2.50 each, TIL312 (similar to MAN4) £2 each—limited quantity, TIL360 6 digit package £15, DL34 four digit package £10, DL62 (7 1/2) £6.50. Phosphor diode displays DG10 or DG12 £2 each.

CLOCKS CLOCKS CLOCKS CLOCKS
Bywood is now foremost in the LSI clock chip market (who else has four different clock chips in stock with two more on order!). MMS311—the original—£11.50, MK5017AN with alarm and radio controls £15.50, MK5017AA with alarm or MK5017BB with calendar, either of these two is offered with a PCB, socket and suitable displays (4 DG12s) at £24.

Don't get bored, if none of the above fascinate you how about liquid crystal displays, DVM chips, etc? This technology, is here to stay, Bywood have got it or can get it—give us a try.

VAT. All prices above EXCLUDE VAT, add 10% P. & P. Please add 10p post and packing.


You can have clock data sheets for a S.A.E. or our 1973 catalogue (2nd issue) for 15p. (And we haven't even mentioned our calculators yet—but they are in the catalogue).

You may phone us for help on 0442-62757 and you can use your ACCESS card for phone or personal purchase—Service from Bywood!

BYWOOD

ELECTRONICS
181 EBBERNS ROAD, HEMEL
HEMPSTEAD, HERTS. 0442 62757

4-STATION INTERCOM

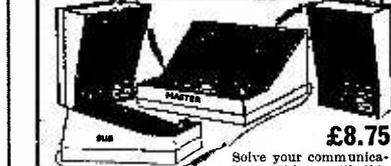

£8.75

Solve your communication problems with this 3 Sub's, in de-luxe plastic cabinets for desk or wall mounting, Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 45p

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £16.95 P. & P. 80p

INTERCOM BABY ALARM



OUR PRICE ONLY £4.50

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Complete with Battery. P. & P. 30p

TRANSFORMER TELEPHONE AMPLIFIER



£3.99

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 25p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.6)
180 KENSINGTON HIGH STREET, LONDON, W.8.


tate SQ*

4 channel decoder modules

Tate 4-channel equipment decodes all quadrasonic matrix records and broadcasts and adds dimensional realism to ordinary stereo programme sources. It also controls 4-channel tapes when played through your system and CD-4** records when used with a separate demodulator.

They are characterized by their ultra low distortion characteristics and six-pole wideband phase shift networks. These combine to produce an acoustic performance giving highly articulate sounds from the back as well as the front channels. The amplitude accuracy is better than ± 1 dB from 5Hz to 100KHz.

tate 2

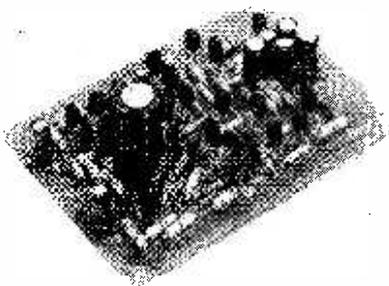

High definition SQ* quadrasonic decoder Fully built home constructor module


features: exclusive wide band phase shift network; distortion typically 0.04%. Ideal for use with other kit projects and even with the world's finest amplifiers.

Recommended retail price (excluding VAT) **£12.95**

Dimensions: 85 x 60 x 25mm

Operating Voltages: 18-30VDC at 11ma

tate 4

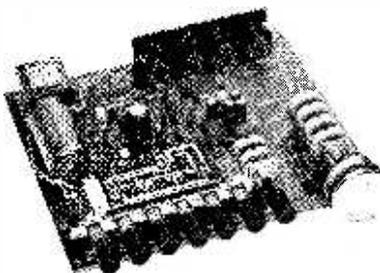

High definition SQ* quadrasonic decoder Fully built home constructor module

featuring **wide band** matrix decoding circuit board with integrated power supply, switching, master gain and exclusive rear level control.

Recommended retail price (excluding VAT) **£21.95**

Dimensions: 165 x 140 x 26mm

Operating Voltages: 110-240VAC at 3watts

Specifications

Input Impedance	40K Ohms
Output Impedance	<300 Ohms
Phase Shift Network 90 \pm 10'	20Hz-18KHz
Nominal Gain	Unity
Frequency Response \pm 1dB	5Hz-100KHz
Nominal Input Level	250mV rms
Nominal Distortion	0.025%
Clipping Point	2.5V rms
Distortion before Clipping	0.08% max.
Front Separation	>60dB
Rear Separation	>20dB

Tate Audio Transmission Equipment Limited
5-7 Covent Garden Cambridge CB1 2HS England
Telephone 0223 67873 Telex 81640

Reg. No. 105 9584

The only way to really understand the difference between ordinary stereo and SQ Quadrasonic sound is to hear it. However, if you remember the difference between mono and stereo upon hearing it for the first time, multiply the recollection of that experience by a factor of ten and you will be able to appreciate what is in store for you when you first hear SQ Quadrasonic sound.

Please send tate 2 at £14.25 each (including VAT)

tate 4 at £24.15 each (including VAT)

I enclose cash/cheque/money order

Name (BLOCK LETTERS)

Address

PW93

*TM CBS Inc. **TM Victor Japan

You'll hardly be able to believe your ears!

Can you really get sound quality like this **FOR LESS THAN £18? YES, YOU CAN! WITH THE NEW**

STEREO 21

Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable **£17.95**, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!

And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for £17.95 (plus the cost of post and packing if you buy by mail), and—to round it all off—a money-back

Guarantee if your pleasure in STEREO 21 is not complete!

Just think—in only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!

Personal shoppers and mail order price

£17.95 plus £1.50 p + p.

Diamond stylii, if required, £1.37 extra



RADIO AND TV COMPONENTS (ACTON) LTD 21C HIGH STREET ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2

Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope Goods not despatched outside U.K.

VISCOUNT III— a boost in the output.

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! And the teak finish will harmonise and enhance virtually any style of interior decor! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back.

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have never experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair + £2.20 p. & p. **Duo Type III** Size approx. 23½in x 11½in x 9½in. Drive unit approx 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM 1

Viscount III R102

amplifier £24.20 + £1 p & p
2 Duo Type II speakers £14.00 + £2.20 p & p
Garrard SP25 Mk III with MAG cartridge
/plinth & cover £18.00 + £1.75 p & p
total **£56.20**

Available complete for only **£49.00** + £3.50 p & p

PRICES: SYSTEM 2

Viscount III R102

amplifier £24.20 + £1 p & p
2 Duo Type III speakers £32.00 + £3.30 p & p
Garrard SP25 Mk III with MAG cartridge
plinth & cover £18.00 + £1.75 p & p
total **£74.20**

Available complete for **£65.00** + £4 p & p

STILL ONLY **£49 COMPLETE**



THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive 'earth' vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms.



Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep. Circuit diagram and comprehensive instructions 55p free with parts. Fully retractable and lockable car aerial £1.37 post paid.

CAR RADIO KIT £6.60 p. and p. 55p. Speaker with baffle and fixing strips £1.65, + 23p p. & p. post free if bought with the kit. Send stamped addressed envelope for leaflet. If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

SOUND 50

45 WATT MONO AMPLIFIER. Ideal for Disco. Output Power: 45 watts R.M.S. (Sine Wave). Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19½ x 10½ x 8ins. Amplifier **£31.35** output for 3, 8 and 15 ohm speakers. + £1.65 p. & p.

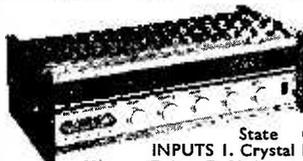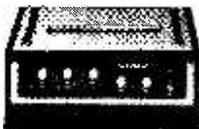

RELIANT Mk IV

*5 Electrically Mixed inputs.
*3 Individual Mixing controls.

*Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid

State Circuitry. *Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil

Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide

range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Output 20 watts into 8 Ω (suitable for 15 Ω.) Size approx. 12½ x 6 x 3½ ins. **£13.50** p. & p. 60p

UNISOUND MODULES


ONLY £7.64 + 55p. p & p

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

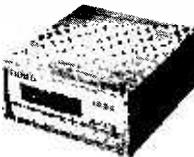With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. The Viscount III, the fabulous Stereo 21 and the Unisound Modules **£9.90** plus p. & p. will accept this unit, simply connect up.



Come and listen at the year's most exciting exhibition


Join thousands of Hi-Fi enthusiasts in an atmosphere that will set your ears tingling with excitement. The 1973 Audio Festival and Fair looks like being the best yet – and will run up to and include Sunday. The international giants of the Hi-Fi industry will be there – showing the latest specialist equipment: unit audio, tape recorders (cassette, cartridge and reel-to-reel), loudspeakers, tuners, receivers, amplifiers, radios, tapes and discs. There will be continuous demonstrations in specially constructed Audio Studios – and the Sunday Mirror is giving away £500 worth of equipment as prizes in exciting competitions. Don't miss this great event.

THE 1973 INTERNATIONAL AUDIO FESTIVAL AND FAIR


Sponsored by the Sunday Mirror

OLYMPIA London

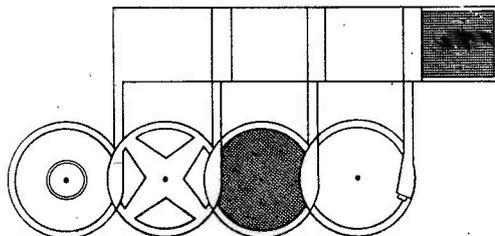Tuesday 23 October to
Sunday 28 October
Weekdays 10 am to 9 pm
Sunday 11 am to 7 pm
Admission 45p



ELECTRONIC ORGAN KITS

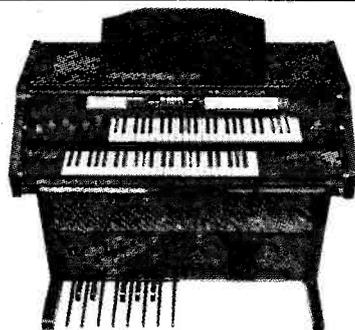

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2x5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55.

V.A.T. please add 10%—show separately on order.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT, ELECTRICAL HOUSEHOLD APPLIANCES AND MUSICAL INSTRUMENTS.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE ROAD, LONDON, S.W.18
TEL: 01-870 4949
ALSO AT BRETT RD., HACKNEY E8, TEL. 986 8455



NEW STEPHENSPEAKERS

A new range of loudspeaker kits and cabinets with a style and specification for every purpose. You'll be cheating a bit if you tell your friends "made it myself". We supply superb craftsmen built fully finished cabinets in beautiful stain and scuff resistant vinyl in white or teak.

Just fit the speaker cloth (supplied) and screw in your speaker.

**HIGH QUALITY
AT LOW COST**

Send for our free booklet
"Choosing a Speaker"



STEPHENSPEAKERS,
WILMSLOW AUDIO, Dept. 'PW', Swan
Works, Bank Square, Wilmslow SK9 1HF

Build yourself a TRANSISTOR RADIO

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

Total building cost

£9.35


P. P. & Ins. 52p

(Overseas P. & P. £1.05)

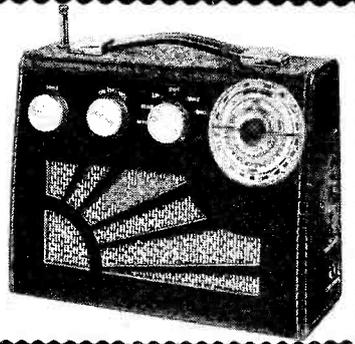

ROAMER EIGHT Mk I


NOW WITH VARIABLE TONE CONTROL

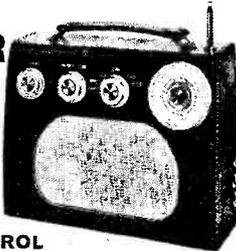

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

Total building cost **£7.68** P. P. & (Overseas P. & P. £1.05) Ins. 47p.

ROAMER SEVEN MK IV

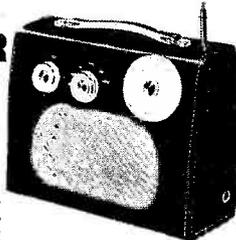

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).


Total building costs **£6.58** P. P. & (Overseas P. & P. £1.05) Ins. 47p.

ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler, band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves.

3in. Speaker. 8 stages—5 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Plans and parts price list 25p (FREE with parts).

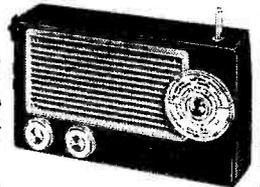Total building costs **£4.38** P. P. & (Overseas P. & P. £1.05) Ins. 31p



POCKET FIVE

8 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors, and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Plans and parts price list 15p (FREE with parts).

Total building costs **£2.50** P. P. & (Overseas P. & P. 65p) Ins. 24p



TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Plans and parts price list 15p (FREE with parts).

Total building costs **£2.75** P. P. & (Overseas P. & P. 65p) Ins. 25p




TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

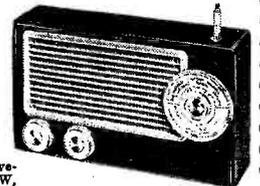Total building costs **£4.95** P. P. & (Overseas P. & P. £1.05) Ins. 35p



"EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.
Parts price list and plans 25p (FREE with parts).

(Overseas P. & P. £1.05)

All parts including **£6.05** P. P. & Case and Plans Ins. 33p

FULL AFTER SALES SERVICE

Callers side entrance "Lavells" Shop
Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.
PLEASE NOTE: ALL PRICES INCLUDE VAT

RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367
Reg. no. 788372

I enclose £..... please send items marked.

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for

Name

Address

(Dept. LPW22.)

TERMS Retail mail order subject to £1.00 minimum order.
Cash with order only. Trade and educational establishments
M/AC on application (minimum £5.00).

Postage 10p inland, 25p, Europe.


GUARANTEE: All goods carry full manufacturer's
warranty. Get in touch today for a complete
run-down of devices available from SCS (include SAE).



SCS COMPONENTS, P.O. Box 26,
Wembley, Middlesex HA0 1YY.

The 'Professional' Amateur Supplier

device of the month ZN414

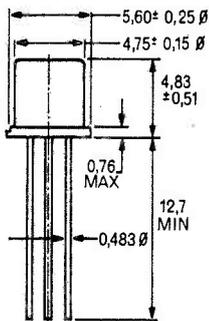


The Ferranti ZN414 is a complete a.m. radio circuit which operates from 1.1 to 1.8 volts and requires only battery, earphones and antenna plus a tuning capacitor and two decoupling capacitors. The ZN414 features: medium and long waveband, good stability on assembly, no setting up of IF coils, plus much more.

a complete a.m radio circuit for just

£1.20
+
VAT

compatible device MFC 4000B

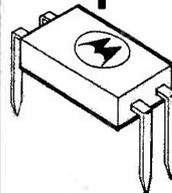

The Motorola 1/4-Watt Audio Amplifier is designed for the output stage of battery powered portable radios.

- * 250 mW of Audio Output Power
- * Low Standby Current—3.5 mA typical
- * Low Harmonic Distortion
- * Reduces Component Count in Portable Radios by Two Transformers and Two Transistors
- * Eliminates Costly Component Matching Requirements

motorola 1/4 watt
audio amplifier
MFC 4000

50p
+
VAT

Multicore Solder Cream for high quality joints in the Electronics Industry

New Multicore Solder Cream was designed for jobs where second best will just not do. Like manufacturing diodes for instance. Or making a tuner chassis or soldering thick film circuits. Multicore Solder Cream, a finely graded solder alloy powder in a thixotropic organic vehicle, is easier, quicker, more economic and more reliable than conventional techniques.

Multicore Solder Cream is different. It doesn't spit or need stirring. It can be applied by syringe, automatic dispensers or screen printing—giving instant soldering with

good spread, strong joints with low contact angles. Suitable as a temporary adhesive during assembly; the clear colour flux residue—without solder globules—makes inspection easier. There are three types of Multicore Solder Cream— one of them may be just what you're looking for.

For full information on this or any other Multicore products, please write on your company's letterhead direct to:



Multicore Solders Ltd., Maylands Avenue, Hemel Hempstead
Herts. HP2 7EP. Tel: Hemel Hempstead 3636. Telex: B23663

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. £2 30p.

P-C BOARDS (not computer panels)

- 1 off 6 transistors single wave band
- 1 off 4 transistor audio
- 1 off 3 transistor £1.60 the three.

Transistor F.M. Stereo Multiplex Decoder. Size: 5 1/2 x 2 1/2 x 1 1/2. As used in well known British stereo units with circuit. £3 75.

GARRARD SP25 MK. II less Cartridge. £10 00.

10 COMPUTER PANELS packed with components including one panel with 2 Power Transistors. £1 00.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 30p each 4 for £1 00.

All Transistor STEREOGRAM CHASSIS. Medium, Long and VHF/FM. 3 Watts per channel S/M rating. With circuit service manual. Less tuning scale which can be obtained from well known British manufacturer. . . £20.

Colour Translator panels, as used on well known British E.V.R. Teleplayer. All new panels and components. Type and contents of transistors listed below. Each panel £3 50 each.

X605 . . 14 off BC148, 2 RCA ca 3054(jc), 1 crystal 4.433618MHz, Z607 . . 12 off BC148, 1 BC158, 1 BC108, 1 RCA ca3046, 1 RCA ca3045 (jc).

Z608 . . 23 off BC148, 2 BC158.

Z612 . . 12 off ME4102, 2 BC251B, 1 BFY50.

CRYSTAL CALIBRATOR (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz-10MHz (harmonics up to 30MHz) power required 300V DC 15mA. 12V 0.3A DC. Test equipment for 62T M/RC. £2 50 each.

ALL ITEMS INCLUDE VAT

All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

Choose a Heathkit project.... make your spare time more rewarding



And your first step is absolutely Free—simply send today for the latest Hi-Fi/Electronics catalogue from Heath, the world leaders in electronic kits. Every model is designed with the beginner in mind, and the assembly manuals are famous for their clarity and easy to follow step-by-step instructions. The latest Heathkit catalogue contains many new kit projects that will appeal to you and all our models offer unbeatable value for money. Payment is so easy too—choose cash or low deposit terms (starting at £2 per month for up to £40 credit).

Anyone can build a Heathkit model using only a few simple tools found in most homes and added to this is a technical consultant service both before and after purchase.

These are just a few of the unshakeable reasons why Heathkits are so popular throughout the world. Some samples from our range are shown here.

LOUDSPEAKER KITS feature fully finished cabinets for fast, easy building.

STEREO HI-FI SYSTEMS and **SEPARATES** offer state-of-the-art performance and design.

AUTOMOTIVE TEST AND ANALYSER KITS make car testing and trouble-shooting a pleasure.

LOW PRICED TESTERS AND INSTRUMENTS for hobbyist and technician.

PORTABLE RADIOS AND HOME/OFFICE INTER-COMS

DESK AND POCKET ELECTRONIC CALCULATORS


METAL LOCATORS of advanced solid-state design.

AMATEUR RADIO AND SWL RECEIVERS etc.

even a robust **BATTERY CHARGER KIT**

And many more models too numerous to mention here.

FREE Catalogue

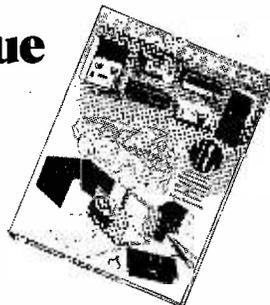


Please send me a FREE Heathkit catalogue and details of your Cash and Low Deposit terms

Name _____

Address _____


HEATH Schlumberger Heath (Gloucester) Limited, Dept. PW-09-73 Gloucester GL2 6EE. Telephone 0452 29451

RADIO & TV SERVICING

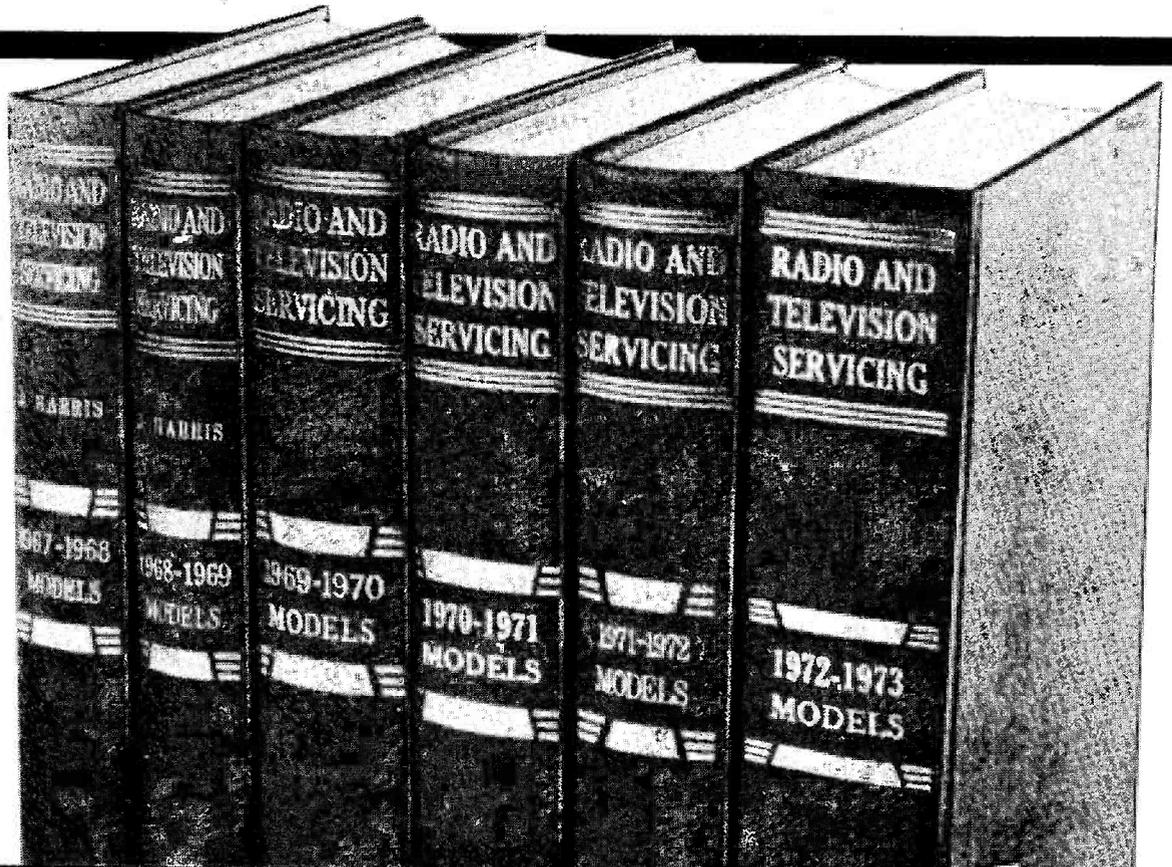

Essential data for over 1500 popular models

With this vast 6-volume library at your fingertips you have all the necessary servicing data you need covering almost every popular model from 1967 to the very latest on the market today. And not only radio and TV but stereograms, record players and tape recorders too. Much of the earlier information on this equipment is quite unobtainable elsewhere and *Radio & TV Servicing* is now the only available source of technical data. The 1973 edition, now ready, brings the library right up-to-date with abstracts from manufacturers' service bulletins issued during the past year. *Radio & TV Servicing* is the only work of its kind - a money-spinner that no service engineer should be without.

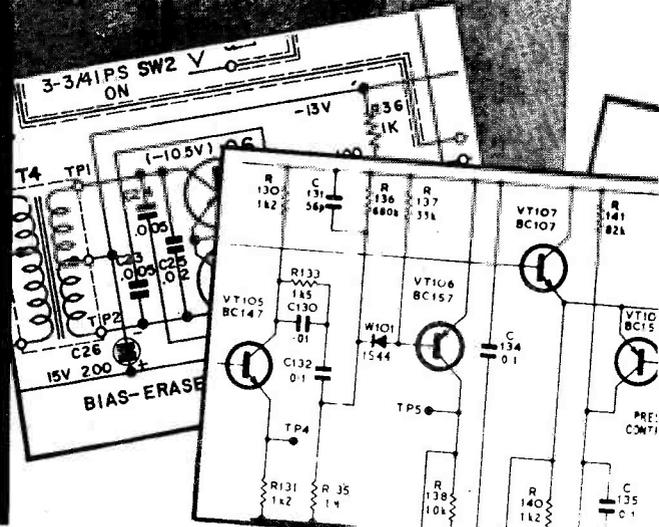

6 volume library '67-'73 is now ready

**the
only work
of its kind
anywhere**

Speedier, more efficient servicing means increased turnover ...

This library is a gold-mine of technical information. Six hard-bound volumes giving vital data on more than 1500 models of Television (colour and mono), Radios, Car Radios, Stereograms, Record Players and Tape Recorders. More than 4000 pages clearly display thousands of circuits, printed panel diagrams, component layout diagrams, waveform graphs, block diagrams, etc. Over 800 pages, devoted entirely to Colour TV, include installation instructions, new term explanations, purity adjustments, colour balance, static convergence and a wealth of invaluable information. Here, in fact, is all the data you need for efficient and speedy repair work.

Your Guarantee

Sending for these valuable books, even though you also enclose your remittance, commits you to nothing. Unless you are absolutely satisfied you are perfectly free to return the set and if you do so within 10 days of delivery your money will be refunded in full and without question.

How to get your 6-volume set

Detach the Order Form below and send it, with the appropriate remittance to :

Purnell Book Service Ltd.,
Box 20 Abingdon, Berks, OX14 4HE

Makes of Colour TV include :

Alba, Baird, Bang and Olufsen, B.R.C., Bush, Decca, Dynatron, Ecko, Ferguson, Ferranti, G.E.C., Invicta, H.M.V., Marconiphone, I.T.T./K.B., Masteradio, Murphy, Philips, Pye, Sobell, Stella, Ultra, Hitachi, Thorn Consumer Electronics, Korting, R.G.D., Sony, Telefunken.

All these makes of Mono TV, Radios, Car Radios,

Stereograms, Record Players, Tape Recorders :

Aiwa, Alba, Baird, Bang and Olufsen, Beogram, Beolit, Blaupunkt, B.R.C., Bush, Cossor, Crown, Dansette, Decca, Defiant, Dulci, Dynatron, Eddystone, Ecko, Elizabethan, Ferguson, Ferranti, Fidelity, G.E.C., Grundig, Hacker, Halcyon, H.M.V., Hitachi, Invicta, I.T.T./K.B., JugoElektra, Klinger, Loewe Opta, Marconiphone, Masteradio, Monogram, Murphy, National, Nivico, Perdio, Peto Scott, Philco, Philips, Portadyne, Pye, Radiomobile, Radionette, R.G.D., Roberts' Radio, Robux, Sanyo, Sharp, Sobell, Sony, Standard, S.T.C., Stella, Stereosound, Telefunken, Teletron, Thorn, Sanyo, Ultra, Unitra, Van Der Molen, World Radio, Thorn Consumer Electronics, Elpico, Rigonda (USSR), Waltham.

Plus such developments as :

Mullard Integrated Units, Electronic Video Recording and Reproduction - EVR system, Radio Receivers - Car radios, Stereo Multiplex reception, Capacitance Diode Tuning, Colour Television Test Equipment - Crosshatch Generator, Degaussing Coil, E.H.T. Meter, Colour Bar Generator, Cathode Ray Oscilloscope, Power Supply requirements, Alignment, Circuit design.

To: Purnell Book Services, P.O. Box 20, Abingdon, Berks OX14 4HE

Please send me the 6-volume set of RADIO & TV SERVICING for which I enclose cheque/P.O. No. _____, crossed and made

payable to Purnell Book Services Ltd.

for the full cash price of £27.75

tick

for £10 deposit to be followed by 4 successive

appropriate

monthly payments of £4.75 (total £29)

box

I understand that unless I am entirely satisfied I may return the volumes in good condition within 10 days and my money will be refunded in full.

BLOCK LETTERS PLEASE

Name _____

Address _____

TRADE APPLICATION (To be accompanied by Trade Order)

Please supply _____ 6-volume set(s) of RADIO & TV SERVICING at £27.75 per set. (Credit 30 days)

BLOCK LETTERS PLEASE

Name _____

Company _____


Signature _____

IMPORTANT : Individual volumes are available on application.

Please return entire form. Available U.K. only

025

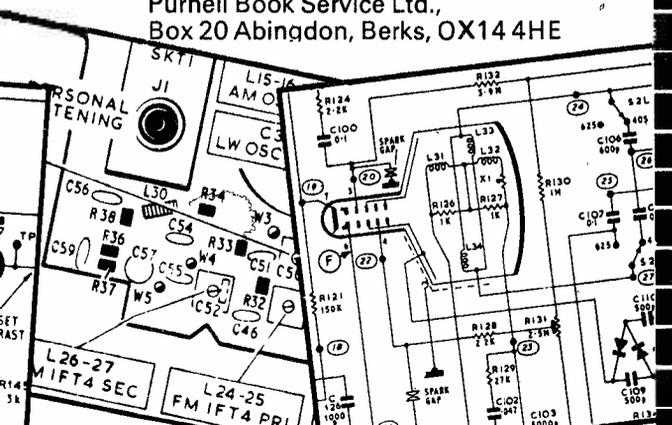Purnell Book Services Ltd. Reg London 958963, 49 Poland St., London W1



DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee
 WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

ALL PRICES ARE INCLUSIVE OF V.A.T.

TURNTABLES

Please add 95p P. & P. & Ins.

ESR MP60	£8-35
Garrard SP25 Mk III	£8-70
Garrard SL65B	£12-30
Garrard AP76	£16-45
Garrard 401	£22-45
Garrard Zero 100 sgle.	£30-55
Garrard Zero 100 auto.	£33-20
Goldring G185/P&C	£59-35
Goldring G101P/P&C	£19-40
Goldring GL72	£21-95
Goldring GL72/P	£28-55
Goldring GL75	£27-40
Goldring GL75B	£31-95
Goldring GL75 Lid	£3-85
Leak Delta	£44-20
Pioneer PL12D	£35-10
Thorens TD125	£55-15
Thorens TD125 AB	£81-40
Thorens TD160 AB&C	£44-90
Wharfedale Linton with cart.	£25-00

SPEAKERS

£1-65 for P. & P. (per pair)

Amstrad Acoustra 1500	£27-95
Amstrad Acoustra 2500	£31-95
Apollo 138	£11-05
B&W DMX 5	£31-95
Celestion Ditton 15	£43-90
Celestion Ditton 44	£74-90
Goodmans D/Maxim	£39-70
Goodmans Mezo 3	£49-70
Goodmans Havant	£34-45
Keltron LS 100	£30-30
Leak 150	£31-95
Sinclair Q16	£10-95
Sinclair Q30	£30-60
Wharfedale Denton II	£25-70

TUNER/AMPLIFIERS

Please add £1-10 P. & P. & Ins.

Alpha FR 3000	£61-35
Goodmans Module 80	£59-90
Goodmans Mod. 80 Com.	£107-75
Goodmans Mod. 90	£74-65
Goodmans One-Ten	£86-65
Leak Delta 75	£107-75
Rogers R/brook cha.	£62-30
Rotel 150A	£81-90
Rotel 200A	£58-95

CARTRIDGES

Please add 11p P. & P. & Ins.

Goldring G850	£2-85
Goldring G800	£3-70
Goldring G800E	£3-45
Goldring G800SE	£12-15
Shure M3D	£3-15
Shure M44E	£4-40
Shure M55E	£5-00
Shure 75ED Type 2	£9-35
Shure V15	£25-95
Shure M75EJ Type 2	£6-10

All prices correct at time of press E. & O. E. and are subject to alterations.

AMPLIFIERS

Please add 95p P. & P. & Ins.

Amstrad 8000 Mk II	£16-45
Amstrad IC2000	£38-80
Amstrad Integra 4000	£33-50
Alpha Highgate FA400	£39-05
Global 10+10	£19-75
Global 20+20	£23-20
Leak Delta 30	£31-95
Leak Delta 70	£63-25
Metrosound ST20E Mk II	£29-60
Metrosound ST60	£50-85
Rogers R/brook Ch.	£41-15
Rogers R/brook Ch.	£44-30
Rogers R/bourne Ca.	£54-25
Rogers R/bourne Ca.	£56-90
Sinclair 2000	£24-15
Sinclair 3000	£31-00
Sinclair 605	£21-45
Sinclair PRO 60 2 x Z30/PZ5	£16-40
Sinclair PRO 60 2 x Z30/PZ6	£19-45
Sinclair PRO 60 2 x Z50/PZ8	£25-25

Trans.

Sinclair AFU (Filter Unit)	£24-95
Sinclair Stereo 60 Pre-amp	£7-35
Sinclair IC 12 (Int. Circ.)	£2-20
Sinclair Z30 Amp.	£3-85
Sinclair Z50 Amp.	£4-50
Sinclair PZ8 Power Supp.	£4-20
Sinclair PZ6 Power Supp.	£6-15
Sinclair PZ8 Mains Trans.	£4-95
Sinclair PZ8 Power Supp.	£6-15

TUNERS

Please add 93p P. & P. & Ins.

Alpha Highgate FT 150	£33-30
Amstrad Multiplex 3000	£24-80
Leak Delta FM (Cased)	£47-45
Leak Delta AM/FM	£36-45
Metrosound FMS 20 Mk II	£34-85
Rogers R/brook FET4 (Cha.)	£29-50
Rogers R/brook FET4 (Cased)	£31-90
Rogers R/bourne FET4 (Cased)	£41-25
Sinclair PRO70 Mod.	£14-90
Sinclair cased tuner	£62-15

SPEAKER UNITS

Wharfedale Unit 3	£15-60
Wharfedale Unit 4	£27-25
Wharfedale Unit 5	£39-60

FANTASTIC OFFER GARRARD SP25 Mk III.

Goldring G800. Teak finish, plinth and tinted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1-75 for P. & P. & Ins. **£14-20**

PLINTH AND COVERS

£3-02*
 For Garrard SP25, 2025 T, 3000, BSR McDonald MP60 £3-08 P. & P. 71p. For AP76, SL72B, SL95B, etc. £4-51 + 71p P. & P.



SURPLUS BARGAINS

The following items are new, **BLOWER MOTORS** small double ended type 6 to 28v DC £1-79. **HEAD & MIKE SETS** for 19 set m.c. type with soft rubber ear pads £1-70. **CABLE** 25 core coloured un screened 2 5/9" lengths for 86p. **METER UNIT X** pointer dual 115 Ua movements for 1155Rx £1-58. **METER UNIT** center reading type scale marked L & R £1. **TRIMMERS** air spaced ceramic 20pf 10 for 55p also ceramic dielectric 10/110pf 5 for 55p. **MIKES** American type T.17 carbon 100 ohm with press to talk switch £1. **HEADPHONE** matching trans & lead high to low res with 5ft cord & standard jack plug 60p. **WAVEMETER & OSC** unit covers 150 to 230 Mc/s with charts, spares, inst etc tested £16-50. **VOLTAGE DIVIDERS** ratio 10 & 100.1 20Kv pk wk for use with scope okay for T.V. servicing £2-45. 10K ohm pots w.w. type 3 for 33p. **C.R.TS** type 7B7A flat face, 6-3 heater blue/yell phosfor with base conn, okay slow scan T.V. £1-73. **CONTROL UNIT** with pot core, luf 1% cond, 3 min valves etc £1. **SILICON DIODES** type ZS78 Ferranti 800 PIV at 750 Ma 15 for £1-10. **METERS** battery charger type M.I. 1.5a FSD 66p. **RADIO TELEMETER UNITS** 240v I/P L.F. Rx unit approx 120Kc with 6 valves, Spk 2, mtrs, tape unit, coin box in neat case, with circ and mods for 200Kc radio 2. £4-18. **SELSYNS** for use on 115v 50c/s supplied in pairs with a 360° scale & pointer. £4. **METER UNIT** vehicle press gauge elec operated scale 0 to 120 with mt brk 44p. **LAMPS & NEONS** 24v double fil type 14 watt ea with silvered reflector 5 for 65p. Neons wire ended type 1/25th watt size 1 x 1/4" req 470K res for 240v 10 for 55p. **BATTERIES** Aircraft type unspillable 24v 25 amp/Hr can be split to make 2 12v if req with inst £12-25. **TRANSFORMERS** all 230v pria. H.T. type sec 1125-0-1125v at 565Ma £7-70. H.T. type sec 415-143-0-143-415 at 360 Ma on 415 and 120 Ma on 143v £3-25. L.T. type sec 27v 41 amps cont £13-20. **TAG STRIPS** solder type 24 way 20 for 55p. The following items are ex equip. **SELECTOR UNIT** with 24v mtr., gears, large 24 way swt, meter 1 Ma 2 1/2sq, all in usefull case size 12 x 6 x 7" £2-70. **RADAR TEST SET** with 3" tube VCR138, 4" dia 50 Ua meter, Klystron, 21 misc valves min & octal all in case size 17 x 11 x 16 contains high cycle P.U. good basis for building scop £10-45. **VIDICON CAMERA TUBES** graded according to scan marks, by E.E. & E.M.I. data supplied £9 & £6 ea. **PANEL METERS** supplied as they come all serviceable 4 different for £1-25. **METAL CASES** size 9 x 7 x 5" inc lid, fitted handle & feet, painted grey 86p also 9 x 3 1/2 x 3" with parts finish black 64p. **RX UNIT** motor tuned approx 180 to 240 Mc/s with I.F. strip, 24v mtr etc £3-15. **METERS** 500Ua scale 0 to 5 1/2" osd on panel with swts £1-25 also 1 Ma fsd with special scale markings 2 1/2 Rd 81p also 500 Ua 2 1/2 OSD scale 0 to 5 £1-20. **DIODES** type Ferranti ZR22 200 P.I.V @ 8 amps 4 for 66p. **PANEL ASS** with 18 200 P.I.V. 1-5a diodes & misc parts 88p. **I.F. STRIPS** 45Mc/s with 6 valves, plugs etc £1-40. **RX UNIT** R4187 xtal controlled Rx covers 2-8 to 18 Mc/s in 3 bands, double conversion req, 24v DC supplied with circ and some notes also 3 xtals for testing £9-90. **TRANSFORMERS** H.V. 230v pria, sec 2-8Kv @ 600 Ma Biphase £14-63. **RELAYS** miniature 12v 2p c/o 2 x 2 x 1/2" 2 for 66p. **INVERTOR TRANS.** 12v to 300v @ 150 Ma with circ. £1.90.

ALL THE ABOVE PRICES INC. CARR./ POST & V.A.T. S.A.E. WITH ENQUIRIES, AND FOR LIST

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL

PHONE 444278 (0742)

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept (PW9) 174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. **LATE NIGHT FRIDAY 7 p.m.**

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, or Cash by Registered Mail. **CALLERS:** Please note that enquiries can only be accepted together with cheque cards (not Barclay Cards).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

SPECIAL OFFER !!!

SMALL ELECTROLYTICS

Ref. No.	Capacity	Voltage	Price	Ref. No.	Capacity	Voltage	Price
H8/2	2.2µf	25v	4p	H7/4A	64µf	35v	5p
H8/2A	3.3µf	25v	4p	H7/5	30µf	15v	4p
H8/3	3µf	50v	4p	H7/6	100µf	25v	5p
H8/3A	4µf	50v	4p	H7/6A	100µf	15v	4p
H8/4	4.7µf	25v	4p	H7/7	100µf	25v	4p
H8/4A	5µf	64v	4p	H7/8	125µf	16v	5p
H8/5	5µf	10v	4p	H7/8A	100µf	35v	6p
H8/5A	5µf	150v	4p	H7/9	100µf	35v	6p
H8/6A	10µf	10v	4p	H7/9A	125µf	4v	4p
H8/7	10µf	70v	4p	H7/10	125µf	25v	6p
H8/8	16µf	35v	4p	H7/10A	160µf	2.5v	3p
H8/8A	16µf	16v	4p	H7/11	160µf	25v	6p
H8/9	20µf	6v	2p	H7/11A	150µf	16v	5p
H8/9A	20µf	70v	4p	H7/13A	200µf	25v	8p
H8/10	22µf	50v	4p	H7/14	220µf	50v	10p
H8/10A	22µf	100v	4p	H7/14A	220µf	18v	6p
H8/11	25µf	12v	4p	H7/15	220µf	25v	5p
H8/11A	24µf	275v	4p	H7/15A	220µf	35v	10p
H8/12	32µf	15v	4p	H6/1A	250µf	4v	3p
H8/12A	30µf	10v	4p	H6/3A	320µf	2.5v	3p
H8/13A	32µf	50v	4p	H6/4	320µf	10v	4p
H8/14	40µf	25v	5p	H6/4A	330µf	16v	5p
H8/14A	40µf	16v	4p	H6/5	330µf	25v	10p
H8/15	47µf	50v	4p	H6/5A	330µf	35v	15p
H8/15A	40µf	35v	4p	H6/7	400µf	15v	5p
H7/1	50µf	6v	3p	H6/8	470µf	25v	10p
H7/1A	50µf	10v	4p	H6/8A	470µf	35v	20p
H7/2	50µf	50v	4p	H6/9A	400µf	40v	20p
H7/2A	64µf	2.5v	2p	H6/10	750µf	12v	5p
H7/3A	64µf	25v	4p	H6/13A	1000µf	25v	16p
H7/4	64µf	15v	4p	H5/2A	2200µf	16v	15p

ALL GOODS PLUS 10% V.A.T.

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series		Working Voltage Vdc.	Capacitance µF	Max. Ripple Current at 50°C	Weight	Price
071 15332	16		3300	2.5 amps	1oz	15p
071 15472	16		4700	3.9 amps	1oz	17p
071 15682	16		6800	5.8 amps	1½oz	22p
071 15103	16		10000	7.9 amps	2½oz	27p
072 15752	16	7500 + 7500		10.5 amps	3oz	37p
072 15113	16	11000 + 11000		13.8 amps	4oz	49p
071 16222	25	2200		2.2 amps	1oz	15p
072 16502	25	5000 + 5000		9.6 amps	3½oz	37p
072 16752	25	7500 + 7500		12.6 amps	4½oz	49p
072 17342	40	3400 + 3400		9.1 amps	3½oz	37p
072 17502	40	5000 + 5000		12.0 amps	4½oz	49p
071 18681	63	680		2.1 amps	1oz	15p
072 18172	63	1650 + 1650		7.8 amps	3oz	37p

106 and 107 Series		Working Voltage Vdc.	Capacitance µF	Max. Ripple Current at 50°C	Weight	Price
106 15103	16		10000	7 amps	2½oz	65p
106 16223	25		22000	17 amps	16oz	£1.12
106 17103	40		10000	12 amps	7½oz	94p
106 18153	63		15000	28 amps	18oz	£1.79
107 10222	100		2200	10 amps	5½oz	74p

A further 10% discount on lots of 100 of any one type.
Please calculate the weight of your order and include appropriate postage.

Not over	Ordinary Parcels	Not over	Ordinary Parcels
1lb	16p	10lb	37p
2lb	21p	14lb	47p
4lb	25p	18lb	57p
6lb	29p	22lb	67p

£1 100 $\frac{1}{2}$ WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

£1 1 VERO-BOARD CUTTER
5 2½ in. x 1 in. x 15 BOARDS
50 SQ. INS. "ODD PIECES"
VERO

£1 20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108 ETC.

£1 6 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS
& CAPACITORS

POSTAGE 15p

POSTAGE 15p

POSTAGE 15p

POSTAGE 25p

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

£1 1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT

£1 100 RESISTORS
100 CERAMIC CAPACITORS
(ASSORTED TYPES)

POSTAGE 15p

POSTAGE 15p

POSTAGE 15p

POSTAGE 15p

NEW

ALL SILICON!



PRACTICAL WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4½" x 3½" x 2". Complete assembly and wiring manual 25p, supplied with de-luxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.
Price: Standard Kit£7.97 U.K. Post Free
De-Luxe Kit£9.62 U.K. Post Free
Quantity Discounts:
Trade and Overseas 1-5 Nett 6-9 Less 10%
Enquiries Invited 10-49 Less 15% 50-99 Less 20%
Mail Order Only 100-999 Less 25% 1000 up Less 30%

ALL PRICES INCLUDE VAT

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365

P. C. BOARDS



FOR P.W. PROJECTS
REVERBERATION UNIT
8 WATT AMPLIFIER & PRE-AMP
LOUDHAILER PRE-AMP & SIREN GENERATOR
WIBRASONIC GUITAR PRE-AMP
DIGITRONIC DIGITAL CLOCK
AND ALSO FOR MANY P.E. PROJECTS
SEND AN S.A.E. FOR OUR FREE LIST
(and with all enquiries please)
P.S. We also have components for most of the PCBs.

PHONOSONICS

DEPT PW8, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
MAIL ORDER ONLY

LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed— build as you learn with the exciting new 'Technatron' kit. No

Extras. Tools, transistors, meter etc. All supplied. You could build a radio in weeks.




SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV, ELECTRONICS, C & G, TELECOMMS ETC.

Dept. BPW19 Aldermaston Court, Reading RG7 4PF
Name.....
Address.....
Age..... CV BPW19



I.L.P. (Electronics) Ltd

100 WATTS!

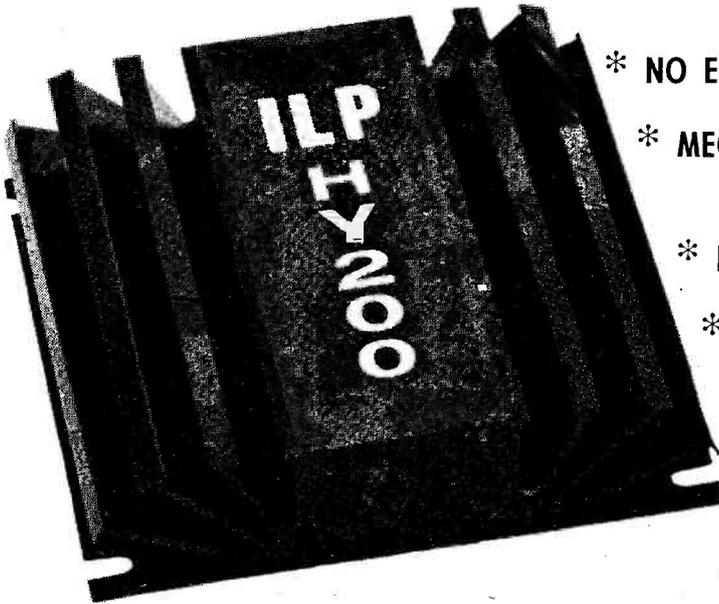

- * NO EXTERNAL COMPONENTS
- * MECHANICALLY & ELECTRICALLY ROBUST
- * INTEGRAL HEATSINK
- * HERMETICALLY SEALED UNIT
- * ATTRACTIVE APPEARANCE
- * LOW COST
- * BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

OUTPUT POWER: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10k Ω . **INPUT SENSITIVITY:** 0Dbm (0.775volt RMS). **LOAD IMPEDANCE:** 4-16 Ω . **TOTAL HARMONIC DISTORTION:** less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz-50KHz \pm 1Db. **SUPPLY VOLTAGE:** \pm 45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE:** £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	Eqvt
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1216 OCS1D
T4	8 2G381T OC81
T5	8 2G382T OC89
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G417 AF117

All 65p each pak

ND 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for ESX 31, C 407, 2N 1893 120vcb.

1	25	100+
0-19	0-17	0-16

Sil. trans. suitable for P.E. Organ. Mip To-18 Eqvt. ZTX300 8p each. Any Qty.

GP 100 TO3 METAL CASE GERMANIUM

Vebo=80V. Vcco=30V. I.C.=10 amps. Ptot=30W. hfe=80-170. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-48	0-44	0-40

GP 300 TO3 METAL CASE SILICON

Vebo=100V. Vcco=60V. I.C.=15 amps. Ptot=115W. hfe=20-100T. 1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1	25	100+
0-55	0-58	0-51

NEW 6th EDITION TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. 99p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

UT 46 UNIUNCTION TRANSISTORS

Direct replacement for TIS 43rand BEN 3000 also electrically equivalent to 2N2646

0-30	0-28	0-22
------	------	------

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM TO 2N706/8, BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in NPN Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	0-55
50	For	1-10
100	For	1-92
500	For	8-25
1000	For	14-30

SIL. G.P. DIODES 2p

300mV 30. 0-55
40pV (Min.) 100. 1-65
Sub-Min. 500. 5-65
Fully Tested, 1,000. 9-90
Ideal for Organ Builders.

R 2400 TO3 NPN SILICON HIGH VOLTAGE

Vebo=250V. Vcco=100V. I.C.=6 amps. Ptot=30W. hfe=typ. 20
1T=5MHz.

1	25	100+
0-55	0-50	0-44

AD161/162

M/P COMP PNP TRANS. OVER GERM. EST PRICE OF 60p PER PAIR.

FOR OUR AUDIO & ELECTRONIC COMPONENTS

See this months PRACTICAL WIRELESS

SILICON PHOTO TRANSISTOR. TO-18 Lens end

NPN Sim. to BP x 25 and P21. BRAND NEW. Full data available. Fully guaranteed.

Qty. 1-24 25-99 100 up
Price ea. 40p 44p 38p

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 2p
Q1	20 Red spot transistors PNP	0-55
Q2	16 White spot R.F. transistors PNP	0-55
Q3	4 OC 77 type transistors	0-55
Q4	6 Matched transistors OC44/45/81/81D	0-55
Q5	4 OC 75 transistors	0-55
Q6	5 OC 72 transistors	0-55
Q7	4 AC 128 transistors PNP high gain.	0-55
Q8	4 AC 126 transistors PNP	0-55
Q9	7 OC 81 type transistors	0-55
Q10	7 2N2996 Sil. Epoxy transistors	0-55
Q11	2 AC 137/138 Complementary pairs PNP/NPN	0-55
Q12	3 AF 116 type transistors	0-55
Q13	3 AF 117 type transistors	0-55
Q14	3 OC 171 H.F. type transistors	0-55
Q15	7 2N2996 Sil. Epoxy transistors mixed couples	0-55
Q16	2 GRT880 low noise Germanium transistors	0-55
Q17	5 NPN 2 x ST.141 & 3 x ST.140.	0-55
Q18	4 MATT 2 x MAT 100 & 2 x MAT 120	0-55
Q19	3 MATT 3 x MAT 101 & 1 x MAT 121	0-55
Q20	4 OC 44 Germanium transistors A.F.	0-55
Q21	4 AC 127 NPN Germanium transistors	0-55
Q22	20 NKT transistors A.P. I.F. coded	0-55
Q23	10 OA 202 Silicon diodes sub-min.	0-55
Q24	3 OA 81 diodes	0-55
Q25	15 IN014 Silicon diodes 75 PIV 50mA	0-55
Q26	8 OA95 Germanium diodes sub-min	0-55
Q27	2 10A PIV Silicon rectifiers IS425.	0-55
Q28	2 Silicon power rectifiers BYZ 13	0-55
Q29	4 Silicon transistors 2 x 2N696. 1 x 2N697. 1 x 2N698	0-55
Q30	7 Silicon switch transistors 2N706 NPN	0-55
Q31	6 Silicon switch transistors 2N708 NPN	0-55
Q32	3 PNP Silicon transistors 2 x 2N1131. 1 x 2N1132	0-55
Q33	3 Silicon NPN transistors 2N1711	0-55
Q34	7 Silicon NPN transistors 2N2369. 500MHz (code P397)	0-55
Q35	3 Silicon PNP TO-5. 2 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3845 TO-18 Plastic 300 MHz NPN	0-55
Q37	3 2N3839 NPN Silicon transistors	0-55
Q38	7 NPN transistors 4 x 2N3703. 3 x 2N3702	0-55

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and f of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and 'e' Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 22 cm x 4cm. Complete with case and instructions. Price each: 53-69

FULL RANGE OF ZENER DIODES

2-33V. 400mW (DO-7 Case) 15 ea. 11W (Top-Hat) 90p ea. 10W (SO-10 Stud) 35p ea.

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price 2p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	60 Mixed Germanium Transistors AF/RF	0-55
U 3	75 Germanium Gold Bounded Sub-Min. like OA6, OA47	0-55
U 4	40 Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil. Planar Trans. NPN like BSY96A, 2N706	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 0-55	
U 8	50 Sil. Planar Diodes DO-7 Glass 260mA like OA200/202	0-55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-55
U 10	20 BA V60 charge storage Diodes DO-7 Glass	0-55
U 11	25 PNP Sil. Planar Trans. TO-5 like AC127, 2N2904	0-55
U 12	12 Silicon Rectifiers Epoxy 600mA up to 800 PIV	0-55
U 13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0-55
U 14	150 Mixed Silicon and Germanium Diodes	0-55
U 15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-55
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-55
U 17	30 Germanium PNP AF Transistors TO-5 like AC17-22	0-55
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-55
U 19	25 Silicon NPN Transistors like BC108	0-55
U 20	12 5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-55
U 22	30 MATT's like MHz Series PNP Transistors	0-55
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-55
U 25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0-55
U 26	30 Fast Switching Silicon Diodes like IN194 Micro-Min.	0-55
U 27	12 NPN Germanium AF Transistors TO-1 like AC127	0-55
U 29	10 1 Amp SCR's TO-5 can. up to 600 PIV CRSI/25-600	1-10
U 30	15 Plastic Silicon Planar Trans. NPN 2N2926	0-55
U 31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-55
U 32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-55
U 33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY36 2S302/4	0-55
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-55
U 36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-55
U 37	30 Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0-55
U 38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-55
U 39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0-55
U 40	10 Dual Transistors 6 lead TO-5 2N2000	0-55
U 41	25 RF Germanium Transistors TO-1, OC45, NKT72	0-55
U 42	10 VHF Germanium PNP Transistors TO-1 NKT687, AF117	0-55
U 43	25 Sil. Trans. Plastic TO-18 AF. RC113/114	0-55
U 44	20 Sil. Trans. Plastic TO-5 RC115/116	0-55
U 45	7 3A SCR. TO66 up to 600PIV	1-10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally untested.

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0-55	UIC46	= 5 x 7446	0-55
UIC01	= 12 x 7401	0-55	UIC47	= 5 x 7447	0-55
UIC02	= 12 x 7402	0-55	UIC48	= 5 x 7448	0-55
UIC03	= 12 x 7403	0-55	UIC60	= 12 x 7450	0-55
UIC04	= 12 x 7404	0-55	UIC61	= 12 x 7451	0-55
UIC05	= 12 x 7405	0-55	UIC63	= 12 x 7453	0-55
UIC06	= 8 x 7406	0-55	UIC64	= 12 x 7454	0-55
UIC07	= 8 x 7407	0-55	UIC65	= 12 x 7455	0-55
UIC10	= 12 x 7410	0-55	UIC70	= 8 x 7470	0-55
UIC13	= 8 x 7413	0-55	UIC72	= 8 x 7472	0-55
UIC20	= 12 x 7420	0-55	UIC73	= 8 x 7473	0-55
UIC30	= 12 x 7430	0-55	UIC74	= 8 x 7474	0-55
UIC35	= 12 x 7435	0-55	UIC75	= 8 x 7475	0-55
UIC41	= 5 x 7441	0-55	UIC76	= 12 x 7476	0-55
UIC42	= 5 x 7442	0-55	UIC80	= 5 x 7480	0-55
UIC43	= 5 x 7443	0-55	UIC81	= 5 x 7481	0-55
UIC44	= 5 x 7444	0-55	UIC82	= 5 x 7482	0-55
UIC45	= 5 x 7445	0-55	UIC83	= 5 x 7483	0-55

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

NEW LOW PRICED TESTED S.C.R.'s

PIV 1A	3A	5A	6A	7A	10A	16A	30A
T05	T06	T06	T06	T04	T04	T04	T04
50	06	06	06	06	06	06	06
100	08	08	08	08	08	08	08
200	09	09	09	09	09	09	09
400	08	08	08	08	08	08	08
600	05	05	05	05	05	05	05
800	07	07	07	07	07	07	07

POST OFFICE TELEPHONE DIALS

2N3819 31p 2N5458 35p
2N3820 55p 2N5459 44p
2N3821 20p BZY10 66p
2N3823 31p MPP105 41p

CADMIUM CELLS

ORP12 48p
ORP60, ORP61 44p each

2N3055

115 WATT SIL POWER NPN 55p EACH

F.E.T.'S

2N3819 31p 2N5458 35p
2N3820 55p 2N5459 44p
2N3821 20p BZY10 66p
2N3823 31p MPP105 41p

DIACS

FOR USE WITH TRIACS.
BR100 (D32) 41p each

TRIACS

FOR USE WITH DIACS.
BVOM 2A 6A 10A TO-5 TO-6 TO-48

	3p	5p	8p
100	33	55	83
200	55	66	89
400	77	82	121

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 10p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

LISTENERS' CHOICE

THINGS are hotting up on the sound broadcasting front.

With a very large part of England now tuned up for local radio from the BBC, we look forward with fascinating interest to see how the Independents, supported nobly by the IBA, will fare this autumn, when they start transmitting official commercially sponsored programmes. Already the test transmissions on the medium wave have acted as a preliminary publicity exercise. Their intentions are to go straight into v.h.f. as well and incorporate pilot-tone stereo facilities. Circular polarisation of transmitting aerials will be used so that car radios and portables stand a very good chance of receiving these broadcasts.

At the same time, the BBC is pressing ahead with expansion of stereo broadcasting using pulse-code modulation systems for better quality reception. It has taken too many years for them to improve stereo capability and (we suspect) it is due largely to pressure from commercial competition that such a hive of buzzing activity has now resulted in the extended service.

One other point not to be forgotten is the influence of television on radio audiences; with colour now commonplace, sound radio (or "steam" as you prefer) must have threatened to fall on hard times.

The much welcome uplift of interest in sound radio provides the manufacturing industry with impetus for meeting the demand for new receivers. In what proportions (a.m. or f.m. or both) these will need to be is anyone's guess. With the improved service of f.m. broadcasting techniques, allowing for the added interest in stereo, as well as the "booming" in-car entertainment business, we have a hunch that there will be a fairly even distribution.

In the following issues of *Practical Wireless*, you will find many articles devoted to sound broadcasting. We kick off this month with an article to help you understand how and why you should pay special attention to your f.m. aerial installation, particularly if you want to get the best from stereo. We also offer the constructor with little experience a simple a.m. radio, using two integrated circuits.

M. A. COLWELL—Editor

PRACTICAL WIRELESS

The October issue (No 800), on sale 7th September, will start you on the road to making your own quadraphonic sound system, will include the first pair of PW Datacards on resistors and capacitors, will commence a tutorial series for learning how circuits work by practical experiments, and will give first details on our audio supplement for the November issue.

Further details on page 431

TELEVISION

The October issue of *Television*, on sale 17th September, will have for the first time an additional Colour TV Fault Finding Chart. Full colour photographs of fault conditions will be provided on a special quality paper in the magazine. With the additional fault-finding chart you can not only find where the trouble lies, but also learn a bit about how colour television works.

Further details on page 417

NEWS...

Britain/Canada telephone cable


Practical Wireless was recently invited to watch the loading of the Cable & Wireless Ltd. cables ship "Mercury" with the first 200 miles of a £30m telephone cable linking Britain and Canada.

CANTAT-2 as it is called, will handle more than 1,800 phone conversations at the same time. It will have 473 repeaters at 6-mile intervals and 31 equalisers at 90 mile intervals.

The 2,800 nautical mile cable is financed by the Post Office and the Canadian Overseas Telecommunications Corp. S.T.C. Limited have supplied the system and the transistors used in the repeater are being supplied to them by the Post Office Research Dept. Dollis Hill. These transistors (2,800 in all) each have a design life of at least 25 years.

The 1,840 circuits in CANTAT-2 are arranged as 23 supergroups transmitting between 312-6,012kHz. in the UK-Canada direction and 8,000-13,700kHz the other way.

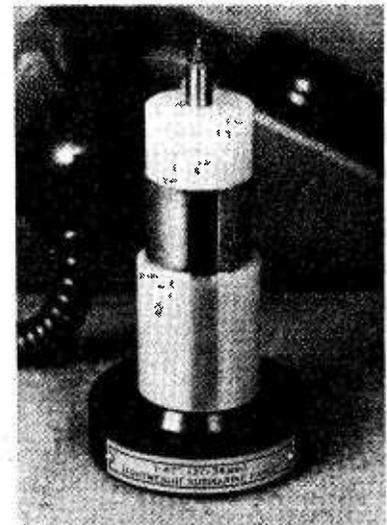The cable (see picture) weighs under 5 tons a mile, it has an outer conductor of aluminium and is strengthened by a core of steel rope inside an inner conductor of copper.



A piece of the cable showing how it is formed

Practical Wireless in Italy

PRACTICAL WIRELESS will be taking part in the Italian International Music and High Fidelity Exhibition at the Milan Fair from September 6th to 10th 1973. This is the seventh time that the exhibition is being held and will cover hi-fi equipment, components and accessories. Also of related interest is the section devoted to musical instruments and amplifier equipment for them. Concerts, audio shows and lecture meetings will be held at the same time.

This exhibition will occupy about 20,000 sq metres and around 35,000 visitors are expected. There will be about 800 foreign buyers expected from 45 countries including African and Middle East countries.

Practical Wireless will take part in the Technical Journals section of the exhibition where visitors from all over the world will see some of the recent work that we have published and be given detailed information of our Project Q4 (see page 431) which will commence publication in next month's issue.

It is worth remembering that, if you are near Milan during that long weekend and hold a non-Italian passport you will be admitted free of charge.

'English as she is spoke'

IMMIGRANT children who speak little or no English are now learning the language with the aid of the "Language Master System", marketed by Bell and Howell A-V Ltd.

This is a new card programme specifically designed for teaching English to foreign children. Entitled "Let's Speak English", the programme teaches the essential elements of everyday speech using the established Language Master technique of sentence repetition and Q&A.

The pupil learns from audio-visual cards bearing words, pictures and a magnetic tape recording of the same words in the teacher's voice. When the pupil places a card in the machine, the teacher's recording is automatically reproduced.

As the phrases and sentences on the cards are seen and heard at the same time, and are backed up by illustrations of the objects and actions described, new language forms and vocabulary can be grasped more easily and retained better. The system also makes provision for the pupil to record his own voice for practise of pronunciation. He can then listen to the teacher's voice and compare it with his own.

London Independent Radio

THE IBA have announced officially the following allocations of broadcasting frequencies for the London area:


London Broadcasting Company (News Service) 719kHz (417 metres) medium wave and 97.3 MHz v.h.f.

Capital Radio (entertainment) 557kHz (539 metres) medium wave and 95.8MHz v.h.f.

At the time of going to press no definite date had been announced for commencement but it is expected to be in October or November.

Berlin F.M. Tx

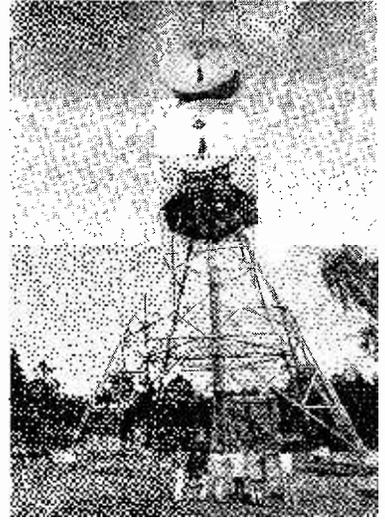NEW f.m. transmitter for broadcasts and mobile radio at Frohnau, West Berlin. See article "Broadcasting in Berlin" on page 411.




Diary Date

September 23—Harlow and District Mobile Rally will be held at Netteswell Comprehensive School, Harlow, Essex. All the information can be obtained by writing to V. Neard, 106 Vicarage Road, Harlow, Essex.





shortwave converter

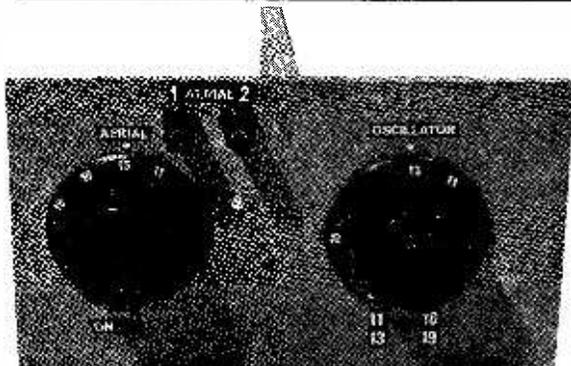

THE shortwave converter is a unit that is connected between the aerial and the receiver and serves to convert radio signals in the shortwave bands into one fixed frequency. In our design, this frequency is 1600kHz (1.6MHz) or 190 metres, medium wave. This choice enables us to use the converter, in conjunction with a normal broadcast receiver tuned to 1.6 MHz, for the reception of the shortwave signals for which the converter was designed.

The connection between the converter and the receiver is effected by a few feet of coaxial cable, which is connected to the aerial and earth inputs of the receiver. So no changes in the circuitry of the receiver are needed, which is available for the reception of other radio signals as soon as the converter is disconnected and the aerial connection restored. The unit described here was designed to be acceptable for the listener with little experience in electronics.

The shortwave range of the unit runs from about 15 to 26.5 MHz, incorporating the 11, 13, 16 and 19 metres broadcasting bands. This range has been selected because it is not available on many radio receivers and yet comprises three of the best shortwave-bands for long-distance communication. For those listeners who prefer the range from 5.5-12 MHz (49-25 metres), we have listed additional data.

THE CIRCUIT

The circuit diagram of the converter is given in Fig. 1 which shows the tunable bandpass filter consisting of L1, L2 and the associated fixed and variable capacitors; the oscillator circuit, of which transistor Tr2 is the heart; and the frequency changer (mixer), comprising, among other things, the transistor Tr1 and

output coil L4. The converter can be powered by a dry battery of between 6 and 12 volts since the current consumption is very small, about 3mA. The connection of the unit to the receiver is effected via the terminals A and E of the secondary winding of coil L4. They are connected respectively to the aerial and earth terminals of the receiver. At the converter, a long wire aerial is connected to Input 1 and Input 2 is connected to the chassis. If, however, a dipole is used this can be connected to both of the inputs. The chassis connection of number 2 is now omitted.

The bandpass filter comprises two circuits, which are mutually coupled. It serves to obtain a preselection for a limited frequency range, in which the desired stations can be found. A dual tuning capacitor of 2 x 470pF or 2 x 365pF is used for this purpose. If we use the 470pF variable capacitors, 330pF fixed (ceramic) series capacitors are necessary to arrive at the right 10-200pF capacity range. If the 365pF variable capacitors are used instead, series capacitors of 470pF must be applied.

The oscillator circuit frequency is determined by the properties of the tuned circuit comprising L3 and the capacities connected in parallel. The 92pF capacity (10pF and 82pF connected in parallel) can be inserted by a switch. This determines the range of the converter: the 15 and 17, or the 21 and 25MHz bands. For the 25 and 17MHz frequency ranges, the oscillator frequency is selected so as to be 1.6 MHz below the frequency to which the bandpass-filter is tuned. For the 21 and 15MHz, respectively, the oscillator frequency is chosen 1.6 MHz above the resonant frequency of the aerial circuit. This makes it possible to use a small tuning capacitor for the oscillator stage of the converter. A 30pF variable is used here, VC3.

The oscillator signal is coupled to the frequency changer stage via capacitor Ck. This consists of two

'Radio Nederland', the Dutch World Broadcasting System, is well-known to short wave listeners throughout the world. It was one of the early pioneers of broadcasting on the high frequencies and today it still keeps in close touch with its listeners through the DX Information Service.

Detailed technical data sheets are issued free of charge under such headings as crystal calibrators, aerial systems, radio interference suppression and many more.

We are pleased to publish here a suitably edited version of the data sheet on the Radio Netherland Short Wave Converter together with our photographs of the prototype so kindly provided by the Engineering Section of Radio Nederland.


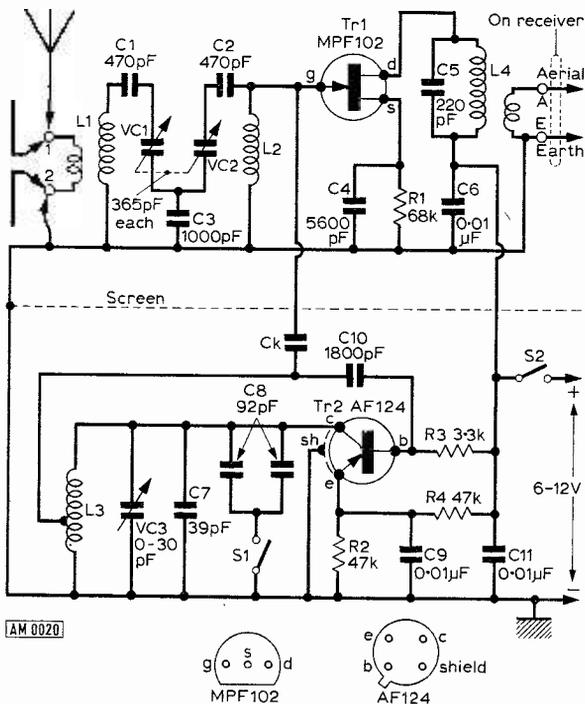


Fig. 1, above, is the complete circuit diagram of the RN converter.

Fig. 2, below, gives winding information for all the coils and illustrates coupling capacitor Ck

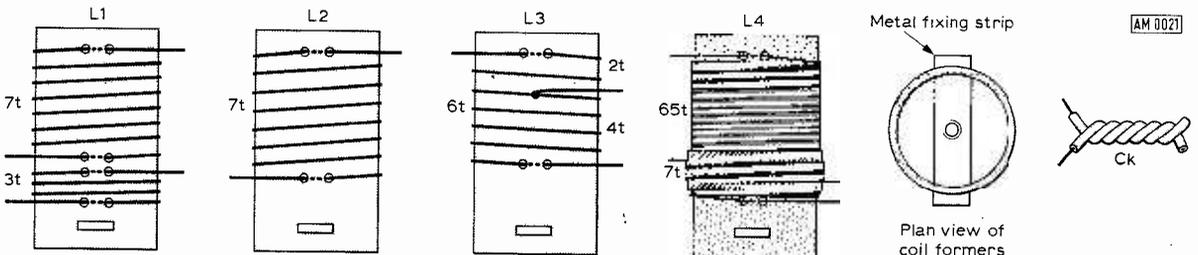

insulated wires, twisted over a length of 1 inch as illustrated in Fig. 2.

The mixer uses a field-effect transistor (FET), Tr1, for best results. In its drain circuit, coil L4 and its 220pF parallel capacitor form a resonant circuit that is tuned to 1.6 MHz. The correct frequency of this circuit can be determined more exactly when the unit is operating when variation of the receiver tuning shows the spot where the combination of converter and receiver works most satisfactorily. If necessary, change the resonant frequency of this circuit by inserting a slightly different capacitor.

CONSTRUCTION

The front panel measures 8" x 4½" and consists of hardboard or plywood, the inside covered with a piece of copper, brass, zinc or tin of the same size. In the middle, and at right angles to it, a piece of plywood measuring 4" x 4½" is fixed. This is also covered with sheet metal of the same dimensions, stuck to it on the left side where the oscillator is located. The two metal sheets are interconnected by soldering while a wooden block of about 3" x ¾" x ¾" serves to reinforce the joint. It is glued in its proper place and also carries the dual tuning capacitor and coil L2.

To further support the dual tuning capacitor, another small wooden block of about 1" x ¾" x ¾" is glued in the appropriate place. It carries coil L4 and a small terminal strip to support the smaller components like the transistor and some capacitors. The woodscrews with which the tuning capacitor is fixed, must not touch the metal sheet on the back of the mounting plate, as they would then short-circuit the 1000pF series capacitor. After the chassis has been made the components can be put in their right positions. Care should be taken to insulate the aerial input terminals from the front panel, and to make the holes for the shafts of the tuning capacitor big enough to prevent metallic contact.

Preferably, the wiring should be made with a small 25 watt soldering iron. Keep the connections short and use the sheet metal for the chassis connections. Go carefully when connecting the transistors. If using the alternative types, make sure the connections are right. To prevent damage to the transistor by heat conduction hold the transistor wire near the semiconductor with a pair of pliers, which will act as a heat sink.

The coils of the converter can be easily home-made. For this, obtain a few short pieces of ⅝" outer diameter pvc (plastic) conduit. Use SWG 22 or 21 enamelled copper wire to wind the coils, each over a length of about ⅝", as illustrated in Fig. 2. Before putting them in their proper place, carefully clean the ends of the wires to remove the enamel insulation, and apply some solder. Proceed in the same manner for making the tap on coil L3. Slots are made in the

★ components list

Resistors

R1 68kΩ ¼W 10% R3 3.3kΩ ¼W 10%
R2 47kΩ ¼W 10% R4 47kΩ ¼W 10%

Capacitors

C1 470pF SM or Ceramic C6 0.01μF tubular
C2 470pF SM or Ceramic C7 39pF SM or tubular
C3 1000pF SM or Ceramic C8 92pF SM or tubular*
C4 5600pF tubular C9 0.01μF tubular
C5 220pF SM or ceramic C10 0.01μF tubular
* see text.

VC1/2 2 x 365pF (Jackson O2)

VC3 30pF variable air spaced (Jackson C804)


Semiconductors

Tr1 MPF102 Tr2 AF124

Note: In the prototype the BF245 and AF106 were used but since difficulty will be experienced in obtaining these types they have been substituted by the MPF102 and AF124.




Miscellaneous

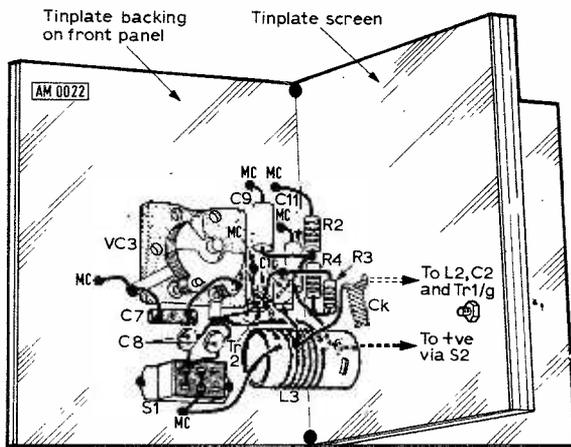Material for chassis, see text. S1, S2, miniature on/off slide switches. Coil formers, see text. Tag strips 2 way (2). Aerial sockets (2). Insulated coupling or rod for VC1/2.



Points marked MC denote earthing connections to chassis (-ve line)

Fig. 3, above, and photograph below show the oscillator section of the converter while to the right are the circuit and photograph of the input and mixer stage.

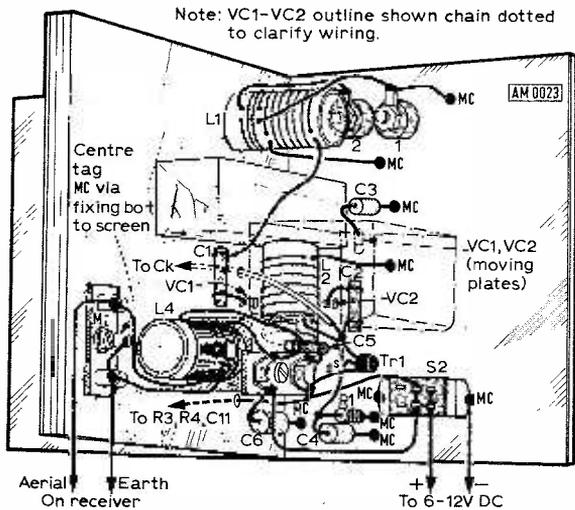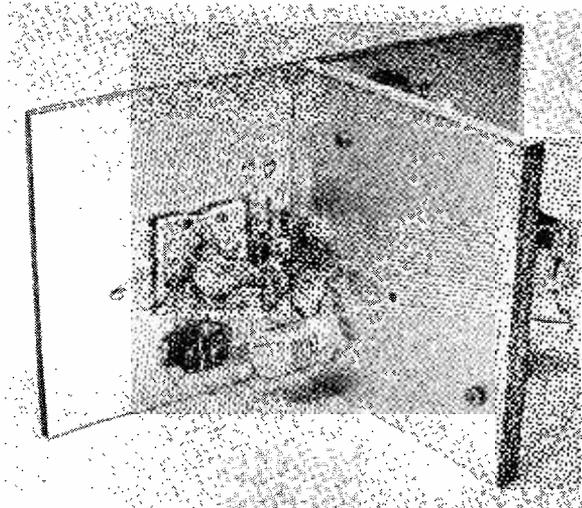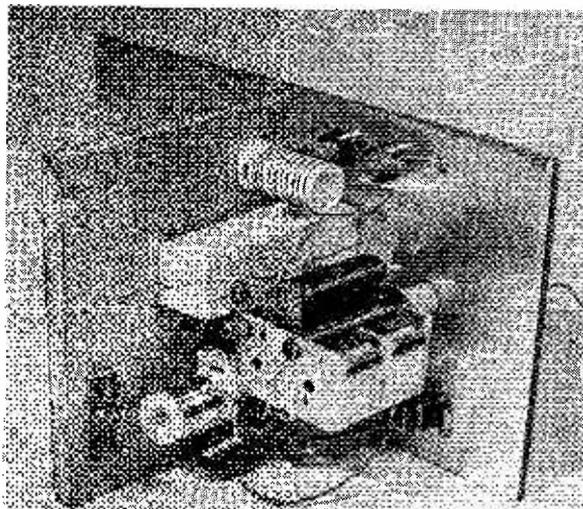

plastic form, through which a small strip of metal is run with a hole in the middle. This is a commonly applied method for mounting the coils. Instead, however, you can use a proper cement, like Araldite, to fix the coils in place.

The wire used for L4 is SWG 30. The primary winding has 65 turns, the secondary is wound around the first one, after a thin strip of plastic is applied, to separate the windings. The secondary winding consists of 7 turns.

The layout of the components is illustrated in Figs. 3 and 4. It is possible to deviate from this design without trouble, but if you have little experience in electronics, we advise that you stick to it.

OPERATION ON 5.5 TO 12.5 MHz

This range covers the 25, 31, 41 and 49 metre bands. L1 should be wound with 15 turns over a length of $5\frac{1}{8}$ " , the coupling winding consisting of 5 turns. L2 is the same as L1. Oscillator coil L3 also is the same as L1 but a tap is taken at 5 turns from the bottom end. L4 remains unchanged. The oscillator tuning capacitor should be increased to 120pF (VC3).

ADJUSTMENT


After all the connections have been made check the wiring thoroughly before the unit is connected. Join the converter output terminals to the aerial and earth terminals on the receiver, preferably with coaxial cable to prevent the direct pick up of signals by the receiver on 1.6MHz to which frequency the receiver should be tuned.

It is advisable to first tune the oscillator to the required signal and then to peak the signal with the aerial tuning which will be found to be comparatively flat. After the proper positions of the knobs have been found for all the bands mark them for easy tuning in the future with the help of some dabs of coloured paint or very small labels typed with the frequency bands.

When the whole unit works satisfactorily it can be put in a small wooden cabinet or preferably an aluminium case, again to protect the receiver from direct pick up.

Information on the DX Information Service can be obtained from Radio Nederland, English Section, POB 222, Hilversum, Holland.

BROADCASTING IN BERLIN

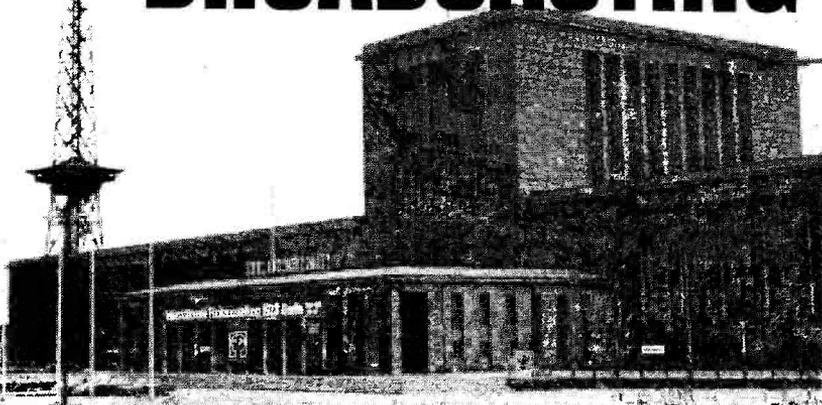

Exhibition halls of the Palace at the Funkturm where the Internationale Funkausstellung is to be held.

SINCE 1920, when the German Post Office broadcast its first test programme from the long wave radio station Königswasterhausen, German broadcasting services and associated equipment manufacturers have earned the respect and admiration of many people all over the world. This year they are celebrating fifty years of broadcasting with special events.

The International Radio and TV Exhibition (Internationale

Funkausstellung 1973) brings together the combined resources of broadcasting organisations of West Germany and twenty other countries in the Palace at the Funkturm, Berlin, from August 31st to September 9th. *Practical Wireless* was privileged to be given a preview of some of the current activities in the industry in West Berlin recently.

The exhibition will cover all aspects of entertainment electronics and will show modern forms of transmission techniques using satellites and pulse code modulation, private radiophones, projection colour television, traffic guidance systems and s.s.b./a.m. radio.

Television Studios

The two television transmitting organisations in West Germany are the Arbeitsgemeinschaft der Rundfunkanstalten (ARD) and the Zweite Deutsche Fernsehen (ZDF) which will broadcast the opening ceremony of the exhibition over the Eurovision network on August 31st. As well as the customary display of domestic equipment from industry there will be additional attractions including a fully operational television studio, transmitting equipment, a radio and television servicing

◀ The new SFB television studios with the parabolic reflectors in the recess near the top.



Some of the remote control equipment in the SFB building used to provide automatic operation of studio cameras and lighting. ▶




workshop, demonstration of historic equipment by the Deutsches Rundfunk Museum, special transmissions by the Deutschen Amateur Radio club and numerous cultural and sporting events for visitors' relaxation.

The Television Centre in West Berlin is run by the SFB which now broadcasts from the new buildings completed in 1971. The photograph shows the tower block on which are mounted the directional parabolic reflectors linking the centre with the transmitting stations and mobile units. Of particular interest in the Centre is the use of unmanned television studios. Computer equipment installed can operate television cameras and lighting from a remote console, so that the control room has direct control of floor equipment.

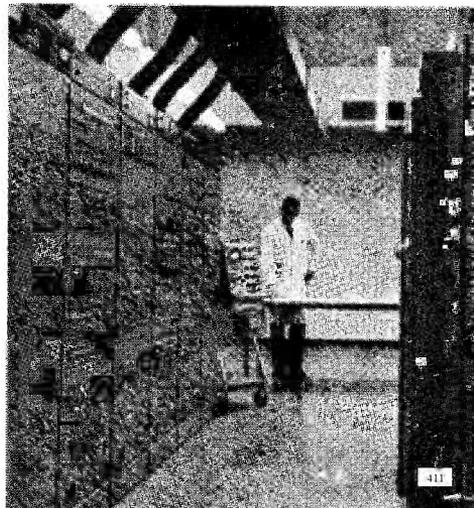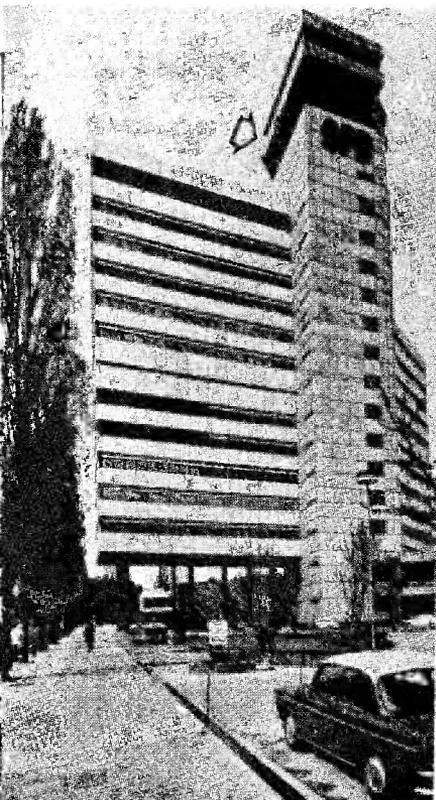SFB (Sender Freies Berlin) has only an 8% share in ARD and



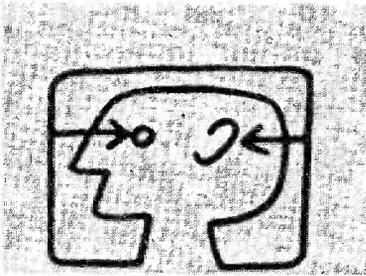

The film scanning room in the technical centre of the SFB.



broadcasts television programmes on Channel 7 (v.h.f.) and Channel 39 (u.h.f.). Sound radio on v.h.f. is on 88.75, 92.4 and 96.3MHz, and on 202m and 530m medium wave, the third programme being distributed through Norddeutscher Rundfunk (NDR). SFB will broadcast during the exhibition using a specially converted hall in the exhibition centre.

New Video Disc

A special feature will be the demonstration of video recording techniques for the home and in particular a new video disc player shown by Telefunken. This system is the production model version of TELDEC (first demonstrated three years ago) and has been developed to provide up to 10 minutes on one side of a 21cm flexible plastic disc. The first demonstration was designed

for monochrome pictures but now the new version, affectionately renamed TED, can provide colour pictures of excellent quality in various simultaneous multiple geometric arrangements, including superimposition. Of significant interest is its ability to be "stopped" to provide still pictures and short excerpt repeats.

The video disc works on the principle of "out-of-contact" pressure scanning, using a small pick-up cartridge about the size of that used for sound record players. The first version introduced in 1970 contained monochrome programme material and a year later the TriPAL-D System was successfully recorded using this medium. Production of disc players is now at an advanced stage and will undoubtedly attract a large market at the exhibition.

The TED System is claimed to be the cheapest of all known

video recording systems but, of course, the domestic unit will not have "record" facilities, only playback.

Other Recording Techniques


Of the five video recording techniques previously known, the only three to become the subject of further development in West Germany are magnetic tape cassettes, which are now enjoying a boom in demand, disc, and the "Super-8" film scanner, although the latter is only being developed by one company for production early next year.

The connection of a video recorder to the television receiver presents two main problems: mains isolation and time base stability. By connecting through the aerial socket the mains isolation problem is solved but this is only suitable for playback


The automatic studio equipment control console in the SFB. Instruction data is displayed on the screen in the background from the computer operated by the central push button panel.



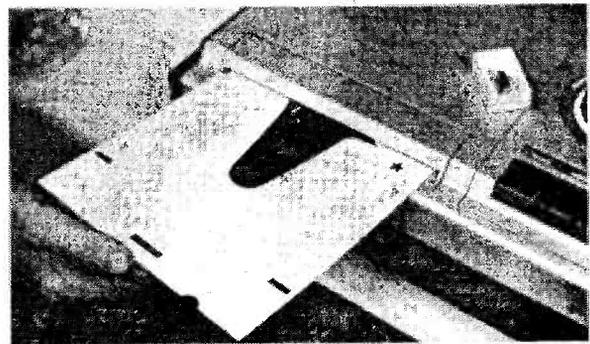Exclusive P.W. picture of the production version of TED, the Telefunken video disc player. The pickup head is seen in its box on the top. The disc is inserted, complete with sleeve into the slot in the front, the function controls being simple push buttons.



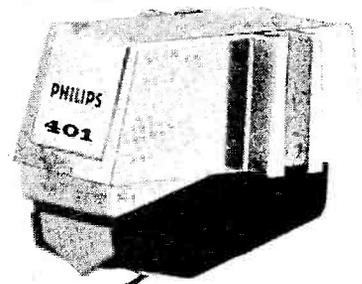The Philips 401 dynamic stereo pickup head manufactured in West Berlin.





A P.W. photograph of the East Berlin television transmitting tower near Checkpoint Charlie.

machines. Video signal recording machines need an adaptor for use with a.c./d.c. sets but these are expensive and a cheaper solution is still being sought.

Timebase stability can be a problem with flywheel sync circuits and result in severe non-linearity in the horizontal deflection. This problem can be overcome to a large extent by reducing the time constant in the phase comparator circuit. This facility will be incorporated in some sets by adding an "AV" switch, the "AV" designating

Audio-Visual. Some sets have already reduced the time constant without the need for a switch. Permissible maximum time deviations that a receiver should accept or a video recorder should produce is the subject of a German Standards Committee dealing with this aspect.

Seven German companies have now adopted the video cassette system and they are manufacturing cassette recorders on a large scale. All have built-in television tuners and timers, and stereo can be provided although up to now is not built-in. Over 40,000 VCR sets have been built and sold in Europe and manufacturers are having to work hard to satisfy a growing demand. The trend is to omit the u.h.f. tuner and connect to the video signal direct. Some domestic receivers are already being fitted with a video socket for this purpose specially for cassette recorders.

The German Post Office will be showing likely future developments in communications and to emphasise the theme they will give light and sound displays for visitors. Their exhibits include work in laser communications via glass fibres using pulse code modulation, which is particularly suitable for stereo broadcasting for sound only and television channels. Part of the work of the German Post Office is in monitoring the "air waves", particularly




as stringent control must be exercised in Berlin because of its geographical position.


The Post Office is extending its transmission service capability by bringing into service its new "twin-dish" f.m. transmitter at Frohnau, Berlin. This station will handle telephone, telegraph, telex, genex, and data traffic in two directions with a similar station in Lower Saxony, so extending communications from West Berlin without interference to East German transmissions. A fully automatic public land mobile service will also transmit via Frohnau.


The exhibition organisers, AMK Berlin, are to be congratulated on the magnificent organisation behind the exhibition programme. In turn they have received full co-operation from several Berlin organisations in promoting the 50 years anniversary celebrations including Philips, Telefunken, German Post Office, and broadcasting companies. We would hope that British exhibition organisers will visit Berlin to take notes. ■

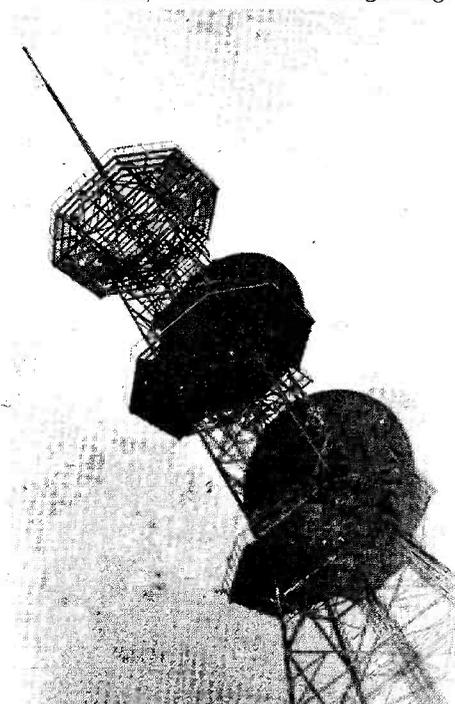F.M. modulator/demodulator equipment in the new transmitting station at Frohnau.



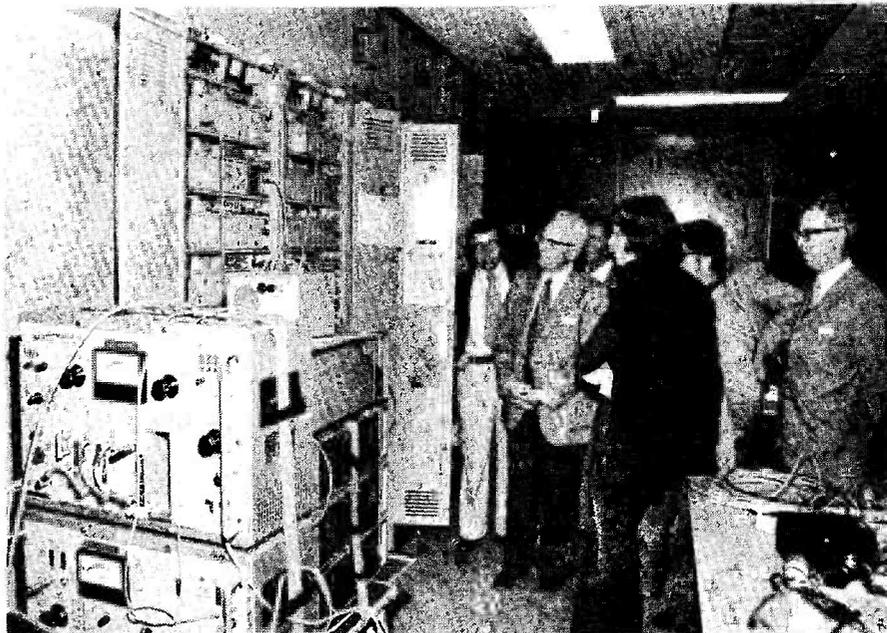The new Post Office scatter systems aerials at Frohnau. The highest section is used for mobile radio transmissions.



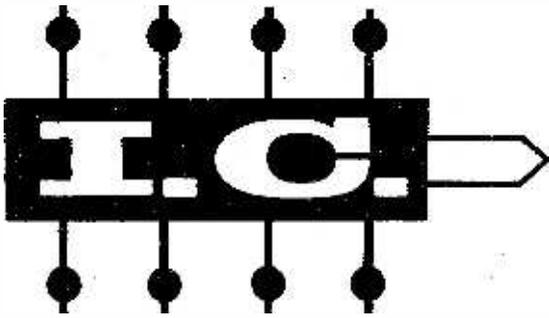

OF THE MONTH

L.A.J. IRELAND

Number 41

LP2000 MICROTRANSMITTER

A few years ago the letters column of Practical Wireless bristled with a controversy regarding the pros and cons as to whether the authorities should allow low level radio communication on a specified band analagous to the citizens band in America, without the requirements of having to pass the morse code test and radio theory examination. Allied to this was the profusion of American and Japanese equipment particularly walkie-talkies, available over the counter from many radio and electrical shops giving rise to the rather curious anomaly whereby a person could legally purchase such equipment and yet find himself in the position of using it illegally.

The sale of such equipment even here is quite high and as each specific market for a particular transistorised unit is identified, it is inevitable that the IC manufacturers should turn their attention to fulfilling this need, in integrated form, if at all possible.

Lithic Systems Inc. have now produced the first monolithic microtransmitter, designated the LP2000, the operating frequency being set by external tuning elements so that the device can operate at any frequency up to 150MHz with a power output in the region of 100mW.

Circuit

The complete circuit diagram of the LP2000 together with a functional block diagram is illustrated in Fig. 1. All the active components of the transmitter are incorporated in the IC with the operating frequency set by an external overtone type crystal and a tuned LC tank circuit picking out the required overtone frequency. Tr8 acts as the transistor oscillator operating with AC grounded base and having its DC bias controlled by the internal regulator. Further stability is ensured by having its emitter current controlled by the constant current source Tr7.

Two emitter follower buffer stages Tr12 and Tr13 directly couple the oscillator to the power output stage Tr15 and this rather unique design does away with the more conventional LC or RC interstage coupling networks. The modulator and output regulator form an integral part of the output stage and this is achieved by inserting Tr14 and Tr16 as the emitter loads with their currents controlled by the modulating preamplifier Tr9 and Tr10. In conjunction

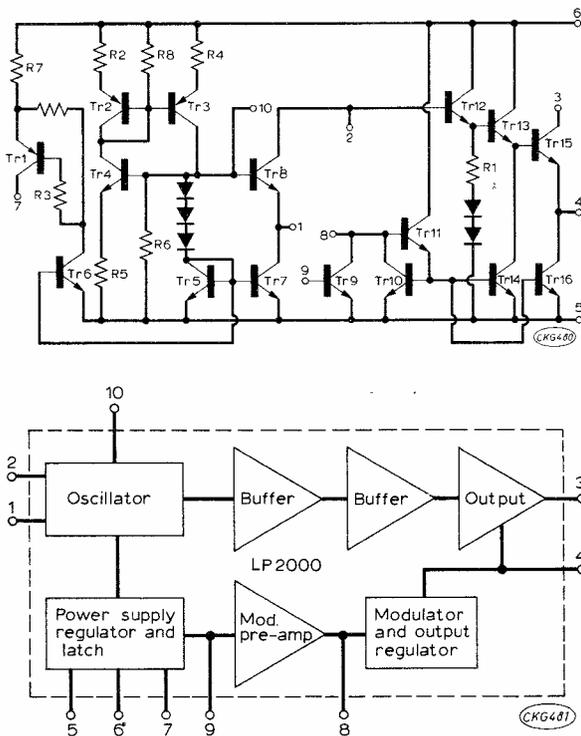


Fig. 1a, top, is the complete circuit of the LP2000.
Fig. 1b, below, shows the circuit by functions.

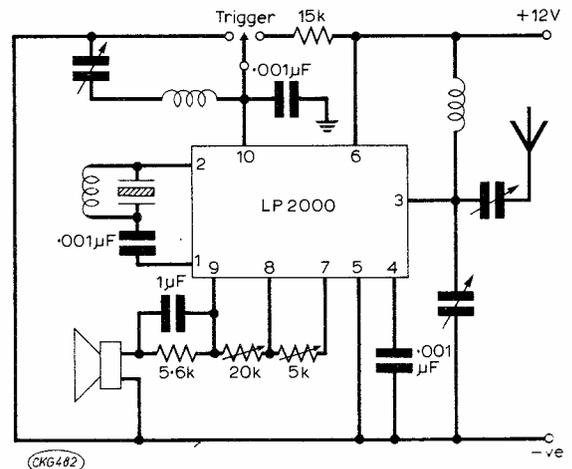


Fig. 2. Circuit for a complete transmitter, based on the LP2000.

The Catalogue you MUST have!

HOME RADIO COMPONENTS

250 pages 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ "

6,785 electronic
components clearly
listed and indexed

1,750 pictures

10 free Vouchers
each worth 5p.

Price list
regularly
updated

Bookmark
with useful
list of
technical
abbreviations

*Details of our popular
Credit Account Service
and our Easy Ordering
System are included
in the catalogue.*

Only 55p. plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

Name _____

Address _____

HOME RADIO (Components) LTD. Regd. No. 912966, London
Dept. PW, 234-240 London Road, Mitcham CR4 3HD

*The price of 77p applies only to customers in the U.K.
and to B.F.P.O. addresses*



parts for PRACTICAL WIRELESS projects


After many requests, Electro Spares are now supplying lists of components for ALL the projects featured in "Practical Wireless" commencing July 1973 issue. Just forward an S.A.E. (preferably 9" x 4" minimum) stating which project is of interest to you—we will forward an individually priced list of components required. No need to buy a full kit—you need only purchase the parts you require at any one time.

All Electro Spares supplied components are new, branded products of reputable manufacturers and carry full makers guarantee.

We regret we cannot supply lists for projects published before July 1973 issue.

"ONE SOURCE" BUYING MAKES SENSE—IT CAN SAVE YOU TIME, MONEY AND POSTAGE.

"p.e." f.m. varicap stereo tuner

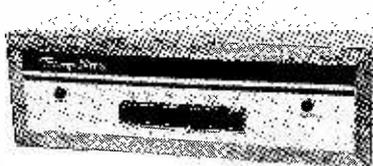

Approx. Size :- 8½" x 2½" x 6½"

Features include push button "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses NEW pre-set modules for R.F. and I.F. Circuits—no circuit alignment. High efficiency Integrated Circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator.

Total Kit price only £28.50 including VAT and postage

With Fibre Glass P.C. Board, neat slimline teak veneered cabinet with brushed aluminium front panel, push buttons, etc.

IDEAL FOR USE WITH THE "TEXAN", "GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER

Please send large S.A.E. for full details.

"p.e. gemini" stereo amplifier

QUALITY HI-FI FOR THE HOME CONSTRUCTOR

30 Watts per channel into 8 ohms Total Harmonic Distortion 0.02% Frequency Response (-3 dB) 20Hz-100kHz

We are still continuing to supply components for this fabulous Amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the Home Constructor—hundreds supplied throughout the world. Booklet available, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc. Price 55p, plus 4p postage.

Our New Low Price List is supplied with each booklet, or supplied separately on receipt of a large S.A.E.

FOR PEOPLE WHO REQUIRE THE BEST, IT HAS TO BE THE "p.e. gemini".

Note Our New Address—With New Mail Order Department For Quick, Efficient Service.

**PLEASE PAY US A CALL—VISITORS WELCOME.
NO PARKING PROBLEMS**



Electro-Spares

288, ECCLESALL ROAD,
SHEFFIELD, S11 8PE

"THE COMPONENT CENTRE OF THE NORTH"

Of course it's not live.



Sorry about that, Roger.

BAND-AID* Washproof Plasters.

© Johnson & Johnson
LTD

* TRADE MARK

BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON S.W.17 01-672 3984

CARTRIDGES—Stereo Sonotone 9TA H/C Diamond £2.47, Ronette S105 Medium Output £1.40, S106 High Output £1.40, Acos GP93/I Sapphire £1.95, GP94/I Sapphire £1.95, Japanese equivalent to B.S.R. TC8: £1.80.

CARTRIDGES—Mono GP91 Stereo Compatible £1.29, B.S.R. TCBH Jap. equivalent £1.29.

HI-FI STEREO HEADPHONES Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms, frequency range 20-20,000 Hz 6ft. cord and standard stereo plug. Only £3.57.



STEREO HEADPHONE JUNCTION BOX Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only £1.74.

YVNAIR Widths from 50 to 54in., 95p yd. off roll. ¼ yard 57p. Send 5p stamps for samples. All prices inclusive of post and packing.

poly-planar

20-Watt Full Range Speaker

Completely replaces the
conventional cone speaker
Super-thin construction
permits new installation ideas.



Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance:
8 ohms. Operating temperature range: -20°F to +175°F. Size
(WxDxL): 1.7/16" x 1.3/4" x 14.1/16". Weight: 19 ounces.

£7.50 each Stereo pair £14.50
post free

web europa

P.O. Box 162, Watford WD1 1AA

with an ordinary dynamic loudspeaker used as a microphone sufficient drive is obtained to allow up to 100% modulation of the output stage.

When the transmitter is used as a portable, a latching mechanism allows the IC to be permanently connected across the power supply drawing little or no current until actuated. A positive going trigger pulse applied to pin 10 causes Tr4 to conduct and the resulting voltage drop across R8 causes Tr2 and Tr3 to conduct thereby providing regulated bias voltages for the oscillator and output stages. This quasi-stable state remains as long as the base of Tr4 is not grounded. Application of a negative going pulse or momentarily earthing pin 10 causes a reversal of the latch to the 'off' state.

A Practical Transmitter

A complete radio transmitter circuit, incorporating the LP2000, is shown in Fig. 2. The two pre-set resistors control the idling current and output modulation. One rather curious feature of the design is the DC short through the tank circuit between the base and collector of Tr8 but monolithic transistors still show a current gain even when operated in this mode. The tank coils and variable capacitors will have to be chosen to suit the operating frequency set by the particular crystal used, and while this IC can operate as a complete transmitter in its own right, it can also provide sufficient drive to operate a more powerful PA stage for amateur transmissions.

Also available is the LP2001, electrically interchangeable with the LP2000 but producing a minimum continuous output power of 250mW.

The suppliers, in this country, are Europartners Ltd., Shirley Lodge, 470 London Road, Slough, Bucks. The LP2000 costs £8.80 and the LP2001 £13.20 to which should be added VAT and postal and packing charges.

PRACTICAL WIRELESS MULTIMETER COMPETITION

THE WINNERS OF
THE FOUR DIGITAL
MULTIMETERS WILL
BE ANNOUNCED
NEXT MONTH



August 1973

Light Operated Switches

The diode D1 in Figs. 1-4 is shown reversed. Positive side of diode should go to positive supply line.

TELEVISION

SEPTEMBER ISSUE

COPING WITH ICs

The i.c. is the thing you suspect but don't know how to test, have no spare for and find it difficult to solder. Their increasing use in TV sets means however that it is essential for anyone concerned with TV servicing to come to terms with them. With this in mind "TELEVISION" is starting a new series intended to make this as easy as possible.

TRANSISTOR FLYWHEEL SYNC CIRCUIT

In modifying a non flywheel sync BRC/900 chassis for CCTV use Keith Cummins found that the set had inadequate line sync performance and couldn't cope with the CCTV signals. As the original optional flywheel sync unit for use with this chassis is no longer available a small transistor version was devised and successfully incorporated.

DEALING WITH DROPPERS

The most common cause of TV set failure is a fault in the mains dropper. In dealing with droppers Peter Graves explains the function of this part of the set, the reasons why failures occur and the recommended ways of putting things right.

RECEIVER DEBUGGING—2

In the second part of this series E. J. Hoare tackles one of the most troublesome areas in home-constructed sets—ensuring good line and field synchronisation under various signal conditions.

PLUS ALL THE REGULAR FEATURES

COMING IN THE OCTOBER ISSUE OF "TELEVISION"

An illustrated guide to basic colour faults, in full colour.

TO
(Name of Newsagent)

Please reserve / deliver the SEPTEMBER issue of
TELEVISION (20p), on sale AUGUST 20 and
continue every month until further notice

NAME.....

ADDRESS

PRODUCTION LINES


colin riches

STORAGE BOXES


Kabi (Electrical & Plastics) Limited of Potters Bar, Herts. have introduced an entirely new series of compartment trays. The range comprises four sizes from 5¼ in x 7 in x 1½ in to 6¼ in x 12 in x 2 in.

The largest model has moveable compartment modules, each module being capable of sub-division, so that compartments of virtually any size up to the total dimensions of the tray can be formed.

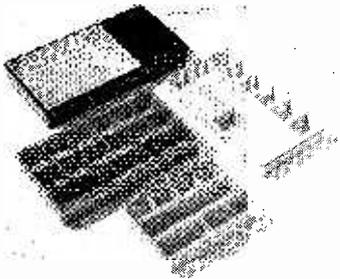Most are available in a range of colours at prices ranging from 45p to £1.50 each according to size. *Kabi Ltd., Cranborne Road, Potters Bar, Herts., EN6 3JP.*



METRIC CUTTERS

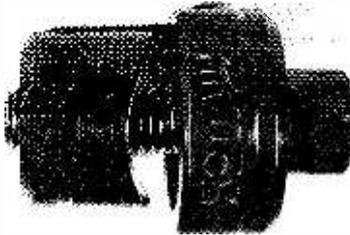

Q-Max (Electronics) Ltd., now supply their chassis cutters in metric sizes and linear sizes.

We have illustrated the 25mm size which is priced at £1.05. An Allen key to fit costs 9p.

To use these punches, a hole must be drilled ensuring that the Allen screw will fit through easily. The screw is then passed through the die (see picture) then passed through the ready-drilled hole. The punch is then screwed onto the projecting Allen screw until it makes contact with the metal to be punched. The screw is then turned by means of an Allen key and the punch cuts cleanly through the metal.

Q-Max (Electronics) Ltd., 44 Penton Street, London, N1 9QA.

SOLDERING ALUMINIUM

In recent months Multicore Solders Limited have introduced to industry their new flux cored solder for soldering aluminium.

Multicore now believe that they have made a significant breakthrough and are announcing the release of ALU-SOL Multicore Solder which readily solders aluminium and many aluminium alloys, does not require any extra flux, and seems to provide joints having significantly better resistance to subsequent electrolytic corrosion than any other soft solder/flux combination considered previously for aluminium soldering.

Now a new pack (ref: Size 4) for Servicemen and Handymen is announced which comprises approximately ¼Kg, 16 swg ALU-SOL Multicore Solder wound on a plastic reel and packed in an attractive carton with full instructions, which will be available from electrical, hardware and do-it-yourself shops.

The recommended retail price is £1.50 per reel, excluding VAT. In case of difficulty please contact the manufacturers direct. *Multicore Solders Ltd., Hemel Hempstead, Herts, HP2 7EP, England.*






LOUDSPEAKER KITS

Helme Audio Products Ltd. announce the introduction of two new hi-fi loudspeaker kits, the XLK-25 and XLK-50. Ready made versions and matching cabinet kits are also available. Kit XLK-25 comprises an 8in. low resonance woofer and 3in. square tweeter with aluminium cone. Kit XLK-50 uses the same high grade tweeter but takes advantage of a 13 x 8in. woofer with Bextrene cone. Both kits offer very good value for money and include a half-section, parallel cross-over network and all leads, terminal panel etc. NO soldering is necessary for their assembly. The kits are also supplied with protective built-in fuse against accidental overload. Prices (incl.VAT):

XLK-25 @ £23.17 per pair.

XLK-50 @ £42.18 per pair.

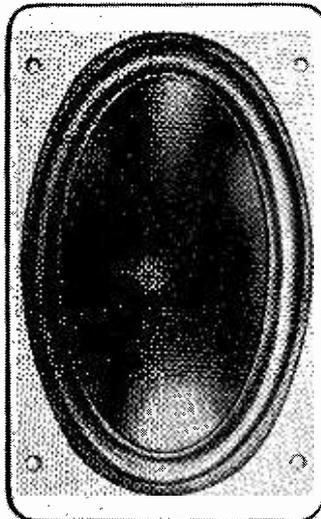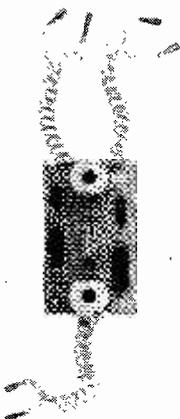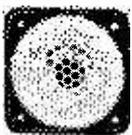Helme Audio Products Ltd., Summerbridge, Harrogate, HG3 4DR.




SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS.
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

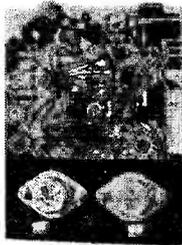New Versions using 3A 'Plastic Power' Driver Transistors Now Available. To meet demand, we have included a more powerful module in our well-established and proven range. These power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



SA35 35 watts RMS. Uses 7 transistors and 7 diodes Carr. paid. **£4-45**

A NEW ADDITION IS THE SA50 at £5-65

Carr. paid. A rugged, well built unit, capable of 50 watts R.M.S. out, with all the advantages of Saxon Amplifier design and quality. Ready now.

SA100 makes an ideal unit in disco assemblies. A real glutton for work. **£10-90**

Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid.

BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA.100.

Freq. response 15-40,000 Hz \pm 1dB
Distortion 0-2% at 1 kHz
Loads 4 to 16 ohms
Quiescent current 15 mA
Noise Better than -75 dB
Supply voltage SA35 25-45 volts
SA50/SA100 40-70 volts
Size 4 1/2" x 4" x 1" (SA100)
4" x 3" x 1" (SA35/SA50)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45 Unstabilized supply for 2 SA25/35 £4-90
PU70 Unstabilized supply for one or two SA100 £7-75 carr. 40p
PS45 Stabilized module for 2 SA25's or two SA35's £3-50 carr. free
MT45 Transformer for above, heavy duty £2-85 carr. 20p
MT30 Transformer for unstabilized supply complete with rectifier diodes mounted £3-50 carr. 20p
PS70 Stabilized supply module for one or two SA100's £4-90 carr. free
MT70 Transformer for PS70 £4-90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

TWO NEW PA/MIXER CONTROL UNITS

Using grouped pairs of inputs and outputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master control. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos etc. Standard jack sockets. Compact design. In strong metal cases. All units guaranteed for 3 years.

●M.4H

4 high Z, 4 low Z inputs, 4 sets of controls. Case 14" x 8" x 2 1/2" Carr. pd.

£18-50 + V.A.T.

●M.6HL

Case 18" x 8" x 2 1/2"

12 inputs (6 high Z, 6 low Z). Carr. pd.

£27-50 + V.A.T.

● Channel section modules, for building your own mixer. Gain—16 x (24dB). Tone controls—18dB swing. Carr. pd. £3-50 + V.A.T.


SAXON CONTROL UNITS

Mono (as shown)

Carr. 20p. **£6-50**

Stereo. Carr. 30p.

£15-80

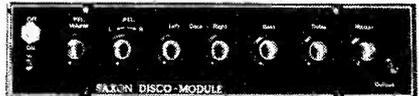

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic Input.)



120 WATT HEAVY DUTY MODULE

Rugged class A driver stage, this module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors. These are the modules where extra power is demanded.

Power output 120 watts into 8 ohms
Freq. response 20-20,000 Hz \pm 2dB
input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)

Module only **£13-90**
(Carr. 20p)

160 watt version with power supply **£27-50**
(Carr. 50p)

Module & power supply **£18-95**
(Carr. 40p)

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3KW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3KW lighting load. Smartly finished steel case. Carr. 30p.

£19-75

SINGLE CHANNEL UNIT


Operates from 5 to 100 watt amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p.

Carr. pd. **£8-90**

COMPLETE AMPLIFIERS

CSE 100. £34-90 carr. free

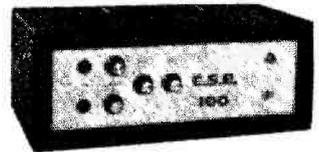This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls.



SAXON 100 £48-50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5-95 carr. 30p. 15" 50 watt 8/15 ohm £14-50 carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11-50 carr. 40p.

A.K.G. MICROPHONES

D11 DHL IDEAL DISCO MIKE ONLY £9-45 (rrp £11-00).

Prices quoted do NOT include V.A.T. 10% must be added on to total value of order for V.A.T.

S.A.E. for special price list.

Orders and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.

Telephone 01-684 6385

Hours 9.30 a.m.—5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED

TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by regd. letter, please

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

5p for 1 Valve.
Each additional Valve add 2p.

DM70	0-83	EF80	0-46	PC86	0-75	PL84	0-88	30C15/	
DY51	0-85	EF83	1-02	PC88	0-75	PL84	0-88	PCF800	1-05
DY86/7	0-42	EF85	0-43	PC90	0-56	PL85	1-05	30C17	1-00
DY802	0-45	EF86	0-40	PC88	0-40	PL802	0-98	PCF805	0-90
EABC80	1-00	EF89	0-81	PC89	0-85	PY33	0-88	30F5/PCF818	
EB01	0-58	EF91	1-30	PC189	0-65	PY81/800	0-50		1-10
EB02	0-75	EF92	1-40	PC80	0-51	PC850	0-55	30FL1/	
EBF80	0-60	EF95	1-35	PC82	1-30	PC850	0-75	30FL2	0-75
EBF83	0-82	EF183	0-80	PC86	0-85	PY800	1-05	30FL12	1-05
EBF89	0-58	EF184	0-80	PC200	0-85	PY801	0-50	30FL14	0-85
EC96	0-75	EH90	0-58	PC201	0-87	U26	1-00	30L1/PC884	
EC98	0-77	EL84	0-95	PC801	0-85	U191	1-00		0-82
EC981	0-45	EL91	1-30	PC809	0-65	U193	0-85	30L15/PC808.5	
EC982	0-43	EL81	0-80	PC806	0-66	UABC80	0-70		1-05
EC983	0-45	EL84	0-47	PC1200	0-88	UBCS1	0-70	30L17	0-90
EC984	0-55	EL86	0-55	PC182	0-54	UBF89	0-60	30P4MR	1-30
EC985	0-53	EL86	0-85	PC183	0-86	UC85	1-00		
EC988	0-75	EL85	0-70	PC184	0-59	UC881	1-60	30P12/PC801	
EC989	0-71	EL91	1-31	PC185	0-63	UC182	0-70		1-05
EC990	0-68	EL80	1-30	PC189	0-63	UC183	0-70	30P19/PC802	
ECF82	0-78	EM84	1-18	PC1805/85		UF89	0-80		1-00
ECF86	0-71	EM87	1-18		0-83	UL84	0-85	30PL1/PC1801	
ECF81	1-00	EY61	0-83	PD500	1-55	UL85	0-95	BC107	0-10
ECF83	0-70	EY86/87	0-42	PF1200	0-80	6/30L2/		BC108	0-10
EC984	0-78	EY88	0-64	PL36	0-88	EC808/4	1-00	BC109	0-10
EC180	0-53	EZ10	0-52	PL81	0-61	6F23/EF81		BC113	0-15
EC181	0-68	EZ21	0-60	PL81A	0-58		1-05	BC117	0-20
EC183	0-68	GY501	0-80	PL82	0-50	30C1/PCF80		BC143	0-35
EC186	0-83	GZ24	0-78	PL83	0-96		0-51	BC147	0-18
								BC148	0-10
								BC169C	0-18
								BC182	0-10
								BC183	0-18
								BC184L	0-11
								BCY32	0-60
								BCY33	0-24
								BCY34	0-25
								BCY70	0-15
								BCY71	9-20
								BCY72	0-18
								BCZ11	0-60
								BD121	0-75
								BD124	0-80
								BD131	0-75

30C15/		30C17	1-00	30C18	0-25	30C19	0-25	30C20	0-25
30C17	1-00	30C18	0-25	30C19	0-25	30C20	0-25	30C21	0-25
30C18	0-25	30C19	0-25	30C20	0-25	30C21	0-25	30C22	0-25
30C19	0-25	30C20	0-25	30C21	0-25	30C22	0-25	30C23	0-25
30C20	0-25	30C21	0-25	30C22	0-25	30C23	0-25	30C24	0-25
30C96	0-25	30C97	0-25	30C98	0-25	30C99	0-25	30C100	0-25


NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0-80	EF80	0-25	PC86	0-80	UF81	0-75	6X4	0-40
AZ31	0-55	EF85	0-35	PC88	0-80	UF89	0-40	6X6	0-40
CB1	1-00	EF86	0-30	PC97	0-45	UL41	0-85	XSGT	0-45
CL33	1-50	EF89	0-28	PC90	0-48	UL84	0-43	7B6	0-75
CY31									

A High Sensitivity DC Voltmeter

D. J. SILVESTER

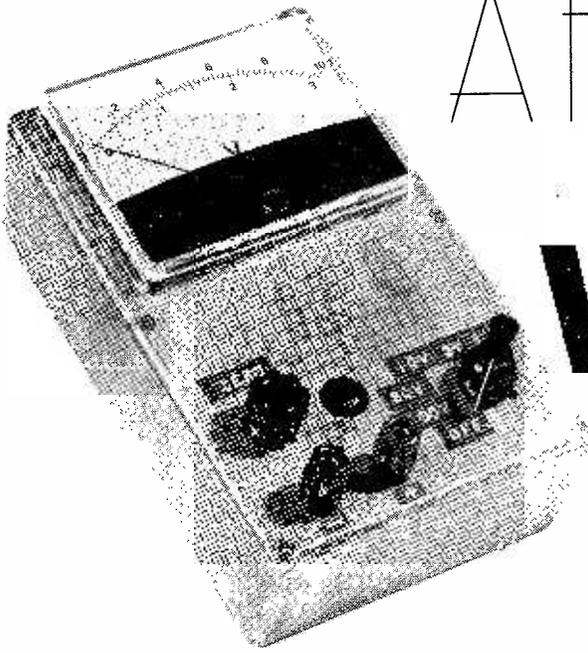


OF ALL of the basic measurements that can be made with a normal multimeter, the determination of voltage is probably the one most commonly attempted and the measurement that is most likely to give rise to erroneous results.

MEASUREMENT ERRORS

Consider for a moment the circuit of a low power audio amplifying stage in any piece of equipment, Fig. 1. The current through R3 will, with no input signal, be of constant value determined by the values of R1, R2 and R4, and will not be altered if the value of R3 is altered providing that the voltage at the collector of the transistor exceeds that at its base by 2 volts or more.

Let us suppose we wish to measure the voltage across R3, and given that the transistor delivers a current of $100\mu\text{A}$ and the value of R3 is $100\text{k}\Omega$, the voltage across the resistor will be 10V.


If we measure the voltage across R3 with a normal multimeter of $20\text{k}\Omega/\text{volt}$ sensitivity then, on the 10V range, the meter will appear as a $200\text{k}\Omega$ resistor. If a $200\text{k}\Omega$ resistor is shunted across the $100\text{k}\Omega$ resistor the apparent resistance drops to $66.7\text{k}\Omega$, and consequently the voltage across the combination drops to 6.67V , vastly different from the 10V correct value.

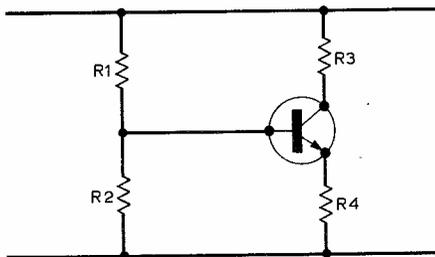

AM 0034

Fig. 1: Basic transistor circuit to demonstrate errors possible when using low sensitivity meters.

It is obvious therefore that a meter with a higher sensitivity would give much less error, but although valve and FET voltmeters can be built by the home constructor, difficulties can occur due to thermal drifts as the components in the circuit warm up. The circuit to be described uses a μA741C integrated circuit as the amplifying element of the circuit hence eliminating drift problems. Since it is difficult for the amateur to obtain high value, high tolerance resistors the sensitivity of the circuit has to be made $100\text{k}\Omega/\text{volt}$ although $1\text{M}\Omega/\text{volt}$ would be preferable.

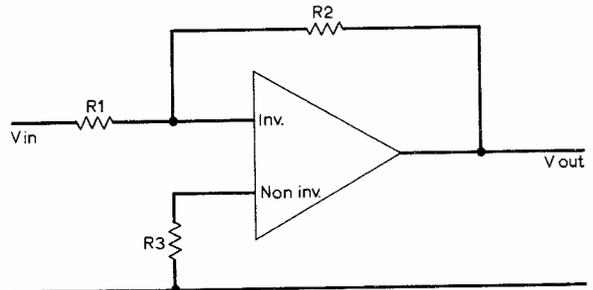

AM 0035

Fig. 2: Use of the μA741C integrated circuit as an amplifier.

★ components list

Resistors

R1	$100\text{k}\Omega$	} $\frac{1}{2}\text{W } 1\%$	R6	$10\text{k}\Omega$	} $\frac{1}{2}\text{W } 5\%$
R2	$300\text{k}\Omega$		R7	$10\text{k}\Omega$	
R3	$1\text{M}\Omega$		R8	$10\text{k}\Omega$	
R4	$3\text{M}\Omega$		R9	820Ω	
R5	$10\text{M}\Omega$				

(R4 is $2 \times 1.5\text{M}\Omega$)

VR1 $10\text{k}\Omega$ linear potentiometer
VR2 500Ω miniature preset pot

Miscellaneous

IC1, μA741C (TO5 or DIL). S1, 4-pole 6-way, (from 2×2 -pole 6 way wafers). M1, $100\mu\text{A}$ FSD, scaled 0-3 and 0-10 (RS-MR31). Case, approx $7" \times 4" \times 2"$. Terminals (2). Knobs (2). Battery clips (2 pairs). Terry spring clips (2). Batteries, PP4 (9V-2 off). Veroboard.

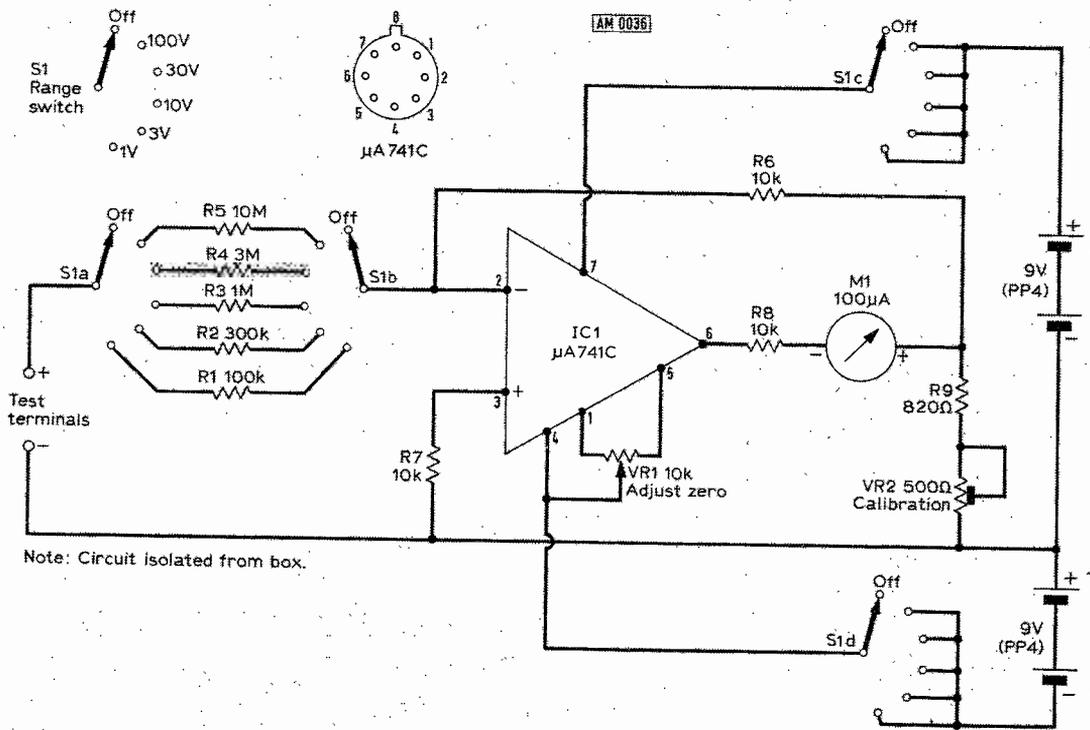


Fig. 3: Full circuit of the high sensitivity voltmeter. If difficulty is experienced in obtaining a suitable wafer switch, S1c and S1d could be replaced by a separate double pole toggle switch.

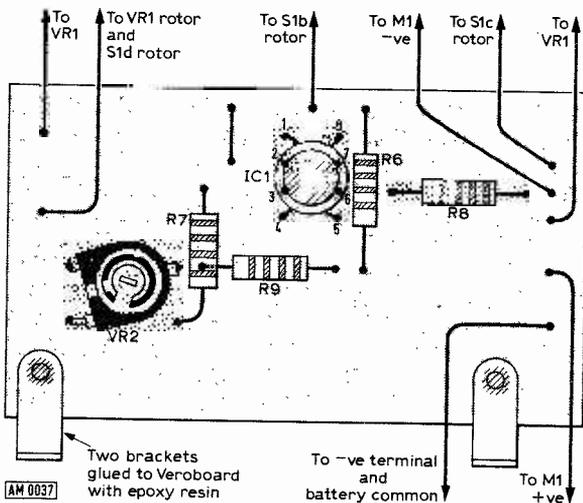


Fig. 4: Layout of the small veroboard carrying the IC. Supporting brackets are cemented to the box lid.

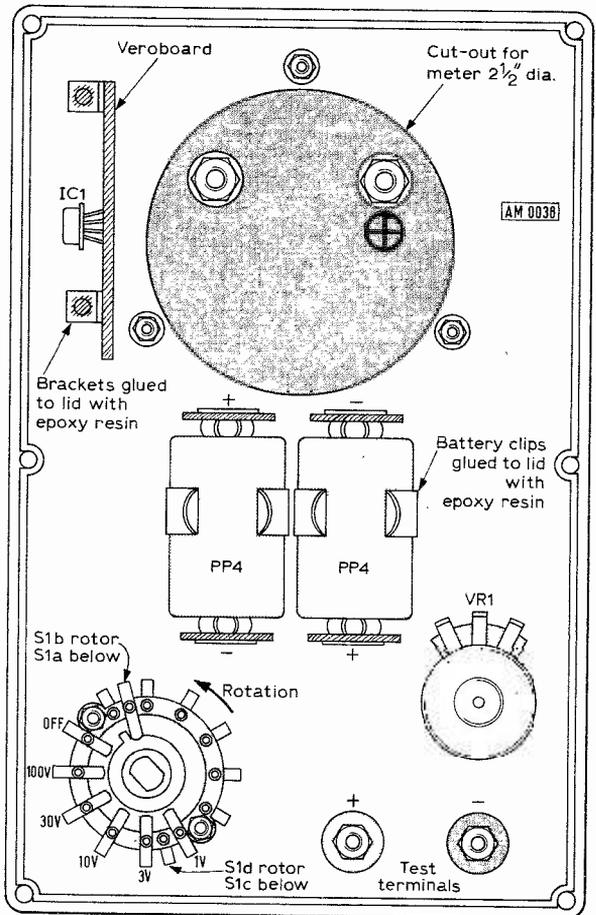


Fig. 5: General layout of components on box lid with connections to range switch.

Fig. 2 shows the basic inverting amplifier used in the meter. If we assume that the IC is perfectly matched (it would give no output if both inputs were earthed), we can prove that if R2 and R3 are not the same value the output voltage will not be zero, due to the currents being drawn through these resistors.


The IC has two terminals for offsetting small differences due to mismatch of components in the IC and the tolerance of the external resistors, as well as frequency compensating components to prevent

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM

STEREO AND MONO

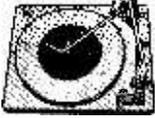Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. ACO 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in.



£8.25 Post 25p.

PORTABLE PLAYER CABINET

Modern design, black resin covered, silver front grille. Suitable for above player. Motor board out for BSR deck.

£4.50 Post 25p.

E.M.I. WOOFER AND TWEETER KIT

Available separately. Post 25p

Woofers 54.25, Tweeter 21.90. Comprising a fine example of a Woofer 10 1/2 x 8 1/2 in. with a massive Ceramic Magnet, 440z. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.



Impedance Standard..... 8 ohms
Maximum Power..... 12 watts
Useful Response..... 35 to 18,000 cps
Baffle Resonance..... 45 cps
SUITABLE ENCLOSURE 20 x 13 x 9 in. £9.90 POST 25p
MODERN GROOVED FRONT DESIGN, TEAK FINISH

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Maker's last list price 24.50. Brand new and fully guaranteed. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. TWO TYPES AVAILABLE: 30 MINUTES OR 0 TO 6 HOURS. OUR PRICE £1.65. P. & P. 15p OR £3 PAIR. (STATE TYPE A OR B WHEN ORDERING.)



WEYRAD P50—TRANSISTOR COILS

RA5W Ferrite Aerial... 72p
Osc. P50/LAC... 33p
I.F. P50/20C 470 kc/s... 36p
3rd I.F. P50/30C... 36p
Spare Coils... 30p
Mullard Ferrite Rod 8 x 1/2 in. 20p. x 1/2 in. 20p.

VOLUME CONTROLS

80 Ohm Coax 4p. yd. BRITISH AERIALITE AERAXIAL-AIR SPACED 40 yd. 21.40; 80 yd. £2. FRINGE LOW LOSS Edge 5K.S.P. Transistor 25p
Ideal 625 & colour 10p yd.

8in & 10in ELAC HI-FI SPEAKERS

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm coil. 8in. 10 watt. 10in. 12 watt. 25p
£3.75 Post 25p



E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 25p
£4.50



With flared tweeter cone and ceramic magnet, 10 watts.

Bass res. 45-60 cps. £2.75
Flux 19,000 gauss. Post 25p
State 3 or 8 or 15 ohm. Post 25p
BOOKSHELF CABINET £5.50 Post 25p

BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2 1/2 x 6 1/2 x 1/2 in. Pre-aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100mV input. Full instructions for any FM Tuner. Some technical experience. £6.95 15p



BLANK ALUMINIUM CHASSIS 18 s.w.g. 2in. sides. 6 x 4in 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 90p; 15 x 14in. 99p; 11 x 7in. 90p; 16 x 10in. £1.
ALUMINIUM BOX 6 x 4 x 1/2 in. 90p.
ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 9p; 8 x 6in. 15p; 14 x 8in. 16p; 10 x 7in. 19p; 12 x 8in. 20p; 12 x 8in. 20p; 16 x 8in. 28p; 14 x 9in. 34p; 12 x 12in. 40p; 16 x 10in. 50p
PAXOLIN PANEL 10 x 8in. 15p.

ANOTHER RCS BARGAIN!

4 Transistor Mono Amplifier

Powerful 3 watt output. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. Size 8in. wide x 4 in. deep x 3 in. high. Suitable 7" x 4" speaker. £1. PRICE £5.95 Post 25p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V. AC. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V. DC. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2.20 POST Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2 in.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12V or H.T. line 200-300V D.C. operation. Size 1 1/2" x 1 1/2" x 1 1/2". Response 25 c.p.s. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. 99p Post Full instructions supplied. Details S.A.E.

NEW ELECTROLYTIC CONDENSERS

2/350V .. 14p	250/25V .. 14p	60+50/350V .. 50p
4/350V .. 14p	500/25V .. 20p	60+100/350V .. 50p
8/450V 18p	1000/25V 30p	32+32/250V .. 20p
18/450V 25p	1000/50V 47p	32+32/450V .. 45p
32/450V 35p	8+8/450V 22p	350+50/325V .. 55p
25/25V .. 10p	8+18/450V 20p	32+32+32/350V 55p
60/50V .. 10p	16+18/450V 40p	100+50+50/850V 55p
100/25V 10p	32+32/350V 40p	

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
60mF. 12V. 15p; 25V. 20p; 50V. 30p.
100mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p.
300mF. 6V. 25p; 25V. 42p; 50V. 57p.
2500mF. 60V. 62p; 3000mF. 55V. 47p; 50V. 65p.
6000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 95p.

CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p

PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 6p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%; 2.2-500pF 8p; 500-2,200 pF 10p; 2,700-5,000pF 20p; 6,800pF-0.01mF 30p; each. TWIN GANG. 10+0.001 20pF = 170pF. 65p; 500pF standard 4p. 355+355 with 25+25V. Slow motion drive 50p. SHORT TAP. 10+0.001 10pF = 55pF 55p; 50pF 55p. NERN PANEL INDICATORS. 250V AC/DC Amber 20p. RESISTORS. 1/4 w. 1/2 w. 1 w. 1 1/2 w. 5, 10 ohms to 10 meg. HIGH STABILITY. 1/4 w. 2% 10 ohms to 6 meg. 10p. Ditto 5% Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS. 6 watt, 10 watt, 15 watt 10 ohms to 100K 10p each. 2 watt, 1 ohm to 5.2 ohms 10p. TAPE OSCILLATOR COIL. Valve Type 35p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 10 x 3 1/2 in. 3 watts per channel, plays all records 33 rpm, 45 rpm. Separate volume and tone controls. 240V AC mains. Attractive Brown colour, weight 13lbs. £25 + 85p carriage.

BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned—requires 10.7 Mc/s IF. Complete with tuning gang. Connections supplied but some technical experience essential. Our Price £3.95 Post 20p.

MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12 v. 50 mA. 90p
250-0-250 80 mA. 3-3 v. 3-5 a. 3-3 v. 1 a. or 5 v. 2 a. £2.50
350-0-350 80 mA. 3-3 v. 3-5 a. 3-3 v. 1 a. or 5 v. 2 a. £3.00
300-0-300 v. 120 mA. 3-3 v. 3-5 a. 1 C.T. 6-3 v. 2 a. £3.25
MINIATURE 200 v. 20 mA. 6-3 v. 1 a. 2.2 x 2 1/2 x 2 1/2 in. 75p
MIDGET 220 v. 45 mA. 6-3 v. 2 a. 2 1/2 x 2 1/2 x 2 1/2 in. 80p
HEATER TRANS. 6.3 v. 3 a. 3 a. 60p
GENERAL PURPOSE LOW VOLTAGE, Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 16, 24 and 30 v. £2.25
1 amp. 6, 8, 10, 12, 16, 20, 24, 30, 36, 40, 48, 60, £2.25
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.25
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.75
3 amp. 5, 8 and 13 v. £1.00; Ditto 5 amp. £1.20
3 amp. 3, 5, 8, 10, 13 and 5-0-5 v. £1.30; Ditto 5 amp. £1.50
3-0-6v. 300 mA., 90p. 9v. 1 amp. 95p. 12v. 300 mA., 75p.
12v. 500 mA., 35p. 12v. 750 mA., 95p.
AUTO TRANSFORMERS 115v. to 250v. or 230v. to 115v. 150w. £2.25; 500w. £2.25; 750w. £1.01; 1000w. £15.
CHARGER TRANSFORMERS. Input 200/250 v. for 6 or 12 v. 1 amp. £1.50; 2 amp. £1.80; 4 amp. £2.50.
BATTERY CHARGERS. 1 1/2 A. £2; 3A £3; 4A 2.5A. £4-50.

FACTORY ACT! MAINS ISOLATING TRANSFORMER

Primary 0-110-240 v. Secondary 0-240 v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing lugs. Famous make. Value £10. SPECIAL PRICE £10 Carriage + 20p.
IDEAL FOR COLOUR TV 50p.
Can be used as 800 watt Auto Transformer 240-110V.

ALL MODELS "BAKER SPEAKERS" IN STOCK Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free

BAKER 12in. MAJOR £10



P. & p. 25p
30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. NOTE 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c.p.s. with tweeter crossover, baffle and instructions. £12.50 P. & p. 25p.

BAKER "BIG-SOUND" SPEAKERS P. & p. 25p

Group 25"	Group 35"	Group 50"
12 inch 25 watt 3 or 8 or 15 ohm	12 inch 35 watt 3 or 8 or 15 ohm	15 inch 50 watt 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS

For 12in. or 10in. dia. speaker 20 x 13 x 9 in. £9.90 Post 25p
For 13 x 8in. or 8in. speaker 16 x 10 x 9 in. £5.50 Post 25p
For 8 x 5in. speaker 16 x 8 x 6 in. £4.40 Post 25p
For 6in. and tweeter 12 x 8 x 6 in. £4.25
LOUDSPEAKER CABINET WADING 18in. wide, 15p It.

GOODMANS 6 1/2 in. HI-FI WOOFER £4

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosures Systems, etc. Suitable Cabinet 12 x 8 x 6, £4.00. Suitable Tweeter, £2.00.



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 x 3/8 in. deep. Rating 10 watts, 3 ohm or 15 ohm models. £1.90 Post 10p

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16k/s, 10W, 15W or 15 ohm £1.95. De Luxe Horn Tweeters 2-18 K/s, 15W, 15 ohm £3.50. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p. LOUDSPEAKERS 3 OHMS. 7 x 4in. £1.25; 8in. £1.50; 8 x 6in. £1.80 8in. £1.75; 10 x 6in. £1.90; 10in. £2.00. SPECIAL OFFER: 80 ohm, 2 1/2 in.; 2 1/2 in. 95 ohm 2in. 3in. 25 ohm 2 1/2 in. dia. 6" x 4" £1 EACH 15 ohm, 3 1/2 in. dia.; 6 x 4 in.; 7 x 4 in.; 8 x 5 in. TYPE 3 ohm, 2 1/2 in.; 3 1/2 in.; 5in. dia. (6 x 4 in. 8 ohm £1.50) RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 3in. diameter 4 watt; 10in. 5 watt £2.20. 12in. 6 watt 3 or 8 or 15 ohm models £2.50 each. Post 25p. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50.1 25p. 6 WATT MULTI-RATIO. 8, 8 and 15 ohms, 80p.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All transistorized. 4 inputs, speech and music. 4-way mixing. Output 8/15 ohm. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free



BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3.95

STEREO VERSION OF ABOVE £5.95

PRINTED FM TUNER 88-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. £14.85

Walnut Cabinet. Size 7 x 5 x 4 in. £9.85

BARGAIN FM TUNER as above less cabinet. £4.50

BARGAIN 8 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, treble and bass controls 18v. £4.50

TWO RPM GEARED MOTOR 240v. A.C. mains. Ideal for displays/disc lightwheels. 95p post 25p.

E.M.I. GRAM MOTOR 130v. or 240V. A.C. 2,400 rpm. 2-pole 70mA. Spindle 1/2 x 1/2 in. Size 2 1/2 x 2 1/2 x 2 1/2 in. Post 25p.

DELUXE 4 POLE MOTOR 1400 rpm. 42W size 3 1/2 x 3 1/2 x 2 1/2 in. £1.00

DELUXE 4 POLE MOTOR 1400 rpm. 42W size 3 1/2 x 3 1/2 x 2 1/2 in. £1.00

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Minimum post 20p. Illustrated Colour Brochure Radio Books & Components Lists 10p. Buses 50, 68, 159 Rail Selhurst. Tel. 01-684-1665.

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 7 removable space dividers. Build up any size cabinet for wall, bench or table top.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT! HARBOR! TIDY!

DISCOUNT PRICES

SINGLE UNITS (5" x 2 1/4" x 2 1/4") £1.25 Dozen

DOUBLE UNITS £2.15 Dozen

TREBLE (3D) £2.20 for 8

DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.25

For extra large size (6D1) £3.10 for 8, Carriage 35p Orders over £10 post free

QUANTITY DISCOUNTS 15% in £1 for orders over £6, 7 1/2% over £10, 10% over £20. Quotation for large quantities.

PLEASE ADD 10% VAT TO TOTAL REMITTANCE.

IVORVET (Dept. PW9) 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

5 SIZES ALL INTERLOCK

ELECTROKIT

12 Lauderdale Road, London, W.9
Telephone 01-286 0011

LIGHT DIMMER. Kit contains all parts including circuit and construction data, 480 watts, fully suppressed.
Price £2.10

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), £9.50. This kit includes all the parts for the assembly of this popular and reliable system. The hardware and the construction data are included.

Send for details of kits available (please enclose S.A.E.). All kits sent POST FREE within the limits of the U.K.

Please note, prices shown do not allow for V.A.T. Please add 10% to your order.

ALL PRICES INCLUDE VAT

BARGAIN PARCELS 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57 1/2p p.p.; 56lb at £4.95 plus £1.37 1/2 p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££s. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £1.55 post paid.

NEW HEAVY COAX CABLE dia. 3/8" 70 ohms approx. 50ft. lengths £1.55, p. & p. 32 1/2p. 100 ft. lengths £2.97, p. & p. 55p.

AERIALS. New Condition Whip Type, 4ft. 22p; 11ft. 82 1/2p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 67 1/2p. p. & p. 27 1/2p.

CRYSTALS AS NEW. Hc 6u, 5,345; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,295 Kc/s. 55p each plus 8p p.p.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 27 1/2p, minimum order of six.

ANY HEIGHT AERIAL TUBULAR SECTIONS 3/8" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 22 1/2p p. & p. 5p each. Minimum order 6.

AS NEW AERIAL TUNER UNIT No. 6 RF, consisting of 1 1/2 inch 500 micro/ampmeter 3 gang tuner 75 PF geared BNC type socket size 5 1/2" x 4 3/8" x 5". Price £1.65, p. & p. 27 1/2p.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft 50p, 100ft. 60p, p. & p. 22p.

AERIAL POLES 4ft high 2" in diameter push-in type as new 75p each p. & p. 25p each minimum four.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1.10 each section. Carriage 37 1/2p each section. 4" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1.10 + 32 1/2p p.p.

AS NEW 500ua PENNY SIZE METERS complete with jack plug price £1.10 each, p. & p. 10p.

COMMUNICATION RECEIVER PCRS price £10. post paid.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

COMPARE OUR PRICES


Speaker Bargains		
E.M.I. 13 x 8 in 3, 8 & 15 OHMS		
PLAIN	£2.00	
WITH TWEETER	£2.25	
TWIN TWEETER	£3.50	
Type 350-20 watt with Tweeter		
8. OHM p. & p. 37p.	£7.25	
8 x 5 in 3, 8 & 15 OHMS	£1.10	
6 1/2" (93850) 8 ohm	£2.20	
8" (14A/1000) 8 ohm 10 watt	£4.00	
E.M.I. 3 1/2" TWEETER C/		
MAGNET 8 ohm	£1.00	
FANE 7 x 4 in 3 & 8 OHMS	.90	
8" 2 OHM DUAL CONE	£2.10	
CELESTION 8" 15 OHM	£1.40	
BAKER GROUP 25" 12" 25		
WATT 8 or 15 OHM	£6.00	
5" 8 ohm C/MAGNET	80p	
	p. & p. 10p	
2 1/2" 8 or 64 OHM p. & p. 10p.	.45	
POSTAGE 25p per SPEAKER		
Kit-Form Cabinets Teak		
(17" x 10" x 6") with a 13" x 8"		
or 8" CUT OUT	£2.95	
18 x 11 x 9 with 13" x 8" cutout for EMI 350	£3.95	
(12" x 12" x 6") with a 8" x 5" or 6" CUT OUT	£2.25	
(PLEASE SPECIFY CUT OUT)		
Add 35p per Cabinet for p. & p.		
Cartridges with standard fittings & styl		
ACOS GP91/2SC or GP91/3SC STEREO COMPATIBLE	.90	
ACOS GP94 STEREO CER.	£1.50	
ACOS GP95 STEREO CRYST.	£1.15	
ACOS GP96 STEREO CER.	£1.50	
9THAC SONOTONE STEREO CERAMIC (DIAMOND)	£1.70	
9THAC/G SONOTONE STEREO CER. (DIAMOND)	£1.70	
SLIMLINE	£1.70	
ACOS GP97/2C MONO CRYST.	.65	
ACOS GP101 COMP. CRYST.	.65	
19-TI SONOTONE STEREO CRYSTAL	.80	
POSTAGE 5p per CARTRIDGE		
Microphone Bargains		
CM 20 Crystal Hand	.45	
DX143 Dynamic, cassette-type styl	£1.00	
CM70 PLANET stick metal, switch crystal	£1.45	
DM160 Dynamic uni-dir, ball metal	£3.75	
UD130 50K/600 OHM uni-dir, ball metal	£4.50	
TW209 LESSON DUAL IMP ball metal, uni-dir.	£3.75	
CONDENSER MIKE uni-dir. 600 OHM	£7.95	
GIUITAR MIKE	.45	
LAPEL TYPE, crystal	.40	
POSTAGE 17p each.		
Battery Eliminators		
240v input 6 or 9v d.c. output at 150 mA	£1.99	
12v d.c. input (for cars, fits in lighter socket) 6, 7 1/2 or 9v d.c. output at 300 mA	£2.50	
P. & P. 10p		
Tapes — "MYLAR" base finest quality British made.		
5" 600 ft 36p	5 1/2" 1800 ft 85p	
5" 900 ft 45p	7" 1200 ft 55p	
5" 1200 ft 60p	7" 1800 ft 80p	
5 1/2" 900 ft 49p	7" 2400 ft 95p	
5 1/2" 1200 ft 55p		
POSTAGE 9p each.		
PLASTIC LIBRARY CASES		
for 5in Reels 16p		
5 1/2in Reels 19p		
7in Reels 21p		
P. & P. 5p each		

THIS MONTH'S SPECIAL OFFER
E.M.I. Loudspeaker Enclosure kit. (LEK 450/8) comprising 2 EMI 450 Speakers (8 ohm 10 watt T/Tweeter, plus cross-over) and 2 EMI Cabinet kits 18" x 10" x 11" plus Acoustic Wadding, Glue, Screws, Instructions. Recom. Retail Price £29.20. Bargain at £18.00 inc. V.A.T. plus 50p p.& p.

SEND 25p FOR COMPLETE CATALOGUE Add 10% VAT on prices, inc. P. & P.

RIVERSDALE ELECTRONICS
Mail Order Department W9/73, P.O. Box 470, Manchester M60 4BU
ALL OUR MERCHANDISE IS FULLY GUARANTEED

RAYMER MICROCHIP RE500

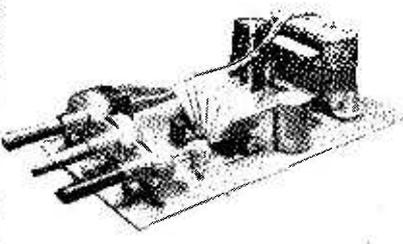

This advanced high-fidelity integrated amplifier is completely self-contained and only requires connecting to mains, speaker and input.

Ideally suited for:
MONO RECORD PLAYERS
MONO CONVERSION TO STEREO
STEREO CONVERSION TO QUADRAPHONIC (x 2 Microchip + Decoder)
T.V. AMPLIFIER
TAPE AMPLIFIER
P.A. INSTALLATIONS
AUDIO ALARM ETC.

SPECIFICATIONS
OUTPUT 5 watt RMS (10w peak)
FREQUENCY RESPONSE 10hz to 50khz ±3db
TOTAL HARMONIC DISTORTION less than 1%
LOAD IMPEDANCE 4 to 16 ohms
INPUT IMPEDANCE 100k ohm Nominal
POWER GAIN 40db Typical
SIZE 140 x 80 x 45mm

With free instruction sheet.
PRICE £6.93 (inc. VAT) plus 25p p. & p.
Guaranteed 12 months against failure in normal use.
TRADE ENQUIRIES WELCOMED

NAME

ADDRESS

Please send


I enclose P.O./Cheque/Money Order

RAYMER ELECTRONICS LTD
STANLEY RD, CAMBRIDGE CB5 8LB
Reg. Bus. 1031205

oscillation. The final circuit, Fig. 3, is very simple to construct and is an excellent project for a beginner, as well as being a very useful instrument.

CONSTRUCTION

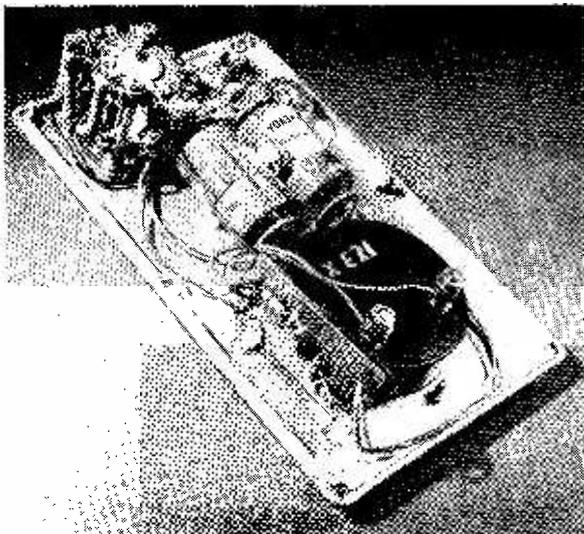The entire circuit is built on the lid of a 7" x 4" x 2" diecast aluminium box using the base as a cover. The switch should be assembled so that the two



Photograph of completed voltmeter, which can be compared with the layout shown in Fig. 5.


wafers are separated by 6BA spacers, 1" long. The switch should only move through six positions, the "off" position being with the switch turned fully anti-clockwise, when viewed from the front panel.

The resistors R1 to R5 are mounted on the switch so that as the switch is turned clockwise the value is reduced. The remaining switch positions are connected so that when the resistors are in circuit the batteries will be connected to the board.

The circuit board, Fig. 4, should present no constructional problems provided that reasonable care is taken and that the copper strips which are supposed to be cut are completely severed. Fig. 5 shows the details of the switch wiring. The remaining work consists of attaching the assembled parts to the lid. The circuit board is stuck to the case, two pieces of bent metal supporting the board, the Terry battery clips being attached in the same way, after which final wiring can take place.

CALIBRATION

The meter should now be in working order and can be switched on. By turning the offset potentiometers VR1 it should be possible to zero the meter. If the direction of rotation of the potentiometer and the movement of the needle do not coincide the wires to the ends of the potentiometer can be interchanged. The meter is calibrated by using either a known voltage source or a 1.35V mercury battery. This voltage is connected to the instrument and by rotating the present VR2 the meter can be set to the correct voltage. ■

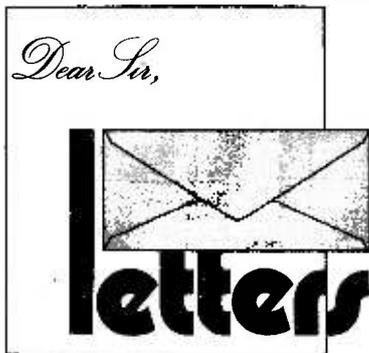

Ideal resist

In recent months there appears to have been increasing use made of Printed circuit boards in projects published in P.W. The commonly used resist mentioned enamel paint suffers from two major disadvantages.

(1) It may take up to six hours for the paint to dry. This increases the chance of smudging and having to start all over again.

(2) It is difficult to remove the enamel while it is wet. This means that any mistakes made when painting on the resist cannot be easily corrected.

After spending many hours sweating over an artist's brush and hot copper laminate, I decided to try using women's nail varnish on the laminate. This has proved far better than enamel paint and dries within minutes. Mistakes can be corrected when dry by just scraping with a modelling knife.—D. K. Baruth (Northumberland).

Improving VHF radio

Further to my article in the April issue of PW, readers in areas of poor reception may obtain higher gain with the FET amplifier, Fig. 2, by shorting out R4 or reducing the value to 82 ohms. Experimentally, a 250 ohm pre-set potentiometer could be fitted and the optimum value found for a particular location.

Alan C. Ainslie
(Workshop, Notts.)

Power supplies

Correspondents have pointed out to me that in "Regulated Power Supplies for your Transistor Radio", PW June 1973, there is a minor error.

It is not, of course, true to say

that the output voltage is higher than the zener voltage, it is *lower*. This hardly affects the operation of a transistor radio, which is designed to function at low voltages, as supplied by a partly exhausted battery.

The mistake crept into the article due to my misreading a hastily written workshop note.
J. N. Watt (Surrey).

Play the game Lads!

Would it be possible to enlist your aid in bringing to the notice of "CQ!" Column participants that some of them are just bad-mannered opportunists.

I am no eccentric old buffer but admit to having had your magazine every month for years. My grouse relates to having, time after time, sending free copies of P.W. P.E. TV etc. to various people who do not even acknowledge receipt—let alone refund any postage. The last time this happened was in response to a "CQ!" published in the February issue. I'll not mention any names or addresses but hope the recipients' consciences will bother them.—R. Williams (Gloucestershire).

BETTER AERIALS



for BETTER STEREO

GORDON KING

PART 1

THE BBC is currently adopting a new approach with regard to the linking of studio centres to transmitters, notably for mono and stereo VHF radio programmes on the FM system of broadcasting. This is facilitating the introduction of stereo to FM transmitters which have hitherto been too remote from studio centres for equalised and balanced linking via the earlier radio and line analogue circuits.

Stereo demands high performance links capable of conveying two audio signals in isolation over hundreds of miles without quality impairment, imbalance or variation in transit time. Unless these requirements are adequately satisfied degradation of the stereo effect at the receiving points is bound to follow. On mono, of course, the requirements are significantly less critical; for a start there is only a single circuit to bother with, and phase distortion (i.e., transit time variation) on this is of minor consequence.

PULSE-CODE MODULATION

The new approach is based on translating the analogue signal (i.e., the type of signal yielded by a microphone or gramophone pickup, for example) to digital form, linking the signal in this form and translating it back to the original analogue for modulating the transmitter. The series of digits so produced corresponds to amplitude samples of the audio analogue. The digits are of simple zero/one form (i.e., binary) and the nature of the series (i.e., 011, 101, 111, etc.) reflects the instantaneous amplitude and polarity of the real audio signal.

In other words, the manner in which the digit series is coded is a direct function of the audio signal at that instant. It is thus a relatively simple matter to decode the pulse chain to reform the original audio analogue.

A major advantage of this scheme is that it is far less worried by noise and repeater non-linearity

than direct analogue linking. Indeed, any noise on the digits or pulses can be sliced off without impairing quality of the ultimately decoded signal.

The system, which is not new—the BBC has been experimenting for ten years with digital techniques applied to audio signals, is known as pulse code modulation (pcm). A high quality pcm system requires more than a mere three digits to secure the necessary number of sampling levels. The number of levels sampled is related to the number of digits n in terms of 2^n . Thus only eight audio amplitude levels can be sampled with a three-digit binary code. The BBC uses a thirteen-digit binary code which corresponds to the sampling of 8192 levels—but the system also employs a parity 'bit' for error correction—and the sampling rate is 32kHz.

13-CHANNEL CAPACITY

The system carries thirteen high-quality audio signals in a single wideband circuit. The sending equipment is located at the London Control Room and the thirteen-channel multiplexed output is communicated by coaxial cable to the microwave system which directs the pcm signals to the transmitters. The thirteen-channel capacity provides the necessary scope for any future activities, since any one circuit can be used either as a mono channel or one of a stereo pair, and it would be possible to utilise four channels for quadrphony. Thus the future is well looked after!

It is noteworthy that the thirteen, high-quality circuits of 15kHz bandwidth and each of thirteen-digit binary code can be accommodated by any link capable of handling a single 625-line television signal. Each channel has a signal/noise ratio of 70dB (peak signal to peak weighted noise).

The pcm linking thus means that listeners will obtain improved quality signals from their FM tuners, even when the programme source is remote from the transmitter, and that transmitters which have hitherto been out of range of an equalised two-channel link of the earlier kind will be able to pick up high-quality signal pairs from the pcm system.

The six element beam aerial shown in the heading is the Antiference Ltd. "Mushkiller", type FM264.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY £1.05

POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	55p
B81	10	Reed Switches, 1" long, 1" dia. High Speed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	55p P & P 15p
H4	250	Mixed Resistors. Approx. quantity counted by weight	55p P & P 15p
H7	40	Wirewound Resistors. Mixed types and values.	55p
H9	2	OC71 Light Sensitive Photo transistor	55p
H28	20	OC200/1/2/3 PNP Silicon unceded TO-5 can	55p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated Circuits. 4 Gates BMC 962, 2 Flip Flaps BMC 945	55p
H40	20	BFY50.7, 2N696, 2N1613 NPN Silicon unceded TO-5	55p
H41	2	Sil Power transistors comp pair BD131/132	55p

UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	55p
B1	50	Germanium Transistors PNP, AF and RF	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts.	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied.	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each



OVER

1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.
Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.
Please state Audio NPN or Audio PNP when ordering.
ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44 P. & P. 11p/1,000.

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN silicon similar ZTX 300 range
TYPE "H" PNP silicon similar ZTX 500 range

8 RELAYS FOR £1.10
P & P 27½

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors. Please ask for Pak P.I. Only 55p. 11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television. **This complete kit of parts costs £3.85, post paid.**

A MUST for Colour T.V. Alignment.

ELECTRONIC TRANSISTOR IGNITION

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions, supplied with these outstanding features—
Transistor and conventional switchability, burglar proof lock up and automatic alarm, negative and positive compatibility. This project is a "star" feature in the September edition of "Electronics Today International" magazine available from Aug. 10th. Our kit is recommended by the ETI magazine.

Complete kit including p & p £7.92
Ready built and tested unit £3.02 extra.

FREE CATALOGUE FOR



TRANSISTORS,
RECTIFIERS,
DIODES,
INTEGRATED
CIRCUITS,
FULL PRE-PAK
LISTS

100,000

Plastic Power Transistors in stock, more on way
NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15.	HFE Min 15.		
	1-12	13-25	26-50
40 Watt	22p	20p	18p
90 Watt	26p	24p	22p

Range 2. VCE. Min 40. HFE Min 40.

	1-12	13-25	26-50
40 Watt	33p	31p	29p
90 Watt	38p	36p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available
This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16½p each } Now new low profile
16 pin type at 18p each } type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes; 40p
This includes many thousands of British U.S.A., European and C.V. equivalents.

The Hiffe Radio Valve & Transistor Data Book 9th Edition; p. & p. 23p.
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. 75p

Send for lists of publications
N.B. Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

ALL PRICES INCLUDE 10% VAT
MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 11p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD
CO. REG. No. 820919

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF
TELEPHONE: SOUTHEND (0702) 46344

Moreover, the capacity of the pcm system allows the transmission of more than one programme in stereo. Already a number of the main FM transmitters are radiating in stereo on several programmes and plans are in hand to extend the coverage with the least delay.

IMPORTANCE OF RECEIVING AERIAL


From the actual receiving point of view the conditions are unchanged. That is, there is no change in the transmission system. It is still FM from the transmitters and the same tuners and FM receivers will work just the same as before the introduction of pcm.

However, since stereo will be available to an increasing number of listeners the receiving aerial will assume a greater importance than for mono-only reception. The reason for this is that for a given mono signal/noise ratio threshold, the aerial input required for a similar ratio on stereo can be up to ten times that required for mono. Thus, while a tuner might require, say $50\mu\text{V}$ for a 50dB mono signal/noise, up to $500\mu\text{V}$ could be required for the same ratio on a stereo signal.

There are some hi-fi tuners significantly more sensitive than implied by this example, of course, where for an acceptable ratio about $10\mu\text{V}$ (or less) might be required on mono and $100\mu\text{V}$ (or less) on stereo, but the fact remains that whatever the tuner or receiver a greater aerial signal at the threshold signal/noise ratio is required for stereo than for mono. If a receiver or tuner is receiving just about enough aerial signal for an acceptable mono signal/noise ratio, the same station switching to stereo would almost certainly give rise to an unacceptable signal/noise ratio (obtrusive background hiss) on the same installation working in the stereo mode.

When a station goes stereo and the receiver is not equipped with a stereo decoder, the reproduction, of course, will be in mono. This results from the compatible design of the stereo system. That is, the mono information is carried by it in the usual manner, with the stereo information on a subcarrier, so a receiver devoid of a decoder responds merely to

the mono information and takes no account at all of the stereo information. Since the stereo information is contained in sidebands centred on a 38kHz subcarrier frequency, the normal after-detector de-emphasis of a mono receiver or tuner eliminates or filters out this information. A 19kHz pilot tone signal is also transmitted on stereo for synchronising the stereo decoder in the receiver or tuner, and this too is rolled-off by the de-emphasis.

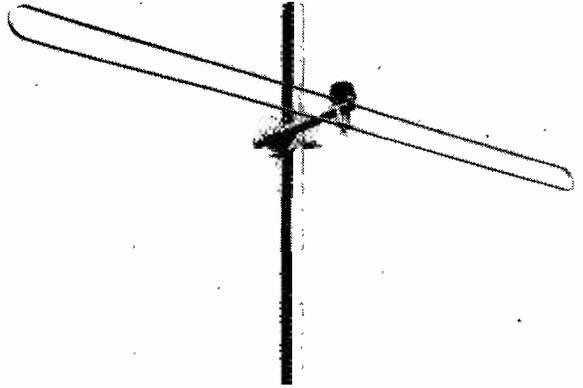

The J-Beam Ltd. SBM1 folded dipole is just about the simplest aerial possible, suitable only for local service areas

Thus a listener using a mono-only receiver or tuner is not aware that the station is transmitting a stereo signal. The signal/noise ratio is barely changed. There is a mild intrinsic impairment to the ratio under this condition owing to the pilot tone accommodating just under 10% of the total deviation of the system and leaving 90% (not 100%) deviation (i.e., modulation depth) for the mono components, but this is rarely detected subjectively by the average mono installation in receipt of a reasonable aerial signal.

SENSITIVITY AND S/N RATIO

A signal/noise ratio much below about 40dB is generally unacceptable by critical listeners. Indeed,

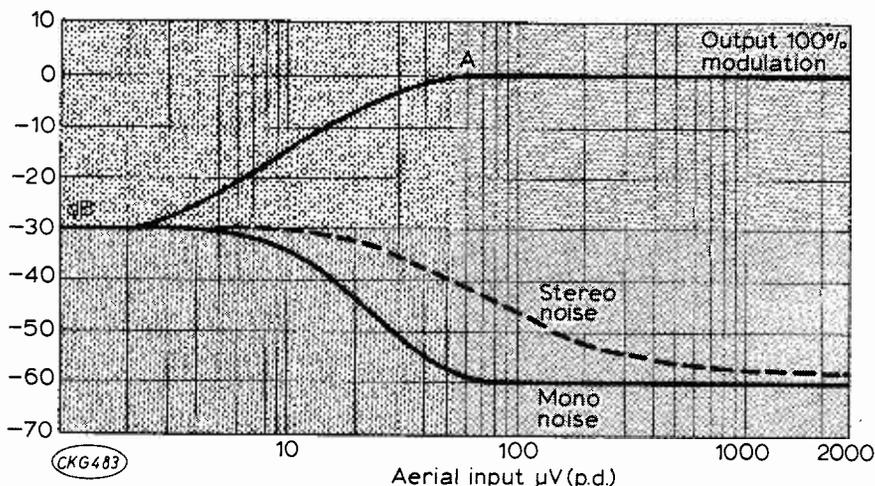


Fig. 1. Curves expressing signal/noise ratio and limiting performance.

for true hi-fi results the ratio should approach 60dB referred to 100% modulation (i.e., $\pm 75\text{kHz}$ deviation on the British system). The top curve in Fig. 1 shows how the audio output gradually increases with rise in aerial signal strength from the very low level. At point A on the curve, corresponding to an aerial input about $60\mu\text{V}$, the output stabilises due to the FM limiting action of the receiver or tuner. This represents the 'limited' output and is referred to 0dB.

The noise on this signal is very low, but at aerial inputs below the limiting level shown the noise constitutes a greater proportion of total output. At zero signal input there is no real signal, of course, just noise, and in the example this corresponds to an output 30dB below the limited output.

The full-line mono noise curve shows how the noise contribution falls as the aerial signal is increased. At $30\mu\text{V}$ input, for example, the noise curve is at -50dB. Now, the signal/noise ratio is the dB difference between the noise and output curves, the ratio thus increasing as the signal strength increases. At $10\mu\text{V}$ input the ratio is just under 20dB, while at $20\mu\text{V}$ it is up to about 38dB. At $100\mu\text{V}$ it has maximised to about 60dB (the ultimate signal/noise ratio of the receiver or tuner), the noise then being so small as to be totally inaudible. This is on mono, but what about stereo?

S/N RATIO AND STEREO

The broken-line stereo noise curve shows this action. At $10\mu\text{V}$ input the ratio is a mere 15dB, and even at $20\mu\text{V}$ it is not much better than about 24dB. Thus noise on stereo at the input would be very troublesome though possibly acceptable on mono. At $60\mu\text{V}$ input there is almost a 20dB difference between the mono and the stereo signal/noise ratios, and on stereo the ultimate signal/noise ratio rarely reaches the mono ultimate. Nevertheless, the ratio of almost 60dB for stereo at highish aerial inputs is perfectly acceptable.

It must be stressed that these curves are not typical of any particular receiver or tuner. The overall design greatly influences the nature of the curves, and the greater the sensitivity of the receiver or tuner the lower the aerial signal required for full limiting and for an acceptable signal/noise ratio, and this applies both to mono and stereo, but with stereo always requiring more signal for a given signal/noise ratio, particularly at the low signal input end of the scale.


RECEIVER REQUIREMENTS

Clearly, then, the type of aerial required for the best stereo reception depends not only on the strength of the prevailing signal field but also on the sensitivity of the receiver or tuner. Some hi-fi tuners are capable of providing a mono signal/noise ratio of 40dB or more from an aerial input as low as 2 or $3\mu\text{V}$ and a similar stereo ratio from 20 or $30\mu\text{V}$, with the ultimate ratio occurring at 10 or $100\mu\text{V}$ respectively. On the other hand, relatively inexpensive receivers might require up to 1mV signal (or more) for an acceptable stereo signal/noise ratio.

It is a fair indication that the aerial signal strength is insufficient should a tuner or receiver exhibit undue background noise on stereo, while producing an

acceptable signal/noise ratio on mono. It is sometimes necessary to have a decoder fitted into a tuner or receiver to take advantage of the stereo signals when the 'local' FM transmitter goes over to stereo. On the other hand, the tuner or receiver may be 'stereo-ready', meaning that the stereo decoder is already incorporated. Most hi-fi tuners are of this kind.

Working with a stereo signal, a stereo tuner delivers signals in the left and right channels for application to the left and right channels of the amplifier, these two channels then feeding the stereo loudspeaker pair. A fully-fledged stereo receiver contains not only the stereo decoder but also the two amplifier channels, two loudspeakers then being required for stereo reproduction in the normal way.

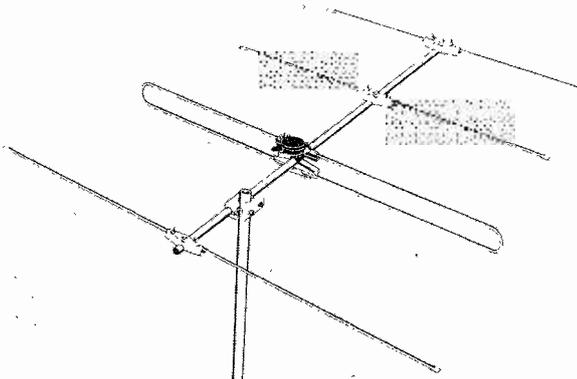

The Antiference FM244 has the usual folded dipole, with two directors and one reflector element.

To glean some idea as to whether the aerial which is feeding a mono receiver is delivering sufficient signal for reasonably noise-free stereo, a 20dB attenuator can be connected in series with the aerial (coaxial plug-in types of various attenuation values can be obtained from dealers). If the mono reception is then still noise-free, it can be basically assumed that the signal will be strong enough to operate a stereo receiver or the same receiver after a decoder has been installed.

SIGNAL FIELD

The strength of the signal field locally from the nearest stereo-encoded station will depend on how far away the site is from the station and on the site elevation, while the amount of signal induced into the receiving aerial will depend on its height above ground, on the degree of local screening (by hills, large buildings, etc.), on the gain of the aerial (how many elements it possesses), on the attenuation of the download or feeder and on how well the aerial is orientated with respect to the station (some high-gain aerials are very directional such that almost half the signal is lost by a mere 30deg. misbeaming).

NEXT MONTH, IN PART 2, GORDON KING DISCUSSES THE NATURE OF THE TRANSMISSION PATH AND GIVES PRACTICAL INFORMATION ON AERIAL DESIGN.

HOTLINES

ON RECENT DEVELOPMENTS

"PAPER" I.C. TRANSISTORS

MANY people have watched and wondered where integrated circuit technology will go next. The amount of semiconductor terminology in current usage gives some idea of the path along which i.c. development has rushed headlong.

In America, development has been quietly proceeding over the past few years with some interesting thin film technology. Yes, it had to come—the paper transistor! Devices have been successfully produced on a variety of flexible materials which include metal foils plus numerous plastic films and paper.

These days one thinks of an i.c. as being very small with the latest ones either smaller still, or the same size but with more packed in them. It is surprising, therefore, to hear of a six-inch square i.c. with some 14,000 transistors on it. Such is the state-of-the-art with these flexible circuits. It is envisaged that when this art is perfected further, some half a million transistors will be put onto the same size i.c.

THIN FILM

The interesting thing about these flexible i.c.'s is that they are not hybrids—the only production method used is that of thin film.

Thin film transistors were announced by one researcher back in 1968. The devices were f.e.t. types with insulated gates and were successfully reproduced on paper. Both p-channel and n-channel devices were made.

At this point, gate voltages around 200V were possible and power dissipation was about 0.5W. Two years later this power dissipation capability had been doubled. These flexible beasts are not fragile, either. The active devices will function happily when bent round a radius of some 0.06in. Production-wise it would appear that the flexible substrate—film, paper or whatever, is simply wound onto a spool. From here, it is fed into a deposition "processor" and is subsequently wound onto a take-up spool much the same way in which a cine film travels through a projector.

Please note: these devices are not on the market and no further information is available to date.

ACTIVE FILTERS

Although the above application may indicate a rise in fame for thin film, there are other areas where this technology could have very stiff competition. Hybrid thin film devices may find this from some miniature active bandpass filters which have just appeared. These have pre-tuned centre frequencies from 3,500Hz down to 200Hz. Gains available range from 0 to 40dB with Q factors from 2 to 50. Twist in the tail of this story is the size. These active filters are only 0.25 x 0.25 x 0.25 inch.

S.H.F. — AND HOW!

Still with components but looking at high frequencies, I note that the quest for higher and higher frequency requirements is still very much an active field in every sense of the word. The r.f. enthusiasts were elated when news of the first 1GHz devices appeared. Goodness knows what realms of ecstasy my news will bring but I have just learnt of oscillators using Impatt diodes which give some 120mW at—wait for it—140GHz. Outputs at 200GHz are expected later this year with 100mW at 170GHz already being mentioned.

8192-BITS

Charge-coupled devices are fascinating creatures. Space does not permit a discussion on how they work. However, as a point of information, one company is currently developing an 8,192-bit shift register which should cause a few hiccups in the computer hardware circles. The result could be a system which is 20–30 times faster than comparable rotating discs.

TIME IS PRECIOUS

For those who like to be in contact with electronics all the time, electronic watches are catching on fast. My own wrist watch has an accuracy (written guarantee) of an error not greater than 60 seconds in any one calendar year which, I thought, was pretty fantastic. Unbelievers might care to work out the number of seconds in 365 days and then work out the percentage error*

Omega has gone one better. This Company's latest wrist time piece

has an accuracy of one second a month or 12 seconds/year. Readers will be pleased to know that these electronic watches will be available next year; and not so pleased to know that prices start from £425. Truly, time is precious.

SPIN OFFS

Very often there is a useful spin off of products for the Amateur. Some professional industrial idea has, say, consumer applications. Tape recorders may benefit further from the design and development of tape heads for data applications. An example is the latest tape heads on the data market which are 0.4mil flying lead types. In practical terms this means a recording density on the record discs of 1,500 tracks per inch. A 600 tracks/inch density can allow storage of something like 60 million bits of information. If this ever spreads to tape recorders, then the cassette tape you get with your new recorder will last you for life. How you would locate a particular item on such a tape is quite another matter.

RED CURRENTS?

Radio waves are attenuated by a variety of things. Often the terrain over which they pass is an important factor although the frequency involved is a major consideration. Workers in Russia have been looking into the effects of forests on medium and long wave radio transmissions. The findings are as follows. A tree with a circulating sap was found to be a good current conductor (no, not a Red current bush). Thus an electric current is induced in the tree when it "interacts" with radio waves. The induced current creates an electrical field, albeit a small one, which is radiated into space and thus dissipated. Doubtless we will now have some ingenious Amateurs using centre-fed sycamores or root-loaded rowans.

* Sixty parts in thirty one million, five hundred and thirty six thousand.



IN NEXT MONTH'S

PRACTICAL WIRELESS

OCTOBER ISSUE No. 800

ON SALE
SEPTEMBER 7th

PW Q4 PROJECT

QUADRAPHONIC SOUND SYSTEM



NOW YOU CAN HAVE QUADRAPHONIC SOUND AT LOW COST.

FOLLOW PW PROJECT Q4 FOR THE FIRST FULLY COMPREHENSIVE DO-IT-YOURSELF QUAD DECODING SOUND SYSTEM TO BE PUBLISHED WITH FULL CONSTRUCTIONAL DETAILS.

Part 1 in the October issue gets you started with "GOING QUADRAPHONIC", a broad outline of the various quad systems that are incorporated in the project. It gives you an understanding of the different principles involved so that you can choose the systems you need. Parts 2 and 3 present the exclusive PW practical design in detail. You can make up one, two or more of the systems as you like but the complete Q4 quad unit shown here is designed to give you decoding for all of them: CD-4 Victor-RCA discrete system. RM Regular matrix surround sound. QS Sansui system. SQ CBS system.

You can use this system with your own choice of amplifier. It will convert two-channel stereo to any four-channel quad system, so you can use it to play any quad or stereo recordings, as well as being ready for any of the quad broadcasting systems that may be adopted.

PLUS EXPERIMENTAL WORKSHOP

First of a new series offering a new approach to learning how circuits operate by making up simple working projects and experimenting with the components. Soldering is not necessary so components can be used repeatedly. This series is recommended for group and class instruction support in schools, colleges and training centres.

**FREE
INSIDE**

PRACTICAL WIRELESS BUILDERS SYSTEM 1973

Don't miss out on this new exclusive scheme for readers of Practical Wireless. PW Databards are designed attractively and clearly to give you at-a-glance technical information that you will be constantly referring to. They are printed in full colour so that you can identify each card easily. Collect the whole series for your workshop. PW Databards will fit into the average jacket pocket, stand on the work bench, hang on the wall, or can be used as a place mat, or even a bookmark. The series will be presented in pairs in the October, November and December issues as follows:—

October issue 1. Standard Resistor values and colour code.
2. Common Capacitor values and colour code.

November issue 3. DIN Plugs and Sockets. 4. Using decibels.
December issue 5. Combined resistance or capacitance calculator.


6. D.C. Circuits and electrical relationships.
Don't miss the first pair in next month's issue. No other radio or electronics magazine has given such a comparable free service to its readers.

**DON'T MISS
ANY ISSUE OF
PRACTICAL WIRELESS**

2

Simple Two I.C. 1

POP STAR★

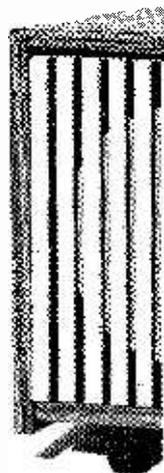

THIS is a neat portable table receiver covering medium waves and 200kHz on long waves and capable of a substantial loudspeaker output. It has an attractive but quite easily made case. Operation is from a 9V battery.

Fig. 1 is the circuit, using the ZN414 10 transistor network in the r.f. section, and SL403D as audio amplifier. The latter incorporates 16 transistors and 4 diodes. The following details will help clarify working of various parts of the receiver.

Tuning

A ready made Litz wound ferrite rod is used, and this will be found to have greater efficiency than a home made winding of ordinary enamel or cotton covered wire. For maximum efficiency the tuning capacitor VC1 is air-dielectric. The small Jackson 208/176pF type of capacitor, extensively used for aerial and oscillator tuning in superhets, is easily obtainable, and is fitted. As L1 is designed for a 208 pF capacitor, this provides correct band coverage, with the added advantage that an attractive ready-calibrated transparent dial is available for tuning.

C1 is fitted to limit h.f. coverage to about 1600kHz, the MW band being approximately 1600-550kHz. For reception of the BBC on 200kHz, S1 is closed. This places TC1 and C2 across L1, and the full swing of VC1 then covers about 195-250kHz. For full LW coverage it would be necessary to have a LW winding on the ferrite rod instead.

RF Section

The ZN414 radio receiver silicon network requires a reasonably stable supply in the 1.1 to 1.8V range, and this is obtained by the potential divider R3 and R4. It was found that best results were obtained with a supply of about 1.4V here.

The best possible supply voltage may depend somewhat on the exact layout of wiring, and in the receiver shown two Veropins were inserted so that R4 could easily be changed. This is scarcely necessary, but the importance of the voltage present here should not be overlooked. It must not exceed 1.8V (this can be checked by clipping a high resistance voltmeter across R3). If it is rather high (in the

F. G. RAYER

1.6 to 1.7V range) instability is likely, and is shown by whistles accompanying the tuning-in of weak signals, though the whistles may disappear with strong transmissions. On the other hand, if the supply is rather low (1.1 to 1.2V or so) receiver sensitivity falls off considerably.

It is thus recommended that the values given are fitted, and R4 only need be change if instability, or very low sensitivity, is apparent when the receiver

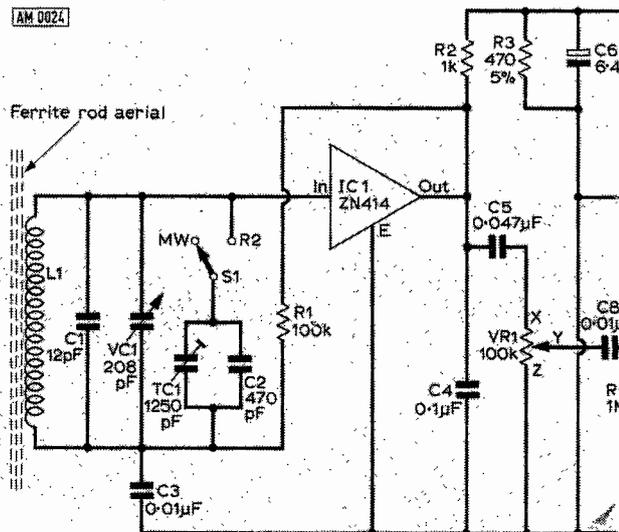


Fig. 1: Circuit of the

1.6 to 1.7V range) instability is likely, and is shown by whistles accompanying the tuning-in of weak signals, though the whistles may disappear with strong transmissions. On the other hand, if the supply is rather low (1.1 to 1.2V or so) receiver sensitivity falls off considerably.

It is thus recommended that the values given are fitted, and R4 only need be change if instability, or very low sensitivity, is apparent when the receiver

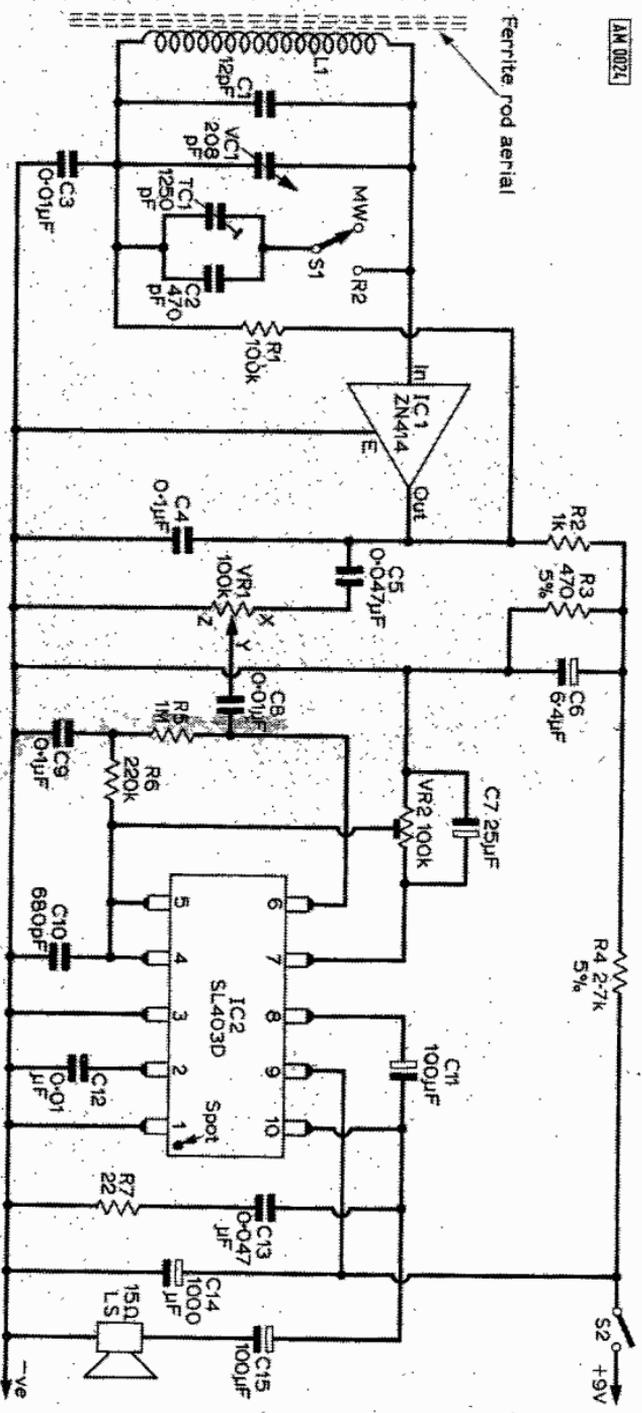


Fig. 1: Circuit of the PW POP STAR receiver.


is tested.

R2 is of somewhat higher value than recommended by the manufacturers, but was found best in this circuit. If experiments are afterwards made to secure the best possible results, the effect of reducing R2 to 680, 560 or 470 ohms can be tried.

Audio output is taken from IC2 to the volume control, VR1. This control incorporates the on-off switch S2 in the usual way.

AM 0024


Two Band Radio

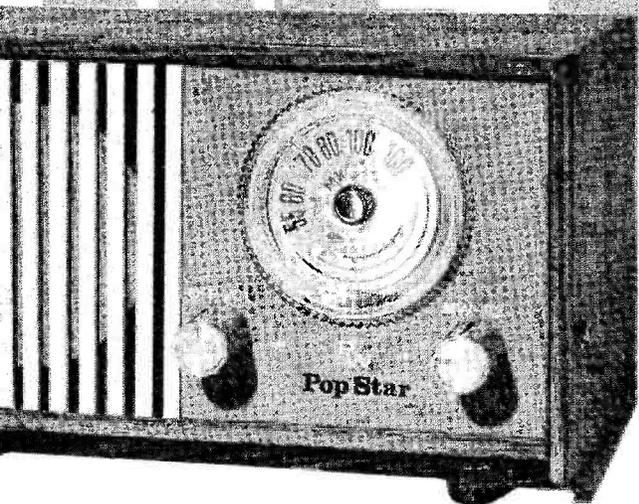

is tested.

R2 is of somewhat higher value than recommended by the manufacturers, but was found best in this circuit. If experiments are afterwards made to secure the best possible results, the effect of reducing R2 to 680, 560 or 470 ohms can be tried.

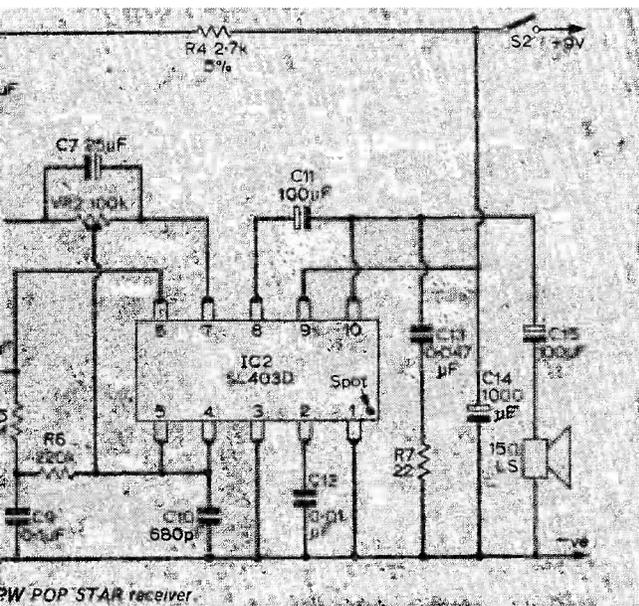Audio output is taken from C5 to the volume control, VR1. This control incorporates the on-off switch S2 in the usual way,



POP STAR receiver

★ components list

Resistors

R1	100kΩ	} All 1/4w 5%
R2	1kΩ	
R3	470Ω	
R4	2.7kΩ	
R5	1MΩ	
R6	220kΩ	
R7	22Ω	
VR1	100kΩ log pot. with switch	
VR2	Miniature 100kΩ pre-set pot	

Capacitors

C1	12pF	C9	0.1μF
C2	470pF	C10	680pF
C3	0.01μF	C11	100μF, 10V
C4	0.1μF	C12	0.01μF
C5	0.047μF	C13	0.047μF
C6	6.4μF, 6.4V	C14	1000μF, 10V
C7	25μF, 10V	C15	100μF, 10V
C8	0.01μF		

Miscellaneous

- VC1 Jackson 00, 208/176pF
- TC1 1250pF compression type
- M1 Denco FR5, medium wave ferrite rod
- Trans aere medium wave 2 1/2 in. diaf (Home Radio)
- IC1 ZN414
- IC2 SL403D
- 15Ω 3 1/2 in. square speaker
- Veroboard, Veropins
- 1-pole 2-way rotary switch
- Two knobs
- Case:
 - 6mm plywood: Top 8 x 4 1/2 in.
 - Bottom 8 x 4 1/2 in.
 - 2 off 4 1/2 x 4 1/2 in.
 - Back 8 x 3 1/2 in.
- Hardboard 8 x 4 in. 1/8 in. thick
- Panel: Universal chassis flanged member 8 x 4 in.

Audio Section

To assist wiring, pins for the SL403D are shown in their actual positions in Fig. 1. Pin 6 is the pre-amplifier input, from the volume control VR1. This employs cascaded emitter followers and a common emitter stage. Output is at pin 5, which is directly connected to the main amplifier input at tag 4.

VR2 is a miniature pre-set potentiometer, provided

to trim the bias operating point, and it requires no further adjustment, when once set.

The main amplifier has 13 transistors, with cascaded emitter followers between stages. Although up to 18V may be applied to the SL403D, the circuit here is intended for a 9V battery. Output is approximately just under 1 watt with a 9V supply, using a 7.5 ohm speaker. The speaker impedance actually selected is 15 ohms, this allowing approximately 400mW with the 9V supply, with additional current economy. This power output is considered easily adequate for a receiver of this kind.

C10 is a by-pass for the main amplifier input, and R7/C13 are for h.f. compensation, and should not be omitted.

Components

R3 and R4 are shown as 5 per cent, for the reason explained. This tolerance is so generally available that it can be used throughout. There is actually no reason why 10 per cent resistors should not be fitted, provided the voltage across R3 is checked as mentioned.

For the 9V supply, all capacitors could be of 10V rating. In numerous circuit positions a lower rating could be fitted. However, there seems little point selecting the lowest possible voltage ratings, as the usual small capacitors of up to 150V rating are of course perfectly suitable.

Circuit Board

This is 0.15in. matrix plain Veroboard approximately 5 x 1 $\frac{7}{8}$ in., see Fig. 2. Brackets are bolted at holes D-D to support the ferrite rod. Holes B-B are to secure the finished board to the bottom of the receiver.

The a.f. amplifier is bolted with the spot (near pin 1) located as shown. Connecting wires then pass down through convenient holes in the board.

Wiring underneath is shown in Fig. 3. Insert a few components at a time as in Fig. 2, turn the board over, and solder as in Fig. 3, cutting the wire ends of components down as required. Insulated sleeving should be put on any leads which may touch other connections.

Veropins are inserted for external connections to L1, the loudspeaker, and battery circuits. The three thin flexible leads X, Y and Z are for connection to VR1.

Leads from the ZN414 are shown in Fig. 3. Position these so that lead E comes between the other wires, when they are in line as in Fig. 2. Stray feedback from output to input circuits may easily cause instability, so the lead is taken directly to C4, which in turn goes directly to the earth or negative line. The usual care to avoid lengthy heating is taken when soldering the two semiconductor devices.

Ferrite Aerial

The usual superhet type aerial has a small coupling winding, provided for base coupling to the mixer. This is not required here and is removed.


Two pieces of $\frac{1}{16}$ in. thick paxolin or similar material are cut, about $\frac{1}{2}$ in. wide and 2in. long. A "V" is cut in the top of each, a small hole being drilled just below this.

Small brackets are bolted to the strips, and secured in the holes D-D, Fig. 2. The rod, with winding, is then secured with string around it and through the holes in the paxolin strips. The ends of L1 are soldered to the pins provided on the board.

Front Panel

This is a 8 x 4in. flanged universal chassis side. An aperture is cut to match the speaker cone—this is most easily done with an adjustable tank or washer cutter. Also position holes for VR1 and S1, as in Fig. 4, and lin. from the bottom edge.

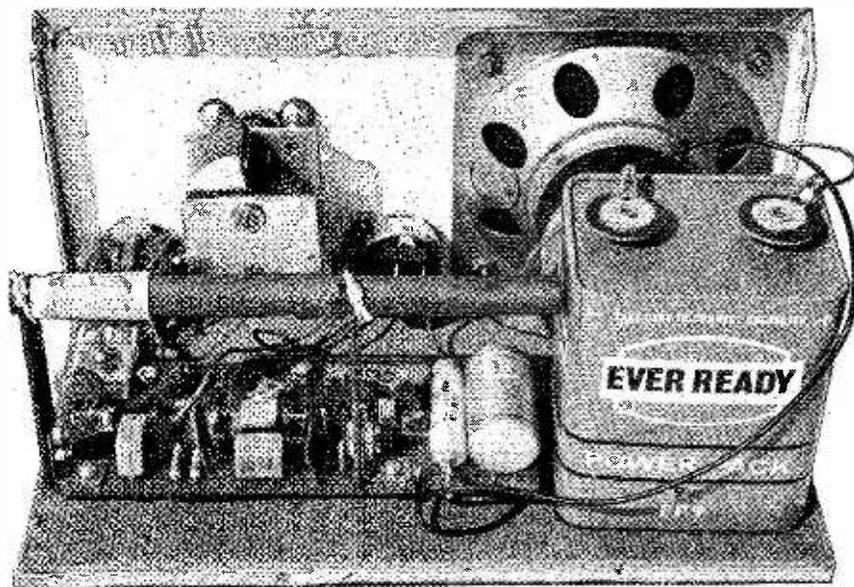VC1 has to be set back as in Fig. 4, to allow the



Photograph showing the inside of the completed receiver.

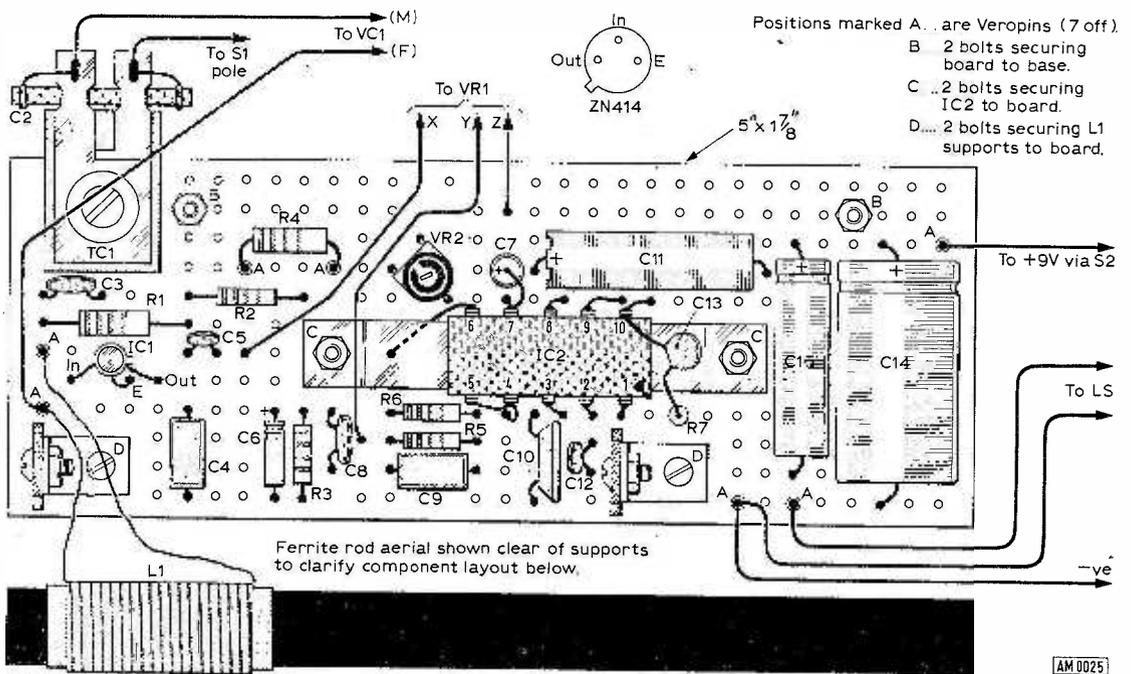


Fig. 2: Component layout on the Veroboard chassis.

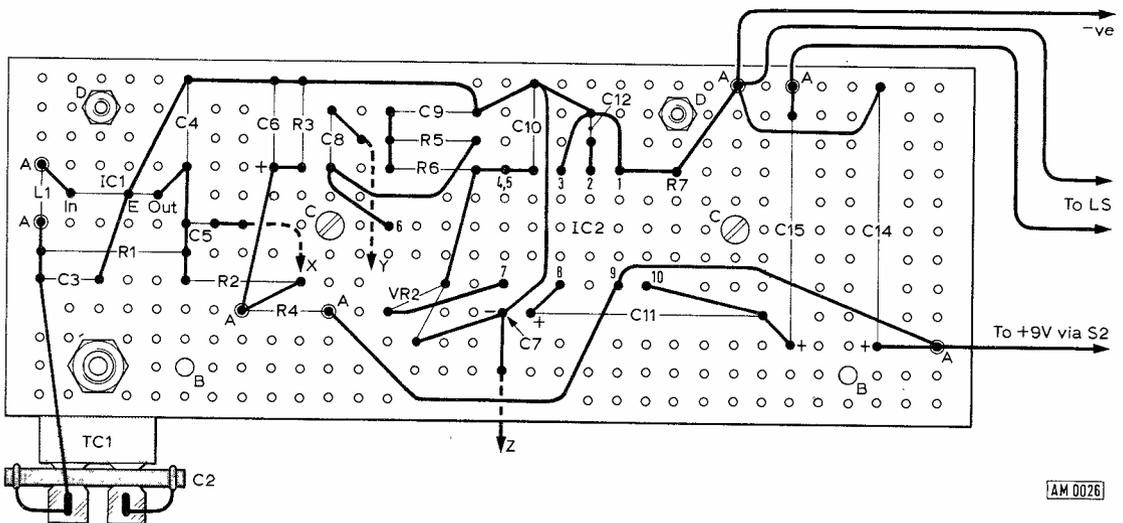


Fig. 3: Underside wiring. Insulated sleeving should be used where necessary.

transparent dial to be fitted, and the frame of VC1 must also be insulated from the aluminium panel. The spindle is $1\frac{1}{2}$ in. from the top.

Three $\frac{3}{4}$ in. 4BA bolts were used to secure the capacitor. A piece of paper with a hole for the spindle is pushed on to the front of the capacitor, so that the location of the fixing holes can be marked. This paper is then placed on the front and drilling positions are marked with a sharp tool. The central hole is $\frac{1}{2}$ in. diameter and the three fixing holes are $\frac{1}{4}$ in.

An insulated bush and washer is placed on each bolt, followed by a plain washer, and two nuts.

The bolts pass into the threaded holes of the capacitor, and are adjusted so that it is square with the panel. The nuts are then locked against the frame, and front washers.

An alternative is to drill two pieces of thin paxolin, about $1\frac{1}{2}$ x lin., to match the capacitor fixing holes. One piece can then be used each side the metal panel. Contact between the bolts and metal can be avoided by carefully locating the bolts before tightening the nuts, or by placing thin insulating washers on them, or using extremely short pieces of insulated sleeving.

The dial is a tight push fit on the spindle, and has a metal clip. A check should be made that this can be fitted. If not, the end of the capacitor spindle will have to be filed slightly, to produce a taper to get the push fit started. If necessary, the centre hole of the dial can be enlarged slightly with a $\frac{1}{4}$ in. drill, using very light pressure indeed.

If an ordinary knob or dial is used instead, the capacitor should be insulated from the panel, but with its spindle projecting.

A piece of $\frac{1}{8}$ in. hardboard 8 x 4in. is fixed to the inside of the lower flange with 6BA bolts. The circuit board can then be fixed as in Fig. 4, using screws or bolts with extra nuts or spacers to give a little clearance to underside wiring.

Connections are then completed as in Fig. 4. Note that the metal panel is earthed to the negative line by the lead Z, from VR1. This was found necessary.

Adjustments

These are very few, as there is no alignment in the manner required with a superhet.

Band coverage is adjusted by the position of the winding on the ferrite rod. This can be placed nearly at one end. Or the dial can be set at 550kHz, with VC1 closed, and the winding moved along the rod to tune to this frequency.

VC1 is then set half open, S1 is closed, and TC1 is rotated to tune in the BBC on 200kHz. When this is done, VC1 merely acts as a fine tuner for this frequency. The position of L1 on the rod has considerable effect on the setting of TC1. Should TC1 be fully open without 200kHz being reached, L1 must

be moved a little towards the end of the rod. On the other hand, if TC1 is fully compressed without 200kHz being reached, L1 must be pushed a little further on the rod. As there is considerable adjustment, and L1 is of suitable inductance, no difficulty should arise here.

VR2 has to be rotated with a small screwdriver, for best audio results. If VR2 is too far one way, reproduction is very distorted indeed. Moving VR2 too far the other way will cause a considerable increase in battery current, as shown by a meter in one battery lead. With normal adjustment, which is not at all critical, current should be about 20mA with low volume, peaking up to 40mA or more with considerable volume. If wrong adjustment of VR2 causes an extremely heavy current, this may persist. If so, momentarily break one battery connection (or switch off). This effect arises from the automatic s.c.r. protection integral in the module, and does not cause damage.

Finish

A piece of self-adhesive material, as used for shelves etc., and about $4\frac{1}{2} \times 5$ in., is placed on the control side of the front. It is better to cut this to clear the bushes before stripping the backing paper.

A piece of silk material about 4 x 5in. is stretched over the speaker, which is secured with countersunk bolts. This material is held at the edges only with Bostik 1 or similar adhesive. A vertical strip about $\frac{3}{8}$ in. wide and 4in. long covers the joint. This can be wood, metal, plastic, or as sold for shelf edgings etc.


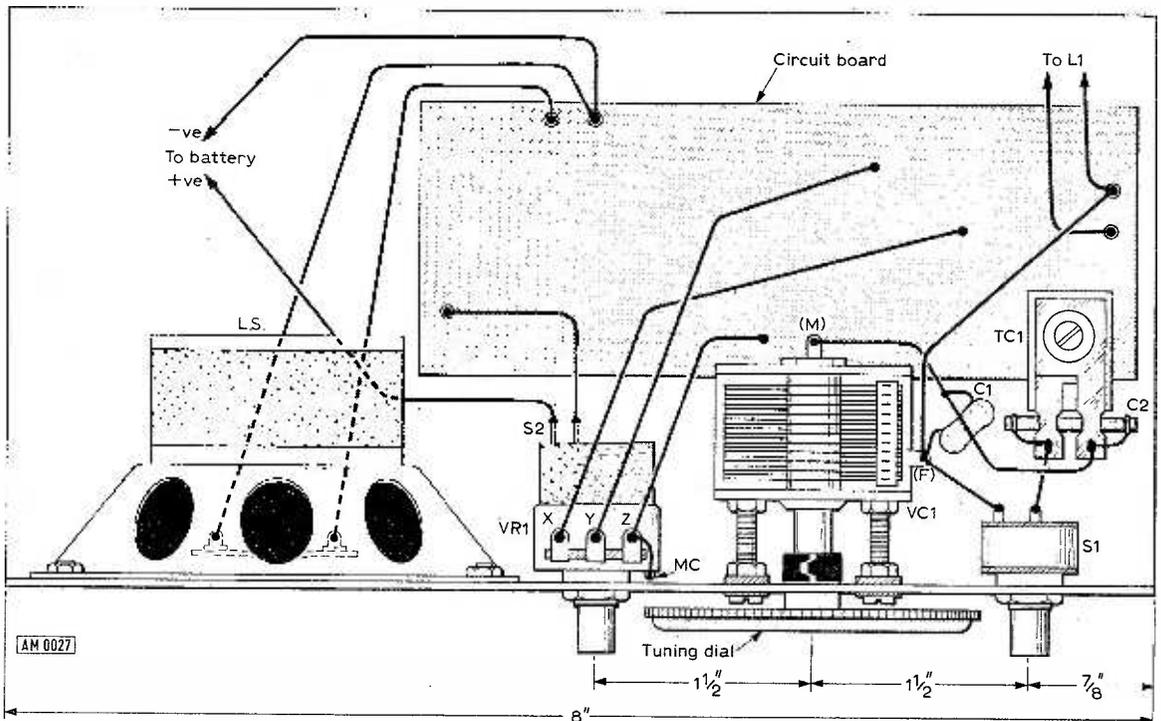


Fig. 4: Above chassis wiring and layout of panel components.

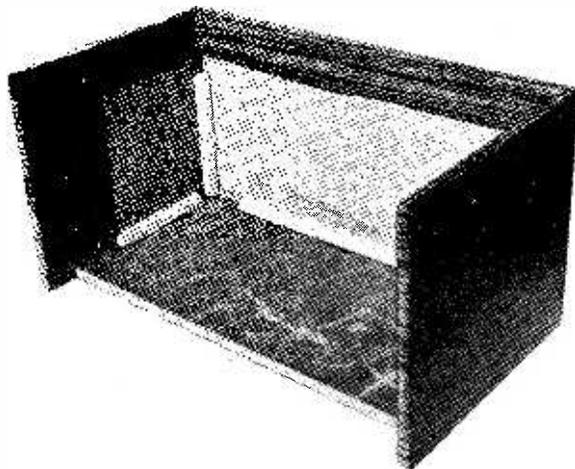

Photograph of the PW POP STAR cabinet. In this photograph the cabinet back is shown face downwards.

In some parts of the country there may be no point in providing 200kHz coverage. If so, TCl, C2 and S1 may be omitted.

Case Construction

This is made just to clear the receiver (see photograph) so really needs to be very slightly outside on the 8in. dimension to avoid a tight fit. The pieces were secured together by spreading adhesive on the meeting surfaces, and securing them with a few panel pins. Some $\frac{1}{4} \times \frac{1}{4}$ in. strips were also cemented inside to strengthen the joints. When the adhesive is hard, the outside is glasspapered. Dust is blown or wiped away (this is essential) and the outside is covered with a wood-grained self-adhesive material.

The case fits over the receiver, and is held by two self-tapping screws, with washers under their heads, which run into the end flanges of the metal front.

At the bottom, strips about 1in. wide and 8in. long were fixed at the front and back, the front strip being covered with the wood-grained material first. Rubber feet at the front raise this a little.

An alternative is to make the case complete with bottom and back the full depth, so that the whole receiver can be slid in from the front.



INFORMATION WANTED

- ...good cond. DX Data Chart (P.W. March 72 issue).—R. A. Haigh, 6 Park Road, Allington, Nr. Grantham, Lincs.
- ...buy or borrow March-May 1970 Sound Effects Synthesiser by Judd or any information on building synth'esisers.—R. J. Lewis, Wynn's Hotel, Church Street, Oswestry Shropshire.
- ...circuit diagram or any information on "Murphy Lowband Mobile Unit". Loan or purchase.—R. McCormack, 44 Mountinview Park, Belfast 14.
- ...does any reader have any modification details for modifying the receiver drawer type 62E AP 67907.—R. S. Jarydon, 5 Princes Park Close, Hays, Middlesex.
- ...Jason AG 10 audio signal generator. Borrow or purchase constructional plans. Expenses met.—G. E. Davies, 41 Dormington Drive, Tupsley, Hereford.
- ...coil data & circuit of "Simplex" T.V. receiver.—J. Búbez, 16 Penn Crescent, Haywards Heath, Sussex, RH16 3HN.
- ...a diagram of the R1155A of P. W. July, 1946.—J. Cerny, Turynskeho C80, Libochovice Nohri, Czechoslovakia.
- ...any information on making a Cossor Oscilloscope type Mod. Ser. 1039, 10119, Mk.2 work.—Dr. M. T. Cooper, 608 Shelburne, Nova Scotia, Canada.
- ...power supply unit 8893 for Marconi Receiver CR300.—B. Rodriguez Oakleigh, Forest Road, Wokingham, Berks, Tele.—Bracknell 29680.
- ...a circuit diagram of a Truivox Twin Selector Tone Amplifier, No. TC1566.—J. Challenge, 84 Stopford Road, Plaistow, London, E13 0LZ.
- ...technical details of the actual coil for the Mini Four, appearing in the March and April issues of P.W. for 1952. I have all the components except the coil type CT9 which was originally made by Stern Radio.—J. Cull, Sunnyside, 10 Ashdene Road, Southampton, Hants.
- ...an e.h.t. transformer rewind please? It is for an E.M.I. type WM2 oscilloscope.—D. Martin, The Bungalow, Marton, Near Rugby, Warwick.
- ...operating instructions for Model RK3 tape recorder made by Robuk Electrical Industries Limited.—H. Edmonds, 4 Mount Pleasant, Ayr Lane, St. Ives, Cornwall.
- ...service sheets/handbooks for: Gramup Blue Peter superhet 40/100c/s 5V Pilot rack combined with Garrard RC110 16W record player and Westminster radiogram (ex-Belcher Electronics Services Ltd.) type WBST obtained from Curry's.—H. W. Clarke, 65 Beccles Road, Oulton Broad, Lowestoft, Suffolk.
- ...the address of a company which will mend loudspeaker cones.—R. V. Jenkin, Berry Cottage, Berry Lane, Bodmin, Cornwall.
- ...circuit for a 6-transistor pocket radio on a printed circuit board by Osmor. It was published in P.W. about 10 years ago and the case measures about 6 x 4in.—R. Harris, 8 Marine Parade, Penarth, Glamorgan.
- ...a copy of the DX Data Chart supplied the March Issue of P.W.—K. Law, 17 Quick-side Hill, Saffron Walden, Essex.
- ...a service sheet or circuit diagram for my Philips EL3549 tape recorder.—S. A. Fryatt, 20 Talbot Road, Accrington, Lincs.
- ...borrow instruction handbook for Cossor Oscilloscope No. 1039M.—J. Noreley, 16 Surrey Street, Latchford, Warrington, Lincs. WA4 1HE.

- ...loan copy or purchase of Practical Wireless April 1960 to copy modifications to the W.S.No. 19, or any other issues with extensive modification to this set (e.g. March 1966).—D. Collings c/o Glossop School, Glossop SK13, Derbyshire.
- ...circuit, valve equivs. & mods., etc. for ex-service crystal calibrator No. 10 with class "b" standard overhaul.—L. McGee, 6 Ripon Road, Newton Hall, Durham, Co. Durham.
- ...any gen on Elpico AC/54 valve amplifier at least 12 years old. Loan or buy if price reasonable.—C. White 38 Kettle Road, Sutton Coldfield, Warks.
- ...circuit diagram and information on surplus oscilloscope 10SB/105, 'Buy or Borrow'.—E. P. Tozer, 21 Pen-yr-heol Dr., Sketty, Swansea, SA2 9J9.
- ...circuit diagram and instructions for No. "19" set aerial variometer. Wish to loan.—P. Herber, 23 Church Road, Horley, Surrey.
- ...a service sheet for Practical Wireless Autocrat Set.—T. C. Vaughan, 13 Old Croft Road, Walton, Stafford.

EQUIPMENT REQUIRED


- ...wanted for new S.W.L., a Codar CR70A in good working order. Will pay around £10.—L. Paget, 50 Western Road, Kilmarnock, Ayrshire, KA3 1LB.
- ...correspond and exchange or buy any technical data with someone in U.K.—V. Jeevaratnam, 33 Main Street, Ettimolty, Ceylon.
- ...wanted October P.W. 1971.—P. Smith, 68 Gatseden Road, Fetcham, Leatherhead, Surrey.
- ...two Electroniques i.f. transformers type D.F./85 series 11 plus electroniques Q-Multiplier coil type QLZ, please state price.—S. J. Dickey, 17 Maley Avenue, West Norwood, S.E.27.
- ...XG8 Novice 95 requires Pye "Cambridge" or similar rig to cut teeth on. Will collect in North East and Yorkshire.—J. McGee, 6 Ripon Road, Newton Hall, Durham, Co. Durham.
- ...a case for an Ultra Road Ranger Transistor portable model 6116 serial 25167.—R. Williams, 204 Dysart Road, Grantham, Lincs.
- ...a cheap X79 valve.—S. Taylor, 39 Openshaw Road, Abbey Wood, London, SE2 0TD.
- ...a cossor 2XP valve. I have tried equivalents but they all have a lower stage gain.—D. R. Goodwin, 3 Hamble House, Gardens, Hamble, Hampshire.
- ...Lafayette HA 600A required operating instructions circuit diagram alignment information.—B. Thomas, 8 Whitehall Road, Barton le Clay, Bedford.
- ...plastic tuning scale (black) for Pye valve car radio, Type No. 145311.—M. Stanley 9 Ormiston Gardens, Belafats BT5 6JD.
- ...Rhythm type 3 speed morse record with books wanted. Reasonable price.—A. Forster, 14 Mandels Court, Norwich 12J.
- ...Coils wanted. Can anybody help me find two off, F243 formers, for transmitter coils. If you can sell me one (or two), please ring me at 01-598 5113.—G. L. Manning 63 The Drive, Edgware, Middlesex, HA8 8PS.
- ...a case for a Murphy type U698. I require the Osc. coil for L.W. & M.W.—A. S. Holmwood 8 Dock Street, Pembroke Dock, Pems.

ISSUES WANTED

- ...issues of P.W. Containing the Three Transistor Amplifier. Take Twenty Project or circuit.—W. L. Brunson, 28 Meadowfoot Road, Wallasey, Cheshire.
- ...issues of P.W. from Nov. 71—Mar 72 inclusive.—C. Wright, 78 Swallow Road, Ipswich, Suffolk, IP2 0T3.
- ...February 1963 issue of Practical Wireless.—T. T. Griffiths, 11 Berryfields Long Buckley, Nr. Rugby.
- ...January 1971 issue required giving details of the stereo tape recorder amplifier.—A. Harris, 204A High St., Brentford, Middlesex.
- ...P.W. May, June, 1972.—C. S. Hyatt, Beach House, Beechway, Guildford, Surrey.
- ...P.T. February 1969, which had a Servicing Television Receivers No. 155, Defiant 9A61 U Series (Part 1) in it.—H. McBeath, 57 Castle Hill Road, Bearsden, G61 4DZ

Copy from readers for inclusion in this reader service is published on a space available basis. Copy must be forwarded on a separate sheet of paper and in the style shown above, otherwise it cannot be accepted.

GOING BACK...

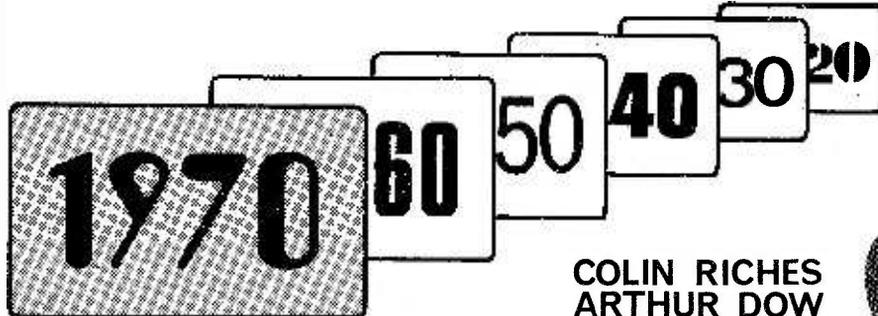

COLIN RICHES
ARTHUR DOW



WHILE visiting Sweden recently, Colin Riches called on one of our Going Back readers—Gunnar Carlström, SM6KT who has a fine collection of Vintage radio equipment.

He told how, when broadcasting started in Sweden about 1925 he was a boy of twelve and became very interested in the new wonder of radio. His financial situation did not permit him to buy much equipment but he managed to build one or two crystal sets then progress to valved receivers. A simple receiver of that time consisted of a one-valve detector. Headphones would have to be used as there was not enough power to drive a speaker.

In some more advanced receivers Gunnar built, one or two valves were used as r.f. amplifiers with tuned circuits. After the detector, one or two stages of audio amplification were used.

A very common type of receiver used in Sweden in the early '20s was equipped with one valve as detector and two others for amplification. This set-up gave good volume over a loudspeaker when tuned to the local station and British and European stations could be picked up but at vastly reduced volume.

Feedback was frequently used in order to increase the amplification and selectivity of Gunnar's re-

ceivers. When he tried using it in some of his home-built sets which had no r.f. amplifier stages it often brought irate neighbours rushing in complaining of oscillations on their receivers!

In those days, the high tension batteries were very expensive and if a 90V supply was required, Gunnar said that poor boys like he had to wire a lot of torch batteries in series so that they could get the required voltage. Accumulators were used for the 4V supply.

Around 1930, receivers working from the mains supply were made available in Sweden and Gunnar told how he remembered his first experiment to build a unit so that he could work his battery receivers from the mains. The great difficulty was to eliminate the hum because only low capacity paper condensers were available at the time.

Gunnar explained that the experimenting of those earlier years really inspired him and made radio his hobby for life. In 1938 he gained his licence to transmit with the callsign SM6KT.


He has found the rapid development of radio very fascinating and he has realised that so many of the old pieces of equipment are very well worth saving.

Some items in his collection of Vintage gear have been in his possession for 40 years but most of the others have been collected quite recently. Gunnar explained how he took great delight in completely restoring old sets to their former glory.

A particular interest of Gunnar's is his collection of old valves. He describes them as his "Aladdin Lamps", and says that it was really them that made radio possible but now their rôle in ordinary receivers is almost terminated, and he feels that this is a great shame. He has a collection of receiving valves which covers 50 years of valve development. They are all put together in chronological order and although Gunnar has only valves dating from the early 1920s at the moment, he hopes to obtain some earlier types. He is also very interested in pre-1920 receivers and speakers.

Incidentally, Gunnar has asked if anyone can help him locate a mains transformer for the Phillips 2514 receiver shown in the pictures. It must have an output of 200-0-200V and two 4V windings. The width must be 72mm. He has one 75mm wide transformer but this will not fit.

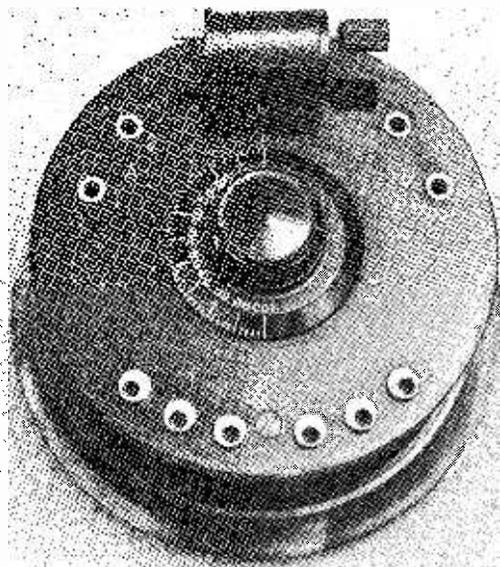If anyone wishes to write to Gunnar on any aspect of Vintage radio, his address is: Gunnar Carlström, S-540 MOHOLM, Sweden.



A crystal set C1925 from SM6KT's collection.

SWEDEN



SM6KT

SINCE 1938




GUNNAR CARLSTRÖM
Granhem - Moholm

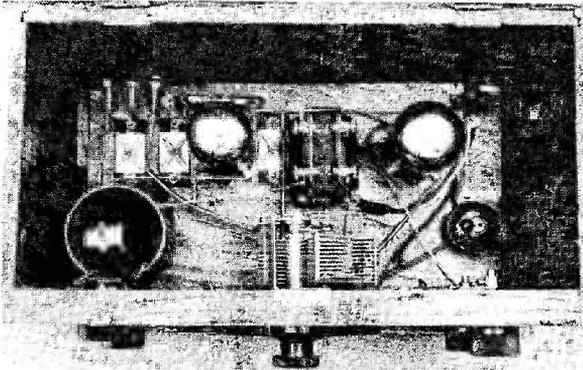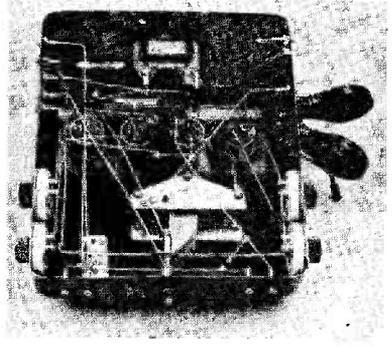
This receiver has four valves—1 detector and 3 audio. The feedback coil is shown on the right of the picture. The manufacturer is unknown but could possibly be VDFI. Date is about 1924 and the type number "E36" is printed on a small panel.



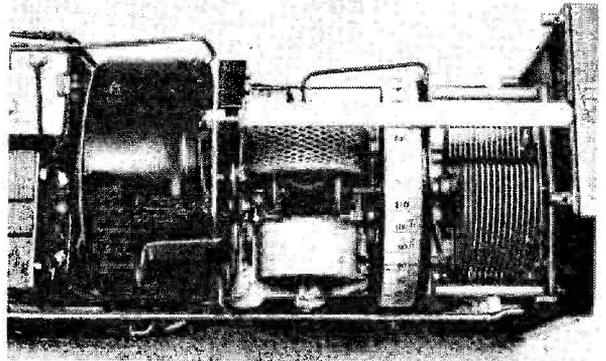Interior view of a home-constructed receiver. It has a detector and audio valves and is dated about 1926. Power supplies are 4V and 60V.



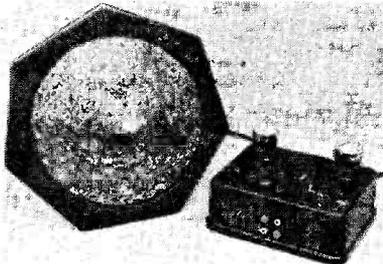
Philips 2514 for a.c. operation. Contains a universal supply unit for filament current, anode current and grid bias. Valves used are SV4, 154V and PM24. The a.f. side of this set could be used with a pickup to reproduce records. A popular design in the mid to late 20's, this set would be quite sensitive using only a short indoor aerial.




This receiver was bought from a local farmer in 1936 and is dated c1926. It is in good working condition and is made by Stern & Stern of Stockholm. Called the "Concerto II" it employs two valves and uses a wirewound pot for the filament supply. The speaker is a Philips type 2016 and was a common design in the 1930's. If anyone has more gen on this speaker, Gunnar would like to hear from you. Philips have not answered his letter to them asking for gen.



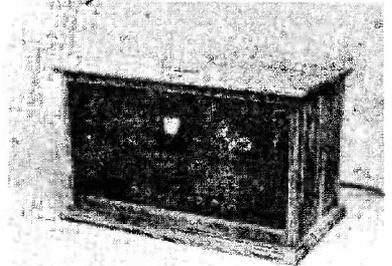
Telefunken receiver. The three valves are held in place by three sprung holders. This set was found in an attic in very bad condition but Gunnar Carlström has completely renovated it and built a new lid to the cabinet. Date is c1927. The speaker is a NORA type and more gen on this would be appreciated.



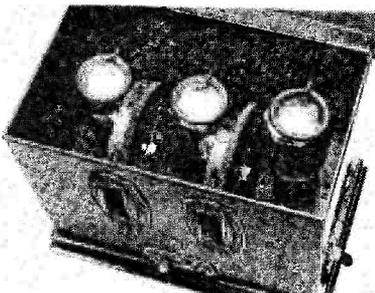
An external view of the above (left) receiver. The cabinet is in very fine condition and the control panel is of black Bakelite.



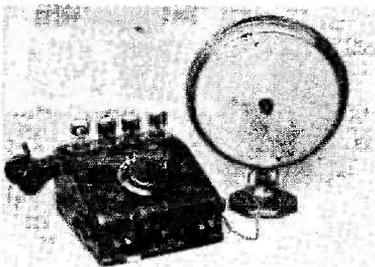Interior view of the Telefunken receiver. Bandswitching for m.w./l.w. is on the front panel. Power supplies are 100V and 4V.



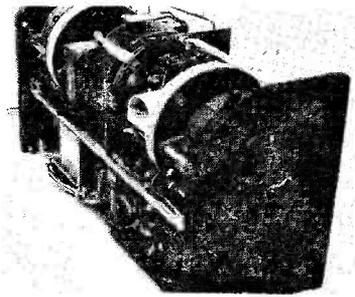The "E36" shown with a "Tefag" loud-speaker. Manufacturer of the speaker is not known.



Another view of the Philips 2514 showing the tuning capacitors. This is the set that lacks a mains transformer (see opposite page).

Lusitania Messages

T. A. Ledward, 4 Haulfryn Terrace, Blaenau Ffestiniog, Merioneth writes . . . "In the year 1910 a school friend, living only a quarter of a mile away, suggested that we should make a transmitter and receiver. We did so and were licensed by the Post Office who allotted us a call sign and wavelength. The transmitter utilised a spark coil and the receiver a crystal, with coil and slider for tuning, and a single headphone. It worked well. I became so interested that after spending some time apprenticed to heavy engineering between the age of fifteen and eighteen, I took a course in Wireless at the Manchester School of Wireless Telegraphy. I quickly became proficient in morse and had quite a thrill when listening at home on my own crystal set I picked up messages passing between the Lusitania at Liverpool Landing Stage (I was only six miles away), and the Seaforth Station. I joined the Marconi Company, as a sea-going operator, and after serving on several merchant ships, I volunteered at the beginning of the first World War in 1914 for service on H.M.S. Victorian, an armed merchant cruiser, only just fitted with guns, etcetera. My sea-going career ended in 1917, when the ship on which I was serving was torpedoed and sunk. The German submarines had been having so much success that there were not enough armed merchant cruisers left to give employment to all the available operators, and I joined the R.A.F. (just re-named from the R.F.C.) and was appointed radio instructor in a home camp.

"Make Your Own Wireless Valves"

W. A. Field, 10 Thurlestone Gardens, Dartmouth, Devon says . . .

"I have been reading your article Going Back with very great interest. My practical experience goes back to 1916. I made my first radio set in 1917, then continued to complete the transmitter in early 1918. The entire equipment was made with the help of "The Boy Electrician", published in 1915 by A. P. Morgan (Duckworth & Co.), 3 Henrietta Street, Covent Garden W.C. (Little did I know that this subject was to be my career). This book was wonderful. It described each item, how to construct it, what it was for, then building the item into a complete circuit.

I constructed everything in this book from the crystal detector, tuning coils and condensers to the complete wireless station for amateurs, which I ran for many years. When the BBC started regular transmissions I constructed sets for the market. I had quite a lot of experience with the S T Manual. This was the first edition. I used the ST 200 as a basis for a radio set which could be used from a car, the audio side had to be altered and increased. Triode valves were coming in, and the famous Model Engineer came out with Make Your Own Wireless Valves. These were made of carbon filament motor car bulbs. The filament acted as the heater and a small ring or copper plating on the outside of the bulb as the anode. The deficiency here was the electrons had to pass through the glass first, later on we improved on these. All through my experiments I kept notes, and I have an old crystal set procured in 1917 and still working by my side now. (Is this a record?)



Amateur Radio Techniques (Fourth Edition)

By Pat Hawker G3VA

Published by the Radio Society of Great Britain

256 pages, 9½ x 7¼in. Price £1.60.

EVERY radio amateur has a few favourite reference manuals on his bookshelf and among these must surely be numbered Amateur Radio Techniques, published by the Radio Society of Great Britain. Their monthly magazine Radio Communication features "Technical Topics" and the reviewer knows that he is not alone in making this priority reading as each copy drops through the letter box. ART is a collection of choice items from TT since Pat Hawker G3VA began the series in 1958. If a quick recap on a particular circuit or idea is needed the chances are that it will be found in ART. It would be quite wrong to imagine that this book is just for the "ham" fraternity because it can be found on the desk of many professional electronics engineer, in Government departments and in the Services. This much enlarged edition contains over 600 diagrams with all necessary component values helping to illustrate and explain the plethora of practical ideas under such headings as Receiver Topics, Oscillator Topics, Transmitter Topics, Audio and Modulation, Aerial Topics and Fault-Finding and Test Units. Chapters on Semiconductors and Components and Construction fill in the gaps to provide an excellent publication. As the author points out, this is an "ideas" book rather than a conventional text book, the reader being left to use his own knowledge and experience in making up a particular circuit but it would be a poor experimenter who would not glory in doing just that. Altogether a fabulous book which can be picked up and read to advantage at any time but particularly useful when inspiration is needed. AED

Guide to Broadcasting Stations—17th Edition

Published by The Butterworth Group—Iliffe Books

201 pages, 7¼ x 4¾in. Price 75p (paper back).

THIS latest edition of a well established reference book lists broadcasting stations from information supplied by the BBC. It includes articles on various related topics for the listener and a listing of V.H.F. Sound Broadcasting Stations.



Construction

Because of the length of the 3BP1 cathode ray tube, it is necessary to use a *deep* chassis. In fact the oscilloscope chassis is 14in. long (from back to front). The overall oscilloscope chassis dimensions are 14 x 9 x 2½in.

The front panel has to accommodate the c.r.t., seven variable controls, two input sockets, sync on/off switch, pilot lamp and an earth terminal. The main panel and chassis dimensions are given in Fig. 4. The drilling layout for the oscilloscope front panel is given in Fig. 5.

The astigmatism (VR7) X shift (VR6) and the X linearity (VR5) controls are mounted along the side of the chassis. The a.c. inputs from the mains transformer sub-chassis (containing T1, T2, and T3 etc) enter the oscilloscope chassis via the 10 way cable. This saves space on the front panel and simplifies the layout.

The Veroboard panel containing the main oscilloscope circuitry is mounted in a 12 x 3½in. cut-out in the oscilloscope chassis. Use the Veroboard panel as a template when drilling the fixing holes in the oscilloscope chassis.

The oscilloscope front panel also has an aperture covered by a piece of laminated plastic sheet. This

is necessary because the brilliance control VR9 is approximately 720 volts negative with respect to the chassis and therefore needs to be well insulated. There is about 50 volts across the brilliance control. The focus control VR8 is also at a high negative potential with respect to the chassis and this has about 300 volts across it.

The laminated plastic sheet is extended to make a mask for the face.

The angle pieces holding the front panel to the chassis should be 16 or 18 s.w.g. aluminium and the bolts are 2BA with shake proof washers and firmly tightened nuts.

The method of supporting the c.r.t. is unconventional but it allows the tube to be adjusted to level the X axis (timebase) and at the same time the tube is held against a rubber ring glued to the back of the front panel.

The bracket which supports the back of the c.r.t. is secured to the chassis by four 4BA bolts which pass through grommets in the chassis and make the tube mounting more flexible. All the bolts have a full nut and a half nut for locking.

The main transformer sub-chassis carrying the three mains transformers, T1, T2 and T3 utilises a

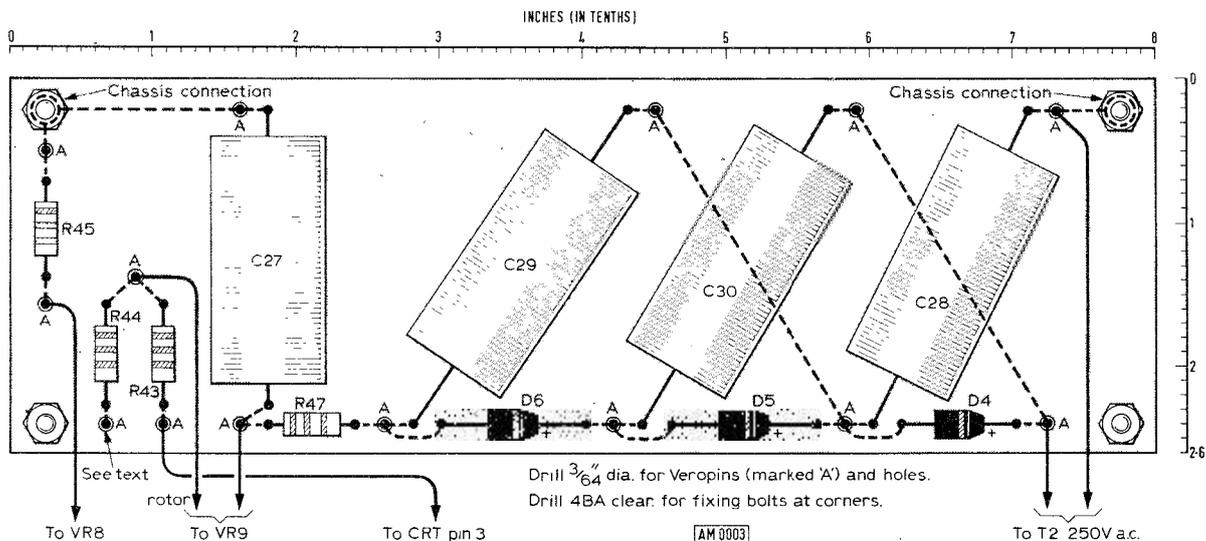


Fig. 3: Component layout and wiring on the EHT panel.

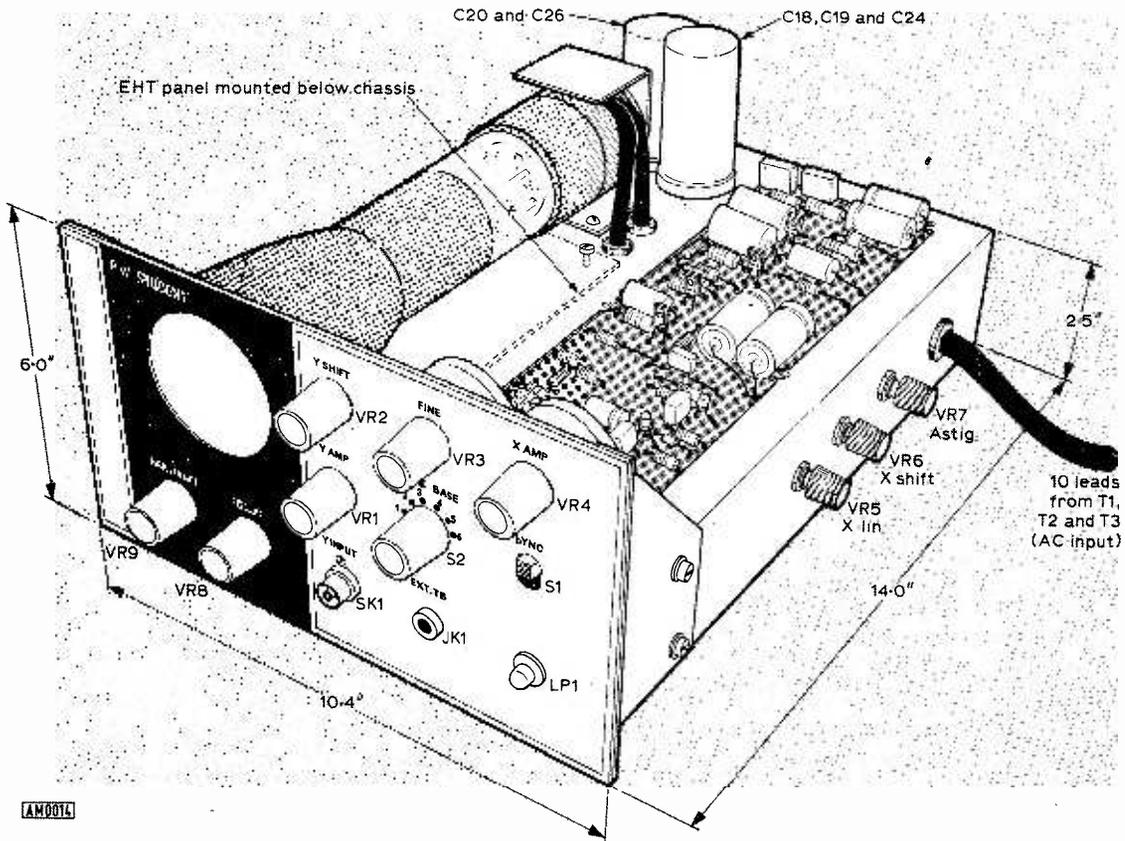


Fig. 4: General view of the PW 'Student' Oscilloscope, showing the location of major components.

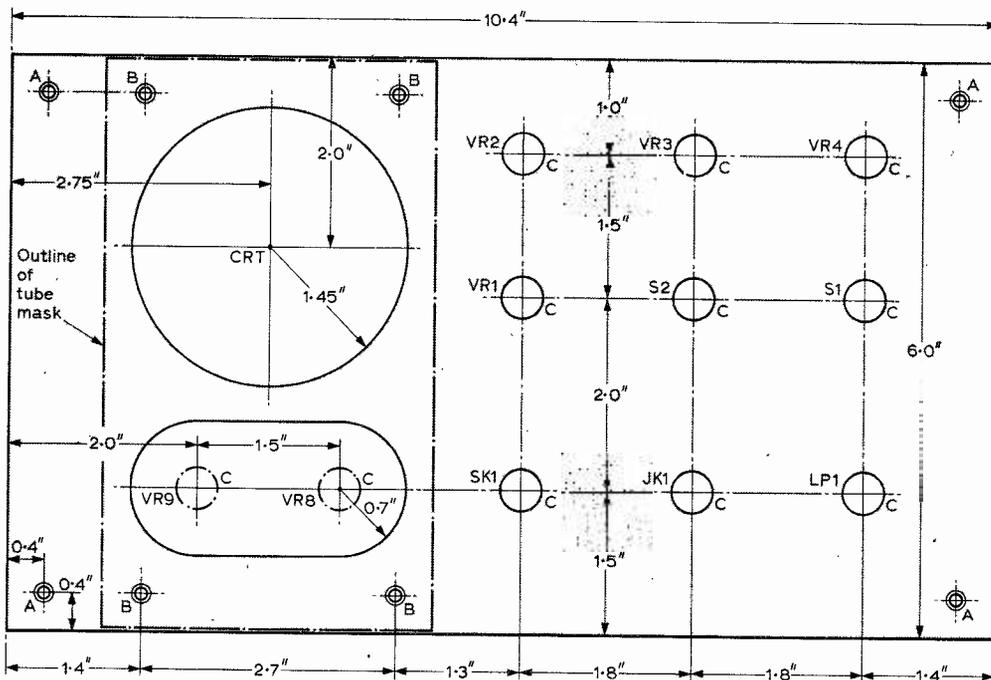


Fig. 5: Drilling layout for the front panel.

Note: left section of S2 is used only for earthing C5,6,7,8,9 and C10.

Rubber gasket stuck onto rear of front panel to cushion CRT face.

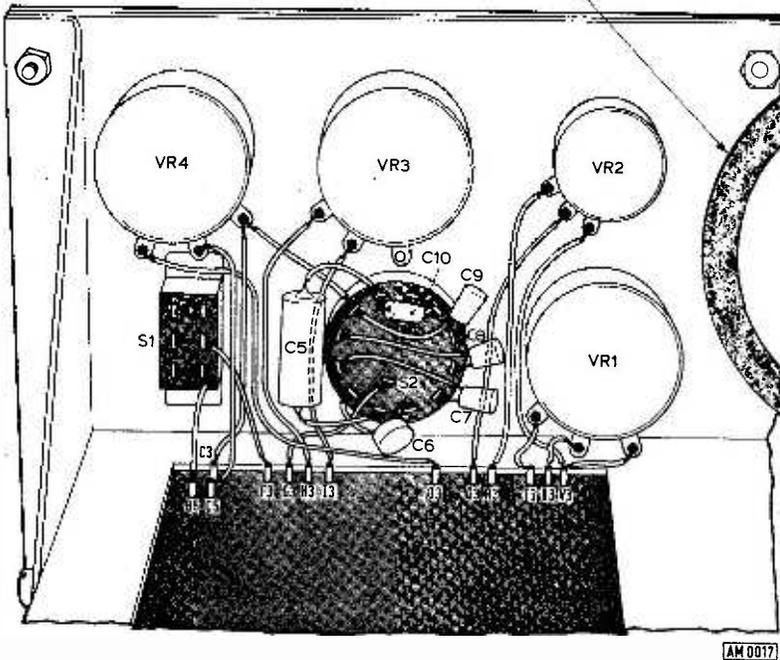


Fig. 6: Interconnection between Veroboard panel and front panel controls.

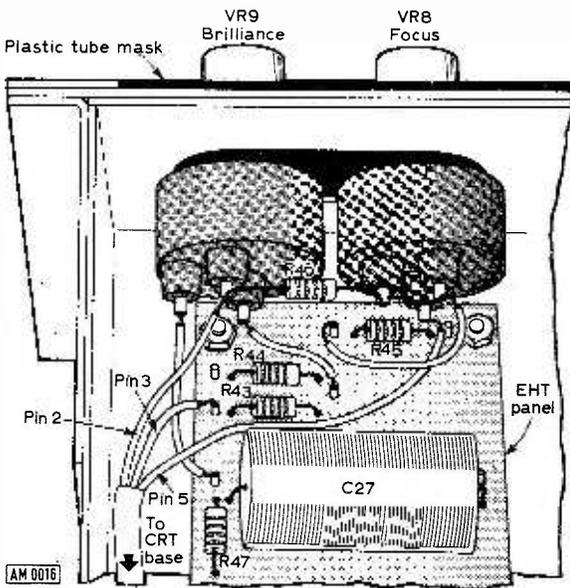


Fig. 7: Interconnection between the EHT panel and front panel controls.

wood base for mounting these components. The size of this base will depend upon the mains transformers used. Mains transformers usually have identifying tags for connection of leads. The arrangement behind the panel (from the 10 way socket to the mains transformer) will depend upon the transformers used, but should be quite straightforward once individual windings have been identified.

A suitable mains on/off switch, pilot lamp and a 2A mains fuse and holder may also be fitted to the sub-chassis front panel. It is recommended that the complete mains transformer sub-chassis is suitably enclosed to avoid accidents.

It is also possible to include a 100mV a.c. calibrating source from the 6.3V winding on T1 mains transformer. This is obtained from a 620Ω and a 10Ω resistor in series across the winding, and the junction is taken to a co-axial socket on the sub-chassis panel. The bottom of the 10Ω resistor goes to chassis. Because the 100mV signal will be fed into the Y input it is important to use a screened lead to avoid stray pick-ups. When wiring the 6.3V winding to the coax-socket, make sure that it is the earthy side of the socket that goes to the earthy side of the 6.3V winding (remember—one side of this winding is earthed on the oscilloscope chassis).

Other Facilities

The design as outlined is a compromise, being mainly concerned with the construction of a basic oscilloscope. For instance, no oscilloscope is complete without flyback suppression, but this requires further circuitry. The author so far has been unable to decide upon a suitable circuit.

Another area in which the instrument could be improved is the Y input, but the author believes that the best solution here would be to design a separate unit which can be plugged into the Y input, capable of accepting any signal from 10mV/cm to 50V/cm.

Beam slitting facilities and a mixer for two inputs could be added. However, such a unit would require complete screening which would be difficult to attain within the present design.

As the instrument is used for checking the performance of Hi-fi equipment as well as general laboratory work, it is housed in $\frac{1}{2}$ in chipboard cases covered with imitation mahogany laminated plastic.

Both cabinets have aluminium instrument case handles, 4 ins centre to centre.

In part 1, last month, LP2 as shown in Fig. 1 would not function. The upper lead from LP2 should go to the top end of the 6.3V winding instead. Attention is drawn to the breaks in the Veroboard strips—especially between Tr3 base and Tr4 collector.

Caution

This instrument **should not** be used on TV or radio or any apparatus where the chassis is live to the mains supply. ■

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit - £29.95! (INC.VAT)

The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £14!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16 batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £29.95!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer - you can't get it anywhere else. Ready assembled, it costs £43.95 - so you're saving £14! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16 batteries. (Replacement set costs about 15p.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

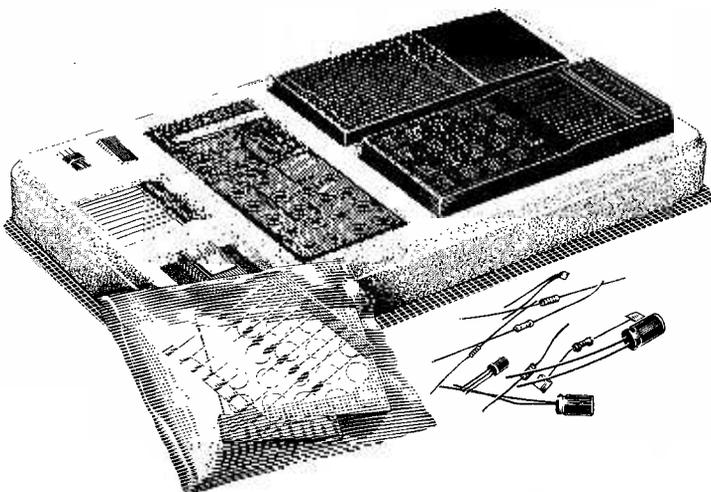
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

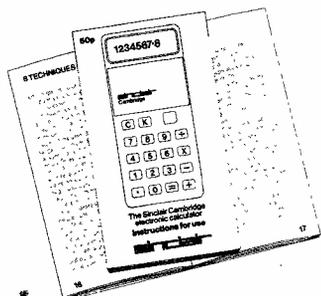But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

Logs Sines Cosines
Tangents Reciprocals nth roots
Currency Compound
conversion interest
and many others...

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £27.23 + £2.72 VAT. (Total: £29.95)

Price fully built: £39.95 + £4.00 VAT. (Total: £43.95)

PW 973	
To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdonshire, PE17 4HJ	
Please send me	Name _____
<input type="checkbox"/> a Sinclair Cambridge calculator kit at £27.23 + £2.72 VAT (Total: £29.95)	_____
<input type="checkbox"/> a Sinclair Cambridge calculator ready built at £39.95 + £4.00 VAT (Total: £43.95)	Address _____
*I enclose cheque for £ _____ made out to Sinclair Radionics Ltd, and crossed.	_____
*Please debit my *Barclaycard/Access account. Account number _____	_____
*Delete as required.	PLEASE PRINT


A series of simple transistor projects, using not more than twenty components.

WE'VE got very good value for the enthusiastic guitarist this month; a very simple Waa Waa unit that gives quite a dramatic effect with either guitars or electronic organs. There might need to be a little work done to the basic circuit to make it suitable for every application, but as there are so many different permutations on signal levels and input/output impedances we thought we would compromise with a circuit that can be inserted into the signal line where there is a typical level of between 50 and 100mV at medium to high impedance. Most equipment should have some point in it where this type of signal can be located.

Circuit

The circuit is basically a phase shift oscillator using the twin T bridge as the frequency selective element. C4, 5, 6 and R6 with R7 and VR2 form the bridge. Feedback is taken from the collector of Tr1 via C2 into the bridge and then back to Tr1's base. Negative feedback is also applied to Tr1 by means of VR1 in its emitter by-pass circuit; the level of the latter has to be adjusted so that the feedback is just insufficient for oscillation to be maintained.

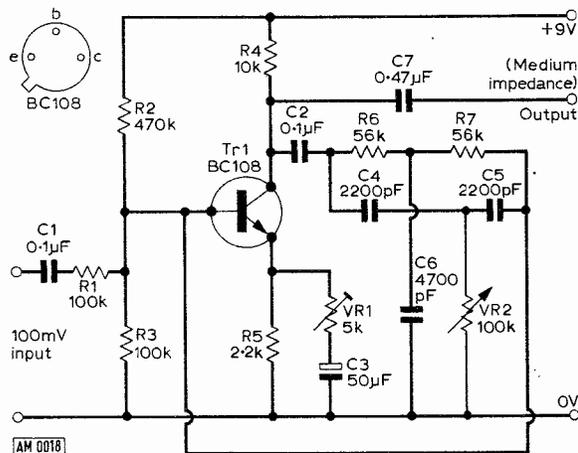The Waa-Waa effect is obtained by giving preferential amplification to certain frequencies within the musical note and then sweeping this frequency up and down. The chosen frequency is set by the component values of the twin T bridge and this can be varied over a useful range by adjustment of VR2. The gain of the circuit is greatest at the frequency when the level of positive feedback is greatest.



Circuit of the Waa-Waa unit which is essentially a phase-shift oscillator.

Chords or single notes will give the effect but in the case of the latter there should be a good range of harmonics present as well as the fundamental. A pure sine wave input, for example the flute stop of an organ, will give no effect whatsoever.

Almost any npn silicon transistor can be used for Tr1; the only feature of importance is that its h_{FE} should be in the order of 150 minimum (this is easily met by most BC108s). C4, 5 and 6 have been chosen to keep the Waa-Waa effect within the higher band of frequencies which adds more "sparkle" to the sound. If, however, a more mellow effect is required increase the values of these capacitors keeping the same ratio between them.

★ components list

R1	100kΩ	1p
R2	470kΩ	1p
R3	100kΩ	1p
R4	10kΩ	1p
R5	2.2kΩ	1p
R6	56kΩ	1p
R7	56kΩ	1p
VR1	5kΩ linear pre-set	8p
VR2	100kΩ linear	15p
C1	0.1µF	4p
C2	0.1µF	4p
C3	50µF 9VW min.	15p
C4	2200pF	4p
C5	2200pF	4p
C6	4700pF	4p
C7	0.47µF	5p
Tr1	BC108	10p
		80p

No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

Adjustment

When wired up it is only necessary to adjust the value of the pre-set potentiometer VR1 to give the correct level of negative feedback. To do this start with VR1 at minimum resistance and then turn VR2 over its full range. At some point a loud howl will be heard from the amplifier; this is the unit oscillating. Leave VR2 in the position for loudest howl and then slowly increase the value of VR1 (increasing the negative feedback) until oscillation stops. Readjust VR2 over its full range; if oscillation occurs at another point carry out the same procedure until VR2 can be swept from one extreme to the other with no oscillation occurring. The unit is then ready

continued on next page

JOINING COAXIAL CABLE


R.A.BUTTERWORTH

THE usual and accepted way of extending coaxial cable is to use the back-to-back coaxial connector. After a few months exposure to the elements it is not uncommon to find that the whole contraption has become oxidised, despite the fact that it was 'protected' by a generous layer of insulation tape of one kind or another. If, after you have managed to get the joint apart, close examination of the plugs and connector will usually reveal your so believed good electrical joint in an advanced state of corrosion.

The method to be described should appeal to those who like the writer, wish to join up these odd lengths of coaxial cable and forget about them.

Proceed as follows referring to the sketches for any clarifications necessary:

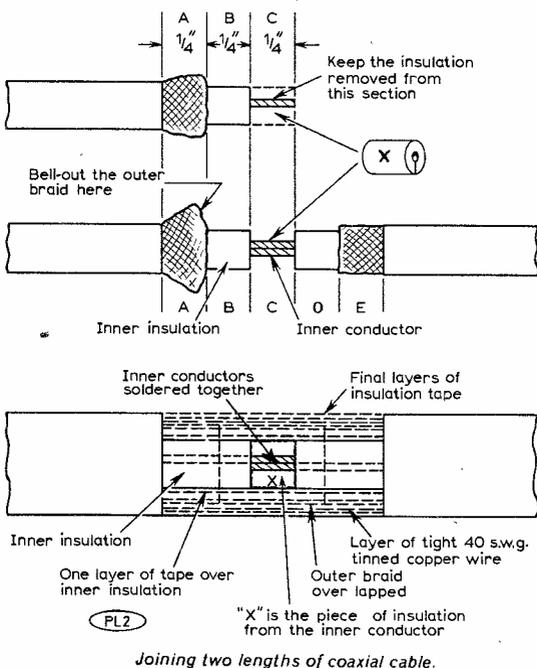1. Cut the ends of the coaxial cable to be joined to give clean ends. Carefully cut off $\frac{3}{4}$ in. of the vinyl covering at the end of each cable, taking care not to cut the outer braid.
2. Loosen and push back the braid like a concertina. Bell-out the outer braid of one cable.
3. Now carefully cut off $\frac{1}{4}$ in. of the inner insulation, again taking great care not to cut any strands of the inner conductor, so that the insulation slides off the wire. Conserve one of these pieces of material, it will be required later.



4. Lay both cables down on the bench and clamp down in position so that the two inner copper conductors lay close together and parallel. Now solder the two inner conductors together.


5. Take one of the pieces of inner insulation and slit it length wise with a sharp razor blade. Slip it over the soldered inner conductors.

6. Cut a piece of aluminium cooking foil $\frac{3}{4}$ in. wide and long enough to make a double thickness cylinder to cover the areas marked 'B', 'C', and 'D'. Heat this cylinder to about 100°C with a soldering iron when the insulation will be pliable enough to weld together. Discard the foil and leave the insulation to cool.

7. Now tightly wrap a single layer of $\frac{3}{4}$ in. adhesive vinyl insulation tape over the section 'B.C.D.'. Now smooth section 'A' over section 'E'. Roll and smooth this overlap to make it even. Spot solder the edges where 'A' overlaps 'E'.

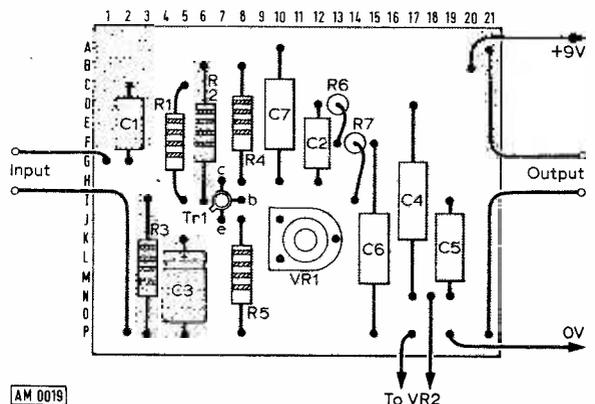8. Starting at one end of the outer conductor braid close wind the whole areas of 'A.B.C.D.E.' with 40 s.w.g. tinned copper wire. Lightly solder several spots of this covering. Don't try to make it a solid soldered job, or you will ruin the inner insulation. ■

TAKE-20 WAA-WAA UNIT—continued from previous page



Suggested layout of components on a piece of 0-1" matrix Veroboard.

for operation. If the Waa Waa effect is too fierce increase the value of VR1 further.

It might be that no oscillation occurs with the above procedure. This means that the transistor has low gain but do not give up—you will probably find you still get a useful effect when signal is applied at the input. ■



SHORT WAVE DX by MALCOLM CONNAH

BRITISH HONDURAS: Radio Belize has been noted with an extended schedule in Spanish. The frequency is 3300kHz and programmes have been heard up to 0730.

El Salvador: Radio Nacional de El Salvador has moved from 5980 to 6010kHz and has been heard at 0050 to 0055 with news, advertisements and music.

Malagasy Republic: RTVM Tananarive is using a new frequency of 6170 for the French Service. The transmissions have been noted in parallel with 7105 from 1400 to after 1900.

U.S.A.: According to 'DX Party Line' on HCJB, WNYW has now been taken over by Family Radio. Programming will, however, remain the same and the schedule for May-September is:

1700-2200 on 21525kHz	} All transmissions in English to Europe
1700-1900 on 17845kHz	
1905-2130 on 17845kHz	
2135-2330 on 15440kHz	
2215-2400 on 11855kHz	

Vietnam: The Voice of Vietnam, 58 Quan-Su Street, Hanoi broadcasts in English at the following times: 0100-0130, 0200-0230, 1000-1030, 1300-1330, 1530-1600, 1800-1830 and 2230-2300. The frequencies announced are 10040 and 15105kHz but the later frequency has been noted at 15012kHz.

South Vietnam Liberation Radio, c/o Bureau d'Information du C.R.P. de la R.S.V.N., 39 Avenue Georges Mandel, Paris 16e, France. Broadcasts in English on 10010 and 7470kHz start at 1100, 1230, 1430 and 2330 respectively. The programme at 2030 uses 14990 and 12115kHz.

(The last two items came from **Adrian Pell** of Wareham in Dorset, other items courtesy of Sweden Calling DXers.)

Readers' Logs

Once again **Roy Patrick** of Derby kicks-off with the following log using his Trio 9R59DS and National 1400 receivers:

- 4854 *R. Clube de Mozambique*, Portuguese at 2130.
- 4940 *R. Abidjan, Ivory Coast*, in French at 2100.
- 4995 *R. Brazil Central* noted as early as 2230.

6030 *T.W.R., Monte Carlo* testing in Norwegian, 2030.

- 9023 *R. Tehran, Iran*, heard in English at 2000.
- 11650 *R. Bangladesh*, news in English at 1700.
- 15084 *R. Iran, Home Sce.* in Farsi at 2100.
- 15415 *R. Kuwait* heard in English at 1700.
- 15520 *R. Bangladesh* in English at 1700.

Fred Wall of Walthamstow returns to the page after a long absence having used his Plessey PR155 and 50 foot long-wire with A.T.U. to hear:

- 6065 *R. Vilnius, Lithuania* in English at 0045.
- 9540 *R. New Zealand* with news at 0800.
- 9655 *R. Damascus, Syria*, light music at 2045.
- 11780 *R. New Zealand* with news at 0800.
- 11855 *Saudi Arabia B.S.* news in English at 1700.
- 15125 *Voice of Free China*, Taiwan, English at 1800.
- 15265 *R. Afghanistan* noted in English at 1810.
- 21545 *R. Accra, Ghana*, with local music at 1730.

Ian Gordon of Birmingham has again been busy using his Codar CR70A receiver, 25 metre (Metrication no less!) long-wire and A.T.U. to hear:

- 7230 *T.W.R., Monaco* in German at 0905.
- 9560 *ORTF, France* in Russian.
- 9620 *R. Belgrade, Yugoslavia* noted at 2200.
- 9640 *Adventist World Radio DX News* at 0935.
- 9745 *R. Baghdad, Iraq* noted at 1955.
- 9912 *All India Radio, Delhi* at 2000.


Christopher Hodgson of Sunderland is a new reporter to this page, his equipment consists of a Codar Multiband-6 receiver with a 50 foot long-wire aerial and the PW A.T.U. His log included:

- 6100 *R. Belgrade, Yugoslavia* at 2200.
- 6130 *R. Norway* from Oslo at 1810.
- 7260 *R. Berlin International* at 1850.
- 9006 *R. Tehran, Iran* noted at 2000.
- 9525 *All India Radio, Delhi* at 2100.
- 9525 *R. Warsaw, Poland* at 1200.
- 9645 *Vatican Radio* noted at 1505.

The last report for this month comes from **Patrick Henderson** of Ledbury, Herefordshire who used a six transistor superhet with a 17 metre Windom aerial to hear the following stations:

- 6025 *Radio Portugal* with DX News at 2105.
- 6070 *Radio Sofia, Bulgaria*, Mailbag at 1930.
- 9570 *Radio Australia* noted at 0730.
- 15012 *Voice of Vietnam, Hanoi* at 1805.
- 15130 *R. New York Worldwide* at 2300.
- 15165 *Kol Israel* noted at 2030.
- 15175 *RSA, South Africa* in English at 1825.

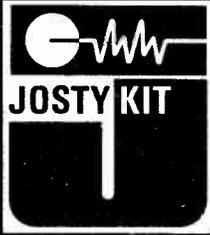During the next few months I hope to devote some space to the topic of ex-government Communication receivers which are now available at very reasonable cost compared with modern sets. I would be grateful if any readers with an interest in this topic would write to me with their opinions and any information that they may have.



NEW FROM DENMARK

Already Established As One Of
The Best Selling Kits in Europe

JOSTY KIT today

is counted among the leading manufacturers of electronic kits in Europe. Constantly the experienced engineers at the **JOSTY** laboratories work on improvement of existing kits and on new developments. Only the best materials and components have been used. The circuit-boards are manufactured according to the newest developments in this field and are supplied with all holes drilled and printed showing the exact placing of the components. Our long standing experience enables us to guarantee every **JOSTY KIT** for **ONE YEAR** for all parts as well as the correct function of the assembled kit. **JOSTY KITS** are a quality produce of DENMARK.

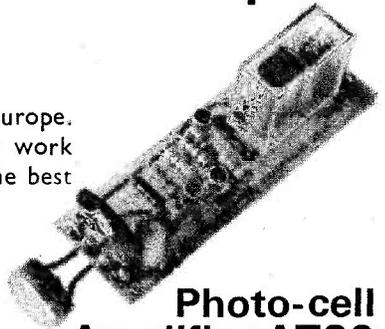


Photo-cell Amplifier AT30

NO more searching for
Components, it's all in the
bag the Josty way.

ELECTRONIC CONSTRUCTION KITS

We are sorry, you may have a little difficulty obtaining these kits at present. We at Josty are doing everything we can to produce more kits but in the meantime they are only available from

APPOINTED JOSTY KIT STOCKISTS

CENTRAL LONDON
G. W. Smith & Co. (Radio) Ltd.,
257/8 Tottenham Court Rd., W.1.
10 Tottenham Court Road, W.1.
27 Tottenham Court Road, W.1.
87 Tottenham Court Road, W.1.
21 Old Compton Street, W.1.
3 Lisle Street, W.C.2.
34 Lisle Street, W.C.2.
118 Edgware Road, W.2.
193 Edgware Road, W.2.
3M Edgware Road, W.2.
382 Edgware Road, W.2.
152/3 Fleet Street, E.C.4.
378 Harrow Road, W.9.

ESSEX
86 South Street, Romford.

SURREY
1046 Whitgift Centre, Croydon.
27 & 21 Eden Street, Kingston.
32 Hill Street, Richmond.

MAIL ORDER ADDRESS
G. W. Smith & Co., Unit 4,
The Hyde Industrial Estate,
The Hyde, NW9 6JJ.

T. Pattison,
5 Maritime Terrace,
Blandford Street,
Sunderland, Co. Durham.

Red Radio Shop,
31 Crowtree Rd.,
Sunderland, Co. Durham.

J. R. Gough,
27 East Smithy St.,
South Shields, Co. Durham.

Payne & Hornsby Ltd.,
3 Andrews House,
Gallowgate, Newcastle-on-Tyne.

Richley & Freeman Ltd.,
100 Percy St.,
Newcastle-on-Tyne.

Aitken Bros. Ltd.,
35 High Bridge,
Newcastle-on-Tyne.

Hamilton Music Store,
Corporation Rd.,
Middlesbrough, Teesside.

B. Williams,
16 Borough Rd.,
Middlesbrough, Teesside.

McKenna & Brown Ltd.,
135 High St.,
Redcar, Teesside.

Jaytron Ltd.,
178/9 Phibsborough Rd.,
Dublin 7, Ireland.

Bond & Mason,
94 Church Rd.,
Stockton, Teesside.

T. Jaques,
Waterdale Rd.,
Doncaster, Yorks.

Modern Electronics,
5 Sunny Bar,
Doncaster, Yorks.

Mitsons,
Citadel Row,
Carlisle, Cumberland.

Television Rentals,
414 Caccote Co.,
Hartlepool, Co. Durham.

JOSTY KIT RETAIL PRICE LIST (APRIL, 1973)

Model No.	Description	RRP Excluding V.A.T.	V.A.T.	Total RRP Incl'd. V.A.T.
AF20	Mono Transistor Amplifier	4.80	0.46	5.28
AF30	Mono Transistor Pre-Amplifier	2.61	0.26	2.87
AF310	Mono Amplifier (for Stereo use two)	5.91	0.59	6.50
AT5	Automatic Light Control	2.58	0.26	2.84
AT30	Photo Cell Switching Unit	5.70	0.57	6.27
AT50	400W Triac Light Dimmer Speed Control	4.80	0.48	5.28
AT55	1,300W Triac Light Dimmer Speed Control	5.70	0.57	6.27
AT56	2,200W Triac Light Dimmer Speed Control	6.00	0.69	7.59
AT60	Psychedelic Light Control, Single Channel	7.80	0.78	8.58
AT65	Psychedelic Light Control, 3 Channel	14.55	1.45	16.00
HF61	Medium Wave Transistor Radio	3.33	0.33	3.66
HF65	F.M. Transistor Transmitter	2.70	0.27	2.97
HF75	F.M. Transistor Receiver	2.88	0.28	3.16
HF310	F.M. Tuner Unit	15.81	1.58	17.39
HF325	De-Luxe F.M. Tuner Unit	24.12	2.41	26.53
HF330	Stereo Decoder for use with HF310 or HF325	9.96	0.99	10.95
HF395	Aerial Amplifier for AM/FM Bands I, II and III	1.77	0.17	1.94
GP310	Stereo Pre-Amp to use with 2, AF310	21.27	2.12	23.39
GU330	Tremelo Unic for guitars, etc.	7.50	0.75	8.25
NT10	Power Supply 100mA 9V Stabilised, 12V Unstabilised	6.15	0.61	6.76
NT300	Professional Stabilised Power Supply 2 x 30V, 2.2A	12.51	1.25	13.76
NT305	Transistor Converter 12/15V, a.c./d.c. to 6V, 7.5V, or 9V d.c.	4.50	0.45	4.95
NT310	Power Supply 240V a.c. to 2 x 18V d.c. at 2A	4.80	0.48	5.28
NT315	Power Supply 240V a.c. to 4.5—15V d.c. 500mA	9.57	0.95	10.52

Sole UK Distributors

RADIO SUPPLIES

(Components) Ltd.

P.O. BOX 27 · 39 WHITBY STREET · HARTLEPOOL TS24 7BR
TELEPHONE 0429-5750 or 68002

Another!
winner!

fane **MODE ONE**

**HIGH FIDELITY
LOUDSPEAKER KIT**



Recommended
retail price

£9.96

including V.A.T.

Please
send S.A.E.
for fully
descriptive
leaflet.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

SPECIFICATION OF UNITS

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	3/8"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	12kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. **SIZE 15 3/4" x 10 3/8" x 9"**.

*When used with above cabinet.

Distributors to the wholesale
and retail trade

LINEAR PRODUCTS LTD.

Electron Works, Armley, Leeds
LS12 3SA. Tel. 630126

Manufactured by

FANE ACOUSTICS LTD.

Hick Lane, Batley, Yorkshire.
Tel. Batley 6431

**New
VAT
EDITION**



**Lasky's
Audio-Tronics Catalogue 1973**

The new 1973 VAT edition of Lasky's famous Audio-Tronics catalogue will be available in early April—FREE on request. The 48 tabloid size pages—many in full colour—have been reprinted with VAT price changes for your convenience, together with many new items. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape Recording and Audio Accessories. Send for your copy now and see for yourself that VAT can mean a saving on many of the 1000's of items we offer.

FREE

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME

ADDRESS

PW14

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

**A Guide to
Broadcasting Stations**

17th Edition

A new edition of a title which has sold more than 250,000 copies. The first few chapters contain useful information on radio receivers, aerials and earths, propagation, signal identification and reception reports. The bulk of the book is devoted to lists of stations broadcasting in the long, medium, short and v.h.f. bands in both frequency and geographical alphabetical order. The lists are based on information provided by the Tatsfield Receiving Station of the BBC.

1973 206 pp., illustrated 0 592 00081 8 75p

Obtainable through any bookseller or from

The Butterworth Group

88 Kingsway, London WC2B 6AB

Showroom: 4-5 Bell Yard, WC2





MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

SEARCHING out BBC local radio stations is becoming popular and there are a number of reporters this month. G. M. Christie (N.L.S. Pole Star) used his Eagle Rx 60 while sailing off the east coast of Shetland to log BBC Radio Newcastle on 1457kHz. **Richard Ellis** (Ruscombe Glos.) has an Eddystone EC10 Mk2 and a 50m longwire feeding and aerial tuning unit. He reports reception of BBC Radio Blackburn on 854kHz; Solent on 998kHz; Sheffield 1034kHz; Birmingham 1457kHz; London 1457kHz; Oxford 1484kHz; Bristol 1546kHz; Leicester 1594kHz.

Martin Hall (Southsea) heard BBC Radio Teesside 1546kHz under Radio Bristol at 0502hrs while during the daytime he logged Radio Blackburn 854kHz and Radio Leeds 1106kHz. Martin has received a QSL card from Radio Blackburn and a QSL letter from Radio Leeds. Hunting out BBC local radios can be interesting at this time of year and all of these stations will confirm a correct reception report with either a letter or a QSL card.

Paul Petty (Canterbury) has been trying his Midland 9 transistor portable on the medium waves using its internal aerial and he has heard programmes in English from Trans World Radio,

Montecarlo 1466kHz at 2130hrs; Radio Tirana, Albania 1394kHz at 2030hrs; Vatican Radio 1529kHz at 2100hrs; American Forces Network, Frankfurt 872kHz; Radio Berlin International 1511kHz at 2130hrs; Radio Prague, Czechoslovakia 1286kHz at 2200hrs, all times in GMT.

Jeff Driver (Woodham, Surrey) reports hearing Milan, Italy 899kHz which is on the air nightly from 2305hrs until 0500hrs GMT with news in English at 3 minutes past the hour. Jeff has also heard Radio Norway 1579kHz which broadcasts in English every Monday at 0200hrs and 0400hrs GMT. **John Thompson** (Gillingham) has heard the IBA on 719kHz. This transmission is in parallel with the tests on 557kHz which are on the air 24 hours a day.

Roger Thomas (Port Talbot) enquires about the possibility of using his AR88LF receiver on the medium waves. There is unfortunately no easy way of doing this as the intermediate frequency of this version of the popular AR88, lies well inside the medium waveband. The writer would be glad to hear from any reader who has successfully made this conversion.

Portugal is well represented on the medium waves. The international service of the Emissora Nacional de Radiodifusao is on the air every night in English at 2245hrs GMT from its transmitters at Lisbon on 755kHz and Norte on 1061kHz and these are easily heard in the UK. Among the commercial stations, look for CSB2 Porto on 1034kHz, which is on the air all night with pops; CSB3 Lisbon on 1286kHz; CSB4 Lisbon on 1594kHz and CSB5 Porto on 1578kHz. All these stations will QSL, the cards issued from the international service being particularly colourful.

Sp-E on VHF by SIMON DAVID

SINCE I last wrote to you, a number of outbursts of "foreign" noises has been taking place. That sporadic-E interference I mentioned has been having a field-day. Continental stations have been coming in all over the place, but in particular around the 65 to 75MHz region. This is outside the usual f.m. band, but it shows that f.m. stations turn up in odd places.

Hugh Cocks of Mayfield, Sussex, tells me that he has picked up several stations from Yugoslavia on 23rd May around midday. He also reports channel-5 television buzz from the vision signal on 93.25MHz. Other signals include Albania television sound on 87.75MHz and vision signal interference on 82.25MHz; a Dutch station on 98.6MHz; AFN Stuttgart, West Germany on 102.4MHz.


The eastern European f.m. stations have come in around 66 to 72 MHz using a four-element aerial and two BF180 pre-amps but Mr. Cocks has a problem. When his aerial is directed north or south he gets i.f. breakthrough which disappears when the aerial is due east or west. He thinks that this is largely due to burbles and interference from Radio Moscow in Austria. Any readers have a theory?

Peter Tyler of Whitton, West Middlesex, has sent in a long and detailed log. His home-made "curtain-rod" three-element Yagi is in his loft and drives an old valve Pye Fen Man I. His long list includes several French, Dutch, Belgian and German stations. The latter were NDR II Oldenburg 99.8MHz, Radio Bremen II 88.3MHz. Peter has also received an

Italian station in 87.7MHz on 23rd May; signal strength was generally very good but subject to fading. On 24th June he received eight different Dutch stations and three German stations. He rightly complains of the effect of police transmissions on the band which spoil DXing. Further to his big bag was a bonanza of 10 Scandinavian stations, possibly Danish, on 16th June between 1400 and 1500 hours, between 87.7MHz and 99.5MHz. There was a high pressure area over the North Sea near Denmark at the time, which could be responsible for the good reception he obtained.

Recent information issued by the BBC includes a complete list of BBC local radio transmitting stations, revised reception area maps to cover BBC Radio Programmes in stereo from Wrotham and BBC Radios London, Brighton, Oxford, Teesside, Leicester, Birmingham, and Bristol. The BBC has also issued information sheet 1608 (1) which has some advice to help listeners to get the best they possibly can from BBC v.h.f. stereo broadcasts (see also Gordon King's article elsewhere in this issue).

Test tone transmissions on Radio 3 v.h.f. for stereo programmes are detailed on information sheet 1605 (9). These transmissions are usually broadcast on Mondays, Tuesdays and Thursdays to facilitate channel identification and adjustment of cross-talk, and on Wednesdays to assist in technical assessment and setting-up of stereo receivers. All such tests occur after close down in the late evening. Full details on these BBC Information Sheets from: Engineering Information Department, BBC Broadcasting House, London W1A 1AA. Please enclose a stamped envelope.

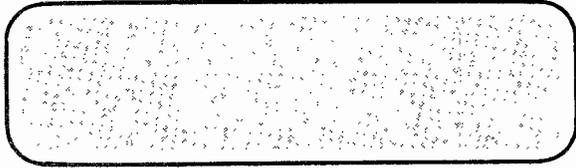

SHORT WAVES

by **DAVID GIBSON, G3JDG**

IT is a strange thing. Summertime is just the time for the DX-type listeners to flap their ever eager earholes all over 14MHz. What ever has happened? Far from multiple earhole flappings there is barely the twitch of a lonesome lobe. Just at the time when this band is the main one for most DX traffic, everyone is sending in logs for—you'll never guess—two metres. Nobody seems interested in hearing juicy jingles on 20 metres from people like SU1MA, XT2AK, KG6AAAY and YB3CW to mention but a few who were about last month.

Equally strange is the marked lack of logs for 21MHz, too. On this band, African countries and most of South America were all happily squirting r.f. everywhere. Wait till I get my 700 element Yagi for 14MHz, I'll put you all to shame.

Twenty eight megacycles (or Hertz?) has apparently been abandoned by practically everyone. This is rather sad because this particular band is probably one of the most interesting now that the sunspot peak has passed.

One station who puts in an appearance is ZS4AA on 28·60MHz. Name is Basil and he also appears on 21·42MHz most weekdays from 1600 hours. Sundays finds Basil on 21·20MHz around 0900 hours. Location is Kroonstad.

Anyone living in the Torquay district and would like to join an Amateur Radio Club you're in luck. The Torbay Amateur Radio Society has its headquarters in Bath Lane (rear of 94 Belgrave Road) Torquay. Hon. Sec. is at 23, Waverley Road, Newton Abbot and the telephone number is Newton Abbot 3025. There is a Club magazine and quite a lot of activity. If you're in the area, give the Secretary a buzz.

Readers' reports

According to **Bill Yates** (Bedford) it is well worth listening for W6KNH on Tuesdays around 1700 hours. Frequency quoted is 14·24MHz and a sked is usually heard with ZK1MA. Another piece of information for DX types is that Andaman Island is due for a surge

of extra activity. Twist is that it could mean yet another callsign change—listen for VU7.

Russell Corner sends in a log of G stations heard on topband and eighty metres. Russell's best from further afield on 3·5MHz includes: ZM1MH, 3A2AOO and 4XZSNJ. All these on a 9R59DE and 360ft. of wire in the loft at Walworth Grove in Middlesbrough.

Tony Mountifield (Gosport) claims to be a member of the RSGB and a passer of RAE. He also says, "I have read your column for a few years" (splendid fellow this Mountifield). Receiver is an R1155L (aren't those the ones you have to light with a match?) and among the best heard on twenty were: A6XF, CT1MA, EA8IX, LX1DU, SV5HH, TF3EB, VE3SR, W6UFG, ZD8RW, 4Z4GH, 9G1AR.

Bernard Hughes (Worcester) has sent in an updated portion of the Potty callsign changes list. In all seriousness, I do hope these will help those with computers to keep up to date with these callsigns. Bernard lists them as follows: HA25—25 years of post war Amateur Radio; HA100—Budapest Centenary; OK5OR—celebrates 50 years of Amateur Radio; KW9WEZ—station operating from Indianapolis car races (now I've heard it all); VE3RCMP—Centenary of the Royal Canadian Mounted Police; IT57—Targa Florio award.

Just to show what's about on 14MHz, Bernard lists the following heard with the aid of his JR-310 and dipole; CR5AJ, HC2YL, JA4FAB, JA3LOJ/MM, JA6CNL, JY5HC, JX9XP, KW9WEZ, MP4BJR, PY9KC, PT2JB, VE8RCS, VP7ND, YA1DT, ZL1AUM, ZL2CE, ZL3FM, ZD7SD, ZD7SS, 7X2MD, 9K2CA.

Andrew May (Bromsgrove) got these on 28MHz with an HA-350 and 67ft. long wire (all s.s.b.); WA7CAE/P/YV5, YV5CWO, YV5DEO, 4X25HF, 4Z25MQ, 5U7BA, 6W8DY.

Lindsay Pennell is leaving Hong Kong and is due back in the UK. Perhaps we will see some UK-type logs (I was getting fed up with translating Chinese, anyway). Heard from Hong Kong on 28MHz; 9M2DQ, A4XFE, CR6SR, 9J2DT.

Two metre tweets heard from; DL7FQ, F1CCP, F6CKU, G1AAAT, GM3BA, GW3UUC/P, ON5NY/P, PA0FHV. These were bagged by **Paul Marks**, G8FVK, who lurks at Woodford Green with an 8-element beam, homebrew converter and Eddystone 730/1A.

Diary dates

The National Agricultural Centre at Stoneleigh, Kenilworth, Warwickshire is the place to be on the 25/26/27 of August. The Town and Country festival is to include a complete introduction to the world of Amateur Radio. This will include morse code demonstrations, display of radio equipment, homebrew demonstration, transmitters on the air, a radio rally and the Amateur Radio Emergency Service in action.

Other Mobile Rallies in August will take place at: Newton Abbot August 12; Derby 12; Bristol 19, Preston 19. Contests for August: WAE DX c.w. 11-13; 70MHz 12; 144MHz low power 18; 144MHz s.s.b. 19.

BROADCAST BANDS

Short Wave Reports by 15th of the month to **Malcolm Connah**, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

Medium Waves Logs to **Charles Molloy**, 182 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to **Simon David**, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

AMATEUR BANDS

Short Wave/VHF

Logs in alphabetical order please by 15th of the month to **David Gibson**, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.



MAINS MOTOR
Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 72p. Postage 20p for first one then 10p for each one ordered.

MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely 65p each or 5 for £2.50. Send for list of titles. We can't repeat when sold out.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, 37p each, 10 for £3.78.

CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system, 38p each or 10 for £3.42.




MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1163 500mW power output 73p. Model 1177 750mW power output 94p. Model EP9000 4 watt power output £1.60. EP9001 twin channel or stereo pre amp. £1.92 10% discount if 10 or more ordered.

CENTRIFUGAL BLOWER

Miniature mains driven blower—centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing fume smoke when soldering etc., etc. A real bargain at £2.05.

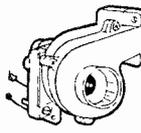

MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January '73. All electronic parts £2.20 post paid.


TAPE PLAYBACK UNITS

Mains operated. Made by Redifume the famous "music in background people". These are complete units for playing tape at standard speed (3 1/2"). These have a superior motor driven fly wheel to control the tape through the capstan and also an even equally useful valve amplifier with EL84 output. In a steel case with carrying handle. Tested and good working order £8.50, or some in need of repair but complete £3.50, cassettes of tape pre-recorded £1.10 (please state type of music required.) 75p carriage up to 200 miles then 50p per 100 miles extra.



RADIO STETHOSCOPE

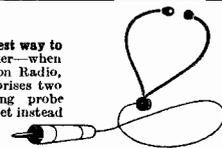Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2.20—twin stethoscopes instead of earpiece 83p. extra—post and ins. 20p



6 MAINS TRANSFORMERS. Our Ref: MTM1 27 volt at 8 amp, Upright mounting fully shrouded—flying leads—fully tappered primary. Price £3.30. Our Ref: MTM2 12v at 1 amp. Upright mounting with fixing lugs, tag connection. 240v primary—12v 1 amp secondary. Price 83p. Our Ref: MTM3 6.3v 2 amp upright mounting with fixing lugs, tag connections, 240v primary 6.3v 2 amp secondary. Price 77p. Our Ref: MTM4 18v 1/2 amp with thermal cut-out, upright mounting with fixing lugs—tag connections. Primary 240v, secondary 18v at 1/2 amp. Price 88p. **MAINS ISOLATION MTM5** 250 watts earth shielded—flex leads—upright mounting lugs for fixing. Price £5.50 each. **MAINS TRANSFORMER BARGAIN.** Standard mains 240v input. Secondary 2.4v 9 amp intermittent. 5 amp continuous. Price 55p.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp. sockets in metal box to take standard 13 amp. fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2.50 plus 20p post and ins.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price £2.55 plus 20p post. When ordering please state whether for positive or negative systems. Also available, ready made ignition systems for 6V. vehicles £7.95.

24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable periods per 24 hours. 5A changeover contacts will switch circuit on or off during these periods. £2.75 post and ins. 25p. Additional time contacts 55p pair.

THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95 plus 20p post and insurance. Industrial, model 5A £3.30.



BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Eveready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2 1/2" with leads and prods. Price £2.48 plus 20p postage.



DRILL CONTROLLER

NEW IKW MODEL
Electronically changed speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.65. Made up model also available. £2.75.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPI, PP3, P14, P16, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.10.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24" x 18" £1.54 13" x 10" £1.10

SUMMER OFFER

Mullard Uniflex stereo amplifier at pre-VAT price, normally £10 for the four module, control units knobs and face plate.

15A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you awake — switch on lights to ward off intruders — have a warm house to come home to. All these and many other things you can do with electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.15 + 20p p. & p. or with glass front, chrome bezel, 83p extra.

PROTECT VALUABLE DEVICES FROM THERMAL RUNAWAY OR OVERHEATING

Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg.F. or with the dial removed range setting is between 80 to 800deg.F. Price 85p.



ROCKER SWITCH

13 amp self-drawing into an oblong hole. Size approximately 1 1/2" x 1 1/2" 9p each, 10 for £1p.

THERMAL CUTOUT

A miniature device 3/4" dia. on one screw fixing mount—can be used for motor overload protection—fire alarm—soldering iron—switch off, etc., etc. 15 amp contacts open with flame—radiant or conducted heat. 11p each or 10 for 99p.

HONEYWELL PUSH BUTTON MICRO SWITCHES

As used in some vending machines, etc. Each switch is a change-over type rated at 15 amps 250v A.C. Intended for panel mounting with fixing nuts and single black push knob. Single change-over switch 28p. Double switch 42p. Triple switch 61p.

KETTLE ELEMENTS

Made by the famous A.E.I. Co. Complete with washers and combined fixing ring and plug shroud. Normal 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1 1/2" (approx.) suitable for Swan and other similar models—1 3/4" (approx.) suitable for G.E.C. Hotpoint, etc. All quick buy 2 1/2 Kw elements at 240v. Price £1.38 each.

MACLAREN THERMOSTAT

Make and break 20 amp A.C. with the sensor probe coupled by 2 feet capillary covering range of 10—100deg.C.—complete with large engraved control knob. Price 83p.

CONNECTING WIRE

7-0076 Copper conductors. 500 metre drums available in the following colours.—Red/Brown—Yellow—Green/Grey—Blue/Green—Red/Orange—Green/White—Grey/White—Blue/Orange—Brown/Red—Brown/White—Red/Grey—Blue/Grey—Blue/Brown. Price £2.20 per drum plus 40p post. State alternative colours. Ditto—but with 200 metres. Price £1.38 per drum plus 20p. Ditto—but with 100 metres. Price 83p per drum.

DOOR SWITCH

As fitted to refrigerators, etc. Switches off as door closes. White 17p each. Black 15p each.

GOODMANS P.M. SPEAKERS

8" x 5" hi flux 15 ohm coil very suitable for use with Mullard Uniflex stereo amplifier or with the EP9000 on it's own. £1.65 plus 20p post each.

7" x 4" also 15 ohm and suitable for use with the EP9000—not this such good quality of course. Price £1.05 each.

U.V. LIGHTING

Useful for flaw detection in metals and for looking for water marks, etc., also for fitting over tropical fish tanks, African violets and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 12" U.V. tube—choke—starter holder and tube ends. Price £2.20 plus 20p post.

SOIL HEATING KIT

Suitable for garden frame or propagating shelf, etc. Comprises 40 watt mains transformer, heating wire, connection strip and insulated wire with connection diagram. £1.65 plus 20p post.

80 WATT TUBULAR ELEMENTS

Brass encased with beaded flex ends. Standard replacements in most absorption refrigerators but also has dozens of other uses. 23p each or 10 for £1.48.

SPIT MOTOR

200-250V Induction Motor, driving a Carter gear box with 1 1/2" of output drive shaft running at 5 revs per minute. Intended for roasting chickens also suitable for driving models—windmills, coloured disc lighting effect, etc., etc. £2.04 plus 20p post and insurance.

TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items. Post free if order for these items is £6.00 otherwise add 20p.

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

PARTRIDGE PACKAGE

is a
COMPLETE RADIO STATION
including
WORLD RECORD JOYSTICK ANTENNA

Phone your order—we send the goods—just give name, address, ACCESS or BARCLAYCARD number—that is all—tel: 0843 62535.

The Space Age WORLD RECORD award winning 7' 6" long All Band JOYSTICK VFA Antenna—JOYMATCH A.T.U.—TRIO RECEIVER or TRANSCEIVER—Matching HEADPHONES—A COMPLETE STATION IN ONE COMPACT PACKAGE—THE FLAT DWELLER'S DREAM!

JOYSTICK VFA £12.54 (A); JOYMATCH ATU 111
★ or 111A £12.54 (B); JOYMATCH ATU LO-Z500 £18.10 (C).

COMMUNICATIONS 8Ω HEADPHONES £2.86 (D)

(All prices include V.A.T., carriage, packing, accessories & insurance)

PARTRIDGE PACKAGE No. 1
JR59DS receiver .. £54.45
* Items (A); (B); (D) above .. £12.10
Complete Gen. Coverage Station .. £66.55

PARTRIDGE PACKAGE No. 2
JR310 receiver .. £82.50
* Items (A); (B); (D) above .. £7.70
Complete Amateur RX Station .. £90.20

PARTRIDGE PACKAGE No. 3
JR599 receiver .. £176.00
* Items (A); (B); (D) above .. FREE
Complete Amateur RX Station .. £176.00

PARTRIDGE PACKAGE No. 4
TS/PS515 Transceiver 180W .. £231.00
* Items (A); (C); (D) above .. FREE
Complete TX-RX Station .. £231.00

ALSO: OA2 MAINS STABILISER 74p. 2KW LINEAR AMP. TL911 £207.90; TR2200 2M Personal transceiver £87.45; TR7200 2M Car transceiver £142.45; Spare set valves for 9R59DS £2.35.

PLEASE CONSULT US REFERENCE SUITABLE SPEAKER

NEW: World-wide reception on the amazing "DX—CRYSTAL SET" £2.20 including unique aerial.

NEW: PARTRIDGE ARE APPOINTED STOCKISTS OF AMTRON QUALITY KITS—send for fully illustrated brochure and price list.

PARTRIDGE BUDGET LINE—

ARTIFICIAL EARTH—SOLVES YOUR EARTH PROBLEMS £5.28; AERIAL BANDSWITCH—TUNED AERIAL £5.28; A.T.U. KIT—FULL COVERAGE TX/RECEIVER £5.28; ASSEMBLED £6.38.

Send 3p stamp for full illustrated details of Partridge Products. TR10 brochures (state which) 3p stamp extra.

NO V.A.T. ON OVERSEAS ORDERS!

CARRIAGE & INSURANCE EXTRA OVERSEAS.


BOX 5
PARTRIDGE ELECTRONICS LTD.
BROADSTAIRS, KENT

Phone: 0843 62535 or 62839 cheap periods.

PRINTED CIRCUIT KIT

BUILD 60 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminated Boards 4 1/2in x 2 1/2in. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dial SWITCHES. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 60 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements.

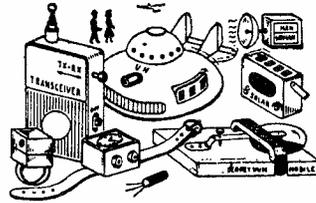

**EXPERIMENTER'S
PRINTED CIRCUIT KIT**
70p

Postage & Pack. 10p (UK)
Commonwealth:
SURFACE MAIL 15p
AIR MAIL 60p
Australia, New Zealand,
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photo-cell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62in x 0.9in x 0.5in. (11) Wristwatch Radio 1.5in x 0.5in x 0.5in. (12) Ring Radio 0.7in x 0.7in x 0.5in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Alarm. Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless-Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. (41) Light Dimmer. (42) I.C. Pre-amplifier. (43) I.C. Amplifier. (44) I.C. Intercom. (45) I.C. Radio. (46) Raudive Voices Receiver. (47) Biased-back Amplifier. (48) Brainwave Detector. (49) Proximity Switch. (50) Laser Projector. Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector, etc.

YORK ELECTRICS, Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details and a brief description of all kits and Projects.



BAKER 12" MAJOR £9.90

30-14500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly flux density 14500 gauss.
Bass resonance 40 c.p.s. 20 watt RMS.

MAJOR MODULE KIT £12.50

30-17000 cps. response
Tweeter, crossover and baffle as illustrated.

Baker Loudspeakers			
Regent 12" 15W	£8.80	Superb 12" 20W	£16.50
Major 12" 20W	£9.90	Group 25 12" 25W	£8.80
Deluxe 12" 15W	£11	Group 35 12" 35W	£9.90

**ALL PRICES
INCLUDE VAT**

**Baker Loudspeaker Co., Bensham Manor Passage,
Thornton Heath, Surrey, Tel. 01-684 1665**
 Loudspeakers Catalogue and Enclosure plan 5p

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Switches, Potentiometers, Knobs, IF's, Tag Strips, Drive Drums, Transistor Panels etc., etc. Save yourself £s on these well selected parcels 6lbs net weight £1.00, p. p. 40p.

Assorted Electrolytic Capacitors. 6lbs net weight £1.00, p. p. 40p.
Brand new Wire-wound Resistors. Good Selection. 100 for £1 p. p. 15p.

Mullard Ferrite Bar Magnets 1 1/8" x 1/8" x 1/8". 100 for £1.25, p. p. 16p.

Assorted Computer Panels. These panels are exceptionally good value and contain a minimum of 75 transistors, stacks of diodes plus Trim Pots, Polyester Capacitors, Resistors and include a few I.C.s. 10 panels for £1.00, p. p. 25p.


Mullard Ferrite Cores. LA3 100 to 500kHz. 50p. LA4 10 to 30kHz 75p. LA2100 3 to 200kHz 50p.

Please include 10% V.A.T. to total cost of goods.

**MAIL ORDER ONLY
XEROZA RADIO**
1, EAST STREET,
BISHOPS TAWTON,
DEVON

power supply module

J. LEWIS B.Sc

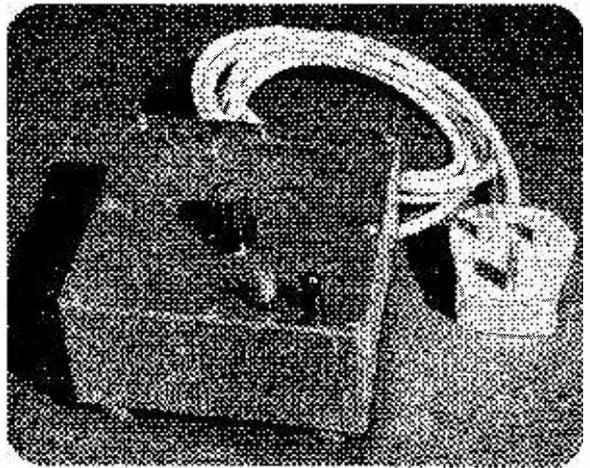

THE majority of circuits constructed by amateurs these days are transistorised and so their power supply requirements are quite modest compared with the valve sets of yesteryear. Most of these modern circuits can be driven either by batteries or by mains derived D.C. supplies. In some cases there is no real necessity to ensure that the power supply provides a constant voltage, this may vary without too much harm to the performance of the equipment. Others, though, may not be so tolerant, oscillators and integrated circuits are two that spring to mind. In these the output and the performance can be directly related to the stability of the supply voltage—especially if the voltage varies with the current drawn.

STABILISING CIRCUITS

To overcome these difficulties it has become common practice to use zener stabilised supplies or to add a transistor to that simple arrangement to give series or shunt stabilised supplies. Examples of these are shown in Figs. 1-3. Fig. 1 shows a simple zener circuit; the trouble here is that when no load is applied the zener has to be capable of dissipating all the power which should be consumed by the circuit, and due to zener spread and tolerance it is sometimes difficult to get an exact voltage. Fig. 2 shows a transistor-aided zener as a shunt regulator whilst Fig. 3 is a series regulator. Both these have the advantage that they can deal with higher currents and the output voltage can be varied continuously. The shunt circuit is also short-circuit proof though it does have

a relatively high output resistance; the series circuit on the other hand has a low output resistance but it is not short-circuit proof. Short the output on this one and the transistor can easily blow.

The stabilisation offered by these simple circuits leaves a lot to be desired and some constructors have devised extra circuitry to add to them to give a feedback sensing of the output voltage. Fig. 4 shows this in block form. The idea is that as the output voltage changes this is sensed and the input to the base of the output transistor is varied to oppose the change. With the advent of cheap integrated operational amplifiers it became easy to replace the sensing circuit with, say, a 741 and this gave very satisfactory control. An outline of such a circuit is shown in Fig. 5.

As the shunt circuit had this high output resistance plus poor efficiency, as all the current flowed through it continuously, the practice was to use a series output transistor—but this suffered from the short circuit trouble. To overcome this a means was devised to sense a short across the output and then to limit the current flowing through it, achieved as shown in Fig. 6.

All these refinements meant that the power supply unit was becoming quite large and complex so the manufacturers started to produce integrated circuits which combined the functions of regulation and protection in one package. One of these is the Signetics 550 which is a precision voltage regulator designed for general purpose use. It will work from input voltages of 8.5 volts to 50 volts making it ideal for amateur use. On its own it can supply an output of up to 150mA and if an external power transistor is added the current output can be increased to a number of amperes. It also features current limiting and continuously variable output.


★ components list

BR1	Bridge rectifier 500V PIV (RS REC65)
C1	2000µF 25V electrolytic
C2	470pF polyester
IC1	NE550A (IC8 Components)
N1	Miniature motor (RS)
R1	2.2k 1/4W
S1	2 pole mains output switch
T1	Transformer 240V/20V + 20V (RS)
Tr1	488245 (IC8 Components)
VR1	10k 500k wire wound potentiometer
VR2	Variable resistor, about 4k x 4k x 2"
Veroboard	0.1" pitch, about 4 1/2" x 1 1/2", to fit box.
	Red and black output terminals


USING THE 550

The 550 is available either as a 14-pin DIL or a 10-lead 'transistor type' can. The actual internal circuitry is complex having some 15 transistors, 7 diodes and 8 resistors in it. To understand its operation it may be better to look at a block diagram of its internal functions, Fig. 7.

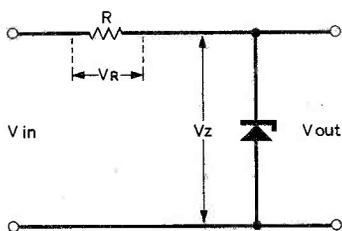
A reference voltage is produced of about 1.6 volts which is independent of supply variations, this being fed into the noninverting input of an operational




1 Zener supply

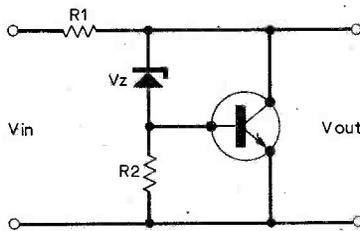


2 Shunt regulator

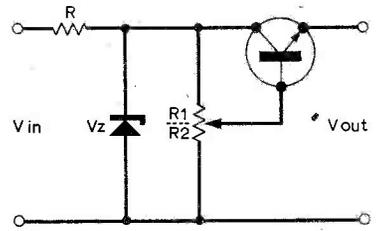


3 Series regulator

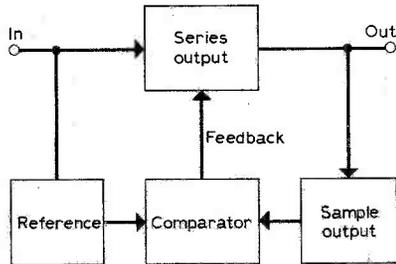

4 Feedback sensing

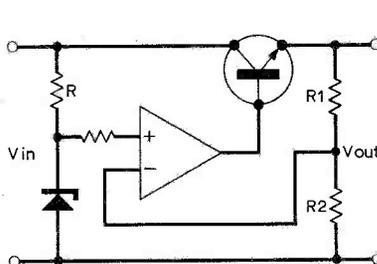


5 Op. amplifier stabiliser

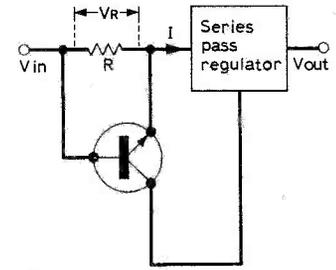

6 Current limiting

AM 0028

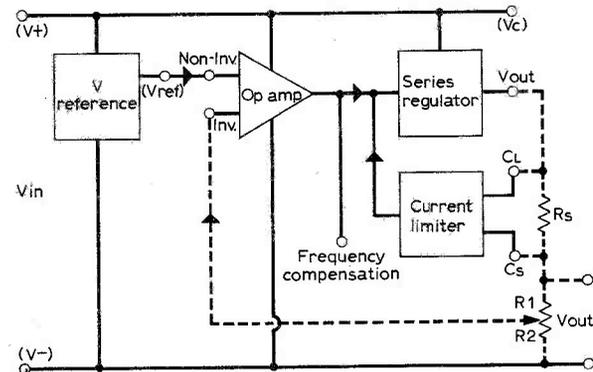


AM 0029

Wiring outside IC package shown dotted

Figs. 1 to 6, above, show the development of a simple zener circuit into one incorporating an IC operational amplifier providing greatly improved stabilisation and proof against short circuits by current limiting.

Fig. 7, left, is a block diagram of the functions performed by the 555 IC voltage regulator.

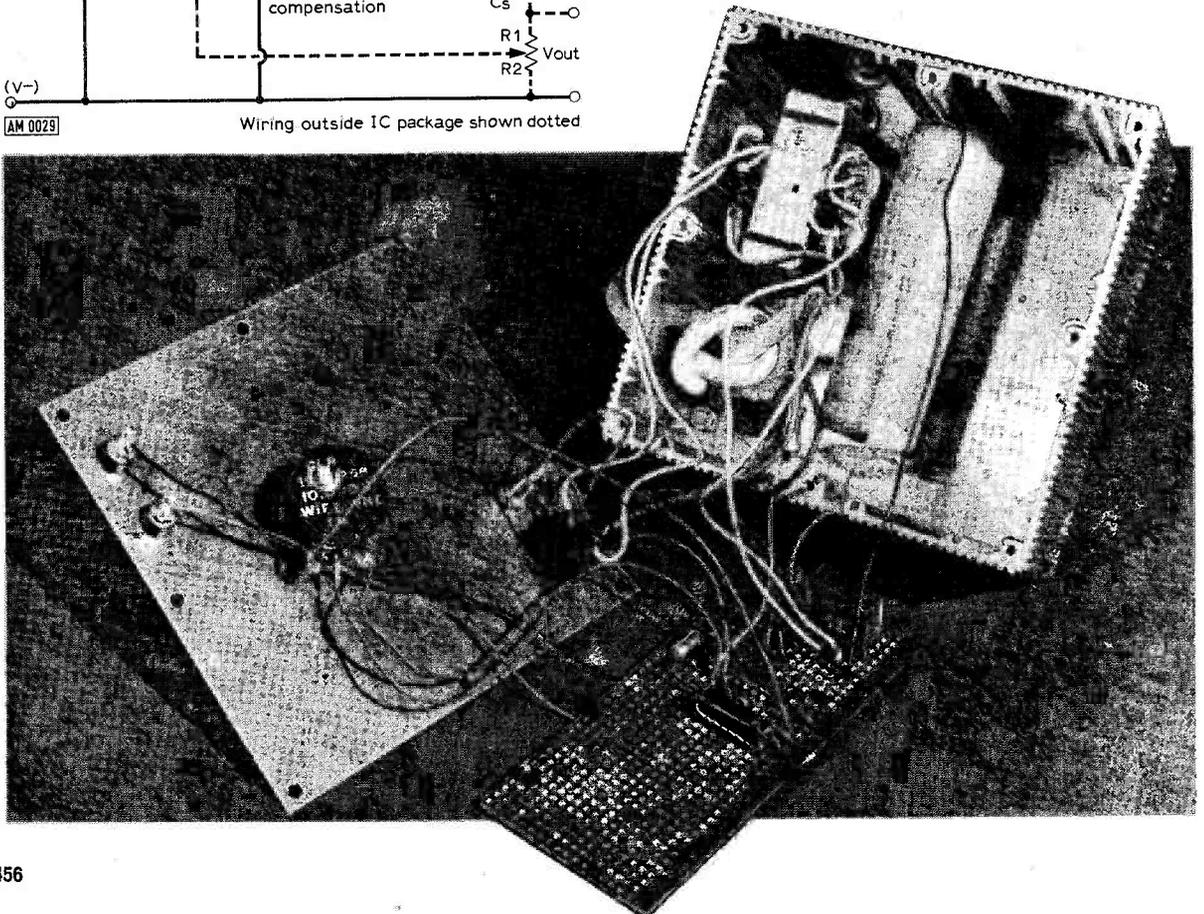The photograph below is of the author's prototype dismantled to show the veroboard carrying the IC and other small components. The board fits into the slots at the right of the box. The output is variable between 1.5 and 20V, current limited to 300mA.



More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. **BRANDED FROM TEXAS I.T.T. FAIRCHILD**



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
SN7400	0-20	0-18	0-16	SN7450	0-20	0-18	0-16	SN74145	1-50	1-40	1-30
SN7401	0-20	0-18	0-16	SN7451	0-20	0-18	0-16	SN74150	3-35	2-95	2-15
SN7402	0-20	0-18	0-16	SN7453	0-20	0-18	0-16	SN74151	1-10	0-95	0-80
SN7403	0-20	0-18	0-16	SN7454	0-20	0-18	0-16	SN74153	1-35	1-27	1-20
SN7404	0-20	0-18	0-16	SN7460	0-20	0-18	0-16	SN74154	2-00	1-75	1-50
SN7405	0-20	0-18	0-16	SN7470	0-30	0-27	0-25	SN74155	1-55	1-47	1-35
SN7406	0-30	0-27	0-25	SN7472	0-30	0-27	0-25	SN74156	1-55	1-47	1-35
SN7407	0-30	0-27	0-25	SN7473	0-40	0-37	0-35	SN74157	1-80	1-70	1-50
SN7408	0-30	0-27	0-25	SN7474	0-40	0-37	0-35	SN74160	2-60	2-40	2-25
SN7409	0-45	0-42	0-35	SN7475	0-55	0-50	0-50	SN74161	2-60	2-40	2-25
SN7410	0-45	0-42	0-35	SN7476	0-45	0-42	0-39	SN74162	3-40	3-25	3-20
SN7411	0-20	0-18	0-16	SN7477	0-75	0-70	0-65	SN74163	2-40	2-25	2-20
SN7412	0-42	0-40	0-35	SN7481	1-25	1-15	1-10	SN74164	2-75	2-60	2-10
SN7413	0-30	0-27	0-25	SN7482	0-87	0-80	0-70	SN74165	4-00	3-60	3-00
SN7416	0-30	0-27	0-25	SN7483	1-00	0-90	0-85	SN74166	4-00	3-60	3-00
SN7417	0-30	0-27	0-25	SN7484	0-80	0-85	0-80	SN74167	6-25	6-00	5-10
SN7420	0-20	0-18	0-16	SN7485	0-45	0-41	0-38	SN74170	4-10	3-65	3-05
SN7422	0-75	0-70	0-65	SN7487	0-45	0-41	0-38	SN74174	2-40	2-25	2-20
SN7423	0-48	0-44	0-40	SN7490	0-75	0-70	0-65	SN74175	3-55	3-27	3-15
SN7425	0-48	0-40	0-35	SN7491	0-75	0-70	0-65	SN74176	1-60	1-35	1-20
SN7427	0-42	0-39	0-35	SN7493	0-75	0-70	0-65	SN74177	1-60	1-35	1-20
SN7428	0-50	0-45	0-42	SN7494	0-80	0-75	0-70	SN74180	1-55	1-30	1-20
SN7430	0-20	0-18	0-16	SN7495	0-80	0-75	0-70	SN74181	7-00	6-00	5-50
SN7432	0-42	0-39	0-35	SN7496	1-00	0-97	0-95	SN74182	2-00	1-80	1-80
SN7433	0-65	0-61	0-54	SN7497	1-00	0-95	0-90	SN74184	2-60	2-25	1-30
SN7437	0-65	0-60	0-50	SN74100	2-50	2-30	2-00	SN74185A	2-40	2-00	1-80
SN7438	0-65	0-60	0-50	SN74104	1-45	1-38	1-20	SN74190	1-95	1-85	1-75
SN7440	0-20	0-18	0-16	SN74105	1-45	1-38	1-20	SN74191	1-95	1-85	1-75
SN7441AN	0-75	0-72	0-70	SN74107	0-50	0-45	0-40	SN74192	2-00	1-90	1-80
SN7442	0-75	0-72	0-70	SN74110	0-80	0-70	0-60	SN74193	2-00	1-90	1-80
SN7443	1-00	0-95	0-90	SN74118	1-00	0-95	0-90	SN74194	2-60	2-25	1-30
SN7445	2-00	1-75	1-60	SN74119	1-90	1-78	1-65	SN74195	1-85	1-70	1-60
SN7446	2-00	1-75	1-60	SN74121	0-60	0-55	0-50	SN74196	1-50	1-40	1-30
SN7447	1-75	1-60	1-45	SN74122	1-35	1-25	1-10	SN74197	1-50	1-40	1-30
SN7448	1-75	1-60	1-45	SN74123	2-70	2-55	2-47	SN74198	4-60	4-30	3-35
				SN74141	1-00	0-95	0-90	SN74199	4-60	4-30	3-35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SM 74 HOO } Now in stock - send for list No. 36
LOW POWER SM 74 LOO }

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AAV30 10p	BC147 12p	HU106 2-25	OC44 15p	TI843 35p	2N3055 55p
AAV42 15p	BC190C 12p	BY100 15p	OC45 15p	V405A 25p	2N3440 75p
AAZ13 10p	BC192 10p	BY128 15p	OC87 50p	BYX108 12p	2N3442 12p
ACR07 35p	BC214 15p	BY127 15p	OC71 15p	ZTX800 12p	2N3525 75p
ACI28 25p	BCY23 75p	BYZ13 35p	OC72 25p	ZTX801 15p	2N3514 55p
ACI27 25p	BCY34 35p	CI08D 85p	OC77 45p	ZTX809 15p	2N3615 75p
ACI28 25p	BCY39 1.00	GET111 55p	OC81 25p	ZTX841 20p	2N3702 10p
ACI76 25p	BCY42 30p	GET115 55p	OC82 25p	ZTX600 15p	2N3704 10p
ACI87 25p	BCY43 25p	GET880 45p	OC140 55p	ZTX603 17p	2N3705 10p
ACI89 25p	BCY65 2-50	LM309 3p	OC170 25p	2G301 25p	2N3714 1-80
ACY17 30p	BCY70 15p	(TO9) 1-87	OC171 30p	2N404 20p	2N3771 1-75
ACY30 25p	BCY71 20p	MJE21 25p	OC20 45p	2N421 25p	2N3773 2-00
ACY21 20p	BCY72 15p	MJE340 50p	OC201 75p	2N696 15p	2N3790 2-25
ACY39 55p	BCY87 2-99	MJE370 70p	OC202 80p	2N697 15p	2N3819 35p
AD140 50p	BCZ11 50p	MJE520 70p	OC303 50p	2N706 10p	2N3820 50p
AD149 50p	BD124 30p	MJE2955 1-10	OC771 1-25	2N930 20p	2N3866 85p
AD161 35p	BD131 75p	MJE3055 1-10	ORF12 50p	2N987 45p	2N3903 15p
AD162 35p	BD132 30p	MJE3055 1-10	ORP60 40p	2N131 25p	2N3904 15p
AF117 20p	BF115 25p	MJE3055 1-10	P346A 20p	2N132 25p	2N4061 12p
AF118 20p	BF167 25p	MJE3055 1-10	RAS310AF 45p	2N1302 18p	2N4062 12p
AF124 25p	BF173 25p	NKT214 20p	RAS508AF 45p	2N1304 22p	2N4128 15p
AF139 30p	BF179 30p	NKT216 40p	RAS508AF 45p	2N1305 22p	2N4871 35p
AF182 40p	BF180 30p	NKT217 40p	RAS508AF 45p	2N1307 20p	2N5457 30p
AF239 40p	BF194 15p	NKT403 70p	RAS508AF 45p	2N1308 25p	2N5777 55p
ASV27 30p	BF196 15p	NKT404 50p	TA A863 75p	2N1619 25p	2N5901 1-00
ASV28 25p	BFS61 25p	OA5 50p	TIP29A 50p	2N1671 1-00	2S012 10-00
BA102 30p	BFS98 25p	OA10 35p	TIP30A 60p	2N147 75p	2S018 6-25
BA115 7p	BFX13 25p	OA81 10p	TIP31A 60p	2N2100 50p	2S026 8-90
BA145 15p	BFX34 75p	OA91 7p	TIP32A 70p	2N2217 25p	2S301 50p
BAX13 5p	BFX37 30p	OA290 7p	TIP33A 30p	2N2221 20p	2S303 65p
BAK18 7p	BFX38 20p	OA292 25p	TIP33A 1-00	2N2222A 1-00	2S322 95p
BC107 30p	BFY50 20p	OC16 75p	TIP34A 1-50	2N2369A 1-50	40620 50p
BC108 10p	BFY51 20p	OC20 85p	TIP35A 1-50	2N2906 20p	40621 40p
BC109 10p	BFY52 20p	OC23 85p	TIP35A 1-50	2N2926 (all) 40p	40622 50p
BC109C 12p	BFY64 50p	OC25 40p	TIP36A 2-50	2N2926 (all) 40p	40623 65p
BCI13 15p	BY90 85p	OC28 65p	TIP36A 2-50	2N2926 (all) 40p	40624 50p
BCI14 15p	BY93 8-00	OC35 50p	TIP41A 75p	2N2926 (all) 40p	40626 75p
BCI17 20p	BSX20 15p	OC36 55p	TIP42A 85p	2N2926 (all) 40p	40636 1-10
BCI43 35p	BSY27 15p	OC42 45p		2N2926 (all) 40p	40430 1-00

QUANTITY DISCOUNTS

10% 12+ ; 15% 25+ ; ANY ONE TYPE
20% 100+ ; 25% 250+ ;

From above sections except Integrated Circuits and Special Orders where discounts are included.

Minimum order value \$1 please. Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	2N2926
1000 MC/S	All Colours
25 + 50p	25 + 9p
100 + 45p	100 + 8p
500 + 40p	500 + 6p
	1000 + 5p
AF117 Mullard 25p	2N3819 Texas 35p
25 + 17p	25 + 30p
100 + 15p	100 + 25p
500 + 12p	500 + 20p
	1000 + 15p
OC170 Mullard 25p	BC107, BC108, BC109 I.O.L. each
25 + 20p	All Makes
100 + 18p	25 + 9p
500 + 15p	100 + 7p
1000 + 13p	500 + 6p
	1000 + 5p
BY127 Mullard 15p	AD161, AD162 35p each
25 + 12p	25 + 32p
100 + 10p	100 + 28p
500 + 9p	500 + 25p
1000 + 8p	1000 + 22p
OA202 10p	2N3053 20p
25 + 8p	25 + 18p
100 + 7p	100 + 15p
500 + 6p	500 + 12p
1000 + 5p	1000 + 10p
OC35 Mullard 50p	2N3055 55p
25 + 45p	25 + 50p
100 + 40p	100 + 45p
500 + 35p	500 + 38p
1000 + 30p	1000 + 33p

ZENER DIODES

400 M/W 5% Miniature
BZY 88 Range
All voltages
3-3 - 33 Volt
10p each.

25 + 8p	100 + 8p	500 + 6.5p	1000 + 5p
---------	----------	------------	-----------

Any one type.

1/4 Watt 5% Wire Ends Metal Case
All voltages
6-8 - 100 Volts
20p each

25 + 18p	100 + 10p	500 + 12p	1000 + 10p
----------	-----------	-----------	------------

Any one type.

LINEAR (O/P AMPS)

709C	TO5	75p
709C	TO99	35p
709C	D.I.L.	35p
723C	TO99	£1.00
723C	D.I.L.	85p
723C	TO99	£2.50
741C	TO99	65p
741C	D.I.L.	55p
747C	TO99	£1.10
747C	D.I.L.	£1.10

72741F D.I.L. 60p
72748F D.I.L. 60p
72748F TO99 65p
IC12 £1.80

TOSHIBA TH0013F
20 WATT AMP
All voltages
£4.47 Post PAID
TH0014F 55p £1.50

DATA AND CIRCUITS REF. 42 10p

FREE WITH PURCHASES

TRANSISTORS, IC's, TRIACS, BRIDGES, SCR's, LDR's

3 Watt Plastic Wire Ends 5% All Voltage
6-8 - 100 Volts
30p each.

SILICON RECTIFIERS WIRE ENDED PLASTIC

Type	P.I.V.1-11
1 amp miniature	
IN4001	50 6
IN4002	100 7
IN4003	200 8
IN4004	400 8
IN4005	600 10
IN4006	800 12
IN4007	1000 15
1.5 amp miniature	
PL4001	50 8
PL4002	100 9
PL4003	200 10
PL4004	400 10
PL4005	600 12
PL4006	800 15
PL4007	1000 16

NEW FREE BOOKLET (No. 36) OVER 1500 TYPES - Send for yours today!

PLESSEY INTEGRATED CIRCUIT
3 Watt Amplifier SL403D
Complete with 8-page booklet, circuits and data
£1.50 each

TRIACS

ESSENTIAL BOOKS FOR RADIO AMATEURS

A GUIDE TO AMATEUR RADIO

by Pat Hawker G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.

90p post paid

VHF-UHF MANUAL

by G. R. Jessop, CEng, MIERE G6JP

Transmitters, receivers and test equipment for use at vhf and uhf are fully covered on a practical basis, from basic information to selection of designs.

£1.80 post paid

AMATEUR RADIO TECHNIQUES

by Pat Hawker G3VA

4th Edn. 256 pages.

A source book for many useful circuits and aerials. An ideas book aimed at extending the reader's awareness of new devices and techniques.

£1.80 post paid

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's UK origin ensures easy availability of components. Complete coverage of technical and constructional fields.

£4.10 post paid


These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send s.a.e. for complete list

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688




SUPERSOUND 13 HI-FI MONO AMPLIFIER

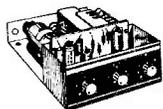

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz ± 3 db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, esoutehon panel, input and output plugs. Overall size 8" high x 6" wide x 7 1/2" deep. AC 200/250V. P. & P.

PRICE £11.60 25p.

DE LUXE STEREO AMPLIFIER

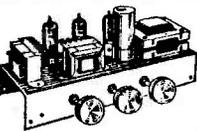

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 3 x ECL86 Triode Pentodes, 1 x E230 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "Balance" control fitted at the rear of the chassis. Input sensitivity is approximately 30mV for full peak output of 4 watts per channel (8 watts mono) into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 6". Ready built & tested to a high standard. PRICE £9.90 P. & P. 45p.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 6100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). NOW ONLY £4.95 P. & P. 35p.

SPECIAL OFFER! HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance. OUR PRICE £9.25. Carr. 70p. Cabinet Available Separately £4.95. Carr. 65p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £7.15. Carr. 70p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. P. & P. 35p. BARGAIN PRICE £3.30


SPECIAL OFFER! LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS

With large ceramic magnet and plasticised cone surround. 8 ohm impedance. P.&P. £2.70 25p.



10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E230 rectifier. Simple instruction booklet 15p + SAE (Free with parts). All parts sold separately. ONLY £8.80 P. & P. 50p. Also available ready built and tested £12.10 P. & P. 60p.

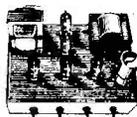

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



New further improved model with higher output and incorporating high quality ready drilled fibre glass printed circuit board with component identification clearly marked for even easier construction.

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre-glass printed circuit board, snare brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: ± 3 dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: ± 3 dB 12-15,000 Hz. Bass boost approx. to ± 12 dB. Treble cut approx. to -16 dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size: 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 15p plus large S.A.E. AMPLIFIER KIT £11.55 P. & P. 15p (Magnetic input components 33p extra) POWER PACK KIT £3.30 P. & P. 33p CABINET £3.20 P. & P. 33p (Post Free if all units purchased at same time)

Also available ready built and tested £23.10. Post Free

QUALITY RECORD PLAYER AMPLIFIER MK. II. A top quality record player amplifier employing heavy duty double wound mains transformer. ECC83, EL54, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £4.40 P. & P. 40p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £5.85 P. & P. 50p.

Open 9-5.30 Monday to Friday, 9-5 Saturday. Early closing Wed. 1 p.m. A few minutes from South Wimbledon Tube Station.

PRICES NOW INCLUDE VAT

HARVERSON SURPLUS CO. LTD.

(DEPT. PW) 170 HIGH ST., MERTON, LONDON, S.W. 19 Tel: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRES

(Please write clearly) PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

amplifier. The inverting input gets its voltage from a potentiometer across the output. The op. amp. senses any change between these two voltages and the output is controlled accordingly. There is also the current limiting part which monitors the voltage developed across an external resistor. When this voltage exceeds a specified value limiting starts, the output voltage starts to fall until the output transistor is switched off, the current remaining at a safe level which is within the capabilities of the IC.

HIGHER CURRENTS

If more than 100mA or so is required all that need be added is a single NPN external power transistor as shown in Fig. 9, which is also the complete circuit of the practical unit.

The max current then available is given by:—

$$I_{max} = I_{limiting} \times h_{FE(min)}$$

For a 2N3055 whose $h_{FE(min)}$ is about 50 the maximum current which can be obtained is 3 amps assuming that one is keeping to an output current of 60mA from the IC. If this is uprated to 100mA then the current is 5 amps.

In order to calculate the value of R_s the following formula is used:—

$$R_s = \frac{0.6}{I_l}$$

Where I_l is the current at which limiting is to start. The wattage rating for the resistor R_s is given by $W = 0.6 \times I_l$.

Thus, in the prototype, the limiting current I_l was set at 300mA which meant that R_s had a calculated value of 2 ohms and a power rating of 0.18 watts. In point of fact the only available resistor of about this value was a 2.2 ohm 3 watt one, so this was used.

ALTERNATIVE TRANSISTORS

There is no need to use a 2N3055 if lower powers are anticipated. In fact almost any silicon NPN power transistor will do provided that its current rating is about twice the expected maximum. Its V_{CE0} should be about $1\frac{1}{2}$ times the maximum unregulated input voltage and the power rating is calculated by:—

$$W = (V_{in(unreg)} - V_{out(max)}) \times I_l$$

CONSTRUCTION

The IC is best mounted on 0.1" matrix veroboard together with R_s and C_1 , and also $VR1$ if this is to be a preset. Should an external transistor be needed then this should go on a heat sink together with the rectifier. The case size will depend on the size of transformer used; a suitable case can be found from the

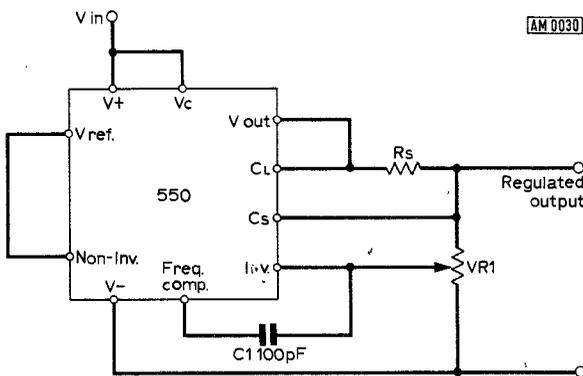


Fig. 8. External circuitry of the 555 to provide currents up to about 60mA from 2 to 20V.

Fig. 8 shows the IC connected for use as a power supply unit to give 2 to 20 volts at a maximum current of 60mA. R_s is chosen to be 10 ohms so that it will limit if the output current should exceed 60mA. If R_s is increased to say 20 ohms the limiting current now drops to about 30mA. If R_s is decreased to 5 ohms the current is increased to about 100mA. Care must be taken not to reduce the value too far or the short-circuit current could exceed 150mA. It is possible to replace R_s by a preset to give adjustable current limiting. The potentiometer $VR1$ is connected so that the output voltage can be adjusted. C_1 is added to provide frequency compensation.

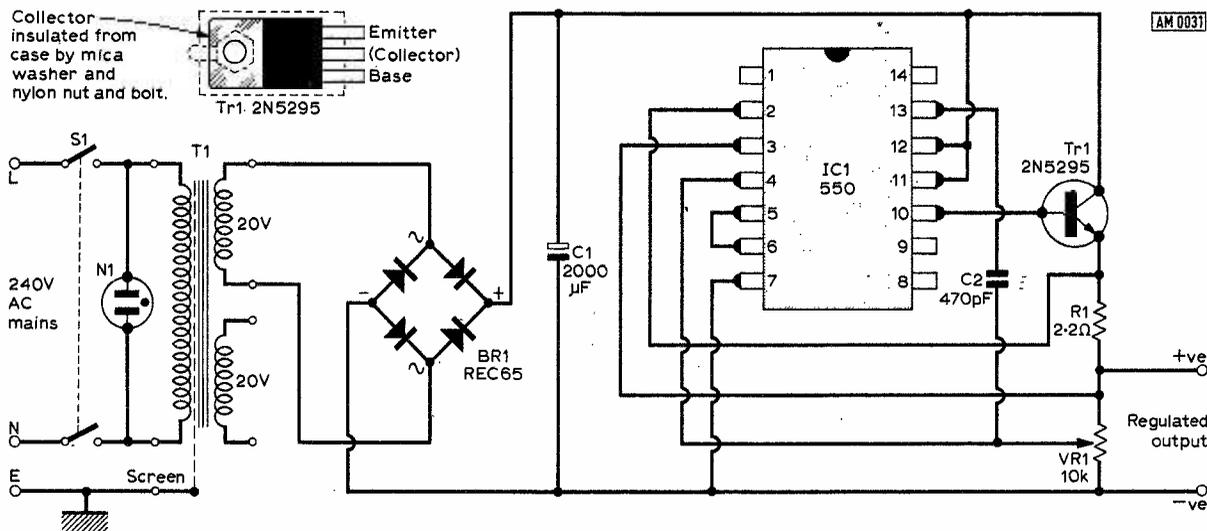


Fig. 9. Complete circuit of the prototype power supply module. The value of R_1 for different output current ratings is discussed in the text.

Why pay more - look at our Fantastic Bargain Offer!

PENTHOUSE

A COMPLETE AUDIO SYSTEM

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder. 4 wavebands Long/Medium/Short/VHF. 8 watts per channel (music power) output. The latest BSR CI29 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.

OUR PRICE £55-00




Credit terms £5-00 deposit plus £2-00 p. & p. followed by 12 payments of £4-80. Total Credit Terms £62-60 SEND £7-00 TODAY.

BENSON

BENSON MW/FM/MPX STEREO 8 TRACK


AM/FM radio with decoder for stereo radio with integral 8 track cartridge player. Portable for operation from internal batteries or A.C. mains or 12V Car/Boat cigar lighter socket. Unit divides into two for stereo reproduction.

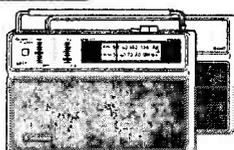Our price £39-95. Credit terms £5-00 deposit plus 12 monthly payments of £3-40 (Total £45-80), p. and p. £1-00. Send £6 Today!



UNIT DIVIDES TO GIVE 2 SEPARATE STEREO SPEAKERS

THE AVON AUDIO SYSTEM

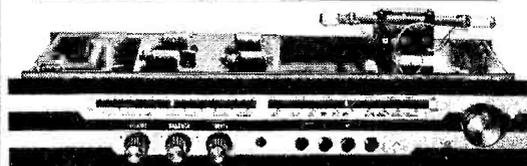

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.


BSR 4 SPEED STEREO/MONO RECORD CHANGER plays all types or 7in., 10in., and 12in. Mono of Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45-74. OUR PRICE £35-00. Credit Terms £3-50

deposit plus £2 Post & Packing followed by 12 payments of £3-10 (Total Credit Terms £40-70) Don't miss this bargain.

SEND £5-50 TODAY

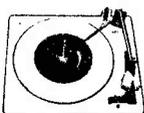

ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

Please send me free details of your range

Name

Address


PW 9/73

LEWIS radio

100, Chase Side London N.14
Tel: 01-886 3733/9666

Post coupon NOW for...
FREE
leaflets


Verobox range and this will make an elegant container. VR1 can be fitted with a suitable pointer and calibrated.

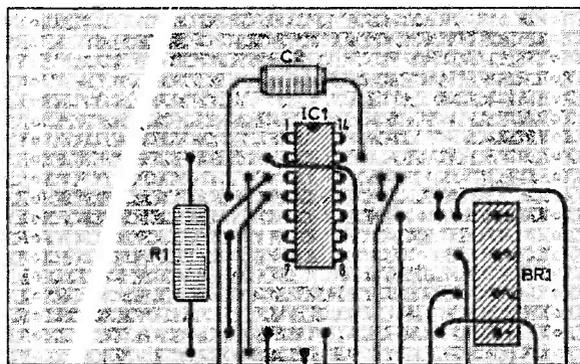

AM 0032

Fig. 10 Layout of components on the strip of veroboard.

It should be noted, with reference to the formulae previously given, that this is not a linear scale and tends to become cramped at the top end. This means that it is better to preset the value or use a voltmeter across the output terminals. The control can then be mounted on the top panel together with a mains switch, neon and output terminals. The circuit of the completed unit is shown in Fig. 9, with the veroboard layout in Fig. 10.

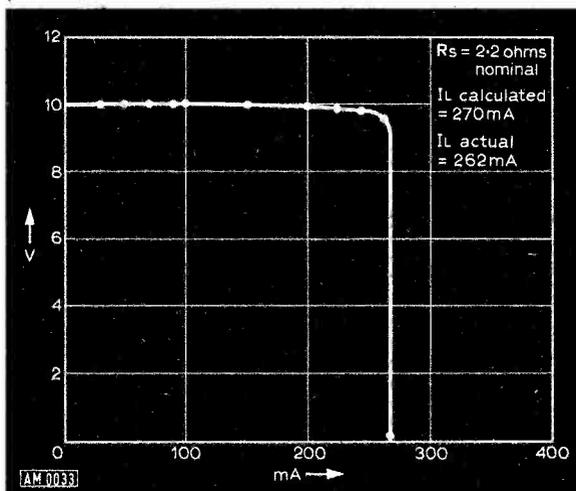

On test the module's output voltage was set to 10V and the load current increased until limiting occurred, as shown by this graph.

It was found that a residual ripple on the output could be eliminated by adding a 100µF capacitor across the output terminals. This also helped to remove some RF noise that was present.

The 550A (DIL) costs 88p and the 550L (10-lead) is 93p inclusive of VAT and post and packing and can be obtained from SCS Components, POB 26, Wembley, Middx. The 2N5295 is also available from SCS at 68p inc.

WGS GWSMITH & CO (RADIO) LTD

AUDIOTRONIC MODEL ATM.1

Top value 1000 o.p.v. pocket multimeter. Ranges: 0/10/50/250/1000V. AC and DC. DC Current 0-1mA/100mA. Resistance 0/150k ohms. Decibels -10 to +22dB. Size 80 x 60 x 25mm. Complete with test leads. £2-50. Post 15p.



LT601 MULTIMETER

New style 20,000 o.p.v. pocket multimeter. Ranges: 5/25/50/250/500/2500 V. D.C. 0/50/100/600/1000V. A.C. 50μA/250mA. 6K/6 meg ohms. -20 to +22 dB. £8-75. Post 20p.



MODEL TH-12

20,000 o.p.v. Overload protection. Slide switch selector 0/25/250/10/50/250/1000V. D.C. 0/10/50/250/1000V. A.C. 0/50μA/25/250mA. D.C. 0/3K/30K/300K/3 meg -20 to +50dB £4-97. Post 15p.



RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 25/10/250/500/1000V. D.C. 2-5/10/50/250/500/1000V. A.C. DC Current 100mA/1/10/100mA/1A. Resistance 800 ohms/3/30/300K/3m Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £25-97. P. & P. 25p



MODEL PL436

20k Ω/Volt D.C. 8k Ω/Volt A.C. Mirror scale. Ranges: 0/5/12/30/120/600 V. D.C. 0/3/30/120/600 V. A.C. 50/800μA/1Meg/600 mA. 10/100K/1 Meg/10 Meg Ω -20 to +46db. £8-97. P. & P. 12p.



MODEL 500

80,000 O.P.V. with overload protection mirror scale 0/5/25/10/25/100/250/500/1,000V. D.C. 0/2/5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/80K/6 Meg. £9-95. Post paid. Leather Case £1-75



U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 607 o.p.v. 0/3/15/75/300/600/1200/2000/5000 VDC and 75mV. A.C. 0/3/15/75/300/600/1500/3000/6000/9000 VAC. 0/300μA/1.5/6/15/60/150/300mA/1.5/6 AMP. A.C. 0/1.5/6/15/60/150/300mA/1.5/6 AMP. A.C. 0/200 Ω/3K/30K Ω. Accuracy DC 1%. AC 1-5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-50. P. & P. 25p.



HIOKI MODEL 70X

100,000 O.P.V. Overload protection. Mirror scale. -3/6/1-2/1-5/3/6/12/30/60/120/600/3000/12000 V. 1-5/3/6/12/30/60/150/300/600 1200 V. A.C. 15/30μA/3/6/30/60/150/300mA 6/12 AMP. DC. 2K/200K/2 Meg/20 Meg ohm -20 to +63dB. £13-50. P. & P. 20p



MODEL C-7080 EN

Giant 6" mirror scale. 20,000 o.p.v. 0/25/1/2-5/10/50/250/1000/5000V. D.C. 0/25/10/50/250/1000/5000V. A.C. 0/25/10/50/250/1000/5000μA/1/10/50/250mA/10 amp. D.C. 0/2K/200K/20 meg -20 to +50 dB. £13-95. Post 35p.



All prices are inclusive of

10% VAT

370 WTR MULTI-METER

Features A.C. current ranges. 0/0.5/5/10/50/100/500/1000 V. D.C. 0/2/5/10/50/250/500/1000V AC 0/50μA/1/10/100mA/1/10 Amp D.C. 0/100mA/1/10 Amp AC 0/5K/50K/500K/5 MEG/50 MEG. -20 +62db. £15. P. & P. 25p.



KAMODEN 72.200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/10/5/3/30/120/600/1200V. D.C. 0/3/12/60/300/11,200V. A.C. 0/6μA/1.2mA/120mA/600mA/12A. D.C. 0/12A. A.C. -20 to +63dB. 0/2K/200K/2 meg/200 meg ohms. £16-95. Post 30p.



TMK LAB TESTER.

100,000 O.P.V. 6 1/2in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K/ Volt A.C. D.C. Volts: 5-2.5-10-50-250-1,000 V. A.C. Volts: 3, 10, 25, 50, 250, 500, 1,000V. D.C. Current: 10, 100μA, 10, 100, 500mA, 2-5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG Ω. Decibels: -10 to +49 dB. Plastic Case with Carrying Handle. Size: 7 1/2in. x 6 1/2in. x 3 1/2in. £18-95. P. & P. 25p.




Model S-100TR MULTIMETER/ TRANSISTOR TESTER

100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V AC. 0/12/600μA/12/300mA/12 AMP DC. 0/10 K/1 MEG/100MEG. -20 to +50db. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £13-50. P/P 25p.



KAMODEN HM.350 TRANSISTOR TESTER

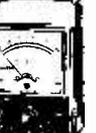High quality instrument to test Reverse leak current and DC current. Amplification factor of NPN, PNP, transistors, diodes. SCR's etc. 4" x 4" clear scale meter. Operates from 6000mAh batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.



MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta in / out. Checks Iobo. Checks diodes in / out. Checks SCR, etc. Beta HI 10 - 500. LO 2 - 50. Iobo 0-5000μA. 220/240 V A.C. operation £17-50. Post 25p.



LB3 TRANSISTOR TESTER

Tests ION and B. PNP / NPN. Operates from 9V battery. Complete with all instructions, etc. £3-95. P. & P. 20p.



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5v batteries. Complete with all instructions, etc. £4-50. P. & P. 20p.



TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/1/002/1/3/10/30/100/300V. R.M.S. 4cps-1.2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17-50. Carr. 25p.



TE-65 VALVE VOLTMETER

28 range D.C. current ranges 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17-50. P. & P. 30p. Additional probes available: R.F. £2-12 1/2; H.V. £2-50.



KAMODEN HM. 720B F.E.T. V.O.M.

Input impedance 10 meg ohms. Ranges: 0/25/1/1/2/5/10/50/250/1000V. D.C. 0/2.5/10/50/250/1000V. A.C. 0/25μA/2.5/5/25/250 MA. D.C. -20 to +62dB 0/5K/80K/500K/5 meg 500meg ohms. £41-95. Post 30p



TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0-3-1200V AC 0-25μA-2-5-20-50V RMS. 8-0-800V P-P. DC CURRENT 12-12MA. Resistance up to 2000M ohm. Decibels -20 to +51dB. Complete with leads/instructions. £17-50. P. & P. 20p.



MODEL L-55 FET V.O.M.

Input impedance 10 meg ohms. 0/-3/1-2/6/30/120/800V. D.C. 0/3/12/60/120/600V. A.C. 0/120μA/12mA/100μA/0/1K/100K/10 meg/100 meg ohms £15-97. Post 15p.



KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1000 Meg-ohms. 500 Volt. Battery operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, instructions. £19-95. Post 30p



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt AC and DC. Accuracy 5% D.C. 1% AC. Scale length 160mm. 0/300/750μA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/AMP DC 0/3/7.5/15/30/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out. Supplied complete with test leads, manual and test certificates. £49-00. Post 50p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C. OSCILLATOR

Size 18 x 200,000 Hz; Square 18 x 50,000 Hz Output max. +10 dB. (10 K ohms) Imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps 300 kHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 10 1/2lb. 220/240V. A.C. Supplied brand new with handbook. £47-50. Carr. 50p.




TO-3 PORTABLE OSCILLOSCOPE

3in. tube, V amp. Sensitivity 0.1v p-p/C.M. Bandwidth 1-5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/C.M. Bandwidth 1-cps-800KHz. Imp. imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps 300 kHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 10 1/2lb. 220/240V. A.C. Supplied brand new with handbook. £47-50. Carr. 50p.



CI-5 PULSE OSCILLOSCOPE

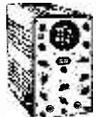For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz VRMS/mm. -1.25; HOR. AMP. Bandwidth 500KHz. Sensitivity at 100KHz, V RMS/mm. -3.25; Preset triggered sweep 1-5,000μsec.; free running 20-200,000Hz in nine ranges. Calibrator dpps. 220 x 350 x 430mm. 115-230V. AC operation. £39-00. Carr. paid.




RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular fin. x 4in. C.R.T. Calibrated triggered sweep from 2 μsec. to 100 milli-sec. per cm. Free running time base 50 c/s-1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual £87. Carr. Paid.



MODEL AT201 DECADE ATTENUATOR

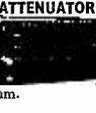Frequency range 0-200KHz. Attenuator 0-11db, 0.1db step. Impedance 600 ohms. Max. input power 300mW. Size 180 x 90 x 55mm. £12-50. Post 37p.



ARF-300 AF/Rf SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine / square 10v. P-P. RF 100 KHz to 200 MHz. Output 200mW maximum. Operation 220/240V. A.C. Complete with instructions and leads. £29-95. Post 50p.



MODEL TE.15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440Kc/s-280Mc/s. 4 coils. 500μA Meter. 9V battery operation. Size 180 x 80 x 40mm. £15-00. Post 20p.



TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covers 120 Kc/s 500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions £17-50. Carr. 37p. Size 140 x 215 x 170 mm.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Size: 20cps to 200 Kc/s on 4 bands. Square: 20cps to 30 Kc/s. Output impedance 5,000 ohms. 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. £17-50. Carr. 37p.



AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.

80 W	£2-10	P. & P. 18p
150 W	£2-70	P. & P. 18p
300 W	£3-80	P. & P. 23p
500 W	£5-25	P. & P. 38p
1000 W	£7-50	P. & P. 35p
1500 W	£10-90	P. & P. 43p
2250 W	£17-95	P. & P. 50p
5000 W	£35-00	P. & P. 21

MGA. 220 AUTOMATIC VOLTAGE STABILISER

Input 88 125 VAC or 176, 250VAC. Output 120VAC or 240VAC. 200VA rating. £11-97. Carr. 50p.




GWS G.W. SMITH & CO (RADIO) LTD

UNR 30 RECEIVER




4 Bands covering 550 kc/s-30 mc/s B.F.O. Built-in Speaker 220/240 v. A.C. Brand new with instructions.
Our Price £15-75 Carr. 37p

UR-1A RECEIVER

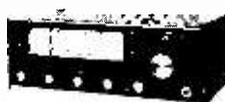

4 Bands covering 550 kc/s-30 mc/s FET, 8 Meter. Variable BFO for SSB. Built-in Speaker, Bandspread, Sensitivity Control. 220/240 v. A.C. or 12 v. D.C. 12 1/2 in. x 4 1/2 in. x 7 1/2 in. Brand new with instructions.
Our Price £25-00 Carr. 37p

SKYWOOD CX203 RECEIVER

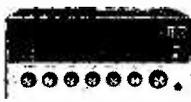

Solid state, 5 bands covering 200-420 KHz and .55 to 30 MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO, AVC, ANL, "S" meter. AM/GW/SSB. Integrated speaker and phone socket. 220/240 v. A.C. or 12 v. D.C. Size 325 x 286 x 150 mm. Complete with instructions and circuit.
Our Price £32-50 Carr. 50p

LAFAYETTE HA-600 RECEIVER



General coverage 150-400 kc/s, 550 kc/s-30 mc/s, FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter Bandspread, RF Gain, 15in. x 9 1/2 in. x 8 1/2 in. 18 lb. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.
Our Price £50-00 Carr. 50p

TRIO 9R59DS RECEIVER



4 bands covering 550 kc/s to 30 mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-GW, ANL, Variable BFO, S meter. Sep. bandspread dial. IF frequency 445 kc/s, audio output 1.5w. Variable RF and AF gain controls 115/250 v. A.C. Size: 7in. x 3 1/2 in. x 10in. with instruction manual.
Our Price £49-50 Carr. Paid. FULL RANGE OF TRIO STOCKED



EMI LOUDSPEAKERS



Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 37p.
 Model 450. 13" x 9" with twin tweeter/crossover. 55-18,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £8-82 each. P. & P. 25p.



SPECIAL OFFER! STEREO SPEAKERS
 Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2" x 9" x 7 1/2". 8 ohms x 8 watt RMS. 16 watt peak. Complete with DIN lead.
Our Price £12-95 Carr. 50p

HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5kVU/100mV. Output 50mW.
Our Price £6-97 P. & P. 15p

1021 STEREO LISTENING STATION




For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2".
Our Price £2-25 P. & P. 15p

MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs: Mic: 3 x 3mV 50K. 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.
Our Price £8-97 P. & P. 20p

EA.41 REVERBERATION AMPLIFIER

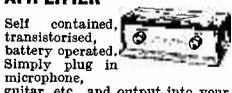

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 4 1/2 x 3 x 4 1/2 in.
Our Price £7-50 P. & P. 15p

AUDIOTRONIC

RANGE OF HIGH QUALITY EQUIPMENT


Audiotronic Products are manufactured exclusively for the Audiotronic Group of Companies and as a member of the group we are pleased to offer you this fabulous range of high quality equipment. Made to our own specifications each item provides outstanding performance and reliability at a value for money price!

ACD.660 Stereo Cassette Deck




A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter normal/chrome tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/DIN line input sockets, 3.5mm mike input sockets etc. Frequency response 100-8KHz (100-12KHz Cr2) S/N-45dB. Crosstalk 45dB. Separation-35dB. Noise Limiter-6dB at 10KHz. Complete with phono connecting leads.
Our Price £39-50 Carr. & Ins. 50p

AHP-8D 8 Track Stereo Tape Deck

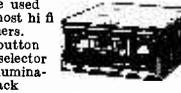

Can be used with most hi fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. A.C. 220/240v.
Our Price £11-95 P. & P. 50p.

APH-8A 8 Track Stereo Tape Player

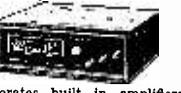

Incorporates built in amplifiers giving 2 1/2 watts rms output. Push button track selector, illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. A.C. 220/240v.
Our Price £17-25 P. & P. 50p.

Stereo Headphones

- LSH.20 Individual volume controls Stereo mono switch 8 ohms. 40-19,000 Hz. £3-50 P & P 30p
- LSH.30 Open back type. Individual tone and volume controls. 8 ohms. 30-20,000 Hz. £5-50 P & P 30p
- LSH.40 Two way speaker system. Individual volume controls. 8 ohms. 20-20,000 Hz. £6-95 P & P 30p
- LSH.60 3" speaker units. 8 ohms. 20-20,000 Hz. Complete with zipped carrying case. £8-50 P & P 30p
- LQH.400 4-channel dynamic head. phones. Each ear-piece has 4 drive units. 4-32 ohms. 20-20,000 Hz. £9-95 P & P 30p
- LSH.50 Electrostatic with self powered energiser and control unit with headphone/speaker selector. 4-32 ohms. 20-24,000 Hz. £15-95 P & P 30p

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS


Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16 1/2" x 8" x 2 1/2". AC 200/250v



PROCESS FOUR
 For use with semi-professional tape recorders. Freq. res. 30Hz-20KHz ± 2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.
Our Price £50-00 P & P 50p

PROCESS TWO
 For use with cassette and tape recorders. Freq. res. 30Hz-20KHz ± 2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.
Our Price £34-50 P & P 50p

ACR.14 Battery Mains Cassette Recorder

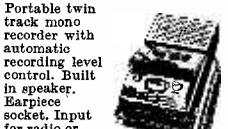

Portable twin track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. A.C. 220/240v or 6v DC operation. Complete with remote control microphone, mains lead, earpiece and batteries.
Our Price £10-50 P. & P. 50p.

LOW NOISE TAPE CASSETTES

TYPE	5	10	25	Cassette
C80	£1.29	£2.83	£5.99	Tape Head
C90	£1.85	£3.82	£8.59	Cleaner 30p
C120	£2.29	£4.48	£10.83	

P. & P. 15p. post free

ACR 3500 CAR RADIO



Manual tuning of Medium and Long waves. 12v pos, or neg, earth. Complete with speaker, mounting brackets and instructions.
Our Price £6-50 P & P 50p

ACP.8 8 TRACK CAR PLAYER



12v neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp, with speakers, mounting brackets and instructions.
Our Price £12-50 P & P 40p

AMR-900 GLOBAL AM/FM PORTABLE RADIO



10 wavebands covering AM: 535-1605 KHz, LW: 150-380 KHz, MB 1.6-4.00 MHz, SW1: 4.0-8 MHz, SW2: 8.0-1.6 MHz, SW3: 16-24 MHz, PSB1: 30-50 MHz, PSB2: 143-174 MHz, FM 88-108 MHz, AIR: 108-136 MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC or FM. 6" x 4" speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm.
Our Price £36-00 P. & P. 50p.

FR.1000 SPORTSMAN AM/FM PORTABLE RADIO



5 wavebands covering AM 535-1665KHz. FM 88-108KHz. AIR 108-135MHz. PB 147-174MHz. V.B. 162, 5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for FM and built in ferrite bar for AM. AFC. 3in. speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 152 x 79 x 219mm. Battery/mains operation. **Our Price £11-50** P. & P. 35p.

AUDIOTRONIC AMB.500 MULTIBAND RADIO




5 wavebands covering MW 535-1605KHz and FM 88-175MHz. All transistor. Battery or mains operation. Built in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.
Our Price £6-95 P & P 35p

ACRI PUSHBUTTON CAR RADIO



Push button tuning of one LW and five MW stations of your choice. 12v pos, or neg, earth. Complete with speaker, mounting brackets and instructions.
Our Price £8-95 P & P 50p

ACASE ELECTRIC CAR AERIAL

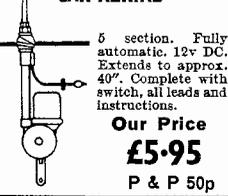

5 section. Fully automatic. 12v DC. Extends to approx. 40". Complete with switch, all leads and instructions.
Our Price £5-95 P & P 50p

SAVE UP TO 33 1/3% OR MORE! GWS

SUPER AKAI HIFI BARGAINS

CS35 STEREO CASSETTE RECORDER

For conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-16kHz (using CR02 tape). distortion better than 2% wow and flutter better than 0.2% RMS. Complete with pair of matching Akai CS88 speakers.
Rec. Price £96.10. P & P. 50p
OUR PRICE £56.50

CS35D STEREO DECK
4 track record/playback deck. Accepts chrome/regular tape cassettes.
Rec. Price £68.30. P & P.
GWS PRICE £44.45 50p.

MICROPHONES (P. & P. 50p)
ADM Dynamic (pair) .. £7.50

STEREO RECEIVERS (P. & P. 75p)
AA6300 20+20 watt .. £61.65
AA8030 25+25 watt .. £92.50
AA8040 40+40 watt .. £117.50
AA81008 2x36 or 4x18 w. £175.00
AA8500 65+65 watt .. £150.50

STEREO AMPLIFIERS (P. & P. 50p)
AA5200 20+20 watt .. £81.75
AA5300 30+30 watt .. £78.50
AA8000 45+45 watt .. £117.50

STEREO TUNERS (P. & P. 50p)
AT550 AM/FM .. £60.50
AT590 AM/FM .. £94.50

4-CHANNEL UNIT (P. & P. 50p)
S51 Synthesiser .. £39.95

SPEAKERS
SW155 (each) .. £51.00

STEREO HEADPHONES
AS111 .. £4.75
AS120 .. £7.30
AS122 .. £5.25

TAPE/GASSETTE (P. & P. 75p)
GX1900D .. £144.60

CARTRIDGE (P. & P. 50p)
CR81 Deck with amps. £65.40
CR81D Deck .. £63.80
CR81T Recorder/Receiver £92.75
CR8055 4 channel Recdr. £114.25
CR8055 4 channel Recdr. £99.95

TAPE (P. & P. 75p)
4000DS Dust Cover .. £3.95
T721L Recorder .. £60.35
X3000 Recorder .. £108.90
X201D Deck .. £108.90
GX220D Deck .. £123.95
GX221D .. £138.40
GX280D Deck .. £198.50
GX370 Deck .. £311.50

RECORD DECKS

SPECIAL GARRARD OFFERS!

STEREO 1025T
4 speed autochanger unit fitted with stereo ceramic cartridge.
Our Price £4.95 Carr. 50p

SP25 III WITH ACOS GP 104
SP25 MK.II. 4 speed single record player fitted with Acos GP104 stereo ceramic cartridge.
Our Price £8.50 Carr. 50p

SINCLAIR PROJECT 60 PACKAGE DEALS

GARRARD
2025 T/C Stereo .. £6.95
SP25 III .. £9.25
SP25 III Acos GP104C .. £8.50
SP25111/9800 .. £10.95
SP26/M75-6 .. £13.80
AP76 .. £11.15
SL72B .. £17.75
SL95B .. £31.15
401 .. £24.35
ZERO 100A .. £34.10
ZERO 100S .. £31.40

GOLDRING
G95 .. £18.99
G101P/C .. £18.99
GL69/2 .. £15.75
GL72 .. £20.97
GL72/P .. £27.80
GL75 .. £26.80
GL75P .. £34.40
GL78P/C .. £46.55
GL85P/C .. £59.85

THORENS
TD125/II .. £56.60
TD125/AB/II .. £85.85
TD160C .. £48.40
TD165 .. £41.70

2 x Z30 Stereo 60/PZ5 £16.95.
P. & P. 37p.

2 x Z30 Stereo 60/PZ6 £16.00.
P. & P. 37p.

2 x Z50 Stereo 60/PZ8 £20.25.
P. & P. 37p.

Transformer for PZ8 £3.65.
Active Filter Unit £4.45.
Pair of Q16 Speakers £10.70
Project 60 FM Tuner £14.95
Sinclair Project 60S £20.97.
P. & P. 37p.

All other Sinclair Products in stock
2000 Amplifier £22.95
3000 Amplifier £28.95
2000/3000 Tuner £38.30
Q830 Speakers £29.98 pair
P. & P. 50p each of above items

RECORD DECK PACKAGES

Carriage and Packing 75p.
Complete units with Stereo cartridge ready wired in plinth cover.

GARRARD
2025 T/C/TAHCD .. £10.85
SP25 111/G800 .. £15.95
BP25 111/M44E .. £18.45
SP25 111/M44-7 .. £18.10
SP25 111/M55E .. £16.90
SP25 111 Module/M75-6 .. £19.45
AP76/G800 .. £23.50
AP76/G800E .. £25.95
AP76/M44E .. £24.95
AP76/M55E .. £25.65
AP76/M75ED .. £31.70
AP76/M75EJ .. £27.85
AP76 Module M75-6 .. £29.10
AP76 Module M75-6 .. £33.20
ZERO 1008 Module/M39E .. £44.15

B.S.R. McDONALD
1010/SC7M .. £7.40
MP60/G800 .. £15.00
MP60/TPD1/G800 .. £15.90
MP60/M44-7 .. £16.80
HT70/TPD1/G800 .. £19.20

GOLDRING
GL72/G800 .. £21.50
GL75/G800 .. £23.65
GL75/G800E .. £29.15

GOODMANS
TD100/G800 Teak .. £46.85
TD100/G800 White .. £48.80

LEAK
Delta/M75-6 .. £48.95

PHILIPS
GA106/GP200 .. £13.80
GA190/GP200 Teak .. £19.50
GA308 (less cartridge) .. £45.25
GA308 (less cartridge) .. £28.95
GA308 P.U. .. £32.75

PIONEER
PL12C (less cartridge) .. £29.80
PL16C (less cartridge) .. £41.25
PL41D (less cartridge) .. £35.25
PL50 (less cartridge) .. £89.90
PL61 (less cartridge) .. £102.75
PLA35 (less cartridge) .. £68.60

THORENS
TD126C/Ortofon M15ES .. £66.95
TD126 AB/11/Ortofon M15E Super .. £104.25
TD165/Ortofon M15E Super .. £59.60

WHARFEDALE
Linton/M44-7 Teak .. £28.70
Linton/M44-7 White .. £28.90

HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. complete with batteries, cable and instructions.

2 Station £2.97, P. & P. 15p.
3 Station £5.25, P. & P. 15p.
4 Station £8.62, P. & P. 17p.

SH628 STEREO HEADPHONES

Outstanding value. Soft ear-pads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

Our Price £1.87 P. & P. 30p

LHO25 STEREO HEADPHONES

Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft. cord and plug.

Our Price £1.95 P. & P. 30p

TEI018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

Our Price £2.25 P. & P. 30p

BH.001 HEAD SET AND BOOM MICROPHONE

Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms.

Our Price £4.95 P. & P. 30p

FM TUNER CHASSIS

6 TRANSISTOR HIGH QUALITY TUNER SIZE ONLY

6 x 4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money.

Our Price £5.95 P. & P. 12p
Stereo multiplex adaptors £4.97.

SPECIAL PURCHASE!

FERGUSON EXPORT MODELS

FERGUSON 3408 STEREO TUNER AMPLIFIER
Covers FM 88-108 MHz. Five push button tuning scales. 3+8 watts rms. Inputs for stereo ceramic cartridge and tape etc. Separate bass treble, balance and volume controls.
Our Price £31.50 P. & P. 50p

3418 STEREO TAPE DECK
4 track. 7 1/2, 3 1/2 i.p.s. Stereo/mono record/play. 7" reels. Inputs for dynamic mikes, radio, gram. Complete with cover.
Our Price £41.95 P. & P. 75p

VAT 10% VAT (10p in the £)
Order with confidence by post - but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY.

SEND LARGE S.A.E. FOR FULL HI-FI DISCOUNT LIST

G.W. SMITH & CO (RADIO) LTD

UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ
TELEPHONE 01-205 3735
PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON
257/8, Tottenham Court Rd, W.1. Tel: 01-580 0670
10, Tottenham Court Rd, W.1. Tel: 01-637 2232
27, Tottenham Court Rd, W.1. Tel: 01-636 3715
87, Tottenham Court Rd, W.1. Tel: 01-580 3739
21, Old Compton Street, W.1. Tel: 01-437 9369
3, Lisle Street, W. C.2. Tel: 01-437 8204
34, Lisle Street, W. C.2. Tel: 01-437 9155
118, Edgware Road, W.2. Tel: 01-723 3789
193, Edgware Road, W.2. Tel: 01-723 6211

311, Edgware Road, W.2. Tel: 01-262 0387
332, Edgware Road, W.2. Tel: 01-723 4194
152/3, Fleet Street, E. C.4. Tel: 01-353 2833
378, Harrow Road, W.9. Tel: 01-286 9530
ESSEX
86, South Street, Romford. Tel: Romford 20218
SURREY
1046, Whitgift Centre, Croydon. Tel: 01-681 3027
27 & 21, Eden Street, Kingston. Tel: 01-546 7845
32, Hill Street, Richmond. Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

CREDIT TERMS FOR CALLERS (£50 and over)

ALL EQUIPMENT IS BRAND NEW, FULLY GUARANTEED AND OFFERED WITH FULL AFTER SALES SERVICE

All items and prices are correct at **20-73** but subject to change without notice. E & O. E.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

EMI 13 x 8, 3, 8 or 15 ohm £2.03
 EMI 13 x 8, 150 d/c 3, 8 or 15 ohm £2.25
 EMI 13 x 8, 450 t/tw 3, 8 or 15 ohm £3.60
 EMI 13 x 8 type 350 8 ohm £8.25
 EMI 6 1/2" 93850 4 or 8 ohm £2.80
 EMI 8 x 5, d/Cone Roll/s 8 ohm £2.50
 Baker Group 25 3, 8 or 15 ohm £6.60
 Baker Group 35 3, 8 or 15 ohm £7.50
 Baker De Luxe 12" d/cone £9.62
 Baker Major 12" £7.50
 Kef T27 £4.67
 Kef T15 £5.50
 Kef B110 £6.16
 Kef B200 £7.42
 Kef B139 £10.72
 Kef DN8 £1.92
 Kef DN9 £1.37
 Kef DN12 £4.12
 Kef DN13 £2.75
 Fane Pop 100 watt 8/15 ohm £21.45
 Fane Pop 60 watt 8/15 ohm £12.26
 Fane Pop 50 watt 8/15 ohm £10.17
 Fane Pop 25/2.25 watt 8/15 ohm £5.94
 Fane Pop 15 watt 8/15 ohm £4.40
 Fane Crescendo 15" 8 or 15 ohm £27.50
 Fane Crescendo 12A 100w 8 or 15ohm £24.20
 Fane Crescendo 12B 75w bass 8 or 15 £24.20
 Fane 807T 8" d/c roll/s 8 or 15 ohm £3.16
 Fane 808T 8" d/cone 8 or 15 ohm £2.64
 Goodmans Axent 100 tweeter £6.60
 Goodmans 8P 8 or 15 ohm £3.80
 Goodmans 10P 8 or 15 ohm £4.49
 Goodmans 12P 8 or 15 ohm £11.55
 Goodmans 15P 8 or 15 ohm £17.05
 Goodmans 18P 8 or 15 ohm £29.70
 Goodmans Twinaxiom 8 £6.79
 Goodmans Twinaxiom 10 £7.61
 Elac 9 x 5 1/2" 59RM109 15 ohm, £2.53
 59RM114 8 ohm £3.22
 Elac 6 1/2" d/c roll/s 8 ohm £3.22
 Elac 6 1/2" d/cone 8 ohm £2.59
 Elac 4" tweeter TW4 £1.21
 Wharfedale Bronze 8 RS/DD £3.11
 Wharfedale Super 8 RS/DD £5.50
 Wharfedale Super 10 RS/DD £9.80
 Coral 6 1/2" d/cone roll/s 8 ohm £2.42
 Siran 6 1/2" 3 or 8 ohm £1.44
 Richard Allan 12" d/c 3 or 15 ohm £2.20
 10" x 6" 3, 8 or 15 ohm £1.92
 8" x 5" 3 or 8 ohm £1.38
 7" x 4" 3 or 8 ohm £1.38
 2 1/2" 64 ohm or 70 mm 80 ohm £0.65
 Adastra Hiten 10" 10w 8 or 15 ohm £2.80
 Eagle DT33 dome tw. £5.45
 Eagle HT15 tweeter £3.66
 Eagle CT5 tweeter £1.25
 Eagle CT10 tweeter £2.54
 Eagle MHT10 tweeter £3.74
 Eagle FR4 £4.45
 Eagle xover CN23, 28, 216 £1.15
 Sp. matching transformer 3-15 ohm £1.10
 Celestion MF1000 25w horn 8 or 15 ohm £10.45
 Celestion P58 (for Unilux) £2.16
 Celestion G12M 8 or 15 ohm £12.00
 Celestion G12H 8 or 15 ohm £15.00
 Celestion G13C 8 or 15 ohm £24.00
 Celestion G18C 8 or 15 ohm £33.00
 Car Stereo speakers—ask for leaflet.

SPEAKER KITS

Wharfedale Unit 3 £8.25
 Wharfedale Unit 4 £14.50
 Wharfedale Unit 5 21.00
 Richard Allan Twinkit £7.33
 Richard Allan Triple 8 £10.76
 Richard Allan Triple Assem. £16.20
 Richard Allan Super Triple £19.36
 Goodmans DIN 20 £8.58
 Fane Mode One £9.00
 Kefkit 2 £24.75
 Kefkit 3 £35.50
 Peerless 2-8 £5.50
 Peerless 3-15 £10.45
 Peerless 3-25 £16.00
 Peerless 10-2 £8.47
 Peerless 20-2 £10.41
 Stephanspeaker kits and cabinets—send for free booklet "Choosing a Speaker".
 Prices include VAT.
 Carriage and insurance 50p per kit.



RADIOS/CASSETTES/AMPS.

Grundig Mariner TR865 £32.00
 Grundig Party Boy 210 £20.00
 Grundig Elite Boy 500 £24.00
 Grundig Melody Boy 500 £24.00
 Grundig Melody Boy 1000 £35.00
 Grundig Yacht Boy 210 £31.00
 Grundig RF430 mains £23.75
 Grundig RF310 mains £21.00
 Grundig Top Boy £16.75
 Grundig Satellit 1000 £116.00
 Grundig C402 cassette £27.00
 Tandberg TP4 £37.75
 Nordmende 7000 £87.00
 BASF 9301 radio/cassette £58.00
 Bush RTP100 radio/cassette £30.50
 Trio KA2000A £33.00
 Trio KA2002 £41.00
 Hitachi TRQ2325 stereo cassette £49.50
 Hitachi TRQ257 cassette £20.00
 Hitachi KCT1210L radio/cassette £37.50
 Hitachi KH986 £18.70
 ITT/KB Golf Preset £21.25
 ITT/KB Weekend Auto £16.00
 ITT/KB Europa £18.00
 ITT/KB SL53 cassette £22.82
 ITT/KB Studio 60M cassette £29.32
 ITT/KB Studio 73 stereo cassette £44.00
 Koyo KTR1664 8 waveband £40.00
 Koyo KRT 1770 11 waveband £56.50
 Prices include VAT.
 Carriage and insurance 50p. FREE with each radio—"Guide to Broadcasting Stations" (160pp)

PA/DISCO AMPLIFIERS

Carriage and insurance £1.00.
 Baker 100 Watt £46.00
 Linear 30/40 £25.00
 Linear 40/60 £30.00
 Linear 80/100 £55.00

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 25p per speaker (tweeters and crossovers 15p)

ALL PRICES QUOTED INCLUDE V.A.T.


WILMSLOW AUDIO Dept. P.W.

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

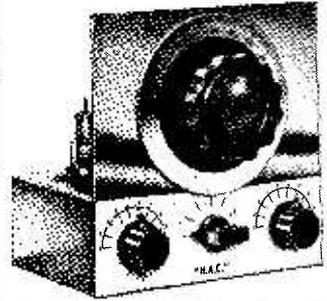

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER


Complete kit—price £3.85 (incl. p. & p. V.A.T.). Customer writes: "Australia, India and America at loud volume." I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world. This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
 29 Old Bond Street, London W.1

SAVE TIME AND MONEY

LIST PRICE £6.87 | OUR PRICE £5.50

INCLUDING V.A.T.

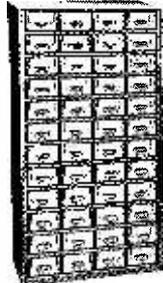

AS SUPPLIED BY US TO SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawer-fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21" x 11 1/2" x 6 1/2". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available. Callers welcome. NEW as illustrated OUR PRICE ONLY £5.50 plus 44p postage on orders less than £10.00. Money back guarantee. SEND FOR FREE LISTS

TRADE AIDS

(DEPT. PW14), 111 CHILTERN DRIVE, BERRYLANDS, SURBITON, SURREY

01-399 4383

100 yds. Berrylands Railway Station.

ZN414 £1.25 POST FREE

The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets

Dual-in-line or Zig-Zag (Dun), 14 and 16 pin
Our Price 1p per pin

VDR's & Thermistors

A15B 75p	E298 ED/A258 10p	VA1005 15p
CZ1 15p	E298 ZZ/06 10p	VA1026 13p
CZ4 13p		VA1033 10p
CZ13A13p		VA1034 10p
CZ19 13p		VA1039 15p
GL16.E1.00		VA1040 10p
GL23A1.00		VA1053 10p
RS3 £1.32		VA1055S10p
RS4 £1.46		VA1077 13p

Potentiometers



5KΩ	50KΩ	500KΩ
10KΩ	100KΩ	1MΩ
25KΩ	250KΩ	2MΩ

log or lin less switch (& 1KΩ lin) 12p
log or lin with switch 24p
dual less switch 40p
dual with switch 10K, 100K & 1M log only 52p
10K log : 10K antilog less switch 40p

Capacitors

disc ceramic	low voltage	
01μF 18v	5p	0.1μF 30v 5p
022μF 18v	5p	0.22μF 5v 5p
047μF 12v	5p	0.47μF 3v 5p
ceramic plate		
30V		
1000pf	10p	4700pf 10p
2200pf	10p	10,000pf 10p

Ceramic - plate 63V (C333)

1.8pf	8.2pf	33pf	120pf
2.2pf	10pf	39pf	150pf
3.3pf	12pf	47pf	180pf
3.9pf	15pf	56pf	220pf
4.7pf	18pf	68pf	270pf
5.6pf	22pf	82pf	330pf
6.8pf	27pf	100pf	

all 5p. each

mylar film 100V

1000pf 2p	0.1μF 3p	0.68μF 4p
2000pf 2p	0.22μF 3p	1μF 4p
5000pf 2p	0.47μF 3p	2μF 5p
	0.5μF 3p	

polystyrene 160V

10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallised polyester 250V (C280)

0.1μF 3p	0.68μF 3p	4.7μF 8p
0.15μF 3p	1μF 4p	11p 4p
0.22μF 3p	1.5μF 4p	15p 13p
0.33μF 3p	2.2μF 4p	15μF 20p
0.47μF 3p	3.3μF 4p	22μF 24p

metallised polyester 400V (C281)

0.1μF 4p	0.47μF 6p	22μF 10p
0.15μF 4p	0.68μF 6p	33μF 14p
0.22μF 4p	1μF 7p	47μF 15p
0.33μF 4p	1.5μF 8p	

silvered mica 1% (-50pf) 500V

2.2p-820pf 7p	4.7n-5600pf 19p
1nF-2.2nF 9p	6800pf-0.1μF 29p
2.7nF-3.6nF 16p	

mixed dielectric 600V

0.1μF 7p	0.47μF 7p	22μF 16p
0.22μF 7p	0.68μF 8p	47μF 24p
0.33μF 7p	1μF 8p	1μF 33p

Slider Pots

Single	Dual	log
10K	10 + 10K	or
25K	25 + 25K	lin
50K	50 + 50K	
100K	100 + 100K	Knobs
30p	50p	10p.


Resistors

1/2 watt 5% Carbon Film - low noise Hi-Stabs

All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value.

1W 10% Carbon Composition 3p each
2W 10% Carbon Composition 6p each
2 1/2W 5% Wire wound 9p each
5W Wire wound 9p each
10W Wire wound 10p each
plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25.

Eliminators

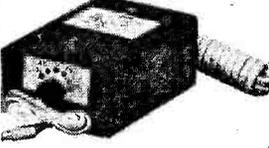

6 volt @ 50mA £1.50
9 volt @ 50mA £1.50
6 + 8 volt, 50mA £2.50
9 + 9 volt, 50mA £2.50
7 1/2 volt for cassette recorders £2.00
6, 7 1/2 or 9 volt £3.00
3, 4, 5, 6, 7 1/2, 9, 12 or 500mA (Illus.) £3.99
Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts £4.99
(p. & p. 15p on all types)

polystyrene 160V

10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallised polyester 250V (C280)

0.1μF 3p	0.68μF 3p	4.7μF 8p
0.15μF 3p	1μF 4p	11p 4p
0.22μF 3p	1.5μF 4p	15p 13p
0.33μF 3p	2.2μF 4p	15μF 20p
0.47μF 3p	3.3μF 4p	22μF 24p

metallised polyester 400V (C281)

0.1μF 4p	0.47μF 6p	22μF 10p
0.15μF 4p	0.68μF 6p	33μF 14p
0.22μF 4p	1μF 7p	47μF 15p
0.33μF 4p	1.5μF 8p	

silvered mica 1% (-50pf) 500V

2.2p-820pf 7p	4.7n-5600pf 19p
1nF-2.2nF 9p	6800pf-0.1μF 29p
2.7nF-3.6nF 16p	

mixed dielectric 600V

0.1μF 7p	0.47μF 7p	22μF 16p
0.22μF 7p	0.68μF 8p	47μF 24p
0.33μF 7p	1μF 8p	1μF 33p

NEW LISTS

LOUDSPEAKERS No. 4
COILS AND INDUCTORS No. 5
TRANSFORMERS No. 6
(postage 5p)

Diodes & Rectifiers

AA119 9p	BA156 15p	BY176 £1.50
AA120 9p	BA243 58p	BY182 £1.50
AA129 9p	OA47 10p	BY250 23p
BA102 25p	OA79 9p	IN4001 6p
BA115 17p	OA90 7p	IN4002 7p
BA130 10p	OA91 7p	IN4003 8p
BA145 20p	OA200 10p	IN4004 8p
BA148 20p	BY100 15p	IN4005 10p
BA154 13p	BY126 15p	IN4006 12p
BA155 14p	BY127 15p	IN4007 15p

8279 ZENER SERIES 10 EACH

SGS

EA1000



3 Watt Audio Amplifier
Our Price inc. handbook £2.49

10+ less 15%
25+ less 25%
100+ less 33%

3 Watt Audio Amplifier
Our Price £3.99
Less quantity discount.



FM TUNER

chassis fully transistorised 9 volt operation
OUR PRICE £8.25

Matching stereo decoder £4.97
Ask for model list No. 11.

Presets



Vertical or Horizontal	0.1 watt 5p	0.25 watt 7p
	100 1KΩ	10K 10KΩ
	250 2.5KΩ	25K 25KΩ
	500 5KΩ	50K 50KΩ
		1M 1MΩ
		2.5M 2.5MΩ
		5M 5MΩ

CHROMASONIC electronics

PRICES DO NOT INCLUDE V.A.T.

MAIL ORDERS: Where no p. & p. charge is shown, a minimum of 7p applies, p. & p. on overseas orders is charged at cost.
ADDRESS: TO: Component Dept., 56, Fortis Green Road, London N10 3HN
Telephone 01-883 3705

Heat Sinks



TOS TO18 5p
TO66 TO3 14p
Power Tab 13p

DIP10/2 for SL403D 13p

10D 50p

Transistors & Integrated Circuits

AC107 25p	BC147 10p	BF196 15p	OC81 15p	2N1304 22p	2N5172 15p
AC126 17p	BC148 10p	BF197 15p	OC140 20p	2N1711 25p	LO5T1 £1.50
AC127 15p	BC149 10p	BF272 53p	OC170 23p	2N1893 30p	LO3T1 £1.50
AC128 15p	BC157 12p	BFY50 24p	OC711 30p	2N2926 all 10p	LO3T7 £1.50
AC176 15p	BC158 10p	BFY51 21p	ZTX107 15p	2N3053 23p	MC1303L £1.75
AC187 25p	BC159 12p	BRY39 36p	ZTX108 12p	2N3054 50p	MC1330 80p
AC187K 25p	BC169 15p	BSX21 26p	ZTX109 15p	2N3055 49p	MC1350 75p
AC188 25p	BC266 15p	BSY95A 14p	ZTX300 12p	2N3702 12p	MC1351 82p
AC188K 25p	BD115 67p	BU105/02 £1.75	ZTX301 15p	2N3703 12p	MC1352 £1.00
ACV20 20p	BD131 70p	MJ540 67p	ZTX302 20p	2N3704 10p	MFC4000B 49p
AD140 40p	BD132 70p	MPF192 40p	ZTX303 20p	2N3705 10p	MFC4010A 55p
AD149 40p	BD133/ZM.P.	MPF103 37p	ZTX304 25p	2N3706 10p	LM380 61.45
AD161 60p	148p	MPF104 37p	ZTX341 20p	2N3707 15p	PA284 £1.99
AD192 40p	BF160 21p	MPF105 40p	ZTX500 15p	2N3708 12p	SU403D £1.50
AF114 18p	BF167 20p	MPF106 45p	ZTX501 15p	2N3709 12p	TAD100 £1.50
AF115 18p	BF173 20p	OC26 40p	ZTX502 20p	2N3710 12p	FILTER LP1175 £1.50
AF116 18p	BF180 25p	OC36 40p	ZTX503 17p	2N3711 12p	μA709C 34p
AF117 18p	BF181 30p	OC44 15p	ZTX504 50p	2N3819 35p	μA710 45p
AF139 20p	BF184 25p	OC45 15p	ZTX505 25p	2N3903 15p	μA723C 95p
BC107 10p	BF185 25p	OC71 11p	2N697 18p	2N3904 17p	μA741C 47p
BC108 10p	BF194 15p	OC72 17p	2N706 12p	2N3905 21p	μA748C 60p
BC109 10p	BF195 15p	OC76 15p	2N708 15p	2N3906 12p	

Mullard B Siemens Electrolytics

CAP μF	VOLTAGE	
1	4	6.3
1.5	16	25
2	16	40
2.5	16	63
3.3	16	63
4.7	16	63
6.8	16	63
10	16	63
15	16	63
22	16	63
33	16	63
47	16	63
68	16	63
100	16	63
150	16	63
220	16	63
330	16	63
470	16	63
680	16	63
1000	16	63
1500	16	63
2200	16	63
3300	16	63
4700	16	63


Veroboard

Copperclad Plain

0.1"	0.15"	0.15"
2 1/2" x 1"	2p	6p
2 1/2" x 3 1/2"	6p	16p (9)
3 1/2" x 5"	24p	21p (7)
3 1/2" x 3 1/2"	24p	21p (8)
3 1/2" x 5"	27p	27p (10)
17" x 2 1/2"	67p	50p 37p
17" x 3 1/2"	90p	70p 52p
17" x 5"		75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

THE TEXAN

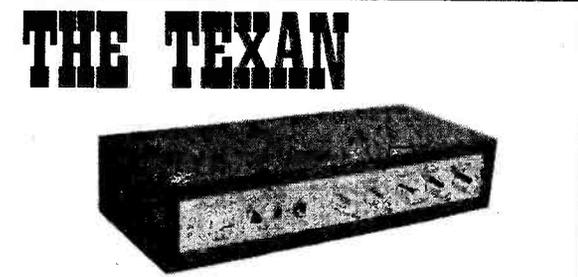

Complete Kit (inc. Teak Case) £28.50 p6p 45p

20 Watts per channel integrated stereo amplifier developed by engineers of Texas Instruments Ltd. This designer approved kit, has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 at -3db. The semiconductor compliment of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistors, 4 rectifiers and 2 zeners. Controls include: bass; treble; volume; balance; on/off; indicator; headphone sockets, selector filter, rumble filter; inputs for magnetic phono; tuner; aux or tape; tape head etc; input; scratch; mono/stereo switch.

The construction of this kit was featured in 'Practical Wireless' May - Aug. 1972.


CAP μF	VOLTAGE	
500	16	25
1250	16	25
1600	16	25
2000	16	25
2500	16	25
3000	16	25
4000	16	25
6400	16	25

Hi-Volt Electrolytics

1; 2; 4; 8μF 150V 14p 32μF 450V 20p
16μF 450V 15p 50μF 32μF 750V 20p
8; 8μF; 450 V.W 18p 32; 32μF; 350 V.W 25p
8; 16μF; 450 V.W 20p 32; 32μF; 450 V.W 43p
16; 16μF; 450 V.W 25p 50; 50μF; 350 V.W 35p

Quantity Prices on application.

TO SPARK YOUR IMAGINATION!

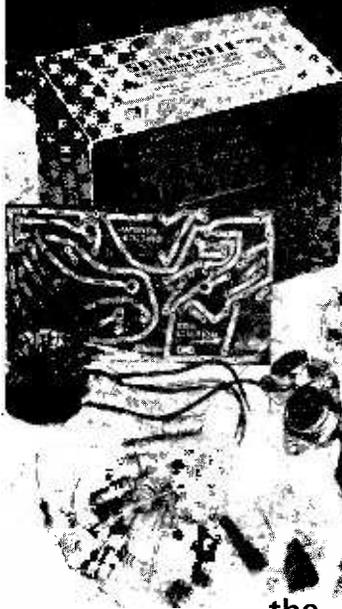

Kit comprises **EVERYTHING**: Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.



the SPARKRITE

Electronic Ignition Kit only £9.35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £9.35 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage. **GUARANTEED 5 YEARS.**

ORDER NOW To: **ELECTRONICS DESIGN ASSOCIATES,**
82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9.35. Or for ready built unit £11.55.

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing).

PW9

FELSTEAD ELECTRONICS (PW 72) LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only—No C.O.D. or Caller service. Charges (Min. 7p) in brackets after all items apply to G.B. and Eire only. Regret orders under 30p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas including Eire and Channel Isles, orders less 10% off prices below, which include V.A.T. **RECORDING TAPE:** Finest quality/value British. Many available: **STANDARD** 3" 6004, 40p, 5" 900ft, 55p; 7" 1200ft, 62p; **LONG PLAY** 5" 900ft, 55p; 5" 1200ft, 62p; 7" 1800ft £1.00 (Charges for 5" and 5 1/2", singles 9p, two to four 8p each; five and over 39p the lot. For 7", one or two 11p each reel, 3, 4 and 5 reels 33p the lot, 6 reels and over 39p the lot.) Other sizes and accessories in list. **CASSETTES,** Two types, Both in Library Cases, C60 33p, C90 48p, C120 72p. Deluxe Types: C90 55p, C90 72p, C120 89p. (Charges for both types, under 5, 9p each; 5 for 12p. All quantities over 5, 25p the lot.) **CARTRIDGES** all with standard fittings and styli. Stereo-compatible Mono GP91/8C 95p; **STEREO** GP93 £1.35, Stereo Ceramic GP94 £1.75. (All at 7p each). Comparatives shown in List, with more types inc. Sonotone 9TAHC, Stereo Ceramic Diamond £1.70 (7p). **DIAMOND STYLI:** single tip types: Acos GP37, GP59, GP65/67, GP71, BSR TCS/LP/ST; COLLARO O.P. and DC284, GARRARD GC2, GC8, GC8/10, GCB12, RONETTE BF40, O.P. and T. PHILLIPS 3301 (3000, 3060, 3302, 3304), 3010/15/15/16, SONOTONE 1PT/2OT ALL AT 36p each (7p). **SAPPHIRE** 16p (7p) **DIAMOND DOUBLE TIP TURNOVER TYPES** (78 sup. on other side). For ACOS GP73, GP91 (for cartridges GP93, GP94 etc.) GP918C (for stereo compat. types) GP104, BSR ST4 (ST3, ST5), ST9 (ST8), ST12/14/15, SONOTONE STA, 9TA, STAHC, PHILLIPS 3306 3310, 3224, 3228/22 GP280, GARRARD GCM21, and 22, GOS23, GKS25 and 26, GCM21T and 22T, GCM24T GCS23, GKS24T and 26T, GCM31, GCS26, GCS35, GCS36, KS40A, KS41B BTC. ALL AT 69p (7p). **SAPPHIRE** 33p (7p). **DOUBLE DIAMOND STYLI:** same dia ST/LP tip each side; no 78) All types £1.35 (7p). **SAPPHIRE DOUBLE ST/LP, TIPPED** 32p (7p). **DIAMOND STYLI GOLDING REPLACEMENTS:** G800, G800H & G850, £2.25 each G800E, £3.75 (8p each). **PICK-UP WIRE:** super thin flex screened, sheathed, TWIN 7p per yard, 4-core 13p per yard (either up to 6 yds. 7p). Over, charges paid. **MICROPHONES:** CRYSTAL: LAPEL 13p, clip/hand, lead 3.5mm jack plug 39p (9p). CM20 Cream Plastic hand 55p (9p); "MIC 45" Curved metal hand grip £1.10 (11p) ALL with leads. DYNAMIC: Excellent Mike, 50K Ω, only 3 1/4" long, black/chrome, switched, lead with 2.5 and 3.5 mm jack plugs £1.87(5p). Cardioid Ball, 50K/600 Ω built in volume control on/off switch, special 20T lead, the best value anywhere at £6.60 (33p); Uni-dir mesh ball 50K/600 Ω jack plug cable, adaptor, £5.28 (33p); Omni-dir. Ball mesh, 50K, cable adaptor, jack plug, £4.20 (33p each). **SPEAKERS:** Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) £3.96 (33p) or pair for stereo £4.65, charges paid. **SMALL** 2 1/2", 3 Ω, 8 Ω or 64 Ω (state which) 41p (9p). More speakers in List. **HEADPHONES:** High resistance 2000 Ω adjustable £1.10 (11p). **EARPIECES:** with lead and min. 2.5mm or 3.5mm (state which) jack plug, MAGNETIC 12p. CRYSTAL (3.5mm plug only) 28p (up to 6 for 9p any size). **SOLDERING IRON:** Slim, modern, British high speed. 8 1/2", all parts replaceable, highest quality, fully guaranteed £1.28 (11p). **TRANSFORMERS:** Sub-min 11 x 11 x 12mm. OUTPUT (3 Ω for OC72, etc.) 16p or DRIVER 17p (Up to 12 for 7p). **CONNECTING WIRE:** Packs of 3 coils, each coil 5yds. Acute coils. **SOLID CORE** 16p (7p). **FLEXIBLE CORE** 18p (9p). **RETRACTABLE FLEXIBLE LEADS (CURLIES)** with phono plug each end, or phono plug one end, phono socket at the other (state which) 6ft. 30p; 12ft. 53p (either 7p). **VIBRATORS:** 12v/4 pin non-synch 121HD4, 2 1/2" ex. pins, 33p. SAME but 3 1/2" ex. pins, USA. 16p. 12v/7 pin synch. (12SR7) 2 1/2" ex. pins, 72p (9p any type). **MAINS BATTERY ELIMINATORS:** Two models, both 240v A.C. input. Suit most radios and cassette recorders/players, with front switch, pilot lights mains and output leads Model SC, 3, 6, 7 1/2 and 9v 400mA, stabilised with multi-output adaptor £5.50 (35p) Model N.R. has additional 12v output and is 500mA £6.00 (35p).

OUR LIST (see heading) has added to the above items Cartridge and Styli Comparison Special Non-repeatable Offers, Aerials, Dials, Transistors, Multi-Leads, Plugs, Sockets of many types, Speakers, Vol. Controls, Multi-testers, Mike Inserts, Neoms, Indicators STEREO Headphones, Pocket Screwdriver Testers, Tel. Pick-ups, Wire, Cable, etc., etc.



become a RADIO-AMATEUR!

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

**BRITISH NATIONAL RADIO &
ELECTRONICS SCHOOL** P.O. Box 156, JERSEY


NAME :

ADDRESS :

WB91

BLOCK CAPS please

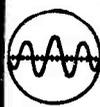**MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.00 a.m. - 6.00 p.m.**



TUAC

**TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD.
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137/9080**

PRE-AMPLIFIER £4.22



All Tuac audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into the various wide range tone control circuits, producing superb sound quality from any signal. Previous range still available. 40V d.c.; 30mV o/p.

VA08 — Vol. Treb. Mid and Bass Controls. HI £4.22 IMP. FET I/P. Suitable Mic, Guitar, Radio, Illus. Crystal/Ceramic P.U. Sensitivity 4mV.


P. & P. 20p Treb +35dB at 16kHz, Mid +20-15dB at 1kHz, Bass +20-10dB at 40Hz.

VA06 — Vol. Treb and Bass Controls. 8mV sensitivity. Treb +28-15dB at 12kHz, P. & P. 20p Bass ± 18dB at 40Hz.

MVA01 — Vol. Tone, Vol. Tone Controls. Ideal for £4.50 Disco. Suitable for Mic I/P. Sensitivity P. & P. 20p 2mV. Tone range +25dB at 12kHz to +20dB at 40Hz.

AMF01 — Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade P. & P. 20p O/P to main Amp. 30mV operating level. Depth and Vol Controls.

POWER AMPLIFIER £15.18

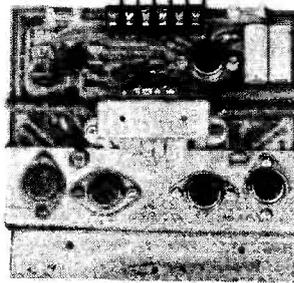

TPI00W with RCA output transistors—150w device 2N6254

TPI00W 100 Watts r.m.s. continuous sine wave into 8Ω. 60mV input into 10kΩ full power frequency response 10Hz-20kHz ± 2dB. Hum and noise better than -75dB. T.H.D. at 100 Watts 1%.


£15.18 This rugged circuit incorporates a special layer wound driver transformer to give increased reliability under all conditions. Short and open circuit proof. An external heatsink area is required. Just bolt on the module.

P. & P. 45p. Illus.

TP50W 50 Watts r.m.s. continuous sine wave into 8-15Ω. With 115 Watt RCA 2N3055 output transistors. Specification as TPI00W.

£10.36

POWER SUPPLY £9.10

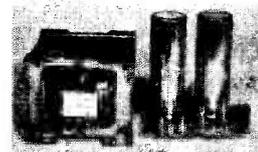

PS100— 100 Watt Power Supply for one TPI00W £9.10 Module. Complete as illus. above.

PS50— 50 Watt Power Supply for one TP50W £6.86 Module. Similar to illus. above. Postage and Packing 50p each.

PSU2— 40V. 250mA. Pre-amp./Disco Mixer £2.95 Supply. P. & P. 25p.

100 W. R.M.S. sine. 200 W. R.M.S. square. £28.50 p & p Trade & export enquiries welcome. Call for a demonstration

ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS

DISCOTHEQUE MIXER FEATURING AUTO-FADE



Panel mounting Cut out 17 x 3 1/2 ins.

£22.00. P. & P. 50p. PSU £2.95

Designed for the discerning D.J. of professional standard. Auto Fade is fitted as standard. Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw. Tape Vol, L & R Deck Faders, Deck Volume, Treb. & Bass. H. Phon Vol, Selector, Master Vol, on/off sw.

HIGH POWER AMPLIFICATION



Suitable for Disco, P.A., Guitar etc. Rugged circuit, rugged case.

100 watt £60.50
100 watt £49.50
50 watt £41.25
P. & P. £1.00

LIGHT MODULATORS

Triac controlled. Safety isolating input transformer. 0-3 Watt sensitivity with controls.

SILMB 3 1000 Watt outputs. £17.45 Bass, Mid & Treb.

S2LMB 1 1500 Watt output. Operates on all frequencies. P. & P. 30p

Now with RCA TRIACS.

ALL TUAC KITS ARE SUPPLIED COMPLETE WITH EASY TO FOLLOW WIRING INSTRUCTIONS AND CIRCUIT DIAGRAM ALL PRICES INCLUDE VAT.

LARGE S.A.E. WITH ALL ENQUIRIES PLEASE.

ALL TUAC MODULES ARE READY ASSEMBLED ON GLASS FIBRE P.C. BOARD AND INDIVIDUALLY TESTED

MAPLIN ELECTRONIC SUPPLIES

★ RETURN OF POST SERVICE

3RD EDITION NOW AVAILABLE

Send for your copy of this beautifully produced fully illustrated catalogue and we will forward it to you by return of post. Please send 9p in stamps.

Everything guaranteed brand new marked by manufacturer

MAPLIN: Projected site of London's third airport.



RESISTORS
Carbon film 5% from 1Ω to 1MΩ, 10% from 1MΩ, 1-2MΩ to 10MΩ. E12 series, 1/4W 1p-1/2W 2p, Metal Oxide 2%, 10Ω to 1MΩ. E24 series 1/4W 4p, Also 1W, 2 1/2W, 5W, 10W types stocked.

POTENTIOMETERS

Miniature carbon track with 1/2 in. spindles. 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ.
Log or lin (and 1kΩ lin), 12p
Log or lin with switch 23p.
Dual gang less switch 38p.

THE OTHER DAY WE RECEIVED A WIRE

It was too long + stop + so we cut it with a pair of our 5 inch diagonal nippers + stop + fully insulated handles + stop + they make a clean cut at only £1.40 a pair + stop + then we had to strip to the bare copper without a nick + stop + our fully adjustable strippers will strip cleanly any size wire from 12 S.W.G. to 26 S.W.G. with no nicked wires even if its stranded + stop + real value at only 54p a pair + stop + finally the wire had to come to an end so we terminated it with our 5 1/2" long nosed wiring pliers + stop + their slender jaws are gap free and the fully insulated handles are gently tensioned apart by leaf springs + stop + ir-resistable at only £1.98 a pair + stop + so the next time you get a wire you'll know what to do, won't you?

8 pin DIL Op Amp 741C 36p.
14 pin 741C 45p.
70V r.m.s. 1-8A full wave bridge rectifier.
REC 41A £1.06
DIODES 1N914 4p, BAX13 5p, 1N4001 6p, 1N4002 6 1/2p, 1N4003 7p, 1N4004 7 1/2p, 1N4005 8p, 1N4006 8 1/2p, 1N4007 9p.

SEMI-CONDUCTORS
We stock a large range of transistors and I.C.s, for details please see our catalogue. LOOK! These popular devices at amazingly low prices. BC107/8/9 10p each, BC169C 12p, BFY51 16p, T1S43 (SS43) 28p, 1N706 10p, 2N2646 45p, 2N3055 49p, 2N3819 24p.

DIN PLUGS. 3 pin, 9p, 5 pin A (180°), 5 pin B (240°), 10p each.
DIN SOCKETS. 3 pin, 5 pin A, 5 pin B, 7p each.
DIN LOUDSPEAKER. 2 pin plug, 8p. Socket 6p.
JACK PLUGS standard 1/2 in plastic barrel, 13p, Stereo, 25p. Bright metal barrel, 17p. Stereo, 29p. Jack sockets standard 1/2 in open type 10p, Moulded 2 break 13p, Moulded stereo 3 break 18p

SPECIAL IC. for organ builders, 7 stage frequency divider in one 14 pin DIL package, £2.63 or special price for pack of 12, £25.
Why not ask us to slip a data sheet in with your catalogue.

HARDWARE

Wide range of nuts and bolts, plated brass and nylon types plus solder tags, shakeproof washers, etc.
SOLDER 10 metres of 22 gauge multi-core, 20p.
Insulating sleeving 3 sizes, 6 colours.

MISCELLANEOUS

LT700 Eagle sub-miniature O/P transformer 1200/50, 200mW max., 35p.
Slide switch DPDT, 12p
Push to make non-locking switch 12p.
Silicon grease in special dispenser, 20ml, 38p.

NUDES!

Clothe those naked projects with our superb instrument cases. We are sole distributors of the



range, designed for the professional market, now available to you at special low prices. S.A.E. please for free illustrated leaflet.

SEE OUR CATALOGUE for details of how you can obtain £1 worth of components.

ABSOLUTELY FREE

V.A.T. Please add 10% V.A.T. to final total. Orders and enquiries for catalogues to **MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex SS6 8LR**

ROTARY SWITCHES
Adjustable stop, 1 pole 2-12 way, 2 pole 2-6 way, 3 pole 2-4 way, 4 pole 2-3 way. Only 24p each.


Postage and packing FREE in U.K. But we have to ask you to send a 10p handling charge with order under 50p.

SANSEI TEST EQUIPMENT



10 IN ONE MINI LAB
10 instruments in one. Including AC & DC Voltmeter, Ohm Meter, etc.

£11-95 including VAT & P.P.

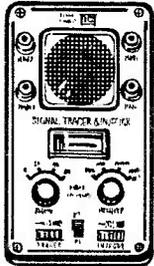

SIGNAL TRACER/INJECTOR
Designed to receive audio frequency, built in amplifier with high gain of 60dB.



£11-55

including VAT & P.P.

SIG MITTER
Powerful trouble shooting signal injector. Model SE260.

£2-20

including VAT & P.P.

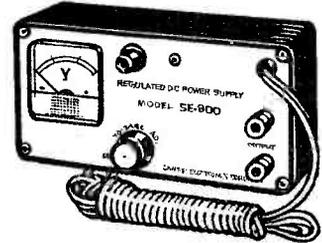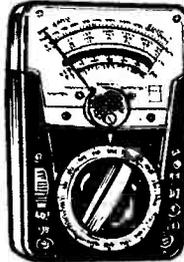

DC POWER SUPPLIES

Regulated power supply variable up to 15V 0.5A. Model SE800... ideal for development work.

£11-00 including VAT & P.P.

NEW HIGHLY SENSITIVE MULTITESTERS


Model M650 with mirror scale.

£7-70 including VAT & P.P.

JH Associates Ltd.

Crickfield Lane, Bishops Stortford, Herts. Tel. 0279 56347

CASED AMPLIFIERS

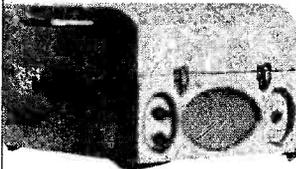

Polished wooden cabinet 14 x 13 x 9" with hinged lid containing a sensitive (20V) 4-valve amplifier with tone and volume controls, giving about 3 watts output to the 7 x 4" 30 speaker. Also a non-standard single motor tape deck. Easily converted to record player, guitar practice amp, baby alarm, etc. Supplied in good

working condition with circuit diagram. Mains operated. Only £3 (£1 up to 200 miles, £1-20 over). Special cassettes £1 (25p). Spare heads £2 (25p), 7lb of lower quality including some broken £2 (40p), 56lb £12 (c.p.). Boards from 5p to callers.

COMPUTER PANELS

Type A: 4 OC35, 4 GET103, etc. 50p; Type D: 4 OC36, 8 GET103, etc. 60p. (5p ea); Type E: 4 OC29, 4 ACY19, 8 other Transistors, 4 Trimpots, 35 Diodes, etc. £1 (10p). Parcel of 12 top quality boards £2 (25p), 7lb of lower quality including some broken £2 (40p), 56lb £12 (c.p.). Boards from 5p to callers.

7lb BARGAIN PARCELS

Hundreds of new components—capacitors, resistors, switches, crystals, pots, PR boards, etc. Outstanding value £1-65 (35p). 500 assorted resistors, good selection £1 (15p); 40 asstd pots £1 (25p); 300 asstd capacitors, all types £1 (25p). Heavy duty heat sinks 6 x 5 x 3". Wt. 3lbs with 2 power transistors, OC36 or 2N1146A £1 (25p). Large selection of panel meters for callers. Audio oscillator 50Hz-20kHz, BFO No. 8 £10; RF Signal generator Marconi TF144G 85kHz-25MHz from £12. Oscilloscopes in stock. 741C TO99 or 8 pin DIL 32p; BC107-9 14 for £1; 2N3055 35p. Varoboard in stock. Post in brackets, small parts 3p. VAT NOT INCLUDED. SAE List, details.

GREENWELD ELECTRONICS (PW4)

24 Goodhart Way, West Wickham, Kent. SHOP AT 21 Deptford Broadway, SE8 (Next to old cinema). Callers most welcome. Tel: 01-692 2009.

FIRST TIME EVER at £42-50

Solartron CD715.2 Double Beam

Oscilloscope d.c.—9MHz; 3mV-cm; trigger delay; crystal callibrator; 4in flat faced tube. In good working condition. Carriage £1-50.

SOLARTRON CT 316 (D300 range)

DC to 6 mcs. 3" tube. TB up to 0.75 micro secs per centimeter. Built in callibrator. Size 8 1/2" x 11" x 20". Price £22-50. Carr. £1-50

MARCONI VALVE VOLTMEETER type TF 958 (CT208)

DC to 100 mcs. 5" mirror backed meter complete with probe, leads etc. £12-50. Carr. £1-25.

GRATICULES, 12cm x 14cm in High Quality plastic. 30p ea. P. & P. 5p.
MODERN TELEPHONES type 706. Two tone grey, £3-75 ea. The same but black, £2-75 ea. P. & P. 25p ea. Also **TOPAZ YELLOW** £4-50 ea. P. & P. 25p.

STANDARD GPO DIAL TELEPHONE (black) with internal bell, 81p ea. P. & P. 50p. Two for £1-50. P. & P. 75p. All telephones complete with bell and dial.

20Hz to 200kHz WB SINE AND SQUARE GENERATOR Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £6-85 each. P. & P. 25p. (Not cased, not calibrated.)

MOTOR MIN SYNCHRONOUS Size 1 1/2" x 2" x 1/2" 240V operation 3-6 RPM 25p each. P. & P. 5p.
5 MOVING COIL METERS various £2 P. & P. 37p.

PLEASE ADD 10% V.A.T.
Open 9 a.m. to 7.30 p.m. any day.

CHILTMEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech. College)

Tel.: Reading 582605/65916

WOBBULATOR

Sweeps 8 to 45MHz ready to use. 6-3V a.c. required. £9 each. P. & P. 25p. (Not cased, not calibrated.)

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 17p.
POTS—10 different values. Brand new—50p. P. & P. 17p.

COMPONENT PACK consisting of 2-2 pole 2 amp push on/off switches; 4 pots, various; brand new; 250 resistors 1/2 and 1/4 watt, many high stabs, etc. Fine value at 50p per pack. P. & P. 17p.

P.C.B. PACK S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.
FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice, 50p. P. & P. 15p.
Matched pairs, 50p per pair. P. & P. 15p.

TRIMMER PACK, 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.


ELECTRONIC TIMER UNITS—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2-50 Incl. carriage.

AMERICAN SCOPE type USM24. A 10 meg scope—all min valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore £20-00. With Step-down transformer £22-50. Carr. £1-50.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 35p ea. Holder 1p ea. Information 5p.
PHOTOCELL edu OCP71—13p ea.
PHOTO-RESIST type Clare 703. Two for 50p.

DELIVERED TO YOUR DOOR
1cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3-50.

BI-PRE-PAK AUDIO BARGAINS

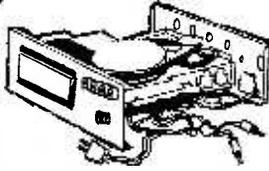


**8 TRACK
ONLY £11**

incl. P. & P. and VAT

The latest **B.S.R. 8 Track cartridge Replay Deck. Ready to install in your Hi-Fi Stereo System.** This unit comes complete with Hi Gain Stereo Pre-Amplifier, 4-Programme Indicator Lamps, Track Selector Switch, all leads and plugs, etc. for 230 volt A.C. mains operation.

5W & 10W AMPS

5W ONLY £1.98
10W ONLY £2.49

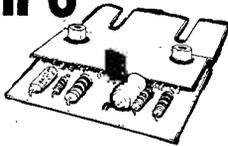

incl. P. & P. and V.A.T.

Specification:-

	5 Watt	10 Watt
Nominal Volts	12-14V	25-30V
Into 3 Ohms	5W	10W
Into 8 Ohms	2W	10W
Into 15 Ohms	1W	5W
Typical Distortion	-5%	-5%
Freq. response at 3dB	10Hz to 30KHz	10Hz to 30KHz
Sensitivity (Typically)	20mV	20mV
Full power consumption (30 Ohms)	650mA	580mA
Size	2 1/2" x 1 1/2"	2 1/2" x 1 1/2"

The **5W matchbox sized amplifier** will run satisfactorily from a 12V car battery. Can also be used for portable voice reinforcement such as public functions where mains supply is not accessible. A small mains unit kit is available. Two amplifiers are ideal for Stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit.

Discounts are available for quantity orders.

Cheapest in the U.K. Built and tested

**STEREO
DECODER
£4.95**



incl. P. & P. and VAT

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner. A tell tale light can be connected to show the presence of a Stereo transmission and correct operation.

The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us at 36p. Supplied with all necessary instructions.

I enclose £..... for 8 Tracks/..... 5W
Amps./.....10W Amps./..... Decoders (Please
insert quantities and delete those not applicable.)

Name

Address

BI-PRE-PAK

Dept. D, 222/224, West Road,
Westcliff-on-Sea, Essex SSO 9DF
Tel: Southend (0702) 46344

Co. Regn. No.820919

Would you spend an hour a day to earn more money in Electronics- Television-Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and our wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics - in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments).

With ICS you study at home - at your own pace, when you choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

ICS your key to the door
of opportunity

Tick or state subject of interest and post to:
International Correspondence Schools, Dept. 232T, \\
Intertext House, Stewarts Road, London SW8 4UJ.

Subject of interest

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name

Address

Occupation Age

■ Accredited by the Council for the Accreditation of Correspondence Colleges ■

Sinclair Project 60

Now—the Z.50 Mk.2


with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50: circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual
£5.48

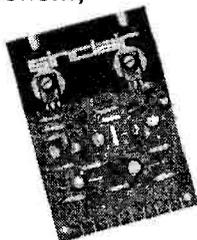Z.30 the power amplifier for quality and economy



with free manual
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/4 x 1/2). Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.


Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

Brilliant new technical specifications

Input impedance 100 K Ω
Input (for 30w into 8 Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8 Ω . See curve
Frequency response 10Hz to more than 200 KHz \pm 1dB
Max. supply voltage 45v (4 Ω to 8 Ω speakers) (50v 15 Ω speakers only)
Min. supply voltage 9v
Load impedance — minimum: 4 Ω at 45v HT
Load impedance — maximum: safe on open circuit

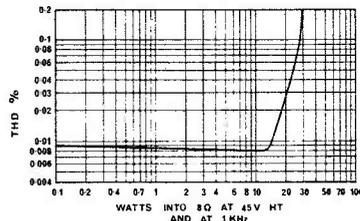

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

sinclair

SINCLAIR RADIONICS LTD., R.O. London Road, St. Ives, Huntingdonshire, PE17 4HJ (Phone St. Ives 4311) Reg. No. 699483 England

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit



Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio — up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A. curve ± 1 dB 20 to 25,000 Hz. Ceramic p.u. — up to 3mV: Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to -12dB at 10KHz: BASS +12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7 μ V for lock-in over full deviation. **Squelch level:** Typically 20 μ V. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10Hz — 15KHz (± 1 dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

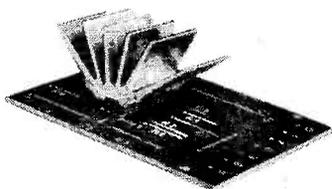Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS


Output power: 6 watts RMS continuous (12 watts peak). 8–8 Ω . **Frequency Response:** 5Hz to 100KHz ± 1 dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** .8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Power Supply Units The new PZ.8 Mk.3

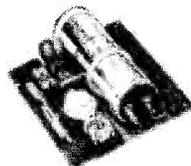

The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage — 45.

PZ.8 Mk.3—£7.98
(Mains transformer, if required) £5.98
PZ.5 30v. un stabilised
(not suitable for Project 60 tuner) £4.98
PZ.6 35v. stabilised
(not suitable for IC. 12) £7.98

Project 605



the easy way to
buy and build
Project 60
without
soldering

Project 605 in one pack contains: one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free
All you need for a superb 30 watt high fidelity stereo amplifier

£29.95

Order form

Please send

I enclose cash/cheque/money order.

Name

Address

PW7

SINCLAIR RADIONICS LTD., R.O. London Road,
St. Ives, Huntingdonshire, PE17 4HJ

sinclair

ADD 10% V.A.T. ON PRICES ON PAGE OPPOSITE AND ABOVE

Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Books and Publications

Radio BOOKS

Handbk of Transistor Equip and Substitutes	45p
Handbook of Tested Transistor Circuits	20p
Rad & Electr Colour Codes and Data Chart	20p
Hi Fi, PA & Disco Amplifier Design H'bk	80p
Boys Bk of Crystal Sets and Simple Circuits	23p
How to make FM & TV Aerials, Bands 1,2,3	25p
Radio Servicing for Amateurs	25p
High Fidelity Loudspeaker Enclosures	45p
Practical Tape Recording Handbook	35p
Practical Stereo Handbook	35p
Practical Radio Inside Cuts for Beginners	45p
Transistor Circuits Manual No. 1	20p
Transistor Circuits Manual No. 2	20p
Coil Design and Construction Manual	35p
Radio TV and Electronics Data Book	30p
Transistor Circuits for Radio Controlled Models	45p
Pract Transistor Audio Amplifiers, Book 1	25p
Transistor Test Equip and Servicing Manual	30p
Handbook of Simple Transistor Circuits	40p
Modern Transistor Circuits for Beginners	45p
Sound and Loudspeaker Manual	55p
Resistor Colour Code Disc Calculator	15p
Manual Transistor Audio Amplifiers	45p
Practical Car Radio Handbook	35p
Radio TV and Industrial Tube & Valve Equip	45p
Practical Transistor Novelty Circuits	45p
Television Servicing Vol. 1	95p
Television Servicing Vol. 2	95p
Television Servicing Vol. 3	95p
Television Servicing Vol. 4	95p
Using an Oscilloscope	80p
Servicing Transistor Radio Receivers	85p
Television Timebase Circuits	£1.10p
Pat-D Colour Receiver Questions & Ans.	78p

All prices include postage & packing

FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwell Way, Beckenham BR3 2RZ

DENCO CLACTON LIMITED
355-7-9 Old Road
Clacton-on-Sea, Essex

Catalogue 20p post paid
S.A.E. all enquiries

TRANSISTOR DATA THE INTERNATIONAL TRANSISTOR DATA MANUAL

1973 EDITION is now ready. Data on upwards of 18,000 transistors of international origin. £6.20 in the U.K., £6.90 elsewhere, includes surface mailing. Brochure available. Order direct from

SEMICON INDEX LTD.,
Freeport, Wokingham, Berks. RG11 2AY.

COMPONENT PROBLEMS?

—write to us for our free catalogue.
Send a stamped addressed envelope to

Dept. PW1,
J. T. EDEN ELECTRONICS,
P.O. Box 5,
LANCASTER, LA1 3HZ

Aerials

GENUINE FULL SIZE
18 element TV aerial
as used by leading
TV companies

FOR ONLY
£2.20
+ 35p carr

ITV, BBC1 & 2/BW & Colour Guaranteed Perfect Pictures. Save ££s. We supply this genuine U.H.F. aerial for only £2.20, can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions advice. Money Back Refund. Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters. SEND DIRECT TO DEPT. PW10
219 Mansfield Rd, Nottingham.

IMPERIAL TRADING LTD.
100, QUEEN'S ROAD, BIRMINGHAM.

BAINES FOR HIGH FREQUENCY AERIALS
Multibeams by J. Beam
MBM 18 £2.90, MBM 30 £3.90, MBM 46 £6,
MBM 70 £11, LBM 2 £5.25.
Stereobeams by J. Beam
SBM 1 £2.10, SBM 2 £2.80, SBM 3 £4.20,
SBM 4 £4.60, SBM 6 £6.95, SP 15 Loft Kit
£2p. Stacking Kit £2.10. Rotators £22.
Masthead Amplifiers £6.75, Wideband £7.75,
Setback £3.75.
Accessories: Large SAE please. VAT add 10%.
Postage paid on all aerials
11 Dale Cres, Tupton, Chesterfield S42 6DR.
Telephone 863755.

Ladders

LADDERS 24½ ft £9.80. Carr 80p.
(Please add 10% V.A.T. to total order).
Leaflet. Home Sales Ladder Centre,
(WLS) Haldane, Halesfield (1) North,
Telford, Salop. Tel: 0952 586644.

Situations Vacant

MEN!
£50 p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators
Training Centre

P1, Oxford House
9-15, Oxford Street, W.1.
Telephone: 01-734 2874

127, The Piazza, Dept. P1,
Piccadilly Plaza, Manchester 1.
Telephone: 061-236 2935

Computer Commissioning Engineers

Resulting from our expansion programme, our Quality Control Department have vacancies in Letchworth and Stevenage factories for Engineers to commission and test computer equipments before delivery to the customer.

We offer attractive conditions and salaries to applicants who should have practical experience in fault finding and testing of complex electronic equipment. Whilst qualifications to ONC standard are desirable they are not essential.

Housing may be available for applicants living in the Greater London Council's area.

Write for an application form, quoting reference PW412M to Area Personnel Recruitment Officer, ICL House, Broadway, Letchworth, Herts SG6 3PG.

**International
Computers**



Service Sheets

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS) Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA 71 BEAUFORT PARK LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

Wanted

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

TOP PRICES PAID for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.
KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

For Sale

TV LINE OUTPUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycroft Rd., Richmond, Surrey. TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items, Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

LARGE QUANTITY Test equipment, receivers, transceiver, meters, variacs, P.S.U.S. over 1,000 items for immediate disposal. S.A.E. Plus 25p refunded on purchase over £2.00. F. J. C. Colnemill, Alvington, Lydney, Glos.

FOR SALE
UK Distributor "W2AU" baluns, antenna hardware, toroid cores also Electro-Voice microphones plus more. Large S.A.E. T.M.P. (Electronic Supplies) admin address, (Dept. PW), 3 Bryn Clyd, Leeswood, Mold, Flintshire, CH7 4RU.

Educational

RADIO, TV, RTEB Certs., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book—FREE. BIET (Dept ZL BPW 30), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

CIE, AMSE, City & Guilds, etc. Thousands of exam successes. Postal courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept ZL BPW 41), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Receivers and Components

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.
0.47µF: ±0% 80p; ±2% 40p; ±1% 60p
1.0µF: ±5% 40p; ±2% 80p; ±1% 60p
2.2µF: ±5% 70p; ±2% 80p; ±1% 70p
4.7µF: ±5% 70p; ±2% 80p; ±1% 80p
6.8µF: ±5% 85p; ±2% 11.15; ±1% 11.80
10µF: ±5% 11.10; ±2% 11.40; ±1% 11.80
15µF: ±5% 11.60; ±2% 12.10; ±1% 12.70

TANTALUM BEAD CAPACITORS—Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (78 capacitors) £5.

NEW—TRANSISTORS. BC107, BC108, BC109, All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178—35p each or 3 for £95p.

POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1. **IN918**—9p each, 6 for 50p, 14 for £1. **1N544**—5p each, 11 for 50p, 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5p mA. All new and marked. Price 9p each, 6 for 50p, 14 for £1.00 Special offer 6 off each voltage (66 zeners) £4.25

RESISTORS, Carbon film 1/8W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 9p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS, 0.1µF, size 1 1/2in x 1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47 and 0.5µF, size 1 1/2in x 1/2in, 35p; 1.0µF, size 2in x 1/2in, 45p; 2.0µF, size 2in x 1/2in, 75p each.

SILICON PLASTIC RECTIFIERS 1.5 Amp Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5. Please add 10% V.A.T. to all orders.

MARCOTRADING

Dept. W.9, The Maltings, Station Road, Wern, Salop

NEW MODEL V.H.F. KIT MK2
Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 + p.4p 10p U.K. only.

Illustrated catalogue of selected kits and components, 20p inc. V.A.T. P&P free.

ALL PRICES PLUS 10% VAT

Galleon Trading Co,
12, Burns Way,
Corringham,
Stanford-le-Hope,
Essex. SS17 9DE

BUILD THE TREASURE TRACER MK III Metal Locator



- Varcap tuning
 - Excellent sensitivity and stability
 - Weighs only 22oz.
 - Speaker and earphone operation
 - Knecks down to only 17in
 - Prebuilt search coil assembly
 - Ministry approved design
 - Thoroughly professional finish
 - You only need soldering iron, screwdriver, pliers and snips
 - Completely new design
- Send s.a.e. for leaflet

Complete kit **£9.80**

Built, tested and guaranteed **£13.75**

MINIKITS ELECTRONICS, 35a LANGLEY DRIVE, WAINSTED, LONDON E11 2LN. (Mail order only)

Trampus electronics

ALL BRAND NEW, no rejects
Money back warranty. 5V DIGITAL INDICATOR 0-999 socket and filter £1.45. LED TYPE 1" 0-999 DIL £2.25 ea. LIGHT EMITTING DIODES. All with data and panel clip. TIL 209 1/4" dia. 24p. Red 1/2" dia type 88p. Green 75p. INFRARED beam LED £1.10. TGS GAS detector £1.69. ULTRASONIC TRANSDUCERS £2. DALO PCB resist marking pen 87p. Copper board 12" x 6" SRBP 40p FeC etch PAK 19p. INTEGRATED CIRCUITS: with data if required. IC LIFE SWITCH: Photo amp/trigger 40ma/11-20 volt or 11V 87p. 100 resist £1.10

IC digital clock

MOS, LSI type 2.5 pin 4 or 6 digit 12/24 hr. Chip with socket £13. PCB £1.45. KIT £21.48. 741 DIL 8 pin 28p, 709 14p, DIL 28p, 748 20p, 710 35p, 555 TIMER mono/astable osc. clock 89p. REGULATOR: 1A 5 to 20V £1.49, 283 57p. RECEIVER ZN414 £1.09. Mini Rx kit £1.99. 1310 stereo decoder for tuners £2.89. KH £3.45. 748 TTL Gates 7400 etc. 15p ea. 7413 27p. 7441 75p. 7447 £1.09. 7490 £1.59. 7497 71p. 741 45p. DIL SOCKETS: New type 8/14/16 pin 13p. SEMICONDUCTORS: 1A rectis. 50V 34p. 400V 6p. 2N3055 32p. BC107 7p. BC108 7p. BC109 7p. BC147/8/9 10p. BC167/8/9 13p. BC177/8/9 15p. BC182/3/4 10p. BC212/3/4 11p. BCY70/72 13p. BD131/2 55p. BFV30/159 13p. TIS48 UJT 24p. 2N706 11p. 2N2869 12p. 2N2920 9p. 2N2964 49p. 2N3053 17p. 2N3814 55p. 2N3702/3/4/5/6/7/8/9/10/11 All 9p ea. FETS: 2N3819E 19p. 2N3819 27p. 2N3823E 19p. ZENERS: BZ788 8p. SCR 400V: 1A 29p. TRANSFORMER 1A 612V £1. Resistors 14p. 450 & 470 mini I.P. transformers—Set 3 40p. CAPACITORS: Disc 22pf to 0.1 of 5p. Electrolytic 25V: 10, 50, 100 of 5p. 1000 of 15p. Presets 6p. CARBON POTS 11p ea. switch 11p. Dual 99p.

FLUORESCENT LIGHTS 12VOLT 2.79
13" 8 watt fully built up with 7000hrs. 3V £3.79. V.A.T. You must add 10% V.A.T. to all prices. FREE CAT. S.A.E. Data shts. 8p ea. P.&P. 8p CWO P.O. BOX 29, BRACKNELL, BERKS.

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfd.—4p. 22, 47—4 1/2p. (50V—5p.) 100—5 1/2p. (50V—7p.) 220—6p. (50V—9p.). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p. 0.04, 0.05—3p. 0.068, 0.1—3 1/2p. Polystyrene 63V. E12 series 10 pf.—1,000 pf.—2p. 1,200 pf.—10,000 pf.—3p. Miniature Highstab resistors, 5%, E.12 series—Carbon Film 1/2 W 1Ω—10MΩ (10% over 1 Meg.) Metal Film 1/2 W 10Ω—2.2MΩ and 1W. 27Ω—10MΩ all 3/4p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 + 10p P & P C.W.O. to Caledonian Components, Fosterton Firs, Strathore Road, Thornton, Fife.

TAPE HEADS

For valve and transistorized recorders from £2 ea.

5-N-CHANNEL FETs 3819E-£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.

Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LIMITED
45 Station Road, Gerrards Cross, Bucks.
Mail Order only

TV'S COLOUR TV'S

Reserviced, perfect working order, repolished.

19in. DECCA	£110
19in. GEC 2028	£115
19in. THORN 2000	£120
25in. DECCA	£125
25in. RBM PHILIPS	£130
25in. THORN 2000	£135

One month comprehensive written guarantee. These are cash and collect prices. Delivery quotations by phone

MONO UHF

Fabulous TVs. No rubbish, from good source. Repolished cabinets. Many working. Recent transistorized models, incl.:

- BUSH TV 148U, TV 166, TV 176
- PHILIPS style 70 and 210
- PYE & ECKO 888 chassis
- THORN 950, 1400, GEC Concorde from £12 each

Value UHF models inc.: BUSH push-button, THORNE 850, SOBELL, 1000, etc. from £5

U.H.F. TUNERS

For FERGUSON 950, 900 chassis but adaptable for most D/ST chassis £2.50 each, cwo postage included. Send s.a.e. for lists of tubes, tvs, valves, etc. For England:

TRADE DISPOSALS, 1043 Leeds Road, Bradford. Tel. Bradford 65670

For Scotland:

TRADE DISPOSALS, Unit 5, Peacock Cross INDUSTRIAL ESTATE, 32 Burnbank Road, Hamilton. Tel. Hamilton 29511/2

ELEVEN BAND RADIO. SW1-4 (4-30 MHz). Marine. LW, MW, FM. PB (76-86). Aircraft (108-136). PB (148-174). Battery/Mains. BFO. AGC. Squelch Control. Output: 1-3W. 15in x 10in x 5 1/2in. £66. Eight Band Model, with BFO, £42. Four Band, MW, FM. Aircraft. PB. £15. SAE. Full Lists. Langtons Radio, High Street, ROCESTER, Staffordshire, Tel. 388.

R ROSLESS SERVICES

GUARANTEED SEMICONDUCTORS FAST SERVICE—LOW PRICES

AC126	13p	BFX84	27p	ZENER DIODES
AC127	13p	BFX85	34p	400mW 5%
AC128	13p	BSX20	18p	3-3 to 33 volts
BC107	9p	2N930	22p	12p each
BC108	9p	2N1182	27p	1 watt 5%
AF114	13p	2N1741	25p	all voltages
AF115	13p	2N2904	35p	6-8 to 200 volts
AF116	13p	2N2904A	42p	16p each.
AF117	13p	2N2905	44p	
BCY71	35p	2N3708	9p	

ALSO CAPACITORS RECTIFIERS, ETC.

PRICES	INCLUDE	VAT
--------	---------	-----

CASH. W.O + P.P. 10p TO ROSLESS SERVICES PARNDON HALL - HAMSTEL ROAD HARLOW - ESSEX

INTEGRATED CIRCUIT and FET modules for construction of low-cost receivers, converters, pre-selectors, etc. SAE details.—P. R. Colledge, Glen Tor, Torrington, Devon.

TRANSISTOR AMPLIFIER 80p. Vol/Tone Control Panel 75p. 465 K/CS IF Panel 75p. Wavechange-OSC Panel 75p. LW-MW Rod Aerial 25p. Colour Television. Chroma Panels £3-50. IF Panels £3.00. EHT Tripler Panel £1-08. Control Panel ON/OFF + Vol/Brightness Controls £1-00. Archer, 9 Pine Grove, Maidstone, Kent.

"Globe-King" V.H.F. & SHORT WAVE KITS

Precision standard, low cost valve and transistor Kits 10-350 m. V.H.F. 80-180 MHz. "Easy-Build" diagrams and simplified instructions. For free literature send S.A.E. to sole manufacturers (Overseas: Int. Reply Coupon)

JOHNSON (RADIO) Est. 1948
Shaw St, Worcester, WR1 3QQ

BRAND NEW FULL SPEC. DEVICES SATISFACTION OR YOUR MONEY BACK

U.K. ORDERS—ADD 10% VAT to total

MICROCIRCUITS: 709 24p; 710 36p; 723 51p; 741 27p; 748 37p; FA230 60p; FET Op. Amp. £1-62. **SOLDERCON IC PIN SOCKETS:** 0-5p per pin. **SOCKETS:** 14 pin DIL HI or LO 12p each. **RECTIFIERS:** 1A: 50V 31p; 100V 4p; 200V 41p; 400V 5p; 800V 6p; 1000V 7p; **ZENERS:** BZY88C 2-7V to 33V 10p each. **DIODES:** IN916 4p; OA90 6p; IN4148 4p. **LED Panel Lamp** with Bush and Data 24p. **DALO PC RESIST PEN 68p.**

TRANSISTORS: 2N2926 BROWN 5p; 2N3053 15p; 2N3055 35p; 2N3702 10p; 2N3704 10p; 2N3819 36p; 2N4038 12p; BC107A 8p; BC108B 8p; BC109E 9p; BC109C 9p; BCY70 15p; BFY50/51/52 15p; OC44/45/17/2 12p; AF114/5/6/7 14p; AC126/7/8 12p.

Above prices on 12th June—Check our list.

JEF ELECTRONICS (I-W9)
York House, 13 York Drive, Grappenhall, Warrington, WA4 2EJ. Mail Order Only. C.W.O. P & P at cost. 10p min. List free.

UNUSED RESISTOR and Capacitor Mixture

Carbon and Wirewound 1 to 2 watt. Paper—Silver Mica—Metalised and Electrolytic. A useful workshop selection of 175 values. Our price 500 for £1.70

Potentiometers, 20 assorted £1.10.

Barsain parcels 141b for £2-50. No heavy chassis, all useful components, Resistors, Valves, Pots, Trimmers, Tag Strips, Rectifiers, Nuts and Bolts, Capacitors. Unbelievable value.

Money back Assurance on all goods.
676 Foxhall Road, Ipswich, Suffolk.

TEXAN STEREO AMPLIFIER.

Designed by engineers of Texas Instruments Ltd., this superb amplifier is now available **READY BUILT.** Features include: 20 + 20 watts at less than 0-1 per cent distortion scratch & rumble filters—and is fully guaranteed. Send cheque/P.O. for £38-50 inc. Louis James Electronics, 63 Southwell Road, Camberwell, S.E.5. Mail Order Only.

20 FREE RESISTORS

1/4W Carbon Film, any mix, with all Aug. Orders. ADD 10% VAT to Total. **BRAND NEW FULL SPEC. COMPONENTS** BC107B, BC108A/B/C, BC109B/C all 8p. BFY51 13p. BCY70 15p. 2N4058 12p. 2N3819 25p. 2N3704 10p. 2N3702 10p. 2N3055 35p. 2N2926GRN 8p. OC44/45/17/2 12p. MICRO 741 27p. Diodes: OA90 6p. IN916 4p. Zeners: BZY88 ser. 8p. Tant. Bead Caps. 8p. Carbon Film Res. 1/4W 5% 28p/50 Any Mix (22Ω-2.2M) Iskra 1/4W 35p/50 All E12 ser. Paks as Before. Money back if not satisfied.

ADFONIC (PW).

18 Yew Lane Ashley New Milton Hants BH25 5BA. C.W.O. P & P at cost 10p, min Mail order Only. Lists Free.

BUILD THE R.S. COMPONENTS (RADIOSPARES) AUDIO AMPLIFIER.

Contained I.C. Preamp and Power Amp incorporating short circuit and overvoltage protection. Output 3W into 7-5 Power req 12-18V nominally. Full circuit and applications data supplied with each I.C. All additional components can be supplied by us if required. Single I.C. £3-25 (Mono). Pair £6-25 (Stereo). p & o 5p. Specially Designed P.C.B. (Sized) 99p. p & o 3p. I.C. Heat-sink. 25p ea. Send to day to:

DISCOUNT CONTROL SYSTEMS.
19 Milverton Avenue,
Sunderland SR2 7TS
Co. Durham.
Telephone: Sunderland 68725.

BATTERY ELIMINATOR KITS.

Our well-known Mini Mains Pack Kits now complete with drilled insulated base 32 x 55mm. Fits into space of most large transistor batteries. Easy wiring instructions. Safe, silent mains transformer, silicon rects, smoothing capacitor, all top grade. For any ONE of these voltages (state which): 3V, 300mA max.; 6V, 180mA; 9V, 120mA; 18V, 60mA. £1-50 VAT included. By mail only, UK post 5p. Amatronics Ltd., 396 Selsdon Rd., South Croydon, Surrey CR2 0DE.

TUNBRIDGE WELLS.

Components from Teleservice, S.A.E. or call in for list. Special offers, limited quantity:—Matched AD161/2 68p, 10 transistors similar 2N3702/3 unmarked 32p, 12 IN914/6 20p unmarked, air spaced twin gang receiver tuning capacitors, unused 50p, thin grey connecting flex 1p yd. Minimum order 40p post free, but add "10% VAT". 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

Miscellaneous

"AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS"

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5-80 (inc. VAT) NOW ('S.A.E. for details') 'MAIL ORDER ONLY'

TO: 'BOFFIN PROJECTS'
DEPT. KW2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

GLASS FIBRE P.C. BOARD.

Large supplies available 1/4in single sided one ounce copper 2p per sq. inches (under 1 foot). 75p per sq. ft. (over 1 foot). 1/2in double sided one ounce copper 1p per sq. inch (under 1 ft.), £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

CONSTRUCTION AIDS—Screws, nuts, spacers etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd., Stratford on Avon, Warwks.

DIMMER SWITCH

200, 300 AND 500 WATT TYPES

Separate on-off switch from the brightness control so that the light can be switched without need to re-adjust the dimmer. Ideal for television room, dining room, bedroom or for that romantic occasion. 250V 50-60Hz. Takes about 2 mins to fit. Can be used on two way switches.

100W	£3-70	plus 10p
200W	£4-40	postage and
300W	£4-75	packing

Also available **SPEED CONTROLLER FOR DRILL** etc. £7-50. 25p 20p p. & p.

From **LECTRON**, Dept. 3, King Alfred Way, Battle Down Trading Estate, Cheltenham Glos

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd. Stratford-on-Avon, Warwks.

Darned Electronic Wizardry

by Dewtron (VAT extra).

Famous kits, e.g. waa-waa complete kit £2.95; Fuzz kit £4.75, auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

Build it in a BEC (Book End Chassis) BEC Standard cabinets (Illustrated) 2 Styles in one cabinet. All cabinets in kit form, much easier to drill for pots, etc. prior to assembling.

GB1 14" x 6" x 2" £3.25
GB2 14" x 7" x 3" £3.50
GB3 14" x 9" x 4" £3.75

Post & Packing 40p.
If required the cabinets can be supplied assembled for 25p extra.

The Bec Professional range illustrated in June 1978 issue Pract. Electronics.

GB3W with simulated wood top (PVC Bonded to metal) and alloy trim along bottom. 14" x 9" x 4" size only £4.50. P. & P. 40p.

GB/BT TYPE. Black front, alloy trim top and bottom, simulated black leatherette top (PVC Bonded to metal)

GB1/BT 14" x 6" x 2" £3.95
GB2/BT 14" x 7" x 3" £4.25 P & P 40p
GB3/BT 14" x 9" x 4" £4.50

Stamped addressed envelope with enquiries please.

H. M. ELECTRONICS (PW2) 275a, Fulwood Road, SHEFFIELD S10 3BD Telephone 55951

AUDIO POWER AMPLIFIERS

10W — £4.00 } 1
25W — £8.00 } OFF
50W — £11.00 } PRICES

GENEROUS QUANTITY DISCOUNTS AVAILABLE

DETAILS FROM:

PHOTAIN CONTROLS LTD.

Randalls Road, Leatherhead, Surrey

PRICES DO NOT INCLUDE VAT

Tel: 72776/75517 STD CODE 037-23

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset, S.A.E. for leaflet. Write now—Right now.

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwick.

TAPE DICTAPHONES: Grundig Stenorette, Graetz, untested/some working/L5, postage 50p. "Markonics," 327 Tildesley Rd., London SW15.

AMTRON KITS. Your Devon Stockist. E. Wenmouth, 50 South Street, Exeter 76058.

TRANSFORMERS

DOUGLAS GUARANTEED Prices include 10% VAT & p. & p. 12 or 24 volts

Output V. & Amps	Ref. No.	Price
12V x 2 250mA x 2	MT110CS**	£1.15
12V x 2 500mA x 2	MT219CT**	£1.56
12V x 2 1A x 2	MT181AT*	£1.87
12V x 2 2A x 2	MT18AT*	£2.70
12V x 2 3A x 2	MT70AT*	£3.94
12V x 2 4A x 2	MT108AT*	£3.74
12V x 2 5A x 2	MT72AT*	£4.30

30 volts. All tapped at 0-12-15-20-30V.

Output Amps	Ref. No.	Price
500mA	MT112CT**	£1.47
1A	MT79AT*	£1.99
2A	MT3AT*	£2.92
3A	MT29AT*	£3.39

Output	Ref. No.	Price
500mA	MT102AT**	£1.92
1A	MT103AT*	£2.87
2A	MT104AT*	£3.93

Output	Ref. No.	Price
500mA	MT124AT**	£2.03
1A	MT126AT*	£2.94

Power output	Winding tapped at	Ref. No.	Price
20VA	0-115-210-240	XMT113CT	£1.26
75VA		XMT84AT	£2.38
150VA	0-115-200-220-240	XMT94AT	£2.85
200VA		XMT65AT	£3.94
400V Output at 50 HZ.	Ref. IT5AT		
C-D Ignition System by R. M. Marston, Esq., Wireless World			£2.98


Sec. output (r.m.s.)	Ref. No.	Price	
3-0-3 V.	200mA	MT239CS**	£1.59
9-0-9	100mA	MT13CS**	£1.24
12-0-12	50mA	MT239CS**	£1.24
20-0-20	30mA	MT241CS**	£1.24
0-20 x 2	300 x 2	MT214CT**	£1.56
0-8-0 x 2	500mA x 2	MT207CT**	£1.87
0-15-0 x 2	500mA x 2	MT208AT**	£2.95
0-15-27 x 2	500mA x 2	MT203AT**	£3.17
0-15-27 x 2	1A x 2	MT204AT*	£4.25
20-12-0-12-20	700mA (d.c.)	MT221AT*	£1.58

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; * with intervening screen; † untapped 240V Primary; ‡ tapped at 210-240V; other Primaries tapped at 200-220-240V.

Over 200 types in stock through agents or direct. Please send for lists.

DOUGLAS ELECTRONIC INDUSTRIES LTD., Direct Sales Dept. P.W., Thames Street, LOUTH, Lincs. LN11 7AD

SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER

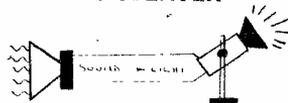

WITH LIGHT DIMMER

Max. load 2kW. at 250v. A.C.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price £7.90 inc. VAT

EXTRA FACILITIES. Push-button for Manual Pulsing 20p extra. Photo-cell for turning on the lights as the ambient light decreases, 75p extra.

3 CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested. Price £3.50 inc. VAT

OIL WHEEL PROJECTOR

Build your own using our

MULTI-COLOURED OIL WHEEL AND MOTOR KIT



Suitable for mounting on virtually all Slide Projectors.

Kit contains:

- ★ 6" dia. or 4" dia. OIL WHEEL (please state size required when ordering).
 - ★ Suitable Miniature mains motor.
 - ★ Full instructions.
- For Professional Discotheque use or home enjoyment. Price £7.15 inc. VAT

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.**
- 1 500 Carbon resistors, ½, 1, 2 watt.
 - 100 Electrolytic Condensers.
 - 250 Ceramic, Polystyrene, Silver Mica etc. condensers.
 - 250 Polyester, Polycarbonate, Paper, etc. condensers.
 - 25 Potentiometers, assorted.
 - 250 High-stab, 1%, 2%, 5% resistors.
 - 750 Assorted Tagstrips.
 - 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
 - 25 Assorted switches, rotary, lever, micro, toggle, etc.
 - 10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED. £1 + 25p p.p. per pack, £5 for 5 packs p/free

C. T. ELECTRONICS

Mail Order, Retail Shop, Components—
287 Acton Lane, LONDON, W4 5DG 01-994-6275
Warehouse, Test Equipment, Surplus Goods—
20-24 Beaumont Road, LONDON, W4
Audio Accessory Shop, Components—
17 Turnham Green Terrace, LONDON, W4

If you have difficulty in obtaining

Practical Wireless

Please place a regular order with your newsgazer or send 1 year's subscription (£2'65) to:—

Subscription Department,
Practical Wireless,
Tower House, Southampton St.,
London, WC2E 9QX

QUALITY KIT ASSEMBLY made easy by AMTRON—send for illustrated brochure. JR599 big price reduction. Trio 9R59DS, JR310, JR599 with FREE headphones, carriage, packing and insurance—from stock. See PARTRIDGE main advert on page 454.

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30:—
ECC82, ECL80, EF80, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PCC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL38, PL81, PL504, PY33, PY82, PY800, PY801, 30L15.

19" UHF/VHF (BBC2) £6.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—65p

‡ to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Capacitors up to 500MFD—£1.10 (our choice).

BARGAINS PARTS

Transistor UHF Tuners—£2.00, 500K-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2.25. Brand New Transistors BF115, BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.


All prices include V.A.T. p. & p. 10p per order. Money back guarantee. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

RECHARGEABLE

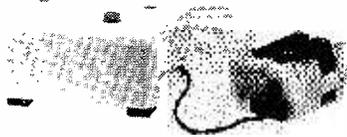Mallory Cells in U2, U11 and Penlite U7 sizes,
KESTREL BATTERY CHARGING UNIT . . .



Use for

Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you *must* have utterly dependable battery power—then these new **Alkaline-Manganese** rechargeable cells will provide it. The cells can be recharged many times, a simple job with the **Kestrel Charging Unit** which has been specially designed for these new type batteries.

PRICES
Batteries U2 equiv. £1-52 tax paid
Penlite U equiv. 55p tax paid
U11 equiv. £1-13 tax paid
Charging unit £7-70 tax paid with one battery holder

ALL PRICES INCLUDE V.A.T.

Send to:

**275 WEST END LANE
LONDON, N.W.6 1QS
01-794 9611**



EX COMPUTER PC PANELS

2 x 4 in. packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (9p)

SPECIAL BARGAIN PACK

25 boards for £1 (25p).
Panels with 4 Power transistors sim OC28 50p (8p)

ELECTROLYTICS

68,000µ 16, 4½ x 2 in. dia. 25,000µ 25v,
20,000µ 30v, 5,000µ 90v, 35,000µ 15v,
8,000µ 4½ x 3 dia. 50p (15p) 15,000µ (5v),
10,000µ 35v, 4½ x 2 in. dia. 30p (10p),
2,000µ 25v wire ends 15p (5p), 12 for £1/50 (15p)

20A DIODES

4 for £1 (7p)

3A DIODES

4 for 50p (5p)

8 BLACK TOGGLES dpst

50p (8p)

250 MIXED CAPACITORS

60p (8p)

250 MIXED RESISTORS

60p (8p)

150 HI-STAB RESISTORS

60p (8p)

200 SI PLANAR DIODES

50p (5p)

SUB. MIN. CO-AX PLUGS & SKTS.

4 pairs 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES

8 for 50p (8p)

ASSORTED RELAYS 8 for £1 (12p)

MIN. GLASS NEONS 12 for 50p (5p)

10 WAY TERMINAL BLOCKS

10 for 55p (5p)

PAPST EXTRACTOR/BLOWER FANS

100 cfm 4½ x 4½ x 2 in £3-50 (28p)

Q-H BULBS 12v 55w 50p (5p)

Postage and package shown in brackets. Please add 10% VAT to prices.

KEYTRONICS

(Mail Order only)

**44 EARLS COURT ROAD
LONDON W8. 01-478 8499**

SINCLAIR EQUIPMENT



Project 60 FM Tuner £15-00 (£1-70)
2 Z30/Stereo 60/PZ5 £16-75 (£2-05)
2 Z30/Stereo 60/PZ6 £18-85 (£2-25)
2 Z50/Stereo 60/PZ8/Trans £23-20 (£2-70)
Z30 £3-50 (55p) Stereo 60 £7-80 (98p)
Z50 £4-30 (65p) Trans for PZ8 £2-95 (50p)
PZ5 £3-87 (59p) 2000 Amp £24-50 (£2-65)
PZ6 £6-30 (83p) 3000 Amp £31-50 (£3-35)
AFU £4-50 (65p) 2000 Tuner £27-00 (£2-90)
PZ8 £6-40 (84p) 3000 Tuner £27-00 (£2-90)
Q18 £5-90 (79p) Project 605 £20-98 (£2-40)

PROJECT 60 KIT £2-50 (36p)

Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuse-holder needed to complete Project 60.

IC RADIO CHIP TBA651 £2-10 (32p)

The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2-10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1-75 (29p).


S-DECS AND T-DECS

S-DECS £1-44 (25p)


T-DECS £2-88 (40p)

µ-DEC A £3-00 (41p)

16 dit IC carriers £1-20 (17p)

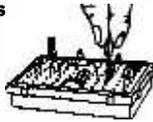

SINCLAIR SUPER IC12

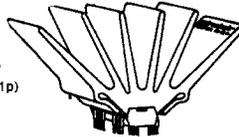

ONLY
£2-00 (31p)

Max. supply volts 28. Power 6 Watts rms. Complete with free printed circuit board and 44 page instruction book.

SWANLEY IC TOMORROW £2-00 (31p)

The World's most powerful IC amplifier. Similar to the above but operates at 35 volts max. supply and gives 12 Watts rms output. Manufactured for us by a leading semiconductor company. Supplied with our instructions and a 6 month guarantee, but no instruction circuit.

KITS FOR IC12 AND IC TOMORROW

Except for the power kits and speakers, all items suit both integrated circuits.

DELUXE KIT

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-45 (25p). Stereo model with balance control £3-30 (44p).

IC12 POWER KIT

A set of components to construct a 28V 0-5 Amp power supply £2-27 (45p)

IC TOMORROW POWER KIT

A set of components to construct a 35V 1 Amp power supply £2-87 (52p)

LOUDSPEAKERS FOR THE IC12


5" 8 ohm £1-00 (26p). 5" x 8" 8 ohm £1-45 (31p). 10" x 6" 15 ohm £2-20 (44p).

PREAMPLIFIER KITS

Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1-30 (24p). Stereo model £2-30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1-20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

SINCLAIR EXECUTIVE CALCULATOR

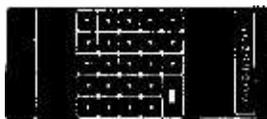

NOW ONLY £45-00 (£4-70).

SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent
Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome. Send SAE for free leaflet on kits, IC Tomorrow and TBA 651. Mail order only. No callers, please.

CAPACITOR DISCHARGE IGNITION KIT



A comprehensive kit of parts with detailed constructional details, ready drilled diecast case, screws, leads, terminals etc.

Available in both 6 and 12v versions. State whether positive or negative earth. £9-62 incl. p. & p. U.K. only.

De-coupling kit for impulse tachometer and interference suppression. £1-10 incl. p. & p. U.K. only. All our kits use guaranteed quality components and have been approved by the Author.

MAGTOR LTD.

68 DALE ST., MANCHESTER
M1 2HS 061-236 3031

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG
Tel.: Bristol 421196. STD Code 0272

Your West Country shop for electronic components and solid state devices

2 METRE CONVERTER KIT

9-12V neg. earth feeding 28-30MHz. Consisting of RF BF180. Fet. mixer. Crystal osc. BF180. Multiplier BF180. Complete with all components, instructions and aluminium box. (Not for beginners). Price £6, post paid.

2 METRE PRE-AMP

Single F.E.T. Pre-amp. neg. earth. Gain app. 12dB. Circuit, instructions and Components. All you need is a tobacco tin.

Price £1-40, post paid.

AIRCRAFT BAND CONVERTER

Circuit, instructions and components. All you need is a tobacco tin. Price £1-40, post paid.

NEW BIGGER 1973 CATALOGUE

Over 25 kits. Over 30 books. Plus components, cases, chassis, etc. Only 10p, post paid.

WE STOCK "WECO" Television Tubes.

All prices include V.A.T.
TRIO STOCKISTS

B.H. COMPONENT FACTORS LIMITED

SPECIAL RESISTOR KITS (1W 5% or 1W 5% CARBON FILM)
10E12 Kit: 10 of each E12 value, 10 ohms—1M, a total of 610, £3.10 net
25E12 Kit: 25 of each E12 value, 10 ohms—1M, a total of 1,525, £7.20 net

POLYESTER CAPACITORS MULLARD C280 250V

μF: 0.01, 0.015, 0.022, 0.033, 0.047, 3½p each; 0.068, 0.1, 0.15, 4½p each;
 0.22, 5½p; 0.33, 8p; 0.47, 9p; 0.68, 11p; 1.0, 15p; 1.5, 22p; 2.2, 25p.

MULLARD POLYESTER CAPACITORS C296 SERIES

160V: (μF) 0.01, 0.015, 0.022, 2½p; 0.047, 0.068, 3½p; 0.1, 0.15, 4½p;
 0.22, 5½p; 0.33, 8p; 0.47, 9p; 0.68, 11p; 1.0, 15p; 1.5, 22p; 2.2, 25p.
 400V: (μF) 0.001, 0.0015, 0.0022, 0.0033, 0.01, 2½p; 0.015, 0.033, 3½p;
 0.068, 4½p.

MINIATURE ELECTROLYTIC MULLARD C426 SERIES (6p each)
 (μF/V) 1/63, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10,
 80/16, 80/25, 100/6.4, 125/16, 200/6.4, 200/10, 320/6.4, 125/10.

MULLARD C437: (μF/V) 64/64, 10p; 160/25, 10p; 160/40, 12p; 640/6.4,
 10p; 1600/6.4, 16p.

ELECTROLYTIC CAPACITORS: Tubular and large can

(μF/V) 2.5-50, 3p; 4.10, 10/25, 16/15, 20/25, 25/15, 25/25, 40/6, 64/10, 200/6,
 250/10, 5p; 10, 6, 10, 50, 25/50, 50/10, 64/25, 100/25, 500/12, 640/10, 1,000/6, 9p;
 250, 15, 1,000 3, 7p; 100/50, 250/25, 400/10, 500/10, 500/12, 640/10, 1,000/6, 9p;
 500, 25, 11p; 500/50, 14p; 1,000/12, 11p; 1,000/25, 2,000/12, 2,500/12, 17p;
 1,000/50, 39p; 2,000/25, 27p; 2,500/25, 33p; 2,500/50, 62p; 3,000/50, 72p;
 5,000/50, 94p; 1,000/100, 66p; 8/350, 14p; 16/350, 19p; 32/350, 25p.

MINIATURE CERAMIC PLATE CAPACITORS

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390,
 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8. (μF) 0.01, 0.015, 0.022, 0.033,
 0.047, 2½p; 0.1, 30V, 4½p; 0.1, 100V, 5½p.

CARBON FILM RESISTORS 1W 5%, 10 ohms—2.2M, ½W 5%, 10 ohms—
 1M, 1p each or 100 for 62p; 1W 5%, 10 ohms—£4.50.

METAL FILM RESISTORS 1W 5% 10 ohms—10M, 1½p each or 100
 for £1.10. **15E12 KIT (15 each valve 10Ω—1M) £8**

Veroboard 0.1 0.15
 2½ x 5in 28p 28p
 2½ x 3½in 26p 19p
 3½ x 5in 32p 33p
 3½ x 3½in 28p 28p
 2½ x 1in 7p 7p
 2½ x 5in (plain) 14p
 2½ x 3½in (plain) 12p
 5 x 3½in (plain) 22p
 Insertion tool 59p 59p
 Track cutter 44p 44p
 Pins, pkt. 25 10p 10p

QUANTITY DISCOUNT
 SPECIAL BULK BUY PRICES
 ARE AVAILABLE BY
 QUOTATION FOR LARGE
 PROJECTS AND TRADE.

S.C.R.
 OC71 13p 50V IA 29p 3A 33p
 OC75 17p 100V IA 33p 3A 40p
 OC83 20p 400V IA 50p 3A 60p

Screened wire, m 5½p
 Twin screened wire, m 10p
 Stereo s.c. wire, m 10p
 Connecting Wire, all colours 2½p
 Neon bulb 90V wire ended 5 for 24p
 Preset skeleton pots 1K—1M 6p

ALL PRICES INCLUDE V.A.T.
 C.W.O. only. P. & P. 10p on orders below £5.
 Discount: £10—10%, £20—15%.
 Export Order enquiries welcome (VAT free)

2 pin DIN Plug, 12p; Skt.,
 10p, 3 pin DIN Plug, 8p;
 Skt., 10p, 5 pin DIN Plug,
 18p, 15p; Skt., 12p. Trans-
 istor Equip. Book, 40p.
 Carbon pots 5K—2M log, &
 lin, single 16½p, single
 with switch 26p, dual 46p.

Dept. P.W. 61, CHEDDINGTON ROAD, PITSTONE
 Near LEIGHTON BUZZARD, BEDS. LU7 9AQ
 Tel.: Cheddington 668446 STD. (0296) GIRO No. 331 7056
 Inquiries—S.A.E. Catalogue FREE. Callers please phone first.

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 4285

THE T.V. GRAVEYARD OF THE NORTH, AS SEEN ON T.V.
 CLOSE TO THE MOTORWAY. PLENTY OF FREE PARKING
 SPACE. EST. 1935.

SPECIAL OFFER

1000 PYE 19" 13 Channel T.V. Sets. Brilliant Picture, Extra Slim
 Bench Tested. Sold with Money Back Guarantee. Hurry, have a
 second set at the price of £5.50. Plus carr. and ins. £1.80.

FAMOUS R. & A. 7x4" Speakers ex T.V. 3 Ohm 2½ Watt 50p.
 Post and Packing 12p.

COMPLETE UNTESTED T.V. SETS. With back and all valves.
 BBC 1 and ITV 17" 90° Tubes £1.10. 17" 110° Tube £2.20. 19"
 £3.30. Carr. and ins. on any set £1.75.

Fifty T.V. Valves. Good assortment non-tested 50p. Post-Paid
 ¼ Cwt. of ex Government Scrap Resistors, Panels and Gears, etc.
 30p. Carr. 80p.

SPEAKERS REMOVED FROM T.V. SETS, all 3 Ohm 2½ Watts.
 7 x 4", 6 x 4", 8 x 2½". All at 27p. Post and packing 12p.

TOP QUALITY TAPE. Reel to Reel 5" ST, 44p 5" LP 55p, 5½" LP
 60p. 7" ST 66p. 7" LP 80p. Cassette Types C60 35p. C90 45p.
 C120 55p. Post on any tape 12p.

Jap Earpiece 8 Ohm Magnetic 3-5 12p.
 Ex Equipment Valves all tested on our Mullard Valve Tester
 before despatch. 3 months guarantee on all valves. Single Valves
 Post 3p, over Post Free.

ARP12	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF60	10p	PCL82	14p	UJ1	20p
EBF89	15p	PCL83	15p	6B7V	12p
ECC81	12p	PCL84	15p	6BWW	12p
ECC82	12p	PL82	10p	6U4	20p
EF91	5p	PL83	10p	6F23	15p
EY86	22p	PL36	17p	20P1	12p
EF183	20p	PY81	10p	20P3	12p
EF184	20p	PY801	17p	30F5	20p
		PY800	17p	30FL1	

ABOVE PRICES INCLUDE V.A.T.

INDEX TO ADVERTISERS

A. H. Supplies ... 400
 Adcola Products Ltd. ... 389
 Adfonic ... 476
 Audio Fair ... 394
 B. H. Component Factors ... 479
 Baines, R. ... 474
 Baker Loudspeakers Ltd. ... 454
 B.I.E.T. ... 402, 475, Cover iii
 Bi-Pak Semiconductors ... 404, 405
 Bi-Pre-Pak Ltd. ... 427, 471
 Boffin Projects ... 476
 British National Radio & Electronic
 School ... Cover ii, 468
 Broadway Electronics ... 416
 Bull, J. (Electrical) Ltd. ... 453
 Butterworth (Publishers) Ltd. ... 450
 Bush & Meissner ... 478
 Bywood Electronics ... 390
 C.T. Electronics ... 477
 Caranna, C. ... 475
 Chiltmead Ltd. ... 470
 Chromasonic Electronics ... 467
 Colomar Electronics Ltd. ... 390
 D.E.W. Ltd. ... 477
 Dabar Electronic Products ... 402
 Denco (Clacton) Ltd. ... 474
 Discosound ... 476
 Douglas Electronic Industries Ltd. ... 477
 Eden Electronics ... 474
 Elektrokit ... 424
 Electronic Mail Order ... 477
 Electronic Design Associates ... 468
 Electrospares ... 416
 Electrovalve ... 401
 Elvins Electronic Musical Instruments ... 394
 Felstead Electronics ... 468
 Francis, J. J. ... 388

Galleon Trading ... 475
 Global Audio ... 400
 Greenweld Electronics ... 470
 H.M. Electronics ... 477
 HAC Shortwave Products ... 466
 Harverson Surplus Co. Ltd. ... 458
 Heath (Gloucester) Ltd. ... 397
 Henry's Radio Ltd. ... 457, Cover iv
 Home Radio (Components) Ltd. ... 415
 I.C.S. ... 471
 I.C.L. ... 474
 I.L.P. (Electronics) Ltd. ... 403
 Imhof Retail Ltd. ... 388
 Imperial Trading ... 474
 Ivoryet Ltd. ... 424
 J. H. Associates ... 470
 Jef Electronics ... 476
 Jermy Industries ... 388
 Johnson & Johnson ... 416
 Johnson (Radio) ... 476
 Kensington Supplies ... 475
 Keytronics ... 478
 Lasky's Radio Ltd. ... 450
 Lectron ... 476
 Lewis Radio ... 460
 Linear Products Ltd. ... 450
 London Computer Operators Training
 Centre ... 474
 Louis-James Electronics ... 476
 Magtor Ltd. ... 478
 Maplin Electronic Supplies ... 469
 Marco Trading Ltd. ... 475
 Milward, G. F. ... 402
 Minikits Electronics ... 475
 Multicore Solders Ltd. ... 396
 Padgetts Radio Store ... 479
 Partridge Electronics Ltd. ... 454
 Phonosonics ... 402
 Photain Controls ... 477
 Purnell Books ... 398, 399

R.D.I. ... 476
 Radio Book Service ... 474
 Radio Component Specialists ... 423
 Radio Exchange Co. Ltd. ... 395
 Radio & T.V. Components (Acton) Ltd. ... 392, 393
 Radio Shop, The ... 478
 Radio Society of Great Britain ... 458
 Radio Supply (Hartlepool) ... 449
 Raymer Electronics ... 424
 Redhawk Sales ... 476
 Riversdale Electronics Ltd. ... 424
 Rosless Services ... 476
 RSC (Hi-Fi Centres) Ltd. ... 386, 387
 R.S.T. Valve Mail Order Co. ... 420
 S.C.S. Components ... 396
 Saxon Entertainments Ltd. ... 419
 Semicon Index Ltd. ... 474
 Sinclair Radionics Ltd. ... 444, 445, 472, 473
 Smith, G. W. & Co. Ltd. ... 462, 463, 464, 465
 Sound Systems Suffolk
 Surpltronics ... 396
 Swanley Electronics ... 478
 Tate Audio ... 391
 Thacker, A. H. & Sons Ltd. ... 424
 Tidman Mail Order ... 475
 Trade Aids ... 466
 Trade Disposals ... 476
 Trampus Electronix ... 475
 Trannies ... 461
 Tuac Ltd. ... 469
 Vero Electronics ... 390
 Web Europa ... 416
 West London Direct Supplies ... 390
 Wilmslow Audio ... 394, 466
 Xeroza Radio ... 454
 York Electrics ... 454
 Z & I Aero Services ... 480

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 12p in £ for postage and handling
MINIMUM CHARGE 15np. No C.O.D. orders accepted
Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

0A2 0.40	6A87G 0.85	6F12 0.50	10D1 0.85	BF92 0.35	HK90 0.50	PL33 0.40	U404 0.70
0A3 0.45	6AT6 0.38	6F14 0.70	10D2 0.55	BF95 0.40	KT66 2.35	PL36 0.55	U801 0.80
0B2 0.40	6AT6 0.30	6F15 0.65	10F1 0.75	BF97 0.65	KT77 1.00	PL81 0.50	UABC80
0B3 0.70	6AV6 0.40	6F18 0.50	10F9 0.65	BF98 0.75	KT88 2.25	PL82 0.45	
0C3 0.40	6AW8A 0.65	6F23 0.80	10F18 0.60	BF183 0.80	N78 1.60	PL83 0.45	UAF41 0.70
0D3 0.40	6BA6 0.28	6F24 0.80	10L1 0.80	BF184 0.55	PABC800.40	PL84 0.40	UAF42 0.60
1B3GT 0.45	6BB6 0.22	6F25 1.00	10L11 0.70	BF804 1.25	PC86 0.60	PL82 0.85	UAF43 0.65
1L4 0.25	6BP8 0.55	6F26 0.35	10P13 0.75	FK90 0.82	PC88 0.60	PL504 0.75	UBC41 0.55
1R4 0.45	6BH6 0.82	6F28 0.70	12A85 0.70	EL34 0.50	PC97 0.50	PL508 0.90	UBC81 0.45
1R5 0.45	6BJ6 0.55	6GK6 0.60	12AC6 0.80	EL36 0.50	PC900 0.48	PL509 1.10	UBF80 0.40
1R4 0.30	6BK7A 0.75	6J4 0.60	12AP6 0.60	EL41 0.75	PC884 0.40	PL801 1.00	UBF89 0.40
1R5 0.30	6BN5 0.40	6J3GT 0.40	12AL5 0.55	EL81 0.55	PC856 0.55	PL802 0.95	UBL1 0.70
1T4 0.30	6BN6 0.83	6J6 0.50	12AG5 0.30	EL82 0.50	PC888 0.55	PM84 0.60	UBI21 0.70
1T4 0.40	6BQ6 0.65	6J7 0.45	12AT6 0.40	EL84 0.25	PC889 0.55	PY31 0.35	UC22 0.45
1T6 0.75	6BR8 0.75	6K4J1 0.80	12AT7 0.40	EL85 0.43	PC8189 0.60	PY33 0.63	UC85 0.45
1V2 0.55	6BR7 1.85	6K6GT 0.75	12A10 0.45	EL86 0.40	PC805 0.95	PY80 0.40	UCF80 0.70
1X2B 0.55	6BW6 0.90	6K7 0.43	12A17 0.33	EL90 0.42	PC806 0.95	PY81 0.30	UCH21 0.60
2D21 0.40	6BW7 0.30	6K8G 0.45	12AV6 0.45	ECC88 0.40	PC808 0.30	PY82 0.35	UCH22 0.70
8A4 0.45	6BX6 0.25	6K25 0.75	12AV7 0.70	ECC89 0.55	PCF80 0.85	PY83 0.33	UCH81 0.40
3B4 0.40	6BZ6 0.45	6L9GT 0.55	12AX7 0.55	ECC90 1.35	PCF82 0.85	PY88 0.40	UCI81 0.60
3V4 0.70	6C4 0.35	6L7 0.45	12AX7 0.75	ECC91 0.60	PCF84 0.60	PY89 0.40	UCI82 0.35
3R4G 0.75	6C5GT 0.55	6L18 0.50	12BA4 0.65	ECC92 0.35	PCF86 0.60	PY500 1.00	UCI83 0.35
5T4G 0.40	6C6GT 0.40	6LD20 0.50	12BA8 0.45	E180F 1.00	PCF87 1.10	PY800 0.47	UCI83 0.65
5V4G 0.50	6CDBA1 0.40	6N7GT 0.55	12BA7 0.50	E181F 2.90	PCF801 0.50	PY801 0.50	UF9 0.65
5Y3GT 0.45	1.30	6P28 0.65	12B2A 0.50	E642 0.70	PCF802 0.50	PZ39 0.38	UF11 0.60
8Z3 0.75	6CG7 0.80	6Q7 0.50	12B26 0.50	6080 1.75	PCF802 0.60	QQV02-0	UF41 0.85
8Z4 0.40	6CL4 0.60	6Q7 0.50	12B27 0.50	6146 1.60	PCF805 0.90	2.25	UF42 0.85
830J2 0.80	6CU6 0.80	6S7 0.45	12B37 0.85	30FL14 0.90	PCF806 0.75	QQV03-10	UF43 0.85
6AB4 0.45	6CW4 0.70	6K7 0.43	12E1 3.00	30FL14 1.25	PCF808 0.00	1.25	UF80 0.35
6AF4A 0.60	6CY5 0.50	6K7 0.43	12E1 3.00	35A5 0.60	PCF808 0.00	TT21 3.80	UF88 0.40
6AG5 0.25	6CV7 0.75	6K7 0.43	12E1 3.00	35A5 0.60	PCF808 0.00	TT22 4.00	UF89 0.40
6AH7 0.45	6D3 0.55	6K7 0.43	12E1 3.00	35B5 0.65	PCF808 0.00	U18 20 0.75	UL41 0.65
6AH6 0.80	6DC6 0.60	6K7 0.43	12E1 3.00	35C5 0.60	PCF808 0.00	U25 0.85	UL84 0.43
6AJ3 0.40	6DE6 0.60	6K7 0.43	12E1 3.00	35DE 2.90	PCF808 0.00	U26 0.85	UM84 0.60
6AK5 0.80	6DQ6B 0.75	6K7 0.43	12E1 3.00	35LG4 0.75	PCF808 0.00	U31 0.70	UV1N 0.50
6AK6 0.60	6DS4 1.25	6K7 0.43	12E1 3.00	35W4 0.40	PCF808 0.00	U37 6.50	UY11 1.80
6AL3 0.43	6EA8 0.65	6K7 0.43	12E1 3.00	35Z3 0.75	PCF808 0.00	U52 0.40	UY41 0.43
6AL5 0.22	6E17 0.30	6K7 0.43	12E1 3.00	35Z4 0.40	PCF808 0.00	U76 0.40	UY82 0.80
6AM6 0.37	6EJ7 0.35	6K7 0.43	12E1 3.00	60A5 0.80	PCF808 0.00	U78 0.40	UY85 0.40
6AQ3 0.42	6EW6 0.70	6K7 0.43	12E1 3.00	50B5 0.70	PCF808 0.00	U91 0.75	W729 0.75
6AQ6 0.70	6F1 0.75	6K7 0.43	12E1 3.00	60C5 0.60	PCF808 0.00	U201 0.50	XC12 0.60
6AR5 0.55	6F5 0.75	6K7 0.43	12E1 3.00	60D6 0.60	PCF808 0.00	U281 0.55	Y63 0.75
6AR6 0.65	6F6G 0.45	6K7 0.43	12E1 3.00	DK92 0.70	PCF808 0.00	U281 0.55	Z769 2.60
6AS5 0.50	6F11 0.50	6K7 0.43	12E1 3.00	50L6 0.65	PCF808 0.00	U282 0.55	Z5048 4.50
		6K7 0.43	12E1 3.00	50L6GT 0.60	PCF808 0.00	U301 0.65	Z5058 7.00
		6K7 0.43	12E1 3.00	85A2 0.65	PCF808 0.00	U403 0.70	Z803U 1.35

First Quality Fully Guaranteed




BRAND

ELECTRONIC VALVES

30C17 1.10	90AG 2.40	DM160 0.68	ECC88 0.40
30C18 0.90	90AV 2.50	DM161 0.55	ECC89 0.50
30F5 1.00	90CV 0.75	DY86 0.35	ECC91 0.30
30FL1 0.30	90CV 2.40	DY87 0.38	ECC189 0.65
30FL12 1.10	807 0.60	DY82 0.87	ECC807 1.90
30FL14 0.90	811A 1.60	E80F 1.35	ECP80 0.35
30L1 0.40	813 4.00	E8CC 0.70	ECP82 0.35
30L15 0.95	866A 0.85	E180F 1.00	ECP8041.65
30L17 0.95	884 0.75	E181F 2.90	ECH42 0.75
30P12 1.00	8642 0.70	EABC800.38	ECH81 0.30
30P19 0.95	6080 1.75	EAF42 0.60	ECH83 0.45
30P19 0.95	6146 1.60	EBC82 0.60	ECH84 0.45
30PL13 1.10	6146B 2.50	EBC41 0.65	ECL80 0.50
30PL14 1.25	6360 1.25	EBC81 0.33	ECL81 0.50
35A5 0.60	6929 2.25	EBF80 0.40	ECL82 0.35
35A5 0.75	7199 0.85	EBF83 0.40	ECL83 0.75
35B5 0.65	7886 1.50	EBF89 0.32	ECL84 0.55
35C5 0.60	7895 1.50	EBL31 1.50	ECL85 0.85
35DE 2.90	A2293 2.90	EBC82 0.60	ECH84 0.45
35LG4 0.75	AZ1 0.60	EBC80 2.65	ECLL800
35W4 0.40	AZ31 0.55	EC86 0.60	3-20
35Z3 0.75	CBL1 0.99	EC88 0.60	EF9 1.00
35Z4 0.40	CBL31 1.00	EC90 0.35	EF97A 0.90
60A5 0.80	CY1 0.80	ECC2 0.45	EF40 0.50
50B5 0.70	CY21 0.50	EC93 0.60	EF41 0.45
60C5 0.60	DAF96 0.50	ECC35 1.00	EF42 0.70
60CD6G1.20	DF96 0.50	ECC40 0.70	EF80 0.30
DK92 0.70	DK92 0.70	ECC81 0.40	EF85 0.35
50L6 0.65	DK96 0.40	ECC82 0.33	EF86 0.30
50L6GT 0.60	DR16 0.55	ECC83 0.33	EF89 0.25
85A2 0.65	DM70 0.60	ECC84 0.30	EF91 0.67
			FABC800.55


TRANSISTORS

2N696 0.15	AC128 0.15	BDJ21 0.65
2N697 0.15	AC132 0.35	BD123 0.80
2N698 0.80	AC135 0.20	BD124 0.60
2N701 0.70	AC154 0.15	BD131 0.75
2N706 0.10	AC157 0.17	BD132 0.80
2N708 0.15	AC169 0.10	BF115 0.20
2N753 0.25	AC176 0.17	BF167 0.18
2N929 0.20	AC187 0.25	BF179 0.30
2N980 0.20	AC188 0.25	BF180 0.30
2N987 0.20	AC198 0.25	BF181 0.30
2N1351 0.25	ACY17 0.20	BF184 0.30
2N1132 0.25	ACY19 0.25	BF185 0.20
2N1184 1.25	ACY20 0.20	BF194 0.14
2N1302 0.17	ACY21 0.20	BF195 0.14
2N1303 0.17	ACY22 0.10	BF196 0.12
2N1804 0.20	AD13 0.20	BF197 0.12
2N1305 0.20	AD19 0.45	BF200 0.35
2N1806 0.25	AD161 0.35	BFW87 0.35
2N1807 0.25	AD162 0.35	BFW88 0.20
2N1808 0.25	ADZ11 1.25	BFW89 0.20
2N1809 0.25	ADZ12 1.25	BFW91 0.20
2N1613 0.17	AF14 0.17	BFX88 0.20
2N1711 0.20	AF15 0.17	BFY17 0.40
2N1766 0.75	AF16 0.17	BFY19 0.25
2N2147 0.75	AF17 0.17	BFY50 0.20
2N2160 0.80	AF18 0.30	BFY51 0.20
2N2217 0.25	AF126 0.30	BFY52 0.20
2N2218 0.20	AF127 0.20	BFY26 0.17
2N2219 0.20	AF180 0.35	BFY27 0.15
2N2389A 0.15	AF181 0.35	BFY28 0.17
2N2477 0.65	AF186 0.40	BFY65 0.20
2N2646 0.40	AF239 0.38	BSY95A 0.12
2N2905 0.25	AFZ11 0.45	OC16 0.50
2N2923 0.18	AFZ12 1.00	OC22 0.50
2N2924 0.18	AS726 0.25	OC23 0.60
2N2936 0.19	AS727 0.30	OC24 0.60
2N3063 0.20	AS728 0.25	OC24 0.35
2N3064 0.50	AS729 0.30	OC26 0.25
2N3065 0.80	AS754 0.25	OC29 0.60
2N3133 0.25	ASZ15 0.70	OC35 0.50
2N3134 0.25	ASZ16 0.70	OC36 0.45
2N3391 0.17	ASZ17 0.75	OC42 0.20
2N3392 0.17	ASZ18 0.75	OC44 0.15
2N3393 0.15	ASZ20 0.25	OC45 0.12
2N3394 0.15	ASZ21 0.40	OC70 0.10
2N3395 0.20	BC107 0.10	OC71 0.12
2N3402 0.15	BC108 0.10	OC72 0.12
2N3403 0.15	BC109 0.10	OC73 0.30
2N3404 0.20	BC110 0.10	OC75 0.15
2N3414 0.20	BC113 0.10	OC76 0.15
2N3415 0.15	BC134 0.20	OC78 0.25
2N3417 0.25	BC147 0.10	OC78D 0.20
2N3702 0.10	BC148 0.10	OC81 0.20
2N3703 0.10	BC149 0.12	OC81D 0.20
2N3704 0.13	BC152 0.15	OC83 0.20
2N3707 0.12	BC159 0.15	OC139 0.30
2N3709 0.10	BC158 0.15	OC140 0.15
2N3710 0.10	BC175 0.20	OC141 0.60
2N3819 0.35	BC186 0.25	OC170 0.25
2N3906 0.25	BCY30 0.25	OC171 0.25
2N3702 0.60	BCY31 0.30	OC200 0.60
2N3745 0.25	BCY32 0.25	OC201 0.30
AC113 0.15	BCY34 0.25	OC202 0.65
AC126 0.80	BCY72 0.15	OC202 0.65
AC126 0.80	BCZ10 0.30	OC203 0.40
AC127 0.17	BCZ11 0.40	OC204 0.40

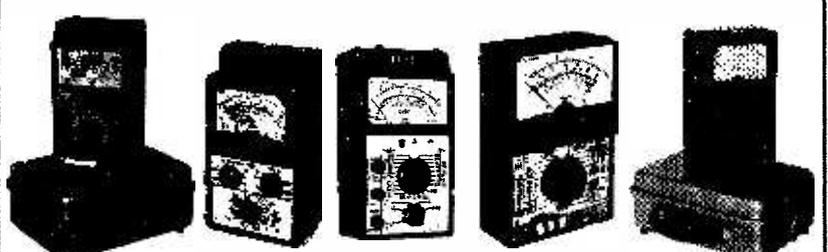

MULTIMETERS MADE IN USSR
Prices of these exceptionally well made instruments range from £4.95 to £10.50. Please write for illustrated catalogue.

SYNCHROSCOPE TYPE C1-5

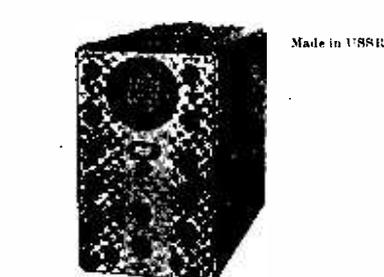

Made in USSR
3-in tube fitted with telescopic viewing hood, giving bright display in full daylight. Sensitivity 10mV/mm (narrow band) to 30mV/mm (wide band). Bandwidth 10 c/s—10 mc/s. Triggered sweep pre-set at 1-2-5-10-30-100-300-1000-3000 μ sec per stroke. Free-running time base 20 c/s to 200kc/s with built-in crystal calibrator providing timing marks at 0.5-2-10-20-100 μ sec. Amplitude calibrator directly calibrated in volts. Input attenuator 1-10-100. Power supplies 127/230v AC. PRICE £39.00. Packing and carriage £1.50.

Series BZXK1 1-watt ZENER Diodes Available in: 7-5-8-2-11-15-16-24-27-30-33-36-62-68 volts. 20-20 each.

DIODES			
OAS 0.25	OASJ 0.07	OAS 0.12	OASB 0.07
OAS 0.15	OASB 0.15	OAS 0.20	OASD 0.07
OAS 0.07	OASE 0.07	OAS 0.07	OASJ 0.07
OAS 0.07	OASK 0.07	OAS 0.07	OASL 0.07
OAS 0.07	OASM 0.07	OAS 0.07	OASN 0.07
OAS 0.07	OASO 0.07	OAS 0.07	OASP 0.07
OAS 0.07	OASQ 0.07	OAS 0.07	OASR 0.07
OAS 0.07	OASS 0.07	OAS 0.07	OAST 0.07
OAS 0.07	OASU 0.07	OAS 0.07	OASV 0.07
OAS 0			

Which of these 165 career opportunities could earn you £10... £15...even £30 extra a week?

How to qualify in your spare time for a better job

In a job you really enjoy

Make yourself *worth* more and you'll earn more. It's as simple as that. There are always plenty of people to do the routine work - but, right now, key jobs are going begging for lack of suitably qualified men to fill them. *The basic qualification is technical know-how.* When you've got that, you're in demand - out in front.

Are you ambitious - willing to set aside about 60 minutes a day for home study? If you are, B.I.E.T. can give you the technical knowledge you need - change your entire future prospects.

It's easier than you think...

Make no mistake about it - you *could* do it. Most people have unused ability. A low-cost B.I.E.T. course helps you discover this hidden ability - makes learning enjoyable and so much easier than it used to be. The B.I.E.T. simplified study system gets results fast.

We've successfully trained thousands of men at home - equipped them for higher pay and better, more satisfying jobs, steered them safely through City and Guilds examinations - enabled many of them to put letters after their name.

With the help of B.I.E.T., you too could soon be on your way to better things.

OTHERS HAVE DONE IT - SO CAN YOU

Many of the successful B.I.E.T. students who get a recognised qualification never thought they had the brains to do it. But you don't need outstanding brain-power or talent - not even any special education. With enthusiasm, a little determination and a B.I.E.T. home training, ordinary, average ability will see you through. We've proved it over and over - *thousands* of times, in fact!

BEST VALUE FOR MONEY HE EVER OBTAINED.

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course" - *Student D.I.B., Yorks.*

HE GOT OUT OF A BAD JOB INTO ONE HE LOVED.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects" - *Student J.A.O., Dublin.*

HE MADE FOUR TIMES AS MUCH MONEY.

"My training with B.I.E.T. quickly changed my earning capacity and in the next few years, my earnings increased fourfold" - *Student C.C.P., Bucks.*

FREE 76-PAGE BOOK

can put you on the road to success through a B.I.E.T. Home Study Course. It's yours for the asking, without obligation. Post coupon for your **FREE COPY TODAY!**

ACT NOW - DISCOVER FOR YOURSELF

It costs no more than a stamp to find out how we can help you. Tick the subject that interests you. Then post the coupon (or write). We'll send you an interesting 76-page book that will open up for you a whole new world of opportunity - and it's **FREE**.

B.I.E.T., Aldermaston Court, Reading RG7 4PF.



Choose from this list

MECHANICAL
A.M.S.E. (Mech.)
C & G Agric.
Mechanics
Diesel Eng.
Eng. Inspection
Eng. Metallurgy
Inst. Eng. & Tech.
Inst. Motor Ind.
Mainten. Eng.
Mechanical Eng.
Sheet Metal Work
Welding

ELECTRICAL & ELECTRONIC
A.M.S.E. (Elec.)
C & G Agric.
Mechanics
C & G Elec. Eng.
C & G Elec. Inst.
C & G Elec. Tech.
Computer Elect.
Elec. Maths
Elec. Science
Electronic Eng.
Electrical Eng.
Install & Wiring

MANAGEMENT & PRODUCTION
Auto. Control
Computer Prog.
Electronic Data
Processing
Estimating
Foremanship
Inst. Cost & Man.
Accountants
Inst. Marketing
Management
Metrication
Motor Trade Man.
Network Plan.
Numerical Cont.
Operational
Research
Personnel Man.
Planning Eng.
Production Eng.
Quality Control
Salesmanship
Storekeeping
Work Study
Works
Management

AUTO & AERO
Aero Eng.
A.M.I.M.I.
A.E.C. Cert.
A.E.C. Engineer.
Auto Repair
C & G Auto. Eng.
Garage
Management
MAA/TMI Dipl.
Motor Vehicle
Mechanics

CONSTRUCTIONAL
A.M.S.E. (Civil)
Architecture
Building
Building Drawing
Build. Foreman
C & G Agric.
Mechanics
Carpentry & Join.
Civil & Municipal
Engineering

DRAUGHTSMANSHIP
A.M.I.E.D.
Design of Elec.
Machines
Die & Press Tool
Design
Electrical
Draughtsman-
ship
Gen. Draughts-
manship
Jig & Tool Des.
Techn. Drawing

RADIO & TELECOMMUNICATIONS
Colour TV
C & G Radio/TV/
Electronics
C & G Telecomm.
Tech.
Prac. Radio Elec.
(with kit)
Radio Amateurs
Exam.
Radio Servicing
& Repairs
Radio & TV Eng.
Trans. Course
TV Main. & Serv.

CONSTRUCTIONAL
Engineering
Construction
Surveyors
Institute
Clerk of Works
Geology
Health Eng.
Hydraulics
Inst. of Builders
Inst. Works &
Highway Sup.
Painting & Dec.
Public Hygiene
Road Engineer.
Structural Eng.
Surveying

GENERAL
Council of Eng.
Inst.
Farm Science
General Educat.
Gen. Plastics
Fract. Maths
Fract. Slide Rule
Pure & Applied
Maths
Refrigeration
Rubber Tech.
Sales Engineers
Tech. Report
Writing
Timber Trade
University Ent.

PLUS 58 'O' & 'A' LEVEL GCE SUBJECTS

tick here

Coaching for many major exams, including C & G and assistance in ONC/HNC.

IT PAYS TO BE QUALIFIED! POST TODAY FOR A BETTER TOMORROW

To **B.I.E.T., Aldermaston Court, Reading RG7 4PF QK** BPW08
Please send full details and FREE 76-Page Book, without obligation.

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____

Accredited by C.A.C.C.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

BUILD THE TEXAN

★ FREE TEAK CABINET with complete kits!

FEATURES. New slim design with 6 x IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).
Constructional details Ref. No. 21 30p

SPECIAL KIT PRICE **£28-50**

P & P 45p COMPLETE WITH FREE TEAK CABINET Designer approved kits distributed by Henry's!

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



P.W. Tricolour as per April/May June 1973. Parts list on request (52A).

★ SLIM DESIGN WITH SILVER TRIM Overall chassis size 14 1/2" x 6" x 2" high

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 or request.

IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January 1973. Article Reprint Ref. No. 19 10p. Price £1-20.

BATTERY TAPE DECK

Garrard 9 volt Tape Deck with heads, etc. As previously advertised. Limited quantity. £9-50, post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish Italian. £1-36 per course. £5-00 per set of four.

DISCO SPOTBANK

3 channel Disco Spotbank for use with any psychedelic lighting display. £12-75, p. & p. 35p.

HI-FI EQUIPMENT

Warehouse of Hi-Fi with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES. FREE—24 page detailed brochure (Ref. No. 17). You can see the savings!

HIGH QUALITY CASSETTES

The best UK low noise tapes but at a special price. 'Living Sound' cassettes meet the highest international standard (IEC 94A). Fantastic price savings.

	3 for	6 for	10 for
C60	1-00	1-80	2-80
C90	1-33	2-14	2-20
C120	1-62	3-15	5-00

Full guarantee. Post paid. Made by EM! especially for Henry's.

ULTRASONIC TRANSDUCERS

Operate at 40Kc up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits. £5-90 per pair. Post 10p.

MARriot TAPE HEADS

4 TRACK 40Kc or 2 TRACK STEREO '17' High Impedance £2-00 '18' Med. Impedance £2-03 '36' Med.-Low Imp. £3-50 Erase Heads for above 75p '63' 2 track mono—£1-75 'Hi Imp. £1-75 '43' Erase Head for above 75p

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6) XN3, XN13, GN6 0-9 side view with data, 85p. GNP7, GNP8 0-9 side view with decimal points and data, 95p. 3015F 7 seg £2 each. £7 per 4 with data. 12 and 24 hour clock circuits Ref. No. 31 15p.


Miniature Amplifier

5 transistor, 300mW o/p. Fitted volume and sensitivity control, 9 volt + operated. £1-75 each P/P 15p.

Quality Slider Controls

60mW stereo singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K. 1 meg, Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged. 60p each.

LOW COST HI-FI SPEAKERS

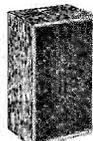

E.M.I. Size 13 1/2" x 8 1/2" Large Ceramic Magnet. TYPE 150 6 watt; 3, 8 or 15 ohms £2-20. Post 22p. TYPE 150 TC Twin cone version £2-75. Post 22p. TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3-50. Post 25p. TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7-50. Post 28p.




POLISHED CABINETS 150, 150TC 450 £4-60. Post 30p. ASSEMBLED IN POLISHED CABINETS (8 ohms) SERIES 6 (Assembled 150 TC) per pair £16-50. Post 70p. SERIES 8 (Assembled 450) per pair £18-95. Post 70p.

TEST EQUIPMENT

Just a selection!
SE250B Pocket Pencil Signal Injector £1-90
SE500 Pocket Pencil Signal Tracer £1-50
THL33D Robust 2K/Volt £4-55 with case £4-95
TE15 Grid Dip Meter 440 KHz-280 mHz £13-45
500 K/V Multimeter £9-25
With leather case £10-50
200H 20K/V Multimeter £4-20. With case £4-95
AF105 50K/V Multimeter £8-50. With case £9-50
U4341 AC/DC Multimeter with transistor tester with steel case £10-50
TE20D RF Generator 120KHz-500MHz £16-50. Carr. 35p
TE22D Audio Generator 20Hz-200KHz £17-50. Carr. 35p
CI-5 Pulse Scope 10Hz-10MHz £39-00. Carr. 50p
TE65 Valve Voltmeter 28 ranges £17-50. Carr. 40p
ALL NOMBEX MODELS IN STOCK



ML-3 MW/LW TUNER TO BUILD

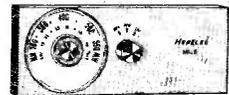

Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4-85. Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD




Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull outputs fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7-98 p.p. 32p. (Battery 22p).

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.


Post Paid 55p (40p FOR CALLERS) PLUS! FIVE 10p VOUCHERS

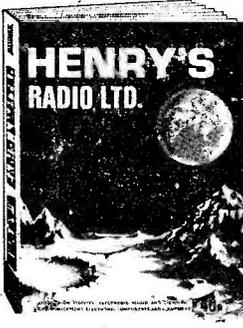Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1— for catalogue by post only. All other mail and callers to "303" see below.



PA-Disco-Lighting

UK's Largest Range—Write phone or call in. Details and demonstrations on request.
DJ30L 3 Channel sound to light unit, 3KW. £29-50
DJ40L 3 channel Mic (built-in) to light, 3KW. £38-75
DJ70S 70 watt Disco amp/mixer. £49-75
DISCOAMP 100 watt amp/mixer. £68-85
DJ105S 30 watt Disco amp/mixer. £32-25
Anti-feedback Quality Mic. £11-50
DJ500 50 watt PA Amplifier £43-95
DJ700 70 watt £52-75
DJ1000 100 watt £63-00
GROUP 300 150 watt rms "Group" Valve Amplifier £86-00
FIBRE OPTICS LIGHTING — MICS, EFFECTS, PROJECTORS, SPOTS, DIMMERS — STANOS, MIXERS, SPEAKERS.
Everything for PA — Disco — Lighting. FREE Stock List Ref. No. 18
● PORTABLE DISCOS — DETAILS ON REQUEST
● CREDIT TERMS FOR CALLERS

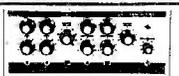

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH PRINTS CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6-97, p.p. 20p. Mk. I Decoder Kit £5-97. Built IC Decoder £6-50. Tuning meter unit £1-75. Mains unit for Tuner and/or Decoder PS6/12 £3-25. Post 20p



SINCLAIR PROJECT 60 MODULES — SAVE POUNDS!

Z30 £3-57; Z50 £4-37
STEREO 60 PZ5 £3-97
£7-97; PZ8 £4-77
PZ6 £6-37;



Transformer for PZ8 £2-99
Active Filter Unit £4-45
Stereo FM Tuner £16-95
IC12 £1-90; Q16's £15 pr.
Post etc. 20p per item

PACKAGE DEALS Post 25p
2xZ30, Stereo 60, PZ5 £15-95
2xZ30, Stereo 60, PZ6 £18-00
2xZ50, Stereo 60, PZ8 £20-25
Transformer for PZ8 £2-95
PROJECT 60S KIT £19-95

VAT All prices are exclusive of 10% VAT which must be added to all orders inc. carr/packing. (Note: Catalogue is not subject to VAT).

See earlier page of this magazine for transistors, I.C.'s and Semi Conductor prices—latest list Ref. no. 36 on request. E. & O.E.

Henry's RADIO LIMITED
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open: 9 am-6 pm
6 days a week
(309 closed Thursday)
All stores open all day Saturday