

PRACTICAL WIRELESS

NOVEMBER
1973

20p

free 2 MORE CARDS



PLUS

extra 8 PAGE
ILLUSTRATED SUPPLEMENT
DICTIONARY
of
AUDIO TERMS

PW

'ferret'

**PHASE
LOCKED
LOOP I.C.**

**METAL
DETECTOR**




Henry's

**DONT RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**

Order your latest Henry's Catalogue Price 55p post paid complete with Discount Vouchers

Henry's
1974 Catalogue

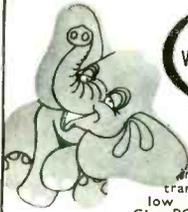

You pay less
VAT with Henry's
Low Prices

BUILD THE TEXAN

**20 + 20 WATT IC
STEREO AMPLIFIER**

As featured by
Practical Wireless
1972



Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15" x 2 1/2" x 6 3/4". 6-IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES.** On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21 30p. Distributed by Henry's throughout UK. FREE—Teak cabinet with complete kit.

Kit price **£28.50** (+VAT +50p carr/packing) or built and tested **£35.00** (+VAT +50p carr/packing) as illustrated.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators. Tuning meter. AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 3/4". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe.





KIT PRICE **£21.00** (+ VAT)
or built and tested **£24.95** (+ VAT)

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98.50**
- 100 watt amplifier for above **£38.75**
- SL100 100 watt mixer/amplifier with slider controls **£69.00**
- R50 50 watt mixer/amplifier **£49.50**
- DISCO AMP 100 watt mixer/amplifier chassis unit. **£65.85**
- DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers)
- SDLI (rotary controls) **£49.50**
- SDLII (slider controls) **£58.50**
- DISCO VOX (slider controls) the complete disco unit **£69.50**
- DJ100 100 watt power amplifier for above **£38.75**
- DJ30L 3 channel 3kw sound to light **£29.50**
- DJ40L as 30L plus built in microphone **£38.75**
- DIMANATIC 1 kW adjustable speed auto dimmer **£25.00**
- SCENE STROBE **£19.00**. ROAD STROBE **£25.00**
- Disco anti-feedback microphone **£11.95**
- Colt 150 watt liquid wheel projector **£22.50**
- 150 watt QI liquid wheel projector **£50.00**
- 150 watt QI cassette wheel projector **£50.00**
- Spare Effects cassettes large range of patterns **£8.00**
- Mini spot bank fitted 3 lamps **£11.00**
- Auto Trilite (mini with flashers) **£17.00**
- Mixer/Mics/Speakers/Lighting UK's largest range.

FREE stock list ref. No. 18 on request.

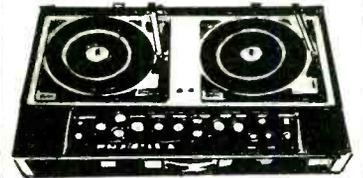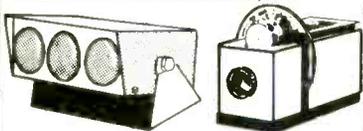

All prices carr. paid (UK) (VAT EXTRA)
Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

TEXAN STEREO SYSTEM PLUS PRICE SAVINGS



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200, 20 watt Speaker-Tweeter systems size 2 1/2" x 1 1/2" x 10" and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

System 25 (list approx. £109) **£79.50**
System 76 (list approx. £117) **£89.50**
(plus 10% VAT and plus £1.45 carr/packing)

Barclaycard/Access, call, write or phone, your order 01 402 4736
EASY TERMS FOR CALLERS

- KITS—TEST GEAR—
- AMPLIFIERS—
- SPEAKERS—DECKS—
- POWER SUPPLIES—
- TRANSISTORS—IC's

See pages 586—588 of this magazine

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S.

ALL TOP PAID LESS THAN 1/3 REC. PRICES

	3 for	6 for	10 for	25 for
C 60	£1.00	£1.80	£2.80	£6.75
C 90	£1.33	£2.57	£4.20	£10.25
C 120	£1.62	£3.15	£5.00	£12.25



Quantity and trade enquiries, invited
LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian £1.36 per course. £5 for any 4.

LOW COST HI-FI SPEAKERS

SPECIAL OFFERS

- EM1 13" x 8" —full range speakers (post 20p each or 30p pair)
- *150TC—8 ohms 1" twin Cone 10 watt **£2.20** each or **£4.00** pair.
- *450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms **£3.50** each or **£6.90** pair.
- EW 15 watt 8 ohms C/o Tweeter **£4.30** each or **£7.90** pair.
- 350 20 watt C/o Tweeters 8 or 15 ohms **£7.50** each or **£14.20** pair.
- * Polished wood cabinet **£4.60** post 35p.



8 ohms full range (post 20p)			
FR4	4"	5 watt	£4.00
FR65	6 1/2"	10 watt	£5.50
FR8	8"	15 watt	£7.60
FR23	9 x 6"	15 watt	£6.00
BASS & MID RANGE—8 ohms (post 20p)			
AA12	5"	15 watt	£3.20
B110	5 1/2"	15 watt	£5.60
B200	8"	15 watt	£6.45
B139/2	13" x 8"	30 watt LF	£10.25
TWEETERS AND CROSSOVERS (post 20p)			
K2006	10 watt	8 or 15 ohms	£1.90
FHT76	15 watt	8 ohms	£3.20
K2011	30 watt	8 ohms	£3.75
T27	KEF	8 ohms	£4.25
Axcnet 100	30 watt	8 ohms	£4.90
K4009	1kHz/5kHz C/o		£2.00
SN75	3kHz var. C/o		£1.75
SPEAKER KIT (carr. etc. 35p)			
20-3	8"	30 watt	£10.00 each
20-3	8"	40 watt	£15.00 each
LINTON 2		20 watt	£15.95 pair
GLENDALE 3		30 watt	£28.95 pair
DOVEDALE 3		50 watt	£42.00 pair
KEF KK2			£20.40 each
KEF KK3			£32.00 each

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines etc.



£24.95 Also available assembled ready to use. **£27.22** + VAT. + VAT.

10% VAT to be added to all orders. Prices and descriptions correct at time of press. E & OE.

Henry's LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:-
9 am-6 pm
6 days a week
All stores
open all day
Saturday

PRACTICAL WIRELESS

VOL. 49 NO. 7

ISSUE 801

NOVEMBER 1973

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR Morris A. Colwell

ASSISTANT EDITOR
Lionel E. Howes, G3AYA

ART EDITOR Peter Metalli

TECHNICAL EDITOR
Richard Dowdeswell, G4AR

**PRODUCTION & NEWS
EDITOR** Colin R. Riches

PROJECTS SUB-EDITOR
Geoffrey C. Arnold

TECHNICAL ARTIST
Alan Martin

SECRETARIAL
Jenny Maunder
01-634 4292 Susan Corne

ADVERTS. MANAGER
01-634 4293 Roy Smith

CLASSIFIED ADVERTS.
01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rates for one year to any part of the world £2.65 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.10) and indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 614 AUTUMN ACTION—Leader article and December preview
- 615 NEWS . . . NEWS . . . NEWS
- 626 TELEVISION—Coming in the November issue
- 629 PRODUCTION LINES—Products reviewed by *Colin Riches*
- 630 SPECIAL PRODUCT REPORT—Sinclair Cambridge Calculator kit
- 640 NEXT MONTH in *Practical Wireless*
- 645 DEAR SIR—Readers' letters to the Editor
- 653 HOTLINES on recent developments by *Ginsberg*
- 659 BASIC COLOUR FAULTS—Colour supplement in Television
- 660 ON THE AIR—Reports on Broadcast Bands
- 660 Short Wave—*Malcolm Connah*
- 663 Medium Wave—*Charles Molloy*
- 663 VHF/FM—*Simon David*
- 664 Amateur Bands, Short Wave/VHF—*David Gibson G3JDG*

● CONSTRUCTIONAL

- 616 PORTABLE VHF RECEIVER—*F. G. Rayer G3OGR*
- 634 "P.W. FERRET" PLL METAL DETECTOR—*R. P. A. Perry*
- 641 EXPERIMENTAL WORKSHOP Bistable Switching—
M. J. Hughes, M.A.
- 648 GOING QUADRAPHONIC—PROJECT Q4, Part 2—*D. Bollen*
- 654 TAKE 20 No. 54 "Radio-Gram"—*David Andrews*
- 657 I.F. WOBULATOR—*W. S. Poel G8CYK*
- 668 SIMPLE TRANSMITTER-RECEIVER CONTROL BOX—
R. H. Longdon

● OTHER FEATURES

- 620 I.C. OF THE MONTH LM101A/LM111—*L. A. J. Ireland*
- 621 TECHNICROSS No. 1—Technical Crossword
- 622 BETTER AERIALS FOR BETTER STEREO Part 3—*Gordon King*
- 633 MORE ON THE ZN414 I.C. radio chip—*L. A. J. Ireland*
- 666 GOING BACK Equipment of yesteryear—
Colin Riches and Arthur Dow

● EXTRA WITH THIS ISSUE

INSET

P.W. DATACARDS in COLOUR
No. 3 Audio Plugs and Sockets
No. 4 Using Decibels

SUPPLEMENT DICTIONARY OF AUDIO TERMS (Illustrated)

FREE BOOKLET

All types of

TRANSISTORS RECTIFIERS
BRIDGES—SCR'S—TRIACS
INTEGRATED CIRCUITS
F.E.T.—LIGHT DEVICES

OVER 1500 DIFFERENT DEVICES

ENTIRELY NEW 1973 EDITION

SEND FOR YOUR FREE COPY TODAY



More Devices
New Prices
New Ranges

This is a must for all

Semi-conductor Users

(ask for booklet No. 36)

INTEGRATED CIRCUITS VERY IMPORTANT. ONLY branded I.C.'s

are to the FULL manufacturers specifications. ALL others are not. Henry's sell only branded Integrated Circuits... From TEXAS... I.T.T. FAIRCHILD... SIGNETICS. So why buy alternatives or under spec. devices when you can purchase the genuine article from us—ex stock... need we say more!



Type	1/11	12/29	30/39	Type	1/11	12/29	30/39	Type	1/11	12/29	30/39
£ p	£ p	£ p	£ p	£ p	£ p	£ p	£ p	£ p	£ p	£ p	£ p
8N7400N	0.20	0.18	0.16	8N7448N	1.50	1.27	1.13	8N74142N	2.88	2.88	2.52
8N7401N	0.20	0.18	0.16	8N7449N	0.20	0.18	0.16	8N74143N	1.44	1.44	1.28
8N7402N	0.38	0.38	0.38	8N7450N	0.20	0.18	0.16	8N74144N	2.30	2.30	1.83
8N7403N	0.20	0.18	0.16	8N7451N	0.20	0.18	0.16	8N74148N	2.01	2.01	1.63
8N7403AN	0.38	0.38	0.38	8N7452N	0.20	0.18	0.16	8N74150N	2.30	2.30	2.01
8N7404N	0.24	0.21	0.18	8N7453N	0.20	0.18	0.16	8N74151N	1.15	1.15	1.00
8N7405N	0.20	0.18	0.16	8N7454N	0.20	0.18	0.16	8N74153N	1.09	1.09	0.95
8N7405AN	0.20	0.18	0.16	8N7455N	0.38	0.38	0.34	8N74156N	2.58	2.58	2.52
8N7406N	0.40	0.38	0.35	8N7456N	0.37	0.41	0.37	8N74158N	1.15	1.15	1.00
8N7407N	0.40	0.38	0.35	8N7457N	0.48	0.48	0.42	8N74159N	1.09	1.09	1.00
8N7408N	0.25	0.22	0.19	8N7458N	0.58	0.55	0.51	8N74160N	2.44	2.44	2.14
8N7409N	0.33	0.33	0.28	8N7459N	0.80	0.70	0.50	8N74161N	1.58	1.58	1.38
8N7409AN	0.44	0.44	0.38	8N7460N	0.20	0.18	0.16	8N74162N	1.58	1.58	1.38
8N7410N	0.27	0.27	0.25	8N7461N	1.25	1.10	0.95	8N74163N	1.58	1.58	1.38
8N7411N	0.25	0.23	0.21	8N7462N	0.87	0.80	0.72	8N74164N	2.01	2.01	1.78
8N7412N	0.28	0.28	0.25	8N7463N	1.20	1.10	1.00	8N74165N	2.01	2.01	1.78
8N7412AN	0.38	0.38	0.33	8N7464N	1.87	1.87	1.63	8N74166N	2.16	2.16	1.89
8N7413N	0.30	0.27	0.25	8N7465N	0.50	0.50	0.44	8N74167N	4.10	4.10	3.58
8N7414N	0.72	0.72	0.63	8N7466N	4.32	4.32	3.78	8N74168N	2.16	2.16	1.89
8N7416N	0.20	0.27	0.25	8N7467N	0.75	0.70	0.63	8N74169N	2.88	2.88	2.52
8N7417N	0.30	0.27	0.25	8N7468N	0.75	0.70	0.63	8N74170N	2.88	2.88	2.52
8N7420N	0.20	0.18	0.16	8N7469N	0.75	0.70	0.63	8N74171N	5.78	5.78	5.04
8N7422N	0.28	0.28	0.25	8N7470N	0.85	0.80	0.75	8N74173N	1.66	1.66	1.45
8N7422AN	0.38	0.38	0.33	8N7471N	0.85	0.80	0.75	8N74174N	1.80	1.80	1.57
8N7423N	0.37	0.34	0.32	8N7472N	0.85	0.80	0.75	8N74175N	1.29	1.29	1.13
8N7425N	0.37	0.37	0.32	8N7473N	1.00	0.90	0.83	8N74176N	1.44	1.44	1.28
8N7427N	0.37	0.37	0.32	8N7474N	0.80	0.58	0.45	8N74177N	1.44	1.44	1.28
8N7428N	0.43	0.43	0.37	8N7475N	0.60	0.58	0.45	8N74178N	1.44	1.44	1.28
8N7430N	0.20	0.18	0.16	8N7476N	0.51	0.51	0.45	8N74181N	5.18	5.18	4.53
8N7432N	0.37	0.37	0.32	8N7477N	0.57	0.57	0.50	8N74182N	1.44	1.44	1.28
8N7433N	0.43	0.43	0.38	8N7478N	0.57	0.57	0.50	8N74184N	2.16	2.16	1.89
8N7434N	0.57	0.57	0.50	8N7479N	1.10	1.00	0.90	8N74185AN	2.16	2.16	1.89
8N7437N	0.43	0.43	0.37	8N7480N	0.57	0.57	0.50	8N74188N	6.48	6.48	5.87
8N7438AN	0.43	0.43	0.37	8N7481N	1.00	0.90	0.83	8N74190N	2.30	2.30	2.01
8N7440N	0.20	0.18	0.16	8N7482N	1.92	1.92	1.68	8N74191N	2.30	2.30	2.01
8N7441AN	0.85	0.79	0.73	8N7483N	1.05	1.05	0.92	8N74192N	2.30	2.30	2.01
8N7442N	0.57	0.57	0.50	8N7484N	0.67	0.67	0.60	8N74193N	2.30	2.30	2.01
8N7443N	1.50	1.27	1.13	8N7485N	0.69	0.69	0.60	8N74194N	1.44	1.44	1.28
8N7444N	1.50	1.27	1.13	8N7486N	0.69	0.69	0.60	8N74196N	1.58	1.58	1.38
8N7445N	2.16	2.16	1.89	8N7487N	0.72	0.72	0.63	8N74197N	1.58	1.58	1.38
8N7446N	2.16	2.16	1.89	8N7488N	0.63	0.63	0.55	8N74198N	3.18	3.18	2.72
8N7447AN	1.80	1.80	1.57	8N7489N	1.00	0.90	0.80	8N74199N	2.88	2.88	2.52

LARGER QUANTITY AND O.E.M. PRICES PHONE (01) 723 8646. PRICING OF
SNT400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED
REGARDLESS OF MIX. SNT4... HIGH POWER... SNT4... LOW POWER
SERIES IN STOCK... SEND FOR LIST 36, FREE ON REQUEST. LOW POWER
SOCKETS 14 PIN... 15p 16 PIN... 17p. 8 PIN... 14p

TRANSISTORS A SELECTION FOR FULL LIST SEND FOR BOOKLET 36 TODAY

AAZ13 10p	BC182 12p	BYZ13 35p	OC36 65p	ZTX108 10p	2N3714 1.60
AC107 35p	BCY39 1.00	C1060 55p	OC44 18p	ZTX300 14p	2N3771 1.75
AC128 20p	BCY55 2.00	GET111 55p	OC45 15p	ZTX302 18p	2N3773 2.25
AC187 20p	BCY65 1.50	GET115 75p	OC71 15p	ZTX600 15p	2N3790 2.25
ACY17 35p	BCY70 1.5p	GET125 75p	OC72 25p	ZG301 40p	2N3819 35p
ACY39 65p	BCY71 20p	GET280 55p	OC77 55p	2N697 15p	2N3866 75p
AD149 50p	BCY72 13p	LM309K	OC81 28p	2N706 10p	2N3903 15p
AD161 39p	BD124 30p	MAT121 87p	OC83 25p	2N930 20p	2N4002 14p
AD192 30p	BD131 45p	MAT121 87p	OC140 65p	2N987 45p	2N4128 15p
AF117 20p	BF115 22p	MJE340 50p	OC170 25p	2N1132 25p	2N4871 35p
AF118 50p	BF180 22p	MJE320 65p	OC210 55p	2N1304 22p	2N4547 38p
AF139 33p	BF194 13p	MJE3055	OC202 90p	2N1613 20p	2S001 3.00
AF186 40p	BFY13 25p	OC271 1.00	OC297 1.00	2N1671 1.00	2N6026 8.90
AF239 44p	BFY44 55p	ORP15 45p	ORP15 45p	2N2147 75p	2S303 70p
AFY37 30p	BFY48 22p	NKT217 45p	ORP60 45p	2N2160 69p	40250 45p
BA115 10p	BFY50 20p	NKT404 60p	P346A 20p	2N2926 10p	40361 45p
BAX13 5p	BFY51 20p	OA5 60p	T1L209 25p	2N3053 20p	40362 40p
BC107 12p	BFY64 45p	OA81 10p	T1P29A 45p	2N3054 45p	40408 50p
BC108 12p	BFY90 75p	OA200 8p	T1P30A 58p	2N3055 45p	40486 75p
BC109 12p	BLY36 6.25	OA202 10p	T1P31A 81p	2N3440 50p	40636 1.00
BC109C 14p	BFY20 15p	OC16 85p	T1P41A 74p	2N3442 1.10	40430 85p
BC113 16p	BU105 2.20	OC20 1.25	T1P42A 90p	2N3525 80p	
BC147 12p	BU100 15p	OC28 65p	T1S43 28p	2N3614 58p	
BC169C 14p	BY127 15p	OC35 55p	V405A 25p	2N3702 11p	

All types offered subject to availability. Prices correct at time of press E. & O. E. 10% VAT to be added to all orders. UK post, etc, 15p. per order.

TBA800 5 WATT I.C.
Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output.
With circuits and data £1 50




Sinclair IC12
with circuits and data. 6 watt IC with printed circuit board
28 volt operated £1 80



ZN414 IC
Integrated circuit radio as featured by many magazines (PW Jan. 73 Reprint Ref. No. 19 for 10p) £1 20



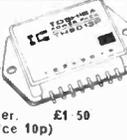
Toshiba Power and Preampifier modules
TH9013P 20 watt Power amplifier 22-0-22 or single 45 volts operated £4 57
TG9014P Stereo on two channel preampifier. £1 50 (circuit book No. 42 price 10p)



Ultrasonic Transducers
Operate at 40Khz up to 100 yds. Ideal remote switching and signalling. Complete with data transmitter and receiver new I.C. circuits.
Per pair £5 90



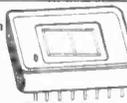3015F 7 SEC.
I.C. size complete with data price £2 each or 4 for £7 (digital clock circuits ref. No. 31, 15p)



TRANSISTORS SPECIAL OFFER

2N3055	25 47p ea	AF117	25 15p ea
100 42p	100 13p	500 38p	500 12p
500 34p	1000 10p		
BY127	25 12p ea	OC35	25 46p ea
100 10p	100 42p	500 9p	1000 8p
500 8p	1000 10p		

ZENER DIODES
400 mw BZY88/BZX83. From 3 volt - 33 volts 10p each

LINEAR I.C.
702C (T05) 75p
709C (T05) 39p
709C (D.I.L.) 39p
723C (T09) 90p
723C (D.I.L.) 90p
728C (D.I.L.) 45p
728C (T09) 45p
741C (T05) 50p
741C (D.I.L.) 50p
747C (T09) £1 0p
748C (D.I.L.) 61p

SILICON RECTIFIERS
1 amp series
IN4001 to IN4007
From 6p ea
PL4001 to PL4007
From 8p ea
3 amp
PL7001/IN5400
From 14p ea
Send for full list 36

MORE OF EVERYTHING AT HENRY'S
See pages 499-501, and Back Cover of this magazine.
BEST VALUE

TRIACS - Std. mounting with accessories
3 AMP RANGE
Type P.I.V. Price ea.
SC35A 100v 80p
SC35B 200v 85p
SC35D 400v 90p
SC35E 500v £1 20



6 AMP RANGE
SC40A 100v 90p
SC40B 200v 95p
SC40D 400v £1 20
SC40E 500v £1 50



10 AMP RANGE
SC45A 100v £1 05
SC45B 200v £1 15
SC45D 400v £1 45
SC45E 500v £1 85



15 AMP RANGE
SC50A 100v £1 45
SC50B 200v £1 65
SC50D 400v £1 95
SC50E 500v £2 25



TRIACS - Additional Types
40430 TRIAC (T066) 85p
40669 TRIAC (Plastic) 90p
40486 TRIAC (T05) 75p

NEW RANGES BRIDGE RECTIFIERS
FEATURES: SMALL SIZE AND LOW COST. Sizes, are approx.
250M/A QUARTER AMP
B025/05 50 PIV 16p
B025/10 100 PIV 18p
± x ± x ± dia.



1 AMP P.I.V.
B105 50v 25p
B110 100v 25p
B05/20 200v 23p
B05/40 400v 25p
B05/60 600v 27p
± x ± x ± dia.



2 AMPS P.I.V.
B205 50v 35p
B210 100v 40p
B220 200

Henry's

PANEL METERS • TRANSFORMERS • CONTROLS • RELAYS
 IRONS • TOOLS • VALVES • POT CORES MOST TYPES OF COMPONENTS
 You need a catalogue! 55p post paid complete with Discount Vouchers



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9.50 carr. 30p

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post. etc. 15p any quantity)
 Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.
 Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 65p each.
 (Quantity discounts available)
 Complete with knobs.

MARRIOTT TAPE HEADS


4 TRACK MONO or 2 TRACK STEREO
 '17' High Impedance £2.00
 '18' Med. Impedance £2.00
 R730/E73 2 track mono Record/Erase low Imp. 75p pair.
 Erase Heads for '17' and '18' 75p
 '83' 2 track mono, Hi Imp. £1.75
 '43' Erase Head for '63' 75p
 (Post. etc. 15p any quantity).

SINCLAIR & MINIATURE AMPLIFIERS

AMPLIFIERS (carr. etc. 20p)
 4-300, 0.3 watt 9 volt 1.75
 104, 1 watt 9 volt 2.20
 304, 3 watt 9 volt 2.50
 555, 3 watt 12 volt 2.85
 E1208, 5 watt 12 volt 4.50
 608, 10 watt 24 volt 4.10
 410, 10 watt 28 volt 4.95
 Z30, 15 watt 30 volt 3.57
 E1206, 30 watt 45 volt 9.75
 Z50, 30 watt 50 volt 4.37
 E1210, 2 1/2 + 2 1/2 watts 12 volt 5.25
 RE500, 5 watt IC mains operated Amplifier with controls £6.30
 SAC14, 7 + 7 watt Stereo with controls £8.00
 SAC13, 15 + 15 watt Stereo with controls £11.00


SINCLAIR UNITS (carr. 20p)
 Z30 3-57 Z50 4-37
 Stereo 60 Preampifier 7.97
 PZ5 £3.97, PZ6 £6.37
 PZ8 (for Z50) £4.77
 (TRANS £2.95)
 AFU £4.45

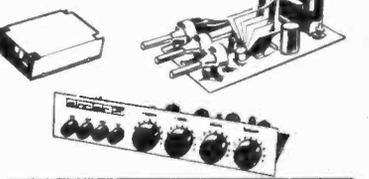SINCLAIR PACKAGE DEALS
 Post 25p
 2 x Z30, Stereo 60, PZ5 15.95
 2 x Z30, Stereo 60, PZ6 18.00
 2 x Z50, Stereo 60, PZ8 20.25
 Transformer for PZ8 2.95
 PROJECT 605 KIT 19.95



POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)
 470C 8 7/8 volt 300 MA (Includes Multi-Adaptor for Tape Recorders, etc.) 1.95 post 20p
 Car Lighter Voltage Adaptors 300mA (State voltage 6v, 7.5v, 9v) 1.95 ea. post 25p
 SC202 3/6/7 1/2 volt 400mA 3.25 carr. 30p
 HC244R Stabilised version 4.25 carr. 30p
 P500 9 volt 500mA 2.80 post 20p
 P11 24 volt 500mA (chassis) 2.80 post 20p
 P15 26/28 volt 1 amp (chassis) 2.70 post 20p
 P1080 12v 1 amp (chassis) 3.25 post 20p
 P1081 45v 0.9 amp (chassis) 4.40 post 20p
 P12 4 1/2-12 volt 0.4-1 amp 6.75 post 30p
 SE101A 3/6/9/12 volt 1 amp (Stab.) 9.15 post 25p
 RP164 6/7 1/2/9/12 1 amp (Stab.) 9.95 post 30p

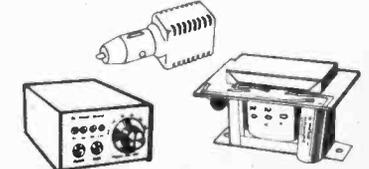


UK LTD

EASY TO BUILD—EVERYTHING SUPPLIED

Model No.	Description	Price
310	Radio control receiver	3.00
300	4-channel R/C transmitter	5.75
345	Superhet R/C receiver	5.08
450	TV sweep generator	10.24
455	AM signal generator	9.25
460	FM signal generator	9.91
65	Simple transistor tester	1.18
115	8 watt Amplifier	2.87
120	12 watt amplifier	3.88
125	Stereo control unit	4.20
130	Mono control unit	3.52
605	Power supply for 115	3.88
610	Power supply for 120	4.08
615	Power supply for 2 x 120	4.85
230	AM/FM aerial amplifier	2.79
240	Auto parking light	5.18
275	Mic. preamplifier	5.83
480	Electronic voltmeter	17.51
485	0-12v 300mA STAB. supply	9.68
570	LF generator 10Hz-1mHz	12.60
575	Sq. wave generator 20Hz-20KHz	12.87
590	SWR meter	10.24
620	NI-CAD Charger 1-2-12v	7.47
630	STAB Power supply 6-12v 0.25-0.1A	7.65
690	DC motor speed Gov.	2.63
700	Electronic Chaffinch	5.96
705	Windscreen wiper timer	5.56
760	Acoustic switch	8.87
780	Metal Detector (electronics only)	7.27
790	Capacitive Burglar alarm	6.16
810	Dynamic Compressor	6.79
835	Guitar preamp.	3.75
840	Delay car alarm	5.20
875	Cap. Discharge ignition for car engine (-Ve Earth)	10.68
80	Scope Calibrator	1.98
255	Level Indicator	5.50
430	3mHz Millivoltmeter	18.23
525	120-160mHz VHF timer	9.33
715	Photo cell switch	6.93
795	Electronic continuity tester	3.88
860	Photo timer	12.04
871	Slide projector auto feed control	8.72
235	Acoustic Alarm for driver	6.96
465	Quartz XTAL checker	7.89

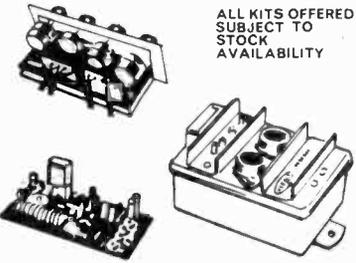ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY



MULTI-USE & RADIONIC KITS

10-1	10 Projects	3.60
50-1	10 Projects	8.00
150-1	150 Projects	13.20
	Telephone Communicator	7.20
X20	20 (Elec.)	4.95
X40	40 (radio)	9.45

(carr./packing 40p)

All transistor circuits with hand books

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order.

UK's LARGEST RANGE OF KITS & GADGETS



TEST EQUIPMENT

MULTIMETERS

(carr. etc. 30p)

200H (M210)	20K/Volt Silimline with case	4.95
TLH33D	2K/Volt Robust with case	4.95
U437	10K/Volt Steel case. AC up to 40KHz	4.95
U432A	20K/Volt with AC current ranges	8.00
AF105	50K/Volt with Leather case	9.50
U4313	20K/Volt AC current. Steel case	10.50
U4341	Plus Built in transistor tester	10.50
Model 500	30K/Volt	9.95

OTHER EQUIPMENT

SE250B	Pocket Signal Injector	1.90 carr. 15p
SE500	Pocket Signal Tracer	1.50 carr. 15p
TE15	Grid Dip meter 440kHz-280mHz	13.45 carr. 30p
TE40	AC Millivoltmeter 1-2mHz	18.75 c & p 35p
TE65	28 Range valve voltmeter	19.25 carr. 40p
TE20D	120kHz-500mHz RF Generator	16.95 carr. 40p
TE22D	20Hz-200kHz Audio Generator	18.75 carr. 40p
SE350A	Deluxe Signal Tracer	9.95 carr. 20p
SE400	Volts/ohms/R-C sub./RF field/RF gen.	11.25 carr. 20p

A SELECTION OF INTERESTING ITEMS

C3025	Compact transistor tester	5.50 p & p 15p
E1300	Mono mag. cart. preamp.	1.95 p & p 15p
E1310	Stereo mag. cart. preamp.	4.95 p & p 25p
E1310	Eisophone telephone amplifier	6.15 p & p 25p
D1203	Teleamp. with PU coil	3.60 p & p 20p
LL1	Door Intercomm. and chime	11.95 p & p 25p
	Chattalite (lights as you talk)	13.90 p & p 20p
	1 Kw Dimmer/controllor	3.00 p & p 10p
	9" Twin spring unit	2.75 p & p 15p
	16" Twin spring unit Revers	6.50 p & p 25p
	Car Tachometer Electronic	7.50 p & p 15p
	VHF 205 Marine band converter	3.95 p & p 15p
	B2005 4 Ch. mic. mixer	2.95 p & p 15p
	B2004 2 ch. Stereo mixer	4.75 p & p 15p

BUILD THIS RADIO



Portable MW / LW radio kit using Mullard RF/IF module. Features MW — bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7.98 (battery 22p), carr. etc. 32p



BUILD THIS TUNER

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4.85, carr. 15p.

FIBRE OPTICS

0-01 Diam. Mono Filament £1.50 per 25 metre reel
 0-13 Diam. 64 Fibres Sheathed. £1.00 per metre
 SPRAYS 15mm Diam Mares Tails £9.50

Henry's RADIO LIMITED

EDGWARE ROAD, W2

SEE FACING PAGE FOR ADDRESSES

STEREO AMPLIFIERS

(carr./packing 50p)		
AKAI	AA5200	61.70
	AA5500	78.50
	AA5800	117.50
AMSTRAD	1C2000 Mk. II	29.50
	4000	23.10
EAGLE	TA149	25.10
	TA151	34.85
	AA2	30.80
	AA4	42.45
	AA6	55.95
HOWLAND WEST	DA1000	22.45
HENELEC WEST	Kit	28.50
HENELEC TEXAN	Built	35.00
NIKKO	TRM300	25.95
	TRM400	32.50
PIONEER	SA500A	34.25
ROTEL	RA310	36.95
	RA610	54.95
	RA810	75.75
	RA1210	92.50
	2000	22.95
	3000	28.95
TANDBERG	TA300	66.10
TELETON	SAQ206B	22.50
	SAQ307	22.50
	GA202	28.50

STEREO RADIO TUNERS

(carr./packing 50p)		
AKAI	AT550	60.50
	AT580	94.50
AMSTRAD	3000	23.55
EAGLE	AA8	40.50
	TST152	29.45
HENELEC Stereo Kit		21.00
HENELEC Stereo Built		24.95
HOWLAND WEST	DA1000T	25.35
PIONEER	TX500A	48.75
ROTEL	RT320	36.95
	RT520	57.95
SINCLAIR	2000	26.95
	3000	26.95
TELETON	GT202	30.50

DECODERS / SYNTHESIZERS

(carr. etc. 30p)		
AKAI	SS1	39.70
DYNACO QUADRATOR		16.90
EAGLE	AA10	12.00
	AA26	16.35
		7.95
TATE 1	} Chassis	15.75
TATE 3		19.95
TATE 4		19.95
TATE 7		25.95
	Boxed	25.95

MATCHED SPEAKER SYSTEMS

Recommended pairs 8 ohms			
(Carr./Packing £1.50 pair)			
MARSDEN HALL			
110	10 watt	19.95 pr.	
150	15 watt	23.50 pr.	
200	20 watt	33.50 pr.	
AMSTRAD			
Acousta	1500 15 watt	24.90 pr.	
Acousta	2500 20 watt	28.50 pr.	
DYNACO			
A10	41.00 pr.		
A25	20-60 watts	65.00 pr.	
A35		78.00 pr.	
WHARFEDALE			
Denton 2	18 watt	24.40 pr.	
Linton 2	20 watt	31.00 pr.	
Trinton	25 watt	37.75 pr.	
LEAK			
160	18 watt	33.50 pr.	
250	18 watt	42.50 pr.	
CELESTION			
120	20 watt	35.95 pr.	
COUNTY	25 watt	31.50 pr.	
15	30 watt	47.95 pr.	
44	44 watt	79.95 pr.	

UK's largest stockists for KEF Acoustic Research, Mordaunt Short & Cambridge Audio speakers. In stock and on demonstration. Phone for keenest price.

RECORD DECK PACKAGES

(carr./packing 75p)		
(H)	SP25 III/800 or H	15.95
(M)	SP25 III/M756S	19.45
(HL)	AP76/G800	24.75
(M)	AP76/M756S	27.35
(HL)	GL75 P/C	32.50
(HL)	GL75 P/C G800	35.50
(HL)	GL75 P/C G800E	37.50
(HL)	MP60 (TRD1) G800	16.25
(HL)	HT70 (TPD1) G800	19.50
	Pioneer PL12D	31.75
	Thorens TD165	43.50

10% VAT to be added to all orders.

Prices & description correct at time of press E&OE. All goods offered subject to stock availability.

STEREO MAGNETIC CARTRIDGES

(carr. etc. 15p)				
SHURE				
M3Dm	3.20	M44G	4.20	
M44.7	3.95	M75/8/11B	6.75	
M44E	4.25	M75 EDII	8.50	
		M75 EIII	7.95	
		M75GII	7.25	
M55E				
GOLDRING	4.95			
G850	2.85	G800SE	10.00	
G800	3.75	G820	6.70	
G800H	3.50	G820E	10.00	
G800E	5.75	G820SE	13.35	
ADC				
Q36	10.70	Q30	5.90	
Q32	8.70			
GRADO				
FTF	5.25	FTE	8.25	
F3E	11.25	MZ	10.75	
EMPIRE				
909EX	7.25	999SEX	10.75	
999EX	8.25	999TEX	14.95	

STEREO COMPACTS

Complete with Speakers		
(carr./packing £1.25)		
Fidelity	UA3	39.90
Sanyo	G2601KL	125.50
Sanyo	G2815N	71.50
Sanyo	GXT4520KL	103.50
Sanyo	GXT4730KL	97.50
Philips	GF908	99.65
Philips	RH802	159.95
Philips	RF836	57.20
Philips	GF826	44.75
Philips	RH819/RH142	129.50
Philips	RH811/RH421	84.95
Philips	RF839	55.95
Philips	GF829	39.95
Philips	GF815	47.75
Philips	GF808	65.75
Philips	RH814/RH411	93.50
Philips	GF603	19.95

8 TRACK STEREO HOME UNITS

(carr./packing 70p)		
Amerlex	ACR301	48.00
(with MW/FM stereo radio)		

PORTABLE TV BATTERY / MAINS

(carr./packing £1.00)			
Elizabeth T9	9"	43.50	
Crown 9TV	9"	46.50	
Elizabethan T12	12"	43.95	
Teleton TW12	12"	46.95	
Sanyo 10T150	12"	49.95	

BATTERY / MAINS CASSETTE

(carr. etc. 35p)			
Wien	RT452	13.65	
Amerex	AC101	12.00	
Elizabethan	LZ315	12.25	
Amerex	AC104	16.00	
Phillips	N2204	20.75	
	N2205	29.50	
	9115	27.75	
	9118	21.20	
Hitachi	TRQ281	27.50	
Sanyo	M2000G	23.25	
	MR4010	28.95	
	M4000G	49.90	
	CC9201	37.25	
BASF	Hitachi	TRQ2335	49.50

BATTERY / MAINS RADIO CASSETTE RECORDERS

(carr. etc. 30p)		
Amerex	ACR200	22.00
	ACR201	30.00
Elizabethan	LZ416	27.25
	LZ516	29.10
BASF	CC9301	50.75
Phillips	RR322	28.75
	RR413	33.90
	RR712	48.30
Sanyo	M4141	39.50
	M2400W	31.50
	M2400FG	31.50
	M4400FC	62.50
	CZ50	47.95
Grundig	TRK1240E	29.50
Hitachi	TRS1161	35.00
	KCT1210L	33.50


STEREO RECORDER DECKS

(carr./packing 50p)		
CASSETTE		
Phillips	N2506	44.50
Pye	9145	44.50
Tandberg	TCD300	112.00
AKAI	GXC40D	57.75
	GXC45D	74.00
	GXC46D	84.30
	GXC65D	93.40
TEAC	A250/A350-A450	Stocked

REEL TO REEL

AKAI	4000DS	59.95
Tandberg	3321X/3341X	102.80
Large range Akai/Tandberg/Revox/Teac stocked.		

BEST VALUE IN U.K.

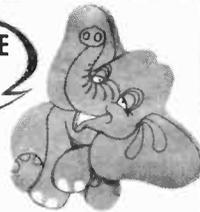

8 TRACK

AKAI	CR81D	54.10
	CR80DSS	94.95

STEREO RECORDERS

(carr./packing 70p)		
AKAI		
	1721L	60.35
CASSETTE		
AKAI	GXC40	67.95
	GXC46	90.75
Phillips	N2400/RH411	63.75
	N2401/RH411	74.50
	N2401S/RH411	79.95
	N2405/RH401	49.50
	N2510	88.75

STEREO TUNER AMPLIFIERS

(carr./packing 75p)		
AKAI		
	AA8030	92.50
Goodmans	Module 80	58.90
Goodmans	Module 90	75.90
Goodmans	One/Ten	88.50
Pioneer	SK525	90.75
	SK526	124.75
ROTEL		
	RX150A	42.95
	RX200A	53.95
	RX400A	65.95
	RX600A	90.50
	RX900	116.50
	TR154A	78.95
Tandberg	TR200MPX	85.00
	TR1000MPX	125.35
	TR1001MPX	135.75
Teleton	TSF55	57.20

8 TRACK

AKAI	CR81	66.20
------	------	-------

8 TRACK PLAYER DECKS

(carr./packing 35p)		
Elizabethan	8/LZ1	13.40
McDonald/BSR	TD8S	12.75
	TD83V	15.25

STEREO PHONES AT SPECIAL PRICES

(carr./packing 20p)		
AKAI		
ASE9S	5.80	
ASE20	7.30	
ASE22	8.25	
DULCI		
SH850D	2.25	
SH850GX	3.95	
SH1300VS	5.25	
K60		
K6	9.25	
ROTEL		
RH630	6.75	
RH700	8.85	
SENHEISSER		
HD414	10.95	
WHARFEDALE		
DD1	9.50	
ISODYN	14.35	
KOSS		
K6	9.95	
K6/LC	11.25	
K711	7.95	
KRD711	7.95	
HV1	17.50	
K0727B	12.45	
K0747	15.95	
PR04AA	21.95	
PR05LC	23.95	
HOWLAND WEST		
CIS200	2.75	
CIS250	5.25	
CIS1000	7.50	
CIS2000	15.25	
TTC		
G3000	6.60	
G2222	5.95	
LOW COST		
MD802	1.95	
MD806	3.75	
PIONEER		
SE20A	5.30	
SE30A	8.90	
SE50	15.20	
SEL20	7.40	
SEL25	10.90	
SEL40	12.50	
ACCESSORIES		
H1012/JB3 Junction Box	1.40	
JB3DE Din Junction Box	1.60	
JB11D De Luxe Junction Box	1.95	
0250 Phone Switch	4.75	
CONTROL BOXES		
G1301 (two phones)	2.62	
G1305 Controller	2.15	
FF17 2-pairs (Sliders)	6.25	
Koss T4A	4.20	
TS4	4.95	
T10A	8.50	
HW Mk. III Controller	6.90	

YOU CAN PAY BY BARCLAYCARD OR ACCESS

For callers or by phone 01-402 4736
Easy credit terms for callers to 309 and 354-356

ALSO STOCKED AND DEMONSTRATED

Armstrong - Acoustic Research
Cambridge Audio Leak - Lux
Marantz - Quad - Revox - Sansul
Tandberg - Sugen - Wharfedale
Goodmans - Celestion - Grundig
Kef - Teac - Bose - Sherwood
Call or phone 01-402 4736 for best prices.


404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA - Disco - Lighting High Power Sound 01-723 6963
303 Special offers and bargains done
All mail to 303 Edgware Road, London W2 1BW

Open -
9 am - 6 pm
6 days a week
All stores
open all day
Saturday

TOP QUALITY — LOW COST



RADIO — STEREO EQUIPMENT

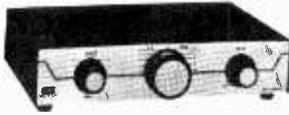

P.R.40

SOLID STATE R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now superceded.

It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio.

Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee.

£10.12 V.A.T./Carr. Paid.



MULTIBAND-6

SOLID STATE
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils.


Hi-Gain FET Regen, Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB.

Separate Electrical Bandsread, Calibrated Main Tuning.

A Quality CODAR-KIT with 12 months Guarantee. No technical. knowledge required, simple to built, printed. circuit and Pictorial Instruction Manual, fully detailed step by step.

Complete Kit with 4 Coils (less standard PP6 battery).

£14.90 V.A.T./Carr. Paid.

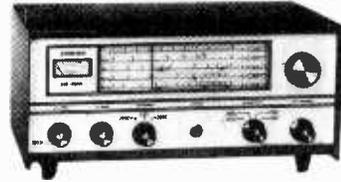

CR70A

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.

It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder.

Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee. Complete ready built. £31.00 V.A.T. /Carr. Paid.

SEND FOR YOURS TODAY!

FREE LEAFLETS ON REQUEST.

NOTE: These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers. Some portable receivers being advertised as Communication Receivers do not meet these requirements.

TRADE DESCRIPTIONS ACT 1968

It is illegal to make false claims or misleading statements in advertising. The following are just a few extracts from the many letters received from satisfied customers. All are unsolicited and can be inspected at any time.

Mr. S. Keightly, Southsea, Hants.

I am delighted with the CODAR equipment I am using . . . everything has come up to your specifications.

Dr. R. E. Wood, Louisiana State University, U.S.A.

Congratulations on an excellent product. The PR40 Preselector is the first preselector I have found to operate efficiently with ample gain, and without feedback or image problems.

Mr. W. R. Jones, Woy, N.S.W., Australia.

The PR40 peaked signals remarkably and performed as you claim. I am very satisfied.

M. G. Bennett, Bath, Somerset.

I am very pleased with my CR70A—results are excellent with many overseas stations I have not heard before and excellent results on the Amateur Bands.

Mr. J. Macdonald, Coningsby, Lincoln.

Received Multiband Kit OK. Assembled it in two hours, worked a treat first time.

Mr. E. Joy, Chesham, Bucks.

The performance of the CR70A is out of this world for its price, and its construction and design, great. I am really delighted . . . I cannot fault it.

NEW! HI-FI STEREO EQUIPMENT

NOW AVAILABLE FROM CODAR—A COMPLETE RANGE OF QUALITY EQUIPMENT SELECTED BY US FOR TOP RESULTS AND MONEY VALUE—PLUS OUR BIG CASH DISCOUNTS!

NEW! AMTRON KITS

We are now also marketing the outstanding range of AMTRON Kits. The quality of these Kits is first class, with circuit details and drawings making construction simplicity itself.

SEND FOR FREE ILLUSTRATED BROCHURES NOW



ON THE DESIGN STAFF—
G3SZM G3IRE


CODAR

TELECOMMUNICATIONS AND ELECTRONIC
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

BN15 - 8TZ

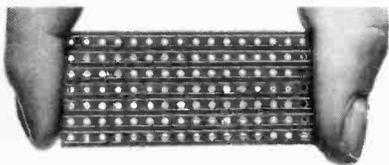


FREE VEROBOARD IN OCTOBER ISSUE

RADIO & ELECTRONICS CONSTRUCTOR

VEROBOARD PROJECTS


ONE

A.F. OSCILLATOR

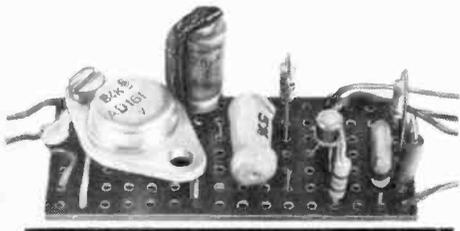

TWO


GRAM AMPLIFIER

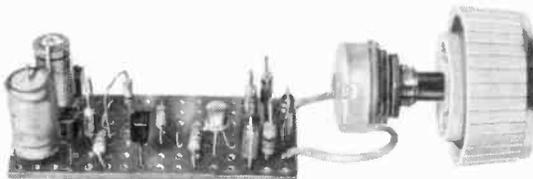

Plus many more
constructional features

*Buy NOW and be sure
of your copy - PRICE 20p*

CASED AMPLIFIERS

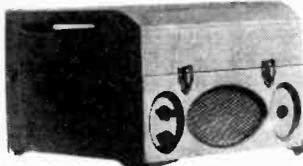

Polished wooden cabinet 14 x 13 x 9" with hinged lid containing a sensitive (20 μ V) 4 valve amplifier with tone and volume controls, giving 3 watts output to the 7 x 4" 3 Ω speaker. Also included is a non-standard tape deck. Supplied in good working condition with cct. diagram. Mains operated. Only £3 (£1 up to 200 miles, £1.20 over). Cassettes £1 (25p); spare heads 40p. Amplifier chassis only, 2xECC83, EL84, EZ80. £1.65 (37p).

71b BARGAIN PARCELS

Hundreds of NEW components—resistors, capacitors, crystals, pots, switches, PC boards containing transistors, diodes etc, loads of odds and ends. Outstanding value at £1.65 (37p).

COMPUTER PANELS: Type E: 4 OC29, 4 ACY19, 8 other transistors, 35 diodes, R's, C's etc. £1 (10p); Type K: 5 OC139 etc. 20p (5p); Type H: 12 ASZ20 + 176 other components 60p (10p); Type M: 17 silicon transistors, 2 trim pots etc. 50p (8p); Parcel of 12 top quality boards, including IC's, trim pots, power transistors etc. £2 (25p); 3lbs lower quality boards £1 (25p); 7lbs £2 (40p); 56lbs £12 (c/p). 2" x 1800 ft. Computer Tape on NAB spool in case 68p (40p).

NEW COMPONENTS: 741C TO99 or DIL 32p; BC107 8p; 2N3055 35p; OC140 25p; OC170 15p; BFY18 12p; BCY72 8p.

COMPONENTS IN BULK: 500 asstd resistors £1 (15p); 5000 £8 (50p); 20000 £25 (£1); 100000 £80 (£2); 300 capacitors, all types £1 (25p). 3 x 24" 0-15A Thermocouple panel meter £1 (10p); 40 asstd. pots £1 (25p); 1M Ω pots 5p; 4p8w switches 40p (10p); 10X crystals, 25 asstd 75p (25p).

TEST GEAR: Marconi TF144G sig gen, 85kHz-25MHz in 8 ranges. From £12; BFO No 8 audio oscillator 50Hz-20kHz in 2 ranges, 10 Ω or 600 Ω output. £10; Oscilloscopes available; CD1212, CD711S2, CD643S. Lots of odd units for callers. Field telephones £2-50. Post in brackets, small parts 4p. SAE list, enquiries.

VAT NOT INCLUDED—ADD 10% TO TOTAL.

GREENWELD ELECTRONICS (PWS)

24 Goodhart Way, West Wickham, Kent, BR4 0ES.
Tel: 01-777 2001. Shop at 21 Deptford Broadway SE8
(Next to old cinema). Tel: 01-692 2009. Callers most
welcome. Also 38 Lower Addiscombe Road, Croydon

PLUGS & LEADS

Plugs	
Pack 107 5 pin Din	22p
Pack 108 3 pin Din	20p
Pack 135 1/2" Jack	27p
Pack 130 1/2" Jack Stereo	50p
Pack 103 Loudspeaker Plug	17p
Pack 100 Phono Plug	7p
Pack 230 3 pin Socket	25p
Pack 236 5 pin Socket	33p
Pack 234 Loudspeaker Socket	33p

Ready-made Leads	
3 pin to 3 pin Din	70p
3 pin to open end	55p
5 pin to 5 pin Din	90p
5 pin to open end	70p
5 pin to 4 phono plugs	£1.00
Speaker lead Din to spade 12ft	40p

Extension lead Din plug to socket 12ft. 70p
All leads approx. 6ft. in length

DIAMOND STYLI

8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8.All at 80p each.
Double Diamond £1.25
Diamond suitable for Orbit NM22; G800; M3D £2.25 each

CARTRIDGES

Goldring G800	£6.00
Orbit NM22	£4.00
Shure 75/6	£6.00
Sonotone 9TAHC (Dia)	£2.00
Sonotone 8T4A (Dia)	£1.50
Ronnette 105 (Dia)	£1.25

All prices include VAT and postage

RECORD CARE

Cecil Watts Dust Bug	£1.20
Parastatic Disc Preener	45p
Antistatic Fluid	20p
Dust Bug Spares (Brush & Roller)	15p

CASSETTE TAPES

Audio-Magnetic C60	
Qty 3 6 10 20	
Price £1.00 £1.90 £3.20 £6.30	
Cassette Caddy £1.20	
Cassette Head Cleaner	35p

ZONAL ILFORD TAPE

5" Standard 600ft	25p
5 1/2" Standard 900ft	50p
7" (Plain boxed) 1200ft	60p
7" (Westminster Boxed) 1800ft	£1.25
7" Reel of Leader Tape (Blue or green)	75p

HEADPHONES

Sennheiser HD414	£10.60
AKG K50	£6.50
Beyer DT48S	£35.00

MICROPHONES

AKG D109	£11.50
AKG D202E1	£39.50
AKG D190C	£17.00
AKG D190E	£18.20
AKG D224	£50.00
Sennheiser MD211N	£45.00
Sennheiser MD413N	£27.00
Sony ECM5	£85.00
Audio RM57F Radio Mike	£210.00

SPEAKERS

E.M.I. 350 Kit Bohms	£8.20
E.M.I. 450 Kit Bohms	£4.50


J. J. Francis (Wood Green) Ltd

MANWOOD HOUSE, MATCHING GREEN, HARLOW,
ESSEX CM17 0RS
Telephone: Matching 476

Cool lighting **for hot parties.**

Velvet dim to full brightness at a touch of the finger. Off/on and infinitely variable.

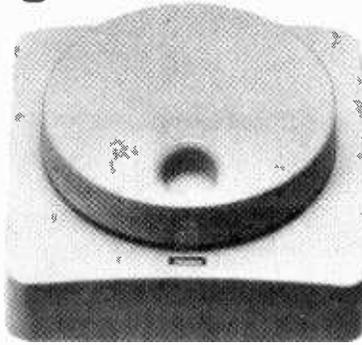
Beta light glow makes switch easy to find in the dark and consumes no current.



Economical too!

As the light is progressively dimmed, so the current consumption drops – think of it as an electric tap. 300 watt capacity, straight replacement for standard light switch.

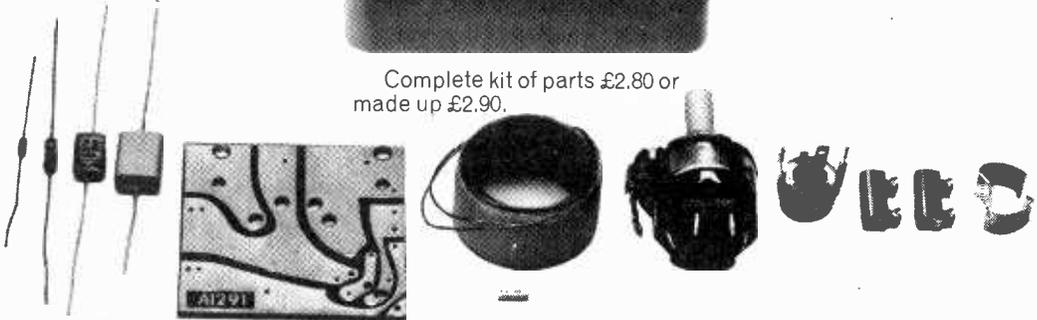Complete kit of parts £2.80 or made up £2.90.



Hot Ignition for cold mornings.

The Jermyn capacitor discharge ignition system.

Instant starting in all weathers. Even with a near flat battery, the unit will produce a full sized spark.


Just one of the many advantages of an electronic ignition system, the others are:

High energy spark even at maximum revs.

Smoother running. Less strain on battery and starter. Lower petrol consumption. Long plug life with infrequent adjustment (typically 20,000 miles, gapped at .050").

No contact breaker arcing giving long life and less adjustment (typically 20,000 – 25,000 miles)

STATE + or – earth when ordering.

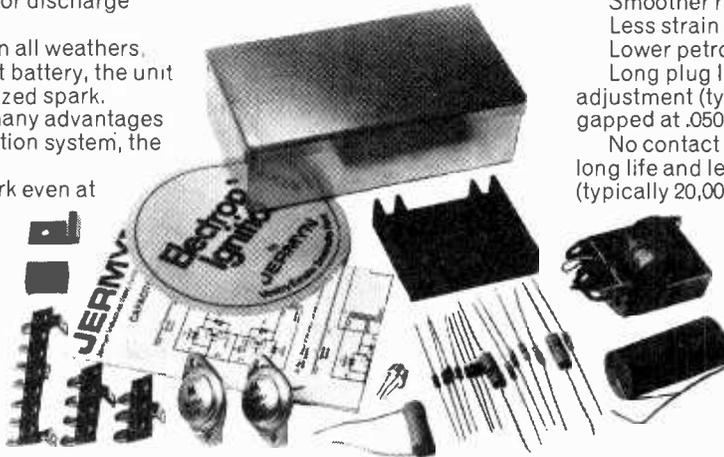

Complete set of parts to build it yourself for only £7.75, as described in Practical Wireless and fully approved by the author.

Save 55p
Buy both for £10.00

Reprints of the two part feature are available at 25p.

To Jermyn Industries. 114 Vestry Estate, Sevoyns, Kent.

All Prices Exclusive of V.A.T.

Please despatch return of post light dimmer kit light dimmer
Ignition Kits + or – earth £10 pair. Enclose cheque or postal order.


BLOCK CAPITALS

NAME.....

ADDRESS.....

JERMYN

NELSON-JONES FM TUNER KIT

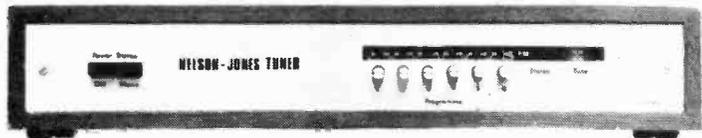

VARICAP TUNING

as in 'W.W.' June '73

Now available to readers of 'Practical Wireless'. The Nelson-Jones tuner uses dual gate MOSFET's in the RF stages, integrated circuits and ceramic filters in the IF stages, for very high performance and quick assembly. Do not confuse with tuners using only bipolar transistors and IF coils!

Tuning is accomplished by variable capacitance diodes and a Push Button Unit with 6 positions. AFC disable is incorporated as well as a pointer for each button showing tuning position in the range 87.5-108MHz, i.e. each 'button' is fully tuneable simply by turning.

Our complete metalwork system is supplied with nuts, bolts, board standoffs, push button mains on/off and stereo mute assembly, sockets, fuse and holder. Printed and Anodised Front Panel and Veneered Teak case. Power supply kits are supplied with complete kits of parts, or separately. Tuning meter is supplied with complete kits. LED tuning ind. is also available.

Prices for complete kits start at £23.75 + 45p pp. + VAT for mono tuners, (phase locked decoders are also available to fit in the cabinet). Please send large SAE for complete details of special offers and our complete lists.

GREEN LED's—the latest for 'stereo' lamps. 1-9 69p, 10+ 59p.


TEXAN AMPLIFIER

The Cabinet of the Nelson-Jones Tuner is specially designed to match the Texan amplifier cabinet, see photographs, so that owners of Texan's are assured of compatibility, both in superb performance and appearance.

Texan amplifier kits are available at £28.50 + 45p pp. + VAT.


Worried about tuner alignment? then let our alignment service take over.

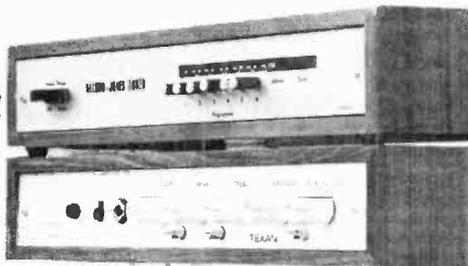Telephone queries. We have REAL ENGINEERS, not salesmen, to answer queries.



INTEGRIX LIMITED, Dept. P.W., P.O. Box 45, Derby, DE1 1TW. Tel. Repton (028389) 3580

verobox

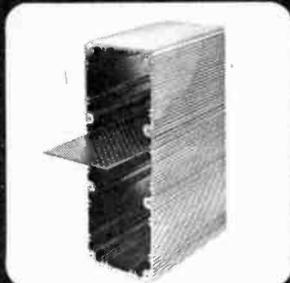

ALUMINIUM ENCLOSURES

- 80 standard sizes available from stock.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.

Eastleigh, Hants. SO5 3ZR

Tel: Chandler's Ford 2952 Telex: 47551

Subsidiaries and Agents throughout the World.

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG
Tel.: Bristol 421196. STD Code 0272

Your West Country shop for electronic components and solid state devices

2 METRE CONVERTER KIT

9-12V neg. earth feeding 28-30 MHz. Consisting of RF BF180. Fet. mixer. Crystal osc. BF180. Multiplier BF180. Complete with all components, instructions and aluminium box. (Not for beginners). Price £6, post paid.

2 METRE PRE-AMP

Single F.E.T. Pre-amp. neg. earth. Gain app. 12dB. Circuit, Instructions and Components. All you need is a tobacco tin. Price £1.40, post paid.

AIRCRAFT BAND CONVERTER

Circuit, instructions and components. All you need is a tobacco tin.

Price £1.40, post paid.

TRANSFORMER

Mains input 240 output—0.75V—5.5V—13V—1 amp. Size, height 3" x 3" x 2 1/2" shrouded + 2 fuse holders.

95p, post paid.

5 COMPUTER PANELS

9" x 7" min 35 trans. OC44 EQ ACY17
2 Trim Pots min 70 condensers. Min 80 diodes inc. OA81 + resistors. Most transistors have long leads.

£1.25, post paid.

NEW BIGGER 1973 CATALOGUE

Over 25 kits. Over 30 books. Plus components, cases, chassis, etc.

Only 10p, post paid.

ALL PRICES INCLUDE V.A.T.

BYWKITS

5017AA-PD: A simple digital alarm clock using phosphor-diode displays, 12 or 24 hour display, 50/60Hz, kit is 4 digit but can be expanded to 6 digit, alarm buzzer is on-chip, DEAC back-up snooze facilities are available. Kit comprises 5017AA chip, socket, PCB and 4 displays, additional components required cost £3-4 (not supplied by us) and are mainly transformer, switches, resistors and diodes. 5017AA-PD kit £24.

5017BB-PD: Similar to AA version above except that chip has calendar function instead of alarm. 5017BB-PD kit £24.

5316-LC: A beautiful little alarm clock using liquid crystal display. The clock works in 24 hour mode and the display in 12 hour mode, 50/60 Hz input. Display is 4 digit but can show any of HH:MM, M:SS, Alarm HH:MM, Sleep MM. Two relay switched outputs are available to switch an alarm buzzer and a radio. The liquid crystal display is the RCA transmission type and is driven AC from the chip, very little setting up required. Kit comprises 5316 chip, socket, PCB, L-C display and socket, additional components required about £4 from any "RS" stockist. 5316-LC kit £33.

VAT. All prices above EXCLUDE VAT, add 10% P. & P. Please add 10p post and packing.

You can have clock data sheets for a S.A.E. or our 1973 catalogue (2nd issue) for 15p.

You may phone us for help on 0442-62757 and you can use your ACCESS card for phone or personal purchase—Service from Bywood!

BYWOOD

ELECTRONICS

181 EBBERS ROAD, HEMEL
HEMPSTEAD, HERTS. 0442 62757

Adcola Soldering Equipment of the Finest Quality

CHRISTMAS GIFTS GALORE

Available from Stock

A Styrene boxed Soldering Kit designed for your immediate needs containing a $\frac{3}{16}$ " Invader soldering instrument, two spare bits, a soldering station and a pack of solder—everything you need.

The versatile Invader Range with a large selection of interchangeable bits

- B** L706 19 watt instrument $\frac{1}{8}$ " bit with cable
- C** L646 23 watt instrument $\frac{3}{16}$ " bit with cable
- D** L1076 27 watt instrument $\frac{1}{4}$ " bit with cable

EF BL646 and BL1076 12 volt battery models $\frac{3}{16}$ " & $\frac{1}{4}$ " bit size come complete with crocodile clips and 12ft PVC cable. Just clip on to a car battery.

GHI 18 swg top quality cored solder in $\frac{1}{2}$ kilo, 3 oz and handy pack sizes.

J Non-corrosive de-soldering braid allows quick easy de-soldering (5 $\frac{1}{2}$ ft spool).

K For extra safety use an L686 soldering station.

L L68 protective shield for your Invader.



Please send me the following items

PRINT NAME

PRINT ADDRESS



PW


- | | | |
|-----------------------------------|-------|--------------------------|
| A INVADER SOLDERING KIT | £4.39 | <input type="checkbox"/> |
| B L706 INVADER | £2.23 | <input type="checkbox"/> |
| C L646 INVADER | £2.42 | <input type="checkbox"/> |
| D L1076 INVADER | £2.48 | <input type="checkbox"/> |
| E BL646 BATTERY MODEL | £3.05 | <input type="checkbox"/> |
| F BL1076 BATTERY MODEL | £3.17 | <input type="checkbox"/> |
| G SOLDER REEL $\frac{1}{2}$ KILLO | £1.40 | <input type="checkbox"/> |
| H SOLDER REEL 3 OZ | £0.48 | <input type="checkbox"/> |
| I SOLDER PACK | £0.07 | <input type="checkbox"/> |
| J DE-SOLDERING BRAID | £0.75 | <input type="checkbox"/> |
| K L686 SOLDERING STATION | £1.88 | <input type="checkbox"/> |
| L L68 PROTECTIVE SHIELD | £1.08 | <input type="checkbox"/> |
| New Catalogue | | <input type="checkbox"/> |

ADCOLA PRODUCTS LTD ADCOLA HOUSE GAUDEN ROAD LONDON, SW4 6LH
V.A.T. REGD. No 235 6153 72 REGD. No 442762

All prices include 10% V.A.T.

Please tick items required.

BIG Discounts

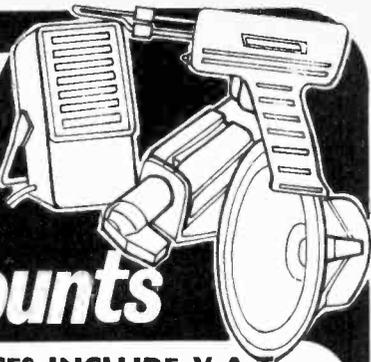

ALL PRICES INCLUDE V.A.P.

SPEAKER BARGAINS		£	£			
EMI 13" x 8" 3, 8 or 15 ohm	Plain	2.05	ELAC 8" ohm Dualcone	2.40		
With Co-Axial Tweeter		2.20	FANE 7" x 4" 3 or 8 ohm	1.00		
Twin Tweeter		3.55	CELESTION 8" 15 ohm	1.55		
Type 350 8 ohm, 20 watt		8.00	ADASTRA 10" 8 or 15 ohm,			
6" 8 ohm, 10 watt		2.70	10 watt	2.75		
8" 8 ohm, 10 watt		3.75	BAKER GROUP 25 12" 8 or			
12" 8 ohm, 20 watt		5.50	15 ohm, 25 watt	6.45		
8" x 5" C/Mag. 5 watt		1.20	P. & P.	.25		
8" x 5" Dualcone			5" 8 ohm, 5 watt C/Mag.	.85		
8 ohm, 10 watt		2.45	2 1/2" 8 ohm or 64 ohm	.50		
GOODMANS 6 1/2" 8 ohm		1.60	P. & P.	.10		
Dualcone						
TWEETER & CROSSOVER						
EMI 3 1/2" 3 or 8 ohm C/Mag		1.00	Dome Tweeter 8 ohm, 30 watt	4.00		
Cone Tweeter 8 or 15 ohm,			Crossovers CN23 (3 ohm),			
10 watt		1.90	CN28 (8 ohm), CN216 (16			
Cone Tweeter 8 ohm, 3 watt		1.00	ohm)	1.00		
Horn Tweeter 8 ohm, 20 watt		5.50	P. & P.	.10		
KIT FORM CABINETS TEAK						
12 x 12 x 6 with 8" 8" x 5" or		2.45	18 x 11 x 9 with 13" x 8" cutout	4.25		
6 1/2" and 3 1/2" cut out			for EMI 350			
17 x 10 x 6 with 8" or 13" x 8"		3.25	P. & P. ea.	.35		
cutout						
MICROPHONES						
CM20 Crystal Hand		.50	TW206	5.75		
CM70 Planet stick metal,			CONDENSER MIKE 600 ohm,			
switch crystal		1.55	uni-dir.	7.90		
DM160 Dynamic uni-dir, ball		3.95	Cassette Stick Mike with R.			
metal			Control on/off switch	1.35		
UD130 50K/600 ohm, uni-dir		4.50	(2.5 & 3.5mm JJ/Ply)	.40		
ball metal			Lapel type, crystal	.15		
			P. & P.			
SOLDERING IRONS						
ANJEX CN240 15 watt		1.60	X25 25 watt (low			
SK 1 Kit (15 watt Iron			leakage)	1.60		
2 spare Bib etc.)		2.65	P. & P.	.10		
CARTRIDGES						
ACOS GP91/2SC or GP91/3SC			9THAC/G Slim fit, stereo	1.80		
Stereo comp.		1.00	cer. diam.			
GP93/1 Stereo crys.		1.35	19-TI Stereo crystal	.80		
GP94/1 Stereo crys.		1.75	BSR SC5M Stereo ceramic	2.25		
GP95/1 Stereo crys.		1.35	SX5M Stereo crystal	1.60		
GP96/1		1.75	SX5M Stereo crystal	1.60		
GP104		.75	X5H Mono/stereo	1.25		
			X5M Mono/stereo	1.25		
SONOTONE						
9THAC Stereo cer. diam.		1.80	GOLDRING G800	£3.85		
			G850	£2.95		
			P. & P.	.05		
STYLI for above cartridges						
Sapphire		.35	GOLDRING G800	1.95		
D. Diamond		1.25	G850	.03		
			P. & P.			
BATTERY ELIMINATORS						
240v Input 6, 7.5 or 9 300mA		2.20	d.c. output at 300mA	2.20		
12v d.c. Input (fits in car			P. & P.	.10		
lighter socket) 6, 7.5 or 9						
TAPES						
	Std.	LP	DP	Std.	LP	DP
5"	45p	55p	70p	65p	95p	110p
5 1/2"	55p	65p	95p			
				P. & P. 1-3, 9p ea. 4 or more, lot 30p		
LOW NOISE CASSETTES						
C60	35p	33p	30p	Cassette Head Cleaner		35p
C90	45p	43p	40p	P. & P. 1-5, 3p ea. 6-10, 15p lot.		
C120	55p	52p	50p	11-20, Post Free.		
PLASTIC LIBRARY CASES						
For 5" Reels			18p	CASSETTE CASES		10p
5 1/2" Reels			22p	P. & P. 1-3, 5p ea. 4 or more, 20p		
7" Reels			25p			
BIB ACCESSORIES						
Compact Tape Head				Hi-Fi Stereo Hints		.25
Cleaning Kit	Ref. J		.45	& Tip Book	Ref. 56	
Tape Editing Kit	Ref. 23		1.30	Stylus Balance	Ref. 32A	1.15
Recording Tape				Spirit Lever	Ref. 46	.50
Splicer	Ref. 20		1.15	Cassette Case (holds 12 cas-		
Cassette Tape,				settes)	Ref. 34	1.00
editing	Ref. 24		1.40	Hi-Fi Stereo Test Cassette		1.00
Cassette Salvage Kit	Ref. 29		.40	Groove-Kleen Record Cleaner		1.00
				P. & P.		.10

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED.

Riversdale Electronics

Mail Order Department **PW1**

P.O. Box 470, Manchester M60 4BU.

NEW
ALL
SILICON!



PRACTICAL
WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P. Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, supplied with de-luxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit £7.97 U.K. Post Free
De-Luxe Kit £9.62 U.K. Post Free

Quantity Discounts:

Trade and Overseas	1-5	Nett	6-9	Less 10%
Enquiries Invited	10-49	Less 15%	50-99	Less 20%
Mail Order Only	100-999	Less 25%	1000 up	Less 30%

ALL PRICES INCLUDE VAT


PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365

RINGBOARD PRINTED CIRCUITS

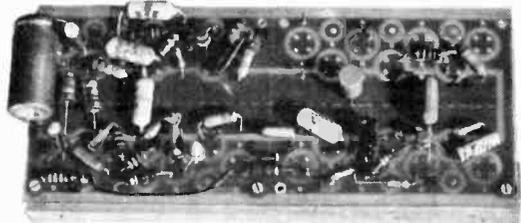259 CHESTERFIELD ROAD, SHEFFIELD S8 0RT
TEL. 52178



Photograph shows a circuit built on RING BOARD containing 42 components

RING BOARD is a fantastic new quick and easy method to transfer an electronic diagram to a workable printed circuit.

Special Opening Price

Normal Price per full board	55p	47p
Normal Price per half board	33p	26p
Normal Price per qtr. board	22p	16p

RING BOARDS can be cut into half and quarter boards and still retain the same characteristics.

Full instructions of method with each RING BOARD purchased.

RING BOARDS are:—

1. Simple to use.
2. Little or no planning.
3. Positive and negative rails easily recognised.
4. Can be used with split volt-age systems.
5. Build what you like when you like.
6. Neat and professional finish.
7. Flux varnished for easy soldering.

LARGE STOCKS ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new & to makers specs.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power 80p
 AC155K pnp germanium low power 32p
 AC176K npn germanium low power 32p
 AD161 npn germanium medium power 42p
 AD162 pnp germanium medium power 40p
 AF139 pnp germanium UHF 49p
 BC 107 13p; BC108 12p; BC109 13p; } npn
 BC107 11p; BC108 10p; BC109 11p
 BC177 21p; BC178 19p; BC179 21p; } pnp
 BC267 12p; BC268 11p; BC269 13p
 Standard groupings available.
 BD136 npn med power 37p
 BD136 pnp med power 88p
DIODES
 OA90, OA91, OA95 each 6p
 OA200 9p; OA202 10p
 Other semiconductors
 AC128 17p; AF117 32p
 BFY61 18p

Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

SIEMENS' THYRISTORS

0 8A 400V 56p, 600V 70p
 3A 400V 60p, 600V 88p

ZENER DIODES full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

DIN PLUGS & SOCKETS

by Hirschmann, 4A rating




2 way LS—socket 10p; plug 12p. 3 way scr. socket 10p; plug 12p. 5 way scr. socket 12p; plug 15p.

TRANSISTOR ACCESSORIES

To3 cover 7p
 Heat sinks 1°C/w, type 6W1, undrilled 60p

SWITCHES

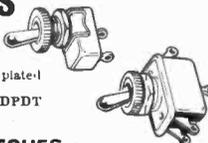1011C SPST toggle 20p
 409 DPDT toggle 28p. (These are chrome plated 2-5A rating)
 7201 Sub-miniature DPDT 260V a.c./2A 48p




ROTARY SWITCHES

Radiospares Miniature Make-switch (in assembly kit form) 48p
 Wafers, MBR-2P5W, 1P11W; BRM-1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each, 6p.

WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, each 24p

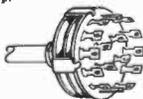

ELECTROLYTIC CAPACITORS

AXIAL LEAD Prices subject to amendment by the manufacturer.

Rated voltage: 8V	6.8V	10V	18V	25V	40V	63V	100V
Capacity μ F							
0.47							
1.0					10p		7p
2.2					7p		8p
4.7			10p		8p		7p
10				7p	8p		7p
22					7p		9p
47	7p		7p	7p	7p		12p
100	8p	7p	7p	7p	9p		11p
220	7p	8p	8p	8p	10p		17p
470	8p	9p	9p	10p	17p		24p
1000	10p	12p	12p	17p	20p		40p
2200	14p	17p	22p	25p	36p		
4700	20p	28p	37p	41p	54p		
10,000	40p	43p					

Polycarbonate -5% Tolerance

280V up to 0.1 μ F; 100V/0.1 μ F and above.
 0.01; 0.012; 0.015; 0.018; 0.022; 0.027; 0.033; 0.047; 0.056; each 4p.
 0.068; 0.082; 0.1; 0.12; 0.15 each 4p.
 0.18; ;22; each 5p.
 0.27; 0.33; 6p. 0.39 7p. 0.47 8p. 0.56 10p.
 0.68 11p. 1 μ F 13p.
 Prices subject to amendment by the manufacturer.

SILVERED MICA non-polarised capacitors in 34 values from 2.2 pF to 680 pF, each 6p

RESISTORS 10%, 5%, 2%

Code	Power	Tolerances	Range	Values available	1 to 9	10 to 99	100 wp
C	1/20W	5%	82 Ω -220K Ω	E12	9	8	7.5
C	1/8W	5%	4.7 Ω -470K Ω	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 Ω -10M Ω	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 Ω -10M Ω	E24	1.2	1	0.9 nett
C	1W	5%	4.7 Ω -10M Ω	E12	2.5	2	1.8 nett
MO	1/2W	2%	10 Ω -1M Ω	E24	4	3	2 nett
WW	1W	10% \pm 1/20 Ω	0.22 Ω -3.9 Ω	E12	7	7	6
WW	3W	5%	1 Ω -10K Ω	E12	7	7	6
WW	7W	5%	1 Ω -10K Ω	E12	9	9	8

Codes: C—carbon film, high stability, low noise.
 MO—metal oxide, Electroli TR5, ultra low noise.
 WW—wire wound, Pleseey.

Values:
 E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
 E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.


Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order).

★ Please remember to add V.A.T. to your order.

If you have already got your No. 6 catalogue and want to know latest additional items and price amendments, send S.A.E. for special supplementary list.

KNOBS

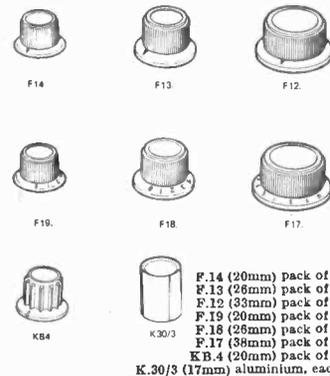All grub screw fitting for 1/8" shafts. Black. For other types—see Catalogue No. 6, P.64



POTENTIOMETERS

Rotary carbon track, double wiper
 SINGLE P20 1in 100 Ω to 2.2M Ω 12p, P20 log 4.7K Ω to 2.2 meg. 12p
 JP20 Log. 4.7K Ω to 2.2M Ω 12p.
 Dual ramp 1in 4.7K Ω to 2.2M Ω 42p; Dual log, 4.7K Ω to 2.2M Ω 42p; Log/antilog, 10K, 22K, 47K, 1M Ω only 42p; Dual anti-log, 10K only, 42p; Any type with 2A D.P. mains switch. 12p extra.
 Only decades of 10, 22 & 47 available in ranges quoted.
 DUAL CONCENTRIC DP20 in any combination of P20 values. 60p; with switch, 72p.
 SLIDER
 Lin or log, 10K to 1meg. in all popular values, each 26p.
 Escutcheons—White, grey, black, 10p each.
 Control knobs: blk/white/red/yel/gr./blue/gk. grey/lt. grey, each 5p.
 CARBON SKELETON PRE-SETS
 Small high quality, PR 1in: 100 Ω , 220 Ω , 470 Ω , 1K, 2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M Ω . Vertical or horizontal mounting, 5p each.

All items offered for sale in accordance with our stated terms of business, copy of which available on request. Prices quoted DO NOT include V.A.T. Orders from U.K. customers must be accompanied by an additional 10% of nett value for V.A.T.

DISCOUNTS Not allowed on nett price items. 10% on orders for 25 or more, 15% on orders for 115 or more. Prices subject to alteration without notice. PLEASE SEE LATEST AMENDMENT LIST. SEND S.A.E.

POSTAGE AND PACKING FREE SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE



No. 6 (4th printing) contains details of 100's of semi-conductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc. Information and equivalent tables, etc. Well illustrated (96 pages 5 1/2" x 8 1/2") 25p. post free with refund voucher for 25p. allowable on orders over 25 or more.

with 25p refund voucher


ELECTROVALUE

(Dept. P.W. 8) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB
 Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 3603 Telex 264475
 ENG. REG. NO. 1047788. R.O. 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB

RSC GROUP/DISCO UNITS

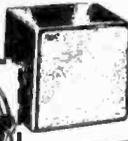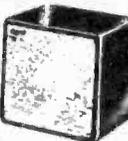50 WATT SPEAKER  **100 WATT AMPLIFIER**  **50 WATT SPEAKER** 

 **HEADPHONES MICROPHONE**

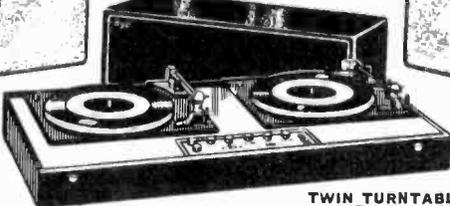 **TWIN TURNTABLE WITH PRE-AMP**

PACKAGE OFFER
Units listed below
(a) 100w POWER AMPLIFIER
(b) PAIR OF HI-FI HEADPHONES
(c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
(d) PAIR 50 WATT SPEAKERS
Black Rexine covered Cabinets Size approx. 18" x 18" x 8"
(e) RSC TDI DISCO CONSOLE
(a) (b) (c) (d) **£149-50**
& (e)
Carr. £2-50

RSC TDI DISCO CONSOLE
Incorporating twin Garrard SP95 or BSR MP60 type turntables and Sonotone or Aoco Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynal covered Cabinet with lid. See illustration on left
Or Dep. £9-55 and 9 monthly pymts £67-55
(Total £77-47)
Carr. £1-50

Terms Deposit £30 and 18 monthly payments of £8-30 (Total £179-40).

 **RSC DISCO MASTER**
DISCOTHEQUE CONSOLE with integrated power supply. 100W OUTPUT TWIN FACE OUTPUT SOCKETS. Inc. twin Garrard SP25 Mk.III or BSR Macdonald MP60 type turntables. Pick-ups with high compliance cartridges and diamond styl. Separate volume controls for each turntable.
£99-75

FULL MONITORING FACILITIES plus Treble and Bass controls. Separate input for mic. with vol. control switch. Rexine covered cabinet size approx. 32" x 18" x 7" with lid
Terms: Deposit £20 and 18 monthly payments £7-80 (Total £111-20). Carr. £2-50.

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS
All types 16 Ohms covered in Rexine and Vynair
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback low characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £2-85 and 9 monthly payments £2-43 (Total £24-82) Carr. 65p. **£21-95**

TYPE C818 50 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 64" x 14" x 11". Dep. £4-72 & 9 monthly pymts **£32-72**
£3-58 (£38-94) Carr. 85p


TYPE C4100 100 WATTS Inc. four 12" 60 watt speakers for conservative rating. Extra heavy construction. Size approx. 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £15-50 & 12 monthly. pymts. £5-48 (Total £81-02). Carr. £1-50 **£71-50**

F.A.L. DISCO PRE-AMPLIFIER **£18-97**
Designed for use with a pair of Player Units and Amplifier with Bass and Treble Controls. Incorporates MONITORING FACILITIES and Mic. input. The 4 inputs are ind. controlled. Selector switch Gram (1), (2), and Tape. 200-250V A.C. Mains 50Hz. Brush Silver finished fascia. Size approx 16 1/2" x 3" x 4" deep. Fully enclosed but can mounted in cabinet.

FANE "CRESCENDO" SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

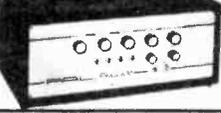FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.
Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speakers 8 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250V. A.C. mains. Output 50 watts music rating.
Or deposit £8-85 & 9 monthly payments £4-22. Total £44-93. **£39-93** Carr. 82p.




RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.
For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £8-95 and 12 monthly payments £4-97 (Total £68-59). Carr. Free
S.A.E. for leaflet UK Mainland **ONLY £59-95**

RSC BASS-REGENT 50 WATT AMPLIFIER
A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.
★ Two extra heavy duty 12in. 50w Loudspeakers.
★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet.
Credit Terms: Deposit £15-50 & 12 monthly payments of £5-48. (Total £81-02.) Carr. £2-20 **£71-50**



RSC GP30 HI-FI AMPLIFIER
For Guitar, Vocal or Instrumental Group
A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valving. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250V. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 9 monthly payments of £25-85 **£25-85** 72p

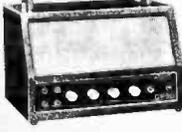

NOW SIX NEW BRANCHES
BOLTON 23 DEANSGATE
COVENTRY 17 SHELTON SQUARE
DONCASTER 3 QUEENSGATE
WATERDALE CENTRE
NOTTINGHAM 19/19A MARKET ST
STOCKPORT 8 LITTLE UNDERBANK
SUNDERLAND 5 MARKET SQUARE
NEW LARGER PREMISES AT HULL, DARLINGTON & NEWCASTLE
See Addresses.

RSC
HI-FI CENTRES LTD.
MAIL ORDERS & EXPORT ENQUIRIES TO:—
AUDIO HOUSE, HENCONNER LANE, LEEDS. 13.
Tel: Pudsey (09735) 77831.
TERMS C.W.O. or C.O.D. No C.O.D. under £1.
POSTAGE 25p EXTRA UNDER £2. 35p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED.
S.A.E. PLEASE WITH ENQUIRIES.
SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.
MAIL ORDERS MUST NOT BE SENT TO SHOPS

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 3 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
£25-95	£14-75	£11-99
Dep. £5-95 and 9 monthly payments £2-56 (Total £28-99)	Dep. £3-75 and 9 monthly payments. £1-50 (Total £17-25)	Dep. £2-99 and 9 monthly payments. £1-50 (Total £14-51)

FOR BASS GUITAR, ELECT. ORGAN, ETC. PAIR SUITABLE ALL PURPOSES

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT
Dual Cone 15 Ω (for use or Dep. £1-25 and 9 other than Bass Guitar or Electronic Organ). Carr. free **£7-95** (Total £9-25)

DISCO PACKAGE OFFER £45
Pair BSR MP60 T/tables GP91 PU Cartridges. FAL Disco Pre-amp. Total Rec. Ret. Price £50-11 Carr. £1

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 Mk.III AMPLIFIER	£87-95	PACKAGE PRICE	£81-00
PR. FANE POP 25/2 5W L/SPEAKERS	£15-90		
Terms: Deposit £7-50 and 12 monthly payments of £4-10 (Total £56-70)	£53-86	£49-50	carr. £1-10
F.A.L. PHASE 50 Mk.III AMPLIFIER	£87-95	PACKAGE PRICE	£81-00
PR. FANE POP 50 L/SPEAKERS	£28-98		
Terms: Deposit £9-80 and 12 monthly payments of £4-68 (Total £65-88)	£61-08	£57-50	carr. £1-10
F.A.L. PHASE 50 Mk.III AMPLIFIER	£87-95	PACKAGE PRICE	£81-00
PAIR LR/30 25W L/S in cabinets	£26-30		
Terms: Deposit £10 and 12 monthly payments of £4-97 (Total £69-84)	£64-25	£61	carr. £1 35
F.A.L. PHASE 100/2 AMPLIFIER	£89-85	PACKAGE PRICE	£81-00
4 FANE POP 50 L/SPEAKERS	£47-98		
Terms: Deposit £20 and 18 monthly payments of £8-35 (Total £134-30)	£117-81	£110	carr. £2

HIGH QUALITY LOUDSPEAKER UNITS
ALL TWO TONE REXINE AND VYNAIR FINISH
L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50
Or deposit £8-95 and 9 monthly pymts. of £4-34. Total £43-01
L12/20 12" 20-25 WATT 13,000 lines 15 ohms
Dep £2-15 & 9 monthly pymts £1-50 (Total £15-65) Carr. 55p. **£13-15**

 L12/10 10-15 Watt vaneer finish cabinet 12" unit 8-15 ohm. Size approx. 14" x 14" x 9". Carr. 60p **£8-25**

CREDIT TERMS AVAILABLE ON PURCHASES OVER £10 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

FAL PHASE 100/2 AMPLIFIER
100 WATTS MUSIC RATING. Solid State. Sep. Bass and Treble Controls. 4 separate controlled inputs plus master control. Output for speakers 3-30 ohms. Includes protective circuit against damage from short circuits.
Terms: Deposit £7-85 & 12 monthly payments £6-05 (Total £80-45). Carr. 75p **£69-85**



FAL TWIN CHANNEL AMPLIFIERS
Solid State. 4 sep. controlled inputs plus master volume control. Individual Bass and Treble controls. Output for speakers 3-30 ohms. Protective circuitry against damage from short circuits.

FAL 'SUPER 50' **£59-50** Carr. 80p
50 WATTS MUSIC RATING
Terms: Dep. £8-50 & 9 monthly. pymts. £6-50 (Total £67)

FAL 'SUPER 100' **£79-95** Carr. 90p
100 WATTS MUSIC RATING
Terms: Dep. £12-50 & 12 monthly. pymts. £6-45 (Total £89-90)



HUGE DISCOUNTS ON LEADING BRAND TAPE AND TURNTABLE UNITS

CREDIT TERMS AVAILABLE

Minimum Deposit 10%

These are only a few of our many discount lines—visit your nearest RSC Hi Fi Centre

AKAI GXC 40D Tape Unit £62.95 (Rec. Price £89.74) Carr. £1

AKAI 4000DS Tape Unit £68.95 (Rec. Price £93.50) Carr. £1

AKAI 1721L Tape Unit £66.95 (Rec. Price £93.87) Carr. £1

AKAI CR81D Tape Unit £58.95 (Rec. Price £84.10) Carr. £1

GOLDRING GL72 T/Table & P.U. £29.95 (Rec. Price £37.29) Carr. 75p

Also FREE with above GL72 Goldring G800 cartridge worth over £10

B.S.R. MACDONALD MP60 TYPE T/Table & P.U. £10.95

Discount prices shown correct at time of going to press

(Rec. Price £14.95) Carr. 40p

FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT

Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite core coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams. Frequency Response 25 Hz-20 kHz. Impedance 8-15 ohms. **£10.98** post free

Or Dep. £2.47 & 8 monthly pymnts. £1.28 (Tot. £13.99)



RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db.

Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation.

Attractive Black and Silver finished metal fascia plate and matching control knobs.

COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and

OR FACTORY BUILT IN TEAK VENEERED CABINET **£12.65** Carr. 40p

as illustrated £16.50 or dep. £2.50 and 9 monthly payments £1.83 (Total £18.97).



COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS **£12.65** Carr. 40p

AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-16 ohms. PLEASE STATE CHOICE.

Exceptional performance at low cost.

HF808T 8" 10W £2.95 HF120D 12" 15W £5.50
HF102D 10" 10W £3.30 HF128 12" 15W £8.85
HF120 12" 15W £4.95 HF128D 12" 15W £6.85



FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-16 Ω. Post Free **£4.99**

PLEASE STATE IMPEDANCE WHEN ORDERING

MODEL 803T 8" 15w. with parasitic Tweeter. **£6.99** Post Free

Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-16 Ω.



ALL R.S.C. PRICES INCLUDE VAT FULL LABOUR AND MATERIAL GUARANTEES FOR 12 MONTHS

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.

JE8 Size 16" x 11" x 9".

Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. **£5.50**

SE8 For optimum performance with any 8in. Hi-Fi speaker. **£6.50**

Size 19 x 10 1/2 x 9in.

SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter Size 25 1/2 x 16 x 9in. **£7.95**

SE10 For outstanding results with 10in. Hi-Fi spkr. Size 25 1/2 x 16 x 9in. Ported **£6.75**



AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£6.50** Carr. 35p

OR SENIOR 15 WATT INCLUDING **£7.65** Carr. 39p



R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. ±2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£8.50** Carr. 40p

OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£12.05**



R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BMI. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 in. approx. Completely replaces batteries supplying 1.5v and 9v, to battery radio where A.C. mains 200/250v. Post 30p 50c/s is available. ASSEMBLED READY FOR USE **£4.15**



R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50c/s. Screened

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.
250v., 60mA, 6-3v. 2a **£1.10**
250-0-250v., 60mA 6-3v. 2a **£1.16**

FULLY SHROUDED UPRIGHT MOUNTING
250-0-250v. 60mA, 6-3v. 2a, 0-5-6-3v. 2a **£1.55**
250-0-250v. 100mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.45**
300-0-300v. 100mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.45**
300-0-300v. 130mA, 6-3v. 4a, c.t., 6-3v. 1a **£2.45**

For Mullard 510 Amplifier **£2.95**
350-0-350v. 100mA, 6-3v. 4a, 0-6-6-3v. 3a **£2.45**
350-0-350v. 150mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.95**
425-0-425v. 200mA, 6-3v. 4a, c.t., 5v. 3a **£5.45**
425-0-425v. 200mA, 6-3v. 4a, 6-3v. 3a, 5v. 3a **£5.40**
450-0-450v. 250mA, 6-3v. 4a, c.t., 5v. 3a **£6.00**

TOP SHROUDED DROP-THTO TYPE
250-0-250v. 70mA, 6-3v. 2a, 0-5-6-3v. 2a **£1.49**
250-0-250v. 100mA, 6-3v. 3.5a **£1.71**
250-0-250v. 100mA, 6-3v. 2a, 6-3v. 1a **£1.76**
250-0-250v. 100mA, 6-3v. 2a, 0-5-6-3v. 2a **£1.81**
350-0-350v. 80mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.45**
250-0-250v. 100mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.45**
300-0-300v. 100mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.45**
300-0-300v. 130mA, 6-3v. 4a, c.t., 6-3v. 1a **£2.45**

Suitable for Mullard 150 Amplifier **£2.85**
350-0-350v. 100mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.45**
350-0-350v. 150mA, 6-3v. 4a, 0-5-6-3v. 3a **£2.85**

FILAMENT or TRANSFORMER POWER PACK

Types 6-3v. 1.5a. 55p; 6-3v. 2a. 60p; 6-3v. 3a. 85p; 6-3v. 6a. £1.45; 12v. 1a. 81p; 12v. 3a. or 24v. 1.5a **£1.50**; 0-9-18v 1 1/2a **£1.25**; 0-12-26-42v 2a **£1.95**

CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. **£1.10**
2 1/2a. **£1.25**; 3a. **£1.40**; 6a. **£1.80**; 6a. **£2.20**

AUTO (Step UP/step DOWN) TRANSFORMERS

0-110-120v. 200-230-250v. 50-80 watts **£1.25**
150 watts, £2-10 250 watts £3-00; 500 watts £6-40

OUTPUT TRANSFORMERS

Standard Pentode 6,000 Ω or 7,000 Ω to 3 Ω 55p
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω **95p**
Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15 Ω **£1.55**

Push-Pull EL84 to 3 or 15 Ω 10-12 watts. **£1.50**
Push-Pull Ultra Linear for Mullard 510, etc. **£2.45**
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω **£2.20**
Push-Pull 20 watt, high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω **£2.65**

SELENIUM RECTIFIERS

F. W. (Bridged) D.C. output. Max. A.C. input 15v.

1a, 28p. 2a, 38p. 3a, 55p. 4a, 72p. 6a, 88p.

SMOOTHING CHOKES

150mA, 7-10H, 250 Ω 77p; 100mA, 10H, 200 Ω 86p; 80mA, 10H, 350 Ω 55p; 60mA, 10H, 400 Ω 28p.

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET

Only high grade components by leading manufacturers

- * Push Button Selector Switching
- * Jack Socket for Headphones
- * Neon Indicator
- * Satin Silver Finish Metal Fascia
- * Solid State Circuitry
- * Twenty Silicon Transistors
- * Four Diodes, Four Rectifiers
- * Find S.A.E. for full descriptive leaflet.

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8 Ω. Frequency Response 7 Hz to 70 KHz ± 1/2 dB.



COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. **£27.50**

£5 extra.

R.S.C. STEREO FM III TUNER. IN CABINET

Visually matches Super 30 Mk. III **£37.50**

FACTORY BUILT UNIT INC. CABINET WITH 12 months' guarantee. Or Dep. £7 and 9 monthly payments **£42.50**

payments £4.54 (Total £47.86).

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

* Moderate size only 25 x 14 x 10in. approx.

* Response 30-20,000 c.p.s. Impedance 15 ohms **£25.25**

* Performance comparable with units costing considerably more Carr. 65p

COMPLETE KIT

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet.

(2) 3-way quarter section series cross-over system.

(3) 8 x 5in. high flux middle range speaker.

(4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet.

(7) Circuit and full instructions. Terms: Deposit £5 and 9 monthly payments **£2.64** (Total £28.76).



R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349

BOLTON 23 Deansgate. (Closed Wed.). Tel. 35512

BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).

COVENTRY 17 Shelton Square, The Precinct.

DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361

DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Wed.).

EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501

GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158

HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505

LEICESTER 32 High Street (Closed Thurs.). Tel. 56420

LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252

LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573

LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778

MIDDLESBROUGH 106 Newport Rd. (Closed Wed.). Tel. 47096

NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068

SHEFFIELD 13 Exchange Street (Castle Mkt. Bids. (Closed Thurs.). Tel. 20716

STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777

SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

MAINS TRANSFORMERS

SAFETY

ISOLATING TRANSFORMERS

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen

VA (watts)	Ref No.	Price £	P & P £
60	149	2-86	0-38
100	150	3-15	0-52
200	151	5-80	0-52
250	152	7-05	0-65
350	153	9-40	0-80
500	154	13-55	1-00
1000	156	24-97	1-20
2000	158	41-25	*
3000	159	64-54	*
4000	160	105-90	*

* On application.

LOW VOLTAGE TRANSFORMERS

Prim. 200-240V. Sec. 12 & 24V.

Amprs	Type	Price £	P & P £
0-5	0-25	1-11	1-00
1	0-5	2-13	0-22
2	1	7-1	1-60
4	2	18	2-25
6	3	7-0	2-70
8	4	108	3-00
10	5	7-2	3-55
12	6	116	4-00
16	8	17	5-50
20	10	115	6-95
30	15	187	12-90
40	20	232	18-30
60	30	226	28-70

60V TRANSFORMERS

Prim. 200-240V. Sec. 24, 30, 40, 48, 60V.

Amprs	Type	Price £	P & P £
0-5	124	1-60	0-38
1	126	2-25	0-38
2	127	3-55	0-42
3	125	5-40	0-52
4	123	6-98	0-67
6	40	8-46	0-67
8	120	9-50	0-82
10	121	11-60	1-00
10	122	16-25	1-10
12	189	16-43	1-10



AUTO TRANSFORMERS

Taps: 115, 210, 240V

VA (watts)	Type	Price £	P & P £
20	113	1-00	0-22
75	64	2-00	0-30
150	4	2-40	0-38
300	66	4-70	0-82
500	87	6-90	0-69
1000	84	12-60	0-82
2000	96	24-00	1-10
3000	73	38-60	1-20

CASED AUTO TRANSFORMERS

220/240V to 115V, Lead & Socket

VA	Type	Price £	P & P £
20	113G	1-95	0-22
600	671G	9-46	0-67
1000	841G	16-80	1-00



30V TRANSFORMERS

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.

Amprs	Type	Price £	P & P £
0-5	112	1-20	0-22
1	79	1-64	0-38
2	3	2-45	0-38
3	20	3-00	0-42
4	21	3-65	0-52
5	31	4-40	0-62
6	117	5-25	0-62
8	86	6-90	0-67
10	89	8-26	0-67

50V TRANSFORMERS

Prim. 200-240V. Sec. 10, 25, 38, 40, 50V.

Amprs	Type	Price £	P & P £
0-5	102	1-60	0-30
1	103	2-35	0-38
2	104	3-25	0-42
3	106	4-40	0-52
4	106	5-45	0-52
6	107	6-65	0-67
8	118	11-27	0-97
10	119	14-15	0-97

MINIATURE AND EQUIPMENT TRANSFORMERS

Prim 240V with screen

Sec. 1 Volts	Sec. 2	Milliamprs	Type	Price £	P & P £
3-0-3	Sec. 2	200	238	1-12	0-10
0-6	0-6	500	234	1-18	0-10
0-6	0-6	1000	212	1-28	0-22
0-9-9	—	100	13	0-95	0-10
0-9-9	0-9	330	235	1-28	0-10
0-9-9	0-8-9	500	207	1-70	0-22
0-9-9	0-8-9	1000	208	2-30	0-30
15-0-15	—	40	240	1-28	0-10
0-15	0-15	200	236	1-28	0-10
20-0-20	—	30	241	1-09	0-10
0-20	0-20	150	237	1-28	0-10
0-15-20	0-15-20	500	205	2-16	0-38
0-20	0-20	300	214	1-36	0-22
20-12-0-12-20	—	700(D/C)	221	1-21	0-30
0-15-20	0-15-20	1000	206	3-10	0-38
0-15-27	—	500	203	2-38	0-38
0-15-27	0-15-27	1000	204	2-40	0-38

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 Volt 25p	50 Volt 35p	100 Volt 55p	50 Volt 65p
100 Volt 25p	100 Volt 40p	200 Volt 55p	100 Volt 70p
200 Volt 25p	200 Volt 45p	400 Volt 65p	200 Volt 80p
600 Volt 50p	600 Volt 75p	600 Volt 75p	400 Volt 80p
1000 Volt 55p	800 Volt 21-00	600 Volt 21-00	



PLEASE ADD 10% FOR V.A.T.

ADD 10p P & P PER ORDER

A.S.P. LTD.

BYRE HOUSE · No. 2 UNIT · WINGCHEAP · CANTERBURY · KENT · CT1 3RW
Tel. Canterbury 52436



The leading U.K. & U.S.A. electronic Manufacturers use

ERSIN MULTICORE SOLDER

containing 5-cores of non corrosive extra active flux.
YOU TOO CAN USE THIS RELIABLE SOLDER obtainable from your retailer. (ask for 'ERSIN MULTICORE')



Multicore Solders Ltd.
Maylands Avenue,
Hemel Hempstead, Hertfordshire, HP2 7EP
Tel: Hemel Hempstead 3636 Telex: 82363

NEW VALVES!

GUARANTEED AND TESTED

24-HOUR SERVICE

PRICES INCLUDE VAT

1R5	25	AZ31	89	ECC83	24	EL41	45	PCF801	27	PY800	30
185	28	DAF91	23	ECC85	30	EL84	20	PCF802	26	PY801	30
1T4	18	DAF96	35	ECH35	46	EM80	35	PCF805	65	U25	62
384	22	DF91	18	ECH42	55	EM81	35	PCL82	28	U26	59
3V4	46	DF96	35	ECH81	21	EM84	30	PCL83	53	U191	80
6/30L2	48	DK91	25	ECH80	27	EY86	27	PCL84	31	U261	80
6BW7	48	DK92	47	ECL82	27	EZ80	19	PCL85	36	UABC80	28
6F23	64	DK96	43	ECL83	48	EZ81	21	PCL86	35	UBC41	40
6F25	49	DL92	22	ECL86	32	KT61	73	PFL200	48	UBF89	31
787	21-75	DL94	46	EF39	43	KT66	75	PL36	45	UCC85	21
12AU7	17	DL96	36	EF41	54	N78	21-00	PL81	41	UCH42	54
25L6GT	19	DY86	21	EF80	23	PC66	43	PL82	27	UCH31	28
30C15	53	DY87	21	EF85	26	PC68	42	PL83	30	UCH22	30
30C17	73	DY802	28	EF86	26	PC97	34	PL84	26	UCL83	48
30C18	66	EABC80	20	EF89	21	PC900	28	PL500	56	UF41	47
30P5	58	EBC33	41	EF91	15	PC834	26	PL504	56	UF89	24
30PL1	58	EBC41	42	EF92	25	PC889	40	PY92	47	UL41	52
30PL14	68	EBF89	24	EF133	26	PCC189	46	PY93	47	UL84	37
30P19	63	ECC81	15	EF184	27	PCF80	25	PY81	24	UY41	36
30PL1	64	ECC82	17	EL33	73	PCF86	44	PY82	23	UY86	22

Post/Packing on 1 valve 7p, plus 3p per valve on each extra valve. Any parcel insured against damage in transit 3p extra. Office address, no callers.

GERALD BERNARD

83 Osbaldeston Road,
Stoke Newington, London N.16

LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed— build as you learn with the exciting new 'Technatron' kit. No Extras. Tools, transistors, meter etc. All supplied. You could build a radio in weeks.

SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV, ELECTRONICS, C & G, TELECOMMS ETC.

Dept. BPW21 Aldermaston Court, Reading RG7 4PF


Name.....

Address.....



Age..... CV BPW21

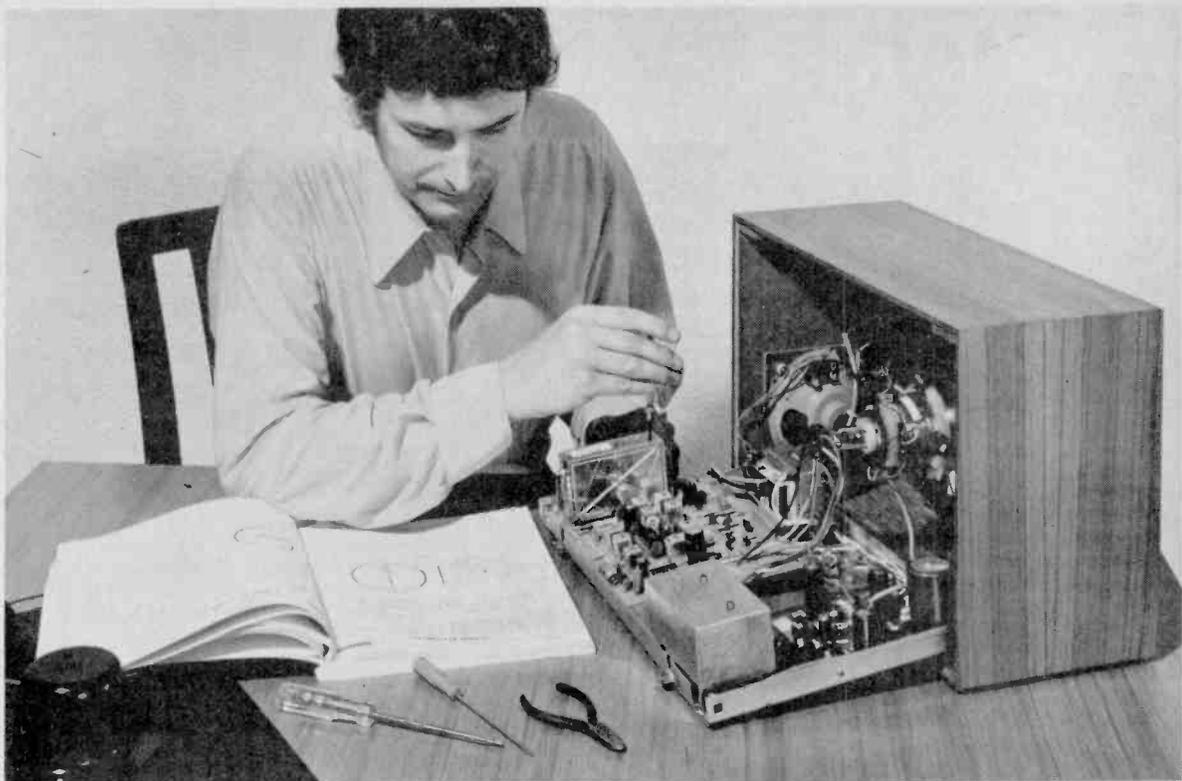BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



LEARN about MODERN TV Design by building this Heathkit 12" B/W Portable

The new Heathkit GR-9900 portable 12" UHF Monochrome Television kit. A unique chance to double the pleasure available from any other television set — because you build this yourself.

We've used the latest modular construction and advanced design concepts to produce an outstandingly high performance TV worthy of the Heathkit name. All the main electronics are mounted on two easy-to-assemble printed circuit boards—this plus the use of no less than four integrated circuits perform the complex function of IF, video, sound, line frame and scan. Factory pre-aligned coils make alignment very easy and there are four presettable pushbutton controls for channel tuning—a luxury found in very few other models. The quality and fidelity is therefore excellent, and of a far higher standard than most ready-built televisions in the shops.

The GR-9900 is portable too—equally at home on

the mains or off your 12 volt battery for car, boat or caravan use. Add to this Heath's world renowned experience in the design of equipment for first-time kit builders, and you will be impressed on all counts of engineering, styling, and performance.

The instruction manual is surprisingly simple with big, clear illustrations to map out your way. Would-be TV engineer? Here's your chance to learn—by actually building a television yourself. The manual not only shows you how to get 100% personalised quality control on your own; in the event of anything going wrong, a Trouble-Shooting section enables you to find the fault—and, in most cases, to put it right unaided.

The GR-9900 is a kit you'll be proud to build and own. You have a choice of fully finished cabinets in teak or modern white and the kit price, £82.70 (carriage extra), includes a FREE high performance indoor aerial.

FREE Heathkit Catalogue

Contains something for everyone: Hi-Fi Stereo, Testers & Instruments, SWL, Metal Detectors... even a Battery charger Kit. Mail the coupon... Today!

Heath (Gloucester) Limited,
Gloucester GL2 6EE.
LONDON showroom
233 Tottenham Court Road
Tel 636 7349



Choose cash or Heath Monthly Budget Plan

(Mail order prices and specifications subject to change without notice)

Please send me a FREE Heathkit catalogue

Name _____

Address _____

HEATH
Schlumberger

Dept. PW/11/73
Heath (Gloucester) Limited,
Gloucester GL2 6EE. Telephone 0452 29451

Another!
winner!

fane MODE ONE HIGH FIDELITY LOUDSPEAKER KIT



Recommended
retail price

£10.98

including V.A.T.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

SPECIFICATION OF UNITS

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	1"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	2kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. SIZE 15½" x 10½" x 9".

*When used with above cabinet.


Please
send S.A.E.
for fully
descriptive
leaflet.

Distributors to the wholesale
and retail trade
LINEAR PRODUCTS LTD.
Electron Works, Armley, Leeds
LS12 3SA. Tel. 630126

Manufactured by
FANE ACOUSTICS LTD.
Hick Lane, Batley, Yorkshire.
Tel. Batley 6431

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

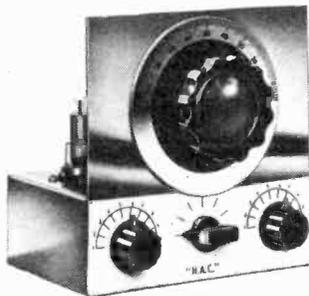

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER

Complete kit—price £4.30 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (Illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. **EXCITING COMPETITION** for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

EX COMPUTER PC PANELS

2 x 4 in. packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (9p)

SPECIAL BARGAIN PACK

25 boards for £1 (25p).
Panels with 4 Power transistors sim OC28 50p (9p)

ELECTROLYTICS

68,000µ 16, 4½ x 2 in. dia. 25,000µ 25v, 20,000µ 30v, 5,000µ 90v, 35,000µ 15v, 8,000µ, 4½ x 3 dia. 50p (15p) 15,000µ (5v), 10,000µ 35v, 4½ x 2 in. dia. 30p (10p), 2,000µ 25v wire ends 15p (5p), 12 for £1/50 (15p)

3A DIODES 4 for 50p (5p)

8 BLACK TOGGLES dpst 50p (8p)

250 MIXED CAPACITORS 60p (8p)

250 MIXED RESISTORS 60p (8p)

150 HI-STAB RESISTORS 60p (8p)

200 SI PLANAR DIODES 50p (5p)

SUB. MIN. CO-AX PLUGS & SKTS. 4 pairs 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES 8 for 50p (8p)

ASSORTED RELAYS 8 for £1 (12p)

MIN. GLASS NEONS 12 for 50p (5p)

10 WAY TERMINAL BLOCKS 10 for 55p (5p)

PAPST EXTRACTOR/BLOWER FANS 100 cfm 4½ x 4½ x 2 in. £3.50 (28p)

Q-H BULBS 12v 55w 50p (5p)

Postage and package shown in brackets.

Please add 10% VAT to prices.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8. 01-478 8499

RECHARGEABLE

Mallory Cells need the new

KESTREL-DOWN

Battery Charger



Battery container and six SA-15AA's

At last a battery charger designed to the limits specified by the Cell manufacturer. Carefully constructed to prevent overcharging or back-leak, the **KESTREL-DOWN** Battery Charger provides you with a convenient method of always having fully charged Mallory Alkaline-Manganese battery cells available at all times.

Specify **KESTREL-DOWN** Charger Model 2, 4 or 6*** depending on the number of batteries you wish to recharge in one go and indicate required battery size as listed below:

CHARGER WITH ONE CONTAINER

£7.70

Batteries:

TYPE SA-13D £1.51 each

TYPE SA-14C £1.13 each

TYPE SA-15AA £0.61 each

Additional Containers

£0.40 each

ALL PRICES INCLUDE VAT

***If model 6 is used with SA-14C or 13D batteries an extra container costing 40p is required.


Send to

Bush & Meissner
LTD

275 West End Lane, London NW6 1QS. 01-794 9811

INTERNET

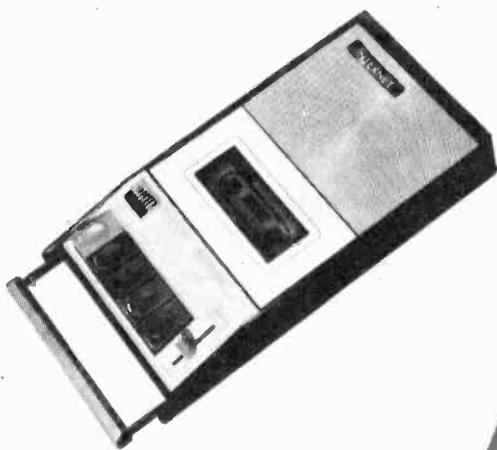ALL OFFERS APPLY TO UK ONLY WHILST STOCKS LAST



Cassette Tape Recorder AC 240V. Works on 6V battery 4 x $\frac{1}{2}$ U11. Plano keys. Sliding, V/C Earphone. Rem. Mic. Built in Condenser Type Microphone.



£9.18 + 92 VAT. Price £10.10, P. & P. Included.

Microphone opt. £2.00 + VAT.

Cassette Tape opt. 35p + VAT.

Car Radio No. S101. 12V. Neg. and Pos. polarity, Fixing Bracket. 4" Speaker.

£6.20 + 62p VAT. Price £6.82.

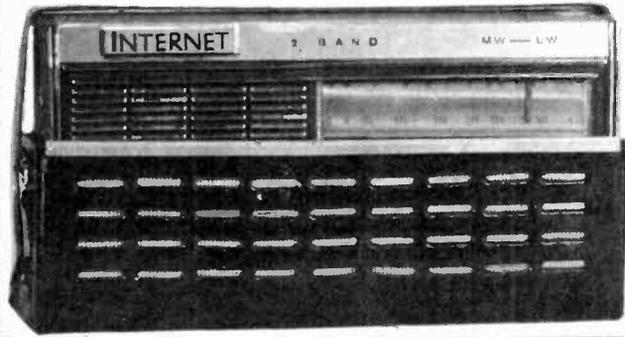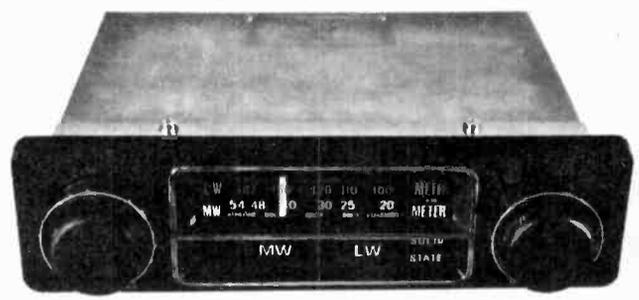

Radio MW/LW No. J70. MW/LW. Battery only, LX12 U12. Pen Light.

£4.20 + 42p VAT. Price £4.72, P. and P. included.

INTERNET RADIO (PRODUCTS) LTD.

100-102 BECKENHAM ROAD, BECKENHAM, KENT, BR3 4RH

NAME

ADDRESS

DISCOUNTS UP TO

60%

FULL 12 MONTH AFTER SALES SERVICE

with probably the best discounts offered in the U.K.

ALL PRICES ARE INCLUSIVE OF V.A.T.

FANTASTIC OFFER
GARRARD SP25 Mk III.
 Goldring G800. Teak finish, plinth and tinted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1.75
 for P. & P. and Ins. **£14.75**

TURNTABLES
 Please add 95p P. & P. & Ins.
 BSR MP60 £9.15
 Garrard SP25 Mk III £9.95
 Garrard SL65B £12.75
 Garrard AP76 £16.75
 Garrard 401 £27.75
 Garrard Zero 100 (spg) £33.95
 Garrard Zero 100 (Auto) £37.45
 Goldring GL85/P & C £59.30
 Goldring G101/P & C £19.35
 Goldring GL72 £21.90
 Goldring GL72/P £28.50
 Goldring GL75 £27.35
 Goldring GL75/P £33.90
 Goldring GL75 Lid £3.55
 Goodmans TD100 P&C G800 Cart £47.15
 Thornes TD125 £59.95
 Thornes TD125 AB Mk II £92.50
 Thornes TD160 AB & C £51.26
 Thornes TD165 AB & C £44.15
 Wharfedale Linton with cart £25.50

TUNERS
 Please add 95p P. & P. & Ins.
 Alpha Highgate FT150 £32.95
 Amstrad Multiplex 3000 £24.50
 Lowther FM Mk 8 N/P £42.75
 Lowther FM Mk 9 N/P £72.50
 Metrosound FMS 20 Mk II £36.95
 Rogers R/brook FET 4 (Cha) £32.95
 Rogers R/brook FET 4 (Cased) £36.50
 Sinclair PRO60 Mod £14.90
 Sinclair cased tuner £25.30

SPEAKERS
 £1.65 for P. & P. (per pair)
 Amstrad Acoustra 1500 £26.90
 Amstrad Acoustra 2500 £30.75
 Apollo 138 £15.95
 B & W DMS £28.50
 Celestion Ditton 15 £50.75
 Celestion Ditton 44 £79.95
 Goodmans D/Maxim £39.70
 Goodmans Mezzo 3 £49.95
 Goodmans Havant £34.95
 Keletron KS4 £13.95
 Keletron KS8 £28.50
 Sinclair Q16 £10.95
 Sinclair Q30 £30.95
 Wharfedale Denton II £26.95

SPEAKER UNITS
 Wharfedale Linton Kit £16.85
 Wharfedale Glendale Kit £29.95
 Goodmans Din 20 Kit £14.85

AMPLIFIERS
 Please add 95p P. & P. & Ins.
 Amstrad 8000 Mk II £15.95
 Amstrad IC2000 Mk II £24.95
 Amstrad Integra 4000 £22.95
 Alpha Highgate FA400 £39.05
 Global 10 + 10 £19.75
 Global 20 + 20 £25.95
 Keletron 700 £18.25
 Keletron 1500 £24.45
 Metrosound ST20E Mk II £29.45
 Metrosound ST60 £50.85
 Rogers R/Brook (Ch) £41.15
 Rogers R/Brook Mk III (Ca) £44.35
 Rogers R/bourne (Ch) £54.25
 Rogers R/bourne (Ca) £56.75
 Sinclair 2000 £24.00
 Sinclair 3000 £30.50
 Sinclair 605 £21.45
 Sinclair PRO 60 2 x Z30/PZ5 £16.40
 Sinclair PRO 60 2 x Z30/PZ6 £19.45
 Sinclair PRO 60 2 x Z50/PZ8 £25.25
 Trans £4.95
 Sinclair AFU (Filter Unit) £7.35
 Sinclair Stereo 60 Pre-amp £7.35
 Sinclair Z30 Amp £3.85
 Sinclair Z50 Amp £4.50
 Sinclair PZ5 Power Supp £4.20
 Sinclair PZ8 Power Supp £6.15
 Sinclair PZ8 Mains Trans £4.95
 Sinclair PZ8 Power Supp £6.15

TUNER/AMPLIFIERS
 Please add £1.10 P. & P. & Ins.
 Alpha FR 3000 £61.35
 Goodmans Module 80 £59.90
 Goodmans Mod 80 Com. £106.50
 Goodmans Mod 90 £74.75
 Goodmans One-Ten £86.50
 Rogers R/brook (Cha) £61.95
 Rotel 150A £45.25
 Rotel 200A £57.95
 Wharfedale WE 40 Receiver £69.95

PLINTH AND COVERS
 £3.20*
 For Garrard SP25, 2025, 3000, BSR, McDonald, MP60 £3.08 P. & P. 71p. For AP76, SL72B, SL95B, etc. £4.75 + 71p P. & P.

CARTRIDGES
 Please add 11p P. & P. & Ins.
 Goldring G850 £2.75
 Goldring G800 £3.95
 Goldring G800E £6.35
 Goldring G800SE £11.00
 Shure M3D £3.30
 Shure M44E £4.45
 Shure M55E £5.00
 Shure 75ED Type 2 £9.95
 Shure V15 £28.00
 Shure M75EJ Type 2 £8.15

Prices correct at time of going to press. (E & OE) and are subject to alteration.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept PW11, 174 Pentonville Road, London, N1. Telephone 01-278 1789
 Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS. EUSTON & ST PANCRAS on main road leading to the East and West Country

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1R5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.20. DAF96, DF96, DK96, DL96, 4 for £1.55.

1R5	30	30L1	29	EBF89	25	EY87	29	PCL85	37	UAF42	50
1R5	25	30L15	54	ECC81	20	EZ40	40	PCL86	37	UBC41	43
1T4	20	30L17	85	ECC82	21	EZ41	40	PCL88	30	UBF80	34
3B4	25	EZ30	64	ECC83	20	EZ42	21	PCL80	89	UBF89	32
3V4	47	30P12	69	ECC85	31	EZ81	22	PCL89	37	UCS4	32
5Y3GT	30	30P19	64	ECC804	50	EZ90	30	PENNA	77	UCS5	32
5Z4G	35	30PL1	58	ECCF80	30	GZ30	34	PEN36C	70	UCF80	30
6J30L2	50	30PL13	75	ECC35	48	GZ32	40	PFL200	49	UCH42	56
6AM6	18	30PL14	75	ECH42	56	KT41	77	PL36	48	UOH81	30
6A05	35	38V4	30	ECH81	23	KT61	75	PL81	43	UOL82	50
6AT6	20	50CD6G	88	ECH83	40	KT66	47	PL81A	78	UOL84	30
6AU6	20	807	55	ECH84	35	KT88	200	PL82	28	UP41	49
6BA6	23	6063	75	ECL80	30	LN319	58	PL83	33	UB99	25
6BE6	23	AZ31	40	ECL82	29	LN329	80	PL84	27	UL41	53
6BJ6	44	B349	70	ECL83	49	LN339	65	PL500	58	UL84	30
6BW7	48	B729	54	ECL86	35	N78	15	PL504	58	UM84	22
6E14	35	CCX35	67	EP37A	95	P81	25	PM84	30	UY41	37
6F23	88	CY31	40	EP39	45	PABC80	31	PX28	125	UY85	23
6F25	50	DAF91	25	EP41	55	PC86	44	PY32	48	W77	43
6V6GT	28	DAF96	36	EP80	23	PC88	44	PY33	48	X148	180
6X4	30	DF91	20	EP85	28	PC96	42	PY80	30	Z77	22
6X6GT	28	DF96	38	EP86	28	PC97	35	PY81	29		
7H7	27	DH77	20	EP89	22	PC90	29	PY82	25	Transistors	
8E14	180	DK91	30	EP91	18	PC84	28	PY83	28	AC107	17
10P13	53	EK92	48	EP92	27	PC85	23	PY88	33	AC127	18
12AT7	20	DK96	45	EP98	30	PC88	38	PY800	31	AD140	37
12AU7	21	DL92	27	EP183	27	PC89	41	PY801	31	AF115	20
12AX7	25	DL94	47	EP184	30	PC189	48	R19	30	AF116	20
19BG6G	75	DL96	38	EP80	38	PC808	70	R20	70	AF117	20
20F2	67	DY86	25	E133	75	PCF80	28	U25	84	AF125	17
20P3	75	DY87	22	EL41	48	PCF86	33	U26	82	AF127	17
26L6GT	19	DY802	30	EL41	47	PCF86	45	U47	73	OC44	12
25U4GT	57	EABC80	32	EL84	23	PCF800	55	U49	70	OC45	12
30C1	26	EAF42	44	EL90	35	PCF801	28	U78	30	OC12	12
30C15	55	EB91	12	EL500	82	PCF802	39	U191	63	OC72	12
30F17	76	EB033	43	EM80	38	PCF805	87	U193	31	OC75	12
30C18	67	EB041	44	EMS1	38	PCF806	58	U251	61	OC81	12
30F5	60	EB081	30	EM84	32	PCF808	65	U301	35	OC812	12
30FL1	60	EB090	22	EM87	47	PCL82	80	U329	68	OC82	12
30FL12	68	EBF80	29	EY51	38	PCL83	55	U801	75	OC82D	12
30FL14	65	EBF83	38	EY86	29	PCL84	33	UABC80	29	OC170	12


READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

PRICES ARE INCLUSIVE OF VAT, ONLY POSTAGE IS EXTRA
 Minimum post/packing on 1 valve 8p., on each additional valve, (3p. per valve extra)
 Any parcel insured against damage in transit 3p. extra.

PHOTOELECTRIC KIT

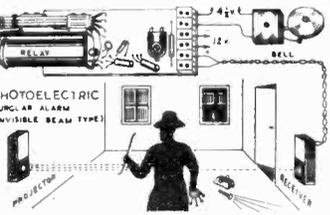CONTENTS: P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



PHOTOELECTRIC KIT
£2.85

Postage and Pack. 15p (U.K.)
 Commonwealth
 SURFACE MAIL 25p
 AIR MAIL £1.40
 Australia, New Zealand,
 S. Africa, Canada and U.S.A.
 Also Essential Data Circuits
 and Plans for Building
 10 advanced Designs

INVISIBLE BEAM OPTICAL KIT
 Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1.45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT
 CONTENTS: As above. Twice the range of standard kit. Large Lenses, Filter, etc. Price £2.10. Postage 15p (U.K.). Commonwealth: Surface Mail 20p, Air Mail £1.15.

BIOFEEDBACK AMPLIFIER KIT
 Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.

CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4.75 postage and pack. 25p (U.K.). Commonwealth: Surface Mail 30p, Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT
 Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.


CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3.25, postage and pack. 15p (U.K.). Commonwealth: Surface Mail 25p, Air Mail 75p.

YORK ELECTRICS Mail Order Dept.
 335 BATTERSEA PARK ROAD, LONDON, S.W.11
 Send S.A.E. for full details, a brief description of all Kits and Projects.



I.L.P. (Electronics) Ltd

100 WATTS!

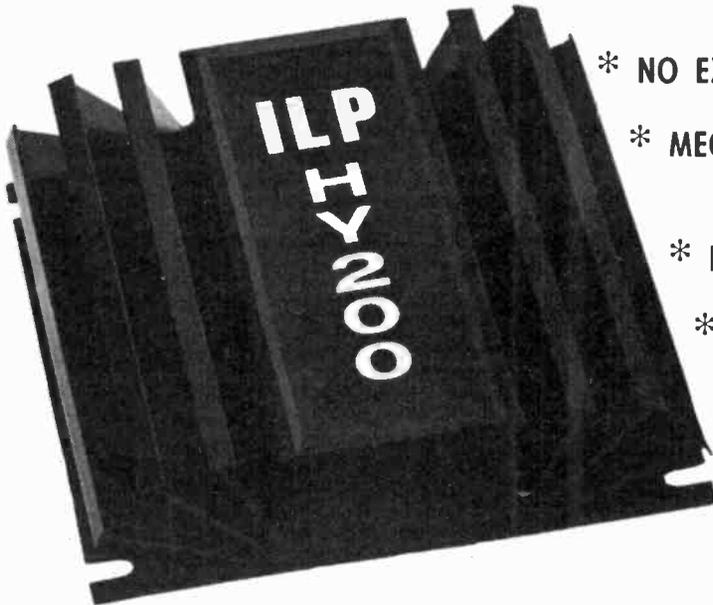

- * NO EXTERNAL COMPONENTS
- * MECHANICALLY & ELECTRICALLY ROBUST
- * INTEGRAL HEATSINK
- * HERMETICALLY SEALED UNIT
- * ATTRACTIVE APPEARANCE
- * LOW COST
- * BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

OUTPUT POWER: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10k Ω . **INPUT SENSITIVITY:** 0Dbm (0.775volt RMS). **LOAD IMPEDANCE:** 4-16 Ω . **TOTAL HARMONIC DISTORTION:** less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz-50KHz \pm 1Db. **SUPPLY VOLTAGE:** \pm 45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE:** £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378B OC78
T9	8 2G389A 2N1302
T10	8 2G417 AF117

All 55p each pak

ND 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for

Part No.	For	Price
BBX 21, C 407, 2N 1893	100	1.10
120vcb.	100	1.92
1 25 100+	500	For 8-20
0-19 0-17 0-18	1000	For 14-35

Sil. trans. suitable for F.E. Organ. Metal TO-18 Epoxy. hfe X 300 6p each. Any Qty.

GP 100 TO3 METAL CASE GERMANIUM

Vebo = 80V. Vceo = 60V. I.C. = 10 amps. Ptot = 30W. hfe = 20. 100vcb. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1 25 100+	0-48 0-44 0-40
-----------	----------------

GP 300 TO3 METAL CASE SILICON

Vebo = 100V. Vceo = 60V. I.C. = 15 amps. Ptot = 15W. hfe = 20. 100vcb. Replaces suitable replacement for 2N 3055, BDY 11 or BDY 20.

1 25 100+	0-55 0-50 0-51
-----------	----------------

NEW 7th EDITION TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. 90p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

UT 46 UNIJUNCTION TRANSISTORS

Direct replacement for T18 46ran. BEN 3000 also electrically equivalent to 2N2646

0 1 25 100+	0-30 0-28 0-22
-------------	----------------

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N708/8. BSY-27/23/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

Part No.	For	Price
20	For	0.55
50	For	1.10
100	For	1.92
500	For	8-20
1000	For	14-35

SIL. G.P. DIODES 5p

300mV 30 0.55
40Piv(Mln.) 100 1.85
Sub-Min. 500 5.50
Fully Tested 1,000 9.90
Ideal for Organ Builders.

R 2400 TO3 NPN SILICON HIGH VOLTAGE

Vebo = 250V. Vceo = 100V. I.C. = 6 amps. Ptot = 30W. hfe = typ 20. IT = 5MHz.

1 25 100+	0-55 0-50 0-44
-----------	----------------

ADI61/162

M/P COMP GERM TRANS. OUR LOWEST PRICE OF 81p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS

SILICON PHOTO TRANSISTOR TO-18 Lens end

NPN SIM. to BPX28 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price ea. 69p 44p 35p

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 15p ea. 1/4W (Top-Hat) 20p ea. 10W (80-10 Stud) 33p ea.

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classified as out-of-spec from the maker's very rigid specifications, but are ideal for learning about IC's and experimental work.

Pak No.	Contents	Price
UIC00	= 12 x 7400	0-55
UIC01	= 12 x 7401	0-55
UIC02	= 12 x 7402	0-55
UIC03	= 12 x 7403	0-55
UIC04	= 12 x 7404	0-55
UIC05	= 12 x 7405	0-55
UIC06	= 8 x 7406	0-55
UIC07	= 8 x 7407	0-55
UIC10	= 12 x 7410	0-55
UIC20	= 12 x 7420	0-55
UIC30	= 12 x 7430	0-55
UIC40	= 12 x 7440	0-55
UIC41	= 6 x 7441	0-55
UIC42	= 6 x 7442	0-55
UIC43	= 6 x 7443	0-55
UIC44	= 6 x 7444	0-55
UIC45	= 6 x 7445	0-55

Packs cannot be split, but 25 assorted pieces (onr mix) is available as PAK UIC X1.

2 A w P. BRIDGE RECTS.

Part No.	Price
50 v RMS 35p each	
100 v RMS 40p each	
400 v RMS 50p each	
Size 16 mm x 16 mm.	

D1889 NPN SILICON DUAL TRANSISTOR (Similar to 2N2060)

Part No.	Price
1 25 100+	0-28 0-26 0-23

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0-55
Q2	16 White spot R.F. transistors PNP	0-55
Q3	4 OC 77 type transistors	0-55
Q4	6 Matched transistors OC44/45/81/81D	0-55
Q5	4 OC 75 transistors	0-55
Q6	5 OC 72 transistors	0-55
Q7	4 AC 128 transistors PNP high gain	0-55
Q8	4 AC 126 transistors PNP	0-55
Q9	7 OC 81 type transistors	0-55
Q10	7 OC 71 type transistors	0-55
Q11	2 AC 127/128 Complementary pairs PNP/PNP	0-55
Q12	3 AF 116 type transistors	0-55
Q13	3 AF 117 type transistors	0-55
Q14	3 OC 171 H.F. type transistors	0-55
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-55
Q16	2 GET890 low noise Germanium transistors	0-55
Q17	0 NPN 2 x ST141 & 3 x ST140	0-55
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-55
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-55
Q20	4 OC 44 Germanium transistors A.F.	0-55
Q21	4 AC 127 NPN Germanium transistors	0-55
Q22	20 NKT Transistors A.F. R.F. coded	0-55
Q23	10 OA 202 Silicon diodes sub-min.	0-55
Q24	8 OA 81 diodes	0-55
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0-55
Q26	8 OA95 Germanium diodes sub-min IN69	0-55
Q27	2 10A PIV Silicon rectifiers IN428R	0-55
Q28	2 Silicon power rectifiers BYZ 13	0-55
Q29	4 Silicon transistors 2 x 2N698, 1 x 2N697, 1 x 2N698	0-55
Q30	7 Silicon switch transistors 2N706 NPN	0-55
Q31	6 Silicon switch transistors 2N708 NPN	0-55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0-55
Q33	3 Silicon NPN transistors 2N1711	0-55
Q34	7 Silicon NPN transistors 2N2369, 500MHz (code P397)	0-55
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0-55
Q37	3 2N3053 NPN Silicon transistors	0-55
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0-55

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:- Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and " Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 22 cm x 4cm. Complete with case and instructions. Price each: 43-89

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	80 Mixed Germanium Transistors AF/BF	0-55
U 3	76 Germanium Gold Bonded Sub-Min. like OA6, OA47	0-55
U 4	40 Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil. Planar Trans. NPN like BS795A, 2N706	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 PIV	0-55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-55
U10	20 BAY80 charge storage Diodes DO-7 Glass	0-55
U11	25 PNP Sil. Planar Trans. TO-6 like 2N1132, 2N2904	0-55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-55
U13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0-55
U14	150 Mixed Silicon and Germanium Diodes	0-55
U15	25 NPN Sil. Planar Trans. TO-6 like BFY61, 2N697	0-55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000 PIV	0-55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-55
U19	25 Silicon NPN Transistors like BC108	0-55
U20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-55
U23	30 MADT'S like MEZ Series PNP Transistors	0-55
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-55
U25	25 300 MHz NPN Silicon Transistors 2N706, BSY27	0-55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-55
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0-55
U29	1 1 Amp SCR's TO-5 can, up to 600 PIV CRB1/25-600	1-10
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0-55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-55
U32	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0-55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 2B302/4	0-55
U35	25 Silicon Planar Transistors PNP TO-6 2N2906	0-55
U36	25 Silicon Planar NPN Transistors TO-5 BFY60/51/52	0-55
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0-55
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-55
U39	30 RF. Germ. PNP Transistors 2N1803/6 TO-5	0-55
U40	10 Dual Transistors 6 lead TO-5 2N2960	0-55
U41	25 RF Germanium Transistors TO-1, OC45, NKT72	0-55
U42	10 VHF Germanium PNP Transistors TO-1, NKT667, AF117	0-55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-55
U44	20 Sil. Trans. Plastic TO-5 BC115/116	0-55
U45	7 3A SCR. TO66 up to 600 PIV	1-10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

NEW LOW PRICED TESTED S.C.R.'s

Part No.	Price
PIV1A 3A 5A 5A 7A 10A 16A 30A	
TO5 TO6 TO6 TO6 TO6 TO48 TO48 TO48 TO48 TO48	
500-26 0-28 0-39 0-39 0-52 0-55 0-59 1-27	
100-0-28 0-37 0-52 0-52 0-55 0-64 0-70 1-64	
200-0-39 0-41 0-54 0-54 0-63 0-67 0-83 1-76	
400-0-48 0-62 0-62 0-62 0-74 0-83 1-03 1-93	
600-0-59 0-63 0-75 0-75 0-85 1-07 1-38	
800-0-70 0-77 0-88 0-88 0-99 1-32 1-65 4-40	

F.E.T.'S

Part No.	Price
2N3819 31p	2N5458 36p
2N3820 56p	2N5469 44p
2N3821 30p	2N5710 60p
2N3823 81p	MPP105 41p

DIACS TRIACS

FOR USE WITH TRIACS. BR100 (D82) 41p each

Part No.	Price
100 83 55 83	
200 55 68 99	
400 77 83 1-21	

CADMIUM CELLS

ORP12 48p ORP60, ORP61 44p each

FREE One 55p Pak of your own choice free with orders valued £4 or over

115 WATT SIL POWER NPN 55p EACH

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 11p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

SPECIAL OFFER !!!

SMALL ELECTROLYTICS

Ref. No.	Capacity	Voltage	Price	Ref. No.	Capacity	Voltage	Price
H8/2	2.2µf	25v	4p	H7/4A	64µf	35v	5p
H8/2A	3.3µf	25v	4p	H7/5	80µf	16v	4p
H8/3	3µf	50v	4p	H7/6	100µf	25v	5p
H8/3A	4µf	50v	4p	H7/6A	100µf	15v	4p
H8/4	4.7µf	25v	4p	H7/7	100µf	25v	4p
H8/4A	5µf	64v	4p	H7/8	125µf	16v	5p
H8/5	5µf	10v	4p	H7/8A	100µf	35v	6p
H8/5A	5µf	150v	4p	H7/9	150µf	16v	6p
H8/6A	10µf	10v	4p	H7/9A	125µf	4v	4p
H8/7	10µf	70v	4p	H7/10	125µf	25v	6p
H8/8	16µf	35v	4p	H7/10A	180µf	2.5v	3p
H8/8A	16µf	16v	4p	H7/11	160µf	25v	6p
H8/9	20µf	8v	2p	H7/11A	150µf	16v	5p
H8/9A	20µf	70v	4p	H7/13A	220µf	25v	8p
H8/10	22µf	50v	4p	H7/14	220µf	50v	10p
H8/10A	22µf	100v	4p	H7/14A	220µf	16v	6p
H8/11	25µf	12v	4p	H7/15	220µf	25v	5p
H8/11A	24µf	275v	4p	H7/15A	220µf	35v	10p
H8/12	32µf	15v	4p	H8/1A	250µf	4v	3p
H8/12A	30µf	10v	4p	H8/3A	320µf	2.5v	3p
H8/13A	32µf	40v	4p	H8/4	320µf	10v	4p
H8/14	40µf	25v	5p	H8/4A	330µf	18v	5p
H8/14A	40µf	16v	4p	H8/5	330µf	25v	10p
H8/15	47µf	50v	4p	H8/5A	330µf	15v	15p
H8/15A	40µf	35v	4p	H8/7	400µf	15v	5p
H7/1	50µf	6v	3p	H8/8	470µf	25v	10p
H7/1A	50µf	10v	4p	H8/8A	470µf	35v	20p
H7/2	50µf	50v	4p	H8/9A	400µf	40v	20p
H7/2A	64µf	2.5v	2p	H8/10	750µf	12v	5p
H7/3A	64µf	25v	4p	H8/13A	1000µf	25v	18p
H7/4	64µf	15v	4p	H5/2A	2200µf	16v	15p

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series		Working Voltage Vdc.	Capacitance µF	Max. Ripple Current at 50°C	Weight	Price
071 15332	16		3300	2.5 amps	1oz	15p
071 15472	16		4700	3.9 amps	1oz	17p
071 15682	16		6800	5.8 amps	1½oz	22p
071 15103	16		10000	7.9 amps	2½oz	27p
072 15152	16	7500 + 7500		10.5 amps	3oz	37p
072 15113	16	11000 + 11000		13.8 amps	4½oz	49p
071 16222	25		2200	2.2 amps	1oz	15p
072 16502	25	5000 + 5000		9.6 amps	3½oz	37p
072 16752	25	7500 + 7500		12.6 amps	4½oz	49p
072 17342	40	3400 + 3400		9.1 amps	3½oz	37p
072 17502	40	5000 + 5000		12.0 amps	4½oz	49p
071 18681	63		680	2.1 amps	1oz	15p
072 18172	63	1850 + 1850		7.8 amps	3oz	37p

106 and 107 Series		Working Voltage Vdc.	Capacitance µF	Max. Ripple Current at 50°C	Weight	Price
106 15103	16		10000	7 amps	2½oz	65p
106 16223	25		22000	17 amps	10oz	£1.12
106 17103	40		10000	12 amps	7½oz	94p
106 18153	63		15000	28 amps	18oz	£1.79
107 10222	100		2200	10 amps	5½oz	74p

Type No.	Voltage	Capacitance	Weight	Price
102 15163	16	16000	8oz	26p
104 90003	20	39000	16oz	36p
102 16802	25	8000	7oz	25p
104 17562	40	5600	5oz	25p
104 90001	45	20000	16oz	56p

A further 10% discount on lots of 100 of any one type.
 Please calculate the weight of your order and include appropriate postage.
 Not over Ordinary Parcels | Not over Ordinary Parcels
 1½lb 16p | 10lb 37p
 2½lb 21p | 14lb 47p
 4lb 25p | 18lb 57p
 6lb 29p | 22lb 67p

ALL GOODS PLUS 10% V.A.T.

£1 100 ½ WATT RESISTORS
 100 CERAMIC CAPACITORS
 100 DIODES

POSTAGE 15p | PACK No. 1

£1 1 VERO-BOARD CUTTER
 5 2 1/2 in. x 1 in. x 15 BOARDS
 50 SQ. INS. "ODD PIECES"

POSTAGE 15p | PACK No. 3

£1 20 ASSORTED UNUSED
 MARKED, TESTED
 TRANSISTORS
 BC108 ETC.

POSTAGE 15p | PACK No. 5

£1 6 COMPUTER PANELS
 CONTAINING MASSES OF
 DIODES, TRANSISTORS,
 INDUCTORS, RESISTORS
 & CAPACITORS

POSTAGE 25p | PACK No. 7

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 100 POLYSTYRENE CAPACITORS

POSTAGE 15p | PACK No. 2

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 50 MULLARD POLYESTER CAPACITORS

POSTAGE 15p | PACK No. 4

£1 1 TRANSISTORISED
 SIGNAL TRACER KIT
 1 TRANSISTORISED
 SIGNAL INJECTOR KIT

POSTAGE 15p | PACK No. 6

£1 100 RESISTORS
 100 CAPACITORS
 (ASSORTED TYPES)

POSTAGE 15p | PACK No. 8



The Pictorial Method

**BASIC ELECTRICITY (5vols)
 BASIC ELECTRONICS (6vols)
 BASIC TELEVISION (3vols)**

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

WHAT READERS SAY

"WHAT A CONTRAST TO OTHER MANUALS", I have grappled with. I am delighted with them. *W.A.F. Durham*

I didn't know this subject could be so easily presented. *J.K. Earlsfield*

Pleased to say how understandable your books are—I now have a sound knowledge of the subject. *A.K. Hull*

Invaluable for my training as a Technician. *W.J. Stockport*

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £4.50
- BASIC ELECTRONICS 6 parts £5.40
- BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME

BLOCK LETTERS

FULL POSTAL.....

ADDRESS

POST NOW FOR THIS OFFER!

BSR LATEST SUPERSLIM

STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 18 1/2 x 11 1/2 in.



Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO and MONO XTAL

£8-25 Post 25p

PORTABLE PLAYER CABINET

Modern design. Black resin covered. Silver front grille. Chrome fittings. Motor board out for BSR deck.

£4.50 Post 25p

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 1 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeaker making it extremely compact.

overall size only 1 1/2 x 10 x 3 1/2 in. 3 watts per channel. plays all records 33 rpm, 45 rpm. Separate volume & tone controls. 240v AC mains



Attractive Teak finish. Weight 18lbs.

Bargain Price **£25** 85p carriage

SPECIAL OFFER SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes Type A or 0 to 6 hours Type B. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated.



OUR PRICE £1-65 or £3 pair

Post 25p (PLEASE STATE TYPE A OR B WHEN ORDERING)

WEYRAD P50-TRANSISTOR COILS

BA2W Ferrite Aerial. 72p
Osc. P50/1A/C 33p
L.F. P50/3C/470 k/c/s. 38p
3rd L.F. P50/3C/700 35p
Sparks Cores 8p
Ferrite Rod 8 x 1/2 in. 80p 6 x 1/2 in. 20p 3 1/2 in. 10p

Driver Trans. LFDT4. 58p
Printed Circuit. PCA1. 58p
J.B. Tuning Gank 65p
Worrad Booklet 10p
OPT1 65p

VOLUME CONTROLS
5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p.
STEREO L/S 55p. D.P. 75p.
Edge 5K.A.P. Transistor 55p

80 ohm Coax 4p. yd.
BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. 21-40; 60p. 22.
FRINGE LOW LOSS OPT1. Ideal 625 & colour 10p yd.

8in & 10in ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 8in. 10 watt. 10in. 12 watt music power



£3-75 Post 25p

E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated)

£4-50 Post 25p



With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-80 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p

£2-75 Post 25p

BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors Plus integrated circuit. Fibre-Glass Printed circuit board. Size 2 1/2 x 8 1/2 in. Pre-Aligned. Complete with stereo bass indicator. 12V d.c. operation. 400mV Output for 100mV Inpt. Full instructions for use with any FM Tuner. Some technical experience essential.

Post 20p

BLANK ALUMINIUM CHASSIS. 18 s.w.c. 2 1/2 in. sides 6 x 4 in. 45p; 3 x 6 in. 53p; 10 x 7 in. 65p; 12 x 8 in. 85p; 14 x 9 in. 90p; 16 x 9 in. 90p; 12 x 3 in. 50p; 16 x 10 in. 21. ALUMINIUM BOX 6 x 4 x 4 in. 80p. ALUMINIUM PANELS 18 s.w.c. 6 x 4 in. 9p; 8 x 6 in. 15p; 14 x 3 in. 16p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 28p; 16 x 6 in. 28p; 14 x 9 in. 34p; 12 x 12 in. 40p; 16 x 10 in. 50p PAXOLIN PANEL 10 x 8 in. 15p.

ANOTHER RGS BARGAIN!

4 Transistor Mono Amplifier

Powerful 3 watt output. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knob. Ready made on printed circuit board. Fused inputs and outputs. Famous make. Size 8in. wide x 4in. deep x 3in. high. Less speaker Suitable 7" x 4" speaker, £1. **PRICE £5-95** Post 25p

R.C.S. STABILISED POWER PACK KITS All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Main Transformer. Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. **£2-20** Post 20p Details S.A.E. Size 3 1/2 x 1 1/2 in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE Ideal for Mike, Tape, P.T., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. d.c. operation. Size 1 1/2" x 1 1/2" x 1". Response 25 c/s to 25 Kc/s, 26 dB gain. For use with valve or transistor equipment. **99p** Post 20p Full instructions supplied. Details S.A.E.

E.M.I. WOOFER AND TWEETER KIT Woofer 10 1/2 x 6 1/2 in. Ceramic Magnet, 4oz. 13,000 lines. Tweeter 3 1/2 in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms, power 12 watts. **£5-75** Post 25p.

BRITISH FM/VHF TUNING HEART

88 to 108 MHz British made. 2 Transistors ready aligned requires 107 MHz Crystal. Complete with tuning scale. Connections supplied but some technical experience essential. **Our price £3-95** Post 20p

MAINS TRANSFORMERS

All post 25p each
Eagle MT12 12-0-12V 50mA 90p
250-0-250 80mA 6-3V 3-5A, 6-3V 1A, or 5V 2A £2-50
350-0-350 80mA, 6-3V 3-5A, 6-3V 1A, or 5V 2A £3
300-0-300 120mA, 6-3V 4A C.T., 6-3V 2A £3-25
MINIATURE 200V, 200A, 6-3V 1A, 2 1/2 x 2 1/2 in 75p
MIDGET 220V 45mA, 6-3V 2A, 2 1/2 x 2 1/2 in 90p
HEATER TRANS. 6-5 3A 60p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 20V £2-80
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V £2-80
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V £3-80
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V £8-75
3A, 5, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V £2-20
4A, 5, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V £1-50
6-0-5 amp 90p
9V 1 amp 95p
12V 300 mA 75p
12V 500 mA 85p
12V 750 mA 95p
AUTO TRANSFORMERS. 110V to 230V or 230V to 110V 150W £2-50, 500W £6-25; 750W £13; 1000W £15.
CHARGER TRANSFORMERS Input 200/250V for 6 or 12V. 1 1/2 A, 21-50; 2A, 31-80; 4A, £2-50.
BATTERY CHARGERS. 1 1/2 A £2; 3A £2; 4A £4; 5A £4-50.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **OUR PRICE £10** Carr. 50p. Famous make. (Value £15) Can be used as 800V auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS
2/250V .14p 100/25V .10p 32+32/350V .40p
4/350V .14p 250/25V .14p 50+50/350V .50p
8/450V .18p 500/25V .20p 60+100/350V .85p
18/450V 22p 1800/25V .25p 32+32/250V .20p
32/450V 25p 1000/50V .47p 32+32/450V .45p
32/500V 50p 8+8/450V 22p 350+50/325V 55p
25/25V .10p 8+18/450V 25p 32+32+32/350V 55p
60/50V .10p 18+18/450V 40p 100+50+50/350V 55p

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 12V. 15p; 25V. 20p; 50V. 30p.
1000mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p.
2000mF. 6V. 25p; 25V. 42p; 50V. 57p.
2500mF. 6V. 25p; 8000mF. 25V. 47p; 50V. 65p.
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 95p.

CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p PAPER 350V-0.1 4p, 0.5 18p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1% ± 2-500pF 5p; 250-2200 pF 10p; 2.700-5.600pF 20p; 6.800pF-0.01, mfd 30p; each. TWIN GANG. "0-0" 208pF+178pF, 65p; 500pF standard 75p; 385+385 with 25+25p 80p motion drive 50p. SHORT WAVE, SINGLE. 10p 30p; 25p 55p; 50p 55p. NEON PANEL INDICATORS. 250V AC/DC Amber 20p. RESISTOR. 1W 1/2W 20p; 1/4W 10p; 1/8W 5p; 10 1/2 to 10M. HIGH STABILITY. 1% ± 2%, 10 ohms to 10 meg., 10p. Ditto 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each; 0.5 ohm to 8 ohms 10p. TAPE OSCILLATOR COIL. Valve Type 35p.

NEW MODEL "BAKER LOUDSPEAKERS" 12in. 50 watt GROUP 50/12 8 or 15 ohm high power full range group speaker £17-60.

BAKER MAJOR 12" £9-90



30-14,500 c/s, 12in. double cone, woofer and tweeter cone with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c/s Rated 20 watts. NOTE: 8 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£12-50** P. & p. 25p. Please state 3 or 8 or 15 ohms. Post 25p

BAKER "BIG-SOUND" SPEAKERS P. & p. 25p
'Group 25' 12 inch £8-80 15 inch £9-90 16 inch £9-90
25 watt 35 watt 50 watt
3 or 8 or 15 ohm 3 or 8 or 15 ohm 8 or 15 ohm

TEAK VENERED HI-FI SPEAKER CABINETS
For 12in. or 10in. dia. speaker 20 x 13 x 6in. £9-90 Post 25p
For 18 x 8in. or 8in. speaker 16 x 10 x 6in. £5-50 Post 25p
For 8 x 6in. speaker 16 x 8 x 6in. £4-40 Post 25p
For 6in. and tweeter 12 x 8 x 6in. £4-00 Post 25p
LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns, Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 24-00. Suitable Tweeter £2-00. **£4**

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt, 3 ohm or 15 ohm models. **£1-90** Post 20p Crossover 95p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16k/c/s, 10W 8 ohm or 15 ohm 21-95 De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £3-50 CROSSOVERS TWO-WAY 8000cps 3 or 8 or 15 ohm 95p- LOUDSPEAKERS 8 OHMS. 7 x 4in. £1-25; 6in. £1-50 8 x 5in. £1-60 8in. 10 x 6in. £1-90; 10in. £2-00. SPECIAL OFFER: 8ohm, 2 1/2 in., 2 1/2 in. 35 ohm. 2in. 5in. 25 ohm. 2 1/2 in. dia. 5in. dia. 6" x 4" £1 EACH 15 ohm, 3 1/2 in. dia.; 6 x 4 in.; 7 x 4 in.; 8 x 6 in. TYPE 8 ohm, 2 1/2 in.; 2 1/2 in.; 3 1/2 in. 5in. dia. 8 ohm 21-50; RICHARD ALLAN TWIN CONE LOUDSPEAKERS: 8 in. diameter 4 watt £2-50. 10in. diameter 5 watt £2-95. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO. 3, 8 and 15 ohms, 80p. Mike trans. mu metal 100:1 41-25.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. **£49** Carr. £1-00 Separate treble and bass controls. VALVE MODEL 100 WATT CALLERS ONLY 25p.

BARGAIN AM TUNER. Medium Wave. £4-95

Transistor Superhet. Ferrite aerial. 9 volt. BARGAIN 4 CHANNEL TRANSLATOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 watt. **£3-95**

2 STEREO VERSION £5-95

BARGAIN 8 WATT AMPLIFIER. 4 Transistor £4-50

Push-Pull Ready built, with vol. control, treble and bass controls 18v. DC4 operation.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p OUTLET BOXES, SURFACE OR FLUSH, 25p. BALANCED TWIN FEEDER 800 ohms 5p yard. JACK SOCKET Std. open-circuit 14p. closed-circuit 25p. Chrome Lead Solder 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p; 4-pin 10p. DIN SOCKETS Lead 3-pin 18p; 6-pin 25p. DIN PLUGS 3-pin 18p; 6-pin 25p. VALVE HOLDERS. 5p; CERAMIC 3p; CAN 5p.

REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt **£1-95** spindle 1 1/2 x 7/16 in. size 3 1/2 x 3". As illustrated. With Cooling Fan 240V A.C. Post 25p

ONE RPM GEARED MOTOR

240v. A.C. mains. Ideal for displays/ disco lightshows. **95p** Post 25p

E.M.I. GRAM MOTOR £1-00

120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 x 1 in. Post 25p.

RADIO COMPONENT SPECIALISTS

Minimum post 20p. Illustrated Colour Brochure, Radio Books & Components Lists. 10p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

TO SPARK YOUR IMAGINATION!



Kit comprises **EVERYTHING:** Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.

the **SPARKRITE**

Electronic Ignition Kit only £9.35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: **£9.35** inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available **£11.55** inc. V.A.T. and postage. **GUARANTEED 5 YEARS.**

ORDER NOW To: **ELECTRONICS DESIGN ASSOCIATES,**
82 Bath Street, Walsall WS1 3OE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9.35. Or for ready built unit £11.55.

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing).

PW11

SPECIAL 40 MHZ SCOPE—SOLARTRON CD1212 ONLY £50. Has to be a snag. There are no plug-in Y amps available.

TB—100 nanosecs per cm to 5 secs per cm in 24 calibrated ranges. 20 nanosecs per cm with times 5 expansion. 5in flat faced tube. Trace locator. 0.2 microsec signal delay. Built-in calibrator 1kHz square wave. 200 micro volts to 100 volts in 18 calibrated ranges. Tube sensitivity 3V/cm. Main Frame Y Amp boosts this to better than 200 MV per cm at 40 MHz. 240V 50 Hz input. Complete with full manual including plug-in circuits. Come and see one working or Carriage £1.50.

12" LONG PERSISTENCE CRT. Full spec. Price £12.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for **ONLY £5.50, P. & P. 25p.** (Not cased, not calibrated.)

NEW WIDE RANGE WOBBULATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for **ONLY £5.75, P. & P. 25p.** (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. **£7.85 each, P. & P. 25p.** (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

PLEASE ADD 10% V.A.T.

Open 9 a.m. to 6.30 p.m. any day.

CHILTMEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech. College)

Tel.: Reading 582605/65916

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors $\frac{1}{2}$ and $\frac{1}{4}$ watt, many high stabs, etc. Fine value at 50p, P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice. 25p, P. & P. 15p.

5 MOVING COIL METERS. Various. £2, P. & P. 37p.

CAPACITOR PACK—50 Brand new components, only 50p, P. & P. 17p.

POTS—10 different values. Brand new. 50p, P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 10p.

FLAT FACED 4" TWIN BEAM TUBE type CV2193. Green trace. Brand new £4 each, P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New. 38p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each.

PHOTO RESISTOR type Clare 703. Two for 50p.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. The same but black, £2.75 each, P. & P. 25p each.

Also **TOPAZ YELLOW** £4.50 each, P. & P. 25p.

Ideal **EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding. £1.75 each, P. & P. 25p.

DELIVERED TO YOUR DOOR
1cwt of Electronic Scrap chassis, boards, etc. No Rubbish. **FOR ONLY £3.50.**

LASKYS 1974 CATALOGUE

FREE

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME


ADDRESS

AUDIOTRONIC HOUSE, THE HYDE, LONDON, NW9 6JJ

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic ASTRAD 17 and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £18.50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! ★ Send quickly, test on mail order 7 day approx. from receipt of goods—refund if not delighted. Or call. Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pinpoint" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day, including all normal transmissions, VHF: FM/USW, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in 'rotatable' telescopic aerial extending to 39 ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. SIZE 13 x 10 x 4 1/2 ins overall approx. Magnificently designed in highly polished cases. Made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!) With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **PLUS** Ultra-sensitive earphone for personal listening. **ONLY £18.50** (with mains/battery eliminator £2.25 extra). **BOX, POST, ETC. 45p. NO MORE TO PAY! ★ BUT WAIT!** For only 55p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to zone & time in a flash for transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K., when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard 'longlife' batteries and converter plug. (Sorry—We cannot change these new radios for any earlier model purchased.) Send quickly to Uxbridge Road address, or call at either store. Many fantastic bargains always on display at both stores.

**THOUSANDS OF MILES REDUCED TO INCHES?
1973 RUSSIAN RADIO TECHNOLOGY
SHRINKS THE WORLD! *COMPUTERISED?**

**THIS FANTASTIC
EARTH SHRINKER**

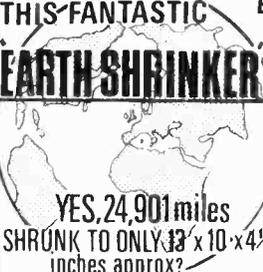

**YES, 24,901 miles
SHRUNK TO ONLY 13" x 10" x 4 1/2"
inches approx?**

**BRAND NEW
FABULOUS ASTRAD 17**
PORTABLE RADIO & COMMUNICATIONS
RECEIVER



28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

BATTERY MODEL £18.50
BOX POST ETC. 45p
MAINS/BATTERY ELIMINATOR £2.25 extra

FIRST TIME EVER!

* NOW AVAILABLE WITH
**FABULOUS "COMPUTERISED"
WORLD TUNING GUIDE!**
NO MORE GUESSWORK—
INSTANT DATA at your fingertips —
enables you to ZONE & TIME IN A FLASH
for transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £23.03 NOW!**

FABULOUS BRAND NEW SOLID STATE

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



This equipment's got EVERYTHING!

RECOMMENDED RETAIL PRICE £44

OUR PRICE £20.97 **CARR. ETC. 43p**

WITH REMOTE CONTROL MICROPHONE

Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord). Record and play back anything, anywhere! **IMPORTERS RECOMMENDED RETAIL PRICE £44! WE OFFER AT UNDER HALF PRICE!** Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveler! ★ Separate ON/OFF and HI-LO volume controls! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker socket! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. AND the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, city and regional stations in every part of the country, plus B.B.C. National. VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £ £ £ more for a Car Radio or Car Cassette player ALONE! **OUR FANTASTIC PRICE ONLY £20.97** carr. etc. 43p. No more to pay! Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, test on 7 days mail order approval from receipt of goods, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 20p extra if required. Callers: ACCESS & BARCLAYCARDS ACCEPTED AT BOTH STORES.

SHOPERTUNITIES LTD.
HOLBORN (opp. Chancery Lane), LONDON, W.C.1 (Thurs. 7)

FIRST TIME EVER! *SAVE £16.02!

BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER



FIRST CLASS MAKERS

With remote control microphone.

WE COULD CHARGE UP TO £26.97!

OUR PRICE £10.95 **POST ETC. 50p**

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb deluxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £10.95!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest **MASTER SWITCH** control) AND **AUTOMATIC LEVEL CONTROL.** No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9 1/2 in x 5 1/2 in x 2 1/2 in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Importers recommended selling price £26.97!) **OUR PRICE ONLY £10.95** post etc. 50p. **NO MORE TO PAY!** ★ Send quickly, test on mail order 7 day approx. from receipt of goods—refund if not delighted. **BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries AND microphone etc. if all for 55p extra, if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn store.)

Dept. WP/NC/34, 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON, W12 8AQ (Thurs. 1, Fri. 7). Also at 37/39 HIGH
BOTH STORES OPEN MON. TO SAT. 9 A.M. UNTIL 6 P.M.

Why pay more - look at our Fantastic Bargain Offer!

PENTHOUSE

A COMPLETE AUDIO SYSTEM

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder, 4 wavebands Long/Medium/Short/VHF, 8 watts per channel (music power) output. The latest BSR C129 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.


OUR PRICE £95.00



Credit terms £5.00 deposit plus £2.00 p. & p. followed by 12 payments of £4.80. Total Credit Terms £62.60 SEND £7.00 TODAY.

KLINGER

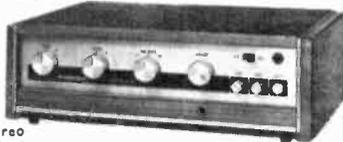
FIVE NINETY THREE UNIT AUDIO SYSTEM with BSR McDonald 4-speed Record Player, matching 4-unit Loud-speaker Systems and FREE Stereo Head-phones.



High performance Stereo Amplifier designed for home entertainment at economical cost. Represents a considerable advance in solid state, high fidelity stereo amplifiers. Outstanding performance is allied to meticulous construction, comprehensive facilities, installation simplicity and attractive styling.

10 watt per channel power; push button selectors: tone controls; balance control; tape record and replay facilities. Stereo headphone socket on front panel with automatic speaker muting; Teak finish. Our price £78.00 + £2.00 p. & p. Credit Terms £7.50 deposit + £2.00 p. & p. 18 monthly payments of £4.46 (total £87.78) Send £9.50 today.

THE AVON AUDIO SYSTEM

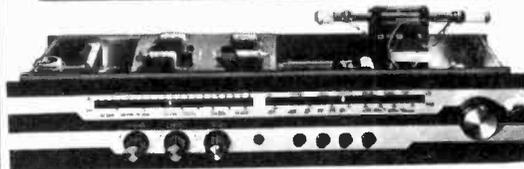

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

BSR 4 SPEED STEREO/MONO RECORD CHANGER plays all types of 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £35.00. Credit Terms £3.50 deposit plus £2 Post & Packing followed by 12 payments of £3.10 (Total Credit Terms £40.70) Dont miss this bargain.

SEND £5.50 TODAY

ALL EQUIPMENT COVERED 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

Please send me free details of your range

Name


Address.....PW11/73

Post coupon NOW for... **FREE** leaflets

LEWIS radio

100, Chase Side London N.14 Tel: 01-886 3733/9666

DABAR MN3 MIXER KIT

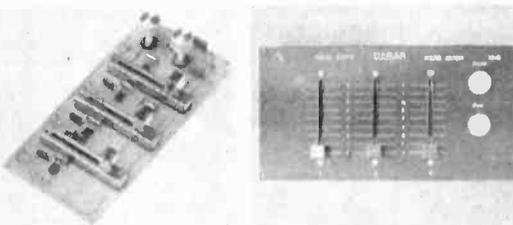

INTRODUCING THE NEW DABAR MINI THREE CHANNEL MIXER KIT WITH THE FOLLOWING FEATURES:

- ★ Three inputs easily adjustable to suit users input requirements, e.g., Mic., Tape, Disc., etc.
- ★ Uses advanced design with five integrated circuits.
- ★ Slider fader volume controls mount directly on P.C. board.
- ★ Full range bass and treble controls.
- ★ Guaranteed top grade components with fibreglass printed circuit board, ready-drilled and tinned.
- ★ Battery operated (2 x PP3) not supplied with kit.
- ★ Easy to follow assembly instructions (available separately 25p).
- ★ Attractive ready punched facia plate, available at extra cost, gives that professional finish to the unit.
- ★ Size: 9.5" x 4.8" x 2".

PRICE: KIT ONLY £11.00
FACIA PLATE £1.50
MANUAL AND ASSEMBLY INSTRUCTIONS 25p
AVAILABLE READY BUILT WITH FACIA £18.00

ALL PRICES INCLUDE V.A.T. & POSTAGE IN U.K.
 S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

98, LICHFIELD STREET, WALSHALL, STAFFS, WS1 1UZ.

ELECTROLYTIC CAPACITORS UF/V 2000/50, 2500/50, 5000/50, 10,000/50, 12,500/50. All at 50p each, post paid.

SPECIAL OFFER: WIRE-ENDED METALLISED FILM CAPACITORS 2-2UF 63V 15p, 4UF 63V 20p, 6UF 63V 20p, 8UF 63V 25p, 10UF 63V 25p. All post paid.

SOKSOL DE-SOLDER KIT: Includes 20ft special copper braid, chemical solution and Instructions £1, post 15p.

DELCO-REMY 12 Volt Car-Horn Relays 50p, post paid.

SUBMINIATURE PLUG-IN CRYSTALS for radio control. 26-985MHz and 27-028MHz 70p each, post paid.

AMERICAN DYNAMOTOR ROTARY TRANSFORMERS. Input 27 Volts D.C. Output 285 Volts D.C. at 75 M/A £1.00, post 30p.

PLESSEY VIBRATORS Type 1214 50p, post paid.

ADD 10% V.A.T.

SEE OUR OTHER ADVERTISEMENTS IN RADIO & ELECTRONICS CONSTRUCTOR


ELEKON ENTERPRISES

224a St Paul's Road, Highbury Corner, London N.1

Telephone 01-359 4224

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT! HANDY! TIDY!

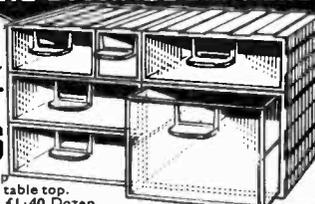

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D, 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.40 Dozen

DOUBLE UNITS £2.30 Dozen

TREBLE (3D) £2.50 for 8

DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.60

for 8 extra large size (6D1) £3.40 for 8, Carriage 35p Orders over £10 post free

QUANTITY DISCOUNTS! 5% in £1 for orders over £10, 7 1/2% over £10, 10% over £50. Quotation for large quantities.

PLEASE ADD 10% VAT TO TOTAL REMITTANCE.

IVORYET LIMITED (Dept. PW11), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

5 SIZES ALL INTERLOCK

Exciting...the Stereo 21!

Can you really get sound quality like this FOR LESS THAN £18?

YES, YOU CAN! WITH THE NEW

STEREO 21

Until now, richly satisfying sound has always cost a richly satisfying price. But not any more! For an almost unbelievable £17.95, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!



And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for £17.95 (plus the cost of post and packing if you buy by mail), and—to round it all off—a money refund if not satisfied if your pleasure in STEREO 21 is not complete!

Just think—in only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!

Personal shoppers and mail order price


£17.95 INCLUDING VAT plus £1.50 p + p.

Diamond styli, if required, £1.37 extra
Suitable pair of stereo headphones with individual level controls, if required £3.85.

EMI SPEAKERS AT UNBELIEVABLE PRICES

950 Kit. Five matched speakers and crossover unit for handling up to 45 watts, from 20 to 20,000 Hz. Huge—19" x 14" (approx.) high efficiency 16, 500-gauss bass unit built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3½" dia. approx., are fed by the crossover with a critically adjusted signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00.

OUR PRICE £25.00 + £1.50 p & p

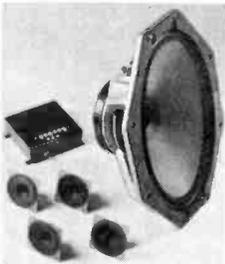

15" 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70 + £1.50 p & p

Just write your order giving your credit card number. **DO NOT SEND YOUR CARD**



Buy it on **BARCLAYCARD** Extended Credit PHONE YOUR ORDER

Access takes the waiting out of wanting

RADIO AND TV COMPONENTS (ACTON) LTD, 21C HIGH STREET ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2

Edgware: 9 a.m. to 5.30 p.m., half day Thurs.
Acton: 9.30 a.m. to 5 p.m. Closed all day Wed.; also see opposite.

Mail orders to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope Goods not despatched outside U.K.



RTVC VISCOUNT III

a boost in the output,

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as value for money! And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! And the teak finish will harmonise and enhance virtually any style of interior decor! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back.

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have never experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair + £2.20 p. & p. **Duo Type III** Size approx. 23½in x 11½in x 9½in. Drive unit approx 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM I

Viscount III R102 amplifier £24.20 + £1 p & p
 2 Duo Type III speakers £14.00 + £2.20 p & p
 Garrard SP25 Mk III with MAG. cartridge /plinth & cover £18.00 + £1.75 p & p
 total **£56.20**

Available complete for only **£49.00** + £3.50 p & p

PRICES: SYSTEM 2

Viscount R102 amplifier £24.20 + £1 p & p
 2 Duo Type III speakers £32.00 + £3.30 p & p
 Garrard SP25 Mk III with MAG cartridge plinth & cover £18.00 + £1.75 p & p
 total **£74.20**

Available complete for **£65.00** + £4 p & p

STILL ONLY **£49** COMPLETE



THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modularised IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep. Circuit diagram and comprehensive instructions 55p free with parts. Fully retractable and lockable car aerial £1.37 post paid.

CAR RADIO KIT £6.60 p. and p. 55p. Speaker with baffle and fixing strips £1.65, + 23p p. & p. post free if bought with the kit. Send stamped addressed envelope for leaflet.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

PE TAPE LINK CONSTRUCTORS



Suitable 3 speed tape deck, less heads. Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty.

£1 p. & p. **£4.00**



RELIANT Mk IV MONO AMPLIFIER


*5 Electrically Mixed inputs.
 *3 Individual Mixing controls.
 *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Output 20 watts into 8 Ω. (suitable for 15 Ω.) Size approx. 12½ x 6 x 3½ ins. **£13.50** p. & p. 60p

UNISOUND MODULES

ONLY £7.64 + 55p. p & p

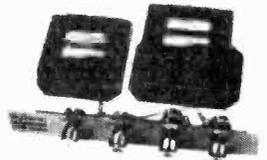For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. The Viscount III, the



fabulous Stereo 21 and the Unisound Modules **£9.90** + 80p. p. & p. will accept this unit, simply connect up.

SEE OPPOSITE PAGE FOR ADDRESS DETAILS

AUTUMN ACTION

If you were fortunate enough to obtain last month's special issue of *Practical Wireless*, and your particular interests are in audio, short wave, broadcast reception, test equipment, or experimental electronics, you will have found at least one item of interest to you. In very general terms, this is what *Practical Wireless* is about, helping and encouraging its readers to have-a-go. This issue is also special in that it is the largest *P.W.* ever produced, carrying 120 pages and two free colour Datacards.

Activities covered by this magazine are, believe it or not, of a seasonal nature and we are always delighted in one sense when the holiday season ends, because we all settle down again after sun-tan(?) and surf-riding to renew our absorbing interest in d.i.y. radio and electronics.

It was often the case in the past when we would expect readers who go away in the summer to leave their tools and *P.W.* at home. Imagine some reader on the Costa Brava wielding a soldering iron on a pair of gritty output transistors—it's just not done is it? We were particularly pleased therefore that the temporary summer recess this year was hardly noticeable; surely the summer was not that bad! And it is known that *P.W.* is read on beaches.

The autumn, therefore, is just the time when, if not already bitten by the bug, our readers look around as if to court the means to satisfy their instinctive curiosity in the techniques of working circuits. You might say that we also provide the necessary bait to give newcomers encouragement to have a go. You might be right, but then if we did not learn something about our readers we would not be the highest selling British magazine of its kind. Some subjects do come up for renewed treatment but unlike some magazines, they are seldom in the same guise as before.

Take our Metal Detector on page 634; not a scrap like the earlier models and certainly easier to make.

October is also the time for the London Audio Fair; it is natural therefore that those readers who will be going to Olympia will want to sort out some of the technical jargon used in the audio world. Very sad that we cannot be there this year so we expect every *P.W.* reader visitor to carry this issue in his pocket, so that he can refer to the extra supplement which we have bound in the centre.

Incidentally, we have heard rumour on the "grape vine" that a certain company is biting its tongue for not having published a multi-systems quad matrix decoder as simple as ours.

M. A. COWELL—*Editor.*

The December issue, on sale 2nd November, will include a 12 volt 15 watt fluorescent light unit for your car, caravan, garage, shed or anywhere that emergency lighting is needed during power failure. Also included will be a 3-band short wave superhet, some simple practical applications of the LM380N integrated circuit audio amplifier and another series of circuits for the Experimental Workshop. Also next month don't miss the third pair of *P.W.* Datacards and first details of our new project that you can add on to the *P.W.* Q4 quad decoder.

Further details on page 640.

NEWS...

Paris Component Show

MEASURING instruments will be featured in addition to the usual sections on electronic components, materials, equipment and products at the Paris Component Show.

Venue is Exhibition Park, Porte de Versailles and date 1st-6th April 1974.

Mullard back out

MULLARD Ltd. have decided to kill off their Educational Service. The service has acted as a valuable aid for the teaching profession for the last 25 years.

Oxidising agent

ENTHONE Inc. Ebonol C Special is an oxidising agent which increases the strength of the bond in the production of single, double-sided and multi-layer printed circuit boards. The process involves producing many thousands of little cupric oxide needles. The oxide coating is obtained by the immersion of suitably treated copper in a solution of 180gm/l Ebonol C at 104°C.

Liquid adhesive may then be brushed or rolled onto the oxidised surface. After the adhesive has "cured" the imbedded needles of cupric oxide maintain a "key", firmly fixing the adhesive to the copper. The prepared copper foil is then affixed to the plastics base.



We settle down when the holiday season ends...

Packaging for professionals

THE Inter-Nepcon conference at Brighton specialises in broad terms in electronic component packaging and assembly. There is a very strong emphasis on printed circuit techniques and integrated circuit encapsulation.

Although not strictly dealing with electronics techniques, this exhibition has a distinctly practical emphasis because it concerns the making of component assemblies and modules. It is being held at the Metropole Hotel on the sea-front at Brighton, from 16th to 18th October and is organised on an international basis by Kiver Communications Ltd of 149-155 Ewell Road, Surbiton, Surrey. Admission is restricted to those who register as being engaged full-time in electronic circuit packaging and production.

No more please!

WITH the Audio Fair about to open its doors on 22nd October (trade only), and 23rd October to the public, it is interesting to learn that one famous British manufacturer, Armstrong Audio, has had to withdraw because it could not contemplate at present the thought of taking on more orders. It seems that the new 600 series has created so much interest that current orders exceed their present manufacturing capacity.

Rather than spend time and money in exhibiting with the prospect of more orders, Armstrong have decided that they should expand their facilities to cope with the rush.

Multimeter competition

WE wish to apologise to readers for the omission of information in last month's issue on the Digital multimeter competition. Due to the fact that so many readers sent in answers that were the best according to the considered opinion of the judges, our Competitions Department is at present organising a further contest for these readers. We will be publishing the result just as soon as we have it.

Derby modellers get together

DERBY and District Amateur Radio Society (G3ERD, G2DJ) are branching into radio control models. The new club is already under way and held its first meeting in September. Anyone interested should contact Ray Webster, c/o 5 Uplands Avenue, Littleover, Derby.

Ham Exhibition

THE Midland National Amateur Radio and Electronics Exhibition will be held at the Granby Halls, Leicester from 25th to 27th October.

Commercials date

AT the time of going to press, we have heard that the London Broadcasting Company will go on the air on Monday 8th October. There will be a special message from the Minister of Posts and Telecommunications. Frequencies 719kHz, 417m and 97.3MHz.

Slimline digital multimeter

OF professional quality, this unusual device is a hand-held digital multimeter from Hewlett-Packard. At £138 (+VAT) this instrument represents a valuable on-line tool for engineers and technicians. A 3½ digit l.e.d. display uses automatic decimal placement and polarity indication.


The heart of the instrument is a "postage-stamp" size thin film hybrid circuit with analogue and digital processing. It is claimed to measure d.c. voltage from 0.1mV to 500V and a.c. voltages from 3mV to 500V. The resistance range measures from 1 ohm to 10MΩ. The input resistance is stated as 10MΩ.

Cassette library system

WITH the current boom in tape cassette recorders, BASF are to show at the Audio Fair two new machines for chromium dioxide tape and a (quote) "unique library system for cassettes", that can be free standing or fitted to the wall.


BIB's own set-up

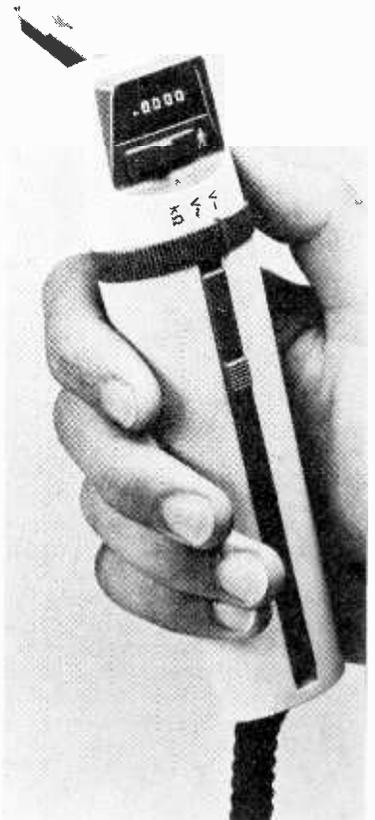MULTICORE Solders Ltd. have set up a subsidiary company, BIB Hi-Fi Accessories Ltd., to look after the interests of growing range of products with the "BIB" trade name, including record and tape cleaning accessories and splicing kits. The board of the new company is selected from the parent company and will continue to operate from P.O. Box 78, Hemel Hempstead, Herts, HP2 7EP.



portable VHF receiver

F. G. RAYER G3OGR

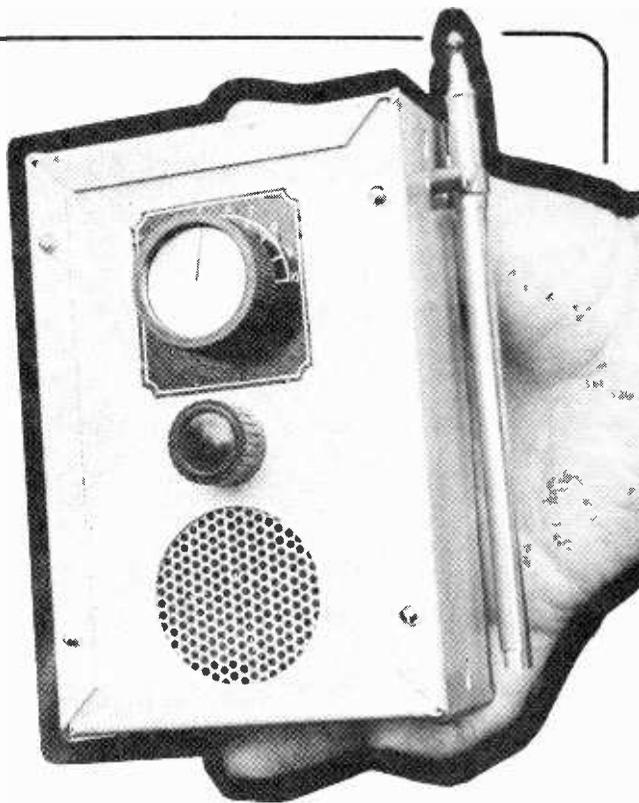

SUPER-REGENERATIVE receivers may use a simple and easily built circuit, and are highly sensitive. There are no gauging or other alignment problems, and frequency coverage is easily modified. A straightforward circuit of this type is thus completely practical, as an alternative to a complicated v.h.f. superhet, or v.h.f. converter used with a short wave receiver.

On the other hand, the disadvantages of the super-regenerative type of circuit should be remembered. One is the lack of selectivity, and another the background hiss which is present when no transmission is tuned in. The lack of selectivity means that a strong, local transmission can prevent reception of a weaker signal on a nearby frequency. The stronger signals are, however, very well received, and any signal which is received at sufficient strength will automatically quiet the background hiss.

A further important point is the extent to which a super-regenerative receiver can cause interference to other receivers. Some radiation of this kind seems unavoidable, but it can be kept within limits by screening the receiver, and using an r.f. stage to help isolate the aerial from the oscillating detector stage. In these circumstances, interference is not caused over a wide area.

Interference is primarily caused on the frequency to which the super-regenerative receiver is tuned, and nearby frequencies. As example, if an un-screened super-regenerative receiver is tuned to 144MHz this is found to cause no interference at all to a normal receiver in the 88-108MHz range, with the equipment side by side. On the other hand, interference would arise with nearby receivers tuned to 144MHz or adjacent frequencies.


This really means that the super-regenerative receiver should be confined to use in those circumstances where other people are not listening on the same or a near-by frequency. In fact, the receiver described has often been used as the only means of reception for 2 metre amateur band contacts, without any complaint. This does not mean, however, that it would be wise to use it for 2 metre reception when there are other 2 metre receivers or converters in use nearby.

Receiver circuit

This is shown in Fig. 1. Though actually constructed for 2 metre reception as a portable, it can be used over the 90MHz to 150MHz range without any change other than re-adjusting the pre-set trimmer TC1. Tr1 is the untuned r.f. stage, with input to the source across the source bias resistor R1. A tuned r.f. stage increases gain, but has to be screened from the detector, and also requires its own means of tuning, unless a small frequency band is adopted. The main purpose of this stage is to reduce radiation caused by coupling an aerial directly to the detector coil L2. The r.f. stage does not provide complete isolation, due to the internal capacitance of Tr1 and other unwanted coupling through leads.

Tr2 is the detector. The operating frequency depends on the coil L2, trimmer TC1, and VC1. There are of course no alignment adjustments at all. With TC1 fully open, VC1 tuned approximately 130-150MHz. Super-regeneration is maintained until TC1 is about two-thirds closed, giving a low frequency limit of about 90MHz. For lower frequencies it would be necessary to increase the number of turns on L2. The upper limit at which the receiver can be made to operate is largely determined by Tr2.

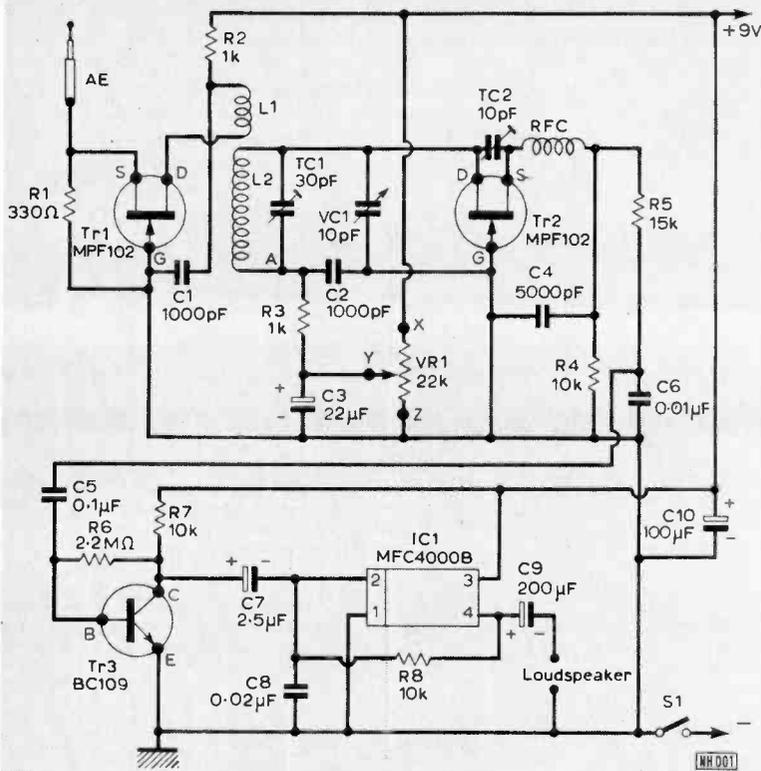Regeneration is controlled by VR1, and it is recommended that the values shown for C4, C6, R4 and R5 are as shown, though VR1 can equally well be 20k Ω or 25k Ω . TC2 from source to drain allows



◀ Fig. 1: Complete circuit of the portable v.h.f. receiver.

adjustment of regeneration, and was found of advantage with various transistors employed for Tr2.

A detector of this type is usually considered to have a sensitivity of about $0.5\mu\text{V}$, which offers a useful range with a simple aerial.

Tr3 is an audio amplifier, followed by the i.c., which contains six transistors in a driver-push-pull arrangement. This gives reasonable loudspeaker volume from the internal miniature speaker. The receiver is free from troublesome hand capacity effects, if constructed as shown.

Circuit board


This is plain Veroboard, 0.15in. matrix, and is approximately $2\frac{5}{8} \times 3\frac{1}{4}\text{in.}$, see Fig. 2. The detector stage is assembled in close proximity to VC1.

L2 is self-supporting, and is wound with 18 or 16 s.w.g. wire, with an outside diameter of $\frac{1}{2}\text{in.}$ The coil is approximately $\frac{3}{4}\text{in.}$ long, and its ends are shaped so that they may be soldered to the fixed plates tag of VC1, and to C2. C2 has the shortest possible leads each end. A stout wire supports TC1 just clear of the plates of VC1, and the outer tag A of TC1 is bent down and soldered to L2 as shown. L1 is 2 turns of insulated wire near L2, and is soldered to two Veropins.

Coverage can be modified to some extent by stretching L2, or by compressing it so that the turns are closer together. For the coverage mentioned, four turns are used. The coil should be at least $\frac{1}{2}\text{in.}$ from the metal case.

A small 3-lead holder is fitted for Tr2, and is of

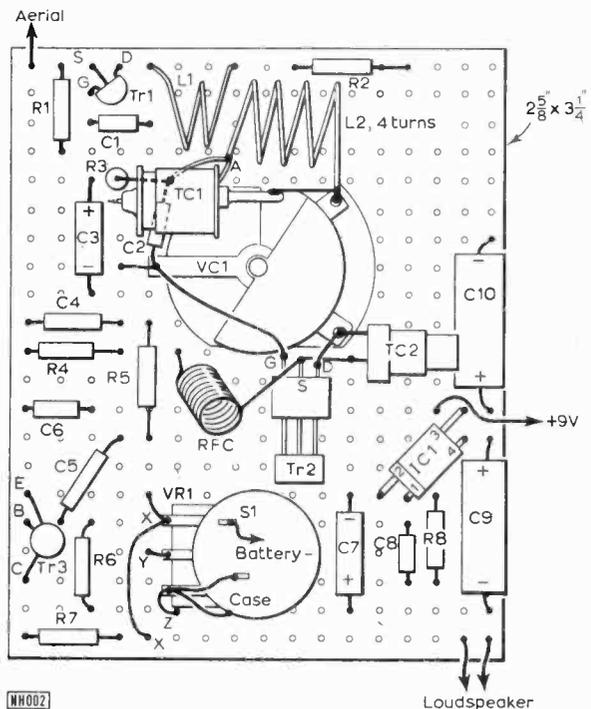▼ Fig. 2: Component layout on the circuit board.



speaker is fixed with more adhesive. Though the speaker is 40Ω, a 75 or 80Ω unit can be fitted with almost similar results, though the best impedance for the i.c. is in the 15 to 40Ω range.

Washers are put on the bush of VC1 to space the insulated board from the metal panel, and these are then secured together with the capacitor nut. Check that all joints etc. are clear of the metal.

Final assembly

The receiver should be tested and adjusted before fitting it in its case. The box is assembled with 4BA bolts through the holes punched in its flanges, and the panel is fixed with 6BA bolts or self-tapping screws.

A 34in. telescopic aerial is used, bolted to the side of the box near R1, but insulated from the metal. This is done by using insulated washers and bushes, or insulated washers and pieces of sleeving on the bolts. One bolt carries a tag, for the aerial lead mentioned.

The battery rests in the bottom of the box, and folded card can be put round it and between battery and speaker. There must be no contact between the battery clips and metal case.

For 2 metre reception, a $\frac{1}{4}$ -wave aerial is around 19 to 20 inches. But it was found that the exact length of the aerial was not important, there being no noticeable change in volume when changing this

★ components list

Resistors

R1	330Ω	R5	15kΩ
R2	1kΩ	R6	2.2MΩ
R3	1kΩ	R7	10kΩ
R4	10kΩ	R8	10kΩ

All 5% $\frac{1}{4}$ W.

VR1 22kΩ linear pot with switch

Capacitors

C1	1000pF disc or tubular ceramic
C2	1000pF disc or tubular ceramic
C3	22μF 10V
C4	5000pF
C5	0.1μF
C6	0.01μF
C7	2.5μF 6V electrolytic
C8	0.02μF
C9	200μF 6.4V electrolytic
C10	100μF 10V electrolytic
VC1	Jackson C804, 10pF
TC1	Beehive trimmer, 30pF
TC2	Jackson 'Tetter' 10pF trimmer

Semiconductors

Tr1	MPF102
Tr2	MPF102
Tr3	BC109
IC	MFC4000B

Miscellaneous

Speaker 2 $\frac{1}{2}$ in. or similar, 15 to 40Ω; plain Vero-board 2 $\frac{1}{2}$ x 3 $\frac{1}{2}$ in., 0.15in. matrix, aluminium panel 6 x 4in. and 6 x 4 x 2in., universal chassis box (Home Radio), telescopic aerial, small knob, large knob, battery clips, transistor holder, insulated washers and bolts, etc.

from about 20in. to 30in. or so. Some strong transmissions were received with the aerial completely closed.

In many cases it is better to have the aerial sloping or near horizontal, but with a hand-held receiver of this sort it is easy to move around to find the best position for the aerial, if needed.

Indoors, reception is modified by the proximity of objects such as metal windows. On a few occasions an outdoor dipole, with a co-axial feeder, has been connected, and this naturally increased range.

Adjustment

Both TC1 and TC2 may be fully unscrewed, for about 130-150MHz. (Exact coverage naturally depends on L1 and other factors, but is likely to be near this.)

When VR1 is rotated to switch on, a point should be reached where a loud hiss commences. This is the point where super-regeneration, upon which sensitivity depends, has commenced. No reception is possible if this is not obtained. Should super-regeneration be absent, TC2 may need screwing down *slightly*. A setting should be found where super-regeneration continues over the whole band tuned by VC1, with only a little re-adjustment of VR1.


When a signal is tuned in, this hiss should cease. Strong signals will produce this effect with most settings of VR1 which permit super-regeneration; but with weak signals VR1 may have to be backed off slightly.

L1 should be quite near L2, but if coupling is very tight this may prevent regeneration in some circumstances. It is possible to boost volume by using more turns on L1 so that it is broadly self-resonant at the wanted frequency. However, this adjustment is fairly touchy. L1 may be unsoldered from the pins, and a new winding may be fitted, with a minimum of disturbance.

If all connections are short and direct, and no fault is present, the absence of super-regeneration can only arise from Tr2 being inefficient at the frequency wanted. Of several quite inexpensive transistors tried here, one failed to operate at any frequency higher than about 100MHz, while another continued to provide regeneration at over 200MHz. As Tr1 and Tr2 are of the same type, the transistor found to give best regeneration may be used for Tr2. Its leads need not be cut down. This test can be made with the aerial temporarily taken to the drain pin of L1.

It is in order to use a 4.5pF or 5pF capacitor at VC1, if a narrower band is required, or to fit a 15pF capacitor for a larger band. The overall drain of the receiver is about 10-20mA, depending on volume.

The amount of activity on these frequencies varies very considerably in different areas, being least in some isolated parts of the country. Amateur activity on the 2 metre band is most likely at certain times at weekends. It may be considerable during v.h.f. contests, while at other times no stations may be operating. Any amateur in the 2 metre band (144-146MHz) will provide a tuning calibration point which can be noted as a guide for future reference when listening. ■

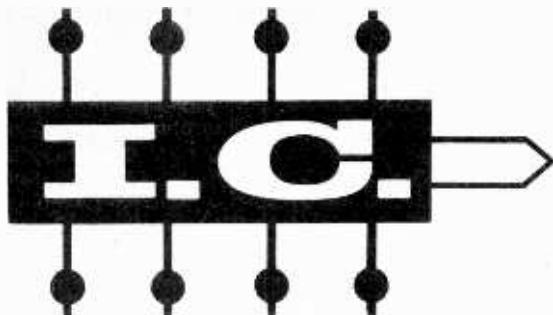

OF THE MONTH

L.A.J. IRELAND

Number 42

National LM101 for Audio Signal Generators

A simple requirement whose realisation in practice can be rather difficult is the tunable audio oscillator with an accurate sine waveform. At frequencies below 20kHz the use of inductive tuned circuits is not practical and the most commonly used circuit is the Wien bridge using RC circuits to determine the time constant of the oscillator feedback loop. The impedance of such a circuit is, of course, frequency dependent; the loop gain therefore also tends to be frequency dependent, with the result that the circuit can produce some variation in waveform and amplitude as the operating frequency is varied.


Any departure from a true sine waveform, such as the square wave produced by an oscillator with excessive loop gain, contains harmonics or overtones of the fundamental frequency and is therefore unsuitable for many applications such as the determination of the frequency response of an audio system. Various improvements on the basic Wien bridge circuit have been introduced to overcome these defects, such as the incorporation of an AGC loop with a thermistor to regulate gain.

Op Amp + Comparator

This month, however, a completely different approach is outlined, one first introduced by engineers of the National Semiconductor Corp. and employing two integrated circuits. One of these is an operational amplifier, the other a voltage comparator. The standard application of a voltage comparator unit is as a sensing element, operating a relay or switching the state of a logic circuit on the application of a low level input signal.

Operation

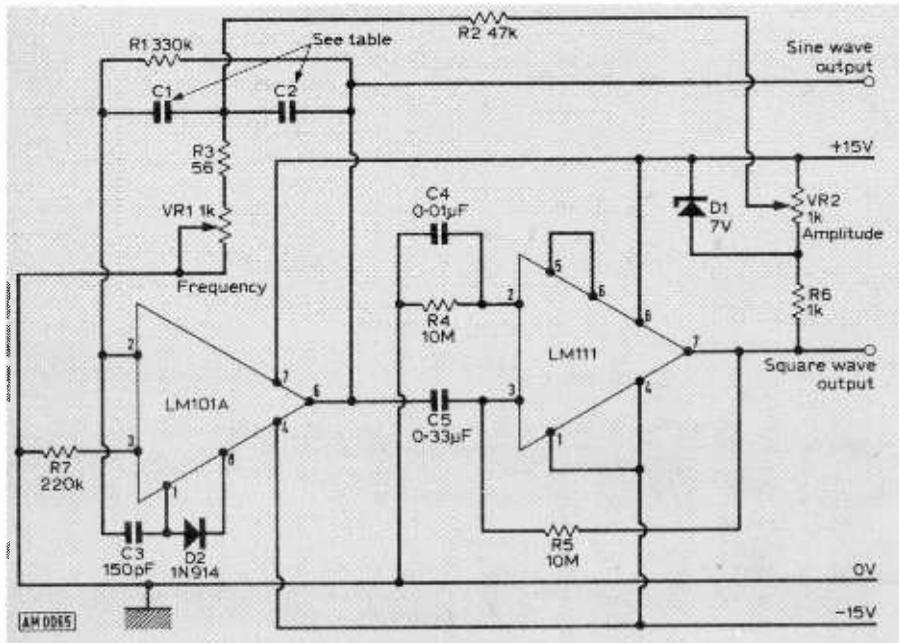In the oscillator circuit to be described, it is accepted that the output of a comparator will alternate between extreme values irrespective of the waveform of the input signal. If, then, the input signal has a fixed period, the output of the comparator will be a square wave with that period and a fixed amplitude. With effective filtering to remove



C1 and C2	Frequency range
0.47µF	18Hz - 80Hz
0.1µF	80Hz - 380Hz
0.022µF	380Hz - 1.7kHz
0.0047µF	1.7kHz - 8kHz
0.002µF	4.4kHz - 20kHz

Practical circuit for an audio signal generator based on the LM101A/LM111 combination. Capacitors C1/C2 may be mounted on a range switch and should be of close tolerance and best quality. The frequency control VR1 should be large, physically, and again, of highest quality, if accurate calibration is to be achieved.

harmonics, a sine wave of fixed amplitude will remain. The filter in question is in this case an active filter incorporating an operational amplifier integrated circuit, with its centre frequency determined by an RC network. In turn, the output of the filter provides the input signal for the voltage comparator, thereby closing the oscillator feedback loop. It is clear that two separate waveforms are available from the oscillator, both stabilised in amplitude and locked together in frequency and phase; a square wave at the output of the voltage comparator, and a sine wave at the output of the operational amplifier.

Simplified Tuning

There is the further advantage that the frequency is set by a single variable resistor, whereas the Wien oscillator requires matched ganged tuning elements. The audio range from 18Hz to 20kHz is covered in five bands with band switching achieved by changing the capacitive elements in the tuned filter. The limitation on the frequency range covered with any given pair of capacitors is applied by the rise in harmonic distortion to some 2% at the maximum value of R3. Further, the principle is not applicable to the construction of RF signal generators since a sufficiently high Q is not available without the use of inductors.

Construction

In construction of these oscillators, however, some care is necessary to follow good high frequency design practice, since the individual IC's are wide

bandwidth devices. Careless construction could therefore lead to an oscillator with RF instability, and plagued by parasitic oscillations. Both power supply lines, therefore, should be decoupled by 0.1µF disc ceramic capacitors. Further, the output of the comparator should be shielded from the op amp input, to ensure that the only feedback occurs via the intended filtered loop.


Radio Control

For those interested in radio control techniques, it can be seen that a simple modification to the circuit can produce a frequency-operated switch. If the operational amplifier and associated tuned circuit are examined alone, it is clear that an output signal is produced only if the input applied via R2 contains a component at the resonant frequency. That output signal can then be detected by a conventional diode, and the resultant DC level applied to the voltage comparator, thereby operating a relay. Such a system therefore would function on the presence or otherwise of an appropriate AF modulation on a radio control signal.

The National Semiconductors devices are available from: ITT Electronic Services, Edinburgh Way, Harlow, Essex.

The LM101A and LM111 are manufactured to military specifications and therefore somewhat expensive. The 'civilian' equivalents LM301A and LM311 are very much cheaper and should perform quite adequately in this application (Technical Editor).

Pw TECHNICAL CROSS PUZZLE No. 1

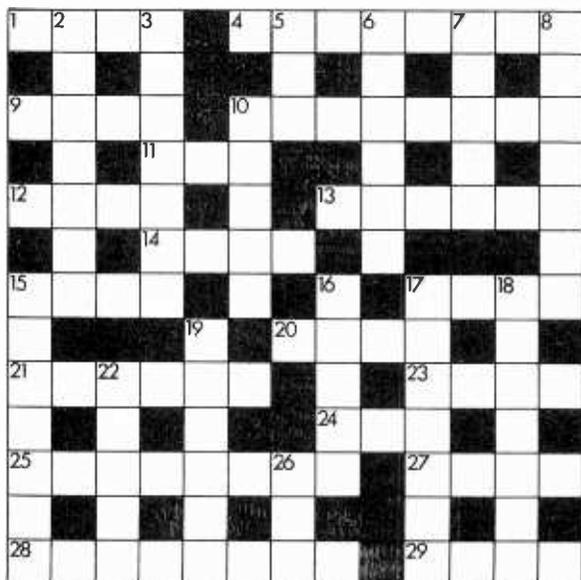

ACROSS


- 1 Sort of band which has been infiltrated? (4)
- 4 Sound representation in broadcasting? (8)
- 9 New Zealander involved in ski wireless? (4)
- 10 Such rule of thumb for a conductor? (4-4)
- 11 The radio's epoch-making centre (3)
- 12 Push with it for amplification (4)
- 13 A feeler for a better receiver? (6)
- 14 Steady Eddie changed colour inside! (4)
- 15 Resistance units of German origin (4)
- 17 Condensed diagrams for fruit production (4)
- 20 No charge for such oscillation (4)
- 21 Overtakes—with or without a car! (6)
- 23 Phone for this type of modulator? (4)
- 24 Torn away from electricity by a dog? (3)
- 25 It returns part of your output! (8)
- 27 Girl in a Fair Isle pullover (4)
- 28 Record needs waxing with this valve? (4-4)
- 29 Natural products of 10 Down (4)

DOWN

- 2 It has an angle in radio communication (7)
- 3 All-rounders in coil protection (7)
- 5 Yes, relay equipment is connected (3)
- 6 Invitation to part of a French meal? (6)
- 7 Took a pitch from the animal within? (5)
- 8 Expression of effective forcefulness (7)
- 10 A piece of cake in ionization? (5)
- 15 Too much connection with 25 Across? (7)
- 16 A circuit may do so, of course (5)
- 17 Good reception for a type like Rod? (7)
- 18 Crew formation for co-ordinating adjustment? (7)
- 19 Revolvers instead of maps for world travellers (6)
- 22 Aches so about a mere game? (5)
- 26 Network of transatlantic origin (1, 1, 1)

**FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH**

BETTER AERIALS

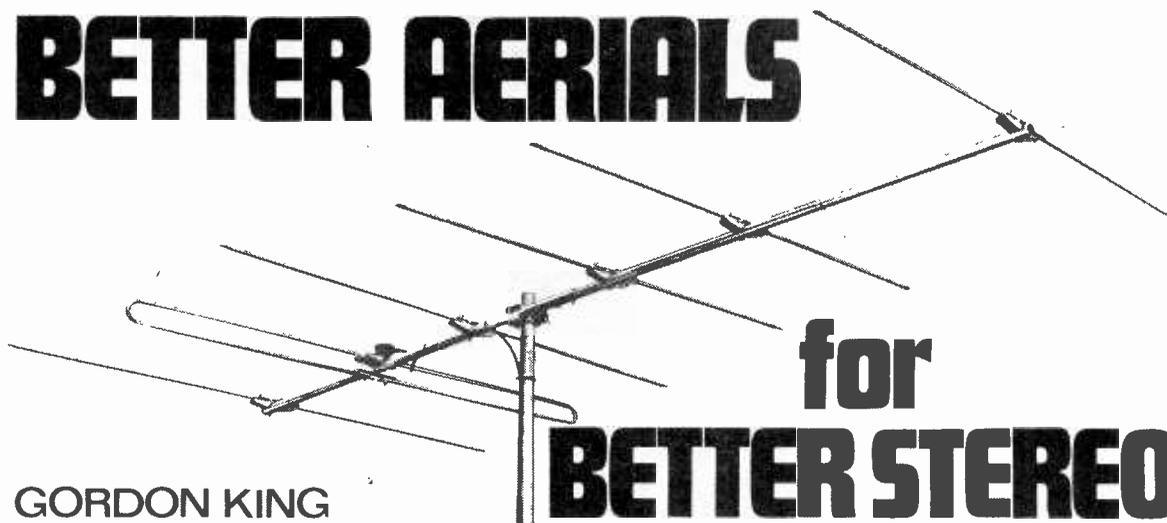

for BETTER STEREO

GORDON KING

PART 3

AERIAL DESIGN

Accurate design of good FM aerials of multi-element composition is complex, and since very good FM aerials of all types are readily available at quite reasonable prices it hardly pays the enthusiast these days to tailor his own design. Discarded television aerials as they stand are useless for FM since their tuned frequency is all wrong. However, it is sometimes possible to make use of some of the components of such aerials in the construction of an FM aerial. The elements and cross-boom of a Band I aerial can be cut down to tune Band II, and the insulator at the dipole and other fittings can often be used to advantage. There is no 'standard' design; the absolute dimensions of the elements and their spacings determine the overall bandwidth, the nature of the polar diagram and the correct impedance matching to the feeder over the bandwidth.

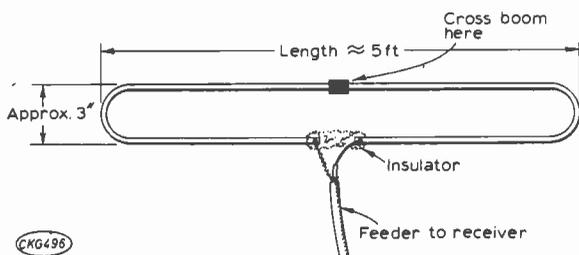


Fig. 7: General construction of a folded dipole which can be used by itself or form the basis of a multi-element aerial.

A simple dipole has a centre impedance of about 72 ohms and thus closely matches 72 ohm coaxial feeder, this being necessary for maximum energy transfer from the aerial to the receiver or tuner. However, when the simple dipole is advanced into a multi-element array by the addition of parasitic elements the impedance at the centre of the dipole falls from the aerial to the receiver or tuner. However, when the simple dipole is advanced into a multi-element array by the addition of parasitic elements the impedance at the centre of the dipole falls and some artifice has to be employed to increase the coupling impedance to a value matching the feeder.

One such artifice is 'folding' the dipole, as shown in Fig. 7. This quadruples the impedance at the

feeder connecting point, increasing it to about 300 ohms in the simple case. However, when a reflector and directors are added the centre impedance of a simple dipole falls to about 24 ohms, so by folding the dipole as shown in Fig. 7 the coupling impedance is restored to about 72 ohms.

HOME-MADE AERIAL

Fig. 8 gives the dimensions for a home-made four-element array which will respond pretty well over the whole of Band II. The dipole can be folded as shown in Fig. 7 and 72 ohm coaxial feeder should be used. Notice that the reflector is slightly longer than the dipole and that the directors are shorter. Additional directors can be used, the third then being 4ft. 3in. and the fourth 4ft. with 1ft. 7in. spacing.

It should be noted that the element dimensions correspond to length plus diameter, so if they are

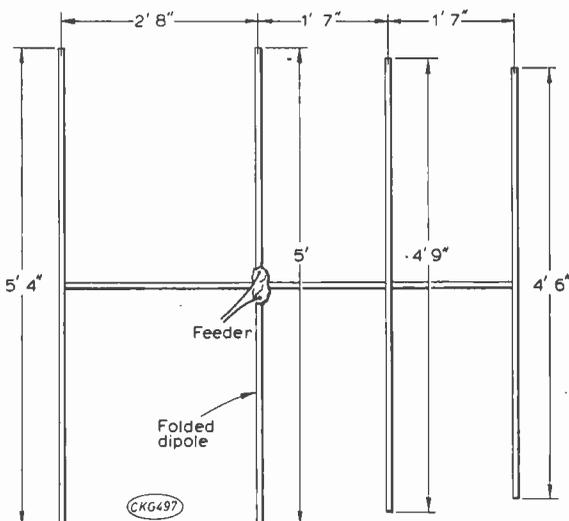





Fig. 8: Dimensions for a four element beam using a folded dipole as shown in Fig. 7.

look!

electronics really mastered

... practical
... visual
... exciting!

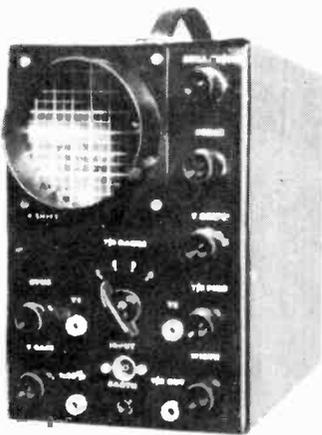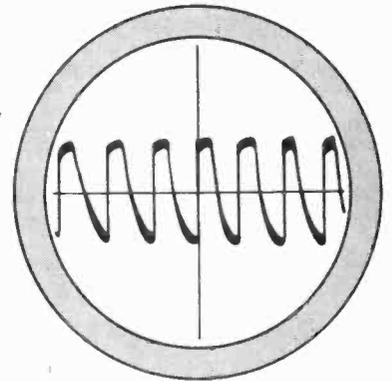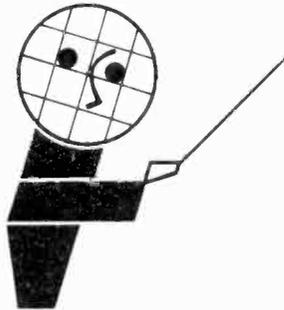no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

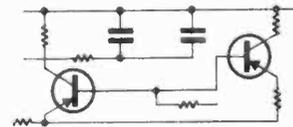2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WLI13

special free gift also to all our students

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

PLEASE ADD 10% VAT

RESISTORS

W Iskra high stability carbon film—very low noise—capless construction.
W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.
W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	Price 1-99	100+
1/4	5%	4.7 Ω - 2 MΩ	E24	1p	0.8p
1/4	10%	3.3 Ω - 10 MΩ	E12	1p	0.8p
1/2	5%	1 Ω - 1 MΩ	E24	3.5p	3p
1/2	10%	1 Ω - 3.9 Ω	E12	1p	0.8p
1	5%	4.7 Ω - 1 MΩ	E12	1p	0.8p
4	10%	1 Ω - 10 Ω	E12	6p	5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7 Ω to 1 MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5k Ω to 2 MΩ, log or linear (log 1/2V, lin 1/2V).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 Ω and decades to 5 MΩ. Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107	15p	AF126	20p	BF115	25p	OC42	12p	SN3707	12p
AC126	12p	AF139	32p	BF173	20p	OC44	12p	2N3708	10p
AC127	15p	AF178	32p	BF177	28p	OC45	12p	2N3709	11p
AC128	15p	AF180	40p	BF178	32p	OC70	12p	2N3710	11p
AC131	12p	AF181	40p	BF179	32p	OC71	12p	2N3711	11p
AC132	12p	BC107	12p	BF180	32p	OC72	12p	2N3819	32p
AC176	15p	BC108	12p	BF181	32p	OC81	12p	2N4062	12p
AC187	22p	BC109	12p	BF194	14p	OC82D	12p	2N4286	20p
AC188	22p	BC147	12p	BF195	14p	2N2646	60p	2N4289	20p
AD140	50p	BC148	12p	BF197	15p	2N2904	20p	40360	35p
AD149	45p	BC149	12p	BF200	32p	2N2926	10p	40361	35p
AD161	33p	BC157	14p	BFY50	20p	2N3054	58p	40362	40p
AD162	36p	BC158	14p	BFY51	20p	2N3055	60p	40408	40p
AF114	20p	BC159	14p	BFY52	20p	2N3702	13p	ZTX108	15p
AF115	20p	BC187	22p	BUY105	225p	2N3703	12p	ZTX300	15p
AF116	20p	BD131	75p	OC26	45p	2N3704	13p	ZTX302	20p
AF117	20p	BD132	75p	OC28	50p	2N3705	12p	ZTX500	15p
AF118	38p	BD133	75p	OC35	50p	2N3706	11p	ZXT503	20p

ZENER DIODES

400mW 5% 3.3V to 30V, 12p. | WIRE WOUND POTS. 3W, 10, 25,
50 Ω and decades to 100k Ω, 35p.

DIODES

RECTIFIER	1250V	1A	12p	SIGNAL	7p
BZY10	800V	6A	25p	OA85	5p
BZY13	200V	6A	20p	OA90	5p
1N4001	50V	1A	7p	OA91	5p
1N4004	400V	1A	8p	OA202	7p
1N4007	1000V	1A	10p	1N4148	5p
				BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in, 25p; 12in x 2 1/2in, 10p; 9in x 2in, 7p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10k, 25k, 100k log. or lin. 40p.
DUAL GANG, 10k + 10k etc. log. or lin. 60p.
KNOB FOR ABOVE, 12p.
FRONT PANEL, 65p.
1/2 Gauge panel 12in x 4in with slots cut for use
with slider pots. Grey or matt black finish com-
plete with fixings for 4 pots.

THERMISTORS

VA10555 15p
VA10665 15p
VA1077 15p
R53 £1.35

THYRISTORS

2N5060 50V 0.8A 30p
2N5064 200V 0.8A 47p
106F 50V 4A 40p
106D 400V 4A 55p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2 1/2p, 0.0068μF, 0.01μF,
0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF,
7 1/2p, 0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 3 1/2p, 0.15μF,
4 1/2p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7 1/2p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF,
3 1/2p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8 1/2p, 0.68μF, 11p, 1.0μF,
13p, 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF,
2 1/2p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS

(μF/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40,
15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3,
68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/6.3, 220/16, 330/4, 6p, 47/63,
100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4, 10p,
470/10, 680/6.3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16, 1500/6.3, 13p,
470/40, 330/25, 1000/16, 1500/10, 2200/6.3, 18p, 330/63, 680/40, 1000/25, 1500/16,
2200/10, 680/6.3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF 35V	2.2μF 35V	22μF 16V	12p
0.22μF 35V	4.7μF 35V	33μF 10V	
0.47μF 35V	6.8μF 25V	47μF 6.3V	
1.0μF 35V	10μF 25V	100μF 3V	

VEROBORD

2 1/2 x 3 1/2	0.1	15
2 1/2 x 5	22p	16p
3 1/2 x 3 1/2	24p	24p
3 1/2 x 5	24p	24p
17 x 2 1/2	27p	27p
17 x 3 1/2	75p	75p
17 x 5 (plain)	100p	82p
17 x 3 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	42p
2 1/2 x 5 (plain)	—	12p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	43p	43p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Screen screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable, 22p/metre.

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF 64V 74p	2500μF 64V 80p	4500μF 16V 50p
2500μF 40V 74p	2800μF 100V £2.60	4500μF 25V £1.18
2500μF 50V 58p	3200μF 16V 50p	5000μF 50V £1.60

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p	0.047μF 13p	0.22μF 20p
0.022μF 12p	0.1μF 13p	0.47μF 22p

POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values, 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas
or smoke into an electrical signal. The sensor decreases its electrical resistance when
it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide,
methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or
smoke. This decrease is usually large enough to be utilized without amplification.
Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but
excluding case. Mains operated detector £5.20, 12 or 24V battery operated audible
alarm £7.30. As above for PP9 battery, £6.40.


PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to
dry, and immerse the board in the etchant. On removal the circuit remains in high
relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7400	18	16	14	13	7450	18	16	14	74121	43	40	38	36
7401	18	16	14	13	7451	18	16	14	74141	100	95	90	85
7402	18	16	14	13	7453	18	16	14	74145	150	140	135	130
7403	18	16	14	13	7454	18	16	14	74150	330	280	250	220
7404	20	18	16	14	7460	18	16	14	74151	110	100	95	89
7405	20	18	16	14	7470	30	28	25	74153	120	110	105	95
7406	50	45	40	35	7472	30	28	27	74154	200	180	170	160
7407	56	50	44	38	7473	40	38	36	74155	150	120	100	86
7408	36	30	27	23	7474	40	36	32	74156	130	120	100	96
7409	36	30	27	23	7475	55	52	50	74180	155	136	112	105
7410	18	16	14	13	7476	40	36	32	74190	195	190	185	180
7411	23	21	20	18	7480	100	95	90	74191	195	190	185	180
7412	36	30	27	23	7481	125	115	110	74192	200	190	180	164
7413	34	28	26	22	7482	100	96	90	74193	200	180	170	150
7414	45	43	39	34	7483	100	97	95	74196	200	190	180	170
7420	18	16	14	13	7484	120	115	110	74197	200	195	180	170
7421	36	30	27	23	7485	250	245	240					
7426	32	29	23	20	7486	45	42	37					
7430	20	18	16	14	7487	45	42	37					
7432	40	36	32	28	7490	75	67	60					
7440	20	18	16	14	7491A	100	92	85					
7441	80	75	70	65	7492	75	65	60	709	14 pin DIL			40p
7442	80	75	70	65	7493	75	68	60	741	8 pin DIL			40p
7443	125	120	115	115	7494	95	90	85	723	14 pin DIL			95p
7447	175	165	150	120	7495	105	100	95	747	14 pin DIL			85p
					7496								

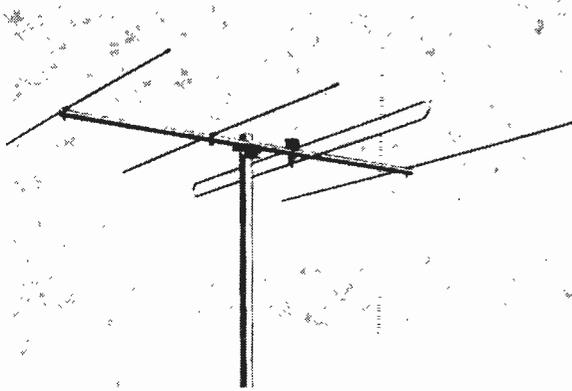

A commercial version of a four element array for FM (J-Beam Aerials Ltd.).

composed of, say, 1/2in. rod the actual lengths are all 1/2in. less than given on the diagram. The spacings are taken from the centre axis of each rod or element.

INPUT MATCHING

Most British receivers and tuners destined for the British market have aerial inputs suitable for 72 ohm coaxial cable (the British 'standard'). Some imported receivers and tuners have inputs for both 72 ohms coaxial (which is unbalanced) and 240/300 ohms balanced twin feeder, used in European areas and American countries. There are times, however, when the receiver or tuner has only a 240/300 ohm balanced input. By connecting the British standard coaxial cable direct to such an input results in a mismatch and hence loss of signal energy transfer.

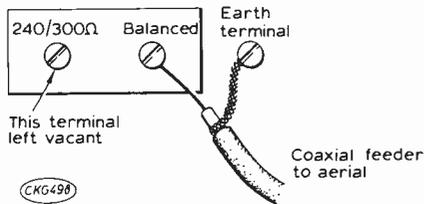


Fig. 9: A useful 'dodge' to permit feeding a balanced input with unbalanced coaxial cable.

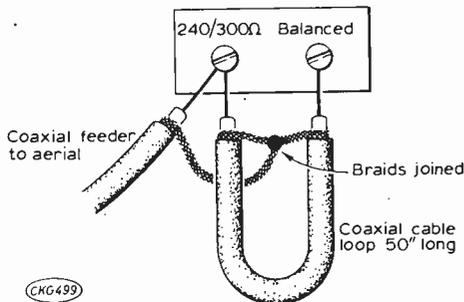


Fig. 10: An alternative method of feeding unbalanced coaxial cable to a balanced input circuit.

In quite a few cases like this it is possible to achieve matching to coaxial cable by connecting the inner conductor to one of the 240/300 ohm sockets or terminals and the braid to an adjacent earth terminal or to the metal part of the chassis (**Important: this must never be done if the receiver is of the 'a.c./d.c.' type which uses no mains transformer for isolation; if in doubt consult a qualified dealer or technician**), as shown in Fig. 9.

This matching results from the centre-tapped winding on the primary of the aerial input transformer, giving a 4:1 impedance transformation since the turns ratio is 2:1.


Should the 300 ohm balanced aerial input circuit of the receiver or tuner be unsuitable for matching this way, then an external impedance matching transformer must be used for the best results. A simple coaxial cable transformer arrangement is shown in Fig. 10. It is also possible to obtain commercially small low-loss balun transformers using ferrite cores.



A multi-element FM aerial can be an awkward brute! Erection of these arrays is best left to the experts (R. Smith Aerials, Luton).

INPUT OVERLOAD

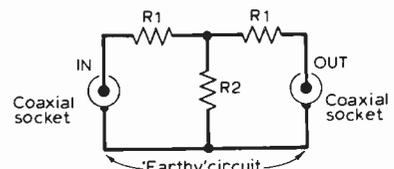When a tuner or receiver is used very close to a powerful station the input stages may be unable to accommodate the multiplicity of strong signals




$$R1 = Z \frac{A-1}{A+1} \quad R2 = Z \frac{2A}{(A+1)(A-1)}$$

$Z = \text{Receiver/feeder input impedance}$
 $A = \text{voltage reduction ratio}$

Fig. 11: Overloading of input circuits can cause all kinds of strange noises on FM. Suitable signal attenuators can be constructed using the above formulae.

without overloading. This is manifested by spurious signals appearing at incorrect tuning points over the scale, and intermodulation may occur between the various programmes.

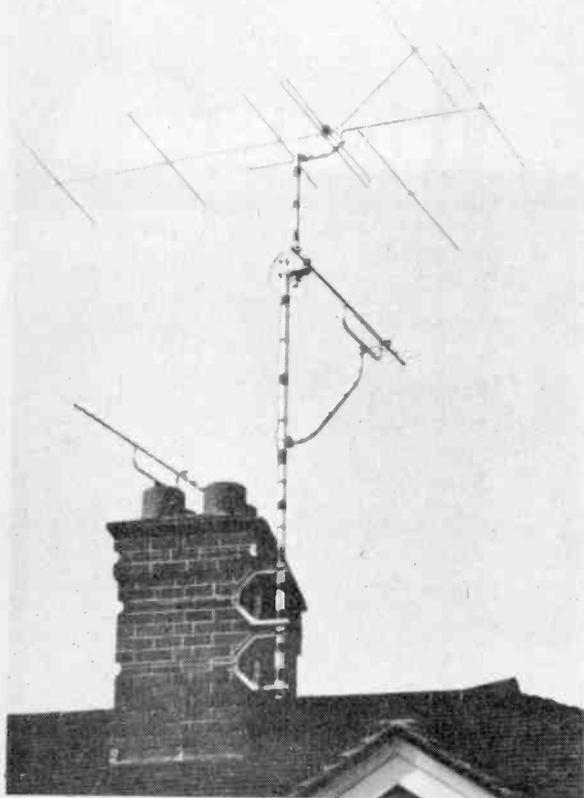This trouble can also incite a 'warbling' type of interference on stereo. The solution to the problem is to reduce the level (attenuate) the signal from the aerial to the receiver or tuner. A less elaborate indoor aerial may reduce the signal input, but in some cases this could be undesirable, notably when



The lower mast carries a fixed TV array plus a Stolle rotator for the Arrow 7 FM beam above (R. Smith Aerials, Luton).

a directional aerial is used to reduce distortion due to reflected signals (Fig. 6).

Plug-in coaxial attenuators in a range of values are obtainable from dealers, and there is a similar type available with adjustable attenuation values. Alternatively, it is not a difficult matter to make one's own attenuators for unbalanced circuits, as shown in Fig. 11. The resistors, which should be of non-inductive type (i.e., cracked carbon), can be mounted in a discarded tobacco tin, using the tin itself as the 'earthy' circuit.

Overloading can also occur under certain conditions at distances of twenty or more miles from a station at elevated sites with open aspects towards the station. It is likely that more overloading problems will occur when the FM commercial stations go on the air, for these may not be co-sited with the regular BBC stations and thus could introduce heavy signal fields in areas where only moderate signals are present from the BBC stations.

In some cases like this it may be necessary to use frequency-selection attenuation adjusted only to the frequency of the powerful offending station, but this is another story which will be examined in greater detail when the time comes. ■

TELEVISION

NOVEMBER ISSUE

TEST SIGNAL EXTRACTOR UNIT

Quite a few test signals are present on the lines transmitted during the field flyback period. These sometimes include experimental Ceefax (BBC) or Oracle (IBA) data transmissions. The lines carrying these test or data signals should not normally be seen since they should appear above the top of the picture. They can be observed however by reducing the setting of the height control. An oscilloscope can be used to display such signals if it has facilities for strobing out particular lines. The test signals themselves are not particularly helpful for general servicing but the ability to strobe out lines can be invaluable for colour servicing since this makes the standard colour bar pattern present at the top of Test Card F available for signal tracing in PAL decoders. The unit featured next month can be used as an economical add-on unit for scopes without strobing facilities and in addition provides good, clean line and field sync pulse outputs.

TACKLING STICKY FAULTS

Most fault-finding is reasonably straightforward, a matter of clear symptoms and obvious causes. Every engineer has his ration of faults that seem to defy analysis however. There are nevertheless some common mechanisms by which these arise and a number of ways in which a goodly proportion of them can be cleared up without the need to spend hours delving into the "unknown". Next month Vivian Capel describes various steps which can provide a short-cut to solving the more obscure types of fault.

PLUS ALL THE REGULAR FEATURES

TO
(Name of Newsagent)


Please reserve/deliver the NOVEMBER Issue of TELEVISION (20p), on sale OCTOBER 22 and continue every month until further notice

NAME

ADDRESS

AMTRON kits for the Audio Enthusiast

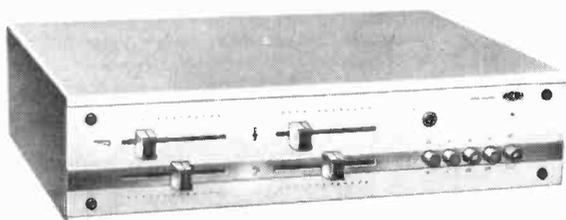These kits have been especially selected from the vast range of 200 AMTRON electronic kits. Each unit comes in an attractive blister pack which contains all components together with full instructions plus solder





HI-FI STEREO AMPLIFIER 20+20W. UK185

The outstanding advantage of the UK185 is its compact size, which simplifies the assembly, thus comparing well with the best stereo amplifiers.

HI-FI STEREO AMPLIFIER 50+50W. UK192

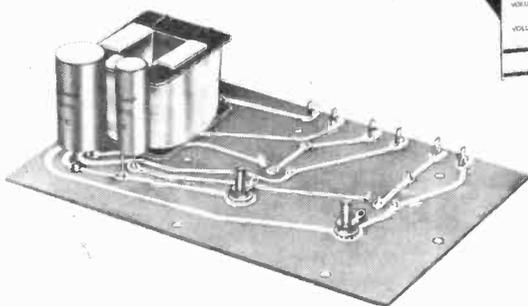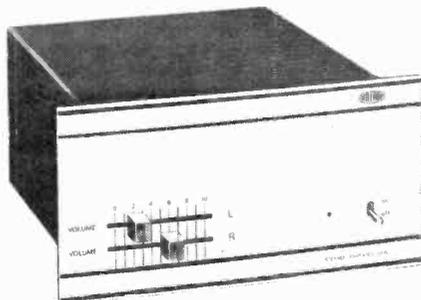The UK192 circuit consists of two UK190 circuits, the 50W output power per channel being obtained by a push-pull arrangement of BD130 transistors driven by a complementary pair (BC141-161)



THREE-WAY CROSS-OVER FILTER 6db/OCTAVE. UK805


The UK805 cross-over filter developed by AMTRON has the function of separating the frequencies and conveying them to the proper speaker with a 6db roll off



THE BIG NAME IN ELECTRONIC KITS

AMTRON UK, 4 & 7 CASTLE STREET, HASTINGS, SUSSEX TN34 3DY TEL: HASTINGS 2875

London's Lighthouse

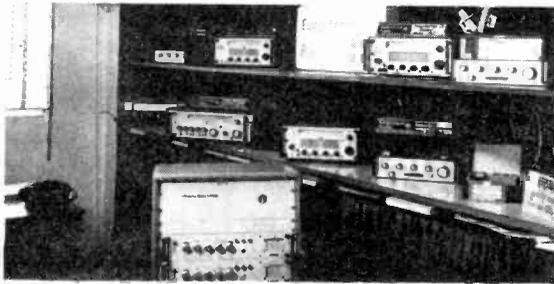

see the



showroom
at

IMHOFS

Here at Imhofs we have a whole showroom entirely devoted to the Eddystone range of communication receivers. From the remarkable little EC10 Mk II, the elegance of the Series 1000 range to the sophistication of the 830/7. Pop in and see us - or write for details to:-

112-116 New Oxford Street
London WC1A 1HJ
Telephone 01-636 7878

R83

Just hold this while I switch on.



Sorry about that, Roger.

BAND-AID* Washproof Plasters.

© Johnson & Johnson LTD

* TRADE MARK

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

C.W.O. Please. P. & P., please add 10p to orders under £2
MAIL ORDER. CALLERS SATURDAYS ONLY

PLEASE ADD 10% TO FINAL TOTAL

TRANSISTORS		DIODES		LINEAR IC's	
AC125	12p	BC109	9p	OA90	5p
AC126	12p	BC147	12p	OA91	5p
AC127	12p	BC148	12p	OA200	8p
AC128	12p	BC149	12p	OA202	8p
AC187	12p	BD131	49p	IN914	5p
AC188	12p	BD132	49p	IN4001	6p
AD161	30p	BF194	15p	IN4002	6p
AD162	30p	BF195	15p	IN4003	7p
AF114	12p	BFY50	22p	IN4004	7p
AF115	12p	BFY51	22p	IN4005	7p
AF116	12p	OC26	40p	IN4006	8p
AF117	12p	OC28	40p	IN4007	8p
AF118	12p	OC35	40p	IN4148	5p
BC107	9p	OC42	10p	WO1	30p
BC108	9p	OC44	10p	WO6	34p

VEROBOARD		JACK PLUGS (chrome) & SOCKETS		DIN PLUGS, SOCKETS, COUPLERS		SWITCHES		COAXIAL		CAR AERIALS	
2 1/2 x 3 1/2 in	0-1	Standard Screened	12p	Standard	12p	Toggle SP/ST	18p	Plugs 10p	Sockets 8p	3-stage, Spring up, lock down type with key 50"	
2 1/2 x 5 in	24p	Stereo Screened	30p	Stereo	15p	DP/DT	22p	Slide DP IA		extended. Price £1.25.	
3 1/2 x 3 1/2 in	18p	2.5 mm Screened	8p	2.5 mm	7p	ROTARY Water	20p	1-12 way			
3 1/2 x 5 in	26p	3.5 mm Screened	10p	3.5 mm	7p						
3 1/2 x 5 in	30p										
2 1/2 x 17 in	80p										
3 1/2 x 17 in	110p										
5 x 17 in	140p										
2 1/2 x 17 in (plain)	45p										
3 1/2 x 17 in (plain)	63p										
5 x 17 in (plain)	89p										
Pkt. 50 pins	20p										
Spot face cutter	42p										
Pin insertion tool	52p										

TGS GAS SENSOR HEAD (ELECTRONIC NOSE) for detection of combustible gases with a proven record for a highly reliable Fire Detection. TGS Head can detect extremely low gas concentration levels without amplification. (PE July '73) "ELECTRONIC NOSE" illustrates amplified alarm system.
TGS HEAD AND CIRCUIT APPLICATION DATA. PRICE £1.85.

ZN414 a complete I.C. receiver. No IF coils required for tuning. As featured in P.W. Sept. 73 issue. Price only £1.05.

RESISTORS

Power Watts	Tol.	Range	Miniature wire wound Values Available	1-9	10-99	100+
1/4	5%	2.2-10 Meg.	E12	1p	0.8p	0.7p
1/2	5%	2.2-10 Meg.	E12	1p	0.8p	0.7p
1	5%	2.2-10 Meg.	E12	2p	1.6p	1.4p
4	10%	1ohm-10ohm	E12	6p	5p	-

Do not mix ohmic values to obtain quantity prices. Ignore fraction.

POLYESTER CAPACITORS. Axial lead type.

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 2½p; 0.01µF, 0.015µF, 0.022µF, 0.047µF, 3p; 0.068µF, 0.1µF, 0.15µF, 4p; 0.22µF, 7p; 0.33µF, 10p; 0.47µF, 13p, 160V: 0.1µF, 0.15µF, 4p; 0.22µF, 5p; 0.33µF, 6p; 0.47µF, 7p; 0.68µF, 10p; 1µF, 13p.

Radial lead P.C. type:

250V: 0.01µF, 0.015µF, 0.022µF, 3p; 0.033µF, 0.047µF, 0.068µF, 3½p; 0.1µF, 4p; 0.15µF, 4p; 0.22µF, 0.33µF, 5p; 0.47µF, 7p; 0.68µF, 10p; 1.0µF, 11p.

ELECTROLYTIC CAPACITORS. Miniature axial lead type.

63V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 47µF, 68µF, 6p each.
40V: 100µF, 6p; 150µF 25V, 6p; 25V: 220µF, 11p; 470µF, 13p; 1,000µF, 25p.

CERAMIC CAPACITORS: 50V d.c. Palette body 25mm leads. Range: 22pF-10,000pF. Price 2p each.

POTENTIOMETERS:	Carbon
Track 0-25V, log and linear values.	
1kΩ-2MΩ Single gang	12p
5kΩ-2MΩ s/gang w/switch	24p
2kΩ-2MΩ Dual gang	37p

PRESET POTENTIOMETERS	
0-25V 1kΩ-1MΩ Hor. and Vert.	6p
0-1V 100Ω-220kΩ Vert. only	3p

SLIDER POTENTIOMETERS	
0-25V log and linear values	
10kΩ-100kΩ Single gang	35p
10kΩ-100kΩ Dual gang	50p

KNOB	
To fit 1" shaft unless specified.	
Black Pointer type	8p
Slim Silvered	10p
Black 1" with chrome rim	15p
Slider Pot knob	10p

WATFORD ELECTRONICS

35 Cardiff Rd., Watford, Herts, England.

Enclose 10p stamps for our comprehensive catalogue.


Name

Address

PRODUCTION LINES

colin riches

IF FILTER BLOCKS

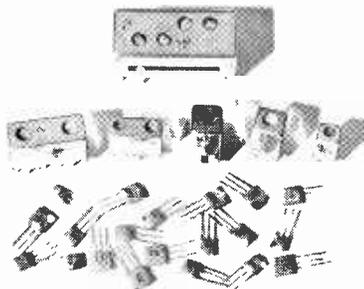

What appear to be small ceramic capacitors, albeit with three leads, are in fact ceramic IF filter blocks made by Toko of Japan. A coloured dot indicates the nominal centre frequency which may range from 10.62 to 10.78MHz. Prices 40p.

The equally minute IF units at the top of the photograph include the MFH51T mechanical filter and its matching transformer type YXE10857 which together cost around £1.50. The filter is available in 4, 5 and 7kHz bandwidths (5kHz) versions being readily available at the moment. The CFU455C and CFT455B are also shown in the group, these being ceramic filters centred on 455kHz. Details and current prices from *Ambit International, 37 High Street, Brentwood, Essex.*

DIGITAL CLOCK

Fonadek have introduced their Copal 602 clock. It shows the day, date and time in white numerals and there is a small fluorescent tube built in which illuminates the digits. The cabinet is finished in simulated Brazilian rosewood and the unit is priced at £15.95 including VAT. *Fonadek International Ltd., Harborne, Birmingham B17 9JS.*




AMATEUR RADIO AWARDS

This new book from the R.S.G.B. compiled by the Society's HF Awards Manager contains details of the world's major awards, where and how to apply for them and illustrations of a number of the certificates.

USEFUL FASTENERS

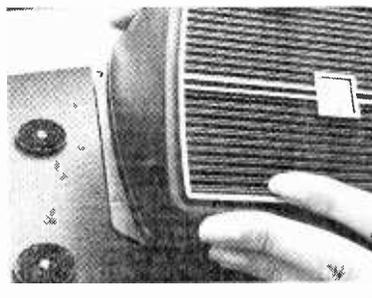Hedlock II fasteners are the latest from 3M. They consist of interlocking "twin" parts which just push together to give a strong bond. They can be screwed to two surfaces, ie: car parcel shelf and speaker (see picture), and make a good push fit. A sharp tug releases the fasteners. *3M, United Kingdom Limited, 3M House, Wigmore Street, London W1A. 1ET.*



20MHz COUNTER/TIMER

Meteronic announce this latest addition to their range of low-cost test instruments. The Type 410 may be used as a frequency meter, multi-period meter or timer. Timebase stability is typically 1 part in 10^6 per °C. Time units are $10\mu\text{s}$ to 1 sec and frequency can be measured to over 20MHz with a resolution of 1Hz. The high impedance input accepts waveforms with slow transition rates. Range selection is manual, with automatic positioning of the decimal point, and allows up to 8 digits to be examined on the large 4 digit display. Overflow indication is provided. Timer start, stop and reset may be operated electronically or by push buttons. The U.K. price exclusive of VAT, is £85. *Meteronic, 114/116 Shipbourne Road, Tonbridge, Kent.*

HIGH-QUALITY STEREO DECODER

A recent addition to the Mullard range of modules for use in radio and audio amplifiers is a stereo decoder, type LP1400. It is intended for use by setmakers in high-quality equipment.

The LP1400 uses the sum and difference separation principle, which allows de-emphasis to be applied to the difference signal before demodulation. This attenuates interference from adjacent channel transmissions and noise components in the 114kHz and 190kHz regions which in a time multiplex system are frequently demodulated by harmonics of the 38kHz signal and transposed to produce unwanted components in the audio outputs.

The LP1400 offers good stereo separation and a better overall performance than is generally obtained with time multiplex systems.

Mullard Ltd., Mullard House, Torrington Place, London WC1E 7HD.

QUADRAPHONIC PHONES

You don't have to have four ears to listen to quadraphonic sound on headphones, because in the new Eagle FF29, four 50mm transducers are so arranged that the effect is similar to four strategically-placed loudspeakers.

The FF29 phones use two coded jack plugs which are also ideally suited for use with the AA26 quadraphonic adaptor. This unit converts any stereo set-up into a 4-channel system with the addition of 2 extra speakers.

Frequency range of the phones is 20Hz-20kHz, impedance 8Ω per channel and matching impedance 8 to 16Ω . The retail price is £16.80 excluding VAT. *Eagle International, Precision Centre, Heather Park Drive, Wembley, HA0 1SU.*



SPECIAL PRODUCT REPORT

ELECTRONIC CALCULATOR


ONE of the latest additions to the electronic home construction market is a pocket calculator available as a complete kit or fully assembled. The Sinclair Cambridge weighs 3½ozs and measures 4½ x 2 x 1½in and has an 8 digit LED display.

The LED display is an 8 digit 7 segment gallium arsenide/phosphide device being driven via diodes directly from the calculator chip. The 8 diodes, D3-D10, and the flat pack resistor package RN1 form both isolation and an integral part of the keyboard's electronic routine. The cathodes of each digit are driven by a sixteen pin integrated circuit.

The keyboard is made from a single sheet of stainless steel with 18 'click fingers' chemically etched into it to enable the keys to have mechanical hysteresis and a positive click action.

The power supply (incorporating Tr1 functioning as an oscillator) generates a stabilised 15 volt d.c. supply for the two IC's. The action of Tr1 is such that it switches fully on and off thereby producing a square wave at the emitter thus providing the clock pulse, which is required to drive the calculator chip.

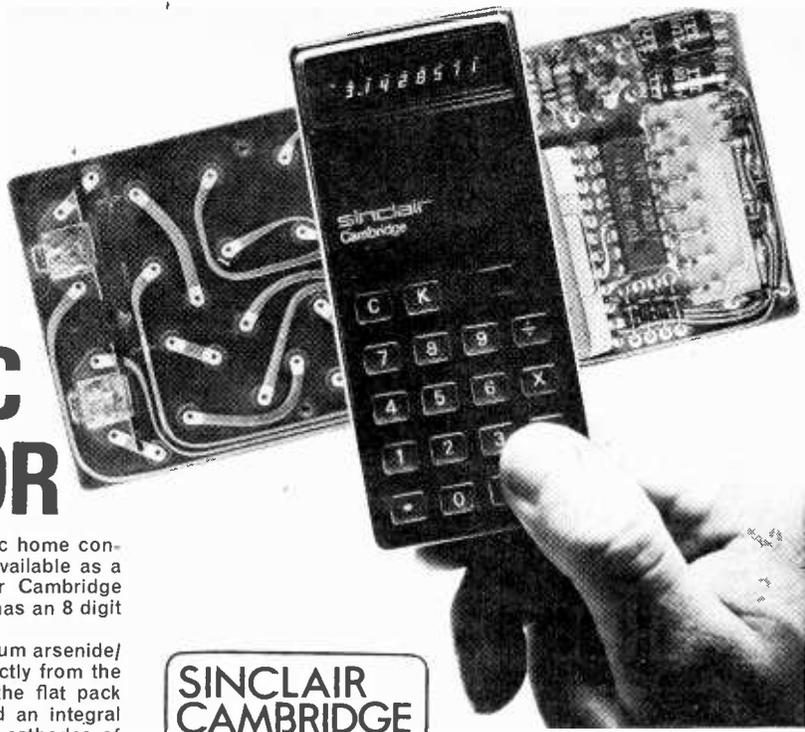The algebraic logic of this calculator—which enables calculation to be entered as you would write it down, or in other words logically, acts together with an advanced constant function to give, in effect, a limited memory, thus




SINCLAIR CAMBRIDGE

extending the calculations which can be carried out as true chains. The constant facility may be used on all four functions—addition, subtraction, multiplication and division (+ - × ÷). These functions are often referred to in calculator terminology as operators.

In addition, the calculator operates across a wide exponent range from 10^{-20} to 10^{29} enabling it to handle large or small numbers without becoming overloaded. Calculations are to 8 significant digits, and incorporate a fully floating decimal.

A dual purpose clear button will remove only the last entry when used in conjunction with a function.

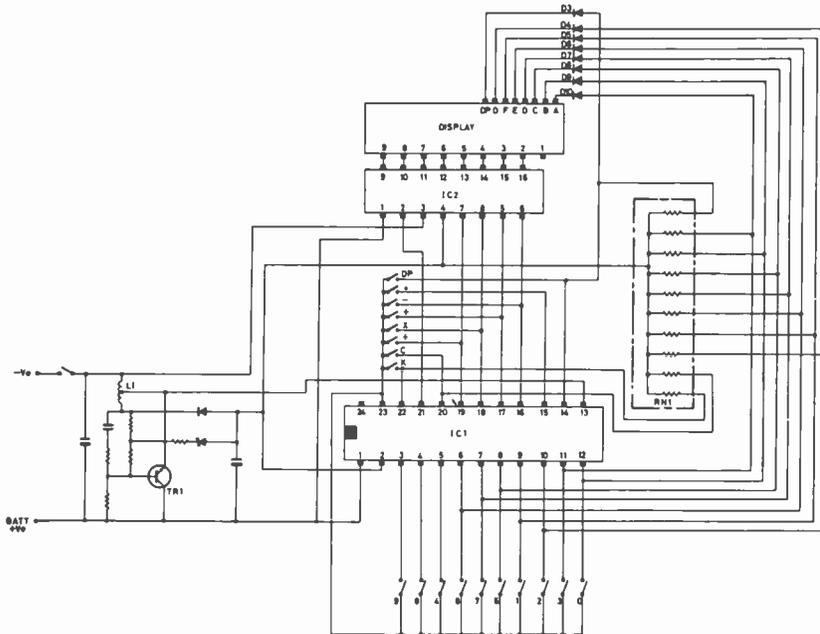The calculator is battery powered by four cells. These may either be ordinary U16 cells (which give limited life) or the MN2400 mercury cells to give the calculator an extended



Basic circuit of the Sinclair Cambridge. A brief description of circuit function is given in the text.

The Catalogue you MUST have!

HOME RADIO COMPONENTS

250 pages 11¼" x 8¼"

6,785 electronic
components clearly
listed and indexed

1,750 pictures

10 free Vouchers
each worth 5p.

Price list
regularly
updated

Bookmark
with useful
list of
technical
abbreviations

*Details of our popular
Credit Account Service
and our Easy Ordering
System are included
in the catalogue.*

Only 55p. plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

The price of 77p applies only to customers
in the U.K. and to BFPO addresses

Name _____

Address _____

HOME RADIO (Components) LTD. (Regn. No. London 912966)
Dept. PW, 234-240 London Road, Mitcham CR4 3HD





FAN/ BLOWER

Precision-built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60MA on run. Size: 5 1/2" dia. x 2 1/2" deep. Backplate is tapped for 4 fixing screws (supplied). Well under maker's price at £3. P. & P. 20p. Similar unit to above but 7 1/2" dia. x 3" deep. £4.50. P. & P. 25p.



SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1 min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.30. 15p P. & P.

GEARED MOTORS




"Parvalux" Reversible 100 rpm geared motor. Type SD14, 230/250v. AC., 22 lb/in. 3/8" spindle. 1st class condition. £7.50 each. 50p P. & P.
Also limited number only as above. BRAND NEW. £12.50 each. P. & P.

REVERSIBLE Parvalux type SD19, 240v. AC. 30rpm. 40 lbs/in. Variable angle drive shaft. ABSOLUTELY AS NEW. £6.30. P. & P. 50p.

SHADED POLE Mains motor. 1 1/2" x 1 1/2" x 2" high. Double ended 3/8" shaft projecting 1 1/2" each side of motor. £1. P. & P. 20p.

OPEN FRAME shaded pole GEARED MOTORS

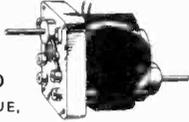


(Dural gear case) 240 AC., 28rpm NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/4" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p.
110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



SPIT MOTOR

5 1/2rpm. 2 1/2" x 1 1/2" x 6 1/2" high. 240v. AC. Shaft 1/4" o/d, 1 1/2" length with hexagon socket inside. £1.80. P. & P. 30p.

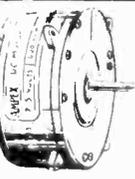

AMPEX 7.5v. DC MOTOR

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. 1/4" dia. x 1" spindle, motor 3" dia. x 1 1/2".

Original cost £16.50. OUR PRICE £3. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available. 75p each. FREE P. & P.

"DAVENSET" MAINS SOLENOID
1" travel, 8lbs. pull (approx.). Size: 2 1/4" long x 2 3/16" x 2" high. Similar in appearance to "SORENG". £1.50. P. & P. 20p.

MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm. 2 1/2". 240V AC. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.



Solenoids by Westool

240 AC type MM6. 3lb. pull, 2 1/2" x 1" x 1 1/2". Travel 1". 85p each. P. & P. 10p.



240AC type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1". Travel 1/2". 60p each. P. & P. 10p.
Quantity discounts: 10-50 10%. 50 upwards 25%.



"DECCO" MAINS SOLENOID

Compact and very powerful. 16lb. pull. 3/4" travel which can be increased to 1" by removing captive-end-plate. Overall size: 2 1/2" x 2 1/2" x 2 1/2" high. £2. P. & P. 20p.



MAINS SOLENOID by MAGNETIC DEVICES LTD.

A (beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/2" x 1 1/2". Pull is approximately 2lbs., plunger travel 1 1/2". Fixing eye takes up to 1/4" bolt, plunger non-captive. NEW in original maker's boxes. £1 P. & P. 20p. Large number available, special price for quantity.

"CROUZET" MOTORS 3 RPM



Type 965
115/240v. 50Hz. 48w. Stoutly constructed, 2 1/16" dia. x 3 1/2" long plus spindle 1" x 1/4" dia. Anti-clock. £3 each P. & P. 25p.

"RE CIRC IT" Mains 10amp cut-out

by "Neimman Electric" Germany. Eliminates fuses. Size: 2" x 3" x 1 1/2" deep, 90p each. P. & P. 10p. 10 or more 70p each. P. & P. 20p.



UNLESS OTHERWISE STATED all items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50. C.W.O., please. Company orders under £2.50. Surcharge 60p unless C.W.O.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1/4"; (80 DB) 3/4" x 5/32" x 1/4". Ex-equipment, all tested. £1.20 each. P. & P. FREE.

PLUG-IN RELAYS by SCHRACK (PERSPEX ENCLOSED)

OCTAL (2 c/o) 6 amp contacts at following voltages: 48 D.C., 60 A.C., 60 A.C., 110 D.C., 380 A.C. PRICE EACH 90p

11 pin (3 c/o) 6 amp contacts: 12 A.C., 48 D.C., 48 A.C., 60 A.C., 60 D.C., 110 D.C., 115 A.C., 240 A.C. PRICE EACH £1

RA and RN Series (4 c/o) 3 amp Gold Plated Contacts. Handsome modern construction 1 1/2" x 2" x 1 1/2" high. Following voltages: 6 A.C., 12 A.C., 24 A.C., 48 A.C., 48 D.C., 60 A.C., 110 D.C., 115 A.C., 120 A.C. PRICE EACH 80p

Base sockets for all above types 10p
Please add 10p towards P & P on all orders.

From JAPAN, TAKAMISAWA Perspex enclosed relays. Type MQ 308. 24V. DC. 600 ohms (4 c/o). Complete with white socket. 80p P. & P. 10p.

SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1 1/2 amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems, etc., and wherever non-mechanical switching is required. 10 for £1.80; P & P 15p. 50 for £9; 100 for £15. FREE P & P over 10.




NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s, etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12"; 24" x 12"; 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

TANGENTIAL HEATER

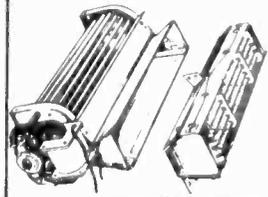Silently driven by shaded pole Mylex motor, powerful and smooth running with aluminium impeller (outlet 5/8" x 1 1/2"). Mains voltage PLUS matching heater unit with spiral element. May be switched for 500 or 1,000w. £1.60. P. & P. 30p.



PLEASE ADD 10% FOR V.A.T. ON ALL PRICES SHOWN INCLUDING P & P

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580

BAKER 12" MAJOR £9.90

30-14500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly flux density 145000 gauss. BASS RESONANCE 40 cps 20 watt RMS

MAJOR MODULE KIT £12.50

30-17000 cps. Woofer, Tweeter, crossover and baffle as illustrated. Size 19 x 13 in. Note: when ordering state 3 or 8 or 15 ohms.

BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12" 15W £8.80	Superb 12" 20W £16.50
Major 12" 20W £9.90	Group 25 12" 25W £8.80
Deluxe 12" 15W £11	Group 35 12" 35W £9.90

ALL PRICES INCLUDE VAT

BAKER LOUSPEAKER CO. Bensham Manor Passage, Thornton Heath, Surrey, Tel. 01-684 1665
Loudspeakers Catalogue and Enclosure plan 5p

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Switches, Potentiometers, Knobs, IF's, Tag Strips, Drive Drums, Transistor Panels etc., etc. Save yourself £s on these well selected parcels 6lbs net weight £1.00, p. p. 40p.

Assorted Electrolytic Capacitors, 6lbs net weight £1.00, p. p. 40p.

Brand new Wire-wound Resistors, Good Selection. 100 for £1, p. p. 15p.

Mullard Ferrite Pencil Magnets 1 1/2" x 7/8". 100 for £1.25, p. p. 16p.

Assorted Computer Panels. These panels are exceptionally good value and contain a minimum of 75 transistors, stacks of diodes plus Trim Pots, Polyester Capacitors, Resistors and include a few I.C.s. 10 panels for £1.00, p. p. 25p.

Mullard Ferrite Cores. LA3 100 to 500kHz 50p, LA4 10 to 30kHz 75p, LA2100 3 to 200kHz 50p.

Please include 10% V.A.T. to total cost of goods. Mail Order Only.

XEROZA RADIO

1 EAST STREET, BISHOPS TAWTON, DEVON


MORE ON THE ZN414

L.A.J. IRELAND

THE first surprise to the reader brought up on radio in the fifties and sixties is to find the TRF (tuned radio frequency or "straight") radio circuit making a comeback in the 1970s. This type of circuitry was discontinued in the thirties, with the development of the superhet, for several good reasons. First, the selectivity of the tuned circuits of the time became inadequate as the number of transmitters on the air increased, with the result that the ability to discriminate between stations closely separated in frequency was impaired. Improved selectivity required more sharply tuned coils, or alternatively the application of reaction or positive feedback. Further, with a series of tuned circuits operating at the same frequency, stray coupling could itself provide sufficient positive feedback to produce instability.

In any event, excessive positive feedback whether due to stray coupling or deliberate application of reaction could, quite simply, cause the circuit to radiate rather than receive and thereby render impossible reception of a broadcast on that frequency, for some distance around. The superhet, in which amplification of the signal occurs mainly at an intermediate frequency separated from that of the received signal, not only guarantees improved selectivity and stability but also permits the easy application of such refinements as automatic gain control (AGC).

The above observations apply generally to valve or transistor systems; it will be noted that, although TRF circuits have a deceptive simplicity, and avoid the purchase, installation and alignment of intermediate frequency transformers, they achieved only a very restricted popularity among the home constructors of the sixties. Also, despite the fact that quality in broadcast sound had been transferred to the FM channels, even the cheapest commercial AM receivers retained the superhet scheme. To be a credible contribution to the radio scene, therefore, the Ferranti ZN414 unit must have featured as distinctly novel in TRF circuits.

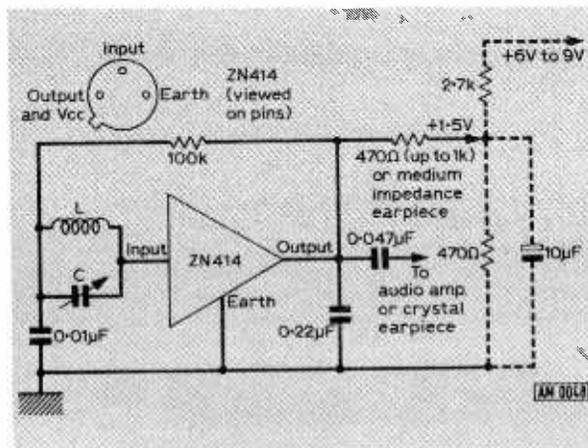

It should be clear, though, that the technology of the monolithic integrated circuit is better adapted to the TRF format. In every single operational amplifier or other high gain IC, methods have had to be developed and applied to enable the transfer of signals through several stages of amplification within a single chip without instability developing through stray capacitances. An integrated circuit IF amplifier for a superhet, however, must either lump all the frequency-selective tuned circuits before or after the amplification stage, or alternatively transfer the signal several times between the chip and external discrete circuitry, each time incurring the risk of instability problems which the superhet was intended to avoid. Further, with the high grade ferrites and litz wire, the tuned aerial circuit currently available has a higher "Q" and therefore an inherently improved selectivity, on the circuits of over thirty years ago. Further, a high input impedance can be developed, in the case of the Ferranti ZN414 typically over 1.5MΩ, so that this selectivity is not degraded by the loading presented by the following circuit. Finally, it has been found possible to incorporate an adequate AGC system.


Low current consumption

The unit incorporates the equivalent of ten transistors packaged in a three pin TO-18 can identical with that used for small NPN transistors. The required power source is a single 1.5V dry cell though the unit will function adequately over the range 1.1 to 1.8V; economy of operation is assured by the very low current drain, some 1mA being typical. Under such conditions, and with the AGC system operating on an incoming signal, the circuit produces an output of some 40mV quite adequate to operate a medium impedance magnetic earpiece (about 500Ω) or a crystal earpiece through a coupling capacitor. In general, though, the unit will be used to drive an audio amplifier, for which the output is adequate.

Constructional details

Now for one or two constructional points. The small capacitor from the output pin to earth bypasses to earth any radio frequency signal appearing at the output. It is therefore necessary that it be mounted as close as possible to the output and earth leads of the ZN414. It will be noted that the time constant of the output circuit, determined by this capacitor and the AGC resistor, is some 4kHz a feature tailored to the characteristics of the AM signal, for which a passband of some 10kHz (double side-band) is allowed.

The aerial used, which may be any of those advertised to cover the medium waveband with an appropriate capacitor, should have its ferrite rod at least an inch away from the IC, otherwise all leads should be as short as possible. Due to the high input impedance already mentioned it is not necessary to tap the tuned coil on the ferrite rod to find a matching point to feed the circuit input. However, on commercial rod aeriels employed with this unit, such a tap, or a small secondary winding, may be available; this may be used experimentally for the connection of an external aerial, if so desired. ■

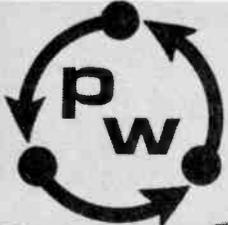

'ferret'



PHASE LOCKED LOOP I.C. METAL DETECTOR

THIS lightweight metal detector operates at a frequency of 120kHz and uses a phase locked loop to provide both an audible and a visual indication of a find. Most detectors use either a variable inductance or a variable mutual inductance as the sensing element. The Ferret is no exception, the inductance of the search coil changing in the presence of metal. Ferrous and non-ferrous metals cause opposite changes in inductance and it is a unique feature of the Ferret that a visual indication of this is provided. The meter deflection is in opposite senses for the two types of metal.

Another feature not found on previous metal detectors is the use of harmonic mixing. Although the two oscillators in the Ferret are both operated at about 120kHz the beat note is derived from their fifth harmonics and the sensitivity is accordingly five times as great.

Main Oscillator

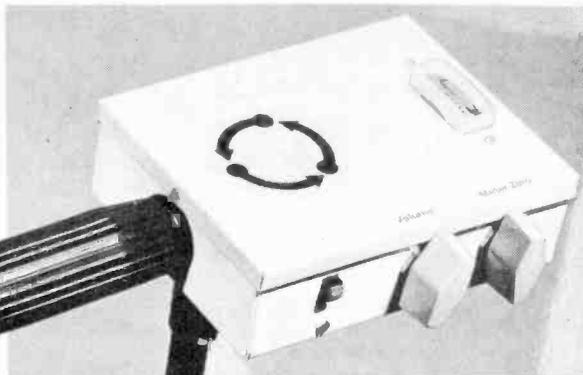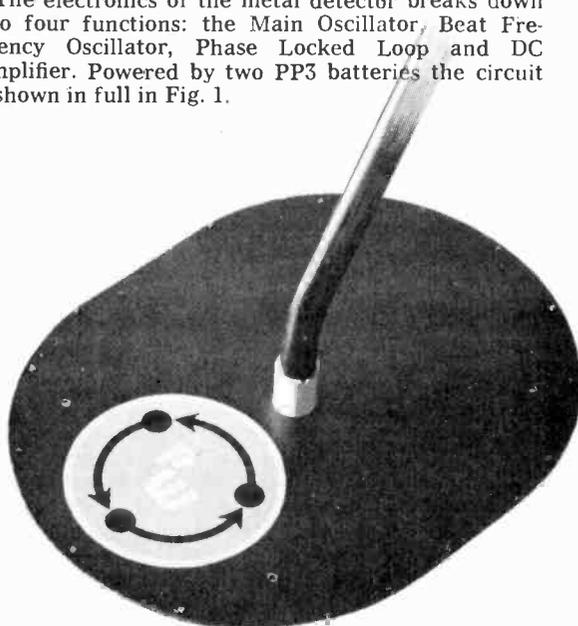The electronics of the metal detector breaks down into four functions: the Main Oscillator, Beat Frequency Oscillator, Phase Locked Loop and DC Amplifier. Powered by two PP3 batteries the circuit is shown in full in Fig. 1.



R.P.A. PERRY
(SIDNEY SUSSEX COLLEGE)

The search coil L1 and the series combination of C4, C5 and C6 form a tuned circuit with Tr1 acting as an oscillator taking the voltage at the C4-C5 junction, amplifying it, and feeding it back to the C6-L1 junction in the correct phase for maintaining the oscillation. Diode D1 clamps the gate of Tr1 below earth potential and provides AGC action to stabilise the output and prevent it from being clipped. DC power is fed to the amplifier through the choke L2 the value of which is not critical, but 25mH should be considered a minimum and the value chosen (40mH) happened to be available to the author in a convenient size. An output of at least 5V peak to peak should be available, the frequency being adjusted by altering the number of turns on L1.

Beat Frequency Oscillator

An NE555 timer IC is used in astable mode to provide a variable frequency oscillator. Suppose C1 is charging up through R1, R2 and VR2; when the voltage across C1, sensed by pin 6, reaches $\frac{2}{3}$ Vcc pin 7 is earthed and C1 begins to discharge through R1. When the voltage across C1, sensed by pin 2, has fallen to $\frac{1}{3}$ Vcc pin 7 is allowed to float and C1 begins to recharge. The switching applied to pin 7 is amplified and presented at the output, pin 3, as a squarewave which swings between earth and Vcc.

$$C1 \text{ charge time} = 0.685(R1 + R2 + VR2)C1$$

$$C1 \text{ discharge time} = 0.685R1C1$$

$$\text{Frequency} = 1 / (\text{Charge time} + \text{Discharge time}) \\ = 1 / (2R1 + R2 + VR2)C1 \times 0.685$$

Substituting the circuit values gives a range of frequencies, as VR2 is varied, of 103-160kHz. The upper frequency is not reached due to stray capacitances and internal resistances (the chip is only specified to 100kHz) but an adequate band to either side of 120kHz can be swept.

Phase Locked Loop

The operation of the NE561B phase locked loop was described last month, but is outlined again below owing to the unconventional used made of it in the Ferret.

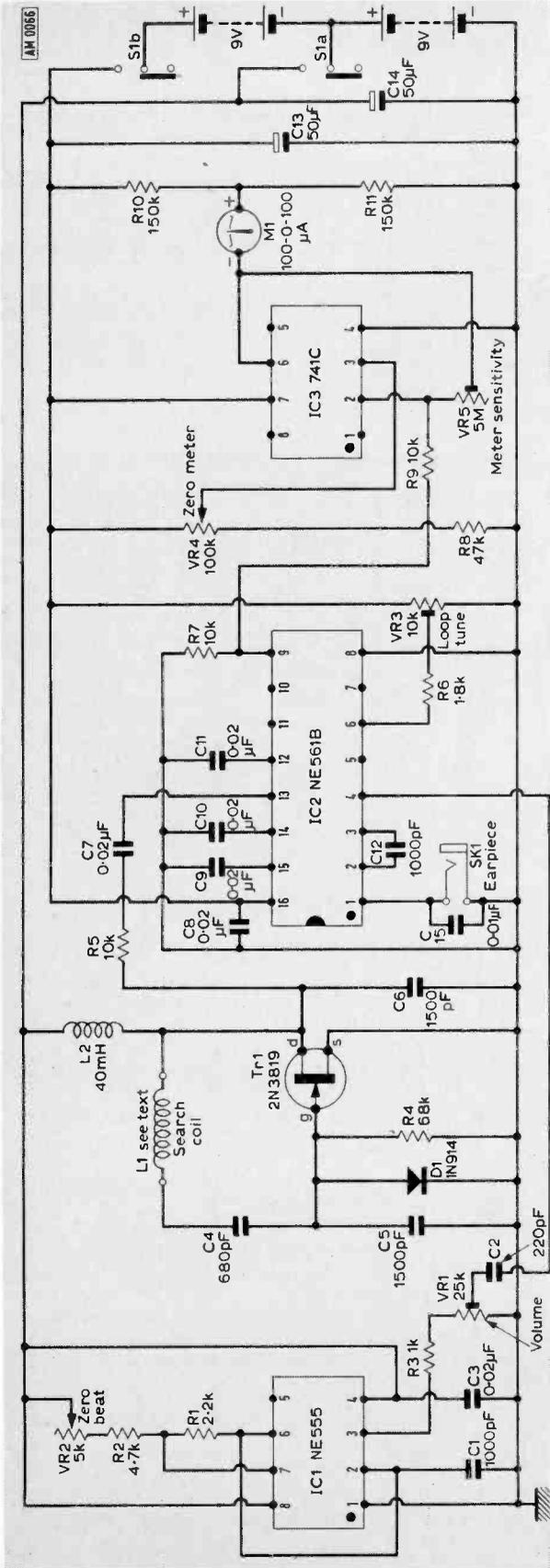


Fig. 1 : Complete circuit of the P.W. Ferret

When the PLL has no input signal, the Voltage Controlled Oscillator (VCO) frequency resulting is called the free-running frequency and is determined by C12 and the current injected into pin 6 from VR3 and R6.


In Fig. 2, Vc assumes a quiescent value. On applying the main oscillator output to the FM input, pin 13, the phase sensitive detector and low pass filter cause Vc to change just enough to make the VCO frequency equal to the input frequency ($5 \times F_0$).

The amount that Vc changes depends on the difference between the free-running frequency and $5 \times F_0$. In this circuit the free-running frequency is fixed so Vc can be regarded as a function of F_0 only.

$$\frac{\text{Change in } V_c}{\text{Change in } F_0} = 200\text{mV}/\%$$

Thus changes in the inductance of L1 have been transformed into changes in F_0 which have in their turn been transformed into changes in Vc.

The VCO frequency, which by PLL action is exactly equal to $5 \times F_0$, is mixed with the Beat Frequency Oscillator output $5 \times F_b$ in the internal multiplier intended for AM demodulation, Fig. 2. An audible beat note, F_a , results where $F_a = (5 \times F_0 \pm 5 \times F_b) = 5(F_0 \pm F_b)$.

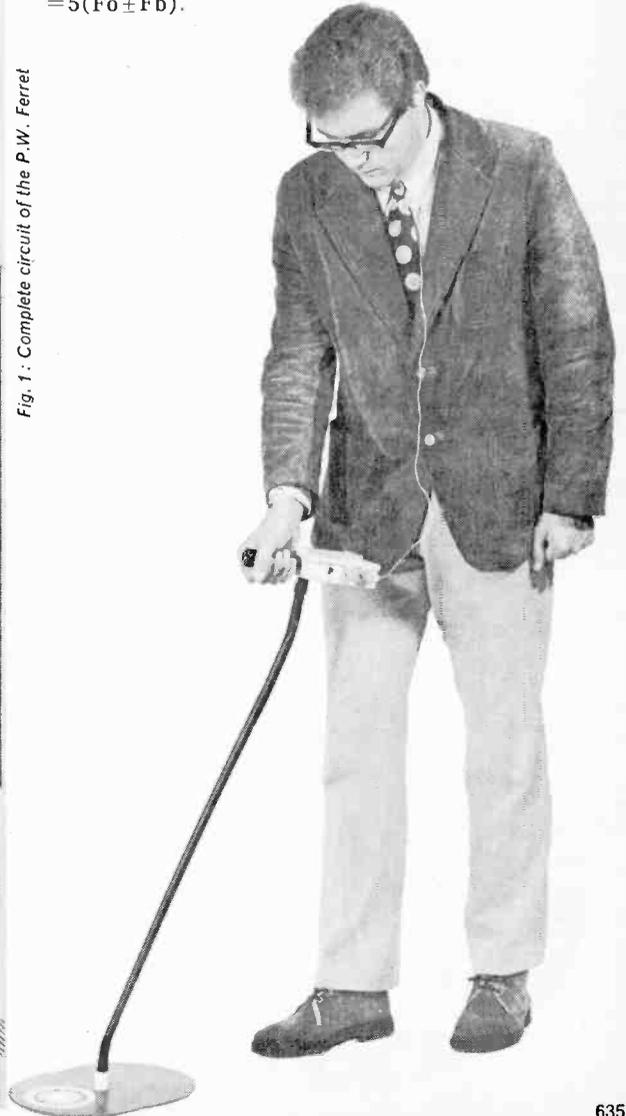

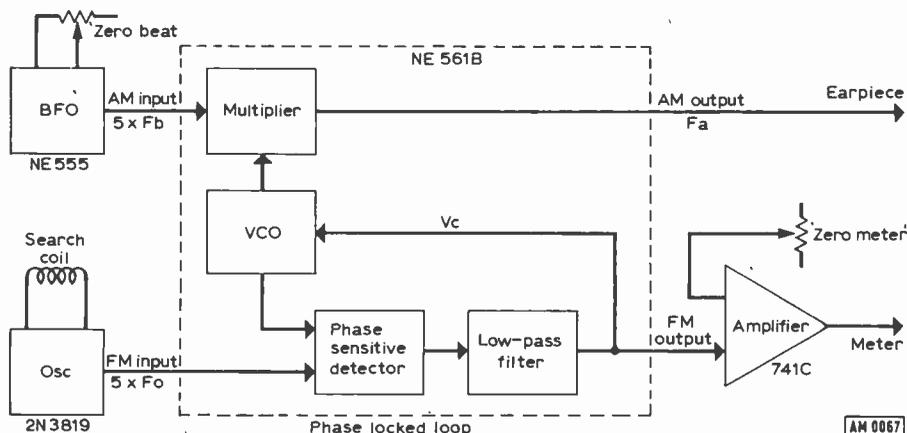


Fig. 3: Block diagram illustrating circuit function.

Fig. 3: The printed circuit board—to scale.

If F_o and F_b are very large compared with F_a , and are nearly equal to each other then very small changes in F_o will produce large changes in F_a . Suppose F_o changes from 120kHz to 120.120kHz, with $F_b = 119.9$ kHz.

V_c will change by

$$\left(\frac{120.120 - 120}{120} \right) \times 100 \times 200\text{mV} = 20\text{mV}$$

and F_a will change from $5(120 - 119.9) = 500\text{Hz}$ to $5(120.120 - 119.9) = 1100\text{Hz}$.

The output from the Beat Frequency Oscillator is dropped by the volume control VR1 to a level suitable for the phase locked loop and C2 tailors the frequency response of the coupling network to attenuate the fundamental of 120kHz but pass the required harmonic of 600kHz. An input of more than two volts will cause damage to the IC. The mixed output is fed directly into a crystal earpiece, and is quite sufficient for all but the most noisy surroundings. As mentioned above, VR1 acts as a preset volume control.

DO NOT attempt to drive a magnetic earpiece directly from the IC as this will seriously overload it. If it is required to run a magnetic earpiece or speaker then it is quite permissible to add a suitable amplifier stage, remembering that the AM output of an NE561B has a DC level of about +14V.


Capacitors C7-C11 perform coupling and bypass functions and any value between $0.01\mu\text{F}$ and $0.1\mu\text{F}$ should be adequate.

D.C. Amplifier

A 741 operational amplifier is used as a variable gain inverting amplifier. By altering the value of VR5, the preset sensitivity control, the gain of the amplifier can be adjusted from $\times 1$ to $\times 500$. At maximum gain an output swing of 1 volt is obtained for a 0.01% change in F_o .

Because the normal output level at pin 9 of IC2 is +12V a voltage divider VR4 and R8 is provided to give a zero-set control. The meter M1 will give a zero indication when the voltage at pin 3 of IC3 equals the voltage at pin 9 of IC2.

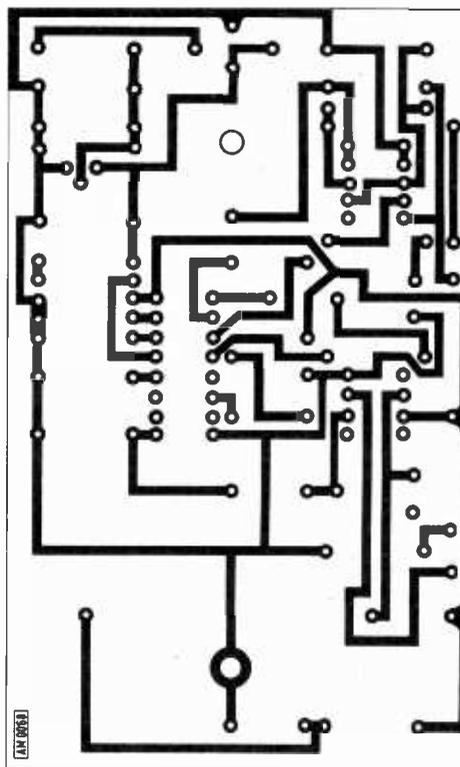Resistors R10 and R11 are equivalent to a single resistance in series with the meter and connected to +9V. Their values should be adjusted so that



full scale deflection of the meter occurs when the amplifier output is either at earth or +18V. 150k Ω was found to suit the miniature meter used in the prototype. Power supply decoupling is provided by C13 and C14.

Transistor enthusiasts may be interested to know that the three integrated circuits contain about seventy-five semiconductor devices although it is not often clear which of these are transistors and which are diodes!

Circuit Board

A printed circuit board $4 \times 2\frac{3}{8}$ in. has been designed to take the Ferret, see Fig. 3. Only one interconnecting wire is used on the board and all terminations

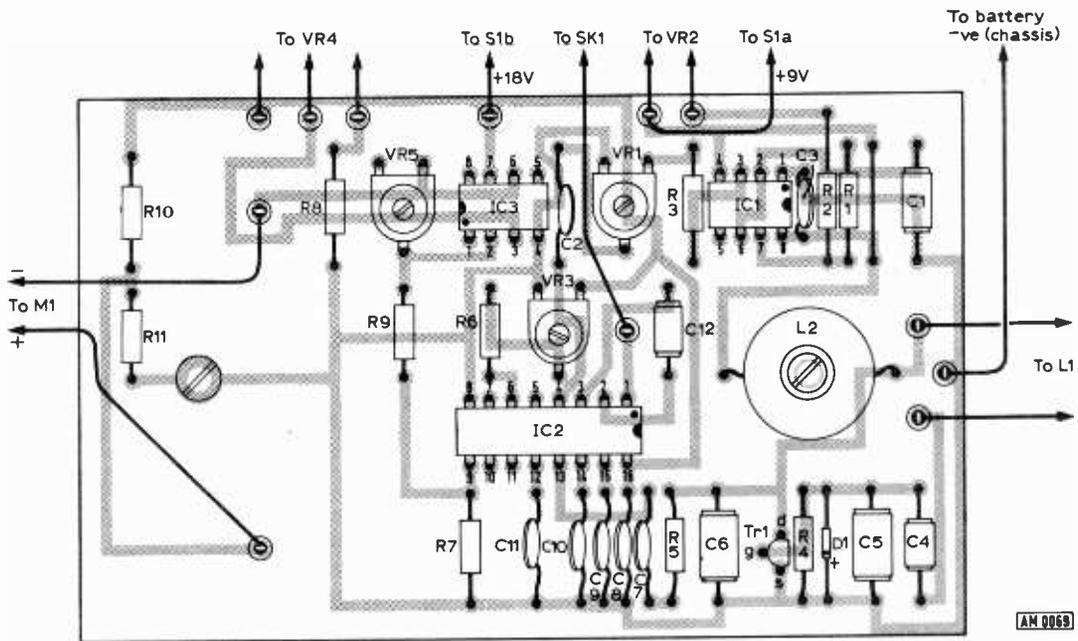


Fig. 4: Component layout and interconnections.

are taken to convenient points. The meter is intended to be positioned over the large clear area at one end of the board. Two holes are drilled to enable the board to be bolted into the box, one being positioned to take the integral screw of the specified pot core L2.

All the component holes except those for the preset potentiometers VR1, VR3 and VR5 are positioned on a 0.1in. matrix so the circuit could be made up as shown on perforated paxolin with pins and underboard connecting wires. Component positions are shown in Fig. 4.

If a new component layout is contemplated then the only precaution to take is to keep the leads to IC2 as short as possible and the circuit basically split up into its four sections, as depicted in Figs. 1 and 4.

Assembly

A small aluminium box $5\frac{1}{4} \times 4 \times 1\frac{1}{2}$ in. has the remaining components mounted inside it with the meter in the lid. It is important to use a metal box in order to keep down stray radiation. Fig. 5 shows the positions of VR2, VR4, S1 and SK1. The cutting details for the meter will depend on the actual type used.

A 6BA bolt is used to augment the 6BA bolt in L2 for holding the circuit board. It is important to see that the case is earthed via the copper conductor pattern by at least one of these screws. The best way to ensure that the component wires do not short out on the case is to introduce a couple of extra nuts on the bolts between the board and the case.

If plastic electrical conduit, as described later, is used to construct the shaft of the Ferret then a hole large enough to accommodate the fixing bush must be punched or cut in the base of the case and a similar one for the handle.

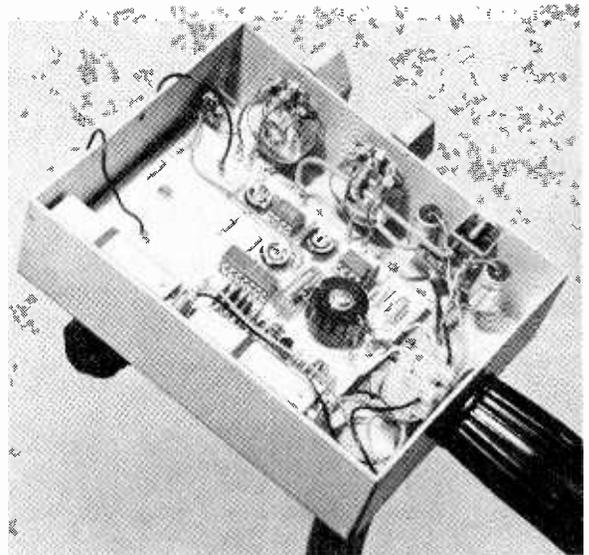


Fig. 5: The positions of the main controls can be clearly seen above.

The search coil, L1, must be wound for an inductance which gives a frequency of 120kHz in the main oscillator. It can be shown that the inductance is proportional to N^2D , where N is the number of turns and D the diameter of the search coil. Many different coils have been wound for the prototype using this formula based on an original made with the aid of a digital frequency meter. All have fallen well within the band that can be tuned in by the rest of the circuitry.

Fig. 6a shows a small coil for localised searches and Fig. 6b a larger coil, which is slightly less sensitive, for extended searches. The number of

turns are respectively 90 and 65. To wind the coil, first nail a few small pins into the upper rim of the top plate and carefully wind the required number of turns from any thin insulated copper wire. When this is complete push the coil down on to the hardboard and secure with a dozen or so blobs of glue. When the glue is dry the pins can be removed and the two pieces of hardboard sandwiched together. Drill four holes in the complete assembly, as shown in Fig. 6, and bring the plates together with 4BA bolts.

The connection to the circuit board is made by a length of coax cable and a terminal block inside the case.

One of the easiest materials to use for the shaft is a length of plastic conduit intended for electrical wiring. Having been bent to the shape shown in Fig. 7, by gently heating the relevant section, it is fixed into the base of the box and the search coil top plate with termination pieces. The fixing to the search coil should be completed before it is finally screwed together.

A short length of conduit, fixed as described above into the end of the case, covered with a bicycle handlebar grip will suffice for a handle.

★ components list

Resistors

R1 2.2k Ω	R5 10k Ω	R9 10k Ω
R2 4.7k Ω	R6 1.8k Ω	R10 150k Ω
R3 1k Ω	R7 10k Ω	R11 150k Ω
R4 68k Ω	R8 47k Ω	

All $\frac{1}{2}$ or $\frac{1}{4}$ watt, 20% or better, see text
 VR1 25k Ω pre-set pot., horizontal, miniature
 VR2 5k Ω pot., standard
 VR3 10k Ω pre-set pot., horizontal, miniature
 VR4 100k Ω pot., standard
 VR5 5M Ω pre-set pot., horizontal, miniature

Capacitors

C1 1000pF polystyrene	C8 0.02 μ F ceramic
C2 220pF ceramic	C9 0.02 μ F ceramic
C3 0.02 μ F ceramic	C10 0.02 μ F ceramic
C4 680pF polystyrene	C11 0.02 μ F ceramic
C5 1500pF polystyrene	C12 1000pF polystyrene
C6 1500pF polystyrene	C13 50 μ F 25V electrolytic
C7 0.02 μ F ceramic	C14 50 μ F 25V electrolytic
	C15 0.01 μ F ceramic

Polystyrene capacitors 5% or better

Semiconductors

IC1 NE555 8 pin DIL	D1 1N914 or similar
IC2 NE561B 16 pin DIL	Tr1 2N3819 or similar
IC3 741C 8 pin DIL	

Miscellaneous

L1, L2 see text. Jack socket, 3.5mm. Crystal ear-piece and plug, 3.5mm. S1, 2 pole c/o slide switch. Aluminium box 5 $\frac{1}{2}$ x 4 x 1 $\frac{1}{2}$ in. (AB10). Batteries PP3 (2) and 2 pairs battery clips. Knobs (2). Plastic conduit, 36in. approx. and conduit terminations (3). Plastic handlebar grip. Terminal block, 2 way. Hardboard and wire for heads. Co-axial cable. Printed circuit board. M1, centre-zero edge panel tuning meter (Henrys F11).

Ambit International, 37 High St., Brentwood, Essex, can supply the pcb for 78p inc., the three IC's and transistor for £4.90 inc. or a complete kit consisting of the pcb, three IC's and transistor, all remaining components, aluminium box and wire for search head for £9.50 inc.

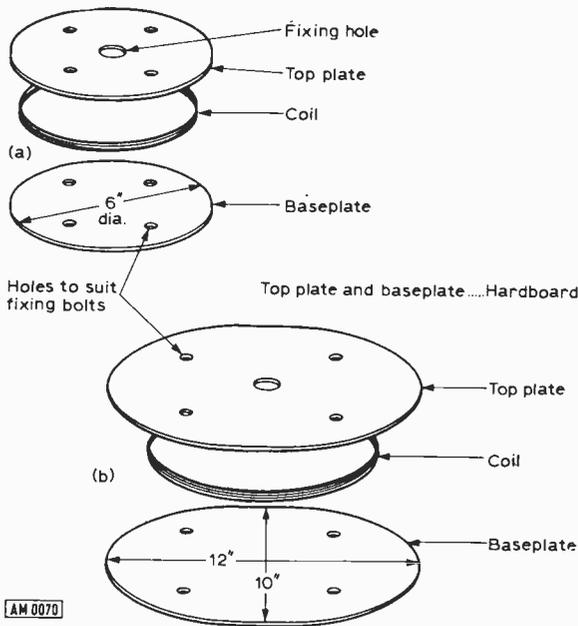


Fig. 6(a): A small coil used for localised searches and Fig. 6(b) a larger coil, although less sensitive, used for extended searches.



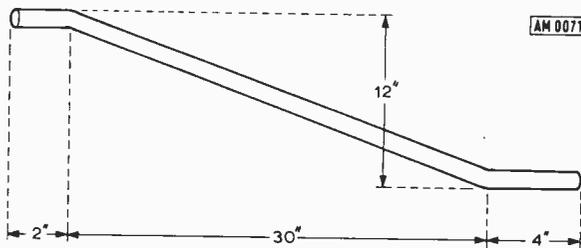


Fig. 7: The handle is formed as shown above.

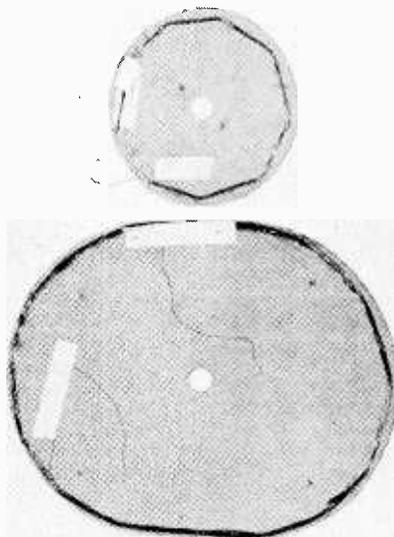

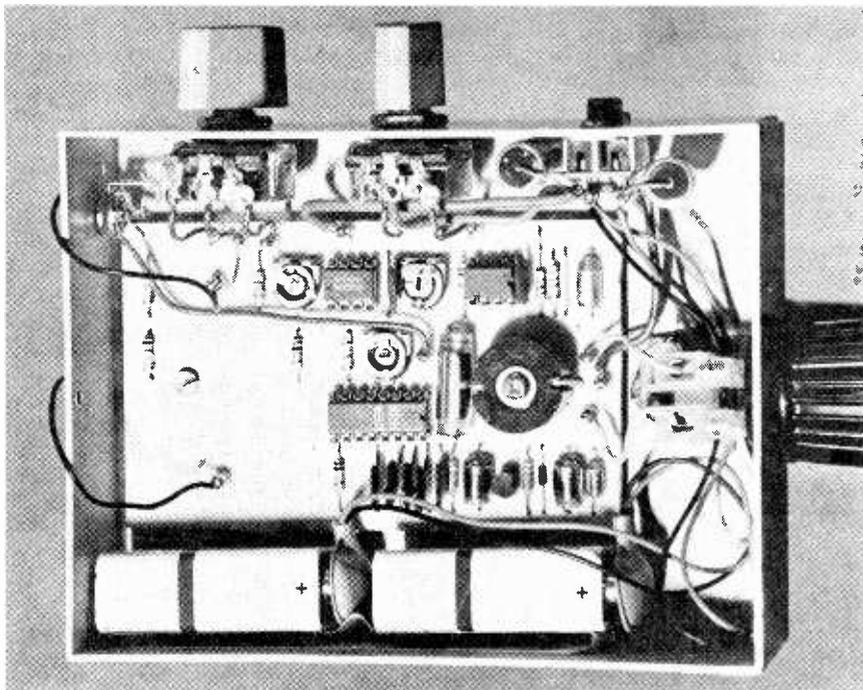Photograph shows two of the coils made by the author.



Close-up view showing the inside of the PW Ferret. Compare this photograph with Fig. 4.

Setting Up

With the search coil connected, set all the preset pots to mid-rotation and switch on. Adjust VR2 for a strong and constant beat note. If only weak and varying notes can be obtained then the loop is not locked and VR3 must be rotated until the required note is heard. Set VR3 in the middle of the portion of its travel over which the beat note is clear. VR1 can then be set for the required volume in the earpiece.

Adjust VR4 to zero the meter, this will be a sensitive setting, and move the Ferret towards a large metal object. An indication should be both heard and seen. VR5 will then determine the strength

of the meter reading when an object comes within range.

It may be possible to obtain beat notes from harmonics other than the fifth. It is sufficient, however, to select that beat note which gives the most sensitive audible response when the Ferret is brought near to some metal test object.

As has been already suggested in the text, a lot of the component values are non-critical and, in general, all except the polystyrene capacitors can have 20% tolerance. It is recommended that first grade integrated circuits are used, especially the NE555. If required, integrated circuit mounting pins can be used. ■

SPECIAL PRODUCT REPORT—continued from page 630

life. Sinclair Radionics claim that mercury cells will give 12 hours continuous operation. Certainly a small mains unit would be an advantage if continuous use of the calculator is contemplated.

The kit is intended for constructors with previous soldering experience. Estimated assembly time is approximately 3 hours. Tools required—and the most important item—is a properly earthed sub-miniature soldering iron with a $\frac{1}{16}$ in. bit or smaller. Other items are wire cutters, tweezers and instrument type pliers.

The 15 page step-by-step assembly instruction booklet contains a section on special safety precautions which should be observed before and during assembly of the kit.

Attention is drawn to the point, that static electricity can be a hazard unless proper precautions are taken. The manufacturers instructions should be carefully read and fully understood before assembly is contemplated.

Care is necessary when assembling the kit, especially because of the numerous tiny solder connections to be made. Blobs of solder must be avoided and close inspection of the completed printed circuit board is essential after soldering has been completed. Examination of the finished p.c.b. with a magnifying glass is recommended to ensure a clean product.

Those constructors who after purchasing the kit and then having read the assembly instructions find that they are 'stumped' may return the kit (untouched) plus a cash balance

in exchange for a built version. What could be more fair? Sinclair Radionics state that full service facilities are available for kits and ready built units.

Also included with the calculator is an informative 32 page booklet detailing the wide range of calculations that can be carried out. From simple arithmetic, compound interest, logarithms, trigonometric functions, roots, polynomials, hyperbolic functions and so on. In addition a credit card size aide-memoire with calculations summarised in formula form is included.

Calculations of all types were performed with the Cambridge and it is surprising how simple it is to use. It brings about a new and refreshing interest to calculations. In the calculation of square roots the iterative Newton-Raphson method is used. This sounds quite complex, but you simply take a (wild) guess at the square root and enter it on the keyboard, using the procedure outlined in the instruction booklet. We tried this method many times—feeding way-out guesses to the keyboard. The correct answer came up every time.

The kit is attractively packaged and includes all necessary components to complete the calculator. Even solder is supplied.

A full money refund guarantee applies to untouched kits if returned within 3 weeks.

At £27.45 (including VAT) for the complete kit, the Sinclair Cambridge provides excellent value for money. Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE14 17HJ.

IN NEXT MONTH'S

PRACTICAL WIRELESS

BEAT THAT POWER FAILURE

DON'T BE LEFT IN THE DARK

Make our simple converter circuit to run a portable 15 watt fluorescent light from a 12 volt car battery.

ALSO FOR:

CARAVANS

SHEDS

LOFTS

CARS

GARAGES

MOBILE RALLIES

WORKSHOPS

or anywhere that a.c. mains is not readily available.


free 2 DATA-CARDS

5. RESISTOR AND CAPACITOR CALCULATOR
6. D.C. CIRCUITS



ALSO:-

3-BAND SW RECEIVER

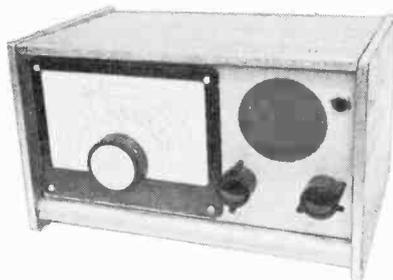

Pick up those unusual broadcasts and amateur transmissions that are found on the short wave band. This receiver is designed to tune 1.7MHz to 30MHz in three bands, using two transistors and two integrated circuits.

AND

INTEGRATED CIRCUIT AUDIO AMPLIFIERS

This fascinating feature shows how you can use one i.c. in any of seven different simple amplifier circuits, including examples for a record player, radio, intercom, or tape player.

DECEMBER ISSUE ON SALE 2nd NOVEMBER

dictionary of audio terms & hi-fi specifications

PRACTICAL WIRELESS 8-PAGE SUPPLEMENT NOV. 1973

A

A-B. This is the kind of audio comparison test where any differences in sound quality can be assessed immediately upon switch-over, i.e. on "A-B" comparison between items of equipment A and B. Often the left and right-hand channels or the record and replay sound signals are designated A and B.

ACOUSTICS. The study of the behaviour of sound. The "acoustic characteristics" of a room are dependent on its size, shape and the reverberation time according to the reflective or absorbent items present.

ACOUSTIC FEEDBACK. Cycling of sound build-up to a continuous squeal as the microphone picks up a signal from a loudspeaker connected to the same microphone amplifier.

ACOUSTIC SUSPENSION. Some loudspeaker systems employ a sealed cabinet. This enables the acoustic pressure of the air enclosed therein to provide the principal restoring force for the diaphragm of the speaker.

A.F.C. Automatic frequency control. A control circuit in a receiver or tuner which compensates for small variations in the carrier signal frequency to provide a stable audio output. A circuit function in a tuner

or receiver which keeps the unit accurately tuned to the desired station, eliminating any tendency to drift.

A.G.C. Automatic gain control. A circuit which stabilises a large variation in the strength of an incoming signal.

A circuit function in a tuner or receiver which maintains the mean amplitude of the modulated signal at almost a constant level. A.G.C. or A.V.C. (Automatic volume control) as it is sometimes called is also used to describe the audio compression system employed in automatic tape recorders, in which the recording signal level is adjusted to compensate for widely differing sound levels.

ALIGNMENT PROTRACTOR. Indicates errors in a pickup's lateral alignment. It fits on the centre spindle of the turntable, and the pick-up stylus fits into a small hole on the device. The correct indication is shown when the angle of lateral movement of the pick-up head is at 90° to the tangent of the groove at any point, although minimal tracking error is expected with most pick-up arms.

AMBIENCE. The "feeling" given to sounds by a room. The effect of the environment on the coloration of sounds produced.

AMBIENT NOISE. Unwanted background noise picked up by a microphone, i.e. any extraneous

clatter in a room. Also any acoustic coloration that influences sounds, brought about by the acoustic properties of a room in which a recording is being made or replayed.

AMPLIFICATION. An increase in the magnitude of a signal brought about by passing it through an amplifier.

AMPLIFICATION FACTOR. The symbol used to signify this is " μ ". It is the measurement of amplification in a circuit usually in voltage or current terms calculated by dividing the output by the input. This figure is often converted to decibels (which see).


AMPLIFIER. A device for increasing the magnitude of a signal by means of a varying control voltage, maintaining the signal's characteristic form as closely as possible to the original.

AMPLITUDE. The level of an audio or other signal in voltage or current terms.

AMPLITUDE DISTORTION. The distortion of a signal by the undesirable influence of a circuit or component and takes place when there is a change of amplitude in part of the input signal bringing about harmonic distortion and inter-modulation distortion. This part is expressed as a percentage of the whole waveform at any given period of time.

AMPLITUDE MODULATION. Commonly known as a.m. and

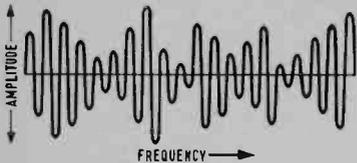refers to the method of radio transmission where the audio modulating signal is made to vary the amplitude of the radio carrier wave.



The audio information is carried on a high frequency radio wave.

ANECHOIC CHAMBER. A special room used for testing audio transducers, where all wall surfaces have been covered with acoustically absorbent materials so that reflections of the sound waves are eliminated. Otherwise known as a "dead room".

ANTI-PHASE. Where two identical signals are disposed in 180° phase opposition. When superimposed, they tend to cancel each other because their waveform patterns are of equal magnitude but opposite polarity.

ANTI-SKATING DEVICE. A device found on many modern pick-ups which provides an "outward" force on a pick-up arm. This counteracts the arm's tendency to move towards the turntable centre due to offset geometry, and reduces stylus/groove friction.

ANTISTATIC CLEANER. Substance used on gramophone records which helps to prevent the build-up of a static charge which attracts dust.

ATTENUATOR. A device which reduces the amplitude of a signal by known proportions.

AUDIO FREQUENCY SPECTRUM. Mainly the full range of sounds we can hear. In a person with good hearing the range of sounds in the audio spectrum is usually between 30Hz and 16,000Hz. In older people this is usually 50Hz to 10,000Hz.

AUDIO OUTPUT. The output signal from any audio equipment. It is generally measured in volts or watts r.m.s.

AUTO-CHANGER. A device on a record-playing turntable which facilitates the automatic positioning of a disc and pickup ready for playing.

AUX. Abbreviation of auxiliary. Often applied to amplifier inputs and refers to an extra input facility as distinct from "mic", "tuner", "pickup", etc.

AZIMUTH. The angle which recording and playback head gaps make with the line along which the tape moves. The head is oriented until this angle is 90°.

B

BAFFLE. The mounting for a loudspeaker usually comprising a flat non-resonant panel. It is used to increase the length of the path of the sound waves between the front and rear of the speaker to minimise bass losses.

BALANCE. Equality of amplifier gain or signal level from right and left channels of a stereo amplifier. In theory the balance between each channel should be electrically perfect but there may be mismatch of nominal signal level from one or other channel which is compensated by adjustment of the "balance control".

BALANCE CONTROL. A variable resistor used to compensate for any slight loss of signal in the right or left channel of a stereo amplifier. To some extent, this control can compensate for unbalanced speakers and be used for adjustment when the listener is not in an equidistant position between the two loudspeakers.

BANDWIDTH. The range of audio frequencies over which an amplifier or receiver will respond and provide a useful output.

BASS. The lower end of the sound spectrum (usually 150Hz and below). An amplifier "bass control" usually provides a variance of decrease or increase in response at frequencies below 1kHz.

BEL. A ratio of two signal levels, such as at the output and input, in logarithmic terms. It is too large a unit to use for precise measurement and we use tenths or "decibels". These are defined in power terms as $10 \log_{10} \frac{\text{output}}{\text{input}}$ or in voltage or

current terms as $20 \log_{10} \frac{\text{output}}{\text{input}}$.

BIAS. A high frequency signal applied to the audio signal at the tape recording head to make the audio signal magnetise the tape over the linear part of head's magnetic characteristic. The bias signal is usually above 40kHz to avoid audible intermodulation distortion. Bias is also a term used to denote the sideways thrust of a pickup arm.

BIAS COMPENSATOR. A device which counteracts the inward bias of a pick-up arm as it tracks the disc. The compensator exerts an outward force on the arm and generally can be adjusted to have a definite relationship to the playing-weight of the pick-up.

BI-RADIAL STYLUS. Also known as elliptical stylus. This is used with lightweight pick-up arms to reduce tracking distortion. The stylus tip has a small radius where it touches the walls of the record grooves as distinct from a conventional stylus which has a hemispherical tip.


BOTTOMING. A situation in which a stylus reaches the bottom of a record groove because its tip radius is smaller than optimum for the groove. Also the opposite of the pinch effect.

BULK ERASER. An instrument which erases recordings from a whole tape at once while it is still on the spool. It does this by producing an a.c. magnetic field of high intensity.

C

CAPSTAN. The drive spindle in a tape recorder, which in conjunction with the pinch-wheel, pulls the tape across the heads at constant speed.

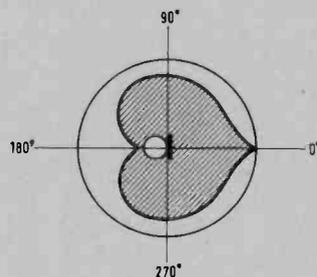CARDIOID MICROPHONE. A microphone which has a sensitive response to sounds on one side.



This makes the response very directional. It is called "cardioid" because it has a heart-shaped polar diagram.

CARTRIDGE. The electro-mechanical transducer of a pick-up head that converts stylus vibrations into an electrical signal. It is generally detachable and fits into the head-shell of a pick-up.

CERAMIC. Piezo-electric part of a pick-up, speaker or microphone that acts as a transducer. It has characteristics similar to a crystal transducer but is more robust.

CHANNEL SEPARATION. The degree to which the two signals in a stereo system are electrically isolated. Usually expressed as a ratio in decibels.

CLASS-A. An amplifier where the output transistors or valves are operating permanently on linear portions of their transfer characteristics. Efficiency is low, but a constant current is drawn from the power supply whatever the signal level. Usually recognised by the use of a single transistor or valve driving the loudspeaker.

CLASS-B. An amplifier where two transistors or valves operate on positive and negative half cycles of the signal wave form. Each operates from a low initial current but this rises as the signal level increases. Usually recognised by the use of two transistors or valves operating in anti-phase to drive the loudspeaker.

CLIPPING. Severe distortion caused by overloading the input of an amplifier. A sine wave signal waveform has a flat top and bottom at the peaks when clipping occurs.

COAXIAL CABLE. A screened cable where the inner conductor is surrounded by a concentric outer screen. Commonly known as "co-ax" the cable is carefully manufactured so that it has a constant characteristic r.f. impedance of 70-80Ω. It is used for aerial down-leads and for sending r.f. from one unit to another. Also used to inter-



connect audio stages or equipment of high impedance to minimise the risk of hum induction.

COLUMN SPEAKER. A loudspeaker cabinet of long "column" shape. Usually the loudspeaker is at one end so that the rear of the drive unit is loaded by a column of air. Often columns are made from drain-pipes. Also the name given to a long speaker cabinet containing several loudspeakers for public address work.

COMPARATOR. Often found in audio showrooms, it is a unit which by switch selection, will connect up a combination of speakers, amplifier, tuner, pick-up, tape player, etc. For comparing different types. Also the name of a circuit which compares two signals and provides a "difference" signal.

COMPATIBILITY. The ability of one unit to be used with another without detrimental effect on the signal through mismatch. A compatible pick-up will play both mono and stereo records.

COMPLIANCE. The ability of a stylus to respond to both horizontal and vertical movement. The degree of compliance is a measure of the

capability of the stylus to follow rapid variations in the groove surface.

COMPRESSION. This occurs when the dynamic range is reduced electronically so that quiet sounds are raised and loud sounds lowered. The most common application is an "automatic" recording where it is important that all sounds recorded are made intelligible when played back. Also used where necessary to avoid over recording and distortion, or to lift the signal level clear of background noise or hum.

CONDENSER MICROPHONE. A microphone which contains a metal plate and a thin metal diaphragm set close together. A polarising voltage is applied to the plates. The capacitance of the microphone is thus affected by movement of the diaphragm from air pressure waves.

CONTROL UNIT. A pre-amplifier unit in an audio set-up. Signals from audio sources, i.e. tuner, pick-up microphone, are fed into it. Equalisation (where necessary) is applied, then the signal is fed to the main amplifier. Volume and tone controls are usually incorporated together with any necessary programme selection switch.

COUNTERBALANCE. Counterbalance is a weight, usually adjustable, fitted at the pivot end of a pickup arm. It counters the weight of the pickup head and cartridge unit and allows adjustment of the stylus pressure to the desired value.

CROSSOVER NETWORK. A circuit usually employing capacitors and coils which feeds low notes to a low frequency speaker (woofer) and high notes to a high frequency speaker (tweeter). The crossover frequency is that at which frequency bands divide. Sometimes the audio spectrum is divided into more than two bands to drive more than two speakers.

CROSSTALK. Breakthrough of the signal from one channel to another by conduction or radiation.

CUT-OFF FREQUENCY. The frequency response limitation, either upper or lower end, of a given component or piece of apparatus where the response falls off by 3dB, then is even lower beyond this frequency.

D

DAMPING FACTOR. The ratio of the impedance of a speaker to the amplifier impedance. A high damping factor is desirable to

subdue speaker resonances.

DECIBEL. One tenth of a Bel (which see).


DE-EMPHASIS. Reduction of the level of the higher audio frequencies during f.m. reception or tape replay, so that they compensate for the pre-emphasis (which see) applied to the transmission. This restores an overall uniform response, with improved signal-to-noise ratio.

DEMAGNETISER. A device which removes residual magnetism from tape heads. This magnetism, if not removed can introduce noise on recordings and cause high frequency loss.

DEVIATION. In f.m. transmissions and reception deviation is the increase or decrease of signal carrier frequency from the nominal; also applied to drifting. Standard maximum deviation rating is ± 75 kHz for f.m. radio.

DIN. Stands for Deutsche Industrie Normenausschuss. This is an organisation in West Germany (similar to the British Standards Institution) which sets certain industrial standards.

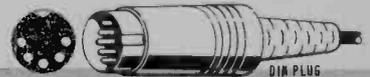A well-known standard is the DIN 45,500 which applies to domestic hi-fi equipment. Various plugs and sockets are popularly known



as "DIN plugs". They have DIN standard geometry and connections.


DIPOLE. An aerial generally used for v.h.f. receivers.

DNL. Dynamic noise limiter. A compatible circuit designed by Philips Ltd. primarily for use with tape recorders. It improves the effective signal-to-noise ratio during replay by selective filtering at low signal levels.

DOLBY SYSTEM. A noise reduction system which compresses signals before they are recorded on tape and expands them again on replay. This results in a reduction of background noise and is particularly designed for use with tape recorders.

DRIFT. Variation of r.f. signal carrier frequency above and below the nominal due to unstable reception conditions. It can be alleviated to a great extent by applying automatic frequency control.

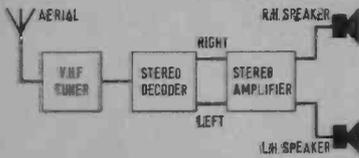DECODER. A circuit built into an f.m. tuner to enable it to translate stereo signal information into two matched stereo audio outputs. Also a



means to extract and process recorded quadrasonic sound information from a complex signal into four matched outputs.


DISTORTION. Unwanted changes in the purity of sound being reproduced or in r.f. signals. In audio it generally implies intermodulation and/or harmonic distortion. These are derived from phase differences and/or amplitude distortion where the amplitude of the output does not bear the same proportion to the input at all frequencies.

DROP-OUT. Sudden decrease in the recorded signal level due to tape imperfections.

DYNAMIC RANGE. The range of signal amplitudes from the loudest to the quietest that can be reproduced effectively by the equipment. The upper limit is set by inherent distortion level, and the lower limit by background noise and/or hum.

E EARTH LOOP

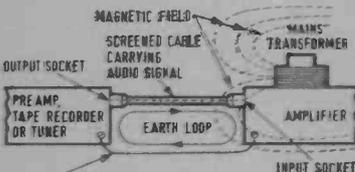The wiring of the interconnections between items of audio or radio equipment such that there is more than one return path for the "ground" side of the signal-carrying



loop is caused by this earth connection between the two chassis as well as by the screen of the signal cable.

wiring. This generally results in a loud hum from the speakers.

ELECTROSTATIC. Applied to loudspeakers and microphones (condenser type). An electrostatic force is used to activate the diaphragm. The charged diaphragm is suspended between two perforated plates. As an a.c. signal is applied to the outer plates, the diaphragm vibrates.

EQUALISATION. A pre-arranged circuit that applies correction to a given recording characteristic dur-

ing replay to result in a uniform frequency response at the output terminals.

ERASE HEAD. A head on a tape recorder which applies a strong high frequency alternating magnetic field to the tape so that earlier recordings may be "erased" as the tape runs past the head.


**F
FADING.** A drift in the level of received radio signals beyond intelligibility. It is often caused by changes in the upper atmosphere. Also applied to deliberate slow reduction of signal level by means of the volume control.

FEEDBACK. A system where part of the output signal from an amplifier is applied to the input. When in antiphase (i.e. negative feedback) this results in reduction of distortion, lowering of the amplifier output impedance, improvement in signal stability.

F.E.T. Field Effect Transistor often used in early stages of an amplifier or tuner to give a high input impedance for minimum loading of the programme source, i.e. aerial or pick-up.

FLUTTER. Rapid variations of pitch or frequency caused by inconsistent speed of a turntable or tape transport mechanism.

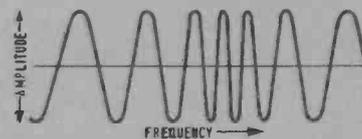F.M. Frequency modulation is a system of transmitting a radio signal where the frequency of the carrier wave is altered by changes in the amplitude of speech or music.



F.M. is applied to v.h.f. sound broadcasting above 87MHz.

FREQUENCY. The number of complete cycles in one second of alternating current, voltage, electromagnetic or sound pressure waves.

FREQUENCY RESPONSE. A graphical characteristic showing relative signal levels at different frequencies with respect to a given reference level. A "flat" frequency response is one that has a uniform level at all frequencies within a given band width.

FRONT END. Refers to the first stage of an amplifier or tuner.

**G
GAIN.** The increase in the power or voltage level of a signal due to amplification, i.e. the ratio that

exists between the output signal level and the input signal level, usually quoted in decibels (which see).

GROOVE. A record "track" which carries the audio signal information in two 45° displacements (stereo). In a long-playing record, groove dimensions could be: width 2.5 mils.; depth 1 mil. and pitch 250-350 groove revolutions per inch.

**H
HARMONIC.** A harmonic of a fundamental frequency is the frequency of its exact multiple. Thus twice the fundamental frequency is the second harmonic (one octave up) and so on. If the fundamental frequency is 1,000Hz, the second harmonic would be 2kHz, the third 3kHz, and the fourth harmonic 4kHz (two octaves up from the fundamental).

**I
IMPEDANCE.** Opposition to a.c. current presented by capacitors, inductors and resistors. This effect is measured in ohms and is related to frequency.

INFINITE Baffle. A loudspeaker mounting where ideally there is no path of air between the back and front of the speaker diaphragm. An infinite baffle improves the forward radiation of sound at low frequencies and preferably should be a very large plane surface like the wall of a room or a screen of very rigid material (e.g. 2in wood) on which a loudspeaker is mounted. In practice truly infinite baffles are rarely accomplished except in sealed boxes, but these give rise to problems of resonance.

I.P.S. Inches per second. Used for signifying the speed of a tape travelling past the heads of a tape recorder. The most common speeds used in this country are 1 7/8 i.p.s. (4.75cm/s); 3 3/4 i.p.s. (9.5cm/s) and 7 1/2 i.p.s. (19cm/s).

**J
JACK.** A type of two-or more-ways concentric contact socket for carrying audio signals.

JOHNSON NOISE. A frying or sizzling sound produced by thermal agitation voltages generated in amplifier circuits. It usually occurs

in the input circuit (or front end) of an amplifier.

L


LEVEL. The voltage or power of a signal, or the relative voltage or power compared with a reference.

LIMITER. A circuit in an amplifier or tape recorder which reduces volume when over-modulation or distortion is likely to occur.

LINE SOURCE SPEAKERS. A chain of speakers used in public address work that are driven from an amplifier with 100V or 600ohm output line.

LOUDNESS. The intensity of a sound as subjectively judged by the human ear. Loudness levels are measured in "phons" and may differ in effect from one person to another.

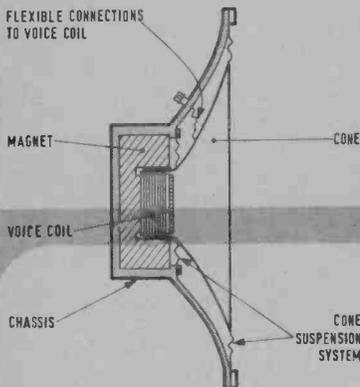LOUDSPEAKERS. A transducer which converts a.c. electrical energy into acoustic energy by movement



of the diaphragm causing air pressure waves.

M

MAGNETIC PICK-UP. A pick-up which employs an electro-magnetic transducer. An armature bears the stylus. The armature is pivoted between the poles of a magnet and stylus movement makes the magnetic field change, inducing a variable voltage in coils wound on the magnet.

The name refers to pick-ups of the moving coil type, moving magnet, moving iron, induced magnet and variable reluctance types.

MATCHING. Equalisation of the input impedance of one unit to the output impedance of another connected to it. Also used to refer to pairs of loudspeakers, microphones or other components which have similar characteristics and which are employed in the two channels of a stereo system.

MICROPHONE. An electro-acoustic transducer which converts sound energy into electrical energy. The method depends on the material used in the microphone.

MIXER. A device which combines two or more separate signals into a common output.

MODULATION. The process whereby an r.f. or other signal is mixed with and caused to vary in accordance with an audio signal. The degree to which a tape or disc recorder is made to record without introducing distortion.

MONITORING. Listening to a signal as it is being recorded so that a check can be made on the quality.

MONOPHONIC. The reproduction of sound through a single channel amplifier.

MUSIQUE CONCRETE. A musical work comprising natural sounds which are recorded, then edited or manipulated and treated so that they do not sound like the original recording, but present an artificial form of musical composition.

MULTIPLEX TRANSMISSION. The transmission of two or more simultaneous signals on a common carrier wave. Used for transmitting stereo broadcasts. A multiplex decoder is needed before these transmissions can be resolved into stereo or other multiple channel audio.

N

NEGATIVE FEEDBACK—See "Feedback".

NOISE. Unwanted sounds of multiple and irregular frequencies and heard as a hiss or click.

O

OFFSET ANGLE. The angle at which the pick-up head is offset from a line through the centre of the arm. Correctly set, it minimises wear on stylus and record groove, and distortion of reproduction by keeping the tracking error down to a minimum.

OMNIDIRECTIONAL. Generally refers to a microphone which has approximately uniform sensitivity in all directions, the polar response being completely spherical.

OVERLOADING. An amplifier or piece of equipment operated beyond its signal-handling capability so as to create a distorted output.

OUTPUT STAGE. A power amplifier's final stage which feeds

the audio signal to a loudspeaker or other device.

P

PARALLEL TRACKING. A pickup cartridge's movement which is exactly parallel to the radius of the record, with the stylus always positioned on that radius for zero lateral tracking error.

PEAK PROGRAMME METER. A meter and associated circuitry which is used for indicating the peak levels of programme volume. Commonly referred to as P.P.M.

PHASE. Phase is the angular relationship in time of an alternating voltage or current with reference to zero voltage (or current) or another comparative waveform. Sound waves are said to be in phase when the voltage of one at any instant is the same polarity and angular displacement as the other and when crossing the zero voltage line in the same direction. "In-phase" sound-waves are identical in frequency and polarity at any instant; out-of-phase, waves may be identical in frequency (but not necessarily) and of opposite polarity at some instant. Anti-phase waves are identical in frequency and exactly opposite in polarity, i.e. 180° out of phase.

PHASING. The arrangement of loudspeaker or connections in a stereo set-up so that when an identical signal is fed to the two speakers, the speech coils are so connected that the cones both move in the same direction at the same time.

PHON. A unit of measurement of loudness allowing for the difference in sensitivity of the ear at differing frequencies. The phon is related to the decibel, but is in terms related to one frequency and determined from sound pressure measurements.

PHONO PLUG. A connecting plug often used in audio equipment. It has a centre "live" pin and an outer "earth" shield. Used with



screened cable for connecting pickups and tuners to an amplifier or control unit.

PICK-UP. The part of a gramophone which extracts recorded information from a disc and

changes it to an electrical signal.

PICKUP ARM. The cantilever support for the pickup head with counterbalance weights, pivots etc. for carrying the cartridge.

PICKUP HEAD. The end of the pickup arm containing the cartridge. It is often removable from the arm and is usually called the "head shell" which carries the actual cartridge.

PIEZO ELECTRIC. An effect whereby a substance generates an electrical current when it is subjected to mechanical stress. This characteristic has been made use of in the design of pickups, microphones and loudspeakers.

PILOT TONE. A 19kHz tone used in stereo broadcasting at the equivalent of 10% f.m. modulation ± 7.5 kHz. It is transmitted with the sum-and-difference signals to assist in the stereo decoding process in the f.m. receiver.

PINCH EFFECT. The vertical movement of a stylus which takes place during record reproduction when irregularities in groove width occur.

PINCH WHEEL. The rubberised wheel in a tape transport mechanism that holds the tape against the capstan so as to ensure that the tape does not slip.

PITCH. The pitch of a sound is the musical term for sound vibrations. Standard U.S. and European pitch is based on $=440$ Hz. When the pitch is raised one octave, the frequency is twice the original.

PLAYBACK. The reproduction of a tape recording or disc through an amplifier and loudspeaker or phones.

PLAYING WEIGHT. Downward force of a pickup on a record. Sometimes called stylus pressure.

POLAR RESPONSE. Polar diagram or circular graph which shows the sensitivity of an aerial or microphone or the output from loudspeakers in an angular mode through 360° .

POLYESTER BASE. A base material used for magnetic tape on which is coated the magnetically sensitive substance. Widely used for long playing tape, it is less prone to stretching than acetate film.

POWER. The energy dissipated in an electrical or electronic circuit or component that is conducting either a.c. or d.c.

POWER AMPLIFIER. The stage of an amplifier which supplies audio signals to a loudspeaker or phones.

POWER-HANDLING CAPACITY. The maximum power rating of a loudspeaker or other

component which determines how much current can be passed safely through without adverse effects.

PRE-AMPLIFIER. An amplifying system for low signal levels. It boosts a low-level signal from a cartridge, for instance, and feeds the signal to a power amplifier. It may contain additional circuitry that affects the frequency response in some way.

PRE-EMPHASIS. The boosting of high frequencies in f.m. broadcasting or recording. Uniform frequency response is restored by "de-emphasis" in the receiver or replay amplifier. The purpose is to reduce the noise level that arises through transmission and tape recording.


PRESSURE PAD. A felt pad which applies a gentle but firm force to keep a moving tape in good contact with the heads of a tape recorder.

PRESSURE UNIT. A moving-coil speaker drive unit which usually has as its diaphragm a small dome of plastic or metal. It is designed for use in the throat of a horn.

Q

QUADRATURE. Two a.c. signals of equal-frequency are said to be in quadrature when they are phase displaced by 90° .

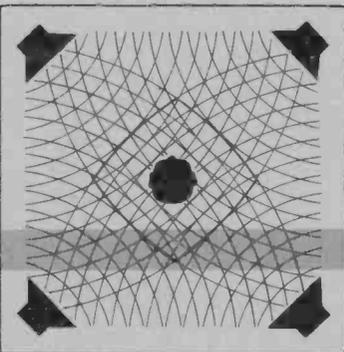QUADRAPHONY. Four matched discrete audio channels are employed in true quadraphony; four matched microphones are used in the recording process, four-track tape or "quad" records are used for replay through a four-channel amplifier which feeds four loudspeakers.



Various modulation or matrix systems are sometimes used so that four channels can be obtained by using some two-channel (stereo) equipment. The signals are then "decoded" so that four channels of sound can be reproduced through four speakers.

Systems known as "surround sound" are used to produce "synthetic" quadraphonic effects. These units use matrix circuits in conjunction with conventional stereo equipment and records.

QUADRUPLE PLAY. Magnetic recording tape which is thinner than "standard play" tape and consequently enables one to make recordings four times longer than with 'SP' tape.

Q4. The name given to the Practical Wireless quadraphonic decoder to enable quadraphony to be reproduced from stereo or quadraphonic recordings.

R

RADIO FREQUENCY. A term describing incoming radio signals to a receiver or outgoing signals from a radio transmitter. There are no finite limits in the r.f. range but it is usually considered to denote frequency above 150kHz and extending up to the infra-red range.

RAKE. The "rake" angle of a stylus is the angle that the stylus bar makes with a gramophone record when viewed from the side.

RANDOM NOISE. Noise generated in a circuit by random movement of electrons caused by thermal agitation. In tape recording it can be caused by uneven distribution of magnetised particles and is reproduced as a background "hiss".

REAR SUSPENSION. Used in moving-coil loudspeakers, it is a pliable support situated near the apex of the cone, and assists in keeping the coil in a concentric position in the air gap between the magnet poles.


REFLECTOR. An element in a v.h.f. aerial which is situated to the rear of the main dipole. It helps to reflect radio waves on to the dipole. Also the name given to the "dish" often employed to reflect quiet or distant sounds in the open air on to a microphone.

REFLEX CABINET. A type of speaker enclosure fitted with a vent or port through which out-of-phase signals from the rear of the cone are "reflexed" by allowing the enclosed air in the cabinet to be tuned for a coupled resonance effect with the cone of the drive unit. The signals are then brought into phase with the front radiation from the cone of the speaker so as to reduce the "boomy" effect of resonance.

REJECTOR. Filter or part of a circuit which rejects a particular frequency or band of frequencies.

RESONANCE. The nature and dimensions of any object or enclosed volume of air will vibrate at a calculable frequency when disturbed by striking. This frequency is said to be the resonant frequency. When the object is made to vibrate at this frequency by a corresponding sound pressure wave the resonance is enhanced, producing a "boomy" effect, i.e. the volume at that frequency is apparently louder than at any other.

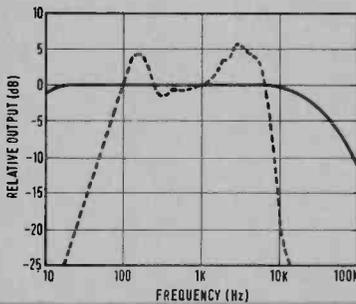RESPONSE CURVES. Usually measured in decibels, with reference a given level, on a vertical scale, the response curve is a graphical representation of frequency response.



When the response curve of an amplifier, pick-up, microphone, etc. is accurately plotted it represents the relative levels of amplitude at all frequencies within a specified bandwidth.

REVERBERATION. Reflected sound. It is produced by the gradual decay of sounds being reflected from ceilings, walls, floors and furniture.

Reverberation units create an artificial representation of the decay of the sounds electronically.

RIBBON MICROPHONE/SPEAKER. Uses a narrow corrugated aluminium alloy strip suspended in a magnetic field. Sound makes the strip vibrate in a direction perpendicular to the magnetic field, resulting in an a.c. current being induced in a coil.

The natural response of a ribbon unit is bi-directional and a ribbon microphone has certain areas of minimum sensitivity. Only a very small response is produced by quite loud noises from the sides, the polar diagram for this type is known as "figure of eight".

A few ribbon microphones will give cardioid and hypercardioid responses.

RMS VALUE. The "root-mean-square" value of a.c. voltage, cur-

rent, or power is calculated as 0.707 of peak amplitude at the given frequency. It represents for mathematical purposes an acceptable level by which relationships between these units can be accurately established.

RUMBLE. Low frequency noise produced by the turntable bearings and motor of a record player, and transmitted mechanically by vibrating the pick-up. These vibrations are then detected by the transducer in the cartridge for conversion into an electrical signal.

RUN-IN. The start of a groove at the beginning of a side of a gramophone record which "runs in" to the recorded section.

S

SCRATCH FILTER. A low-pass filter, often an integral part of an amplifier circuit, which attenuates the higher frequency noise derived from disc recordings. The scratch filter is also suitable for the suppression of background noise produced by tape background hiss.

SCREENED LEAD. A cable which has an outer sheath of braiding which provides electrostatic screening of the inner conductor and so makes it ideal for connecting high impedance pick-ups, microphones and tuners to the input of an amplifier. Its purpose is to reduce the effects of hum caused by radiation from a.c.-carrying wiring or components.

SELECTIVITY. A tuner's ability to discriminate between a wanted signal and an interfering signal on adjacent frequency settings of the tuning dial.

SENSITIVITY. The ability of any communications equipment, including audio to reproduce very low signals.

SEPARATION. The degree to which right and left stereo signals are isolated in pickup or stereo amplifier.

SHELL. Refers to that part of the pick-up which carries the cartridge. The head shell can often be detached from the pick-up arm.

SIBILANCE. The strong emphasis in pronunciation of the letters "S" and "SH" in speech. It can be exaggerated by microphones having peaks in their high frequency response.

SIDE-THRUST. The tendency of the stylus to "skate" towards the centre of a record causing increased wear on the inner groove wall. With low tracking weight, side thrust can cause the stylus to "jump" the record's groove.


SIGNAL-TO-NOISE RATIO.

The difference, measured in decibels, between a specified signal reference level and the level of unwanted noise. The higher the ratio, the better the equipment.

SINE WAVE. A waveform (often viewed on an oscilloscope) of a pure alternating current or voltage. It is drawn on a graph of amplitude versus time or radial degrees and follows the rules of sine and cosine values in relation to angular rotation of an alternator. It can be simulated by means of an electronic oscillator.

SOLID-STATE. A general term that applies to any semiconductor device such as transistors, diodes, an integrated circuit. Can also be used to describe equipment that employs miniaturised modules or building blocks, integrated circuits or micro-circuits.

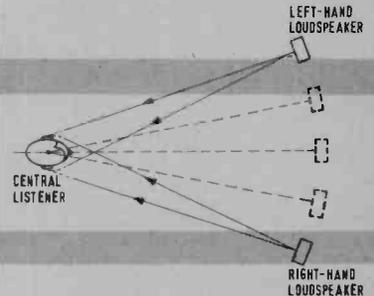SOUND STAGE. The area between the two or more loudspeakers of a stereo or quad set-up where subjective sound images or imagin-



ary loudspeakers seem to be, providing a wide area of apparent sound source.

SPEECH COIL. The moving coil in a dynamic loudspeaker. It is suspended in the field of a permanent magnet and is fixed to the speaker diaphragm.

SPLICE. A joint in a length of magnetic tape. For a good strong splice, the two ends of tape should be cut at an angle of 45° so that they butt together in line without any gaps.

SQUARE WAVE. An a.c. periodic waveform in which voltage alternates rapidly from a positive peak value to the negative peak value, and vice versa after a delay.

A waveform with these characteristics is ideal for testing audio equipment with an oscilloscope to test for good transient and frequency response. Square waves are also used in switching circuits.

STANDARD PLAY. An arbitrary description given to identify a spool of thick recording tape with a specified playing time according to reel size. For example, a 7in. spool will hold 1,200ft of "standard play" tape a 5in. spool 600ft. The actual playing time is then dependent on tape speed.

STANDING WAVES. The behaviour of air pressure waves in an enclosed room or box, giving rise to resonances which occur. They are created by the effects of multiple sound reflections between opposite walls and cycle at frequencies determined by the distance between them. In effect, the room acts as a resonator.

STEREOPHONY. A two channel recording and reproduction system more popularly referred to as "stereo". At the recording studio separate microphones are used for each recorded channel. The correct reproduction of stereo signals in the home gives to the listener a sense of direction of sound and thus enhances the realism.

STYLUS. A small piece of industrial grade diamond or artificial sapphire, conically-shaped, which tracks the groove in a gramophone record.



STYLUS ARM/BAR. Cantilever which carries the pickup stylus. It is suspended at one end so that it can be allowed to vibrate in a magnetic field or transmit mechanical stresses through a piece of piezo-electric material.

SUPERIMPOSE. To record one or more signals over another without erasure, so that when a tape is played back, all recordings can be heard simultaneously. This is particularly useful if one wishes to have a spoken commentary with a musical background.

SURFACE NOISE. Noise generated by contact of a gramophone stylus with minute particles of dust or other irregularities in a record groove. Can also be caused by excessive wear of a disc or by poor quality coating on recording tape.

TANGENT. A straight line that meets a curve or circumference at

one point only, such that it is at 90° to the radial line between the centre of the circle and that point. A tangential pick-up arm is one that maintains this condition throughout its tracking across a disc.

TAPE DECK. The mechanical part of a tape recorder. It comprises the complete tape transport system, motors and drive mechanisms. It may also include the heads.


TAPE HEAD. The transducer on a tape recorder past which the tape runs during record or replay. It applies a magnetic field to the tape during the recording process and provides electrical output during replay.

T.P. Triple-play tape. Very thin recording tape of which it is possible to wind 3,600ft. onto a 7in. spool. This would give 180 minutes of playing time at 3 $\frac{3}{4}$ i.p.s.

TRACING. The ability of a stylus to follow the variations or modulation pattern of a record groove.

TRACKING. The movement of the record player stylus across a gramophone record.

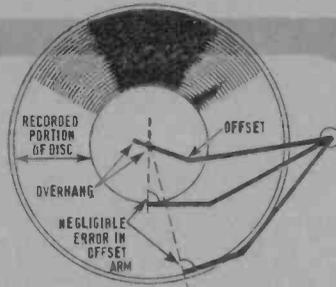TRACKING ERROR. The deviation of angle between the stylus bar axis and the radial line between the disc centre and stylus point.



This is a factor applied to pickup arms with offset angle heads.

TRACKING WEIGHT. The downward force of a pick-up stylus which ensures optimum reproduction of recorded groove modulation with minimum wear of groove wall and stylus.

TRANSCRIPTION. Word commonly used to describe high quality pick-up and turntable units. Literally it is a copy or a recording of an audio programme onto tape or disc.

TRANSIENT RESPONSE. The ability of an amplifier or transducer to handle and faithfully reproduce rapid changes in signal amplitude. A very short "rise-time" is a measure of this characteristic.

TREBLE. The high frequency end of the audio spectrum.

TWEETER. A loudspeaker de-

signed specially for reproducing high frequencies. It is used in conjunction with a "woofer" (bass speaker) and a crossover unit for audio reproduction.

VARIABLE RELUCTANCE. Principle employed in certain pick-ups. Deflections of the stylus when playing a record, make an armature vibrate between the poles of an electromagnet. The reluctance is the ratio of magnetic force to magnetic flux in a magnetic field. Variations due to stylus movement create variations in the current through the electromagnet.

VERTICAL TRACKING. Stylus motion path which is near "vertical". Applies to "hill-and-dale" recordings on stereo discs.

V.H.F. Very high frequency radio band. Broadcast v.h.f. Band 2 is the 87 to 108MHz range. Also applies to frequencies above 30MHz for radio or television.

WAFER SPEAKER. Thin compact loudspeaker with an "inverted" cone where the magnet is sited forward of the cone.

WATT. Unit of electrical power, often used to signify the signal power output from an amplifier.

WAVEFORM. A graphical representation of the relationship between voltage, current or power against time. It also provides a picture of the behaviour of signals at given frequencies.

WHITE NOISE. The random motion of electrons in a conductor which, when reproduced through a loudspeaker or phones, sounds like noise and covers a wide frequency range. It is used to test loudspeakers and phones for resonance and sensitivity.

WOOFER. A low-frequency or bass loudspeaker for reproducing musical notes in the approximate range of 25-2,500Hz. Employed with a "tweeter" and crossover network to reproduce a range of frequencies for audio reproduction.

WOW. Slow regular variations in the speed of a record turntable or tape transport mechanism. It is heard through a loudspeaker system as a wavering of musical pitch. ■

EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

LEARNING BY PRACTICAL PROJECT STEPS

PART 2—THE BISTABLE

WE are going to look at a very fundamental switching circuit this month that is based on the principles we developed in the last part. It is called the *bistable switch*—the reason for this name should become clearer as its story progresses. If you look at the basic circuit in Fig. 9a you will notice a marked similarity to the experiments we did last month; two transistors are cross connected—the base current for each being drawn from the collector circuit of the other. Notice, however, that both base resistors (R2 and R3) are permanently connected in and we are not using switches this time!

Basic assumptions

For those who like to sweat over puzzles try this one before reading on. Assuming that the circuit is completely wired up and power is supplied use your knowledge regarding base current and driving voltages to work out whether Tr1 and Tr2 are conducting or not conducting!

Unless you have made an assumption you should be completely stuck because the system does not seem to make sense. In stages you could have said that when power is not applied both transistors must be non-conducting hence at the instant you apply power both points A and B will be at +9V. This set of circumstances, however, provides base current for the opposite transistor and the effect of this is to make each transistor go into conduction and *both* the respective voltages will fall cutting off the base current; the result of this would be to make both collectors rise back to +9V and we are again at the start point of a vicious circle! To arrive at a sensible result we must make a practical assumption—that there is bound to be a slight difference in the current gains of the two transistors used and the one that has the higher value will go more rapidly into conduction when power is applied. Let us assume Tr1 has a nominally higher current gain than Tr2.

When power is applied Tr1 will draw base current from point B through R3 and the voltage at A will fall rapidly—cutting off the supply of base current to

Tr2. The latter therefore will *not* go into conduction and the voltage at B will stay at +9V while that at A will fall to nearly zero. Try this with your experimental circuit making and breaking the power line and you should find that it is always the same transistor that goes into conduction—in your case, of course, it might be Tr2.

Anyway we shall carry on with our assumption that after switch on point A is at zero volts and we have—after all—a stable state. Let's assume

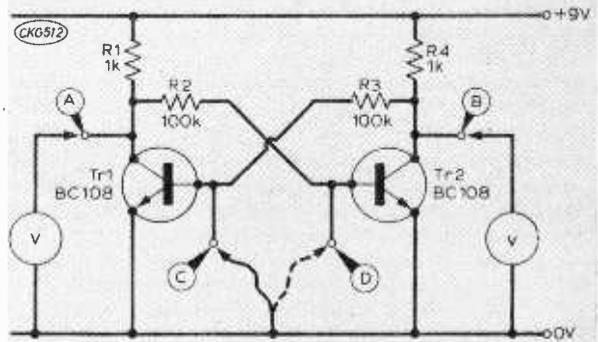


Fig. 9a: A conventional bistable circuit.

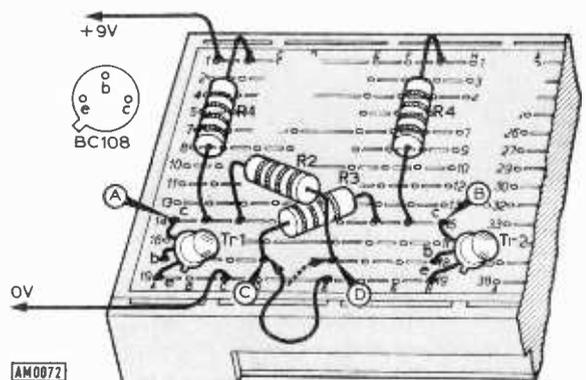


Fig. 9b: T-Dec layout for Fig. 9a.

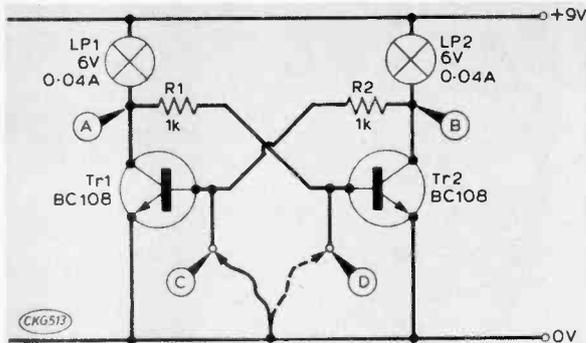


Fig. 10a: A bistable with components modified to drive lamps direct.

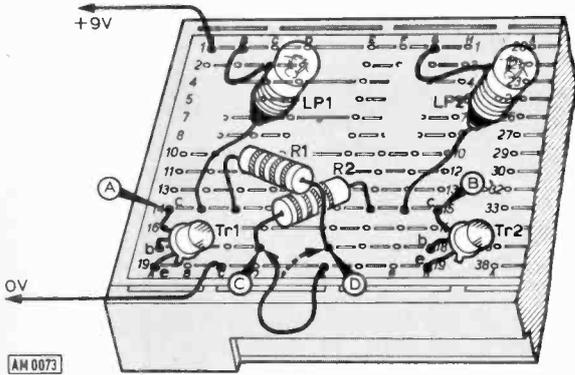


Fig. 10b: T-Dec layout for Fig. 10a.

that we really wanted point B to go to zero volts. For this to happen we must, somehow, make base current flow into Tr2. To do this we must make the voltage at A rise to +9V by momentarily removing Tr1's supply of base current—conveniently done by shorting point C to ground. Do just that and watch the voltage at B as you make the short. Sure enough, it falls to zero while you make the short, but notice that when you have removed the shorting link from C point B stays at zero volts—not only that, but A is now at +9V and the system is again stable. You can make the circuit revert to its original state by momentarily shorting point D to ground. The circuit has two possible stable states (hence its name) and we can make it go into either of them by externally tampering with the base current supplies.

Alternative loads

The rules of current gain apply in this circuit without undue complication and taking into account the normal current limitations of transistors you can use collector loads other than pure resistors. Fig. 10a is an identical circuit in which lamps are used; the cross coupling resistors have to be of lower values to ensure that enough base current flows to control the larger load. Alternatively connect the flying lead to points C and D and you will see that you can make LP1 go on—and stay on—when point D is quickly shorted to ground and similarly with LP2 and point C.

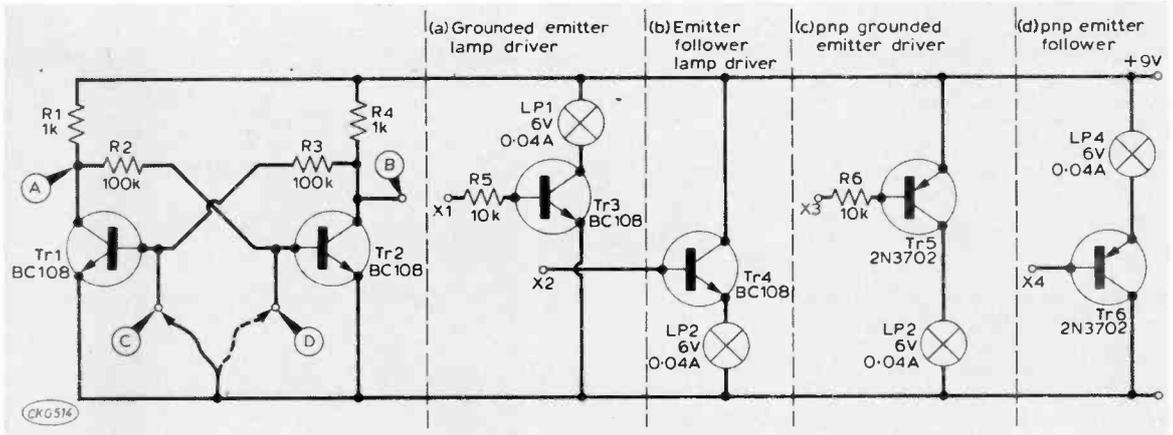


Fig. 11a: Alternative ways of driving low voltage lamps from a bistable. Low voltage relays (requiring less than 100mA) can be substituted for the lamps provided protection diodes are inserted (see part 1, last month).

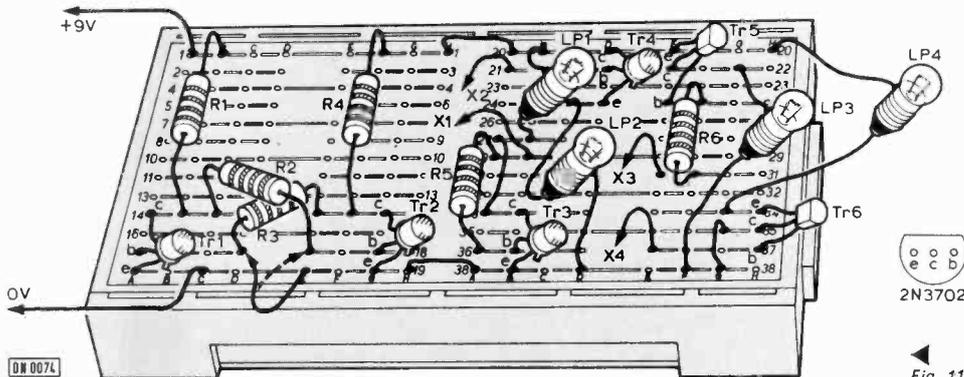


Fig. 11b: T-Dec layout for Fig. 11a.

If you wish to you can use the voltage swings at the collectors of the bistable transistors to drive other circuits. A selection of lamp driver stages (with inputs marked X1, 2, 3 and 4) can be connected to either points A or B. (We shall assume they are connected to B.) Take driver (a) which is a simple grounded emitter inverter stage. When point B is +9V Tr3 can draw base current through R5 and the lamp will light. Notice that we have to put a 10kΩ resistor in to prevent the base emitter circuit of Tr3 pulling the voltage at B down to +600mV; if that were to happen the action of the bistable would be interfered with.

Circuit (b) is a simple form of emitter follower and in this case we can do away with the 10kΩ resistor. The reason for this is that when point B goes "high" we immediately pass base current into Tr4 and it starts to conduct, but when this happens the voltage at its emitter rises as current flows through the lamp. The voltage rises to a value 600mV less than the voltage at B; the difference in voltage is due to the standard base emitter forward voltage drop associated with silicon transistors. If, say, point B went to +9V we would end up with approximately 8.4V across the bulb. The only drawback of this circuit—although it does not bother us in this application—is that we will always lose 600mV of driving voltage across the bulb and it will not glow quite so brightly.

In both these two drivers the lamp went on when point B went to +9V. The remaining two drivers use pnp transistors in grounded emitter and emitter follower configurations and because they are sensitive to opposite polarity signals the lamp goes off when point B goes high. In circuits it is often useful to make use of opposite polarity transistors to get this type of inversion. It is not very impressive in this application because if we had wanted any inversion we could have used point A as the driving source.

Dividing

An interesting development of the bistable circuit is the *divider* shown in Fig. 12a. The basic circuit of Fig. 9a is still there and you can ignore Tr3 because it is only a lamp driver. We have added a couple of diodes and capacitors and a few more resistors. The object of the circuit is to make Tr1 and Tr2 take up their alternative stable states each time we make a single short circuit path to ground (we shall be shorting point G to ground as a signal).

Let's assume that point A is at +9V (B will be zero and so will C, and D will be at approximately +600mV). The voltage at A effectively reverse biases D1, and D2 is just on the edge of conduction through R6 to point B—which is just slightly more

Fig. 12a: A bistable with built in gating so that it switches in alternate directions each time point G is connected to ground. This is sometimes called a divider.

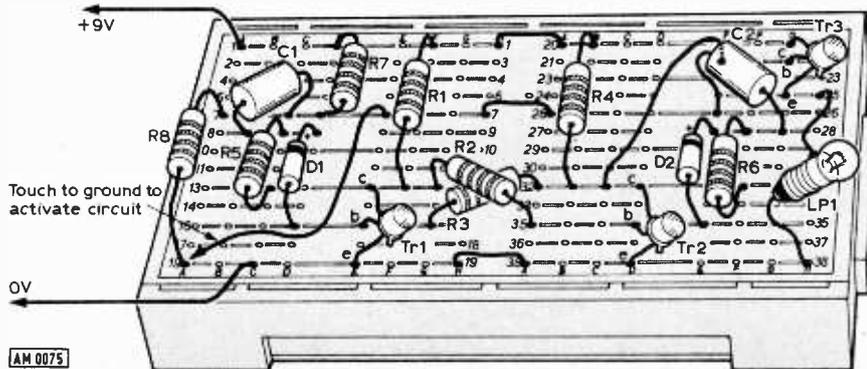
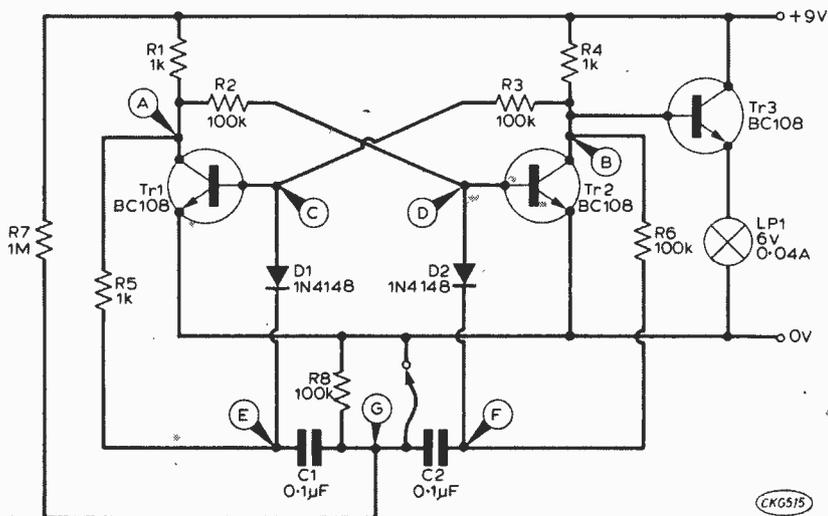


Fig. 12b: T-Dec layout for Fig. 12a.

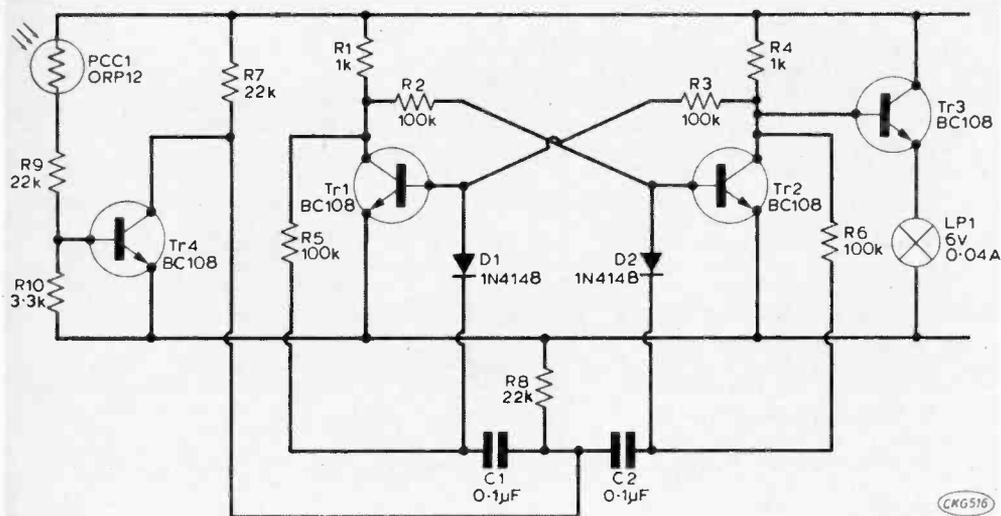


Fig. 13a: With the addition of a few more components, the divider can be made to "toggle" whenever bright light falls on the photoconductive cell.

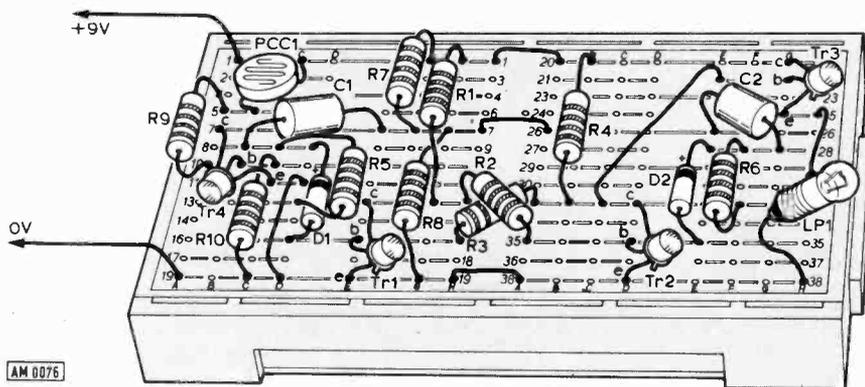


Fig. 13b: T-Dec layout for Fig. 13a

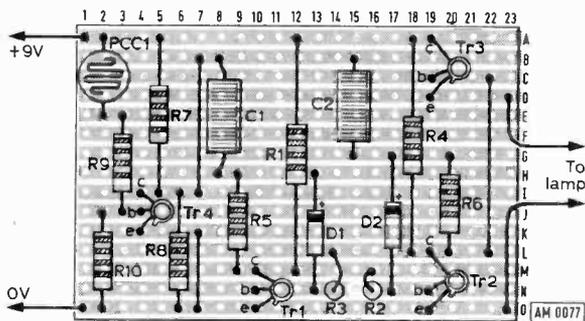


Fig. 13c: Veroboard layout for Fig. 13a.

negative than D. The potential at G (without the shorting link made) will be just under 1V because of the potential divide action of R7 and R8.

By repeated dabbing of the shorting link to ground you can make the lamp go on and off alternatively. There is something that you have to note, however. The circuit is very sensitive and you must make very good clean makes and breaks of the shorting operation; it is very easy to accidentally give a double "pulse" when you think you have, in fact, only made one. R7 has deliberately been made a high value to allow time for the voltage at G to recover and this

helps to eliminate what appears to be erratic action. Nevertheless the time constant of 1MΩ with the 0.1μF capacitors is still quite short so do not be too surprised if sometimes the lamp appears not to respond. What actually happens is that the lamp switches on and back to off so quickly you do not see it happen! Try reducing R7 to 100kΩ and R8 to 10kΩ and you will deliberately aggravate the problem. In a circuit of this nature it is wiser to use some form of non-mechanical switch to do the triggering so that we lose the "bounce" problem.

When you short point G to ground there will be a change in voltage at point E by about 0.8V in a negative direction but because D1 is reverse biased there will be little effect on the base circuit of Tr1. On the other hand the similar drop developed at point F will put D2 into sufficient conduction to momentarily drop the voltage at D and hence remove the base current from Tr2. The voltage at B will rise and bistable action will take place and the voltage at A will fall as the circuit takes up its other stable state. The set of circumstances is now reversed and if the shortening link is removed to allow the two capacitors to regain their original equilibrium the operation can be repeated to make the circuit flip back to its first stable state.

—continued on page 645

—continued from page 644

Fig. 13a shows a very crude electronic form of trigger for the divider. A sudden transition of from near darkness to full room light on PCC1 will make Tr4 go suddenly into conduction and the voltage at the junction of C1 and C2 will fall rapidly to zero—stimulating the divider. Switch off the room light and switch it on again and the circuit reverts. The reason for doing this experiment is to show that it needs two complete operations of switching the room light on and off to make the lamp in the circuit go on and off once. We are effectively dividing the number of operations by a factor of two—the reason why the circuit gets its name. While doing this experiment it is worth noting that slow signals do not have any effect on the divider; slowly covering and uncovering PCC1 will not be an effective trigger—you need the very fast action of switching a light on and off to get reliable results. The reason for this is that C1 and C2 are not able to pass slow waveform signals. You need a wide range of lighting levels to make this circuit switch rapidly but there are a range of switching circuits called "triggers" which speed up the action of slow stimuli. We shall be looking at this effect next month.

TO BE CONTINUED

**DO YOU HAVE A STANDARD
SIZE "COMPACT CASSETTE"
TAPE RECORDER ?**

If so, why not send us a "taped"
letter for the letters page ?

WE WILL AWARD

**TWO FREE CASSETTE TAPES
FOR EACH "TAPED" LETTER
PUBLISHED IN**


**"PRACTICAL WIRELESS"
and return your original cassette*
as well.**

Please note that we cannot accept nor deal with cassettes which contain queries or any other message than a letter of comment or discussion for "Dear Sir." Although we will return cassettes to readers, we cannot be held responsible for any cassettes that are lost or damaged in transit. If you wish to have your cassette returned*, please write your full name and address on it in block capitals and enclose a 4p stamp. "Tapedletters" on cassettes only can be sent to:

"Dear Sir," Practical Wireless, Fleetway House, Farringdon Street, London EC4A 4AD.

We can still accept handwritten letters, too!

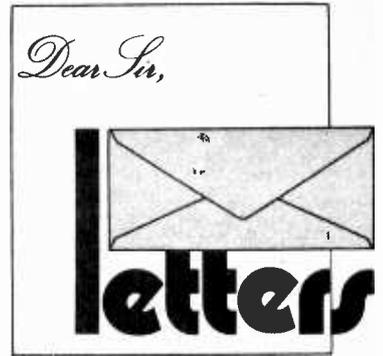*We can only send cassettes to U.K. addresses.



Mum writes in

I am writing as a 'Mum' of one of your enthusiastic readers. Do you by any chance know the ages of some of your younger readers?

My son Edward is 6½ years old and has taken *Practical Wireless* for over a year now. It is used for bedtime stories together with Aesop's Fables (I insist on that!)

Thus one outcome of the enthusiasm of one small boy is that his mother now knows the difference between a diode and a triode, step-up transformers and step-down transformers.

I must confess I find the whole subject of wireless very difficult and show no enthusiasm myself but if you could see a certain little boy's eyes light up when "P.W." as it is affectionately called arrives, it persuades me once more to plough through details of digital multimeters and who is selling what component at the cheaper price!

Through your magazine, Edward bought a pocket multimeter from an advertiser, so we are all having our resistance tested!—Mrs. Pat Russell (Herts.).

Darkroom thermometer

Some time ago, you published an article by R. A. Bottomley on the construction of a darkroom thermometer. I have built this unit with great success but I found it was necessary to increase R3 to obtain balance at the mid-point on the scale. I arranged for 24° and 29° by duplicating R3, VR1 and R4. R3 then became 1.5 + 2.2k and 1.5 + 3.3k. A changeover switch completed the revised arrangement, the two temperatures being respectively for developing colour film and colour prints. The meter I used was a Japanese Henelec 0-100uA.—C. G. Dahl (Surrey).

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit - £24.95! (PLUS VAT)

The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 - so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.

Features of the Sinclair Cambridge

- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended.)




A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

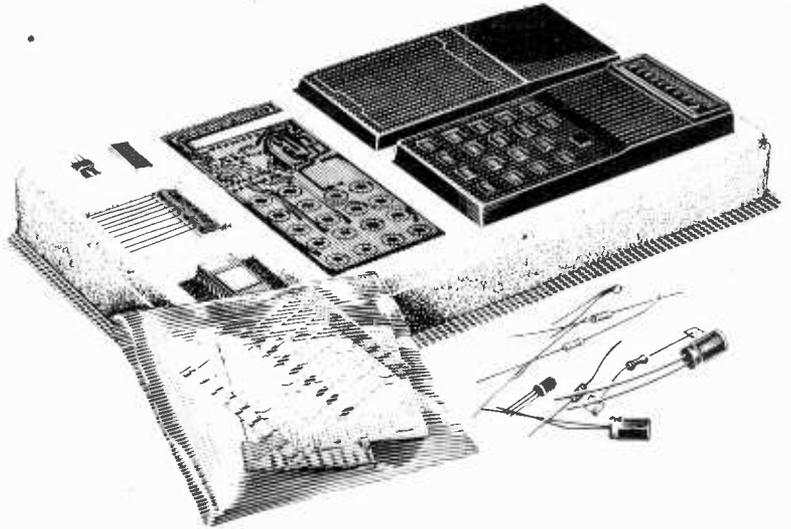1. Coil
2. Large-scale integrated circuit
3. Interface chip
4. Thick-film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

Logs Sines Cosines
Tangents Reciprocals nth roots
Currency Compound
conversion interest
and many others...

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)

Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

PW 11 73

Please send me

a Sinclair Cambridge calculator kit at
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready
built at £29.95 + £3.00 VAT
(Total: £32.95)

*I enclose cheque for £ _____ made
out to Sinclair Radionics Ltd, and
crossed.

*Please debit my *Barclaycard/Access
account. Account number _____

*Delete as required.

Name _____

Address _____

PLEASE PRINT

GOING QUADRAPHONIC

PW

Q4 PROJECT

PART 2 D. BOLLEN

- QS recordings
- SQ recordings
- Discrete CD-4 recordings
- SURROUND SOUND

It is easy to see how several resistance networks, plus variable separation, could be combined by switching to offer multi-system decoding, but before considering this it would be as well to look first at the circuits of Units A and B.



Unit A circuit

The circuit of unit A is shown in Fig. 12. Tr1 and Tr2 act as unity gain phase splitters, with an input impedance of $47k\Omega$ and an output impedance of about $1k\Omega$. Mixers Tr3-Tr6 are of the virtual earth type, with an output impedance of $2k\Omega$, and a gain of two when employed with input resistors of a nominal $100k\Omega$.

Apart from matrixing, the mixers will accept additional input resistors for mixing in other signals such as reverberation or echo. To keep noise to a minimum, and maintain the correct working point for each transistor, it is advisable to use metal oxide resistors of 5 per cent tolerance or better in the circuit of Fig 12.

Unit B circuit

A constant phase shift of 90° throughout the audio spectrum presents circuit problems. It is arguable how wide the frequency bandwidth needs to be. Some authors maintain that the ear is incapable of detecting phase differences from loudspeakers beyond the limits of 100Hz - 8kHz , while decoder manufacturers are currently aiming at a constant phase shift bandwidth of 20Hz - 20kHz . Some commercial decoders seem to get by with a bandwidth of 100Hz - 10kHz , with a variation of ± 10 per cent on 90° so this standard was adopted for the PW Q4 decoder. The graph of Fig. 11 shows the phase shift characteristic of the unit B circuit.

A 90° phase shifter consists of a phase splitter followed by a network of resistors and capacitors, but a simple splitter of the type used in unit A has insufficient power output to drive such a network

effectively, so IC operational amplifiers were employed instead.

In the circuit of unit B, left and right channels are identical and it will suffice to examine the left channel only. IC1 package contains two operational amplifiers of the 741 type, here labelled A and B. The inverting input of amplifier B is connected to the output of amplifier A, which also inverts. Operational amplifier A has a gain of 2.3 and B a unity gain, so the combined outputs of the amplifier pair will be 180° out of phase and 2.3 times the level of the input signal; this gain is just sufficient to offset the gain loss in the following phase shift network.

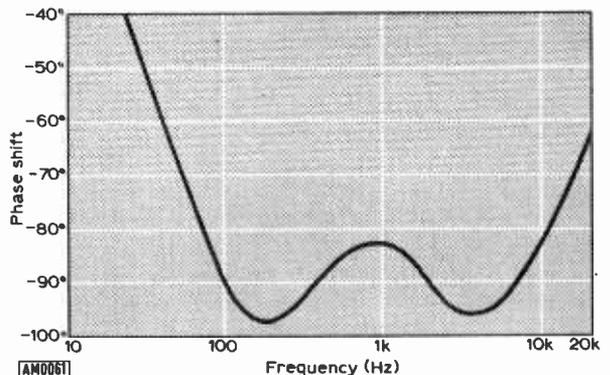


Fig. 11: Phase shift characteristics.

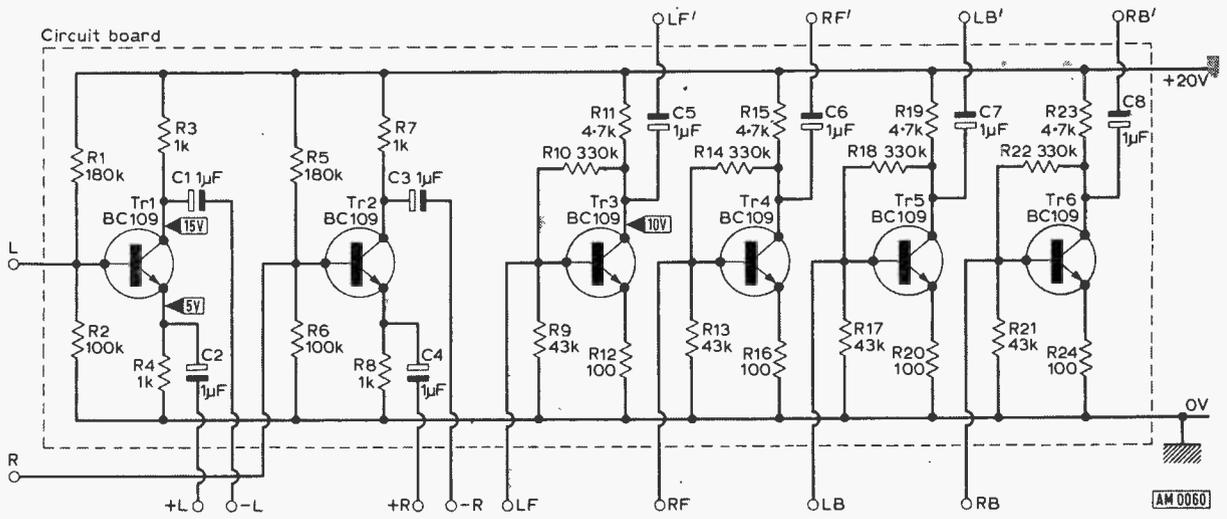


Fig. 12: Circuit of unit A.

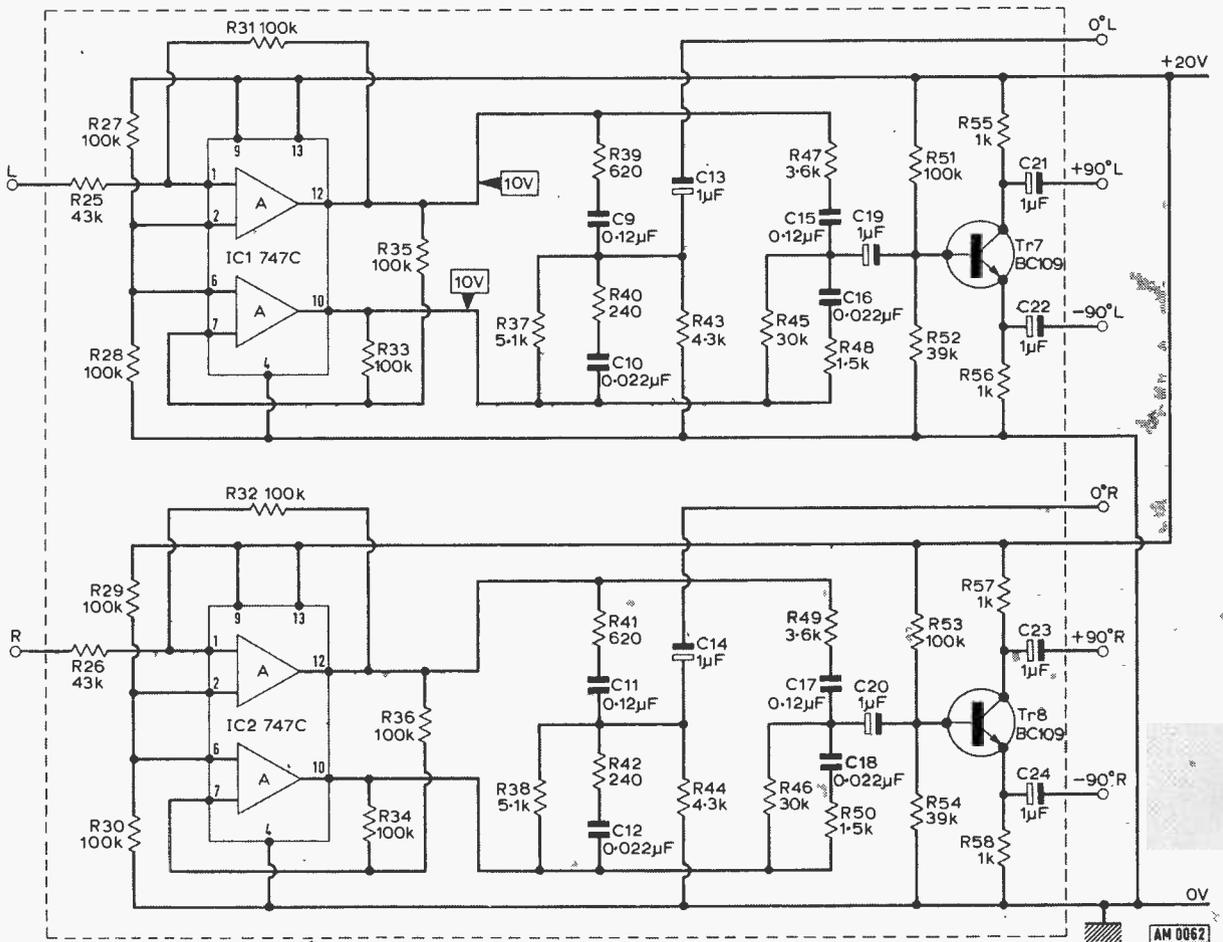


Fig. 13: Circuit of unit B.

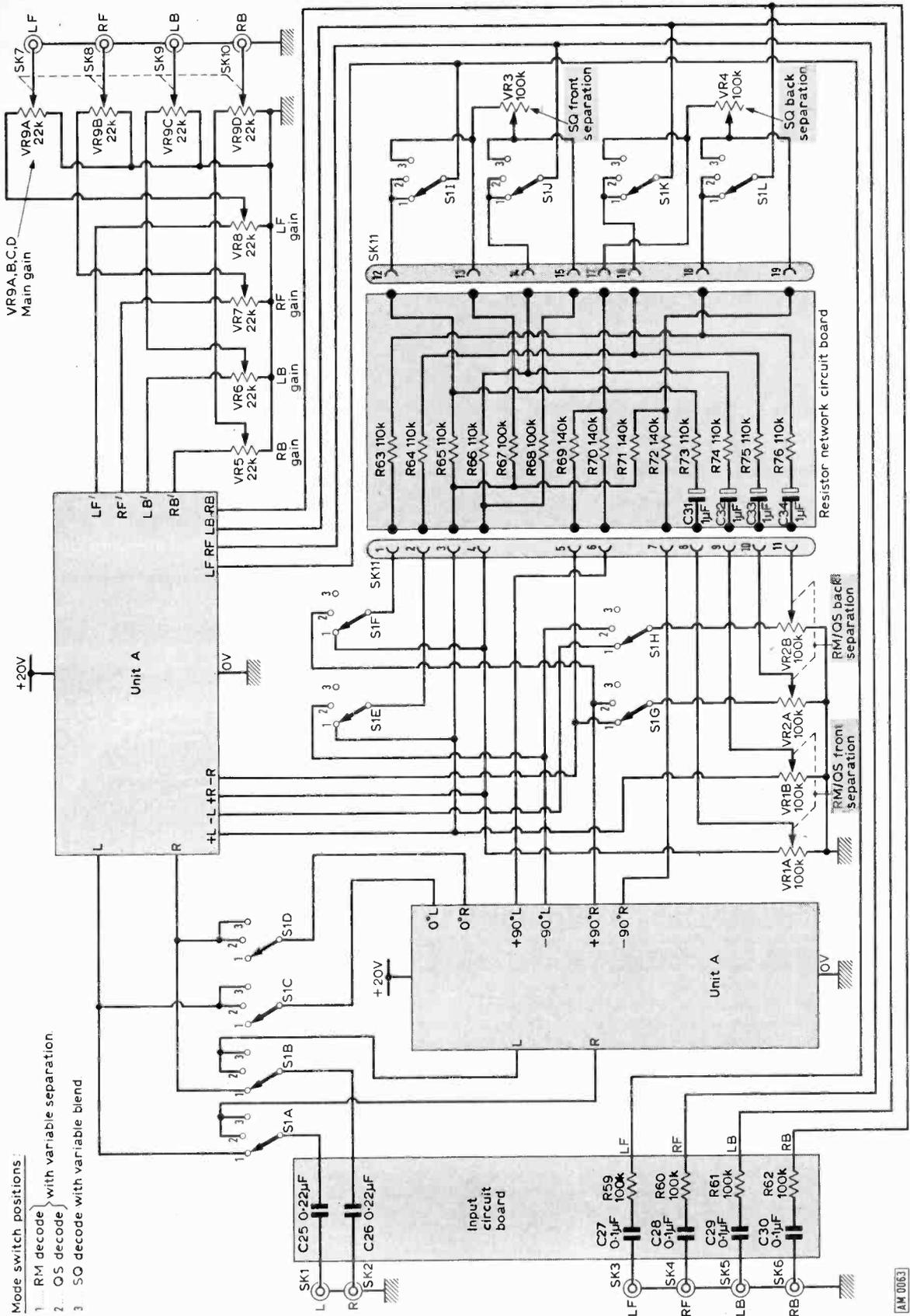


Fig. 14: Circuit diagram of the Q4 multi-system decoder with infinitely variable separation and discrete inputs.

★ Q4 COMPONENTS LIST

UNIT A

Resistors

R1 180kΩ	R13 43kΩ
R2 100kΩ	R14 330kΩ
R3 1kΩ	R15 4·7kΩ
R4 1kΩ	R16 100Ω
R5 180kΩ	R17 43kΩ
R6 100kΩ	R18 330kΩ
R7 1kΩ	R19 4·7kΩ
R8 1kΩ	R20 100Ω
R9 43kΩ	R21 43kΩ
R10 330kΩ	R22 330kΩ
R11 4·7kΩ	R23 4·7kΩ
R12 100Ω	R24 100Ω

All $\frac{1}{2}$ W metal oxide

Capacitors

C1-C8 1μF 25V electrolytic

Transistors

Tr1-Tr6 BC109

Miscellaneous

0·1in pitch Veroboard 0·9in x 4in; terminal pins.

UNIT B

Resistors

R25 43kΩ	R42 240Ω
R26 43kΩ	R43 4·3kΩ
R27 100kΩ	R44 4·3kΩ
R28 100kΩ	R45 30kΩ
R29 100kΩ	R46 30kΩ
R30 100kΩ	R47 3·6kΩ
R31 100kΩ	R48 1·5kΩ
R32 100kΩ	R49 3·6kΩ
R33 100kΩ	R50 1·5kΩ
R34 100kΩ	R51 100kΩ
R35 100kΩ	R52 39kΩ
R36 100kΩ	R53 100kΩ
R37 5·1kΩ	R54 39kΩ
R38 5·1kΩ	R55 1kΩ
R39 620Ω	R56 1kΩ
R40 240Ω	R57 1kΩ
R41 620Ω	R58 1kΩ

All $\frac{1}{2}$ W metal oxide

Capacitors

C9 0·12μF
C10 0·022μF
C11 0·12μF
C12 0·022μF
C13 1μF 25V electrolytic
C14 1μF 25V electrolytic
C15 0·12μF
C16 0·022μF
C17 0·12μF
C18 0·022μF
C19 1μF 25V electrolytic
C20 1μF 25V electrolytic
C21 1μF 25V electrolytic
C22 1μF 25V electrolytic
C23 1μF 25V electrolytic
C24 1μF 25V electrolytic

All capacitors $\pm 5\%$ polycarbonate unless otherwise specified

Transistors

Tr7 BC109 Tr8 BC109

Integrated Circuits

IC1 747C 14 pin DIL
IC2 747C 14 pin DIL

Miscellaneous

0·1in pitch Veroboard 1·8in x 3in; terminal pins

Additional components for multi-system decoder

Resistors

R59 100kΩ	R66 110kΩ
R60 100kΩ	R67 100kΩ
R61 100kΩ	R68 100kΩ
R62 100kΩ	R69 140kΩ
R63 110kΩ	R70 140kΩ
R64 110kΩ	R71 140kΩ
R65 110kΩ	R72 140kΩ

All resistors $\frac{1}{2}$ W metal oxide

Potentiometers

VR1 100kΩ linear dual-gang
VR2 100kΩ linear dual-gang
VR3 100kΩ linear
VR4 100kΩ linear
VR5 22kΩ linear
VR6 22kΩ linear
VR7 22kΩ linear
VR8 22kΩ linear
VR9 22kΩ log (two dual-gang, see text)

Capacitors

C25 0·22μF
C26 0·22μF
C27 0·1μF
C28 0·1μF
C29 0·1μF
C30 0·1μF
C31 1μF 25V electrolytic
C32 1μF 25V electrolytic
C33 1μF 25V electrolytic
C34 1μF 25V electrolytic

All capacitors tubular polyester unless otherwise specified

Switch

S1 12 pole 3 way (RS Components miniature Mako-switch with three 4 pole 3 way wafers)

Sockets

SK1-SK10 phono panel mounting
SK11 0·1in pitch edge connector cut down to 19 way (see text)

Miscellaneous

0·1in pitch Veroboard 1·9in x 3in and 2in x 1·2in; knobs; phono plugs; 18 s.w.g. aluminium sheet 20cm x 29cm and 14·5cm x 35cm.

POWER SUPPLY

Resistors

R77 1kΩ 10% $\frac{1}{2}$ W carbon

Capacitors

C35 1000μF 35V electrolytic
C36 1000μF 25V electrolytic
C37 0·1μF tubular polyester

Transistors

Tr9 BFY52

Diodes

D1 1N4001
D2 1N4001
D3 BZX61 (1·3W zener)

Transformer

T1 0-20V, 0-20V (RS Components Ltd. miniature mains transformer)

Miscellaneous

0·1in pitch Veroboard 1·9in x 2·1in; TO5 heat sink; terminal pins.

The phase splitters in Fig. 13 are Tr7 and Tr8. Phase shift capacitors for the left channel are C9, C10, C15, and C16, and these must have a tolerance of ± 5 per cent or better if the performance indicated in Fig. 11 is to be realised. All resistors used in the Unit B circuit should also be 5 per cent or better and preferably of the metal oxide type.

The input impedance of unit B is $43k\Omega$ and the output impedance from the phase splitters approximately $1k\Omega$. As the 0°L and R outputs are only to be connected to the phase splitters of unit A their impedance may be ignored.

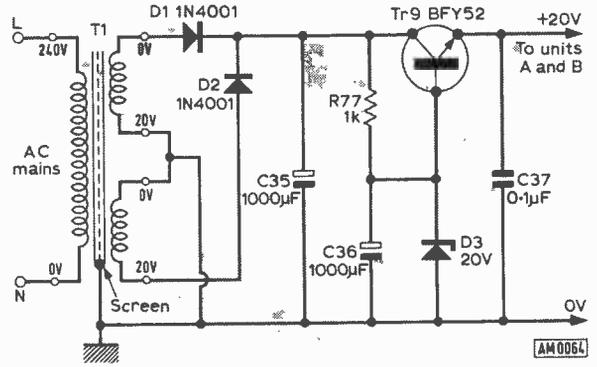


Fig. 15: Power supply circuit.

Multi-system decoder

Fig. 14 shows the circuit of a multi-system decoder based on units A and B. In the RM position of switch S1, with VR1 and VR2 set to mid-track the circuit adheres to the Schieber code with constants of 0.92 and 0.38, giving 3dB separation with a similarly coded recording. When VR1 and VR2 sliders are at the earthed ends of their tracks, left to right separation is virtually infinite, and front to back separation is zero, thus giving centre of the room stereo, and an effect similar to stereophones. At the other extreme, with sliders at the live ends of tracks, left to right separation will be zero and front to back separation is infinite, giving a stereo recording as centre front mono with centre back ambience.

Adjustment of VR1 and VR2 will cover the codes of all early American material, and will also compensate for the widely differing recording techniques used for stereo, to give a well balanced surround-sound result. The resistors associated with the RM decode are R63-R66 and R73-R76.

With S1 switched to QS, the RM resistors are rearranged for Sansui-Pye decode, when VR1 and VR2 are at mid-track. Here, adjustment of VR1 and VR2 can be used to alter the sound stage proportions and to compensate for an oblong speaker array.

In the SQ decode S1 position, resistors R67-R72 are brought into circuit to satisfy the CBS decode constants of 1 and 0 on the front channels, and 0.707 on the back channels, with the required phase shifts in the back channels. At the same time, the controls and resistors associated with RM and QS are rendered inoperative, and VR3 and VR4 are brought in to control SQ front and back separation. With VR3 and VR4 at mid-track, left to right separation will be 10 per cent or 20dB, and this setting will give satisfactory results with SQ recordings where a strong centre front image is not important. The blend values may be varied to compensate for an unusual speaker layout, or to boost a centre front image.

SK3 to SK6 in Fig. 14 are for discrete inputs, and may be used at any setting of S1 when the two-channel inputs to SK1 and SK2 are switched off. Using two and four channel inputs simultaneously would give a mix between the two, so SK3-SK6 can also be employed for mixing in other signals while decoding matrixed material. An output from a reverberation unit could be fed into SK5 and SK6 for increased ambience on certain recordings, or a voice announcement could be mixed into any one of the four channels while music is playing.

Power supply

The supply requirements of units A and B together are 33-40mA at 20V with a low ripple content and a low supply impedance throughout the frequency range. This is provided by the semi-regulated supply circuit of Fig. 15.

C36 and R77 time constant ensures a slow-rise switch on to prevent loudspeaker 'plop' and at the same time keeps impedance down at very low frequencies. C37 offers a low impedance at high frequencies.

The article to follow next month will give constructional details of the multi-system decoder, with notes on testing and setting up.



TUT! TUT!!

P.W. STUDENT OSCILLOSCOPE

On page 340 of the August issue a Veroboard layout was shown. To assist constructors, the co-ordinates of the conductor breaks are listed below:

A43	B1	C4	E15	F24	G15	H5	K66
	B4	C76	E24	F28	G19	H15	
	B27		E36	F33			
	B83						
L54	M57	N34	O39	P24	Q48	R8	S14
L67	M63	N39	O43	P39	Q74	R23	
	M66	N51	O48	P48	Q80		
	M72	N57	O76	P51			
		N63	O80	P76			
		N66		P80			
	T5	U13	V36	W1	W63		X43
	T25	U75	V53	W5	W67		
	T32	U80	V75	W40	W73		
			V80	W50	W80		
				W59	W83		

HOT LINES

ON RECENT DEVELOPMENTS

ON AN IMPULSE

WHILE it is always interesting to record the latest developments in electronic components, instruments, etc, it often works out that an application of established principles and equipment is equally fascinating.

One such application is that of amplifying tiny—really tiny—electrical signals or impulses and causing these to control things. Human beings have been doing this since the year one. Signals from the brain control limbs, etc. The twist in this story comes when you take signals generated by the body and couple them to external sources.

A series of experiments has been conducted (another series is in current progress) which shows that well over a dozen different muscle patterns can be produced on cue. The idea is that the subject thinks of raising (say) his right thumb but does not actually move it upwards. Gold electrodes taped to the hands are able to detect these impulse commands.

The experiments to date have involved a subject causing different patterns in an array of lights. Consider the possibilities. You could think that the grass needed cutting—and immediately a radio-controlled E-type lawn mower would belt out of the shed. Obviously there are limits. Imagine being introduced to Raquel Welch, an experience which should produce an impulse or two in most men. Perhaps a built-in manual control could restrict reaction on such occasions to a well-willed wink.

PACEMAKERS

Pacemakers, those devices which keep an internal eye on hearts which don't function as reliably as they should, have to be replaced surgically about every two years. Nuclear-powered pacemakers can last ten times as long but can cost five times as much compared to "conventional" ones. They also radiate and are more bulky and heavier than their "conventional" counterparts.

A new pacemaker has arrived. It can be implanted in the patient using only a local anaesthetic. This unit triggers and "fires" only if the heart doesn't beat after a predetermined time. There's more to come too. The unit may be recharged by the patient! The user has a portable recharging unit and a special "vest" which is donned. A special acoustic coupler also enables the wearer to telephone his doctor and transmit heart signs and signals directly for study.

TEMPIS FUGIT

In a previous issue, I wrote of electronic clocks and watches. This seemed to stir a chord in some people and a few even wrote to me. Prices for these items will doubtless come down as production goes up. Not all electronic time pieces cost hundreds of pounds. An electronic stop-watch about to launch itself onto the American market is reckoned to sell there for less than \$200. It has a crystal oscillator, LED display and a rechargeable battery. A 28-pin C.M.O.S. chip is employed and the watch measures 0.5in. wide, 1.4in. long and 0.75in. deep. The 24hr read-out will happily stay illuminated for about 12 weeks before the battery needs recharging and there is a small button which will switch off the display if it is desired to conserve power.

The electronic watch market in the U.S. alone is estimated at \$50 million for this year which might account for all the activity. One manufacturer has recently introduced what is claimed to be the first watch ever which employs field effect liquid crystal displays.

One of the interesting things about the particular display used in these watches is that it is the reverse of the image usually associated with liquid crystal displays. Normally, these adopt a frosted-glass effect for the legends against a mirror background. The field effect LCD's absorb the incident light via polariser filters and the legends (figures, letters, etc) are easily

seen as dark outlines against a diffused white background. The lowest price model in this range of wrist watches is around \$150. The field effect displays are guaranteed by the manufacturer for 3 years, but it is expressed that they will last for nearer 10 years. Looks as though proud owners will be taking their time-pieces to electronic beauty salons every so often for a face change?

One of the most vital parts in the electronic watch, employing a crystal oscillator, is the crystal itself—the electronic heart of the beast. Favourite crystal frequency is 32kHz which is then divided down to supply pulses which in turn feed the displays via display drivers. But there's a snag. Difficulty is being experienced in some areas because the clock/watch maker cannot get enough crystals at 32kHz.

THEY'RE RESISTANT!

One company offers some intriguing resistors which are described as ceramic-insulated and flame-proof. Apparently, these will not burn even if the open flame of a blow-lamp is played on them. Well I'm blown! Resistance values range from 1Ω to 60kΩ in wattage ratings from 1-10 Watts.

POWER STRUGGLE

Remember the first transistors? Red spot for a.f. with a cut-off around 800kHz. Then White spot transistors which, with luck, managed the 1.8-2MHz Amateur band. They were delicate and couldn't handle too much power. The latest power transistors from one manufacturer are rated to handle 400V at 60A (down to 100V at 200A). A 500V 100A component is in the design stage. Note: these are transistors not thyristors. Perhaps we have a struggle for Power here?

Ginsberg

TAKE 20

DAVID ANDREWS

No. 54 RADIO-GRAM

A series of simple transistor projects, using not more than twenty components.

BEFORE you complain that you have been misled by this month's title I had better explain that this device enables you to play records via any type of transistor portable radio without having to make any internal connections to the radio. Thus it is ideal for use with the modern miniature portables that do not have pick-up sockets and thus might save Dad a bit of money when "junior" demands a record player! Apart from the unit to be described you will, of course, need a turntable unit with a CRYSTAL CARTRIDGE pick-up. We stress crystal cartridge not only because it is the cheapest but because the "Radio-Gram" will not work with other types.

Circuit

The circuit shown in Fig. 1 is basically an oscillator that can be tuned with TC1 to operate between about 700kHz and 1.5MHz (i.e. across the range of the medium wave band). The amplitude of oscillation is modulated by direct connection of the pick-up across R2. The modulation process works simply by shifting the bias level of the transistor at audio frequencies and this is remarkably effective. C1 is necessary to help decouple the junction of R1 and R2 to r.f. and it also prevents overmodulation at high frequencies.

Construction and Testing

The coil is wound on a 4 to 6in length of $\frac{3}{8}$ in diameter ferrite aerial rod, Fig. 2, but when doing this be careful to take note of the sense and start points of the windings; if the connections from the 5 turn feedback coil are reversed the circuit will refuse to operate! The BC108 used should have a gain in the order of 200, which is in the centre of the production spread, but the circuit will operate with devices of widely differing gain.

If, on test, the signal is distorted it is likely that the transistor has too high a gain and the carrier is being clipped. To prevent this increase the value of R3 and reduce R4, keeping the sum of the two about $2k\Omega$, to introduce a little more negative feedback. Conversely, if the signal strength is weak change the values in the opposite direction. No problem should be encountered here, however, so we have made R3 and R4 fixed values instead of using a more expensive preset.

The unit can be built on veroboard and fitted within a screened metal box. The signal is fed out via a screened lead (very loosely coupled to the ferrite rod as shown) and the centre conductor connected into the aerial socket of the transistor radio. To operate it, select a quiet portion of the medium waveband, put on a record and adjust TC1 until the music is clearly received. First tuning is best carried out on the receiver.

The current drawn by the Radio-Gram is minute, less than 100 microamps, so any small 9V battery will operate it for almost the battery's shelf life.


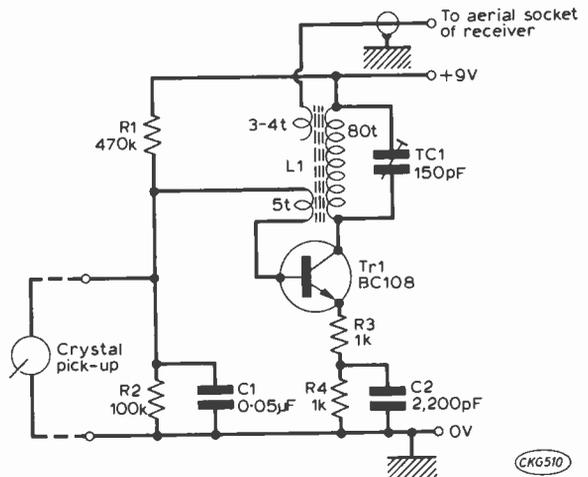


Fig. 1 above, shows the circuit of the Radio Gram. One end of the output coupling coil is left free. Fig. 2, below, is a suitable layout on veroboard.

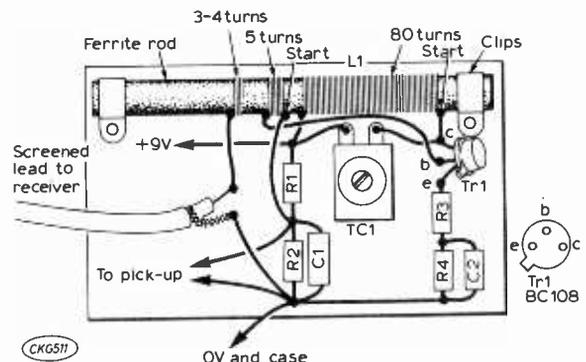

★ components list

R1	470k Ω	1p
R2	100k Ω	1p
R3	1k Ω	1p
R4	1k Ω	1p
C1	0.05 μ F	4p
C2	2200pF	4p
TC1	150pF preset	15p
Tr1	BC108	10p
L1	Ferrite rod	25p
		62p

No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

is this the price you pay?

Probably if you're still using an ordinary soldering iron Ordinary soldering irons can cause damage to transistors and integrated circuits — damage which wastes time and costs money. Now, with the unique ANTEX X25 and CCN low leakage soldering irons no harm can come to the most delicate equipment, even when soldered 'Live'.
(You could be making quite a saving).
All prices include V.A.T. at 10%



MODEL X25

220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with it's truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction advantages.


Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.
PRICE: £1.93 (rec. retail) P & P 8p.
Suitable for production work and as a general purpose iron.



MODEL CCN

270 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft.

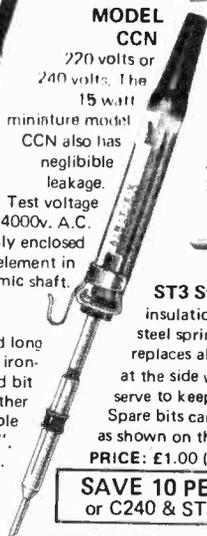Fitted long life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".
PRICE: £2.15 (rec. retail). P & P 5p.




MODEL G — 18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110. **PRICE: £2.15** (rec. retail). P & P 5p.



MODEL C — Miniature 15 watt soldering Iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE: £1.93** (rec. retail). P & P 5p.



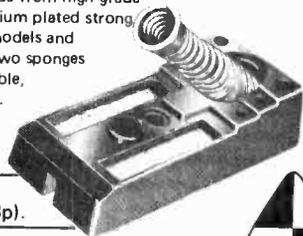ST3 Stand — This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable, serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration.
PRICE: £1.00 (P & P 8p).



SAVE 10 PENCE X25 & ST3 or C240 & ST3 for £2.83 (P & P 13p).

MODEL MLX KIT

Battery-operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"

PRICE: £2.27 (rec. retail). P & P 12p



MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.
PRICE: £3.25 (rec. retail). P&P 12p



MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.
PRICE: £2.97 (rec. retail). P & P 8p.



From radio or electrical dealers, car accessory shops or in case of difficulty direct from:—
ANTEX LTD. FREEPOST
(no stamp required) **PLYMOUTH**
PL1 1BR Tel: 0752 67377.

- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME

ADDRESS

PW11



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

EMI 13 x 8, 3, 8 or 15 ohm	£2.03
EMI 13 x 8, 150 d/c 3, 8 or 15 ohm	£2.25
EMI 13 x 8, 450 t/tw 3, 8 or 15 ohm	£3.60
EMI 13 x 8 type 350 8 ohm	£8.25
EMI 6 1/2" 93850 4 or 8 ohm	£2.80
EMI 8 x 5, d/Cone Roll/s 8 ohm	£2.50
Baker Group 25 3, 8 or 15 ohm	£6.60
Baker Group 35 3, 8 or 15 ohm	£7.50
Baker De Luxe 12" d/cone	£9.62
Baker Major 12"	£7.50
Kef T27	£4.67
Kef T15	£5.50
Kef B110	£6.16
Kef B200	£7.42
Kef B139	£10.72
Kef DN8	£1.92
Kef DN9	£1.37
Kef DN12	£4.12
Kef DN13	£2.75
Fane Pop 100 watt 8/15 ohm	£21.45
Fane Pop 60 watt 8/15 ohm	£12.26
Fane Pop 50 watt 8/15 ohm	£10.17
Fane Pop 25/2 25 watt 8/15 ohm	£5.94
Fane Pop 15 watt 8/15 ohm	£4.40
Fane Crescendo 15" 8 or 15 ohm	£27.50
Fane Crescendo 12A 100w 8 or 15ohm	£24.20
Fane Crescendo 12B 75w bass 8 or 15	£24.20
Fane 807T 8" d/c roll/s 8 or 15 ohm	£3.85
Fane 808T 8" d/cone 8 or 15 ohm	£2.64
Goodmans Axent 100 tweeter	£6.60
Goodmans 8P 8 or 15 ohm	£3.80
Goodmans 10P 8 or 15 ohm	£4.49
Goodmans 12P 8 or 15 ohm	£11.55
Goodmans 15P 8 or 15 ohm	£17.05
Goodmans 18P 8 or 15 ohm	£29.70
Goodmans Twinaxiom 8	£6.79
Goodmans Twinaxiom 10	£7.61
Elac 9 x 5 5" 59RM109 15 ohm.	£2.53
59RM114 8 ohm	£3.22
Elac 6 1/2" d/c roll/s 8 ohm	£2.59
Elac 6 1/2" d/cone 8 ohm	£1.21
Elac 4" tweeter TW4	£3.11
Wharfedale Bronze 8 RS/DD	£5.50
Wharfedale Super 8 RS/DD	£9.80
Wharfedale Super 10 RS/DD	£9.80
Coral 6 1/2" d/cone roll/s 8 ohm	£2.42
Siran 6 1/2" 3 or 8 ohm	£1.44
Richard Allan 12" d/c 3 or 15 ohm	£2.20
10" x 6" 3, 8 or 15 ohm	£1.92
8" x 5" 3 or 8 ohm	£1.38
7" x 4" 3 or 8 ohm	£1.38
2 1/2" 64 ohm or 70 mm 80 ohm	£0.65
Adastra Hiten 10" 10w 8 or 15 ohm	£2.80
Eagle DT33 dome tw.	£5.45
Eagle HT15 tweeter	£3.66
Eagle CT5 tweeter	£1.25
Eagle CT10 tweeter	£2.54
Eagle MHT10 tweeter	£3.74
Eagle FR4	£4.45
Eagle xover CN23, 28, 216	£1.10
Sp. matching transformer 3-15 ohm	£1.10
Celestion MF1000 25w horn 8 or 15 ohm	£1.10
Celestion PS8 (for Unilex)	£10.45
Celestion G12M 8 or 15 ohm	£2.16
Celestion G12H 8 or 15 ohm	£12.00
Celestion G15C 8 or 15 ohm	£15.00
Celestion G15C 8 or 15 ohm	£24.00
Celestion G18C 8 or 15 ohm	£33.00
Car Stereo speakers—ask for leaflet.	£33.00

SPEAKER KITS

Wharfedale Unit 3	£8.25
Wharfedale Unit 4	£14.50
Wharfedale Unit 5	£1.00
Richard Allan Twinkit	£7.33
Richard Allan Triple 8	£10.76
Richard Allan Triple Assem.	£16.20
Richard Allan Super Triple	£19.36
Goodmans DIN 20	£8.58
Fane Mode One	£9.00
Kefkit 2	£25.75
Kefkit 3	£35.50
Peerless 2-8	£5.50
Peerless 10-2	£8.47
Peerless 20-2	£10.41
Helme XLK 25 (Pair)	£18.17
Helme XLK 50 (Pair)	£37.18
Stephenspeaker kits and cabinets—send for free booklet "Choosing a Speaker". Prices include VAT.	
Carriage and insurance 50p per kit.	



RADIOS/CASSETTES/AMPS.

Grundig Mariner TR865	£22.00
Grundig Elite Boy 500	£27.00
Grundig Melody Boy 500	£27.00
Grundig Melody Boy 1000	£38.75
Grundig Yacht Boy 210	£34.25
Grundig RF430 mains	£27.00
Grundig RF310 mains	£22.75
Grundig RF310	£21.25
Grundig Top Boy	£16.75
Grundig Satellit 1000	£121.00
Grundig C402 cassette	£27.00
Grundig Signal 500	£27.00
Grundig C230 Cassette	£28.00
Tandberg TP41	£42.00
BASF 9301 radio/cassette	£58.00
Bush VTR178 5 Band (Inc. Air)	£29.00
Trio KA2000A	£33.00
Trio KA2002	£41.00
ITT Colt	£9.95
ITT/KB Golf Preset	£21.25
ITT/KB Weekend Auto	£16.00
ITT/KB Europa	£18.00
ITT/KB SL53 cassette	£22.82
ITT/KB Studio 73 stereo cassette	£44.00
Koyo KTR1664 8 waveband	£40.00
Koyo KRT 1770 11 waveband	£56.50
Koyo KTR1883 5 Band (Inc. Air)	£23.50
Tec C200 Radio/Cassette	£31.00

Prices include VAT.
Carriage and insurance 50p. FREE with each radio—"World Radio Stations Book"

PA/DISCO AMPLIFIERS

Carriage and insurance £1.00	
Baker 100 Watt	£40.00
Linear 30/40	£25.00
Linear 40/60	£30.00
Linear 80/100	£55.00

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 25p per speaker (tweeters and crossovers 15p)

ALL PRICES QUOTED INCLUDE V.A.T.

WILMSLOW AUDIO Dept. P.W.

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression. 600 watt £3.52 Kit form £2.97 300 watt £2.97 Kit form £2.42

All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY

2 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO M.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

Stove Enamelled STEEL CABINET



List price £6.87
OUR PRICE
£5.50
incl. V.A.T.
Carriage 44p

With 48 see-through Drawers
Ideal for the Radio Constructor

As supplied by us to SCHOOLS, TECHNICAL COLLEGES, HOSPITALS, SHOPS and industry throughout the country. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at a small extra charge to enable each drawer to be sub-divided into six compartments. See-through drawers allow swift selection of contents at a glance. A really first-class time and space saving unit. Size of cabinet 21 1/2" x 11 1/2" x 6 1/2", size of drawers 6 1/2" x 2 1/2" x 1 1/2".

Callers welcome.

SEND FOR FREE ILLUSTRATED LEAFLETS

Trade Aids 111 Chiltern Drive, Surbiton Surrey
100 yards from 01-399 4383
Berrylands Railway Station

I.F. WOBBULATOR

W.S. POEL G8CYK

THERE can be little doubt that the wobulator method is by far the best means of setting up an IF strip for optimum bandpass characteristic, combined with optimum sensitivity. There are a number of commercial units made, aimed mainly at the 'trade' and priced accordingly. However, the wobulator described here costs about £1, whilst providing all the necessary features. An oscilloscope is necessary and preferably one with a simple means of getting at the timebase. (Horizontal X output).

PRINCIPLE OF OPERATION

The wobulator consists basically of a voltage controlled oscillator whose frequency is being constantly swept across the IF band of the receiver in question. The control is by means of a varicap diode, which can either be one of the purpose-made devices, or more simply, a power rectifier, such as the 1N4001/2/3.



Fig. 1: Typical waveform of a timebase oscillator, used to control the sweep of the wobulator.

The timebase output on an oscilloscope looks like Fig. 1, which is applied to the diode so that the voltage on the diode is constantly changing in step with the oscilloscope trace. So we have three variables coordinated, namely:—

1. The trace.
2. The voltage on the varicap diode.
3. The varicap capacity and consequently the wobulator frequency.

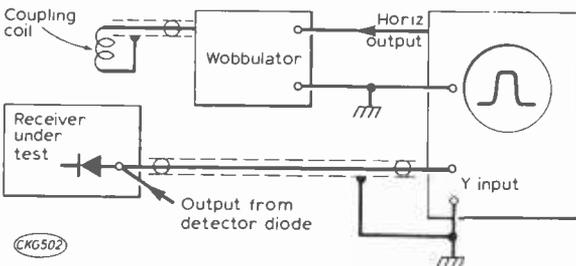


Fig. 2: Interconnections of the scope, wobulator and IF strip being aligned.

As the frequency sweeps through the IF frequency of the receiver, the IF response curve is displayed on the scope, which is itself monitoring the output from the receiver detector, Fig. 2.

CIRCUIT


The heart of the device is the single FET Vackar VFO, Fig. 3. The choice of FET is very large, and almost anything in the standard N-channel series will do, e.g. 2N3819, 3823E, TIS88, BFW10. Remember to check the base connections.

The centre frequency is mainly determined by L1, C3 and C5 and VC1. By experimentation with values, it is possible to make the VFO operate past 50MHz, though most sets designed for AM operation use an IF between 455 and 470kHz. An ordinary 455 or 470kHz IFT can be used for L1, the internal capacitor being disconnected.

It is advisable to check the timebase output from the scope when choosing the varicap diode, since many scopes have a high voltage at the X output. (The author found out the hard way!) Choose a diode with adequate PIV ratings.

CONSTRUCTION

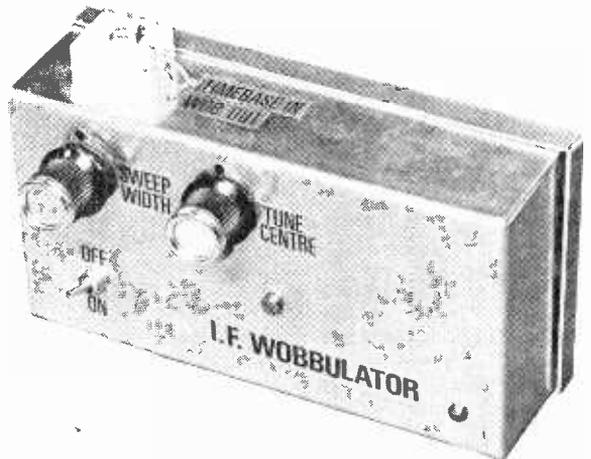It will be seen from the diagrams that the layout is quite straightforward. A printed circuit board layout is given, Fig. 4, though at 455kHz there is no objection to Veroboard if that is considered



General view of the prototype wobulator. Co-axial sockets could be used instead of the terminal block.

Fig. 3: Circuit of the wobulator. VC1 may be any suitably sized variable of about 200pF.


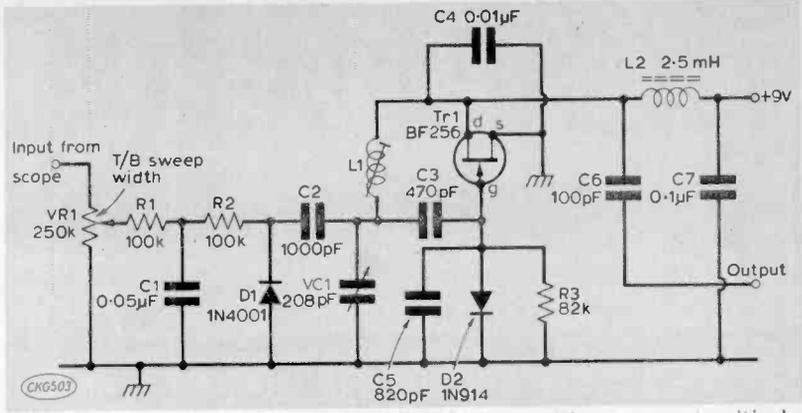


Fig. 4: The printed circuit board, actual size, with component layout.

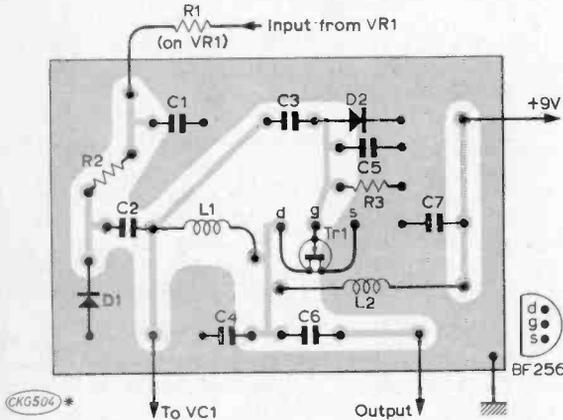


more convenient. Relative positions are not critical, and the wobulator can very largely be adapted to fit any convenient case.

No particular types of sockets are necessary since most people seem to have adopted their own 'standard,' most probably the standard TV coax system. Remembering the comments on the timebase output it is best to use either a shielded plug or directly soldered connections to avoid shocks when setting up.

OPERATION

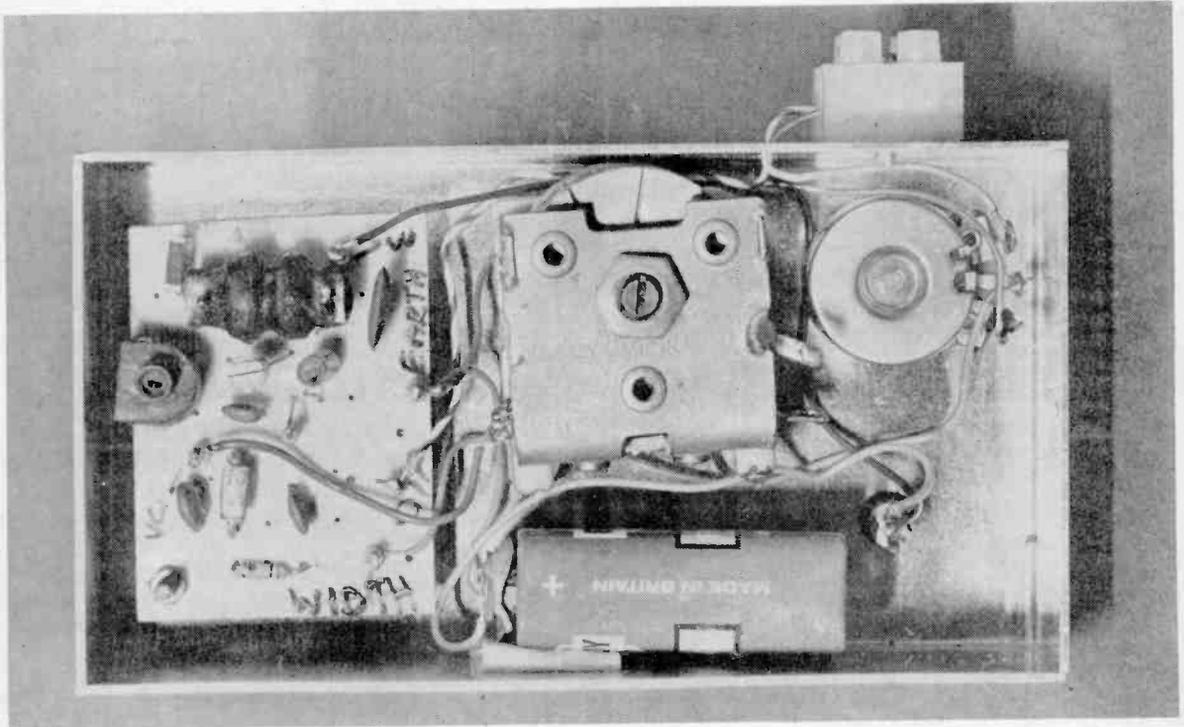The current drawn by the wobulator is typically 5mA, and any big discrepancy should be investigated before going further. When the system is coupled



The p.c.b. is mounted in the box with bolts and spacing nuts. General layout is not at all critical. An on/off switch could form part of VR1.

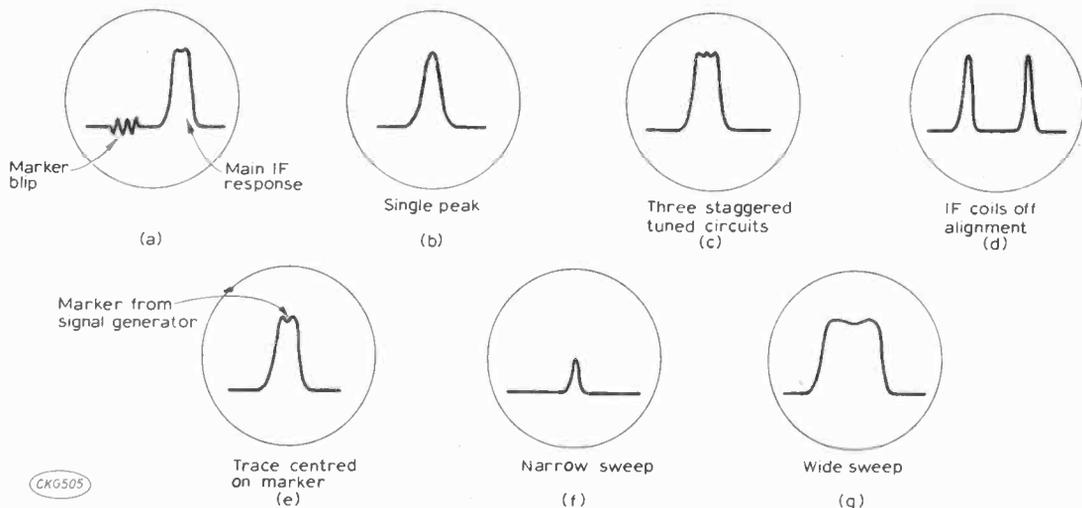


Fig. 5: Various i.f. response curves, obtained with the set-up of Fig. 2.

together as shown in Fig. 2, set the frequency of the wobulator approximately by the variable capacitor, until a trace of the IF is seen on the scope screen. The sweep frequency should be set at around 50Hz for best results when a 50Hz buzz from the set's loudspeaker will be heard when the wobulator is correctly aligned. The centre frequency of the IF can then be determined by using an accurately calibrated signal generator, Fig. 5a.

The output from the signal generator is coupled to the IF strip in the same way as the wobulator, namely a few turns of wire placed near to the mixer input/output. Remember to disable the set's local oscillator before alignment, since this will

otherwise lead to spurious traces. A few traces likely to be seen are shown in Fig. 5b-c.

The sweep width potentiometer determines the length of sweep, which may represent from 0 to 20kHz. The narrower the sweep, the more of the IF is displayed on the scope, but it must sweep at least as far as the ends of the IF bandwidth, Figs. 5f-g.

There only remains to align the IF by adjusting the cores in the IFT's to get the desired response. Bandwidth can be determined by using the signal generator to determine the points on the response curve corresponding, say, to 452 and 458kHz (455kHz centre frequency).

Want to know more about colour television?
Get the Pull-Out COLOUR SUPPLEMENT:-

BASIC

COLOUR FAULTS

GUIDE

SPECIAL SUPPLEMENT TO 'TELEVISION' OCTOBER 1973

A FIRST-TIME FULL-COLOUR
SUPPLEMENT EXCLUSIVE TO THE
OCTOBER ISSUE OF

TELEVISION

Don't miss this unique opportunity to see what some of the basic colour faults look like. We give full descriptions of the fault symptoms and tell you how to go about correcting them. Take this supplement out of the magazine and hang it on your workshop wall. It makes a superb, attractive and valuable wall chart you will always want to keep.

Also in the October Issue:
110° COLOUR CHASSIS—The new "look"
VARICAP TUNERS—to help DX-TV



BROADCAST BANDS

MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

THE International Short Wave Club conducts a poll every three years to determine the most popular short wave stations.

Listeners are asked to participate by sending to the ISWC, 47 Harridge Road, Leigh-on-Sea, Essex SS9 4HE; a list of their five most popular short wave stations in order of merit, together with a short note of *not more than 30 words* why they consider their No. 1 choice to be their most popular station. More than 30 words will automatically disqualify any listener from any award that may be given in connection with the Poll. The final date for voting is December 31st. 1973.

Ex-W.D. Equipment

The short paragraph at the end of the September column announcing that I would be devoting some space to the subject of ex-government Communication receivers has sparked off an even larger than usual postbag. The problem has become so bad that I have had to install a larger letterbox to assist the postman. I would, however, like to remind you all that any letter requiring an answer should be accompanied by a stamped addressed envelope.

I still require information on some of the rarer receivers and if any of you can supply me with this I can assure you that it will be well treated and returned as soon as possible. In particular I would be grateful for any information on the ex-Admiralty B40 receiver.

Readers' Logs

The first log this month comes from **Alan Carpenter** who lives in Aborfield near Reading. Alan's equipment consists of a Heathkit 'Mohican' GC-1U receiver and its 50 inch telescopic aerial. However, a 70 foot long-wire was added to pull in Radio Ceylon.

- 4915 *Radio Ghana, Accra*, nx. in English at 2245.
- 6250 *World Music Radio* in English at 0900.
- 7310 *Radio Vilnius, Lithuania*. English at 2230.
- 11725 *Radio Ceylon* with Religious programme at 1700.

- 11725 *R. Free Europe, Lisbon*. Pop music at 2315.
- 11730 *R. Tashkent, Uzbek* in English at 1400.
- 15445 *R. Nacional de Brasilia*. English at 2230.

A. W. Guzelian of Coniston in Lancashire has an HRO receiver and a 45 foot long-wire aerial which enabled him to hear:

- 7105 *R. Nacional de Espana*, in Spanish at 1300.
- 9555 *R. Baghdad, Iraq* in English at 1940.
- 11350 *R. Pyongyang, N. Korea*, English at 2100.
- 11765 *R. Yerevan, Armenia* noted at 2030.
- 11880 *Voice of Turkey*, in English at 2200.
- 15115 *R. Tashkent* in English at 1400.
- 15415 *R. Kuwait* in English at 1730.

Simon Wormleighton and **J. P. Fletcher** of Rendcomb College, Cirencester, Glos. have again sent in a report using the following equipment, Astrad-Altair with 80 foot long-wire; HRO with 8 metre folded dipole; Bush PB63 with 35 foot long-wire. Stations logged included:

- 6010 *R.T.B., Belgium* in French at 1505.
- 9022 *Voice of Iran* in English at 2005.
- 9600 *R. Kuwait*. Nx. in English at 1730.
- 9670 *Adventist World Radio, Lisbon* at 0935.
- 11730 *R. Vilnius, Lithuania* in English at 2250.
- 11850 *R. Norway* in English at 0824.
- 15325 *R. Canada International* at 1634.

Chris Greenway and **John Greenlees** sent in a combined log from Brandiston in Norfolk. The equipment used being a Lafayette HA600A receiver; Codar PR40 preselector; 100 foot long-wire; 15MHZ dipole and homebrew A.T.U. An extract from their log with more than 60 entries is as follows:


- 9545 *R. Ghana, Accra* in English at 2135.
- 9655 *R. Damascus, Syria*, English at 2000.
- 11650 *R. Bangladesh* with music at 1715.
- 11710 *R. Kiev, Ukraine* noted at 1945.
- 11725 *R. Ceylon* in English at 1700.
- 11935 *R. Pakistan*, news in English at 1725.
- 15105 *R. Grenada, Windward Islands* at 2120.
- 15105 *BBC, Ascension Is.* relay noted at 1510.
- 15185 *R. Nigeria, Lagos*, in English at 0715.
- 15195 *R. Japan*, news in English at 2215.
- 15265 *R. Afghanistan* in English at 1800.
- 15310 *BBC, Tebrau, Malaysia* relay at 1745.

The last log for this month comes from **Christopher Hodgson** of Sunderland who used a Codar Multiband-6 receiver, the PW A.T.U. and a 50 foot long-wire aerial to hear the following stations:

- 6130 *Radio Norway* at 1800. (Sundays).
- 9005 *R. Tehran, the Voice of Iran* at 2000.
- 9840 *Voice of Vietnam, Hanoi* noted at 1815.
- 15012 *Voice of Vietnam, Hanoi* noted at 1800.
- 15165 *Radio Denmark* in Danish at 1400
- 15185 *Radio Finland* at 1810.
- 15325 *R. Canada International*, s/off at 1313.

RAYMER ELECTRONICS

MICROCHIP SERIES HIGH FIDELITY MODULES

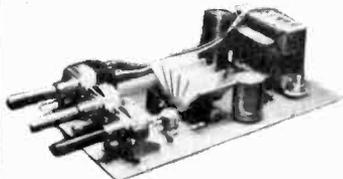

RE 500

Advanced integrated Hi-Fi Amplifier only requires connection to mains speaker and input.

Specifications: load imp 4-16 ohm. Output: 5 watts. Frequency response 20Hz to 35kHz ± 3 dB.

Total distortion less than 1%.


I/P Imp 100k ohm Nom.

£6.30. Post free.

Size: 140 x 80 x 45mm.

MICROCHIP I.C.

5 watts RMS

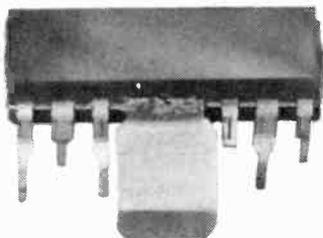


A general purpose Audio i.c. for the constructor capable of 5 watts RMS O/P at less than 1% total distortion, forms an ideal basis for an excellent Hi-Fi system.

Free Data I.C. £1.50.

Data, Printed Circuit Board, 75p. Post paid.

RE 602S

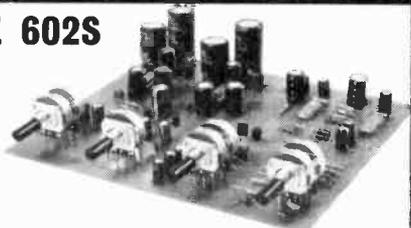

This amplifier forms an ideal basis for the construction of an advanced stereo system at minimum cost with complete ease of assembly. Designed for use with magnetic preamp inputs and main amplifiers on same PCB.

Specifications:

Power O/P 5W RMS per channel (simultaneously).

Total distortion less than 1%.

Active tone controls.

Bass ± 10 dB, Treble ± 12 dB @ 100Hz-10kHz.

Freq. response 20Hz to 35kHz ± 3 dB.

Sensitivity for full O/P 35mV (Ceramic), 3mV (Magnetic).

Input impedance 60K and 200K Ohms.

Load impedance 8-16 ohms.

Operating Voltage 18-28 Volts D.C.

£16.50. Post free.

Power Supply Extra (RE 30 psu)

COMPLETE QUADRAPHONIC AMPLIFIER KIT : RE 4K

A Hi-Fi kit comprising CBS SQ decoder, preamplifier and four channel main amplifier. All modules built and tested.

Specifications:

Similar to the Quadrix system (see below) but with four channel main amplifier giving 40 watts total peak power.

This is an opportunity to experience quadrasonic sound at the very minimum of cost.



(Power Amp only shown)

£39.00. Post free

Power Supply Extra (RE 35 psu)

POWER SUPPLIES RE 30 PSU

Input 240V AC

O/P 26V DC of 0.6 Amps

£3.60. Post free

RE 35 PSU

Input 240V AC

O/P 26V DC of 1.2 Amps

£4.60. Post free

RE QUADRIX

This is a high quality CBS specification SQ decoder with Hi-Fi stereo amplifier. Designed to allow the conversion of any stereo system to full quadrasonic performance with minimum cost. Extraordinary new presence and reality of sound. More than 20 Watts total peak power.

Specifications:

Decoder

I/P impedance 40K ohms
O/P impedance <300 ohms
Nominal I/P 100mV RMS
Front separation >60dB
Rear separation >20dB

Amplifier

Power O/P 5W RMS per channel (simultaneously)
Distortion at full O/P less than 1%
Sensitivity for full O/P 100mV
Active tone control Bass ± 10 dB, Treble ± 12 dB @ 100Hz-10kHz
Load impedance 8-16 ohms



£49.00. Post free

Special Offer SQ records (full quadrasonic sound) available direct. Comprehensive list free on request.

GUARANTEE

ALL PRODUCTS ARE GUARANTEED AGAINST FAILURE FOR A PERIOD OF 12 MONTHS AND WILL BE SERVICED FREE OF CHARGE IF PURCHASED DIRECT AND REFUNDED TO US FOR REPAIR.

NAME

ADDRESS

PLEASE SEND

(enclose PO/cheque/M.O.)

RAYMER ELECTRONICS LTD.,
Stanley Road, Cambridge CB5 8LB, England.
(0223) 54414. Reg. No. 1021205

PLEASE ADD
10% FOR V.A.T.

NO EXTRAS
ALL PRICES INC. VAT
FREE! P. & P.

AMPLIFIERS

Keltron	KSA 700	7+7 watt	23.00
	RSA 1500	15+15 watt	32.50
Tripletone	Hi-Fi 77	7+7 watt	27.50
	Hi-Fi 1818	18+18 watt	35.00
Teleton	8AQ307	8+8 watt	27.00
EMI	1515	15+15 watt	37.00
Rotel	RA210		32.00
	RA310		44.00
Rotel Tuner/Amp.	RX150A		51.00
SANSUI models in stock.			

RECORD DECKS

Garrard	2025TC/9TAHC/4	11.00
	SP25 Mk. III	11.00
BSR	MP60/SX5H	11.00
Connoisseur	BH1 KH	11.00
	B12 Classics	29.50
	BAU2 Pick-up Arm	12.25
	SCU1 Cartridge	4.85

RECORD DECK PACKAGES

SP25 Mk. III/G800 C. & P.	19.50
AP76/G800 C. & P.	30.00

PLINTH & COVER FOR GARRARD

SP25/2025TC	3.95
-------------	------

SPEAKER BARGAINS

EMI 13" x 8" 3, 8 or 15 ohm	
Plain	2.35
with Co-Axial Tweeter	2.50
Twin Tweeter	3.95
Type 350 8 ohm, 20 watt	8.50
6 1/2" 8 ohm, 10 watt	2.65
8" 8 ohm, 10 watt	3.90
12" 8 ohm, 20 watt	5.75
8" x 5" C/Mag. 5 watt	1.40
8" x 5" Dualcone 8 ohm, 10 watt	2.70

FANE 7" x 4" 3 or 8 ohm	1.15
8" Dualcone 8 ohm	2.50
CELESTION 8" 15 ohm	1.75
ADAPTRA 10" 8 or 15 ohm, 10 watt	2.95
BAKER GROUP 25	
12" 8 or 15 ohm, 25 watt	6.50
5" 8 ohm, 5 watt C/Mag.	.95
2 1/2" 8 ohm or 64 ohm	.60
RELECTION OF GOODMAN AN1	
12 x 12 x 6 with 8", 8" x 5", or 6 1/2" and 3 1/2" cutout	2.75
17 x 10 x 6 with 8" or 13" x 8" cutout	3.50
18 x 11 x 9 with 13" x 8" cutout for EMI 350	4.80

WHARFEDALE SPEAKERS ALSO AVAILABLE.

KIT FORM CABINETS - TEAK

12 x 12 x 6 with 8", 8" x 5", or 6 1/2" and 3 1/2" cutout	2.75
17 x 10 x 6 with 8" or 13" x 8" cutout	3.50
18 x 11 x 9 with 13" x 8" cutout for EMI 350	4.80

TWEETER & CROSSOVER

EMI 34" 3 or 8 ohm C/Mag.	1.10
Cone Tweeter 8 or 15 ohm, 10 watt	2.00
Cone Tweeter 8 ohm, 3 watt	1.10
Horn Tweeter 8 ohm, 20 watt	5.60
Home Tweeter 8 ohm, 30 watt	4.00
Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1.10

CARTRIDGES

ACOR GP91/28C or GP91/38C Stereo comp.	1.05
GP93/1 Stereo crsk.	1.35
GP94/1 Stereo crsk.	1.75
GP95/1	1.35
GP96/1	1.75
GP104	.75

SONOTONE

9TAHC Stereo ceramic, diam.	1.80
STARC/G Silhu Rt. stereo ceramic, diam.	1.80
19-T1 Stereo crystal	.85
BSR SC5M Stereo ceramic	2.25
SX2H Stereo crystal	1.85
SX3M Stereo crystal	1.85
X511 Mono/stereo	1.30
X5M Mono/stereo	1.30

GOLDRING G800	3.85
G850	2.95
STYLI For Above Cartridges	
Sapphire	.30
D. Diamond	1.25
GOLDRING G800 G850	1.95

MICROPHONES

CM20 Crystal Hand	.60
CM70 Planet stick metal, switch crystal	1.70
DM160 Dynamic uni-dir. ball metal	4.00
UD130 50K/600 ohm, uni-dir. ball metal	4.65
TW206	5.80

CONDENSER MIKE 600 ohm, uni-dir.

Cassette STICK MIKE with R. Control on/off switch (2.5 & 3.5 mm J/Ply)	1.45
410 Mono/stereo de luxe	4.10
MIKE MIXERS Mono	5.50
45 Lapel type, crystal	4.50

CASSETTES

Type	Low noise	Ph-nucle	Philips	Memorex	Am-pex
C45	36p	40p	50p	55p	55p
C80	45p	55p	69p	75p	75p
C120	55p	75p	105p	110p	110p
Cassette Head Cleaner				.45	
BIB Stereo Test Cassette				1.65	
AMPEX Head Cleaner De-magnetiser				1.65	

PLASTIC LIBRARY CASSES FOR 6"

Reels 20p, 6 1/2" Reels 25p, 7" Reels 30p	12p
CASSETTE CASES	D.P.
TAPES	Std. L.P.
5"	55p 65p 80p
6 1/2"	65p 75p 90p
7"	75p 90p 110p

ABAI TAPE DECK

4000DB Tape	73.50
CX40D Cassette	64.95
CS35 + CS58	79.95



Credit Terms for Callers

BUDGET SYSTEMS
BUSH Stereo System with independent Volume, Bass and Treble controls on each Speaker for optimum reproduction. Using GARRARD 2025TC Auto Change Deck with cueing device and SONOTONE 9TAHC ceramic cartridge with diamond stylus in deluxe teak plinth and cover. Today's Value £49.50. OUR PRICE £27.50 + £1.50 p. & p. 12 months Guarantee by Maker. THIS IS A BARGAIN NOT TO BE MISSED!

HEADPHONES

AMSTRAD HP55A	4.95
ROTEL 430	4.90
630	6.80
700	8.25
AKAI ABE 115	5.75
ABE 20	7.95
ABE 22	9.25
KOSS K711 (Black or Red)	9.95
K6	11.95
K6LC (with Vol. control)	13.25
K072B	15.75
K0747	18.50
HV1	18.50
PRO4AA	26.95
PRO5LC	28.75
EBP6	42.75

LENCO ELECTROSTATIC

Mono/stereo super de luxe 8-16Ω	2.75
Headphone Adaptor	2.50

IN-CAR ENTERTAINMENT SECTION

Car Cassette Stereo Player and Two Speakers	20.95
Car 8-track Stereo Player and Two Speakers	16.50
SHIBUYA 8-track Player/Main/Car detachable with 2 separate sets of Speakers	39.95
Pair of Car Stereo Speakers	3.85
Pair of Car Stereo Speakers (Door Mounting)	3.95

NEWMART ELECTRONICS

MAIL ORDER DEPT. (PW/11)
BELMONT STREET
MONTON, ECCLES
MANCHESTER

CALLERS WELCOME AT OUR BRANCHES

Manchester 30-32 Shudehill 061-832 7710	Liverpool 15 Whitechapel 051-236 0738
Leeds 4 New Market St. 0532 42708	Sheffield 20 Pinatone St. 0742 79308

ALL MERCHANDISE FULLY GUARANTEED Tel. 061-789 5268

COMPLETELY NEW!

NOW YOU CAN BUILD AN ERNIE IN YOUR OWN HOME



LEARN THE DIGITAL LOGIC COMPUTER TECHNIQUES.

A MULTIPURPOSE ELECTRONIC DICE. AVAILABLE AS A COMPLETE KIT.

Build something completely out of the ordinary: something different and more exciting than everyday repeated stuff. MINICOMP 100* is effectively a miniaturised ERNIE that displays truly RANDOM NUMBERS using NIXIE tubes: at the mere touch of a button. Four range selections are included according to the application: between 1-6 (DICE), 0-36 (ROULETTE), 1-57 (POOLS DRAWS), and between 0-99 (BINGO), BATTLESIPS AND ALL OTHER NUMBER GAMES). The numbers revolve round at high speed in a spectacular DICE fashion before a random number is selected and displayed. Building Minicomp will familiarise you with sophisticated logic techniques and elements used in a digital computer.

A COMPLETE KIT includes 7 latest LOGIC I.C.'s, 3 transistors, 2 NIXIES, 3 printed circuits, the power supply and various other components. Elegant-sized and finished case, approx. 7" x 5" x 3". Easy to build with illustrated instructions and descriptions of the LOGIC circuits.

APPLICATIONS: With the MINICOMP it is now possible to play electronically all possible NUMBER GAMES e.g. ROULETTE, BINGO, BATTLESIPS, CRAP DICE. An interesting application is filling in the POOLS DRAWS. The pure random nature of the DRAWS could well contribute to the winning combination.

A PROFOUND ATTRACTION FOR PARTY GAMES, FETES & BAZAARS. U.K. PRICES: COMPLETE KIT WITH ILLUSTRATED INSTRUCTIONS. Mains operated unit, 240V 50HZ or 110V 60HZ.

MINICOMP 100 £21.97, including P. & P. & V.A.T.
Fully built, tested units with a year's guarantee £24.87

TERMS: C.W.O. MAIL ORDER ONLY.

MICROELECTRONICS
51 Mexfield Road, London SW15 2RG. Tel: 01-870 2368
* Patent applied for.

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88-108Mcs, with circuit diagram. £2.30p.

P-C BOARDS (not computer panels)
1 off 6 transistors single wave band
1 off 4 transistor audio
1 off 3 transistor £1.60 the three.

10 COMPUTER PANELS packed with components including one panel with 2 Power Transistors. £1.00.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 30p each, 4 for £1.00.

All Transistor STEREOGRAM CHASSIS. Medium, Long and VHF/FM. 3 Watts per channel S/M rating. With circuit service manual. Less tuning scale which can be obtained from well known British manufacturer . . . £20.

Colour Translator panels, as used on well known British E.V.R. Teleplayer. All new panels and components. Type and contents of transistors listed below. Each panel £3.50 each.

X605	.14 off BC148, 2 RCA ca3054(ic), 1 crystal 4.433618MHz.
Z607	.12 off BC148, 1 BC158, 1 BC108, 1 RCA ca3046, 1 RCA ca3045(ic).
Z608	.23 off BC148, 2 BC158.
Z612	.12 off ME4102, 2 BC251B, 1 BFY50.

CRYSTAL CALIBRATOR (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz-10MHz (harmonics up to 30MHz) power required 300V DC 15mA. 12V 0.3A DC. Test equipment for 62T M/R.C. £2.50 each.

WIRE-WOUND RESISTORS. Our selection of mixed Ohms and Watts. 25 for £1.50, 50 for £2.50, parcel of 1,000 £30.00.

ALL ITEMS INCLUDE VAT
All items post paid in GREAT BRITAIN

SURPLECTRONICS
216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.



MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

A W. GUZELIAN (Coniston, Lake District) has been trying his H.R.O. receiver and 45ft outdoor aerial on the medium waves. His log includes BBC local radio stations at Blackburn on 854kHz; Sheffield 1034kHz; Leeds 1106kHz; Merseyside 1484kHz; Stoke 1502kHz; Nottingham 1520kHz; Teesside 1546kHz; together with programmes in English from the Voice of America (VOA) Munich 173kHz (1734m) on the longwaves at 1600hrs; Milan, Italy on 899kHz at 2300hrs; American Forces Network (AFN) Berlin 935kHz at 2325hrs; Radio Eireann 1250kHz at 1430hrs (low power relay at either Dublin or Cork).

Keith Lavelle (Manchester) has a 10 transistor radio and an outdoor spring-loaded whip antenna. He reports hearing BBC Radio Leeds on 1106kHz; Sheffield 1034kHz; Stoke 1502kHz; Bristol 1546kHz; Manx Radio (Isle of Man) 1594kHz; Trans World Radio, Montecarlo 1466kHz.

J. Hallos (Warrington, Lancs) has built the *Practical Wireless* General Coverage receiver which he is using with a 12ft indoor aerial attached to a 6ft curtain rail. He reports hearing Manx Radio 1594kHz at 0800hrs; Radio Eireann 1250kHz; Radio Leicester 1594kHz at 1400hrs; Bristol 1546kHz; Nottingham 1520kHz; Stoke 1502kHz.

VHF/FM DXING

by SIMON DAVID

FOLLOWING a report a few months ago, **David Gardner** of Dublin has kindly forwarded to me a copy of RTE Guide which covers v.h.f. and television broadcasts from the Republic of Ireland. Radio Na Gaeltachta has only recently opened, broadcasting news, local events and Irish music. Stations have been set up to transmit from Truskmore 91.90MHz, Maghera 97MHz, Mullaghinish 91.30MHz, Kippure 89.10MHz, and Mt. Leinster 90.40MHz all on the v.h.f./f.m. band. Others are on medium wave 240m, 556m, 312m. Irish is spoken throughout while RTE maintains a mainly English speaking service on 89.7MHz, 94.1MHz, 95.3MHz, 94.9MHz respectively.

David says that RTE will verify reception reports, but is still awaiting acknowledgement from R. Na Gael, who have small studios at Casla, Connemara, Co. Galway, Eire. They are a part of RTE, but do not carry commercials. It apparently arose following the setting up of a "pirate" station in the west. This resulted in the "pirate" operator being engaged officially to run R. Na Gael.

Roy Patrick of Derby has taken his v.h.f. receiver on holiday with him on the East Coast (keen DXer!), but unfortunately did not have much DX success. Moving on to Farnborough, Hampshire he picked up Rouen 96.5MHz (loud and clear), Boulogne 99.9MHz (excellent quality) and back in hometown just managed to pick up Boulogne again.

Tim Thorpe (Lowbands, Glos.) has become intrigued with the performance of his Murphy transistor portable after dark. Using its internal aerial he has logged programmes in English from AFN Germany on 872kHz and 1142kHz; Vatican Radio 1529kHz at 2045hrs; TWR Montecarlo 1466kHz at 2100hrs; Radio Berlin International 1511kHz at 2145hrs; Radio Tirana, Albania 1394kHz at 2200hrs; Radio Prague 1286kHz at 2200hrs; Radio Warsaw 1502kHz at 2230hrs; Radio Portugal 755kHz at 2245hrs; Radio Sweden 1178kHz at 2245hrs.

Harold Emblem (Mirfield Yorkshire) has received a verification from the low power Radio Rabat, Morocco 818kHz and he mentions that this station signs off at 0300hrs GMT with "Huna Rabat". This is a good time of year to listen to medium wave stations from North Africa and the Middle East. During the period of Ramadhan, which falls between the 28th September and 27th October this year, many stations are on the air all night and some of them are quite conspicuous after 2300hrs GMT. Listen for Algeria on 533kHz, 548kHz, 890kHz and 980kHz; Tunisia on 629kHz and 962kHz; Libya 1124kHz and 1250kHz; Egypt on 620kHz; Kuwait 1345kHz; Baghdad 760kHz; Beirut 836kHz; Morocco 935kHz; Saudi Arabia 587kHz; Syria 957kHz; Turkey 1061kHz. On the long waves look for Azilal, Morocco on 209kHz (1435m) in Arabic and Tipaza, Algeria 251kHz (1195m) in French.

The BBC transmitter at Moorside Edge on 692kHz (434m) is being increased from 150kW to 300kW to help listeners whose reception is affected by interference from a station in East Germany. The Radio 4 transmitter at Swindon on 692kHz has been changed to 1340kHz (224m) which is marked "Northern Ireland" on many tuning scales.


Charles Molloy

Mr. Patrick used a Grundig "Music Boy" receiver.

In some places it is possible for the aerial to pick up not only the direct signal from the transmitter but also signals which have been reflected from tall buildings, hills or other large objects. This is known as multipath interference and it can cause very unpleasant distortion. The directional properties of a carefully-positioned multi-rod aerial can often be exploited to reduce the pick-up of the reflected signals and thus eliminate the interference. If the received signals are too strong this could give rise to 'intermodulation' or interaction between two or more received signals which may result in a 'birdie' background noise on one of the channels—usually Radio 3. Modern receivers are tending to overcome this effect by using special circuitry.

If this form of interference is experienced, it is better to reduce the signal input by using an attenuator in the aerial lead, other than by using a less efficient, and therefore less directional, aerial. Variable attenuators are available and the value to choose is the one which reduces the signal input just sufficiently to remove the 'birdies' without allowing background hiss to be introduced.

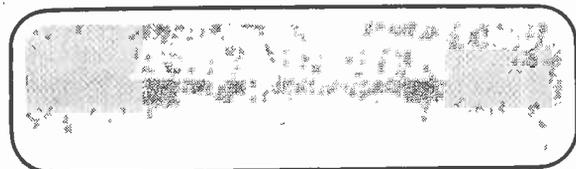If any readers have taken a v.h.f. f.m. receiver on holiday with them, especially when travelling abroad, I shall be pleased to hear from them. We are particularly interested in reception, DX or otherwise, from foreign stations. I would also welcome cassette tape recordings of readers' f.m. reports. Please enclose your full name and address and 4p stamp for the return of your cassette.



SHORT WAVES

by DAVID GIBSON, G3JDG

THE summer is now firmly behind us. No more mobile rallies and outings. Which means, I hope, that everyone will have a concentrated onslaught of listening on the Amateur Bands. How about making it a 40 metre autumn/winter? A listen for a minimum of fifteen minutes on 7MHz before you nip off to the more lucrative DX segments of 14 and 21MHz. Spare a thought too for ten metres. Could be interesting bearing in mind that we are only a couple of years away from a sunspot minimum.

One person keeping an r.f. eye on the l.f. end of things is **Stanley Sharred** (Birmingham). He managed to locate a "good" CR100 for the princely sum of £2. He uses it as a back-up to his CR150/2. Using a horizontal Vee antenna (60ft./leg) the following c.w. titbits were logged on topband; GM8MJ, EI9J, LU5HFI, OL1API, PY1RO, ZP9AY, with a couple of GW's and PA0HHV on s.s.b. A sniff around 3.5MHz raised s.s.b. squeaks from; C31DM, FP8DH, KP4AN, PY2FUS, VO1FG, W1FVD, WA3OVC, 3A2EE, 7X2MD. Even the dreaded forty metres was given a "Sharreding" to yield goodies on the c.w. like; CM2BG, CP5GM, K4JO, LU5HFI, WA5WPB, YV3TMD, Z12MM, ZM2AFH, and s.s.b. from; LU7BDZ, PY7BHX, VK2WC, YV5CYS.

Readers' Logs

Guy Dean (Ringwood) is the proud possessor of a FR50B amateur bands receiver plus a PR30 pre-selector. Antenna is an inverted Vee trap dipole with the apex at 44ft. Three band log is as follows. Eighty metres; HC1HA, K2LWR, K4CYU, OY5NS, VE1DI, VE1ED, VO1BT, VO1FG, PY1HA, WA2CLQ, W2NR, W3HFV, W5BS. Twenty metres; CE3AEV, CP1WB, CR6RJ, EP2MJ, ET3DS, ET3USA, HC2WF, HC7RD, HP1IW, HR1RSP, HZ1AB, JA4ZA, JY3ZH, JY6GT, JY8LE, KG4CA, KG4FS, KP4DSC, OA4HI, PZ1DR, TF3SV, T12KF, VE8RC, VE8RCS, VK3BJB, VK3PA, VK5AS, VP3MKE, VU2DK, VU2JM, WA7UKQ, W6KMC, W7IJZ, YV4TY, YV5EED, 5Z4JE, 6Y5GB, 9J2DC, 9X5NA, 9Y4BO. Fifteen metres; A4XFJ, A6XP, CE3ABZ, CE3EGW, CP1FG, CR6AD,

CR6AG, CR7OL, EL1G, EL9C, HK3AUE, HK3LT, KP4AOW, KZ5USA, LU1DAB, LU3KAX, OJ0AM, PY2BFJ, TR8AF, VQ9BP, YV3VU, ZD7FT, ZD8AW, ZE1AD, ZE4JW, ZE7JR, ZP5HJ, ZS1FH, ZS4GF, ZS5EL, ZS6QD, 5H3JL, 5T5DY, 5Y4XNH, 5Z4JE, 3D6AU, 9K2JM.

Listening on a CR70A receiver, PR40, a.t.u. and 264ft. end fed, **D. Dance** (Roxburghshire) heard some nice tweets on the h.f. bands. On twenty metres c.w., for example; CN8BO, CR6BX, DU1OR, OA4XK, PY2BOS, PY7VOU, PZ1CP, VP9CB, with s.s.b. from; DU1JMG, EL9C, HV3SJ, VE8RCS, 7X2MD, 9M2LN. Up on fifteen metres c.w.; CN8BO, CR6AL, CR6MX, EA8FE, EA8FS, EL0S/MM (near the Brazilian coast), FG7TG, KZ5EK, LU1HDC, VP9CB, YV3VU, ZC4BI, 9X5NA. Best on ten metres were; ZC4CY, 9H1CH on c.w. with LX1PD, MIC and 9J2DT on s.s.b.

J. England (Brighouse) has a "30ft. long wire aerial, arranged as a spiral in the loft". Dizzy signals arriving from it are fed unmercifully into a CR45 receiver. The log for twenty metres reads; CE3AIU, HC1SS, HK6CPS, LU3FAQ, LX1DAV, PZ6AA, VE2WF, VE7XF, VK2BHR, VK3MO, VR1FL, VP1TB, W9XRP, XE1PO, ZD3D. The same gear on eighty metres managed to locate; CN8HD, CT2AK, OY7JO, OY2X, VE1ZAN, VE3GCS, W2NIN, XE1CV, 4X4KT.

Signals arriving at the ears of **L. Large** (Hassocks) have to walk a 600ft. tightrope. At least that's the length of the antenna which can truthfully be described as a long wire. Apparently it was 1,000ft. long but low-flying motor vehicles proved a hazard. At the end of the line is a 9R59DS receiver and a page in the log marked 14MHz which reads; EI6S, F9JA, G13GRD, HZ1SH, LX1RR, K6UA, VO5BZ, TF5TP, VE1AM, VE8RCS, YV5AS, 3A2C. On 21MHz the best were CR6QR, and TR8VE.

Loose on 14MHz with an R107, homebrew a.t.u. and 132ft. end fed is **D. Douglas** (Leicester). His best on 14MHz were; CE3AX, CN8BO, CP5CW, CR3WB, CR7EH, EA6BG, EA8CR, EP3SP, ET3RS, ET3USA, HM1AQ, HR1BS, HZ1AB, JW1SO, JY6ZZ, KG6JBE, KP4DDO, KZ5JM, MP4BJP, OX3BH, VE1PV, VO1JR, YN9GL, YV3VU, ZB2BZ, ZE4JG, ZL3UY, ZP5GE, 3V8CA, 4S7BR, 4W1BC, 4X4BA, 4Z4BA, 7X2MD, 9J2DT, 9L1VW, 9Y4PL.

Bernard Hughes (Worcester), JR310 receiver, dipole, bagged these on 14MHz; CR7AG, HR1RSP, HZ1AB, HM1AQ, JX3P, JY6KAM, JA3AJW, KG6JAP, KZ5OH, LG5LG, VQ9MC, VP2VAP, VP2VS, VK2BKG, VK3ALL, WA7PMI, WA7BPS, ZL1JJ, ZD7FT, ZD3D, ZK1DX, 5W1AU, 9V1QO, (9G1HE, 9J2EP. Curses, all Gibbies best gone for a chop—

Events

Contests and events for October include: October 6-7, Oceana contest (phone); 6-7, u.h.f. national field day; 6-7, 432/1296MHz contest; 13-14, Oceana contest (c.w.); 13-14, fifteen/ten metre contest; 20-21, WADM contest (c.w.); 20-21, forty metre contest (c.w.). November 3-4, forty metre contest (phone); 3-4, two metre and 70cms contest.

BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

Medium Waves Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

AMATEUR BANDS

Short Wave/VHF

Logs in alphabetical order please by 15th of the month to David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.


SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS.
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

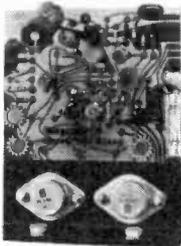New Versions using 3A 'Plastic Power' Driver Transistors Now Available. To meet demand, we have included a more powerful module in our well-established and proven range. These power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



SA35 35 watts RMS. Uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

A NEW ADDITION IS THE

SA50 at £5.65

Carr. paid. A rugged, well built unit, capable of 50 watts R.M.S. out, with all the advantages of Saxon Amplifier design and quality. Ready now.

SA100 makes an ideal unit in disco assemblies. A real glutton for work. **£10.90**

Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid.

BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN and SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA100.

Freq. response 15-40,000 Hz \pm 1dB
Distortion 0.2% at 1 kHz
Loads 4 to 16 ohms
Quiescent current 15 mA
Noise Better than -75 dB
Supply voltage SA35 25-45 volts
SA50/SA100 40-70 volts
Size 4" x 4" x 1" (SA100)
4" x 3" x 1" (SA35/SA50)

Circuits, connecting Instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilized supply for 2 SA25/35	£4.90
PU70	Unstabilized supply for one or two SA100	£7.75 carr. 40p
PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

Orders and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.

Telephone 01-684 6385

Hours 9.30 a.m.-5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED

TWO NEW PA/MIXER CONTROL UNITS

Using grouped pairs of inputs and outputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master control. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos etc. Standard jack sockets. Compact design. In strong metal cases. All units guaranteed for 3 years.

•M.4H

4 high Z, 4 low Z inputs, 4 sets of controls. Case 14" x 8" x 2 1/2". Carr. pd.

£18.50 + V.A.T.

•M.6HL Case 18" x 8" x 2 1/2"

12 inputs (6 high Z, 6 low Z). Carr. pd.

£27.50 + V.A.T.

• Channel section modules, for building your own mixer. Gain—16 x (24dB). Tone controls—18dB swing. Carr. pd. £3.50 + V.A.T.

SAXON CONTROL UNITS

Mono (as shown)

Carr. 20p. **£6.50**

Stereo. Carr. 30p.

£15.80



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic input.)



120 WATT HEAVY DUTY MODULE

Rugged class A driver stage, this module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 T03 can (15 watt) output transistors. These are the modules where extra power is demanded.

Power output 120 watts into 8 ohms
Freq. response 20-20,000 Hz \pm 2dB
Input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)

Module only **£13.90**
(Carr. 20p)

Low distortion parallel push-pull output stage.

Module & power supply **£18.95**
(Carr. 40p)

160 watt version with power supply **£27.50**
(Carr. 50p)

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3KW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3KW lighting load. Smartly finished steel case. Carr. 30p.

£19.75

SINGLE CHANNEL UNIT


Operates from 5 to 100 watt amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p.

Carr. pd. **£8.90**

COMPLETE AMPLIFIERS

CSE 100. £34.90 carr. free

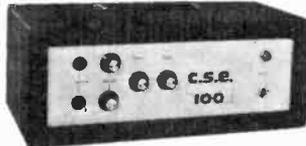This versatile unit is now available in a black vinylde case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls.



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

600 Watt 3 colour Light Boxes Smart Raxine finish £15 carr. free.



SAXON 100 £48.50 carr. free

LOUDSPEAKERS British made bargains!!
12" 25 watt 8/15 ohms £5.95 carr. 30p. 15" 50 watt 8/15 ohm £14.50 carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.

A.K.G. MICROPHONES

D11 DHL IDEAL DISCO MIKE ONLY £9.45 (rrp £11.00).


Prices quoted do NOT include V.A.T. 10% must be added on to total value of order for V.A.T.

S.A.E. for special price list.


TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by regd. letter, please

GOING BACK...

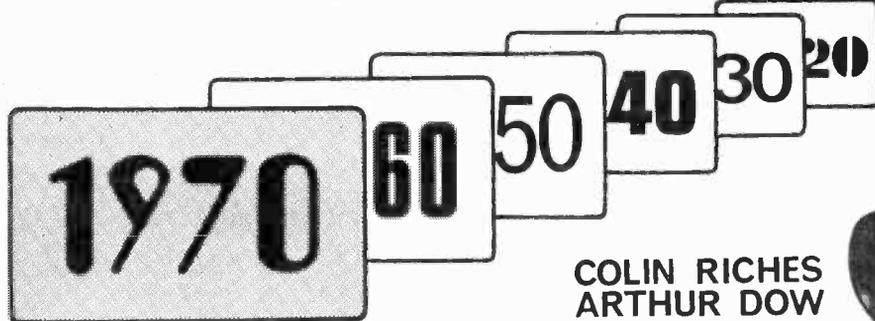

COLIN RICHES
ARTHUR DOW

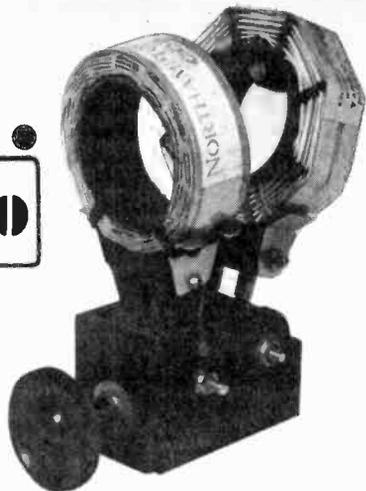

WE'D like some help and information as soon as possible on early wireless equipment manufactured by "H.P.R. Wireless Ltd." Mr. R. J. I. Moon, lately of Guildford, Surrey, has, in the process of moving down to Cornwall, kindly passed on to us some single valve units comprising tuners, detectors and audio stages. These used to be connected together to form a complete receiver and we even have the original heavy copper wires used for that purpose, with end loops perfectly formed.

So far we have not been able to trace the makers in any of our old catalogues but we believe the units are typical of the early 1920's. The units are housed in the inevitable mahogany boxes with black ebonite panels and the equally inevitable brass terminals, each panel being engraved "H.P.R. Wireless Ltd."

Mr. Ray Williams of Grantham, Lincs, thinks enough of our humble efforts to have extracted all the Going Back pages from past issues of the magazine and to have bound them together to form a 'useful reference work'. Another reader wonders if we are going to do a reprint of our offerings! Any

more letters like that and we shall have enough evidence to demand of the Editor that something be done!

Not quite vintage but of great interest to Ray Williams are two Utility receivers of the last war, both in perfect working order. In view of the vast numbers of these sets that must have been turned out at the time there must still be many thousands out of sight in attics, storerooms, garages etc. So, go to it, Going Back'ers and follow Ray's favourite haunts, 'derelict buildings, under wood piles and in odd corners'. One ancient set was brought round by a neighbour who thought it was a war-time bomb!

Mr. Williams was also kind enough to send along a photograph, reproduced herewith, of some of his treasures which number twenty eight, so far. He specialises in early crystal sets and has collected some specimens in mint condition. The apple of his eye is an Ediswan crystal set, as new, in its original carton! This was featured on BBC TV in 'Nationwide' in July last year. So . . . oh, when you buy that transceiver keep the carton, it could be worth a bomb in fifty years time!




Mr. Ray Williams from Grantham is pictured here with some items from his vintage radio collection.

QR! QR! QR! QR! QR!


Information Wanted

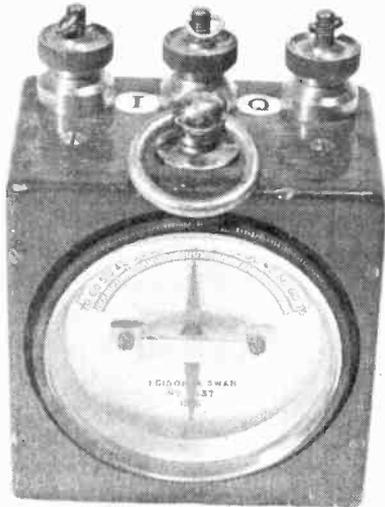... any information appreciated on this meter. Front dial reads 70-0-70 Edison and Swan No. 11637—1916. Top terminals read I and Q.—**R. J. Goodman**, 26 Killarney Road, Wandsworth, London, SW18 2DX.



... I wish to restore a Gecophone 3-valve a.c. receiver, Frequency is 50/80m and voltage input 200-250V. Number is BC 3130. Inst. No. 7327. I would be glad of any information on this set and a suitable speaker to use with it.—**Maurice Dean**, 29 Lea Road, Dronfield, Sheffield, Yorks.

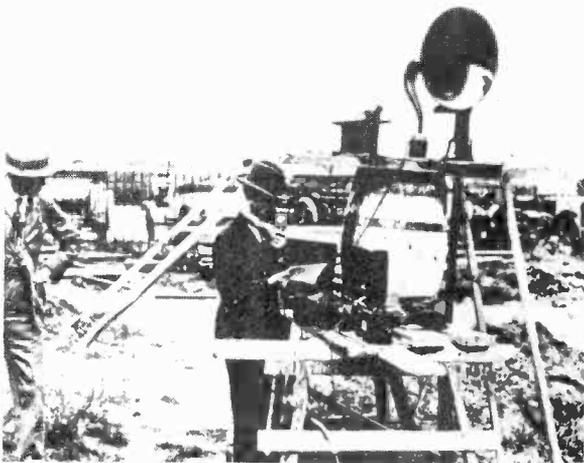... information regarding valves in a two-valve Gecophone model BC 3250 (c1926)—**David James**, 12 Circus Street, Greenwich, London, S.E.10.



This BBC photograph shows an Outside Broadcast commentator at the Brooklands Race Track in 1922.

TRANSFORMERS

MAINS ISOLATING SERIES
Primary 120/240 Volts Secondary 120/240 Volts Centre Tapped and Earth Shielded

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	£	P & P p
07	20	1 8	7.0 x 6.0 x 6.0	1.94	30
149	60	3 12	9.9 x 7.7 x 8.6	2.88	36
150	100	5 8	9.9 x 8.9 x 8.6	3.16	52
151	200	8 0	12.1 x 9.3 x 10.2	5.31	52
152	250	13 12	12.1 x 11.8 x 10.2	7.01	67
153	350	15 0	14.0 x 10.8 x 11.8	9.40	82
154	500	19 8	14.0 x 13.4 x 11.8	13.55	—
156	1000	38 0	17.2 x 16.6 x 14.0	24.97	—
158	2000	60 0	21.6 x 15.3 x 18.1	41.25	—

PLEASE NOTE NEW ADDRESS AS BELOW

AUTO SERIES

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	£	P & P p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.02	22
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.00	30
4	150	3 4	8.9 x 7.7 x 7.0	0-115-200-220-240	2.42	36
66	300	6 4	9.9 x 9.6 x 8.6	"	4.70	52
67	500	12 8	12.1 x 11.2 x 10.2	"	6.93	67
84	1000	19 8	14.0 x 13.4 x 14.3	"	12.69	82
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.39	—
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.00	—
73	3000	40 0	21.6 x 13.4 x 18.1	"	32.67	*

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets. £9.49. P & P 67p. Also available a 20 Watt version 12-02 P & P 27p.

LOW VOLTAGE SERIES (ISOLATED)

PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	£	P & P p
111	0.5	0 25	8	4.8 x 2.9 x 3.5 0-12V at 0.25A	2.10	22
213	1.0	0 5	12	6.1 x 5.8 x 4.8 0-12V at 0.5A	2.12	22
71	2	1 1	12	7.0 x 6.4 x 6.1 0-12V at 1A	2.16	22
18	4	2 2	12	8.3 x 7.7 x 7.0 0-12V at 2A	2.24	30
70	6	3 3	8	8.9 x 8.0 x 7.7 0-12V at 3A	2.70	42
108	8	4 5	8	9.9 x 8.9 x 8.6 0-12V at 4A	3.00	52
72	10	5 6	4	9.9 x 9.6 x 8.6 0-12V at 5A	3.55	52
17	16	0 8	12	12.1 x 9.9 x 10.2 0-12V at 8A	5.48	52
115	20	10 11	8	14.0 x 9.6 x 11.8 0-12V at 10A	6.98	67
187	30	15 15	8	14.0 x 12.1 x 11.8 0-12V at 15A	12.90	82
226	60	30 32	0	17.2 x 15.3 x 14.0 0-12V at 30A	23.72	*

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.22	22
79	1.0	2 4	7.0 x 6.7 x 6.1	"	1.62	36
3	2.0	3 4	8.9 x 7.7 x 7.7	"	2.43	36
20	3.0	4 8	9.9 x 8.3 x 8.6	"	2.99	42
21	4.0	6 4	9.9 x 9.6 x 8.6	"	3.55	52
51	5.0	6 12	12.1 x 8.6 x 10.2	"	4.42	52
117	6.0	8 0	12.1 x 9.3 x 10.2	"	5.28	52
88	8.0	12 0	12.1 x 11.8 x 10.2	"	6.82	67
89	19.0	13 12	14.0 x 10.2 x 11.8	"	8.36	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	1.60	30
103	1.0	2 12	8.3 x 7.4 x 7.0	"	2.34	36
104	2.0	5 8	9.9 x 8.9 x 8.6	"	3.25	42
105	3.0	6 12	9.9 x 10.2 x 8.6	"	4.41	52
106	4.0	10 0	12.1 x 10.5 x 10.2	"	5.48	52
107	6.0	12 0	14.0 x 10.2 x 11.8	"	8.63	67
118	8.0	15 8	14.0 x 12.7 x 11.8	"	10.12	82
119	10.0	25 0	17.2 x 12.7 x 14.0	"	14.13	*

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-428-69C	1.62	36
126	1.0	3 4	8.9 x 7.7 x 7.7	"	2.26	36
127	2.0	6 4	9.9 x 9.6 x 8.6	"	3.55	42
125	3.0	8 12	12.1 x 11.8 x 10.2	"	5.41	52
123	4.0	13 12	12.1 x 11.8 x 10.2	"	6.98	67
120	6.0	15 8	14.0 x 12.1 x 11.8	"	10.12	82
122	10.0	25 0	17.2 x 12.7 x 14.0	"	16.75	*


LEAD ACID BATTERY CHARGED TYPES

Ref. No.	Amps.	Weight lb oz	Size cm.	£	P & P p
43	1.5	1 8	7.0 x 6.1 x 6.1	1.61	30
5	4.0	3 4	8.9 x 7.7 x 7.7	2.45	42
83	6.0	6 4	9.9 x 9.6 x 8.6	3.70	52
146	8.0	6 12	9.9 x 10.2 x 8.6	4.22	52
58	12.5	12 0	14.0 x 10.2 x 11.8	6.19	67

All ratings are continuous. Standard construction; open with solder tags and vacuum impregnation. * Carriage via B.R.S.
FULL SPEC. TRANSISTORS
BC107/108/109 12p each | 2N 3055 60p each | AD161 162 60p pair
+ mica and bushes | + mica and bushes

ELECTROSIL RESISTORS · AVOMETERS
PLEASE ADD 10% FOR V.A.T.
INCLUDING P. & P.

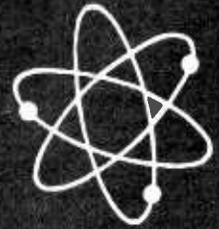BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE 01-488 3316/8
NEAREST TUBE STATIONS ALDGATE & LIVERPOOL ST.



TRANSMIT/RECEIVE CONTROL BOX

R. H. LONGDON

THIS device is intended to control a transmitter and receiver, but can be used for other purposes, as explained. It gives complete control of suitable home-built equipment, without the need for any relay, or relay supplies.

Fig. 1 is the circuit, based upon the use of a 4-wafer 3-way rotary switch. Switch positions are numbered 1, 2 and 3. The back wafer S1a transfers the circuit from co-axial socket Sk1 to either co-axial socket Sk2 or Sk3. Wafer S1b closes the circuit in position 3. Wafer S1c closes in positions 2 and 3, while the front wafer S1d closes in positions 1 and 2.

METHODS FOR USE

Uses for the control box in an amateur station include the following:

Rx/Tx Control

Plug the aerial or tuner lead into Sk1. Run a co-axial lead from Sk2 to the receiver, and a similar lead from Sk3 to the transmitter. Disconnect the transmitter p.a. h.t. lead from the power pack, and take to A, running a lead from the second terminal A to the power pack. Similarly place B-B in the v.f.o. or v.f.o. h.t. circuit. Disconnect one receiver speaker lead from the speaker and take to C, adding a lead from the speaker to the second terminal C.

Position 1 then provides reception. Position 2 allows the v.f.o. to be tuned to the receiver frequency. Position 3 puts the transmitter on, and receiver off.

Aerial Selection

A dipole may be available for one band, and an end-connected wire for other bands. For such purposes, or a direct comparison of aerials, connect one aerial to Sk2, the other aerial to Sk3, and the receiver to Sk1.

Aerial/dummy load

It is sometimes convenient to run a transmitter output temporarily into a dummy load. For this, connect the Tx to Sk1, the aerial (or tuner) to Sk2, and dummy load to Sk3. For modulation and other tests the dummy load can be a household lamp. Should the dummy load be of known impedance, such as 75 ohms, it can be useful to load the transmitter into this correctly. Then switch to the aerial tuner and adjust the tuner for the same Tx p.a. input reading. A dummy load with r.f. meter is also very useful for obtaining optimum transmitter output.

Receivers

It is sometimes convenient to switch from one receiver to another, for comparison, or because they are most suitable for different purposes (such as general coverage and amateur band only receivers, or h.f. band and l.f. band receivers). This can

be done by using Sk2 for one receiver, and Sk3 for the other. Where necessary, the speaker of the receiver not in use can be muted by using terminals A-A, and C-C.

Transmitters

Sometimes a 10W Tx may be used for 160m, and a larger transmitter for other bands. Sk2 can then go to one Tx, Sk3 to the other Tx, and Sk1 to the aerial tuner.

Transmitting Aerials

It is sometimes useful to compare one transmitting aerial with another (e.g., a vertical and long wire) while transmitting. This can be done by taking the Tx to Sk1, and the aerials (with tuners, where required) to Sk2 and Sk3. Other uses will no doubt suggest themselves.

EFFICIENCY

When this method of change-over was first used, there was some doubt about r.f. efficiency, and the possibility of switching high voltages.

R.F. efficiency was compared by feeding r.f. from a Tx to an r.f. wattmeter direct, then through the control box, on 28MHz and lower frequencies. No difference in wattmeter readings could be seen.

R.F. feedthrough from Tx to Rx when transmitting depends on the equipment and layout elsewhere, as well as on stray coupling in the box. It was never large enough to cause trouble. An extra wafer was tried with the control of a large transmitter, to short Sk2 (receiver aerial) to earth, when transmitting. This was not incorporated in the control box as it was felt to be unnecessary.

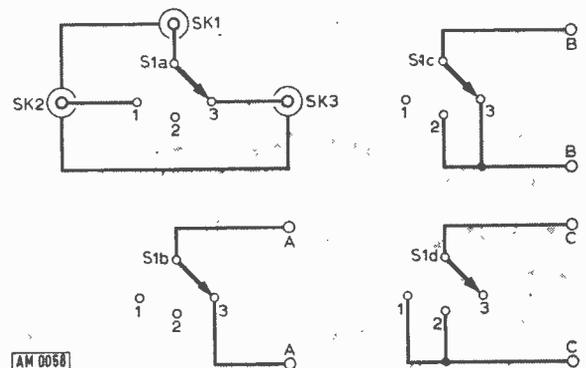


Fig. 1: Circuit of the tx/rx control box

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £11.90. P. & P. 40p.

DE LUXE STEREO AMPLIFIER



A.C. mains 200-240 v. U.S. & J. heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: -2 x ECL86 Triode Pentodes. 1 x EZ90 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono). Into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £9.90 P. & P. 50p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7v, and 9v, and 12v. at 1 amp continuous (1amp intermittent).

Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready PRICE £5.00 P. & P. 35p. built and tested.

BLACK ANODISED 16G. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 6p.

HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" 5 for 55p P. & P. 23p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-10-15-20-25-30-35-40-50V. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30, at 2amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2-10 P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri 200/240V. Sec. 9-0-9 at 500mA. £1.00. P. & P. 25p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.10. P. & P. 25p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.65. P. & P. 35p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100uA. For bass or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 86p. P. & P. 12p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300V. Frequency response 15Hz-25kHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price £1.00 P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

Must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents 80p
Transistor Equivalents 90p
Transistor Characteristics £2.15
POST FREE.
All three together £1.60

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias. 95p, Post Free

Open 9-5.30 Monday to Friday, 9-5 Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C129 AUTOCHANGER UNITS with latest stereo/mono compatible cartridge £7-80 + 50p P. & P.

GARRARD SP25 Mk III with heavy precision machined die cast turntable £10-58, carr. 55p.
PRECISION ENGINEERED PLINTHS
Beautifully constructed heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover).
NOW ONLY £4-85, P. & P. 70p.

LATEST ACOS GP91/100 mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 15p.
SONOTONE STANO COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-30 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2-80. P. & P. 15p.
LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/80/78. £1-63 P. & P. 15p.
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £4-50 P. & P. 50p
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £5-85 P. & P. 60p.

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Ynairn front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohm impedance.

OUR PRICE £9.25 Carr. 75p
Cabinet Available Separately £4-95 Carr. 65p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £7-15 Carr. 75p

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. £3.30 P. & P. 40p BARGAIN PRICE

LOUDSPEAKER BARGAINS

5in. 3 ohm £1-05, P. & P. 15p. 7 x 4in. 3 ohm £1-15, P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-90, P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1-62, P. & P. 20p. E.M.I. 13 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £2-50, P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4-65, P. & P. 30p. EMI Ceramic magnet heavy duty tweeter. Approx 3 1/2". Available 3 or 8 or 15 ohm £1-25 + 20p p. & p.
BRAND NEW 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hifur ceramic ferrobar magnet assembly £7-50. Guitar models: 25w. £7-50 35w. £9-85. P. & P. 45p



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS

With large ceramic magnet and Plastolene cone surround. 8 ohm impedance. £2-70. P. & P. 35p.


Also available specification as above but size 10" x 6" £2-70 and size 8" round £2-60. P. & P. 35p.
12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm £2-45, P. & P. 36p.
35 ohm SPEAKERS 3in. only 70p P. & P. 25p.
"POLY PLANAR" WAFER-TYPE. WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceiling, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £2-55 each. P. & P. 34p.

VELAR & HEXINEX SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price 85p yd. length. P. & P. 25p per yd. (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 1/4 inch jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £2-80, P. & P. 25p.

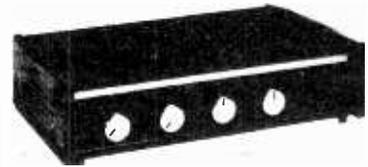HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first 5 stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 15-20,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -18dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Full detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. AMPLIFIER KIT £11-55 P. & P. 25p (Magnetic input components 33p extra) POWER PACK KIT £2-30 P. & P. 35p CABINET £2-30 P. & P. 35p (Post Free if all units purchased at same time) Full after sales service.

Also available ready built and tested £23.10. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HA3 MK II

Designed for Hi-Fi reproduction of records, A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ90 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £2-50. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA3 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4-50. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Superior reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 15p + S.A.E. (Free with parts). All parts sold separately. ONLY £2-80 P. & P. 60p. Also available ready built and tested £12-10 P. & P. 70p.

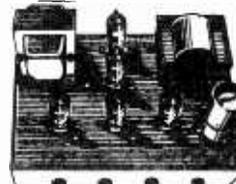

PRICES NOW INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES



GIRO NO. 331 7056
C.W.O. only. P. & P. 10p on orders below £5
Discount: £10-10%, £20-15% (except net items)
Export Order enquiries welcome (VAT free)
Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS
10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3.10 net
10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3.20 net
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7.20 net
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7.35 net
20E12 1W KIT: 20 of each E12 value, 10 ohms—1M, a total of 1220 (METAL FILM 5%), £7.50 net
15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £8.15 net
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £12.65 net

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 10000µF

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 10000µF

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 20, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000

RESISTORS
CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%
V. Type Range 1-9 10-49 50-99 100-249 250-499 500-999 1000+ Size mm
± CF 22-2M2 1 0.8 0.65 0.62 0.55 0.5 0.45 3.9x10.5
± CF 22-2M1 1 0.8 0.65 0.62 0.55 0.5 0.45 5.5x16
± MF 10-2M7 1 0.9 0.8 0.7 0.65 0.6 0.55 6.3x17
± MF 10-2M1 1.5 1.25 1.25 1 1 0.95 0.88 6.6x13
2 MF 10-10M3 2 2.5 2.5 2 1.75 1.75 1.6 8x17.5
For value mixing prices, please refer to our catalogue. (price in pence each)
VALUES AVAILABLE—E12 Series only.

PRESET SKELETON POTENTIOMETERS
MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1MΩ
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 5p each

B. H. COMPONENT FACTORS LTD. (P.W.) 61 CHEDDINGTON ROAD, PITSTONE, N.R. LEIGHTON BUZZARD, BEDS, LU7 9AQ
Tel.: Cheddington 668446 (Std. Code 0296)
PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electrolytics

1.0µF 63V	6p	68µF	16V	6p
1.5µF 63V	6p	68µF	63V	12p
2.2µF 63V	6p	100µF	10V	6p
3.3µF 63V	6p	100µF	25V	6p
4.0µF 40V	6p	100µF	63V	14p
4.7µF 63V	6p	150µF	16V	6p
6.8µF 63V	6p	150µF	63V	15p
8.0µF 40V	6p	220µF	6.4V	6p
10µF 16V	6p	220µF	10V	6p
10µF 25V	6p	220µF	16V	8p
10µF 63V	6p	220µF	63V	21p
15µF 16V	6p	330µF	16V	12p
15µF 63V	6p	330µF	63V	25p
16µF 40V	6p	470µF	6.4V	9p
22µF 25V	6p	470µF	10V	20p
22µF 63V	6p	680µF	16V	20p
32µF 10V	6p	680µF	40V	25p
33µF 16V	6p	1000µF	16V	20p
33µF 40V	6p	1000µF	25V	25p
32µF 63V	6p	1500µF	6.4V	15p
47µF 10V	6p	1500µF	16V	25p
47µF 25V	6p	2200µF	10V	25p
47µF 63V	8p	3300µF	6.4V	26p

VEROBOARD 0.1 0.15

2 1/2 x 5"	28p	28p
2 1/2 x 3 1/2"	20p	19p
2 1/2 x 3"	32p	33p
3 1/2 x 3 1/2"	28p	28p
2 1/2 x 1"	7p	7p
2 1/2 x 5" (Plain)	—	14p
2 1/2 x 3 1/2" (Plain)	—	12p
5 x 3 1/2" (Plain)	—	22p
Insertion tool	59p	59p
Track Cutter	44p	44p
Pins, Pkt. 25	10p	10p

TRANSISTORS

AC127 16p	BC212L 12p
AC128 22p	BC213L 12p
BC107 11p	BC142 17p
BC108 12p	OC44 18p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	T1543 33p
BC183L 12p	2N2926 11p
BC184L 13p	2N3702 11p

POTENTIOMETERS
Carbon Track 5K Ω to 2M Ω, log or linear. Single, 16p; Dual Gang 46p. Log Single with DP switch 26p

DIODES

IN4001 6p	IN4002 7p
IN4003 9p	IN4004 9p
IN4005 12p	IN4006 14p
IN914 7p	IN916 7p
BA100 10p	OA5 42p
OA47 9p	OA81 11p
OA200 8p	

PLUGS

DIN 2 Pin 12p	5 Pin 180° 12p
5 Pin 180° 12p	5 Pin 180° 14p
2.5mm Jack 11p	Phono 5p

SOCKETS

DIN 2 Pin 10p	3 Pin 10p
5 Pin 180° 12p	5 Pin 180° 14p
2.5mm Jack 11p	1000V 11p
Phono 5p	

Integrated Circuits

µA709C	50p
µA741C	55p
µA723C	£1
µL914	35p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans
(µF/V): 2.2/25, 2.2/63, 4.7/10, 4.7/25, 4.7/63, 22/10, 22/25, 22/63, 5p, 2/10, 10/10, 50/10, 100/10, 10/25, 10/25, 10/50, 5/1p, 200/10, 100/25, 50/50, 6p, 500/10, 200/25, 100/50, 9p, 1000/10, 500/25, 200/50, 100/100, 100/25, 50/50, 16p, 1000/50, 3p, 1000/100, 66p, 2000/25, 27p, 2500/12, 17p, 2500/25, 33p, 2500/50, 62p, 3000/50, 72p, 5000/25, 66p, 5000/50, 94p, 7000/50, 60p, 25,000/25, 74p. HI-VOLT: 8/350, 14p, 16/350, 19p, 32/350, 25p, 50/250, 18p, 100/500, 33p.

METALLISED PAPER CAPACITORS
250V: 0.05µF, 0.1µF, 0.2µF, 0.5µF, 1µF, 2µF, 5µF, 10µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 10000µF

QUANTITY DISCOUNT
SPECIAL BULK BUY PRICES
ARE AVAILABLE BY
QUOTATION FOR LARGE
PROJECTS AND TRADE

Train for television

Course commences 2nd January, 1974

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept. PW7) 34a Hereford Rd., London W2 5AJ

FELSTEAD ELECTRONICS (PW 73)
LONGLEY LAKE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only. No C.O.D. or Callie service. Charges (Min. 7p) in brackets after all items apply to I.B. and Eire only. Regret orders under 30p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas, including Eire and Channel Isles, orders less 10% off prices below, which include V.A.T.

RECORDING TAPE: Finest quality value British Mylar available: STANDARD 5" 600ft. 40p, 5" 900ft. 65p; 7" 1200ft. 82p; LONG PLAY 5" 900ft. 55p; 5" 1200ft. 69p; 7" 1800ft. £1-00 (Charges for 5" and 5 1/2" singles 9p, two to four 8p each; five and over 35p the lot. For 7" one or two 11p each reel, 3, 4 and 5 reels 33p the lot, 6 reels and over 39p the lot.) Other sizes and accessories in list. CASSETTES, Two types, Both in Library Cases, C60 33p, C90 48p, C120 72p. Deluxe Types: C60 55p, C90 72p, C120 98p. (Charges for both types, under 5.9p each, 5 for 17p). All quantities over 5.25p the lot.)

CARTRIDGES all with standard fittings and styli. Stereo-compatible Mono GP91/8C with 98p; STEREO GP93 £1.35, Stereo Ceraminc GP94 £1.75. Comparatives shown in List, with Mono types in. Sonotone 9TA/HC, Stereo Ceraminc Diamond £1.70 (All at 8p each). DIAMOND STYLII: single tip types: Acos GP37, GP69, GP65/67, GP71, BSR TCR/LP/ST, COLLARO O.P. and DC284, GARRARD GC2, GC8, GC810, GCE12, SONETTE BF40, O.P. and T. PHILIPS 3301 (3066, 3066, 3202, 3304), 3010/12/13/16, SONOTONE 19T/20T ALL AT 38p each. SAPPHIRE 16p. DIAMOND DOUBLE TIP TURNOVER TYPES (78 sap. on other side). For ACOS (GP73, GP91) for cartridges GP93, GP94, etc.: GP18C (for stereo compat. types) GP104, BSR 874, (STC), 879 (STB), 8T12/14/15, SONOTONE 9TA, 9TA, STABC, PHILIPS 3306, 3301, 3224, 3228/32, GP280, GARRARD GCM21, and 22, GCS23, GK825 and 26, GCM21 and 22T, GCM24T, CG823, GK825T and 26T, GCM31, GC835, GC835, GC838, K840A, K841B, ETC. ALL AT 68p. SAPPHIRE 32p. DOUBLE DIAMOND STYLII: same dia 8T/1P tip each side: no. 78) All types £1.35. SAPPHIRE DOUBLE 8T/1P, TIPPED 32p. DIAMOND STYLII GOLD-RING REPLICEMENTS: G800, G800H & G850, £2.25 each, G800E 23.75 (All 8T/1P 8p up to 3). PICK-UP WIRE: super thin flex, screened, sheathed, TWIN 7p per yard, 4-core 13p per yard, (either up to 6 yards, 7p). Over, charges paid. MICROPHONES: CRYSTAL: LAPL 14", clip/hand, lead 3.5mm jack plug 39p (9p). CM30 Cream Plastic hand 58p (9p); "MIC 45". Curved metal hand grip £1.10 (11p) ALL with leads. DYNAMIC: Excellent Mike, 50K Ω, only 3 1/2" long, black/chrome, switched, lead with 2.5 and 3.5 mm jack plugs £1.37 (9p). Cardoid Bal., 50K/600 Ω built in volume control, on/off switch, special 20ft lead, the best value anywhere at £6.00 (33p): Uni-dir. mesh ball 50K/600 Ω jack plug cable, adaptor, £5.28 (33p): Omni-dir. Ball mesh, 50K, cable adaptor, jack plug, £4.28 (33p) each. SPEAKERS: Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) £2.06 (33p) or pair for stereo £4.65, charges paid. SMALL 2 1/2", 3 Ω, 8 Ω or 64 Ω (state which) 41p (9p). More speakers in List. HEADPHONES: 1 1/2" resistors 2.2000 Ω adjustable £1.10 (11p). EARPIECES: with lead and min. 3.5mm or 3.5mm (state which) jack plug cable. MAGNETIC 12p. CRYSTAL (3.5mm plug only) 28p (up to 6 for 9p any size). SOLDERING IRON: Slim, modern, British high speed, 8 1/2", all parts replaceable, highest quality, fully guaranteed £1.29 (11p). TRANSFORMERS: sub-min. 11 x 11 x 12mm. OUTPUT (3 Ω for OC72, etc.) 16p or DRIVER 17p (Up to 12 for 7p), CONNECTING WIRE: Packs of 5 coils, each coil 5yds. Ass'ts. coils. SOLID CORE 16p (7p). LEXIBLE CORE 18p (9p). RETRACTABLE FLEXIBLE LEADS (COURTESY) with phono plug each end, or phono plug one end, phono socket at the other (state which) 61t, 30p; 12ft, 53p (either 7p).

VIBRATORS: 12v/4 pin non-synch. 121HD4, 2 1/2" ex. pins. 33p. SAME but 3 1/2" ex. pins. USA. 16p. 12v/7 pin synch. (12SR7) 2 1/2" ex. pins. 72p (9p any type). MAINS BATTERY ELIMINATORS: Two models, both 240V A.C. input. Suit most radios and cassette recorders/players, with front switch, pilot lights, mains and output leads Model N.R. 3, 6, 7 and 9v 400mA, stabilised with multi-output adaptor 55.50 (35p). Model S.C. has additional 12v output and is 500mA 55.00 (35p).

OUR LIST (see heading) has added to the above items more Cartridge and Stylus and Equivalent Table, Special Non-repeatable Offers, Aerials, Dials, Transistors, Multi-Leads, Plugs, Sockets of many types, Speakers, Vol. Controls, Multi-testers, Professional Microphones, Mike Inserts, Neons, Indicators, STEREO Headphones, Pocket Screwdrivers Testers, Tel. Pick-ups, Wire, Cable, etc., etc.

NEW EDU-KIT MAJOR



Total Building Costs
£7-23 P P & Ins. 44p
 (Overseas P & P £1-05)

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-FNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.
- ★ Parts Price List and Plans 40p (Free with parts).

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors, 9 Tunable wavebands as Roamer Ten Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 30p (Free with parts).

Total Building Costs **£6-95** P P & Ins. 44p
 (Overseas P & P £1-05)

POCKET FIVE



3 Tunable wavebands. M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, super-sensitive ferrite rod aerial, moving coil loudspeaker, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List 15p (Free with parts).

Total Building Costs **£2-28** P P & Ins. 24p
 (Overseas P & P 65p)

TRANSONA FIVE



Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts).

Total Building Costs **£2-50** P P & Ins. 25p
 (Overseas P & P 65p)

TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 Improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

Total building costs **£4-48** P P & Ins. 33p
 (Overseas P & P £1-05)

ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3. Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—5 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Total Building Costs

£3-98 P P & Ins. 31p
 (Overseas P & P £1-05)

Please add 10% for VAT INC. P&P

NEW Everyday Series

Build this exciting New series of designs

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 15p. Free with parts.

Total Building costs **£2-73** P P & Ins. 30p
 (Overseas P & P 70p)

E.V.6. Case and looks as above. 8 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£3-60** P P & Ins. 30p
 (Overseas P & P 95p)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. Parts Price List and Plans 15p. Free with parts.


Total Building Costs **£4-08** P P & Ins. 31p

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL


7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4 1/2 in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

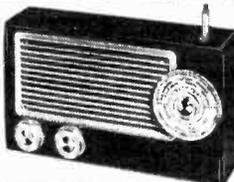Total building costs **£6-98** P P & Ins. 47p
 (Overseas P & P £1-05)



ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

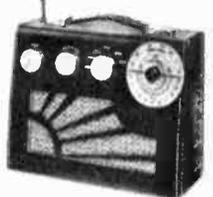


10 Transistors, 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Station also Aircraft Band

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

Total building costs **£8-50** P P & Ins. 50p
 (Overseas P & P £1-00)

"EDU-KIT"

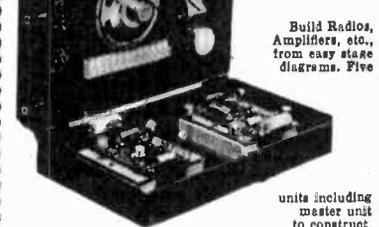

Build Radios, Amplifiers, etc., from easy stage diagrams. Five units including master unit to construct.

Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

Total building costs **£5-50** P P & Ins. 33p
 (Overseas P & P £1-05)

RADIO EXCHANGE LTD

★ Callers side entrance "Lavells" shop.
 ★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
 Tel.: 0234 52367. Reg. No. 788372.

I enclose £..... for.....
 Name


Address

(Dept. LPW23.)

THE G.W. SMITH & CO (RADIO) LTD

AUDIOTRONIC MODEL ATM.1

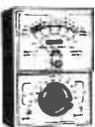Top value 1000 o.p.v. pocket multimeter. Ranges: 0/10/50/250/1000V. AC and DC. DC Current 0-1mA/100mA. Resistance 0/150k ohms. Decibels -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads. £2-95. Post 15p.



RUSSIAN 22 RANGE MULTIMETER

U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100mA/1/10/100mA/1A. Resistance 800 ohms/3/30/300k/3m Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. £4-95. P. & P. 25p.



MODEL 500

30,000 O.P.V. with overload protection, mirror scale. 0/1/2-5/10/25/100/250/500/1,000V. D.C. 0/2-5/10/25/100/250/500/1,000V. A.C. DC Current 100mA/1/10/100mA/1A. Resistance 800 ohms/3/30/300k/3m Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. £4-95. Post paid. Leather Case £1-75.



U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/3/1-5/7-5/30/60/150/300/600/900 VDC and 75mV. Accuracy DC 1%. AC 1-5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-75. P. & P. 25p.



HIOKI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 0/1-5/1-5/5/15/30/60/120/300/600/1200V DC. 1-5/3/6/12/30/60/150/300/600 1200 V. A.C. 15/30mA/3/6/30/60/150/300mA 6/12 AMP. DC. 2K/200K/2 Meg/20 Meg ohm 20 to +63dB. £14-95. P. & P. 25p.



MODEL C-7080 EN

Giant 6" mirror scale. 20,000 o.p.v. 0/25/1/2-5/10/50/250/1000/5000V. D.C. 0/2-5/10/50/250/1000/5000V. A.C. 0/50μA/1/10/100/500mA/10 amp. D.C. 0/2K/200K/20 meg -20 to +60 dB. £13-95. Post 35p.



370 WTR MULTI-METER

Features A.C. current ranges. 30,000 o.p.v. 0/2-5/10/50/250/500 1000 V. D.C. 0/2-5/10/50/250/500/1000V AC. 0/50μA/1/10/100/500mA/10 amp. D.C. 0/100mA/1/10 Amp AC 0/5K/50K/500K/5 meg/50 meg. +62dB. £17-50. P. & P. 25p.



KAMODEN 72.200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0-8/3/3/30/120/600/1200V. D.C. 0/1/3/12/60/300/11,200V. A.C. 0/6μA/1/2mA/120mA/600mA/12A. D.C. 0/12A. A.C. -20 to +63dB. 0/2K/200K/2 meg/200 meg ohms. £14-95. Post 30p.



TMK LAB TESTER.

100,000 O.P.V. 6 1/2in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K/Volt A.C. D.C. Volt: 5, 2-5, 10, 50, 260, 1,000 V. A.C. Volts: 3, 10, 50, 250, 500, 1,000V. D.C. Current: 10, 100μA, 10, 100, 500mA, 2-5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG Ω. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size: 7 1/2in. x 6 1/2in. x 3 1/2in. £19-95. P. & P. 25p.



Model S-100TR MULTIMETER/TRANSISTOR TESTER

100,000 o.p.v. mirror scale/overload protection. 0/12/6/12/30/120/600 V D.C. 0/5/50/120/600 V A.C. 0/12/600μA/12/300mA/12 AMP DC. 0/10 K/1 MEG/100MEG. -20 to +60dB. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £14-95. P/P 25p.



KAMODEN HM.350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and DC current. Amplification factor of NPN, PNP, transistors, diodes. SCR's etc. 4" x 4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.



MODEL 449A IN-CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta in/out. Checks Ico. Checks diodes in/out. Checks SCR, etc. Beta HI 10 - 500. Ico 2 - 50. Ico 0-5000μA. 220/240 V A.C. operation £17-50. Post 25p.



LB3 TRANSISTOR TESTER

Tests Ico and B. PNP/PNP. Operates from 9V battery. Complete with all instructions, etc. £8-95. P. & P. 20p.



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with all instructions, etc. £4-50. P. & P. 20p.



TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0-01/0-3/1/3/10/30/100/300V. R.M.S. 5cps. 1-2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17-50. Carr. 25p.



TE-65 VALVE VOLTMETER

28 ranges. D.C. volts 1-8-1500V. A.C. volts 1-5-1500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17-50. P. & P. 30p. Additional probes available. R.P. £2-18. H.V. £2-50.



KAMODEN HM. 720B F.E.T. V.O.M.

Input impedance 10 meg ohms. Ranges: 0/1/25/1/2-5/10/50/250/1000V. D.C. 0/2-5/10/50/250/1000V. A.C. 0/25μA/2-5/25/250 mA. -20 to +62dB. 0/5K/50K/500K/5meg 600meg ohms. £14-95. Post 30p.



TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 28 ranges. Large 4" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0-3-1200V AC VOLTS 3-300V R.M.S. 50-800V P-P. DC CURRENT 12-12mA. Resistance up to 2000M ohm. Decibels -20 to +51dB. Complete with leads/instructions. £17-50. P. & P. 20p.



KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1000 Megohms. 500 Volt. Battery operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. £19-95. Post 30p.



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohm/Volt AC and DC. Accuracy 0-5% D.C. 1% AC. Scale length 165mm. 0/300/750μA/1-5/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5/15/30/75/150/300/750mV/1-5/3/7-5/15/30/75/150/300/750V A.C. Automatic cut out. Supplied complete with test leads, manual and test certificates. £49-00. Post 50p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18 x 200,000 Hz; Square 18 x 20,000 Hz Output max. +10 dB (10 K ohms) Operation internal batteries Attractive 2-tone case 7 1/2" x 5 1/2" Price £17-50. Carr. 17p.



TO-3 PORTABLE OSCILLOSCOPE

3in. tube. Y amp. Sensitivity 0-1V p-p/CM. Bandwidth 1-5 cps-1-5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0-9V p-p/CM. Bandwidth 1-5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps 300 kHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2lb. 220/240V. A.C. Supplied brand new with handbook. £52-80. Carr. 50p.



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz V RMS/mm. 3-25; mm. 1-25; HOK. AMP. Bandwidth 500KHz. Sensitivity at 100KHz. V RMS/mm. 3-25; mm. 1-25; HOK. AMP. Bandwidth 500KHz. Preset triggered sweep 1-3,000μsec.; free running 20-200,000Hz in nine ranges. Calibrator plps. 220 x 360 x 430mm. 115-230V. AC operation. £39-00. Carr. paid.



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 Mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in. x 4in. C.R.T. Calibrated triggered sweep from 2 μsec. to 100 mill-sec. per cm. Free running time base 50 c/s-1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual £87. Carr. Paid.



MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-111dB. 0-1dB step. Impedance 600 ohms. Max. input power 30dBm. Size 180 x 90 x 55mm. £12-50. Post 37p.



ARF-300 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine / square 10V. P-P. RF 100 KHz to 200 MHz. Output 1V maximum. Operation 220/240V. AC. Complete with instructions and leads. £29-95. Post 50p.




MODEL TE.15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillation Detector. Frequency range 440Kc/s-280Mc/s in 6 colla. 500μA. Meter. 9V battery operation. Size 180 x 80 x 40mm. £15-00. Post 20p.




TE-20D RF SIGNAL GENERATOR

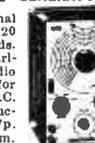Accurate wide range signal generator covering 120 Kc/s 500 Mc/s on 8 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions £17-50. Carr. 37p. Size 140 x 215 x 170 mm.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

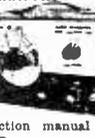Sine: 20cps to 200 kc/s on 4 bands. Square: 20cps to 50 kc/s. Output impedance 5,000 ohms. 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. £17-50. Carr. 37p.



AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.

80 W	£2-35	P. & P. 18p
150 W	£3-00	P. & P. 18p
300 W	£4-00	P. & P. 33p
500 W	£5-80	P. & P. 33p
1000 W	£9-25	P. & P. 38p
1600 W	£11-25	P. & P. 43p
2250 W	£19-00	P. & P. 50p
5000 W	£40-00	P. & P. £1

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230V. 50/60 c/s. Variable output 0-260V.

MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

1 Amp	£7-00
2-5 Amp	£9-05
5 Amp	£11-75
8 Amp	£15-90
10 Amp	£22-50
12 Amp	£23-60
20 Amp	£49-00
25 Amp	£58-00
40 Amp	£82-50



Panel Mounting

1 Amp	£7-00
2-5 Amp	£8-05



Carriage and Packing Extra

240° Wide Angle 1mA Meters

MW 1-6 60mm square	£3-97
MW 1-8 80mm square	£4-97

P. & P. extra



230 VOLT A.C. 50 CYCLES RELAYS

3 sets of changeover contacts at 5 amp rating, 40p each. P. & P. 10p (100 lots) £30. Quantities available.



ALL PRICES ARE SUBJECT TO 10% VAT



HIGH QUALITY CONSTRUCTION KITS
 Appointed stockists at all branches
 Complete with comprehensive, easy to
 follow instructions, and covered by
 full guarantee.
 Post and packing 15p per kit

- AF20 Mono transistor amplifier..... £4.80
- AF30 Mono transistor Pre-amplifier..... £2.61
- AF310 Mono amplifier (use two for stereo)..... £5.91
- ATS Automatic light control..... £2.58
- AT30 Photo cell twitching unit..... £5.70
- AT50 400W Trac light dimmer/speed control..... £4.80
- AT55 1,200W Trac light dimmer/speed control..... £5.70
- AT56 2,200W Trac light dimmer/speed control..... £6.90
- AT60 Psychedelic light control, single channel..... £7.50
- AT65 Psychedelic light control, 3 channel..... £14.55
- HF1 Medium wave transistor radio..... £3.33
- HF75 FM transistor receiver..... £2.88
- HF310 FM tuner unit..... £2.81
- HF325 De-luxe FM tuner unit..... £24.12
- HF330 Stereo decoder for HF310/HF325..... £9.96
- HF395 Aerial amplifier for use with 2x AF310..... £11.77
- GP310 Stereo pre-amp for use with 2x AF310..... £21.27
- GU330 Termino unit for guitars etc..... £7.50
- NT10 Power supply 100mA 5V stab 12V unstab..... £16.51
- NT300 Professional stabilized power supply 2x 20 Volt, 2.2 Amp..... £12.15
- NT305 Transistor converter 12/15V AC/DC to 6V, 7.5V or 9V DC..... £4.50
- NT310 Power supply 240V AC to 2x 18V DC at 2 Amps..... £4.80
- NT315 Power supply 240V AC to 4x 15V DC 500 mA..... £9.57

PS.200 REGULATED P.S.U.

Solid state. Variable output of 1-20 Volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240 V. A.C. Size 7 1/2" x 5 1/2" x 3 1/2".
£19.95. P. & P. 25p.

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amp. Meter to monitor current. Input 220/240V AC. Size 4" x 3 1/2" x 6 1/2".
£11.97. P. & P. 25p.

MOA. 820 AUTOMATIC VOLTAGE STABILISER

Input 88 125 VAC or 176, 260VAC. Output 120VAC or 240VAC. 200VA rating.
£11.97. Carr. 50p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 1/4 in. dia. shafts. Bulk quantities available.

- 25 WATT, 10/25/50/100/250/500/1000 ohms. 85p. P. & P. 10p.
- 50 WATT, 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.85. P. & P. 10p.
- 100 WATT, 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £1.95. P. & P. 15p.

230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 80 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RPH CW.
50p each Post 12p.

REFLEX HORN SPEAKER RH.6

Built in driver unit. Impedance 16 ohm. Power rating 10 watt. Response 380-7000Hz. Approx. size 6" x 8". Weatherproof and shock proof.
OUR PRICE £4.97 P. & P. 30p.

BVD.5 VERNIER TUNING DIAL

Approx. 7-1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1 to 6. Scale width 4 1/4". Dial size 5" x 3". Overall size 7 1/2" x 4 1/2" x 1 1/2" deep including knob and coupling. 1" dia. shaft.
OUR PRICE £1.62 P. & P. 15p.

1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2".
Our Price £2.25 P. & P. 15p

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

Type SW.100 100 x 80 mm.

50µA	£4.15
50-0-50µA	£8.95
100µA	£8.95
100-0-100µA	£9.70
500µA	£8.70
1mA	£8.60
20V. D.C.	£8.60
50V. D.C.	£8.60
300V. D.C.	£8.60
1 amp. D.C.	£8.60

5 amp. D.C. £8.60
 5 amp. A.C. £8.70
 VU Meter £4.30

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts

50mA	£8.90
100mA	£8.90
500mA	£8.90
1 amp.	£8.90
5 amp.	£8.90
15 amp.	£8.90
30 amp.	£8.90
20V. D.C.	£8.90
50V. D.C.	£8.90
150V. D.C.	£8.90
60-0-50µA	£4.25
100µA	£4.25
100-0-100µA	£4.05
200µA	£4.05
500µA	£3.90
500-0-500µA	£3.90
1mA	£3.90
1-0-1mA	£3.90
5mA	£3.90
10mA	£3.90

Type MR.52P. 2 1/2 in. square fronts

50µA	£3.50
50-0-50µA	£3.06
100µA	£3.00
100-0-100µA	£2.95
500µA	£2.85
1mA	£2.80
5mA	£2.80
10mA	£2.80
50mA	£2.80
100mA	£2.80
5 amp.	£2.80

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts

50µA	£3.70
50-0-50µA	£3.15
100µA	£3.10
100-0-100µA	£3.10
200µA	£3.05
500µA	£2.95
500-0-500µA	£2.80
1mA	£2.80
10mA	£2.80
50mA	£2.80
100mA	£2.80
5 amp.	£2.80
10 amp.	£2.80
15 amp.	£2.80
20 amp.	£2.80
30 amp.	£2.80
50 amp.	£2.80
5V. D.C.	£2.80

Type MR.38P. 1 1/2 3 1/2 in. square fronts

200mA	£2.85
300mA	£2.85
500mA	£2.85
750mA	£2.85
1 amp.	£2.85
2 amp.	£2.85
5 amp.	£2.85
10 amp.	£2.85
15 amp.	£2.85
3V. D.C.	£2.85
10V. D.C.	£2.85
15V. D.C.	£2.85
20V. D.C.	£2.85
50V. D.C.	£2.85
100V. D.C.	£2.85
150V. D.C.	£2.85
5 amp. A.C.*	£2.85
10 amp. A.C.*	£2.85
15 amp. A.C.*	£2.85
20 amp. A.C.*	£2.85
30 amp. A.C.*	£2.85

Type MR.45P. 2 in. square fronts

50µA	£2.70
50-0-50µA	£2.65
100µA	£2.60
100-0-100µA	£2.50
200µA	£2.50
500µA	£2.45
500-0-500µA	£2.40
1mA	£2.40
5mA	£2.40
10mA	£2.40
50mA	£2.40
100mA	£2.40
500mA	£2.40
1 amp.	£2.40

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts

1 amp.	£2.60
5 amp.	£2.60
15 amp.	£2.60
30 amp.	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
15 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
5V. D.C.	£2.60
10V. D.C.	£2.60
15V. D.C.	£2.60
20V. D.C.	£2.60
30V. D.C.	£2.60
50V. D.C.	£2.60
100V. D.C.	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
15 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
50V. D.C.	£2.60
100V. D.C.	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
15 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
50V. D.C.	£2.60
100V. D.C.	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
15 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
50V. D.C.	£2.60
100V. D.C.	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
15 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
50V. D.C.	£2.60
100V. D.C.	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60

G.W. SMITH & CO (RADIO) LTD

TRIO JR599 RECEIVER



9 wavebands covering 1.8-29.7MHz 144-146MHz and 10-100MHz WWV. SSB, CW, AM and FM. AF output more than 1 watt. 8 Meter. Squelch control. BFO. Variable RF and AF controls. 4-16 ohm output and 100% Zapping. Power requirements 110/240v. AC. 12-14v. DC.


Our Price £155.00 Carr. Paid

TRIO TR2000 TRANSCIEVER

Fully transistorized portable VHF Transciever. Will transmit and receive on 6 channels between 144-146MHz. 1 watt transmitter. 12v DC internal or external supply. Built in charger for ni-cad cells. Power/volume switch, squelch control, channel selector, mike socket, earphone/external speaker socket. Complete with microphone. 144.48, 144.72 and 145.32 crystals. Size 134 x 58 x 180mm.

Our Price £79.50 Carr. Paid

TRIO TS515/PS515 TRANSCIEVER

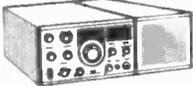

High quality TS515 SSB/CW amateur band receiver covering 80, 40, 20, 15 and 10 metre bands with PS515 power supply and speaker unit. Transmit/receive frequency 3.5-29.7MHz. Output 1.5 watts. Power requirements 110-120/220-240v. AC.

Our Price £210.00 Carr. Paid

BELTEK W5400 CAR TRANSCIEVER



Build state mobile transciever for 12v DC neg. use. Transmits and Receives on any 12 of 28 channels between 144 and 146MHz. Power output 10w and 1w switchable. Internal 3" speaker. Complete with dynamic mike, PTT switch, three sets of crystals for 144.48MHz, 144.60MHz, 145.00MHz. mounting bracket and instructions. Size approx. 150 x 60 x 220mm.

Our Price £75.00 P & P 50p

TRIO JR310 SSB RECEIVER



Covers 3.5, 7, 14, 21, 28, 28.5 and 29.1 MHz band and WWV 15MHz. SSB, AM and CW. AF output more than 1 watt. Crystal controlled BFO for SSB. 8 meter. ANL etc. AC 110/120-220/240v.

Our Price £75.00 Carr. Paid

UNR 30 RECEIVER



4 Bands covering 550 Kc/s-30 Mc/s B.F.O. Built-in Speaker 220/240 v. A.C. Brand new with instructions.

UR-1A RECEIVER



4 Bands covering 550 Kc/s-30 Mc/s. FET. 8 Meter. Variable BFO for SSB. Built-in Speaker, Bandspread, Sensitivity Control. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price £25.00 Carr. 37p

LAFAYETTE HA-600 RECEIVER



General Coverage 150-400 Kc/s. 550 Kc/s-30 Mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter Bandspread. RF Gain. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price £50.00 Carr. 50p

TRIO 9R59DS RECEIVER



4 bands covering 550 Kc/s to 30 Mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW, ANL, Variable BFO. 8 meter. Sep. bandspread dial. IF frequency 445 kc/s, and audio output 1.5w. Variable RF and AF gain controls. 110/250 v. A.C. with instruction manual.

Our Price £49.50 Carr. Paid



HAND-HELD 2-WAY WALKIE-TALKIES

P. & P. 50p.

SKYFON-100MW. £24.95 pair, P302-2 CHANNEL 300MW. £58.50 pair. P1003-3 CHANNEL 1 Watt £71.25 pair. LICENSE REQUIRED FOR OPERATION IN U.K.

3-STATION INTERCOM KE.630



Master and two sub stations. Can be used on desk or wall mounted. Complete with cable and batteries.

Our Price £5.25 P & P 50p

AUDIOTRONIC

RANGE OF HIGH QUALITY EQUIPMENT

Audiotronic Products are manufactured exclusively for the Audiotronic Group of Companies and as a member of the group we are pleased to offer you this fabulous range of high quality equipment. Made to our own specifications each item provides outstanding performance and reliability at a value for money price!

ACD.660 Stereo Cassette Deck



A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter normal/chrome tape selector, twin VU meter, alder record/playback level controls, front panel headphone socket, recording indicator lamp, phono/DIN line input sockets, 3.5mm mike input sockets etc. etc. Frequency response 100-8KHz (100-12KHz. C95) 8/N-45dB. Crosstalk 45dB. Separation-35dB. Noise limiter-6dB at 10KHz. Complete with phono connecting leads.

OUR PRICE £39.50 Carr. & Ins. 50p

AHP-8D 8 Track Stereo Tape Deck



Can be used with most hi fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. AC 220/240v.

OUR PRICE £11.95 P. & P. 50p.

AHP-8A 8 Track Stereo Tape Player



Incorporates built in amplifiers giving 21 + 21 watts rms output. Push button track selector, illuminated track indicators, alder controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. AC 220/240v.

OUR PRICE £17.25 P. & P. 50p.

Stereo Headphones

- L3H.20 Individual volume controls Stereo mono switch. 8 ohms. 40-19,000 Hz. £3.50 P & P 30p
- L3H.30 Open back type. Individual tone and volume controls. 8 ohms. 30-20,000 Hz. £5.50 P & P 30p
- L3H.40 Two way speaker system. Individual volume controls. 8 ohms. 20-20,000 Hz. £6.95 P & P 30p
- L3H.60 3" speaker units. 8 ohms. 20-20,000 Hz. Complete with zippered carrying case. £8.50 P & P. 30p
- LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4-32 ohms. 20-20,000 Hz. £9.95 P & P. 30p
- L3H.50 Electrostatic with self powered energiser and control unit with headphone/speaker selector. 4-32 ohms. 20-24,000 Hz. £18.95 P. & P. 30p

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 161/2" x 8" x 2 1/2". AC 200/250v



PROCESS FOUR For use with semi-professional tape recorders. Freq. res. 30Hz-20KHz. ± 2dB. 8/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

Our Price £50.00 P & P 50p

PROCESS TWO

For use with cassette and tape recorders. Freq. res. 30Hz-20KHz. ± 2dB. On tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. 8/N better than 70dB. Supplied with test cassette or tape as required.

Our Price £34.50 P & P 50p

ACR.14 Battery Mains Cassette Recorder



Portable twin track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. AC 220/240v or 6v DC operation. Complete with remote control microphone, mains lead, earpiece and batteries.

OUR PRICE £10.50 P. & P. 50p.

ACR 3500 CAR RADIO



Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

Our Price £6.50 P & P 50p

ACP.8 8 TRACK CAR PLAYER



12v neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp, with speakers, mounting brackets and instructions.

Our Price £12.50 P & P 40p

LOW NOISE CASSETTES

TYPE	5	10	25
C60	£1.29	£2.53	£5.99
C90	£1.85	£3.62	£8.59
C120	£2.29	£4.48	£10.63

P. & P. 15p.
Cassette Tape Head Cleaner 30p

AMR-900 GLOBAL AM/FM PORTABLE RADIO



10 wavebands covering AM: 535-1605 kHz. LW: 160-380 kHz. MW: 15-400 kHz. SW: 1.4-0-8 MHz. SW2: 8.0-1.6 MHz, SW3: 16-24 MHz, PBBI: 30-50 MHz, PBB2: 148-174 MHz, FM: 68-108 MHz, AIR: 108-136 MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC or FM. 6" x 4" speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm. **OUR PRICE £36.00** P. & P. 50p.

AR.1000 SPORTSMAN AM/FM PORTABLE RADIO



6 wavebands covering AM 535-1605KHz. FM 68-108MHz. AIR 108-135MHz. PB 147-174MHz. WB 162.6MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for FM and built in ferrite bar for AM. AFC. 3in. speaker. Earpiece socket. Size 152 x 76 x 219mm. Battery/mains operation. **OUR PRICE £11.50** P. & P. 55p.

AUDIOTRONIC AMB.500 MULTIBAND RADIO



8 wavebands covering MW 535-1605KHz and FM 68-175MHz. All transistor. Battery or mains operation. Built in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece. **OUR PRICE £6.95** P & P 35p

AM/FM Portable Radio AR3000



4 wavebands covering FM 87-108 MHz, MW510 - 1605 KHz., LW 145 - 285 KHz., SW 5.8 - 12.5 MHz. Push button wave change plus AFC and on/off. Thumbwheel tuning. Slider volume and tone controls. Earphone socket. Built in and telescopic aerials. Car aerial socket. Battery/mains operation. **OUR PRICE £14.95** P. & P. 50p

DIGITAL CLOCK RADIO ADC.1



Covers AM 540 - 1600 KHz. FM 88 - 108 MHz with AFC. Illuminated dial. 24 hour alarm setting. Wake up to the sound of music or loud buzzer. Sleep switch will automatically turn off radio etc. Internal speaker plus socket for earpiece or pillow speaker. AC 240v. Size 254 x 92 x 178mm. Complete with earpiece, FM aerial and operating instructions. **OUR PRICE £12.50** P. & P. 50p.



SAVE UP TO 33 1/3% OR MORE! GWS

SH628 STEREO HEADPHONES

Outstanding value. Soft ear-pads, adjustable headband. 8-16 ohms, 20-20,000 Hz. Complete with lead and stereo plug.

Our Price £1-87 P. & P. 30p

HH025 STEREO HEADPHONES

Lightweight headphones with padded earpieces. 4-16 ohms, 20-20,000 Hz. Complete with 6 ft. cord and plug.

Our Price £1-97 P. & P. 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

Our Price £2-25 P. & P. 30p

BH.001 HEAD SET AND BOOM MICROPHONE

Moving Coil. Ideal for language teaching, communications. Headphone Imp. 16 ohms. Microphone Imp. 200 ohms.

Our Price £4-95 P. & P. 30p

DH025 STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug.

Our Price £2-25 P. & P. 30p

SPECIAL OFFER I STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2" x 9" x 7 1/2" 8 ohms, 8 watt RMS. 16 watt peak. Complete with DIN lead.

Our Price £12-95 Carr. 50p

SUPER AKAI HIFI BARGAINS

CS35 Stereo Cassette Recorder

For conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-18kHz (using CrO2 tape), distortion better than 2%, wow and flutter better than 0.2% RMS. Complete with pair of matching Akai CS88 speakers.

Rec. Price £96-10 **OUR PRICE £56-50 P. & P. 50p**

CS35D STEREO DECK

4 track record/playback deck. Accepts chrome/regular tape cassettes.

Rec. Price £68-30 **£44-45 P. & P. GWS PRICE 50p**

MICROPHONES (P. & P. 50p)
ADM Dynamic (pair) **£7-50**

FERGUSON EXPORT MODELS

FERGUSON 3408 STEREO TUNER AMPLIFIER

Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape etc. Separate bass treble, balance and volume controls.

Our Price £31-50 P. & P. 50p

3418 STEREO TAPE DECK

4 track. 7 1/2, 3 1/2, 1 1/2 i.p.s. Stereo/mono record/play. 7" reels. Inputs for dynamic mikes, radio, gram. Complete with cover.

Our Price £41-95 P. & P. 75p

EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 16 watt RMS. Available 8 or 16 ohms. **£7-25 each. P. & P. 37p.**

Model 450. 13" x 8" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 16 ohms. **£3-82 each. P. & P. 25p.**

RECORD DECK PACKAGES

Carriage and Packing 75p. Complete units with Stereo cartridge ready wired in plinth cover.

GARRARD
2025 TC/TAHCD .. £11-35
8P25 111/G800 .. £16-50
8P25 111/M44E .. £17-95
8P25 111/M44-F .. £17-50
8P25 111/M46 E .. £18-60
8P25 111 Module/M75-8 .. £19-45
8P25 IV Module/M75-68M .. £21-15
AP76/G800 .. £28-45
AP76/G800E .. £28-65
AP76/M44E .. £27-70
AP76/M44-F .. £27-20
AP76/M55B .. £28-30
AP76/M75E D .. £34-90
AP76/M75E J .. £30-90
AP76 Module M75-6 .. £28-10
868B Module/M75-68M .. £32-30
AP96 Module M75-8 .. £38-20
ZERO 100B Module/M03E .. £44-15
Zero 100SB Module M75-68M/£44-20

B.S.R. McDONALD
210/SC7M .. £7-40
MP60/G800 .. £15-00
MP60/TPD1/G800 .. £15-80
MP70/M75 .. £16-60
HT70/TPD1/G800 .. £19-20

GOLDRING
GL72/G800 .. £34-20
GL75/G800 .. £39-10
GL75/G800E .. £41-55

RECORD DECKS

Carriage and Packing 50p

B.S.R. McDONALD
C114 Mini .. £3-95
C129 Mono .. £5-50
C137 .. £7-00
510/TPD1 .. £13-95
610 .. £10-55
610/TPD1 .. £15-45
710 .. £21-15
810 .. £28-30
MP60 .. £8-25
MP60/G800 .. £10-90
MP60/TPD1 .. £13-25
MP60/TPD2 .. £11-25
HT70 .. £11-80
HT70/G800 .. £14-25
HT70/TPD1 .. £16-55

CONNOISSEUR
BD1 Kit .. £9-10
BD1 Chassis .. £11-35
BD2/SAU2/Chassis .. £22-70
BD2/SAU2/Plinth/Cover .. £28-20

GARRARD
2025 T .. £8-35
2025 TC/KS40A .. £8-95
8P25 III .. £9-25
8P25 III Acos GP104C .. £8-50
8P25 III G800 .. £10-95
8P25/M75-6 .. £13-80
8P25 IV .. £10-20
AP76 .. £18-00
868B .. £18-50
8163B .. £11-15
8172B .. £17-75
8193B .. £31-15
401 .. £24-35
ZERO 100A .. £34-10
ZERO 100B .. £31-40
Zero 100 SB .. £27-00

GOLDRING
G99 .. £29-50
G101P/C .. £22-50
GL69/2 .. £16-75
GL72 .. £26-45
GL72/P .. £33-75
GL75 .. £38-20
GL75 .. £41-60
GL78P/C .. £56-25
GL78/G800 .. £31-50
GL78/G800E .. £44-95
GL88P/C .. £78-00

BSR 8 TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model TD8s complete with silver and black excutcheon ready to fit into cabinet. Output 126mV. AC 240v. Overall size approx. 185 x 215 x 80mm.

OUR PRICE £8-95 P. & P. 50p.

PORTABLE CASSETTE RECORDER

CTS50
Instant recording and playing. Piano key controls. Automatic level control. Built in speaker. Complete with remote control microphone, carrying case and shoulder strap.

OUR PRICE £8-50 P. & P. 50p.

NEW! SINCLAIR CAMBRIDGE CALCULATOR

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator.

OUR PRICE £24-95 P. & P. 50p.

(Also available ready built. (Rec. Price £29-95))

OUR PRICE £27-20 P. & P. 25p

MINUTEMAN MM3 POCKET CALCULATOR

Size only 4 1/2" x 3" x 1 1/2". 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.

OUR PRICE £23-95 P. & P. 25p

MINUTEMAN MM3M

as above with addition of memory key, per cent key and a fixed or floating decimal. Complete with rechargeable batteries, AC adaptor, instructions and case.

OUR PRICE £38-50 P. & P. 25p

BINATONE DS100 DIGITAL CLOCK

240v. mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Approx. size 6 1/2" x 3" x 3 1/2".

OUR PRICE £4-50 P. & P. 30p.

SINCLAIR PROJECT 60 PACKAGE DEALS



2 x Z30 Stereo 60/P/Z5 £16-65. P. & P. 37p.
2 x Z30/Stereo 60/P/Z6 £18-00. P. & P. 37p.
2 x Z50/Stereo 60/P/Z8 £20-25. P. & P. 37p.
Transformer for PZ8 £3-65.
Active Filter Unit £4-45.
Pair of Q16 Speakers £10-70
Sinclair Project 60s £20-97.
P. & P. 37p.

All other Sinclair Products in stock
2000 Amplifier £22-95
3000 Amplifier £28-95
2000/3000 Tuner £28-80
Q330 Speakers £28-98 pair
P. & P. 50p each of above items

FM TUNER CHASSIS

6 TRANSISTOR HI G H QUALITY TUNER. SIZE ONLY 6" x 4" x 2 1/2". 5 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money.

Our Price £5-95 P. & P. 20p

Stereo multiplex adaptors £4-97.

Our Price £5-95 P. & P. 20p

A1018 FM TUNER

Specification as above chassis but complete in cabinet with on/off switch. Size 7 1/2" x 3 1/2" x 5".

Our Price £9-65 P & P 30p

Stereo multiplex adaptor £4-97.

DIGITAL CLOCK MECHANISM DT.55B

Features 24 hour alarm setting with built-in buzzer. On/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off TV, radio, light, etc. and with autotuning will switch on again when required. AC 240v. operation. Switch rating 250v. 3A.

OUR PRICE £5-95 P. & P. 30p.

LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY -

ARMSTRONG
KEF-LUX NIKKO
SANSUI-SANYO
SONY-TEAC
TRANSCRIPTORS
TRIO-UMER
YAMAHA

Prices on request or send S.A.E. for full Discount List

ALL EQUIPMENT IS FULLY GUARANTEED AND COVERED BY 12 MONTHS FREE SERVICE!

G.W. SMITH & CO (RADIO) LTD

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON
267/8, Tottenham Court Rd. W.1. Tel: 01-580 0670
10, Tottenham Court Rd. W.1. Tel: 01-637 2232
27, Tottenham Court Rd. W.1. Tel: 01-636 3715
87, Tottenham Court Rd. W.1. Tel: 01-580 3739
21, Old Compton Street, W.1. Tel: 01-437 9369
3, Lisle Street, W.2. Tel: 01-437 8204
34, Lisle Street, W.2. Tel: 01-437 9155
118, Edgware Road, W.2. Tel: 01-723 9789
193, Edgware Road, W.2. Tel: 01-723 6211

311, Edgware Road, W.2. Tel: 01-262 0387
382, Edgware Road, W.2. Tel: 01-723 4194
152/3, Fleet Street, C.C.A. Tel: 01-353 2833
378, Harrow Road, W.5. Tel: 01-266 9530
ESSEX
86, South Street, Romford. Tel: Romford 20218
SURREY
1006 Whitgift Centre, Croydon. Tel: 01-681 3027
27, Eden Street, Kingston. Tel: 01-546 7845
32, Hill Street, Richmond. Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

HEAD OFFICE AND MAIL ORDER DEPARTMENT
UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ
TELEPHONE 01-205 3735

PRICES SUBJECT TO 10% VAT
Order with confidence by Post-but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.

TELEPHONED ORDERS ACCEPTED FROM ACCESS and BARCLAYCARD HOLDERS

CREDIT TERMS FOR PERSONAL CALLERS (on sales of £50 and over)

Always with Access

All prices correct at 25-9-73 but subject to change without notice. E & O.E.

FREE

Headphones or Speakers; Suitably Terminated Connectors; Handbook; Carriage; Insurance. In addition a JOYSTICK V.F.A.; JOYMATCH A.T.U.; feeder external mounting insulators are supplied FREE or greatly reduced when you buy a PARTRIDGE PACKAGE.

A PARTRIDGE PACKAGE constitutes a COMPLETE RADIO STATION—ready to use however confined your domestic space. The World renowned TRIO range of Communications Receivers and Transceivers, the WORLD RECORD, internationally patented JOYSTICK V.F.A. (all band aerial) only 7' 6" long (assembled) and a JOYMATCH aerial tuning unit, a pair of matching headphones or internal speaker, plus accessories, go to complete your READY TO USE RADIO STATION at a price that truly represents VALUE FOR MONEY!

PARTRIDGE PACKAGE

No. 1 with Gen. Coverage AM/CW/SSB (MW/SW) 9R59DS Receiver	£87.77 (Save £17.16)
No. 2 with Amateur Bands 80 thru 10m AM/CW/SSB JR310 Receiver	£90.97 (Save £22.35)
No. 3 with Amateur Bands 160 thru 10m plus 2m AM/CW/SSB JR599	£176.00 (Save £30.48)
No. 4 with Amateur Bands 80 thru 10m TS/PS515 Transceiver, 180w	£231.00 (Save £37.08)

NOTHING MORE TO PAY!

Access/Barclaycard orders accepted by 'phone

JOYSTICK V.F.A. £13.75; JOYMATCH TX/RX A.T.U. 111A 1.6-32MHz £13.75; JOYMATCH A.T.U. 111 RX only 500kHz-32MHz £13.75; JOYMATCH A.T.U. LO-Z500 TX/RX 500w SSB (PA input), Built-in RF meter £19.91; Communications 8Ω headphones (suitable TRIO, EC10 etc.) £3.14; Matching Speaker (with instructions for internal fitting in 9R59DS & JR310) £2.00; TRIO: Linear Amplifier TL911 £172.15; TR2200 2m personal transceiver £87.45; TR7200 2m car transceiver £142.45; Spare set valves for 9R59DS £2.35; OA2 Mains Stabiliser 74p.

NEW: World-wide reception on the amazing "DX-CRYSTAL SET" £2.42 incl. unique aerial.

NEW: AMTRON QUALITY KITS—send for brochure and prices.

PARTRIDGE BUDGET LINE

Artificial Earth—solves receive and transmit earth problems (as used on North Sea Oil Rigs!) £5.80; Aerial Bandswitch—tuned aerial for domestic receivers £5.80; A.T.U. KIT—for use with transmitters and Communications Receivers £5.80; (assembled £7.01); Mini SWR Bridge—1.8 to 180MHz, 2kw P.E.P., 75 or 50Ω, SO239 sockets; 1:1 to 1:3 ratio, 80 x 30 x 30mm £5.60. (All prices quoted INCLUDE V.A.T., CARRIAGE, PACKING, INSURANCE.)

Send 3p stamp for full illustrated details. Special TRIO brochures (state which) 3p stamp extra.

NO V.A.T. ON OVERSEAS ORDERS!

Carriage and insurance extra overseas orders

BOX 5



G3CED — G3VFA

Telephone: 0843 62535 or 62839 evenings and weekends



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

WB113
BLOCK CAPS please

An extensive range of semi-conductors; Electrolytic capacitors; Mylar, Polyester and Ceramic capacitors; Fixed and variable resistors. Brand new by well known manufacturers.

Send S.A.E. for comprehensive list to:

W.P. COMPONENTS

7 Brook Avenue,
Edgware, Middx.


Dimmit

range of light dimmers

Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppression. 60mm slider range: size 12 x 5 x 4 cm, ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc.. Complete with scale plate, fixing screws and full instructions. £5.50 inc. VAT, add 10p P. & P. Also available in 2kV, with separate heatsink.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors etc. Rotary and Slider control versions. Ratings: 400W, 1,000W, 2,000W.

NEW addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Black Al case—size 12 x 4 x 7cm. Full instructions. £6.50 inc. VAT. add 10p P. & P. Send for complete illustrated catalogue and price list.

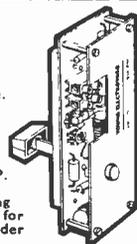

YOUNG ELECTRONICS Mail Order Dept.
54 Lawford Road, London NW5 2LN. Telephone 01-267 0201

ESSENTIAL BOOKS FOR RADIO AMATEURS

**New book *
AMATEUR
RADIO AWARDS**
compiled by C.R. Emery
G5GH

Lists of all the world's major awards from national societies and how to obtain them. Includes reproductions of certificates, maps and operating information. Loose-leaf binding to facilitate insertion of amendments and additions.
£1.40 post paid

**A GUIDE TO
AMATEUR
RADIO**
by Pat Hawker
G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.
90p post paid

**RAE
MANUAL**
by G.L. Benbow
G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination.
90p post paid

**TELEVISION
INTERFERENCE
MANUAL**

by B. Priestley
G3JGO

The causes of interference to TV receivers are examined, and ways in which they can be overcome are suggested in this latest RSGB publication.
90p post paid

These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send s.a.e. for complete list

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



D.I.Y. ELECTRONIC ORGAN KITS

*In use throughout
the world by
professionals*



★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2x5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55.

V.A.T. please add 10%—show separately on order.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT, ELECTRICAL HOUSEHOLD APPLIANCES AND MUSICAL INSTRUMENTS.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

YOU ARE WELCOME TO VISIT THE ONLY D.I.Y. ELECTRONIC ORGAN CENTRE IN EUROPE AT 12 BRETT RD., HACKNEY E8, TEL. 986 8455

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 405285

THE T.V. GRAVEYARD OF THE NORTH, AS SEEN ON T.V. CLOSE TO THE MOTORWAY. PLENTY OF FREE PARKING SPACE. EST. 1935.

SPECIAL OFFER

1000 PYE 19" 13 Channel T.V. Sets. Brilliant Picture, Extra Slim Bench Tested. Sold with Money Back Guarantee. Hurry, have a second set at the price of £5.50. Plus carr. and ins. £1.80. Students Wireless Procedure Training Set comprising mike, single LR phone and connector in small wood box, 80p post paid.

COMPLETE UNTESTED T.V. SETS. With back and all valves. BBC 1 and ITV 17" 90° Tubes £1.10. 17" 110° Tube £2.20. 19" £3.30. Carr. and ins. on any set £1.75.

Fifty T.V. Valves. Good assortment not-tested 50p. Post-Paid ½ Cwt. of ex Government Scrap Resistors, Panels and Gears, etc. 30p. Carr. 80p.

SPEAKERS REMOVED FROM T.V. SETS, all 3 Ohm 2½ Watts. 7 x 4", 6 x 4", 8 x 2½". All at 27p. Post and packing 12p.

TOP QUALITY TAPE. Reel to Reel 5" ST, 44p 5" LP 55p. 5½" LP 60p. 7" ST 66p. 7" LP 80p. Cassette Types C60 35p. C90 45p. C120 55p. Post on any tape 12p.

Jap Earpiece 8 Ohm Magnetic 3-5 12p. Ex Equipment Valves all tested on our Mullard Valve Tester before despatch. 3 months guarantee on all valves. Single Valves Post 3p. over Post Free.

ARPI2	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	14p	UJ91	20p
EBF89	15p	PCL83	15p	6BWW7	12p
ECC81	12p	PCL84	15p	6U4	20p
ECC82	12p	PL82	10p	6F23	15p
EF91	5p	PL83	10p	20P1	12p
EY86	22p	PL86	17p	20P3	12p
EF183	20p	PY81	10p	30F5	20p
EF184	20p	PY801	17p	30FLI	
		PY800	17p		

ABOVE PRICES INCLUDE V.A.T.

TRANNIES

1 Dockyard Station Road,
Old Harlow,
Essex

All prices
inclusive
of V.A.T.

P/P 12½p.

Catalogue 10p.

(Saturday callers welcome)

74 Series TTL



1		25		1		25		1		25	
SN7400	0.17	0.18	SN7426	0.50	0.46	SN7454	0.17	0.16	SN7494	0.85	0.82
SN7401	0.17	0.18	SN7427	0.50	0.46	SN7460	0.17	0.16	SN7495	0.85	0.82
SN7402	0.17	0.18	SN7428	0.77	0.76	SN7470	0.32	0.29	SN7496	0.96	0.93
SN7403	0.17	0.18	SN7430	0.17	0.16	SN7472	0.32	0.29	SN74100	£1.82	£1.76
SN7404	0.17	0.18	SN7432	0.50	0.46	SN7473	0.41	0.39	SN74104	£1.07	£1.04
SN7405	0.17	0.18	SN7433	0.88	0.83	SN7474	0.41	0.39	SN74105	£1.07	£1.04
SN7406	0.89	0.84	SN7437	0.71	0.68	SN7475	0.50	0.48	SN74107	0.44	0.42
SN7407	0.39	0.34	SN7438	0.71	0.68	SN7476	0.44	0.43	SN74110	0.61	0.59
SN7408	0.20	0.19	SN7440	0.17	0.16	SN7480	0.74	0.71	SN74111	£1.38	£1.27
SN7409	0.20	0.19	SN7441	0.74	0.71	SN7481	£1.32	£1.27	SN74118	£1.10	£1.05
SN7410	0.17	0.16	SN7442	0.74	0.71	SN7482	0.96	0.95	SN74119	£1.49	£1.38
SN7411	0.28	0.27	SN7443	£1.43	£1.38	SN7483	£1.21	£1.16	SN74121	0.44	0.41
SN7412	0.39	0.34	SN7444	£1.43	£1.38	SN7484	£1.10	£1.05	SN74122	£1.54	£1.43
SN7413	0.32	0.29	SN7445	£1.98	£1.95	SN7485	£3.98	£2.85	SN74123	£3.08	£2.97
SN7416	0.48	0.44	SN7446	£1.07	£1.04	SN7486	0.35	0.34	* Devices may be mixed to qualify for price breaks.		
SN7417	0.48	0.44	SN7447	0.98	0.88	SN7489	£6.05	£5.78	* 100 plus less 10% off 25 plus break.		
SN7420	0.17	0.16	SN7448	£1.10	£1.07	SN7490	0.68	0.60			
SN7422	0.55	0.53	SN7450	0.17	0.16	SN7491	£1.10	£1.05			
SN7423	0.55	0.53	SN7453	0.17	0.16	SN7492	0.74	0.71			
SN7425	0.55	0.53	SN7453	0.17	0.16	SN7493	0.74	0.71			

Linear Integrated Circuits

301 DIL	0.50	307 TO99	0.89	710C TO99	0.46	748C DIL	0.52
301 TO99	0.55	307 8 Pin DIL	0.86	723C DIL	0.89	748C TO99	0.42
301 8 Pin DIL	0.48	308 TO99	£6.90	723C TO99	£1.00	1437 DIL	£1.30
301A DIL	0.89	308A TO99	£7.40	741C 8 Pin DIL	0.35	1458 TO99	£1.30
301A TO99	0.89	709C DIL	0.35	741C 14 Pin DIL	0.38	3048 DIL	0.84
301A 8 Pin DIL	0.86	709C TO99	0.34	741C TO99	0.38		
307 DIL	0.89	710C DIL	0.44	747C DIL	0.80		

Electrolytic Capacitors



4 VOLT		10 VOLT		16 VOLT		25 VOLT		63 VOLT	
47µF	6½p	22µF	6½p	1000µF	17p	2200µF	39p	1µF	6½p
100µF	6½p	47µF	6½p	1500µF	25p	5000µF	68p	2.2µF	6½p
220µF	6½p	100µF	6½p	2000µF	43p			4.7µF	6½p
330µF	6½p	220µF	8p	3300µF	38p			6.8µF	6½p
1000µF	13p	330µF	10p	6800µF	65p			10µF	6½p
4700µF	29p	470µF	10p					22µF	6½p
		1000µF	11p					68µF	10p
		1500µF	20p					100µF	11p
		2200µF	24p					150µF	13p
		68µF	6½p					220µF	19p
		150µF	6½p					330µF	22p
		470µF	11p					470µF	26p
		680µF	13p					1000µF	44p
		1500µF	18p						
		2200µF	18p						
		3300µF	26p						
		6800µF	40p						

Mullard Polyester's

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 10000µF, 15000µF, 22000µF, 33000µF, 47000µF, 68000µF, 100000µF, 150000µF, 220000µF, 330000µF, 470000µF, 680000µF, 1000000µF, 1500000µF, 2200000µF, 3300000µF, 4700000µF, 6800000µF, 10000000µF, 15000000µF, 22000000µF, 33000000µF, 47000000µF, 68000000µF, 100000000µF, 150000000µF, 220000000µF, 330000000µF, 470000000µF, 680000000µF, 1000000000µF, 1500000000µF, 2200000000µF, 3300000000µF, 4700000000µF, 6800000000µF, 10000000000µF, 15000000000µF, 22000000000µF, 33000000000µF, 47000000000µF, 68000000000µF, 100000000000µF, 150000000000µF, 220000000000µF, 330000000000µF, 470000000000µF, 680000000000µF, 1000000000000µF, 1500000000000µF, 2200000000000µF, 3300000000000µF, 4700000000000µF, 6800000000000µF, 10000000000000µF, 15000000000000µF, 22000000000000µF, 33000000000000µF, 47000000000000µF, 68000000000000µF, 100000000000000µF, 150000000000000µF, 220000000000000µF, 330000000000000µF, 470000000000000µF, 680000000000000µF, 1000000000000000µF, 1500000000000000µF, 2200000000000000µF, 3300000000000000µF, 4700000000000000µF, 6800000000000000µF, 10000000000000000µF, 15000000000000000µF, 22000000000000000µF, 33000000000000000µF, 47000000000000000µF, 68000000000000000µF, 100000000000000000µF, 150000000000000000µF, 220000000000000000µF, 330000000000000000µF, 470000000000000000µF, 680000000000000000µF, 1000000000000000000µF, 1500000000000000000µF, 2200000000000000000µF, 3300000000000000000µF, 4700000000000000000µF, 6800000000000000000µF, 10000000000000000000µF, 15000000000000000000µF, 22000000000000000000µF, 33000000000000000000µF, 47000000000000000000µF, 68000000000000000000µF, 100000000000000000000µF, 150000000000000000000µF, 220000000000000000000µF, 330000000000000000000µF, 470000000000000000000µF, 680000000000000000000µF, 1000000000000000000000µF, 1500000000000000000000µF, 2200000000000000000000µF, 3300000000000000000000µF, 4700000000000000000000µF, 6800000000000000000000µF, 10000000000000000000000µF, 15000000000000000000000µF, 22000000000000000000000µF, 33000000000000000000000µF, 47000000000000000000000µF, 68000000000000000000000µF, 100000000000000000000000µF, 150000000000000000000000µF, 220000000000000000000000µF, 330000000000000000000000µF, 470000000000000000000000µF, 680000000000000000000000µF, 1000000000000000000000000µF, 1500000000000000000000000µF, 2200000000000000000000000µF, 3300000000000000000000000µF, 4700000000000000000000000µF, 6800000000000000000000000µF, 10000000000000000000000000µF, 15000000000000000000000000µF, 22000000000000000000000000µF, 33000000000000000000000000µF, 47000000000000000000000000µF, 68000000000000000000000000µF, 100000000000000000000000000µF, 150000000000000000000000000µF, 220000000000000000000000000µF, 330000000000000000000000000µF, 470000000000000000000000000µF, 680000000000000000000000000µF, 1000000000000000000000000000µF, 1500000000000000000000000000µF, 2200000000000000000000000000µF, 3300000000000000000000000000µF, 4700000000000000000000000000µF, 6800000000000000000000000000µF, 10000000000000000000000000000µF, 15000000000000000000000000000µF, 22000000000000000000000000000µF, 33000000000000000000000000000µF, 47000000000000000000000000000µF, 68000000000000000000000000000µF, 100000000000000000000000000000µF, 150000000000000000000000000000µF, 220000000000000000000000000000µF, 330000000000000000000000000000µF, 470000000000000000000000000000µF, 680000000000000000000000000000µF, 1000000000000000000000000000000µF, 1500000000000000000000000000000µF, 2200000000000000000000000000000µF, 3300000000000000000000000000000µF, 4700000000000000000000000000000µF, 6800000000000000000000000000000µF, 10000000000000000000000000000000µF, 15000000000000000000000000000000µF, 22000000000000000000000000000000µF, 33000000000000000000000000000000µF, 47000000000000000000000000000000µF, 68000000000000000000000000000000µF, 100000000000000000000000000000000µF, 150000000000000000000000000000000µF, 220000000000000000000000000000000µF, 330000000000000000000000000000000µF, 470000000000000000000000000000000µF, 680000000000000000000000000000000µF, 1000000000000000000000000000000000µF, 1500000000000000000000000000000000µF, 2200000000000000000000000000000000µF, 3300000000000000000000000000000000µF, 4700000000000000000000000000000000µF, 6800000000000000000000000000000000µF, 10000000000000000000000000000000000µF, 15000000000000000000000000000000000µF, 22000000000000000000000000000000000µF, 33000000000000000000000000000000000µF, 47000000000000000000000000000000000µF, 68000000000000000000000000000000000µF, 100000000000000000000000000000000000µF, 150000000000000000000000000000000000µF, 220000000000000000000000000000000000µF, 330000000000000000000000000000000000µF, 470000000000000000000000000000000000µF, 680000000000000000000000000000000000µF, 1000000000000000000000000000000000000µF, 1500000000000000000000000000000000000µF, 2200000000000000000000000000000000000µF, 3300000000000000000000000000000000000µF, 4700000000000000000000000000000000000µF, 6800000000000000000000000000000000000µF, 10000000000000000000000000000000000000µF, 15000000000000000000000000000000000000µF, 22000000000000000000000000000000000000µF, 33000000000000000000000000000000000000µF, 47000000000000000000000000000000000000µF, 68000000000000000000000000000000000000µF, 100000000000000000000000000000000000000µF, 150000000000000000000000000000000000000µF, 220000000000000000000000000000000000000µF, 330000000000000000000000000000000000000µF, 470000000000000000000000000000000000000µF, 680000000000000000000000000000000000000µF, 1000000000000000000000000000000000000000µF, 1500000000000000000000000000000000000000µF, 2200000000000000000000000000000000000000µF, 3300000000000000000000000000000000000000µF, 4700000000000000000000000000000000000000µF, 6800000000000000000000000000000000000000µF, 100µF, 15000000000000000000000000000000000000000µF, 22000000000000000000000000000000000000000µF, 33000000000000000000000000000000000000000µF, 47000000000000000000000000000000000000000µF, 68000000000000000000000000000000000000000µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 100µF, 15000µF, 22000µF, 33000µF, 47000µF, 68000µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 100µF, 15000µF, 22000µF, 330000000000000000

Audio


THE HI-FI MAGAZINE FOR LEISURE LISTENING

Britain's exciting new-style magazine in music and hi-fi, AUDIO is about every important aspect of the modern sound scene—from the make-up of sound, to the latest means of reproducing it... the equipment, its installation and its operation. AUDIO examines new trends, looks at the latest discs and tapes, shows you how to get the most for your money—in clarity, definition and craftsmanship.

IN THE NOVEMBER ISSUE

OUT FRIDAY OCT. 19

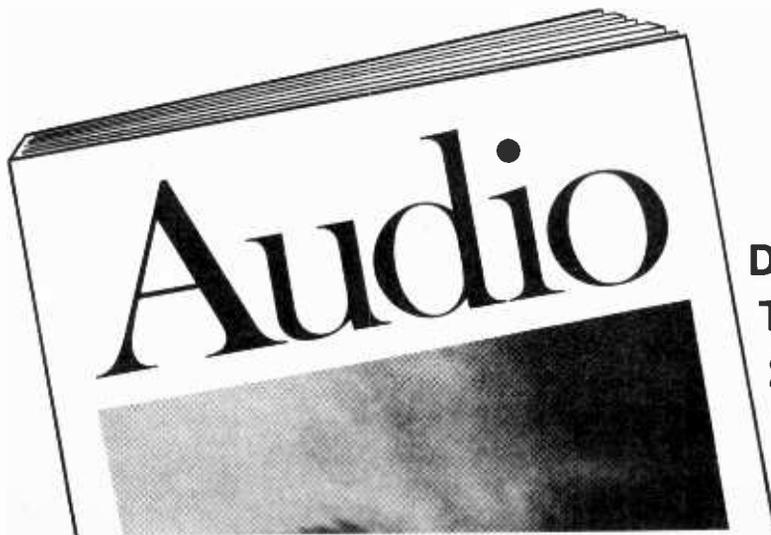**Exclusive interview with André Previn.
Tape recording for beginners. Is that heavy
turntable really necessary. Up-to-the-
minute report on Video. Record reviews.**



**DON'T MISS
THIS ISSUE
20p**

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY £1.05

POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	55p
B81	10	Reed Switches, 1" long, 1/4 dia. High Speed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	55p P & P 15p
H4	250	Mixed Resistors. Approx. quantity counted by weight	55p P & P 15p
H7	40	Wirewound Resistors. Mixed types and values	55p
H9	2	OCPT71 Light Sensitive Photo Transistor	55p
H28	20	OC2001/2/3 PNP Silicon uncoded TO-5 can	55p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	55p
H33	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	55p
H38	30	Short lead Transistors. NPN Silicon Planar types.	55p
H39	6	Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945	55p
H40	20	BFY50/2, 2N696, 2N1613 NPN Silicon uncoded TO-5	55p
H41	2	Sil Power transistors comp pair BD131/132	55p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each



OVER
1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Silicon planar plastic transistors. Unmarked, untested-factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.
Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.
Please state Audio NPN or Audio PNP when ordering.
ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44 P. & P. 11p/1,000.

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" NPN Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon similar ZTX 300 range
TYPE "G" NPN Silicon plastic encapsulation.
TYPE "H" PNP Silicon similar ZTX 500 range

8 RELAYS FOR 8 VARIOUS TYPES £1.10
P & P 27½

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors. Please ask for Pak P1. Only 55p. 11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television. **This complete kit of parts costs £3.85, post paid.**

A MUST for Colour T.V. Alignment.

ELECTRONIC TRANSISTOR IGNITION

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features:—
Transistor and conventional switchability, burglar proof lock up and automatic alarm, negative and positive compatibility. This project is a "star" feature in the September edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine.

Complete kit including p & p £7.92
Ready built and tested unit £3.02 extra.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

PLASTIC POWER TRANSISTORS

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms. Range 1. VCE. Min 15. HFE Min 15.
40 Watt 22p 13-25 26-50
90 Watt 22p 20p 18p
Range 2. VCE. Min 40. HFE Min 40.
40 Watt 33p 31p 28-50
90 Watt 38p 36p 33p
Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16½p each / Now new low profile 16 pin type at 18p each / type

BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes: 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.

The Hiffie Radio Valve & Transistor Data Book 9th Edition; p. & p. 23½p 75p
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications.
N.B. Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% VAT
MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE.
BUY THESE GOODS WITH ACCESS.

BI-PRE-PAK LTD
CO. REG. No. 820919

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF
TELEPHONE: SOUTHEND (0702) 46344

TRANSFORMERS

DOUGLAS GUARANTEED
Prices include 10% VAT & p. & d.
12 or 24 volts

Output V. & Amps	Ref. No.	Price
12V x 2 250mA x 2	MT113CS*†	£1.22
12V x 2 500mA x 2	MT121CT*†	£1.50
12V x 2 1A x 2	MT17AT†	£1.96
12V x 2 2A x 2	MT18AT	£2.72
12V x 2 3A x 2	MT70AT	£3.85
12V x 2 4A x 2	MT108AT	£3.77
12V x 2 5A x 2	MT72AT	£4.18

Output Amps	Ref. No.	Price
500mA	MT112CT*†	£1.47
1A	MT78AT†	£2.13
2A	MT3AT	£2.89
3A	MT20AT	£2.43

Output Amps	Ref. No.	Price
500mA	MT102AT	£1.82
1A	MT103AT	£2.87
2A	MT104AT	£4.20

Output Amps	Ref. No.	Price
500mA	MT124AT†	£2.03
1A	MT126AT	£2.94

AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price
20VA	0-115-210-240	XMT113CT	£1.22
75VA		XMT64AT	£2.82
150VA	0-115-200-220-240	XMT4AT	£2.85
200VA		XMT65AT	£3.84

400V Output at 50 HZ. Ref. IT3AT
C-D Ignition System by R. M. Marston, Esq., Wireless World

EQUIPMENT RANGE

Sec. output (r.m.s.)	Ref. No.	Price
3-0-3 V.	200mA MT238CS*†	£1.12
9-0-9	100mA MT13CS*†	£1.12
12-0-12	50mA MT239CS*†	£1.12
20-0-20	30mA MT241CS*†	£1.12
0-20 x 2	300 x 2 MT214CT*†	£1.74
0-8-9 x 2	500mA x 2 MT207CT*†	£2.06
0-15-20 x 2	500mA x 2 MT205AT*†	£2.95
0-15-27 x 2	500mA x 2 MT203AT*†	£3.46
0-15-27 x 2	1A x 2 MT204AT*†	£4.70
20-12-0-12-20	700mA (d.c.) MT221AT*	£1.82

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; * with interwinding screen; † untapped 240V Primary; ‡ tapped at 210-240V; other Primaries tapped at 200-220-240V.

Over 200 types in stock through agents or direct. Please send for lists.
DOUGLAS ELECTRONIC INDUSTRIES LTD.
Direct Sales Dept. F.W., Thames Street, LOUTH, Lincs. LN11 7AD

4-STATION INTERCOM



£8.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Slaves), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Slaves and Slaves to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 43p

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On Off switch and volume control. Price £18-95 P. & P. 60p

INTERCOM/BABY ALARM



OUR PRICE ONLY £4.95

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. De-Luxe Model complete with 66ft. connecting wire. Complete with Battery. P. & P. 33p




£3.99

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 25p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.11)
169 KENSINGTON HIGH STREET, LONDON, W.8.

SINCLAIR EQUIPMENT

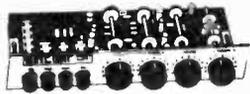


Project 60 FM Tuner	£15-95 (£1-85)	
2 Z30/Stereo 60/PZ5	£18-75 (£2-05)	
2 Z30/Stereo 60/PZ6	£18-85 (£2-25)	
2 Z50/Stereo 60/PZ8/Trans	£23-20 (£2-70)	
Z30 £3-50 (55p)	Stereo 60	£7-80 (98p)
Z50 £4-30 (65p)	Trans for PZ8	£2-95 (50p)
PZ5 £3-47 (57p)	2000 Amp	£22-00 (£2-70)
PZ6 £6-30 (83p)	3000 Amp	£31-50 (£3-35)
AFU £4-40 (64p)	2000 Tuner	£27-00 (£2-90)
PZ8 £6-40 (84p)	3000 Tuner	£27-00 (£2-90)
Q16 £5-90 (79p)	Project 605	£20-90 (£2-40)

PROJECT 60 KIT £2-70 (49p)
Our extremely popular kit contains the extra capacitors, diode plugs and sockets, cable and fuse-holder needed to complete Project 60.

BATTERY ELIMINATOR BARGAIN

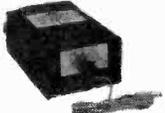Introducing the most versatile battery eliminator ever offered, with a high current output that makes it suitable for operating most battery tape recorders, record players, cassette recorders and shavers. Input 200/240V. Output voltage selected by front panel switch may be set to 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500mA.




IC RADIO CHIP TBA651 £2-10 (32p)
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2-10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1-75 (29p).

S-DECS AND T-DECS

S-DECS	£1-44 (25p)
T-DECS	£2-88 (40p)
µ-DECS A	£3-18 (43p)

16 diode IC carriers £1-20 (17p)

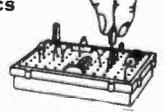

SINCLAIR SUPER IC12

Supplied complete with free 44 page Instruction booklet and printed circuit



DELUXE KIT
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-55 (26p). Stereo model with balance control £3-50 (46p).

BASIC KIT FOR THE IC12
Contains components for P.C. board and volume and simple tone controls. Mono version £1-25 (24p). Stereo model with balance control £2-90 (40p).

IC12 POWER KIT
A set of components to construct a 28V 0.5 Amp power supply £2-47 (50p).

LOUDSPEAKERS FOR THE IC12
5" x 8 ohm £1-10 (27p). 5" x 8" 8 ohm £1-55 (37p). 10" x 6" 15 ohm £2-20 (44p).

PREAMPLIFIER KITS FOR THE IC12
Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1-30 (24p). Stereo model £2-30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1-20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

SINCLAIR EXECUTIVE CALCULATOR



NOW ONLY £38-00 (£4-00).

SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent
Please add the sum shown in brackets after the price to cover the cost of post and VAT. Mail order only. No callers, please.

ambit international

W. S. POEL—P. L. A. BURTON

FND70—matched 7 segment LED displays £2-10 each, with data. 5v working. 4 for £7-90. (2" x 4")
9368—custom LED driver IC. More than a 7447. It includes decoder/divider/latch/triple blanking. £2-20 each (with data). 4 for £7-50 (161dL)
LM380—a versatile 2w/12v, 4w/18v audio IC. Only one external component, apart from input/output capacitors. £1-45 (with data).
NE561B PLL £3-50, **NE565A PLL** £2-80, **NE567 PLL** £2-50.
NEW FROM LITHIC: twin 567 tone decoders in one package, only £4-10 each. (All PLL with data)
TAD100—well tried AM receiver IC. £1-55.
TBA651—SGS radio IC, with r/osc/mix/lf. AM or FM. £2-50 each, with 12-page data and ceramic IF filter.
All LITHIC/FAIRCHILD/RCA/TEXAS/MOTOROLA etc. devices obtainable to order. SAE for quotes, please.
Discretes Include RF power:—
BLY33/40290 £1-40. Sets of 4 devices that give 30W out (min) at 145 MHz, 100mW drive needed. £3-20. 40673 (prot. gate 400 MHz mosfet) 57p.
BF256LB (1000 MHz working J FET) 37p.
Other bits:—
Dalo PCB marker pens 8p. **NICADS** 1-2v/1-8Ah £1-75 each, 10 nicads=12v for £17-50. Full range of ignition suppressors, shrouded plug caps only 50p, etc., etc.

We believe that there isn't much point in trying to sell people advanced technology if there isn't the data and application advice service to back it up. Who wants an LED 7 segment display with special decoder, latch and driver if there is no advice on what to do with it? So, when you take a look at AMBIT's catalogue (10p), you will be pleasantly surprised to find full data on all the ICs, PLUS applications circuits, PLUS references to magazine articles which have employed the device. (Copies of the articles available too.) Here are a few samples of the AMBIT range:—

A full range of TOKO ceramic and mechanical filters
CFT455C 6kHz ceramic filter (with data) .. 50p
CFT455B 8kHz 50p
CFT455C 4-8kHz 55p
4, 5 or 7kHz mechanical filters £1-40
Plus the range of TOKO Inductors for stereo, radio and tv, ultra stereo etc.

CFS 10-7 ceramic 10-7 MHz FM filters, 40p each. (Block filters mean an end to twiddling cores to allign receivers etc.)

SPECIAL: STEREO pilot tone filter, two channel for £2-10 each (with data). Removes 19/38kHz. See our catalogue for full details.

Unused surplus at silly prices:—
Ceramic capacitors (many low values between 0.4pf and 11pf) then 13, 16, 33pf. All 1p each.
Polystyrenes: 2-7p, 5, 6-8, 10, 15, 22, 27, 33, 47, 68, 100, 150, 220, 470 all at 1.5p each.
1000pf solder feedtrus 1p each. 1000+1000 with filter type ferrite bead built in, 2p each.

BNC plugs 50 & 75 ohm Straight, plus 50 ohm angle, only 8p each (in makers packets).

Discs. -001, 100v at 1p; -0047, 25v at 1p; -047, 25v and -1, 18v at 2p.

Terms:—CWO, credit accounts available. ALL PRICES INCLUDE VAT. Post 5p per order under £1. Free over £1. Send to:—
37 HIGH ST., BRENTWOOD, ESSEX

SURPLUS BARGAINS

POWER UNIT I/P 115v 50c/s, O/P 0 to 26v DC smoothed at 3 amps cont. can be adjusted from 0 to 26v by means of small variac on front panel, supplied tested with circ and Auto Trans to use unit on 240v £7-70. **SCOPES** Hartley type 13a D.B. gen purpose scope for use on 230v mains supplied with probe, leads, circ & copy of service manual tested £26-95. **SCOPES** American type TS.34 portable type single beam gen purpose 2" tube with magnifier, Y amp bandwidth to 2 Mc/s T.B. 10c/s to 50Kc supplied with leads, copy of service manual tested, these are for use on 115v 50c/s 240/115v Auto trans supplied £23-65. **FIELD TELEPHONES** type J metal cased req 2x1.5v cells tested £10-50 per pair. **POWER UNIT** 917 I/P 230v 50c/s O/Ps EHT 2Kv at 5 Ma, H.T. 600v at 160 Ma supplied from two separate 320v trans, 4v 2a for CRT heaters, 6.3v 2a twice supplied with circ, these will supply most surplus Ind units £6-38. **BATTERIES** as follows 24v 25 A/Hr made up of two 12v units size 12x8x6" £10-10 also 24v 4 A/Hr 24v only size 9x4x2 1/2 £4 also 6v 40 A/Hr metal cases £3-19 all new supplied with filling & charging inst. **TEST SET** with meter 2.5 Ma FSD scale 0 to 25 linear, 2 1/2" dia, 3 yaxley type rot swts 2p 8w, 3p 11w, 4p 11w, also terminals close tol res, neon ind etc' in neat carrying case. Note these can be modified to make a 5 range DC voltmeter instructions supplied (no extra parts required) £2. **SLOW MOTION DIAL UNIT** overhaul ratio 16:1 4" dia dial, as 1/2" dia O/P shaft parallel to front panel both fast & slow knobs are fitted precision unit £1-70 **RACK CABINETS** 19" type fully enclosed with front door overhaul size 41" H 22 1/2 x 22 1/2" side & back panels can be removed good quality unit made for Auto Elec USA £11. **TRANSISTOR INV TRANS** 12v to 300v at 150 Ma with circ £1-90. **TRANSISTOR MOD TRANS** 2xOC35 to QQV3-20 with driver trans £1-35. **COAX CABLE** high quality cable 1/2 OSD 75 ohm 20yds for £1-32. **COAX SKS** B.N.C. type single nut fixing UG910 75 ohm PTFE 5 for 55p, I.F. **TRANS** valve type 10-7 Mc/s 3 for 55p. **HEAD & MIKE SETS** moving coil type for 19 set new £1-70. **BLOWER MOTORS** double ended type 6 to 28v DC overhaul size 6x4" new £1-79. **SPEAKERS** 3 ohm size 3x3" 55p. **TUNING CONDS** split stator 25pf per section 1/2x1" shaft 2 for 55p. **CODER UNIT** contains 10 valves 12AT7, 6X4, 12AU7 etc 13 min relays will work on 12v, swt unit with 12 min micro swts complete in case £2-70. **HEADPHONE MATCHING TRANS & LEAD** matches high impedance O/P to low Z phones 5ft lead with standard plug new 60p. **COAX PLUGS & SKS** Belling Lee T.V. type 5 pairs for 60p. **YAXLEY SWTS** 4p 11w 4b with low value res & knob 76p 4p 4w 2b with res & knob 40p. **SWT UNIT** part of motor driven ass 4p 12w 4b & 2p 12w 2b with shorting wafer 64p. **LAMPS** aircraft type double fil with silvered reflector dual 14 watt 28v new 5 for 65p. **NEONS** wire ended type 1/25th watt req 470K res for 240v new 10 for 55p. **METER UNIT X POINTER** scale marked L & R FSD 115 µA can be used as Stereo Balance Ind circ supplied new £1-58. **VALVES** 5U4, 6X5, 6SN7, 6SL7, 85A2, 12AT7, 12AX7, 6AK5, 6BH6, 6H6, 6SK7M, 6SA7, 6N7, 5Y3GT, 6J6, 6X4, CV173, EF50, 6BA6, 6SA6, CV2179 (Sim to N78), OB2, ECC88, any 3 for 55p also 5763 44p, QQVO3-20 with base & TC £2. **RELAYS** R.F. switching type coil 12v uses sealed reeds as 2 NC & 1 NO R.F. contacts & 2 NO aux contacts size 1x1x1 1/2" suitable for RF, Video & A.F. swt 55p ea 10 for £4-40 **AUDIO OSC** type TS-382 covers 20c/s to 200Kc in 4 ranges, O/P 1µV to 10 volts R.M.S. in 7 ranges, built in freq check at 60 & 400c/s, fitted O/P voltmeter, I/P 115v 50c/s supplied with Auto trans & copy of Service Manual tested £28-15. **NIC CAD BATTS.** 6v units 2.5 A/Hr £2 ea.

List of circs and manuals available, S.A.E. please.

THE ABOVE PRICES INCLUDE POST/CARR. AND V.A.T. CHARGES.

Carr. charges apply to mainland only, all goods ex equip unless stated otherwise, S.A.E. with enquiries.

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL
Tel. 444278 (0742)

QUALIFY TO EARN MORE MONEY In a better job

Exciting new career opportunities! They're just waiting to be grasped—in the ever-growing industries of electronics, radio and television. And with ICS behind you, you can soon win the qualifications you need to assure your career success. Win them in your own time, in your own home, by starting an ICS learn-as-you-earn correspondence course now. You get personal, individual attention from really expert and experienced tutors. We teach you the theory, we teach you the practice. Books and components are provided. So is all the assistance, all the backing you need.

We also have a complete range of courses at the ready for people keen to score success in other fields. Whatever qualification you're after, we can help you get it, whether you're pushing ahead where you are or switching to something completely new.

Take your first step now towards a better paid, more assured future. Send for your FREE Careers Guide today.

Take one of these courses

Society of Engineers Graduateship (Electrical Engineering)
C & G Telecommunications Technicians Certificates
C & G Electrical Installation Work
C & G Certificate in Technical Communication Techniques
C & G Radio Amateurs
MPT General Certificate in Radio Telegraphy
Audio, Radio and TV Engineering & Servicing
Electronic Engineering Maintenance. Engineering systems
Instrumentation & Control systems
Computer Engineering & Technology
Electrical Engineering, Installations, Contracting, Appliances
Self-build radio courses

... or take one of these if your future lies in other fields

- | | |
|---|---|
| GCE O and A Level
Basic foundation for success in a thousand and one careers—recognised by everybody. | Management, Marketing and Business
Instruction in the latest proved principles and techniques used in each highly specialised area. |
| All Boards—64 subjects | *Personnel
*Administrative
*Works
*Transport
*Business
*Sales
*Marketing
*Advertising
*Marketing
*Public Relations
*Sales |
| Building
Tuition for recognised technical qualifications in all fields. | *Computers
*Purchasing
*Book-keeping
*Work Study
*Storekeeping
*Small Business Owners
*Fire Service
*Promotion and Institute of Fire Engineers
*Police
*Entrance and Promotion |
| Architecture
Builders Quantities
Carpentry, Joinery
Draughtsmanship
*Quantity Surveyors
Clerk of Works
Heating, Ventilating | *Promotion and Institute of Fire Engineers
*Police
*Entrance and Promotion |
| Engineering
Theoretical and practical tuition geared either to professional and technical examinations or to vocational (non-exam) courses.
Mechanical, Motor, Diesel, Chemical
Welding
Refrigeration
Draughtsmanship
Garage Management | *Courses for appropriate professional exams available in addition to ICS Diploma courses. |

POST TODAY FOR FREE DETAILS

ICS your key to a brighter better future

To: International Correspondence Schools, Dept. 232X
Intertext House, Stewarts Road, London, SW8 4UJ.

Name

Address

Age Occupation

Accredited by the C.A.C.C.

TRANSISTORS, ZENER DIODES etc.



ALL valves guaranteed

Fully guaranteed Individually packed VALVES

B19H	£1-75	ECH84	40p	OA2	38p
CV31	40p	ECL90	40p	OB2	35p
DAF96	40p	ECL82	31p	PAC850	35p
DF96	40p	ECL83	63p	PC7	41p
KD56	51p	ECL86	36p	PC900	42p
DL92	32p	EF36	50p	PC824	30p
DL84	46p	EF37A	80p	PC285	45p
DL96	40p	EF40	60p	PC189	40p
DM70	40p	EF41	65p	PC8200	75p
DY86	28p	EF80	25p	PCF80	25p
DY87	28p	EF83	60p	PCF82	27p
DY802	30p	EF85	31p	PCF84	54p
E88C0/01	£1-08	EF86	27p	PCF86	50p
E180CC	37p	EF89	25p	PCF90	50p
E181CC	90p	EF91	27p	PCP201	60p
E182CC	£1-08	EF92	31p	PCP801	44p
EA50	18p	EF95	31p	PCF802	45p
EAB380	27p	EF183	28p	PCF805	60p
EAF42	45p	EF184	31p	PCF806	65p
EB01	20p	EF1200	67p	PCF908	85p
EB33	40p	EF42	45p	PC189	40p
EB41	50p	EL41	55p	PC181	50p
EB42	50p	EL84	21p	PC182	30p
EB43	45p	EL85	37p	PC183	30p
EB44	50p	EL86	38p	PC184	35p
EB45	50p	EL90	31p	PC185	40p
EB46	50p	EL96	30p	PC186	43p
EB47	50p	EL97	32p	PC1200	60p
EB48	50p	EL98	33p	PL260	50p
EB49	50p	EL99	34p	PL36	50p
EB50	50p	EL00	35p	PL41	40p
EB51	50p	EL01	36p	PL42	35p
EB52	50p	EL02	37p	PL43	38p
EB53	50p	EL03	38p	PL44	30p
EB54	50p	EL04	39p	PL50	82p
EB55	50p	EL05	40p	PL60	62p
EB56	50p	EL06	41p	PL64	62p
EB57	50p	EL07	42p	PL68	70p
EB58	50p	EL08	43p	PL69	85p
EB59	50p	EL09	44p	PL70	85p
EB60	50p	EL10	45p	PL80	85p
EB61	50p	EL11	46p	PL82	85p
EB62	50p	EL12	47p	PL83	85p
EB63	50p	EL13	48p	PL84	85p
EB64	50p	EL14	49p	PL85	85p
EB65	50p	EL15	50p	PL86	85p
EB66	50p	EL16	51p	PL87	85p
EB67	50p	EL17	52p	PL88	85p
EB68	50p	EL18	53p	PL89	85p
EB69	50p	EL19	54p	PL90	85p
EB70	50p	EL20	55p	PL91	85p
EB71	50p	EL21	56p	PL92	85p
EB72	50p	EL22	57p	PL93	85p
EB73	50p	EL23	58p	PL94	85p
EB74	50p	EL24	59p	PL95	85p
EB75	50p	EL25	60p	PL96	85p
EB76	50p	EL26	61p	PL97	85p
EB77	50p	EL27	62p	PL98	85p
EB78	50p	EL28	63p	PL99	85p
EB79	50p	EL29	64p	PL00	85p
EB80	50p	EL30	65p	PL01	85p
EB81	50p	EL31	66p	PL02	85p
EB82	50p	EL32	67p	PL03	85p
EB83	50p	EL33	68p	PL04	85p
EB84	50p	EL34	69p	PL05	85p
EB85	50p	EL35	70p	PL06	85p
EB86	50p	EL36	71p	PL07	85p
EB87	50p	EL37	72p	PL08	85p
EB88	50p	EL38	73p	PL09	85p
EB89	50p	EL39	74p	PL10	85p
EB90	50p	EL40	75p	PL11	85p
EB91	50p	EL41	76p	PL12	85p
EB92	50p	EL42	77p	PL13	85p
EB93	50p	EL43	78p	PL14	85p
EB94	50p	EL44	79p	PL15	85p
EB95	50p	EL45	80p	PL16	85p
EB96	50p	EL46	81p	PL17	85p
EB97	50p	EL47	82p	PL18	85p
EB98	50p	EL48	83p	PL19	85p
EB99	50p	EL49	84p	PL20	85p
EB00	50p	EL50	85p	PL21	85p

OA5	20p	OC71	12p	IN283A	£1-30	3N154	95p	BC108	10p	GET115	45p
OA10	25p	OC72	20p	IN4785	50p	3N159	£1-45	BC113	10p	GET116	50p
OA70	10p	OC73	30p	IZMT5	35p	6FR5	45p	BC118	20p	GEX66	£1-80
OA71	10p	OC75	25p	IZMT10	82p	12FR60	73p	BCY72	15p	NKT222	20p
OA73	7p	OC76	25p	IZT5	67p	40854	£1-25	BF115	25p	NKT304	50p
OA74	7p	OC81	20p	IZT10	63p	40856	£1-25	BY213	20p	RAS10A	50p
OA79 (6D15)	10p	OC81D	20p	IG403	51p	40668	£1-25	BFY51	20p	SD918	35p
OA81	8p	OC82	25p	2N918	37p	40669	£1-40	B8	45p	SD928	31p
OA91	7p	OC82DM	30p	2N1304	22p	AC126	25p	B2	45p	RF438	32p
OA200	7p	OC83	25p	2N1306	25p	AC127	25p	BBY29	25p	SD94	23p
OA202	10p	OC83B	16p	2N1307	25p	AC128	20p	BU100	£1-30	SD98	45p
OA210	25p	OC84	25p	2N2147	64p	AC178	80p	BYZ13	25p	V405A	40p
OA211	30p	OC82	50p	2N2441	£1-50	AC179	25p	BYZ16	30p	Z2A51CF	78p
OC22	50p	OC139	25p	2N2904A	25p	ACY28	17p	CRS1/10	25p	ZR1	31p
OC25	40p	OC140	25p	2N2989	£4-00	AD149	50p	CRS1/30	38p	ZR21	46p
OC26	25p	OC170	25p	2N2985	20p	AD161	35p	CRS1/35	45p	ZR22	42p
OC28	60p	OC172	37p	2N3054	50p	AD162	35p	CRS1/40	45p		
OC29	60p	OC200	80p	2N3055	64p	AF118	50p	CRS1/45	30p		
OC35	50p	OC201	75p	2N3056	50p	AF127	20p	CRS1/50	30p		
OC36	56p	OC206	85p	2N4179	50p	AF178	45p	CRS2/20	38p		
OC38	42p	OC217	30p	2N4179	50p	AF178	45p	CRS2/30	45p		
OC44	17p	OC218	30p	2N4179	50p	AF178	45p	CRS2/40	45p		
OC45	18p	OC219	30p	2N4179	50p	AF178	45p	CRS2/50	45p		
OC70	18p	OC220	80p	2N4179	50p	AF178	45p	CRS2/50/25	55p		

6J34WA	65p	12S47	40p	6060	50p
6J5	35p	1A87	70p	6064	45p
6J5GT	30p	19AQ5	40p	6065	65p
6J6	25p	19G3	25-75	6080	£1-55
6J7	30p	19G6	25-75	6146	£1-75
6J7M	31p	19H4	25-25	6020	33-75
6K6GT	55p	20F4	£1-00	9001	15p
6K7	40p	2516GT	50p	9002	40p
6K7G	17p	30C15	70p	9003	45p
6K8GT	40p	30C17	85p	9004	12p
6K25	70p	30C18	75p	9006	12p
6L6M	1-35	30F5	80p		
6A7	40p	30PL1	70p		
6A7GT	25p	30PL12	80p		
6B7GT	20p	30PL14	80p		
6B7	40p	30L15	80p		
6B7J	40p	30L17	80p		
6B7GT	25p	30L12	75p		
6B7	45p	30P19	70p		
6B7GT	25p	30PL11	70p		
6B7GT	25p	30PL13	90p		
6B7GT	25p	30PL14	85p		
6B7GT	25p	35L6GT	50p		
6V6G	15p	35W4	30p		
6V6GT	35p	35Z4GT	50p		
6X4	35p	50C5	45p		
6X5G	25p	50C6G	£1-10		
6X6	35p	50RH5	55p		
6X6GT	35p	50RH6	55p		
6Y6	75p	75	50p		
6-30L2	85p	76	55p		
6Z4	40p	78	50p		
7B7	50p	80	55p		
7Y4	60p	723A/B	£7-00		
806	30p	803	£5-50		
11E2	£3-70	806	£12-00		
12AT6	35p	807	50p		
12AT7	27p	813	24-70		
12AU7	24p	832A	£2-70		
12AV6	40p	866A	£1-25		
12AX7	25p	931A	£4-75		
12BA6	25p	954	£3-75		
12BE6	35p	955	35p		
12BH7	32p	956	30p		
12C8	30p	957	35p		
12E1	£2-85	991	40p		
12K5	85p	991	70p		
12K7GT	45p	2051	70p		
12K8GT	40p	5933	£1-00		
12QGT	40p	6057	55p		


ZENER DIODES

All preferred voltage	
1W	0-17
1/2W	0-87
1/4W	0-87
1/8W	0-87
1/16W	0-87
1/32W	0-87
1/64W	0-87
1/128W	0-87
1/256W	0-87
1/512W	0-87
1/1024W	0-87
1/2048W	0-87
1/4096W	0-87
1/8192W	0-87
1/16384W	0-87
1/32768W	0-87
1/65536W	0-87
1/131072W	0-87
1/262144W	0-87
1/524288W	0-87
1/1048576W	0-87
1/2097152W	0-87
1/4194304W	0-87
1/8388608W	0-87
1/16777216W	0-87
1/33554432W	0-87
1/67108864W	0-87
1/134217728W	0-87
1/268435456W	0-87
1/536870912W	0-87
1/1073741824W	0-87
1/2147483648W	0-87
1/4294967296W	0-87
1/8589934592W	0-87
1/17179869184W	0-87
1/34359738368W	0-87
1/68719476736W	0-87
1/137438953472W	0-87
1/274877906944W	0-87
1/549755813888W	0-87
1/1099511627776W	0-87
1/2199023255552W	0-87
1/4398046511104W	0-87
1/8796093022208W	0-87
1/1759218044416W	0-87
1/3518436088832W	0-87
1/7036872177664W	0-87
1/14073744353328W	0-87
1/28147488706656W	0-87
1/56294977413312W	0-87
1/112589954826624W	0-87
1/225179909653248W	0-87
1/450359819306496W	0-87
1/900719638612992W	0-87
1/180143917724992W	0-87
1/360287835449984W	0-87
1/720575670899968W	0-87
1/1441151341799936W	0-87
1/2882302683599872W	0-87
1/5764605367199744W	0-87
1/11529210734399488W	0-87
1/23058421468798976W	0-87
1/46116842937597952W	0-87
1/92233685875195904W	0-87
1/184467371702391808W	0-87
1/368934743404783616W	0-87
1/737869486809567232W	0-87
1/1475738936191344464W	0-87
1/2951477872382688928W	0-87
1/5902955744765377856W	0-87
1/11805911489531155392W	0-87
1/236118229790623106784W	0-87
1/4722364595812462135616W	0-87
1/94447291916249247122304W	0-87
1/18889458392498494244608W	0-87
1/37778916784996988489216W	0-87
1/75557833569993976974434432W	0-87
1/15111567139997995348888864W	0-87
1/	


now...

Project 80

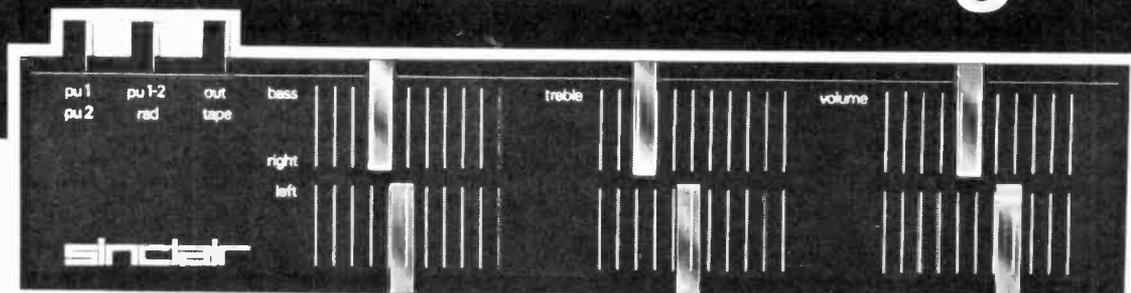...exciting new thinking
in modular hi-fi design



Stereo 80 pre-amplifier/control unit

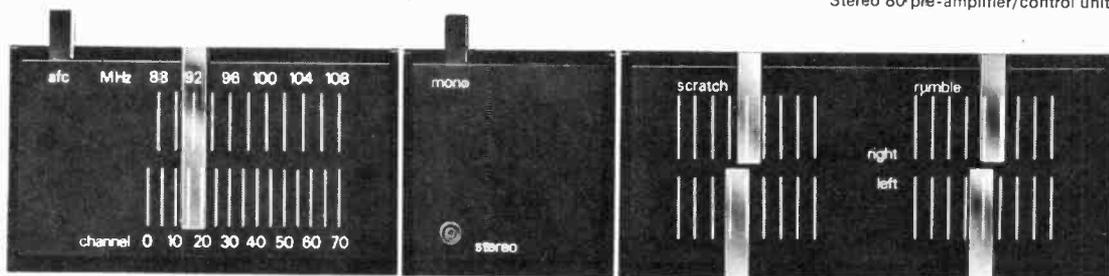


Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

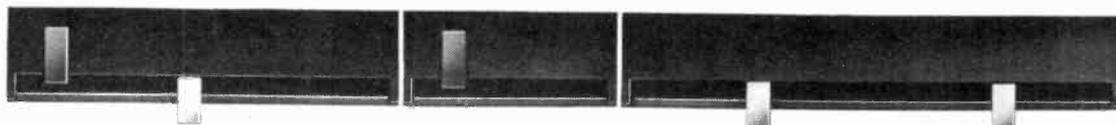the slimmest, most elegant hi-fi modules ever made



Living with hi-fi takes on new meaning now that Project 80 is here. These amazing new modules mark a brilliant technical advance all round; their size and presentation bring exciting new opportunities to install systems in ways hitherto only dreamed about but never before made practical. You can build a Project 80 system virtually anywhere and it is unbelievably simple to install and connect up. Everything that could possibly be wanted in a top quality do-it-yourself domestic hi-fi system will be found in Project 80 – compactness, elegantly ultra-modern styling, ease of fixing and operation, new control methods, and above all superb performance. New as well as popular established ideas on installation are featured on page four of this announcement to provide just a few examples of the system's fantastic versatility.

sincclair

INTERNATIONAL AUDIO FAIR STAND C. 8

Project 80 new modules


Stereo 80 pre-amplifier and control unit

As with other Project 80 units, the Stereo 80 is mounted by means of two bolts fixed at the rear which pass through holes drilled in the wood or plastic on which modules are to be mounted. *All the electronics are contained within the 2" deep front panel!* Connecting leads are taken away similarly out of sight. Each channel in the Stereo 80 has its own independent tone and volume controls operated by sliders. This enables exceptionally good environmental matching to be obtained. Provision is made for magnetic and ceramic pick-ups, radio and tape in and out. A virtual earth input stage forms part of the up-dated circuitry of the Stereo 80 to ensure the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS


Size - 260 x 50 x 20mm (10 1/2 x 2 x 3/8 ins)
 Finish - Black, with white markings
 Inputs - Mag. P.U. 3mV RIAA corrected; Ceramic P.U. 300mV
 Radio 300mV; Tape 30mV
 S/N ratio - 60db
 Frequency range - 20Hz to 15KHz ± 1dB; 10Hz to 25KHz ± 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV + AB monitoring for tape
 Controls - Press button for tape, radio and P.U. selection Volume.
 Bass + 12dB to -14dB at 100Hz; Treble + 11dB to -12dB at 10KHz

NEW

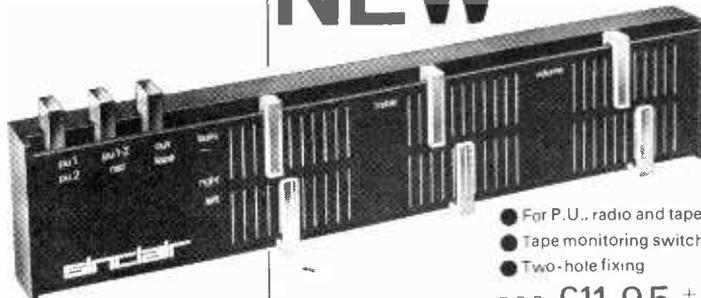

- For P.U., radio and tape
- Tape monitoring switch
- Two-hole fixing

R.R.P. £11.95 + £1.19 V.A.T.

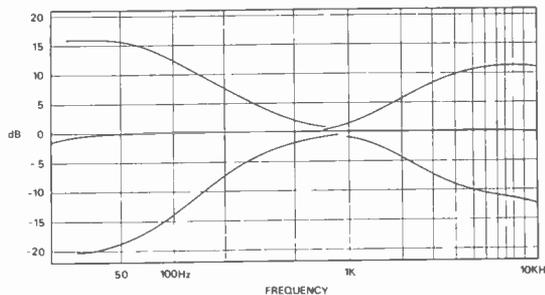


Project 80 FM tuner smaller, more efficient

A truly remarkable tuner in every way - its unbelievably compact size - its original circuitry - its dependable performance - all this in a boldly designed modern case measuring 85 x 50 x 20mm (3 1/2 x 2 x 3/8 ins). Greater adaptability (and possibly financial convenience) results from the tuner and stereo decoder section being made available separately.

TECHNICAL SPECIFICATIONS

Size - 85 x 50 x 20mm (approx. 3 1/2 x 2 x 3/8 ins)
 Tuning range - 87 to 108 MHz
 Detector - I.C. balanced coincidence, for good A.M. rejection
 AFC - Switchable, with thermistor control to prevent from drift
 One 26 transistor I.C.
 Twin dual varicap tuning
 Distortion - 0.3% at 1KHz for 75KHz deviation
 Ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Power requirements - 12 to 45 volts

NEW

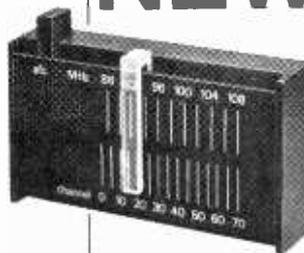

- AFC switch
- Twin dual varicap tuning
- 4-hole ceramic filter
- Slider tuning

R.R.P. £11.95 + £1.19 V.A.T.

Project 80 stereo decoder

Making the Project 80 decoder separate from the F.M. tuner gives the constructor a wider choice of systems as well as saving money in cases where stereo reception may not be required. This unit gives a 40dB channel separation with an output of 150mV per channel. The gallium arsenide light emitting beacon automatically lights up to show when a stereo transmission is tuned in. Designed essentially as an integral part of Project 80 systems, this multiplex stereo demodulator may be used in many cases with existing single channel frequency modulated tuners to provide stereo reception.
 Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/8 ins)
 One 19 transistor I.C.

NEW



- Solid-state stereo indicating beacon
- Readily adaptable for use with other tuners

R.R.P. £7.45 + 0.74p V.A.T.

new constructional techniques

...and again Sinclair leads the world

- 1962 Micro-miniature power amp small enough to stand on a 10p. piece. Slimline pocket receiver smaller than a 20 cigarette pack
- 1963 Micro-6 receiver, smaller than a matchbox
- 1964 Pocket F.M. receiver: PWM amp.
- 1965 Z.12 power amplifier module. PZ.3 power supply
- 1966 Stereo 25 pre-amp/control unit
- 1967 Micromatic Q.14 loudspeaker: the first Neoteric
- 1968 IC.10, the first ever integrated circuit for constructors use

- 1969 Q.16 - improved version of Q.14 Systems 2000 and 3000: Project 60 launched
- 1970 IC.12 Project 60S
- 1971 Project 60 stereo FM tuner. Z.50 PZ.8
- 1972 Improvements to Project 60 with Z.50 MK.2 and PZ.8 Mk.3 The Executive Calculator: Digital multi-meter Q.30 speaker
- 1973 Cambridge Calculator
PROJECT 80 LAUNCHED


...and next?

Project 80 active filter unit

This efficiently designed unit makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls are applied to each channel thereby making it easier to obtain ideal stereo balance in any kind of indoor environment

TECHNICAL SPECIFICATIONS

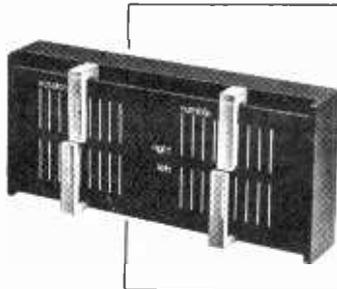Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/8 ins)
Voltage gain - minus 0.2dB
Frequency response - 36Hz to 22KHz, controls minimum
Distortion - at 1KHz - 0.03% using 30V supply
HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct slope
LF cut off (rumble) - 28dB at 20Hz, 9dB/oct. slope



NEW

- For scratch and rumble control
- Transistorised active circuitry


R.R.P. **£6.95** + 0.69p V.A.T.

Z.40 & Z.60 power amplifiers totally short-circuit proof

Either of these entirely new power amplifiers is intended for use in Project 80 installations although, of course, they are readily adaptable to an even wider range of applications. Both Z.40 and Z.60 incorporate built-in protection against shortcircuiting and risk of damage arising from mis-use is greatly reduced. Comprehensive instructions are supplied with each of the modules.

Z.40 Technical Specifications
Size - 55 x 80 x 20mm (2 1/8 x 3 1/8 x 3/8 ins) 9 transistors
Input sensitivity - 100mV
Output - 15 watts RMS continuous into 8 Ω (35V), 30 watts music power into 4 Ω (30V)
Frequency response - 10Hz - 100KHz ± 1dB
Signal to noise ratio - 64dB
Distortion - at 10 watts into 8 Ω less than 0.1%
Power requirements - 12-35 volts

Z.60 Technical Specifications
Size - 55 x 98 x 20mm (2 1/8 x 3 7/8 x 3/8 ins) 12 transistors
Input sensitivity - 100-250mV
Output - 25 watts RMS into 8 Ω (45V), 50 watts music power into 4 Ω (50V)
Distortion - typically 0.03%
Frequency response - 10Hz to more than 200KHz ± 1dB
Signal to noise ratio - better than 70dB
Built-in protection against transient overload and short circuit
Load impedance - 4Ωmin; max. safe on open circuit

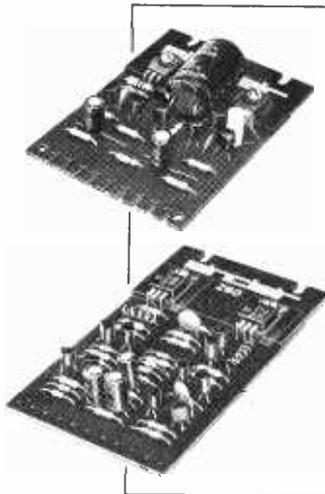

NEW


Z.40
R.R.P. **£5.45** + 0.54p V.A.T.

Z.60
R.R.P. **£6.95** + 0.69p V.A.T.

Sinclair power supply units PZ.8

the worlds most advanced unit in its class

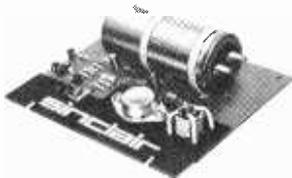Stabilised power supply unit Re-entrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V.
R.R.P. £7.98 + 0.79p V.A.T.
Without mains transformer PZ.5 30V unstabilised
R.R.P. £4.98 + 0.49p V.A.T.
PZ.6 35V, stabilised
R.R.P. £7.98 + 0.79p V.A.T.




Recommended Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	£5.45 + 54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10.43 + £1.04 V.A.T.
30W, RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; PZ.8	£30.83 + £3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amplifier	2 x Z.60s, Stereo 80; PZ.8	£33.83 + £3.38 V.A.T.
Indoor P.A.	Z.60, PZ.8	£14.93 + £1.49 V.A.T.
Car Radio	F.M. tuner, Z.40	£16.40 + £1.64 V.A.T.


sinclair

From Sinclair the worlds most advanced hi-fi modules

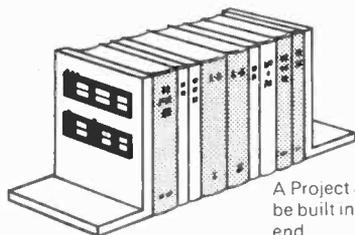
Sinclair Project 80 the ultra-modern non-obtrusive hi-fi



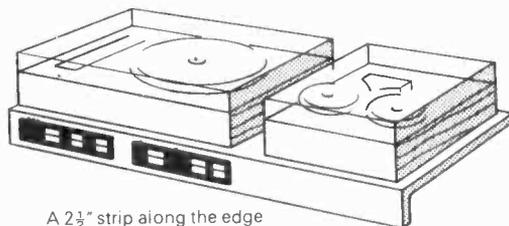
A Project 80 system could be built into a book-shelf end



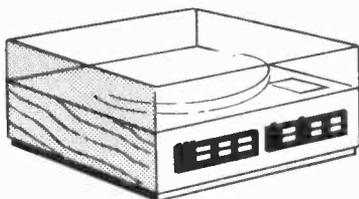
A 2 1/2" strip along the edge of a shelf could be sufficient to contain a complete system



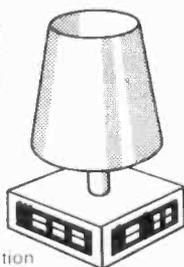
The modules mount very easily onto a playing plinth



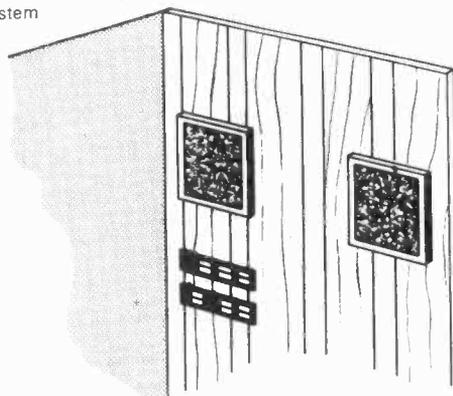
A novel application would be to build around the base of a lampshade



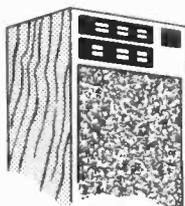Two Sinclair Q.16 loudspeakers suitably positioned together with Project 80 could be mounted on to a false wall.



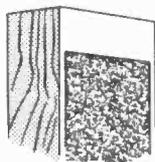Project 80 could be easily mounted onto a loudspeaker cabinet



When you have seen for yourself how fantastically slim and cleverly designed these modules are, further ways will suggest themselves in which they can become a pleasing part of your particular domestic environment.

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

PW11

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a small charge (typically £1.00) will be made.

sinclair

Sinclair Radionics Ltd.
London Road, St. Ives,
Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64311

MAPLIN ELECTRONIC SUPPLIES

*** SAME DAY SERVICE**



Model 120

LARGE or SMALL Centurion

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer detachable front panel finished in white.



Model 320

Dimensions in inches.

Model	W	H	D	Price
120	8	2 1/2	6	£1 85
220	8	6	6	22 65
221	8	6	6	22 80
320	12	8	12	25 00

Chassis for model 320 £1.75 extra.

Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C3 to C9 ★ Each frequency digitally derived from a SINGLE h.f. master oscillator.
★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra.
★ Gold-plated plug-in edge connection. ★ Complete fibre glass board (including tremulant if required) ONLY 3-7in. x 4-5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2T (with tremulant) ONLY £14.25.

DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.83 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.



MAPLIN: Projected site of London's third airport.

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboard. Send s.a.e. now for our detailed price lists.

YOU SIMPLY MUST SEE OUR PRICES!

Spring line reverberation unit (as specified)	£2 89
UA 7815 (15V 1.5A) voltage regulator	£2 30
REC 41A bridge rectifier	£1 06
741C 8-pin DIL	38p
MFC 6040 electronic attenuator	£0 95
RG 3402N for Ring Modulator	£1 69

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd	V	Price	Mfd	V	Price
1	63	6p	68	6-3	8p
1.5	63	6p	68	16	8p
2.2	63	6p	68	33	10p
3.3	63	6p	100	4	6p
4.7	63	6p	100	10	6p
8-8	40	6p	100	25	8p
6-6	63	6p	100	40	8p
10	25	6p	100	63	12p
10	63	6p	150	4-3	8p
15	16	6p	150	16	6p
15	40	6p	150	25	6p
15	63	6p	150	40	10p
22	10	6p	150	63	12p
22	25	6p	220	4	6p
22	63	6p	220	16	8p
33	6-3	6p	220	16	8p
33	16	6p	220	25	10p
33	40	6p	220	40	12p
47	10	6p	220	63	18p
47	25	6p	330	10	6p
47	40	6p	330	16	10p
47	63	6p	330	63	22p
47	63	6p	330	63	22p
47	63	6p	330	63	22p

Tantalum Bead

Mfd	V	Price	Mfd	V	Price
0.1	35	12p	10	16	14p
0.22	35	12p	10	25	18p
0.47	35	12p	15	16	16p
1.0	35	12p	22	16	16p
2.2	35	12p	47	6-3	18p
4.7	35	14p	100	3	18p

Trimmers—compression type

3 to 40pF	13p	30 to 250pF	18p
30 to 140pF	13p	100 to 500pF	21p

Silver Mica 50pF ± 1pF, ≥ 50pF ± 1%
2.2, 3.3, 5, 10, 18, 20, 22, 25, 27, 30, 33, 39, 47, 50, 56, 68, 75, 82, 100, 120, 150, 180, 200, 220, 270, 250, 270, 300, 330, 380, 470, 500, 560, 680, 820 8p; 1000, 1500 10p; 1800 11p; 2200 13p; 2700 15p; 3600 16p; 4700, 5000 20p; 6800 27p; 8200, 10,000 34p.

MIXED DIELECTRIC

1000VDC: 300VAC: Non-inductive.
0.001uF, 0.0022uF, 0.0033uF, 0.0047uF 7p;
0.01uF, 0.022uF 10p; 0.047uF, 0.1uF 12p;
0.22uF 23p; 0.47uF 30p.

POLYESTER FILM METALLISED 250VDC

0.01uF, 0.015uF, 0.022uF 3p; 0.033uF, 0.047uF, 0.068uF 3p; 0.1uF 4p; 0.15uF 4p;
0.22uF 5p; 0.33uF 7p; 0.47 8p; 0.68uF 12p;
1uF 14p; 1.5uF 21p; 2.2uF 25p.

Wide range of transistors, diodes and I.C.'s in stock see our catalogue for details.

PLUGS AND SOCKETS



DIN PLUGS

2 pin (1 flat) 8p
3 pin 12p
4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 10p

DIN Sockets

2 pin 8p
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 7p

MAINS

P360 3 pin 1.5A chassis plug with line socket. 28p
SA 2190 3 pin 5A chassis plug 17p
SA 1882 Line socket for above 18p

RS8 8 way chassis socket

52p

PHONO

Plug plastic 5p
Plug screened 9p
Chassis socket 4p

JACK

Std. 1/4" mono plug 13p
Screened 17p

POTENTIOMETERS

Rotary miniature carbon track 1/4" spindle

Single gang Lin or Log
5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p



Dual gang (Stereo) without switch Log or Lin

5k to 2M as above 38p

Single gang with DP switch

250V 2A Log or Lin 5k to 2M as above 23p

PRESETS

Sub-miniature 0-1W Vert or Horiz
100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p

Wirewound 10% 1W 1/4" spindle 10, 50, 100R 34p; 250, 500, 1k, 5k 33p; 10k, 37p; 25k 40p; 50k 44p.


RESISTORS

Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 11Ω to 910k E12 & E24 1p
Carbon Film 1/4W 5% 10Ω to 10M E12 3p
Metal Oxide 1/4W 2% 10Ω to 1M E12 & E24 4p
Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms E12 10p
Wirewound 2 1/2W 5% 1ohm to 270ohms E12 10p
E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

KNOBS

All 1/4" shaft. Grub screw fixing

Diameter shown in brackets

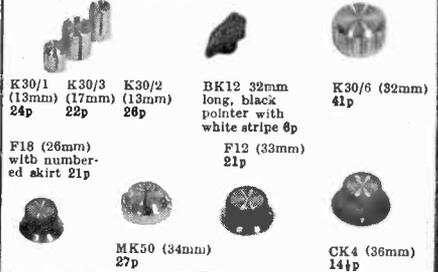

K30/1 (13mm) 24p

K30/3 (17mm) 22p

K30/2 (13mm) 28p

BK12 32mm long, black pointer with white stripe 6p

K30/6 (32mm) 41p

F18 (26mm) with numbered skirt 21p


F12 (33mm) 21p

MK50 (34mm) 27p

CK4 (36mm) 141p

SWITCHES

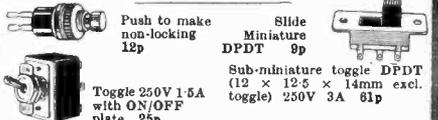Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p.
Mains rotary DPDT 250V 2A 20p.



Push to make non-locking 12p

Slide Miniature DPDT 9p

Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl. toggle) 250V 3A 61p

Toggle 250V 1.5A with ON/OFF plate 25p

VAT

Please add 10% to the final total.

For our fully illustrated catalogue please send 9p in stamps. Post and Packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex.

Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Aerials

GENUINE FULL SIZE

18 element TV aerial
as used by leading
TV companies

FOR ONLY
£2.20
+ 35p cart



ITV, BBC1 & 2B/W & Colour Guaranteed Perfect Pictures. Save ££s. We supply this genuine UHF aerial for only £2.20, can be fitted outside or inside. Dual ty made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions advice. Money Back Refund. Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters. SEND DIRECT TO DEPT. PW10 219 Mansfield Rd. Nottingham.

IMPERIAL TRADING AERIALS LTD.
the quality Aerial Specialists

BAINES FOR HIGH FREQUENCY AERIALS
Parabeams: PBM 6 £2.40, PBM 12 £3.35, PBM 18 £4.30, LBM 2 £6.00, LBM 2/CK £10.50.
Multibeams: MBM 18 £3.24, MBM 30 £4.40, MBM 45 £6.90, MBM 70 £12.10.
Stereobeams: SBM 1 £2.20, SBM 2 £2.95, SBM 3 £4.40, SBM 4 £4.80, SBM 6 £7.25, PM 3 harness £2.20, 75/300 Balun £1.60.
Rotators £22 and £28.
Amplifiers: VHF or UHF Masthead £5.75, Setback £4.00.
Accessories. SAE for full list. Co-ax 4p and 8p. These prices cover postage on the mainland.
11 Dale Cres. Tupton, Chesterfield S42 6DR. Telephone 863755.

Books and Publications

Radio BOOKS

- Servicing Transistor Radio Receivers£0.75
- Using an Oscilloscope£0.70
- Fault Location Exercises in Rad & TV Vol 1.....£0.80
- Fault Location Exercises in Rad & TV Vol 2.....£1.35
- Television Servicing Vol 1£0.85
- Television Servicing Vol 2£0.85
- Television Servicing Vol 3£0.60
- Television Servicing Vol 4£0.85
- Pal-D Colour Receiver Questions & Ans.£0.68
- Hi Fi, PA & Disco Amplifier Design H'bk.....£0.75
- Colour Television Picture Faults.....£2.50
- Television Timebase Circuits£1.00
- Understanding Television£2.10
- Electronic Novelties for the Motorist£0.50
- Modern Electronic Troubleshooting£1.30
- Semiconductors from A to Z£1.50
- Test Instruments for Electronics£1.30
- Manual of Electronic Circuits for the Home£0.50
- Getting Started with Transistors£1.20
- How to Test almost anything Electronic£1.30
- How to build Solid State Audio Circuits£1.75
- How to solve Solid State Circuit Troubles£1.75
- Jack Darr's Service Clinic£1.35
- 104 Ham Rad Projects for Novice & Technician £1.25

PLEASE ADD 10% FOR POSTAGE & PACKING
FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Ewllway, Beckenham BR3 2RZ

"SHORTWAVE VOICES OF THE WORLD," £1.70, postage and VAT 11p.
"SWL Address Book," £1.55+11p.
"Confidential Frequency List," £1.70+11p.
"Guide to International Medium Wave Broadcasts," 20p+4p. Books and full details from any bookshop, or in difficulty write to: David McGarva, PO Box 114, Edinburgh EH1 1HP.

TRANSISTOR DATA THE INTERNATIONAL TRANSISTOR DATA MANUAL

1973 EDITION is now ready. Data on upwards of 18,000 transistors of international origin. £6.20 in the U.K.. £6.90 elsewhere, includes surface mailing. Brochure available. Order direct from

SEMICON INDEX LTD.,
Freeport, Wokingham, Berks. RG11 2AY.

DENCO CLACTON LIMITED

355-7-9 Old Road

Clacton-on-Sea, Essex

Catalogue 20p post paid

S.A.E. all enquiries

WORLD RADIO TV HANDBOOK 1974 (published December), £3.15! Delivered direct from Denmark if ordered now! How to Listen to the World (late October), £2.00! Postage and VAT included! Every order acknowledged immediately! David McGarva, PO Box 114, Edinburgh EH1 1HP

Ladders

LADDERS. 24 1/2 ft £12.39. Carr £1.10. Leaflet. Home Sales Ladder Centre, (WLS2) Haldane, Halesfield (1) North, Telford, Shropshire. Tel: 0952 586644. Order C.O.D.

Service Sheets

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ **SERVICE SHEET CATALOGUE** 25p
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

- NEW BOOKS & PUBLICATIONS** PRICE
- DICTIONARY OF RADIO AND TELEVISION by W.E. Pannett. 380 pp. £1.80
- TELEVISION ENGINEERS POCKET BOOK 6th Edition, by P. J. McGoldrick. 400 pp. £2.50
- WORLD RADIO TV HANDBOOK 1972, 26th Edition. 384 pp. Special reduced offer. £1.10
- GUIDE TO BROADCASTING STATIONS, 17th Edition. 178 pp. £0.75
- OUTLINE OF RADIO & TELEVISION by J.P. Hawker. 408 pp. 300 Illustrations. £2.50
- UNDERSTANDING TELEVISION, 405/625/Colour Edition, by J.R. Davies. 512 pp. £2.10
- PRACTICAL TELEVISION CIRCUITS, 2nd Edition, by R.E.F. Street. 376 pp. 236 Illu. £1.80
- VIDEO RECORDING: RECORD & REPLAY SYSTEMS, by G.White. 216 pp. £3.25
- TELEVISION SERVICING by G.N. Patchett. Vol. 1. Principles, Video, Sound, Tuners. £0.85
- TELEVISION SERVICING by G.N. Patchett. Vol. 2. CRT, Sync-Seps, Timebases, etc. £0.85
- TELEVISION SERVICING by G.N. Patchett. Vol. 3. Limiters, Acc, Flywheel, Sync etc. £0.60
- TELEVISION SERVICING by G.N. Patchett. Vol. 4. Practical Servicing, Fault-finding. £0.85
- RADIO SERVICING by G.N. Patchett. Vol. 1. Basic Electro-Technology. £0.60
- RADIO SERVICING by G.N. Patchett. Vol. 2. Intermediate Radio Theory. £1.00
- RADIO SERVICING by G.N. Patchett. Vol. 4. Fault-Finding. £0.85
- PRACTICAL WIRELESS CIRCUITS, 18th Edition, by Staff of "Practical Wireless". £1.20
- RADIO CIRCUITS, 5th Edition, by W.E. Miller. 238 pp. Illustrated. £2.20
- PRACTICAL WIRELESS SERVICE MANUALS by R. Lewis. 265 pp. by H.W. Hellyer. 288 pp. £3.00
- WIRELESS SERVICING MANUAL, 10th Edition, by W.T. Cocking. 302 pp. £1.50
- FOUNDATIONS OF WIRELESS & ELECTRONICS by M.G. Scroggie. 552 pp. £3.00
- PHOTO-ELECTRONIC DEVICES by J.B. Dance. 182 pp. Illustrated. £2.10
- SEMICONDUCTOR PHOTOELECTRONIC DEVICES by Dr. inz. A. Ambroziak. 344 pp. £4.50
- UNDERSTANDING THE SEMICONDUCTOR by C.N. Matthews. 128 pp. £1.00
- PRACTICAL INTEGRATED CIRCUITS by A.J. McEvoy & L. McNamara. 144 pp. £0.90
- SOLID STATE DEVICES SERVICE MANUALS by R. Lewis. 265 pp. 182 Illustrations. £3.00
- NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good prices paid. Send large S.A.E. for FREE booklists. Postage on above books is 5p in the £1.00 (UK only) ..

BELL'S TELEVISION SERVICES

ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,
RECORD PLAYERS, TRANSISTORS,
STEREOGRAMS, RADIOGRAMS,
CAR RADIOS)
ALL AT 40p EACH

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7 days of posting your order.

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs) RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 732X INTERTEXT HOUSE,
STEWARTS RD., LONDON, SW8 4UJ

Situations Vacant

MEN!
£50 p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London

Computer Operators
Training Centre

P3, Oxford House

9-15, Oxford Street, W.1.
Telephone: 01-734 2874

For Sale

TV LINE OUTPUT TRANSFORMERS. Tidman Mail Order Ltd., 236 Sandycombe Rd., Richmond, Surrey TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

AMIDON type toroid cores. Details SAE to T.M.P. (Electronic Supplies), Office address 3 Bryn Clyd, Leeswood, Mold, CH7 4RU.

NEWNES RADIO and Television servicing. 8 volumes 1943-1961. Offers. Harvey, 27 Linchmere Road, Birmingham, B21 8JL.

AUDIO MIXER MODULES for hi-fi applications. Catalogue free, large S.A.E.; Hillcrest Electronics, 123 Harestone Hill, Caterham, Surrey.

CODAR CR45 with speaker, works excellently. Offers. MacMillan, 165 Stoke Road, Slough, SL2 5BQ.

Wanted

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

TOP PRICES PAID FOR NEW VALVES and TRANSISTORS

popular T.V. and Radio types.
KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

Receivers and Components

**TAPE
HEADS**

Send stamp for lists.

R.D.I. Ltd.

Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

For valve and
transistorized re-
corders from £2 ea.

Trampolite electronics

ALL BRAND NEW, no rejects.
Money back warranty. 5V
DIGITAL INDICATOR. 0-9DP
socket and filter £1.45. LED
TYPE 1" 0-9DP DIL £2.85 ea.
LIGHT EMITTING DIODES. All
with data and panel clip.
TIL 209 1/2" dia. 24p. Red 1/2" dia.
type 33p. Green 75p. INFRA
RED beam LED £1.10. TGS
GAS detector £1.69. ULTRA-
SONIC TRANSDUCERS £2.

DALO PCB resist marking pen 87p. Copper board
12" x 6" BRBP 40p FeC etch PAK 18p.
INTEGRATED CIRCUITS: with data if required.
IC LITE SWITCH: Photo amp/trigger 40ma/11-20
relax or TTL 37p. DIL relay £1.10.

IC digital clock

MOS/LSI type 28 pin 4 or 6 digit 12/24 hr. Chip
with socket £18. PCB £1.69. KIT £21.49. 741 DIL
8 pin 25p. 709 14p. DIL 8pin, 748 29p, 710 33p. 555
TIMER mono/stable osc. clock 87p. REGULATORS:
14A 5 to 20V £1.49. 723 57p.
RECEIVER ZN414 £1.09. Mini Rx kit £1.99. 1310
stereo decoder for tuners £2.69. Kit £2.45.

748 TTL: Gates 7400 etc. 15p ea. 7413 57p. 7441
75p. 7447 £1.99. 7499 89p. 7492 87p. 74121 45p.
DIL SOCKETS: New type 8/14/16 pin 18p.
SEMICONDUCTORS: 1A rect. 50V 84p. 400V 6p.
2N3055 33p. BC107 7p. BC108 7p. BC109 7p.
BC147/8/9 10p. BC167/8/9 13p. BC177/8/9 15p.
BC182/3/4 10p. BC212/9/4 11p. BCY70/72 13p.
BD131/3 55p. BFY50/52 13p. T1843 UJT 24p.
2N706 11p. 2N2869 13p. 2N2928 OY 8p. 2N2846 49p.
2N3053 17p. 2N3814 55p. 2N3702/3/4/5/6/7/8/9/10/11
All 9p ea. FETS: 2N3819E 10p. 2N3819 27p.
2N3823E 19p. ZENERS: B2788 8p. SCR 400V:
1A 25p.

TRANSFORMER 1A 8/12V £1. Resistors 11p.
450 & 470 mini IF transformers—Set 3 40p.
CAPACITORS: Disc 22p to 0.1 vF 3p. Electrolytic
25V: 10, 50, 100 vF 5p. 1000 vF 15p. Presets 5p.
CARBON POTS: 11p ea. switch + 11p. Dual 39p.

FLUORESCENT LIGHTS 12VOLT £2.79

13" 8 watt fully built with diffuser. 13W £2.79.
V.A.T. You must add 10% (1/10) to all prices.
FREE CAT. S.A.E. Data sheet. 8p ea. P.&P. 8p CWO
P.O. BOX 29, BRACKNELL, BERKS.

COMPONENTS GALORE. Pack of 500
mixed components manufacturers surplus
plus once used. Pack includes
resistors, carbon and W.W., capacitors
various, transistors, diodes, trimmers,
potentiometers etc. Send £1+10p p&p.
C.W.O. To: Caledonian Components,
Strathore Road, Thornton, Fife.

INTEGRATED CIRCUIT and FET
modules for construction of low-cost
receivers, converters, pre-selectors,
etc. SAE details.—P. R. Colledge, Glen
Tor, Torrington, Devon.

BUILD THE



TREASURE TRACER MK III Metal Locator

- Versicap tuning
- Excellent sensitivity and stability
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Ministry approved design
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- Completely new design

Send a e for leaflet

Complete kit
£9.80

Built, tested
and guaranteed
Post 35p
£13.75

MINKITS ELECTRONICS, 35a LANGLEY DRIVE, WANSTEAD,
LONDON E11 2LN. (Mail order only)

5-N-CHANNEL FETs 3819E—£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.

Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LIMITED

45 Station Road, Gerrards Cross, Bucks.
Mail Order only

"Globe-King"

V.H.F. & SHORT WAVE KITS

Precision standard, low cost valve and transistor kits 10-350 m. V.H.F. 80-180 MHz. "Easy-Build" diagrams and simplified instructions. For free literature send S.A.E. to sole manufacturers. (Overseas: Int. Reply Coupon).

JOHNSONS (RADIO) Est. 1943
Shaw St, Worcester, WR1 3QQ

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateur, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 + p.&p 10p U.K. only.

Illustrated catalogue of selected kits and components. 20p inc. VAT. P&P free.

ALL PRICES PLUS 10% VAT

Galleon Trading Co,
12, Burns Way,
Coringham,
Stanford-Le-Hope,
Essex. SS17 5DE

TEXAN AMPLIFIER



- | | | |
|---------------------------|-------|----------|
| Pack | | |
| 1. P.C. Board | £2.00 | p.p. 15p |
| 2. Chassis | 3.00 | " 25p |
| 3. Front Panel | 1.25 | " 15p |
| 4. Resistors | .80 | " 15p |
| 5. Capacitors | 2.90 | " 15p |
| 6. Semi Conductors | 8.00 | " 15p |
| 7. Transformer | 5.95 | " 25p |
| 8. Sundries | 2.50 | " 15p |
| 9. Cables | .40 | " 15p |
| 10. Instructions | .30 | " 15p |
| 11. 100K/100K control pot | .30 | " 15p |

VAT EXTRA

TELERADIO ELECTRONICS,
325 FORE ST., LONDON, N.9.
Tel. 01-807 3719

Send 4p for catalogue of Hi Fi Kits including the Quadrophonic System as in Practical Electronics.

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.
0.47µF: ±0% 80p; ±2% 40p; ±1% 50p
1.0µF: ±0% 40p; ±2% 60p; ±1% 60p
2.2µF: ±0% 60p; ±2% 80p; ±1% 75p
4.7µF: ±0% 70p; ±2% 90p; ±1% 81.15
6.8µF: ±0% 95p; ±2% 81.15; ±1% 81.80
10µF: ±0% 81.10; ±2% 81.40; ±1% 81.80
10µF: ±0% 81.80; ±2% 88.10; ±1% 88.70

TANTALUM BEAD CAPACITORS—
Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7,
6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF
15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 8p
each; 6 for 45p; 14 for 95p. Special pack 6 off
each value (78 capacitors) £4.50.

NEW—TRANSISTORS. BC107, BC108,
BC109. All at 9p each; 6 for 50p; 14 for £1. All
brand new and marked. Full spec. devices. May
be mixed to qualify for quantity prices. AF178—
38p each or 3 for 85p.

POPULAR DIODES. IN914, 6p each; 8 for
45p; 18 for 90p IN916, 8p each; 6 for 45p; 14
for 90p; IS44, 5p each; 11 for 50p; 24 for £1.
All brand new and marked.

NEW LOW PRICE—400 mW Zeners
Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11,
12, 13.5, 15V. Tol. ± 5% at 5 mA. All new and
marked. Price 7p each; 6 for 39p; 14 for 84p.
Special offer 6 off each voltage (66 zeners)
£3.65.

RESISTORS. Carbon film 5%, 1W at 40°C, 4W
at 70°C. Range from 2.2Ω to 2.2MΩ in E12
series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56,
68, 82 and their decades. High stability, low
noise. All at 1p each; 8p for 10 of any one
value; 70p for 100 of any one value. Special
pack—10 of each value 2.2Ω to 2.2MΩ (730
resistors) 45p.

400V A.C. CAPACITORS. 0.1µF, size 1 1/2in x
1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47
and 0.5µF, size 1 1/2in x 1/2in, 35p; 1.0µF, size 2in
x 1/2in, 45p; 2.0µF, size 2in x 1in, 75p each.

SILICON PLASTIC RECTIFIERS 1.5 Amp
Brand new wire-wound 0.027, 100PIV at 8p each
or 4 for 30p; 400PIV at 9p each or 4 for 34p;
800PIV at 14p each or 4 for 50p.
5p post and packing on all orders below £5.
Please add 10% VAT to all orders.

MARCO TRADING

Dept. W11, The Maltings, Station Road
Wam, Shropshire

TEXAN STEREO AMPLIFIER. Designed
by engineers of Texas Instruments
Ltd., this superb amplifier is now available
READY BUILT. Features include: 20 + 20
watts at less than 0.1 per cent distortion
scratch & rumble filters—and is fully guar-
anteed. Send cheque/P.O. for £38.50 inc.
Louis James Electronics, 63 Southwell
Road, Camberwell, S.E.5. Mail Order Only.

BRAND NEW COMPONENTS by
return. Electrolytics 16V, 25V, 50V—
0.47, 1, 2.2, 4.7, 10mfd.—4p, 22, 47—
4 1/2p. (50V—5p.) 100—5 1/2p. (50V—7p.)
220—6p. (50V—9p.). Subminiature
bead-type tantalums 0.1/35V, 0.22/35V,
0.47/35V, 1/35V, 2.2/35V, 4.7/35V,
10/16V—8p. Mylar Film 100V—0.001,
0.002, 0.005, 0.01, 0.02—2p. 0.04, 0.05—
3p. 0.068, 0.1—3 1/2p. Polystyrene 63V,
E12 series 10 pf.—1,000 pf.—2p. 1,200
pf.—10,000 pf.—3p. Miniature Highstab
resistors, 5%, E12 series—Carbon Film
1/2W 10—10MΩ (10% over 1 Meg.)
Metal Film 1/2W 10Ω—2.2MΩ and 1W,
2W—10MΩ all 3/4p each. Postage 8p.
The C.R. Supply Co., 127 Chesterfield
Rd., Sheffield S8.

TUNBRIDGE WELLS. Components
from Teleservice, S.A.E. or call in for
list. Special offers, limited quantity:
Matched AD161/2 68p, 10 transistors
similar 2N3702/3 unmarked 32p, 12
IN914/6 20p unmarked, air spaced twin
gang receiver tuning capacitors un-
used 50p, thin grey connecting flex 1p
yd. Minimum order 40p post free, but
add "10% VAT". 108 Camden Road,
Tunbridge Wells, Kent. Telephone
31803.

TRANSISTOR. 465 kc/s IF Strip 75p.
Amplifier 80p. Tone Control—Pre-Amp
75p. All with circuit. Record Player
Cabinets £3.50; Radio Cabinets 12in x
6in x 2 1/2. Suitable for Ext. speakers;
colours blue, brown or yellow. 60p.
AM/FM tuning gangs 50p. Archer, 9
Pine Grove, Maidstone, Kent.

GUARANTEED SEMICONDUCTORS FAST SERVICE . LOW PRICES

AC107	16p	2N706	10p	ZENER DIODES
AC126	15p	2N990	20p	400mW 5%
AC127	15p	2N1131	25p	3-3 to 33 volts
AC128	18p	2N1132	22p	10p each
BC107	9p	2N1711	20p	1 watt 5%
BC108	9p	2N2904	18p	6-8 to 200 volts
AF114	14p	2N2904A	28p	15p each
AF115	14p	2N2906	28p	
AF116	14p	2N3035	15p	
AF117	14p	2N3054	50p	
BCY70	20p	2N3055	38p	
BCY71	20p	2N3702	9p	RECTIFIERS
BCY72	18p	2N3703	9p	P.I.V. 1 AMP
BFX84	24p	2N3704	9p	60 IN4001 4 1/2p
BFX85	25p	2N3705	9p	100 IN4002 4 1/2p
BFX86	21p	2N3706	9p	200 IN4003 5p
BFX87	24p	2N3707	9p	400 IN4004 6p
BFX88	20p	2N3708	8p	600 IN4005 7p
BSX20	18p	2N3709	8p	1000 IN4006 8p
				800 IN4007 9p

CASH W.O. PLUS P.P. 10p TO
ROLESSE SERVICES
PARNDON HALL . HAMSTEL ROAD
HARLOW . ESSEX

'KINGDOM ELECTRONICS' offers
mono power amplifier, cca. 10 Watts,
with gain control, meter, and Test
Oscillator, 0-100kHz, £20 and £3 carr.
On view at Westwoods, 49 George
Street, Oxford. Mail orders to 4
Harberton Mead, Headington, Oxford.

BATTERY ELIMINATOR KITS. Our
well-known Mini Mains Pack Kits
now complete with drilled insulated
base 32 x 55mm. Fits into space of
most large transistor batteries. Easy
wiring instructions. Safe, silent mains
transformer, silicon rects, smoothing
capacitor, all top grade. For any ONE
of these voltages (state which): 3V,
300mA max.; 6V, 180mA; 9V, 120mA;
18V, 60mA. £1.50 VAT included. By
mail only, UK post 5p. Amatronix
Ltd., 396 Selsdon Rd., South Croydon,
Surrey CR2 0DE.

UNUSED RESISTOR and Capacitor Mixture
Carbon and Wirewound 1/2 to 2 watt. Paper—
Silver Mica—Metalised and Electrolytic. A
useful workshop selection of 175 values. Our
price 500 for £1.70

Potentiometers, 20 assorted £1.10.
Bargain parcels 141b for £2.60. No heavy
chassis. all useful components, Resistors,
Valves, Pots, Trimmers, Tag Strips, Rectifiers,
Nuts and Bolts, Capacitors. Unbelievable value.

Money back Assurance on all goods.
676 Foxhall Road, Ipswich, Suffolk.

Miscellaneous

AUDIO POWER AMPLIFIERS

10W — £4.00 } 1
25W — £8.00 } OFF
50W — £11.00 } PRICES

GENEROUS QUANTITY
DISCOUNTS AVAILABLE

DETAILS FROM:
PHOTAIN CONTROLS LTD.
Randalls Road, Leatherhead, Surrey

PRICES DO NOT INCLUDE VAT
Tel: 72776/75517 STD CODE 037-23

CONSTRUCTION AIDS—Screws, nuts,
spacers etc., in small quantities. Alu-
minium panels punched to spec. or
plain sheet supplied. Fascia panels
etched aluminium to individual re-
quirements. Printed circuit boards—
masters, negatives and boards, one-off
or small numbers. Send 6p for list.
Ramar Constructor Services, 29 Shel-
bourne Rd., Stratford on Avon,
Warwicks.

DON'T LOOK

unless you can resist the temptation to
get these super 'attention-getters'

★ Pocket-sized **MAXI-VOLT** Big
inch Spark Generator (instant
15,000 volts!). Ready-made, needs
no batteries. Carry it around any-
where. Only weighs about 3 oz.
(89g.) send £1.35 for your Maxi-
Volt now!

★ Unique **TRANSMITTER/RE-
CEIVER** Kit. No licence examina-
tions or tests required to operate
this transistorised equipment. Easy
to build. Get transmitting. Send
£5.90 for yours now!

★ Psychedelic **MINI-STROBE** Kit.
Take a pocket-sized lightning storm
to Disco's & parties. 'Brain-freeze'
'em with vari-speed stop-motion
flashes. Includes super case too.
Send £2.20 now!
(all prices include V.A.T., packing
& postage.)

Send remittance to
BOFFIN PROJECTS,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY
(Mail order only)

Or for more details, send 15p for lists.
plus free design project sheet.

Darned Electronic Wizardry

by Dewtron (VAT extra)

Famous kits, e.g. waa-waa complete
kit £2.95; Fuzz kit £5.50 auto
rhythm modules P & P 20p min.
Ring Modulator modules 28 and
whole range of synthesiser modules,
musical novelties, etc. Catalogue 15p
from D.E.W. Ltd., 254 Ringwood
Road, Ferndown, Dorset.

STABILISED 6, 7.5 & 9V. FROM SINGLE UNIT



AUTO ADAPTOR
In-Car Entertainment.
Battery operated cas-
sette recorders, radios
etc., powered by 12v
car battery by means
of ingenious electronic
adaptor—at virtually no cost. One lead in-
cluded. Only £3.95 inc. VAT + 12p (p.p.).
Also Mains Battery Eliminator £3.00. Lead
(optional) 60p. State type of plug. Partics.—
**OMNIA PRODUCTS, 25 Wilbury Gdns.,
Hove, Sussex.**

BUILD IT in a DEWBOX quality
cabinet. 2in x 2 1/2in x any length.
D.E.W. Ltd., Ringwood Road, FERN-
DOWN, Dorset. S.A.E. for leaflet. Write
now—Right now.

ALUMINIUM SHEET to individual
sizes or in standard packs, 3p stamp
for details. Ramar Constructor Ser-
vices, 29 Shelbourne Road, Stratford
on Avon, Warwicks.

GLASS FIBRE P.C. BOARD. Large
supplies available 1/2in single sided
one ounce copper 2p per sq. inches
(under 1 foot). 75p per sq. ft. (over
1 foot). 1/2in double sided one ounce
copper 1p per sq. inch (under 1 ft.),
£1 per sq. ft. (over 1 foot). Please add
10p per sq. foot postage and packing.
We can cut to your size at 1p per cut.
Solid State Lighting, The Firs, Small-
wood Lane, Garboldisham, Diss, Nor-
folk.

**FIBREGLASS PRINTED
CIRCUIT BOARD**

1/16-1/32 Single—5p per 12sq.ins,
50p per sq. foot. Double—8p per
12sq.ins, 70 per sq.foot.
Post—10p—1sq.ft. 25p—4sq.ft.
S.A.E. for larger. NO V.A.T.
NOW! DRAW-DRY-ETCH!
The quick easy way to make your
circuit, use the DALO 33
MARKER (Spare tip included).
NO MESS—NO MASKING. A
P E R F E C T C I R C U I T E V E R Y
T I M E . P E N 80p Post free.
From: BRB, 17, Southbreck Rise,
Worksop, Notts. S80 2UP.

PROFESSIONAL CASES

FOR THE PRICE OF A PLAIN ALUMINIUM
OR DIECAST BOX

Attractive Black Anodised Alloy case. Polished
Mahogany-veneer Wood Block ends. Complete
with front panel, ventilated rear panel, Chrome
screws and rubber feet. Assembled in seconds
with 8 screws. Size 6 1/2", 4", 5" depth. Price
£1.30 + VAT. P. & P. 9p. Trade enquiries
welcome. Other sizes available.
We can also supply a full range of BRANDED
semiconductors, components, hardware,
aluminium etc. at ridiculously low prices.
Free Cat. 3p stamp.

ADFONIC (PW), 18 Yew Lane, Ashley,
New Milton, Hants BH25 5BA.
C.W.O. Mail Order Only.

**A
L
S**

**A.L.S. PRESENTS OUR
E.C.100 WATT HI-FI AMPLIFIER**

Ready drilled P.C.B. with full instructions
only £2—plus 10p post. We also supply:
Service Sheets, Manuals, Books etc.
See our Main Advertisement in "TELE-
VISION" or send S.A.E. for details.

10 DRYDEN CHAMBERS, 119 OXFORD ST.,
LONDON W1R 1PA (B)

HARDWARE—Screws, nuts, washers
and other useful items in small quan-
tities. Sheet aluminium to individual
requirements, punched/drilled. Send
6p for list. Ramar Constructor Services,
29 Shelbourne Rd. Stratford-on-Avon,
Warwks.

EXPERIMENTERS! Hundreds of un-
usual items cheap. Catalogue 5 1/2p.
Grimsby Electronics, 64 Tennyson
Road, Cleethorpes, Lincs. (Mail Order
Only).

AMTRON KITS. Your Devon Stockist.
E. Wenmouth, 50 South Street, Exeter
EX6 5SH.

STOP THIEF. New Burglar Alarm Kit
only £18.50. Battery operated. Easy
installation. Choice of three security
patterns. Or build our transistorised
Alarm Circuit, complete Kit £2.75.
CASTLE ALARMS, Po Box W06,
Windsor, Berks.

A. H. SUPPLIES Technical Handbooks

R1155, B, F, L, N £2.42. R1392 £1.43. B40 A, B, C, D £3.85.
52 Set £1.10. R107 £1.21. R210 £5.40. R216 £4.62. R209 £1.21.
19 Set £2.42. 31 Set £1.65. 88 Set £1.21. W.M. D No 2 £1.65.
CT38 £2.42. TF144G £1.21. 13A £2.42. CD518 (CT316) £2.20.
AR88D or LF £2.42. 62 Set £2.42. CT52/84 £1.32. HRO VARIOUS
£1.43. CIRCUITS ONLY R1475 66p, R3673 66p, CRT26 66p,
R4187 £1.10. TF801A 88p, 1035 Mk 1, 2 or 3 66p, 1049 Mk 3 66p,
ARR-2 66p, APN-9 66p, OS-8 66p.
Manuals also available for American equipment.
Above prices inc. post and V.A.T. S.A.E. with enquiries.
Note above are Photostat copies.

A. H. Supplies, 57 Main Road, Sheffield, S9. 5HL

Phone 444278 (0742)

**UNIQUE
HI-FI SPEAKER
SYSTEM**

24 WATTS PEAK!

Beautiful bookshelf units in mahogany
type finish. Employs infinite baffle
enclosure with dual cone 8 ohm
drive unit. Brand new with 6' leads.

£9.80 Per Pair P&P 60p

GREGG Electronics
PW3, 24 Cranbourn Street
Leicester Sq. London WC2

AN INTERNATIONAL ELECTRONICS
marketing company operating on a
World-wide basis would be pleased to
receive information from potential
suppliers on all ranges of electronic
components. Agency or distributorship
will be considered. Please telephone
or write to Brian Ricketts, Managing
Director, Milton Keynes Electronics
Ltd., 138 Glebe Road, Deanshanger,
Milton Keynes, Bucks. MK19 6NB.
Tel: Stony Stratford 2664.

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-
UHF 825, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30—
ECC82, ECL80, E881, EBF89, EF80, EF85, EF183,
EF184, EY88, PCC24, PCC89, PCC189, PC97,
PCF80, PCF88, PCF808, PCF808, PCL122, PCL123,
PCL84, PCL85, PFL200, PL36, PL11, PL504, PY33,
PY82, PY800, PY801, 30L15.

19" UHF/VHF (BBC2) £6.00

Thorn-850 or Pye, with set of spare valves.
Carriage £2.00 (Untested).

100 MIXED RESISTORS—65p

‡ to 2 watt—10 ohms to above 1m-ohms (our
choice) 100 mixed Capacitors up to 500MFD—
£1.10 (our choice).

BARGAINS PARTS

Transistor UHF Tuners—£2.00, 500K-ohms V/C
with Switch—20p. 50 mixed Tuner Valves—£2.25.
Brand New Transistors BF173, BC171, BC153,
BC135, BC113, BC117, BC115, BA102, BA120.
All 10p each.

All prices include V.A.T. p. & p. 10p per order
Money back guarantee. S.A.E. for leaflets.

**ELECTRONIC MAILORDER
(BURY) LTD.**

62 Bridge St., Ramsbottom, Bury,
Lancs. Tel. Rams 3036

OMNI-DETECTORS

(Featured ★ TV ★ Radio ★ Nat. Press)

Ancient art of Dowsing in Modern Guise. Thrill to
new discovery in this overlooked aspect of the
Electro-Magnetic Spectrum. A LABORATORY IN
A SINGLE PACK. Treasure Hunters! Use Omni-
detectors to:

- ★ Locate ANY buried substance. ANY depth.
- ★ Save hours of fruitless searching — MAP -
DOWSING pinpoint search area before you
leave home.
- ★ Limitless other uses.

Dowsing used in World War 2 and by U.S.A. troops
in Vietnam to locate underground springs, tunnels,
mines.

Send only £2.80 + 15p p. & p. for unique pack of
4 dowsing instruments (non-electronic) and explicit
40-page manual to sole suppliers: Omni-Detector Co.
(Dept. PW), 27 Latham Road, Twickenham, Midd.
TW1 1BN.

★ ★ ★ ★ ★
**ANNUAL WAREHOUSE
CLEARANCE SALE**
★ ★ ★ ★ ★

SATURDAY, OCTOBER 8—NOVEMBER 3
TUESDAY — SATURDAY, 10 a.m. — 5 p.m.

★ THOUSANDS OF BARGAINS ★

- ★ Test Equipment ★
- ★ Oscilloscopes ★
- ★ Signal Generators ★
- ★ Counters ★
- ★ Cabinets ★
- ★ Bridges ★
- ★ Meters ★
- ★ Transmitters ★
- ★ Receivers ★
- ★ Power Supplies ★
- ★ Laboratory Equipment ★
- ★ Galvanometers ★
- ★ Audio Equipment ★
- ★ Video Equipment ★
- ★ Meters ★
- ★ Battery Chargers ★
- ★ Motors ★ ETC., ETC.

★ ★ ★ ★ ★
**20 TONS OF
ELECTRONIC COMPONENTS**
★ ★ ★ ★ ★

- ★ Resistors ★ Relays
- ★ Capacitors ★ Switches
- ★ Transformers ★ Meters
- ★ Potentiometers ★ Component Parts
- ★ Semiconductors ★ Valves
- ★ Cable ★ ETC., ETC., ETC.

**REGRET NO LISTS AVAILABLE.
PERSONAL CALLERS ONLY.
CASH AND CARRY ONLY.**

**ELECTRONIC COMPONENTS
BARGAIN COMPONENT PACKS**

- Pack No.
- 1 500 Carbon resistors, 1, 1/2, 2 watt.
 - 2 100 Electrolytic Condensers.
 - 3 250 Ceramic, Polystyrene, Silver Mica etc.
condensers.
 - 4 250 Polyester, Polycarbonate, Paper, etc.
condensers.
 - 5 25 Potentiometers, assorted.
 - 6 250 High-stab, 1%, 2%, 5% resistors.
 - 7 50 Assorted Tagstrips.
 - 8 1lb wt. Assorted Nuts, bolts, washers, spacers,
etc.
 - 9 25 Assorted switches, rotary, lever, micro, toggle,
etc.
 - 10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED.
£1 + 25p p.p. per pack, £5 for 5 packs p/free

C. T. ELECTRONICS

Mail Order, Retail Shop, Components—
267 Acton Lane, LONDON, W4 SDG 01-864-8275
Warehouse, Test Equipment, Surplus Goods—
28-24 Beaumont Road, LONDON, W4
Audio Accessory Shop, Components—
17 Turnham Green Terrace, LONDON, W4



MAINS MOTOR
Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 75p. Postage 20p for first one then 10p for each one ordered.

MUSIC ON TAPE

A further buy enables us to offer these to an even lower price—namely 65p each or 5 for £3-00. Send for list of titles. We can't repeat when sold out.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits. 27p each, 10 for £3-76.



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 55p each or 10 for £3-48.



12 VOLT 1/2 AMP. POWER PACK

This comprises double-wound transformer with full wave rectifier and 2000 mF smoothing. Price £2-30 plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 10-40V in steps—maximum load 250W—that is from 5 amp at 40V to 15 amp at 10V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6-38 plus 65p post.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price each. Pizolin lid 11p extra.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 25p each.

CONNECTING WIRE

7-0076 Copper conductors. 500 metre drums available in the following colours—Red/Black—Yellow—Green/Grey—Blue/Green—Red/Orange—Green/White—Grey/White—Blue/Orange—Brown/Red—Brown/White—Red/Grey—Blue/Grey—Blue/Brown. Price £2-20 per drum plus 10p post. State alternative colours.

Screened Gage 70076 core suitable for pick up or mike lead or for inter-connecting amplifiers. 10 metres. 85p.

DOOR SWITCH

As fitted to refrigerators, etc. Switches off as door closes. White 17p each. Black 15p each.

U.V. LIGHTING

Useful for light detectors in metals and for looking for water marks, etc., also for fitting over tropical fish tanks. African violets and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 12" U.V. tube—choke—starter holder and tube ends. Price £2-20 plus 20p post.

80 WATT TUBULAR ELEMENTS

Brass encased with beaded flex ends. Standard replacements in most absorption refrigerators but also has dozens of other uses. 85p each

SPIT MOTOR

200-250V Induction Motor, driving a Carter gear box with 1 1/2" of output drive shaft running at 5 revs per minute. Intended for roasting chickens also suitable for driving models—windmills, coloured disc lighting effect, etc., etc. £2-04 plus 20p post and insurance.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24" x 18" £1-69
18" x 10" £1-21

ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1 1/2" x 3/4" 9p each. 10 for 81p.

KETTLE ELEMENTS

Made by the famous A.E.I. Co. Complete with washers and combined firing ring and plug shroud. Norms 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1 1/2" (approx.) suitable for Swan and other similar models—1 1/4" (approx.) suitable for G.E.C., Hotpoint, etc. All quick boil 2 1/2kw elements at 240V. Price £2-81 each.

WINDSCREEN WIPER CONTROL

Very speed of your wiper to suit conditions. All parts and instructions to make. £3-68.



MULLARD AUDIO AMPLIFIERS
All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 800mW power output 75p. Model 1172 750mW power output 84p. Model EP9000 4 watt power output £1-60. Unless DIY STEREO. Complete £11-80.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cased induction motor with specially built low noise bearings. Overall size 4 1/4" x 4 1/4" x 4". When mounted by flange, air is blown into the equipment but to snak air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing fume smoke when soldering etc., etc. A real bargain at £3-05.



MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January 75. All electronic parts £2-20 post paid.

TAPE PLAYBACK UNITS

Mains operated. Made by Reditone the famous "music in background people". These are complete units for playing tape at standard speed (3 1/2"). These have a superior motor driven fly wheel to control the tape through the capstan and also an even equally useful valve amplifier with EL84 output. In a steel case with carrying handle. Tested and good working order £8-50, or some in need of repair but complete £8-50, cassettes of tape pre-recorded £11-10 (please state type of music required), 75p carriage up to 200 miles then 60p per 100 miles extra.



6 MAINS TRANSFORMERS

Our Ref: **MTM1** 27 volt at 8 amp Upright mounting fully shrouded—57yng leads—fully tapped primary. Price £3-20.
Our Ref: **MTM2** 12v at 1 amp. Upright mounting with fixing lugs, tag connection. 240v primary—12v 1 amp secondary. Price 85p.
Our Ref: **MTM3** 6-3v 2 amp upright mounting with fixing lugs, tag connections, 240v primary 6-3v 2 amp secondary. Price 77p.
Our Ref: **MTM4** 18v 4 amp with thermal cut-out, upright mounting with fixing lugs, tag connections. Primary 240v, secondary 18v at 4 amp. Price 85p.
MAINS ISOLATION 350 watts earth shielded—flex leads—upright mounting lugs for fixing terminals for output. Price £6-50 each.
MAINS TRANSFORMER BARGAIN. Standard mains 240v input. Secondary 2-4v 9 amp intermittent. 5 amp continuous. Price 55p.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp. sockets in metal box to take standard 13 amp. fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2-50 plus 20p post and ins.

24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 2A during these periods. £2-75 post and ins. 20p. Additional time contacts 55p pair.

THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2-95 plus 20p post and insurance. Industrial model 5A £3-30. (Not on plate).

THIS MONTH'S SNIP

WALL THERMOSTATS. Made by the famous Smiths Instrument Co. called Colourstat. Wall mounting and in a handsome plastic case. (Cream and beige). Adjustable by slider (lockable) and may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost) (very warm), etc. The thermostat will control heaters, etc. up to 15 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse, etc. Price £1-65. Don't miss this.

TWENTYLITE
Fluorescent lighting units with polyester choke and finished white enamel. 40in. model. Ideal kitchen, bedroom, hall, way porch, lift, etc., with tube. Assembled ready to install. Price £2-20 + 40p p. & p.

10 AMP DIMMER/CONTROLLER

For the control of lighting of stage or studio or portable equipment in workshops etc. This has socket outlets each controlled by 5 AMP Solid State regulator. Also fitted with master switch fuse and neon indicator and terminating with 6 feet of flex. Overall length 17in. 3 1/2in x 1 1/2in. deep. £7-50, plus 25p P. & P.

TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW, and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £3-85. 2kW. Model as above except 2kW. £2-75. Don't miss this. Control Switch 44p, P. & P. 40p.



TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6-00 otherwise add 80p.

NEW ITEMS THIS MONTH

VOLTAGE CHANGING TRANSFORMERS made by Ferriso. Upright mounting, fully shrouded and with terminal blocks for input and output. For changing mains voltage, ideal for working low voltage equipment from 230/240 mains and for increasing voltage due to losses in long leads. Voltage up or down between 190-250v, 250 watts. Price £1-85 plus 30p post, etc.

DOOR OPERATED PLATFORM ROTATING MOTORS. Very powerful motors estimated rating at 1/2 H.P. Reversible with gearbox and "V" belt drive wheel of 7" diameter. Price of motor which weighs approx. 15lbs. is £10. Note: These are ex-equipment but guaranteed for six months.

Gas and Smoke detector/Sensor-ref GD1- recently referred to as the electronic nose—£2 each; circuit of smoke detector alarm included. Practical details appeared in September's Practical Wireless, so we can supply the 5L 08D at £1-76, the 2N414 at £1-85 also most other items, send for FW 10 radio parts list.

SPRING RETURN WAFER SWITCH. As used in intercom and other similar equipment a two water 6 pole 3 way switch, spring return from centre position when turned clockwise and permanent off or on when turned anti-clockwise. Price 55p each.

A.C. BUZZERS. 12v. Fix these into a box which will resonate and they will give a loud piercing note. Suitable for alarms or signal. 25p each.

PUSH ON TAG CONNECTORS. These are being increasingly used on cars and domestic appliances. 2 sizes prevail, the most popular being for 3" tag. We offer these at attractive prices. 10 for 10p. 50 for 40p. 100 for 70p and 1,000 for 85p.

4 MINUTE TIMED SWITCH by Smiths. Our ref. TS AU1. This is for processing photographic prints, etc. Has a scale graduated 0-4 min. Turn the pointer knob, and set it at the desired time—switch will stay closed until pointer knob returns to Zero. Clockwork motor, so can be independent of mains if desired, but the switch itself is double pole, rates 250v. 15 amps. Price £1-65p.

ONE HOUR TIMED ON SWITCH by Smiths. Our ref. TS AU2. As TS AU1 except that the complete rotation of the pointer knob lasts for one hour. Price £1-10p each.

CONTROLER, 3 EXHIB. Bell rubber band or friction drive as fitted to Tape Recorders and similar. Counts or takes away up to 999. Re-settable from any count by processing knob. 55p each.

DRILL CONTROLLER
NEW IKW MODEL
Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-95.

Made up model also available. £2-25.
MAINS TRANSISTOR P. P.
Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP8, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, smoothing and load resistor condensers and instructions. Real snip only £1-10.



STEREO PRE-AMP MODULE
Mullard ref LP 7182/2—transistors and all ancillary components mounted on PC board £1-28 with connection dig.

15A ELECTRICAL PROGRAMMER
Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do with famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2-15 + 20p p. & p. or with glass front, chrome bezel, 85p extra.

THERMAL CUTOUT
A miniature device 1/2" dia. on one screw fixing mount—can be used for motor overload protection—fire alarm—soldering iron—switch off, etc., etc. 15 amp contacts open with flame—radiant or conducted heat. 1 1/2" each or 10 for 99p.

HONEYWELL PUSH BUTTON MICRO SWITCHES
As used in some vending machines, etc. Each switch is a change-over type rated at 15 amps 250v A.C. Intended for panel mounting with fixing nuts and single black push knob. Single change-over switch 28p. Double switch 45p. Triple switch 61p.

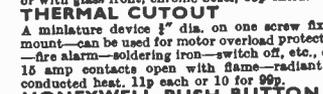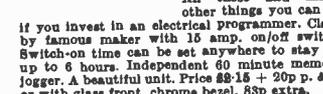MACLAREN THERMOSTAT
Make and break 20 amp A.C. with the sensor probe coupled by 2 feet capillary covering range of 10-100°C—complete with large engraved control knob. Price 85p.



J. BULL (ELECTRICAL) LTD.
(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 162/3 Tamworth Road, CROYDON

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 12½p in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted
Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

0A2	0.40	6A87G	0.85	6F11	0.50	10D1	0.85
0A3	0.48	6AT6	0.45	6F13	0.50	10D2	0.55
0B2	0.40	6AU6	0.30	6F14	0.70	10F1	0.75
0B3	0.70	6AV6	0.45	6F15	0.65	10F2	0.65
0C3	0.40	6AW6	0.65	6F18	0.50	10F18	0.60
0D2	0.40	6BA6	0.35	6F23	0.90	10L1	0.60
1B3GT	0.48	6BE6	0.25	6F24	0.80	10LD110	0.70
1L4	0.88	6BF6	0.65	6F25	1.00	10P13	0.75
1R4	0.50	6BH6	0.75	6F26	0.35	12AB5	0.70
1R5	0.45	6BJ6	0.55	6F28	0.70	12A6	0.65
1S4	0.80	6BK7A	0.75	6F36	0.80	12A6E	0.65
1T4	0.30	6BN6	0.45	6J4	0.60	12AL5	0.55
1U4	0.60	6BQ6	0.25	6J5GT	0.45	12AQ5	0.50
1U5	0.75	6BR7	1.00	6J7	0.45	12AT6	0.40
1V2	0.60	6BR8	0.30	6K47J	0.60	12A0T	0.45
1X2B	0.60	6BT7	1.35	6K6GT	0.75	12A0T	0.25
2D91	0.45	6BW6	0.90	6K7	0.45	12A0V	0.50
2E4	0.50	6BW7	0.90	6K8G	0.45	12AV7	0.70
3V4	0.40	6BX6	0.25	6K25	0.75	12AX7	0.75
3V4	0.70	6BZ6	0.45	6L6GT	0.55	12AY7	0.35
3V4GY	0.80	6BZ7	0.70	6L7	0.45	12BA4	0.70
3U4G	0.40	6C4	0.35	6L18	0.50	12BA5	0.45
3V4G	0.50	6CGT	0.55	6L20	0.50	12B5	0.70
3Y8GT	0.45	6CH6A	0.75	6M7GT	0.55	12BH7	0.50
3Z9	0.75	6C6GA	0.60	6Q7	0.50	12BY7	0.65
5Z4G	0.45	6C7	1.40	6R47	0.45	12E1	3.00
6/30L2	0.90	6CG7	0.65	6R67	0.45	12E5	1.00
6A3	0.45	6CL6	0.65	6R7	0.50	12E7	0.50
6AB5	1.00	6CU6	0.80	6R8G	0.45	12G7GT	0.50
6AF4A	0.65	6D4	1.00	6R9GT	0.45	12H7GT	0.45
6A5	0.25	6CY6	0.50	6R9GT	0.45	12H7GT	0.45
6AG7	0.45	6C7	0.75	6R7	0.50	20D1	1.00
6AH6	0.60	6D3	0.55	6S5	0.65	20P1	0.50
6AJ8	0.30	6D6	0.65	6U4GT	0.75	20P4	1.10
6AK6	0.40	6DK6	0.80	6U8A	0.45	20P7GT	0.50
6AK6	0.90	6DQ6B	0.80	6V8GT	0.50	25C5	0.70
6AL3	0.45	6D4	0.35	6X4	0.40	25L6GT	0.40
6AL5	0.25	6E4B	0.70	6X5GT	0.45	25Z4G	0.40
6AM6	0.57	6E7H	0.30	6X8	0.70	25Z6GT	0.75
6AQ5	0.45	6EJ7	0.35	6Y6G	0.30	30A5	0.60
6AQ6	0.70	6EW6	0.70	7Y4	0.75	30AE3	0.40
6AR5	0.80	6F1	0.75	9W6V	0.75	30C1	1.30
6AR6	0.65	6F5	0.75	10C2	0.60	30C15	0.30
6AB5	0.55	6F6G	0.50				

First Quality Fully Guaranteed Zapex BRAND ELECTRONIC VALVES

30C17	1.00	90A4	2.40	DM160	0.70	KCC88	0.40
30C18	0.90	90A5	3.00	DY51	0.55	ECC99	0.50
30P5	1.00	90C1	0.5	DY86	0.35	ECC91	0.30
30FL1	0.90	90CV	0.60	DY87	0.35	ECC189	0.65
30FL12	1.10	807	0.50	DY802	0.37	ECC807	1.00
30FL18	0.50	811A	1.60	E80F	1.40	ECCF80	0.35
30FL14	0.90	811A	1.50	E88CC	0.75	ECCF82	0.35
30L1	0.40	866A	1.00	E180F	1.00	ECCF84	0.65
30L15	0.95	5442	0.80	E181F	0.90	ECC81	0.30
30L17	0.95	6080	2.25	E180F	1.00	ECC83	0.45
30P12	1.00	6146	2.00	EAP42	0.60	ECC84	0.45
30P19	0.95	6146B	3.00	EBC33	0.80	ECC84	0.45
30P1L1	0.95	6360	1.25	EBC41	0.45	ECC80	0.75
30P1L3	1.10	4939	3.00	EBC81	0.35	ECC80	0.75
30P1L4	1.10	7199	1.00	EBCF80	0.40	ECC82	0.25
35A3	0.65	7586	2.50	EBCF83	0.40	ECC83	0.70
35A5	0.75	7895	1.50	EBCF89	0.32	ECC84	0.55
35B5	0.65	A2293	2.50	EBC131	1.50	ECC86	0.40
35C5	0.80	AZ1	0.80	ECC5	0.50	ECC86	0.40
35D5	0.75	AZ31	0.55	ECC9	0.35	ECC1800	0.20
35L8GT	0.75	CB1	0.90	ECC9	0.35	ECC9	0.35
35W4	0.50	CBL31	1.20	ECC88	0.50	ECC9	0.35
35Z3	0.75	CY1	0.50	ECC92	0.35	ECC92	0.35
35Z4G	0.40	CY31	0.50	ECC95	0.45	ECC95	0.45
50A5	1.00	DAP96	0.50	ECC95	0.45	ECC95	0.45
50B5	0.85	DP96	0.50	ECC40	0.70	ECC40	0.70
50C5	0.80	DK92	0.70	ECC81	0.40	ECC81	0.40
50CDD6G1.20		DK96	0.65	ECC82	0.35	ECC82	0.35
50L6GT	0.60	DL96	0.55	ECC83	0.35	ECC83	0.35
50A2	0.60	DM70	0.60	ECC84	0.30	ECC84	0.30

EP92	0.50	HK90	0.50	PL33	0.40	U404	0.70
EP95	0.40	KT66	2.50	PL36	0.55	U801	0.80
EP97	0.65	KT77	1.00	PL81	0.50	UABC80	
EP98	0.75	KT88	2.80	PL82	0.45	UAF41	0.40
EP183	0.30	N78	1.80	PL83	0.45	UAF42	0.80
EP184	0.35	PABC800.40		PL84	0.40	UAF43	0.80
EP804	1.25	PC86	0.80	PL85	0.65	UB41	0.75
EL85	0.45	PC88	0.60	PL86	0.45	UB41	0.75
EL8A	0.50	PC97	0.50	PL508	0.90	UBC81	0.45
EL36	0.50	PC900	0.48	PL509	1.10	UBF80	0.40
EL41	0.75	PC84	0.40	PL801	1.00	UBF89	0.40
EL81	0.55	PC85	0.40	PL802	0.95	UBL1	0.70
EL83	0.50	PC88	0.55	PM84	0.65	UBI21	0.70
EL84	0.25	PC89	0.50	PY81	0.40	UC92	0.45
EL85	0.45	PC189	0.60	PY82	0.45	UC95	0.45
EL86	0.40	PC805	0.95	PY80	0.40	UCF80	0.70
EL90	0.45	PC806	0.95	PY81	0.30	UCF81	0.60
EL860	1.25	PCF80	0.30	PY82	0.35	UCH42	0.75
EL822	1.60	PCF82	0.35	PY83	0.35	UCH81	0.40
EL880	0.85	PCF84	0.60	PY88	0.40	UCL81	0.60
EM71	0.50	PCF85	0.60	PY89	0.40	UCL82	0.35
EM83	0.50	PCF87	1.00	PY800	0.47	UCL83	0.65
EM84	0.35	PCF801	0.50	PY801	0.50	UF9	0.65
EM85	1.00	PCF802	0.50	PZ30	0.35	UF11	0.80
EM87	0.70	PCF805	0.90	QQV02-6		UF41	0.85
EN91	0.40	PCF806	0.90	QQV03-10	3.00	UF42	0.85
EV61	0.45	PCF808	0.75	QQV03-1.25	1.25	UF80	0.25
EV68	0.40	PCF809	0.90	TT21	0.80	UF85	0.40
EV83	0.55	PCF2000	0.70	TT22	0.40	UF89	0.40
EV84	0.40	PCL81	0.50	U18/20	0.75	UL41	0.65
EV85	0.45	PCL82	0.35	U25	0.55	UL84	0.45
EV86	0.45	PCL83	0.65	U26	0.85	UM84	0.30
EZ40	0.50	PCF83	0.65	U31	0.70	UY1N	0.50
EZ41	0.75	PCL84	0.45	U52	0.40	UY41	0.45
EZ80	0.25	PCL86	0.45	U76	0.40	UY82	0.50
EZ81	0.25	PCL88	1.10	U78	0.40	UY85	0.40
EZ82	0.35	PCL89	0.70	U191	0.75	W729	0.75
EZ83	0.45	PCL90	0.95	U201	0.55	XC12	0.60
EZ84	0.40	PCL900	0.80	U281	0.55	Z769	4.00
EZ85	0.30	PD500	1.30	U282	0.55	Z8048	4.50
EZ86	0.65	PF86	1.70	U301	0.55	Z8059	6.00
EZ87	0.65	PF88	1.00	U403	0.70	Z8059	1.88

TRANSISTORS

2N696	0.15	2B746	0.25	BD121	0.65
2N697	0.15	AC113	0.15	BD123	0.90
2N698	0.30	AC125	0.30	BD124	0.60
2N705	0.70	AC126	0.30	BD131	0.40
2N706	0.10	AC127	0.17	BF115	0.80
2N708	0.15	AC128	0.15	BF117	0.25
2N753	0.55	AC182	0.25	BF179	0.80
2N929	0.20	AC183	0.30	BF180	0.35
2N930	0.20	AC184	0.15	BF181	0.35
2N987	0.45	AC187	0.17	BF185	0.20
2N1181	0.25	AC176	0.25	BF194	0.10
2N1182	0.25	AC187	0.20	BF195	0.10
2N1184	1.25	AC188	0.20	BF197	0.12
2N1302	0.17	ACY17	0.25	BF200	0.32
2N1303	0.15	ACY18	0.25	BFW87	0.25
2N1304	0.20	ACY19	0.20	BFW88	0.20
2N1305	0.20	ACY20	0.20	BFW89	0.20
2N1306	0.20	ACY21	0.20	BFW91	0.20
2N1307	0.25	ACY22	0.14	BFX88	0.20
2N1309	0.25	AD139	0.40	BFY17	0.40
2N1309	0.30	AD149	0.40	BFY19	0.25
2N1813	0.17	AD161	0.25	BFY50	0.20
2N1711	0.25	AD162	0.25	BFY51	0.20
2N1710	0.75	ADZ11	1.25	BFY52	0.20
2N1847	0.75	ADZ12	1.25	BSY26	0.17
2N1960	1.00	AF114	0.17	BSY27	0.20
2N217	0.25	AF116	0.17	BSY28	0.17
2N218	0.20	AF116	0.17	BSY65	0.20
2N255A	0.15	AF117	0.17	BSY95A	0.12
2N277	0.65	AF118	0.25	BU105	1.60
2N2646	0.40	AF180	0.50	OC14	1.00
2N2905	0.32	AF181	0.50	OC22	0.50
2N2923	0.18	AF196	0.40	OC23	0.60
2N2924	0.13	AF212	1.00	OC24	0.60
2N2926	0.10	AS236	0.25	OC25	0.25
2N3063	0.20	AS272	0.30	OC26	0.20
2N3054	0.50	AS278	0.35	OC29	0.60
2N3055	0.60	ASY29	0.30	OC35	0.50
2N3123	0.25	ASY54	0.25	OC36	0.65
2N3134	0.25	AZ215	0.90	OC42	0.30
2N3391	0.17	AZ216	0.80	OC44	0.15
2N3392	0.17	AZ217	0.80	OC45	0.12
2N3393	0.15	AZ218	0.80	OC70	0.10
2N3394	0.15	BC107	0.10	OC71	0.12
2N3395	0.20	BC108	0.10	OC72	0.12
2N3402	0.15	BC109	0.10	OC73	0.30
2N3403	0.15	BC113	0.15	OC75	0.15
2N3404	0.33	BC118	0.20	OC76	0.15
2N3414	0.20	BC134	0.20	OC77	0.20
2N3415	0.15	BC134	0.20	OC78D	0.20
2N3417	0.25	BC147	0.10	OC81	0.20
2N3646	0.30	BC149	0.11	OC81D</	

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course!"—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects!"—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold!"—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters—and there are many more on file at Aldermaston Court—speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*. Write to **B.I.E.T. Dept. BPW10, Aldermaston Court, Reading RG7 4PF.**

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2-63.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build

3 transistor radio kit.

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

MECHANICAL	<input type="checkbox"/>	Man. Prod.—cont.	<input type="checkbox"/>	Constructional-cont.	<input type="checkbox"/>
A.M.S.E. (Mech.)	<input type="checkbox"/>	Quality Control	<input type="checkbox"/>	Building	<input type="checkbox"/>
Boiler Inspect.	<input type="checkbox"/>	Salesmanship	<input type="checkbox"/>	Building Drawing	<input type="checkbox"/>
& Operation	<input type="checkbox"/>	Storekeeping	<input type="checkbox"/>	Build Foreman	<input type="checkbox"/>
C & G Eng. Crafts	<input type="checkbox"/>	Work Study	<input type="checkbox"/>	Carpentry & Join.	<input type="checkbox"/>
C & G Fabricat.	<input type="checkbox"/>	Works	<input type="checkbox"/>	Civil & Municipal	<input type="checkbox"/>
Diesel Eng.	<input type="checkbox"/>	Management	<input type="checkbox"/>	Engineering	<input type="checkbox"/>
Eng. Inspection	<input type="checkbox"/>	DRAUGHTSMANSHIP	<input type="checkbox"/>	Constructional	<input type="checkbox"/>
Eng. Metallurgy	<input type="checkbox"/>	A.M.I.E.D.	<input type="checkbox"/>	Engineering	<input type="checkbox"/>
Inst. Eng. & Tech.	<input type="checkbox"/>	Design of Elec.	<input type="checkbox"/>	Construction	<input type="checkbox"/>
Inst. Motor Ind.	<input type="checkbox"/>	Machines	<input type="checkbox"/>	Surveyors	<input type="checkbox"/>
Mainten. Eng.	<input type="checkbox"/>	Die & Press Tool	<input type="checkbox"/>	Institute	<input type="checkbox"/>
Mechanical Eng.	<input type="checkbox"/>	Design	<input type="checkbox"/>	Clerk of Works	<input type="checkbox"/>
Sheet Metal Work	<input type="checkbox"/>	Electrical	<input type="checkbox"/>	Council Eng.	<input type="checkbox"/>
Welding	<input type="checkbox"/>	Draughtsman-	<input type="checkbox"/>	Geology	<input type="checkbox"/>
		ship	<input type="checkbox"/>	Hydraulics	<input type="checkbox"/>
ELECTRICAL & ELECTRONIC	<input type="checkbox"/>	Gen. Draughts-	<input type="checkbox"/>	Inst. of Builders	<input type="checkbox"/>
A.M.S.E. (Elec.)	<input type="checkbox"/>	manship	<input type="checkbox"/>	Inst. Works &	<input type="checkbox"/>
C & G Elec. Eng.	<input type="checkbox"/>	Jig & Tool Des.	<input type="checkbox"/>	Highway Sup.	<input type="checkbox"/>
C & G Elec. Inst.	<input type="checkbox"/>	Tech. Drawing	<input type="checkbox"/>	Painting & Dec.	<input type="checkbox"/>
C & G Elec. Tech.	<input type="checkbox"/>	RADIO & TELE-	<input type="checkbox"/>	Public Hygiene	<input type="checkbox"/>
Computer Elect.	<input type="checkbox"/>	COMMUNICATIONS	<input type="checkbox"/>	Road Engineer.	<input type="checkbox"/>
Elec. Maths	<input type="checkbox"/>	Colour TV	<input type="checkbox"/>	Structural Eng.	<input type="checkbox"/>
Elec. Science	<input type="checkbox"/>	C & G Radio/TV/	<input type="checkbox"/>	Surveying	<input type="checkbox"/>
Electronic Eng.	<input type="checkbox"/>	Electronics	<input type="checkbox"/>	GENERAL	<input type="checkbox"/>
Electrical Eng.	<input type="checkbox"/>	C & G Telecomm.	<input type="checkbox"/>	Agricultural Eng.	<input type="checkbox"/>
Install. & Wiring	<input type="checkbox"/>	Tech.	<input type="checkbox"/>	Council of Eng.	<input type="checkbox"/>
Meters	<input type="checkbox"/>	Prac. Rad. Elec.	<input type="checkbox"/>	Inst.	<input type="checkbox"/>
& Measuring	<input type="checkbox"/>	(with Kit)	<input type="checkbox"/>	Farm Science	<input type="checkbox"/>
Instruments	<input type="checkbox"/>	Radio Amateurs	<input type="checkbox"/>	General Educat.	<input type="checkbox"/>
MANAGEMENT & PRODUCTION	<input type="checkbox"/>	Exam.	<input type="checkbox"/>	Gen. Plastics	<input type="checkbox"/>
Auto. Control	<input type="checkbox"/>	Radio Servicing	<input type="checkbox"/>	Pract. Maths	<input type="checkbox"/>
Computer Prog.	<input type="checkbox"/>	& Repairs	<input type="checkbox"/>	Pract. Slide Rule	<input type="checkbox"/>
Electronic Data	<input type="checkbox"/>	Radio & TV Eng.	<input type="checkbox"/>	Pure & Applied	<input type="checkbox"/>
Processing	<input type="checkbox"/>	Trans. Course	<input type="checkbox"/>	Maths	<input type="checkbox"/>
Estimating	<input type="checkbox"/>	TV Main. & Serv.	<input type="checkbox"/>	Refrigeration	<input type="checkbox"/>
Foremanship	<input type="checkbox"/>	AUTO & AERO	<input type="checkbox"/>	Rubber Tech.	<input type="checkbox"/>
Inst. Cost & Man	<input type="checkbox"/>	Aero Eng.	<input type="checkbox"/>	Sales Engineers	<input type="checkbox"/>
Accountants	<input type="checkbox"/>	A.M.I.M.I.	<input type="checkbox"/>	Tech. Report	<input type="checkbox"/>
Inst. Marketing	<input type="checkbox"/>	A.E.C. Cert.	<input type="checkbox"/>	Writing	<input type="checkbox"/>
Management	<input type="checkbox"/>	Auto Engineer.	<input type="checkbox"/>	Timber Trade	<input type="checkbox"/>
Metrication	<input type="checkbox"/>	Auto Repair	<input type="checkbox"/>	University Ent.	<input type="checkbox"/>
Motor Trade Man.	<input type="checkbox"/>	C & G Auto. Eng.	<input type="checkbox"/>		
Network Plan.	<input type="checkbox"/>	Garage	<input type="checkbox"/>		
Numerical Cont.	<input type="checkbox"/>	Management	<input type="checkbox"/>		
Operational	<input type="checkbox"/>	MAA/IMI Dipl.	<input type="checkbox"/>		
Research	<input type="checkbox"/>	Motor Vehicle	<input type="checkbox"/>		
Personnel Man.	<input type="checkbox"/>	Mechanics	<input type="checkbox"/>		
Planning Eng.	<input type="checkbox"/>	CONSTRUCTIONAL	<input type="checkbox"/>		
Production Eng.	<input type="checkbox"/>	A.M.S.E. (Civil)	<input type="checkbox"/>		
		Architecture	<input type="checkbox"/>		
		Coaching for many major exams, including C & G and assistance in ONCIHNC.			

G.C.E.
58 'O' & 'A' LEVELS SUBJECTS
Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW10 QN BPW10
Aldermaston Court, Reading RG7 4PF

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____




Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

PORT WAVE TWO

PRICE
5/-

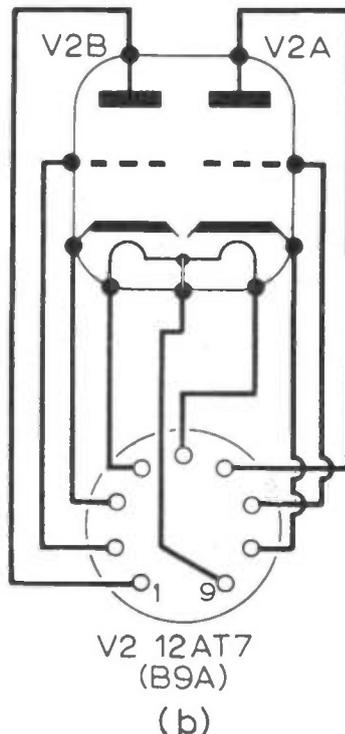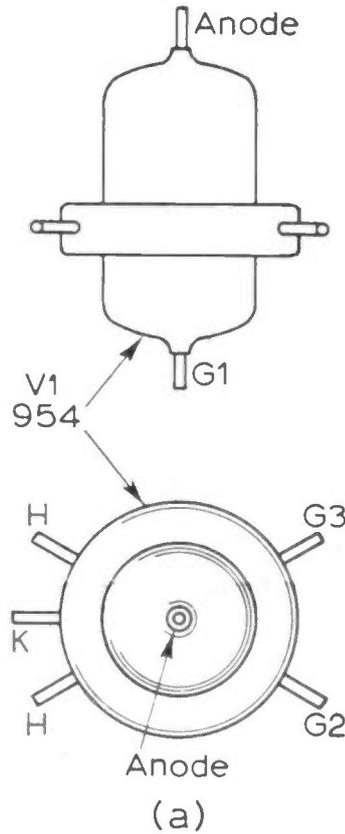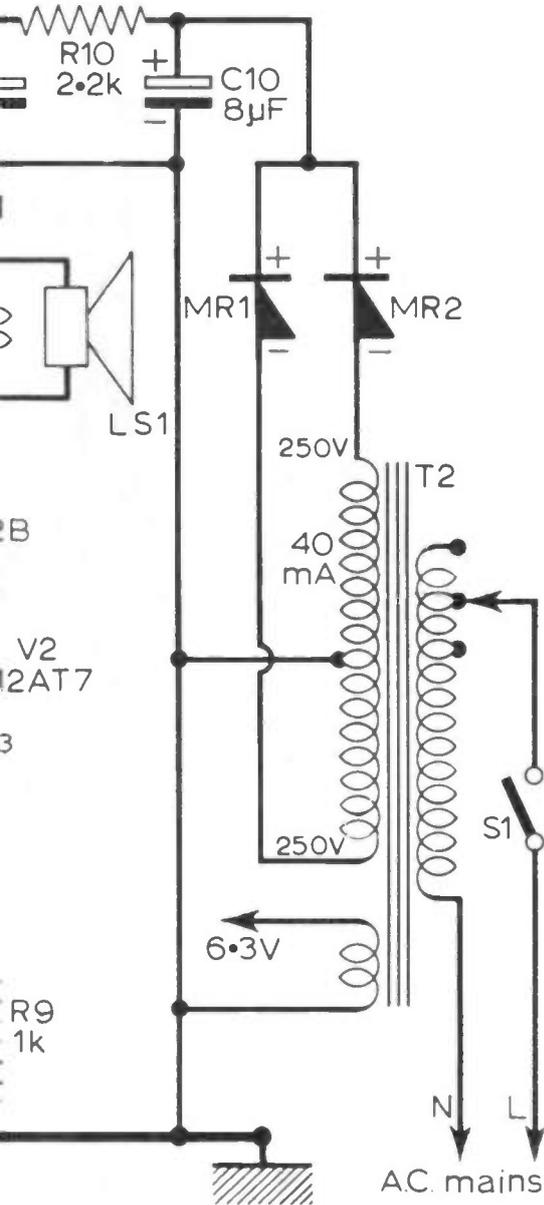TD., TOWER HOUSE, SOUTHAMPTON STREET, LONDON W.C.2.



COMPONENTS LIST

Resistors:

R1	2.2MΩ	R6	220kΩ
R2	150kΩ	R7	2.2kΩ
R3	220kΩ	R8	470kΩ
R4	20kΩ	R9	1kΩ
R5	33kΩ	R10	2.2kΩ 3W w.w.

All 10%, 1/2W carbon, except where otherwise indicated

VR1 100kΩ wire-wound potentiometer
VR2 500kΩ carbon potentiometer

Capacitors:

C1	50pF mica or ceramic
C2	50pF mica or ceramic
C3	0.1μF paper
C4	500pF mica or ceramic
C5	4μF electrolytic 350V
C6	0.01μF paper
C7	0.01μF paper
C8	12μF electrolytic 25V
C9	16μF } dual electrolytic 350V
C10	8μF }
VC1	150pF air dielectric variable

Transformers:

T1 Output transformer 60 : 1
T2 Small mains transformer. Tapped primary. Secondaries: 250-0-250V 40mA; 6.3V 1A

Valves:

V1 954 V2 12AT7

Other Circuit Components:

LS1 2 1/2 in. diameter loudspeaker 2-3Ω
S1 Toggle switch s.p.s.t.
MR1, 2 Contact cooled rectifier 250V 40mA




Miscellaneous:

Ball drive 6 : 1 ratio. Knobs: one 2 in. diameter, two 1 in. diameter. One B9A valveholder. Ribbed 4-pin plug-in coil formers (Eddystone). Coil holder (Eddystone). Aerial-earth socket strip. Tag strip (2 insulated). Chassis 7 in. x 4 in. x 2 1/4 in. approx. Panel 6 in. x 7 1/4 in.

COIL WINDING DATA

- 1.2-4Mc/s (250-75 metres)
100 turns 34s.w.g., tap at 2 turns. Aerial coupling, 20 turns.
- 2.5-7.5Mc/s (120-40 metres)
50 turns 32s.w.g., tap at 1 1/2 turns. Aerial coupling, 15 turns.
- 6.75-22Mc/s (44-13.6 metres)
16 turns 30s.w.g., tap at 3/4 turn. Aerial coupling, five turns.
- 14.5-50Mc/s (20.6-6 metres)
5 1/2 turns 30s.w.g., tap 1/2 to 1/4 turn. Aerial coupling, two turns.
- 40-100Mc/s (7.5-3 metres)
2 1/2 turns 20s.w.g., double spaced, tap at 1/2 turn. Aerial coupling, one turn.

The two larger coils are close wound. The other coils are on threaded formers, and spaced 21 turns per inch. Aerial windings are near the tuned winding as indicated in Fig. 4(d).

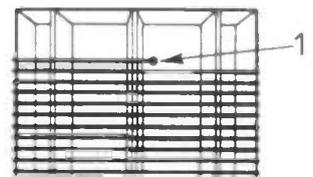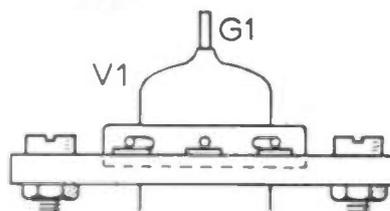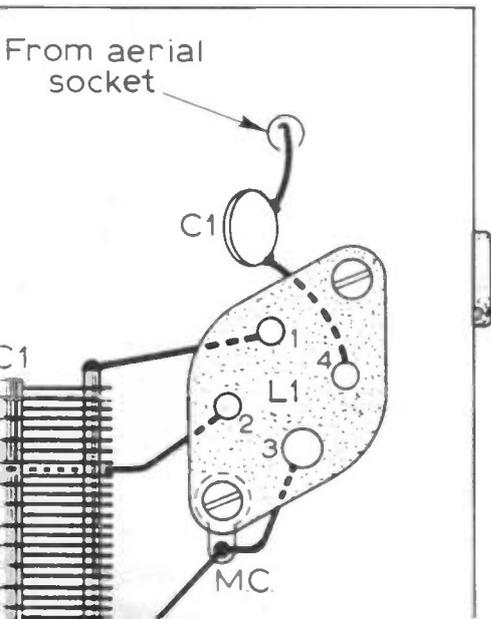

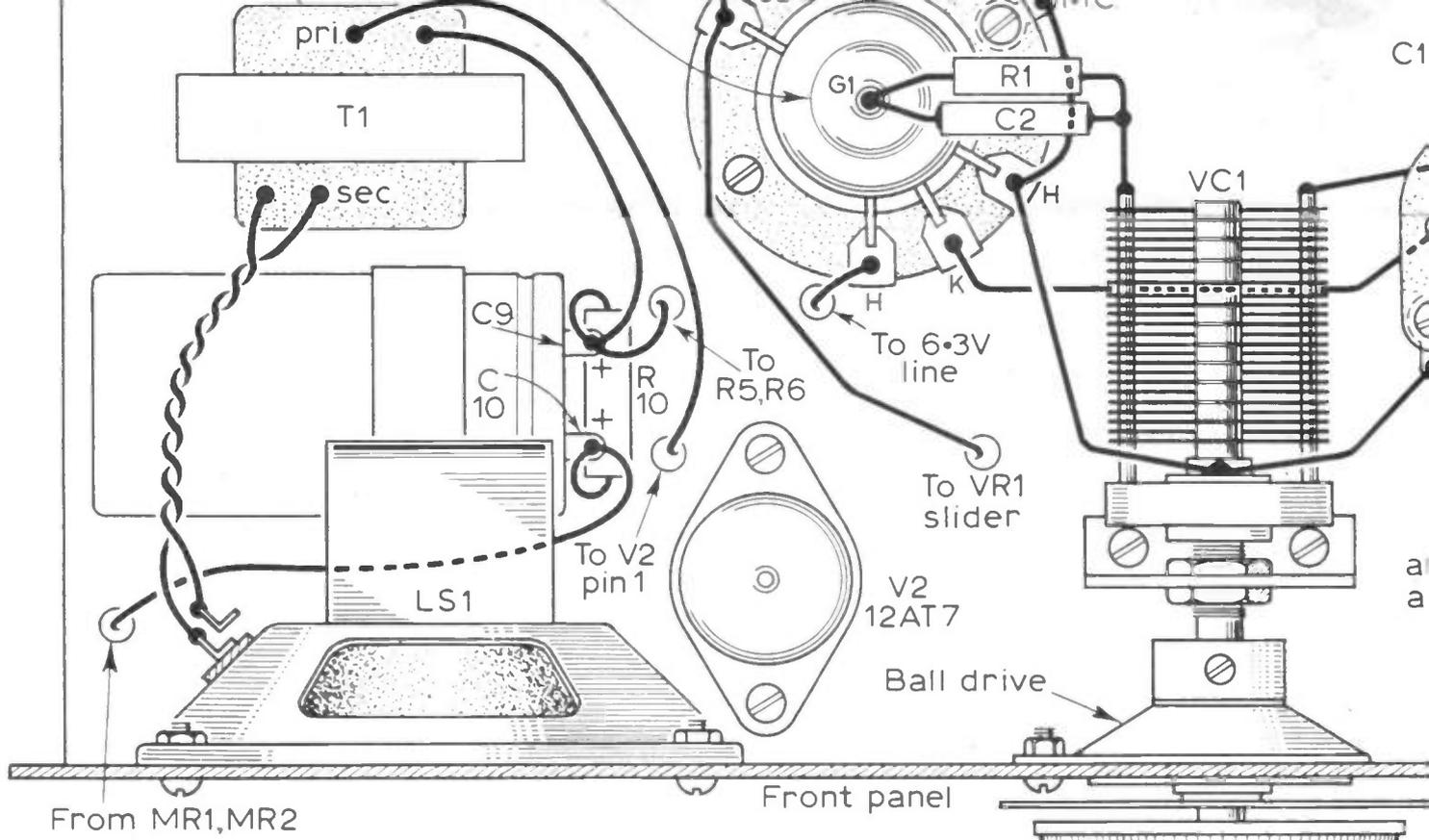


Fig. 2 - Above-chassis wiring.


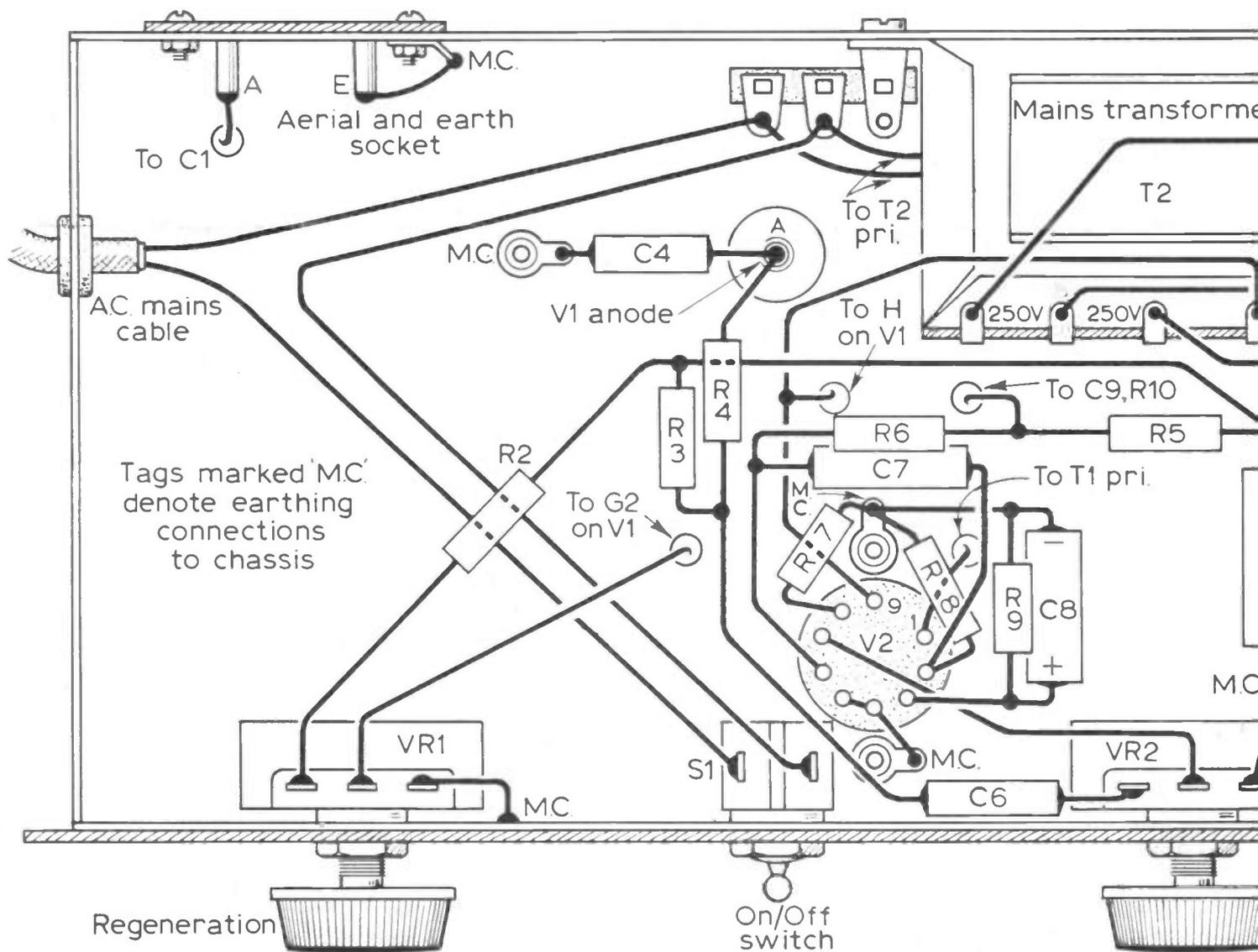
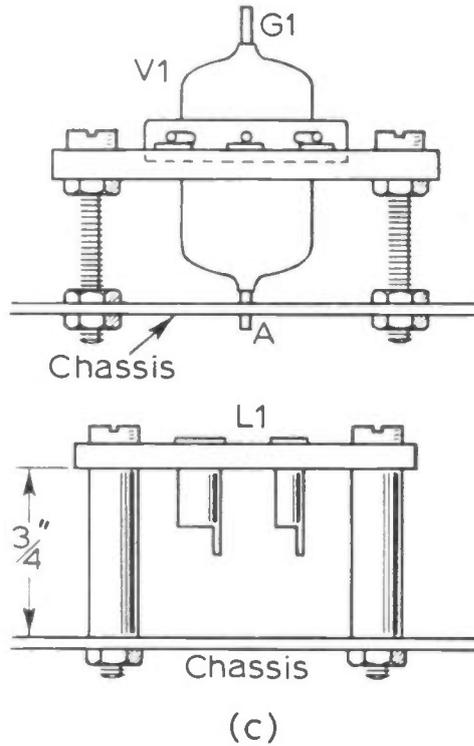


Fig. 3 - Below-chassis wiring.

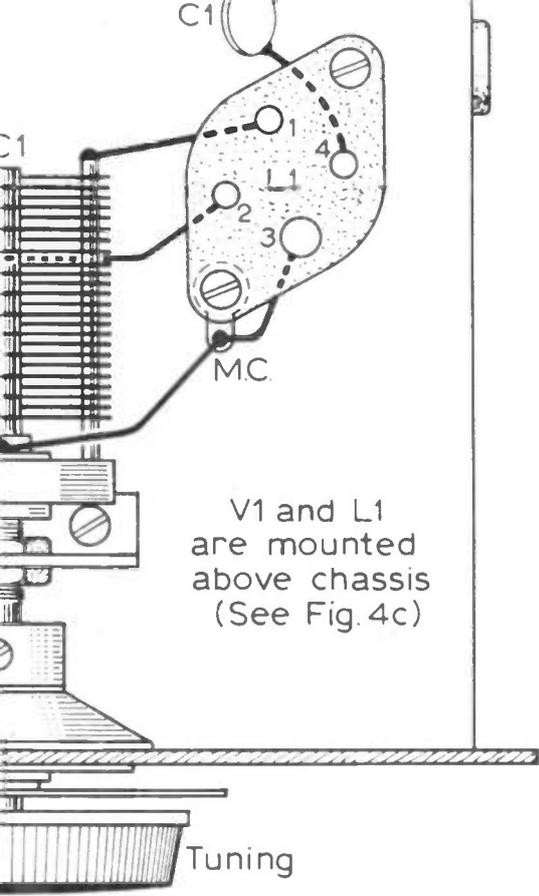

The two larger coils are close wound. The other coils are on threaded formers, and spaced 21 turns per inch. Aerial windings are near the tuned winding as indicated in Fig. 4(d).


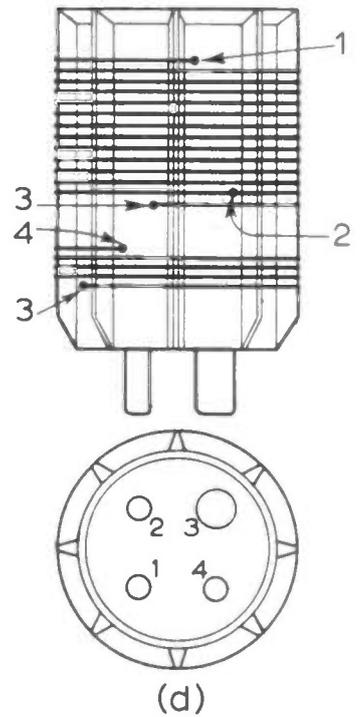


Fig. 4 - Coil and valve details.

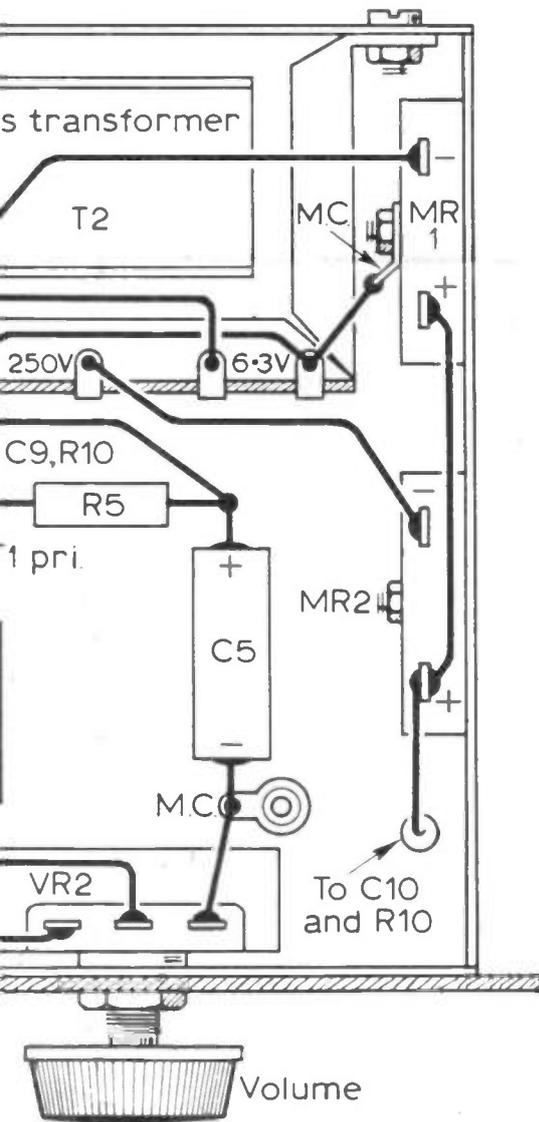

Material... 18swg. aluminium

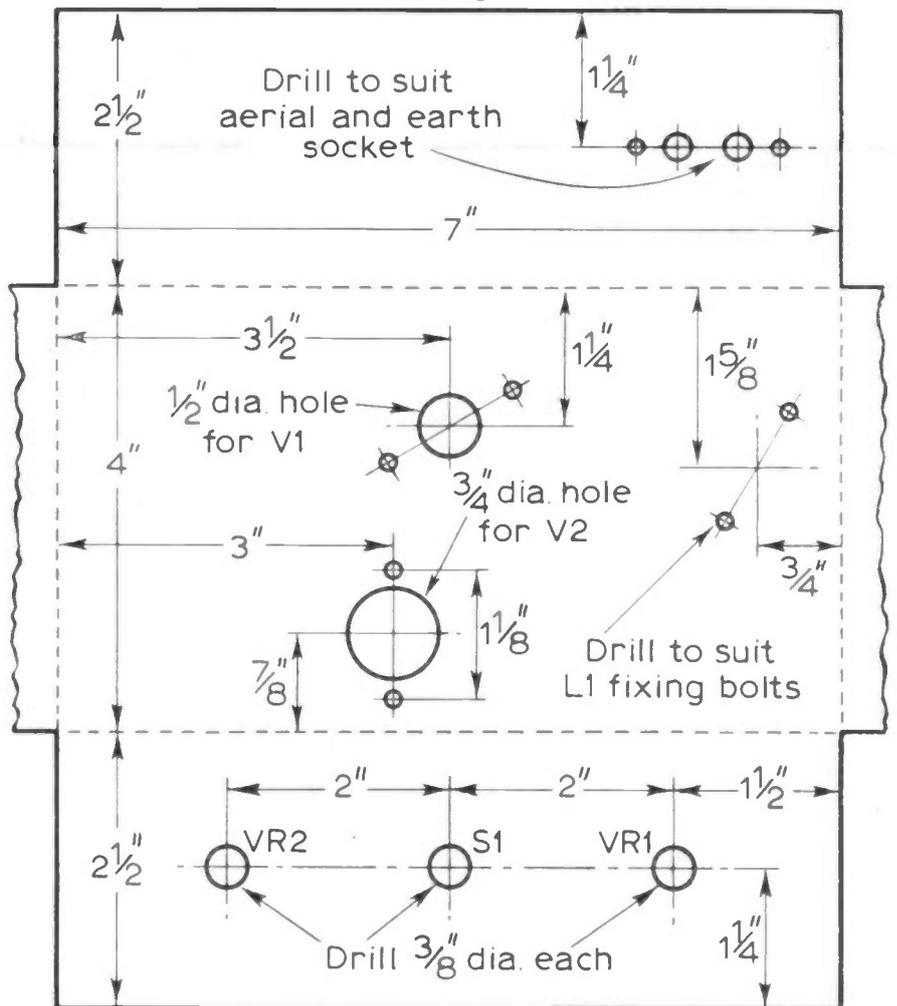


Fig 5 - Chassis drilling details.

SHORT WAVE

BROADCASTING STATIONS

THIS list is not intended to be a complete guide to the many hundreds of short wave broadcasting stations in operation, but it does indicate the stations which, in normal conditions, are most easily heard.

Frequency (kc/s)	Wavelength (metres)	Station
5930	50-57	Prague, Czechoslovakia
5960	50-34	Rome, Italy
5990	50-08	Bucharest, Roumania
6005	49-96	R.I.A.S., Berlin, Germany
6010	49-92	Rome, Italy
6025	49-79	Radio Nederland, Holland
6025	49-79	Lisbon, Portugal
6030	49-75	Muhlacker, W. Germany
6035	49-71	Monte Carlo, Monaco
6055	49-55	Schwarzenburg, Switzerland
6065	49-46	Horby, Sweden
6070	49-42	Sofia, Bulgaria
6075	49-38	Osterloog, W. Germany
6090	49-26	Radio Luxembourg
6100	49-18	Belgrade, Yugoslavia
6140	48-86	Voice of America, Tangier
6145	48-82	Allouis, France
6160	48-70	Voice of America, Munich, W. Germany
6165	48-66	Schwarzenburg, Switzerland
6175	48-58	Allouis, France
6190	48-47	Bremen, W. Germany
6190	48-47	Vatican City
7050	42-55	Cairo, Egypt
7105	42-22	Madrid, Spain
7125	42-11	Warsaw, Poland
7135	42-05	Monte Carlo, Monaco
7180	41-78	Baghdad, Iraq
7195	41-70	Bucharest, Roumania
7200	41-67	Belgrade, Yugoslavia
7220	41-55	Budapest, Hungary
7255	41-35	Sofia, Bulgaria
7275	41-24	Rome, Italy
7280	41-21	Allouis, France
7285	41-18	Ankara, Turkey
9009	33-03	Tel Aviv, Israel
9410	31-88	B.B.C. Overseas Service
9475	31-66	Cairo, Egypt
9505	31-56	Prague, Czechoslovakia
9510	31-55	B.B.C. Overseas Service
9515	31-53	Rome, Italy
9520	31-51	Voice of America, Tangier
9535	31-46	Schwarzenburg, Switzerland
9540	31-45	Warsaw, Poland
9570	31-35	Shepparton, Australia
9575	31-33	Rome, Italy
9585	31-30	Allouis, France
9620	31-19	Horby, Sweden
9630	31-15	Sackville, Radio Canada
9645	31-10	Vatican City
9665	31-04	Schwarzenburg, Switzerland
9675	31-01	Warsaw, Poland
9700	30-93	Sofia, Bulgaria
9715	30-88	Radio Nederland, Holland
9720	30-86	Radio Nacional, Rio de Janeiro, Brazil
9735	30-82	Deutsche Welle, W. Germany
9745	30-78	Ankara, Turkey
9770	30-71	Vienna, Austria
9780	30-67	Cairo, Egypt
9865	30-40	Djakarta, Indonesia
11705	25-63	Horby, Sweden
11715	25-61	Schwarzenburg, Switzerland
11720	25-60	Sackville, Radio Canada
11755	25-52	Leopoldville, Congo
11800	25-42	Accra, Ghana
11810	25-40	Rome, Italy
11820	25-38	B.B.C. Overseas Service
11830	25-36	Voice of America, Munich, W. Germany and Tangier
11835	25-35	Algiers, Algeria
11865	25-28	Schwarzenburg, Switzerland
11865	25-28	Havana, Cuba
11900	25-21	Paradys, South Africa
11910	25-19	Armed Forces Radio Service, Greenville, U.S.A.
11915	25-18	Voice of the Andes, Quito, Ecuador
11920	25-17	Allouis, France
11925	25-16	Radio Bandeirantes, Sao Paulo, Brazil
11965	25-06	Conakry, Guinea
11990	25-02	Prague, Czechoslovakia
12095	24-80	B.B.C. Overseas Service
15070	19-91	B.B.C. Overseas Service
15080	19-89	Paradys, South Africa
15115	19-85	Voice of the Andes, Quito, Ecuador
15125	19-83	Lisbon, Portugal
15155	19-80	ELWA, Monrovia, Liberia
15165	19-78	Damascus, Syria
15190	19-75	Brazzaville, Congo
15205	19-73	Voice of America, Greenville, U.S.A.

When and Where To

THIS is a far from easy task on which to give specific information. Forecasting propagation on short waves is, in some ways, as difficult as forecasting the weather. There are certain overall patterns but there are very many variable factors which can affect conditions at any one time. The main changes to be borne in mind are the seasonal ones, the difference between daytime and night-time conditions and, above all, the 11-year sunspot cycle.

From now until around 1966 conditions will not change greatly in their main features as we are in a period of low sunspot numbers, and the information given below is meant to apply to this period. Once sunspot numbers begin to increase, the pattern of band usage will change in many ways.

One useful pointer to remember is that broadcasting stations will beam their transmissions to Britain at the time and on the frequencies giving the best chance of good reception. Thus, if Radio Australia broadcasts to us around 07.00 G.M.T. on the 31 and 25 metre bands, that is when expert opinion expects best conditions for the path, although reception from Australia may be possible at other times.

All times quoted below are in G.M.T., using the 24-hour clock system. Let us consider various areas of the world and suggest the best times and frequencies for receiving stations in those areas.

1. North America and Caribbean area The best time for this area is between 15.00 and 23.00 during the whole year; in winter the peak is around 18.00 but in summer it is around 20.00/21.00. Western North America is harder to hear, and usually best around 15.00 to 18.00. For broadcast stations, the best bands in winter are 19 metres in the afternoon, then 25 metres after dark. In the summer period, 19 metres is usually best. For the amateur bands, 20 metres is the most reliable all the year, during the winter 40 metres and 80 metres can provide North American stations between 23.00 and 05.00.

2. Central America This can be an awkward area to hear and the best times are similar to those for North America. For the broadcast bands, as there are not many stations in this area which use the higher frequencies, the best band tends to be 49 metres around 04.00 to 06.00. On the amateur bands, 20 metres is again the most useful, but this area can come through on 15 metres at times when no North Americans can be heard.

3. South America The best times are around 09.00 to 11.00 and from 17.00 to 01.00. The Pacific coast tends to be best around 07.00 to 10.00 and later around 20.00 to 02.00. On the broadcast bands, during spring, winter and autumn, 19 metres is best for the morning period, with 25 and 31 metres best for the evening and night. In summer, the early period is not usually feasible, and 19 metres is best for the evening, but this area is not usually heard too well during the summer. On the amateur bands, 20 metres is usually best, with 40 metres possible later at night, and 15 metres is also a good possibility for the early evening.

4. North Africa 12.00 to 23.00, the clock. On usually good in after dark. C usually best, on

5. Central Africa are between 13 daylight 19 metres better, especially metres is likely to 20.00. This heard during ar

6. North America and around 20 Japan. On the On the amateur while recommen

7. South America 11.00 to 17.00. for the earlier towards the en 20 metres must that 15 metres: During the win extend on to a casting bands b

8. Australasia 10.00 and, in w New Zealand d around 09.00 to winter and autu the best broadc 31 and 41 metr opening which is the favourite

9. Pacific 06.00 to 11.00. in the area, an Of the amateur

10. Europe day. On the b Southern Euro Europe, 19 metr day. On the ar and 80 metres occurs on 15 a

Signal Reporting Systems

IT has become the usual practice to use some type of code for giving signal reports. The most usual system in use on the amateur bands is a Readability/Signal Strength code, using a scale from 1 to 5 for readability and from 1 to 9 for signal strength. These are not always used correctly and often when incorrectly adjusted "signal strength meters" are used, reports such as "S9 plus 40 dB" are heard. As will be seen below, S9 means "extremely strong" which can hardly be improved on! Following are the scales for readability and signal strength:

Readability:

- R1 Unreadable
- R2 Only just readable, and only occasional words heard
- R3 Readable, but with considerable difficulty
- R4 Readable with almost no difficulty
- R5 Perfectly readable

Signal Strength:

- S1 Signals only just perceptible
- S2 Very weak signals
- S3 Weak signals
- S4 Fair signals
- S5 Fairly good signals
- S6 Good signals
- S7 Moderately strong signals
- S8 Strong signals
- S9 Extremely strong signals

For reporting on telegraphy (CW) signals, an additional scale for "tone" is used to indicate the quality of the note. This is also a 1 to 9 scale, as follows:

Tone:

- T1 Extremely rough note
- T2
- T3
- T4
- T5
- T6 Modulated note, slight

THE "C"

THE "Q" C and other its full form. two letters) of "what is your location is ... groups to the usual ones wi

QRA Full ad
QRH Your f
QRK Signal
price c
ously)

QRL Busy
QRM Man-m
QRN Atmos
ence: s

QRO High p
QRP Low p
QRT Closed
QRU Nothin
QRV Ready

QRO High p
QRP Low p
QRT Closed
QRU Nothin
QRV Ready

QRO High p
QRP Low p
QRT Closed
QRU Nothin
QRV Ready

QRO High p
QRP Low p
QRT Closed
QRU Nothin
QRV Ready

QRO High p
QRP Low p
QRT Closed
QRU Nothin
QRV Ready

STANDARD

THE frequ kc/s are se standards are stations are

here To Listen

4. North Africa and Near East This area is best around 12.00 to 23.00, although it is possible to hear it almost round the clock. On the broadcast bands, 16, 19 and 25 metres are usually good in daylight, with 31 and 41 metres being better after dark. On the amateur bands, 15 and 20 metres are usually best, on 15 metres 08.00 to 11.00 is often a good time.

5. Central and South Africa The best times for this area are between 13.00 and 22.00. On the broadcast bands, during daylight 19 metres is best, but after dark 25 and 31 metres are better, especially in the winter half. On the amateur bands 15 metres is likely to be useful, with 20 metres best around 17.00 to 20.00. This area is possibly one of the few which will be heard during any openings on 10 metres.

6. North Asia The best times are around 06.00 to 09.00 and around 20.00, this is not an easy area to hear, especially Japan. On the broadcast bands, 19 and 25 metres are the best. On the amateur bands, 20 metres is probably the only worthwhile recommendation.

7. South and South-East Asia This is usually best around 11.00 to 17.00. The best broadcast bands are 16 and 19 metres for the earlier part, with 25 metres being most useful later towards the end of the best period. On the amateur bands 20 metres must again be the best suggestion, with just a chance that 15 metres might occasionally open in that direction. During the winter half it is likely that the best period may extend on to around 21.00 with the 31 and 41 metre broadcasting bands being best for this.

8. Australasia The best times for this area are 06.00 to 10.00 and, in winter, around 14.00 to 17.00 and around 22.00. New Zealand is not too easy to hear, and is usually better around 09.00 to 11.00. Reception is much better in the spring, winter and autumn than in the summer. In the better seasons, the best broadcast bands are 25 and 31 metres for the morning, 31 and 41 metres in the afternoon and 19 metres for the night opening which is less reliable. On the amateur bands, 20 metres is the favourite with 40 metres useful in winter in the mornings.

9. Pacific This is a difficult area usually, and is best around 06.00 to 11.00. There are few high power broadcasting stations in the area, and 19 and 25 metres are the most likely bands. Of the amateur bands, 20 metres is best.

10. Europe Obviously, this area can be heard 24 hours a day. On the broadcast bands, 25 and 31 metres are best for Southern Europe with 41 and 49 metres best for Northern Europe, 19 metres can provide European reception during the day. On the amateur bands 20 metres during the day, and 40 and 80 metres after dark are best, but in summer short skip occurs on 15 and 10 metres at times.

THE SHORT WAVE SPECTRUM

THE International Telecommunications Union is the controlling body over the whole of the radio frequency spectrum and allocations have been made from 10 kc/s to 40 kc/s. The accompanying chart shows the allocations between 1605 kc/s and 30000 kc/s, which is the range generally known as the "short waves". The I.T.U. divides the world into three regions for frequency allocation purposes; Region 1 comprises Europe, Africa, the Near East and the whole of the U.S.S.R.; Region 2 is made up of North America, Central America, South America and Greenland; and Region 3 contains Asia (except the U.S.S.R.) Australasia and the Pacific.

In the main, the allocations in the s.w. range are fairly uniform over all three Regions, but there are a few differences which should be noted.


1. The amateur band 1800 to 2000 kc/s is only available in a limited number of countries.

2. The broadcasting bands 2300 to 2500 kc/s, 3200 to 3400 kc/s and 4750 to 5060 kc/s are classed as "tropical" and are limited to countries in these regions.

3. In Region 2 the amateur band beginning at 3500 kc/s extends through to 4000 kc/s.

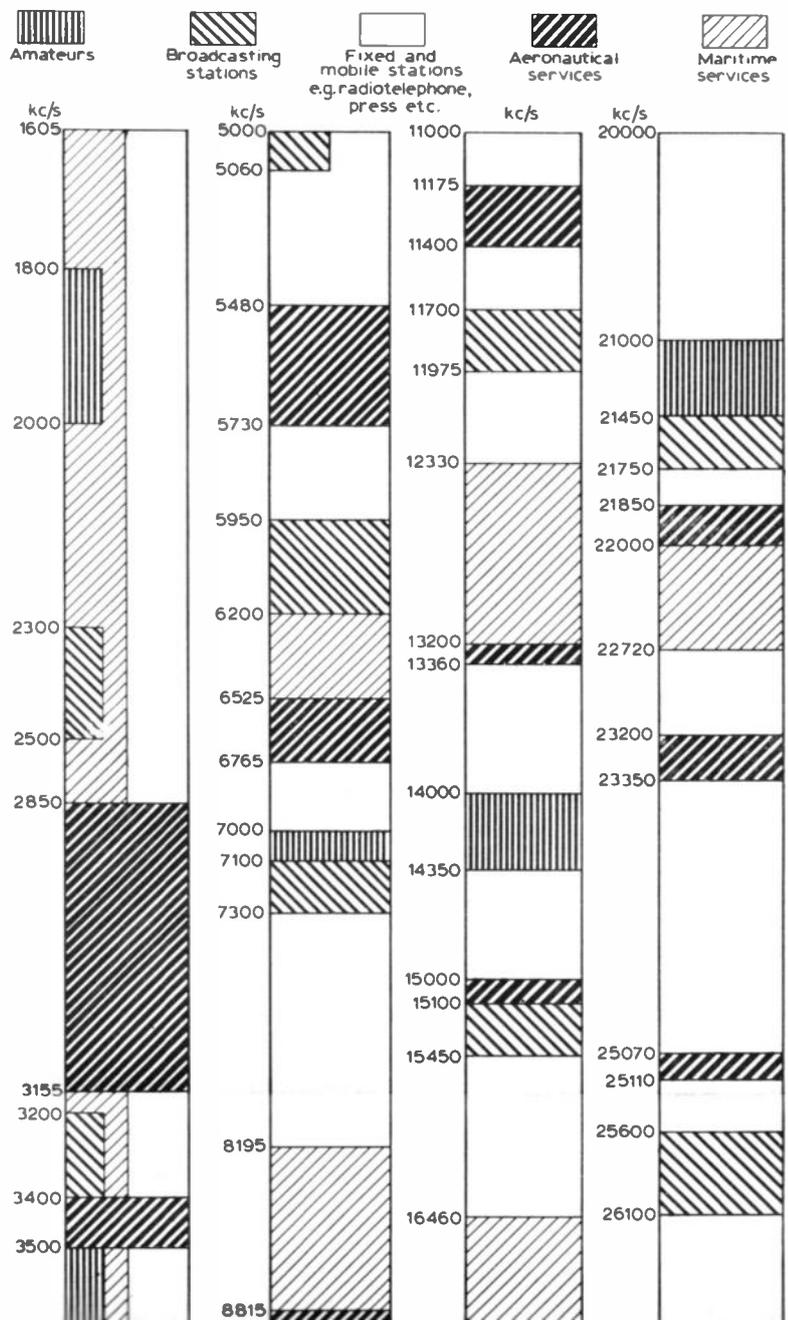4. In Region 2 the amateur band beginning at 7000 kc/s extends through to 7300 kc/s and the allocation 7100 to 7300 kc/s is not available for broadcasting.

The chart obviously has to leave out several minor points of difference, but these are mainly confined to the lower frequencies. The main classes of service are indicated as follows:



THE "Q" CODE

THE "Q" Code is used by aeronautical and maritime services and other commercial services and is very comprehensive in its full form. In its correct use, each group (made up of Q and two letters) can stand either for a question (e.g. QTH? means "what is your location?"), or the answer (e.g. QTH means "my location is ..."). Amateurs have adopted certain of the code groups to their own use and the following list shows the more usual ones with their meanings.

QRA Full address	QRX Wait
QRH Your frequency varies	QSA Readability of signal
QRK Signal strength (also price or value, humorously)	QSB Fading
QRL Busy	QSL Acknowledgement of receipt; confirmation of contact
QRM Man-made interference	QSO Contact
QRN Atmospheric interference; static	QSP Pass on a message
QRO High power	QSY Change frequency
QRP Low power	QTC Telegram, message
QRT Closed down	QTH Location
QRU Nothing further to say	QTR Time check
QRV Ready to operate	

STANDARD FREQUENCY STATIONS

THE frequencies 2500, 5000, 10000, 15000, 20000 and 25000 kc/s are set aside for station transmitting accurate frequency standards and also time signals in many cases. Some of these stations are:

ATA, New Delhi, India, operating on 10000 kc/s.
 RRV, Beijing, China, operating on 5000, 10000, 15000, 20000, 25000 kc/s.

11865	25-28	Schwarzenburg, Switzerland
11865	25-28	Havana, Cuba
11900	25-21	Paradys, South Africa
11910	25-19	Armed Forces Radio Service, Greenville, U.S.A.
11915	25-18	Voice of the Andes, Quito, Ecuador
11920	25-17	Allouis, France
11925	25-16	Radio Bandeirantes, Sao Paulo, Brazil
11965	25-06	Conakry, Guinea
11990	25-02	Prague, Czechoslovakia
12095	24-80	B.B.C. Overseas Service
15070	19-91	B.B.C. Overseas Service
15080	19-89	Paradys, South Africa
15115	19-85	Voice of the Andes, Quito, Ecuador
15125	19-83	Lisbon, Portugal
15155	19-80	ELWA, Monrovia, Liberia
15165	19-78	Damascus, Syria
15190	19-75	Brazzaville, Congo
15205	19-73	Voice of America, Greenville, U.S.A.
15220	19-71	Shepparton, Radio Australia
15250	19-67	Voice of America, Bethany, U.S.A.
15260	19-66	B.B.C. Far Eastern Station, Malaya
15280	19-63	Armed Forces Radio Service, Greenville, U.S.A.
15290	19-62	Voice of America, Tangier
15305	19-60	Voice of America, Greenville, U.S.A.
15320	19-58	Sackville, Radio Canada
15330	19-57	Voice of America, Greenville, U.S.A.
15370	19-52	Radio Tupi, Rio de Janeiro, Brazil
15385	19-50	WRUL, Boston, U.S.A.
15400	19-48	Rome, Italy
15445	19-43	Brazzaville, Congo
15475	19-38	Cairo, Egypt
17695	16-95	B.B.C. Overseas Service
17780	16-87	Voice of America, Bound Brook, U.S.A.
17795	16-86	Schwarzenburg, Switzerland
17820	16-84	Sackville, Radio Canada
17895	16-76	Lisbon, Portugal
17920	16-74	Cairo, Egypt
21470	13-97	B.B.C. Overseas Service
21495	13-96	Lisbon, Portugal
21560	13-91	Rome, Italy

N.B.—No frequencies are given for *Radio Moscow* or *Radio Free Europe* as the schedules of these stations vary more often than others, but they will usually be heard on several frequencies in each band.

- Readability:**
R1 Unreadable
R2 Only just readable, and only occasional words heard
R3 Readable, but with considerable difficulty
R4 Readable with almost no difficulty
R5 Perfectly readable
- Signal Strength:**
S1 Signals only just perceptible
S2 Very weak signals
S3 Weak signals
S4 Fair signals
S5 Fairly good signals
S6 Good signals
S7 Moderately strong signals
S8 Strong signals
S9 Extremely strong signals

For reporting on telegraphy (CW) signals, an additional scale for "tone" is used to indicate the quality of the note. This is also a 1 to 9 scale, as follows:

- Tone:**
T1 Extremely rough note
T2 Very rough note
T3 Rough, low pitched note
T4 Rather rough note
T5 Musically modulated note
T6 Modulated note, slight whistle
T7 Fairly good note, smooth ripple
T8 Good note, slight ripple
T9 Pure DC note

(If the note seems to be crystal controlled, an "x" is added, if the note is chirpy, a "c" is added.)

The readability/strength code can be used for reporting to broadcasting stations, but a better system for this purpose is the SINPO code. This has five scales, each of 1 to 5, as indicated by the letters S (Signal Strength), I (Interference), N (Noise, i.e. static), P (Propagation Disturbance, i.e. fading) and O (Overall quality of reception).

The scale for signal strength is: 1—barely audible; 2—poor; 3—fair; 4—good; 5—excellent. The scales for Interference, Noise and Propagation Disturbance are: 1—extreme; 2—severe; 3—moderate; 4—slight; 5—nil. The scale for Overall quality is: 1—unusable; 2—poor; 3—fair; 4—good; 5—excellent. Thus, in the SINPO code, a perfectly received signal would be given 55555.

- QRL Signal price (possibly)
QRM Busy
QRN Man-mance; s
QRO High p
QRP Low p
QRT Closed
QRU Nothin
QRV Ready

STANDARD

- THE frequ
kc/s are se
standards a
stations are:
- ATA, New
 - BPV, Peking
 - FFH, Paris
 - HBN, Neu
 - IAM, Rome
 - IBF, Turin
 - JJY, Tokyo
 - 15000 kc/s
 - LOL, Buen
 - 15000 kc/s
 - MSF, Rugby
 - OMA, Prag
 - RWM, Mos
 - 15000 kc/s
 - WWV, Wa
 - 15000, 20
 - WWVH, H
 - ZUO, Joha
 - 10000 kc/s
- In addition,
and 14670 kc/s
Most of th
intervals, and
time checks a

AMATEUR CALLSIGN PREFIXES

AMATEUR radio stations, in common with all other communications stations, have to identify themselves by call signs. Each station has an individual officially allocated call sign which follows a standard pattern, being made up of a prefix, a numeral, and a suffix. The prefix may be one letter, two letters or a numeral and letter, but it is derived from the international list of call sign allocations. The numeral may have some geographical significance, but this is not always so. The suffix may be one, two or three letters; in the bigger countries they are issued in alphabetical order, but in smaller countries they are often issued haphazardly, a popular idea being to allow the operator to use his initials as his call.

To take an example of a call sign—G3AKA. The G is the prefix allocated to England, the figure 3 has no special meaning and the AKA is the suffix. In another case—say W7XYZ. Here the W is the U.S.A. prefix, but in this case the figure 7 indicates that the station is located in a particular area of the U.S.A., and the XYZ is the suffix. One final example—say 5N2ABC. In this case 5N is the prefix for Nigeria, the figure 2 has no significance, and the ABC is the suffix.

The following is an up-to-date list of prefixes, the numeral is only given here where it is necessary to distinguish between countries, for instance VQ is the general prefix for Commonwealth countries in East Africa, but VQ1 is Zanzibar and VQ2 is Northern Rhodesia, so the numeral is virtually part of the prefix in these cases. This list is not intended to be an "official" list of countries, the various clubs and societies each issue their own lists of this kind, which only differ where some of the more out of the way places are concerned.

Occasionally, stations can be heard with additional letters, such as /P or /M after the call sign. Examples of these and their meanings are: /A indicates the station is being operated from another address than that given in the licence. /P means the

station is being operated "portable", i.e. not from a mains electricity supply; this letter is usually heard when Field Day contests are being held. /M means that the station is "mobile", i.e. in a car or other vehicle. /MM means "maritime mobile", on board a ship. /AM is "aeronautical mobile", on an aircraft. In the U.S.A., however, /P and /A are not used; instead, the call area in which the station is temporarily operating is added, for instance W2ZZZ operating portable in the W2 area would sign W2ZZZ/2, if he went over to California he would sign W2ZZZ/6. If he crossed into Canada, he might sign W2ZZZ/VE3 and so on.

CALL AREAS

As mentioned above, in certain countries, there is a subdivision into call areas, indicated by the figure in the call sign. Most of the South American countries use this system, and it also applies in Australia, Canada, New Zealand and the U.S.A. Details for these latter four countries are:

Australia VK1—Canberra; VK2—New South Wales; VK3—Victoria; VK4—Queensland; VK5—South Australia; VK6—Western Australia; VK7—Tasmania; VK8—Northern Territory.

Canada VE1—Nova Scotia, New Brunswick and Prince Edward Island; VE2—Province of Quebec; VE3—Ontario; VE4—Manitoba; VE5—Saskatchewan; VE6—Alberta; VE7—British Columbia; VE8—Yukon and North West Territories; VO1—Newfoundland; VO2—Labrador.

New Zealand ZL1—Auckland; ZL2—Wellington; ZL3—Canterbury; ZL4—Otago.

United States of America K/KN/W/WA/WB/WN/WV prefixes: 1—Connecticut, Maine, Massachusetts, New Hampshire, Rhode Island and Vermont. 2—New Jersey and New York. 3—Delaware, Maryland, Pennsylvania and District of Columbia. 4—Alabama, Florida, Georgia, Kentucky, North Carolina, South Carolina, Tennessee, Virginia. 5—Arkansas, Louisiana, Mississippi, New Mexico, Oklahoma and Texas. 6—California. 7—Arizona, Idaho, Montana, Nevada, Oregon, Utah, Washington and Wyoming. 8—Michigan, Ohio and West Virginia. 9—Illinois, Indiana and Wisconsin. Ø—Colorado, Iowa, Kansas, Minnesota, Missouri, Nebraska, North Dakota, South Dakota.

AC3	Sikkim	CO	Cuba
AC4	Tibet	CP	Bolivia
AC5	Bhutan	CR4	Cape Verde Islands
AP	Pakistan	CR5	Portuguese Guinea, Principe Is., and Sao Thome
BY	China	CR6	Angola
BV	Taiwan	CR7	Mozambique
CE	Chile	CR8	Portuguese Timor
CE9	Chilean Antarctic	CR9	Macao
CEØ	Easter Island	CTI	Portugal
CM	Cuba		
CN	Morocco		

CT2	Azores Islands	EAØ	Spanish Guinea and Fernando Poo
CT3	Madeira Islands	EI	Eire
CX	Uruguay	EL	Liberia
DJ	Germany (West)	EP	Iran
DL	Germany (West)	EQ	Iran
DM	Germany (East)	ET	Ethiopia
DU	Philippine Islands	F	France
EA	Spain	FB	Amsterdam and St. Paul Is., Crozet and Kerguelen Is.
EA6	Balearic Islands		
EA8	Canary Islands		
EA9	Ceuta, Melilla and Ifni		

FC	Corsica
FG	Guadeloupe
FH	Comoro Islands
FK	New Caledonia
FL	French Somaliland
FM	Martinique
FO	Marquesas Is., Is., Tuamoto, Clipperton Is.
FP	St. Pierre and Is.
FR	Reunion Islands
FS	St. Martin Island
FU	New Hebrides
FW	Wallis and Futuna
FY	French Guiana
GE	England
GB	United Kingdom (special stations)
GC	Channel Islands
GD	Isle of Man
GI	Northern Ireland
GM	Scotland
GW	Wales
HA	Hungary
HB	Switzerland
HBØ	Liechtenstein
HC	Ecuador
HCB	Galapagos Islands
HH	Haiti
HI	Dominican Republic
HK	Colombia
HL	Korea
HM	Korea
HP	Panama
HR	Honduras
HS	Thailand
HV	Vatican
HZ	Saudi Arabia
I	Italy
IL	Pelagian Islands
IP	Pantellaria Islands
IS	Sardinia
IT	Sicily
JA	Japan
JT	Mongolia
JY	Jordan
JZØ	Netherlands New Guinea
K	United States of America
KA	Japan (U.S. Forces)
KB	Baker, Howland, American Phoenix
KC4	U.S. Antarctic and Navassa Island

ously)
 QRL Busy
 QRM Man-made interference
 QRN Atmospheric interference; static
 QRO High power
 QRP Low power
 QRT Closed down
 QRU Nothing further to say
 QRV Ready to operate

receipt; confirmation of contact
 QSO Contact
 QSP Pass on a message
 QSY Change frequency
 QTC Telegram, message
 QTH Location
 QTR Time check


STANDARD FREQUENCY STATIONS

THE frequencies 2500, 5000, 10000, 15000, 20000 and 25000 kc/s are set aside for station transmitting accurate frequency standards and also time signals in many cases. Some of these stations are:

- ATA, New Delhi, India, operating on 10000 kc/s.
- BPV, Peking, China, operating on 5000, 10000 and 15000 kc/s.
- FFH, Paris, France, operating on 2500 kc/s.
- HBN, Neuchatel, Switzerland, operating on 5000 kc/s.
- IAM, Rome, Italy, operating on 5000 kc/s.
- IBF, Turin, Italy, operating on 5000 kc/s.
- JJY, Tokyo, Japan, operating on 2500, 5000, 10000 and 15000 kc/s.
- LOL, Buenos Aires, Argentina, operating on 5000, 10000 and 15000 kc/s.
- MSF, Rugby, England, operating on 2500, 5000 and 10000 kc/s.
- OMA, Prague, Czechoslovakia, operating on 2500 kc/s.
- RWM, Moscow, U.S.S.R., operating on 5000, 10000 and 15000 kc/s.
- WWV, Washington, U.S.A., operating on 2500, 5000, 10000, 15000, 20000 and 25000 kc/s.
- WWVH, Hawaii, operating on 5000, 10000 and 15000 kc/s.
- ZUO, Johannesburg, South Africa, operating on 5000 and 10000 kc/s.

In addition, CHU, Ottawa, Canada, transmits on 3330, 7335 and 14670 kc/s.

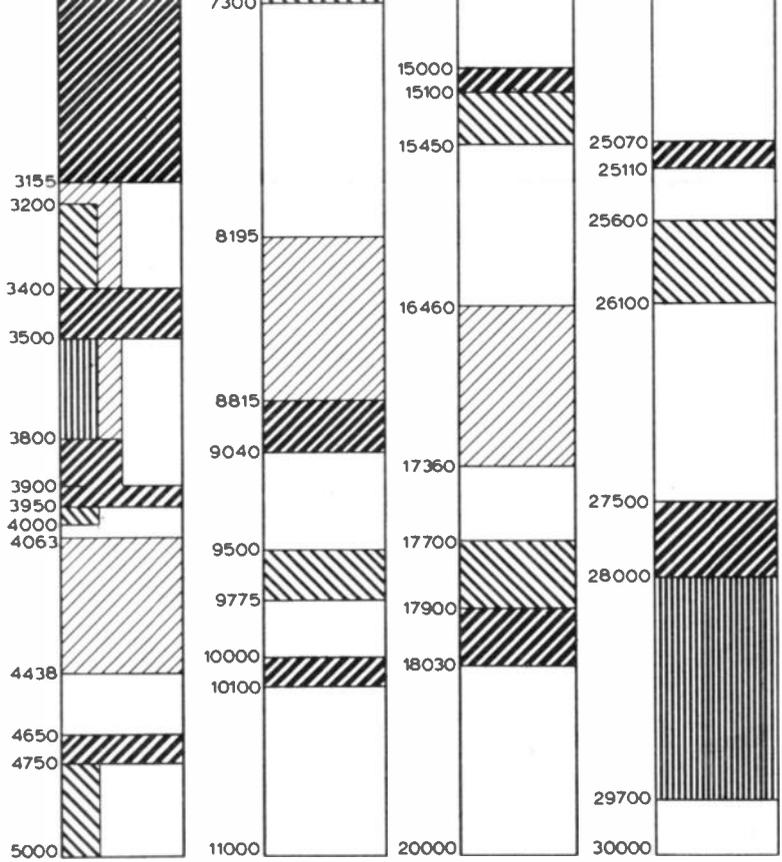
Most of these stations make speech announcements at intervals, and give their call signs in morse code. WWV gives time checks and also propagation forecasts.



FC Corsica	KC4 Caroline Islands	TL Central African Republic	VQ2 Northern Rhodesia	ZB1 Malta
FG Guadeloupe	KG1 Greenland (U.S. Forces)	TN Republic of Congo	VQ4 Kenya	ZB2 Gibraltar
FH Comoro Islands	KG4 Guantanamo Bay	TR Gabon	VQ7 Aldabra Islands	ZC5 North Borneo
FK New Caledonia	KG6 Guam, Mariana Islands and Marcus Islands	TT Tchad	VQ8 Mauritius	ZD3 Gambia
FL French Somaliland	KH Hawaiian Islands	TU Ivory Coast	VQ9 Seychelles	ZD6 Nyasaland
FM Martinique	KJ Johnston Island	TY Dahomey	VR1 Gilbert & Ellice Islands, Ocean Islands, British Phoenix Islands	ZD7 St. Helena
FO Marquesas Is., Society Is., Tuamotu, Tubuai Is., Clipperton Is.	KL Alaska	TZ Mali	VR2 Fiji Islands	ZD8 Ascension Island
FP St. Pierre and Miquelon Is.	KM Midway Islands	UA U.S.S.R.	VR3 Line Islands	ZD9 Tristan da Cunha and Gough Islands
FR Reunion Islands	KN United States of America (novice stations)	UB Ukraine	VR4 Solomon Islands	ZE Southern Rhodesia
FS St. Martin Island	KP4 Puerto Rico	UC White Russia	VR5 Tonga	ZK1 Cook Islands
FU New Hebrides	KP6 Palmyra and Jarvis Is.	UD Azerbaijan	VR6 Pitcairn Island	ZK2 Niue
FW Wallis and Fortuna Is.	KR Ryukyu Islands	UG Armenia	VS1 Singapore	ZL New Zealand
FY French Guiana and Inini England	KS4 Swan Island	UH Turkoman	VS4 Sarawak	ZL0 New Zealand Antarctica
GB United Kingdom (special stations)	KS6 American Samoa	UI Uzbek	VS5 Brunei	ZM6 Western Samoa
GC Channel Islands	KV American Virgin Islands	UJ Tadjik	VS6 Hong Kong	ZM7 Tokelau Islands
GD Isle of Man	KW Wake Island	UL Kazakh	VS9 Aden, Socotra, Maldiv Islands, Kamarin Islands	ZP Paraguay
GI Northern Ireland	KX Marshall Islands	UM Kirghiz	VU India	ZS South Africa
GM Scotland	KZ Panama Canal Zone	UO Moldavia	W United States of America	ZS3 South West Africa
GW Wales	LA Norway	UP Lithuania	WA United States of America	ZS7 Swaziland
HA Hungary	LU Argentina	UQ Latvia	WB United States of America	ZS8 Basutoland
HB Switzerland	LX Luxembourg	UR Estonia	WG Mariana Is. (novice stations)	ZS9 Bechuanaland Protectorate
HB0 Liechtenstein	LZ Bulgaria	UT Ukraine	WL Alaska (novice stations)	3A Monaco
HC Ecuador	MP4 Bahrain, Muscat and Oman, Qatar & Trucial Oman	UV U.S.S.R.	WN United States of America (novice stations)	3V Tunisia
HC8 Galapagos Islands	OA Dominican Republic	UW U.S.S.R.	WP4 Puerto Rico (novice stations)	3W Vietnam
HH Haiti	OD Lebanon	VE Canada	WS6 American Samoa (novice stations)	3X Guinea
HI Dominican Republic	OE Austria	VK Australia	WV United States of America (novice stations)	4S Ceylon
HK Colombia	OH Finland	VK9 New Guinea, Papua, Norfolk Island, Nauru, Cocos Is., Lord Howe Islands	XE Mexico	4U United Nations
HL Korea	OK Czechoslovakia	VK0 Australian Antarctica, Heard Island and Macquarie Islands	XT Upper Volta	4W Yemen
HM Korea	ON Belgium	VO Canada (Newfoundland and Labrador)	XU Cambodia	4X Israel
HP Panama	OX Greenland	VPI British Honduras	XV Vietnam	5A Libya
HR Honduras	OY Faroe Islands	VP2 Anguilla, Antigua, Barbuda, Brit. Virgin Is., Dominica, Grenada, Montserrat, St. Kitts, Nevis, St. Lucia, St. Vincent	XW Laos	5B4 Cyprus
HS Thailand	OZ Denmark	VP3 British Guiana	XZ Burma	5H3 Tanganyika
HV Vatican	PA Netherlands	VP4 Trinidad and Tobago	YI Iraq	5N2 Nigeria
HZ Saudi Arabia	PL Netherlands	VP5 Cayman & Turks & Caicos Islands	YJ New Hebrides	5R Malagasy Republic
I Italy	PJ Netherlands Antilles	VP6 Barbados	YK Syria	5T Mauritania
IL Pelagian Islands	PK Indonesia	VP7 Bahama Islands	YN Nicaragua	5U Niger
IP Pantellaria Island	PX Andorra	VP8 Falkland Islands and Dependencies, Grahamland, South Georgia	YO Roumania	5V Togolese Republic
IS Sardinia	PY Brazil	VP9 Bermuda	YS El Salvador	5W Western Samoa
IT Sicily	PZ Surinam	VQ1 Zanzibar	YU Yugoslavia	5X5 Uganda
JA Japan	SL Sweden (Forces)		YV Venezuela	6O Somali Republic
JT Mongolia	SM Sweden		ZA Albania	6T Sudan
JY Jordan	SP Poland			6W Senegal
JZ0 Netherlands New Guinea	SU Egypt			6Y Jamaica
K United States of America	SV Greece			7X Algeria
KA Japan (U.S. Forces)	TA Turkey			9A San Marino
KB Baker, Howland and American Phoenix Is.	TF Iceland			9G Ghana
KC4 U.S. Antarctic and Navassa Island	TG Guatemala			9K Kuwait
	TI Costa Rica			9L Sierra Leone
	TJ Cameroon			9M Federation of Malaya
				9N Nepal
				9Q Congo Republic
				9U Burundi
				9X Ruanda

PICCADILLY

Britain's finest cigarette.

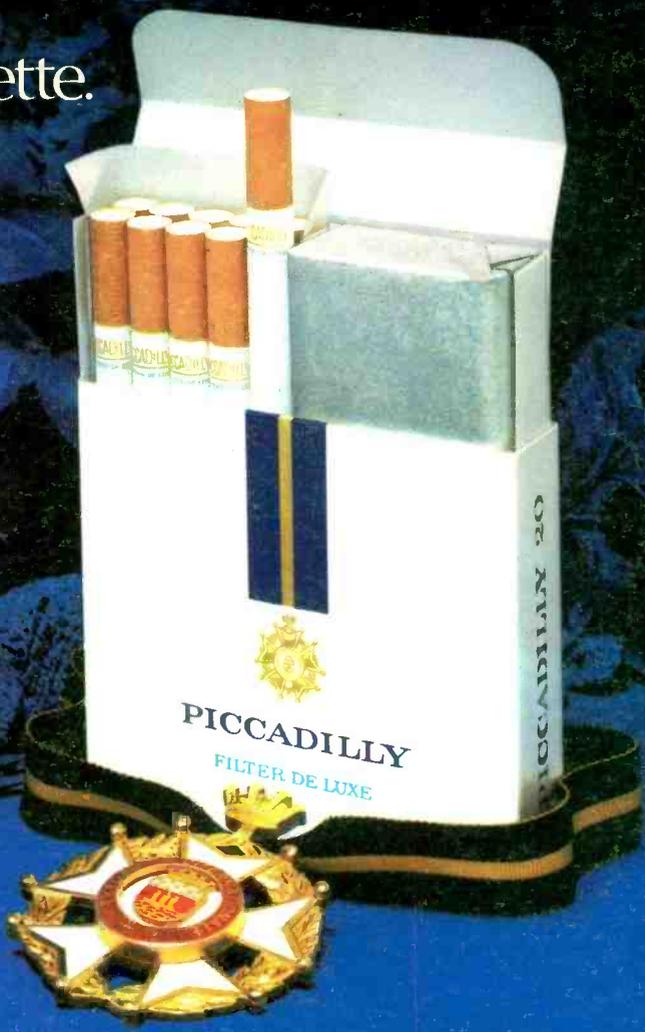

EVERY PACKET CARRIES A GOVERNMENT HEALTH WARNING