

# PRACTICAL WIRELESS

MARCH  
1974

25p

**FREE INSIDE**



# CASSETTE RECORDER AND TUNER AMPLIFIER

Australia 50c  
New Zealand 50c  
South Africa 45c  
Rhodesia 45c  
Nigeria X40  
Malaysia 31.80  
Sweden 42.80  
Malta 22.00  
Norway 33.10



**also:** IC WAVEFORM GENERATOR  
CRYSTAL HARMONIC CALIBRATOR

# Write the Specification of your perfect iron

and compare it with an Antex

*low leakage and  
Precision for delicate  
equipment  
Interchangeable Bit  
Iron-coated  
large*



**MODEL X25** Soldering Iron 220 240 or 100-120 Volts. The leakage current of the NEW X25 is only a few micro-amps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element, ceramic and steel shaft. Bits do not "freeze" and can easily be removed. **PRICE £2-05** (rec. retail) P & P 10p. Suitable for production work and as a general purpose iron.

**MODEL CCN** 220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64" including Heat Shield. **PRICE £2-48** (rec. retail) P & P 10p.

**MODEL C** Miniature 15 watt soldering iron fitted 3/32" iron coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE £2-05** (rec. retail) P & P 10p.

**MODEL MLX KIT** Battery operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet and with booklet "How to Solder". **PRICE £2-54** (rec. retail) P & P 12p.


**ST3 Stand** - This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable, serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration. **PRICE: £1-00** (rec. retail) P & P 10p.



**MODEL G** 18 watt miniature iron, fitted with long-life iron-coated bit 3/32". Voltage 240, 220 or 110. **PRICE £2-26** (rec. retail) P & P 10p.



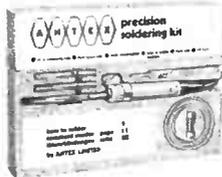**MODEL SK.2 KIT** Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, and "How to Solder" booklet. **PRICE £3-25** (rec. retail) P & P 10p.



**MODEL SK.1 KIT** Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet. **PRICE £3-48** (rec. retail) P & P 12p.



**ANTEX**

ALL PRICES include VAT at 10%

Please send the following:

Please send the ANTEX colour catalogue

I enclose cheque/P.O./Cash (Giro No. 258 1000)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PW3

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:  
**ANTEX LTD. FREEPOST PLYMOUTH PL1 1BR**  
(no stamp required) Tel 0752 67377.

# PRACTICAL WIRELESS

VOL. 49 NO. 11

ISSUE 805

MARCH 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

**EDITOR** Morris A. Colwell

**ASSISTANT EDITOR**

Lionel E. Howes, G3AYA

**ART EDITOR** Peter Metalli

**TECHNICAL EDITOR**

Eric Dowdeswell, G4AR

**PRODUCTION & NEWS**

**EDITOR** Colin R. Riches

**PROJECTS SUB-EDITOR**

Geoffrey C. Arnold

**TECHNICAL ARTIST**

Alan Martin

**SECRETARIAL**

Jenny Maunder

01-634 4292 Susan Corne

**ADVERTS. MANAGER**

01-634 4293 Roy Smith

**CLASSIFIED ADVERTS.**

01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,  
Fleetway House, Farringdon Street,  
London EC4A 4AD. Tel. 01-634 4444

## Price increase

**L**IKE many other magazines and paper products "Practical Wireless" has become victim of a world paper shortage resulting in massive increases in the cost of raw materials. In order to maintain the high standard of providing technical information and projects to our readers, we regret that we have been compelled to increase the cover price to 25p.

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

## ● NEWS & COMMENT

- 1048 SAVE MONEY—Leader article and April preview
- 1049 NEWS... NEWS... NEWS...
- 1061 TELEVISION—Coming in the March issue
- 1062 PRODUCTION LINES—Products reviewed by Colin Riches
- 1071 NEXT MONTH IN PRACTICAL WIRELESS
- 1081 HOTLINES on recent developments by Ginsberg
- 1097 ON THE AIR
- 1097 Broadcast Short Wave—Malcolm Connah
- 1098 VHF/FM—Simon David
- 1098 Medium Wave—Charles Molloy
- 1101 Amateur Bands, Short Wave/VHF—David Gibson G3JDG

## ● CONSTRUCTIONAL

- 1050 VERSATILE WAVEFORM GENERATOR—J. B. Dance, M.Sc.
- 1058 DRY BATTERY CHARGER—R. A. Butterworth
- 1065 I.C. CRYSTAL HARMONIC CALIBRATOR—J. Andrews
- 1070 FLUORESCENT LAMP UNIT—from your 12V battery—Paul Cooper
- 1072 "P.W. CRATA" Cassette Recorder and Tuner Amplifier—Richard Collin
- 1085 PRESELECTOR FOR 10-30MHz—F. G. Rayer, G3OGR
- 1094 TAKE 20 No. 58 GRIP TESTER—David Andrews

## ● OTHER FEATURES

- 1080 TECHNICROSS No. 3
- 1082 IC of the MONTH—LM377N 2+ 2W Audio Amplifier—M. J. Darby
- 1087 RADIO BY CABLE & SATELLITE
- 1088 OSCILLOSCOPE TECHNIQUES PART 1—Alan C. Ainslie


## ● EXTRA WITH THIS ISSUE

INSET P. W. DATACARDS in COLOUR

No. 7 F.M. Aerial Systems

No. 8 BBC VHF Radio Stations.

# RSC DISCO SYSTEM

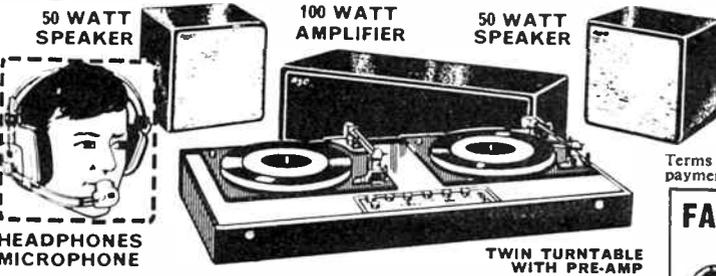

HEADPHONES  
MICROPHONE

## R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS


All types 15 Ohms covered in Rexine and Vynair  
**TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN**

**TYPE C132 30-40 WATTS** Fitted two exceptionally efficient, low feedback hifi characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £3-95 and 8 mthly payments £2-67 (Total £25-31) Carr. 65p

**TYPE C318 50 WATTS** Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £4-72 & 8 mthly pymts. Carr. 65p

**TYPE C4100 100 WATTS** Inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 58" x 18" x 10" Acoustically filled and pressurized. Terms: Dep. £22-00 & 12 mthly. pmts. £4-29 (Total £78-48). Carr. £1-50

## ALL RSC PRICES INCLUDE VAT

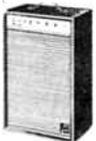

### MINSTREL 8W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: Deposit £3-95 and 8 monthly payments £2-39 (Total £23-07). Carr. free

**£19-95**

## FANE CRESCENDO SPEAKERS

Full range available at ALL BRANCHES

### FAL PHASE 50 MK.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speakers 3 to 30 ohms. Size 17" x 7" x 7" 200-250v. A.C. mains. Output 60 watts music rating. Or deposit £4-93 & 8 monthly payments £4-31. Total £44-41.



**£39-93**



### RSC PHANTOM '50'

Combined 50W Amplifier and 12in. Loudspeaker. For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £20-00 and 12 monthly payments £3-90 (Total £26-80). Carr. £1-50 SAE for leaflet



**ONLY £59-95**

### CREDIT INTEREST CHARGES REFUNDED

if account cleared in 3 months

### REGENT 50 AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.  
 \* Two extra heavy duty 12in. 50w Loudspeakers.  
 \* Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet.  
 Credit Terms: Deposit £24-50  
 A 12 monthly payments of £4-88. (Total £280-66.) Carr. £2-50



**£72-50**

### R.S.C. BATTERY/MAINS CONVERSION UNITS

**TYPE BM1.** An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v and 90v. to battery radio where A.C. mains 200/250v. 60c/ls available. Carr. 30p. **£4-15**

### R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED.

**MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.**  
 250v., 60mA, 6-3v. 2a ..... £1-10  
 250-0-250v., 60mA 6-3v. 2a ..... £1-16

**FULLY SHROUDED UPRIGHT MOUNTING**  
 250-0-250v. 60mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-55  
 250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45  
 300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45  
 300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a. £2-45  
 For Mullard 510 Amplifier ..... £2-95  
 350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45  
 350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-95  
 425-0-425v. 200mA, 6-3v. 4a., c.t., 5v. 3a. £2-45  
 425-0-425v. 200mA, 6-3v. 4a., Twice 5v. 3a. £2-80  
 450-0-450v. 250mA, 6-3v. 4a., c.t., 5v. 3a. £2-80

**TOP SHROUDED DROP-THRU TYPE**  
 250-0-250v. 70mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-49  
 250-0-250v. 100mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-71  
 250-0-250v. 100mA, 6-3v. 2a., 6-3v. 1a. £1-75  
 350-0-350v. 80mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-81  
 250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45  
 300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45  
 300-0-300v. 130mA, 6-3v. 4a., c.t., 6-3v. 1a. £2-85  
 Suitable for Mullard 510 Amplifier. .... £2-85  
 350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-45  
 300-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-85

**FILAMENT or TRANSISTOR POWER PACK**  
 Types 6-3v. 1-5a. 55p; 6-3v. 2a. 60p; 6-3v. 3a. 85p;  
 6-3v. 5a. £1 45; 12v. 1a. 61p; 12v. 3a. or 24v. 1-5a. £1-50; 0-9-18v 1 1/2a. £1-25; 0-12-25-42v 2a. £1-95.

Units listed below  
 (a) 100w POWER AMPLIFIER  
 (b) PAIR OF HI-FI HEAD- PHONES  
 (c) MATCHING DYNAMIC "MIKE" (attached to h'phone)  
 (d) PAIR 50 WATT SPEAKERS Black, Rexine covered Cabinets Size approx. 18" x 18" x 8"  
 (e) RSC TDI DISCO CONSOLE

# RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonotone or Acco Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid. See illustration on left.  
 Or Dep. £23-50 and 12 mthly pymts £4-54 (Total £77-88) Carr. £1-50

(a) (b) (c) (d) **£149-95**  
 Carr. £3-00

Terms Deposit £50 and 18 monthly payments of £7-06 (Total £177-08).

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

| 'POP' 100   | 'POP' 60   | 'POP' 50  |
|---|--|---|
| 18" 100Watt<br>14,000 gauss<br>8/15Ω                                  | 15" 60 Watt<br>14,000 gauss<br>8/15Ω                                     | 12" 50 Watt<br>13,000 gauss<br>15Ω  |
| <b>£27-50</b><br>Dep: £3-32 and 8 mthly payments £3-32 (Total £28-88) | <b>£15-75</b><br>Dep. £1-92 and 8 monthly payments. £1-92 (Total £17-28) | Dep. £1-61 and 8 monthly payments £1-61 (Total £14-49) PAIR SUITABLE ALL PURPOSES |

FOR BASS GUITAR, ELECT. ORGAN, ETC.

POP 40 10" 40W (Gauss 16,000 Imp 8/15) **£10-95** POP 55 12" 60W (Gauss 15,000 Imp 8/15) **£15-95**

## FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for use or other than Bass Guitar or Electronic Organ). Carr. free **£8-75** or Dep. £1-25 and 8 mthly payments £1-00 (Total £9-25).

## GROUP EQUIPMENT PACKAGE OFFERS


|   |        |                           |
|---|--------|---------------------------|
| F.A.L. PHASE 50 MK.III AMPLIFIER                                      | £39-93 | PACKAGE PRICE             |
| PR. FANE POP 25/2 5W L/SPEAKERS                                       | £17-50 |                           |
| Terms: Deposit £17-32 and 12 monthly payments of £3-28 (Total £27-88) | £57-43 | <b>£51-95</b> carr. £1-10 |
| F.A.L. PHASE 50 MK.III AMPLIFIER                                      | £39-93 | PACKAGE PRICE             |
| PR. FANE POP 50 L/SPEAKERS  | £28-98 |                           |
| Terms: Deposit £19-19 and 12 monthly payments of £4-00 (Total £27-99) | £68-91 | <b>£59-99</b> carr. £1-10 |
| F.A.L. PHASE 50 AMPLIFIER   | £39-93 | PACKAGE PRICE             |
| PAIR L12/20 SPEKRS (in Cabinets)                                      | £28-80 |                           |
| Terms: Deposit £20-00 and 12 monthly payments £3-90 (Total £26-80)    | £68-73 | <b>£59-99</b> carr. £2-00 |

## HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH  
**L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50**  
 Or deposit £5-95 and 8 monthly pmts. of £4-72. Total £48-71  
**L12/20 12" 20-25 WATT 13,000 Gauss 15 Ohm. Carr. £1-50**  
 L12/10 10-15 Watt veneer finish cabinet 12" 8-15 ohm. Size approx. 14" x 14" x 9". Carr. 50p. Dep. £2-25 & 8 mthly pymts £1-04 (Total £10-57)



**£37-95**  
**£8-25**

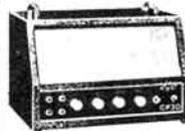

### GP30 AMPLIFIER For Guitar, Vocal or Instrumental Group

A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 8 monthly payments of £3-09 (Total £29-12).

**£25-85** Carr. 75p

### FAL TWIN CHANNEL AMPLIFIERS



Solid State. 4 sep. controlled inputs plus master volume control. Individual Bass and Treble controls. Output for speakers 3-30 ohms. Protective circuitry against damage from short circuits.

### FAL 'SUPER 50' from short circuits.

50W ATTS MUSIC RATING **£59-50**  
 Terms: Dep. £19-85 & 12 mthly. payments £3-90 (Total £26-85) Post free

### FAL 'SUPER 100'

100 WATTS MUSIC RATING. Terms: Dep. £26-65 & 12 mthly. pmts. £5-17 (Total £38-85). Prices include protective dust cover. Post free

### FAL PHASE 100/2 AMPLIFIER

100 WATTS MUSIC RATING. Solid State. Sep. Bass and Treble Controls. 4 separate controlled inputs plus master control. Output for speakers 3-30 ohms. Includes protective circuit against damage from short circuits. Terms: Deposit £23-29 & 12 monthly payments £4-54 (Total £77-77).



**£69-85** Carr. free

### SELENIUM RECTIFIERS F.W. (Bridged)

All 6/12v. D.C. output. Max. A.C. input 18v. 1a. 28p. 2a. 30p. 3a. 55p. 4a. 72p. 5a. 88p.

### SMOOTHING CHOKES

150mA, 7-10H, 250 Ω 77p. 100mA, 10H, 20 Ω 66p. 80mA, 10H, 350 Ω 55p. 60mA, 10H, 400 Ω 28p.

# HUGE DISCOUNTS

ON LEADING BRAND TAPE AND TURNTABLE UNITS

**ALL R.S.C. PRICES INCLUDE VAT**

★ FULL LABOUR AND MATERIAL GUARANTEES FOR 12 MONTHS  
LOW DEPOSIT TERMS OVER 8 MONTHS

LEAK, WHARFEDALE etc. at LOWEST Discount Prices

Prices shown correct at time of going to press 2.1.74

AKAI GXC 36D Tape Unit £71.75 (Rec. Price £99.50) Carr. £1  
AKAI 4000DS Tape Unit £69.95 (Rec. Price £97.50) Carr. £1  
AKAI 1721L Tape Unit £72.95 (Rec. Price £104.50) Carr. £1  
AKAI CR81D Tape Unit £58.95 (Rec. Price £84.10) Carr. £1  
GOLDRING GL72 T/Table & P.U. £29.95 (Rec. Price £37.29) Carr. 75p  
with Goldring G800 Cartridge worth over £10 fitted to above unit.  
GOLDRING GL75 T/Table P.U. £34.95 (Rec. Price £47.19) Carr. 85p  
with Goldring G800 Cartridge worth over £10 fitted to above unit.  
BSR MP60 T/Table & P.U. £9.95 (Rec. Price £14.95) Carr. 40p  
T/TABLES with MAGNETIC CARTRIDGE; PLINTH & COVER  
GARRARD SP25 with G800 £16.95 SPECIAL PRICE (Carr. £1)  
BSR MP60 with G800 £17.95 SPECIAL PRICE (Carr. £1)  
GARRARD AP76 with G800 £28.95 SPECIAL PRICE (Carr. £1)



## A HIGH FIDELITY 30 + 30W STEREO SYSTEM

AUDIO FIDELITY MODEL 60 AMP-LIFIER. PAIR AUDIO FIDELITY MARQUESS 30 SPEAKERS. McDONALD MP60 with G800 Cartridge Ready wired on Plinth with Cover. Send S.A.E. for leaflet.

Total Value over £165  
**£99.95**

### RSC G66 MkII 6.6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs.



COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and DIAGRAMS & INSTRUCTIONS £12.75 Carr. 40p  
Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.50 or dep. £8.75 and 8 monthly payments £1.59 (Total £15.47).

### AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plastiflored Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 8 or 8-15 ohms. PLEASE STATE CHOICE.


Exceptional performance at low cost.  
HF808T 8" 10W £2.95 HF180D 12" 15W £6.50  
HF108D 10" 10W £3.50 HF126 12" 15W £6.85  
HF120 12" 15W £4.95 HF182D 12" 15W £6.85

### FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality. In suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-16 Ω. £3.99  
PLEASE STATE IMPEDANCE REQUIRED List £4.99  
MODEL 808T 8" 15w. with parasitic Tweeter. £5.50  
Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-16 Ω. List £6.99
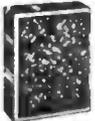
### HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 45p. per enclosure.  
JE8 Size 16" x 11" x 9". SE8 For optimum performance - results with any 8in. Hi-Fi speaker. £6.50  
8in. Hi-Fi speaker. £5.50  
SE10 For outstanding results with 10in. Hi-Fi speaker. Size 25 1/2" x 16" x 9in. Ported £6.75  
SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter £7.95



### AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. £6.50 Carr. 33p  
OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER £7.65 Carr. 39p

### R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. A.C. mains operated. Response 30-20,000 c.p.s. - 2db. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-16 ohm speakers. Max. sensitivity 5mV. Output rating I.H.F.M. Enclosed enamelled case. 9 1/2" x 2 1/2" x 5 1/2". Attractive silver finish fascia 10 1/2" x 3 1/2". matching knobs. Complete kit with full wiring diagrams and instructions. £8.50 Carr. 40p  
OR FACTORY BUILT £10.95

### AUDIO FIDELITY FR1 SPEAKER KIT

Response 30Hz-15KHz. Imp. 8-15 ohm 8" Bass Unit. Pressure Tweeter. Cross-over etc. Carr. Free  
SPECIAL NEW YEAR OFFER £15.95 Pair Carr. 45p. £10.95

### R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET Only high grade components by leading manufacturers

- Push Button Selector Switching
  - Jack Socket for Headphones
  - Neon Indicator
  - Satin Silver Finish Metal Fascia
  - Solid State Circuitry
  - Twenty Silicon Transistors
  - Four Diodes, Four Rectifiers
- Send S.A.E. for full descriptive leaflet.

R.S.C. STEREO FM III TUNER. in cabinet. Visually matches Super 30 Mk. III £37.50



For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8 Ω. Frequency Response 7 Hz to 70 KHz ± 1 1/2 db. £5 extra.  
COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £22.50  
FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 8 monthly payments £5.17 (Total £48.36). £42.50

### 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in. approx. COMPLETE KIT
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more £25 Carr. 75p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Deposit £3.71 and 8 monthly payments £3.12 (Total £28.67).



NOW SEVEN NEW BRANCHES  
BOLTON, COVENTRY  
DONCASTER, STOCKPORT  
SUNDERLAND, PRESTON  
and NOTTINGHAM

NEW LARGER PREMISES AT HULL, DARLINGTON, NEWCASTLE & DERBY



All items subject to availability. Price correct at 2.1.74 E. & O.E.


HI-FI CENTRES LTD.

### R.S.C. BRANCHES OPERATE A 5-DAY WEEK

OPEN ALL DAY SATURDAY  
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349  
BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512  
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).  
COVENTRY 17 Shelton Square, The Precinct.  
DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361  
DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs)  
EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501  
GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158  
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505  
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420  
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252  
LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 238 3573  
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

MAIL ORDERS & EXPORT ENQUIRIES TO:-  
AUDIO HOUSE, HENNONNER LANE, LEWDS. 18. Tel: Pudsey (09785) 77631.  
TERMS O.W.O. or C.O.D. No C.O.D. under £1. POSTAGE 25p EXTRA UNDER £5. 50p EXTRA OVER £5 OR AS QUOTED. TRADE SUPPLIED. S.A.E. PLEASE WITH ENQUIRIES.  
SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.  
MAIL ORDERS MUST NOT BE SENT TO SHOPS  
MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2776  
MIDDLESBROUGH 108 Newport Rd. (Closed Wed.).  
NEWCASTLE UPON TYNE 24 Nowgate Shopping Centre (Closed Wed.). Tel. 21489  
NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068  
PRESTON 41 Friargate Walk  
SHEFFIELD 13 Exchange Street (Castle Mkt. Bids.  
STOCKPORT (Closed Thurs.). Tel. 20718  
SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

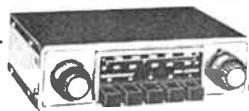


Car Radio,  
Kit K/CR-9502.



Metal  
Locator,  
Kit K/GD-348




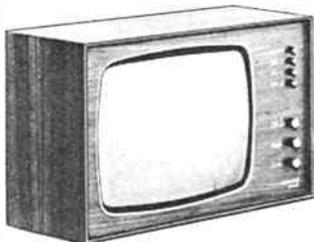Electronic  
Calculator,  
Kit K/IC-2108.



Black and White  
Portable Television,  
Kit K/GR-9900.

Hi-Fi Stereo  
Receiver,  
Kit K/AR-1214

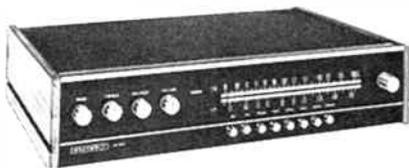

# Get the Heathkit Catalogue..and save

Handcrafted electronics with built-in quality and kit form savings.

Hundreds of models to choose from.

Heath offer you outstanding specifications and plus values that will impress you, your family and friends. Want to know more? Send for your personal introduction to the international world of Heathkit electronics... the Free Heathkit Catalogue.



## Free

Please send me the FREE Heathkit Catalogue & details of Monthly budget plans.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

HEATH

Schlumberger

HEATH (GLOS.) LTD. DEPT. PW/03/74  
Bristol Road,  
Gloucester GL2-6EE

# NEW ALL SILICON!



## PRACTICAL WIRELESS

### ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, supplied with de-luxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit .....£7.97 U.K. Post Free  
De-Luxe Kit .....£9.62 U.K. Post Free

Quantity Discounts:

|                    |         |          |         |          |
|--------------------|---------|----------|---------|----------|
| Trade and Overseas | 1-5     | Nett     | 6-9     | Less 10% |
| Enquiries Invited  | 10-49   | Less 15% | 50-99   | Less 20% |
| Mail Order Only    | 100-999 | Less 25% | 1000 up | Less 30% |

ALL PRICES INCLUDE VAT

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.

### DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ  
Tel. Walsall 34385

## ERNIE



### LEARN THE DIGITAL COMPUTER LOGIC TECHNIQUES

### A MULTIPURPOSE & MULTIRANGE ELECTRONIC DICE

Build something completely out of the ordinary. Build the fascinating MINICOMP\* the miniaturised ERNIE.

The MINICOMP employs sophisticated LOGIC techniques and brilliant NIXIE tubes to display truly RANDOM NUMBERS. At the mere touch of a button the neon numbers "WHIP" round spectacularly at high speed, before a random number within a pre-set range is selected and displayed.

**MINICOMP 100**  
Includes four range selections within 00-99.  
\* DICE : 1-6 \* ROULETTE : 00-36 \* POOLS : 00-59 \* BINGO : 00-99  
Kit includes 7 latest LOGIC I.C.'s, 3 transistors, 2 NIXIES, fibreglass P.C. board, the power supply and various other components.

**MINICOMP 1000**  
After tremendous popularity of MINICOMP 100 we are now pleased to introduce MINICOMP 1000, which has all the original features of MINICOMP 100 but in addition it provides two higher ranges:  
\* QUARTO : 000-399 \* KILO : 000-999

Kit includes 9 latest LOGIC I.C.'s, 3 transistors, 3 NIXIES, 2 P.C. boards, the power supply and various other components.

The MINICOMP is extremely easy to build as the P.C. boards are supplied with I.C.'s fully assembled and tested. The illustrated instructions include an introduction to the LOGIC techniques employed in the MINICOMP. Attractive NYLON coated and elegantly sized case, approx. 7", 4 1/2", 3" and silk aluminium panel.

**APPLICATIONS:** The MINICOMP simulates electronically all phenomenon in nature or activity in daily life with random occurrence. **RANDOM PULSE TRAINS** are found useful in medical and statistical research. **Digital LOGIC** makes possible a modern and exciting means of playing any number of **NUMBER GAMES** the human mind can conjure up.

**A PROFOUND ATTRACTION FOR PARTY GAMES, FETES, RAFFLE AND POOLS DRAWS.** A purely random selection of the draws could well contribute to your winning combination.

U.K. PRICES: Overseas and quantity prices on request.  
240V, 50 HZ. OR 110V, 60 HZ. mains operated.  
MINICOMP100, KIT: £42.50 Built & Guaranteed Units: £45.00 | All prices include V.A.T. and P&P.  
MINICOMP1000, KIT: £58.00 .. : £59.00  
TERMS: C.W.O., MAIL ORDER ONLY. \* Patent applied for.

MICROELECTRONICS **MICRO**  
51 Mexfield Road, London SW15 2RG. Tel: 01-870 2368

# THE SPECIALISTS IN QUADRAPHONIC KITS

**AVAILABLE NOW!**

THE COMPREHENSIVE KIT FOR THE

## P.W. Q4 PROJECT

SEND NOW FOR FULL DETAILS AND PRICES—SEE COUPON BELOW

FULLY COMPREHENSIVE HOME CONSTRUCTOR KITS AS SPECIFIED  
IN PRACTICAL ELECTRONICS

# P.E. RONDO

COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ (TM CBS INC.) MATRIX DECODER. COMPLETE KIT

PRE AMPLIFIER BOARD. COMPLETE KIT

MASTER VOL./TONE/4 CH. BALANCE BOARD. COMPLETE KIT

POWER AMP. BOARD & HEAT SINKS (STEREO PAIR). COMPLETE KIT

POWER SUPPLY BOARD. COMPLETE KIT

MAIN SMOOTHING CAPACITORS (2 REQUIRED) INC. CLIPS

MAINS TRANSFORMER

CHASSIS, PUNCHED & DRILLED WITH SCREENS

WOOD CASE SURROUNDING

HARDWARE PACK

CONTROL SECTION FASCIA

SUPERB 20W QUADRAPHONIC SPEAKERS TEAK OR WHITE (Please Classify)

GOLDRING G101/2 Turntable LESS CARTRIDGE (Special Introductory Offer)

DEUSCHE ELAC STS 144/17 CARTRIDGE

£8.00 Post Free + 80p V.A.T.  
Inc. CBS Licence Fee  
£3.00 Post Free + 30p V.A.T.  
£8.50 Post Free + 85p V.A.T.  
£7.50 Post Free + 75p V.A.T.  
£5.00 Post Free + 50p V.A.T.  
£0.75 Post Free + 7p V.A.T.  
£6.25 Post Free + 62p V.A.T.  
£3.25 Post Free + 32p V.A.T.  
£1.75 Post Free + 17p V.A.T.  
£2.00 Post Free + 20p V.A.T.  
£3.50 Post Free + 35p V.A.T.  
£42 per pair + £2 p & p  
+ £4.40 V.A.T.  
£23.90 Post Free + £2.39 V.A.T.  
£6.90 Post Free + 69p V.A.T.

ALL KITS ARE FULLY TO SPECIFICATION AND COMPLETE IN EVERY  
DETAIL. TRADE AND EXPORT ENQUIRIES WELCOME

## STUDIO ELECTRONICS

P.O. BOX 18,  
HARLOW, ESSEX, CM18 6SH

Telephone HARLOW 25457 (STD 0279)

| Please send me:      | Please tick box          |                              |                               |
|----------------------|--------------------------|------------------------------|-------------------------------|
| CBS SQ DECODER       | <input type="checkbox"/> | CHASSIS                      | <input type="checkbox"/>      |
| PRE AMPLIFIER BOARD  | <input type="checkbox"/> | P.W. Q4 PROJECT Full Details | <input type="checkbox"/>      |
| MASTER VOL. BOARD    | <input type="checkbox"/> | CASE                         | <input type="checkbox"/>      |
| POWER AMP. BOARD     | <input type="checkbox"/> | HARDWARE                     | <input type="checkbox"/>      |
| POWER SUPPLY BOARD   | <input type="checkbox"/> | FASCIA                       | <input type="checkbox"/>      |
| SMOOTHING CAPACITORS | <input type="checkbox"/> | TEAK/WHITE SPEAKERS PR.      | T.K. <input type="checkbox"/> |
| MAINS TRANSFORMER    | <input type="checkbox"/> |                              | W.H. <input type="checkbox"/> |
|                      |                          | GOLDRING TURNTABLE           | <input type="checkbox"/>      |
|                      |                          | ELAC CARTRIDGE               | <input type="checkbox"/>      |

MONEY ENCLOSED £ .....  
CHEQUE/P.O./MONEY ORDER

Block capitals please

NAME .....  
ADDRESS .....  
P.W.2

# TRANSFORMERS

## SAFETY MAINS ISOLATING TRANSFORMERS

Pr. 120/240 V Sec. 120 240 V Centre Tapped and Screened

| Ref. No. | VA (Watts) | Weight lb oz | Size cm.           | £     | P & P |
|----------|------------|--------------|--------------------|-------|-------|
| 07       | 20         | 1 8          | 7.0 x 6.0 x 6.0    | 2.32  | 30    |
| 149      | 60         | 3 12         | 9.9 x 7.7 x 8.6    | 3.45  | 36    |
| 150      | 100        | 5 8          | 9.9 x 8.9 x 8.6    | 3.79  | 52    |
| 151      | 200        | 8 0          | 12.1 x 11.8 x 10.2 | 6.45  | 52    |
| 152      | 250        | 13 12        | 12.1 x 11.8 x 10.2 | 8.41  | 67    |
| 153      | 350        | 15 0         | 14.0 x 10.8 x 11.8 | 11.22 | 67    |
| 154      | 500        | 19 8         | 14.0 x 13.4 x 11.8 | 16.25 | -     |
| 155      | 750        | 29 0         | 17.2 x 14.0 x 14.0 | 22.10 | -     |
| 156      | 1000       | 38 0         | 17.2 x 16.6 x 14.0 | 29.87 | -     |
| 158      | 2000       | 60 0         | 21.6 x 15.3 x 18.1 | 49.25 | -     |

PLEASE NOTE  
NEW ADDRESS  
AS BELOW

## AUTO TRANSFORMERS

| Ref. No. | VA (Watts) | Weight lb oz | Size cm.           | Auto Taps        | £     | P & P |
|----------|------------|--------------|--------------------|------------------|-------|-------|
| 113      | 20         | 1 0          | 5.8 x 5.1 x 4.5    | 0-15-210-240     | 1.22  | 22    |
| 64       | 75         | 2 4          | 7.4 x 6.7 x 6.1    | 0-15-210-240     | 2.40  | 30    |
| 4        | 150        | 3 4          | 8.9 x 7.7 x 7.7    | 0-15-200-220-240 | 2.89  | 36    |
| 66       | 300        | 6 4          | 9.9 x 9.6 x 8.6    | ..               | 5.63  | 52    |
| 67       | 500        | 12 8         | 12.1 x 11.2 x 10.2 | ..               | 8.34  | 67    |
| 84       | 1000       | 19 8         | 14.0 x 13.4 x 14.3 | ..               | 15.19 | 82    |
| 93       | 1500       | 30 4         | 17.2 x 15.9 x 14.0 | ..               | 21.99 | -     |
| 95       | 2000       | 32 0         | 17.2 x 16.6 x 14.0 | ..               | 28.70 | -     |
| 73       | 3000       | 40 0         | 21.6 x 13.4 x 18.1 | ..               | 39.17 | -     |

## CASED AUTO TRANSFORMERS

115V 500W enclosed transformer, with mains lead and two 115V outlet sockets. £9.49, P & P 67p. 20 Watt version £2.02 P & P 27p

## TRANSFORMERS

PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RAGE

| Ref. No. | Amps. 12V 24V | Weight lb oz | Size cm.           | Secondary Windings | £     | P & P |
|----------|---------------|--------------|--------------------|--------------------|-------|-------|
| 111      | 0.5-0.25      | 8            | 4.8 x 2.9 x 3.5    | 0-12V at 0.25A x 2 | 1.22  | 22    |
| 213      | 1 0           | 1 4          | 6.1 x 5.8 x 4.8    | 0-12V at 0.5A x 2  | 1.44  | 22    |
| 71       | 2 1           | 1 12         | 7.0 x 6.4 x 6.1    | 0-12V at 1A x 2    | 1.90  | 22    |
| 18       | 4 2           | 1 12         | 7.0 x 6.4 x 6.1    | 0-12V at 2A x 2    | 2.68  | 30    |
| 70       | 6 3           | 3 8          | 8.3 x 8.0 x 7.7    | 0-12V at 2A x 2    | 3.20  | 42    |
| 108      | 8 4           | 5 8          | 9.9 x 8.9 x 8.6    | 0-12V at 4A x 2    | 3.60  | 52    |
| 72       | 10 5          | 6 4          | 9.9 x 9.6 x 8.6    | 0-12V at 5A x 2    | 4.25  | 52    |
| 116      | 12 6          | 6 12         | 9.9 x 10.2 x 8.6   | 0-12V at 5A x 2    | 5.10  | 52    |
| 17       | 0 8           | 12 12        | 12.1 x 9.9 x 10.2  | 0-12V at 8A x 2    | 6.56  | 52    |
| 115      | 20 10         | 11 8         | 14.0 x 9.6 x 11.8  | 0-12V at 10A x 2   | 8.36  | 67    |
| 187      | 30 15         | 15 8         | 14.0 x 12.1 x 11.8 | 0-12V at 15A x 2   | 15.40 | 82    |
| 226      | 60 30         | 32 0         | 17.2 x 15.3 x 14.0 | 0-12V at 30A x 2   | 28.44 | -     |

## 30 VOLT RANGE

| Ref. No. | Amps. | Weight lb oz | Size cm.           | Secondary Taps    | £     | P & P |
|----------|-------|--------------|--------------------|-------------------|-------|-------|
| 112      | 0.5   | 1 4          | 6.1 x 5.8 x 4.8    | 0-12-15-20-24-30V | 1.42  | 22    |
| 79       | 1 0   | 2 4          | 7.0 x 6.7 x 6.1    | ..                | 1.92  | 36    |
| 3        | 2 0   | 3 4          | 8.9 x 7.7 x 7.7    | ..                | 2.30  | 36    |
| 20       | 3 0   | 4 8          | 9.9 x 9.6 x 8.6    | ..                | 3.58  | 42    |
| 21       | 4 0   | 6 4          | 9.9 x 9.6 x 8.6    | ..                | 4.25  | 52    |
| 51       | 5 0   | 6 12         | 12.1 x 8.6 x 10.2  | ..                | 5.30  | 52    |
| 117      | 6 0   | 8 0          | 12.1 x 9.3 x 10.2  | ..                | 6.31  | 52    |
| 88       | 8 0   | 12 0         | 12.1 x 11.8 x 10.2 | ..                | 8.18  | 67    |
| 89       | 19 0  | 13 12        | 14.0 x 10.2 x 11.8 | ..                | 10.33 | 67    |

## 50 VOLT RANGE

| Ref. No. | Amps. | Weight lb oz | Size cm.           | Secondary Taps    | £     | P & P |
|----------|-------|--------------|--------------------|-------------------|-------|-------|
| 102      | 0.5   | 1 2          | 7.0 x 6.4 x 6.1    | 0-19-25-33-40-50V | 1.90  | 30    |
| 103      | 1 0   | 2 12         | 8.3 x 7.4 x 7.0    | ..                | 2.80  | 36    |
| 104      | 2 0   | 5 8          | 9.9 x 8.9 x 8.6    | ..                | 3.87  | 42    |
| 105      | 3 0   | 6 12         | 9.9 x 10.2 x 8.6   | ..                | 5.26  | 52    |
| 106      | 4 0   | 10 0         | 12.1 x 10.5 x 10.2 | ..                | 6.99  | 52    |
| 107      | 6 0   | 12 0         | 14.0 x 10.2 x 11.8 | ..                | 10.35 | 67    |
| 118      | 8 0   | 18 0         | 17.2 x 12.7 x 11.8 | ..                | 13.51 | 97    |
| 119      | 10 0  | 25 0         | 17.2 x 12.7 x 14.0 | ..                | 16.93 | -     |

## 60 VOLT RANGE

| Ref. No. | Amps. | Weight lb oz | Size cm.           | Secondary Taps      | £     | P & P |
|----------|-------|--------------|--------------------|---------------------|-------|-------|
| 124      | 0.5   | 2 4          | 7.0 x 6.7 x 6.1    | 0-24-30-40-42.8-69C | 1.93  | 36    |
| 126      | 1 0   | 3 4          | 8.9 x 7.7 x 7.7    | ..                  | 2.70  | 36    |
| 127      | 2 0   | 6 4          | 9.9 x 9.6 x 8.6    | ..                  | 4.25  | 42    |
| 125      | 3 0   | 8 12         | 12.1 x 9.9 x 10.2  | ..                  | 6.46  | 52    |
| 123      | 4 0   | 13 12        | 12.1 x 11.8 x 10.2 | ..                  | 8.36  | 67    |
| 40       | 5 0   | 12 00        | 14.0 x 10.2 x 11.8 | ..                  | 9.85  | 87    |
| 120      | 6 0   | 15 8         | 14.0 x 12.1 x 11.8 | ..                  | 12.14 | 82    |
| 121      | 8-0   | 25 00        | 14.0 x 14.7 x 11.8 | ..                  | 13.65 | *     |
| 122      | 10-0  | 35 00        | 17.2 x 12.7 x 14.0 | ..                  | 20.09 | *     |
| 189      | 12-0  | 29 00        | 17.2 x 14.0 x 14.0 | ..                  | 22.49 | *     |

## MINIATURE TRANSFORMERS WITH SCREENS

| Ref. No. | MA         | Weight lb oz | Size cm.    | VOLTS            | £    | P & P |
|----------|------------|--------------|-------------|------------------|------|-------|
| 238      | 200        | 1 2          | 2.8x2.6x2.0 | 3-0-3            | 1.31 | 10    |
| 212      | 1A 1A      | 1 4          | 6.1x5.8x4.8 | 0-6-0-6          | 1.52 | 22    |
| 13       | 100        | 4 4          | 3.9x2.6x2.9 | 9-0-9            | 1.12 | 10    |
| 235      | 330,330    | 4 4          | 4.8x2.9x3.5 | 0-9, 0-9         | 1.52 | 10    |
| 207      | 500, 500   | 1 00         | 6.1x5.4x4.8 | 0-8-9, 0-8-9     | 2.03 | 22    |
| 208      | 1A, 1A     | 1 12         | 4.0x6.4x6.1 | 0-8, 0-8-9       | 2.73 | 30    |
| 236      | 200, 200   | 1 4          | 4.8x2.9x3.5 | 0-15, 0-15       | 1.52 | 10    |
| 214      | 300, 300   | 1 4          | 6.1x5.8x4.8 | 0-20, 0-20       | 1.60 | 22    |
| 221      | 700 (D.C.) | 1 8          | 7.0x6.1x6.1 | 20-12.0-12.20    | 1.41 | 30    |
| 206      | 1A, 1A     | 2 12         | 8.3x7.7x7.0 | 0-15-20, 0-15-20 | 3.08 | 36    |
| 203      | 500, 500   | 2 4          | 8.3x7.0x7.0 | 0-15-27, 0-15-27 | 2.82 | 38    |
| 204      | 1A, 1A     | 3 4          | 8.9x7.7x7.7 | 0-15-27, 0-15-27 | 2.86 | 38    |

PLEASE ADD 10% FOR V.A.T.  
INCLUDING P. & P.

**BARRIE electronics**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/8  
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST



for fast, easy  
reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

## EASY-TO-USE DISPENSERS



Size 5  
Savbit alloy  
18 swg, 20p (illustrated).  
Size 19A  
60/40 alloy  
18 swg, 22p  
Size 15  
60/40 alloy  
22 swg, 25p

## IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 30p



Size 12 REEL for Service Engineers and Electricians.  
18 swg  
Savbit alloy, 95p



## BIB WIRE STRIPPER AND CUTTER

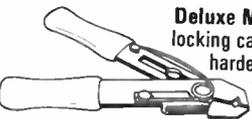

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding VAT. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to: Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

## ALL PRICES INCLUDE VAT

**BARGAIN PARCELS** 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57p p.p.; 56lb at £4.95 plus £1.37 p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

**FANTASTIC BARGAIN.** New 6 inch tubes. E450 4 B 16 4VH, medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £1.55 post paid.

**NEW HEAVY COAX CABLE** dia. 1" 70 ohms approx. 50ft. lengths £1.55, p. & p. 32p; 100 ft. lengths £2.97, p. & p. 53p.

**AERIALS.** New Condition Whip Type, 4ft, 22p; 11ft, 82p; all collapsible type. P. & p. 4ft, 10p, 11ft, 15p. New bases on adjustable clamp for the above, 67p; p. & p. 27p.

**CRYSTALS AS NEW.** Hc 6u: 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,295 Kc/s. 55p each plus 8p p.p.

**TRANSISTOR BOARDS**—consisting of transistors, diodes and resistors etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 25p. Quotations for quantity.

**OUR SELECTION OF 6-Ex. Equ. METERS** consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 27p, minimum order of six.

**AERIAL POLES** 4ft high 2" in diameter push-in type as new 75p each p. & p. 25p each minimum four.

**AERIAL MALE POSTS** approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1.10 each section. Carriage 37p each section. 1" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1.10 + 32p p.p.

**AS NEW 500ua PENNY SIZE METERS** complete with jack plus price £1.10 each, p. & p. 10p.

**COMMUNICATION RECEIVER PCRS** price £10, post paid. PCR No. 2 6 to 22 Mexs.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS

**A. H. THACKER & SONS LTD.**  
Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.





# WILMSLOW AUDIO

**THE Firm for speakers!**

## SPEAKERS

EMI 13 x 8, 3, 8 or 15 ohm  
EMI 13 x 8,150 d/c 3, 8 or 15 ohm  
EMI 13 x 8,450 t/tw 3, 8 or 15 ohm  
EMI 13 x 8 type 350 8 ohm  
EMI 6 1/2" 93850 4 or 8 ohm  
EMI 8 x 5, d /Cone Roll/s 8 ohm  
Baker Group 25 3, 8 or 15 ohm  
Baker Group 35 3, 8 or 15 ohm  
Baker De Luxe 12" d/cone  
Baker Major 12"

Kef T27  
Kef T15  
Kef B110  
Kef B200  
Kef B139  
Kef DN8  
Kef DN12  
Kef DN13

Fane Pop 100 watt 8/15 ohm £25-50  
Fane Pop 60 watt 8/15 ohm £13-00  
Fane Pop 50 watt 8/15 ohm £11-00  
Fane Pop 25/2 25 watt 8/15 ohm £6-40  
Fane Pop 15 watt 8/15 ohm £4-40  
Fane Crescendo 15" 8 or 15 ohm £27-50  
Fane Crescendo 12A 100w 8 or 15ohm £24-20  
Fane Crescendo 12B 75w bass 8 or 15 £24-20  
Fane 8077 8" d/c roll/s 8 or 15 ohm £3-85  
Fane 808T 8" d/cone 8 or 15 ohm £2-64

Goodmans Axent 100 tweeter £6-60  
Goodmans 8P 8 or 15 ohm £3-80  
Goodmans 10P 8 or 15 ohm £4-49  
Goodmans 12P 8 or 15 ohm £11-55  
Goodmans 15P 8 or 15 ohm £17-05  
Goodmans 18P 8 or 15 ohm £29-70  
Goodmans Twinaxiom 8 £6-79  
Goodmans Twinaxiom 10 £7-61

Elac 9 x 5 5" S9RM109 15 ohm, £2-53  
S9RM114 8 ohm

Elac 6 1/2" d/c roll/s 8 ohm £3-22  
Elac 6 1/2" d/cone 8 ohm £2-59  
Elac 4" tweeter TW4 £1-21

Wharfedale Super 10 R5/DD £9-80

Coral 6 1/2" d/cone roll/s 8 ohm £2-42

Siran 6 1/2" 3 or 8 ohm £1-44

Richard Allan 12" d/c 3 or 15 ohm £2-20  
10" x 6" 3, 8 or 15 ohm £1-92

8" x 5" 3 or 8 ohm £1-38

7" x 4" 3 or 8 ohm £1-38

2 1/2" 64 ohm or 70 mm 80 ohm £0-65

Adastr Hiten 10" 10w 8 or 15 ohm £2-80

Eagle DT33 dome tw. £5-45

Eagle HT15 tweeter £3-66

Eagle CT5 tweeter £1-25

Eagle CT10 tweeter £2-54

Eagle MHT10 tweeter £3-74

Eagle FR4 £4-45

Eagle xover CN23, 28, 216 £1-10

Sp. matching transformer 3-15 ohm £1-10

Celestion MF1000 25w horn 8 or 15 ohm £10-45

Celestion P58 (for Unilex) £2-16

Celestion G12M 8 or 15 ohm £12-00

Celestion G12H 8 or 15 ohm £15-00


Celestion G15C 8 or 15 ohm £24-00

Celestion G18C 8 or 15 ohm £33-00

Car Stereo speakers—ask for leaflet.
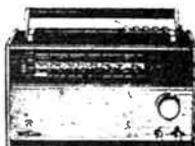
## SPEAKER KITS

Wharfedale Linton 2 £8-75  
Wharfedale Glendale 3 £15-75  
Wharfedale Dovedale 3 £24-25  
Richard Allan Twinkit £7-95  
Richard Allan Triple 8 £11-75  
Richard Allan Triple Assem. £17-50  
Richard Allan Super Triple £20-75  
Goodmans DIN 20 £8-58  
Fane Mode One £9-00  
Kefkit 2 £25-75  
Kefkit 3 £35-50  
Peerless 2-8 £5-50  
Peerless 10-2 £8-47  
Peerless 20-2 £10-41  
Helme XLK 25 (Pair) £18-17  
Helme XLK 50 (Pair) £37-18  
Stephenspeaker kits and cabinets—send for free booklet "Choosing a Speaker".  
Prices include VAT.  
Carriage and insurance 75p per kit.



## RADIOS/CASSETTES/AMPS.

Grundig Mariner TR865 £32-00  
Grundig Elite Boy 500 £27-00  
Grundig Melody Boy 500 £27-00  
Grundig Melody Boy 1000 £38-75  
Grundig Yacht Boy 210 £34-25  
Grundig RF430 mains £27-00  
Grundig RF310 mains £22-75  
Grundig RF310 £21-25  
Grundig Top Boy £16-75  
Grundig Satellit 1000 £121-00  
Grundig C402 cassette £27-00  
Grundig Signal 500 £27-00  
Grundig C230 Cassette £28-00  
Tandberg TP41 £42-00  
BASF 9301 radio/cassette £64-00  
Bush VTR178 5 Band (Inc. Air) £29-00  
Trio KA2000A £33-00  
Trio KA2002 £41-00  
ITT Colt £9-95  
ITT/KB Golf Preset £21-25  
ITT/KB Weekend Auto £16-00  
ITT/KB Europa £18-00  
ITT/KB SL53 cassette £22-82  
ITT/KB Studio 73 stereo cassette £44-00  
Koyo KTR1664 8 waveband £40-00  
Koyo KRT 1770 11 waveband £56-50  
Koyo KTR1883 5 Band (Inc. Air) £23-50  
Tec C200 Radio/Cassette £31-00

Prices include VAT.  
Carriage and insurance 75p. FREE with each radio—"World Radio Stations Book"

## PA/DISCO AMPLIFIERS

Carriage and insurance £1-00  
Baker 100 Watt £40-00  
Linear 30/40 £25-00  
Linear 40/60 £30-00  
Linear 80/100 £55-00

## SINCLAIR CALCULATORS

Subject to the maker's full guarantee. An incomparably fast and comprehensive after sales service is provided by Sinclair's famous service department.

Cambridge Kit £23 95 (£3 00)  
Cambridge Assembled £25 95 (£3 00)  
Executive £33 95 (£3 70)  
Executive Memory £39 95 (£4 40)

## FERRANTI ZN414

Fabulous integrated circuit radio chip supplied with instructions £1 20 (23p). Also available a kit of parts to construct a MW and LW radio. Send sae for free leaflet.

## SINCLAIR EQUIPMENT



Z40 £4 25 (63p) Project 605 £18 95 (£2 30)  
Z60 £5-38 (74p) Stereo 80 Pre-amp £9 43 (£1-05)  
Q18 £5-90 (75p) Project 80 Tuner £8 95 (£1-10)  
P25 £3 47 (57p) Project 80 Decoder £5-49 (77p)  
P26 £5-95 (99p) Project 80 AFU £5-38 (74p)  
P28 £6-20 (84p) Trans for P28 £2-95 (50p)

## SINCLAIR SUPER IC12

6W rms power with 44 page booklet and printed circuit £2-10 (43p)



## SWANLEY IC TOMORROW £2-60 (47p)

The world's most powerful IC amplifier. Similar appearance to the IC12 but rated at 10W rms power. Supplied with data but no printed circuit board.

## BATTERY ELIMINATOR BARGAIN

£3-75 (60p)

The most versatile battery eliminator ever offered. Switched output of 3V, 4.5V 6V, 7.5V, 9V and 12V at 500mA.




Other eliminators stocked  
50 mA unless stated—  
4 1/2V £1-50 (30p); 6V £1-50 (30p); 9V £1-50 (30p);  
7 1/2V cassette type £2-25 (30p); Ooubie 4 1/2V £2-50 (32p); Ooubie 6V + 6V £2-50 (35p); Ooubie 9V + 9V £2-50 (35p).

## IC RADIO CHIP TBA651 £2-10 (32p)

The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2-10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1-75 (29p).
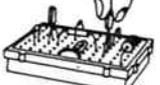
## S-DECS AND T-DECS

S-DECS £1-98 (31p)  
T-DECS £3-63 (41p)  
μ-DEC A £3-99 (51p)  
μ-DEC B £6-99 (81p)  
16 dil IC carriers £1-77 (25p)



## DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-55 (26p). Stereo model with balance control £3-50 (46p).

## IC12 POWER KIT

Supplies 28V 0-5 Amps £2 47 (50p)

## LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1-10 (27p). 5" x 8" ohm £1-55 (37p).

## PREAMPLIFIER KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1-30 (24p). Stereo model £2-30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1-20 (23p).

## SENO SAE FOR FREE LEAFLET ON KITS

## ECONOMICAL QUADRAPHONICS

Eagle AA10 Quadraphonic Synthesizer. Complete, self-contained matrix system in attractive cabinet. Just feed ordinary 2 channel stereo into it and connect outputs to 4 loudspeakers to obtain the latest experience in sound, 35 watts rms/channel.

## SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome. Mail order only. No callers, please.

No vat on overseas orders which are most welcome.

**FREE with speaker orders over £7**

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 35p per speaker (tweeters and crossovers 20p)

ALL PRICES QUOTED INCLUDE V.A.T.

**WILMSLOW AUDIO Dept. P.W.**

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

# C. T. ELECTRONICS

267 ACTON LANE, LONDON  
W4 5DG 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

## SEMICONDUCTORS

|        |       |        |       |          |       |        |       |         |       |        |       |
|--------|-------|--------|-------|----------|-------|--------|-------|---------|-------|--------|-------|
| AC107  | 35p   | BCY30  | 40p   | MJ340    | 55p   | OC36   | 65p   | TIP36C  | £4.10 | 2N2398 | 70p   |
| AC125  | 25p   | BCY31  | 55p   | MJ481    | 95p   | OC42   | 40p   | TIP41C  | 95p   | 2N2646 | 50p   |
| AC126  | 25p   | BCY32  | 95p   | MJ2801   | £1.25 | OC44   | 20p   | TIP42C  | £1.10 | 2N2846 | £1.50 |
| AC127  | 27p   | BCY33  | 45p   | MJ2901   | £2.20 | OC45   | 20p   | TIS50   | 15p   | 2N2904 | 25p   |
| AC128  | 28p   | BCY34  | 60p   | MJE370   | 75p   | OC71   | 17p   | ZTX300  | 15p   | 2N2905 | 25p   |
| AC176  | 27p   | BCY38  | 65p   | MJE370   | 75p   | OC71   | 17p   | ZTX300  | 15p   | 2N2906 | 25p   |
| AC177  | 25p   | BCY39  | £1.00 | MJE371   | 90p   | OC72   | 20p   | ZTX500  | 16p   | 2N2907 | 25p   |
| AC181  | 30p   | BCY55  | £1.60 | MJE520   | 65p   | OC75   | 25p   | ZTX501  | 20p   | 2N2926 | 12p   |
| AC190  | 30p   | BCY70  | 22p   | MJE2955  | £1.95 | OC76   | 25p   | ZTX504  | 50p   | 2N3053 | 25p   |
| AC192  | 20p   | BD121  | 75p   | MM1172   | 50p   | OC81   | 25p   | ZTX531  | 30p   | 2N3054 | 65p   |
| AD140  | 80p   | BD123  | 75p   | MPI102   | 45p   | OC83   | 25p   | IN659   | 8p    | 2N3055 | 25p   |
| AD149  | 65p   | BD124  | 80p   | MPI103   | 45p   | OC139  | 30p   | IN916   | 8p    | 2N3232 | 70p   |
| AD161  | 40p   | BD131  | 75p   | (2N5457) | 35p   | OC140  | 30p   | IN4001  | 8p    | 2N3702 | 14p   |
| AD162  | 40p   | BD132  | 75p   | MPI104   | 45p   | OC170  | 25p   | IN4002  | 8p    | 2N3703 | 12p   |
| AD211  | £1.80 | BD153  | 75p   | (2N5458) | 35p   | OC171  | 30p   | IN4003  | 8p    | 2N3704 | 12p   |
| AF114  | 25p   | BD156  | 75p   | MPI105   | 45p   | OC200  | 50p   | IN4004  | 10p   | 2N3706 | 12p   |
| AF115  | 25p   | BDY11  | £1.40 | (2N5459) | 35p   | OC201  | 60p   | IN4005  | 12p   | 2N3707 | 12p   |
| AF116  | 25p   | BDY17  | £1.60 | MPS A06  | 35p   | OC202  | 75p   | IN4006  | 15p   | 2N3708 | 12p   |
| AF117  | 25p   | BDY19  | £1.95 | MPS A16  | 30p   | TIP29A | 49p   | IN4007  | 18p   | 2N3709 | 12p   |
| AF118  | 60p   | BF152  | 20p   | MPS A56  | 35p   | TIP30A | 58p   | IN4148  | 7p    | 2N3712 | £2.75 |
| AF172  | 30p   | BF194  | 14p   | MPS O06  | 75p   | TIP31A | 62p   | 2N696   | 25p   | 2N3712 | £2.75 |
| AS221  | 80p   | BF195  | 15p   | MPS O56  | 70p   | TIP32A | 74p   | 2N697   | 20p   | 2N3773 | £2.95 |
| BA102  | 33p   | BFX84  | 30p   | NKT135   | 35p   | TIP33A | £1.05 | 2N698   | 25p   | 2N3819 | 35p   |
| BA112  | 50p   | BFX85  | 30p   | NKT221   | 25p   | TIP34A | £1.55 | 2N706   | 12p   | 2N3820 | 55p   |
| BA114  | 18p   | BFX86  | 30p   | NKT404   | 80p   | TIP36A | £2.65 | 2N708   | 15p   | 2N3866 | 85p   |
| BA156  | 15p   | BFX88  | 30p   | NKT773   | 30p   | TIP41A | 75p   | 2N930   | 20p   | 2N3904 | 22p   |
| BC107  | 12p   | BFY10  | 35p   | NKT774   | 30p   | TIP42A | 90p   | 2N132   | 25p   | 2N4058 | 12p   |
| BC108  | 12p   | BFY14  | 50p   | OA5      | 20p   | TIP29B | 58p   | 2N1302  | 16p   | 2N4059 | 12p   |
| BC109  | 12p   | BFY50  | 25p   | OA10     | 20p   | TIP30B | 66p   | 2N1303  | 16p   | 2N4060 | 12p   |
| BC147  | 12p   | BFY51  | 25p   | OA47     | 10p   | TIP31B | 70p   | 2N1304  | 25p   | 2N4061 | 12p   |
| BC148  | 12p   | BFY52  | 25p   | OA70     | 12p   | TIP32B | 82p   | 2N1305  | 25p   | 2N4126 | 17p   |
| BC149  | 12p   | BFY53  | 25p   | OA79     | 12p   | TIP33B | £1.12 | 2N1306  | 25p   | 2N4285 | 15p   |
| BC153  | 15p   | BFY90  | 66p   | OA81     | 10p   | TIP41A | £1.68 | 2N1307  | 25p   | 2N4287 | 15p   |
| BC157  | 14p   | BSW43  | 65p   | OA90     | 10p   | TIP35B | £2.81 | 2N1308  | 25p   | 2N4288 | 15p   |
| BC158  | 15p   | BSW68  | 80p   | OA91     | 10p   | TIP36B | £3.64 | 2N1309  | 25p   | 2N4289 | 15p   |
| BC159  | 15p   | BSY95A | 12p   | OA200    | 10p   | TIP41B | 83p   | 2N1613  | 25p   | 2N4290 | 15p   |
| BC169C | 14p   | C111   | 50p   | OA202    | 10p   | TIP42B | 98p   | 2N1711  | 25p   | 2N4444 | £1.90 |
| BC182  | 14p   | CA26   | 40p   | OA210    | 35p   | TIP29C | 71p   | 2N2147  | 70p   | 2N4671 | 35p   |
| BC183  | 14p   | BY100  | 15p   | OA211    | 35p   | TIP34B | £1.68 | 2N2150  | 70p   | 2N4920 | 60p   |
| BC184  | 14p   | BY122  | 65p   | OC19     | 85p   | TIP31C | £5.05 | 2N2217  | 25p   | 2N5191 | 96p   |
| BC212  | 14p   | BY125  | 65p   | OC19     | 85p   | TIP32C | £1.05 | 2N2218  | 25p   | 2N5194 | £1.10 |
| BC213  | 14p   | BY127  | 20p   | OC22     | 55p   | TIP33C | £1.30 | 2N2219  | 25p   | 40360  | 50p   |
| BC214  | 14p   | BY164  | 65p   | OC26     | 65p   | TIP34C | £1.90 | 2N2220  | 25p   | 40361  | 50p   |
| BC238  | 12p   | IS100  | 15p   | OC28     | 65p   | TIP35C | £3.20 | 2N2222A | 25p   | 40362  | 55p   |
| BC239  | 12p   | IS103  | 20p   | OC35     | 65p   |        |       |         |       |        |       |

|                |                            |         |         |        |         |              |         |              |       |
|----------------|----------------------------|---------|---------|--------|---------|--------------|---------|--------------|-------|
| <b>DIGITAL</b> | <b>INTEGRATED CIRCUITS</b> | SN7491A | SN74145 | £1.50  | SN74176 | £1.60        |         |              |       |
| SN7400         | 20p                        | SN7422  | 48p     | SN7450 | 20p     | SN74150E3-35 | SN74177 | £1.00        |       |
| SN7401         | 20p                        | SN7423  | 48p     | SN7451 | 20p     | SN74151      | £1.10   | SN74180      | £1.55 |
| SN7402         | 20p                        | SN7425  | 48p     | SN7453 | 20p     | SN74153      | £1.35   | SN74181      | £7.00 |
| SN7403         | 20p                        | SN7427  | 42p     | SN7454 | 20p     | SN74154      | £2.00   | SN74182      | £2.00 |
| SN7404         | 20p                        | SN7428  | 50p     | SN7460 | 20p     | SN74155      | £1.55   | SN74184      | £2.45 |
| SN7405         | 20p                        | SN7430  | 20p     | SN7470 | 30p     | SN74156      | £1.55   | SN74185A     | £2.40 |
| SN7406         | 30p                        | SN7432  | 42p     | SN7472 | 30p     | SN74157      | £1.80   | SN74186      | £2.40 |
| SN7407         | 30p                        | SN7433  | 70p     | SN7473 | 40p     | SN74100      | £2.50   | SN74190      | £1.85 |
| SN7408         | 20p                        | SN7437  | 65p     | SN7474 | 40p     | SN74104      | £1.45   | SN74191      | £1.95 |
| SN7409         | 45p                        | SN7438  | 65p     | SN7475 | 55p     | SN74105      | £1.45   | SN74192      | £2.00 |
| SN7410         | 20p                        | SN7440  | 20p     | SN7476 | 45p     | SN74107      | 80p     | SN74193      | £2.00 |
| SN7411         | 23p                        | SN7441  | AN75p   | SN7478 | 80p     | SN74110      | 80p     | SN74194      | £2.50 |
| SN7412         | 42p                        | SN7442  | 75p     | SN7481 | £1.25   | SN74118      | £1.00   | SN74195      | £1.85 |
| SN7413         | 30p                        | SN7443  | £1.00   | SN7482 | 37p     | SN74119      | £1.90   | SN74196      | £1.85 |
| SN7413         | 30p                        | SN7445  | £2.00   | SN7483 | £1.00   | SN74121      | 95p     | SN74197      | £1.50 |
| SN7416         | 30p                        | SN7446  | £2.00   | SN7484 | 90p     | SN74122      | £1.35   | SN74198      | £4.60 |
| SN7417         | 20p                        | SN7447  | £1.75   | SN7486 | 45p     | SN74123      | £2.70   | SN74199      | £4.60 |
| SN7420         | 20p                        | SN7448  | £1.75   | SN7490 | 75p     | SN74145      | £1.50   | SN74199E4-60 |       |

|               |                 |       |
|---------------|-----------------|-------|
| <b>S.C.R.</b> | <b>TRIACS</b>   |       |
| BTY79400R     | SC40D 8A, 400V  | £1.00 |
| CRS 1/05      | SC40E 6A, 500V  | £1.20 |
| CRS 1/10      | SC45D 10A, 400V | £1.25 |
| CRS 1/20      | SC45E 10A, 500V | £1.45 |
| CRS 1/40      | SC50S 15A, 500V | £1.85 |
| CRS 3/035     | 40430 6A, 400V  | 85p   |
| CRS 3/40      | DIAC            | 25p   |
| CRS 3/60      |                 |       |
| CRS 7/400     |                 |       |
| CRS 7/600     |                 |       |
| CRS 16/100    |                 |       |
| CRS 16/200    |                 |       |
| CRS16/600     |                 |       |
| C106D         |                 |       |
| TIC 44        |                 |       |
| 16RC/20       |                 |       |
| 2N3525        |                 |       |

|                        |       |
|------------------------|-------|
| <b>LINEAR OP. AMPS</b> |       |
| 709C TO99/DIL          | 40p   |
| 723C TO99/DIL          | £1.05 |
| 741C DIL               | 50p   |
| 747C TO99/DIL          | £1.10 |
| 72748P DIL             | 65p   |
| 723C TO99              | £1.05 |
| CA3014                 | £1.55 |
| CA3018                 | £1.00 |
| CA3028                 | £1.20 |
| CA3036                 | £1.00 |
| CA3046                 | £0.95 |
| CA3048                 | £2.34 |
| CA3075                 | £1.60 |
| CA3090Q                | £4.85 |
| MCI303L                | £1.85 |
| MFC4000D               | 35p   |
| MFC4000B               | 50p   |
| EL400P DIL             | £1.50 |
| ZN414                  | £1.25 |
| LM309K                 | £1.90 |
| TAD 100                | £1.90 |
| TOKO FILTER            | 45p   |
| TAD 110                | £2.00 |

|                               |           |
|-------------------------------|-----------|
| <b>LOW COST OSCILLOSCOPES</b> |           |
| Cossor                        | Solartron |
| 1035 D.B.                     | CD643.1   |
| 1049 Mk. 3A                   | CD711S.2  |
| D.B.                          |           |
| 1049 Mk.4                     | EMI       |
| D.B.                          | WM2       |
| Solartron                     | WM3B      |
| AD557                         | WM7       |
| CD513.2                       | WM8       |
| CD523 S.2                     | WM16      |
| CD643                         | WM18      |
|                               | WM26      |

All prices and details on application, phone 01-994 6275. Inspection welcome—call at warehouse.

**V.A.T.**  
Unless otherwise stated all prices are EXCL. V.A.T. Please add 10% to all orders. Carriage: orders under £5 + 20p. Over £5 post free.

|                          |     |
|--------------------------|-----|
| <b>BRIDGE RECTIFIERS</b> |     |
| BY122 1.5A 40V           | 40p |
| BY164 1.4A 200V          | 57p |
| CZC-100 2A 100V          | 39p |
| 6A 100V                  | 65p |
| <b>GENER DIODES</b>      |     |
| BZY88 Series 400mW       |     |
| 3-3-33V 5%               | 15p |
| 1-5 watt range           | 25p |
| 10 watt range            | 45p |
| <b>L.E.D.</b>            |     |
| TIL 209 H.P.5082         | 28p |
| <b>L.D.R.</b>            |     |
| ORP12                    | 50p |

## WAREHOUSE

20-24 BEAUMONT ROAD, W.4.  
SURPLUS COMPONENTS, TEST EQUIPMENT, etc. etc.

**THOUSANDS OF BARGAINS**  
Test Equipment ★ Oscilloscopes ★ Signal Generators ★ Counters  
Cabinets ★ Bridges ★ Meters ★ Transmitters ★ Receivers ★ Power  
Supplies ★ Laboratory Equipment ★ Galvanometers ★ Audio Equipment  
★ Video Equipment ★ Meters ★ Battery Chargers ★ Motors etc. ★ etc.

**20 TONS OF ELECTRONIC EQUIPMENT**  
Resistors ★ Relays ★ Capacitors ★ Switches ★ Transformers ★ Meters  
★ Potentiometers ★ Component Panels ★ Semiconductors ★ Cable ★  
Values ★ etc. ★ etc. ★ etc.  
Regret no flats available. Personal callers only. Cash and Carry only.

## AUDIO ACCESSORY SHOP

17, TURNHAM GREEN, TERRACE,  
CHISWICK W4.  
**VALVE AMPLIFIERS**

|         |        |          |         |
|---------|--------|----------|---------|
| 5 Watt  | £12.50 | 50 Watt  | £36.25  |
| 15 Watt | £24.50 | 150 Watt | £75.90  |
| 30 Watt | £29.50 | 500 Watt | £124.50 |

**TRANSISTOR AMPLIFIERS**  
FAL Phase 50W ..... £39.93 FAL Phase 100W ..... £69.95

**DISCO CONSOLES**  
FAL Disco Mk 2 ..... £82.99 FAL Power Disco ..... £123.75  
(with 70W RMS Amp)

**HEAVY DUTY LOUDSPEAKERS**  
★ SPECIAL OFFER PRICE ★  
Decca 8in 10 watt Hi-Fi speaker, plus matching tweeter £7.50 complete  
Suitable 2 way Xover ..... £1.21  
15in. 70W E.M.I. 8 ohm ..... £19.50  
40362

**DISCO LIGHTING**  
Sound-lighting module ..... £7.90  
3 channel sound-light ..... £22.50  
Oilwheel 6in dia. .... £5.25  
Suitable 1rpm motor ..... £1.00  
Strobe 4 Joule ..... £25.00  
Single flash box ..... £7.50  
(100W Red, Blue, Gn. Yel.)  
Triple flash box ..... £16.25

**TEAK VENEERED SPEAKER CABINETS**  
For 8 x 5in speaker ..... £3.50 each  
For 8in. + Tweeter ..... £5.00 each  
For 13 x 8in. .... £6.50 each  
For 12in. + Tweeter ..... £9.90 each

ALSO: Audio Connecting Leads, Tape, Cassettes, Stereo Systems, Mixers, Mic. Stands, Speaker Cloth, Turntables, Plyths, Covers, etc. etc.


## ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

|                   |  |
|-------------------|--|
| <b>SGS EA1000</b> | <b>Pack No.</b>  |
| 3W AMPLIFIER      | 1 500 Carbon resistors, 1, 1/2, 2 watt                     |
| MODULE £2.45.     | 2 100 Electrolytic Condensers                              |
| Handbook 10p      | 3 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers  |
|                   | 4 250 Polyester, Polycarbonate, Paper, etc., Condensers    |
|                   | 5 25 Potentiometers, assorted                              |
|                   | 6 250 High-stab, 1%, 2%, 5% resistors.                     |
|                   | 7 50 Assorted Tagstrips                                    |
|                   | 8 11b Assorted nuts, bolts, washers, spacers, etc.         |
|                   | 9 25 Assorted switches, rotary, lever, micro, toggle, etc. |
|                   | 10 50 Preset Potentiometers.                               |
|                   | <b>ALL COMPONENTS NEW AND UNUSED</b>                       |
|                   | £1 + 25p p.p. per pack, £5 for 5 packs p/free.             |

## TEST EQUIPMENT

|   |      |
|---|------|
| TEKTRONIX Type 109 Pulse Generator                        | £75  |
| H P Transfer Oscillator, 540B, 100-200 MHz                | £100 |
| H P Sweep Oscillator, HO1-686C, 7-11 GHz                  | £120 |
| H P Sweep Oscillator, 684C, 4-8 GHz                       | £150 |
| MARCONI VHF-SHF Signal Generator, TF 105B                 | £200 |
| <b>KLYSTON POWER SUPPLIES</b>                             |      |
| Large selection in stock. £20 each.                       |      |
| PYE LING Automatic Cycling Oscillator, A.C. 0-1, 5Hz-5LHz | £50  |
| MARCONI TF 1400 Double Pulse Generator                    | £85  |
| CINTEL 1873 Square Wave and Pulse Generator               | £59  |

# R T V C

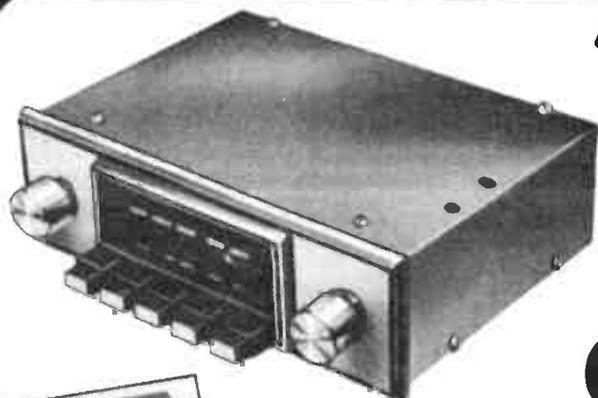

## BUILD YOUR OWN TOURIST PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
- 2.) Integrated circuit output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.

Size Chassis 7 ins. wide, 2 ins. high and 4 1/4 ins. deep approx.

## Remember! one of the Top Ten Accessory Awards from Motor magazine

# PUSH BUTTON CAR RADIO KIT

*NOTE:* The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p.free with kit.

### Car Radio Kit

£6.60 + 55p. postage & packing.


Speaker including baffle and fixing strips

£1.65 + 23p. postage & packing.

Recommended Car Aerial - fully retractable and locking.

£1.35 post paid.

## STEREO 21

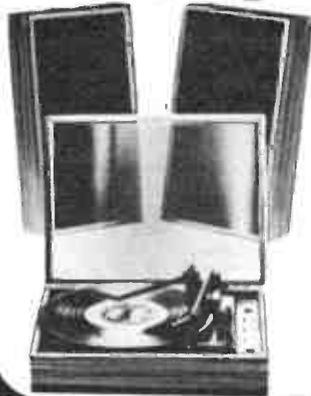

## QUALITY SOUND FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit. - no soldering required. Includes:-

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two 8" 5" speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded:-

Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8-15 ohms.

Stereo headphone socket with automatic speaker cutout.

Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx.

15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6". Complete only £18.45. 16p. p & p

Extras if required. £1.37

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. £3.85.



## DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs \*5 Electrically Mixed Inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling.

- 1) Crystal Mic or Guitar 9mV.
- 2) Moving coil Mic or Guitar 8mV.
- 3), 4), 5) Medium output equipment (Gram, Tuner, Monitor, Organ, etc.) - all 250mV sensitivity.

Size approx. 12 1/2 ins x 6 ins x 3 1/2 ins

£13.50 + 60p. postage & packing.



## 8 TRACK CARTRIDGE PLAYER

Elegant self selector push button player for use with your own stereo system. Compatible with Viscount III system, the Stereo 21 and the Unisound module. Technical specification.

Mains input. 240V. Output sensitivity 125mV

Comparable unit sold elsewhere at £24.00 approx.

Yours for only £10.60 + 90p. p & p



## BUILD YOUR OWN STEREO AMPLIFIER

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.

£7.64 + 55p. p & p

## PE TAPE LINK CONSTRUCTORS



A suitable 3 speed tape deck, less heads. Caters up to 5 1/2 ins. spools. 240V AC mains.

Unused but store soiled hence no warranty. £4.00 + £1.00 p & p



**£49-00**

**40 Watt Amplifier.**  
**Viscount III - R102** now 20 watts per channel.  
**System I** includes:  
**Viscount III amplifier** - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket  
**Specification**  
 20 watts per channel into 8 ohms  
 Total distortion @ 10W @ 1kHz 0.1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within 1dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power).  
 Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: 12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble 12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.  
 Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 1/2" x 9" x 3 1/2".  
**Garrard SP. 25 Mk III deck** with magnetic cartridge, plinth and cover.  
**Two Duo Type II matched speakers** - Enclosure size approx. 17" x 10 1/2" x 6 1/2" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. **Complete System £49-00**


**£65-00**

**System II**  
**Viscount III amplifier** (As System I)  
**Garrard SP. 25 Mk III deck** (As System I)  
**Two Duo Type III matched speakers**  
 Enclosure size approx. 23" x 11" x 9"  
 Finished in teak veneer. Drive units approx. 13" x 8" with 3" HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.  
**Complete System £65-00**

**PRICES: SYSTEM 1**  
 Viscount III R102 amplifier £24 20 £1 p 8 p  
 2 Duo Type II speakers £14 00 £2 20 p 6 p  
 Garrard SP25 Mk III with  
 MAG cartridge plinth & cover £18 00 £1 75 p 6 p  
 total £56 20  
 Available complete for only **£49 00 £3 50 p 6 p.**

**PRICES: SYSTEM 2**  
 Viscount R102 amplifier £24 20 £1 p 8 p  
 2 Duo Type III speakers £32 00 £3 30 p 6 p  
 Garrard SP25 Mk III with  
 MAG cartridge plinth & cover £19 00 £1 75 p 6 p  
 total £74 20  
 Available complete for **£65 00 £4 p 6 p.**
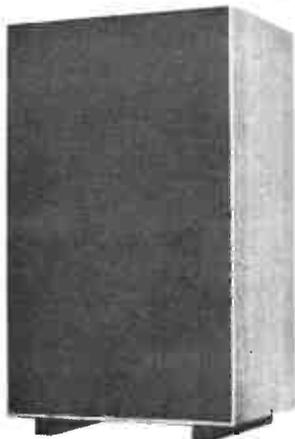
## THE ULTIMATE COMPLETE SPEAKER SYSTEM EMI LE 315



Recommended retail selling price, £86-00.

**Our price £45-00 + £3.50 postage & packing.**

A professional standard five way speaker system with enclosure giving top quality performance.

**Enclosure Dimensions** approx. (3ft. x 2ft. x 1ft.).

**Drive Units**

Hand built - 15" diameter bass with 3" voice coil, - two 5" diameter Mid Range units, - two 3 1/2" HF. units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.

**Powder Handling**

Continuous rating 35 W rms., Peak power rating 70 W.

**Frequency Response** 20 Hz 20,000 Hz.

## EMI SPEAKERS FANTASTIC REDUCTION



**15" 14A/780.** Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price **£40-80.**

**OUR PRICE £18-70 + £1-50 p & p**



**950 Kit** - Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

**Huge 19" 14** (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price **£44 00.**

**OUR PRICE £25-00 + £1-50 p & p Special Offer.**



Just write your order giving your credit card number

**DO NOT SEND YOUR CARD**

- Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.

- Leaflets available for all items listed.\* Send stamped addressed envelope.

\*No leaflet available on Reliant Mk IV Mono amplifier



Radio and TV Components (Acton) Ltd.  
**21 High Street, Acton, London W3 6NG**  
**323 Edgware Road, London W2**  
 Edgware: 9 a.m.-5.30 p.m. Half day Thurs.  
 Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

**SPECIAL OFFER !!!**

**SMALL ELECTROLYTICS**

| Ref. No. | Capacity | Voltage | Price | Ref. No. | Capacity | Voltage | Price |
|----------|----------|---------|-------|----------|----------|---------|-------|
| H8/1     | 1μF      | 150V    | 4p    | H7/4A    | 64μF     | 35V     | 5p    |
| H8/1A    | 2μF      | 150V    | 4p    | H7/5     | 80μF     | 16V     | 4p    |
| H8/2     | 2.2μF    | 25V     | 4p    | H7/6     | 100μF    | 25V     | 5p    |
| H8/2A    | 3-3μF    | 25V     | 4p    | H7/7     | 100μF    | 25V     | 4p    |
| H8/3     | 3μF      | 50V     | 4p    | H7/8     | 125μF    | 16V     | 4p    |
| H8/3A    | 4μF      | 50V     | 4p    | H7/8A    | 100μF    | 35V     | 6p    |
| H8/4     | 4.7μF    | 25V     | 4p    | H7/9     | 100μF    | 63V     | 6p    |
| H8/4A    | 6μF      | 64V     | 4p    | H7/9A    | 125μF    | 4V      | 4p    |
| H8/5     | 5μF      | 10V     | 4p    | H7/10    | 150μF    | 2-5V    | 3p    |
| H8/5A    | 5μF      | 150V    | 4p    | H7/11    | 160μF    | 25V     | 6p    |
| H8/6A    | 10μF     | 10V     | 4p    | H7/11A   | 150μF    | 16V     | 5p    |
| H8/7     | 10μF     | 70V     | 4p    | H7/13A   | 200μF    | 25V     | 8p    |
| H8/7A    | 16μF     | 35V     | 4p    | H7/14    | 220μF    | 50V     | 10p   |
| H8/8     | 16μF     | 35V     | 4p    | H7/14A   | 220μF    | 16V     | 6p    |
| H8/8A    | 16μF     | 16V     | 4p    | H7/15    | 220μF    | 25V     | 6p    |
| H8/9     | 20μF     | 6V      | 2p    | H7/15A   | 220μF    | 35V     | 10p   |
| H8/9A    | 20μF     | 70V     | 4p    | H6/1     | 250μF    | 4V      | 3p    |
| H8/10    | 22μF     | 50V     | 4p    | H5/3A    | 320μF    | 2-5V    | 3p    |
| H8/10A   | 22μF     | 100V    | 4p    | H6/4     | 320μF    | 10V     | 4p    |
| H8/11    | 25μF     | 12V     | 4p    | H6/4A    | 330μF    | 16V     | 5p    |
| H8/11A   | 24μF     | 275V    | 4p    | H6/5     | 330μF    | 25V     | 10p   |
| H8/12    | 32μF     | 15V     | 4p    | H6/5A    | 370μF    | 35V     | 15p   |
| H8/12A   | 32μF     | 10V     | 4p    | H6/8     | 470μF    | 25V     | 10p   |
| H8/13A   | 32μF     | 50V     | 4p    | H6/8A    | 470μF    | 35V     | 20p   |
| H8/14    | 40μF     | 25V     | 4p    | H6/9A    | 400μF    | 40V     | 20p   |
| H8/14A   | 40μF     | 16V     | 4p    | H6/13A   | 1000μF   | 25V     | 10p   |
| H8/15    | 47μF     | 50V     | 4p    |          |          |         |       |
| H8/15A   | 40μF     | 35V     | 4p    |          |          |         |       |
| H7/1     | 50μF     | 6V      | 3p    |          |          |         |       |
| H7/1A    | 50μF     | 10V     | 4p    |          |          |         |       |
| H7/2A    | 64μF     | 2-5V    | 5p    |          |          |         |       |
| H7/3A    | 64μF     | 25V     | 4p    |          |          |         |       |
| H7/4     | 64μF     | 15V     | 4p    |          |          |         |       |

**POSTAGE: 15p PER ORDER**

**ALL GOODS PLUS 10% V.A.T.**

**MULLARD ELECTROLYTIC CAPACITORS**

| Type No.  | Working Voltage Vdc. | Capacitance μF | Max. Ripple Current at 50°C | Weight | Price |
|-----------|----------------------|----------------|-----------------------------|--------|-------|
| 071 15332 | 16                   | 3300           | 2.4 amps                    | 1oz    | 15p   |
| 071 15472 | 16                   | 4700           | 3.9 amps                    | 1oz    | 17p   |
| 071 15682 | 16                   | 6800           | 5.8 amps                    | 1½oz   | 22p   |
| 072 15752 | 16                   | 7500 + 7500    | 10.5 amps                   | 3oz    | 37p   |
| 072 15113 | 16                   | 11000 + 11000  | 13.8 amps                   | 4½oz   | 48p   |
| 071 18472 | 25                   | 4700           | 6.4 amps                    | 1½oz   | 22p   |
| 072 18502 | 25                   | 5000 + 5000    | 9.6 amps                    | 3½oz   | 37p   |
| 072 18752 | 25                   | 7500 + 7500    | 12.6 amps                   | 4½oz   | 48p   |
| 071 18681 | 63                   | 680            | 2.1 amps                    | 1oz    | 15p   |

| Type No.  | Working Voltage Vdc. | Capacitance μF | Max. Ripple Current at 50°C | Weight | Price |
|-----------|----------------------|----------------|-----------------------------|--------|-------|
| 106 18223 | 25                   | 22000          | 17 amps                     | 10oz   | £1-12 |
| 106 17103 | 40                   | 10000          | 12 amps                     | 7½oz   | 84p   |
| 107 10222 | 100                  | 2200           | 10 amps                     | 5½oz   | 74p   |

| Type No.  | Voltage | Capacitance | Weight | Price |
|-----------|---------|-------------|--------|-------|
| 102 15163 | 16      | 16000       | 8oz    | 25p   |
| 104 90003 | 20      | 39000       | 16oz   | 36p   |
| 102 16802 | 25      | 8000        | 7oz    | 25p   |
| 104 90001 | 45      | 20000       | 16oz   | 50p   |

A further 10% discount on lots of 100 of any one type.

Please calculate the weight of your order and include appropriate postage.

| Not over | Ordinary Parcels | Not over | Ordinary Parcels |
|----------|------------------|----------|------------------|
| 11b      | 18p              | 101b     | 37p              |
| 21b      | 21p              | 141b     | 47p              |
| 41b      | 25p              | 181b     | 57p              |
| 61b      | 29p              | 221b     | 67p              |

**UNIUNION TRANSISTORS SIMILAR TO 2N 2646 25p**

**£1** 100 1/4 WATT RESISTORS  
100 CERAMIC CAPACITORS  
100 DIODES

POSTAGE 20p

**£1** 1 VERO-BOARD CUTTER  
3 1/2 in. x 1 in. x 15 BOARDS  
50 5/8 in. "ODD PIECES"  
VERO

POSTAGE 20p

**£1** 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC106 ETC.

POSTAGE 20p

**£1** 5 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS & CAPACITORS

POSTAGE 27p

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
100 POLYSTYRENE CAPACITORS

POSTAGE 20p

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
50 MULLARD POLYESTER CAPACITORS

POSTAGE 20p

**£1** 1 TRANSISTORISED SIGNAL TRACER KIT  
1 TRANSISTORISED SIGNAL INJECTOR KIT

POSTAGE 20p

**£1** 100 RESISTORS  
100 CAPACITORS (ASSORTED TYPES)

POSTAGE 20p



Which type of Shopper are YOU?

Shopper A, enthusiastic to a fault, is determined to track down the components he needs for his next project. We'll overlook the fact that he'll probably end up with pneumonia!

Shopper B learnt his lesson long ago—now he simply sits back and orders all his requirements from his Home Radio Components' catalogue. The worst that could happen to him is that, being so absorbed in the catalogue, he might burn his toast! That's a small price to pay though for the comfort, convenience and economy of ordering components this way.

You too can join the blissful "B's"—there must be about 100,000 of them! To get your catalogue (240 large pages packed with 6,800 items, 1,770 of them illustrated) simply post the coupon with your P.O. or cheque for 77p (55p plus 22p post and packing). Every catalogue contains 5 vouchers, each worth 10p when used as directed. Send now.

Please write your Name and Address in block capitals

Name \_\_\_\_\_

Address \_\_\_\_\_




HOME RADIO (Components) LTD., Regd. No. 912966 London, Dept. PW, 234-240 London Road, Mitcham CR4 3HD



**I.L.P. (Electronics) Ltd**

## SECOND GENERATION 25 WATT HYBRID

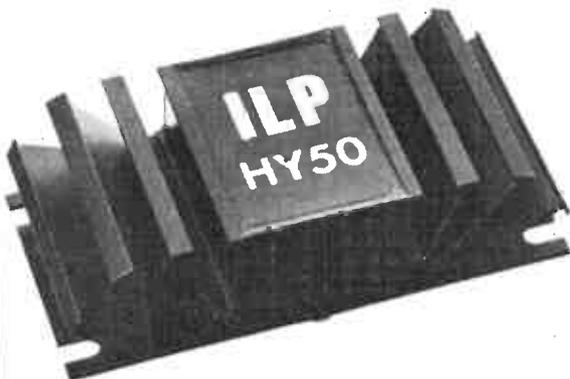

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular amplifier to a simple input/output device requiring only the addition of a basic unregulated (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy, sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of 'King-size' cigarettes.


Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

**OUTPUT POWER:** 25 watts RMS, 50 watts peak music power  
**LOAD IMPEDANCE:** 4-16Ω into 8Ω  
**INPUT SENSITIVITY:** 0db (0.775 volts RMS)  
**INPUT IMPEDANCE:** 47KΩ  
**TOTAL HARMONIC DISTORTION:** Less than 0.1% at 25 watts typically 0.05  
**SIGNAL/NOISE RATIO:** better than 75db  
**FREQUENCY RESPONSE:** 10Hz-50KHz ± 1db  
**SUPPLY VOLTAGE:** ± 25 volts  
**SIZE:** 105 x 50 x 25 mm

Price £5.40 mono, £10.80 stereo

Price inclusive of VAT & P & P

## NEW HY5 PRE-AMPLIFIER

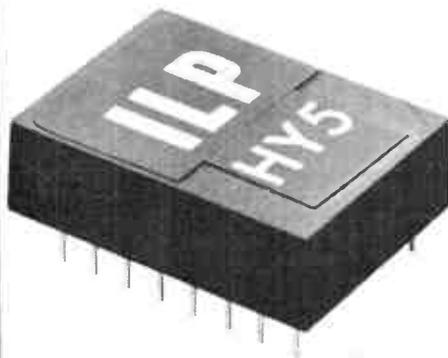

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids. Like the HY50, the new HY5 has no external components & has been redesigned to run off a split power-line with improvements in signal/noise, overload, capability & reduced distortion. The output has been increased to match the power module (Odb), and to share the same power supply. Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 & power supply only potentiometers are required to complete a simple mono amplifier with input & output facilities expected to be found on Hi-Fi amplifiers. The combination of two HY5's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

**INPUTS**  
Magnetic Pick-up 3mV (within 1db RIAA curve)  
Ceramic Pick-up up to 3mV  
Microphone 10mV  
Tuner 250mV  
Auxiliary 3-100mV  
Input impedance 47kΩ 1kHz

**SPEC.**

**OUTPUTS**  
Tape 100mV  
Main output, 0db (0.775volts)

**ACTIVE TONE CONTROLS**  
Treble ± 12db at 10kHz  
Bass ± 12db at 100Hz

**OVERLOAD CAPABILITY** (equalization stage) 40db on most sensitive input  
**OUTPUT NOISE LEVEL** (below 10mV magnetic input) 68db  
**DISTORTION** 0.05% at 1kHz

**SUPPLY VOLTAGE** ± 16-25 volts  
**SUPPLY CURRENT** 15mA  
Price £4.51 mono, £9.02 stereo  
Price inclusive of VAT & P & P

## POWER SUPPLY PSU50



The new PSU50 has a low profile look being only 2 1/2 inches high and can be used for either mono or stereo systems.

**SPEC.**  
**OUTPUT VOLTAGE** ± 25 volts  
**INPUT VOLTAGE** 210-240 volts  
**SIZE** L. 70, D. 90, H. 60 mm

Price £5.23  
Price inclusive of VAT & P & P

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.



# become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

RPAPY

**Free!**

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

WB43  
BLOCK CAPS please

# 'WORTH WAITING'

A JOINT ANNOUNCEMENT FROM



Due to contractual commitments both at home and overseas Eddystone Receivers are in short supply. Whilst the manufacturers are doing their best to meet these requirements we would ask your forbearance and understanding of the present delivery situation. Limited supplies of the ever popular EC10 and EB37 will continue to be available. Apologies for the necessity to "DIM THE LIGHT" — normal brilliance will be resumed as soon as possible.

IMHOFS  
112-116 New Oxford St.  
London WC1A 1HJ  
telephone 01 636 7878

EDDYSTONE RADIO Ltd.  
Alvechurch Rd.  
Birmingham B31 3PP  
telephone 021 475 2231

R85



## WORK WITH ADCOLA AND YOU KNOW YOU ARE USING! THE BEST ELECTRICAL SOLDERING EQUIPMENT!

When you buy ADCOLA equipment you are purchasing the best soldering merchandise. These instruments identical to those used in industry world wide. The electronics industry use ADCOLA for our reliability, efficiency, precision and high safety standards. ADCOLA must be right for you! Treat yourself to the BEST! Order on your coupon NOW

Please send me the following items

- A L706 INVADER Soldering instrument £2.42
- B L646 INVADER Soldering instrument £2.66
- C L1676 INVADER Soldering instrument £2.73
- D BL646 INVADER 12v Battery model £3.35
- E BL1076 INVADER 12v Battery model £3.50
- F INVADER Soldering Kit £4.73
- G R500 ELECTRIC Desoldering tool £9.79
- H REEL Desoldering Braid £0.75
- I L686 SOLDERING stand £1.97
- J L68 PROTECTIVE stand £1.31
- K 1/2 KILO SOLDER REEL £1.74
- L 3oz SOLDER REEL £0.52
- M SOLDER PACK £0.10

New Catalogue

All prices include 10% VAT

Please tick items required

PRINT NAME \_\_\_\_\_

PRINT ADDRESS \_\_\_\_\_

18w  
1/8" BIT

23w  
3/16" BIT

27w  
1/4" BIT

12v  
3/16" BIT  
1/4" BIT



Post to: ADCOLA PRODUCTS LTD. ADCOLA HOUSE GAUDEN ROAD LONDON SW4 6LH VAT REGD No. 235 6153 72 REGD No. 442762

# DON'T BUY TRIO

(UNTIL YOU SEE THIS!)

**SENSATIONAL DISCOUNTS !** 9R59DS £52.59 (incl VAT) PLUS FREE SPEAKER  
JR599 £165.00 (incl VAT) PLUS FREE HEADPHONES  
DELIVERED—OUR RISK!

FOR ANY LOCATION

## A COMPLETE RADIO STATION

at a cost (delivered at our risk), little, if any more than the cost of the **TRIO** equipment alone !!!

Including — in gold hammer finish stove enamel —  
the world record award winning

**JOYSTICK V.F.A. and JOYMATCH A.T.U.**  
REGD. & PAT. REGD.

# FREE

Headphones or Speakers; Suitably Terminated Connectors; Handbook; Carriage; Insurance. In addition a **JOYSTICK V.F.A.**; **JOYMATCH A.T.U.**; feeder external mounting insulators are supplied **FREE** or greatly reduced when you buy a **PARTRIDGE PACKAGE**.

A **PARTRIDGE PACKAGE** constitutes a **COMPLETE RADIO STATION**—ready to use however confined your domestic space. The World renowned **TRIO** range of Communications Receivers and Transceivers, the **WORLD RECORD**, internationally patented **JOYSTICK V.F.A.** (all band aerial) only 7" 6" long (assembled) and a **JOYMATCH** aerial tuning unit, a pair of matching headphones or internal speaker, plus accessories, go to complete your **READY TO USE RADIO STATION** at a price that truly represents **VALUE FOR MONEY!** **H.P. FACILITIES** WHERE POSSIBLE—**24 HOUR DELIVERY (MON-FRI.)** **ADD £4.00—OUR RISK!**

### PARTRIDGE PACKAGE

No. 1 with Gen. Coverage AM/CW/SSB (MW/SW) 9R59DS Receiver .. .. . £65.91 (Save £15.30)  
No. 2 with Amateur Bands 80 thru 10m AM/CW/SSB JR310 Receiver .. .. . £90.87 (Save £22.35)  
No. 3 with Amateur Bands 160 thru 10m plus 2m AM/CW/SSB JR599 .. .. . £165.00 (Save £19.48)  
No. 4 with Amateur Bands 80 thru 10m TS/PS 515 Transceiver, 180w .. .. . £231.00 (Save £37.08)

### NOTHING MORE TO PAY!

### OUR RISK

Access/Barclaycard orders accepted by 'phone

**JOYSTICK V.F.A.** £13.75; **JOYMATCH TX/RX A.T.U. 111A 1.6-32MHz** £13.75; **JOYMATCH A.T.U. 111 RX** only 500kHz-32MHz £13.75; **JOYMATCH A.T.U. LO-Z500 TX/RX 500w SSB (PA input)**, Built-in RF meter £19.91; Communications 8Ω headphones (suitable TRIO, EC10 etc.) £3.14; Matching Speaker (with instructions for internal fitting in 9R59DS & JR310) £2.00; **TRIO: Linear Amplifier TL911** £172.15; TR2200 2m personal transceiver £87.45; TR7200 2m car transceiver £142.45; Spare set valves for 9R59DS £2.35; OA2 Mains Stabiliser 74p.

**NEW : World-wide reception on the amazing "DX-CRYSTAL SET" £2.42 incl. unique aerial.**

**NEW : AMTRON QUALITY KITS—send for brochure and prices.**

### PARTRIDGE BUDGET LINE

**Artificial Earth—solves receive and transmit earth problems (as used on North Sea Oil Rigs!)** £5.80; **Aerial Bandswitch—tuned aerial for domestic receivers** £5.80; **A.T.U. KIT—for use with transmitters and Communications Receivers** £5.80; (assembled £7.01); **Mini SWR Bridge—1.8 to 180mHz, 2kw P.E.P., 75 or 50Ω, SO239 sockets; 1:1 to 1:3 ratio, 80 x 30 x 30mm** £5.60. (All prices quoted **INCLUDE V.A.T., CARRIAGE, PACKING, INSURANCE.**)

Send 3½p stamp for full illustrated details. Special **TRIO** brochures (state which) 3½p stamp extra.

**NO V.A.T. ON OVERSEAS ORDERS!**

Carriage and insurance extra overseas orders

BOX 5



G3CED — G3VFA

FOR EXPERT ADVICE AND INFORMATION

Telephone: 0843 62535 or 62839 evenings and weekends

# Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS  
IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS  
You need a catalogue! 55p post paid complete with Discount Vouchers



UK's  
LARGEST RANGE  
OF KITS &  
GADGETS

## TEST EQUIPMENT

### MULTIMETERS

|                  |                                      |       |
|------------------|--------------------------------------|-------|
| (carr. etc. 30p) |                                      |       |
| M210             | 20K/Volt Slimline                    | 6 75  |
| ULH33D           | 2K/Volt Robust                       | 7 50  |
| T437             | 10K/Volt Steel case. AC up to 40 KHz | 4 95  |
| U4324            | 20K/Volt with AC current ranges      | 8 00  |
| AF105            | 50K/Volt                             | 10 50 |
| U4313            | 20K/Volt AC current. Steel case      | 11 95 |
| U4341            | Plus Built in transistor tester      | 10 50 |
| Model 500        | 30K/Volt                             | 9 95  |



### OTHER EQUIPMENT

|        |                                     |                 |
|--------|-------------------------------------|-----------------|
| SE250B | Pocket Signal Injector              | 2 10 carr. 15p  |
| SE500  | Pocket Signal Tracer                | 1 70 carr. 15p  |
| TE15   | Grid Dip meter 440kHz-280mHz        | 15 00 carr. 30p |
| TE40   | AC Millivoltmeter 1.2mHz            | 18 95 carr. 35p |
| TE85   | 28 Range valve voltmeter            | 18 95 carr. 40p |
| TE22D  | 120kHz-500mHz RF Generator          | 17 95 carr. 40p |
| TE22D  | 20Hz-200kHz Audio Generator         | 18 95 carr. 40p |
| SE350A | Deluxe Signal Tracer                | 12 50 carr. 20p |
| SE400  | Volts/ohm/R/C sub./RF field/RF gen. | 14 75 carr. 20p |

### New Revolutionary Supertester 680R


|                      |        |
|----------------------|--------|
| 680R Multi-tester    | £18 50 |
| Accessories          |        |
| Transistor tester    | 11 00  |
| Electronic voltmeter | 18 00  |
| Amplclamp            | 11 95  |
| Temperature probe    | 11 95  |
| Gauss meter          | 11 95  |
| Signal injector      | 5 95   |
| Phase Sequence       | 5 95   |
| EHT Probe            | 5 95   |
| Shunts 25/50/100A    | 4 50   |

### A SELECTION OF INTERESTING ITEMS

|   |                              |                 |
|---|------------------------------|-----------------|
| C3025                                   | Compact transistor tester    | 6 30 p & p 15p  |
| E1300                                   | Mono mag. cart. preamp       | 2 75 p & p 15p  |
| E1310                                   | Stereo mag. cart. preamp.    | 4 67 p & p 25p  |
| EA100                                   | Earphone telephone amplifier | 7 95 p & p 25p  |
| D1203                                   | Telemag. with PU coil        | 4 40 p & p 20p  |
| LL1                                     | Door Intercom, and chime     | 13 90 p & p 25p |
| Chattalite                              | (lights as you talk)         | 3 00 p & p 10p  |
| 1 Kw Dimmer/controller                  |                              | 3 30 p & p 15p  |
| 9" Twin spring unit For                 |                              | 6 85 p & p 25p  |
| 16" Twin spring unit Reverbs            |                              | 8 95 p & p 15p  |
| Car Tachometer Electronic               |                              | 4 50 p & p 15p  |
| VHF 105 Aircraft Band Corrector         |                              | 3 75 p & p 15p  |
| B2005 4 Ch. mic. mixer                  |                              | 5 95 p & p 15p  |
| B2004 2 ch. Stereo mixer                |                              | 5 95 p & p 15p  |
| PK3 Kit. Etch your own printed circuits |                              | £1 50 p & n 20n |
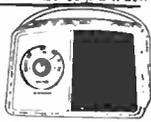
### BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW — bandspread for extra selectivity. Slow motion tuning. Fibreglass PVC cabinet. 600MW output. All parts £7.98 (battery 22p), carr. etc. 32p.



### EXCLUSIVE: SPECIAL OFFERS

|   |  |                         |
|---|--|-------------------------|
| MW/LW CAR RADIO (- Earth) with speaker                  | Rotel RA310 15+15 watt   | £12 50                  |
| Pod & fixings.  | Stereo Amplifier (List and fixings. £6.50 carr.)                                   | £52.00/£34.52.          |
| 3 TRACK CAR STEREO (- Earth) with speakers in AKAI GX40 | Wain W500 Battery/Mains Cassette Recorder  | £12 75                  |
| Pod & fixings.  | Stereo cassette recorder, carr./pack, 40p.   | £39 95 carr./pack, 50p. |
| Portable Battery Cassette Tape Player £7.25.            | Pair Akai ADM microphones.   | £6 95 carr./pack, 20p.  |
| Car Lighter Plug and adaptor for all cassette and radio | PORTABLE CASSETTE 6/7 1/2 volt output (state TAPE PLAYER— for car or carry around. | £7 25 carr./pack, 20p.  |
| Rotel Stereophones                                      |  |                         |
| RH530   | £4 50 HANIMAX BC808 PCKET  |                         |
| RH700   | £6 75 CALCULATOR WITH  |                         |
| RH430   | £3 30 % KEY. £28 95  |                         |


### SPECIAL PURCHASES

AVOMETER MOVEMENTS  
AVO 8 or 9 50mA MOVEMENTS  
Ex Brand New AVO's £3 50  
Post 20p


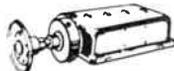
### UHF TV TUNERS CHANNELS 21 TO 64

Brand new transistorised geared tuners for 625 Line Receiver IF output. £2.50, Post 20p.




### EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

|           |  |       |
|-----------|--|-------|
| Model No. |  |       |
| 310       | Radio control receiver                             | 2 90  |
| 300       | 4 channel R/C transmitter                          | 5 95  |
| 345       | Superhet R/C receiver                              | 5 95  |
| 455       | AM signal generator                                | 12 33 |
| 65        | Simple transistor tester                           | 1 40  |
| 115       | 8 watt Amplifier                                   | 3 90  |
| 120       | 12 watt amplifier                                  | 4 70  |
| 125       | Stereo control unit                                | 5 70  |
| 130       | Mono control unit                                  | 3 60  |
| 605       | Power supply for 115                               | 4 55  |
| 610       | Power supply for 120                               | 4 55  |
| 615       | Power supply for 2 x 120                           | 5 73  |
| 230       | AM/FM aerial amplifier                             | 2 83  |
| 240       | Auto parking light                                 | 3 60  |
| 275       | Mic. preamplifier                                  | 5 90  |
| 570       | LF generator 10Hz-1mHz                             | 6 08  |
| 575       | Sq. wave generator 20Hz-20KHz                      | 15 80 |
| 580       | SWR meter  | 14 60 |
| 620       | NI-CAD Charger 1-2-12v                             | 12 85 |
| 630       | STAB Power supply 8-12v 0 25-0 1 A                 | 8 00  |
| 690       | DC motor speed Gov.                                | 8 15  |
| 700       | Electronic Chaffinch                               | 2 87  |
| 705       | Windscreen wiper timer                             | 7 00  |
| 760       | Acoustic switch                                    | 6 80  |
| 780       | Metal Detector (electronics only)                  | 10 75 |
| 790       | Capacitive Burglar alarm                           | 9 65  |
| 835       | Guitar preamp.                                     | 6 85  |
| 840       | Delay car alarm                                    | 4 25  |
| 875       | Car. Discharge ignition for car engine (-Ve Earth) | 6 15  |
| 80        | Scope Calibrator                                   | 13 15 |
| 255       | Level indicator                                    | 2 25  |
| 525       | 120-180mHz VHF timer                               | 6 15  |
| 715       | Photo cell switch                                  | 11 30 |
| 795       | Electronic continuity tester                       | 7 70  |
| 860       | Photo timer  | 4 30  |
| 871       | Slide projector auto feed control                  | 13 25 |
| 235       | Acoustic Alarm for driver                          | 7 15  |
| 455       | Quartz XTAL checker                                | 7 60  |
| 220       | Signal injector                                    | 8 75  |
| 390       | VOX  | 2 30  |
| 432       | Testakit   | 15 50 |
| 670       | Buffer Battery Charger                             | 19 30 |
| 885       | Capacitive Contact Alarm                           | 6 55  |
| 850       | Electronic Keyer                                   | 6 25  |
| 820       | Electronic Digital Clock                           | 18 75 |
|           |  | 58 50 |

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY

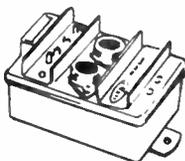Prices correct at time of preparation. Subject to change without notice.



### BUILD THIS TUNER

MW/LW Radio Turner with tuner with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4.85, carr. 15p.

### MULTI-USE & RADIONIC KITS

|       |                        |       |
|-------|------------------------|-------|
| 10-1  | 10 Projects            | 3 60  |
| 50-1  | 10 Projects            | 8 00  |
| 150-1 | 150 Projects           | 13 20 |
|       | Telephone Communicator | 7 20  |
| X20   | 20 (Elec.)             | 4 95  |
| X40   | 40 (radio)             | 8 45  |
|       | (carr./packing 40p)    |       |

### All transistor circuits with hand books

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.



### GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/Play and oscillator/Erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits £9.50 carr. 30p

### TOP QUALITY SLIDER CONTROLS


60mm stroke high quality controls complete with knobs (post. etc. 15p any quantity).  
Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg 45p each.  
Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 85p each. (Quantity discounts available)

### MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO  
'17' High Impedance £2 00  
'18' Med. Impedance £2 00  
R730/E73 2 track mono Record/Erase low imp. 75p pair  
Erase Heads for '17' and '18' 75p  
'63' 2 track mono, HI imp. £1 75  
'43' Erase Head for '63' 75p  
(Post. etc. 15p any quantity).

### SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

|   |        |                                 |
|---|--------|---------------------------------|
| AMPLIFIERS (carr., etc. 20p)                            |        |                                 |
| 4-300, 0-3 watt 9 volt                                  | 1 75   | SINCLAIR (carr. 20p) PROJECT 60 |
| 104, 1 watt 9 volt                                      | 2 80   | Z50 4-37                        |
| 304, 3 watt 9 volt                                      | 2 95   | Stereo 60 Preamp. 7 97          |
| 555, 3 watt 12 volt                                     | 3 10   | PZ5 £3-97, PZ6 £8-37            |
| E208, 5 watt 12 volt 5-10                               | 4 10   | PZ8 (for Z50) £4-77             |
| 608, 10 watt 24 volt 4-10                               | 4 95   | (TRANS £2-95)                   |
| 410, 10 watt 28 volt 4-95                               | 9 95   | AFU £4 45                       |
| E206, 30 watt 45 volt                                   | 11 75  | New SINCLAIR PROJECT 80         |
| E210, 2 1/2 + 2 1/2 watts                               | 7 25   | Stereo Preamp. 11 95            |
| 12 volt   | 7 25   | Audio Filter Unit 9 95          |
| RE500, 5 watt IC mains operated Amplifier with controls | £5 30  | Z40 15 Watt Amp. 5 45           |
| SAC14, 7 + 7 watt Stereo with controls                  | £8 70  | Z60 25 Watt Amp. 6 95           |
| SAC13, 15 + 15 watt Stereo with controls                | £11 75 | PZ5 Mod. for 1 on 2 Z40 4 98    |
|   |        | PZ6 Mod. (S Tab) 7 98           |
|   |        | PZ8 Mod. (S Tab) 7 98           |
|   |        | 1 on 2 Z50 7 98                 |
|   |        | TRANSFORMER FOR PZ8 2 95        |
|   |        | Project 605 Kit 19 95           |

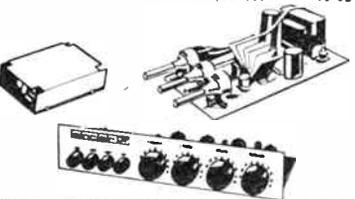


### POWER SUPPLIES FOR EVERY PURPOSE

|   |                   |  |
|---|-------------------|--|
| (All cases unless 300 mA stated chassis)                                  |                   |  |
| 470 6/7 1/2 volt 300 mA (Includes Multi-Adaptor for Tape Recorders, etc.) | 2 15 post 20p     |  |
| Car Lighter Voltage Adaptors 300mA (State voltage 6v, 7 1/2v, 9v)         | 1 95 ea. post 25p |  |
| SC202 31/6/7 1/2 volt 400mA   | 3 35 carr. 30p    |  |
| HC244R Stabilised version   | 4 35 carr. 30p    |  |
| P500 9 volt 500mA   | 2 90 post 20p     |  |
| P11 24 volt 500mA (chassis)   | 2 90 post 20p     |  |
| P15 26/28 volt 1 amp (chassis)  | 4 25 post 20p     |  |
| P1080 12v 1 amp (chassis)   | 7 50 post 20p     |  |
| P1081 45v 0 9 amp (chassis)   | 7 15 post 30p     |  |
| P12 44-12 volt 0 4-1 amp  | 10 30 post 25p    |  |
| SE101A 31/6/9/12 volt 1 amp (Stab.)                                       | 10 20 post 30p    |  |
| RP164 6/7 1/2/9/12 1 amp (Stab.)  |                   |  |

### FIBRE OPTICS

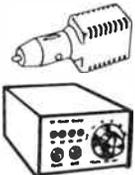0-01 Diam. Mono Filament £1 50 per 25 metre reel  
0-13 Diam. 64 Fibres Sheathed. £1 00 per metre  
SPRAYS 15mm Diam. Mares Tails £9 50.



**Henry's RADIO LIMITED**  
EDGWARE ROAD, W2  
SEE FACING PAGE FOR ADDRESSES

# Henry's

## UK'S LARGEST RANGE OF TRANSISTORS, IC'S RECTIFIERS, ALL SEMICONDUCTOR DEVICES

BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL

### FREE BOOKLET

All types of  
TRANSISTORS — RECTIFIERS  
BRIDGES — SCR'S — TRIACS  
INTEGRATED CIRCUITS  
F.E.T. — LIGHT DEVICES

OVER 1500 DIFFERENT DEVICES

ENTIRELY NEW EDITION

SEND FOR YOUR FREE COPY TODAY

INTEGRATED CIRCUITS VERY IMPORTANT. ONLY branded IC's

are the FULL manufacturers specifications. ALL others are not. Henry's sell only branded Integrated Circuits... From TEXAS... I.T.T. ... FAIRCHILD ... SIGNETICS. So why buy alternatives or under spec. devices when you can purchase the genuine article from us — ex stock... need we say more!

More Devices  
New Prices  
New Ranges

This is a must for all

Semi-conductor Users

(ask for booklet No. 36)

TBA800 5 WATT I.C.  
Suitable alternative to  
SL403, 5/30 volt approx.  
rated, 8/16 ohm 5 watt  
output.  
With circuits and  
data £1 50



Sinclair IC12  
with IC12s and data.  
6 watt IC with printed  
circuit board  
28 volt operated £2-00



ZN414 IC  
Integrated circuit radio as  
featured by many magazines  
(PW Jan. 73 Reprint  
Ref. No. 19 for 10p) £1-20



STROBE TUBE  
ZFT4A/XTF2. Suit-  
able for Dec. '73  
Pract. Electronics  
£2-50



ST2 (D32) DIAC 25p  
CRS1/40 SCR 45p

Ultrasonic Transducers  
Operate at 40KHz up to 100 yds.  
Ideal remote switching and signalling.  
Complete with data transmitter and  
receiver new I.C. circuits.  
Per pair £5-90  
TA960 IC with socket £1-80



3015F 7 SEG.  
I.C. size complete with  
data price £1-70 each  
(digital clock circuits  
ref. No. 31, 15p)



### TRANSISTORS SPECIAL OFFER

| 2N3055 |             | AF117 |             |
|--------|-------------|-------|-------------|
| 25     | .....42p ea | 25    | .....15p ea |
| 100    | .....47p    | 100   | .....13p    |
| 500    | .....39p    | 500   | .....12p    |
| 1000   | .....34p    | 1000  | .....10p    |

### ZENER DIODES

400 mW BZY88/  
BZX83. From 3-3  
volt - 33 volts 10p  
each

1-3 watts 5% Mini-  
ature Tubulars  
IN4700 series. £2-00 20 01  
From 3-3 volt - 33  
volt 18p each.

10 watts. Std  
Mounting. Z5  
series 6-8 volts -  
100 volts 5% 40p  
each.

### SILICON RECTIFIERS

1 amp series  
IN4001 to IN4007  
From 6p ea

1-5 amp  
PL4001 to PL4007  
From 8p ea

3 amp  
PL7001/IN5400  
From 14p ea

Send for full list 36

MORE OF EVERYTHING  
AT  
**HENRY'S**  
See pages 1040,  
1041 and Outside  
Back Cover of this  
magazine.  
**BEST VALUE**


### TRIACS - Std. mounting with accessories

| 3 AMP RANGE |            | 1-11      |  |
|-------------|------------|-----------|--|
| Type        | P.I.V.     | Price ea. |  |
| SC35A       | 100v 80p   |           |  |
| SC35B       | 200v 85p   |           |  |
| SC35D       | 400v 90p   |           |  |
| SC35E       | 500v £1-20 |           |  |

| 6 AMP RANGE |            | 3 Amp T048 |  |
|-------------|------------|------------|--|
| SC40A       | 200v 90p   |            |  |
| SC40B       | 200v 95p   |            |  |
| SC40D       | 400v £1-20 |            |  |
| SC40E       | 500v £1-50 |            |  |

| 10 AMP RANGE |            | 15 AMP RANGE |            |
|--------------|------------|--------------|------------|
| SC45A        | 100v £1-05 | SC50A        | 100v £1-45 |
| SC45B        | 200v £1-15 | SC50B        | 200v £1-85 |
| SC45D        | 400v £1-45 | SC50D        | 400v £1-95 |
| SC45E        | 500v £1-85 | SC50E        | 500v £2-25 |

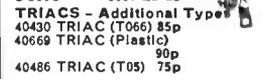TRIACS - Additional Types  
40630 TRIAC (T066) 85p  
40669 TRIAC (Plastic) 90p  
40486 TRIAC (T05) 75p



### NEW RANGES BRIDGE RECTIFIERS

FEATURES SMALL SIZE AND LOW COST Sizes are approx.  
250M/A QUARTER AMP  
B025/05 50 PIV 16p  
B025/10 100 PIV 18p  
B05/60 500v

1 amp 1-11 Pricing

| Type   | P.I.V. | Price ea. |
|--------|--------|-----------|
| B05/05 | 50v    | 20p       |
| B05/10 | 100v   | 22p       |
| B05/20 | 200v   | 23p       |
| B05/40 | 400v   | 25p       |
| B05/60 | 500v   | 27p       |

1 AMP P.I.V.

|       |      |     |
|-------|------|-----|
| B1/05 | 50v  | 25p |
| B1/10 | 100v | 25p |
| B1/20 | 200v | 28p |
| B1/60 | 600v | 30p |

1 AMP P.I.V.

|     |      |     |
|-----|------|-----|
| W05 | 50v  | 29p |
| W01 | 100v | 30p |
| W02 | 200v | 32p |
| W06 | 600v | 35p |

2 AMPS P.I.V.

|        |       |     |
|--------|-------|-----|
| B2/05  | 50v   | 35p |
| B2/10  | 100v  | 40p |
| B2/20  | 200v  | 45p |
| B2/60  | 600v  | 55p |
| B2/100 | 1000v | 55p |

4 AMPS P.I.V.

|        |      |       |
|--------|------|-------|
| B4/100 | 100v | 55p   |
| B4/200 | 200v | 55p   |
| B4/400 | 400v | 65p   |
| B4/600 | 600v | 75p   |
| B4/800 | 800v | £1-00 |

6 AMPS P.I.V.

|       |      |       |
|-------|------|-------|
| B6/05 | 50v  | 65p   |
| B6/10 | 100v | 70p   |
| B6/20 | 200v | 80p   |
| B6/40 | 400v | 90p   |
| B6/60 | 600v | £1-00 |

SILICON CONTROLLED RECTIFIERS

| Type      | P.I.V. | Price ea. |
|-----------|--------|-----------|
| CRS1/05AF | 50v    | 30p       |
| CRS1/10AF | 100v   | 30p       |
| CRS1/20AF | 200v   | 35p       |
| CRS1/40AF | 400v   | 45p       |
| CRS1/60AF | 600v   | 55p       |

THREE AMP (T048)

|           |      |     |
|-----------|------|-----|
| CRS3/05AF | 50v  | 40p |
| CRS3/10AF | 100v | 40p |
| CRS3/20AF | 200v | 45p |
| CRS3/40AF | 400v | 55p |
| CRS3/60AF | 600v | 65p |

FIVE AMP

|                  |      |     |
|------------------|------|-----|
| CRS5/400         | 400v | 60p |
| SEVEN AMP (T048) |      |     |
| CRS7/100         | 100v | 60p |
| CRS7/200         | 200v | 67p |
| CRS7/400         | 400v | 85p |
| CRS7/600         | 600v | 95p |

| Type     | 1/11 | 12/29 | 30/99 | Type     | 1/11 | 12/29 | 30/99 | Type      | 1/11 | 12/29 | 30/99 |
|----------|------|-------|-------|----------|------|-------|-------|-----------|------|-------|-------|
| 8N7400N  | 0-20 | 0-18  | 0-16  | 8N7448N  | 0-50 | 1-27  | 1-13  | 8N74142N  | 2-80 | 2-88  | 2-52  |
| 8N7401N  | 0-20 | 0-18  | 0-16  | 8N7450N  | 0-20 | 0-18  | 0-16  | 8N74145N  | 1-44 | 1-44  | 1-26  |
| 8N7401AN | 0-38 | 0-38  | 0-33  | 8N7451N  | 0-20 | 0-18  | 0-16  | 8N74147N  | 2-30 | 2-30  | 1-83  |
| 8N7402N  | 0-20 | 0-18  | 0-16  | 8N7453N  | 0-20 | 0-18  | 0-16  | 8N74148N  | 2-01 | 2-01  | 1-63  |
| 8N7403N  | 0-20 | 0-18  | 0-16  | 8N7454AN | 0-20 | 0-18  | 0-16  | 8N74150N  | 2-30 | 2-30  | 2-01  |
| 8N7403AN | 0-38 | 0-38  | 0-33  | 8N7460N  | 0-20 | 0-18  | 0-16  | 8N74151N  | 1-15 | 1-15  | 1-00  |
| 8N7404N  | 0-24 | 0-21  | 0-18  | 8N7470N  | 0-33 | 0-30  | 0-27  | 8N74153N  | 1-09 | 1-09  | 0-95  |
| 8N7405N  | 0-20 | 0-18  | 0-16  | 8N7472N  | 0-38 | 0-38  | 0-34  | 8N74154N  | 2-30 | 2-30  | 2-01  |
| 8N7405AN | 0-44 | 0-44  | 0-38  | 8N7473N  | 0-44 | 0-41  | 0-37  | 8N74155N  | 1-15 | 1-15  | 1-00  |
| 8N7406N  | 0-40 | 0-38  | 0-35  | 8N7474AN | 0-48 | 0-48  | 0-42  | 8N74156N  | 1-09 | 1-09  | 1-00  |
| 8N7407N  | 0-40 | 0-38  | 0-35  | 8N7475N  | 0-59 | 0-55  | 0-51  | 8N74157N  | 1-09 | 1-09  | 0-95  |
| 8N7408N  | 0-25 | 0-22  | 0-19  | 8N7476N  | 0-45 | 0-38  | 0-32  | 8N74158N  | 2-44 | 2-44  | 2-14  |
| 8N7409N  | 0-35 | 0-33  | 0-28  | 8N7480N  | 0-50 | 0-70  | 0-50  | 8N74160N  | 1-58 | 1-58  | 1-38  |
| 8N7409AN | 0-44 | 0-44  | 0-39  | 8N7481N  | 1-25 | 1-10  | 0-95  | 8N74161N  | 1-58 | 1-58  | 1-38  |
| 8N7410N  | 0-20 | 0-18  | 0-16  | 8N7482N  | 0-87 | 0-80  | 0-72  | 8N74162N  | 1-58 | 1-58  | 1-38  |
| 8N7411N  | 0-25 | 0-23  | 0-21  | 8N7483N  | 1-20 | 1-10  | 1-00  | 8N74163N  | 1-58 | 1-58  | 1-38  |
| 8N7412N  | 0-28 | 0-28  | 0-25  | 8N7485N  | 1-87 | 1-87  | 1-63  | 8N74164AN | 2-01 | 2-01  | 1-76  |
| 8N7412AN | 0-38 | 0-38  | 0-33  | 8N7486N  | 0-50 | 0-50  | 0-44  | 8N74166N  | 2-01 | 2-01  | 1-76  |
| 8N7413N  | 0-30 | 0-27  | 0-25  | 8N7489N  | 4-32 | 4-32  | 3-78  | 8N74169N  | 2-16 | 2-16  | 1-89  |
| 8N7414N  | 0-72 | 0-72  | 0-63  | 8N7490N  | 0-75 | 0-70  | 0-63  | 8N74167AN | 4-10 | 4-10  | 3-59  |
| 8N7414AN | 0-30 | 0-27  | 0-25  | 8N7491AN | 1-10 | 1-10  | 0-90  | 8N74170N  | 2-88 | 2-88  | 2-52  |
| 8N7417N  | 0-30 | 0-27  | 0-25  | 8N7492N  | 0-75 | 0-70  | 0-63  | 8N74172N  | 5-78 | 5-78  | 5-04  |
| 8N7420N  | 0-20 | 0-18  | 0-16  | 8N7493N  | 0-75 | 0-70  | 0-63  | 8N74173N  | 1-66 | 1-66  | 1-45  |
| 8N7422N  | 0-28 | 0-28  | 0-25  | 8N7494AN | 0-85 | 0-80  | 0-75  | 8N74174AN | 1-80 | 1-80  | 1-57  |
| 8N7422AN | 0-38 | 0-38  | 0-33  | 8N7495N  | 0-85 | 0-80  | 0-75  | 8N74175N  | 1-29 | 1-29  | 1-28  |
| 8N7423N  | 0-37 | 0-34  | 0-28  | 8N7496N  | 1-00 | 0-90  | 0-83  | 8N74176N  | 1-44 | 1-44  | 1-26  |
| 8N7425N  | 0-37 | 0-37  | 0-32  | 8N74100N | 2-16 | 1-89  | 1-89  | 8N74177N  | 1-44 | 1-44  | 1-26  |
| 8N7427N  | 0-37 | 0-37  | 0-32  | 8N74104N | 0-60 | 0-53  | 0-45  | 8N74180N  | 1-44 | 1-44  | 1-26  |
| 8N7428N  | 0-43 | 0-43  | 0-37  | 8N74105N | 0-60 | 0-53  | 0-45  | 8N74181N  | 5-18 | 5-18  | 4-53  |
| 8N7430N  | 0-20 | 0-18  | 0-16  | 8N74107N | 0-51 | 0-51  | 0-45  | 8N74182N  | 1-44 | 1-44  | 1-26  |
| 8N7432N  | 0-37 | 0-37  | 0-32  | 8N74110N | 0-57 | 0-57  | 0-50  | 8N74184N  | 2-16 | 2-16  | 1-89  |
| 8N7433N  | 0-43 | 0-43  | 0-38  | 8N74111N | 0-50 | 0-50  | 0-45  | 8N74185AN | 2-16 | 2-16  | 1-89  |
| 8N7434AN | 0-57 | 0-57  | 0-50  | 8N74112N | 2-16 | 2-16  | 1-89  |           |      |       |       |
| 8N7437N  | 0-43 | 0-43  | 0-37  | 8N74118N | 1-00 | 0-90  | 0-83  | 8N74188N  | 6-48 | 6-48  | 5-87  |
| 8N7438N  | 0-43 | 0-43  | 0-37  | 8N74119N | 1-92 | 1-92  | 1-68  | 8N74190N  | 2-30 | 2-30  | 2-01  |
| 8N7438AN | 0-57 | 0-57  | 0-50  | 8N74120N | 1-05 | 1-06  | 0-92  | 8N74191N  | 2-30 | 2-30  | 2-01  |
| 8N7440N  | 0-20 | 0-18  | 0-16  | 8N74121N | 0-57 | 0-57  | 0-50  | 8N74192N  | 2-30 | 2-30  | 2-01  |
| 8N7441AN | 0-85 | 0-79  | 0-73  | 8N74122N | 0-80 | 0-80  | 0-70  | 8N74193N  | 2-30 | 2-30  | 2-01  |
| 8N7442N  | 0-85 | 0-79  | 0-73  | 8N74123N | 1-44 | 1-44  | 1-26  | 8N74194AN | 1-72 | 1-72  | 1-51  |
| 8N7443AN | 1-50 | 1-27  | 1-13  | 8N74125N | 0-69 | 0-69  | 0-60  | 8N74195N  | 1-44 | 1-44  | 1-26  |
| 8N7444AN | 1-50 | 1-27  | 1-13  | 8N74126N | 0-69 | 0-69  | 0-60  | 8N74196N  | 1-58 | 1-58  | 1-38  |
| 8N7445AN | 2-16 | 2-16  | 1-89  | 8N74132N | 0-72 | 0-72  | 0-63  | 8N74197N  | 1-58 | 1-58  | 1-38  |
| 8N7446N  | 2-16 | 2-16  | 1-89  | 8N74136N | 0-63 | 0-63  | 0-55  | 8N74198N  | 3-18 | 3-18  | 2-77  |
| 8N7447AN | 1-80 | 1-80  | 1-57  | 8N74141N | 1-00 | 0-90  | 0-80  | 8N74199N  | 2-88 | 2-88  | 2-52  |

LARGER QUANTITY AND O.E.M. PRICES. PHONE (01) 723 3646.  
SN7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED  
REGARDLESS OF MIX. SN74 HIGH POWER. SN74 LOW POWER  
SERIES IN STOCK... SEND FOR LIST 36, FREE ON REQUEST. LOW PROFILE  
SOCKETS 14 PIN... 15p. 16 PIN... 17p. 8 PIN... 14p

### TRANSISTORS A SELECTION FOR FULL LIST SEND FOR BOOKLET 36 TODAY

|           |            |            |          |            |             |
|-----------|------------|------------|----------|------------|-------------|
| AAZ13 10p | BC182 12p  | BY213 35p  | OC36 65p | ZTX108 10p | 2N3714 1-60 |
| AC107 35p | BCY32 35p  | CI06D 55p  | OC44 18p | ZTX300 14p | 2N3717 1-75 |
| AC187 20p | BCY65 2-50 | GET111 55p | OC71 15p | ZTX302 18p | 2N3773 2-25 |
| ACY       |            |            |          |            |             |

# TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

## POP 40 10" 40 Watt

Impedance 8-15 ohms  
Gauss 12,000  
Voice Coil Diam. 2"  
Fitted Tweeter Cone  
Range 50-15,000 Hz



Rec. Retail Price

**£10.95**

Also for those who can  
afford the very best  
For Bass Instrument  
Reproduction

## BASS CRESCENDO '12'

12" 100 Watt 3" Pole Diam.

## BASS CRESCENDO '15'

15" 100 Watt 3" Pole Diam.



Rec. Retail Price  
CRESCENDO '12'

**£39.95**

Rec. Retail Price  
CRESCENDO '15'

**£48.83**

## POP 55 12" 60 Watt

Impedance 8-15 ohms  
Gauss 15,000  
Voice Coil Diam. 2"  
Range 50-9,000 Hz  
AN ALL PURPOSE  
UNIT OF HIGH  
SENSITIVITY



Rec. Retail Price

**£15.95**

### BRIEF DETAILS OF OTHER 'POP' SPEAKERS

| POP                          | Rec. Retail Price |
|------------------------------|-------------------|
| '15' 12" 15 W. 1" Voice Coil | £5.75             |
| '25/2' 12" 30 W. 2" " "      | £8.75             |
| '50' 12" 50 W. 2" " "        | £12.75            |
| '60' 15" 60 W. 2" " "        | £15.75            |
| '100' 18" 100 W. 3" " "      | £27.50            |

THERE IS ALSO A 12" CRESCENDO  
SPEAKER FOR GENERAL PURPOSE  
PUBLIC ADDRESS, AND ANOTHER  
ONE FOR LEAD or RHYTHM GUITAR.

## PRICES QUOTED INCLUDE VAT

Distributors to Wholesale & Retail Traders  
LINEAR PRODUCTS LTD., Electron Works, Armley, Leeds.

Please send S.A.E. for leaflet on 'POP' or 'CRESCENDO'  
Range Speakers

Manufacturers enquiries to  
FANE ACOUSTICS LTD., 286 Bradford Road, Batley, Yorks.

## MAINS UNITS for all types of TRANSISTOR EQUIPMENT

### RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied  
complete and ready to  
plug into your cas-  
sette-recorder. (State  
voltage, make and  
type of plug required,  
if in doubt send dia-  
gram of recorder  
socket).



ONLY **£2.75** P & P 20p

### PLUS-3 MAINS UNIT

Provides three separate  
switched output voltages  
6v., 7½v. and 9v. DC.  
Attractive case mains lead  
output socket, plug and  
lead. Size 4½ x 3½ x 2½in.

ONLY **£3.30**

Extra lead with plug to fit your cassette recorder  
50p. (State model and plug required.)

### MAINS UNIT FOR TRANSISTOR RADIO ONLY

For single outputs, 6v, 9v **£2.20**  
For two separate outputs, 6v. + 6v.,  
9v. + 9v. **£2.75** P. & P. 20p per unit.  
(Please state outputs required).

All units are completely isolated from mains by  
double wound transformer ensuring 100% safety.

ALL PRICES INC VAT

R.C.S. PRODUCTS (RADIO) LTD.  
(Dept. P.W.)  
36 Raymond Ave., South Woodford  
London, E18 2HG

## Stove Enamelled STEEL CABINET



List price £8 25  
OUR PRICE  
**£6.50**  
incl. V.A.T.  
Carriage 44p

With 48 see-through Drawers  
Ideal for the Radio Constructor

As supplied by us to SCHOOLS,  
TECHNICAL COLLEGES, HOSPI-  
TALS, SHOPS and industry  
throughout the country. Silver grey  
stove enamelled steel cabinet with  
48 transparent styrene drawers fitted  
with moulded handles and label slots.  
Dividers can be supplied at a small  
extra charge to enable each drawer  
to be sub-divided into six compart-  
ments. See-through drawers allow  
swift selection of contents at a  
glance. A really first-class time and  
space saving unit. Size of cabinet  
21½" x 11½" x 6½", size of drawers  
6½" x 2½" x 1½".

Callers welcome.

SEND FOR FREE ILLUSTRATED LEAFLETS

Trade **111 Chiltern Drive-Surbiton Surrey**  
**Aids** (100 yards from **01-399 4383**  
Berrylands Railway Station)

## A DEXTER DIMMASWITCH

ALLOWS COMPLETE

LIGHTING CONTROL



The DEXTER DIMMASWITCH is an attractive  
Dimma unit which simply replaces the normal  
light switch. It is available as a complete "ready  
to install" unit or "simple to assemble" kit. Two  
models are available controlling up to 300W or  
600W of all lights, except fluorescents, at mains  
200-250V, 50Hz. All DEXTER DIMMASWITCH  
models have built-in radio interference suppres-  
sion. 600 watt **£3.52** Kit form **£2.97**  
300 watt **£2.97** Kit form **£2.42**

All plus 12p post and packing

Prices include VAT. Please send c.w.o. to:

### DEXTER & COMPANY

5 ULVER HOUSE  
19 KING STREET  
CHESTER CH1 2AH  
Tel: 0244-25883

AS SUPPLIED  
TO H.M. GOVERNMENT  
DEPARTMENTS, HOSPITALS,  
LOCAL AUTHORITIES,  
ETC.

# ELECTROVALUE

## CATALOGUE 7



## An A to Z guide to component buying

On the index page of Catalogue 7, between "Aluminium Boxes" and "Zener Diodes" are over 200 references to contents amounting in all to thousands of items, classified, described, often illustrated, and priced. There is a wealth of technical diagrams and data. At 25p, Catalogue 7 is excellent value by any standard. With the 25p Refund Voucher it costs you virtually nothing when you order £5-worth or more.

**25p** INCLUDING 25p REFUND VOUCHER ALLOWABLE ON ORDERS £5 OR MORE LIST VALUE

### ★ A SELECTION FROM EV CATALOGUE 7

#### TRANSISTORS

and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc. etc.

#### MINITRON DIGITAL INDICATORS

30151F Seven segment filament, compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL (some alphabetical symbols available) £1-20  
Suitable BCO decoder driver £1-15  
3015G showing + or - & 1 & dec. pt. £1-20

#### DALY ELECTROLYTIC CAPACITORS

*in cans, plastic sleeved*  
1000mF/25V 28p 1000/50 41p 1000/100 82p  
2000mF/25V 37p 2000/50 57p 2200/100 £1-56  
5000mF/25V 62p 5000/50 £1-18 5000/100 £2-91

#### POLYESTER CAPACITORS TYPE C.280

*Radial leads for P.C.B. mounting. Working voltage 250V d.c.*  
0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p  
0-068, 0-1, 0-15 ea. 4p  
0-22, 5p; 0-33 7p; 0-47 8p; 0-68 11p; 1-0 14p;  
1-5 21p; 2-2 24p

#### SILVERED MICA CAPACITORS

*Working voltage 500V d.c.*  
Values in pFs—2-2 to 820 in 32 stages ea. 6p  
1000, 1500 7p; 1800 8p; 2200 10p; 2700, 3600 12p;  
4700, 5000 15p; 6800 20p; 8200, 10,000 25p

#### POTENTIOMETERS

**ROTARY, CARBON TRACK.** *Double wipers for good contact and long working life*

P-20 SINGLE linear 100ohms to 2-2megohms. ea. 14p

P-20 SINGLE log. 4-7Kohms to 2-2megohms. ea. 14p

JP-20 OUAL GANG lin. 4-7Kohms to 2-2megohms. ea. 48p

JP-20 OUAL GANG log. 4-7Kohms to 2-2megohms. ea. 48p

JP-20 OUAL GANG Log/antilog 10L, 22K, 47K, 1 megohm only ea. 48p

JP-20 OUAL GANG antilog 10K only ea. 48p

2A OP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets Type PR, horizontal or vertical 6p each.

Slider Potentiometers

Linear or log. 10K to 1 meg. In all popular values ea. 30p

Escutcheon plates, black, white or light grey. ea. 10p

Control knobs, blk/wht/red/yel/grn/blue/dk. grey/lt. grey ea. 7p

ZENER DIODES

Full range E24 values: 400mW: 2-7V to 36V, 14p each;

1W: 6-8V to 82V, 21p each; 1-5W: 4-7V to 75V, 48p each. Clip to increase 1-5W rating to 3 watts (type 266F), 4p.

#### RESISTORS

| Code | Watts | Ohms     | 1 to 9 | 10 to 99 | 100 up   |
|------|-------|----------|--------|----------|----------|
| C    | 1/20  | 82-220K  | 9      | 8        | 7-5      |
| C    | 1/3   | 4-7-470K | 1-3    | 1-1      | 0-9 nett |
| C    | 1/2   | 4-7-10M  | 1-3    | 1-1      | 0-9 nett |
| C    | 3/4   | 4-7-10M  | 1-5    | 1-2      | 0-9 nett |
| C    | 1     | 4-7-10M  | 3-2    | 2-5      | 1-9 nett |
| MO   | 1/2   | 10-1M    | 4      | 3-3      | 2-3 nett |
| WW   | 1     | 0-22-3-9 | 9      | 9        | 8        |
| WW   | 3     | 1-10K    | 7      | 7        | 6        |
| WW   | 7     | 1-10K    | 9      | 9        | 8 nett   |

#### Codes:

C = carbon film, high stability, low noise.  
MO = metal oxide, Electrofil TR5, ultra low noise.  
WW = wire wound, Pleessey.

Values: All E12 except C 1W, C 1/2W, and MO 1/2W.

E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.

E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances: 5% except WW1 10% ±0-05Ω and MO 1/2W 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

VEROBOARD

Copper clad 0-1 matrix—2-5 x 3-75 ins. 24p; 3-75 x 3-75 ins.—27p; 2-5 x 5 ins.—27p; 3-75 x 5 ins.—30p.

Copper clad 0-15 In. matrix 2-5 x 3-75 ins.—18p; 3-75 x 3-75 ins.—27p; 2-5 x 5 ins.—27p; 3-75 x 5 ins.—33p.

Vero spot face cutter (any matrix) 43p.

0-040 pins (for 0-1 matrix) per 100—30p.

0-052 pins (for 0-15 matrix) per 100—30p.

#### BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-90. The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2-30. Loudspeaker Unit 59RM109, £2-45. Cabinet Kit (to Baxandall design), £10-45. Cross-over choke included in full kit above, £1-30.

**This is EV Service**

#### DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14-99. 15% on orders £15 and over.

#### PACKING AND POSTAGE FREE

in U.K. For mail orders for £2 list value and under there is an additional handling charge of 10p.

#### GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, "seconds" or sub-standard merchandise is offered for sale.

Prices quoted do not include V.A.T., for which 10% must be added to total nett value of order. Prices subject to alteration without notice.

#### GIRO ACCOUNT No. 38/671/4002

All postal communications, mail orders etc. to Head Office at Egham address.

S.A.E. with enquiries requiring answers.

## ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB

Telephone Egham 3603 Telex 264475

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA

Telephone (061) 432 4945

Hours of business (both addresses) 9-5.30 p.m., 9-1.30 Saturdays.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O.

Box 27, Swarthmore PA 19081.

# TECHNICAL TRAINING

## *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunications Techns'. Certs.
- Radio Amateurs' Examination
- General Radiocommunications Certificate
- C. & G. Radio Servicing Theory
- General Certificate of Education, etc.

Now available Colour T.V. Servicing

**Examination Students coached until successful**

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

Accredited by the CACC

Member of the ABCC

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam) .....

NAME .....  
(BLOCK CAPITALS PLEASE)

ADDRESS .....


AGE.....OCCUPATION .....

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Dept. 232D, Intertext House,  
Stewarts Road,  
London, S.W.8 4UJ

**ICS**

## DABAR MN3 MIXER KIT

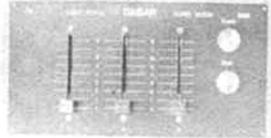

### INTRODUCING THE NEW DABAR MINI THREE CHANNEL MIXER KIT WITH THE FOLLOWING FEATURES:

- ★ Three inputs easily adjustable to suit users input requirements, e.g., Mic., Tape, Disc., etc.
- ★ Uses advanced design with five integrated circuits.
- ★ Slider fader volume controls mount directly on P.C. board.
- ★ Full range bass and treble controls.
- ★ Guaranteed top grade components with fibreglass printed circuit board, ready-drilled and tinned.
- ★ Battery operated (2 x PP3) not supplied with kit.
- ★ Easy to follow assembly instructions (available separately 25p).
- ★ Attractive ready punched fascia plate, available at extra cost, gives that professional finish to the unit.
- ★ Size: 9.5" x 4.8" x 2".

PRICE: KIT ONLY £11.00  
FACIA PLATE £1.50  
MANUAL AND ASSEMBLY INSTRUCTIONS 25p  
AVAILABLE READY BUILT WITH FACIA £15.00

ALL PRICES INCLUDE V.A.T. & POSTAGE IN U.K.  
S.A.E. ALL ENQUIRIES.

### DABAR ELECTRONIC PRODUCTS

98, LICHFIELD STREET, WALSALL, STAFFS, WS1 1UZ.

**TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. £2.30p.**

**P-C BOARDS** (not computer panels)

1 off 6 transistors single wave band

1 off 4 transistor audio

1 off 3 transistor £1.60 the three.

**LIGHT DEPENDENT RESISTORS** (RCA sq3536) 30p each, 4 for £1.00.

**All Transistor STEREOGRAM CHASSIS.** Medium, Long and VHF/FM. 3 Watts per channel S/M rating. With circuit service manual. Less tuning scale which can be obtained from well known British manufacturer . . . £20.

**Colour Translator panels,** as used on well known British E.V.R. Teleplayer. All new panels and components. Type and contents of transistors listed below. Each panel £3.50 each.

X605. .14 off BC148. 2 RCA ca3054(ic). 1 crystal 4.433618MHz. Z607. .12 off BC148. 1 BC158. 1 BC108. 1 RCA ca3046. 1 RCA ca3045(jc).

Z608. .23 off BC148. 2 BC158.

Z612. .12 off ME4102. 2 BC251B. 1 BFY50.

**CRYSTAL CALIBRATOR** (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz—10MHz (harmonics up to 30MHz) power required 300V DC 15mA. 12V 0.3A DC. Test equipment for 62T M/R.C. £2.50 each.

**WIRE-WOUND RESISTORS.** Our selection of mixed Ohms and Watts. 25 for £1.50, 50 for £2.50, parcel of 1,000 £30.00.

**CONDENSER-ELECTRET MIC INSERT** incorporating FET Preamp 1½ volt Supply. Details of connections included £1.75.

**AUDIO AMPLIFIER MODULE.** Due to bulk purchase we can now offer the Audio Amplifier Module (Mullard LP1173) output power, nominal 10 watt. Supply voltage +24 volt, with reference data for £2.50.

ALL ITEMS INCLUDE VAT

All items post paid in GREAT BRITAIN

## SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.



# NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit  
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteryless Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 2 Transistor Regenerative Radio.
- ★ Signal Injector.
- ★ 5 Transistor Short Wave Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP.
- ★ Electronic Metronome.
- ★ Available Continuity Tester.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator.
- ★ Sensitive Pre-Amplifier.

**Total Building Costs**  
**£7-23**  
P P & Ins. 44p  
(Overseas P & P £1-85)  
(+ 10% VAT 72p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3½" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6½ yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors, 9 Tunable wavebands as Roamer Ten Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors, 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9½" x 7" x 2½" approx. Parts Price List and Plans 30p (Free with parts).

**Total Building Costs**  
**£6-95**  
P P & Ins. 44p  
(Overseas P & P £1-85)  
(+ 10% VAT 69p)

## NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5½" x 2½" approx. Parts Price List and Plans 15p. Free with parts.

**Total Building Costs**  
**£2-73**  
P P & Ins. 30p  
(+ 10% VAT 27p)  
(Overseas P & P £1-25)

E.V.8. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc.. MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

**Total Building Costs**  
**£3-60**  
P P & Ins. 30p  
(+ 10% VAT 36p)  
(Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. SW coverage. MW/LW. Trawler Band. SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 20p. Free with parts. Overseas P & P £1-05.

**Total Building Costs**  
**£4-08**  
P P & Ins. 31p  
(Overseas P & P £1-85)  
(+ 10% VAT 40p)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

**Total building costs**  
**£6-98**  
P P & Ins. 47p  
(Overseas P & P £1-85) (+ 10% VAT 69p)

## POCKET FIVE

3 Tunable wavebands. MW, LW, and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive black and coil case. Size 5½" x 1½" x 3½" approx. Plans and Parts Price List 15p (Free with parts).



**Total Building Costs**  
**£2-28**  
P P & Ins. 20p  
(Overseas P & P £1-25)  
(+ 10% VAT 23p)




## TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts).

**Total Building Costs**  
**£2-50**  
P P & Ins. 26p  
(+ 10% VAT 25p)
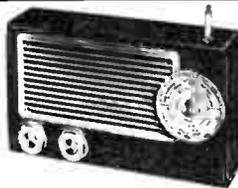
## TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for MW, LW, and LW. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).



**Total building costs**  
**£4-48**  
P P & Ins. 33p  
(+ 10% VAT 44p)  
(Overseas P & P £1-25)


## ROAMER SIX

Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc.. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Plans and parts price list 25p (FREE with parts).

**Total building costs**  
**£3-98**  
P P & Ins. 31p  
(Overseas P & P £1-85)  
(+ 10% VAT 39p)

## ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

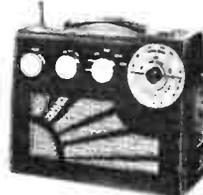

10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers. 9 Tunable Wavebands. MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes, Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off, Wave Change and tone controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

**Total building costs**  
**£8-50**  
P P & Ins. 52p  
(Overseas P & P £1-85) (+ 10% VAT 85p)



## "EDU-KIT"

Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct.

Components include:

Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine Tune 3" Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; 2 Plugs and Sockets; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 4" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

**Total building costs**  
**£5-50**  
P P & Ins. 33p  
(Overseas P & P £1-85) (+ 10% VAT 53p)

## RADIO EXCHANGE LTD

★ Callers side entrance "Lavelle" shop  
★ Open 10-1 2.30-4.30 Mon-Fri 9-12 Sat

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 15A  
Tel.: 0234 52367. Ref. No. 788372.

I enclose £..... for.....  
Name.....  
Address.....  
(Dept. PW24.)

# The largest selection

## EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50, 3 for ONLY 55p + p & p 30p

**SPECIAL ONE.** As above PLUS Power Transistors ONLY 55p each + p & p 15p

**STABILISED POWER MODULES**  
Complete with circuit diagrams, etc. 99p each + p & p 15p

**PAXOLINE BOARDS** 7½" x 9" approx. 4 for 30p + p & p 20p.

## FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½ x 4" approx. 2 for 55p

## DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen 90p each

## VEROBOARDS

Packs containing approx. 50sq. ins. various sizes, all 1 matrix 55p

## REPANCO CHOKES & COILS

RF Chokes  
CH1. 2.0mH 25p CH2. 5.0mH 25p  
CH3. 7.5mH 25p CH4. 10mH 25p  
CH5. 1.5mH 25p

## COILS

DRX1 Crystal set 81p DRR2 Dual range 45p

## COIL FORMERS & CORES

NORMAN 1" Cores & Formers 7p  
1" Cores & Formers 8p

## SWITCHES

DP/DT Toggle 25p 8P/8T Toggle 18p

## FUSES

1½" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A  
QUICK-BLOW 4p ea. ANTI-BURGE 5p ea.

## EARPHONES

Crystal 2.5mm plug 33p  
Crystal 3.5mm plug 35p  
8 ohms 2.5mm plug 22p  
8 ohms 3.5mm plug 22p

## DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.60

## 3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

## 2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB @ 21.2

## CAR STEREO SPEAKERS

(Angled) £3.95 per pair.

## BI-PAK

CATALOGUE AND LISTS  
Send S.A.E. and 10p.

## INSTRUMENT CASES



| No. | Length | Width | Height | Price |
|-----|--------|-------|--------|-------|
| BV1 | 8"     | 4½"   | 2"     | 90p   |
| BV2 | 11"    | 6"    | 3"     | £1.20 |

(Black Vinyl covered)

## ALUMINIUM BOXES

|     |     |     |     |     |
|-----|-----|-----|-----|-----|
| BA1 | 5½" | 4"  | 1½" | 42p |
| BA2 | 4"  | 4"  | 1½" | 41p |
| BA3 | 4"  | 2½" | 1½" | 41p |
| BA4 | 5½" | 4"  | 1½" | 47p |
| BA5 | 4"  | 2½" | 2"  | 41p |
| BA6 | 3"  | 2"  | 1"  | 34p |
| BA7 | 7"  | 5"  | 2"  | 66p |
| BA8 | 8"  | 6"  | 3"  | 84p |
| BA9 | 6"  | 4"  | 2"  | 54p |

## VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)


Open Mon.-Thurs. 9.15-6 p.m. Sat. 9.15-5.30. Late Night Shopping until 7 Fri. Tel. 01593

## BIB HI-FI ACCESSORIES

### De Luxe Groov-Kleen

Model 42 £1.84

Chrome Finish Model 60 £1.50

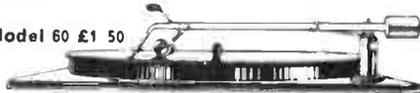

Ref. 30A. Record/Stylet Cleaning Kit 28p  
Ref. 43. Record Care Kit £2.35  
Ref. 31. Cassette Head Cleaner 54p  
Ref. 32. Tape editing Kit £1.54  
Model 9. Wire Stripper/Cutter 88p

Ref. 57. Model 10 cleaner 31p  
Ref. 32A. Stylus Balance £1.35  
Ref. J. Tape Head Cleaning Kit 51p  
Ref. 34. Cassette Case £1.97  
Ref. 56. Hi-Fi Stereo Hints & Tips 32p

## ANTEX SOLDERING IRONS

X25. 25 watt £1.93  
CCN 240. 15 watt £2.15  
Model G. 14 watt £2.15  
STANDB: 8T1 £1.21. 8T2 77p  
SOLDER: 188WG Multicores 7oz 82p  
228WG 7oz 82p. 188WG 22ft 28p  
228WG Tube 22p

## ANTEX BITS AND ELEMENTS

Bits No.  
102 For model CN240 3/32" 38p  
104 For model CN240 3/16" 38p  
1100 For model CCN240 3/32" 88p  
1101 For model CCN240 3/16" 88p  
1102 For model CCN240 1" 38p  
1020 For model G240 3/32" 38p  
1021 For model G240 1/8" 38p  
1022 For model G240 3/16" 38p  
50 For model X25 3/32" 38p  
51 For model X25 1/8" 38p  
52 For model X25 3/16" 38p

## ELEMENTS

ECN 240 £1.16 ECUN 240 £1.32  
EG 240 £1.16 EX 25 £1.16

## ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

## NEW COMPONENT PAK BARGAINS

| Pack No. | Qty. | Description                                       | Price |
|----------|------|---|-------|
| C1       | 250  | Resistors mixed values approx. count by weight    | 0.55  |
| C2       | 200  | Capacitors mixed values approx. count by weight   | 0.55  |
| C3       | 50   | Precision Resistors 1%, 2% mixed values           | 0.55  |
| C4       | 75   | 1/4W Resistors mixed preferred values             | 0.55  |
| C5       | 5    | Pieces assorted Ferrite Rods                      | 0.55  |
| C6       | 2    | Tuning Gangs, MW/LW VHF                           | 0.55  |
| C7       | 1    | Pack Wire 50 metres assorted colours              | 0.55  |
| C 8      | 10   | Reed Switches                                     | 0.55  |
| C 9      | 3    | Micro Switches                                    | 0.55  |
| C10      | 15   | Assorted Pots & Pre-Set                           | 0.55  |
| C11      | 5    | Jack Sockets 3 x 3.5m 2" Standard Switch Type     | 0.55  |
| C12      | 40   | Paper Condensers preferred types mixed values     | 0.55  |
| C13      | 20   | Electrolytics Trans. types                        | 0.55  |
| C14      | 1    | Pack assorted Hardware—Nuts/Bolts, Grunimets etc. | 0.55  |
| C15      | 4    | Mains Slide Switches                              | 0.55  |
| C16      | 20   | Assorted Tag strips & Panels                      | 0.55  |
| C17      | 10   | Assorted Control Knobs                            | 0.55  |
| C18      | 4    | Rotary Wave Change Switches                       | 0.55  |
| C19      | 3    | Relays 6—24V Operating                            | 0.55  |
| C20      | 4    | Sheets Copper Laminite approx. 10" x 7"           | 0.55  |

## PLUGS AND SOCKETS

SOCKETS  
PB 35 DIN 2 Pin (Speaker) 0.08  
PB 36 DIN 3 Pin 0.10  
PB 37 DIN 5 Pin 180° 0.10  
PB 38 DIN 5 Pin 240° 0.10  
PB 39 Jack 2.5mm Switched 0.09  
PB 40 Jack 3.5mm Switched 0.10  
PB 41 Jack 1" Switched 0.17  
PB 42 Jack Stereo Switched 0.26  
PB 43 Phono Single 0.06  
PB 44 Phono Double 0.10  
PB 45 Car Aerial 0.09  
PB 46 Co-Axial Surface 0.09  
PB 47 Co-Axial Flush 0.14

## INLINE SOCKETS

PB 21 D.I.N. 2 Pin (Speaker) 0.13  
PB 22 D.I.N. 3 Pin 0.17  
PB 23 D.I.N. 5 Pin 180° 0.17  
PB 24 D.I.N. 5 Pin 240° 0.17  
PB 25 Jack 2.5mm Plastic 0.10  
PB 26 Jack 3.5mm Plastic 0.12  
PB 27 Jack 1" Plastic 0.24  
PB 28 Jack 1" Screened 0.28  
PB 29 Jack Stereo Plastic 0.22  
PB 30 Jack Stereo Screened 0.22  
PB 31 Phono Screened 0.14  
PB 32 Car Aerial 0.15  
PB 33 Co-Axial 0.17

## PLUGS

PB 1 D.I.N. 2 Pin (Speaker) 0.11  
PB 2 D.I.N. 3 Pin 0.12  
PB 3 D.I.N. 4 Pin 0.15  
PB 4 D.I.N. 5 Pin 180° 0.14  
PB 5 D.I.N. 5 Pin 240° 0.15  
PB 6 D.I.N. 6 Pin 0.15  
PB 7 S.I.N. 7 Pin 0.15  
PB 8 Jack 2.5mm Screened 0.10  
PB 9 Jack 3.5mm Plastic 0.09  
PB 10 Jack 3.5mm Screened 0.12  
PB 11 Jack 1" Plastic 0.18  
PB 12 Jack 1" Screened 0.18  
PB 13 Jack Stereo Screened 0.29  
PB 14 Phono 0.06  
PB 15 Car Aerial 0.15  
PB 16 Co-Axial 0.10

## CABLES

CP 1 Single Lapped Screen 0.08  
CP 2 Twin Common Screen 0.08  
CP 3 Stereo Screened 0.08  
CP 4 Four Core Common Screen 0.23  
CP 5 Four Core Individually Screened 0.30  
CP 6 Microphone Fully Braided Cable 0.10  
CP 7 Three Core Mains Cable 0.07  
CP 8 Twin Oval Mains Cable 0.06  
CP 9 Speaker Cable 0.04  
CP 10 Low Loss Co-Axial 0.10

## CARBON POTENTIOMETERS

Log and Lin  
4.7K, 10K, 22K, 47K, 100K, 200K, 470K, 1M, 2M  
VC 1 Single lead Switch 0.14  
VC 2 Single D.P. Switch 0.28  
VC 3 Tandem Lead Switch 0.44  
VC 4 1K Lin Lead Switch 0.14  
VC 5 100K Log anti-Log 0.44

## HORIZONTAL CARBON PRESETS

0.1 watt 0.08 each  
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

## BOOK BARGAIN BUNDLE

8 Books comprising  
2 Transistor Equivalent Books  
1 Radio and Electronic Colour Codes and Data Chart  
1 Radio Valve Guide PLUS  
3 other Constructional books on Receivers, FM Tuners, etc.  
Also 1 General Constructional book  
Value £3 Our Price £2 10p p & p

|      |  |     |
|------|--|-----|
| BP1  | Handbook of Transistor Equivalents and Substitutes   | 40p |
| BP2  | Handbook of Radio, T.V. and Industrial Tube & Valve Equiv. 40p   | 40p |
| BP3  | Handbook of Tested Transistor Circuits   | 40p |
| BP4  | International Handbook of the World's Short Wave, Medium and Long Wave Radio Stations and FM/TV Listings | 85p |
| BP5  | Handbook of Simple Transistor Circuits   | 35p |
| BP7  | Radio & Electronic Colour Codes and Data Chart   | 15p |
| BP8  | Mound and Loud-speaker Manual  | 50p |
| BP9  | 3M Practical Tested Diode Circuits for the Home Constructor  | 85p |
| BP11 | Practical Transistor Novelty Circuits  | 40p |
| 129  | Universal Gram-Motor Speed Indicator   | 8p  |
| 138  | How to make FM & TV Aerials, Bands 1, 2 and 3  | 18p |
| 141  | Radio Servicing for Amateurs   | 20p |
| 146  | High Fidelity Loudspeaker Enclosures   | 87p |
| 156  | Transistor Circuits Manual No.1  | 25p |
| 160  | Coil Design & Constructional Manual  | 80p |
| 161  | Radio, TV and Electronics Data Book  | 25p |
| 170  | Transistor Circuits for Radio Controlled Models  | 40p |
| 174  | Transistor Subminiature Receivers  | 85p |
| 176  | Transistor Test Equipment and Servicing Manual   | 25p |
| 176  | Transistor Audio Amplifier Manual  | 40p |
| 177  | Modern Transistor Circuits for Beginners   | 40p |
| 178  | A Comprehensive Radio Valve Guide, Book 5  | 80p |
| 183  | How to Receive Foreign TV Programmes on your set by simple modifications                                 | 55p |
| 185  | Tested Shortwave Receiver Circuits using MAT's   | 80p |
| 187  | The T&L Mark '4' Valved FM Tuner and its construction  | 20p |
| 196  | Reactance-Frequency Chart for Audio & RF use   | 15p |
|      | Resistor Colour Code Disc Calculator   | 10p |

## CARTRIDGES

ACOS GP91-18C. 200mV at 1.2cm/sec £1.16  
ACOS GP93-1. 280mV at 1cm/sec £1.65  
ACOS GP90-1. 100mV at 1cm/sec £2.65  
TTC J-2005. Crystal/Hi Output 95p  
TTC J-200 10C Crystal/Hi Output Compatible £1.10  
TTC J-200 US Stereo/Hi Output £1.50  
TTC J-2105 Ceramic/Med. Output £1.64

## CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 1/8th watt available in PAKS of 50 pieces, assorted into the following groups:—  
R1 50 Mixed 100 ohms-820 ohms 40p  
R2 50 Mixed 1K ohms-8.2K ohms 40p  
R3 50 Mixed 10K ohms-82K ohms 40p  
R4 50 Mixed 100K ohms-1 Meg. ohms 40p  
THESE ARE UNBEATABLE PRICES—LESS THAN 1p EACH INCL. V.A.T.


## BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C80, 32p C90, 41p C120, 52p

# -the lowest prices!

## BI-PAK QUALITY COMES TO AUDIO!
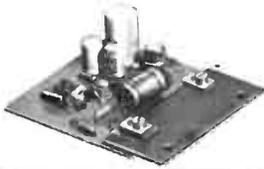
### AL10/AL20/AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

| Parameter                     | Conditions                           | Performance      |
|-------------------------------|--------------------------------------|------------------|
| HARMONIC DISTORTION           | $P_o$ 3 WATTS $f$ 1 KHz              | 0.25%            |
| LOAD IMPEDANCE                |                                      | 8 16 $\Omega$    |
| INPUT IMPEDANCE               | $f$ 1 KHz                            | 100 k $\Omega$   |
| FREQUENCY RESPONSE $\pm 3$ dB | $P_o$ 2 WATTS                        | 50 Hz - 25KHz    |
| SENSITIVITY for RATED O/P     | $V_s$ 25V $R_i$ 8 $\Omega$ $f$ 1 KHz | 75mV R.M.S.      |
| DIMENSIONS                    |                                      | 3" x 2 1/2" x 1" |

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

| Parameter  | AL10               | AL20               | AL30                |
|--|--------------------|--------------------|---------------------|
| Maximum Supply Voltage                                   | 25                 | 30                 | 30                  |
| Power output for 2% T.H.D. ( $R_L$ 8 $\Omega$ $f$ 1 KHz) | 3 watts R.M.S. Min | 5 watts R.M.S. Min | 10 watts R.M.S. Min |

#### AUDIO AMPLIFIER MODULES

|                       |       |
|-----------------------|-------|
| AL 10 3 watts R.M.S.  | £2.10 |
| AL 20 5 watts R.M.S.  | £2.50 |
| AL 30 10 watts R.M.S. | £3.01 |

#### POWER SUPPLIES

|                                    |       |
|------------------------------------|-------|
| PS 12 (Use with AL10 & AL20)       | 88p   |
| SPM 80 (Use with also AL30 & AL50) | £3.25 |

FRONT PANELS SP 12 with knobs £1.10

#### PRE-AMPLIFIERS

|                               |        |
|-------------------------------|--------|
| PA 12 (Use with AL10 & AL20)  | £4.35  |
| PA 100 (Use with AL30 & AL50) | £13.15 |

#### TRANSFORMERS

|                              |                 |
|------------------------------|-----------------|
| T461 (Use with AL10)         | £1.38 P & P 15p |
| T534 (Use with AL20)         | £1.83 P & P 15p |
| BMT80 (Use with AL30 & AL50) | £2.15 P & P 25p |

#### PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response  
20Hz - 20KHz  $\pm 3$ dB  
Bass control  
 $\pm 12$ dB at 60Hz  
Treble control  
 $\pm 14$ dB at 14KHz  
Input 1. Impedance  
1 Meg. ohm  
Sensitivity 300mV  
Input 2. Impedance  
30 K ohms  
Sensitivity 4mV

Look for our  
SEMICONDUCTOR ADVERTISEMENTS in


Practical Electronics  
Wireless World  
Radio Constructor  
Electronics Today

ALL PRICES INCLUDE V.A.T.

### The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch, volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control  $\pm 12$ dB at 60Hz typically 0.25% at 1 watt. Treble con.  $\pm 14$ dB at 14KHz.

£14.45

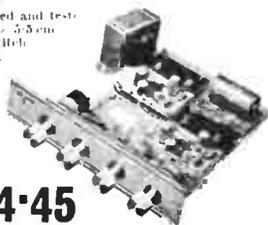


### 50W pk 25w (RMS)

0.1% DISTORTION!  
HI-FI AUDIO AMPLIFIER
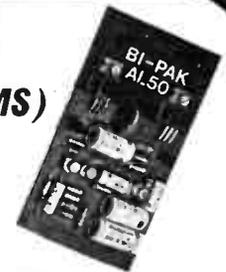
### THE AL50

- ★ Frequency Response 15Hz to 100,000-1dB.
- ★ Load—3, 4, 8 or 16 ohms.
- ★ Distortion—better than 1% at 1 KHz.
- ★ Signal to noise ratio 80dB.



ONLY  
£3.58 each

- ★ Supply voltage 10-35 Volts.
- ★ Overall size 63mm 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.  
FULLY BUILT - TESTED - GUARANTEED

### STABILISED POWER MODULE SPM80



SPM80 is especially designed to power 2 of the AL50 amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest component and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer MT80, the unit will provide outputs of up to 1.5amps at 35 volts. Size 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disc Systems, Public Address Intercom Units, etc. Handbook available 10p. PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p

### STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100. Also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

#### SPECIFICATION

Frequency Response  
20Hz - 20KHz  $\pm 1$ dB  
Harmonic Distortion  
better than 0.1%  
Inputs: 1. Tape Head  
1.25 mV into 50K  $\Omega$   
2. Radio, Tuner  
35 mV into 50K  $\Omega$   
3. Magnetic P.I.  
1.5 mV into 50K  $\Omega$   
All input voltages are for an output of 250mV. Tape and P.C. Input equalised to RIAA curve within  $\pm 1$ dB, from 20Hz to 20KHz.  
Bass Control  
 $\pm 15$ dB at 20Hz  
Treble Control  
 $\pm 15$ dB at 20 KHz  
Filters: Rumble (High Pass)  
100Hz  
Scratch (Low Pass)  
8KHz  
Signal/Noise Ratio  
better than 65dB  
Input overload  
 $\pm 26$ dB  
supply  
35 volts at 20mA  
222mm x 82mm x 35mm  
Dhew-jous



ONLY £13.15  
SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

# SAVE MONEY

SO the winter's economic crunch has come as most realistic prophets have forecast. We have read, heard, seen and experienced at first hand some of the revivals of the immediate post-war social and economic problems, not forgetting that dreaded winter of 1947. We do not intend here to rub the salt further into the wound but rather to look at ways and means of making our lives just a little more bearable.

*Practical Wireless* showed foresight in the autumn of 1973 which paid off. The power crises ever looming in our midst, we grabbed at the expected misfortunes in the electricity supply industry by publishing at the right time an emergency lighting unit to operate from a car battery. This proved so popular that we are now short of copies for office use. For those of you who missed it we publish in this issue a slightly different version (suggested by a *P.W.* reader) that uses a ready-made oscillator coil.

If you have thoughts about visiting the SONEX or other hi-fi exhibitions in the vicinity of London Airport in March, but are seriously wondering where the money to buy is going to come from, because of the Chancellor's mini-budget restrictions, again take a crumb of comfort from *P.W.* For less than a pound you can have not only the widest variety of do-it-yourself designs over the next three months, but also the freedom to control your own spending over whatever period you choose. You can purchase components and build your own equipment at leisure without worrying about interest charges.

This month's issue sees the start of a new hi-fi project with a difference. We do not recall ever seeing a similar project before in a magazine that incorporates a cassette recorder. We could then be justified in claiming yet another first for the do-it-yourselfer. The result is that you can save on the cost of a system for the home that gives you a.m. and f.m. radio, tape record/playback, the playing of pre-recorded cassettes, and with an added pick-up you can play back stereo discs. This quality system is in stereo and the cassette machine is left to your choice to suit your requirements and, most important, your pocket. If you are seriously interested in quadrasonic sound there is ample room in the unit to include a second pair of amplifiers and an uprated mains transformer.

If you have your own hi-fi set-up already, but you could do with a useful piece of test gear to help you set it up or locate some of those obscure faults, you will be interested in the Trouble Tracer that we published in the last two issues and the Waveform Generator in this issue.

Finally, most of you will already be hooked on our *P.W.* Data-card system; numbers 7 and 8 in this issue are specially designed for those who require "finger-tip" information on local reception and guidance on aerial installations.

M. A. COLWELL—*Editor.*

The April issue will include a new unique portable 5-band radio receiver; a "short-wipe" unit for clearing April showers from your car windscreen; an article that explains impedance matching in audio equipment; a special tool kit arranged by *Practical Wireless* for its readers at a favourable price. Cut your costs again—order the April issue of *P.W.* now. See the footnote and further details on page 1075.

# NEWS...

## IMPORTANT MESSAGE TO ALL READERS

Readers of "*Practical Wireless*" and most other magazines will be aware of the restrictions imposed by the Government and as a result of Trades Union action in various industries. To ensure that you receive your copy of "*Practical Wireless*" at the earliest possible date, we have to rely on effective communications and delivery through the post and by railway. We also depend on the operation of electrical equipment and printing machinery. Petrol and diesel oil are vital to the needs of our job in quick and effective processing of editorial and advertising material.

We are sure that you will understand the many problems that confront all of us. We therefore request your patience and understanding during any temporary period when publication may be delayed.

We regret that due to the effects of the current industrial situation, the number of pages in this issue has had to be limited. We apologise to advertisers who were unable to insert their full allocation of product announcements and to those unable to appear at all in this issue. Such is the "pulling-power" of *Practical Wireless* and its advertisements that we recommend booking early for the next available issue.

## Plessey IC book

PLESSEY Semiconductors has produced a comprehensive 235-page Databook giving details of its extensive range of silicon integrated circuits.

Continuous emphasis on the development of processes and circuits by Plessey has been demonstrated by the successful introduction of Bipolar Process III circuits and MNOS electrically-alterable non-volatile memories. The first products from these new processes are detailed in the Databook along with the wide range of both special and standard products currently available.

Copies of the Integrated Circuit Databook are available on application to *Plessey Semiconductors Limited, Cheney Manor, Swindon, Wiltshire.*

## Sonex rival

H I-FIDELITY '74 is a rival exhibition which will run concurrently with Sonex at the Heathrow Hotel. More details next month.

### ISB for broadcast radio?

**W**ORK on the problems of a.m. broadcasting on medium and long waves has been carried out at Siemens laboratories in West Germany. The independent sideband (ISB) system, proposed by the Hamburg Institute of Radio Engineering is being seriously considered to overcome some of the problems of increasing mutual interference.

Siemens engineers are quick to point out that the review of broadcasting frequency allocation, due within the next eighteen months, should recommend ISB to enable expansion up to double the number of programme channels for the same number of transmitters. An added advantage is that ISB offers the equivalent to SSB in terms of interference, bandwidth and fading, and could be implemented locally without the need for international agreement.

The major drawback is that receiver design will have to be altered so that a phase shift network can be employed for the 150 to 4kHz band to separate the two side-bands by at least 40dB. ISB receivers would be capable of processing signals in the SSB and DSB modes, with improved reception on DSB by listener selection. Transmitters would probably handle signals with the dynamic range reduced by 30dB.

### Modules and valves

**A**T a recent visit to the huge Mullard manufacturing complex at Blackburn recently, we were privileged to see the making of those "liquorice allsorts" coloured capacitors that are now familiar on printed circuit assemblies. Readers will also be pleased to learn that valves, mostly for television, are still being made in millions although the range of types has been rationalised to fit the economic needs of setmakers and servicemen.

We also saw the assembly of Mullard modules: the LP1185 f.m. i.f. strip; LP1186 d.c. voltage controlled tuner for Band II; LP1159 a.m. i.f. strip; LP1162 4 watt amplifier; LP1164/1 r.f./i.f. amplifier for a.m./f.m. radio; LP1402 f.m. tuner with capacitor tuning. Mullard are working on a modular design stereo decoder for release soon.

Our picture here shows the polyester foil type capacitor going through the colour code dip painting process. These are only a few of the vast activities on this 46 acre site employing approximately 4,000 people.

### Radar pioneer dies

**S**IR Robert Watson-Watt, C.B., F.R.S. died on 5th December at the age of 81. Sir Robert will be one of those famous names in the U.K. associated with great electronic inventions and in his case radar.

Early in his career he worked on the use of radio to detect thunderstorms. Radio direction finding found fame for him in World War II. Civil applications include airlines and shipping; a fitting tribute being the recently opened computer assisted radar tower and communications system for shipping within a 20 mile range of Liverpool.

The communications system was installed by Decca Radar Limited.

### Torbay A.R.S.

**T**HE Torbay Amateur Radio Society, G3NJA, has produced its first magazine. One of the main features is that of v.h.f./u.h.f. conversions of commercial equipment for the Amateur. This has been written by E. Hayman, G3ABU.

The T.A.R.S. are willing to add any readers' names to their magazine mailing list. Alternatively readers may become Associate Members for the sum of 50p annual subscription. They would then receive a free copy.

The magazine will be produced on alternate months and further copies may be obtained by sending a s.a.e. to *Frederick J. E. Bolton, G3VTQ, Top Flat, 23 Waverley Road, Newton Abbot, Devon.*



# A Versatile WAVEFORM GENERATOR

J. B. DANCE M.Sc

current passing to this latter pin is determined by the value of the voltage at this pin and by the resistance between it and the positive line. This current is used to charge and discharge the capacitor selected by S1b.

A Beckman 'Helipot' precision ten-turn helical potentiometer is employed for VR1 together with a Beckman turns counting dial; this enables the frequency of oscillation to be set reasonably accurately. The value of R1 has been chosen so that the potential at pin 5 never falls below three-quarters of the positive power supply line potential (as recommended by the manufacturers of the integrated circuit).

The frequency of oscillation is proportional to the voltage between the positive power supply line and pin 5; this voltage is in turn proportional to the resistance of VR1 between the positive line and the slider. In the circuit of Fig. 1, the frequency of oscillation is set to 10Hz, 100Hz, 1kHz, 10kHz, 100kHz


**T**HE Signetics NE566 integrated circuit function generator can be used to construct a simple unit which will provide a variety of waveforms over a very wide frequency range.

The prototype unit will be described in detail. However, a number of variations will be discussed so that individual readers can make modifications which may make the unit more useful for their own particular purposes.

The basic waveform generator produces triangular waves and square waves, and it is especially suitable for use in audio amplifier testing. An additional circuit can be used to produce sine waves in addition to the other two waveforms. The circuit can be modified to produce rising or falling waveforms of high linearity instead of the triangular waveforms. In this case short rectangular pulses are available at the output which previously provided square waves.
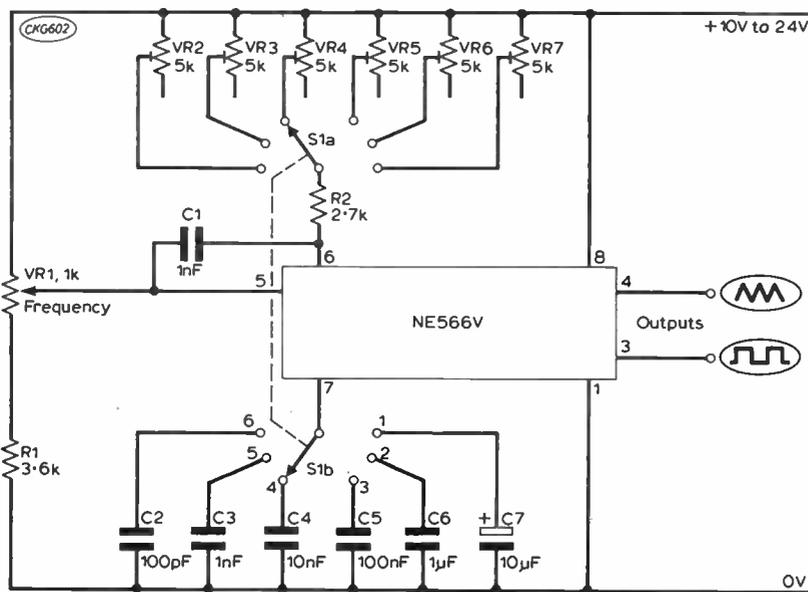
## THE BASIC CIRCUIT

The circuit of the basic function generator is shown in Fig. 1. The voltage at the slider of VR1 is applied to pin 5 of the NE566V and also pin 6 via C1. The



▲ The finished waveform generator with its direct reading dial. The necessary components to produce a ramp waveform can be added to the circuit board. For converting triangular waveforms to sinewaves a separate unit is required.

◀ Fig. 1: Circuit of generator producing square and triangular waves over a wide range of frequencies.

or 1MHz (depending on the range) when the slider of VR1 is set at 10.0. At other settings of the dial, the frequency is closely proportional to the dial setting. For example, a dial setting of 5.67 on the kHz range produces an output of 567Hz.

Many types of capacitor (especially electrolytic types) have very wide tolerances in their capacitance value. It is therefore necessary to calibrate the frequency at one point on each range to obtain accurate frequency readings. In the circuit of Fig. 1 this is accomplished by the adjustment of a different trimmer potentiometer (VR2 to VR7) for each range used. The switch which selects the trimmer, S1a, is ganged with that which selects the range capacitor, S1b.

## FREQUENCY COVERAGE

The frequencies available from the six adjustable ranges employed are shown in Table 1. The upper frequency limit of 1MHz is determined by the characteristics of the integrated circuit used. In the table it has been assumed that a frequency range of 20:1 may be covered using any one capacitor. However, more accurate frequency settings may be obtained by limiting the coverage of each range to 10:1, as was done in the prototype.

| RANGE | CAPACITOR  | FREQ. COVERAGE |
|-------|------------|----------------|
| 1     | 10 $\mu$ F | 0.5Hz- 10Hz    |
| 2     | 1 $\mu$ F  | 5Hz-100Hz      |
| 3     | 100nF      | 50Hz- 1kHz     |
| 4     | 10nF       | 500Hz-10kHz    |
| 5     | 1nF        | 5kHz-100kHz    |
| 6     | 100pF      | 50kHz- 1MHz    |

TABLE 1. Total frequency coverage possible with six capacitors. In practice each range is reduced to a ratio of 10:1.

The writer has found that a frequency range of about 30:1 is about the limit with any one capacitor. At settings of the frequency dial of less than about 0.3 the output waveforms become distorted, whilst oscillation ceases at settings below about 0.25. It was noted that the square waveform at 1MHz was somewhat distorted. The lowest frequency range in the prototype was 0.5 to 10Hz and it is assumed that most readers will not require frequencies below this value. Extra ranges can easily be added if required. However, an additional trimming potentiometer must be included in the S1a circuit for each extra range. A 100 $\mu$ F capacitor in the S1b circuit can be used to produce a range of 0.05 to 1Hz, and a 1000 $\mu$ F capacitor a range of 0.005 to 0.1Hz and a 10000 $\mu$ F capacitor a range of 0.0005 to 0.01Hz (0.0005Hz is one cycle in about 33 minutes).

When using very large capacitors, check that their leakage current is not excessive. The lowest possible frequency is probably about one cycle every few hours, but the writer has not tried to obtain frequencies quite as low as this. Some industrial applications may be found for generators of extremely low frequencies.

## CONSTRUCTIONAL NOTES

The basic oscillator circuit of Fig. 1 was constructed in an Eddystone die-cast box of approximate dimensions 4 $\frac{1}{2}$  x 3 $\frac{1}{2}$  x 2 $\frac{1}{4}$ in. (Cat. 6908P). The Helipot VR1 and switch S1 are mounted in the base of the box and the circuit board along one of the

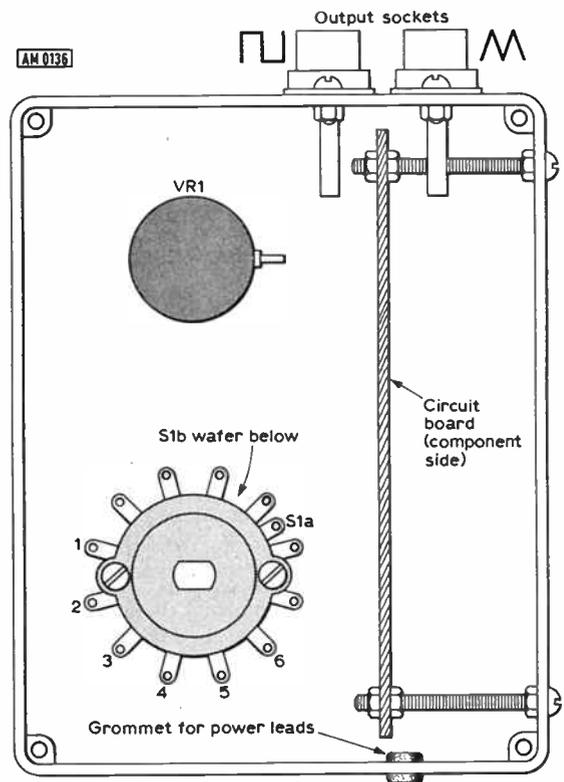


Fig. 2: General layout of components in the die-cast box.

longer sides Fig. 2. No components were mounted on the lid of the box since this procedure enables the lid to be removed without the inconvenience of having wires between it and the main part of the box.

The six miniature Beckman trimmer potentiometers are mounted on the circuit board Fig. 3, their connecting tags being inserted through holes in the board and bent over before the connecting wires are soldered. The integrated circuit socket is also mounted on the circuit board by passing the pins through holes in the board and soldering the connections to them.

C1 is mounted on the circuit board, but C2 to C7 are mounted around the switch S1. No power supply was included in the box, since it is generally more convenient to employ an external 12V battery. However, a mains power supply could be included if a rather larger box is employed.

If the circuits for the ramp and short pulse generator are required, they must be included in the basic oscillator unit itself. However, if the triangle-to-sine wave converter is made, it will probably be more convenient to construct it on a separate circuit board.

## CALIBRATION

The best way of calibrating the frequency settings involves the use of a digital frequency meter which automatically counts the pulses from the oscillator over a timed period. Alternatively a pulse counter may be used with a manually operated stop watch.

Calibration may also be carried out using a good oscilloscope with a calibrated time base. Alternatively the calibration may be set by adjusting the

trimming potentiometers so that the output 'zero beats' with the signal from a calibrated generator. At higher operating frequencies harmonics of the square wave output may be allowed to beat with a radio signal, using a receiver.

If very low frequency ranges are incorporated in the unit, the operating frequencies are best determined by connecting a voltmeter across the square wave output and timing the movements of the meter needle.

It is normally best to calibrate the unit at a point near to the highest frequency on each range. The linearity of the resistance of VR1 with the dial setting is very good (better than 0.25%). However, the writer has found that the frequency of oscillation of the NE566V may depart from linearity by up to about  $\pm 1\%$  at the lower frequencies in each range.

If a constructor does not like an instrument in which the oscillation ceases at the very low frequency end of each range, it is possible to set the dial so that it reads from 1.0 to 11.0. In this case a 100 ohm resistor, preferably of 0.5% tolerance, should be inserted between the upper end of VR1 and the positive supply line in Fig. 1 so that the readings are directly related to the frequency of oscillation. Operation in this way is likely to increase the errors in the frequency settings, since the percentage linearity tolerance of a precision helical potentiometer is typically about ten times better than the resistance value tolerance.

## OUTPUTS

The circuit of Fig. 1 provides good square waves and also linear triangular waves, both at 50 ohm output impedance. These outputs are adequate for many applications, since the triangular waves can

often be used instead of sine waves when their harmonic content is not disadvantageous.

Both of these output waveforms are superimposed on steady positive potentials. The latter can be removed by capacitive coupling except at low frequencies where it is difficult to obtain an adequate time constant to preserve the waveform. The average potential of either of the output waveforms can be made equal to earth potential by employing a power supply consisting of suitable positive and negative supply voltages both isolated from earth.

## TRIANGLE-TO-SINE CONVERSION

If a sine wave with a relatively low harmonic content is required, a diode-resistor shaping network may be employed. A fairly complex circuit is required if the shaping must be carried out reasonably accurately. A simpler solution involves the use of the conversion circuit described below.

At a fixed gate voltage, the first part of the drain characteristic of a junction field effect transistor (FET) approximates to half a sine wave. However, further increase of the drain voltage produces little effect on the drain current. The first part of this characteristic can be employed to shape a triangular wave into a reasonably good sine wave. If a triangular wave is applied to this circuit the positive going part of this waveform will produce a drain current of half a sine wave. In order that both the positive and negative parts of the triangular wave shall produce the corresponding parts of a sine wave, the type of circuit shown in Fig. 4 may be employed. This utilises the fact that the drain and source electrodes of an FET are essentially interchangeable.

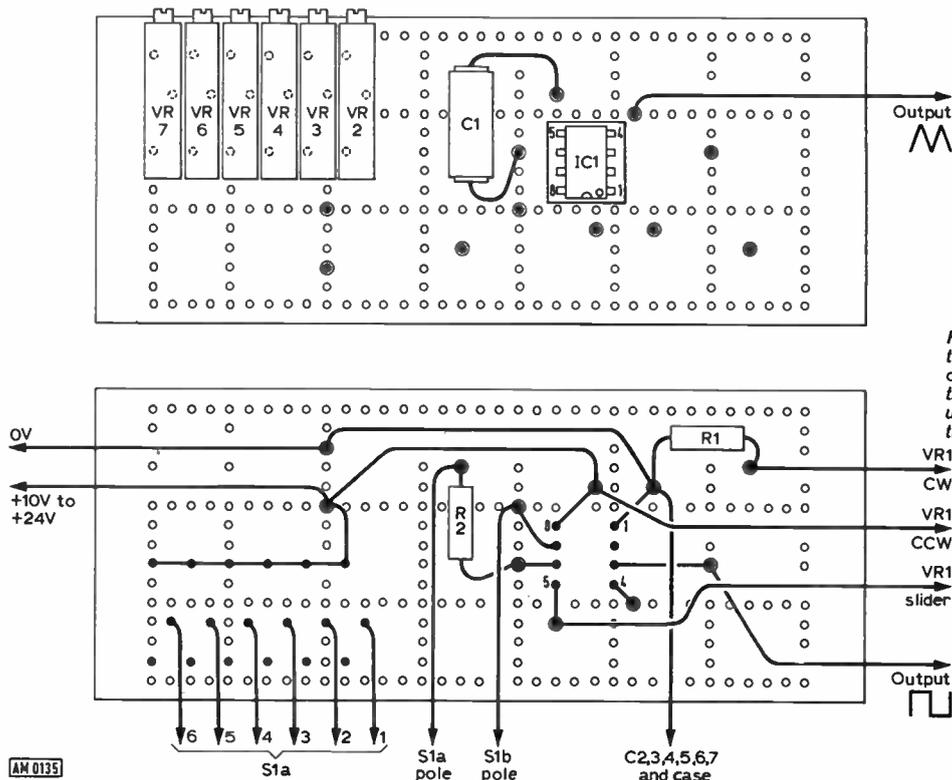


Fig. 3: Veroboard pins are used to support the few components on the circuit board. The trimmer potentiometers are used to adjust the calibration of the six frequency ranges.

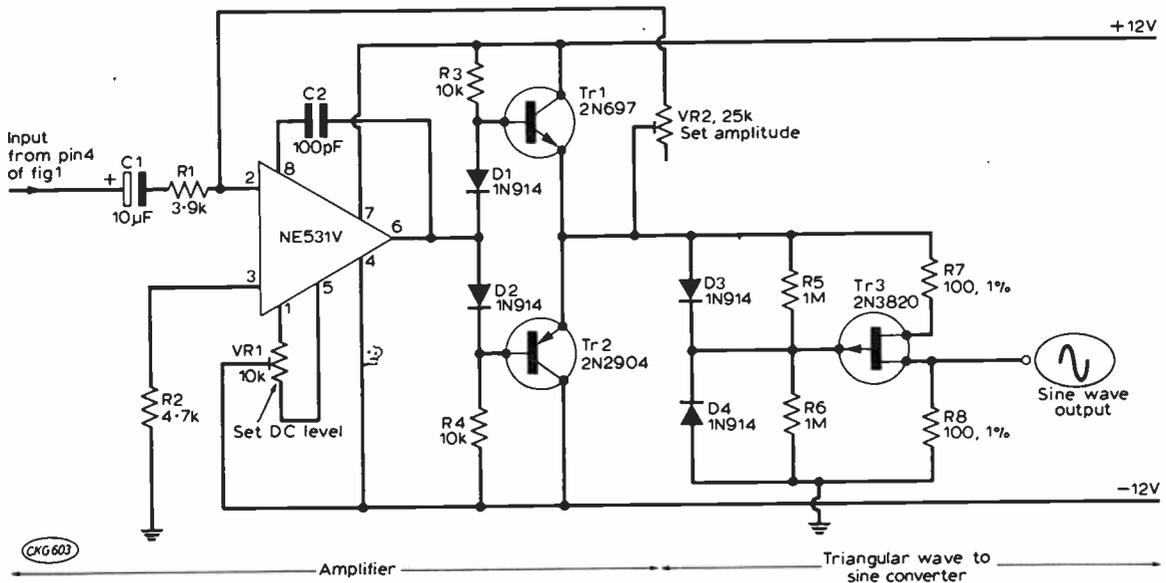


Fig. 4: Suitable circuit for converting a triangular wave to a sine wave.

## PRACTICAL SINE CONVERTERS

It should be clear that the amplitude of the triangular wave applied to the circuit of Fig. 4 is quite critical if one requires a good sine wave output. If the input to this circuit is too large in amplitude, the output pulses will have fairly flat sections in place of the normal sine wave peaks. If the input amplitude is too small, the output will be approximately the same form of triangular wave as the input.

It must therefore be possible to alter the amplitude of the triangular wave fed to the circuit of Fig. 4. In addition, the output impedance of the source of the triangular waves must be small and there must be no steady voltage superimposed on the triangular waves. An amplifier of variable gain and of low output impedance is therefore employed between the output of the 566 circuit and the input of the triangle-to-sine converter.

## CONVERTER CIRCUIT

The circuit of a practical triangle-to-sine wave converter is shown in Fig. 4. The triangular wave input from the circuit of Fig. 1 is capacitively coupled to the input of a Signetics NE531V high slew rate operational amplifier; it therefore follows that this circuit is unsuitable for use at very low frequencies with the values shown, since the coupling time constant would be inadequate.


The complementary output transistors Tr1 and Tr2 provide a low impedance output to the converter circuit of Tr3. The preset potentiometer VR1 is set so that the potential at the emitters of Tr1 and Tr2 is zero volts when no input is applied to the circuit.

The voltage gain of the circuit of Fig. 4 from the input to the emitters of Tr1 and Tr2 is equal to the resistance of VR2 divided by R1. The amplified triangular wave is applied to the circuit of Tr3, the operation of which has already been discussed. The author found that the sine wave output voltage was of the order of 0.7V peak to peak and that it has no steady component superimposed on it.

The gain control, VR2, must be set carefully so that the output waveform shows minimum distortion, adjusting the gain whilst examining the output waveform by means of an oscilloscope. If, however, a waveform analyser is available, VR2 may be adjusted for minimum third harmonic distortion.

A satisfactory sine wave was obtained using fixed resistors for R7 and R8. However, one of these resistors may be replaced by a 50 ohm resistor in series with a 100 ohm preset trimmer so that the output may be adjusted for minimum second harmonic distortion (preferably using a waveform analyser). It should then be possible to obtain a sine wave output with very low distortion.

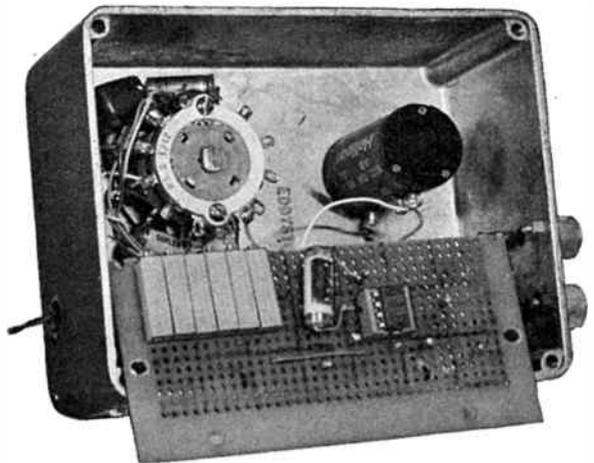The writer tried replacing the NE531V integrated circuit with a  $\mu$ A741V which has the same connections. It was found that the NE531V could operate at higher frequencies, but in neither case could satisfactory operation at 1MHz be obtained.



The secret of the direct frequency read-out lies in the use of the multi-turn Hellipot potentiometer, right centre.

A simple circuit using two cascaded emitter followers for driving an FET triangle-to-sine converter was published in the February 1973 issue of *Wireless World*. However, a circuit with voltage gain is required when the triangular wave output from a 566, operated from a 12V supply, is to be converted into a sine wave.

## RAMP WAVEFORM GENERATORS

The circuit of Fig. 1 can be easily converted into a generator which produces either a rising or a falling linear ramp waveform. At the end of each ramp the output quickly returns to its initial level and another ramp commences.

In order to produce a rising ramp waveform, the capacitor connected to pin 7 is allowed to charge, but at the end of the charging period it is rapidly discharged. The ramp waveform appears at pin 3 of the 566 in place of the triangular wave. A falling ramp is produced in a similar way; at the end of the discharging period, the capacitor connected to pin 7 is rapidly re-charged.

## RAMP CIRCUITS

Fig. 5 shows the components which must be added to the circuit of Fig. 1 to allow either rising or falling ramps to be produced. When the switch S2 is in position 1, the additional components shown dotted are not used and the circuit therefore provides the normal square and triangular output waveforms. When S2 is in position 2, a falling ramp waveform is generated, whilst in position 3 a rising ramp is formed. Short negative going pulses are available at pin 4 when S2 is in position 2 and short positive pulses when S2 is in position 3.

Let us now consider in detail the operation of the falling ramp generator when S2 is in position 2.

If the output from pin 4 is in its high voltage state, little current passes through D1 of Fig. 8. The base and emitter of Tr1 are therefore at about the same potential and this transistor passes little

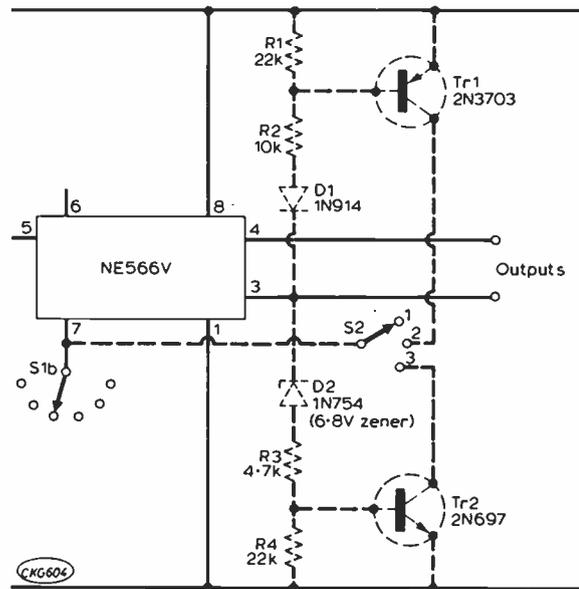


Fig. 5: Additional circuitry, shown dotted, to produce rising or falling ramp waveforms.

## ★ components list

R1 3.6kΩ 5% ½W R2 2.7kΩ 10% ½W  
 VR1 1kΩ 0.25% linearity (Beckman 'Helipot' Type 7246)  
 VR2-7 5kΩ trimmer pots (Beckman Type 89P)  
 C1 1nF C2 100pF C3 1nF  
 All 25V polystyrene  
 C4 10nF C5 100nF C6 1μF  
 All 25V polyester  
 C7 10μF 24V electrolytic

### Miscellaneous

IC1, NE566V (Low cost alternative is LM566—Ambit International), 8 pin DIL socket. S1, 2 pole, 6 way rotary switch. Turns counting dial for Helipot (Beckman Type RB). Die-cast box (Eddystone Type 6908P). Piece of plain veroboard. (Note: VR1 with dial and VR2-7 available from Athena SMC Ltd., 140 High Street, Egham, Surrey).

### Basic Components for Triangular-Sine Wave Converter

R1 3.9kΩ R2 4.7kΩ R3 10kΩ  
 R4 10kΩ R5 1MΩ R6 1MΩ  
 All 10% ½W  
 R7 100Ω R8 100Ω  
 Both 1% ½W  
 VR1 10kΩ VR2 25kΩ (Beckman Type 89P)  
 C1 10μF 15V C2 100μF 15V  
 D1-4 1N914 Tr1 2N697 Tr2 2N2904  
 Tr3 2N3820 NE531V (Low cost alternative is LM318H—check leadout connections)

### Basic Components for Ramp Wave Converter

R1 22kΩ R2 10kΩ  
 R3 4.7kΩ R4 22kΩ  
 All 10% ½W  
 D1 1N914 D2 1N754 (6.8V)  
 Tr1 2N3703 Tr2 2N697

current. The output from pin 3 therefore falls linearly with time, unaffected by the additional components.

When the output from pin 4 falls to its low voltage state, however, D1 conducts and the base of Tr1 becomes negative. This PNP transistor therefore conducts and rapidly charges the capacitor selected by S1b. The voltage at pin 3 therefore rises rapidly to its maximum value before a further falling ramp is generated.

The output from pin 4 consists of short negative going pulses which occur each time the ramp waveform at pin 3 rises to its maximum value. These waveforms are shown in Fig. 6. When the capacitor selected by S1b is small, the negative going pulses at pin 4 were found to be about 0.2μs in length.

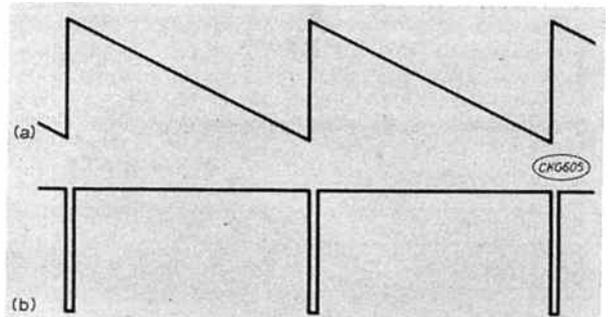


Fig. 6: Waveforms obtainable from the circuit of Fig. 5.




# Why pay more - look at our Fantastic Bargain Offer!

## PENTHOUSE
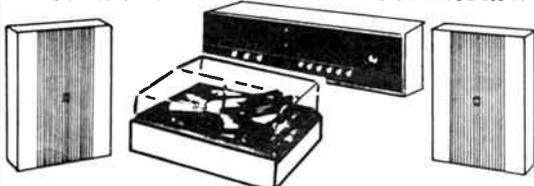
### A COMPLETE AUDIO SYSTEM

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder. 4 wavebands Long/Medium/Short/VHF. 8 watts per channel (music power) output. The latest BSR C129 3 speed Mono/Stereo record changer. Two white matching bookshelf speaker units. Also available in teak finish. **OUR PRICE £55-00**



Credit terms £5 00 deposit plus £2 50 p. & p. followed by 9 payments of £6 40. Total Credit Terms £62 60 SEND £7 50 TODAY

## KLINGER


FIVE NINETY THREE UNIT AUDIO SYSTEMS with BSR McDonald 3-speed Record Player, matching 4-unit Loudspeaker Systems and FREE Stereo Headphones.

High performance Stereo Amplifier designed for home entertainment at economical cost. Represents a considerable advance in solid state, high fidelity stereo amplifiers. Outstanding performance is allied to meticulous construction, comprehensive facilities, installation simplicity and attractive styling.

10 watt RMS per channel; push button selectors; tone controls; balance control; tape record and replay facilities. Stereo headphone socket on front panel with automatic speaker muting; Teak finish. Our price £75-00 + £2-50 p. & p. Credit Terms £7-50 deposit + £2-50 p. & p. 9 monthly payments of £8-70 (total £85-80) SEND £10-00 TODAY.



## THE AVON AUDIO SYSTEM

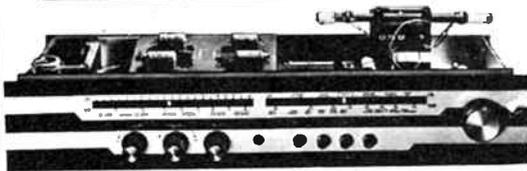

The uncabineted system is ideal as an economical replacement for an outdated chassis. Stereo Amplifier for Stereo/Mono record reproduction. Tuner with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

LATEST BSR STEREO/MONO RECORD CHANGER plays all types of 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKERS These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.



EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45-74, OUR PRICE £35-00. Credit Terms £3-50 deposit plus £2 Post & Packing followed by 9 payments of £4-10 (Total Credit Terms £44-40) Don't miss this bargain. **SEND £5-50 TODAY**

ALL EQUIPMENT COVERED BY OUR 12 MONTHS FULL GUARANTEE

## CALLERS WELCOME

100 Chase Side, Southgate,  
London N14 5PL  
Tel: 01-886 3733/9666

LEWIS radio

PW 3/74

### STILL at £42-50

Solartron CD 711S.2 Double Beam Oscilloscope DC-9 mc/s; 3 mw/cm; trigger delay; crystal calibrator; 4; flat faced tube, in good working condition. Carr. £1-50.

12" LONG PERSISTENCE CRT. Full spec. Price £7-50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5-50. P. & P. 25p. (Not cased, not calibrated.)

NEW WIDE RANGE WOBBLATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6 3V A.C. and use within minutes of receiving. All this for ONLY £5-75. P. & P. 25p. (Not cased, not calibrated.)

### 20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermostat stabilised. Ready to use. 9V supply required. £7-85 each. P. & P. 25p. (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each. P. & P. 5p. £1 worth of 'UFS'. Six Brand New capacitors all between 15V and 100V. Total capacitance not less than 7,000md. P. & P. 45p.

PHOTOMULTIPLIER type 931A £3-25 ea. P. & P. 25p.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 2 off 4pole 2 way etc.). 50p P. & P. 20p.

PLEASE ADD 10% V.A.T.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3-50.

Open 9 a.m. to 6.30 p.m. anyday.

**CHILTMead LTD**

7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech. College) Tel.: Reading 582605/65916

## BAKER 12" MAJOR £9-90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

## MAJOR MODULE KIT £12-50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in. NOTE—When ordering state 3 or 8 or 15 ohms.

### BAKER LOUSPEAKERS 100% BRITISH MADE

|                   |        |                     |        |                 |        |
|-------------------|--------|---------------------|--------|-----------------|--------|
| Regent 12 in. 15W | £9-90  | Superb 12 in. 20W   | £16-50 | New Group 50/12 |        |
| Major 12 in. 20W  | £9-90  | Group 25 12 in. 25W | £9-90  | 12 in. 50W      | £17-60 |
| Deluxe 12 in. 15W | £11-00 | Group 25 12 in. 35W | £9-90  |                 |        |

### BAKER LOUSPEAKER CO., BENSHAM MANOR PASSAGE

THORNTON HEATH, SURREY Tel. 01-684 1665

ALL PRICES INCLUDE V.A.T. HI-FI ENCLOSURE PLANS 42p

## MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary, Slide, Key Switches, I.F.'s, Tag Strips, Drive Drums, Springs, Handles, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels, etc., etc.

Save yourself £'s on these well selected parcels. 6lbs net weight £1-00. P. & P. 40p.

Brand new Wire-Wound Resistors 1-7 Watts Good selection 100 for £1. P. & P. 15p.

Assorted Computer Panels. These panels are exceptionally good value and contain a minimum of 75 Transistors, Slacks of Diodes, plus Trim Pots, Polyester Capacitors, Resistors and include a few I.C.'s. 10 panels for £1. P. & P. 27p.

Mullard Ferrite Cores LA3 100 to 500kHz 50p, LA4 10 to 30kHz 75p. LA 2100 3 to 200kHz 50p.

Mullard Electrolytic Capacitors, C432 4500µF, 25V 35p.

Please include 10% V.A.T. to total cost of goods.

MAIL ORDER ONLY

## XEROZA RADIO

1 EAST STREET, BISHOPS TAWTON, DEVON

When a large capacitor is in circuit, however, it takes longer to charge from the current passing through Tr1. Nevertheless, the time for which the waveform at pin 4 is in its low voltage state is a very small fraction of the total operating time.

The operation of the rising ramp generator, when S2 is in position 3, is rather similar. When the output at pin 4 is in its low voltage state, the zener diode D2 passes little current and Tr2 remains cut off. During this time the ramp waveform at pin 3 is rising.

When the voltage at pin 4 switches to its upper level, however, the zener diode conducts and Tr2 receives a positive bias at its base. This NPN transistor therefore conducts and rapidly discharges the capacitor selected by S1b. The potential at pin 3 therefore returns quickly to its lowest level and the ramp commences to rise again.

The output from pin 4 consists of short positive pulses which occur each time the ramp at pin 3 returns to its lowest level.

The rising ramp generator was found to give a poor waveform on the 1MHz range. However, the rising and falling ramp generators both operated satisfactorily on the other ranges and also at very low frequencies. The writer tried them at frequencies down to about 0.01Hz and at such frequencies the waveform takes a fraction of a second to return at the end of each ramp.

When either of the ramp generators is employed, the one half of the triangular waveform is eliminated. The frequency of oscillation of the 566 is therefore approximately doubled when S2 is in position 2 or 3. Constructors who intend to use the unit mainly for ramp waveform generation may wish to calibrate the unit so that the ramp frequency can be read directly from the Helipot dial. The dial reading must then be halved to obtain the frequency of the triangular or square wave.

## APPLICATIONS

The fundamental frequencies from the waveform generator can be used to test the functioning of audio amplifiers; they also cover the long wave band and the low frequency end of the medium wave band. In addition, the outputs contain harmonics (mainly odd harmonics) which can be used to test the functioning of radio receivers throughout the medium wave band and also at somewhat higher frequencies.

Both the triangular waves and the ramp waveforms are very suitable for the detection of cross-over distortion in audio amplifiers, since these waveforms are essentially linear. If the triangular wave output is fed to the input of an audio amplifier which introduces cross-over distortion in its output stage, the type of waveform shown in Fig. 7a is obtained. The values of the resistors in the audio amplifier which control the quiescent current in the output stage may be altered so as to increase this current slightly; the cross-over distortion should disappear when the quiescent current is sufficient.

It is easier to detect cross-over distortion when using the triangular or ramp waveforms than when the more conventional sine wave is employed. A frequency in the mid-audio region is ideal for this test (perhaps 1kHz). The linearity of the waveform on the oscilloscope screen may be measured by placing a straight edge along the tips of the waveform.

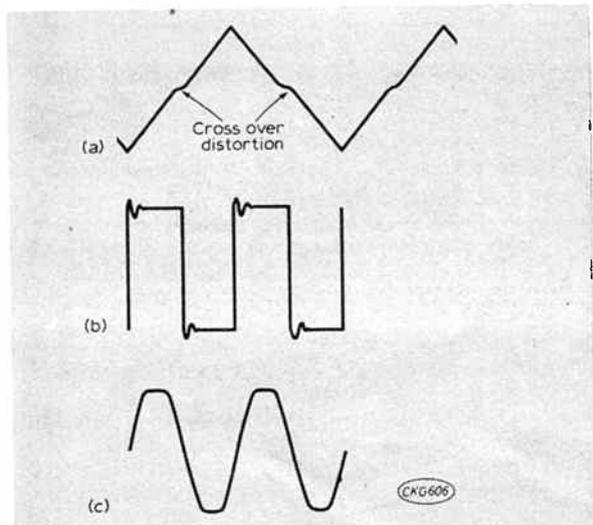


Fig. 7a-b-c: Waveforms at the output of an audio amplifier using input signals from the waveform generator.

The square wave output is also very useful for testing audio amplifiers. At fairly high frequencies one may examine the output from an amplifier for ringing of the type shown in Fig. 7b. Ideally there should be no overshoot or ringing. An audio amplifier which can faithfully reproduce a square wave at a frequency of about 10kHz must have a good frequency response in the high audio frequency region since square waves contain many harmonics and will be reproduced satisfactorily only if the amplifier has a fairly level response at frequencies of up to at least three times the fundamental frequency of the square wave.

If an audio amplifier has only a moderately good high frequency response, the corners of the output waveform will be rounded off at 10kHz, as shown in Fig. 7c. An approximate value for the frequency response of the amplifier may be obtained by estimating the time taken for the output waveform from the amplifier to rise from 10% to 90% of its final value. The maximum frequency at which the response is reasonably constant is of the order of  $1/(3 \times \text{the rise time})$ . If the rise time of a square wave is very short, one sees only the lines at the top and bottom of the oscilloscope display, the rising and falling parts of the waveform being so short that they are barely visible.

One can also use the square wave output from the 566 unit to examine the low frequency response of audio amplifiers. As one reduces the frequency of the square wave, the upper and lower horizontal parts of the output waveform do not remain horizontal, but develop a definite slope. At very low frequencies, a differentiated waveform will be obtained. The input of the oscilloscope marked 'DC' should be used for these low frequency tests, since the 'AC' input is connected to a series capacitor inside the oscilloscope which may distort the waveform.

In the audio amplifier tests discussed above, it has been assumed that the amplifier under test has a volume control at its input which can be adjusted to provide the required signal output level. At high levels it will be necessary to include a series capacitor in the input circuit to block the steady voltage at the 566 outputs. In this case care should be taken to ensure that the coupling time constant is adequate for the lowest frequency to be employed.

# DRY BATTERY CHARGER

R.A. Butterworth

**M**OST of us either make or buy a mains supply unit to operate our battery tape recorders, receivers etc., when used at home to save the cost of dry batteries. However batteries are still needed around the home and unfortunately they seem to cost more each time. One could of course use rechargeable cells but they are expensive and need a rather special charging unit which is also expensive.

If we could get a few more hours out of our dry battery we could cut our costs considerably, even one more 'run' would be equivalent to cutting the cost by a half. With the charging units described here two, three or more 'lives' can be given to a set of batteries, perhaps not quite as long a period of operation as the first but certainly for periods long enough to make the building of a charger show an economical return for the effort involved.


The idea of reforming dry cells is by no means new. Investigation of the possibilities were made as long ago as the early 1950's with encouraging results. With modern methods of manufacture and materials, the life of the primary cell can be considerably extended if a few basic rules are born in mind. These are:

- 1 The battery must be charged before its voltage (on load) drops from 1.5V to below 1V.
- 2 It must be put on charge as soon as possible after being removed from service and put into service as soon as possible after re-charge.
- 3 It is not economical to charge a single unit, a 1.5V 'pen light' HP7 for example. Therefore it is better to have one set of batteries in service and another on charge.
- 4 The charging rate should be adjusted to distribute the charge, in other words avoid heating up the cell by charging at too high a current.
- 5 If there is the slightest suspicion of battery leakage throw them away or you will have a horrible mess to clear up.

The cylindrical types like the U2, U11 and HP7, respond much better than the layer batteries, such as the PP3. The use/charge cycle is less than half that of the cylindrical types. The table gives details for popular zinc-carbon types which have responded successfully to several use/charge cycles with the equipment shown.
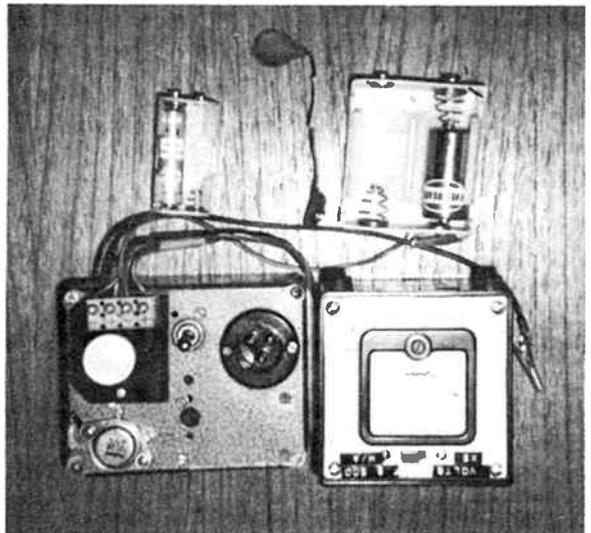
## Battery holders

Standard battery holders can be used to hold the cells whilst charging in blocks of 2, 4, or 6. From experience it would appear that, after setting at the current shown, if after the first couple of hours there



is no drop in the charging current, then discard the battery as the electrolyte has probably dried out. If the batteries get appreciably warm or show signs of leaking throw them out. Different sets of batteries have given a different number of cycles. This, the author believes, is due to 'freshness' of the unit cells when first purchased; in other words how long they had been on the shelf in store.

## DRY BATTERY CHARGING

| Battery | Use                         | No. of Cells | Charging Current mA |      | Approx. hours of charging | No. of cycles |
|---------|-----------------------------|--------------|---------------------|------|---------------------------|---------------|
|         |                             |              | Min.                | Max. |                           |               |
| U2      | Torches, Hand lamps, Radios | 2            | 150                 | 300  | 5                         | 3             |
|         |                             | 4            |                     |      |                           |               |
|         |                             | 6            |                     |      |                           |               |
| U7      | Small Torches, Radios       | 1 or 2       | 100                 | 150  | 4                         | 4             |
|         |                             | 4            |                     |      |                           |               |
| U11     | Cassette Tape Recorders     | 4            | 100                 | 250  | 5                         | 4             |

In the circuits shown in Figs. 1 and 2 it will be noted that very little smoothing of the d.c. output has been incorporated. This is deliberate; investigation has shown that it is advantageous to have a little a.c. present. This "dirty d.c." appears to shake up the electrolyte and therefore assists in the reforming.

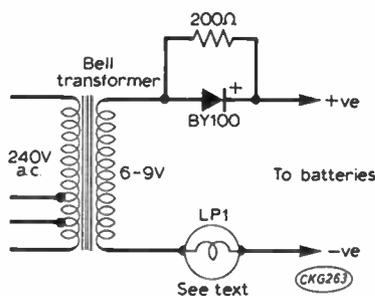


Fig. 1: Circuit shows a simple charging unit.

—continued on page 1061

# MAPLIN ELECTRONIC SUPPLIES

★ SAME DAY SERVICE



Model 120

**LARGE OR SMALL Centurion**

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others' mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white.



Model 320

| Model | W  | H  | D     | Price |
|-------|----|----|-------|-------|
| 120   | 8  | 6  | 6     | £1.85 |
| 220   | 8  | 24 | 3 1/2 | £2.85 |
| 221   | 8  | 6  | 6     | £2.80 |
| 320   | 12 | 8  | 12    | £5.00 |

Chassis for model 320 £1.75 extra  
Please send s.a.e. for free illustrated leaflet.

## ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

### THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3-7in. x 4-5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2T (with tremulant) ONLY £14.25.  
DMO2 (without tremulant) £12.25.  
SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.

## TRANSISTORS, DIODES & IC's.

|         |       |         |     |                |        |
|---------|-------|---------|-----|----------------|--------|
| AC127   | 25p   | BF194   | 15p | OA90           | 7p     |
| AC128   | 20p   | BFY51   | 13p | OA91           | 6p     |
| AC176   | 17p   | MPP102  | 36p | 1N914          | 4p     |
| AD149   | 47p   | OC44    | 20p | 1N4148         | 8p     |
| AD161/2 | 69p   | OC71    | 20p | 1N4001         | 6p     |
| BC107   | 10p   | T1843   | 28p | 1N4002         | 6 1/2p |
| BC108   | 10p   | 2N1711  | 24p | 1N4003         | 7p     |
| BC109   | 10p   | 2N2219  | 25p | 1N4004         | 7 1/2p |
| BC147   | 10p   | 2N2646  | 46p | 1N4005         | 8p     |
| BC148   | 10p   | 2N2905  | 33p | 1N4006         | 8 1/2p |
| BC149   | 12p   | 2N2907  | 25p | 1N4007         | 8p     |
| BC168   | 13p   | 2N2926G | 10p | W005           | 30p    |
| BC169C  | 18p   | 2N2926Y | 10p | W04            | 33p    |
| BC182L  | 10p   | 2N2926G | 10p | 741C 8-pin     | 38p    |
| BC204   | 14p   | 2N3053  | 18p | D.I.L.         |        |
| BC209C  | 14p   | 2N3055  | 49p | 741C 14-pin    | 45p    |
| BD131   | 45p   | 2N3819  | 24p | D.I.L.         |        |
| BD132   | 54p   | AA118   | 7p  | D.I.L. Sockets |        |
| BD131/2 | £1.20 | BY127   | 16p | 8-pin          | 20p    |
| BD135   | 38p   | BY164   | 49p | 14-pin         | 15p    |

See our catalogue for our full range of transistors. 74 series I.C.'s bridges etc.

## CAPACITORS

Sub-miniature Axial lead electrolytic

| Mfd V     | Price | Mfd V  | Price   |
|-----------|-------|--------|---------|
| 1.5 63 6p | 88    | 6.3 6p | 6p      |
| 2.2 63 6p | 88    | 10 6p  | 10p     |
| 3.3 63 6p | 100   | 4 6p   | 10p     |
| 4.7 63 6p | 100   | 10 6p  | 10p     |
| 6.8 40 6p | 100   | 25 8p  | 47p     |
| 6.8 63 6p | 100   | 40 6p  | 47p     |
| 10 25 8p  | 100   | 63 12p | 47p     |
| 10 63 6p  | 150   | 6.3 6p | 6.3 10p |
| 15 16 6p  | 150   | 16 8p  | 68p     |
| 15 40 6p  | 150   | 25 8p  | 68p     |
| 15 63 6p  | 150   | 40 10p | 68p     |
| 22 10 6p  | 150   | 63 12p | 1000    |
| 22 25 6p  | 220   | 4 6p   | 1000    |
| 22 63 6p  | 220   | 10 6p  | 1000    |
| 33 6.3 6p | 220   | 16 8p  | 1000    |
| 33 16 6p  | 220   | 25 10p | 1500    |
| 33 40 6p  | 220   | 40 12p | 1500    |
| 47 4 6p   | 220   | 63 18p | 1500    |
| 47 10 6p  | 330   | 4 6p   | 2200    |
| 47 25 6p  | 330   | 10 6p  | 2200    |
| 47 40 6p  | 330   | 16 10p | 3300    |
| 47 63 6p  | 330   | 63 22p | 4700    |

## OMNIUM GATHERUM

|  |       |
|--|-------|
| PP3, 6 etc. battery clip dual min.   | 9p    |
| PP1, 9 etc. battery clip separate per pair                                 | 6p.   |
| Pair crocodile clips 1 red, 1 black insulated sleeve.                      | 7p    |
| Solder Multicores 22swg 10 metres  | 20p   |
| Silicone grease in special dispenser 20ml.                                 | 43p   |
| Red neon 240V panel mounting   | 25p   |
| Lacing Cord Strong rayon cored PVC 25m.                                    | 43p   |
| Panel fuse holders 20mm 20p; 1 1/4"  | 30p   |
| Transformers   |       |
| LT700 min. output transformer Pri. 1.2k Ω Sec. 5 Ω 200mW                   | 35p   |
| Sub-min. Mains Transformer 6.0-6V 100mA                                    | 95p   |
| 12.0-12V 60mA  | 95p   |
| Size: Both approx. 30 x 27 x 23mm.   |       |
| Min. Mains Transformer (Size: 46 x 31 x 38mm) 0-12V 250mA, 0-12V 250mA     | £1.35 |
| Mains transformer MT3AT Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A         | £2.48 |
| Mains Transformer MT206AT Pri. 200-220-240V, Sec. 0-15-20V 1A, 0-15-20V 1A | £3.10 |

Also in stock: Wide range of brass and nylon nuts, bolts and washers + solder tags, shakeproof washers etc.

## PLUGS AND SOCKETS



|  |  |                                 |  |
|--|--|---------------------------------|--|
| <b>DIN PLUGS</b>                                 | <b>MAINS</b>                             | <b>R88 8 way chassis socket</b> | <b>Std. 1/4" stereo plug</b>   |
| 2 pin (1 nat) 8p                                 | P360 3 pin 15A line socket. Per pair 24p | 52p                             | Plastic 18p  |
| 3 pin 9p   | SA 2190 3 pin 5A chassis plug 17p        |                                 | Screened 25p   |
| 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 10p | SA 1802 Line socket for above 19p        | <b>PHONO</b>                    | Open mono socket 1/4" 10p; Moulded mono socket 1/4" with 2 break contacts 18p; Moulded stereo socket 1/4" with 3 break contacts 18p; 3.5mm. plug plastic 8p; screened 11p; open socket 8p. |
| <b>DIN Sockets</b>                               | <b>McMURDO</b>                           | <b>JACK</b>                     |  |
| 2 pin 6p   | RP8 8 way chassis plug 36p               | Std. 1/4" mono plug Plastic 18p |  |
| 3 pin, 4 pin, 5 pin (240°), 6 pin 7p             |  | Screened 17p                    |  |

## POTENTIOMETERS

Rotary miniature carbon track 1/4" spindle

Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p

|  |  |
|--|--|
| <b>Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 38p.</b> | <b>Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 23p</b> |
| <b>PRESETS</b>   |  |
| Sub-miniature 0-1W   |  |
| 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p        |  |

Wirewound 10% 1W 1/4" spindle 10, 50, 100R 84p; 250, 500, 1k, 5k 83p; 10k, 87p; 25k 40p; 50k 44p.

## RESISTORS

|  |              |
|--|--------------|
| Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12        | 1p           |
| Carbon Film 1/4W 5% 1Ω to 10G; 10% 1.2M to 10M E12 & E24 | 1p           |
| Carbon Film 1W 5% 10Ω to 10M                             | E12 & E24 1p |
| Metal Oxide 1/4W 2% 10Ω to 1M                            | E12 & E24 4p |
| Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms                | E12 10p      |
| Wirewound 2 1/2W 5% 1ohm to 270ohms                      | E12 10p      |

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

## WE KNOW YOU NEED IT!



The MES 1974 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY.

You'll be IMPRESSED with our POST FREE ordering system, EXCITED by our BIG VALUE discount vouchers, STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

## KNOBS

All 1/4" shaft. Grub screw fixing

|   |                         |                         |   |                         |
|---|-------------------------|-------------------------|---|-------------------------|
| <b>K30/1 (13mm) 24p</b>                   | <b>K30/3 (17mm) 22p</b> | <b>K30/2 (13mm) 28p</b> | <b>BK12 32mm long, black pointer with white stripe 6p</b> | <b>K30/6 (32mm) 41p</b> |
| <b>F18 (26mm) with numbered skirt 21p</b> | <b>F12 (33mm) 21p</b>   | <b>MK50 (34mm) 27p</b>  | <b>CK4 (36mm) 14 1/2p</b>                                 |                         |

## SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p. Mains rotary DPDT 250V 2A 20p.

|  |  |
|--|--|
| <b>Push to make non-locking 12p</b>            | <b>Slide Miniature DPDT 9p</b>   |
| <b>Toggle 250V 1.5A with ON/OFF plate 25p.</b> | <b>Sub-miniature toggle DPDT (12 x 12.5 x 15mm excl. toggle) 250V 3A 61p</b> |

**VAT**

Please add 10% to the final total.

**Post & packing FREE in U.K.**

(10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. PHONE SOUTHDEN (0702) 44101

# YOU AIN'T HEARD NOTHIN' YET !!

... until you tune in to stereo  
perfection with 'Varicap'



'p.e.' f.m.  
varicap stereo tuner

Size approx.  
8 1/2" x 2 1/2" x 6 1/2"

This elegant and practical stereo tuner features push button 'spot-on' tuning with up to five simple pre-set stations (no difficult tuning dial and drive cord). It's easy 'no problem' construction requires only a few simple setting adjustments with a O.C. Voltmeter. It incorporates NEW pre-set modules for R.F. and I.F. circuits, this eliminates the need for the usually difficult circuit alignment.

All this, coupled with the latest Motorola high efficiency, Integrated Circuit 'phase lock loop' stereo decoder and automatic stereo lamp indicator, ensures perfect stereo reception.

The 'Varicap' is, in our opinion, THE most easily constructed stereo tuner available which will achieve professional results.

The kit comprises Fibre glass P.C. board, elegant slimline leak vaneer cabinet, brushed aluminium front panel, push buttons, instructions, in fact everything you need.

We also supply any of these kit components as separate items.

**Total kit price ONLY £28.50 (inclusive of VAT and postage).**

**IDEAL FOR USE WITH THE 'TEXAN', 'GEMINI' OR ANY OTHER GOOD QUALITY STEREO AMPLIFIER.**

### PARTS FOR PRACTICAL WIRELESS PROJECTS:

After many requests, Electro Spares are supplying lists of components for ALL projects featured in 'Practical Wireless' from July 1973 issue onwards. We regret that we cannot supply lists for projects published before this date.

All you have to do is send us a stamped addressed envelope, not less than 9" x 4", stating which project is of interest to you. We will then forward you an individually priced list of the components required, there is, of course, no necessity to purchase a full kit, you may purchase only the parts you require at any one given time. We believe this method of 'one source' buying can save you time and postage—AND THAT MEANS MONEY !!

**ALL COMPONENTS SUPPLIED BY ELECTRO SPARES ARE NEW, BRANDED PRODUCTS OF REPUTABLE MANUFACTURERS AND THEREFORE CARRY THE MAKERS FULL GUARANTEE.**

### 'P.E.' 'GEMINI' STEREO AMPLIFIER

The 'Gemini' is a quality hi-fi stereo amplifier for the home constructor, featuring a genuine 30 watt R.M.S. per channel output into 8 ohms. Total harmonic distortion of 0.02% and a frequency response (-3dB) 20Hz - 100kHz, at all power levels.

We are continuing to supply components for this fabulous amplifier, which is now recognised as practically THE ultimate in High-Fidelity.

We know no better unit for the home constructor—hundreds have been supplied throughout the world.

Electro Spares have available a booklet containing full specification, complete constructional information, wiring diagrams and fault finding guide etc.

The price is 55p + 4p postage, along with which we will send you our new LOW PRICE LIST. Price list available separately on receipt of a large S.A.E.

Our new Mail Order department address is set below. We aim for quick, efficient service—or why not pay us a call, we make all enthusiasts welcome and there are no parking problems.

# ELECTRO SPARES

288 ECCLESALL ROAD  
SHEFFIELD S11 8PE  
Tel. (0742) 668888

es

'The Component Centre of the North'

### PLUGS & LEADS

|                             |     |
|-----------------------------|-----|
| Plugs                       |     |
| Pack 107 5 pin Din          | 22p |
| Pack 108 3 pin Din          | 20p |
| Pack 135 1/2" jack          | 27p |
| Pack 130 1/2" jack Stereo   | 50p |
| Pack 103 Loudspeaker Plug   | 17p |
| Pack 100 Phono Plug         | 7p  |
| Pack 230 3 pin Socket       | 25p |
| Pack 236 5 pin Socket       | 33p |
| Pack 234 Loudspeaker Socket | 33p |

|   |       |
|---|-------|
| Ready-made Leads                        |       |
| 3 pin to 3 pin Din                      | 70p   |
| 3 pin to open end                       | 55p   |
| 5 pin to 5 pin Din                      | 90p   |
| 5 pin to open end                       | 70p   |
| 5 pin to 4 phono plugs                  | £1.00 |
| Speaker lead Din to spade 12ft          | 40p   |
| Extension lead Din plug to socket 12ft. | 70p   |
| All leads approx. 6ft. in length        |       |

### DIAMOND STYLI

|   |            |
|---|------------|
| 8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8.All at 80p each. |            |
| Double Diamond  | £1.25      |
| Diamond suitable for Orbit NM22; G800; M3D                  | £2.25 each |

### CARTRIDGES

|                      |       |
|----------------------|-------|
| Goldring G800        | £6.00 |
| Orbit NM22           | £4.00 |
| Shure 75/6           | £6.00 |
| Sonotone 9TAHC (Dia) | £2.00 |
| Sonotone 8T4A (Dia)  | £1.50 |
| Ronnette 105 (Dia)   | £1.25 |

All prices include VAT and postage

### RECORD CARE

|                                  |       |
|----------------------------------|-------|
| Cecil Watts Dust Bug             | £1.20 |
| Parastatic Disc Preener          | 45p   |
| Antistatic Fluid                 | 20p   |
| Dust Bug Spares (Brush & Roller) | 15p   |

### CASSETTE TAPES

|                                  |       |
|----------------------------------|-------|
| Audio-Magnetic C60 Qty 3 6 10 20 |       |
| Price/£1.00/£1.90/£3.20/£6.30    |       |
| Cassette Caddy                   | £1.20 |
| Cassette Head Cleaner            | 35p   |

### ZONAL ILFORD TAPE

|  |       |
|--|-------|
| 5" Standard 600ft                      | 25p   |
| 5 1/2" Standard 900ft                  | 50p   |
| 7" (Plain boxed) 1200ft                | 60p   |
| 7" (Westminster Boxed) 1800ft          | £1.25 |
| 7" Reel of Leader Tape (Blue or green) | 75p   |

### HEADPHONES

|                  |        |
|------------------|--------|
| Sennheiser HD414 | £12.50 |
| AKG K50          | £6.50  |
| Beyer DT485      | £35.00 |

### MICROPHONES

|                        |         |
|------------------------|---------|
| AKG D109               | £11.50  |
| AKG D202E1             | £39.50  |
| AKG D190C              | £17.00  |
| AKG D190E              | £18.20  |
| AKG D224               | £50.00  |
| Sennheiser MD211N      | £45.00  |
| Sennheiser MD413N      | £27.00  |
| Sony ECM50             | £85.00  |
| Audio RMS7F Radio Mike | £210.00 |

### SPEAKERS

|                      |       |
|----------------------|-------|
| E.M.I. 350 Kit 8ohms | £8.20 |
| E.M.I. 450 Kit 8ohms | £4.50 |

## J. J. Francis (Wood Green) Ltd

MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS Telephone; Matching 476

## NOW! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified HOME STUDY method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

|  |                          |  |                          |
|--|--------------------------|--|--------------------------|
| Practical Radio and Electronics (Technatron) | <input type="checkbox"/> | Radio Amateurs                                   | <input type="checkbox"/> |
| Radio and Television                         | <input type="checkbox"/> | City and Guilds Radio and T.V. Electronics Mech. | <input type="checkbox"/> |
| General Radio and T.V. Engineering           | <input type="checkbox"/> | City and Guilds Electrical Engineering Practice  | <input type="checkbox"/> |
| Radio servicing, maintenance and repairs     | <input type="checkbox"/> | Gen. Electrical Engineering Society of Engineers | <input type="checkbox"/> |
| Colour T.V.                                  | <input type="checkbox"/> | (Elec. Eng.)                                     | <input type="checkbox"/> |
| Practical T.V.                               | <input type="checkbox"/> | C. & G. Elec. Tech.—Primary                      | <input type="checkbox"/> |
| Electronic Engineering                       | <input type="checkbox"/> | Electrical Installations and Wiring              | <input type="checkbox"/> |
| Television Maintenance and Servicing         | <input type="checkbox"/> |  |                          |

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY  
DEPT. BPW 70, ALDERMASTON COURT, READING RG7 4PF

POST THIS COUPON FOR FREE BOOK

27 BPW 70

NAME .....

ADDRESS .....

.....AGE.....

SUBJECT OF INTEREST .....

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

## Charger units

Fig. 1 shows a simple unit which can be easily put together and used to try out the idea. A good quality bell transformer, BY100 diode, m.e.s. lamps, lamp holder and a 220Ω 1W resistor and you are in business. The writer found this unit successful but it lacked flexibility. If the bell transformer shown in Fig. 1 has various outputs then the number of cells to be charged can be varied and by changing the lamp the charging current can be varied within limits.

Fig. 2 is a more elaborate unit and in the author's case serves two purposes; A dry battery charger and mains unit for various equipment used in the shack. Should additional smoothing be required then it is a simple matter to add this. It is advisable to install the meter permanently so that the charging current can be monitored. A d.p.d.t. switch with a suitable shunt series resistor would enable both voltage and the current to be monitored. Diode D6 provides for reversal protection and prevents the battery discharging through the 470Ω resistor.

Zinc-carbon batteries are very amenable to re-charging.

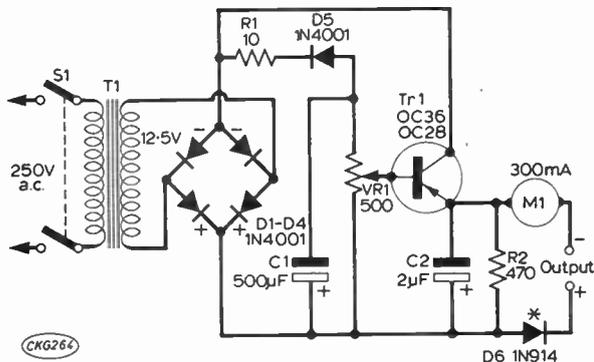


Fig. 2: A more elaborate design.

### ★ components list (Fig. 2)

|       |                                      |
|-------|--------------------------------------|
| R1    | 10Ω ½W                               |
| R2    | 470Ω 1W                              |
| VR1   | 500Ω 3 W linear wirewound            |
| C1    | 500μF 20V                            |
| C2    | 2μF 20V                              |
| Tr1   | OC36, OC28 or similar rating         |
| T1    | Mains transformer 12.5V 1A secondary |
| D1-D4 | 1N4001 diodes                        |
| D5    | 1N4001 diode                         |
| D6    | 1N914 diode (see text)               |
| M1    | Meter 300mA f.s.d.                   |
| S1    | Double-pole on/off toggle switch     |
| LP1   | 3.5V or 6.5V 0.1/0.2A (Fig. 1)       |

## NEXT MONTH

An Automatic Battery Charger for 12 volt car batteries.

# TELEVISION

## IN THE MARCH ISSUE

### ASSEMBLING A MODULAR COLOUR SET

There are various ways of going about building a colour receiver. One approach is to make use where possible of manufacturers' surplus units. David Robinson describes the set he built on this basis and how the various problems of interfacing different units not originally intended for use together were overcome.

### LOG-PERIODIC SET-TOP AERIAL

A simple log-periodic set-top aerial can be made using printed circuit board. Full constructional details will be provided.

### TV SET SAFETY

With the introduction of the BEAB television receiver testing system and BS415:1972 there has been a tightening up in safety requirements. It is essential that anyone handling TV sets should be aware of what is involved. A detailed account starts next month.

### FAULT FINDING

John Law looks at the power supply and line timebase circuits used in BRC 16in. dual-standard portable models. These make excellent second sets.

### PHASE IN COLOUR TV

The phase of the chrominance signal indicates the colour being transmitted: phase is thus the key to colour television. A special article next month describes the basic technique and PAL signal processing, paying particular attention to practical points that are not always made clear.

### PLUS ALL THE REGULAR FEATURES

Details of the March issue are subject to the current national situation at the time of going to press.

TO .....  
(Name of Newsagent)

Please reserve/deliver the MARCH issue of TELEVISION (25p) and continue every month until further notice.

NAME .....

ADDRESS .....

# PRODUCTION LINES

colin riches

## JOSTY KITS

Our Advertisement Manager has asked me to point out that Swanley Electronics will not be supplying "Josty" kits as per their December advertisement.

## HEATHKIT CATALOGUE


The latest catalogue from Heath (Gloucester) Limited contains details of the company's kits and some new models featured for the first time include the GR-990 12in. Black and White Television kit for either 12V or mains operation; the GD-39 Home Intrusion Alarm, disguised as an unobtrusive book — an ultrasonic burglar alarm/surveillance system; the CR-1008 a.m. Radio and the CM - 1045 Small Engine Tune - up Meter.

Also included are the 10-104 Solid State 15MHz Oscilloscope; IB-1103 180MHz Frequency Counter; the GC-1005 Electronic Digital Clock which incorporates a 'snooze' alarm; the CR9502 Push-Button a.m. Car Radio and the IC-2108 Desk Top Electronic Calculator.

Readers may obtain their free catalogue by writing to *Heath (Gloucester) Limited, Bristol Road, Gloucester, GL2 6EE.*



## SCREW DRIVING BOON

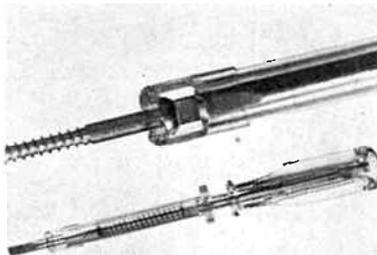

Thunder Screw Anchors Ltd. announce an addition to their range of screwdrivers by the introduction of four screwholding screwdrivers. Two are suitable for slotted head screws and two for recessed head screws, their dimensions being  $8\frac{1}{2}$ in. and  $9\frac{1}{4}$ in. overall length,  $3/16$ in. and  $1/4$ in. blade diameter respectively. The screw is firmly held at the tip of the screwdriver by sliding the spring-loaded shank over the head of the screw, (see picture) leaving one hand free to hold the article to be fixed. It is possible to fix screws or bolts in the most difficult of places, where to hold a screw in the hand might normally be impossible.

Prices, excluding V.A.T. are 20372 and 20376 69p each, 20374 and 20378 79p each.

We understand that due to the shortage in the foreign plastics industry, supplies of these screwdrivers may be subjected to extended delay. However, this firm does have some further useful and novel tools that would be of interest to readers. Supplies are through retail outlets. *Thunder Screw Anchors Ltd., Victoria Way, Burgess Hill, Sussex, RH15 9NF.*

## MICROELECTRONICS

We apologise to Microelectronics for being unable to include their advertisement in the Feb. issue. If readers refer to this month's issue, page 1028, they will see that the company markets the Minicomp 100 Random Number Selector. When the button

on the front panel is pressed, numbers are displayed at high speed on a Nixietube read-out before a random number is displayed—in effect a miniature "ERNIE".

The circuit includes 6 TTL logic i.c.'s and three transistors and the manufacturers say that typical applications include number selection for dice, roulette, bingo etc. Price of the Minicomp 100 kit is £42.50. A fully assembled version is available at £45.00.—*Microelectronics, 51 Mexfield Road, London, SW15 2RG. (Tel. 01-870 2368).*

## ONE-HAND DESOLDERER

When desoldering, have you ever wished you had three hands? Well, here is something that will brighten your day!

Only one hand is required to operate the Picard soldering/desoldering iron. The whole body of the tool forms a suction tube which is pressed down towards the job during heating and released to produce suction.

The unit has a rating of 20W and uses an 8V supply, a transformer being available if required. For desoldering, it reaches a temperature of 340°C in four minutes. Only three minutes' heating is however required for soldering. The heating element is sealed with a ceramic insulating paste which, by preventing burning and corrosion, prolongs its life quite considerably.

The bit is made of alloy steel and molten solder is sucked through it by the release of the spring-loaded body. The faster the release, the stronger the suction. The solder collecting chamber is easy to clean out while the bit is still warm.

A soldering stand is supplied with every tool and the price of the complete unit is £6.49. *Henry Picard & Frere Limited, 357/359 Kennington Lane, London, S.E.11.*



# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



## Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1-05p** P & P 45p each

### TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **27 1/2p** POST & PACKING 16p

## Tested and Guaranteed Paks



- B79 4 IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic 55p
- B81 10 Reed Switches, 1" long, 1/4" dia. High Speed P.O. type 55p
- B99 200 Mixed Capacitors. Approx. quantity, counted by weight P & P 15p 55p
- H4 250 Mixed Resistors. Approx. quantity, counted by weight P & P 15p 55p
- H35 100 Mixed Diodes, Germ, Gold bonded, etc. Marked and Unmarked. 55p
- H38 30 Short lead Transistors, NPN Silicon Planar types 55p
- H39 6 Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945 55p
- H41 2 Sil Power transistors comp pair BD131/132 55p



## Unmarked Untested Paks

- B1 50 Germanium Transistors PNP, AF and RF 55p
- B66 150 Germanium Diodes Min. glass type 55p
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202 55p
- B86 100 Sil. Diodes sub. min. IN914 and IN916 types 55p
- H16 15 Experimenters' Pak of Integrated Circuits, Daja supplied 55p
- H20 20 BY125/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts. 55p
- H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can. 55p

## Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1-10p** each

## Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

**£2.75 p.p. 38 1/2p** Per Instrument

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73p.  
Extension Telephones, 71p each. p.p 27p. £1-37 1/2 for 2. P.&P. 55p.  
These phones are extensions and do not contain bells.

## A Cross Hatch Generator £3-85 post paid

A complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. A project in the Sept. '72 edition of Television.

## New Paks

- TESTED & GUARANTEED**
- H63 4 2N3055 type NPN Sil. power transistors. Below spec. devices 55p
  - H64 4 3819 N Channel FETs 2N3819 in plastic case 55p
  - H65 4 40361 Type NPN Sil. transistors TO-5 can comp to H66 55p
- UNTESTED, UNMARKED**
- H66 4 40362 Type PNP Sil. transistors TO-5 can comp to H65 55p
  - H67 10 3819N Channel FETs plastic case type 55p

## Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors

TYPE "A": PNP Silicon alloy, TO-5 can  
TYPE "B": PNP Silicon, plastic encapsulation  
TYPE "E": PNP Germanium AF or RF  
TYPE "F": NPN Silicon plastic encapsulation  
TYPE "G": NPN silicon similar ZTX 300 range  
TYPE "H": PNP silicon similar ZTX 500 range

**8 RELAYS FOR VARIOUS TYPES P & P 27p £1-10p**

## High Speed Magnetic Counter



4 digit (non-reset) 24V or 48V (state which) 4 x 1 x 1 in. 33p. P.&P. 5p.

## Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

|                                    |         |         |     |
|------------------------------------|---------|---------|-----|
| Range 1. V.CE. Min 15. HFE Min 15. |         |         |     |
| 1-12                               | 13-25   | 26-50   |     |
| 40 Watt                            | 22p     | 20p     | 18p |
| 90 Watt                            | 26 1/2p | 24 1/2p | 22p |
| Range 2. V.CE. Min. 40. HFE Min 40 |         |         |     |
| 1-12                               | 13-25   | 26-50   |     |
| 40 Watt                            | 33p     | 31p     | 29p |
| 90 Watt                            | 38 1/2p | 36 1/2p | 33p |

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in *Practical Wireless* Dec. issue, complete with application data £1-10p.

### INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

**METRICATION CHARTS** now available  
This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 15p Wall Chart 18p

**LOW COST DUEL IN LINE I.C. SOCKETS**  
14 pin type at 16p each } Now new low profile  
16 pin type at 18p each } type

### BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

## Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak.  
**Please ask for Pak P.1. only 55p**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME .....

ADDRESS .....

ALL PRICES INCLUDE 10% VAT  
MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order  
OVERSEAS ADD EXTRA FOR POSTAGE  
**BUY THESE GOODS WITH ACCESS**

**BI-PRE-PAK LTD**

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.  
TELEPHONE: SOUTHEND (0702) 46344.

Co. Reg. No 820319

# SAXON

Money saving high performance audio equipment DIRECT FROM OUR OWN FACTORY

**Better built  
Better performance  
Better value**

## SAXON HI-FI POWER AMPS FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



**SA35** 35 watts RMS. Uses 7 transistors and 7 diodes Carr. paid. **£4.45**

**SA50** 50 watts RMS. 7 transistors, 7 diodes. Carr. paid. **£5.65**

**SA100** makes an ideal unit in disco assemblies. A real glutton for work. **£10.90**

Reliable, tough and compact, 11 transistors, 6 diodes. Carr. paid.

### BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA.100.

|                   |   |
|-------------------|---|
| Freq. response    | 15-40,000 Hz ± 1dB  |
| Distortion        | 0-2% at 1kHz  |
| Loads             | 4 to 16 ohms  |
| Quiescent current | 15 mA   |
| Noise             | Better than 75dB  |
| Supply voltage    | SA35 45 volts<br>SA50 45-65 volts<br>SA100 40-70 volts    |
| Size              | 4 1/2" x 4" x 1" (SA 100)<br>4 1/2" x 3" x 1" (SA35/SA50) |

Circuits, connecting instruction and application data are supplied free with all modules.

### POWER SUPPLIES

FOR THE SA35, SA50 AND SA100 POWER AMPS. ABOVE

**PU.45** Unstabilised supply for 2 SA35's **£4.90**

**PU.70** Unstabilised supply for one or two SA50 or SA100 Carr. 40p **£7.75**

**PS.45** Stabilised module for two SA35's or one SA50 Carr. free **£3.50**

**MT.45** Transformer for above, heavy duty Carr. 20p **£2.85**

**MT.30** Transformer for unstabilised supply complete with rectifier diodes mounted Carr. 20p **£3.50**

**PS.70** Stabilised supply module for one or two SA100's Carr. free **£4.90**

**MT.70** Transformer for PS70 Carr. 40p **£4.90**

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

Orders and personal shoppers to

**SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.**

Telephone 01-684 6385

Hours 9.30 a.m. - 5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED

## SAXON P/A MIXER CONTROL UNITS

In extra slimline easy-fit case

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos etc. Standard jack sockets. Compact design. In strong metal cases. All units guaranteed for 3 years.

- HIGH AND LOW IMPEDANCE INPUTS
- BASS/TREBLE/VOLUME ON EACH PAIR
- MASTER CONTROL ON OUTPUT



●M4H 4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" x 2 1/2" Carr. paid. + V.A.T. **£18.50**

●M6HL Case 18" x 8" x 2 1/2" 12 inputs (6 high Z, 6 low Z). Carr. paid. + V.A.T. **£27.50**

Channel section modules, for building your own: gain-16 x (24dB). Tone controls-18dB swing. Carr. paid. + V.A.T. **£3.50**

## CONTROL UNITS — Unbeatable for quality & value

EXCITING NEW STEREO VERSION. MK. II With Mic. override and case (carr. 30p) **£19.75**

Mono (as shown) For 9v battery operation. As stereo module less mic. input Carr. 20p **£6.50**



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume. Microphone volume, bass, treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.**

## AKG MICROPHONES

World famous D.190C—the one the professionals use—at special bargain price of

**£19.50** + V.A.T.

GENERAL PURPOSE DYNAMIC MIC. Professional quality. Special offer carr. paid **£9.90**

## 120 WATT HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 TO3 can (115 watt) output transistors.

### SPECIFICATION

Power output 120 watts into 8 ohms  
Freq. response 20-20,000 Hz ± 2dB  
Input sensitivity 200 mV into 10K  
Construction Fibreglass board  
Size 8" x 4" x 4" (5" with supply)

Module & power supply (Carr. 40p) **£18.95**

●160 watt version with power supply **£27.90** (Carr. 50p)

Low distortion parallel push-pull output stage.

## SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.



### 3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. Carr. 30p. **£19.75**

### SINGLE CHANNEL UNIT

Operates from 5 to 100 watt amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£7.50**

## COMPLETE AMPLIFIERS CSE 100

The versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls.



**£34.90** carr. free



## SAXON 100

**£48.50** carr. free

With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

## LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms **£8.95** carr. 30p 15" 50 watt 8/15 ohm **£14.50** carr. 50p. 12" 40 watt 15,000 gauss magnet system 8/15 ohm **£11.50** carr. 40p.

Prices subject to alteration without notice. E. & O.E.

V.A.T. Please add 10% to total value of order (inc. carr.) for Value Added Tax.

Please include S.A.E. with written enquiries.

## TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by regd. letter, please



J. ANDREWS

# crystal

# HARMONIC CALIBRATOR

**C**RYSTAL calibrators have always found wide application with radio amateurs and short wave listeners. They fill a need for low cost frequency measurement and now that the price of transistors and integrated circuits is at an all time low, may be constructed relatively cheaply, depending upon the source of components. The crystal, if purchased new, should cost no more than £1.50-£2.00.

The object was to design a unit which would provide 1MHz, 100kHz, 10kHz markers at good strength to at least 30MHz or higher. The calibrator to be described will, when used with the average receiver, provide strong frequency markers to above 30MHz and will give markers as high as 144MHz at reduced level.

## OPERATION

The crystal oscillator runs at 1MHz and is based on the Colpitts circuit. In the design, good stability results in respect of both temperature variation and variation of supply rail voltage. In order to maintain this performance silver mica capacitors are specified for C2 and C3. The crystal in the prototype required about 40pF in series and this is made up by C1 plus TC1. If necessary, C1 can be altered to suit different crystals.

The output from the crystal oscillator is taken from the collector of Tr1. The waveform is roughly a sine wave and in order to drive the dividers must

be squared. Tr2 acts as a buffer amplifier and is biased into saturation on positive half cycles. This gives a square wave output of five volts peak to peak, which is used to drive the dividers.

The SN7490N (IC1-IC2) are TTL logic binary dividers and contain two gates and four bistables. They are used in this circuit to divide the 1MHz square wave by a factor of ten, giving in the first case 100kHz and in the second 10kHz. The output is a square wave of five volts (approx.).

The three outputs, one from each divider and the 1MHz waveform from Tr2 buffer are selected by S1 and are used to drive IC3 and Tr3. These stages form the harmonic generator.

## HARMONIC GENERATOR

From a pulse rising at an infinite rate an infinite frequency spectrum could be derived, and if the pulse were to be repetitive at some frequency, say 1MHz, then the spectrum would be related to the repetition rate of the pulse. However after the rise the pulse amplitude must decay again in time for next transition. If the decay is fast and at half the pulse repetition time then obviously a square wave would result. This could be shown to contain, in a pure case only, odd harmonics of the basic repetition rate. Now if the decay point were to be shifted from the half repetition rate time, then the even harmonic content would become apparent. Therefore in generating both odd and even harmonics of a fre-

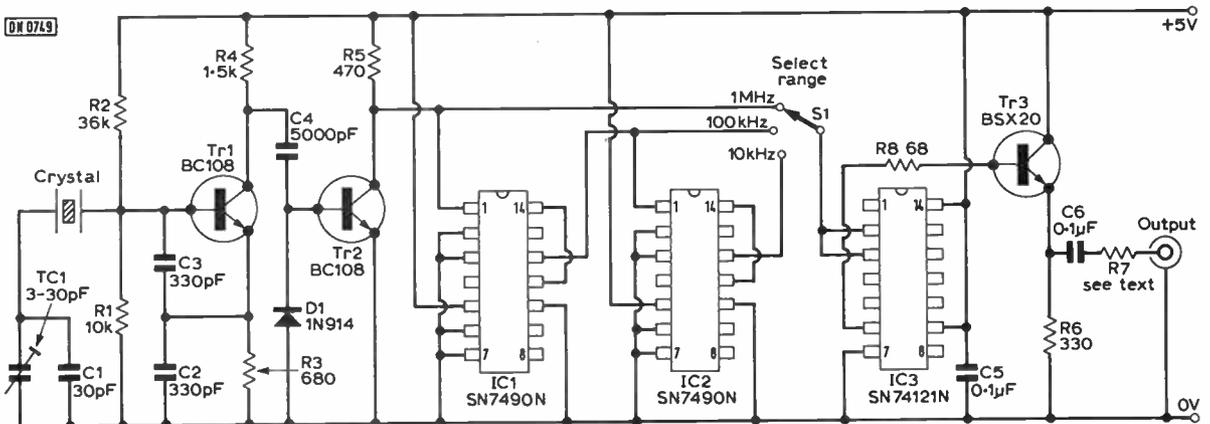


Fig. 1: Circuit of the calibrator

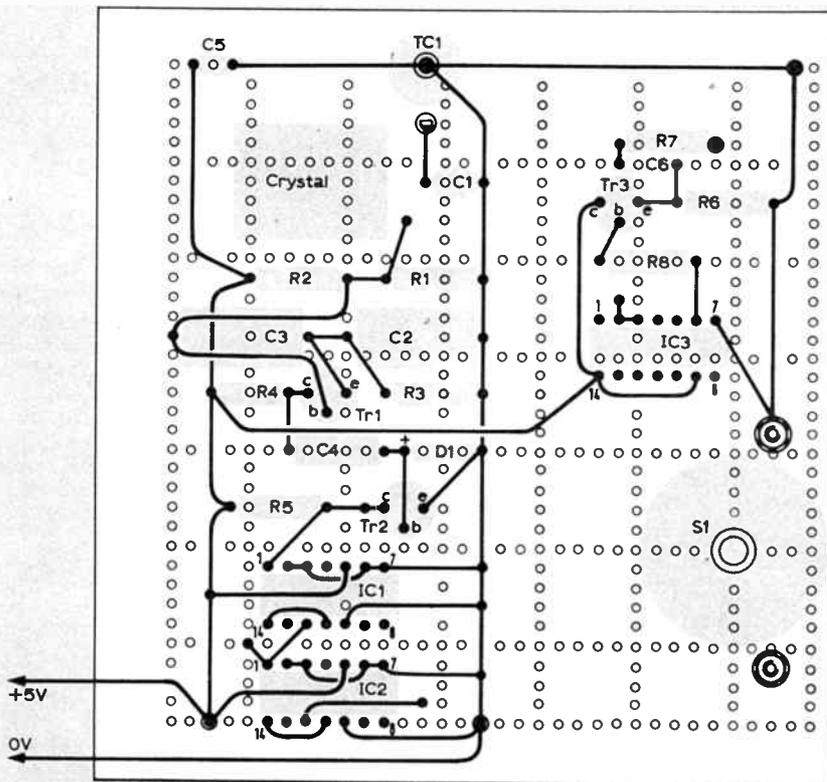
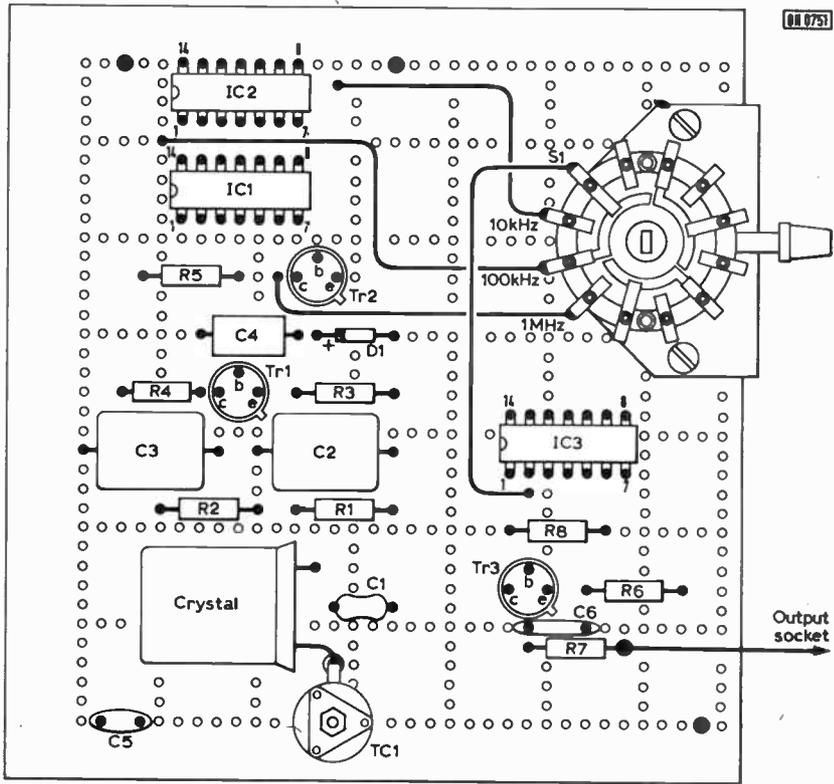


Fig. 2: Veroboard layout for the i.c. crystal harmonic calibrator


—continued on page 1069

# look!
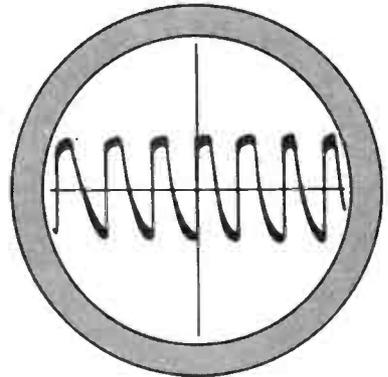
# electronics really mastered

**... practical  
... visual  
... exciting!**

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
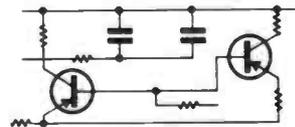
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL 34.

**special free gift also to all our students**

### Sine and Square Wave Osc. Kit Type 700

General purpose A.F. test osc. covering range sine and square 10c/s to 100Kc in 4 decade ranges, features include stabilised amplitude sine and sq. low o/p impedance, L.E.D. on indicator, both O/Ps fully variable and available simultaneously, fast sq wave rise time, all parts supplied and no special equipment required for construction and calibration, leaflet available on request. Requires PP9 batt. or 9v supply not supplied. Available in kit form only. Price **£16.20**

### Scope American Service Type TS.34

Portable general purpose scope uses 2" tube with magnifier single beam, uses 11 valves, Y amp 10c/s to 2 Mc/s, T.B. 20 Usec to 100 Mil/Sec, as fine and coarse Y atten, supplied with leads in transit container, also copy of service manual, tested. Note these are for 115v 50c/s but are supplied with a 240/110 Auto trans. Few only. Price **£23.65**

### Signal Generators

Marconi type TF144G covers range 85Kc to 25Mc/s in 8 bands. O/P 1 Vv to 1 volt, fitted O/P meter to read RF and Modulation, supplied tested with circ and Inst book, for 200/250v mains. Note supplied less R.F. connecting lead (mains lead supplied). Price **£19.25**

### Variable O/P DC P.U.

O/P variable from 0 to 26v DC smoothed at up to 3 amps uses silicon rect and variac, supplied with circ. Note for use on 115v 50c/s supplied with 240/115v Auto trans, American surplus. Price **£7.70**

### V.H.F. Test OSC Type 210

Test osc covers range 20 to 88Mc/s in 4 bands, also as noise generator, 2 Mc/s xtal check, var pulse mod. complete in case with chart. Req 250v HT and 6.3v to operate. Price **£5.50**

### Batteries

Lead Acid type Aircraft batteries 24v 25 Amp/Hr made up of 2 12v units in carrying case, new with instructions. Price **£10.20**

### Altimeter T.S.

Modern unit contains mains P.U. giving 250v 60 Ma and 6.3v, 4x valves, 2 panel meters sq type 100Ua FSD and centre reading type, 1600 Mc/s absorb W.M. ass, also large number of high grade parts inc 1% conds etc, good cond in case. Price **£5.50**

### Low Speed Motors

For use on 230v 50c/s have two stage g.b. to give O/P speed of 1.15 RPM, reversible, good quality enclosed motor, eq. equip. Price **£4.74**

### Vidicon Camera Tubes

Standard type 1" Industrial grade by E.E. and E.M.I. supplied with data sheet graded according to scan marks. Price type A **£9**, B **£6**

### W.M. and OSC Type OAP

Radio Radar T.S. covers range 150 to 230 Mc/s as Osc and Absorb W.M. also as int dummy load 50 ohms and provision for connection of scope. Supplied new boxed with inst and spares kit. Note for use on 115v 240/115v Auto trans supplied, American surplus. Price **£16.50**

### H.V. Transformers

Pris 230v 50c/s Sec 1125-0-1125v at 565 Ma, new boxed American Surplus. Price **£7.70**. Matching choke **£1.50**

### NEW STOCK ALSO AVAILABLE

Insul terminals in 8 colours, 4mm plugs and sks in 6 colours, Croc clips, Mains Inst cable, Mike cables 1, 2 and 4 core, Pax panels, H.F. chokes, Knobs with Perspex Cursors in 6, 5, 4 and 3" dia, A.F. connecting leads, Coaxial Leads in BNC, UHF and N type, Coax Test leads and fittings etc. Note above prices inc VAT and Carr. mainland only, SAE for lists.

## A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL  
Tel. 444278 (0742)

## PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 405285

### SPECIAL OFFER

Used 19" TV Tubes. Type AW 47-91. Perfect condition. 6 months guarantee. **£3** carr. paid.

Complete untested TV Sets 19" 405-line Types **£3.50** carr. and ins. paid.

19" 625-line types untested. Complete with UHF Tuner **£5.50** carr. and ins. paid.

One Students and One Instructors Wireless Procedure Training Set, each unit housed in a small wood box and comprises Mike, Single L.R. Phone and connectors. Requiring Bell Battery (not supplied) to make intercom. **£1.30** post paid.

Small Clock Type Sangamo Weston 200-250v 200 r.p.m. mains motor with Gear train (ex slot machine) Fair condition **60p** post paid.

$\frac{1}{2}$  cwt. of ex Government Scrap Resistors. Panels, Gears, etc **30p** carr. 80p.

Speakers removed from TV sets. All 3 ohm, 2 $\frac{1}{2}$  watts 7 x 4. 6 x 4, 8 x 2 $\frac{1}{2}$ . All at 27p. Post and packing 12p.

Top Quality Tape, Reel to Reel 5" LP 55p. 5 $\frac{1}{2}$ " LP 60p. 7" ST 66p. 7" LP 80p. Cassette Types C60 35p. C90 45p. Post on any tape 12p.

Jap Earpiece, 8 ohm, magnetic, 3 5 12p post paid.

Ex Equipment Valves all Tested before despatched. 3 months guarantee on all valves. Single valves post 3p, over post paid.

|       |     |       |     |       |     |
|-------|-----|-------|-----|-------|-----|
| ARP12 | 6p  | EF184 | 20p | PY801 | 17p |
| DY86  | 20p | PCC80 | 6p  | PY82  | 10p |
| EB91  | 5p  | PCC84 | 6p  | PY33  | 20p |
| EF80  | 10p | PCL82 | 15p | UI91  | 20p |
| EBF89 | 15p | PCL84 | 15p | 6BV7  | 12p |
| ECC81 | 12p | PCL85 | 20p | 6F23  | 15p |
| ECC82 | 12p | PL36  | 17p | 30F5  | 12p |
| EY86  | 20p | PY81  | 10p | 30FL1 | 20p |
| EF183 | 20p | PY800 | 17p | 30P19 | 10p |

ABOVE PRICES INCLUDE V.A.T.

## poly-planar

### 20-Watt Full Range Speaker

Completely replaces the conventional cone speaker  
Super-thin construction  
permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£7.50 each Stereo pair £14.50

INCLUSIVE OF VAT AND POSTAGE

## web europa

P.O. Box 162, Watford WD1 1AA



## PW Q4 PROJECT

UNIT "A" (Rs, Cs, S/c's) ... .. **£1.20**  
UNIT "B" (Rs, Cs, S/c's) ... .. **£3.88**

### MULTI-SYSTEM DECODER ADDITIONAL

PARTS (Rs, Cs, Pots, Switch) ... .. **£4.91**  
POWER SUPPLY (R, Cs, S/c's T/former) ... .. **£2.52**  
PRINTED CIRCUIT BOARDS (set of 5) ... .. **£2.25**  
(Fibreglass, drilled, tinned)

ADD 10p P & P

ADD 10% V.A.T.

S.A.E. for free list of Q4 and other kits and PCB's for P.W. and P.E. Projects, and with all other enquiries.

## PHONOSONICS

Dept PW3, 25 KENTISH ROAD, SELVEDERE, KENT, DA17 5BW  
MAIL ORDER ONLY

quency or rate, the main functions governing them are the rise or transition time of the pulse and its duration with respect to repetition rate.

It can now be seen that the principal requirement for a harmonic generator is that it must generate a pulse with a rapid transition or rise time which is as narrow as possible with respect to the repetition rate.

A number of methods exist whereby a fast pulse may be generated, these include tunnel diodes, reverse recovery effect of diodes, fast switching transistors etc.

For ease and cheapness the method used here is a standard SN74121N monostable (IC3) which drives Tr3 the emitter follower into saturation. The SN74121N has provision for external timing components, but none are used here. This gives a pulse width of 30-40nS. The output rise time (transition time) is quoted as 10nS, but this is speeded up considerably by Tr3, which is a high speed switching device. Tr3 also provides a low output impedance.

The 75Ω resistor R7 is worth mentioning. The output impedance of the emitter follower (Tr3) is not governed directly by R6. It is in fact much lower than this and for matching purposes may be taken as zero. If it is desired to pass the signal along a coaxial line or to use an attenuator then R7 should be chosen to match the impedance of the cable in use, in the range of 50-300Ω. However, many people will simply want to connect receivers or to squirt the output into a few feet of wire in which case make R7 50Ω.

## POWER SUPPLIES

The limiting factors here are the integrated circuits. The voltage required is five volts  $\pm 10\%$ . The design of the oscillator assures stability to within a few Hz for a  $\pm 20\%$  change in supply potential. This should not however present too great a problem as many constructors now run some form of equipment from which a five volt supply could be borrowed to operate the calibrator.

Fig. 3 shows the circuit of a simple stabiliser for use with this calibrator.

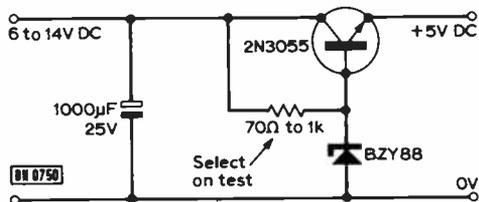


Fig. 3: Simple stabiliser

## CONSTRUCTION

Building the calibrator should not present any problems, all components may be assembled on perforated board of suitable matrix. However in order to realise the best h.f. performance the leads around IC3 Tr3 should be kept as short as possible and the output socket wired direct to Tr3 emitter. In particular, ensure that the output lead from pin 6 of IC3 is short and direct to Tr3 base.

The crystal, if of a miniature type, may be fastened to the board and secured with a loop of wire. Solid

vibration free wiring in the crystal oscillator circuit will avoid microphony. If S1 cannot be wired direct to the board, all leads to it should be kept short. When completed and tested the board may be fitted in a small metal case or die-cast box.

## ★ components list

### Resistors

|    |       |    |         |
|----|-------|----|---------|
| R1 | 10kΩ  | R5 | 470Ω    |
| R2 | 36kΩ  | R6 | 330Ω    |
| R3 | 680Ω  | R7 | 50-300Ω |
| R4 | 1.5kΩ | R8 | 68Ω     |

### Capacitors:

|     |                        |
|-----|------------------------|
| C1  | 30pF silver mica       |
| C2  | 330pF silver mica 2%   |
| C3  | 330pF silver mica 2%   |
| C4  | 5000pF polystyrene     |
| C5  | 0.1µF ceramic          |
| C6  | 0.1µF ceramic          |
| TC1 | 3-30pF Philips trimmer |

### Semiconductors:

|     |       |                   |
|-----|-------|-------------------|
| Tr1 | BC108 |                   |
| Tr2 | BC108 | Texas Instruments |
| Tr3 | BSX20 |                   |

### Integrated Circuits

|     |          |                   |
|-----|----------|-------------------|
| IC1 | SN7490N  |                   |
| IC2 | SN7490N  | Texas Instruments |
| IC3 | SN74121N |                   |

### Miscellaneous

|    |                              |
|----|------------------------------|
| S1 | 1 pole 3 way                 |
|    | Crystal 1Mhz HC6U or similar |

## TESTING

Connect a suitable five volt supply to the calibrator and couple the output to a receiver (b.f.o. on) tuned to 1MHz. If all is in order a marker will be heard. Tune the receiver throughout its range and check that markers are present. Switch S1 to 100kHz and check that there are 100kHz markers present. Switch to 10kHz and carefully check that 10kHz markers are present.

If no markers are present on any range first check the oscillator circuitry. If markers appear only at 1MHz intervals check the dividers for a fault.

The simplest way of controlling the injection of markers to a receiver is to vary the coupling. Obviously the markers are less strong around 30MHz and the coupling may have to be increased. Direct coupling without the use of an attenuator is likely to overload the receiver and may introduce spurious responses. A little experiment will reveal the best method of operation.

Once the unit has been checked the frequency may be accurately set against WWV or MSF on either 2.5, 5.0 or 10MHz. The calibrator should be re-checked from time to time against the standard frequency services to maintain its accuracy. TC1 may be adjusted as necessary to maintain this accuracy. ■

We regret that the  
December 1973 issue  
of *Practical Wireless*  
is now out of print

# PORTABLE FLUORESCENT LAMP UNIT

## A FURTHER DESIGN

PAUL COOPER

A 12 volt d.c. portable fluorescent lamp unit is a very useful piece of equipment to own—especially in these days of power cuts! This article describes an alternative to the unit described in the December 1973 issue of *Practical Wireless*. There is the bonus that it is easier to build the circuit on a standard piece of veroboard than to produce a special printed circuit board and, by using a ready made transformer, reduces the cost.

### TRANSFORMER

A transformer specifically for 12 volt inverters to run fluorescent tubes from car batteries is available from G. F. Milward\* for only 50p + post packing & VAT. It saves the time taken to wind the transformer, which is something which might put off the inexperienced amateur from building the project.

The revised circuit diagram is shown opposite.

The circuit is basically the same as in the original article except for the extra tertiary winding on the transformer which is connected in parallel with capacitor C3. The unit will work without this winding connected but in the circuit shown it tunes the transformer thus producing a better output.

It is most important that terminals 1, 2, 3 & 4 of the transformer are connected to the right points on the circuit diagram (as shown by the dots) since if, say, 3 and 4 are reversed the circuit will not oscillate. To cure this, should it occur, connections 3 and 4 should be interchanged and the circuit should then oscillate. (For the complete setting-up procedure see the original article.)

### LAYOUT

The Veroboard layout is shown opposite for 0.1 inch matrix veroboard. The board size is the same as for the original printed circuit board so no problems should occur in mounting this board in the completed unit. Note that the fixing hole in this circuit board is in a different place to that of the original board, so a different hole will have to be drilled in the unit case.


The transformer is fixed to the circuit board by two links of insulated copper wire as shown in the circuit board layout diagram.

Resistor R1 should be mounted about 1/4 in clear of the circuit board and clear from C1 as it gets hot! Since drilling of the holes for the legs of potentiometer VR1 cuts the circuit board tracks completely, care must be taken to ensure contact when soldering the legs in.


Exact values of R1 and VR1 are not very critical. Values were chosen because of availability.

As my unit was built primarily as an emergency light for use in power cuts, the case has been designed to stand on a table with the tube vertical, and it is made of wood.

\* G. F. Milward, 369 Alum Rock Rd, Birmingham, B8 3DR.

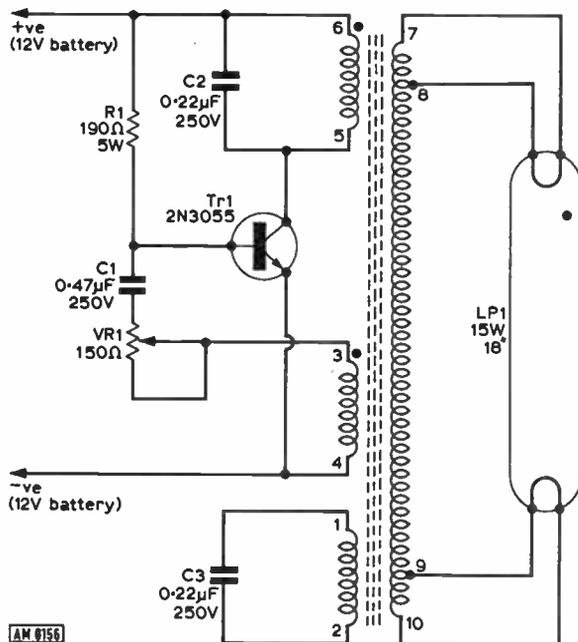

AM 0156

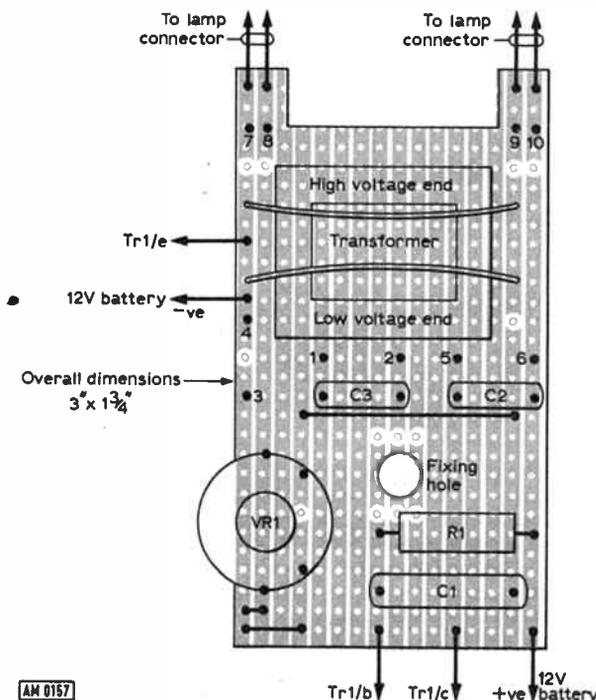

AM 0157

# IN NEXT MONTH'S

# PRACTICAL WIRELESS

## CUT YOUR COSTS WITH P. W.

**SAVE** on your tools. Get this exclusive **TOOL-KIT OFFER** at reduced price when you buy the April issue of Practical Wireless. The kit contains soldering iron kit, wire cutters, wiring pliers with wire stripper blades, small screwdriver with neon tester, large screwdriver for cabinet and chassis work. All these tools are of high quality and of well established manufacture. They are available to Practical Wireless readers at a special low price. Use the coupon in the April issue.



# Special offer

**SAVE** your Windscreen Wiper blades by making the "Quick-Wipe" to give a quick clearance of April showers from your car windscreen.



**ALSO:-**

### GUIDE TO MULTI-RANGE TEST- METERS : IMPEDANCE MATCHING

Supplies of Practical Wireless are limited. Don't be disappointed—order early from your newsagent.

## APRIL ISSUE ON SALE IN MARCH

## THE 'SLIMLINE' 5-BAND RECEIVER

This unusual receiver is designed to give five ranges from 160kHz to 27MHz, using simple plug-in coils to cover broadcast and amateur transmissions. Only eight transistors are used, and, with a telescopic aerial the "Slimline" becomes a versatile a.m. receiver to take almost anywhere.



The above details are subject to the current national industrial situation at the time of going to press.

1071

# CASSETTE RECORDER AND TUNER... AMPLIFIER



**T**HIS constructional feature describes a stereo-multiplex AM/FM tuner-amplifier providing 10 watts RMS output per channel into  $8\Omega$  loads with facilities for incorporating a cassette tape recorder. The integrated unit provides very good results which, although not to true high fidelity standards, will give satisfying listening for a moderate outlay.

Facilities on the prototype included full Band II FM coverage together with one preset AM station and an input for a ceramic cartridge. Additional circuitry and printed boards are shown in this article so that inputs for magnetic cartridge and tape heads can be accommodated, together with record/playback connections for a cassette or reel-to-reel tape recorder. Additional tuning capacitors may also be fitted along with a selector switch to provide more extensive AM coverage. The AM section uses an internal ferrite aerial, but an external aerial may be added if required. The stereo decoder incorporates automatic mono/stereo switching and stereo beacon lamp drive.


The complete unit is built up on five main circuit boards. The power supply is built directly onto the chassis which is constructed from aluminium angle and strip. The following unit numbers will be used as a prefix to identify components which are mounted off the circuit boards:—

- 1 Pre-amplifiers
- 2 Power amplifiers
- 3 Tuner and IF
- 4 Stereo decoder
- 5 Power unit and input/output sockets.

The front panel is fashioned from 3mm Perspex, using Letraset marking and gives a very professional finish to the unit.

The complete circuit uses 3 integrated circuits, 19 transistors and 7 semiconductor diodes. The FM tuner head is a Mullard module, simplifying construction and greatly reducing alignment problems.

## PART 1

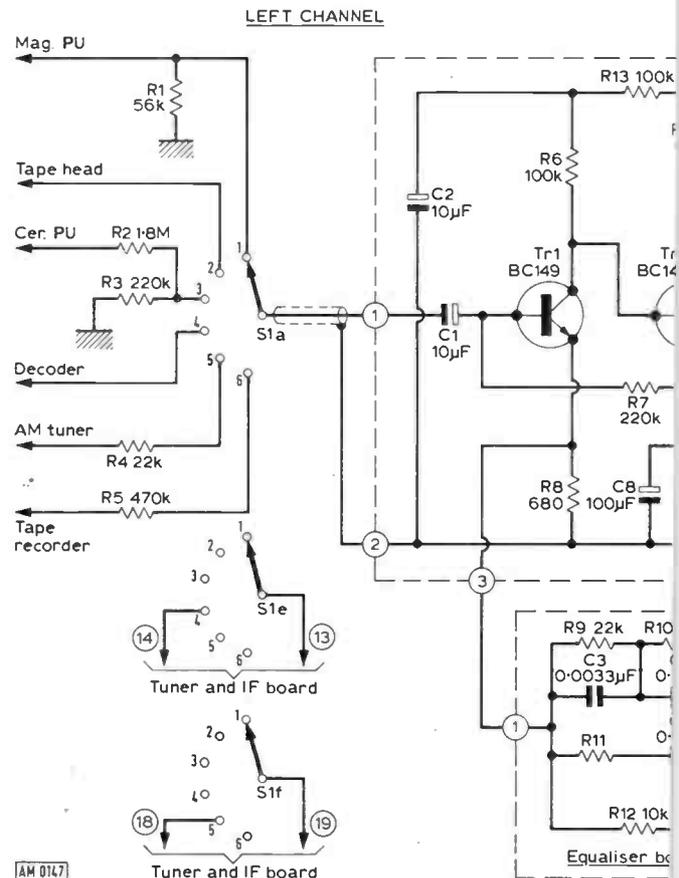



## RICHARD COLLIN

## ★ Performance Specification

### AMPLIFIER

**Power output:** 10 watts RMS per channel into 8Ω  
**Frequency response:** 20Hz to 30kHz ± 3dB at full power  
 50Hz to 20kHz ± 1dB (power amplifier)  
**Channel separation:** 54dB at 1kHz and 10 watts  
**Noise:** -60dB at 10 watts (ceramic cartridge input)  
**Total harmonic distortion:** < 0.2% at 1kHz and 10 watts  
**Tone controls:** Bass ± 16dB at 50Hz  
 Treble ± 14dB at 15kHz

### F.M. TUNER

**Frequency range:** 88 to 104MHz  
**Channel separation:** 40dB

### PRE-AMPLIFIER (UNIT 1)

The inputs from the various programme sources, attenuated and matched as necessary by R1-R5, are selected by S1a (S1c for the Right channel). Transistors Tr1 and Tr2 are connected as a high-gain pair and amplify the input signals to a level sufficient to drive the tone control circuit. The bias resistor R7 for the first stage may need to be selected for optimum operation. This will be dealt with in a later part of the article. Its final value should lie between 120 and 270kΩ.

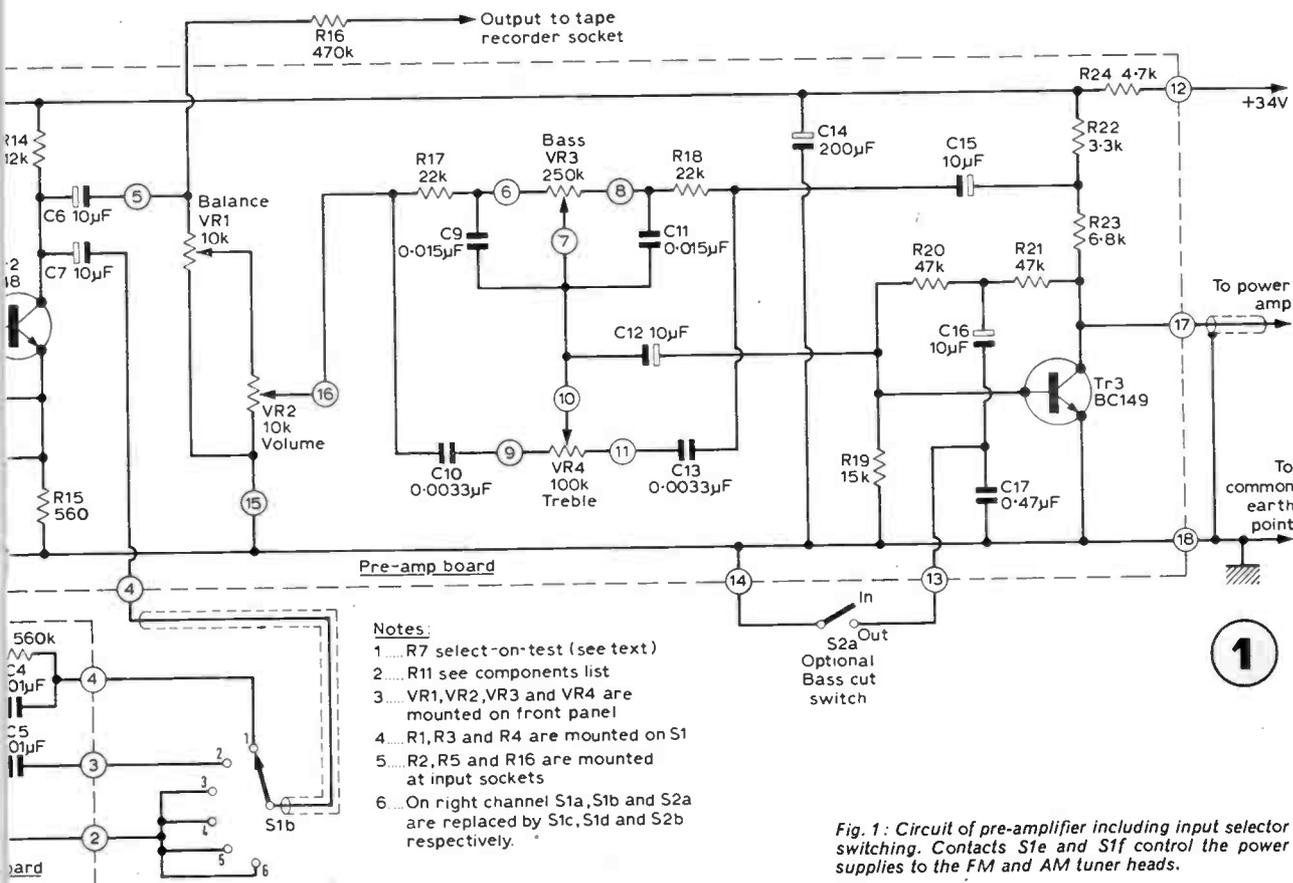


Fig. 1: Circuit of pre-amplifier including input selector switching. Contacts S1e and S1f control the power supplies to the FM and AM tuner heads.

## ★ components list

### PRE-AMPLIFIERS

#### Resistors

|                    |  |                   |
|--------------------|--|-------------------|
| R1 56k $\Omega$    | R10 560k $\Omega$                        | R17 22k $\Omega$  |
| R2 1.8M $\Omega$   | R11 22k $\Omega$ for 1 $\frac{1}{2}$ ips | R18 22k $\Omega$  |
| R3 220k $\Omega$   | 12k $\Omega$ for 3 $\frac{1}{2}$ ips     | R19 15k $\Omega$  |
| R4 22k $\Omega$    | 6.8k $\Omega$ for 7 $\frac{1}{2}$ ips    | R20 47k $\Omega$  |
| R5 470k $\Omega$   | R12 10k $\Omega$                         | R21 47k $\Omega$  |
| R6 100k $\Omega$   | R13 100k $\Omega$                        | R22 3.3k $\Omega$ |
| R7 220k $\Omega$ * | R14 12k $\Omega$                         | R23 6.8k $\Omega$ |
| R8 680 $\Omega$    | R15 560 $\Omega$                         | R24 4.7k $\Omega$ |
| R9 22k $\Omega$    | R16 470k $\Omega$                        |                   |

\* See text

All resistors  $\frac{1}{2}$ W 5% carbon film

|                           |                            |
|---------------------------|----------------------------|
| VR1 10k $\Omega$ dual lin | VR3 250k $\Omega$ dual lin |
| VR2 10k $\Omega$ dual log | VR4 100k $\Omega$ dual lin |

#### Capacitors

|                   |                    |                     |
|-------------------|--------------------|---------------------|
| C1 10 $\mu$ F 16V | C7 10 $\mu$ F 16V  | C13 3300pF          |
| C2 10 $\mu$ F 16V | C8 100 $\mu$ F 10V | C14 200 $\mu$ F 30V |
| C3 3300pF         | C9 0.015 $\mu$ F   | C15 10 $\mu$ F 16V  |
| C4 0.01 $\mu$ F   | C10 3300pF         | C16 10 $\mu$ F 16V  |
| C5 0.01 $\mu$ F   | C11 0.015 $\mu$ F  | C17 0.47 $\mu$ F    |
| C6 10 $\mu$ F 16V | C12 10 $\mu$ F 16V |                     |

Non-electrolytic capacitors should be polyester or polystyrene

#### Semiconductors

Tr1 BC149 Tr2 BC148 Tr3 BC149

NOTE—With the exception of the four dual-ganged potentiometers, two sets of the above components are required for the two channels.

#### Miscellaneous

S1 6 pole, 6 way, 3 wafer rotary switch  
S2 DPST miniature toggle switch

Pre-amplifier printed circuit board  
Equaliser printed circuit board

### POWER AMPLIFIERS

#### Resistors

|                  |                          |  |
|------------------|--------------------------|--|
| R1 91k $\Omega$  | R6 10k $\Omega$          | R11 0.47 $\Omega$ 2.5W w/w                                 |
| R2 100k $\Omega$ | R7 47 $\Omega$           | R12 0.47 $\Omega$ 2.5W w/w                                 |
| R3 22 $\Omega$   | R8 100 $\Omega$ 2.5W w/w | R13 10 $\Omega$  |
| R4 470 $\Omega$  | R9 100 $\Omega$ 2.5W w/w | All $\frac{1}{2}$ W 5% Carbon film unless stated otherwise |
| R5 470 $\Omega$  | R10 10 $\Omega$          |  |

VR1 50k $\Omega$

VR2 100 $\Omega$  miniature presets (horizontal mounting)

#### Capacitors

|                      |                       |                       |
|----------------------|-----------------------|-----------------------|
| C1 25 $\mu$ F 25V    | C4 0.01 $\mu$ F 100V  | C7 200 $\mu$ F 30V    |
| C2 47 $\mu$ F 40V    | C5 0.22 $\mu$ F 100V  | C8 1,500 $\mu$ F 25V  |
| C3 1,000 $\mu$ F 25V | C6 0.001 $\mu$ F 750V | C9 0.047 $\mu$ F 100V |

#### Semiconductors

Tr1 BC158 Tr4 2N6288 (RCA)  
Tr2 BC148 Tr5 2N6111 (RCA)  
Tr3 2N6288 (RCA)

Tr3, 4 and 5 are supplied with the necessary mounting hardware

NOTE—Two sets of the above components are required for the two channels.

#### Miscellaneous

Printed circuit board. Heat sinks and brackets (see Figs. 8 and 9)

NOTE—RCA Semiconductors for this project are available from E.C.S. (Windsor) Ltd., Thames Avenue, Windsor, Berks.

Total requirements are: 2 2N6111 at 50p  
5 2N6288 at 54p  
1 CA 3089 E at £1.96  
1 CA 3090 Q at £4.23


Add 40p post and packing per order and 10% VAT

Feedback around Tr1/Tr2 provides high stability and is also used to set the gain and, for the magnetic pick-up and tape-head inputs, the frequency response. The appropriate feedback path is selected by S1b (S1d for the Right channel). The value of R11, which with C5 provides equalisation for the tape-head input, must be chosen according to the tape speed to be used.


A constructor not requiring the full complement of input facilities may of course omit the unwanted circuitry and connectors.

An output is taken via R16 for connection to a tape recorder, allowing recording of a programme being played through the amplifier (subject to the provisions of the Copyright Act, 1956). The signal at this point is equalised but is unaffected by the Volume and Tone controls. Because of the high value of R16, the two channels can be paralleled at the input of a mono recorder with only slight worsening of stereo crosstalk within the amplifier.

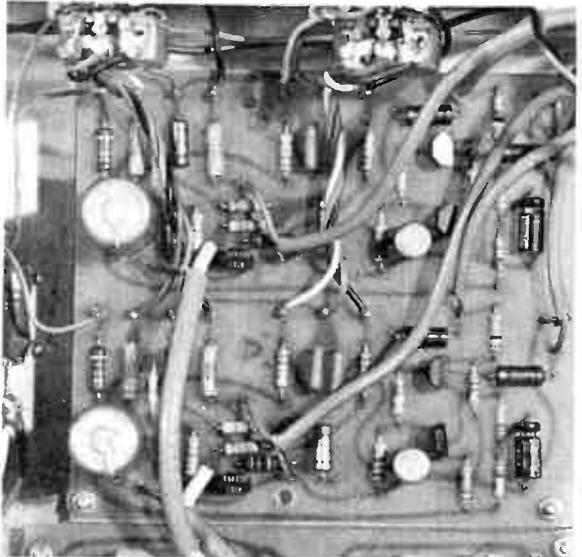The tone controls are in the familiar Baxandall configuration, providing both lift and cut at bass and treble frequencies. Transistor Tr3 is the active



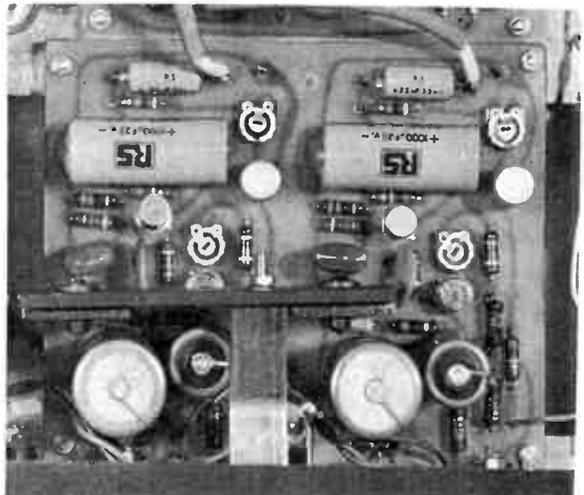Prototype boards for the pre-amplifier (above) and power amplifier (below)



element of this stage and also makes up for the losses incurred by the frequency selective circuits. A bass cut or rumble filter may be provided by removing the short circuit from across C17.

Ensure correct polarity of the electrolytic capacitors when assembling the circuit boards. In the R7 position fit 220kΩ resistors, leaving the wires long as the value may need to be changed later. Once

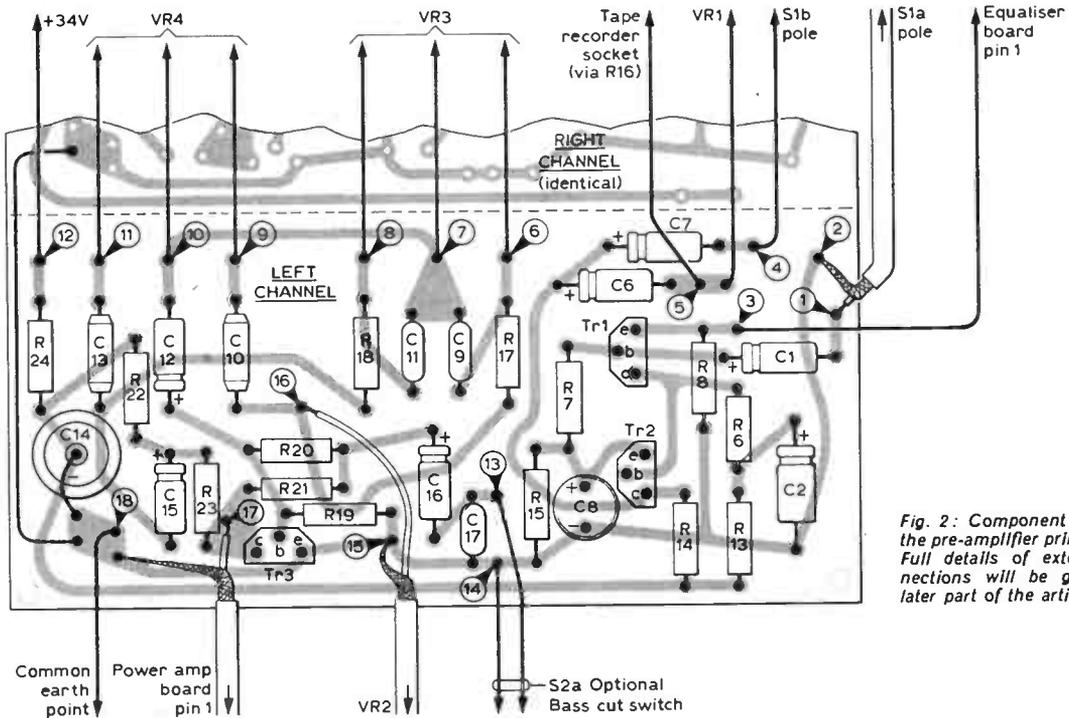


Fig. 2: Component layout for the pre-amplifier printed board. Full details of external connections will be given in a later part of the article

AM 0148

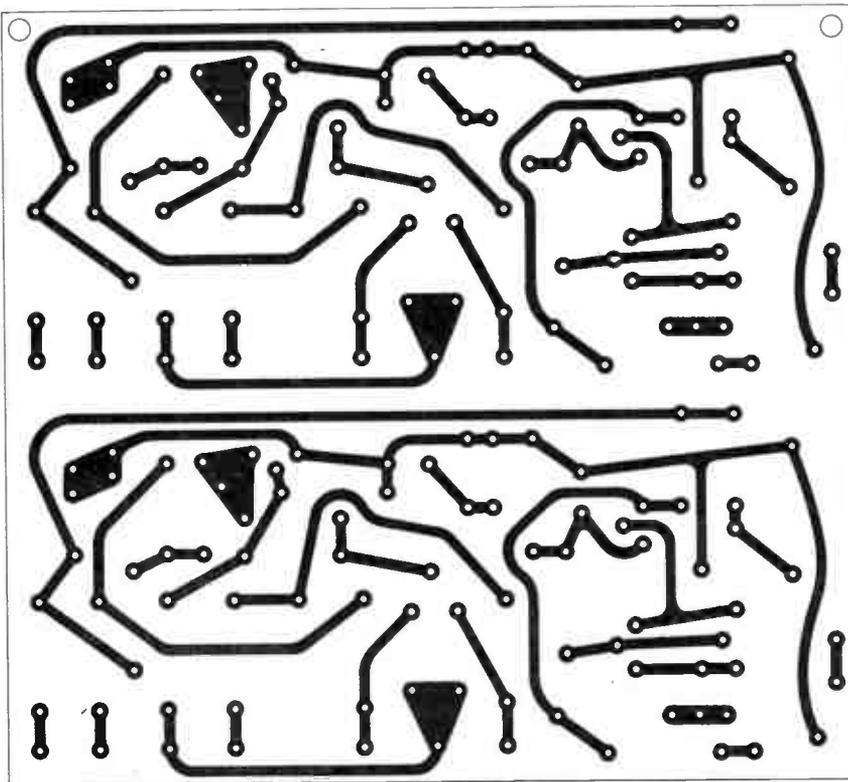


Fig. 3: Actual size layout for the pre-amplifier printed circuit board


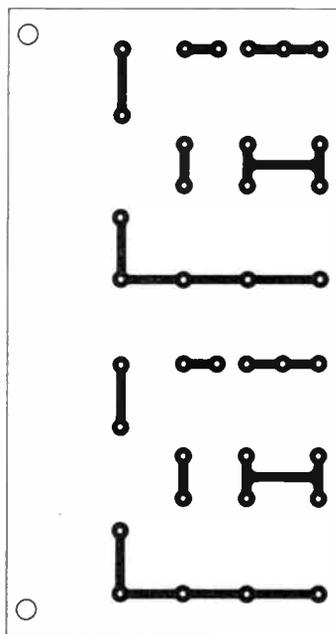
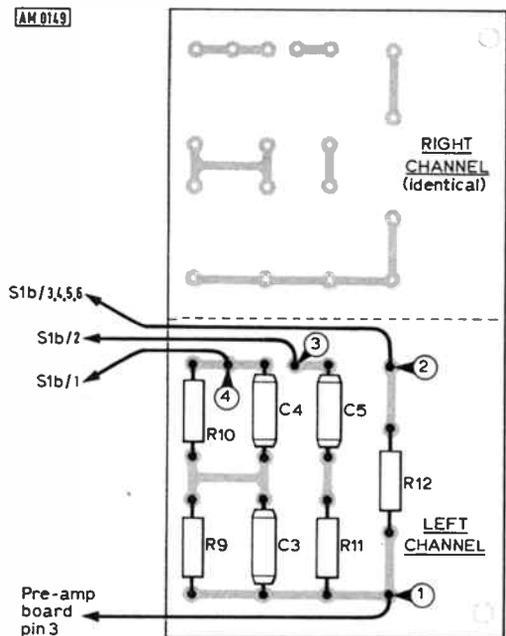


Fig. 4: Actual size layout of equaliser printed circuit board and location of components

Fig. 5: Circuit of the power amplifier. One channel only shown. The other channel is identical

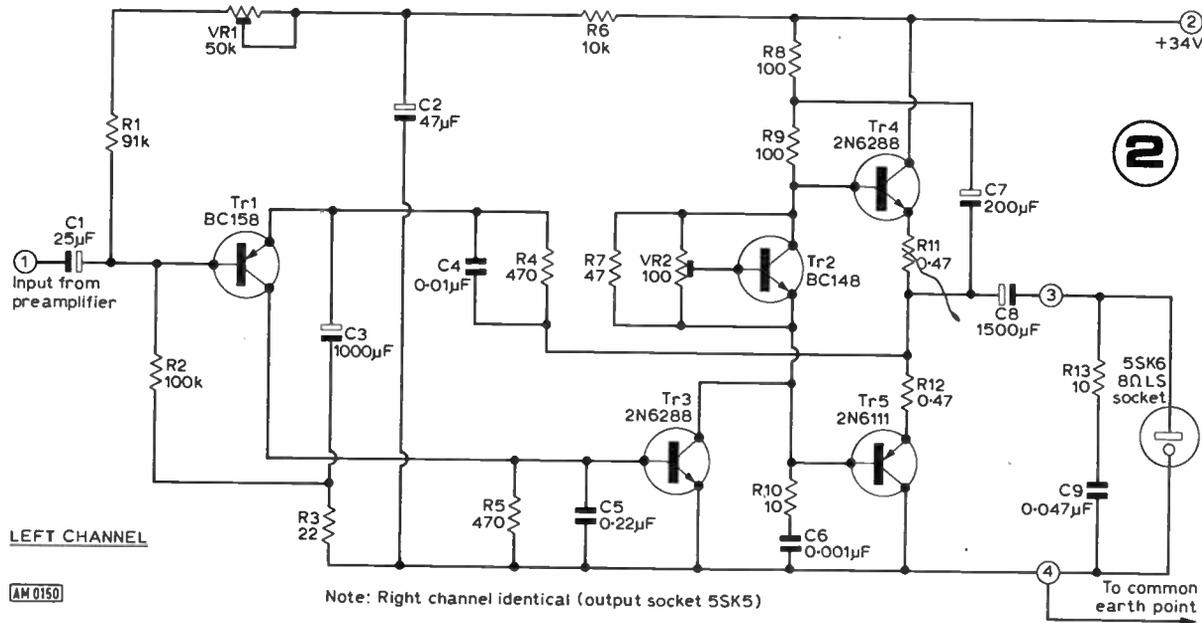

Note: Right channel identical (output socket 5SK5)

complete, these boards may be placed in a safe place until the chassis and power unit are completed. A number of components included in the pre-amplifier circuit diagram are not mounted on the boards. These are dealt with in a subsequent part of the article.

### POWER AMPLIFIER (UNIT 2)

The familiar complementary—symmetry configuration is used and designed around silicon transistors. Good low frequency response and stability is ensured by the use of DC coupling throughout the amplifier. The output pair, RCA plastic packaged 'Versawatt' devices, deliver 10 watts RMS into an 8Ω load. A similar device Tr3 operates as a class 'A' driver.

The small forward bias required to minimise cross-over distortion is provided by a small signal transistor Tr2 connected between the bases of the output pair. The first stage Tr1 provides amplification of the input signal and in addition acts as a DC comparator, enabling the output stage to be set up for symmetrical clipping under overload conditions. The DC potential at the output mid-point is connected to the emitter of Tr1 via R4. The base potential of Tr1 is determined by the potential divider R1, R2, VR1 and R6. The high loop gain of the circuit keeps the small difference between V<sub>b</sub> and V<sub>e</sub> constant, so that the output mid-point voltage is defined by the base potential of Tr1 regardless of component tolerances. Negative feedback is provided by R4, C3 and R3.

Fig. 6: Component location for the power amplifier printed board


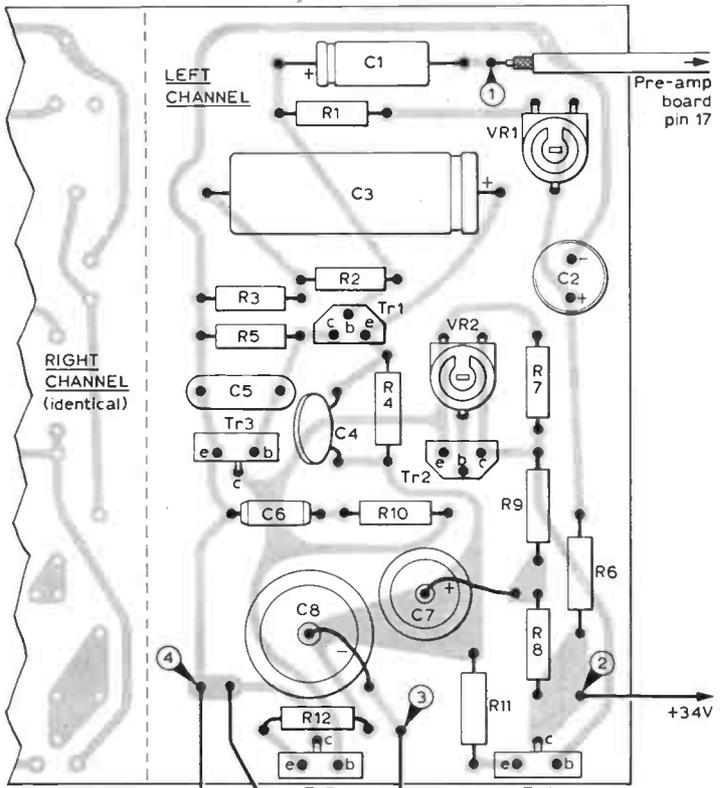


Fig. 7: Actual size layout for the power amplifier printed circuit board

AM 0151

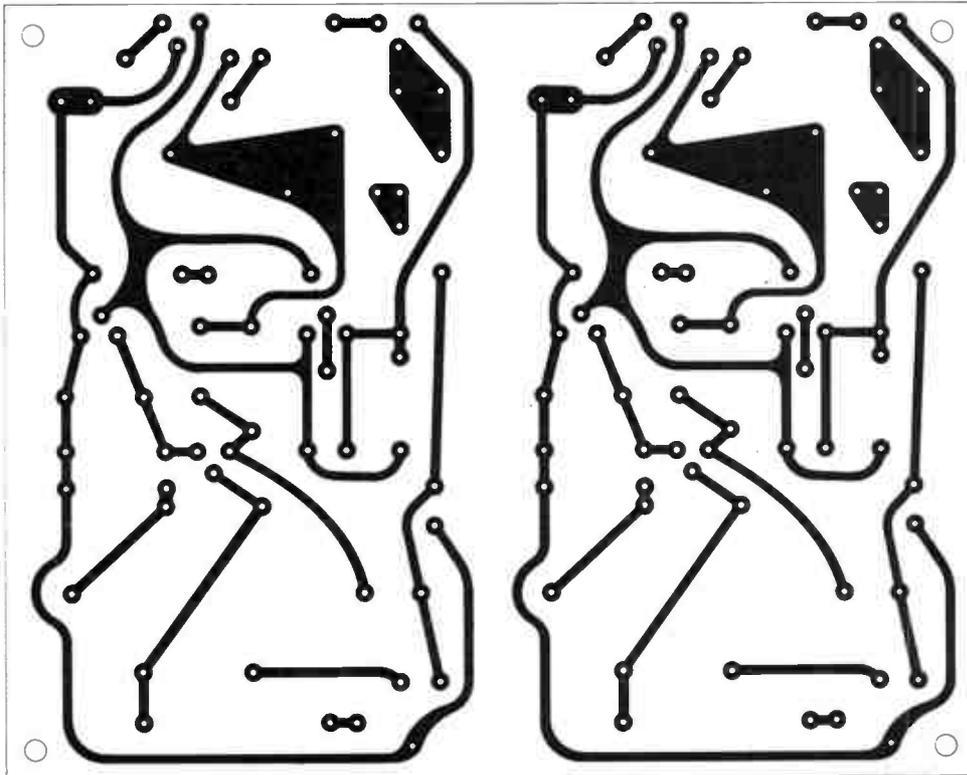

—continued on page 1080

# The Sinclair Cambridge... no other calculator is so powerful and so compact.

## Complete kit - £24.95! (PLUS VAT)

### The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £5.50!

### Truly pocket-sized

With all its calculating capability, the Cambridge still measures just  $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$ . That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

### Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

### Total cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 - so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.

### Features of the Sinclair Cambridge

- \* Uniquely handy package.  $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$ , weight  $3\frac{1}{2}$  oz.
- \* Standard keyboard. All you need for complex calculations.
- \* Clear-last-entry feature.
- \* Fully-floating decimal point.
- \* Algebraic logic.
- \* Four operators (+, -, x, ÷), with constant on all four.
- \* Constant acts as last entry in a calculation.
- \* Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- \* Calculates to 8 significant digits, with exponent range from  $10^{-20}$  to  $10^{79}$ .
- \* Clear, bright 8-digit display.
- \* Operates for weeks on four U16-type batteries. (MN 2400 recommended.)




# A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

## Contents :

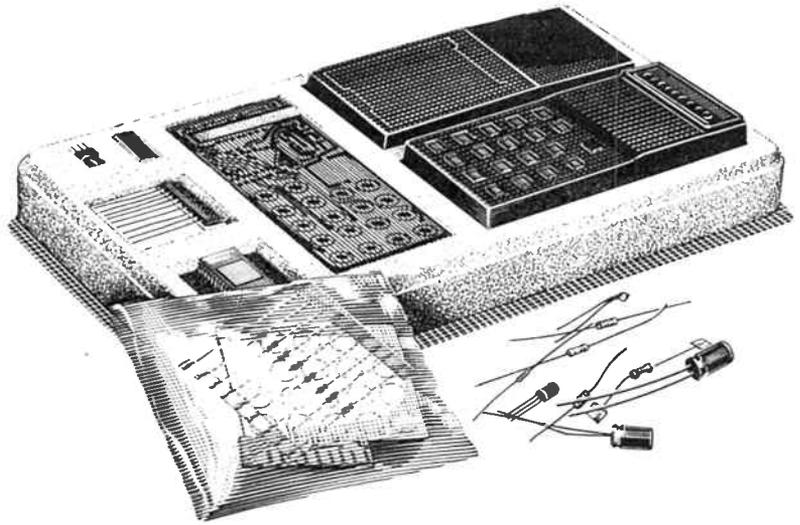1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



## This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

# sinclair

Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire  
Reg. no: 699483 England  
VAT Reg. no: 213 8170 88

## Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

## Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

**Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)**

**Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)**

PW 374

To: Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire, PE17 4HJ

Please send me

a Sinclair Cambridge calculator kit at  
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready  
built at £29.95 + £3.00 VAT  
(Total: £32.95)

\*I enclose cheque for £ \_\_\_\_\_, made  
out to Sinclair Radionics Ltd, and  
crossed.

\*Please debit my \*Barclaycard/Access  
account. Account number \_\_\_\_\_

\*Delete as required.

Name \_\_\_\_\_

Address \_\_\_\_\_

PLEASE PRINT



# HOTLINES

ON RECENT DEVELOPMENTS

## WATCH IT!

I AM looking at a Swiss electronics journal. There's a circuit which uses two ICs, a readout chip, and a one-transistor oscillator. Connected together they form an electronic clock complete with digital readout. The only circuitry which needs "building" is the single transistor oscillator and this comprises five resistors, five capacitors, a crystal and one of the ICs mentioned. For the record, the two chips are the SCL5437F (oscillator) and SCL5424F which drives the liquid crystal readout direct.

## UNIVERSITIES HELP

One of the major criticisms levelled at universities is that their experiments are all too often of academic value only. While this may be true in some instances, it certainly is not true in the case of the University of Utah in the U.S. This establishment has a section devoted to making blind people see again. Although in the experimental stages, blind people have been able to see light patterns which have been simulated by an external "eye" and fed into their brains by small electrodes.

The light images or patterns are called phosphenes and are stimulated (in these experiments) by the generation (and careful control) of pulses, in other words, the vision has been created by purely electronic means. The width of the pulse and its duration determined the intensity or "shades" of the image which the totally (otherwise) blind person can "see". Researchers see no reason why some form of imaging device (like a solid state t.v. camera) should be used and the impulses fed into the brain—after suitable processing, of course. This latter idea is well within the realms of readily available electronics which one can obtain today.

Embedded image sensors could even be controlled by the eye muscles themselves. Already,

computer-generated images have been drawn quite accurately by a totally blind person. The image was viewed on a c.r.t. so that a fair comparison could be made.

If you know of a blind person, it would be unkindly premature to mention these experiments with too great an enthusiasm because it may well take many years to perfect it into a practical device.

## A TOOTHGRAPH?

Still in the realms of medicine—well, almost, is the latest use of lasers. Now, the dental profession have taken an interest. By using a small laser it is possible to take holographic photographs of a person's teeth. One interesting thing to emerge from this useage is not that it will offer an invaluable aid in dental practice (although this is very true) but its use for security purposes. Apparently no two peoples teeth are the same so instead of fingerprints one could have toothgraphs or teggypix.

Criminals of the future will do well to heed the old adage—when in doubt, keep your mouth shut. In any case the idea should give Scotland Yard something to get its teeth into.

## LARGE-SCREEN COLOUR

Perhaps one of the most interesting battles currently being fought is the one for television screens/tubes/systems. All sorts of ideas are currently under examination including a flat screen solid state beast. News has arrived about another contender. This one is called a Video-Beam projector and houses optics inside the colour tubes. It shows promise for large screen colour television and claims the advantages of doing away with colour dots, lattices and shadow masks.

Each electron beam (one for each of the three colours) is fired at a "target" which has the relevant colour phosphor. This beam is reflected back inside the tube to a concave mirror which in turn reflects the image out of the tube onto the screen. Extremely good results are reported, however,

there is a snag—the projection distance is fixed at eight feet and is unalterable. The company working on the device do not see this as a problem and claim that once the colour tube "projector" has been adjusted at the manufacturing facility, it requires no adjustment or fiddling by the user.

No mention is made of the power requirements but one presumes that they are considerably lower than the 25–30kV needed for the earlier black-and-white projection systems where many people expressed concern about radiation from such a set up.

## MULTI- CHIPS

A new IC chip, the 2240, is claimed by its makers to do just about anything. It is currently hailed as a programmable timer, binary counter, music synthesiser, A/D converter, ultra-long delay generator, digital sample and hold circuit, frequency synthesiser, pulse counter, binary pattern generator, precision oscillator... etc., all in one innocent looking sixteen-pin dual in-line package. I have contacted the company with a view to obtaining further information which I will pass on as and when it arrives. It may be possible to include some circuitry of the more practical applications for the home constructor.

## BIG CHIPS!

Remember the days when semiconductor devices were fragile and sensitive to fluctuations in power. Contrast that with the latest beast from International Rectifier. This is a silicon controlled rectifier which handles 2,500 Amps r.m.s. at up to 1,200 volts. A 2,000V version is already planned. The wafer for this device is almost 2½ inches in diameter. This is probably the largest chip which has ever been employed in any semiconductor device.

*Ginsberg*

# IC OF THE MONTH

Number 44

National LM377N 2 + 2W AUDIO AMPLIFIER

THE LM377N is an IC, manufactured by the National Semiconductor Company, which contains two separate two-watt amplifiers in a single device. The connections are shown in Fig.1. A 14 pin dual-in-line encapsulation is employed which can be fitted into a socket or soldered into a printed circuit board. A similar device, the LM377N-10, has metal tab connections which may be soldered to a printed circuit board. Pins 3, 4 and 5 and also 10, 11 and 12 of Fig. 1 are replaced by metal tabs on each side of the device. These are very convenient for soldering to a heat sink.

- (ii) The LM377N contains internal circuits which protect it from overheating. If the silicon chip becomes too hot, the device switches itself off until it becomes cooler.
- (iii) Protective circuits prevent the device from being damaged by excessive current. Such currents are likely to flow if either of the outputs is accidentally shorted to earth.
- (iv) The input impedance is relatively high,  $3M\Omega$ , and this increases the versatility of the device.
- (v) Any hum on the power supply line is reduced by 80dB. The separation between the two channels is typically 70dB.

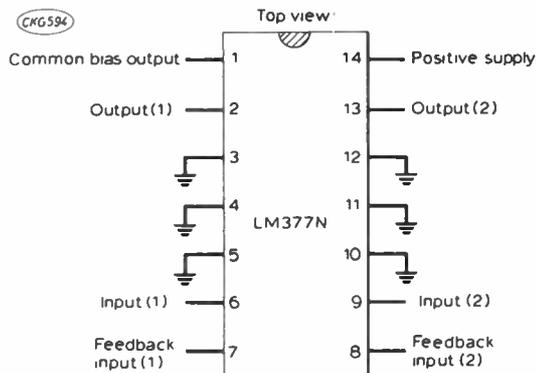


Fig. 1. Pin connections to the 14 pin DIL LM377N.

The LM377 devices are intended mainly for use in stereo equipment where the output power required does not exceed 2W. However, they can also be used in a bridge circuit where the two amplifiers in the device are used in push-pull to provide a monaural output of up to 4W.

## Advantages


The following features make the LM377N especially attractive to the amateur constructor as well as to the professional circuit designer:—

- (i) The output stages are automatically centred at the correct bias so that the output voltage can swing an equal amount in either direction resulting in maximum power output at a given distortion level. (Some power amplifiers circuits require a preset potentiometer so that the bias can be adjusted manually.)
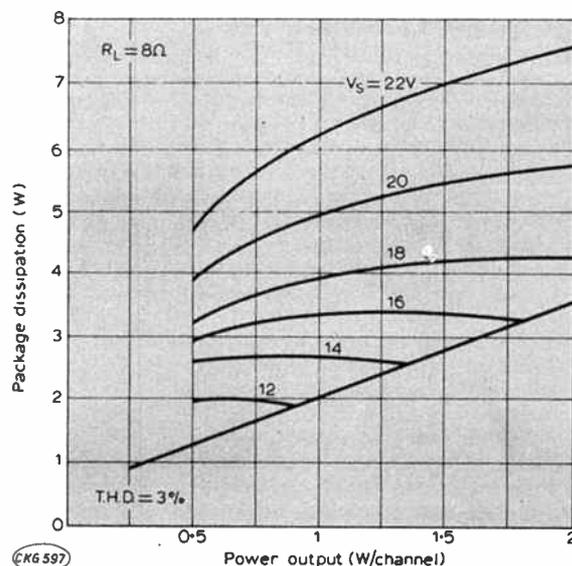
## Circuits

In all circuits the inputs of both amplifiers should be biased by the voltage from pin 1. The bias current is typically  $0.5\mu A$  to each amplifier.

In addition, feedback from each output should be applied to the feedback input of the same amplifier. The amount of feedback controls the gain.



Graphs relating supply voltage to output power for the LM377N.

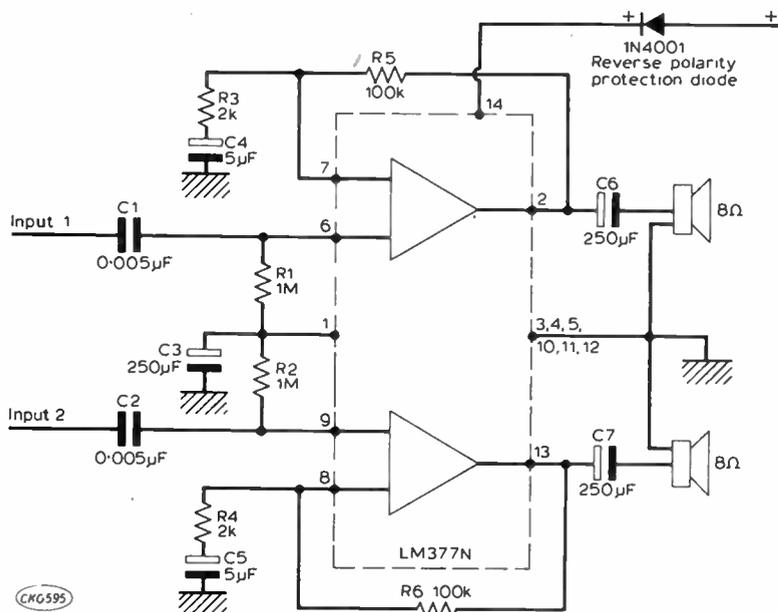


Fig. 2. Circuit of a practical stereo amplifier suitable for a record player. A volume control will be required on the input circuit.

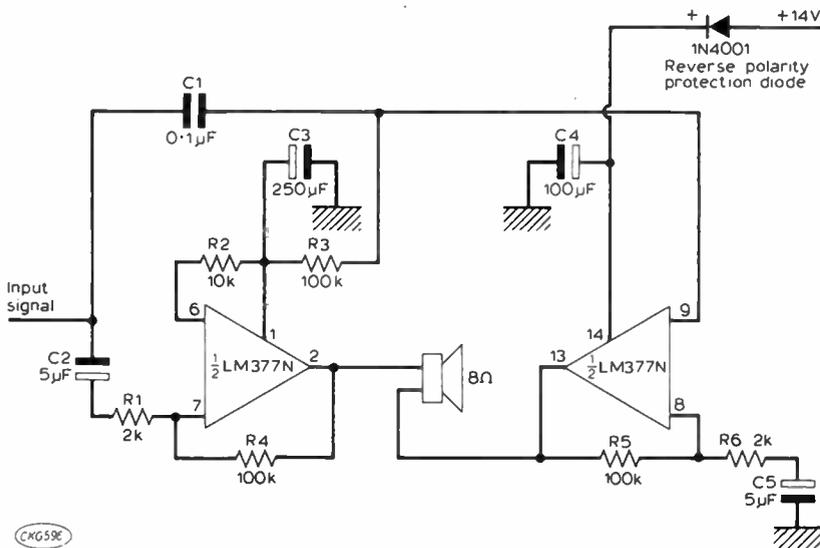


Fig. 3. This mono circuit utilises both amplifiers to provide 4W output.

A typical circuit for the use of the LM377N as the two power amplifiers of a stereo system is shown in Fig. 2.

Bias from pin 1 is decoupled by C3 and applied to the inputs at pin 6 and 9 via R1 and R2. The input signals are capacitively coupled through C1 and C2 respectively in order to prevent the bias from being affected by the impedance of any previous stage. The input impedance of the LM377N is relatively high and therefore the coupling capacitors can be fairly small in value.

In the upper amplifier of Fig. 2, the feedback is taken from the output at pin 2 through R5 to pin 7. The voltage gain is equal to  $R5/R3$  which is 50 times or 34dB. The gain may be increased by reducing R3 but the distortion will increase.

Similarly, the gain of the lower amplifier is  $R6/R4 = 50$ . The typical gain of an amplifier without any feedback is 30,000 (90dB).

The mean output potential is equal to approximately half the supply voltage. An electrolytic capacitor (C6 and C7) must therefore be placed between the outputs of the device and each speaker so that direct current cannot flow. If the value of the capacitors is reduced, an inferior bass response will be obtained.

### Power supply

The LM377N can be fed from a supply line having any value between 10V and 22V. The absolute maximum supply voltage is 26V, but one should always allow a safety margin to avoid the risk of damage to the device.

A current of about 15mA is taken from a 20V supply when no signal is applied to either input, but the current rises towards 1A when full output power is being delivered to the speakers.

The maximum output power which can be obtained from each channel depends on the supply voltage used and also by the speaker impedance. A typical LM377N provides 2.5W per channel when fed from a 20V supply into 8Ω speakers, whilst all devices should provide a minimum of 2W per channel under these conditions.

The LM377N can dissipate up to about 2.5W continuously without a heat sink, but if the centre pins of the device are soldered to 2.5 sq. in of copper on a printed circuit board, the maximum dissipation is increased to about 4.2W. Some form of heat sink seems required when an 8Ω speaker is employed, unless the power supply voltage does not exceed about 14V. In practice, however, the device is seldom operated at maximum power level for more than a moment (unless one likes to listen to sine waves!). Normally one is not likely to require a heat sink when using supply voltages of up to 18V provided that the speaker impedance is not less than 8Ω.

### Mono Amplifier

A single LM377N device can be used in a single channel system to provide an output power of 4W. Fig. 3.

*continued on page 1086*

# PRESELECTOR for 10-30 MHz


F. G. RAYER G30GR

**M**ANY receivers are susceptible to second channel interference when working on the higher frequencies. This means that if the receiver employs an intermediate frequency of 470kHz, the oscillator is working at a frequency 470kHz higher than that of the wanted transmission and signals which are 470kHz higher than this, or 940kHz higher in frequency than the wanted transmission, can beat with the receiver oscillator frequency, to produce a signal which passes through the 470kHz amplifier, interfering with the wanted signal. On the lower frequencies, there is usually sufficient selectivity ahead of the mixer to avoid difficulty from this cause. But on higher frequencies, the receiver is unable to totally eliminate the offending signals which cause interference and whistles.

Even a well-designed receiver with one RF stage may not provide second channel rejection better than 15dB at 30MHz. If a signal strength scale of 6dB per S-point were used, as is quite usual, this would mean that if a wanted signal read S9, an unwanted signal of equal strength 940kHz higher in frequency would read S6+, which is a severe level of interference.

Such interference can be greatly reduced by raising the receiver intermediate frequency, or by increasing the second channel rejection ahead of the mixer. Changing the IF is probably impossible, but the unit here will enormously increase the second channel rejection.

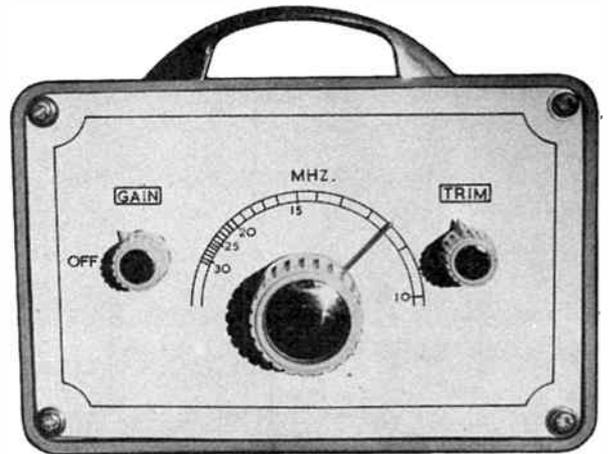The maximum benefit will be found with receivers which have no tuned RF stage, or only one RF stage, and employ a 455-470kHz intermediate



Completed preselector in its 6x4x4in cabinet.

frequency. With such receivers, 19m broadcasts may greatly mar reception of 20m amateur signals, for example. The unit can also be employed with other receivers including those with a 1.6MHz or other IF.

## CIRCUIT

This is shown in Fig. 1. As second channel interference is not usually troublesome at signal frequencies lower than about 10MHz, the unit covers approximately 10MHz to 30MHz in a single band, thus avoiding any need for band switching. L2 and

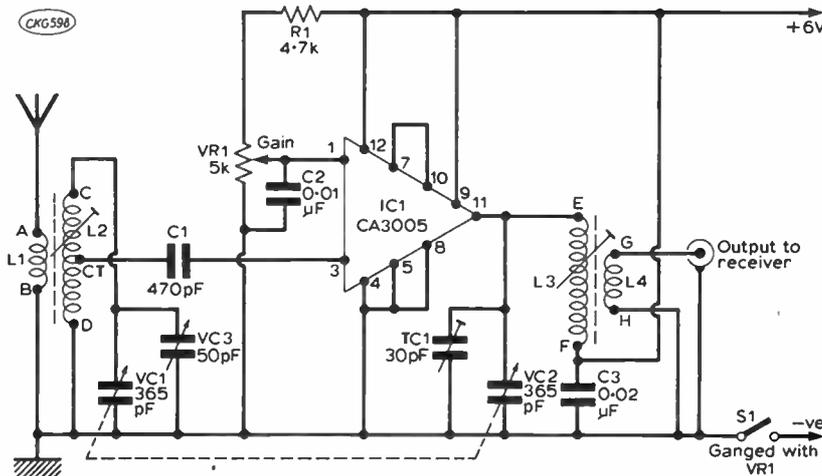


Fig. 1. Circuit of preselector using a single integrated circuit. Input, output and battery connections are at the rear. When placed between aerial and receiver useful gain will result as well as a reduction in second channel interference.

L3 are tuned with the ganged capacitor VC1/VC2 providing two extra tuned circuits before the receiver. In most cases this will almost completely eliminate second channel interference. VC3 is a panel trimmer to allow peaking the aerial circuit with almost any aerial.

The CA3005 IC operates with a 6V supply. It is listed as giving 20dB gain at 100MHz, but the full gain is not achieved here due to the circuit being arranged for operation from a single power supply, and because of the difficulty of matching the input and output impedances at all frequencies. The input is approximately matched by the centre tap on L2, while the transformer L3/L4 is arranged to give an output impedance suitable for most receivers.

Gain control is provided by VR1, to avoid overloading the receiver on strong signals.

## IC BOARD

The board is wired as in Fig.2. Note that the projection on the IC corresponds to lead 12. Spread the leads slightly so that they may pass through the Veroboard holes as indicated.

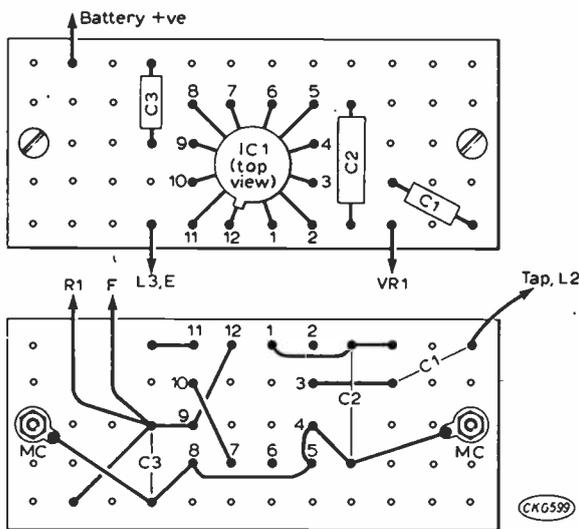


Fig. 2. Both sides of the small circuit board that carries the IC.

Two 6BA bolts with tags form the earthing points MC. Leave projecting leads from C1, for battery positive, VR1 and for VC2. Also solder on R1.

## COILS

These use 24swg enamelled wire throughout, Fig. 3. For the aerial coil, begin at C as near the top of the former as possible, and wind on  $4\frac{1}{2}$  turns. Scrape the wire and twist the centre tap. Wind a further  $4\frac{1}{2}$  turns and finish at D. Leave a small space and beginning at A wind on 4 turns, finishing at B.

For the second coil, wind 9 turns from E to F, leave a space as before, and put on 5 turns from H to G.

The ends of the windings can be secured with a loop of cotton lightly smeared with quick-drying adhesive, and given a turn or two round the former. Fix one end by this means, wind on the turns mentioned, and secure the finish of the winding in the same way, pulling it tight by the cotton.

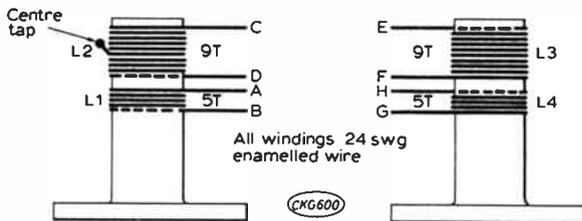


Fig. 3. Details for winding the two coils used in the preselector.

## CHASSIS

The panel for the case listed is approximately 6 x 4in. Punch a clearance hole for the spindle of VC1/2. As this capacitor has an integral drive and the spindle cannot be cut shorter, it can be spaced back from the panel as in Fig. 4, to bring the knob nearer the front. This requires three 4BA bolts, each with two nuts, locked against panel and capacitor. VR1 and VC3 are also set back a little by extra nuts or washers.

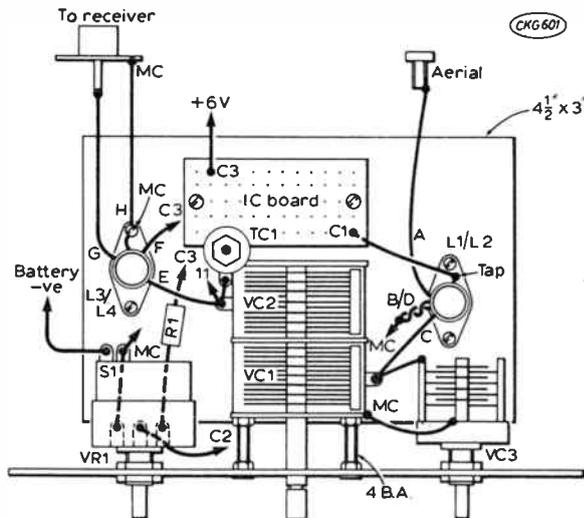


Fig. 4. Top view of the chassis showing position of the IC board and major components.

The chassis is a flat plate  $4\frac{1}{2} \times 3$ in. It is secured by two short 4BA bolts which pass through it and into the threaded holes in the capacitor frame. Place a few washers between plate and capacitor.

## ★ components list

### Resistors


R1 4.7kΩ  $\frac{1}{4}$ W VR1 5kΩ linear with switch S1.

### Capacitors

C1 470pF, C2 0.01μF disc C3 0.02μF disc.  
VC1/2 2 x 365pF with slow motion drive.  
VC3 50pF (Jackson C804) TC1 30pF trimmer
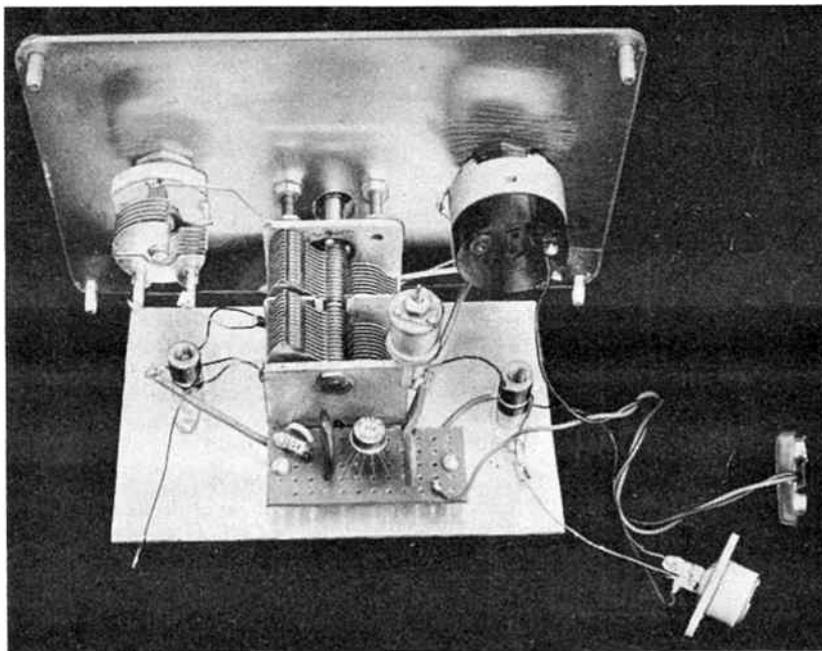
### Miscellaneous

Formers for coils,  $\frac{1}{2}$ in dia. with cores (2).  
Knobs. ICI, CA3005. Aerial socket and output socket. Instrument case about 6 x 4 x 4in.



*Finished preselector. Flexible connections are made to battery connector and output socket.*

Holes are drilled to take the circuit board bolts which are locked with extra nuts. Wiring must be clear of the metal. The coils are held with 8BA bolts and nuts.

## WIRING

Wiring is then completed as in Fig. 4. TC1 has its lower tag soldered directly to the frame of VC1/2, the second tag being connected to VC2, together with the lead from pin 11, IC1.

The coil leads are cut to length, scraped, and soldered to the points shown. Note that H goes to the chassis at a bolt securing L3/L4.

The battery consists of four HP7 or similar cells, in a 4-cell holder. The holder is secured in the back of the insulated case, near the top, by a small bolt.

As the receiver employed a co-axial lead, a socket for this was provided as in Fig. 4. An earth circuit to the unit is then available through the co-axial outer conductor. If the receiver does not employ this type of aerial input lead, take a wire from G, L4, to the receiver aerial socket, and connect H and the chassis to the receiver earth terminal.

## OPERATION

TC1 can be set at about half maximum capacitance. Tune in a transmission on about 10MHz, set VC1/2 nearly fully closed and rotate the cores of the coils for best reception.

Subsequently check that 30MHz signals peak with VC1/2 nearly fully open, and that VC3 also peaks up signals or background noise. If necessary, re-adjust TC1 to allow proper tuning with VC3, and check the core positions, so that little adjustment of VC3 is required, when tuning across the whole band.

Adjustments are best carried out by observing the receiver signal strength meter, or with the receiver AGC switched off, or by selecting weak signals which do not operate the receiver AGC. VR1 should be set for maximum gain when doing this. As an aid, a very short aerial may be temporarily taken to A. VC3 should then have quite a sharp peak, but this effect will be reduced with a long aerial when it may be preferable to place a small capacitor in the lead from aerial to A. ■

## IC of the Month—continued from page 1083

The two amplifiers are used in a 'bridge' or push-pull circuit. The input signal is fed through C2 and R1 to the feedback input (pin 7) of the first amplifier and the same signal also passes through C1 to the non-inverting input (pin 9) of the second amplifier.

When the voltage at the pin 2 output increases, that at pin 13 therefore decreases by the same amount and vice-versa. The speaker is thus driven by this push-pull signal. This circuit has the advantage that no capacitor is required in series with the speaker, since the mean potentials of pins 2 and 13 are almost identical.

The bias from pin 1 is decoupled by C3 and fed through R2 to pin 6. It also passes through R3 to pin 9.

The gain of each amplifier is equal to the ratio of the feedback resistors, namely  $R4/R1 = R5/R6 = 50$ . However, the push-pull action gives an effective overall gain of twice this value.

The LM377N is available from Athena Semiconductor Marketing Company Ltd., 140 High St., Egham, Surrey, at £2.70 plus VAT for small quantities, inclusive of p & p. ■

## RADIO BY CABLE & SATELLITE


—continued from page 1087

Many countries have determined that this is unavoidable within the boundaries of the technical possibilities and it has been recognised by the UNO associated International Telecommunications Union in 1971 in Geneva. At the same time, however, it was established that the use of TV satellites is only possible by observing frequency, positioning and ground coverage plans which are to be drawn up at a special planning conference for this purpose which will take place in 1975/76. ■

## EXPERIMENTAL WORKSHOP

We regret that due to pressure on editorial space this month, Part 6 of this series has been held over until the April issue.

# RADIO by Cable & SATELLITE

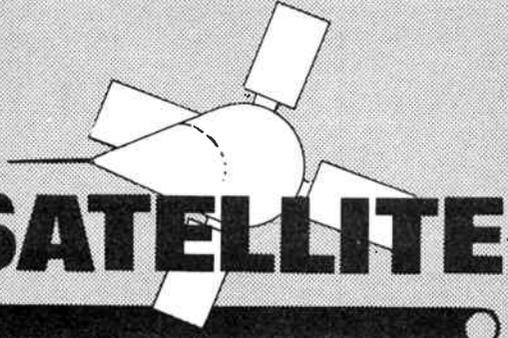

**A**LTHOUGH it is a task of exchange technology to handle the signals, in connecting individual communications (telephone, telex), in such a way that the connection is made quickly and reliably, broadcasting must ensure that the primary signal is transported long distances without distortion, be they telephone signals or for telegraphy, music, TV, picture transmission, data transfer or remote control. But what are the problems that arise?

A modern carrier frequency system with 2700 channels for speech has an amplifier spacing of 4.5 km; at a distance of 4500 km as is found in the trade area between the USA and Canada, 1000 amplifiers are operated one after the other.

Assuming a medium amplification of 30dB (i.e. the signal output is increased each time by a factor of  $10^3=1000$ , the voltage by around a factor of 31.6) the overall amplification over the whole section amounts to the almost unbelievable figure of  $10^{3000}$ . For comparison: the entire universe contains "only" around  $10^{83}$  protons, since the creation of the earth approximately 15 billion years ago a total of "only"  $5 \cdot 10^{17}$  seconds has passed.

## Cables

To guarantee the necessary quality over so many stages, extremely high demands must be made, both on the technical equipment (amplifiers, converters, modulators etc.) as well as on the directions of transmission. With regard to the latter there are three "media" which have proved themselves and which are to be found predominantly or exclusively in long-distance traffic: cables, directional radio including satellites and—as a medium of the long-term future, suitably directed laser beams.

Cable, especially coaxial, is already considerably protected by its construction and laying against outside influences from space, the atmosphere and from technical installations, so that in cable transmission systems non-linearity and noise must be kept as low as possible.

Disregarding the "symmetrical" carrier frequency cables, used predominantly with up to 120 speech channels for regional systems, there is a whole series of coaxial types at an impedance of around 75 ohm. There are many various internal sizes, e.g. from 1.2 mm for 300 speech channels or 2.6 mm for a choice of 960, 1260 or 2700 channels. If one is prepared to reduce the amplifier spacing even more, one could increase the basic bandwidth considerably (e.g. to 40 to 60MHz or even higher).

"Hollow" cable recently developed can theoretically provide a transmittable overall bandwidth of around 100,000MHz. It is, in fact, a radio wave guide which should be most suitable for the transmission of digital signals (e.g. for pulse code modulation). Technically hollow cables are well advanced although there are certain reservations with regard to their economic application.

## Satellites

The directional radio line, widely used for the transmission of TV modulation (video band) but also for multi-channel speech bands, is physically an ideal transmission medium. However, it requires the application of special "noise reducer" procedures due to the influences of extra-terrestrial, tropospheric and industrial radio signals. Partial bandwidths of up to 30MHz have shown themselves to be the best for the transmission of television or telephone channels in various frequency ranges between 2 and 12GHz. Transmitter output is in the area of several watts.

Satellite paths are basically extended directional radio lines with fields of  $2 \times 36\,000$  km length (to and from) with high transmitter outputs, extra large aerials and extremely sensitive receivers (maser) on the terrestrial stations. They are particularly suitable for trans-continental and trans-oceanic relays, operating at frequencies corresponding to those in directional radio technology.

A transmission medium of the future is the laser beam which is strictly monochromatic, polarised and coherent. In a free field of dissemination they are not practicable because of absorption as with normal light, but when suitably guided by lens conduction and glass fibre, it reveals its full potential.

In particular the glass fibre bundle cable, offering an extreme bandwidth even with individual fibres, combined with the multifarious operating possibilities of universal cable, promises to be an important transmitting medium, both in long distance communications and in local traffic in densely populated areas. All of this is of course dependent on a corresponding advance in the components and subsystems in the field of optronics—an advancing technology being fully exploited now.

Satellites providing a country with programmes via only one transmitter can of course be received across borders. Even with rays with a one degree focusing, whose focal area is accommodated within the boundaries of the country cannot prevent this.

—continued on page 1086

# Oscilloscope

## PART 1 **techniques** ALAN AINSLIE

**I**N this series we shall be taking a close look at oscilloscopes of the kind likely to be used by the average electronics enthusiast. This leaves a large range of classes of instruments, but we shall not be too concerned with the developments incorporated in the brand new, four figure price oscilloscopes as these can generally be classed as purely professional in appeal and application.

The instruments to be considered will range from the simplest types of scope, through TV service scopes to the laboratory scopes of a few years ago, now available to the keen amateur—but at a price!

We shall consider design principles, the basis for modifications, and calibration. This last point is rather important as manufacturers can charge a lot for recalibration of their instruments, especially if not of current manufacture.

We shall also look at some oscilloscope applications and at a few pieces of additional equipment in order to carry out an increased range of tests and measurements.

Oscilloscopes fall broadly into four main classes:—

1. AUDIO FREQUENCY
2. TELEVISION AND PULSE
3. LABORATORY
4. SPECIAL PURPOSE

Ignoring the special purpose scopes for the time being, the oscilloscopes are grouped into a convenient scale of ascending bandwidth.

### BANDWIDTHS


As most scopes have a low frequency limit of DC (DC coupled) or a few Hz, the bandwidth figure quoted is the upper frequency limit at 3dB down (or however else the manufacturer specifies).

The bandwidth information gives an indication of the highest frequency that the scope can predictably handle.

Considering the two curves in Fig. 1, both scopes would have a written bandwidth of 5MHz, but scope A would in fact perform quite well past this figure whilst scope B drops straight off. Scope A could be used but with loss of calibration up to perhaps 10MHz or so, scope B being totally useless at this frequency.

Incorporated in any statement concerning bandwidth is an implication of the rise time of the scope.

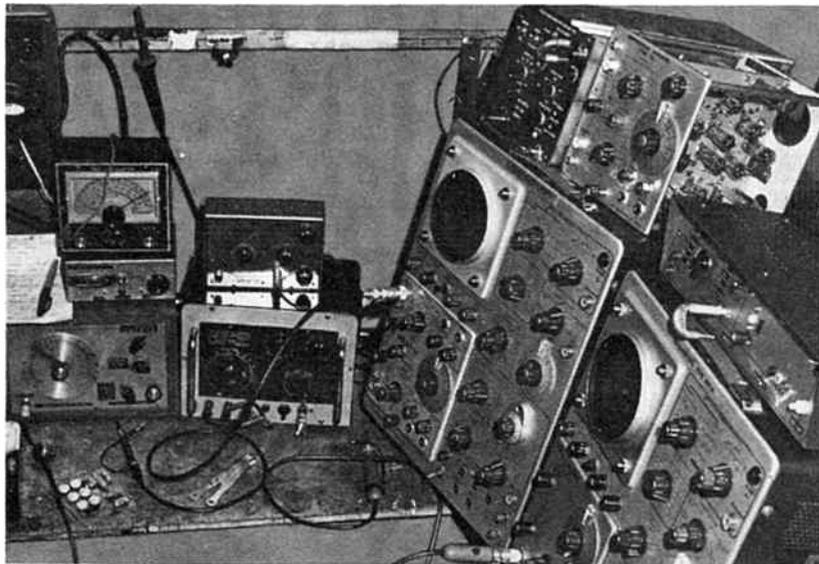If we consider an oscilloscope amplifier displaying a 1MHz signal, and this signal is at the -3dB point, we can arrive at some justification for the rather mysterious equation used to express rise time in terms of bandwidth.



*This imposing array of test equipment in just one corner of the author's workshop will serve to underline the fact that this series of articles on the oscilloscope contains much practical information as well as theoretical discussion.*

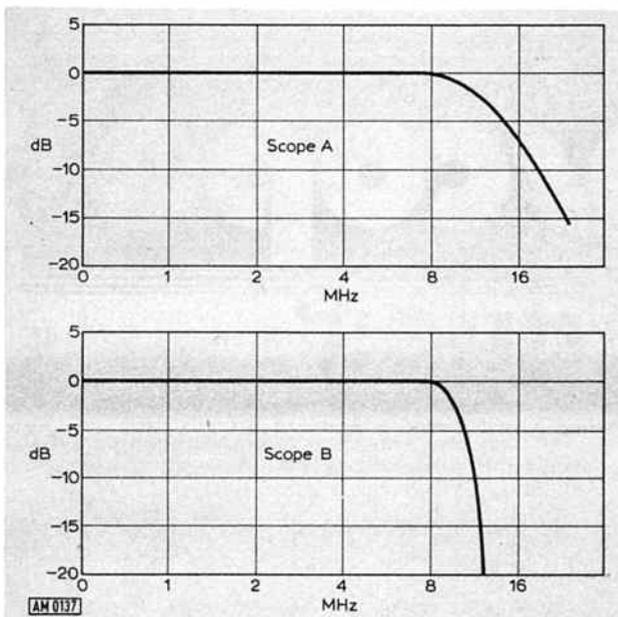


Fig. 1. The response curve of the Y amplifier in two different oscilloscopes, to illustrate the meaning of "bandwidth."

The time period of the 1MHz signal is  $1\mu\text{sec}$ . Thus for one half period the time is 500ns and for the rising portion 250ns. If now the slope of the upward going part of the cycle is taken to represent the step function applied to the scope, then the rise time of this 1MHz (3dB down) scope would appear to be 150ns.

But the 1MHz signal is not of 100% amplitude (it is 3dB down), and as rise time  $T_r$  is defined as the time to increase a step function from 10% to 90%, a correction is required, Fig. 2.

As 3dB down corresponds approximately to 30% down, i.e. the trace height at the -3dB point is only 70% of what it should be.

It is necessary to bring the 70% trace to 90% and in doing this  $T_r$  is increased by  $90/70$  giving a theoretical rise time of 322ns.

In practice the figure is found to be between 350 and 390ns, depending on the shape of the response. The response curve of Fig. 1, scope A would give a faster rise time than that of scope B, although both have the same bandwidth.

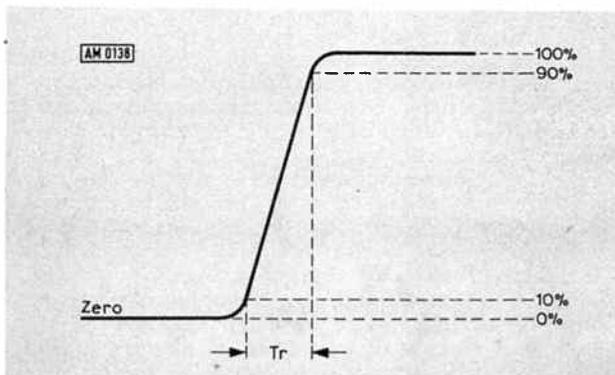


Fig. 2. First part of a response curve with a step function input to the scope. The rise time is a function of the bandwidth of the amplifier.

Taking the rise time to be 365ns for a 1MHz scope and applying the laws of proportion we get the expression:—

$$\text{Rise Time (ns)} \times \text{Bandwidth (MHz)} = 365$$

This expression holds true for the vast majority of cases, but more about that when we come to consider the Y amplifiers in more detail.

Returning to our classification of oscilloscopes it seems reasonable that the audio oscilloscope has but a limited bandwidth (1MHz or so) while the TV or pulse oscilloscope has a bandwidth of perhaps 10 or 15MHz and is capable of displaying more complex and more rapidly recurring waveforms. The laboratory scope on the other hand has a bandwidth extending from 15MHz and up and into the hundreds of MHz on the very latest real time oscilloscopes.

Using sampling techniques (imaginary or virtual time) bandwidths into the GHz region have been achieved but this type of scope belongs to the special purpose class. It is interesting to think of the real time response of say a 5GHz scope, 10% to 90% in  $7 \times 10^{-11}$  sec, quite fast!

Returning to earth, although it is convenient to classify a scope by bandwidth (or rise time) there are other, perhaps more striking, differences between the classes of scopes.

## TIMEBASES

The uses of an audio oscilloscope are confined usually to periodic waveforms that can be adequately displayed by the use of a synchronised timebase without the need for complex and expensive trigger circuits. The difference between a sync or trig timebase will become clear when we come to consider more fully the numerous methods used to provide a timebase. Suffice to say that the sync timebase is a free running oscillator which is pushed along by a portion of the Y signal applied as sync, whereas the trig timebase waits for a suitable signal before commencing a sweep.

One consequence of the sync mode is that the input signal (Y) must have a repetition frequency higher than that of the timebase for a stable image to result, as in Fig. 3. If the timebase is run faster than the repetition rate of the waveform, in order to view detail the trace folds up into a jumble.

Applied to the audio scope this latter effect is not of too great a consequence as there is usually little detail lurking in a signal repeating at 10kHz. However in TV work we immediately become faced with complex waveforms to lock and also the possibility that the waveform may be required to be investigated more closely.

The triggered timebase becomes a necessity together with the improved Y amplifier bandwidth. The timebase speed ranges are also increased for greater versatility and various modes of timebase operation are employed, including the important addition of an "EXTERNAL TRIG" connection enabling the timebase to be controlled externally. This facility is invaluable in TV work as it enables the frame generator in the receiver to work as a delay timebase generator, the trig level control on the scope selecting the lines to be viewed in isolation on the screen.

This sort of facility necessitates yet another improvement to be made to the simple audio scope, namely the trace brightness.

Fig. 3. The top display occurs when the timebase runs faster than the repetition rate of the input waveform. The consequence of a timebase running slower than the repetition rate is shown in the lower display.

A recurring 1kHz sine wave may be bright enough, but when the trace is scanning say 10cm in 64 $\mu$ sec, and then only 25 or 50 times a second, the trace brilliance falls to almost vanishing point unless high CRT potentials are employed. Usually between 2 and 5kV are used on oscilloscopes of this nature, as opposed to possibly less than 1kV for the audio scope.

The TV or pulse oscilloscope then has, apart from an improved bandwidth, a fairly sophisticated timebase system and an improved display mechanism, together with a few other improvements such as DC coupling and the provision of calibrators.

Oscilloscopes intended for reasonably accurate measurement, but that are built to a price, usually incorporate some method of generating standard waveforms of precise voltage and/or time, this being cheaper than trying to stabilise the Y amplifier gain and timebase against variations.

A fairly typical example of the type of calibration provided is the Cossor 2000 oscilloscope, a 5MHz double beam scope suitable for general TV service and measurement.

The Y amplifiers are calibrated against an internally generated signal of 300mV. The Y amplifier control is set to give 3cm deflection with the input attenuator set at 0.1V/cm.

The 300mV signal is obtained from 50Hz from the scope mains transformer and a small neon is used to provide a reference level of about 70V from this high voltage AC. The resulting 70V square wave is then attenuated and is available as the 300mV calibration signal.

Time calibration is available as a 20MHz oscillator providing intensity modulation of the beam. This means that a display brightens up at every 50ns enabling accurate time measurements at the higher sweep speeds.


## LABORATORY SCOPES

The final class of scope that we shall consider is the laboratory scope and in this class we can conveniently consider the special purpose oscilloscopes.

In general one expects to find that a laboratory scope has a good bandwidth, versatile timebase with fast sweep speeds, high tube voltage and is capable of long lasting calibration to within a few per cent, depending on the measurement methods employed.

Intended for use in research and for the investigation of complex waveforms, the laboratory oscilloscope needs to be versatile and has therefore rather a lot of controls and tends to be physically large.

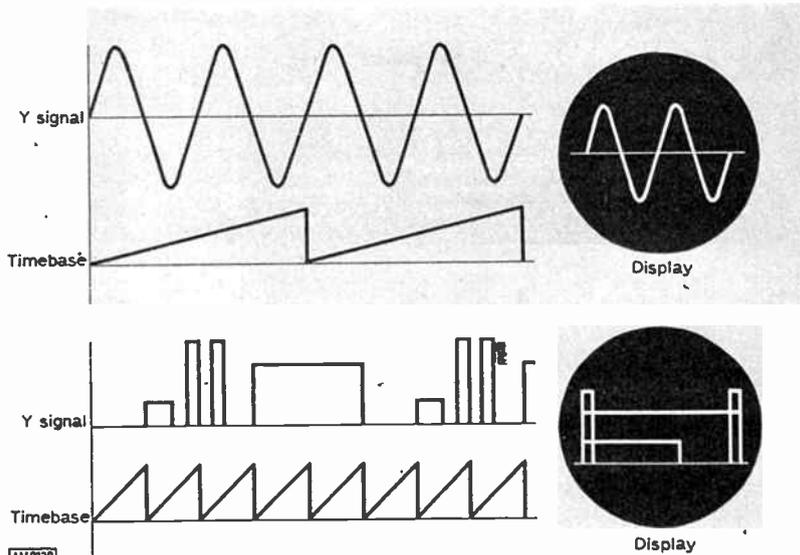As we shall see later, wide bandwidth deflection systems require a large number of valves passing



fairly high currents. This, together with the number of valves in the timebase (usually two are provided) and the supply regulator needed to maintain calibration, means that the valve count is sometimes over a hundred and a power consumption of almost 1kW is not uncommon. These big scopes are usually trolley mounted with a fan to keep the operating temperature at a reasonable level.

## TEKTRONIX TRENDS

Pioneers in this field of scopes were undoubtedly the American firm Tektronix and many other manufacturers have done a lot of copying from the Tektronix design. The Tektronix format of tube in the top left corner, Y amplifier below, and timebase down the right-hand side is now familiar to users of laboratory scopes.

With the advent of Tektronix styling came another innovation, perhaps conceived initially by the same company and now copied by many, that of plug-in Y amplifiers, followed by plug-in almost everything! This means that a wideband (33MHz for Tektronix) main frame can be used for a number of special purposes just by changing plug-in units.

The main frame houses the CRT, power supplies, Y drive amplifier, X amplifier and the timebase if this is not plug-in. A range of Y plug-ins would then be used with the scope, providing double beam operation, differential inputs, very high sensitivity or a special function such as a spectrum analyser or four channel display. If plug-in timebases are provided these could be normal timebase, delay plus normal, very slow, or a straightforward amplifier plug-in for XY display.

Whilst appreciating that these plug-ins can cost a great deal of money it is fairly obvious that a selection of plug-ins is cheaper than a selection of scopes! The user is also able to keep in touch with current technology by the purchase of recent plug-ins offering such facilities as sampled inputs giving very high apparent bandwidths, although not in real time. One other advantage of plug-ins is that the Y amplifier controls probably get the hardest use on a scope and it is an easy matter to remove the plug-in for maintenance without having to disembody the whole scope.

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

MAIL ORDER. CALLERS SATURDAYS

C.W.O. Please. P. & P. add 10p to orders under £2. Prices exclusive of VAT  
PLEASE ADD 10% TO FINAL TOTAL

Send 10p Postage for our comprehensive catalogue.

| TRANSISTORS |     |       |     | DIODES |     |        |     |
|-------------|-----|-------|-----|--------|-----|--------|-----|
| AC125       | 12p | AF126 | 15p | OC81   | 13p | OA85   | 7p  |
| AC126       | 12p | AF127 | 20p | BFY50  | 22p | T1S43  | 30p |
| AC127       | 12p | BC107 | 10p | BFY51  | 22p | 2N1306 | 23p |
| AC128       | 12p | BC108 | 10p | MJE370 | 57p | 2N1307 | 23p |
| AC176       | 14p | BC109 | 11p | MJE520 | 52p | 2N2926 | 9p  |
| AC187       | 12p | BC147 | 12p | OC26   | 40p | 2N3054 | 10p |
| AC188       | 12p | BC148 | 12p | OC28   | 40p | 2N3053 | 20p |
| AD161       | 30p | BC149 | 12p | OC35   | 40p | 2N3054 | 43p |
| AD162       | 30p | BC177 | 14p | OC42   | 10p | 2N3055 | 55p |
| AF114       | 12p | BC178 | 14p | OC44   | 10p | 2N3704 | 12p |
| AF115       | 12p | BC179 | 14p | OC45   | 10p | 2N3705 | 11p |
| AF116       | 12p | BD131 | 49p | OC70   | 10p | 2N3706 | 11p |
| AF117       | 12p | BD132 | 49p | OC71   | 10p | 2N3707 | 11p |
| AF118       | 40p | BD132 | 49p | OC71   | 10p | 2N3707 | 11p |
| AF124       | 22p | BF194 | 15p | OC72   | 10p | 2N3819 | 25p |

**POLYESTER CAPACITORS.** Axial lead type.  
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 2½p; 0.01µF, 0.015µF, 0.022µF, 3p; 0.047µF, 0.068µF, 0.1µF, 0.15µF, 4p; 0.22µF, 7p; 0.33µF, 10p; 0.47µF, 13p  
160V: 0.1µF, 0.15µF, 4p; 0.22µF, 5p; 0.33µF, 6p; 0.47µF, 7p; 0.68µF, 10p; 1µF, 13p.  
Radial lead P.C. type:  
250V: 0.01µF, 0.015µF, 0.022µF, 3p; 0.033µF, 0.047µF, 0.068µF, 3½p; 0.1µF, 4p; 0.15µF, 4p; 0.22µF, 0.33µF, 5p; 0.47µF, 7p; 0.68µF, 10p; 1.0µF, 11p.

**ELECTROLYTIC CAPACITORS.** Miniature axial lead type.  
63V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 47µF, 68µF, 5p each.  
40V: 100µF, 6p; 150µF, 25V, 6p; 25V: 220µF, 11p; 470µF, 13p; 1,000µF, 25p.  
16V: 1000µF, 1500µF 10p

**CERAMIC CAPACITORS:** 50V d.c. Plaquelette body 25mm leads  
Range: 22pF-10,000pF. Price 2p each.  
0.015µF, 0.022µF, 0.033µF, 0.047µF 3p.

**POTENTIOMETERS:** Carbon  
Track 0-25W, log and linear values.  
1kΩ-2MΩ Single gang 12p  
5KΩ-2MΩ s/gang w/switch 24p  
2kΩ-2MΩ Dual gang 37p

**SLIDER POTENTIOMETERS**  
0-25W log and linear values  
10kΩ-100kΩ Single gang 40p  
10kΩ-100kΩ Dual gang 55p

**RESISTORS**

| ±W | Tol | Range     | Values | 1-9 | 10-99 | LM300 | T099      | £1-70 |
|----|-----|-----------|--------|-----|-------|-------|-----------|-------|
| ½W | 5%  | 2R-10M    | E12    | 1p  | 0.8p  | LM304 | T099      | £1-70 |
| 1W | 5%  | 2R-10M    | E12    | 1p  | 0.8p  | 709C  | T099      | 30p   |
| 1W | 5%  | 2R-10M    | E12    | 2p  | 1.5p  | 709C  | 8pin DIL  | 32p   |
| 4W | 10% | 1-10 ohm: | E12    | 6p  | —     | 741C  | 14pin DIL | 32p   |

**MYLAR FILM CAPACITORS**  
100V: 0.00µF, 0.002µF, 0.005µF, 0.01µF, 0.02µF, 0.04µF, 0.05µF 3p.  
100V: 0.1µF, 0.2µF, 50V: 0.47µF 6p.

**PRESET POTENTIOMETERS**  
0-25W 1kΩ-1MΩ Hor. and Vert. 5p  
0-1W 100Ω-220kΩ Vert. only 3p

**KNOBES**  
To fit ½" shaft unless specified  
Black Pointer type 6p  
Silver 10p  
Black 1" with chrome rim 15p  
Slider Pot knob (Black) 10p  
Slider Pot knob (Silvered) 10p

| THYRISTORS |             | SWITCHES                     |     | ZENER DIODES |                |
|------------|-------------|------------------------------|-----|--------------|----------------|
| CRS 1/05   | 50V 1A 20p  | Toggle SPST                  | 18p | BZY88        | Series 400mW   |
| CRS 1/60   | 600V 1A 38p | DPDT                         | 22p | 3-3V-33V     | Price 10p each |
| CRS 3/60   | 600V 3A 48p | Slide 1 amp DP               | 10p |              |                |
| C107B      | 200V 4A 52p | Wafer 1/12, 2/8, 3/4, 4/324p |     |              |                |

| VEROBOARDS |               | JACK PLUGS (CHROME) |     | SOCKETS  |     |
|------------|---------------|---------------------|-----|----------|-----|
| PITCH      | 0.1 0.15 0.15 | Standard Screened   | 12p | Standard | 12p |
|            |               | Stereo Screened     | 30p | Stereo   | 15p |
|            |               | 2.5mm Screened      | 8p  | 2.5mm    | 7p  |
|            |               | 3.5mm Screened      | 10p | 3.5mm    | 7p  |

**DIN PLUGS, SOCKETS AND COUPLERS**  
Pins: 2, 3, 4, 5 (180°, 240°), 6, 7  
PLUGS: 12p, SOCKETS: 8p, COUPLERS: 10p

**PHONO PLUGS, SOCKETS AND COUPLERS**  
Assorted Coloured Plugs: 5p, COUPLERS: 8p  
SOCKETS single: 5p, Double: 7p, Triple: 10p

**TTL 74 SERIES**

| 7400 | 7401 | 7402 | 7403 | 7404 | 7405 | 7406 | 7416 | 7417 | 7418 | 7419 | 7420 | 7421 | 7422 | 7423 | 7424 | 7425 | 7426 | 7427 | 7428 | 7429 | 7430 | 7431 | 7432 | 7433 | 7434 | 7435 | 7436 | 7437 | 7438 | 7439 | 7440 | 7441 | 7442 | 7443 | 7444 | 7445 | 7446 | 7447 | 7448 | 7449 | 7450 | 7451 | 7452 | 7453 | 7454 | 7455 | 7456 | 7457 | 7458 | 7459 | 7460 | 7461 | 7462 | 7463 | 7464 | 7465 | 7466 | 7467 | 7468 | 7469 | 7470 | 7471 | 7472 | 7473 | 7474 | 7475 | 7476 | 7477 | 7478 | 7479 | 7480 | 7481 | 7482 | 7483 | 7484 | 7485 | 7486 | 7487 | 7488 | 7489 | 7490 | 7491 | 7492 | 7493 | 7494 | 7495 | 7496 | 7497 | 7498 | 7499 | 7500 | 7501 | 7502 | 7503 | 7504 | 7505 | 7506 | 7507 | 7508 | 7509 | 7510 | 7511 | 7512 | 7513 | 7514 | 7515 | 7516 | 7517 | 7518 | 7519 | 7520 | 7521 | 7522 | 7523 | 7524 | 7525 | 7526 | 7527 | 7528 | 7529 | 7530 | 7531 | 7532 | 7533 | 7534 | 7535 | 7536 | 7537 | 7538 | 7539 | 7540 | 7541 | 7542 | 7543 | 7544 | 7545 | 7546 | 7547 | 7548 | 7549 | 7550 | 7551 | 7552 | 7553 | 7554 | 7555 | 7556 | 7557 | 7558 | 7559 | 7560 | 7561 | 7562 | 7563 | 7564 | 7565 | 7566 | 7567 | 7568 | 7569 | 7570 | 7571 | 7572 | 7573 | 7574 | 7575 | 7576 | 7577 | 7578 | 7579 | 7580 | 7581 | 7582 | 7583 | 7584 | 7585 | 7586 | 7587 | 7588 | 7589 | 7590 | 7591 | 7592 | 7593 | 7594 | 7595 | 7596 | 7597 | 7598 | 7599 | 7600 | 7601 | 7602 | 7603 | 7604 | 7605 | 7606 | 7607 | 7608 | 7609 | 7610 | 7611 | 7612 | 7613 | 7614 | 7615 | 7616 | 7617 | 7618 | 7619 | 7620 | 7621 | 7622 | 7623 | 7624 | 7625 | 7626 | 7627 | 7628 | 7629 | 7630 | 7631 | 7632 | 7633 | 7634 | 7635 | 7636 | 7637 | 7638 | 7639 | 7640 | 7641 | 7642 | 7643 | 7644 | 7645 | 7646 | 7647 | 7648 | 7649 | 7650 | 7651 | 7652 | 7653 | 7654 | 7655 | 7656 | 7657 | 7658 | 7659 | 7660 | 7661 | 7662 | 7663 | 7664 | 7665 | 7666 | 7667 | 7668 | 7669 | 7670 | 7671 | 7672 | 7673 | 7674 | 7675 | 7676 | 7677 | 7678 | 7679 | 7680 | 7681 | 7682 | 7683 | 7684 | 7685 | 7686 | 7687 | 7688 | 7689 | 7690 | 7691 | 7692 | 7693 | 7694 | 7695 | 7696 | 7697 | 7698 | 7699 | 7700 | 7701 | 7702 | 7703 | 7704 | 7705 | 7706 | 7707 | 7708 | 7709 | 7710 | 7711 | 7712 | 7713 | 7714 | 7715 | 7716 | 7717 | 7718 | 7719 | 7720 | 7721 | 7722 | 7723 | 7724 | 7725 | 7726 | 7727 | 7728 | 7729 | 7730 | 7731 | 7732 | 7733 | 7734 | 7735 | 7736 | 7737 | 7738 | 7739 | 7740 | 7741 | 7742 | 7743 | 7744 | 7745 | 7746 | 7747 | 7748 | 7749 | 7750 | 7751 | 7752 | 7753 | 7754 | 7755 | 7756 | 7757 | 7758 | 7759 | 7760 | 7761 | 7762 | 7763 | 7764 | 7765 | 7766 | 7767 | 7768 | 7769 | 7770 | 7771 | 7772 | 7773 | 7774 | 7775 | 7776 | 7777 | 7778 | 7779 | 7780 | 7781 | 7782 | 7783 | 7784 | 7785 | 7786 | 7787 | 7788 | 7789 | 7790 | 7791 | 7792 | 7793 | 7794 | 7795 | 7796 | 7797 | 7798 | 7799 | 7800 | 7801 | 7802 | 7803 | 7804 | 7805 | 7806 | 7807 | 7808 | 7809 | 7810 | 7811 | 7812 | 7813 | 7814 | 7815 | 7816 | 7817 | 7818 | 7819 | 7820 | 7821 | 7822 | 7823 | 7824 | 7825 | 7826 | 7827 | 7828 | 7829 | 7830 | 7831 | 7832 | 7833 | 7834 | 7835 | 7836 | 7837 | 7838 | 7839 | 7840 | 7841 | 7842 | 7843 | 7844 | 7845 | 7846 | 7847 | 7848 | 7849 | 7850 | 7851 | 7852 | 7853 | 7854 | 7855 | 7856 | 7857 | 7858 | 7859 | 7860 | 7861 | 7862 | 7863 | 7864 | 7865 | 7866 | 7867 | 7868 | 7869 | 7870 | 7871 | 7872 | 7873 | 7874 | 7875 | 7876 | 7877 | 7878 | 7879 | 7880 | 7881 | 7882 | 7883 | 7884 | 7885 | 7886 | 7887 | 7888 | 7889 | 7890 | 7891 | 7892 | 7893 | 7894 | 7895 | 7896 | 7897 | 7898 | 7899 | 7900 | 7901 | 7902 | 7903 | 7904 | 7905 | 7906 | 7907 | 7908 | 7909 | 7910 | 7911 | 7912 | 7913 | 7914 | 7915 | 7916 | 7917 | 7918 | 7919 | 7920 | 7921 | 7922 | 7923 | 7924 | 7925 | 7926 | 7927 | 7928 | 7929 | 7930 | 7931 | 7932 | 7933 | 7934 | 7935 | 7936 | 7937 | 7938 | 7939 | 7940 | 7941 | 7942 | 7943 | 7944 | 7945 | 7946 | 7947 | 7948 | 7949 | 7950 | 7951 | 7952 | 7953 | 7954 | 7955 | 7956 | 7957 | 7958 | 7959 | 7960 | 7961 | 7962 | 7963 | 7964 | 7965 | 7966 | 7967 | 7968 | 7969 | 7970 | 7971 | 7972 | 7973 | 7974 | 7975 | 7976 | 7977 | 7978 | 7979 | 7980 | 7981 | 7982 | 7983 | 7984 | 7985 | 7986 | 7987 | 7988 | 7989 | 7990 | 7991 | 7992 | 7993 | 7994 | 7995 | 7996 | 7997 | 7998 | 7999 | 8000 |
|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|
|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|------|

**BARGAIN OFFER OF THE MONTH**  
**ELECTROLYTIC CAPACITORS**  
Axial Lead: 4µF/10V 33µF/16V, 40µF/16V, 80µF/6.4V, 100µF/16V, 125µF/16V  
4p each. 250µF/15V, 640µF/10V, 1000µF/10V 8p each.

## ELECTRONIC MAINS TIMER

A reliable unit ideal for timing Bathroom/Tollet Ventilators Stairway/Cloakroom Lighting etc.  
Gives up to 30 mins delay before switching off.  
Delay: 1-30 mins adjustable.  
Max Load: 400VA or 1000 watts relative.  
Ivory Case: 3 1/2" x 3 1/2" x 2". Fitting instructions included.  
Trade Price: £5.80. Post 20p.

## DIMMER SWITCH

Type C1, 300 Watt Light Dimmer for 200/240 Volt A/C operation.  
Ivory Case: 3 1/2" x 3 1/2" x 1 1/2".  
Fitting instructions included.  
Price: £2.60. Post 20p. 10 for £21.50 each. £6.00 per pair. Post 25p. Post 30p.

## POWER UNIT Type P1076

Output switched 3, 4.5, 6, 7.5 9 and 12 Volts at 500mA D.C. Operates from 240 V. mains, suitable for Radios, Tape Recorders, Record Players, etc. Size 7.5 x 5.0 x 14.0 cm Price £2.85. Post 25p.

## SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen

| VA (watts) | Ref. No. | Price £ | P & P £ |
|------------|----------|---------|---------|
| 60         | 149      | 2.88    | 0.38    |
| 100        | 150      | 3.15    | 0.42    |
| 200        | 151      | 5.30    | 0.52    |
| 250        | 152      | 7.05    | 0.55    |
| 350        | 153      | 9.40    | 0.60    |
| 500        | 154      | 13.55   | 1.00    |
| 1000       | 156      | 24.97   | 1.20    |
| 2000       | 158      | 41.25   | *       |
| 3000       | 159      | 64.54   | *       |

## LOW VOLTAGE

Prim. 200-240V. Sec. 12 & 24V.

| Amps | Type | Price £ | P & P £    |
|------|------|---------|------------|
| 12V  | 24V  | No.     |            |
| 0.5  | 0.25 | 111     | 1.00 0.22  |
| 1    | 0.5  | 213     | 1.23 0.22  |
| 2    | 1    | 71      | 1.60 0.22  |
| 4    | 2    | 15      | 2.25 0.38  |
| 6    | 3    | 70      | 2.70 0.42  |
| 8    | 4    | 108     | 3.00 0.52  |
| 10   | 5    | 72      | 3.55 0.52  |
| 12   | 6    | 116     | 4.50 0.52  |
| 16   | 8    | 17      | 5.50 0.62  |
| 20   | 10   | 115     | 6.95 0.69  |
| 30   | 15   | 187     | 12.90 0.97 |
| 40   | 20   | 232     | 18.30 1.00 |
| 60   | 30   | 228     | 23.70 1.10 |

## 30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.

| Amps | Type | Price £ | P & P £ |
|------|------|---------|---------|
| 0.5  | 112  | 1.20    | 0.22    |
| 1    | 79   | 1.64    | 0.38    |
| 2    | 3    | 2.45    | 0.38    |
| 3    | 20   | 3.00    | 0.42    |
| 4    | 21   | 3.55    | 0.52    |
| 6    | 51   | 4.40    | 0.52    |
| 8    | 117  | 6.25    | 0.62    |
| 8    | 88   | 6.50    | 0.67    |
| 10   | 89   | 8       |         |

# TO SPARK YOUR IMAGINATION!

Kit comprises **EVERYTHING:** Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.



## the **SPARKRITE** Electronic Ignition Kit only £9.35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £9.35 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage.

**READY BUILT UNIT      GUARANTEED 5 YEARS**

**ORDER NOW** To: **ELECTRONICS DESIGN ASSOCIATES,** 82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9.35. Or for ready built unit £11.55.

NAME

ADDRESS

*(Live near Walsall? Call in for an actual workshop demo. It really is convincing.)*

PW 3

## ELECTRONIC & AUDIO BARGAINS

**HILLS HEADPHONE JUNCTION BOX MODEL JB3**  
For connecting headphones to amplifiers.  
OUR PRICE £1.37



**CAR STEREO SPEAKERS MODEL CRB200**  
Designed for door and shell mounting, 5 watts.  
OUR PRICE £3.05 P/P 27p



**VYNIAR SPEAKER CLOTH**  
Black or Black and Silver.  
Sizes: 18in. x 25in. 66p  
36in. x 25in. £1.10  
36in. x 50in. £2.20  
Send 7p stamp for our samples of Vyniar and Audio Components Catalogue.

**SOLDERING IRONS**  
CCN240 15 Watt £1.90  
X25 25 Watts £1.65  
Replacement Elements £1.10  
Replacement Bits 38p  
S13 Stand 96p

**SWITCHES**  
Small Slide Switch 10p  
Large Slide Switch 10p  
SPST Toggle Switch 16p  
DPDT Toggle Switch 20p  
Small (Biased) Push to Test Switch 10p

**VEROBOARD**

|                    |     |      |       |
|--------------------|-----|------|-------|
|                    | 0-1 | 0-15 | Plain |
| 2-5in. x 3-75in.   | 19p | 18p  | 10p   |
| 2-5in. x 5in.      | 23p | 22p  | 11p   |
| 3-75in. x 3-75in.  | 24p | 22p  | —     |
| 3-75in. x 5in.     | 26p | 26p  | 17p   |
| Spot Face Cutter   | 39p | 39p  | —     |
| Pin Insertion Tool | 50p | 50p  | —     |

**HILLS DYNAMIC HEADPHONES MODEL H87VS DE LUXE**  
Extremely high quality with padded Headband & Earcups & Slider Volume Controls.  
OUR PRICE £8.30 P/P 27p



**"HOMER" INTERCOM**  
2 Station Inc. Volume Control On-Off Switch. Batteries & 6ft of Cable.  
OUR PRICE £3.50



**CARTRIDGES**  
Acos  
GP91-3SC Mono Crystal £1.15  
GP93-1 Stereo Crystal £1.15  
GP90-1 Stereo Ceramic £1.65  
Sonotone 9TAC Diam. £1.00

**SPEAKERS**  
6 x 4 Std. Magnet 8Ω £1.10  
7 x 4 Std. Magnet 3Ω £1.10  
6 x 3 Std. Magnet 8Ω & 3Ω £1.20

**ALUMINIUM BOXES**  
HB1 5 1/2" x 2 1/2" x 1 1/2" 42p  
HB2 4" x 4" x 1 1/2" 41p  
HB3 4" x 2 1/2" x 1 1/2" 41p  
HB4 5 1/2" x 4" x 1 1/2" 47p  
HB5 4" x 2 1/2" x 2" 41p  
HB6 3" x 2" x 1 1/2" 34p  
HB7 7" x 5" x 1 1/2" 66p  
HB8 8" x 6" x 3" 84p  
HB9 6" x 4" x 2" 54p

**CASSETTE TAPE RECORDER DYNAMIC MICROPHONE**  
with Remote Control On-Off Switch.  
OUR PRICE £1.40

**TELEPHONE PICKUP COIL** for Amplifiers or Tape Recorders.  
OUR PRICE 35p  
VISIT OUR TRADE COUNTER  
ALL CALLERS WELCOME  
MON.-SAT. 9 a.m. till 6.30 p.m.

**HILLS COMPONENTS LTD.**

DEPT. (PW3) UNIT NO. 6, MELNITE INDUSTRIAL ESTATE, BRIXTON ROAD, WATFORD, HERTS. WD2 5SL. Tel. Watford 27711

ALL PRICES INCLUDE V.A.T. Please add 10% for P.P. Min. Order £1.00

# KEEP WARM AT A COOL PRICE.

## Slash central heating costs with AMKIT.

If you can put in electric wiring, you can install Amkit. The unique nylon pipe hot water central heating system, that you install yourself in hours.

Look at these advantages:

- No soldering
- No 'T' junctions
- No special equipment
- No leaks, no lagging, no corrosion
- No structural upheaval

Just reliable, effective central heating (Guaranteed 25 years) at a saving of between £150 & £250. This famous system has been successfully marketed since 1968.

Clip the coupon, and we'll tell you more.

To **Autocon Manufacturing Co.**

Spring House, 10, Spring Place, London, NW5, 3BH  
Please send your brochure telling me all about Amkit.

Name

Address

PW3




or see for yourself at: **THE AMKIT D.I.Y. CENTRE,** 15, Procter St., London, W.C.1. (opp Holborn Underground).  
Open Mon-Fri 9.30 am-5.30 pm. Sat 9 am-1 p.m.
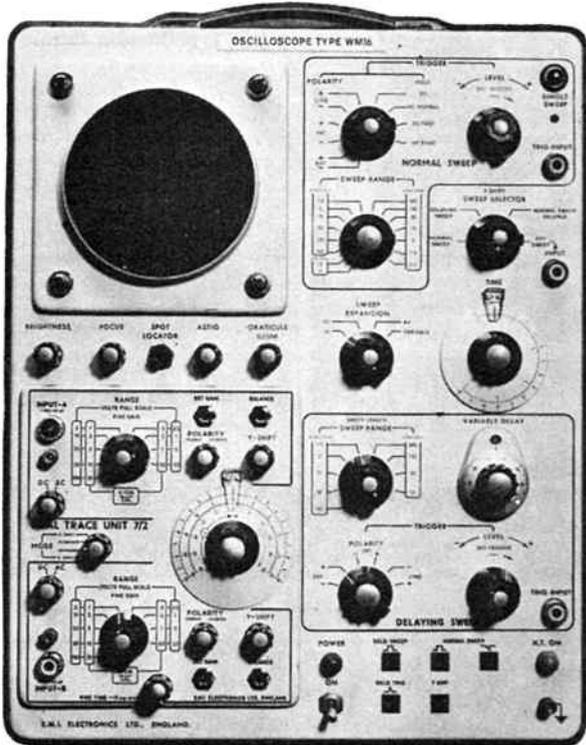
## SAMPLING TECHNIQUES

The group of scopes classed as "special purpose" can be extended to virtually any scope not corresponding to the norm, and, in a way, most scopes have a little something special since they have to appeal to buyers, just like motor cars.

Perhaps the most important special purpose scope, to be found in few amateur labs, is the sampling oscilloscope.



A close-up of the front panel of one of the author's scopes. This EMI WM16 has plug-in facilities, dual timebases and a bandwidth of better than 40MHz.

Considered on a real time basis the sampling scope has a bandwidth of a few tens of MHz. However, a special input circuit, usually contained in the probe, samples the instantaneous level of the signal at a rapid rate and the probe output when fed through the Y amplifier produces a display that builds up in a very short space of time to a continuous display.


Various manufacturers use different sampling techniques but the results obtainable represent bandwidths well into the hundreds of MHz and beyond.

A useful result of the development of sampling techniques has been the production of a circuit which when connected to an oscilloscope deflection amplifier's outputs, enables the trace on the screen, perhaps a 5MHz pulse, to be drawn by a mechanical plotter which takes about 10secs to complete one accurate scan. The technique used is similar to sampling oscilloscopes, the input to the XY plotter being sampled over say 10 seconds. The resulting XY plot is a faithful reproduction, within the plotter resolution, of the trace that was on the scope face, although not in real time as it takes 10 seconds to draw a signal of, say, 100ns width.

Other special oscilloscopes are designed to do specific jobs and there are such things as spectrum analyser scopes produced. In this scope the Y channel is narrow band, the precise band being determined by the X deflection voltage. Thus as the timebase sweeps, usually fairly slowly, the Y amplifier sweeps a certain range of frequencies, the Y deflection being proportional to the signal at that frequency. The X axis can be calibrated in frequency and such a scope can be used for investigating modulation sidebands etc.

Storage scopes also fall into the category of "special purpose" if only by virtue of the very high price. We shall consider storage tubes in the next section dealing with displays, but suffice it to say here that a special tube is employed which enables a trace to be retained after the scan is completed. These scopes are very useful for low speed servo work and in conjunction with spectrum analyser facilities, as mentioned above, flicker can be completely eliminated.

To be continued

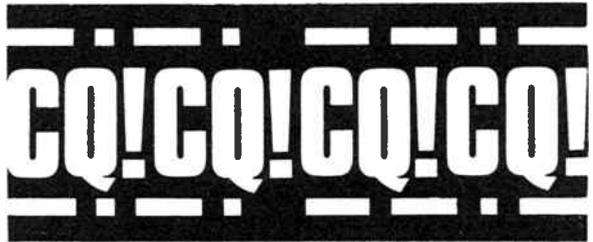

### EQUIPMENT WANTED

...Wanted urgently two octal plug and sockets, cash refund available.—Colin Machin, Pontson, Aberedu, Bullth Wells, Breconshire.  
 ...Trio 9R59DS must be in good condition with handbook and working.—C. H. Brain, 7 Elverlands Close, Ferring, Sussex BN12 5PL  
 ...Urgently required, Mazda valve, type AC/VPI; also any info. on massive, old Murphy set type A240. Info. or price required for that ancient valve to:—N. Penny, "Nanook", The Creek, Sunbury-on-Thames, Middx.  
 ...Tape head cover for Grundig Portable Battery TKE Tape Recorder and circuit diagram.—Lai Sai Kiew, 65A Union Flats, Jalan Sentul, Kuala Lumpur, Malaysia.  
 ...Codar PR40 Pre-Selector in good condition wanted.—P. Dimpleton, 37 Mountview Avenue, Dunstable, Beds.

### INFORMATION WANTED

...Technical details of, or the actual coil for the Mini Four, appearing in the March and April issues of P.W. for 1952. I have all the components except the coil type CT9 which was originally made by Stern Radio.—J. Cull, Sunnyside, 10 Ashdene Road, Southampton, Hants.  
 ...Info wanted on Rx type 103A, RF unit 24 and circuit diagram of Rx type BC-453-B a U.S. Army job.—M. Bracewell, 26 Selwyn Crescent, Hatfield, Herts.  
 ...borrow or buy circuit diagram for an Armstrong receiver Type AS105.—John King, 4 Eastbourne Road, Polegate, Sussex.  
 ...Detailed instructions required for fitting new belt to Akai 4000D tape deck.—T. Fieldhouse, 100 Wortley Heights, Leeds LS12 1JF.  
 ...Any info on BUSH EBS 4 RADIO all replies answered.—K. Eskriett, 63 Paley Road, Bradford, Yorks. BD4 7EL.  
 ...For. AP61335 Freq. Swept Generator, CT202. Handbook BR171(14) or circuit diagram. Buy loan of copy, any info welcome.—T. E. Wicks, 12 Kensington Ave, Watford, Herts. WD1 7RY.  
 ...ang gen on the U.S.N. transceiver Type CR1-4344—a unit of Model TBY-8 made by Colonial Radio Corporation, Buffalo, N.Y. Even band-coverage gen would help.—H. W. Boyett, G6GZG, 66 Freshbrook Road, Lancing, Sussex BN15 6DA.  
 ...can you please supply me with data and servicing instructions also circuit diagram for the Grundig TK120 Tape Recorder.—G. E. Simkin, 20 Wensleydale Drive, Forest Hill, Newcastle upon Tyne, NE12 0JH.  
 ...Information required regarding the R107 will buy or borrow handbook or circuit also any details of possible conversions.—D. A. Douglas, 38 Alton Road, Leicester.  
 ...Circuit and details of Windoc Model 30A Cathode Ray Oscillograph.—J. Hollis, 15 Pickering Rise, Derby DE2 4ES.  
 ...circuit diagram, manual, etc. wanted for Veritine Communication Receiver 150 buy or loan.—D. Jones, 12 Welby Place, Sheffield, S8 9DA.  
 ...Instruction manual/handbook for RCA AR88D receiver.—P. Lawler, 34 Hanover Gardens, Hainault, Ilford, Essex IG6 2RA. Tel: 01-500 5107.  
 ...any information, including circuit diagram on the American AR88 receiver.—L. Rainey, Wood Barton, Woodleigh, Kingsbridge, Devon.  
 ...circuit diagram of "Beam Echo Ltd Avantic" Audio Amplifier Type PL6-21. Loan or purchase.—P. C. Warne, 16 Western Place, Penryn, Cornwall.  
 ...handbook or information on Advance signal generator B4B.—W. H. Rees, Brendon, Carlton Road, South Godstone, Surrey RH9 6LD.  
 ...Service sheet wanted on Sobell receiver (model no.) type 615. Data on the following valves, 5Z4G, KT61, 6QT6 & 8K8G.—G. A. Hunt, 38 Garrick Close, Ings Road East, Hull, Yorkshire.  
 ...I would be grateful to anyone of your readers who can let me have the serial number of the FOUR VALVES contained in the "UNICA" UNR 30 Communications Receiver as I need to replace same, and the existing numbers on the valves are unreadable.—E. Longstaff, 6 Meadow Lane, Northallerton, Yorkshire DL5 1RE.  
 ...circuit diagram, alignment instructions or handbook for Lafayette receiver HE30 Will gladly refund postage.—P. Harston, 6 Burlington St., Bath BA1 2SA.  
 ...manual for CD711, for sale 13A1 scope working.—T. Bailey, Chaucer Lodge, Maresfield Park, Uckfield, Sussex.  
 ...Wanted, manual for R1155B. Sell or loan.—G. R. Christie, 9E Talisman Avenue, Westcliffe, Dumbaronshire, Scotland.  
 ...R.G.D. 1050C receiver, service manual or circuit. Buy or borrow.—Wilson, 39 Corporation Road, Darlington, Co. Durham.

# TAKE 20

DAVID ANDREWS

## No. 58 GRIP TESTER

A series of simple transistor projects, using not more than twenty components.

THE objective when using this piece of equipment is to hold a probe (made of aluminium foil folded round a piece of wooden broom handle) in each hand and squeeze the probes as hard as possible. The tighter the grip the more the lamps will become illuminated. But more than this; the lamps come on in a set sequence. A weak grip will make only one lamp glow faintly but a very strong grip could make all three lamps glow brightly. An intermediate grip may only illuminate two lamps. The circuit shown in Fig. 1 is designed to operate three lamps this way but can be extended to operate as many as are required if the instructions are followed.

is reached when it might be more economic to use a zener diode. For more than four indicating stages R2 ought to be reduced to 220 ohm. The sensitivity of the unit is controlled by VR1. Reducing its value lowers the sensitivity and requires a stronger grip to get the lamps to light up.

### ★ components list

|             |                                |               |
|-------------|--------------------------------|---------------|
| R1 1kΩ ±W   | R2 470Ω ±W                     | R3-5 1kΩ ±W   |
| D1-6 1N4148 | Tr1-4 BC108                    | LP1-3 6V 40mA |
| Battery 9V  | VR1 200kΩ linear potentiometer | Probes        |
|             |                                | Veroboard     |

### Circuit

Tr1 is an emitter follower and the potential at its emitter is set by the potential divider effect of R1, VR1 and the body's resistance plus contact resistance between the palms of the hands and the probes. The lower the skin and body resistance the higher will be the emitter potential. Skin contact resistance can, to some extent, be controlled by the pressure of grip on the probes and this affects the emitter potential.

This potential is used to provide base current into each of the following grounded emitter lamp drivers but the silicon diodes in series with each of the bases ensures that in the case of Tr2 the output from Tr1 must be higher than 1.2V while for Tr3 it must be 1.8V and for Tr4 should exceed 2.4V. Thus, when the grip is weak the potential from Tr1 might only be 1.6V and in this case LP1 will be the only lamp illuminated but if it is 2.2V Tr3 will be starting to conduct and LP2 will start to glow while LP1 glows even more brightly. The diodes are there simply to provide potential increments for consecutive stages and the technique of adding one extra to each stage could be continued until some point


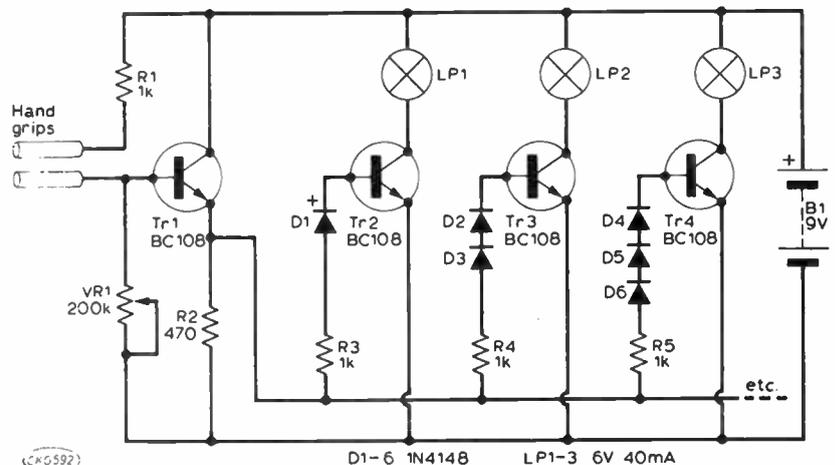


Fig. 1, above, is the circuit for a four stage tester and a suggested layout on plain veroboard is shown in Fig. 2, below.

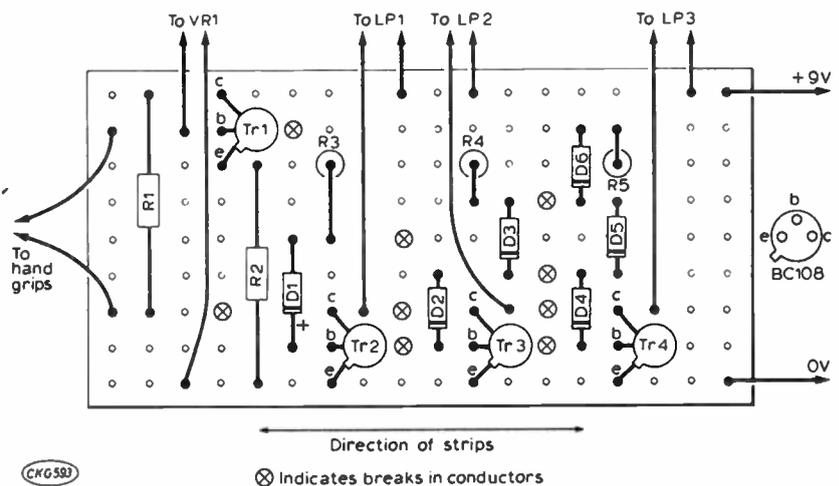



## "SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



be applied to give DC. to winding for a maximum holding torque of 300oz in with 35v at 0.35 amps through winding. For AC. (synchronous) operation at 120v., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 3/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing Offered at less than maker's price.

OUR PRICE ONLY £15

### MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/4" x 1 1/2". Pull is approximately 2lbs., plunger travel 1 1/2". Fixing eye takes up to 3/4" bolt, plunger non-captive. NEW in original maker's boxes. £1 20. P. & P. 20p. Large number available, special price for quantity.



### SMITHS RINGER-TIMER

Reliable 15 minute timer, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1 40. 15p P. & P.

### KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deal aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1/4"; (80 DB) 3/4" x 5/32" x 1/4". Equipment, all tested. £1 20 each. P. & P. FREE.


### MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "e l b o w". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1 FREE P. & P. Special quotes for quantities


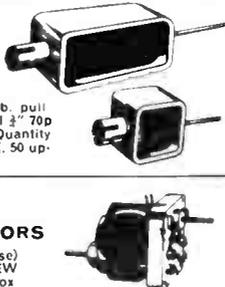
### SOLENOIDS by WESTOOL

240AC type MM6 3lb. pull, 2 1/2" x 1 1/2" x 1 1/2". Travel 1" 90p each. P. & P. 10p  
240AC type MM4 2lb. pull 1 1/2" x 1 1/2" x 1 1/2". Travel 3/4" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%



### OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm. NEW HIGH TORQUE, approx overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2 70. P. & P. 30p  
Similar to above, 19rpm. £2 70. P. & P. 30p.  
110rpm with pressed steel gear case (similar to above but slightly smaller). £2 70. P. & P. 30p.



### NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12", 24" x 12", 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.


### SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v, 1 1/2amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2 10. P. & P. 15p 50 for £8; 100 for £16 50. FREE P. & P. over 10.

### AMPEX 7.5v. D.C. MOTOR

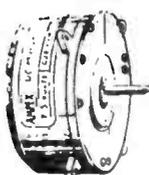

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 50ma on run, 600rpm ± speed adjustment. Internal AFRR suppression 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16 50. OUR PRICE £3 30. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available 75p each. FREE P. & P.

### ALL PRICES NOW INCLUDE V.A.T. UNLESS OTHERWISE STATED

All items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2 50 C.W.O., please. Company orders under £2 50, surcharge 60p unless C.W.O.

315/317, EDGWARE ROAD, LONDON, W2.  
Tel: 01-723 5667 01-402 5580

# ELECTRO-TECH COMPONENTS LTD.

## THE RADIO SHOP

16 Cherry Lane Bristol BS1 3NG  
Tel.: Bristol 421196. STD Code 0272

Your West Country shop for electronic components and solid state devices

Mains operated relays. B11A base 3 pole change-over 10A. 35p post paid. Bases 16p.

Multiturn Potentiometers  
Ex Equip. Relcon 1K ±1%  
Good condition 25" spindle 30p post paid.

Mains Slow Motion Motors  
1 Rev. per 6 mins. 2" dia 1 1/2" Deep 45p post paid.

Hook up Wire 1/024 PVC ins Asst colours 4x100yd Reels only £1 75 post paid.

AIRCRAFT BAND CONVERTER  
Circuit, instructions and components.  
All you need is a tobacco tin.  
Price £1 40, post paid.

### TRANSFORMER

Mains input 240, output—0 75V—5 5V—13V—1 amp. Size, height 3" x 3" x 2 1/2" shrouded + 2 fuse holders.

95p, post paid.

### 5 COMPUTER PANELS

9" x 7" min 35 trans. OC44 EQ ACY17  
2 Trim Pots min 70 condensers.  
Min 80 diodes inc. OA81 + resistors.  
Most transistors have long leads.

£1 25, post paid.

### 1973 CATALOGUE

Over 25 kits. Over 30 books. Plus components, cases, etc.

Only 10p, post paid.

ALL PRICES INCLUDE V.A.T.

## TRANSFORMERS

DOUGLAS GUARANTEED  
Prices include P. & P. and 10% VAT  
12 or 24 Volt

| Output V. & Amps. | Ref. No.  | Price |
|-------------------|-----------|-------|
| 12V x 2.250mA x 2 | MT111C8** | £1 55 |
| 12V x 2.500mA x 2 | MT213**   | £1 99 |
| 12V x 2.1A x 2    | MT710T*   | £2 45 |
| 12V x 2.2A x 2    | MT186T    | £3 08 |
| 12V x 2.3A x 2    | MT70AT    | £3 95 |
| 12V x 2.4A x 2    | MT108AT   | £4 49 |
| 12V x 2.5A x 2    | MT 72AT   | £5 28 |

| Output                                  | Ref. No. | Price | Output | Ref. No. | Price  |
|---|----------|-------|--------|----------|--------|
| 30 Volts. All tapped at 0-12-15-20-30V. |          |       |        |          |        |
| 500mA                                   | MT112AT  | £1 81 | 4A     | MT21AT   | £5 22  |
| 1A                                      | MT79AT   | £2 51 | 3A     | MT51AT   | £6 10  |
| 2A                                      | MT 3AT   | £3 77 | 8A     | MT88AT   | £9 88  |
| 3A                                      | MT20AT   | £4 31 | 10A    | MT89AT   | £11 97 |

| 50 Volts. All tapped at 0-19-25-33-40-50V | Ref. No. | Price |
|---|----------|-------|
| 500mA                                     | MT102AT  | £2 36 |
| 1A  | MT103AT  | £3 50 |
| 2A  | MT104AT  | £4 74 |

| 60 Volts. All tapped at 0-24-30-40-48-60V. | Ref. No. | Price |
|--|----------|-------|
| 500mA                                      | MT124AT  | £2 60 |
| 1A   | MT128AT  | £3 70 |
| 2A   | MT127AT  | £5 15 |
| 3A   | MT125AT  | £7 50 |

### AUTO-WOUND RANGE

| Power output | Winding tapped at | Ref. No. | Price |
|--------------|-------------------|----------|-------|
| 20VA         | 0-115-210-240     | MT1130T  | £1 48 |
| 75VA         | ...               | MT94AT   | £2 10 |
| 150VA        | 0-115-200-220-240 | MT4AT    | £3 61 |
| 200VA        | ...               | MT85AT   | £4 31 |

400V. Output at 50HZ.

C-D Ignition System by R. M. Marston, Esq., Wireless World. Reference IT3AT £4 26

### EQUIPMENT RANGE

| Sec. Output (r.m.s.) | Ref. No.     | Price     |       |
|----------------------|--------------|-----------|-------|
| 3-0-3V               | 200mA        | MT239C8** | £1 39 |
| 10-0-9               | 100mA        | MT130C8** | £1 39 |
| 12-0-12              | 50mA         | MT239C8** | £1 39 |
| 20-0-20              | 30mA         | MT211C8** | £1 39 |
| 0-20 x 2             | 300mA x 2    | MT144T**  | £2 13 |
| 0-8-9 x 2            | 500mA x 2    | MT207T**  | £2 53 |
| 0-15-20 x 2          | 500mA x 2    | MT205AT** | £3 39 |
| 0-15-27 x 2          | 500mA x 2    | MT203AT*  | £3 78 |
| 0-15-27 x 2          | 1A x 2       | MT204AT*  | £3 78 |
| 20-12-0-12-20        | 700mA (d.c.) | MT221AT*  | £1 98 |

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; \* with interlocking screws; \* untapped 240 primary; † tapped at 210-240V; ‡ other primaries tapped at 200-220-240V.  
OVER 200 TYPES IN STOCK through Agents or Direct. Please enquire for lists.

DOUGLAS ELECTRONIC INDUSTRIES LTD.  
Direct Sales Dept. F.W., Thames Street, LOUGH, Lincs.  
LN11 7AD

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, H.M.S., etc.

1974 "DX" RECEIVER  
Complete kit—Price £4 30 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume." "I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits & components. Test Report available. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1



## BROADCAST BANDS

### SHORT WAVE DX

by MALCOLM CONNAH

THE receivers used by Broadcast Bands listeners vary enormously; they may be ex-government sets or brand-new commercial units; but all receivers have one thing in common: They will not give their best performance until they are used with a good aerial system.

When we talk of an aerial system we include any devices, such as aerial tuning units, which are placed between the aerial and the receiver.

In order to get optimum reception the aerial system must be resonant at the frequency of reception. Amateur Bands listeners, and operators, have an advantage here because their bands, with the exception of 15 metres, are closely related. These bands are 10, 20, 40, 80 and 160 metres. If an aerial system is resonant on 80 metres it is a relatively simple matter to get it to resonate on 40, 20 and 10 metres.

The Broadcast Bands, however, are completely unrelated being 11, 13, 16, 19, 25, 31, 41, 49, 60, 75, 90 and 120 metres. If one of these bands is of particular interest a half-wave dipole may be erected for that band. The only practical solution for all band reception is to use some form of end-fed aerial. It should be noted that the term 'long-wire' is often used incorrectly, a misuse of which I have been guilty, as this is strictly an end-fed aerial which is long in relation to the wavelength being received.

The length of aerial that can be erected depends on the amount of space available, but the usual compromise is between 50 and 100 feet long. Theory dictates that the aerial should be straight, but many people have had very good results with aerials that have been bent in order to fit them into the space available.

The aerial should, preferably, be an outdoor one erected at a reasonable height and located as far away as possible from such obstructions as buildings and trees. A very simple aerial tuning unit (such as that described by David Gibson in the January 1974 issue) should then be constructed in order to make the aerial system resonant on the desired bands.

### Readers' Logs

David Kernick of Prescot, Lancashire used his Grundig TR600A portable with only just the built-in telescopic antenna to hear the following.

- 6070 R. Sofia, Bulgaria at 1930.
- 7145 R. Kiev in English at 0030.
- 7215 All India Radio in English at 2000.
- 9550 R. Finland noted at 1805.
- 9670 Adventist World Radio at 0930.
- 9695 V. of Saudi Arabia, Arabic at 0405.
- 9745 R. Baghdad, Iraq noted at 1945.
- 9770 R. Australia, English at 1605.
- 9833 R. Budapest, Hungary at 1615.
- 11920 R. Algiers noted at 1900.
- 11970 R. Tunis in Arabic at 0920.
- 15140 R. Havana, Cuba in French at 1935.
- 15165 R. Denmark in Danish at 1850.
- 15240 R. Belgrade, Yugoslavia at 1530.
- 15410 United Nations Radio at 1600.
- 17755 HCJB, Quito, Ecuador at 1930.
- 17780 RSA, South Africa noted at 1600.
- 17845 WYFR noted in English at 1730.
- 17865 WINB, Red Lion, music at 1930.
- 21630 V. of Saudi Arabia, testing at 1110.

Richard Staples has found an Eddystone 680X in the loft (excuse me whilst I return my ladder to garage) and the addition of a 100 foot end-fed aerial produced:

- 3999 R. Godthab, Greenland in Danish at 0840.
- 4820 Voz Evangelica, Honduras at 1805.
- 4940 R. Yaracuy, Venezuela, Spanish at 1740.
- 5920 R. Kiev, news in English at 1800.
- 9590 R. Australia noted in English.
- 9610 R. Canada in English at 2115.
- 11720 R. Nacional, Brazil, Portuguese at 0705.
- 11935 R. Pakistan, news in English at 1715.
- 15200 RSA, South Africa in English at 0840.
- 21695 Greek Military Radio, Athens at 0905.

Christopher Hodgson of Sunderland reports that Radio WYFR (Family Radio Inc.) broadcasts in English to Europe at 1810 GMT on 15130kHz. The station replied to his report in about two weeks and the address for reports is: WYFR, 290 Hegenberger Road, Oakland, California 94621, U.S.A.

With his usual equipment; Codar Multiband 6, P.W. A.T.U. and 50 foot end-fed; Christopher also heard:

- 7080 Voice of Vietnam, Hanoi at 1820.
- 7210 Red Cross Broadcasting at 1700.
- 9505 VOA, Tangier, in Rumanian at 1930.
- 9525 All India Radio at 2010.
- 9540 Radio Tashkent noted at 1210.
- 9545 Radio Ghana, s/off at 2215.
- 11805 WYFR—Family Radio at 2100.
- 15130 WYFR—Family Radio at 1810.
- 15175 RSA, South Africa, s/off at 1850.
- 15185 R. Finland noted at 1830.
- 15290 ORTF, Paris, s/off at 1115.
- 15415 Radio Kuwait, s/on at 1730.
- 15420 BBC, East Med. relay noted at 1600.
- 17820 R. Canada, s/on in Polish at 1530.



## BROADCAST BANDS

VHF/FM

by SIMON DAVID

**H**OGMANAY was celebrated in Scotland in a different way than usual. No doubt the timing was deliberate for Radio Clyde, Scotland's first commercial radio station, broadcast on 95.1MHz on December 31st. The station started at 10.30 p.m. with news and introductions to the staff. The 4kW transmitter is at Black Hill.

The criticisms and doubts surrounding London Broadcasting, the London news stations, resulted in the resignations recently of the Managing Director and Chief Editor. Former Lord Mayor of London, Sir Charles Trinder, also walked out issuing an ad-

mission that the finances had not lived up to expectations. One thing evident is the difference between some commercial and BBC local radio broadcasts from a technical standpoint and although both have severe financial restrictions, it is only to be expected that the latter has the advantage of drawing on the resources of its "great-auntie".

I have been informed that BBC Radio Derby is still operating on 96.5MHz from Sutton Coldfield using slant polarisation. The 94.2MHz transmitter that I mentioned recently is installed at the studio to fill-in the town centre area because of surrounding high ground. It uses a vertically polarised aerial and 10 watt transmitter.

The Radio Derby aerial at Sutton Coldfield is a 5-element Yagi array 500 feet above ground level. It provides a maximum e.r.p. of 5kW in the Derby direction.

Also from Derby, Roy Patrick reports that the Lichfield IBA transmitter for the Birmingham area is due on the air on 94.8MHz in February; the Manchester commercial station is due on 97.0MHz (2kW) in March; the Swansea station is expected to start transmitting on 95.1MHz (1kW), using the circular type of aerial, later on in the summer of 1974.

Last month I reported on the results of using the Antiference FM264T six-element aerial. Results since then have been repeated with the addition of Rouen on 96.6MHz. Unfortunately conditions have not favoured reception from Rheims.

## MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

**D**AVE KERNICK (Prescot, Lancs) has a Grundig TR600A transistor portable with a built-in ferrite rod antenna, which he has found to be an excellent receiver for pulling-in distant stations. He reports hearing programmes in English from AFN Frankfurt 872kHz; Deutschlandfunk, West Germany 1268kHz at 1745hrs; Radio Norway 1578kHz at midnight; Radio Sweden 1178kHz at 2245hrs; Radio Tirana, Albania 1457kHz (additional frequency for the English Service) at 0330hrs; together with Sud Radio, Andorra in French at 2245hrs on 818kHz and Tripoli, Libya in Arabic at 0025hrs on 1250kHz. Dave asks if it is possible to hear North America on the medium waves using a portable receiver. This is unlikely as a ferrite rod aerial does not have enough pick-up to receive really distant stations. DXers who want to try for North Americans should use an external aerial or a medium wave loop such as the DXers MW Loop Aerial described in the April 1973 issue of *Practical Wireless*.

### Readers' Logs

Roy Patrick (Derby) reports hearing the new Independent Broadcasting Authority (IBA) station at Manchester testing on 1151kHz at 1100hrs on December 1st and IBA Birmingham using test tones on the same channel. IBA stations in the provinces are expected to use 1151kHz for stations at Manchester, Birmingham and Glasgow (R. Clyde); 1169kHz for Swansea and 1546kHz for Liverpool and Edinburgh.

R. B. Callwood (Munich, West Germany) reports hearing BBC Radio 1 (1214kHz) at 1300hrs on his

car radio while driving on the autobahn between Munich and Frankfurt. Reception was on a single occasion only and he wonders if any other reader has received BBC Radio 1 in Germany.

Bill Thorne (London) asks for information about the French broadcasts on 584kHz (513m) which he listens to regularly. The station on this frequency produces programmes for the Paris area for the greater part of the day and has a power of only 5kW. The address is O.R.T.F., 116 Avenue du President Kennedy, Paris 16eme France.

Brian Murray has heard IBA Radio Clyde testing on 1151kHz at 1345hrs and he reports that this station is due on the air on December 31st, 1973. Brian has been busy again with his Astrad VEF 204 receiver using an old band 1 TV aerial as a medium wave antenna. His log includes programmes in English from Radio Warsaw 1502kHz at 0115hrs; Radio Sweden 1178kHz at 0025hrs; Manx Radio, Isle of Man 1295kHz at 1350hrs; Radio Eireann 1250kHz at 2120hrs; Trans World Radio, Montecarlo 1466 kHz at 2325hrs and Radio Portugal 755kHz at 2312hrs.

A last-minute phone call from T. McCann (Belfast) reports reception of Newfoundland on 930kHz (CJON in St. John's) with the comment "I was surprised at the strength of this station." Propagation on the North American path is rather variable with periods of a week or more when nothing can be heard. At other times, many stations in Canada and the United States can be heard, the limiting factor being interference from Europeans. During the winter listen around midnight on 600kHz, 640kHz, 710kHz, 930kHz, 940kHz, 950kHz, 1070kHz, 1130kHz. North Americans are easy to identify as all stations are allocated call-signs which are used frequently together with the name of the town or city where the studios are located.

**ALL OUR PRICES INCLUDE V.A.T.**

**BSR LATEST SUPERSLIM**

**STEREO AND MONO**  
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AO 200/260V.  
Size 15 1/2" x 11 1/2".  
Below motor board 8 1/2".  
With STEREO and MONO XTAL PORTABLE PLAYER CABINET £4.50



£6.25 Post 25p.

Modern design. Black resin covered. Silver front grille. Chrome fittings. Motor board cut for BSR deck.

**COMPACT PORTABLE STEREO HI-FI**

Two full size loudspeakers 1 1/2" x 10" x 8 1/2". Player unit clips to loudspeakers making it extremely compact. Overall size only 18 1/2" x 10" x 8 1/2". 3 watts per channel, plays



Attractive Teak finish Weight 18lbs. Bargain Price £25 85p carriage

**SPECIAL OFFER**  
**SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES**  
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob turn on or off at full or intermediate settings. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated.  
OUR PRICE £1.65 or 28 pair



Driver Trans. LEDT4. 65p Printed Circuit. POA1. 65p J.B. Tuning Gang. 40p Weyrad Booklet. 10p Spare Cores. 8p OPT1. 65p Ferrite Rod 3 x 1/4in. 80p 6 x 1/4in. 20p-3 x 1/4in. 10p

**WEYRAD P50—TRANSISTOR COILS**  
RASW Ferrite Aerial. 85p Osc. P50/LA0. 40p I.F. P50/2C0 470 kc/s. 40p S.R.F. P50/3C0. 40p Spare Cores. 8p Ferrite Rod 3 x 1/4in. 80p 6 x 1/4in. 20p-3 x 1/4in. 10p

**VOLUME CONTROLS**  
5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K.R.P. Transistor 25p

80 Ohm Coax 4p. yd. BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40; 60 yd. 25p. FINE LOW LOSS Ideal 635 & colour 10p yd.

**8in & 10in ELAC HI-FI SPEAKER**

Dual cone plasticised roll surround. Large ceramic magnet. 50-14,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 8in. 10 watt. 10in. 12 watt music power.



£3.75 Each Post 25p

**E.M.I. 13 1/2 x 8in. SPEAKER SALE!**

With twin tweeters and crossover, 10 watt. State 8 or 8 or 15 ohm. (As illustrated) Post 25p



£2.75 Post 25p

With flared tweeter cone and ceramic magnet, 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 8 or 8 or 15 ohm. Post 25p

**BOOKSHELF CABINET**  
Size 18 x 10 x 9 1/2 in. teak finish £5.50 Post 25p

**SET OF 8 MOTORS FOR COLLARO STUDIO, 116 VOLT TAPE DECK £2.50 Post 50p.**

**BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides 6 x 4in. 65p; 8 x 6in. 55p; 10 x 7in. 65p; 12 x 8in. 85p; 14 x 9in. 80p; 16 x 10in. 90p; 18 x 10in. 50p; 16 x 10in. 51p; 18 x 10in. 51p; 14 x 8in. 18p; 10 x 7in. 10p; 12 x 8in. 20p; 14 x 9in. 25p; 16 x 6in. 28p; 14 x 9in. 84p; 12 x 12in. 40p; 16 x 10in. 50p PAKOLIN PANEL 10 x 8in. 15p.**

**SPECIAL OFFER**

3 inch panel metre 50 micro amps, unusual scale requires recalibrating Post 25p. £1.75

**RADIO COMPONENT SPECIALISTS**

Minimum post 20p. Illustrated Colour Brochure, Radio Books & Components Lists 10p.

**ANOTHER RCS BARGAIN!**

**4 Transistor Mono Amplifier**

Powerful 8 watt output. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. £5.95 Post 25p  
Size 6in. wide x 4in. deep x 8in. high. 85p  
Suitable 7" x 4" speaker, £1.

**R.C.S. STABILISED POWER PACK KITS**  
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. output voltages available 6 or 9 or 12 or 15 or 18 or 20V a.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2.20 Post 80p  
Details S.A.E. Size 8 1/2 x 1 1/2 x 1 1/2 in.

**R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE**

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-18V. or H.T. line 200-300V. A.C. operation. Size 1 1/2" x 4 1/2" x 1 1/2". Response 25 c/s to 25 Kc/s. 95 dB gain. For use with valve or transistor equipment. 99p Post Full instructions supplied. Details S.A.E. 20p

**E.M.I. WOOFER AND TWEETER KIT**

Woofer 10 1/2" x 6 1/2in. Ceramic Magnet, 440s. 13,000 lines. Tweeter 8 1/2in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms. Power 12 watts. £5.75 Post 25p.

**BRITISH FM/VHF TUNING HEART**

88 to 108 M/C/S British made. 2 Transistors ready aligned requires 10-7 M/C/S I.F. Complete with tuning gang. Connections supplied but some technical experience essential. Our price £3.95 Post 20p

**MAINS TRANSFORMERS**

All post 25p each  
Eagle MT12 12-0-12V 50mA. 90p  
250-0-250 80 mA 6.3V 5A 6.3V 1A or 5V 2A. 43.50  
350-0-350 80 mA 6.3V 3-6A. 6.3V 1A or 5V 2A. 43.00  
300-0-300 120mA. 6.3V 4A C.T. 6.3V 2A. 43.25  
MINIATURE 200V 20mA. 6.3V 1A 2 1/2" x 2 1/2" x 1 1/2" 75p  
MIDGET 220V 45mA. 18. 20. 24. 30. 36. 40. 48. 60 82.80  
HEATER TRANS. 6.3V 2A 2 1/2" x 2 1/2" x 1 1/2" 75p  
GENERAL PURPOSE LOW VOLTAGE. Trapped output at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V 25 20  
1 amp. 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 22.25  
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 22.25  
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 22.80  
3 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 22.75  
5, 8 and 12V 5 amp 12.0. 5 amp. 3, 5, 8, 10, 12, 15 and 5-0V 11-30. DITTO 5 amp. 11-50; 6-0-6V 500mA 20p  
9V 1 amp 95p 12V 800mA 75p 12V 500mA 55p 12V 750mA 85p. 40V 1 amp 11.75.  
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 160V 43.25; 500V 46.25; 750V 51.00; 1000V 11.5  
CHARGER TRANSFORMERS. Input 200/240V. for 6 or 12V. 1 1/2 amp 11.50; 3 amp 11.80; 4 amp 22.50  
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp 22; 4 amp 24; 5 amp 24.50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

**MAINS ISOLATING TRANSFORMER**

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE £10 Carr. 50p  
Famous make. (Value 13)  
Can be used as 800V auto transformers 240-110V.  
IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

**NEW ELECTROLYTIC CONDENSERS**

2/350V . 14p 100/25V . 10p 33+33/350V . 40p  
4/350V . 14p 250/25V . 14p 50+50/350V . 50p  
8/450V . 18p 500/25V . 20p 60+100/350V . 85p  
16/450V 22p 1000/25V . 35p 22+22/350V . 20p  
33/450V 35p 1000/50V . 47p 33+33/450V . 60p  
33/600V 50p 3+3/450V . 25p 280+50/282V . 55p  
25/25V . 10p 8+16/450V . 25p 100+50+50/350V 55p  
50/50V . 10p 16+16/450V 40p

**LOW VOLTAGE ELECTROLYTICS**

1, 2, 4, 5, 8, 15, 25, 30, 50, 100, 2000pF. 15V. 10p.  
500mF. 12V. 15p; 25V. 20p; 50V. 30p.  
1000mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p.  
2000mF. 6V. 25p; 25V. 45p; 50V. 57p.  
2500mF. 50V. 65p; 3000mF. 25V. 47p; 60V. 65p.  
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 85p.

CERAMIC 1pF to 0.1mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 850V-0.1 4p. 0-5 15p; 1mF 15p; 2mF 150V 15p. 500V-0.01 to 0.15 4p. 0.1 5p; 0.25 5p; 0.47 25p. SILVER MICA. Close tolerance 1%: 2-2-500pF 5p; 250-2,200 pF 10p; 2,700-5,600pF 20p; 6,800pF-0.01, 0.01 80p; each. TWIN GANG. "0-0" 208pF+176pF. 65p. mtd 80p; standard 75p; 385+385 with 25+25pF 30w motion drive 50p. SHORT WAVE. SINGLE. 10pF 20p; 25pF 55p; 50pF 65p. NEON PANEL INDICATORS. 250V AC/DC Amber 30p. RESISTOR. 1W 25p; 1/2W 25p; 1/4W 5p; 10 1/2 to 10M. HIGH STABILITY. 1W 25p; 10 ohms to 5 meg. 10p. DITTO 5% Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each; 0.5 ohm to 3-ohms 10p. TAPE OSCILLATOR COIL. Valve Type 35p.

**NEW MODEL "BAKER LOUDSPEAKER" 12in. 50 watt GROUP 50/18 8 or 15 ohm high power full range. Professional quality. £17.60**

**BAKER MAJOR 12" £9.90**



80-14,500 c/s. Post free  
12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 30 watts. NOTE: 3 or 8 or 15 ohms must be stated.  
Module kit, 80-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50  
Post free  
Please state 3 or 8 or 15 ohms.

**BAKER "BIG-SOUND" SPEAKERS Post free**

'Group 25' 12 inch 15 ohm £8.80  
'Group 35' 12 inch 15 ohm £9.90  
'Group 50' 15 inch 50 watt 8 or 15 ohm £22

**TEAK VENEERED HI-FI SPEAKER CABINETS**  
For 12in. or 10in. dia. speaker 20 x 18 x 9in. 29-90 Post 25p  
For 12 x 6in. or 8in. speaker 18 x 10 x 9in. 25-50 Post 25p  
For 8 x 6in. speaker 18 x 8 x 6in. 24-40 Post 25p  
For 6in. and tweeter 18 x 8 x 6in. 24-40 Post 25p  
LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

**GOODMANS 6 1/2in. HI-FI WOOFER**

8 ohm, 10 watt. Large ceramic magnet. Special Cambrio cone surround. Frequency response 30-12,000 c/s. Ideal F.A. Columns, Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2 in. Suitable Tweeter 22-00. £4



**ELAC CONE TWEETER**

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in. diam. deep. Rating 10 watt, 8 ohm Suitable Crossover 21-80 £1.90 Post 20p

**SPEAKER COVERING MATERIALS. Samples Large S.A.E.**

Horn Tweeters 2-16ko/1s, 10W 8 ohm or 15 ohm £1.95  
De Luxe Horn Tweeters 2-18 Ko/1s, 15W, 15 ohm 23-50  
CROSSOVERS TWO-WAY 5000cps 3 or 8 or 15 ohm 21-80  
LOUDSPEAKERS 5 OHMS. 7 x 4in. 21-25; 6in. 21-20. 3 x 6in. 21-30. 4in. 21-25. 10 x 6in. 21-30. 10 x 8in. 21-30. SPECIAL OFFER: 80 ohm 8 1/2in. 21in. 25 ohm 8in. 21in. 25 ohm 8 1/2in. dia. 6" x 4" £1 EACH  
5 ohm, 3 1/2in. dia.; 6 x 4in.; 7 x 4in.; 8 x 4in. TYPE 8 ohm, 2 1/2in. 8 1/2in.; 3 1/2in.; 5in. dia. (6 x 4in. 8 ohm 21-60)  
RICHAUD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. diameter 4 watt 22-50. 10in. diameter 5 watt 22-60; 12in. diameter, 6 watt 22-95  
VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50c 40p. 5 WATT MULTI-RATIO. 8, 3 and 15 ohms. 80p. Mike trans. mu metal 100:1 21.25.

**MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER**

All purpose transistorized. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8 1/2 ohm a.c. Mains. Separate treble and bass controls. SUPER VALUE MODEL 100 WATT CALLERS ONLY 68p. £49 Carr. 11.00



**BARGAIN AM TUNER. Medium Wave. £4.95**

Transistor Superhet. Ferrite aerial. 9 volt.

**BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. £3.95**

Add musical highlights and sound effects to recordings. Will mix Microphones, records, tape and tuner 12V with separate controls into single output. 9 volt.

**TWO CHANNEL STEREO VERSION £5.95**

**BARGAIN 3 WATT AMPLIFIER. 4 Transistor £4.50**

Fush-Full Ready built, with volume, treble and bass controls 18V. DC operation.

**COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 13p**

COAXIAL OUTLET BOXES surface, 85p. BALANCED TWIN FEEDER 800 ohms 5p yard. JACK SOCKET Std. open-circuit 14p. closed-circuit 28p. Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 29p; 3-5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 15p; 5-pin 25p. DIN PLUGS 3-pin 15p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 10p; CAN5 5p.

**REVERSIBLE 4 POLE MOTOR £1.95**

1,400 r.p.m. Reversible 42 Watt Post 25p spindle 1 1/2" x 7/32", size 3 1/2" x 3". As Illustrated. With Cooling Fan 240V A.C.

**E.M.I. GRAM MOTOR £1.00**

120v. or 240v. A.C. 2,400 rpm. 2-pole Post 25p. 70mA. Size 2 1/2 x 2 1/2 x 1 1/2 in.

337 WHITEHORSE ROAD, CROYDON  
Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)  
Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

# Ambit International

We are not just another component retailer—but a complete semiconductor service. We can either supply or tell you where to get any 'hard to find' I.C.'s, and can now provide data on most devices you can think of. See our latest catalogue issue for full information.

15p—no S.A.E. required

For those of you who already have an AMBIT catalogue, send us an A5 S.A.E. plus 10p, stating the number on the last page in your catalogue—and we will send you all the latest update releases (to page 25).

**AMBIT—the linear microcircuit specialists—for Phase Locked Loops**

NE561B AM/FM coil-less radio receiver or IF strip £3-19

NE562B Similar to the 561, but without AM facility. The VCO output is separately available for synthesizer applications £3-15

NE565 High stability-low frequency telemetry demodulator and NBFM demodulator £2-55

567 A P.L.L. for tone, NBFM and AM decoding (5-9V) working £2-75

555 Versatile timing IC, use as 'one-shot' of multi-vibrator £0-78

LS8038 A unique triangle/square/sine wave function generator with 1MHz complete signal generator in a chip. A data sheet is included with each device on request £2-70

for Audio

LM380N Simple, safe and versatile 2W RMS at 12V: 4W RMS at 18V £1-30

Stereo Stereo AMP P.C.B. for 2 x LM380N £80-80

**SPECIAL OFFER**

5 LM380 for £5-50

for Radio

(see last month's advertisement for our radio IC features)

TBA651 1µV sensitivity AM/FM/SSB with RF mixer and IF low external parts count £1-82

TBA120 FM IF strip and detector £1-00

CA3089E FM IF system AFC-AGC-SQUELCH-TUNING-METER OUTPUT—the very best FM IC £1-95

MC1310P P.L.L. Stereo decoder IC with layout spec. £2-85

(14 DIL) FULL kit with P.C.B. £4-00

for TOKO filters at 455KHz and 10-7MHz

Ceramic CFT455B 8KHz bandwidth £0-45

CFT455C 6KHz bandwidth £0-45

CFU455C 4-8KHz bandwidth £0-50

CFS10-7 Wide band FM (2 required per set) £0-37

455KHz MFH-T 4, 5 or 7KHz versions £1-45

Mech-anical LFP2016 A stereo pilot tone notch filter (19 and 38KHz) for HiFi, recording, etc. Both channels £2-20

Plus LED displays, 28MHz decade counters, voltage regulators kits for tone coders, NI Cads—in fact everything to lead you through the microcircuit maze.

**ULTRASONIC REMOTE CONTROL PROJECT.** S.A.E. for details of kits and availability.

**PW FERRET KIT.** Electronics only £9-50

**LARSOLT VHF FM TUNERSSETS** 1µV input for 2668 Set INCLUDES SQUELCH, TUNING METER DRIVE BAND SCAN FACILITY, 4 VARICAP CONTROL £16-00

S.A.E. for specification details

**FOR ELECTRONIC SUB ASSEMBLIES** Audio SINE/SQUARE/TRIANGLE generator with sweep facility 0.01Hz-1MHz. Full kit of components and instructions £11-50

**STOP PRESS . . .** Mk. II Ferret: Phase Locked Loop IC metal detector (BFO type) Features: \*Audible/meter/LED indication of presence of metal \*Varicap control of search oscillator \*Phase locked harmonic selection \*FET reference and search oscillator for extra stability \*Speaker output

Electronics only kit—P.C.B.—components—Instructions £14-50

PLUS box, meter, LED, Speaker £18-00

Positively the most technological BFO metal detector at the price! Ready built and tested—guaranteed 12 months £37-50

PLEASE NOTE ALL PRICES NOW EXCLUDE VAT

37A HIGH STREET, BRENTWOOD, ESSEX CM14 4RH Tel: (0277) 216029

Terms: C.W.O. All prices EXCLUDE VAT. Handling charge of 10p per order. FIRST CLASS POSTAGE on all items under 80z.

# RECHARGEABLE

## Mallory Cells in U2, U11 and Penlite U7 sizes, KESTREL BATTERY CHARGING UNIT . . .



Use for

**Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.**

Whenever you *must* have utterly dependable battery power—then these new **Alkaline-Manganese** rechargeable cells will provide it. The cells can be recharged many times, a simple job with the **Kestrel Charging Unit** which has been specially designed for these new type batteries.

**PRICES** Batteries U2 equiv. £1-52 tax paid

Penlite U equiv. 6tp tax paid

U11 equiv. £1-24 tax paid

Charging unit £8-72 tax paid with one battery holder

ALL PRICES INCLUDE V.A.T.



Send to:

275 WEST END LANE LONDON, N.W.6 1QS 01-794 9611

## 4-STATION INTERCOM



£10.95

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 56ft. and other accessories. P. & P. 47p.

**MAINS INTERCOM NEW MODEL** No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £19-95 per pair P. & P. 60p.

## INTERCOM/BABY ALARM



OUR PRICE ONLY £5.95

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire and Battery. P. & P. 35p.



£4.95

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.12) 169 KENSINGTON HIGH STREET, LONDON, W.8.

## HONEYWELL PROGRAMMER

This is a drum type timing device. The drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 change-over micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor a mains operated 5 revs. per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £8-33 plus 25p post and insurance. Don't miss this terrific bargain!



## 12 VOLT 1 1/2 AMP. POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2-20 plus 20p post & packing. Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 260W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—slippery inter-change push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £2-33 plus 25p post.

## 15A ELECTRICAL PROGRAMMER



Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do

with our electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2-15 + 20p p. & p. with glass front, chrome bezel, 83p extra.

## CASSETTE RECORDER AND TUNER AMPLIFIER

As featured this issue! Our 1974 catalogue lists hundreds of bargains and probably many of the parts needed for this project. 66p brings the catalogue and the next 6 monthly supplements.

## DRILL CONTROL NEW IKW MODEL



Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-95. Made up model also available. £2-95

## THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2-95 plus 20p post and insurance. Industrial model 5A £3-30. (Not on plate).



## MINIATURE SEALED RELAY

American made. Our Ref. No. REL A1. Measures only 1/2" wide x 1/2" thick and 1 1/2" high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 28p including base.



## MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 28p each.

TERMS: 10% discount if ten of an item ordered—send postage where quoted—other items, post free if order for these items is £6-00 otherwise add 20p.

ADD 10% VAT

## J. BULL (ELECTRAL) LTD.

(Dept. PW), 7 Park St., Croydon CRO 1YD Callers to: 102/3 Tamworth Rd., CROYDON



## AMATEUR BANDS

### SHORT WAVES

by DAVID GIBSON, G3JDG

**A** thank you to the many sharp-eared r.f. sleuths who sent in logs. Everyone seems to have bagged far more DX than I did—well done.

**John Powell** (Essex) sends in some useful information regarding "who's where and when". John says look out for VQ9HCS on Astove Island (look it up; I had to!). New Ham on Campbell Island is ZL4NJ/A.

A listening MUST. Havering Amateur Radio Club are running a station in Rutland from Saturday, March 30 to Monday April 1 1974. Listen on topband, eighty and v.h.f. Why? Because after that date there will be no County of Rutland, its being absorbed into the surrounding counties so this is your very last chance. Full marks for initiative to the Havering A.R.C.

**Michael Watson** (Kent) tells that a station in Teheran, EP2BQ, has put up an inverted V for topband. Listen for the EP2 callsign in the bottom 5kHz of 160 metres. Who will hear him first?

Several people have written taking me to task for omitting the list of Happenings in the radio world. It appears that we have a number of keen Contest types among us. The calendar for February is as follows: 9-10, 1.8MHz contest; 16-17, ARRL Contest (c.w.); 23-24, REF contest (phone); March 3-4, 144MHz Open and s.w.l. contest; March 3-4, ARRL DX contest (phone). National Field Day this year will be on June 1-2.

**Robert Beebe** (Derby) reports hoards of G stations on topband. He tells that members of the Derby club have worked some juicy DX around 1830kHz and quotes calls like W1, KV4, DJ and OK etc.

Vice Chairman (wonder what sort of vice?) **David Andrews** writes to tell of the Droitwich High School Radio Club. Ten members so far and all going in for the R.A.E. The Club has both Rx and Tx but no antenna up as yet. (How about a base-loaded Maths Master—a sure sine of success).

**Keith Rowlings** (Herts) has a UR1A, PR40, 75ft. long wire—and a problem. He's heard N20 and L50 on 7MHz and wants to know where they are (and so do I). Anyone any information on these or are they Japanese postal districts?

**Graham Nicholls** (Oxon) has a homebrew 70cm converter feeding a homebrew 144MHz converter which feeds an R107 (not homebrew). His 15 element 70cm Parabeam rests in his bedroom, but it still heard the following; F1CTH, G3BA, G3COJ, G3DAH, G3YXN, G3KEQ, G3UHT, G3WSN, G3ZFP, G3ZMD, G3YC, G4ABF, G4AHU, G4BEL, G4BMP, G6XM, G8ADC, G8FMK, GW8AWS/P, HW6BQH/P, HW7FY, ON5FF, ON5HN. On two metres with a homebrew 6—ele Yagi (also in the bedroom) Graham logged; GW8HEZ, HW1CS, HW5SY, PA0ADY, PA0CIO, PA0EZR/A, PA0FHV, PA0PEP, PA0PRY, PA0TAR, SM7DT.

Ye fantastic logge has been sent in by **Stanley Sharred**. I note that it's on IBM paper—it's cheating if you get the computer to listen and log. No gear is mentioned (bet it's a regenerative cats whisker feeding a 100 Watt light bulb) but the following are claimed for 160 metres; GM3ANO, GM4ALK, GM4ASY, GW3UCB, DK3BJ, EI8H, K2ANR, K3RUQ, KV4FZ, OE5KE, OK1AXD, OK1FCW, OK1KRS, OK1KPU, OK2BKT, OK5KWA, OL6AQJ, OL8CCS, PA0HIP, VE1CD, VE1MX, VE1ASJ, VO1KE, W1DX, W1MX, W2DED, W2LWI, W2UEZ, WA2WLN/2, WA8IJI, WB8APM. On 3-5MHz, Stanley excelled with; CT1ADV, CT2BG, EL7D, K2BT, VE1AIH, VO1FG, 7X2MD, 9Y4HR. An excursion to 7MHz revealed DX like; C3IMO, CR4BS, CR6TP, EP2TW, K4DX, PY4MA, PY6WF, PY6AOV, SV1CH, TY1ABE, YV1BI, 5U7BB, 9G1HE.

Eighty metres found **Martin Ward** listening with a JR500S and 60ft. end fed plus an "L-match device" (Oh L). Squeaks of s.s.b. reported from; CT1GC, LX1GC, KG4CB, VE1AIH, VO1FG, 9H1CE, 9J2AE, and a late arrival—CN8CG. Martin reports hearing the Panama City Radio Club on 21MHz with the callsign 3E1KC.

**Stephen Day** (Suffolk) made an "adjustment" to his R1155 and claims the signals went up by some 20dB. (You can come and make the same adjustment to my receiver—anytime). Antenna is 50ft. end fed and main interest is eighty metres. Stephen bagged mostly G stations but managed foreign signals from; ZK5AFZ and 9H4L.

**John Turner** says, "I have been giving the Pye Cambridge a rest". What a thoughtful lad. This compassion for a trusty friend has not prevented John from listening with his homebrew t.r.f. (P.W. November 1963). The bandsread is the small tuning capacitor from the 235MHz section of an Ex 19 set. The t.r.f. 85ft. end fed and lots of patience produced; CT2BK, EA6CK, EA8IH, EL7C, HB0LL, H13XCP, HK3AVK, HR1RSP, HZ1SH, JY4GN, JY6UMS, K4PWC/AM, KP4BBW, PY2ELV, PY4LW, PZ1DR, TF5TP, TG8KT, VE1AF, VE3AI/SU, VK2AHM, VK2LW, VK2SG, VK3AD, VK3AX, VK3XJ, VK5FH, VK6SB, VS9MJ, VU2GBG, YV4AGT, ZB2CS, ZB2DL, ZD7SD, ZD7SS, ZM3FO, 3A2CP, 4Z4MQ, 5B4F, 7X2MD. Think what could have been received if Stephen Day (above) had made an "adjustment"!

#### BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

Medium Waves Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

#### AMATEUR BANDS

##### Short Wave/VHF

Logs in alphabetical order please by 15th of the month to David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.



**INCORPORATING LASKYS RADIO  
AND G. W. SMITH & CO. (RAIOI).**

**AUDIOTRONIC Model ATM1**

Top value 10,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0-1mA/100mA. Resistance 0/150k ohms. Decibels -10 to +22dB. Size 90x60x28mm. Complete with test leads.



**OUR PRICE £2.95** P&P 15p

**AUDIOTRONIC Model ATM5**

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0-315/150/300/1200V AC, (2500 opv), 0-6/30/200/600V DC, (5000 opv), 0-300 uA/0-300mA DC. Resistance: x 10 & x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm



**OUR PRICE £3.50** P&P 15p

**MODEL TE200**

20,000opv. Mirror scale, overload protection, 0/5/25/125/1000V DC. 0/10/50/250/1000V AC, 0/50uA/0.5/5mA DC. Resistance 300 ohms/250mA, 0/6/6k Ohm.



**OUR PRICE £4.95** P&P 15p

**MODEL UA437 MULTIMETER**

10,000opv. A first class instrument manufactured in USSR to the highest standards. Ranges: 2.5/10/50/250/500/1000V DC. 2.5/10/50/250/500/1000V AC. DC current 100uA/1/10/100mA/1A. Resistance 300 ohms/3/30/300k/3 Meg. ohms. Complete with batteries, test leads, instructions and a sturdy steel carrying case.



**OUR PRICE £4.95** P&P 25p

**MODEL TH12**

20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/50uA/25/250mA DC. 0/3k/30k/300k/3 Meg. ohms. -20 to +50dB.



**OUR PRICE £5.95** P&P 15p

**HIKI Model 720X VOM**

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50uA. 0-20k/2 Megohms.



**OUR PRICE £5.97** P&P 20p

**TMK MODEL TW50K**

46 ranges, mirror scale. 50kV/DC. 50kV/AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts: 1.5/3/15/25/50/125/250/500/1000. DC current 26/50uA/2.5/5/15/50/250/500mA/10A. Resistance 10k/100k/1 Meg/10 Meg ohms. -10 to +81.5dB.



**OUR PRICE £8.50** P&P 17p

**ALL PRICES EXCLUDE VAT**

**UA4323 MULTIMETER**

20,000opv. Simple unit with audio/1Hz oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance 5/50/500 ohms/5/10/100k ohms/1Meg. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



**OUR PRICE £7.00** P&P 20p

**MODEL TE300**

30,000opv. Mirror scale. Overload protection. 0/0.6/3/15/80/300/1200V DC. 0/5/20/120/600/1200V AC. 0/30uA/1.2mA/6/60mA/300mA/600mA. 0/8k/80k/800k Ohm. -20 to +63dB.



**OUR PRICE £7.50** P&P 15p

**UA4324 MULTIMETER**

High sensitivity, overload protected. Ranges: 0.5/1.2/3/12/30/60/120/600/1200V DC. 0.5/1.5/5/15/50/100/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



**OUR PRICE £8.00** P&P 20p

**UA35 MULTIMETER**

20,000opv. Overload protected. Ranges: 75mV/2.5/10/50/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2.5A DC. 0.5/2.5A AC. Resistance: 0.5/3/30/300k Ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.



**OUR PRICE £8.75** P&P 20p

**UA312 MULTIMETER**

extremely sturdy instrument for general electrical use. 687opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/6A/60mA/1/1.5/6A DC. 0/1.5/6/15/60/150/600mA/1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



**OUR PRICE £9.75** P&P 25p

**U91 Clamp VOLT AMMETER**

For measuring AC voltage and current without breaking circuit. Ranges 300/800V AC. Current: 10/25/100mA. Accuracy 4%. Size 263 x 94 x 36mm. Complete with carrying case, leads and instructions.



**OUR PRICE £10.50** P&P 20p

**MODEL C7080EN**

Giant 6" mirror scale. 20,000 opv. 0/0.25/1.25/10/50/250/1000V DC. 0/2.5/10/50/250/1000/5000V AC. 0/50uA/1/10/100/500/5000mA/10A DC. 0/2k/200k/20 Meg. -20 to +50dB.



**OUR PRICE £13.95** P&P 35p

**MODEL 500**

30,000opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA. 12A DC. 0/60k/6 meg/60 megohms.



**OUR PRICE £10.95** Carr. paid Leather case for above £1.75

**KAMODEN 360 MULTIMETER**

High sensitivity. DC 100kohm/V. AC 10kohm/V. 5" mirror scale, overload protected. Ranges: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/10/100M ohms. Decibels -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc.



**OUR PRICE £13.95** P&P 25p

**HIKI Model 700X**

100,000opv. Overload protection. Mirror scale 0.3/0.6/1.2/1.5/3/8/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/60/150/300/600/12A DC. 2k/20k/2M/20M Ohms -20 to +63dB.



**OUR PRICE £14.95** P&P 20p

**KAMODEN HM720B FET VOM**

Input impedance 10 Megohms. Ranges: 0/0.25/1.2/5/10/50/100V DC. 0/2.5/10/50/250/1000V AC. 0.5/2.5/25/250mA DC. 0/5k/50k/500k/5M 50 Megohms



**OUR PRICE £14.95** P&P 30p

**TMK MODEL 117 FET ELECTRONIC VOLT METER**

Battery operated. 1 Meg input. 26 ranges. Large 4 1/2" mirror scale. Size: 149 x 117 x 60mm. 0/0.3/1.5/3/30/60/150/300V AC. 6-800V DC. DC current 0.12-12mA. Resistance up to 2000M Ohms. Decibels: -20 to +51dB. Supplied complete with leads and instructions.



**OUR PRICE £17.50** P&P 20p

**KAMODEN 72200 Multitester**


High sensitivity tester. 200,000 opv Overload protected Mirror scale. Ranges: -0/0.6/3/30/120/600/1200V DC. 0/3/12/60/1200V AC. 0/6uA/1.2mA/120mA/600mA/12A DC. 0/1k/1A AC. -20 to +63dB. 0/2k/200k/2 Meg/200 Megohms



**OUR PRICE £16.95** P&P 30p

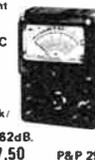**370WTR MULTIMETER**

Features AC current ranges. 20 000opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500V AC. 0/50uA/1/10/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.



**OUR PRICE £17.50** P&P 25p

**UA317 MULTIMETER**

High sensitivity instrument for field and laboratory work. Knife edge pointer, 86mm. mirror scale. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. 0.25/0.5/1/5/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.



**OUR PRICE £15.00** P&P 20p

**TE40 HIGH SENSITIVITY AC VOLT METER**

10 Meg input. 10 ranges: 0.001/0.03/0.1/0.3/1/3/10/30/100/300V RMS. Seps -12MHz. -40 to +50dB supplied brand new complete with leads and instructions.



**OUR PRICE £17.50** P&P 25p

**TE85 VALVE VOLTMETER**

28 ranges. DC volts 1.5-1500V. AC volts 1.5-1500V. Resistance up to 1000 Megohms. 200/240V AC operation. Complete with leads and instructions.



**OUR PRICE £17.50** P&P 30p

**TMK LAB TESTER**

100,000opv. 6V scale. buzzer short circuit check Sensitivity 100,000 opv DC. 5kV AC DC Volts: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC. current 10/100uA/10/100/500mA/2.5/10A. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. DC: 0.5/5/50V AC. Plastic case with carrying handle. Size: 190 x 172 x 99mm.



**OUR PRICE £19.95** P&P 25p

**MODEL UA311 Sub-standard Multi-range Volt-Ammeter**

Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750uA/1.5/3/7.5/15/30/75/150/300V AC. 0/30/75/150/300V DC. 0/3/7.5/15/30/75/150/300V AC. 0/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300V AC. 0/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300V AC. 0/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300V AC. 0/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300V AC.



**OUR PRICE £49.00** P&P 50p

**LB3 TRANSISTOR TESTER**

Tests ICO and B. PNP/NPN. Operates from 9V battery. Complete with all instructions etc.



**OUR PRICE £3.95** P&P 20p

**LB4 TRANSISTOR TESTER**

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.



**OUR PRICE £4.50** P&P 20p

**U4341 MULTIMETER**

TRANSISTOR TEST 27 ranges. 18,700opv. Overload protected. Ranges: 0.3/1.5/8/30/60/150/300/900V DC. 1.5/3/15/30/150/300/750V AC. Current: 0.06/0.6/8/80/800mA DC. 0.3/3/30/300mA AC. Resistance: 0.06/0.6/2/6/20/60/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.



**OUR PRICE £10.50** P&P 20p

**KAMODEN HM350 TRANSISTOR TESTER**

High quality instrument to test reverse leak current and DC current. Amplification section of PNP, PNP, diodes, transistors, SCR's etc. 4" square clear scale. Operates from internal batteries. Complete with instructions, leads carrying handle.



**OUR PRICE £12.50** P&P 30p

**S100TR MULTIMETER-TRANSISTOR TESTER**

100,000opv. Mirror 10 ranges: 0.001/0.03/0.1/0.3/1/3/10/30/100/300V RMS. Seps -12MHz. -40 to +50dB supplied brand new complete with leads and instructions.



**OUR PRICE £14.95** P&P 25p

**Model 449A In Circuit TRANSISTOR TESTER**

Checks true AC. Beta in/out. Checks ICO. Checks diodes in/out. Checks SCR's etc. Beta HI LO -500 LO 2-50. ICO 0-5000A. 220/240V AC operation.



**OUR PRICE £17.50** P&P 25p

**KAMODEN HMG500 insulation resistance tester**

Range 0-1,000 Megohms. 500V Battery-operated. Wide range clamp meter 4" x 4". Complete with deluxe carrying case, batteries and instructions.



**OUR PRICE £19.95** P&P 30p

**TE16A TRANSISTORISED SIGNAL GENERATOR**

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.



**OUR PRICE £8.97** P&P 25p

**TE22 SINE SQUARE WAVE AUDIO GENERATOR**

Sine 20cps to 20kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.



**OUR PRICE £17.50** P&P 37p

**ARF 300 AF/RF SIGNAL GENERATOR**

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/P-P RF 100kHz to 200MHz. Output 2V maximum. 220/240V AC operation. Complete with instructions and leads.



**OUR PRICE £29.95** P&P 50p



INCORPORATING LASKYS RADIO  
AND G. W. SMITH & CO. (RADIO).

Send s.a.e. for 8 page list of  
Semi-Conductors & Valves

**NEW SINCLAIR PROJECT 80  
HI-FI MODULES & PACKAGES**

- Z40 Power Amplifier..... £5.45
  - Z60 Power Amplifier..... £6.95
  - Stereo 80 Pre-Amplifier..... £11.95
  - Active Filter Unit..... £6.95
  - Project 80S..... £26.95
  - P25 Power Supply..... £4.98
  - P26 Power Supply..... £7.98
  - P28 Power Supply..... £26.90
  - 2 x Z40/Stereo 80/P26..... £27.75
  - 2 x Z60/Stereo 80/P28..... £30.45
  - Transfer for P28..... £4.05
- POST & PACKING 35p each

# SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.  
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

**ATZ01 Decade ATTENUATOR**  
Frequency range 0-200kHz. Attenuator 0-111dB, 0.1dB steps. Impedance 600 ohms. Input power maximum 30dBm. Size: 180 x 90 x 56mm.  
**OUR PRICE £12.50** P&P 37p



**BELCO Sine Square Wave CR OSCILLATOR**  
Sine 18 to 200,000Hz Square 18 x 127 x 50mm Hz. Maximum output +10dB (10k ohms) Operates from internal batteries. Attractive two tone case. Size: 196 x 127 x 50mm  
**OUR PRICE £17.50** P&P 17p



**SWR METER Model SWR3**  
Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedance 52 $\Omega$  Indicator 100uA DC. Low scale 5 section collapsible antenna. Size 145 x 50 x 60mm.  
**OUR PRICE £4.25** P&P 25p



**MOEL TE15 GRIODIP METER**  
Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz-280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.  
**OUR PRICE £15.00** P&P 20p



**BV05 Vernier TUNING DIAL**  
App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm deep including knob and coupling. 3/8" diam. shaft  
**OUR PRICE £1.62** P&P 15p



**VAMABISHI VARIABLE VOLTAGE TRANSFORMERS**  
Excellent quality at low cost. All models—Input 230V 50/60Hz. Variable output 0-260V  
**MODEL S260 GENERAL PURPOSE BENCH MOUNTING**

| P&P  |              |
|------|--------------|
| 1A   | £8.75 30p    |
| 2.5A | £10.00 35p   |
| 5A   | £14.70 37p   |
| 8A   | £25.50 50p   |
| 10A  | £28.10 75p   |
| 12A  | £29.50 100p  |
| 20A  | £72.50 125p  |
| 25A  | £72.50 130p  |
| 40A  | £103.10 150p |

**MODEL S260B**

|      |            |
|------|------------|
| 2.5A | £8.75 30p  |
| 1A   | £10.00 35p |



**POWER RHEOSTATS**  
High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 3/8" diameter shafts. Bulk quantities available.

| P&P 10p   |       |
|---|-------|
| 25 WATT 10/25/50/100/250/500/1000 Ohms.           | £1.15 |
| P&P 10p   |       |
| 50 WATT 10/25/50/100/250/500/1000/2500/5000 Ohms. | £1.62 |
| P&P 15p   |       |
| 100 WATT 15/10/25/50/100/250/500/1000/2500 Ohms.  | £2.34 |



**RUH6 Reflex Horn Speaker**  
Built-in driver unit. Impedance 16 ohms. Power rating 10W. Response 380-7000Hz. Size app. 6" x 6". Weather and shock protected.  
**OUR PRICE £4.97** P&P 30p



**CLEAR PLASTIC MODEL S0640**  
Size: 85 x 64mm

|             |       |          |       |
|-------------|-------|----------|-------|
| 50uA        | £3.35 |          |       |
| 100uA       | £3.30 |          |       |
| 200uA       | £3.30 |          |       |
| 500uA       | £3.25 |          |       |
| 50-0-50uA   | £3.35 |          |       |
| 100-0-100uA | £3.30 |          |       |
| 1mA         | £3.20 |          |       |
| 5mA         | £3.20 |          |       |
| 10mA        | £3.20 |          |       |
| 50mA        | £3.20 |          |       |
| 100mA       | £3.20 | 20V DC   | £3.20 |
| 500mA       | £3.20 | 50V DC   | £3.20 |
| 1A DC       | £3.20 | 300V DC  | £3.20 |
| 5A DC       | £3.20 | 15V AC   | £3.30 |
| 10A DC      | £3.20 | 300V AC  | £3.30 |
| 5V DC       | £3.20 | VU Meter | £3.45 |



**CLEAR PLASTIC MODEL SW100**  
Size: 100 x 80mm

|             |       |          |       |
|-------------|-------|----------|-------|
| 50uA        | £4.55 |          |       |
| 100uA       | £4.35 |          |       |
| 500uA       | £4.10 |          |       |
| 50-0-50uA   | £4.35 |          |       |
| 100-0-100uA | £4.30 |          |       |
| 1mA         | £3.95 |          |       |
| 1A DC       | £3.95 |          |       |
| 5A DC       | £3.95 |          |       |
| 20V DC      | £3.95 |          |       |
| 50V DC      | £3.95 |          |       |
| 300V DC     | £3.95 | 300V AC  | £4.00 |
|             |       | VU Meter | £4.75 |



**EOGWISE MODEL PE70**  
Size: 90 x 34mm

|             |       |  |  |
|-------------|-------|--|--|
| 50uA        | £4.15 |  |  |
| 100uA       | £3.95 |  |  |
| 200uA       | £3.75 |  |  |
| 500uA       | £3.50 |  |  |
| 50-0-50uA   | £3.95 |  |  |
| 100-0-100uA | £3.85 |  |  |
| 1mA         | £3.50 |  |  |
| 300V AC     | £3.50 |  |  |
| VU Meter    | £4.25 |  |  |



**MOEL EO107 EDUCATIONAL METER**  
Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

|           |       |             |       |
|-----------|-------|-------------|-------|
| 50uA      | £7.60 |             |       |
| 100uA     | £7.05 |             |       |
| 50-0-50uA | £7.05 |             |       |
| 1A DC     | £6.55 |             |       |
| 5A DC     | £6.55 |             |       |
| 5V DC     | £6.55 |             |       |
| 10V DC    | £6.55 | 300V DC     | £6.55 |
| 15V DC    | £6.55 | 500mA/5A DC | £7.10 |
| 20V DC    | £6.55 | 5V/15V DC   | £7.70 |
| 50V DC    | £6.55 | 5V/15V DC   | £7.70 |



**CLEAR PLASTIC MODEL 85P**  
Size: 120 x 110mm

|             |       |             |       |
|-------------|-------|-------------|-------|
| 50uA        | £4.85 |             |       |
| 100uA       | £4.70 |             |       |
| 200uA       | £4.45 |             |       |
| 500uA       | £4.30 |             |       |
| 50-0-50uA   | £4.40 |             |       |
| 100-0-100uA | £4.45 |             |       |
| 500-0-500uA | £4.30 |             |       |
| 1mA         | £4.30 |             |       |
| 1-0-1mA     | £4.30 |             |       |
| 5mA         | £4.30 |             |       |
| 10mA        | £4.30 |             |       |
| 50mA        | £4.30 |             |       |
| 100mA       | £4.30 | 300V DC     | £4.30 |
| 500mA       | £4.30 | 15V AC      | £4.35 |
| 1A DC       | £4.30 | 300V AC     | £4.35 |
| 5A DC       | £4.30 | S Meter 1mA | £4.30 |
| 15A DC      | £4.30 | VU Meter    | £5.00 |
| 30A DC      | £4.35 | 1A AC       | £4.30 |
| 10V DC      | £4.30 | 5A AC       | £4.30 |
| 20V DC      | £4.30 | 10A AC      | £4.30 |
| 50V DC      | £4.30 | 20A AC      | £4.30 |
| 150V DC     | £4.30 | 30A AC      | £4.30 |



**\*Items with asterisk are Moving Iron type, all others are Moving Coil**

**CLEAR PLASTIC MODEL S0830**  
Size: 110 x 83mm

|             |       |          |       |
|-------------|-------|----------|-------|
| 50uA        | £3.75 |          |       |
| 100uA       | £3.70 |          |       |
| 200uA       | £3.65 |          |       |
| 500uA       | £3.65 |          |       |
| 50-0-50uA   | £3.75 |          |       |
| 100-0-100uA | £3.70 |          |       |
| 1mA         | £3.40 |          |       |
| 5mA         | £3.40 |          |       |
| 10mA        | £3.40 |          |       |
| 50mA        | £3.40 |          |       |
| 100mA       | £3.40 | 10V DC   | £3.40 |
| 500mA       | £3.40 | 20V DC   | £3.40 |
| 1A DC       | £3.40 | 50V DC   | £3.40 |
| 5A DC       | £3.40 | 300V DC  | £3.40 |
| 10A DC      | £3.40 | 15V AC   | £3.85 |
| 5V DC       | £3.40 | 300V AC  | £3.85 |
|             |       | VU Meter | £3.85 |




**CLEAR PLASTIC MODEL 45P**  
Size: 50 x 50mm

|            |       |             |       |
|------------|-------|-------------|-------|
| 50uA       | £3.00 |             |       |
| 100uA      | £2.85 |             |       |
| 200uA      | £2.75 |             |       |
| 500uA      | £2.70 |             |       |
| 5mA        | £2.85 |             |       |
| 10-0-100uA | £2.90 |             |       |
| 50-0-500uA | £2.65 |             |       |
| 1mA        | £2.65 |             |       |
| 5mA        | £2.65 |             |       |
| 50mA       | £2.65 |             |       |
| 100mA      | £2.65 |             |       |
| 500mA      | £2.65 | 300V AC     | £2.70 |
| 1A DC      | £2.65 | S Meter 1mA | £2.75 |
| 5A DC      | £2.65 | VU Meter    | £3.00 |
| 10V DC     | £2.65 | 1A AC       | £2.65 |
| 20V DC     | £2.65 | 5A AC       | £2.65 |
| 50V DC     | £2.65 | 10A AC      | £2.65 |
| 300V DC    | £2.65 | 20A AC      | £2.65 |
| 15V AC     | £2.70 | 30A AC      | £2.65 |



**CLEAR PLASTIC MODEL 38P**  
Size: 42 x 42mm

|             |       |             |       |
|-------------|-------|-------------|-------|
| 50uA        | £2.80 |             |       |
| 100uA       | £2.70 |             |       |
| 200uA       | £2.65 |             |       |
| 500uA       | £2.65 |             |       |
| 50-0-50uA   | £2.75 |             |       |
| 100-0-100uA | £2.65 |             |       |
| 500-0-500uA | £2.75 |             |       |
| 1mA         | £2.50 |             |       |
| 1-0-1mA     | £2.50 |             |       |
| 2mA         | £2.50 |             |       |
| 5mA         | £2.50 |             |       |
| 10mA        | £2.50 |             |       |
| 20mA        | £2.50 |             |       |
| 50mA        | £2.50 |             |       |
| 100mA       | £2.50 |             |       |
| 150mA       | £2.50 |             |       |
| 200mA       | £2.50 |             |       |
| 300mA       | £2.50 |             |       |
| 500mA       | £2.50 |             |       |
| 750mA       | £2.50 |             |       |
| 1A DC       | £2.50 |             |       |
| 10A DC      | £2.50 |             |       |
| 5A DC       | £2.50 |             |       |
| 10A DC      | £2.50 |             |       |
| 15A DC      | £2.50 |             |       |
| 20A DC      | £2.50 |             |       |
| 3V DC       | £2.50 |             |       |
| 10V DC      | £2.50 |             |       |
|             |       | 15V DC      | £2.50 |
|             |       | 50V AC      | £2.55 |
|             |       | 100V DC     | £2.50 |
|             |       | 150V DC     | £2.50 |
|             |       | 20V DC      | £2.50 |
|             |       | 300V DC     | £2.50 |
|             |       | 500V DC     | £2.50 |
|             |       | 750V DC     | £2.50 |
|             |       | 15V AC      | £2.55 |
|             |       | 50V AC      | £2.55 |
|             |       | 150V AC     | £2.55 |
|             |       | 300V AC     | £2.55 |
|             |       | 500V AC     | £2.55 |
|             |       | S Meter 1mA | £2.55 |
|             |       | VU Meter    | £2.90 |

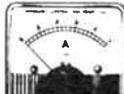

**CLEAR PLASTIC MODEL S0460**  
Size: 59 x 46mm

|             |       |          |       |
|-------------|-------|----------|-------|
| 50uA        | £3.10 |          |       |
| 100uA       | £3.05 |          |       |
| 200uA       | £3.00 |          |       |
| 500uA       | £3.00 |          |       |
| 50-0-50uA   | £3.10 |          |       |
| 100-0-100uA | £3.05 |          |       |
| 1mA         | £2.85 |          |       |
| 5mA         | £2.85 |          |       |
| 10mA        | £2.85 |          |       |
| 50mA        | £2.85 |          |       |
| 100mA       | £2.85 |          |       |
| 500mA       | £2.85 |          |       |
| 1A DC       | £2.85 |          |       |
| 5A DC       | £2.85 |          |       |
| 10A DC      | £2.85 |          |       |
| 5V DC       | £2.85 |          |       |
|             |       | 10V DC   | £2.85 |
|             |       | 50V DC   | £2.85 |
|             |       | 300V DC  | £2.85 |
|             |       | 15V AC   | £3.00 |
|             |       | 300V AC  | £3.00 |
|             |       | VU Meter | £3.20 |



POSTAGE & PACKING 15p

**240° Wide Angle 1mA METERS**  
MW 1-6 60x60mm  
**£3.97** P&P 15p  
MW 1-8 80x80mm  
**£4.97** P&P 15p



**AUTO TRANSFORMERS**  
0/15/250V. Step up or step down. Fully shrouded.

|      |       |         |       |        |
|------|-------|---------|-------|--------|
| 80W  | £2.75 | P&P 18p | 1500W | £12.50 |
| 150W | £3.50 | P&P 18p | 2250W | £20.95 |
| 300W | £4.50 | P&P 23p | 5000W | £44.95 |

- P&P 33p
- P&P 38p
- P&P 43p
- P&P 50p
- P&P £1

Also see following pages  
**ALL PRICES EXCLUDE VAT**



**INCORPORATING LASKYS RADIO  
AND G. W. SMITH & CO. (RADIO).**

**C15 PULSE OSCILLOSCOPE**

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25. HORIZ. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Triggered sweep 1-3000µsec. Free running 20-200 kHz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V AC. **OUR PRICE £39.00** Carr. paid



**T03 Portable OSCILLOSCOPE**

3" tube. Y amp sensitivity 0.1Vp-p/CM. Bandwidth: 1.5Hz-1.6MHz. Input Impedance: 2M Ohms, 25pF. X amp. sensitivity: 0.9Vp-p/CM. Bandwidth 1.5Hz-100kHz. Input impedance 2 Meg Ohms, 20pF. Time base, five ranges 10Hz to 300kHz. Synchronisation. Internal or external. Illuminated scale 140 x 215 x 330mm. Weight 15lbs. 220/240V AC. Supplied brand new with handbook. **OUR PRICE £52.50** P&P 50p



**RUSSIAN C116 Double Beam OSCILLOSCOPE**

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangle 5" x 4" CR. Calibrated triggered sweep from 0.2µsec to 100 milli-sec/cm. Free running time base, 50Hz-1MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual. **OUR PRICE £87.00** Carr. paid



**MCA220 Automatic Voltage Stabiliser**

Input 85-125V AC or 175-250 V AC. Output 120V AC or 240V AC. 200V A rating. **OUR PRICE £11.97** P&P 50p



**PS100B Regulated POWER SUPPLY UNIT**

Solid state. Output 6, 8 or 12V DC up to 2 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x 160mm. **OUR PRICE £11.97** P&P 25p



**PS200 Regulated POWER SUPPLY UNIT**

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm. **OUR PRICE £19.95** P&P 25p



**EMI LOUDSPEAKERS**

Model 350 13 x 8" with twin tweeter/crossover 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms. **OUR PRICE £7.25** each P&P 37p  
Model 450 13 x 8" with twin tweeter/crossover 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms. **OUR PRICE £3.62** each P&P 25p



Also see previous pages

**ALL PRICES EXCLUDE VAT**

**SUPER VALUE TOP QUALITY TRIO communications equipment**

**TRIO JR599 RECEIVER**



Nine wave-bands covering 1.8-29.7 MHz. 144-146MHz and 10MHz WVVV SSB, CW, AM and FM. AF output is more than 1W. 5 Meter. Squelch control. BFO. Variable AF and RF controls. 4-16 ohm output and jack for phones. Power requirement 100/240V AC. 12/14V DC. Size: 270 x 140 x 310mm. **Our Price £132.50** CARR. PAID

**TRIO 9R590S RECEIVER**



Four bands covering 550kHz to 30 MHz continuous and electrical band-spread on 10, 15, 20, 40, and 80 meters. 8 valve plus 7 diode circuit. 4 to 8 ohm output and phone jack. SSB-CW, ANL, variable BFO. 5 Meter and separate band spread dial. 1F frequency 46kHz. audio output 1W watt. Variable RF and AF gain controls. 115/250V AC, with instructions. **Our Price £42.50** CARR. PAID

**TRIO JR310 SSB RECEIVER**



Covers 3.5, 7, 14, 21, 28, 28.5 and 29.7MHz bands and WVVV 15MHz. SSB, AM and CW. AF output more than 1W. Crystal controlled BFO for SSB. 5 Meter. ANL etc. AC 110/120-220/240V. Size: 330 x 179 x 310mm. **OUR PRICE £75.00** Carr. paid

**TRIO TR220 RECEIVER**


Fully transistorised portable VHF transceiver. Will transmit and receive on six channels between 144-146MHz. 1 watt transmitter. 12V DC internal or external supply. Built-in charger for Ni-Cad cells. Power/volume switch, squelch control, channel selector, mic, socket, earphone/external speaker socket. Complete with microphone and 144.48, 144.72 & 145.32 crystals. Size: 134 x 58 x 180mm. **OUR PRICE £79.50** Carr. paid

**UNR30 RECEIVER**



Four bands covering 550 KHz/30MHz BFO. Built-in speaker. Operates from 220/240V AC. Brand new with instructions. **OUR PRICE £15.75** P&P 37p

**BELTEK W5400 CAR TRANSCEIVER**

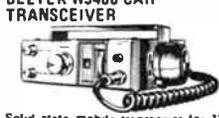

Solid state mobile transceiver for 12 volt DC neg. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: On/off/volume, squelch and channel selector. Internal 3" speaker. Complete with dynamic mic. PTT switch, three sets of crystals for 144.48, 144.6 and 145MHz, mounting bracket and instructions. Size: 150 x 70 x 220mm. **OUR PRICE £75.00** P&P 50p

**LAFAYETTE HA600 Receiver**



General coverage 150-400kHz. 550 kHz-30MHz. PET front end 2 mechanical filters, product detector. Noise limiter, variable BFO. 5 Meter. Band-spread and RF gain. 220/240V AC or 12V DC. Brand new with instructions. **OUR PRICE £50.00** P&P 50p

**SH62S STEREO HEADPHONES**

Outstanding value. With soft ear pads and adjustable headband. 86 ohms. 20-20,000Hz. Complete with lead and stereo plug. **OUR PRICE £1.87** P&P 30p

**LH02S STEREO HEADPHONES**

Light weight head phones with padded ear pieces. 4/16 ohms 20-20,000Hz. Complete with 6' lead and plug. **OUR PRICE £1.97** P&P 30p

**TE1018 Deluxe Mono High Impedance Headset.**

Sensitive magnetic headset with soft ear pads. Impedance 2,800 ohms (600 ohms OC) Frequency response: 200-4,000Hz. **OUR PRICE £2.25** P&P 30p

**DH02S STEREO HEADPHONES**

Wonderful value and excellent performance combined. Adjustable head band. Impedance 8 ohms 20-12,000Hz. Complete with 6' lead and plug. **OUR PRICE £2.25** P&P 30p

**BH001 HEADSET and Boom Microphone**

Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms. **OUR PRICE £5.95** P&P 30p

**SPECIAL BARGAIN !! STEREO SOUND SPEAKERS**

Matched pair of stereo bookshelf speakers. Deluxe task veneered finish. Size: 368 x 229 x 190mm. 8 ohms. 8 watts RMS, 16 watts peak. Complete with 0in lead. **OUR PRICE £12.95** P&P 50p

**HIGH QUALITY CONSTRUCTION KITS WE ARE APPOINTED STOCKISTS AT ALL BRANCHES**

- All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Pecking 15p per kit.
- AF20 Mono amplifier..... £4.80
  - AF30 Mono pre-amplifier..... £2.61
  - AF310 Mono amplifier..... £5.91
  - AT5 Auto light control..... £2.58
  - AT30 Photo cell switch unit..... £5.70
  - AT50 400W Light dimmer/ speed control..... £4.80
  - AT55 1,300W Light control/ speed control..... £5.70
  - AT56 2,200W Light dimmer/ speed control..... £6.90
  - AT60 1 channel light control..... £7.80
  - AT65 3 channel light control..... £14.55
  - HF61 MW transistor radio..... £3.33
  - HF65 FM Transmitter..... £2.70
  - HF75 FM transistor radio..... £2.88
  - HF310 FM tuner unit..... £18.81
  - HF325 Dux FM tuner unit..... £24.12
  - HF330 FM stereo decoder..... £9.96
  - HF395 Aerial amplifier for AM/FM bands I, II, & III..... £1.77
  - GP21 Stereo pre-amplifier..... £21.27
  - GU330 Tremolo unit..... £7.50
  - NT10 PSU 100mA/9-12V..... £6.15
  - NT300 Professional stabilised PSU 2 x 30V, 2.2A..... £12.51
  - NT305 Transistor converter 12/15V AC/DC to 6V, 7.5V or 9V DC..... £4.50
  - NT310 PSU 240V AC to 2 x 18V DC at 2A..... £4.80
  - NT315 PSU 240V AC to 4.5-15V DC at 500mA..... £8.57
  - AE1 100W output stage..... £1.65
  - AE2 Pre-amplifier..... £1.26
  - AE3 Diode receiver..... £2.00
  - AE4 Flasher..... £1.09
  - AE5 Astable multivibrator..... £1.05
  - AE6 Monostable multivibrator..... £1.02
  - AE7 RC generator..... £1.06
  - AE8 Bass filter..... 99
  - AE9 Treble filter..... 99
  - AE10 CCIR filter..... 99

**NEW FROM JOSTY-KIT 'Amateur Electronics'**  
The professional book for the amateur - covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for making ten of the kits listed above. **OUR PRICE £3.30** (No VAT) P & P 25p plus VAT

**FRUSTRATED EXPORT ORDER !!**

Philco Ford 5245 Mains Tape Recorder.  
2 track BSR deck with push button controls for easy operation. Tape counter and volume control. Complete with hand telephone, direct recording lead, 1,200' reel of tape and spare reel. 200/250V AC. Fully guaranteed. **OUR PRICE £17.50** P&P 75p


**Philco Ford 5248 Mains Tape Recorder.**

Four track, two speeds. Piano key type counter, recording level meter, volume and tone controls etc. Complete with two, microphone lead for direct recording 1,800' of tape and spare reel. 200/250V AC. Fully guaranteed. **OUR PRICE £27.50** P&P 75p

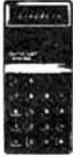**KE630 3 Station INTERCOM**

Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries. **OUR PRICE £5.25** P&P 50p

**SINCLAIR CAMBRIDGE CALCULATOR**  
To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator. **OUR PRICE £24.95** P&P free



ALSO AVAILABLE REAO BUY  
Recommended Price £29.95 **OUR PRICE £27.20** P&P 25p

Also available -  
**SINCLAIR EXECUTIVE**  
Recommended Price £39.00 **OUR PRICE £35.45** P&P 25p

**SINCLAIR EXECUTIVE with MEMORY**  
Recommended Price £49.00 **OUR PRICE £40.75** P&P 25p

**SPECIAL PURCHASE!!**

**BSR 8 Track Player Chassis**  
Famous BSR 8 track chassis as used in model TD85 complete with silver and black escutcheon, ready to fit into cabinet. Output: 125mV, 2.2V. Overall size approx. 185 x 215 x 80mm. **OUR PRICE £8.95** P&P 50p



**MP7 MIXER-PREAMPLIFIER**

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 78mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 4mV 50k; 100m Ohm Ceramic 100mV 1 Meg. Output 250mV 100k. **OUR PRICE £8.97** P&P 20p



**FM TUNER CHASSIS**

6 transistor high quality tuner. Size 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money. **OUR PRICE £5.95** P&P 20p




**A1018 FM TUNER**

Specification as above FM tuner chassis but complete in cabinet with on/off switch. Size: 184 x 86 x 127mm. **OUR PRICE £9.65** P&P 30p  
Stereo multiplex adapter £4.97



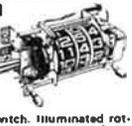**DT55B DIGITAL CLOCK MECHANISM**

Features 24 hour auto reset setting with built in alarm. On/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V, 3 Amp. **OUR PRICE £.95** P&P 30p



**BINATONE OS100 Digital Clock**

240V mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Size 156 x 76 x 82mm. **OUR PRICE £4.50** P&P 30p



**AUDIOTRONIC AH101 Stereo Headphone Amplifier**

All silicon, transistor amplifier operates from ceramic or tube inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel. **OUR PRICE £7.50** P&P 20p





**INCORPORATING LASKYS RADIO AND G. W. SMITH & CO. (RADIO).**

**AUDIOTRONIC AMR9000 Global AM/FM Portable Radio**

10 wave-bands covering AM: 535-1606kHz. LW: 150-380 kHz. MB 1.5-4MHz. SW1: 4-8MHz. SW2: 8-1.6 MHz. SW3: 16-24MHz. PSB1: 30-50 MHz. PSB2: 148-174MHz. FM: 88-108MHz. Air: 108-136MHz. Feature time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC on FM. 6" x 4" speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm. **OUR PRICE £36.00** P&P 50p



**AUDIOTRONIC LOW NOISE CASSETTES**

|      |       |       |        |
|------|-------|-------|--------|
| TYPE | 5     | 10    | 25     |
| C60  | £1.37 | £2.61 | £3.16  |
| C90  | £1.95 | £3.70 | £3.71  |
| C120 | £2.38 | £4.50 | £10.65 |

**AUDIOTRONIC CROZ CASSETTES**

|      |       |       |        |
|------|-------|-------|--------|
| TYPE | 5     | 10    | 25     |
| CR90 | £3.41 | £6.72 | £16.63 |
| CR90 | £4.63 | £9.19 | £22.80 |


**AUDIOTRONIC 8 TRACK CARTRIDGES**

|      |      |       |       |
|------|------|-------|-------|
| TYPE | Each | 5     | 10    |
| 40M  | 75p  | £3.50 | £5.50 |
| 80M  | 99p  | £4.70 | £8.90 |

P&P Cassettes 3p. Cartridges 5p each OVER 10 of either FREE.

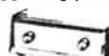**E441 REVERBERATION AMPLIFIER**

Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverb control only. Beautiful walnut cabinet, 184 x 77 x 108mm. **OUR PRICE £7.50** P&P 20p



**LINEAR 202 STEREO AMPLIFIER**



20 Watts RMS Stereo Amplifier with controls for volume, balance, bass and treble, Mono/Stereo switch, loudness and scratch filters. Uses 20 Silicon transistors. Inputs for magnetic and crystal cartridge, Aux. and tape. **OUR PRICE £22.50** P&P 50p


**SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS**

High quality 2 way speaker system. 25 Watts. 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 255mm. approx. Wood grain finish with black fronts. **OUR PRICE £29.95 PR. P&P £1**



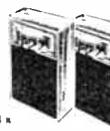**SPECIAL BARGAIN!! PHONIC 10 Two Way Speakers**

Matched pair of compact book-shelf speakers of unique design incorporating a 2" high frequency unit & 6" woofer. 8 ohms impedance. Size: 345 x 228 x 110mm. **OUR PRICE £8.85 PAIR** P&P 50p



**RECORD DECKS** P&P 50p

|                        |        |
|------------------------|--------|
| BSR McDONALD C114 Mini | £3.95  |
| C129 Mono              | £5.50  |
| C137                   | £7.00  |
| 510/TPD1               | £12.55 |
| 610                    | £11.30 |
| 610/TPD1               | £15.35 |
| 710                    | £23.10 |
| 810                    | £28.25 |
| MP60                   | £8.85  |
| MP60/ADK K8            | £10.90 |
| MP60/TPD1              | £14.15 |
| HT70/ADK K7E           | £14.25 |
| HT70/TPD1              | £16.55 |

**CONNOISSEUR**

|                       |        |
|-----------------------|--------|
| BD1 Kit               | £10.20 |
| BD1 Chassis           | £12.50 |
| BD2/SAU2/Chassis      | £25.50 |
| BD2/SAU2/Plinth/Cover | £32.25 |

|                       |        |
|-----------------------|--------|
| GARRARD 1025T Stereo  | £4.95  |
| 2025TC Less Cartridge | £6.35  |
| 2025TC/K540A          | £6.95  |
| SP25 Mk3              | £9.25  |
| SP25 Mk3/G800         | £10.95 |
| SP25 Mk4/M75-6        | £13.90 |
| SP25 Mk4              | £10.90 |

|            |        |
|------------|--------|
| 865B       | £20.00 |
| SL65B      | £11.15 |
| SL72B      | £17.75 |
| SL95B      | £28.00 |
| 401        | £28.60 |
| 400        | £31.10 |
| ZERO 100S  | £31.40 |
| ZERO 100SB | £29.20 |

**RECORD DECK PACKAGES**

|                       |         |       |
|-----------------------|---------|-------|
| BSR McDONALD 210/SC7M | P&P 75p | £7.90 |
| C129                  | £9.50   |       |
| MP60/TPD1 Console     | £17.85  |       |
| MP60/TPD1/ADK K8      | £18.97  |       |
| MP60/M44-7 Console    | £17.50  |       |
| HT70/TPD1/ADK K7E     | £19.20  |       |
| 610/TPD1/ADK K8       | £19.42  |       |

|                        |        |
|------------------------|--------|
| GARRARD 2025TC/9TA-HCD | £11.35 |
| SP25 Mk3/G800          | £17.10 |
| SP25 Mk3/M44E          | £18.25 |
| SP25 Mk3/M44-7         | £18.60 |
| SP25 Mk3/M55E          | £18.80 |
| SP25 Mk3 Module/M75-6  | £19.45 |
| AP78/G800              | £26.75 |
| AP78/G800E             | £28.95 |
| AP78/M44-7             | £27.40 |
| AP78/M44E              | £28.00 |
| AP78/M55E              | £28.60 |
| AP78/M75E              | £35.20 |
| AP78/M75EJ             | £31.20 |

|                    |        |
|--------------------|--------|
| GOLDRING GL72/G800 | £36.65 |
| GL75/G800          | £40.90 |
| GL75/G800E         | £42.35 |
| GL78/G800          | £45.65 |
| GL78/G800E         | £48.15 |
| G101/PC/G800       | £23.70 |

|                     |        |
|---------------------|--------|
| PHILIPS GA105/GP200 | £12.40 |
| GA205               | £17.40 |
| GA207               | £20.90 |
| RANK DOMUS BD2000   | £43.60 |
| BA4000              | £33.90 |
| BD6000              | £87.50 |

|                            |        |
|----------------------------|--------|
| WHARFEDALE Linton W30 Talk | £23.90 |
| Linton W30 White           | £25.10 |

**AUDIOTRONIC OOLBY B Noise Reduction Units**

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size: 460 x 203 x 79mm. AC 220/240V



**OUTSTANDING VALUE!**

**PROCESS 4**  
For use with semi-professional tape recorders. Frequency response 30Hz-20kHz. 2dB. S/N better than 70dB. Full source/tape monitoring. Switchable multiplex filter. Supplied with test tape. **OUR PRICE £50.00** P&P 50p

**PROCESS 2**  
For use with cassette and tape recorders. Frequency response 30Hz-20kHz. Switchable multiplex filter. 2 Dolby calibration meters. Off tape monitoring. S/N better than 70dB. Supplied complete with test tape or cassette. **OUR PRICE £34.50** P&P 50p

**CT5050 Cassette Recorder**



Instant recording and playing. Piano key controls. Automatic level control. Built-in speaker. Complete with remote control microphone, carrying case and shoulder strap. **OUR PRICE £8.50** P&P 50p

**AUDIOTRONIC AC0660 Stereo Cassette Deck**



A beautifully styled four track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm microphone inputs etc. etc. Frequency response: 40-12kHz (40-16kHz CrO2), S/N: -45dB. Crosstalk 45dB. Separation: -35dB. Noise limiter -5dB at 10kHz. Complete with connecting leads. **OUR PRICE £39.50** P&P 50p



**WALKIE TALKIES**

SK V F On 100mW **OUR PRICE £24.95** per pair  
P302 Two Channel 300mW **OUR PRICE £52.50** per pair  
P1003 Three Channel 1 Watt **OUR PRICE £71.25** per pair  
P&P 50p per pair  
NB. Licence required for use in UK

**1021 Stereo Listening Station**

For balancing and gain selection of loudspeakers with additional facility for stereo headroom switching. Two gain controls, speakers on/off slide switch, stereo headphone socket. **OUR PRICE £22.55** P&P 15p

**AUDIOTRONIC STEREO HEADPHONES**

LSH20 Individual volume controls. Stereo/mono switch. 8 ohms. 40-19,000Hz. **£3.75** P&P 30p

LSH30 Open back type. Individual tone and volume controls. 8 ohms. 30-20,000Hz. **OUR PRICE £5.95** P&P 30p

LSH40 Two way speaker system. Individual volume controls. 8 ohms. 20-20,000Hz. **OUR PRICE £7.50** P&P 30p

LSH60 3" speaker units. 8 ohms. Complete with tripod carrying case. 20-20,000Hz. **OUR PRICE £8.95** P&P 30p

LSH50 Electrostatic with self powered energiser, and control unit, with headphone speaker selector. 4-32 ohms. 20-24,000Hz. **OUR PRICE £16.95** P&P 30p

LQH400 4 channel dynamic head phones. Each earpiece has four drive units. 4-32 ohms. 20-20,000Hz. **OUR PRICE £9.95** P&P 30p

**CALL INTO YOUR NEAREST BRANCH OR ORDER WITH CONFIDENCE BY MAIL ORDER**

**CENTRAL LONDON**

- 10 TOTENHAM CT. RD. 01-437 2232
- 27 TOTENHAM CT. RD. 01-437 3715
- 33 TOTENHAM CT. RD. 01-436 2605
- 42/45 TOTENHAM CT. RD. 01-436 0845
- 87 TOTENHAM CT. RD. 01-580 3739
- 257/B TOTENHAM CT. RD. 01-580 0670
- 21 OLD COMPTON ST. 01-437 9369
- 3 LISLE ST. WC2 01-437 8204
- 34 LISLE ST. WC2 01-437 9155
- 118 EDGWARE RD. W2 01-723 9789
- 193 EDGWARE RD. W2 01-723 6211
- 202 EDGWARE RD. W2 01-723 3271
- 311 EDGWARE RD. W2 01-437 0387
- 346 EDGWARE RD. W2 01-723 4453
- 382 EDGWARE RD. W2 01-723 4194
- 109 FLEET ST. EC4 01-353 5812
- 152/3 FLEET ST. EC4 01-353 2833
- 378 HARROW RD. W9 01-286 9530

**ESSEX**

86 SOUTH ST. ROMFORD 70-20218

**SURREY**

1046 WHITGIFT CENTRE, CROYDON 01-681 3077  
27 EDEN ST. KINGSTON 01-546 7845  
32 HILL ST. RICHMOND 01-948 1441

**KENT**

53/57 CAMDEN RO., TUNBRIDGE WELLS 0892-23242

**LEICESTERSHIRE**

45 MARKET PLACE, LEICESTER 0533-537678

ALL BRANCHES OPEN FROM 9am to 6pm MON. TO SAT.

**HEAD OFFICE AND MAIL ORDER DEPARTMENT**

AUDIOTRONIC HOUSE, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ. TELEPHONE: 01-205 3735 & 5651

**MAIL ORDER SPECIALISTS**  
We offer a speedy and efficient service by mail order. Remember to add 10% VAT to total value of goods including carriage and packing and send cash with orders to head office. TO AVOID DELAYS PLEASE PRINT NAME AND ADDRESS CLEARLY IN CAPITALS.

**BARCLAYCARD & ACCESS**

Holders welcome call into any branch or telephone your order to head office. CREDIT TERMS available for Personal Shoppers on sales of £50 and over.

**BARGAIN CENTRE**

Many special clearance offers and end of stock lines at 87 TOTENHAM COURT RD. FOR PERSONAL SHOPPERS.

**EXPORT** Personal exports arranged for overseas visitors at all our branches. Goods dispatched to all parts of the world through our Export Mail Order Department. Immediate attention given to orders.

CHEQUES ACCEPTED FROM PERSONAL SHOPPERS ONLY WITH BANKERS CARD. ALL PRICES CORRECT AT 14.1.74 BUT SUBJECT TO CHANGE E. & O. E.



# BI-PRE-PAK

## AUDIO BARGAINS

STEREO



DECODER  
**£4.95**

Incl. P. & P. and V.A.T.

Ready built unit, ready for connection to the I.F. stages of existing FM Radio or Tuner. A tell tale light can be connected. The Unit is a small printed circuit, no further alignment necessary.


L.E.D. is recommended as the indicating light. Suitable device available from us at 38p. Instructions included.

## 3 W<sub>r.m.s.</sub> I.C. AMP


only **£1.65** Incl. P. & P. and VAT  
Order Code I.C.A. 1

on P.C. Board with all components  
or 2 on one board for £2.46

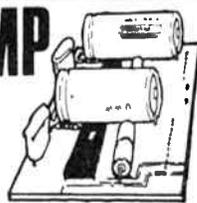Order Code I.C.A.1/S  
These amps. are supplied with a free booklet  
on connecting up, specifications and easy to  
build projects using the I.C.A.1



## 5W & 10W AMPS

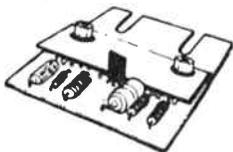

**5W ONLY £1.98**  
**10W ONLY £2.49**

incl. P. & P. and VAT

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/2" x 1 1/2". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the UK. Built and tested.

## Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit -15 edge connector.

**Stereo Pre-Amp 1 (Pre 1).** This unit is for use with low gain crystal or ceramic pick-up cartridges. **£1.21**

**Stereo Pre-Amp 2 (Pre 2).** This unit is for use with magnetic pick-up cartridges. **£1.69**

**Stereo Tone Control (STC).** This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.21**

Instruction leaflet supplied with all units. Post and packing and VAT included in prices.

I enclose £..... for..... Decoders,.....  
3W Amps/..... 5W Amps..... 10W Amps.....  
Stereo Pre-Amps 1..... Stereo Pre-Amps 2.....  
Stereo Tone Controls.....  
(Please insert quantities and delete those not applicable)  
Name.....  
Address.....

**BI-PRE-PAK**  
Co. Regn. No. 820919

Dept. D, 222/224 West Road,  
Westcliffe-on-Sea, Essex SS0 9DF  
Telephone: Southend (0702) 46344

# TRAMPUS

**MONEY BACK IF NOT SATISFIED**

All brand new, full spec. Top grade.

FREE fabulous NEW catalogue. Send S.A.E.



Red + data. 1/8" pin source LED's 17p. TTL 20p and clip 22p  
810 i" panel clip and RED LED 28p. GREEN and clip 59p.  
INFRA RED LED £1. IC photo amp 44p and amp/switch 85p.

**DIGITAL DISPLAY.** LEO 1/3" 0-9 DP. DIL. £1.69. Mintron type 0-9 DP DIL  
£1.19. SOCKETS 13p. Calculator batt/mains for £19.

**IC DIGITAL CLOCK CHIPS.** Texas etc. with 4 displays £12-6 displays  
and chip £14. Mostek data and alarm chips with 6 displays £19. pcb £1-49.  
KIT: All parts and case. National chip. 4 digit £20. 6 x £23.

GAS sensor TGS 308 £2. KIT £4-89. Fully built £2.  
With data **INTEGRATED CIRCUITS** 741: 8 pin 29p. to 99 and 14 pin 27p.  
748 33p. 709 21p. 710 35p. 723 59p. 555 timer 79p. 2N414 rx. £1-10. 703 r/l if 28p.  
mc 1310 and led £2-76. mc 1339 £1-20. TAD 100 and I £2

**1 AMP + REGULATOR** 7805, 5 (& 7-20) V. also 12 & 15V £1-49.

**AUDIO AMPS:** mfc 4000 50p; 1 and 2W £1-19; 3W £1-29.

74N TTL low prices

Gates 7400, etc. 18p. 7413 32p. 7447 £1-25. 7470/72 32p. 7474/76 39p. 7490 63p.  
7492 89p. 74121 48p and all others in cat.

**NEW 16 pin counter/driver** 90/47 £2-25. DALO p.c.b. PEN 69p.  
**DIL SOCKETS:** Professional/gold P. Pins hi or lo Profile 8, 14, 16 Pin 13p.

**2N3055 33p** four £1. **BC107, BC108, BC109** all 7p each.  
IN814 3p. ZENERS BZY88 8p. 1A RECTS 50V 34p. 400V 5p. BRIDGE 20p.  
FETs: 2N3819 19p. 2N3823E 20p. 4416E 25p. BC182/3/4 10p. BC212/3/4 11p.  
BCY70 13p. BD131/2 35p ea.. BFY51/2/3 15p. T1343 25p. 2N2926 0y 7p. 2N3053 15p.  
2N3702/3/4/5/6/7/8/9/10/11 all 9p ea. 2N3904/6 14p. HEATSINKS 51/705. 181/7018  
5p. T03: 4YL 28p. TV3 14p

**CAPACITORS:** 25V 10, 50, 100 uf 5p. DISCS 4p. PRESETS 3p. CARBON-  
PTS 11p. Switch + 11p. Dual 55p. ULTRASONIC TRANSDUCERS £2 ea.  
**FLUORESCENT LIGHTS,** 8W 13" 12 VOLT £2-99.


**Trampus**  
**electronics**

ADD 10% VAT TO PRICES.

P. & P. 10p CWO.

P.O. BOX 29, BRACKNELL, BERKS.

### CASED AMPLIFIERS

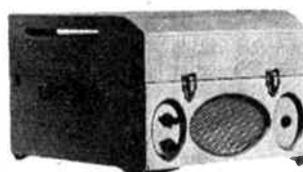

Polished wooden cabinet 14 x  
13 x 9" containing a sensitive  
(20uV) 4 valve amplifier with  
tone and vol. controls. 3 watts  
output to 7 x 4" 3 Ω speaker.  
Also included is a non-  
standard tape deck with  
solenoid operation. Supplied  
in good working condition  
complete with circuit diagram.  
Standard mains operation.  
Only £3 (£1 up to 200 miles,  
£1-25 over). Suitable cassette  
£1. Spare head 30p; Amplifier  
chassis only. complete and tested £1-65 (40p). 7 x 4" Speaker 40p (12p).

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, crystals, pots, switches,  
computer panels with transistors and loads of odds and ends. Still only £1-85  
(40p).

### COMPUTER PANELS

31b asstd. panels £1 (30p); 71b £2 (40p); 801b £13 (c. pd.). 12 top quality panels  
containing power transistors, IC's, trim pots, etc. £2 (30p); 100 boards £12 (£1).  
Pack containing at least 500 components, inc. at least 50 Transistors 60p (20p).

### NEW COMPONENTS

SCR's: 200V 5A 40p; 400V 5A 60p; BYZ10 1200V 6A 40p; OC16 20p, OC45 8p;  
OC71 8p; OC140 25p; OC170 15p; OC171 15p; BFY18 12p; BCY72 8p; 2N3055  
35p; XC121 3p; BC107 8p; 2N3708 8p; 741C T099 or 8 pin DIL 32p; 100V 8A  
diodes 20p; 3-9V or 27V 400mV zeners 7p; 22V 1W 10p.

### BULK COMPONENTS

500 asstd. resistors £1 (20p); 300 capacitors, all types £1 (30p) 25 asstd 10X  
crystals 75p (30p); 40 asstd. pots £1 (30p).

### EX-COMPUTER EQUIPMENT

1200 i" tape on 7" NAB spool 85p (30p); 1800 i" tape on 10 1/2" NAB spool in  
case 8p (40p); Screw top electrolytic capacitors: 20,000uF 50V 6p (25p);  
46,500uF 25V 6p (25p); 35,000uF 15V 40p (20p); 40,000uF 10V 40p (20p); 20,000uF  
30V 40p (20p); 25,000uF 25V 40p (20p).  
Fans: 230V 50Hz 61" dia. blades 2800 rpm complete with grill and mounting  
plate £2-50 (40p).  
Heavy duty heat sinks 6 x 5 x 3" with 2 power transistors 80p (30p).

### TEST GEAR

TF144G sig gen, 85kHz-25MHz, 1/2V-1V output £16. BFO No. 8 audio oscillator,  
50Hz-20kHz 10 Ω or 600 Ω output, m.t.ered. £9. Oscilloscope in stock, ring for  
details.

### ODD UNITS

Useful module containing OC35, 2x OC44, GET103, R's, C's, etc. 40p (10p).  
Cats whisker and crystal 15p; Unit with 2 modern c/o lever switches, 3 trim-  
pots. etc. 60p (10p).

### ADD 10% TO TOTAL FOR VAT

Carr. in brackets; small parts 5p.

**GREENWELD ELECTRONICS (PW11)**  
24 Goodhart Way, West Wickham, Kent. Shops at 21 Dapford Broadway  
SE8. Tel. 01-892 2009 and 38 Lower Addiscombe Road, Croydon.



**NO EXTRAS**  
ALL PRICES INC. VAT  
**FREE! P. & P.**

**AMPLIFIERS**

|                                   |       |
|-----------------------------------|-------|
| Keleton KSA 700 7+7 watt          | 23.00 |
| MK II KSA 1500 16+16 watt         | 32.50 |
| Tripletone MkII Hi-Fi 777 +7 watt | 27.50 |
| MK II Hi-Fi 1616 16+16 watt       | 35.00 |
| Teleton MKII 8AQ307 8+8 watt      | 27.00 |
| EMI 1515 16+16 watt               | 37.00 |
| Rotel RA210                       | 32.00 |
| RA310                             | 44.00 |
| Rotel Tuner/Amp. RX150A           | 51.00 |

**SANSUI models in stock.**

|                        |       |
|------------------------|-------|
| <b>RECORD DECKS</b>    |       |
| Garrard 2025TC/STAHG/G | 11.00 |
| SP25 Mk. III           | 11.00 |
| BSR MP60/8X5H          | 11.00 |
| Connoisseur BD1 Kit    | 11.00 |
| BD2 Chassis            | 29.50 |
| SAU2 Pick-up Arm       | 12.25 |
| SCU1 Cartridge         | 4.95  |

**RECORD DECK PACKAGES**

|  |       |
|--|-------|
| Garrard SP25 Mk. III/G800 C. & P.      | 19.50 |
| AP76/G800 C. & P.                      | 30.00 |
| Plinth & Cover for Garrard SP25/2025TC | 3.95  |

**SPEAKER BARGAINS**

|                                 |      |
|---------------------------------|------|
| EMI 13" x 8" 3, 8 or 16 ohm     |      |
| Plain                           | 2.85 |
| with Co-Axial Tweeter           | 2.50 |
| Twin Tweeter                    | 3.95 |
| Type 350 8 ohm, 20 watt         | 8.50 |
| 8 1/2" 8 ohm, 10 watt           | 2.65 |
| 8" 8 ohm, 10 watt               | 3.90 |
| 12" 8 ohm, 20 watt              | 5.75 |
| 8" x 5" C/Mag. 5 watt           | 1.40 |
| 8" x 5" Dualcone 8 ohm, 10 watt | 2.70 |

|   |      |
|---|------|
| FANE 7" x 4" 3 or 8 ohm   | 1.15 |
| 8" Dualcone 8 ohm   | 2.50 |
| CELESTION 8" 15 ohm   | 1.75 |
| ADABTRA 10" 8 or 15 ohm, 10 watt                                    | 2.95 |
| <b>BAKER GROUP 25</b>   |      |
| 12" 8 or 15 ohm, 25 watt  | 6.50 |
| 5" 8 ohm, 5 watt C/Mag.   | .95  |
| 3 1/2" 8 ohm or 64 ohm  | .60  |
| <b>SELECTION OF GOODMAN AND WHARFEDALE SPEAKERS ALSO AVAILABLE.</b> |      |
| <b>KIT FORM CABINETS - TEAK VENEER</b>                              |      |
| 12 x 12 x 6 with 8", 8" x 5", or 6 1/2" and 3 1/2" cutout           | 2.75 |
| 17 x 10 x 9 with 8" or 13" x 8" cutout                              | 2.95 |
| 18 x 11 x 9 with 13" x 8" cutout for EMI 350                        | 4.60 |
| <b>TWEETER &amp; CROSSOVER</b>                                      |      |
| EMI 3 1/2" 3 or 8 ohm C/Mag.  | 1.10 |
| Cone Tweeter 8 or 15 ohm, 10 watt                                   | 2.90 |
| Cone Tweeter 8 ohm, 3 watt  | 1.10 |
| Horn Tweeter 8 ohm, 20 watt   | 8.50 |
| Dome Tweeter 8 ohm, 30 watt   | 4.00 |
| Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)               | 1.10 |
| <b>CARTRIDGES</b>   |      |
| ACOS GP91/28C or GP91/38C Stereo comp.                              | 1.05 |
| GP93/1 Stereo crys.   | 1.35 |
| GP94/1 Stereo crys.   | 1.75 |
| GP95/1  | 1.35 |
| GP96/1  | 1.75 |
| GP101   | .75  |
| <b>SONOTONE</b>   |      |
| 9TACH Stereo ceramic, diam.   | 1.80 |
| 9TACH/G Slim fit, stereo ceramic, diam.                             | 1.80 |
| 19-TI Stereo crystal  | .85  |
| BSR 8CSM Stereo ceramic   | 2.25 |
| BX6H Stereo crystal   | 1.65 |
| BX6M Stereo crystal   | 1.85 |
| N5H Mono/stereo   | 1.80 |

|  |                     |
|--|---------------------|
| X6M Mono/stereo  | 1.30                |
| GOLDRRING G800   | 3.85                |
| G850   | 2.95                |
| <b>STYL For Above Cartridges</b>   |                     |
| Sapphire   | 1.30                |
| D Diamond  | .80                 |
| GOLDRRING G800 G850  | 1.85                |
| <b>MICROPHONES</b>   |                     |
| CM20 Crystal Hand  | .60                 |
| CM70 Planet atick metal, switch crystal  | 1.70                |
| DM160 Dynamic uni-dir, ball metal  | 4.00                |
| UD130 50K/600 ohm, uni-dir, ball metal   | 4.85                |
| TW208  | 5.90                |
| <b>CONDENSER MIKE 600 ohm, uni-dir.</b>  | 7.90                |
| Cassette STICK MIKE with R Control on/off switch (2.5 & 3.5 mm J/Play)         | 1.45                |
| MIKE MIXERS Mono.  | 4.10                |
| Mono/stereo de luxe  | 5.50                |
| <b>CASSETTES</b>   |                     |
| Type Low Pin. Phll. Mem. noise nacle lips orex pex                             |                     |
| C45  | 45p                 |
| C60  | 35p 40p 50p 55p 59p |
| C90  | 45p 55p 69p 75p 79p |
| C120   | 55p 75p 105p 110p   |
| Cassette Head Cleaner  | .45                 |
| BIB Stereo Test Cassette   | 1.65                |
| AMPEX Head Cleaner Demagnetiser  | 1.65                |
| <b>PLASTIC LIBRARY CASES for 5" Reels 30p. 5 1/2" Reels 25p. 7" Reels 30p.</b> |                     |
| <b>CASSETTE CASES</b>  |                     |
| TAPES Bstd. L.P. D.P.  |                     |
| 5" 55p 65p 80p   |                     |
| 5 1/2" 65p 75p 81.00   |                     |
| 7" 75p 81.00   |                     |
| <b>AKAI TAPE DECK</b>  |                     |
| 400DS Tape   | 79.50               |
| GXC40D Cassette  | 64.95               |
| CB35 + CB58  | 79.95               |

**BARCLAYCARD**  
Buy it with Access

**Credit Terms for Callers**

**BUDGET SYSTEMS**  
BUSH Stereo System with independent Volume, Bass and Treble controls on each Speaker for optimum reproduction. Using GARRARD 2025TC Auto Change Deck in deluxe teak plinth and cover.  
Today's Value £49.50.  
**OUR PRICE £27.50**  
+ £1.50 p. & p.  
12 months Guarantee by Maker.  
**THIS IS A BARGAIN NOT TO BE MISSED!**

|   |       |
|---|-------|
| <b>HEADPHONES</b>   |       |
| AMSTRAD HP85A   | 4.95  |
| ROTEL 430   | 4.90  |
| 630   | 6.90  |
| 700   | 8.95  |
| AKAI ASE 115  | 5.75  |
| ASE 20  | 7.95  |
| ASE 22  | 9.25  |
| KOBS K711 (Black or Red) K4   | 9.95  |
| K4  | 11.95 |
| <b>K6LC (with Vol. control)</b>   | 13.25 |
| K0727B  | 15.75 |
| K0747   | 19.50 |
| HVI   | 19.50 |
| PRO4AA  | 28.95 |
| PRO6LC  | 28.75 |
| ESP6  | 42.75 |
| <b>LEEBSOON ELECTROSTATIC</b>   | 19.50 |
| Mono/stereo super de luxe 8-16Ω   | 2.75  |
| Headphone Adaptor   | 2.50  |
| Curly Rx. Lead 20ft.  | 1.10  |
| <b>IN-CAR ENTERTAINMENT SECTION</b>   |       |
| Car Cassette Stereo Player and Two Speakers                                 | 20.95 |
| Car 8-track Stereo Player and Two Speakers                                  | 16.50 |
| SHIBUYA 8-track Player/Main/Car detachable with 2 separate sets of Speakers | 39.95 |
| Pair of Car Stereo Speakers   | 3.85  |
| Pair of Car Stereo Speakers (Door Mounting)                                 | 3.95  |

**NEWMART ELECTRONICS**

**MAIL ORDER DEPT.**  
(PW/3)  
**BELMONT STREET**  
**MONTON, ECCLES**  
**MANCHESTER**  
Tel. 061-789 5268

**CALLERS WELCOME AT OUR BRANCHES**

|                  |                 |
|------------------|-----------------|
| Manchester       | Liverpool       |
| 30-32 Shudehill  | 15 Whitechapel  |
| 061-832 7710     | 051-236 0738    |
| Leeds            | Sheffield       |
| 4 New Market St. | 20 Pinstone St. |
| 0532 42708       | 0742 79308      |

**TWO NEW SOLDER SIPPERS MAKE DE-SOLDERING QUICK & EASY**

**A SUPER PRESENT ANYTIME!**

**Longs**

Longs Ltd.  
Hanworth Lane  
Trading Estate  
Chertsey Surrey  
KT16 9LZ.

**Maxi-Super HT 1810 and Maxi-Mini HT 1800 Solder Sippers**

Designed for use when working or re-working P.C. Boards. Permits removal of molten solder from Multi-leg components, enabling easy extraction. The solder is 'sipped' through the nozzle, and automatically ejected when the instrument is next used. A Swiss precision instrument manufactured to a high degree of accuracy.

The anti-corrosive outside casing has a knurled finish for more positive grip, and encases plated internal parts.

The Maxi-Super has been designed with a 3.5 kg. spring action recoilless plunger, whilst the Maxi-Mini with its conveniently shaped operating button, has a 2.5 kg. spring action plunger, protected by a channel guard.

Both models have been designed with an easy-to-replace 'dupont' teflon screw-in nozzle.

**AMAZING MINI-DRILL**

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £6.35 p.p. 13p. De Luxe Professional Kit with 17 tools £9.40 p.p. 13p. Prices include V.A.T.

**FOR PRECISION MODEL WORK**

**+ 6 TOOLS**

Money ref. g'ter **MERLIN SUPPLY CO.**

Dept. PW 374 Nailsea, Bristol BS19 2LP

**INTER-LOCKING PLASTIC STORAGE DRAWERS**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D, 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

**DISCOUNT PRICES**

**SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.40 Dozen**

**DOUBLE UNITS £2.30 Dozen**

**TREBLE (3D) £2.50 for 8**

**DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.60 for 8 EXTRA LARGESIZE (6D1) £3.40 for 8, Carriage 35p Orders over £10 post free. QUANTITY DISCOUNTS! 5% in £1 for orders over £10, 7 1/2% over £20, 10% over £50. Quotations for large quantities. PLEASE ADD 10% VAT TO TOTAL REMITTANCE.**

**FLAIRLINE** (Dept. PW3), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

# YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m. 5 p.m.

PLEASE ADD 10% VAT

## RESISTORS

1W Iskra High stability carbon film—very low noise—capless construction.  
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.  
1W 2% ELECTROSIL TRS.

| Power<br>watts | Tolerance | Range        | Values<br>available | Price     |
|----------------|-----------|--------------|---------------------|-----------|
| 1              | 5%        | 4.7 Ω-2.2M Ω | E24                 | 1-99 100+ |
| 1              | 10%       | 3.3M Ω-10M Ω | E12                 | 1p 0-8p   |
| 1              | 2%        | 10 Ω-1M Ω    | E24                 | 3-5p 3p   |
| 1              | 10%       | 1 Ω-3.9 Ω    | E12                 | 1p 0-8p   |
| 1              | 5%        | 4.7 Ω-1M Ω   | E12                 | 1p 0-8p   |
| 1              | 10%       | 1 Ω-10 Ω     | E12                 | 5p 5-5p   |

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7 Ω to 1M Ω.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5k Ω to 2M Ω. log or linear (log 1/2W, lin 1/2W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 Ω and decades to 5M Ω. Horizontal or vertical P.C.  
mounting (0-1 matrix).  
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 7p each.

## TRANSISTORS

|       |     |       |     |        |      |        |     |        |     |
|-------|-----|-------|-----|--------|------|--------|-----|--------|-----|
| AC107 | 15p | AF126 | 20p | BF115  | 25p  | OC42   | 12p | 2N3707 | 12p |
| AC126 | 12p | AF139 | 32p | BF173  | 20p  | OC44   | 12p | 2N3708 | 10p |
| AC127 | 15p | AF178 | 32p | BF177  | 20p  | OC75   | 12p | 2N3709 | 11p |
| AC128 | 15p | AF180 | 40p | BF178  | 20p  | OC70   | 12p | 2N3710 | 11p |
| AC131 | 12p | AF181 | 40p | BF179  | 32p  | OC71   | 12p | 2N3711 | 11p |
| AC132 | 12p | BC107 | 12p | BF180  | 32p  | OC72   | 12p | 2N3819 | 32p |
| AC176 | 15p | BC108 | 12p | BF181  | 32p  | OC81   | 12p | 2N4062 | 12p |
| AC187 | 22p | BC109 | 12p | BF194  | 14p  | OC82D  | 12p | 2N4286 | 20p |
| AC188 | 22p | BC147 | 12p | BF195  | 14p  | 2N2646 | 60p | 2N4289 | 20p |
| AD140 | 50p | BC148 | 12p | BF197  | 15p  | 2N2904 | 20p | 40361  | 32p |
| AD149 | 45p | BC149 | 12p | BF200  | 32p  | 2N2926 | 10p | 40362  | 40p |
| AD161 | 33p | BC157 | 14p | BFY50  | 20p  | 2N3054 | 58p | 40408  | 40p |
| AD162 | 36p | BC158 | 14p | BFY51  | 20p  | 2N3055 | 60p | 40408  | 40p |
| AF114 | 20p | BC159 | 14p | BFY52  | 20p  | 2N3702 | 13p | ZTX108 | 15p |
| AF115 | 20p | BC187 | 22p | BUY105 | 225p | 2N3703 | 12p | ZTX300 | 15p |
| AF116 | 20p | BD131 | 75p | OC26   | 45p  | 2N3704 | 13p | ZTX302 | 20p |
| AF117 | 20p | BD132 | 75p | OC28   | 50p  | 2N3705 | 12p | ZTX500 | 15p |
| AF118 | 38p | BD133 | 75p | OC35   | 50p  | 2N3706 | 11p | ZXT503 | 20p |

## ZENER DIODES

400mW 5% 3.3V to 30V, 12p. | WIRE WOUND POTS. 3W, 10, 25,  
50 Ω and decades to 100k Ω, 35p.

## DIODES

| DIODES<br>RECTIFIER | 1250V | 1A | 12p | SIGNAL | 7p |
|---------------------|-------|----|-----|--------|----|
| BY127               | 1250V | 1A | 12p | OA85   | 7p |
| IN4001              | 50V   | 1A | 7p  | OA90   | 5p |
| IN4002              | 100V  | 1A | 8p  | OA91   | 5p |
| IN4004              | 50V   | 1A | 8p  | OA202  | 7p |
| IN4006              | 800V  | 1A | 10p | IN4148 | 5p |
| IN4007              | 1000V | 1A | 10p | BA114  | 8p |

## SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K log. or lin. 40p.

DUAL GANG, 10K + 10K etc. log. or lin. 60p.

KNOB FOR ABOVE, 12p.

FRONT PANEL, 65p.

18 Gauge panel 12in x 4in with slots cut for use  
with slider pots. Grey or matt black finish com-  
plete with fixings for 4 pots.

## BRUSHED ALUMINIUM PANELS

12in x 6in, 25p

12 in x 2 1/2 in, 10p

9in x 2in, 7p

## THYRISTORS

2N5060 50V 0-8A 30p

2N5064 200V 0-8A 47p

106F 50V 4A 40p

106D 400V 4A 55p

## ALUMINIUM BOXES

|      |                          |     |      |                       |      |
|------|--------------------------|-----|------|-----------------------|------|
| AB7  | 2 1/2" x 5 1/2" x 1 1/2" | 50p | AB14 | 7" x 5" x 2 1/2"      | 84p  |
| AB8  | 4" x 4" x 1 1/2"         | 50p | AB15 | 8" x 6" x 3"          | 108p |
| AB9  | 4" x 2 1/2" x 1 1/2"     | 50p | AB16 | 10" x 7" x 3"         | 122p |
| AB10 | 4" x 5 1/2" x 1 1/2"     | 50p | AB17 | 10" x 4 1/2" x 1 1/2" | 108p |
| AB11 | 4" x 2 1/2" x 2"         | 60p | AB18 | 12" x 5" x 3"         | 120p |
| AB12 | 3" x 2" x 1"             | 44p | AB19 | 12" x 8" x 3"         | 160p |

## HEATSINKS—REDPOINT

|    |     |     |           |    |            |    |
|----|-----|-----|-----------|----|------------|----|
| 2W | 24p | 45p | TO5 Clip  | 5p | TO1 Single | 5p |
| 3W | 36p | 60p | TO18 Clip | 5p | TO1 Double | 8p |

## TRANSFORMERS All have 240V primary

|        |                   |    |       |
|--------|-------------------|----|-------|
| MT30/2 | 0-12-15-20-24-30V | 2A | £2.85 |
| MT50/1 | 0-19-25-33-40-50V | 1A | £1.90 |
| MT50/1 | 0-19-25-33-40-50V | 1A | £2.55 |
| MT50/2 | 0-19-25-33-40-50V | 2A | £3.50 |
| MT60/1 | 0-24-30-40-48-60V | 1A | £2.10 |
| MT60/1 | 0-24-30-40-48-60V | 1A | £2.80 |
| MT60/2 | 0-24-30-40-48-60V | 2A | £3.80 |

## MULLARD POLYESTER CAPACITORS C204 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 21p, 0.0068μF, 0.01μF,  
0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF,  
7p, 0.33μF, 11p, 0.47μF, 13p.  
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 3p, 0.15μF,  
4p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7p, 0.68μF, 11p, 1.0μF, 13p.

## MULLARD POLYESTER CAPACITORS C200 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF,  
3p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF,  
13p, 1.5μF, 20p, 2.2μF, 24p.

## MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 0.033μF, 0.047μF, 0.068μF, 0.1μF, 3p, 0.15μF, 4p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS

(μF/v) 1/63, 1/5.63, 2/2.63, 3/3.63, 4/7.63, 6/8.40, 6/8.63, 10/25, 10/63, 15/16, 15/40,  
15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3,  
68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63,  
100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4, 10p,  
470/40, 680/6.3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16, 1500/6.3, 13p,  
470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 18p, 330/63, 680/40, 1000/25, 1500/16,  
2200/10, 3300/6.3, 4700/4, 21p.

## SOLID TANTALUM BEAD CAPACITORS

|        |     |       |     |       |      |     |
|--------|-----|-------|-----|-------|------|-----|
| 0.1μF  | 35V | 2.2μF | 35V | 22μF  | 16V  | 12p |
| 0.22μF | 35V | 4.7μF | 35V | 33μF  | 10V  |     |
| 0.47μF | 35V | 6.8μF | 25V | 47μF  | 6.3V |     |
| 1.0μF  | 35V | 10μF  | 25V | 100μF | 3V   |     |

## VEROBOARD

|                       |      |      |
|-----------------------|------|------|
| 2 x 3                 | 0.1  | 0.15 |
| 2 x 5                 | 24p  | 16p  |
| 3 x 3                 | 24p  | 24p  |
| 3 x 5                 | 27p  | 27p  |
| 17 x 2 1/2            | 75p  | 57p  |
| 17 x 3 1/2            | 100p | 78p  |
| 17 x 3 1/2 (plain)    | —    | 82p  |
| 17 x 2 1/2 (plain)    | —    | 60p  |
| 17 x 2 1/2 (plain)    | —    | 60p  |
| 2 1/2 x 3 (plain)     | —    | 12p  |
| 2 1/2 x 3 1/2 (plain) | —    | 11p  |
| Pin insertion tool    | 52p  | 52p  |
| Spot face cutter      | 42p  | 42p  |
| Pkt. 50 pins          | 20p  | 20p  |

## JACK PLUGS AND SOCKETS

|                    |     |                 |     |
|--------------------|-----|-----------------|-----|
| Standard screened  | 18p | 2.5mm insulated | 8p  |
| Standard insulated | 12p | 3.5mm insulated | 8p  |
| Stereo screened    | 35p | 3.5mm screened  | 13p |
| Standard socket    | 15p | 2.5mm socket    | 8p  |
| Stereo socket      | 18p | 3.5mm socket    | 8p  |

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 15p/metre.  
6 way screened cable, 22p/metre.

## BATTERY ELIMINATOR

9V mains power supply. Same size as PP9 battery. £1.50

## LARGE (CAN) ELECTROLYTICS

|        |     |     |        |      |       |        |     |       |
|--------|-----|-----|--------|------|-------|--------|-----|-------|
| 1600μF | 64V | 74p | 2500μF | 64V  | 80p   | 4500μF | 16V | 50p   |
| 2500μF | 40V | 74p | 2800μF | 100V | £2.60 | 4500μF | 25V | £1.68 |
| 2500μF | 50V | 58p | 3200μF | 16V  | 50p   | 5000μF | 50V | £1.10 |

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

|         |     |         |     |
|---------|-----|---------|-----|
| 0.01μF  | 10p | 0.047μF | 13p |
| 0.022μF | 12p | 0.1μF   | 13p |
|         |     | 0.22μF  | 20p |
|         |     | 0.47μF  | 22p |

## POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values, 4p each.

## SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas  
or smoke into an electrical signal. The sensor decreases its electrical resistance when  
it absorbs oxidizing or combustible gases such as hydrogen, carbon monoxide,  
methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or  
smoke. This decrease is usually large enough to be utilized without amplification.  
Full details and circuits are supplied with each detector.

Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but  
excluding case. Mains operated detector £5.20, 12 or 24V battery operated audible  
alarm £7.30. As above for PP9 battery, £6.40.

## PRINTED BOARD MARKER

97p  
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to  
dry and immerse the board in the etchant. On removal the circuit remains in high  
relief.

## METERS

1 1/2" Scale-500uA, 1mA, 10mA, 100mA £1.90

## BULGIN MAINS CONNECTORS

|              |              |     |              |                |     |
|--------------|--------------|-----|--------------|----------------|-----|
| 3 Pin 1 1/2A | Chassis Plug | 10p | 3 Pin 1 1/2A | Chassis Socket | 18p |
|              | Line Socket  | 13p |              | Line Plug      | 13p |
| 3 Pin 3A     | Chassis Plug | 10p | 3 Pin 3A     | Chassis Socket | 21p |
|              | Line Socket  | 14p |              | Line Plug      | 23p |
| 3 Pin 5A     | Chassis Plug | 16p | 2 Pin 5A     | Line Plug      | 20p |
|              | Line Socket  | 15p |              |                |     |

## THERMISTORS

|         |       |
|---------|-------|
| VA1005  | 15p   |
| VA1026  | 15p   |
| VA1033  | 15p   |
| VA10555 | 15p   |
| VA10665 | 15p   |
| VA1077  | 15p   |
| R53     | £1.35 |

## ROTARY MAINS SWITCH

D.P. 2A 32p

## LINEAR IC's

|            |                   |     |
|------------|-------------------|-----|
| 709        | 14 pin DIL        | 40p |
| 741        | 8 pin DIL         | 40p |
| 741        | 14 pin DIL        | 38p |
| 723        | 14 pin DIL        | 95p |
| 747        | 14 pin DIL        | 85p |
| 748        | 8 pin DIL         | 45p |
| DIL Socket | 14 pin and 16 pin | 16p |


## WAVECHANGE SWITCH 23p

1p 12W, 3p 4W, 2p 2W, 2p 6W.

4p 3W



# BIG Discounts

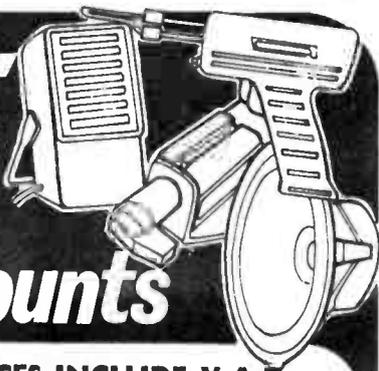

## ALL PRICES INCLUDE V.A.T.

| SPEAKER BARGAINS            |                          | £    | £    |
|-----------------------------|--------------------------|------|------|
| EMI 13" x 8" 3, 8 or 15 ohm | ELAC 8" 8ohm Dualcone    | 2-10 | 2-10 |
| Plain                       | FANE 7" x 4" 3 or 8 ohm  | 1-00 | 1-00 |
| With Co-Axial Tweeter       | 8" Dualcone 8 ohm        | 2-40 | 2-40 |
| Twin Tweeter                | CELESTION 8" 15 ohm      | 1-85 | 1-85 |
| Type 350 8 ohm, 20 watt     | ADASTRA 10" 8 or 15 ohm, | 2-75 | 2-75 |
| 8 1/2" 8 ohm, 10 watt       | 10 watt                  | 6-45 | 6-45 |
| 8" 8 ohm, 10 watt           | BAKER GROUP 25 12" 8 or  | 25   | 25   |
| 12" 8 ohm, 20 watt          | 15 ohm, 25 watt          | 85   | 85   |
| 8" x 5" C/Mag. 5 watt       | P. & P.                  | 50   | 50   |
| 8" x 5" Dualcone            | 5" 8 ohm, 5 watt C/Mag.  | 1-60 | 1-60 |
| GOODMANS 5 1/2" 8 ohm       | 2 1/2" 8 ohm or 64 ohm   |      |      |
| Dualcone                    | P. & P.                  |      |      |

| TWEETER & CROSSOVER          |                             | £    | £    |
|------------------------------|-----------------------------|------|------|
| EMI 3 1/2" 3 or 8 ohm C/Mag. | Dome Tweeter 8 ohm, 30 watt | 1-00 | 1-00 |
| Cone Tweeter 8 or 15 ohm,    | Crossovers CN23 (3 ohm),    | 1-90 | 1-90 |
| 10 watt                      | CN28 (8 ohm), CN216 (16     | 1-00 | 1-00 |
| Cone Tweeter 8 ohm, 3 watt   | ohm)                        |      |      |
| Horn Tweeter 8 ohm, 20 watt  | P. & P.                     |      |      |

| KIT FORM CABINETS TEAK VENEER    |                                  | £    | £    |
|----------------------------------|----------------------------------|------|------|
| 12 x 12 x 5 with 8" x 8" x 5" or | 18 x 11 x 9 with 13" x 8" cutout | 4-25 | 4-25 |
| 5 1/2" and 3 1/2" cut out.       | for EMI 350                      |      |      |
| 17 x 10 x 9 with 8" or 13" x 8"  | P. & P. ea.                      | -35  | -35  |
| cutout                           |                                  |      |      |

| MICROPHONES                 |                             | £    | £    |
|-----------------------------|-----------------------------|------|------|
| CM20 Crystal Hand           | TW206                       | 5-75 | 5-75 |
| CM70 Planet stick metal,    | CONDENSER MIKE 600 ohm,     | 7-90 | 7-90 |
| switch crystal              | uni-dir                     |      |      |
| DM160 Dynamic uni-dir, ball | Cassette Stick Mike with R. | 1-35 | 1-35 |
| metal                       | Control on/off switch       |      |      |
| UD130 50K/600 ohm, uni-dir  | (2.5 & 3.5mm J/Ply)         | 1-15 | 1-15 |
| ball metal                  | P. & P.                     |      |      |

| SOLDERING IRONS       |                  | £    | £    |
|-----------------------|------------------|------|------|
| ANTEX CN240 15 watt   | X25 25 watt (low | 1-60 | 1-60 |
| SK1 Kit (15 watt iron | leakage)         |      |      |
| 2 spare Bib etc.)     | P. & P.          |      |      |

| CARTRIDGES                |                            | £           | £           |
|---------------------------|----------------------------|-------------|-------------|
| ACOS GP91/2SC or GP91/3SC | 19-TI Stereo crystal       | 2-25        | 2-25        |
| Stereo comp.              | BSR SC5M Stereo ceramic    | 1-60        | 1-60        |
| GP3/1 Stereo crys...      | SX5H Stereo crystal        | 1-60        | 1-60        |
| GP4/1 Stereo crys...      | SX5M Stereo crystal        | 1-25        | 1-25        |
| GP95/1                    | X5H Mono/stereo            | 1-25        | 1-25        |
| GP95/1                    | X5M Mono/stereo            | 1-25        | 1-25        |
| GP101                     | GOLDRING G800 G850         | £3-85 £2-95 | £3-85 £2-95 |
| SONOTONE                  | STYLI for above cartridges | 1-25        | 1-25        |
| 9THAC Stereo cer. diam.   | Sapphire .35 D. Diamond    | 1-85        | 1-85        |
|                           | GOLDRING G800 G850         | 1-05        | 1-05        |
|                           | P. & P.                    |             |             |

| BATTERY ELIMINATORS          |                            | £    | £    |
|------------------------------|----------------------------|------|------|
| 240v Input 6, 7.5 or 9 300mA | lighter socket 6, 7.5 or 9 | 2-20 | 2-20 |
| 12v d.c. input (fits in car  | d.c. output at 300mA       |      |      |
|                              | P. & P.                    |      |      |

| TAPES              |  | £    | £    |
|--------------------|--|------|------|
| 5" Std. LP DP      | 7" Std. LP DP                          | 110p | 110p |
| 45p 55p 70p        | 65p 85p                                |      |      |
| 5 1/2" 55p 65p 85p | P. & P. 1-3, 8p ea. 4 or more, lot 30p |      |      |

| LOW NOISE CASSETTES |                 | £                | £   |
|---------------------|-----------------|------------------|-----|
| 1-5                 | 6-10            | 11-20            | 35p |
| C60 35p 33p 30p     | C90 45p 43p 40p | C120 55p 52p 50p |     |

| PLASTIC LIBRARY CASES |     | £                                  | £   |
|-----------------------|-----|------------------------------------|-----|
| For 5" Reels          | 18p | CASSETTE CASES                     | 10p |
| 5 1/2" Reels          | 22p | P. & P. 1-3, 8p ea. 4 or more, 20p |     |
| 7" Reels              | 25p |                                    |     |

| BIB ACCESSORIES              |       | £   | £ |
|------------------------------|-------|---|---|
| Tape Editing Kit Ref. 23     | 1-30  | <b>SPECIAL OFFER</b><br>BUSH Stereo System with<br>Indep. Vol., Bass & Treble<br>controls on each Speaker for<br>optimum reprodu. Using Gar-<br>rard 2025TC Auto Change<br>Deck in deluxe teak plinth and<br>cover. Today's Value £49.50.<br>OUR PRICE £27.50 + £1.50<br>P. & P. 12 months Guarantee<br>by Maker.<br>THIS IS A BARGAIN NOT<br>TO BE MISSED! |   |
| Recording Tapes              |       |   |   |
| Splicer Ref. 20              | 1-15  |   |   |
| Cassette Tape                |       |   |   |
| editing Ref. 24              | 1-40  |   |   |
| Cassette Salvage Kit Ref. 29 | 40p   |   |   |
| 12's Cassette Case Ref. 34   | £1-00 |   |   |
| Stylus Balance Ref. 32A      | 1-15  |   |   |
| Spirit Lever Ref. 46         | 50    |   |   |
| Hi-Fi Stereo Test Cassette   | 1-80  |   |   |
| Groove-Kleen Record Cleaner  | 1-90  |   |   |
| P. & P.                      | -10   |   |   |

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED.

## Riversdale Electronics

Mail Order Department PW3

P.O. Box 470, Manchester M60 4BU.

# Declon Polyester Speaker Fronts

\*Declon speaker front material is a fully reticulated flexible polyester foam.


\*Acoustically transparent over all audible frequencies.

DIAMOND PATTERN 3/4" Thickness Black

24" x 16" £ 2.97 each inc. VAT or Brown

36" x 18" £4.75 each inc. VAT

36" x 24" £5.61 each inc. VAT

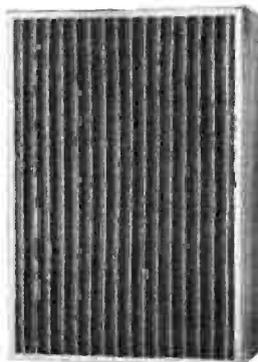

\*Attractive designs and colours.

\*Washable. \*Easily cut to size.

FLUTED PATTERN 3/4" Thickness Black

12" x 18" £1.90 each inc. VAT or Brown

24" x 16" £2.78 each inc. VAT

36" x 18" £4.56 each inc. VAT

36" x 24" £5.42 each inc. VAT


Obtainable from sole UK Distributors AMTRON U.K.

4 & 7 CASTLE ST. HASTINGS. SUSSEX

Telephone: HASTINGS 2875

# Sinclair Project 80

## exciting

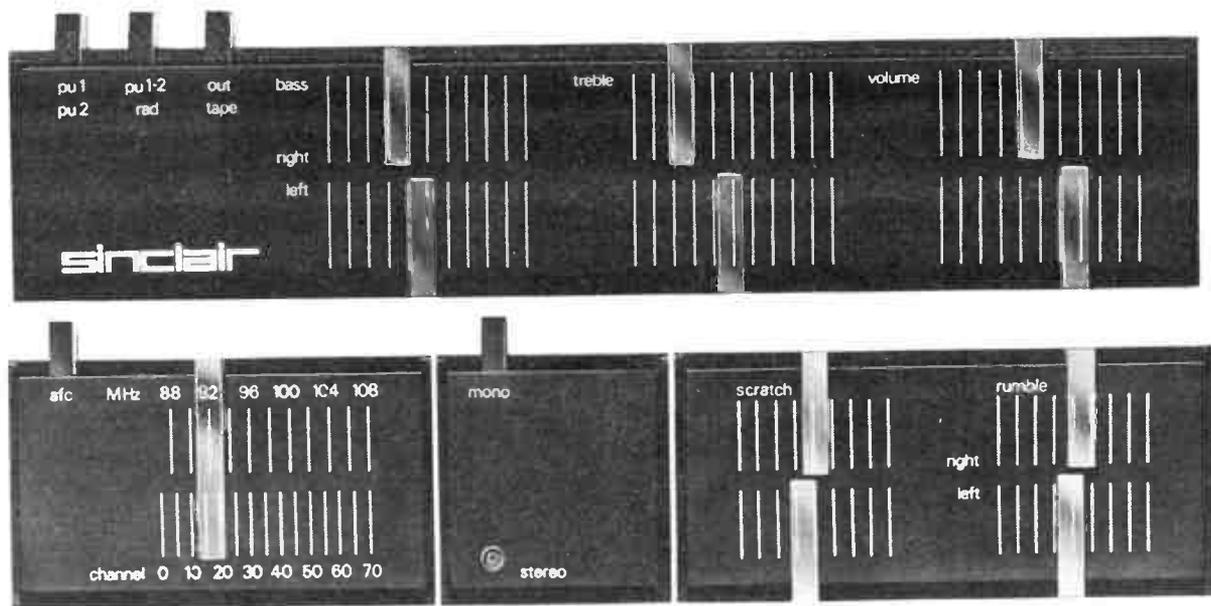

only  $\frac{3}{4}$ " deep x 2" high


Living with hi-fi takes on new meaning with Sinclair Project 80. The electronics of these revolutionary new modules are all contained within elegantly designed matching cases no more than three-quarters of an inch deep. They are designed for mounting on any appropriate flat surface by means of 6BA bolts extending from the rear of each module and which pass through suitably drilled holes. Connections are taken away out of sight in a similar manner. The possibilities opened up by Project 80 are endless – superb hi-fi systems can be installed in ways hitherto only dreamed about and never before made practical. No more cutting out and shaping to put modules in position. A few holes drilled with the aid of templates supplied and the job is done. Now you need never again be faced with problems of keeping the hi-fi from clashing with carefully thought-out furnishing schemes. (That will surely please wives!) Slider controls have been introduced in place of knobs and all modules in the range incorporate new up-dated circuitry with emphasis on performance standards and built-in protection against overload and shorting. The aim was to re-think modular construction completely – to make it infinitely more versatile, even simpler and more reliable – the result – Project 80 – another triumph for Sinclair, and the most exciting construction modules ever.

the slimmest, most elegant hi-fi modules ever made

### Typical Project 80 applications

| System   | The Units to use              | Units cost               |
|--|-------------------------------|--------------------------|
| Simple battery record player                           | Z.40                          | £5.45<br>+ 54p V.A.T.    |
| Mains powered record player                            | Z.40, PZ.5                    | £10.43<br>+ £1.04 V.A.T. |
| 30W. RMS continuous sine wave stereo amp.              | 2 x Z.40s, Stereo<br>80; PZ.6 | £30.83<br>+ £3.08 V.A.T. |
| 50W (8 Ω) RMS continuous sine wave de luxe stereo amp. | 2 x Z.60s, Stereo<br>80; PZ.8 | £33.83<br>+ £3.38 V.A.T. |
| Indoor P.A.  | Z.60, PZ.8                    | £14.93<br>+ £1.49 V.A.T. |

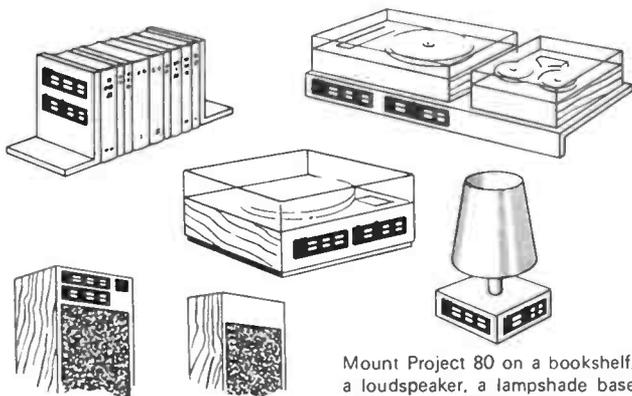
Project 80 FM tuner, decoder, and A.F.U. may be added as required



Mount Project 80 on a bookshelf, a loudspeaker, a lampshade base a false wall with two Q.16 loudspeakers... almost anywhere.

# new thinking in modular hi-fi
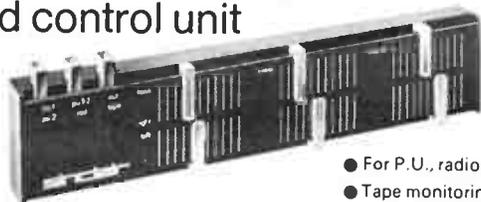
## Stereo 80 pre-amplifier and control unit



- For P.U., radio and tape
- Tape monitoring switch
- Simplest ever fixing


Each channel has its own separate tone and volume controls operated by sliders, enabling ideal environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry that ensures the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

### TECHNICAL SPECIFICATIONS

Size - 260 x 50 x 20mm (10 1/4 x 2 x 3/4 ins)  
 Finish - Black with white indicators and transparent sliders  
 Inputs - Magnetic pick-up 3mV RIAA corrected; Ceramic pick-up 300mV  
 Radio 300mV; Tape 30mV  
 Signal/noise ratio - 60dB  
 Frequency range - 20Hz to 15KHz  $\pm$  1dB 10Hz to 25KHz  $\pm$  3dB  
 Power requirements - 20 to 35 volts  
 Outputs - 100mV  $\rightarrow$  AB monitoring for tape  
 Controls - Press button for tape, radio and P.U. Sliders for volume, bass (-12dB to -14dB at 100Hz) treble (+11dB to -12dB at 10KHz)

R.R.P. £11.95 +£1.19 V.A.T.
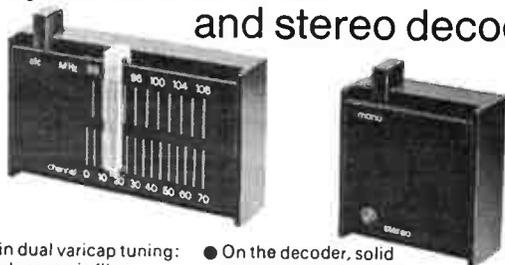
## Project 80 FM tuner and stereo decoder



- Twin dual varicap tuning: 4 pole ceramic filter; switchable A.F.C.
- On the decoder, solid state stereo indicating beacon.

Making the Project 80 F.M. tuner and decoder available separately gives a wider choice of systems and saves money where stereo reception may not be required. The tuner is a triumph of electronic design and assures excellent performance. The decoder gives a 40dB channel separation with 150mV output per channel. Both units may be used with other than Project 80 systems.

### TECHNICAL SPECIFICATIONS OF TUNER

Size - 85 x 50 x 20mm (3 1/4 x 2 x 3/4 ins)  
 Tuning range - 87.5 to 108 MHz  
 Detector - I.C. balanced coincidence for good A.M. rejection  
 One I.C. equal to 26 transistors  
 Distortion - 0.2% at 1KHz for 30% modulation  
 4 pole ceramic filter in I.F. section  
 Aerial impedance - 75  $\Omega$  or 240-300  $\Omega$   
 Sensitivity - 4 microvolts for 30dB quieting  
 Output - 300 mV for 30% modulation  
 Power requirements - 23 to 33 volts

### DECODER

Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/4 ins)  
 One 19 transistor I.C.

R.R.P. £11.95 +£1.19 V.A.T.

R.R.P. £7.45 +0.74 V.A.T.


## Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a charge (typically £1.00) will be made.

# sinclair

Sinclair Radionics Ltd. London Road, St. Ives, Huntingdon PE17 4HJ  
 Telephone St. Ives (0480) 64646
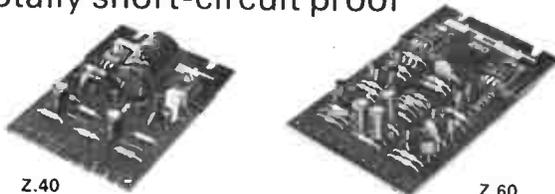
## Z.40 & Z.60 power amplifiers totally short-circuit proof



Z.40

Z.60

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.

### Z.40 TECHNICAL SPECIFICATIONS

Size - 55 x 80 x 20mm (2 1/4 x 3 1/4 x 3/4 ins) 9 transistors  
 Input sensitivity - 100mV  
 Output - 15 watts RMS continuous into 8  $\Omega$  (35V)  
 Frequency response - 10Hz - 100KHz  $\pm$  1dB  
 Signal/noise ratio - 64dB  
 Distortion - at 10 watts into 8  $\Omega$  less than 0.1%  
 Power requirements - 12 to 35 volts


### Z.60 TECHNICAL SPECIFICATIONS

Size - 55 x 98 x 15mm (2 1/4 x 3 7/8 x 3/8 ins) 12 transistors  
 Input sensitivity - 100-250mV  
 Output - 25 watts RMS continuous into 8  $\Omega$  (45V)  
 Distortion - typically 0.03%  
 Frequency response - 10Hz to more than 200KHz  $\pm$  1dB  
 Signal/noise ratio - better than 70dB  
 Built-in protection against transient overload and short circuiting  
 Load impedance - 4  $\Omega$  min. max safe on open circuit

Z.40 R.R.P. £5.45 + 0.54 V.A.T. Z.60 R.R.P. £6.95 + 0.69p V.A.T.
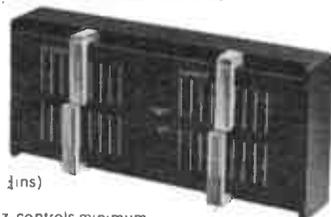
## Project 80 active filter unit

Makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls applied to each channel make it easier to obtain ideal stereo balance.



### TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/4 ins)  
 Voltage gain - minus 0.2dB  
 Frequency response - 36Hz to 22KHz controls minimum  
 Distortion - at 1KHz - 0.03% using 30V supply  
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct. slope  
 L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct. slope

- For scratch and rumble control
- Transistorised active circuitry

R.R.P. £6.95 +0.69 V.A.T.

## Power supply units

### PZ.8

Stabilised. Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 45V.



R.R.P. £7.98 + 0.79p V.A.T.  
 Without mains transformer

PZ.5 30V unstabilised  
 R.R.P. £4.98 + 0.49p V.A.T.

PZ.6 35V stabilised  
 R.R.P. £7.98 + 0.79p V.A.T.

To SINCLAIR RADIONICS LTD, ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid

for which I enclose Cash/Cheque for £ \_\_\_\_\_ including V.A.T.

Name

Address

# Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

## Aerials

**GENUINE FULL SIZE**  
**18 element TV aerial**  
as used by leading  
TV companies



**IMPERIAL TRADING (AERIALS) LTD.**  
the quality Aerial Specialists

## BAINES High Frequency Aerials

Postage paid on aerials inland.  
Parabeam UHF Aerials: PBM6 £2.40, PBM12 £3.35, PBM18 £4.30.  
Multibeam UHF Aerials: MBM18 £3.24, MBM30 £4.40, MBM46 £6.90, MBM70 £12.10.  
Stereobeam VHF/FM Aerials: SBM2 £2.95, SBM3 £4.40, SBM4 £4.90, SBM6 £7.25, 300/75 Balun £1.60, £2100 Alignment Bearing £7.90, Rotators £25.52  
Amplifiers: Masthead with Power supply £8.25, Setback battery £4.00.  
Accessories: Large SAE. Co-ax 4p and 8p/m.  
11 Dale Cres., Tupton, Chesterfield S42 6DR  
Telephone 863755

VHF/F.M. Aerials. Loft Type, Ten for £6. Roof Type, Ten for £15. Samples each type £3. J. E. Cook, 90 Ewhurst Road, Crawley, 23885 Sussex.

## Ladders

LADDERS 'Special Offer', Unvarnished triples. 9ft 7in closed—24ft 7in extended. £18.70 delivered. Home Sales Ladder Centre (WLS2) Haldane (North) Halesfield (1) Telford, Shropshire. Tel: 0952-586644.

## Service Sheets

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

## SERVICE SHEETS · MANUALS · BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 25p  
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS  
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

|   | PRICE |
|---|-------|
| NEW BOOKS & PUBLICATIONS  |       |
| HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES. 1st. Book by Babani...          | £0.40 |
| HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES. 2nd. Book by Babani...          | £0.95 |
| HANDBOOK OF RADIO TV TUBE & VALVE EQUIVALENTS by Babani...                        | £0.40 |
| HANDBOOK OF INTEGRATED CIRCUITS (ICs) EQUIVALENTS & SUBSTITUTES...                | £0.75 |
| TV FAULT FINDING BOOK by Data Publications Ltd. 405/625 Edition. 124 pp...        | £0.50 |
| COMPREHENSIVE COLOUR TV MANUAL. Lists common faults on most colour TVs...         | £2.25 |
| UNDERSTANDING TELEVISION by J.R. Davies. 405/625/Colour Edition. 512 pp...        | £2.10 |
| USING AN OSCILLOSCOPE by D.W. Easterling. 108 pp...                               | £0.70 |
| Fault Location Exercises in Radio & TV Servicing by K.J. Bohlman. Volume 1...     | £0.80 |
| Fault Location Exercises in Radio & TV Servicing by K.J. Bohlman. Volume 2...     | £1.35 |
| Mechanics Course in Radio, TV & Electronics 222 (433) by B.Fozard & G.N.Patchett. |       |
| First Year. Principles and Calculations. (Fozard) .....                           | £0.50 |
| Part 1. Electronic Systems. (Patchett) .....                                      | £0.85 |
| Part 2. Second Year. Electronic Systems. (Patchett) .....                         | £0.95 |
| Part 3. Third Year. Electronic Systems. (Patchett) .....                          | £2.00 |
| MAZDA BOOK OF PAL RECEIVER SERVICING by D.J.Seal. 288 pp .....                    | £3.80 |
| DICTIONARY OF RADIO & TELEVISION by W.E.Pannett. 380 pp .....                     | £1.80 |
| TELEVISION ENGINEERS POCKET BOOK by P.J.McGoldrick. 6th Edition. 400 pp ..        | £2.50 |
| WORLD RADIO TV HANDBOOK 1972. 26th Edition. 384 pp. Special reduced offer ..      | £0.90 |
| ELECTRONICS IN MUSIC by F.C.Judd. 169 pp. Circuit designs and operation .....     | £3.15 |
| HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P.J.Guy. 142 pp .....            | £1.50 |

A LARGE SELECTION OF OTHER BOOKS AVAILABLE AT OUR NEW SHOP PREMISES  
OPEN UNTIL 8pm. MONDAY TO SATURDAY. CALLERS WELCOME TO COME AND BROWSE  
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) good prices paid  
Please add 10% for Postage and Packing on all books. Send large S.A.E. for FREE booklists

## BELL'S TELEVISION SERVICES

190. KINGS ROAD. HARROGATE. YORKSHIRE. Telephone 0423-55885

## Service Sheets

### LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,  
RECORD PLAYERS, TRANSISTORS,  
STEREOGRAMS, RADIOGRAMS,  
CAR RADIOS)  
ALL AT 40p EACH

"PLEASE ENCLOSE LARGE S.A.E  
WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to  
(Uncrossed P.O.'s please, original  
returned if service sheets not available.)

#### PLEASE NOTE

We operate a "by return of post" service. Any  
claims for non-delivery should be made within  
7-days of posting your order.

## C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service  
Sheets (strictly by return of post). Please  
state make and model number alternative.  
Free TV fault tracing chart or TV list on  
request with order.

Mail order or phone 01-458 4882

## Educational

GO TO SEA as a Radio Officer. Write:  
Principal, Nautical College, Broad-  
water, Fleetwood FY7 8JZ.

AMIMI, MAA/LMI DIPLOMA, City &  
Guilds, etc. Thousands of passes. For  
details of postal courses in all  
branches of Engineering and illus-  
trated book—FREE—BIET (Dept.  
BPWCL/02) Aldermaston Court, Read-  
ing RG7 4PF. Accredited by CACC.

## CITY & GUILDS EXAMINATIONS

Make sure you succeed with an ICS home study  
course for C & G Electrical Installations, Tele-  
communications Technicians and Radio Ama-  
teurs. Free details from: International Correspondence  
Schools, Dept. 732D, Intertext House,  
London, SW8 4UJ.

## COLOUR TV SERVICING

Make the most of the current boom. Learn the  
techniques of servicing Colour & Mono TV sets  
through new home study courses, approved by  
leading manufacturers. Also radio and audio  
courses. Free details from: International Correspondence  
Schools, Dept. 732D2, Intertext House,  
London, SW8 4UJ.

## TECHNICAL TRAINING

Get the qualifications you need to succeed.  
Home study courses in Electronics and Electrical  
Engineering, Maintenance, Radio, TV, Audio,  
Computer Engineering & Programming. Also self  
build radio kits. Free details from: International  
Correspondence Schools, Dept. 732D3, Intertext  
House, London, SW8 4UJ.

ENGINEERS—get a technical certifi-  
cate. Postal courses in Engineering,  
Electronics, Radio, T.V. Computers,  
Draughtsmanship, Building, etc. FREE  
book from: BIET (Dept. BPWCL/32)  
Aldermaston Court, Reading, RG7 4PF.  
Accredited by CACC.

## Situations Vacant

### WORK IN CENTRAL AMERICA

Radio Technician needed for Guatemala.  
Radio Engineer needed for Honduras.  
Work with the British Volunteer Pro-  
gramme.

Information: Fran Chadwick, CIIR Overseas  
Volunteers, 41 Holland Park, London, W.11.

## MEN! £70p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 - p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London  
Computer Operators  
Training Centre

S65, Oxford Road,  
9-15, Oxford Street, W.1.  
Telephone: 01-734 2874

### For Sale

TV LINE OUTPUT TRANSFORMERS  
Tidman Mail Order Ltd., 236 Sandy-  
combe Rd., Richmond, Surrey, TW9  
2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NAE MILLS, Stockport.

### Books and Publications

## Technical Books — Radio & Electronics

|   |       |
|---|-------|
| Handbook of Tested Transistor Circuits.....       | £0-40 |
| Radio Servicing for Amateurs.....                 | £0-20 |
| Practical Radio Inside Out.....                   | £0-40 |
| Coil Design and Construction Manual.....          | £0-30 |
| Boys Bk of Crystal Sets and Simple Circuits.....  | £0-18 |
| Transistor Circuits Manual No. 1.....             | £0-15 |
| Transistor Circuits Manual No. 2.....             | £0-15 |
| Transistor Circuits Manual No. 4.....             | £0-15 |
| Transis Circuits for Radio Controlled Models..... | £0-40 |
| Rad & Elect Colour Codes and Oats Chart.....      | £0-10 |
| Handbk of Transistor Equiv and Substitutes.....   | £0-15 |
| Hi Fi, PA & Disco Amplifier Design Hndbk.....     | £0-75 |
| High Fidelity Loudspeaker Enclosures.....         | £0-40 |
| Transistor Test Equip and Servicing Manual.....   | £0-25 |
| Handbook of Simple Transistor Circuits.....       | £0-35 |
| Modern Transistor Circuits for Beginners.....     | £0-40 |
| Sound and Loudspeaker Manual.....                 | £0-50 |
| Practical Car Radio Handbook.....                 | £0-30 |
| Radio TV and Industrial Tube & Valve Equip.....   | £0-40 |
| Know Your Oscilloscope.....                       | £1-70 |
| Television Servicing Vol. No. 1.....              | £0-85 |
| Television Servicing Vol. No. 3.....              | £0-60 |
| Television Servicing Vol. No. 4.....              | £0-95 |
| Using an Oscilloscope.....                        | £0-70 |
| Servicing Transistor Radio Receivers.....         | £0-75 |
| Television Timebase Circuits.....                 | £1-00 |
| Jack Daws Service Clinic.....                     | £1-35 |

### NEW TITLES NOW AVAILABLE

|  |       |
|--|-------|
| Manual of Electronic Circuits for the Home.....    | £0-60 |
| Modern Crystal Set Circuits for Beginners.....     | £0-35 |
| Electronic Novelties for the Motorist.....         | £0-50 |
| 2nd Book of Transistor Equiv. & Substitutes.....   | £0-95 |
| Handbook of Electronic Musical Novelties.....      | £0-50 |
| Transistorised Novelties for Hi Fi Enthusiast..... | £0-35 |
| Fault Location Exercises in Rad. & TV Vol.1.....   | £0-80 |
| Fault Location Exercises in Rad. & TV Vol.2.....   | £1-35 |
| Colour TV Picture Faults.....                      | £2-50 |
| 99 Ways to Improve your Sh. Wave Listening.....    | £1-90 |
| Semi-conductors from A-Z.....                      | £1-50 |
| Modern Electronic Troubleshooting.....             | £1-30 |
| 104 Ham Rad. Proj. for Novice & Technician.....    | £1-25 |
| How to Solve Solid State Circuit Troubles.....     | £1-75 |
| Integrated Circuits Equiv. & Substitutes Hbk.....  | £0-75 |

PLEASE ADD 10% FOR POSTAGE & PACKING

FREE lists of other titles avail on request. Send to:

**RADIO BOOK SERVICE**  
40 Elwill Way, Beckenham BR3 2RZ

**WORLD RADIO TV HANDBOOK 1974.** £3.15. How to Listen to the World. £2.00. Postage and VAT included. David McGarva, PO Box 114, Edinburgh EH1 1HP.

**SW-BC LOG** with time indication, post free. Pay £0.80 at any post office to National Giro account 651-4154. SVERIGES RADIOKLUBB, UK treasurer.

**DIRECT FROM MANUFACTURER**—a comprehensive catalogue of UHF & VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (PW), 261 Hardess Street, London S.E.24.

**"SHORTWAVE VOICES OF THE WORLD,"** £1.70, postage and VAT 11p. "SWL Address Book," £1.55+11p. "Confidential Frequency List," £1.70+11p. "Guide to International Medium Wave Broadcasts," 20p+4p. Books and full details from any bookshop, or in difficulty write to: David McGarva, PO Box 114, Edinburgh EH1 1HP.

### Wanted

**TOP PRICES PAID** for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.  
**KENSINGTON SUPPLIES (C).**  
367 Kensington Street, Bradford 8,  
Yorkshire.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

**EARLY WIRELESS LITERATURE** before 1934. Johnson Raffles, Haverbreaks, Lancaster. Telephone 67770 evenings.

**WANTED**, buy not rent. Used telephone answering machine in working order, G.P.O.-approved, record caller's message. Fergus, 38 Salisbury Avenue, Belfast BT15 5DZ.

### Receivers and Components

## TAPE HEADS

Send stamp for lists.

**R.D.I. Ltd.**

Chilton Works,  
Garden Rd.,  
Richmond,  
Surrey,  
TW9 4NS

For valve and transistorized recorders from £2 ea.

**NEW MODEL V.H.F. KIT MK2**  
Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc. this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.  
Only £3.50 + p.p. 15p U.K. only.  
Illustrated catalogue of selected kits and components, 20p inc. VAT. P&P free.

**ALL PRICES PLUS 10% VAT**  
Galleon Trading Co.  
12, Burra Way,  
Corringham,  
Stanford-Le-Hope,  
Essex. SS17 9DE

### PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. Extremely low leakage. All 63v. D.C. Plus or minus 1% tolerance: 0.47µF—56p; 1.0µF—66p; 2.2µF—80p; 4.7µF—£1.30; 6.8µF—£1.64; 10.0µF—£2.00; 15µF—£2.75. Also available ±2% and ±5% ex. Stock.

### FANTALUM BEAD CAPACITORS—

Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15v/25v or 35v; 10.0µF at 16/20v or 25v; 15.0µF at 10/16v or 20v; 22.0µF at 6/10v or 16v; 33.0µF at 6v or 10v; 47.0µF at 3v or 6v; 100µF at 3v.  
All at 10p each; 10 for 95p; 50 for £4.00. BC109, BC107, BC108, BC109. All at 9p each; 6 for 51p; 12 for 96p. May be mixed for quantity price. BC182 and BC212 at 10p each; AF178 at 30p each. All brand new and marked. Full spec. devices.

### POPULAR DIODES. IN914, 6p each; 8 for 45p; 18 for 90p. IN916, 8p each; 6 for 45p; 14 for 90p; 1544, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

### NEW LOW PRICE—400 mW Zeners.

Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10.1, 12, 13.5, 15V. Tot. : 5% to 5mA. All new and marked. Price 7p each; 6 for 39p; 14 for 84p. Special offer 6 off each voltage (66 zeners): £3.65.

### RESISTORS. Carbon film 5%. ¼W at 40°C ¼W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.

### 440v A.C. CAPACITORS: 0.1µF, size 1½in x ½in—40p; 0.25µF (1½" x 1½")—55p; 0.47 and 0.5µF (1½" x 2½")—66p; 1.0µF (2" x 2")—85p; 2.0µF (2" x 1½")—£1.15.

### SILICON PLASTIC RECTIFIERS 1.5 amp.

Brand new wire-ended DO27. 100 P.I.V. at 7p each; 4 for 26p. 400 P.I.V. at 8p each; 4 for 30p; 800 P.I.V. at 11p each; 4 for 42p.  
7p Post and Packing on all orders below £5.00. Export orders—please add cost of air/sea mail.

PLEASE ADD 10% V.A.T. TO ALL ORDERS

Send S.A.E. for lists of other ex-stock items. L.E.D.'s, disc capacitors, electrolytics etc. Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. W3, The Maltings, Station Road,  
WEM, Salop.  
Tel: NANTWICH (Cheshire) 63291.

## ANGLIA TRANSFORMERS

### SUB MINIATURE MAINS

Primary 0-240 V 50/60 Hz  
3 V Type. Output 3-0-3 V rms. 200 mA  
9 V Type. Output 9-0-9 V rms. 70 mA  
12 V Type. Output 12-0-12 V rms. 50 mA  
20 V Type. Output 20-0-20 V rms. 30 mA  
E.S. Screen. Clamp Construction.  
Size 28mm x 27 x 21H. F.C. 35 x 4 BA  
£1.05 each inc. U.K. P & P.

### MINIATURE MAINS

Primary 0-240 V 50/60 Hz  
6 V Type. Output 0-6, 0-6 V. 6 VA  
9 V Type. Output 0-9, 0-9 V. 6 VA  
12 V Type. Output 0-12, 0-12 V. 6 VA  
20 V Type. Output 0-20, 0-20 V. 6 VA  
Two Separate Secondaries  
E.S. Screen. Clamp Construction.  
Size 46mm x 31 x 38H. F.C. 53.5 x 4 BA.  
£1.10 each inc. U.K. P & P  
Plus VAT 10%.

### ANGLIA CONTROLS LTD

GRANGE ROAD . TONGHAM  
FARNHAM . SURREY

**COMPONENTS GALORE.** Pack of 500 mixed components manufacturers surplus plus once used; Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p.p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

**TUNBRIDGE WELLS,** Components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

**TREASURE TRACER MK III Metal Locator**



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.o. for leaflet

Complete kit **£9.80** Post 25p  
Built, tested and guaranteed Post 25p **£13.75**

**MINIKITS ELECTRONICS**  
35a LANGLEY DRIVE, WANSTEAD LONDON, E11 2LN (Mail order only)

|                  |     |      |            |
|------------------|-----|------|------------|
| <b>VEROBOARD</b> | 0-1 | 0-15 | Plain 0-15 |
| 24 x 5 in        | 26p | 26p  | 13p        |
| 24 x 3 1/2 in    | 23p | 18p  | 12p        |
| 32 x 5 in        | 30p | 32p  | 20p        |
| 32 x 3 1/2 in    | 26p | 26p  | —          |
| Track cutter     | 40p | 40p  | —          |

**MINIATURE CERAMIC CAPACITOR KITS**

|   |           |
|---|-----------|
| KIT 1 10 each E6 value 22pf to 1000pf 50V | Total 110 |
|   | £1.55     |
| KIT 2 25 each E6 value 22pf to 1000pf 50V | Total 275 |
|   | £3.05     |

**SEMICONDUCTORS**

8 pin dill 741 39p, BC 107 10p, BC 108 10p, BC109 10p, 1N914 4p

**SWITCHES**

Toggle switch, 250V 1-5A SPST 18p, OPOT 25p Slide Switch, OPOT miniature or standard 11p Push to make, non locking 12p

**MINIATURE VERTICAL PRESETS**

100Ω, 220Ω, 470Ω, 680Ω, 1K, 2-2K, 4-7K, 6-8K, 10K, 22K, 68K, 100K, 4p each.

**NEK ELECTRONICS (W2)**

28 Carnegie Road, St. Albans, Herts  
Please add 10p P. & P. Mail order only

**"Globe-King"**

**V.H.F. & SHORT WAVE KITS**

Precision standard, low cost valve and transistor Kits 10-350 MHz. V.H.F. 80-180 MHz. "Easy-Build" diagrams and simplified instructions. For free literature send S.A.E. to sole manufacturers. (Overseas: Int. Reply Coupon).

**JOHNSONS (RADIO) Est. 1943**  
Shaw St, Worcester, WRI 3QQ  
Tel. 24864 A JOHN BANNER CO.

**BRAND NEW COMPONENTS** by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2-2, 4-7, 10mfd.—4p, 22, 47, 4 1/2p, (50V—5p.) 100—5 1/2p, (50V—7p.) 220—6p, (50V—9p.). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2-2/35V, 4-7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p, 0.04, 0.05—3p, 0.068, 0.1—3 1/2p. Polystyrene 63V, E12 series 10 pf.—1,000 pf.—2p, 1,200 pf.—10,000 pf.—3p. Miniature Highstab resistors, 5%, E.12 series—Carbon Film 1/2W 1Ω—10MΩ (10% over 1 Meg.) Metal Film 1/2W 10Ω—2.2MΩ and 1W, 27Ω—10MΩ all 3/4p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

**TRANSISTOR AMPLIFIERS** 50p Vol/Tone Pre-Amps 30p. LW-MW Mixer-osc panels 50p all with circuits. Record player cabinets £3. Radio cabinets, suitable ext speakers, colours blue, brown, yellow. 50p Mains droppers 76Ω + 66Ω + 66Ω + 25Ω + 24Ω + 26Ω 30p. Archer, 9 Pine Grove, Maidstone, Kent.

**MANUFACTURERS** Surplus components. Mixed packs all post free. Resistors 20p. Capacitors 60p. Discs 40p. Hardware 25p. Relays 60p. Four digit magnetic counters 20p. Ferric Chloride LB 52p. Samples and lists 20p stamps. Derwent Radio, Scarborough.

**ELEVEN BAND RADIO.** SW 1-4. Marine, LW, MW, FM, PSB (76-86). Aircraft (108-136). PSB (148-174). Batt/Mains, BFO, Fine Tune, Squelch. Output 1-3W. £58. SAE full lists, multi band radios, also Grundig Bargains, Satellit, 12 band, £118. Langtons Radio, High Street, ROCESTER, Staffs. 088-923 388.

**INTEGRATED CIRCUIT** and FET modules for construction of low-cost receivers, converters, pre-selectors, etc. SAE details,—P. R. Golledge, Glen Tor, Torrington, Devon.

**5-N CHANNEL FETS TYPE 3819E—£1** (incl VAT). Full spec devices complete with circuit details for building voltmeter, timer, etc. For full list of fets and other transistors available, send 10p. Redhawk Sales Ltd, 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

**SL403D AUDIO I.C.—£1.65.** Finned heat-sink—16p. Fibre Glass P.C.B.s for latest Mullard stereo pre-amp. Input board—75p. Tone/Filter board—85p. P&P—10p. Quantec Multitechnic Ltd., Morpeth, Northumberland.

**Miscellaneous**

**Darned Electronic Wizardry**

by Dewtron (VAT extra).

Famous kits, e.g. waa-waa complete kit £2.95. Fuzz kit £5.50 auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**UNIQUE HI-FI SPEAKER SYSTEM**

**24 WATTS PEAK!**

Beautiful bookshelf units in mahogany type finish. Employs infinite baffle enclosure with dual cone 8 ohm drive unit. Brand new with 6' leads.

£9.80 Per Pair P&P 60p

**GREGG Electronics**  
PW3, 24 Cranbourn Street  
Leicester Sq, London WC2

**GLASS FIBRE P.C. BOARD.** Large supplies available in single sided one ounce copper 2p per sq. ft. (over 1 foot). 75p per sq. ft. (over 1 foot). In double sided one ounce copper 1p per sq. inch (under 1 ft.). £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

**AMTRON KITS.** Your Devon Stockist. E. Wenmouth, 50 South Street, Exeter 76058.

**DON'T LOOK**

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big finch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £1.35 for your Maxi-Volt now!
- ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5.90 for yours now!
- ★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. "Brain-freeze" 'em with vari-speed stop-motion flashes. Includes super case too. Send £2.20 now! (all prices include V.A.T., packing & postage.)

Send remittance to:  
**BOFFIN PROJECTS,**  
4 CUNLIFFE ROAD,  
STONELEIGH, EWELL, SURREY  
(Mail order only)  
Or for more details, send 15p for lists, plus free design project sheet.

**MORE RANGES FOR LESS MONEY!**



**MULTIMETER AC-DC Type U-437**  
10kOhms/V 2.5% Precision  
A-DC 0-1-1A - 5 Ranges.  
V-DC/AC 2-5 to 1000 V - 6 Ranges.  
Ohms-100 to 1 MegOhm - 4 Ranges.  
Frequency: 45-40kHz - 2 Ranges.

**TAUT SUSPENSIONS MOVEMENT.**  
Complete with steel case. Dimensions without case: 212x118x75mm **£4.95**

**AC/DC Multimeter type U4324**  
A-OC 0-06-3A - 6 Ranges.  
A-AC 0-3-3A - 5 Ranges.  
V-OC 0-6-1200-V - 9 Ranges.  
V-AC 3-900 V - 8 Ranges.  
Frequency: 45 to 20kHz-2 Ranges.  
Resistance: 500 Ohm to 5 MOhm-5 Ranges. Decibel: -10 to +12dB -2 Ranges. Accuracy: ± 2.5%.  
Dimensions: 167 x 98 x 63 mm.

Only **£8.00**



**SUPERTESTER 680 R ICE**  
10 Fields - 80 Ranges. Plus a lot of accessories for measurements of 500A-AC 100 A/OC - Temperature -50C to +200C - Magnetic fields up to 15 KGauss - Phase indicator - EHT 25kV Electronic Volt Ohm - meter Transistor, Diode Tester etc.

Dimensions: 128 x 95 x 32 mm - 300 grams 20kOhm/V Accuracy **£18.50**  
1% OC Ask for free catalogue Accessories Extra  
Add 10% VAT to all items + 35p P&P

**ELECTRONIC BROKERS LTD.**  
49-53 Pancras Road, London NW1 2QB Tel: 837 7781

**HARDWARE SUPPLIES.** Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon. Warwks. CV37 9JP.

**AERIAL WIRE.** PVC covered multi-strand tinned copper. 25ft-23p. 50ft-45p. 75ft-67p. 100ft-89p. 150ft-£1.32p. 200ft-£1.76p. Including VAT. All plus 12p P&P. Al Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

Versatile  
**10 in ONE**



**MIN-LAB**

Comprising:

- AC and DC Voltmeter
- Ohm Meter
- Capacitance Substitution
- Battery Supply
- RF Field Strength Indicator.
- Audio Generator
- Resistance Substitution
- DC Ammeter
- RF Signal Generator

This new, unique instrument combines all you need for testing. Money back if not satisfied.

**£11.95**

includes VAT & p. & p.

Cash with order or send s.a.e. for illustrated data sheet to:

**J. H. ASSOCIATES LTD. (DEPT. PW)**  
Cricketfield Lane, Bishop's Stortford, Herts.

**Build your next project in a BEC (Book end chassis)**



New Improved with alloy trim on bottom of all cabinets. Now in easy to assemble kits.

GB3 (Illustrated) ... 14" x 9" x 4" ... £4.00 P & P 45p.  
Other sizes. SAE with enquiries  
**H. M. ELECTRONICS 275a, Fulwood Rd, Sheffield S10 3BD**


**PRINTED CIRCUIT BOARDS**

Professional printed circuit boards custom made for your design. Delivery 4 days. Typ. price: 3" x 2" board £3.36, plus VAT. Trade and retail. S.A.E. for details or phone Colchester (0206) 47010.

**B. J. CLUES (Electronic and Radio Engineer), Shaftsbury House, 40a Culver Street, Colchester.**

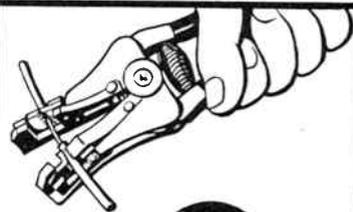**AUTOMATIC WIRE STRIPPER**

AS SUPPLIED TO LEADING ELECTRONIC COMPANIES



PRICE  
**£2.95**

INCL. PP & VAT

GRIPS AND STRIPS

WIRE

IN ONE OPERATION

**IDEAL GIFT**

**ELECTROLINK**

ULLSWATER CRESCENT  
COULSDON CR3 2UG SURREY

|  |                                       |   |
|--|---------------------------------------|---|
| <b>BA NUTS BOLTS and WASHERS</b>                                       |                                       | Per 100   |
| Assorted length bolts, shake-proof washers.                            | Size                                  | Nuts Bolts W/rs   |
|  | 0                                     | 53p 75p 29p   |
|  | 4                                     | 46p 33p 22p   |
|  | 6                                     | 29p 46p 18p   |
|  | 6                                     | 29p 35p 18p   |
| <b>SELF TAPPING SCREWS</b><br>Box of 100 Assrt.                        | <b>FASTENERS</b><br>Box of 100 Assrt. | <b>PVC 100 GROMMETS</b><br>1/4" 9/32" or 3/8" Hole State size |
| 29p  | 51p                                   | 44p   |
| <b>5" SIDE CUTTERS</b>   | <b>5" PLIERS</b>                      |   |
| 59p  | 59p                                   |   |
| Post free over £2 Orders under £2 add p & p 15p All prices include VAT |                                       |   |
| <b>SILHILL PRODUCTS</b>  |                                       |   |
| Dept. WP3, 226 Mary Street, Birmingham B12 9RJ<br>Tel. 021-440 3600    |                                       |   |

**LOW COST I.C. Mounting.** I.C. pin sockets in lengths of 100 for 60p (p&p 5p). Quantity rates. S.A.E. details and sample. **GASKELL, Oak Lodge, Tansley, Derbyshire.**

**BUILD IT in a DEWBOX** quality cabinet. 2in x 2 1/2in x any length. **D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.**

**EXPERIMENTERS!** Hundreds of unusual items cheap. 1974 catalogue 5 1/2 p. **GRIMSBY ELECTRONICS, 64 Tennyson Road, Cleethorpes, Lincs. (Mail Order Only.)**

**EXPERIMENTERS**  
LOOKING FOR SOMETHING DIFFERENT

**SPECIALLY DESIGNED FOR USE WHERE SPACE IS LIMITED**  
Alloy cased. Ideal for S.W. Enthusiasts  
Beam rotary reception

**UNIQUE DESIGN**  
Complete Kit, Base, mast, aerial, charts  
Fabulous Value  
£3.50 PP Paid

ALL WAVE

Also included in this Kit, CHARTS of Frequency Allocations. International call signs. World time, Codes, Map, etc.

**TUBULAR METAL PRODUCTS**  
7 LOWESMOOR TERRACE, WORCESTER ENGLAND

**AERIAL BOOSTERS—£3.25**  
We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF RADIO

**VALVE BARGAINS**

ANY 5—50p, 10—75p, 50—£3.30—  
ECC82, ECL80, EB91, EBF69, EF80, EF65, EF183, EF184, EY86, PCC64, PCC69, PCC169, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, PC86, PC88.

**19" UHF/VHF (BBC2) £6.00**

Thorn-850 or Pye, with set of spare valves.  
Carriage £2.00 (Untested).

**100 MIXED RESISTORS—65p**

1/2 to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Ceramic Capacitors from 1PF to 6200PF (our choice) 65p.

**BARGAINS PARTS**

Translator UHF Tuners—£2.00, 500K-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2.25.  
Brand New Transistors BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order  
Money back guarantee. S.A.E. for leaflets.

**ELECTRONIC MAILORDER (BURY) LTD.**

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

**12 VOLT FLUORESCENT LIGHTS**  
(as illustrated by Thorn AEI)

Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12 ins. 8 watt £4.00 post paid } Including 21 ins. 13 watt £5.00 post paid } V.A.T.

Callers welcome.

For lists or enquiries, large s.a.e.  
**SALOP ELECTRONICS, 23 WYLE COP SHREWSBURY, SHROPSHIRE.**

Please mention  
**PRACTICAL WIRELESS**  
when replying to  
Advertisements

**EX COMPUTER PC PANELS**  
4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data. 10 boards 50p (12p)

**Special Bargain Pack**

25 boards for £1 (30p)

Panels with 4 Power transistors sim OC28 50p (10p)

**COMPUTER GRADE ELECTROLYTICS**

12,000µ 100v, 5 x 2 1/2 dia 75p (25p)  
30,000µ 25v 65p (20p)

**ELECTROLYTICS**

4,000µ 70v, 7,000µ 70v, 3,600µ 40v, 10,000µ 50v. 4 1/2 x 2 in dia 55p (14p)  
10,000µ 35v, 5,000µ 35v, 4 1/2 x 2 in 40p (12p)

2,000µ 30v, 400µ 40v, wire ends 15p (6p)  
100 piv 20A, Si diodes 4 for £1 (10p)

100 piv 3A, Si diodes 4 for 50p (7p)

250 mixed resistors 60p (9p)  
250 mixed capacitors 60p (9p)

200 Si planar diodes 50p (7p)

Sub-min co-ax connectors 4 prs 50p (7p)

Min. glass neons 12 for 50p (7p)

Reed relays mixed 10 for 50p (7p)

Micro switches 8 for 50p (9p)

Assorted relays 8 for £1 (18p)

Papst extractor/blower fans 100 c.f.m. 4 1/2 x 4 1/2 x 2in £3.50 (28p)

QH bulbs 12v 55w (also some 6v bulbs) 50p (6p)

Postage and package shown in brackets. Please add 10% VAT to prices.

**KEYTRONICS**

(Mail Order only)

**44 EARLS COURT ROAD LONDON W8. 01-478 8499**

TOP QUALITY—LOW COST




AMATEUR RADIO EQUIPMENT



**P.R.40**  
SOLID STATE  
R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now superceded. It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio.  
Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee . . . £11.13 Carr./VAT Paid

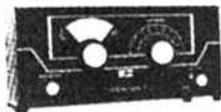

**MULTIBAND-6**  
SOLID STATE  
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands. 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery). £16.40 Carr./VAT Paid Stamp brings illustrated leaflets.



**CR70A**  
COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning. Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

Complete ready built £32.56 Carr./VAT Paid  
**SEND FOR YOURS TODAY!**

**NOTE:** These CODAR Receivers meet the BREMA specification for Communication Receivers. Some portable receivers being advertised as Communication Receivers do not meet these requirements. Illustrated leaflets and H.P. details free.



ON THE DESIGN STAFF—  
G3SZM G3IRE

**CODAR**®

TELECOMMUNICATIONS AND ELECTRONIC  
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS  
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX  
Tel. 090-63-61901 BN15-8TZ

**ESSENTIAL BOOKS FOR RADIO AMATEURS**

**RADIO AMATEURS' EXAMINATION  
MANUAL**

by G. L. Benbow, G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. Success in the RAE should be assured if all that it contains is understood and remembered.

84 pages

Price 90p post paid

**TELEPRINTER HANDBOOK**

by D. J. Goacher, G3LLZ, and  
J. G. Denny, G3NTT

A brand new book covering all aspects of modern teleprinter techniques. Full descriptions and maintenance data for all widely-used machines, together with design and use of ancillary equipment. Definitely a book for the teleprinter enthusiast's work bench.

376 pages

£5.35 post paid

**A GUIDE TO AMATEUR RADIO**  
by Pat Hawker, G3VA

This extensively revised 15th edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby, it covers technical, operating and licensing matters.

96 pages

Price 90p post paid

**AMATEUR RADIO AWARDS**  
by C. R. Emary, G5GH

Lists all the world's major awards from national societies and how to obtain them. Includes reproductions of certificates and maps, and operating information.

Loose-leaf binding allows insertion of amendment pages at a later date.

194 pages

Price £1.40 post paid

These are just four of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.

**RADIO SOCIETY OF GREAT BRITAIN**

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688




## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 15 watts approx. 12Hz-20KHz  $\pm$  3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, esuchphon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £11.60. P. & P. 50p.

## DE LUXE STEREO AMPLIFIER

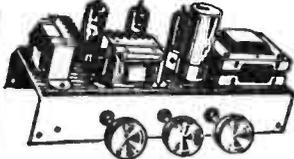

A.C. mains 200-240 V. Using heavy duty fully isolated main transformer or with full wave rectification giving additional smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x E780 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w. x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £29.90. P. & P. 50p.

**POWER SUPPLY UNIT 200/240V.** A.C. Input. Four switched fully smoothed D.C. outputs giving 6v. and 74v. and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radio, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5.00 P. & P. 35p.

**BLACK ANODISED 16g. ALUMINIUM HEAT SINKS.** For TO3, complete with nuts and bushes. Size 2 1/2" x 3" approx. 28p pair. P. & P. 6p.

**HIGH GRADE COPPER LAMINATE BOARDS 8" x 6"** 5 for 55p P. & P. 23p.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0.5-10-15-20-25-30-35-40-50V. Half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.31 P. & P. 40p.

**MAINS TRANSFORMER.** For transistor power supplies. P1. 200/240V. Sec. 0-9-9 at 500 mA. £1.10. P. & P. 25p. P2. 200/240V. Sec. 12-0-12 at 1 amp. £1.21. P. & P. 26p. P3. 200/240V. Sec. 10-0-10 at 2 amp. £1.82. P. & P. 35p.

**For personal callers only!** Limited number of stereo radiogram chassis, covering L.V./M.F.M. bands. Mono radio and stereo gram. Overall size approx. 16 1/2" W. 6 1/2" H. 8" Depth. 4 watts per channel output. only £16.50.

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price £1.00. P. & P. 15p.

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents . . . . . 80p  
Transistor Equivalents . . . . . 80p  
Transistor Characteristics . . . . . £1.15  
POST FREE  
All three together . . . . . £2.80

### NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias 85p, Post Free

8 pole 3 way 2 bank low loss Yaxley type switches 1 1/2" sections. Standard spindle. 2 switches 66p + 10p P. & P.

Open 9-5.30 Monday to Friday. 9-5 Saturday

Early closing Wed.

A few minutes from South Wimbledon Tube Station.

# HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

### RECORD PLAYER BARGAINS

Main models. All brand new in maker's packing. LATEST B.S.R. C109/C129 AUTOCHANGER UNITS with latest stereo/mono compatible cartridge £7.60 + 50p P. & P.

GARRARD SP25 Mk III with heavy precision machined die cast turntable £10.58, carr. 55p.

### PRECISION ENGINEERED PLINTS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025CT, 2500, 3000, 2500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high including rigid smoked acrylic cover). NOW ONLY £4.95, P. & P. 70p.

LATEST ACOS GP91/15C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 15p.

SONOTONE STARC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.30 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.80. P. & P. 15p.

LATEST BONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78 £1.63 P. & P. 15p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.50, P. & P. 15p.

**QUALITY RECORD PLAYER AMPLIFIER MK. II** A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £4.40. P. & P. 50p.

ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £5.85, P. & P. 60p.

## SPECIAL OFFER ! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tegan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohm impedance.

**OUR PRICE £9.25** Carr. 75p. Cabinet Available Separately £4.85, Carr. 65p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £7.15, Carr. 75p.

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. PRICE £3.30 P. & P. 40p BARGAIN PRICE

### LOUDSPEAKER BARGAINS

5in. 3 ohm £1.05, P. & P. 15p. 7 x 4in. 3 ohm £1.15, P. & P. 20p. 10 x 6in. 3 or 15 ohm £1.90, P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.62, P. & P. 20p. E.M.I. 13" x 8in. with high flux ceramic magnet with parasitic tweeter, 3 or 15 ohm £3.50, P. & P. 30p. E.M.I. 13" x 8in. 3, 8 or 15 ohm with two in-built tweeters and crossover network £4.65, P. & P. 30p. E.M.I. Ceramic magnet heavy duty tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. £1.25 + 20p. P. & P. BRAND NEW. 12in. 15w. 11/2D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly £7.50. Guitars models: 25w. £7.80, 35w. £9.35, P. & P. 45p.



### SPECIAL OFFER! LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS

With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £2.70. P. & P. 35p.

Also available specification as above but size 10" x 6" £2.70 and size 8" round £2.80. P. & P. 35p.

**LIMITED NUMBER EMI 2 1/2" 8 ohm Tweeters.** Mounted on flat bracket size 2 1/2" wide x 7 1/2" long. 70p per pair plus 15p P. & P.

Ex equipment but new and tested 70p per pair plus 15p P. & P.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 15 ohm £2.45, P. & P. 30p. 35 ohm SPEAKERS 3in. only 70p P. & P. 25p.

"POLY PLANAR" WAFER-TYPE. WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11" x 1 1/2" x 3 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceiling, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6.55 each. P. & P. 34p.

**VYNAIR & REXINE SPEAKERS & CABINET FABRICS** app. 54 in. wide. Our price £1.10 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A very first-class Hi-Fi Stereo Amplifier Kit. Uses 14 resistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm$  3dB 15-20,000 Hz. Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx.  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 30v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or sent 18p plus large S.A.E. **AMPLIFIER KIT £11.55** P. & P. 25p (Magnetic input components 33p extra) **POWER PACK KIT £3.30** P. & P. 35p **CABINET £3.30** P. & P. 35p (Post Free if all units purchased at same time)

Also available ready built and tested £23.10. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, tin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.



### 3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. Incorporates ECC83, EL84, E780 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5.50. P. & P. 45p.

**EMI "TOR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4.50. P. & P. 45p.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.

Fully shrouded section wound output transformer to match 3 or 12 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E780 rectifier. Simple instruction booklet 15p + S.A.E. (Free with parts) All parts sold separately. ONLY £8.80 P. & P. 65p. Also available ready built and tested £12.10. P. & P. 70p.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexform earmuffs. Wired and fitted with standard stereo 3 1/2" jack plug. Frequency response 30-15,000Hz. Matching Impedance 8-16 ohms. Easily converted for Mono. PRICE £3.30. P. & P. 25p.

## PRICES INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



GIRO NO. 331 7056  
C.W.O. only. P. & P. 10p on orders below £5  
Discount: £10-10%, £20-15% (except net items)  
Export Order enquiries welcome (VAT free)

Official Orders accepted from  
Educational & Government Departments  
**ALL PRICES INCLUDE VAT**

**SPECIAL RESISTOR KITS**

10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3-10 net  
10E12 1/2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3-20 net  
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7-35 net  
25E12 1/2W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7-35 net  
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £8-15 net  
10E12 2V KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £12-65 net

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
250V P.C. Mounting: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 3½p, 0-068µF, 0-1µF, 4½p, 0-15µF, 4½p, 0-22µF, 5½p, 0-33µF, 8p, 0-47µF, 9p, 0-68µF, 11p, 1µF, 15p, 1-5µF, 22p, 2-2µF, 25p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 2½p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3½p, 0-047µF, 0-068µF, 0-1µF, 4½p, 0-15µF, 6½p, 0-22µF, 8½p, 0-33µF, 12p, 0-47µF, 14p, 0-68µF, 16p, 1µF, 18p, 1-5µF, 22p, 2-2µF, 25p.  
160V: 0-01µF, 0-015µF, 0-022µF, 2½p, 0-047µF, 0-068µF, 3½p, 0-1µF, 0-15µF, 4½p, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 7½p, 0-68µF, 11p, 1µF, 12½p.

**MINIATURE CERAMIC PLATE CAPACITORS**  
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0-01, 0-015, 0-022, 0-033, 0-047, 0-07, 0-1, 0-15, 0-22, 0-33, 0-47, 0-7, 1, 1-5, 2, 3, 4, 5, 10, 15, 20, 25, 30, 40, 50, 75, 100, 150, 200, 300, 400, 500, 750, 1000, 1500, 2000, 3000, 4700, 4p, 6800, 10,000, 4½p.

**POLYSTYRENE CAPACITORS 160V 5%**  
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p, 6800, 10,000, 4½p.

**RESISTORS**

CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%.

| W. Type Range   | 1-9  | 10-49 | 50-99 | 100-249 | 250-499 | 500-999 | 1000+    | Size mm    |
|-----------------|------|-------|-------|---------|---------|---------|----------|------------|
| † CF 22-1M 1    | 0-8  | 0-65  | 0-62  | 0-55    | 0-5     | 0-5     | 0-45     | 2-4 x 7-5  |
| † CF 22-2M2 1   | 0-8  | 0-65  | 0-62  | 0-55    | 0-5     | 0-5     | 0-45     | 3-9 x 10-5 |
| † CF 22-1M 1    | 0-8  | 0-65  | 0-62  | 0-55    | 0-5     | 0-5     | 0-45     | 5-5 x 16   |
| † MF 10-2M7 1   | 0-9  | 0-8   | 0-7   | 0-65    | 0-65    | 0-65    | 0-6      | 3x7        |
| † MF 10-2M2 1   | 0-9  | 0-8   | 0-7   | 0-65    | 0-65    | 0-65    | 0-6      | 4-2 x 10-8 |
| † MF 10-10M 1-5 | 1-25 | 1-25  | 1-1   | 1       | 0-95    | 0-88    | 6-6 x 13 |            |
| 2 MF 10-10M 3   | 2-5  | 2-5   | 2     | 1-75    | 1-75    | 1-6     | 8x17-5   |            |

For value mixing prices, please refer to our catalogue. (price in pence each)  
VALUES AVAILABLE—E12 Series only.

**PRESET SKELETON POTENTIOMETERS**

MINIATURE 0-25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω  
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 5p each

(P.W.) 61 CHEDDINGTON ROAD, PITSTONE,  
NR. LEIGHTON BUZZARD BEDS, LU7 9AQ  
Tel.: Cheddington 66846 (Std. Code 0296)  
PLEASE WRITE FOR FREE CATALOGUE

**B. H. COMPONENT FACTORS LTD.**

**Miniature Mullard Electrolytics**

|              |                |
|--------------|----------------|
| 1-0µF 63V 6p | 68µF 16V 6p    |
| 2-2µF 63V 6p | 68µF 63V 12p   |
| 3-3µF 63V 6p | 100µF 10V 6p   |
| 4-0µF 63V 6p | 100µF 25V 6p   |
| 6-8µF 63V 6p | 100µF 63V 14p  |
| 8-0µF 63V 6p | 150µF 16V 6p   |
| 10µF 63V 6p  | 150µF 63V 15p  |
| 10µF 25V 6p  | 220µF 6-4V 9p  |
| 10µF 16V 6p  | 220µF 10V 6p   |
| 10µF 63V 6p  | 220µF 63V 21p  |
| 15µF 16V 6p  | 330µF 16V 12p  |
| 15µF 63V 6p  | 330µF 63V 25p  |
| 16µF 40V 6p  | 470µF 6-4V 9p  |
| 22µF 25V 6p  | 470µF 40V 20p  |
| 22µF 63V 6p  | 680µF 16V 15p  |
| 32µF 10V 6p  | 680µF 40V 25p  |
| 33µF 16V 6p  | 1000µF 16V 20p |
| 33µF 40V 6p  | 1000µF 25V 25p |
| 47µF 10V 6p  | 1500µF 6-4 13p |
| 47µF 25V 6p  | 1500µF 16V 25p |
| 47µF 63V 6p  | 2200µF 10V 25p |
|              | 3300µF 6-4 26p |

**VEROBOARD 0-1 0-15**

|                 |         |
|-----------------|---------|
| 2½ x 5"         | 28p 28p |
| 3½ x 5"         | 26p 19p |
| 3½ x 5"         | 32p 33p |
| 3½ x 5"         | 28p 28p |
| 2½ x 5" (Plain) | 7p 7p   |
| 2½ x 5" (Plain) | — 14p   |
| 2½ x 5" (Plain) | — 12p   |
| 5½ x 3" (Plain) | — 22p   |
| Insertion tool  | 59p 59p |
| Track Cutter    | 44p 44p |
| Pins, Pkt. 25   | 10p 10p |

**TRANSISTORS**

|            |            |
|------------|------------|
| AC127 16p  | BC212L 12p |
| AC128 25p  | BC213L 12p |
| BC107 11p  | BC214L 17p |
| BC108 12p  | OC44 18p   |
| BC109 13p  | OC71 13p   |
| BC149 12p  | OC81 16p   |
| BC182L 12p | OC170 23p  |
| BC183L 12p | T1543 33p  |
| BC184L 13p | 2N2926 11p |
|            | 2N3702 11p |

**POTENTIOMETERS**

Carbon Track 5K Ω to 2M Ω, log or lin. Single, 16p Dual Gang 46p. Log Single with switch 26p  
Slider Pots. 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 55p.

**DIODES**

|            |                |
|------------|----------------|
| IN4001 6p  | DIN 2 Pin 12p  |
| IN4002 7p  | 3 Pin 13p      |
| IN4003 9p  | 5 Pin 180° 15p |
| IN4004 9p  | Std. Jack 14p  |
| IN4005 12p | 2.5mm Jack 11p |
| IN4006 14p | Phono 5p       |
| IN914 7p   |                |
| IN914 7p   |                |
| BA100 10p  |                |
| OAS 42p    |                |
| OA47 9p    |                |
| OA81 11p   |                |
| OA200 8p   |                |

**PLUGS**

|            |                |
|------------|----------------|
| IN4001 6p  | DIN 2 Pin 12p  |
| IN4002 7p  | 3 Pin 13p      |
| IN4003 9p  | 5 Pin 180° 15p |
| IN4004 9p  | Std. Jack 14p  |
| IN4005 12p | 2.5mm Jack 11p |
| IN4006 14p | Phono 5p       |
| IN914 7p   |                |
| IN914 7p   |                |
| BA100 10p  |                |
| OAS 42p    |                |
| OA47 9p    |                |
| OA81 11p   |                |
| OA200 8p   |                |

**ELECTROLYTIC CAPACITORS. Tubular & Large Cans**

(µF/V): 2-2/25, 2-2/63, 4-7/10, 4-7/25, 4-7/63, 22/10, 22/25, 22/63, 5p, 2/10, 10/10, 50/10, 100/10, 10/25, 50/25, 10/50, 5½p, 200/10, 100/25, 50/50, 6p, 500/10, 200/25, 100/50, 9p, 1000/10, 500/25, 200/50, 11p, 2000/10, 1000/25, 500/50, 16p, 1000/50, 39p, 1000/100, 66p, 2000/25, 27p, 2500/12, 17p, 2500/25, 33p, 2500/50, 62p, 3000/50, 72p, 5000/25, 66p, 5000/50, 94p, 7000/50, 60p, 25,000/25, 74p, Hi-VOLT: 8/350, 14p, 16/350, 19p, 32/350, 25p, 50/250, 18p 100/500, 33p.

**METALLISED PAPER CAPACITORS**

250V: 0-05µF, 0-1µF 4½p, 0-25µF, 5½p, 0-5µF, 6½p, 1µF, 9p, 500V: 0-025µF, 0-05µF, 4½p, 0-1µF, 5½p, 0-25µF, 6½p, 0-5µF, 9p, 1000V: 0-01µF, 10p, 0-022µF, 12p, 0-047µF, 0-1µF, 16p, 0-22µF, 31p, 0-47µF, 39p.

**QUANTITY DISCOUNT**  
SPECIAL BULK BUY PRICES  
ARE AVAILABLE BY  
QUOTATION FOR LARGE  
PROJECTS AND TRADE

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

**Z & I AERO SERVICES LTD.**

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 0-15 in £ for postage and handling  
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

THE MANAGEMENT ADVISES WITH REGRET THAT DUE TO RISING COSTS AND STAFF SHORTAGE THE MAIL ORDER SERVICE HAS TO BE CURTAILED. FROM 1ST JANUARY 1974 ALL MAIL ORDERS ACCOMPANIED BY REMITTANCE WILL BE SUBJECT TO A MINIMUM CHARGE OF £5-00 EXCLUDING V.A.T., I.E. £5-50 INCLUDING V.A.T. GOODS OF VALUE UNDER £5-00 WILL BE AVAILABLE ONLY TO PERSONAL CALLERS, EITHER AT OUR RETAIL BRANCH, 85, TOTTENHAM COURT ROAD, W1, OR TRADE COUNTER AT 44A WESTBOURNE GROVE, LONDON W2. MINIMUM ORDER CHARGE FOR APPROVED ACCOUNT CUSTOMERS IS £10-00 EXCLUSIVE OF V.A.T.

**TAUT SUSPENSION MULTIMETERS**

MADE IN USSR



8 models of multimeters from simple 22-range instrument priced at £4-95 to sophisticated 43-range instrument with full transistorised safety trip circuit, priced at £17-00. Models available with transistor testing facilities (U4341) and built-in audio/i.f. oscillator (U4323).

All the above instruments and full range of other test equipment are included in our new 1973/74 combined catalogue/price list which covers valves, semiconductor and passive components, basic specifications of semiconductors, cathode ray tubes, klystrons and magnetrons, as well as transistor substitution list.

# FREE!

## Over 150 ways to engineer a better future

**HIGHER PAY**      **A BETTER JOB**

**SECURITY**

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course" - Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects" - Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold" - Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T., Dept. BPW50 Aldermaston Court, Reading RG7 4PF.

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand - Gordon and Gotch (Asia) Ltd.; South Africa - Central News Agency Ltd. Publisher's subscription rate (including postage): for one year UK £3-25, Overseas £3-50. International Giro facilities Account No. 5122007. Please state reason for payment "message to page". **Practical Wireless** is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.** Everything you need to know

about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

|   |   |   |
|---|---|---|
| <b>MECHANICAL</b>   | <b>DRAUGHTSMANSHIP</b>  | <b>A.B.T. Clerk of Works</b>  |
| Society of Engineers—   | Institute of Engineers  | Construction  |
| A.M.S.E. (Mech.) <input type="checkbox"/>   | Designers (A.M.I.E.D.) <input type="checkbox"/>                 | Surveyors Institute—L.C.S.I. CITY & GUILDS                          |
| Institute of Engineers & Technicians (A.M.I.E.) <input type="checkbox"/>          | General Draughtsmanship <input type="checkbox"/>                | General Building (all branches)                                     |
| CITY & GUILDS <input type="checkbox"/>  | Elec. Draughtsmanship <input type="checkbox"/>                  | Heating & Vent. Inst. Clerk of Works                                |
| Gen. Mech. Eng. Maintenance Eng. <input type="checkbox"/>                         | Architectural Draughtsmanship <input type="checkbox"/>          | Site Surveying  |
| Welding <input type="checkbox"/>  | Technical Drawing <input type="checkbox"/>                      | Health Engineering  |
| Gen. Diesel Eng. Sheet Metal Work <input type="checkbox"/>                        | <b>RADIO &amp; TELE-COMMUNICATIONS</b>                          | Road Construction   |
| Eng. Inspection <input type="checkbox"/>  | CITY & GUILDS. Radio, TV, Electronics                           | Quantities, Estimates   |
| Eng. Metallurgy <input type="checkbox"/>  | CITY & GUILDS. Telecoms. <input type="checkbox"/>               | Hydraulics  |
| <b>ELECTRICAL &amp; ELECTRONIC</b>  | Gen. Radio & TV Eng. <input type="checkbox"/>                   | Structural Eng. <input type="checkbox"/>                            |
| Society of Engineers—   | Radio Amateurs Exam <input type="checkbox"/>                    | <b>GENERAL</b>  |
| A.M.S.E. (Elec.) CITY & GUILDS <input type="checkbox"/>                           | Radio Servicing <input type="checkbox"/>                        | Agricultural Eng. Council of Eng. <input type="checkbox"/>          |
| Gen. Electrical Engineering <input type="checkbox"/>                              | TV Servicing <input type="checkbox"/>                           | Conditions <input type="checkbox"/>                                 |
| Electrical Installations <input type="checkbox"/>                                 | Colour TV <input type="checkbox"/>                              | Farm Science <input type="checkbox"/>                               |
| Electrical Maths <input type="checkbox"/>   | <b>AUTOMOBILE &amp; AERONAUTICAL</b>                            | Plastics <input type="checkbox"/>                                   |
| Computer Electronics <input type="checkbox"/>                                     | Institute of the Motor Industry A.M.I.I. M.A./IMI CITY & GUILDS | Supplementary courses for Nat. Certificates.                        |
| Electronic Eng. Practical Radio & Electronics (with kit) <input type="checkbox"/> | Auto Eng. <input type="checkbox"/>                              |   |
| <b>MANAGEMENT &amp; PRODUCTION</b>  | Gen. Auto Eng. <input type="checkbox"/>                         | <b>G.C.E.</b>   |
| Institute of Cost & Management Accnts. <input type="checkbox"/>                   | Motor Mechanics <input type="checkbox"/>                        | - choose from 58 'O' & 'A' level subjects.                          |
| Computer Programming <input type="checkbox"/>                                     | Auto Diesel Eng. <input type="checkbox"/>                       |   |
| Works M'nt. <input type="checkbox"/>  | Garage M'nt. <input type="checkbox"/>                           |   |
| Work Study <input type="checkbox"/>   | ARB Aero Engineering Certs. <input type="checkbox"/>            |   |
| Gen. Production Eng. <input type="checkbox"/>                                     | Gen. Aero Eng. <input type="checkbox"/>                         |   |
| Estimating & Planning <input type="checkbox"/>                                    | <b>CONSTRUCTIONAL</b>   |   |
| Storekeeping <input type="checkbox"/>   | Society of Engineers—   |   |
| Management <input type="checkbox"/>   | A.M.S.E. (Civ.) <input type="checkbox"/>                        | Coaching for many exams, including C & G and assistance in ONC/HNC. |
| Skills <input type="checkbox"/>   | Institute of Building—L.I.O.B. <input type="checkbox"/>         |   |
| Quality Control <input type="checkbox"/>  |   |   |

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW50 Aldermaston Court, Reading RG7 4PF

NAME \_\_\_\_\_ QN \_\_\_\_\_ BPW50

Block Capitals Please ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by C.A.C.C. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

# Henry's

**DONT RELY ON YOUR MEMORY  
BUY NOW AT BARGAIN PRICES**

Order your latest Henry's Catalogue Price 55p post paid complete with Discount Vouchers

Henry's  
Catalogue



You pay less  
VAT with Henry's  
Low Prices

## BUILD THE TEXAN

**20 + 20 WATT IC  
STEREO AMPLIFIER**

As featured by  
Practical Wireless  
1972




Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6-IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES.** On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21

Kit price **£28.50** (+VAT +50p carr/packing) or built and tested **£35.00** (+VAT +50p carr/packing) as illustrated.
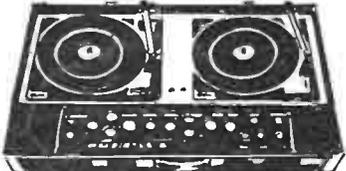
### EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

**DISCO MINI A** complete portable disco, fitted mixer/preamp, 2 decks all facilities. £98.50  
As above but with Slider Controls £118.50  
100 watt amplifier for above £42.50  
**SL100** 100 watt mixer/amplifier with slider controls. £69.00  
**RS50** 50 watt mixer/amplifier £49.50  
**R100** 100 watt mixer/amplifier £57.50  
**DISCO AMP** 100 watt mixer/amplifier chassis unit. £69.50  
**DISCO MIXER/PREAMPLIFIERS** (OP for up to 6-100 watt amplifiers)  
**SDL1** (rotary controls) £49.50  
**SDLII** (slider controls) £58.50  
**DISCO VOX** (slider controls) the complete disco preamp £69.50  
**DJ100** 100 watt power amplifier for above £42.50  
**DJ30L** 3 channel 3kw sound to light £31.50  
**DJ40L** as 30L plus built in microphone £41.95  
**DIMAMATIC** 1 kW adjustable speed auto dimmer £25.00  
**Carlsbro Reverberation Unit** £44.00  
**SCENE STROBE** £19.00. **ROAD STROBE** £25.00. **SUPER STROBE** £45.  
Disco anti-feedback microphone £11.95  
Colt 150 watt liquid wheel projector £22.50  
150 watt QI liquid wheel projector £50.00  
150 watt QI cassette wheel projector £50.00  
Spare Effects and liquid cassettes large range of patterns £6.00  
6 inch liquid wheels £5.00  
Mini spot bank fitted 3 lamps £12.95  
Auto Trillite (mini with flashers) £17.00  
Bubblemaster with 1 gall. liquid Mixers/Mics/Speakers/Lighting  
U.K.'s largest range of Disco Lighting, **FREE STOCK LIST REF. No. 18 ON REQUEST.**  
**AKG / RESLO / DJ / CARLSBRO / EAGLE MICS., STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURN-TABLES, PUBLIC ADDRESS COMPONENTS.**



All prices carr. paid (UK) (VAT EXTRA)  
Barleycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

### TEXAN STEREO SYSTEM PLUS PRICE SAVINGS



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems size 21" x 12" x 10" and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

**System 25** (list approx. £109) £79.50  
**System 76** (list approx. £117) £89.50  
(plus 10% VAT and plus £1.45 carr/packing)

Barleycard/Access, call, write or phone, your order 01 402 4736 EASY TERMS FOR CALLERS

#### NEW SINCLAIR PROJECT 80

Stereo Pre-Amplifier £11.95  
Audio Filter Unit £6.95  
Z40 15 Watt Amplifier £5.45  
Z60 25 Watt Amplifier £6.95  
PZ5 Mod. for 1 on 2 Z40 £4.98  
PZ6 Mod. (5 Tab) 1 on 2 Z40 £7.98  
PZ8 Mod. (5 Tab) 1 on 2 Z60 £7.98  
TRANSFORMER FOR PZ8 £2.95

**NEW FM TUNER** £11.95  
**STEREO DECODER** £7.45

All items post paid.  
Best price on request.

### BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 9" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe.



Kit price **£21.00** (+ VAT)  
or built and tested **£24.95** (+ VAT)

**LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S.**  
ALL POST PAID LESS THAN 1/4 REC. PRICES COMPLETE WITH LIBRARY CASES

|       |       |       |        |        |
|-------|-------|-------|--------|--------|
|       | 3 for | 6 for | 10 for | 25 for |
| C 60  | £1.00 | £1.80 | £2.80  | £6.75  |
| C 90  | £1.33 | £2.57 | £4.20  | £10.25 |
| C 120 | £1.62 | £3.15 | £5.00  | £12.25 |

Quantity and trade enquiries, invited



LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian £1.36 per course. £5 for any 4.

### LOW COST HI-FI SPEAKERS

**SPECIAL OFFERS**  
EMI 13" x 8"—full range speakers (post 20p each or 30p pair)  
\*150TC—8 ohms Twin Cone 10 watt £2.20 each or £4.00 pair.  
\*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms £3.50 each or £6.90 pair.  
EW 15 watt 8 ohms C/o Tweeter £4.30 each or £7.90 pair.  
350 20 watt C/o Tweeters 8 or 15 ohms £7.50 each or £14.00 pair.  
\* Polished wood cabinet £4.60 post 35p.



|   |                      |             |        |
|---|----------------------|-------------|--------|
| <b>8 ohms full range (post 20p)</b>           |                      |             |        |
| FR4   | 5 watt               |             | £4.00  |
| FR65  | 6 1/2" 10 watt       |             | £5.50  |
| FR8   | 8" 15 watt           |             | £7.60  |
| FR23  | 9 x 6" 15 watt       |             | £6.00  |
| <b>BASS &amp; MID RANGE—8 ohms (post 20p)</b> |                      |             |        |
| AA12  | 5" 15 watt           |             | £3.20  |
| B110  | 5 1/2" 15 watt       |             | £5.60  |
| B200  | 8" 15 watt           |             | £6.45  |
| B139/2  | 13" x 8" 30 watt LF  |             | £10.25 |
| <b>TWEETERS AND CROSSOVERS (post 20p)</b>     |                      |             |        |
| K2006   | 10 watt 8 or 15 ohms |             | £1.90  |
| FHT6  | 15 watt 8 ohms       |             | £3.75  |
| K2011   | 30 watt 8 ohms       |             | £4.25  |
| T27   | KEF                  |             | £4.90  |
| Accent 100                                    | 30 watt 8 ohms       |             | £2.00  |
| K4009   | 1kHz/5kHz C/o        |             | £2.00  |
| SN75  | 3kHz var. C/o        |             | £1.75  |
| <b>SPEAKER KITS (carr. etc. 35p)</b>          |                      |             |        |
| 20-2  | 8" 40 watt           | £10.00 each |        |
| 20-3  | 8" 40 watt           | £15.00 each |        |
| LINTON 2                                      | 20 watt              | £15.95 pair |        |
| GLENDALE 3                                    | 30 watt              | £28.95 pair |        |
| DOVEDALE 3                                    | 30 watt              | £42.00 pair |        |
| KEF KK2                                       | 50 watt              | £20.40 each |        |
| KEF KK3                                       |                      | £32.00 each |        |

### BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—thats the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs. Tangents. Sines etc.



**£24.95** Also available assembled ready to use. **£27.22** + VAT. + VAT.

10% VAT to be added to all orders. Prices and descriptions correct at time of press. E & OE.  
Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791.

See pages 818—820 of this magazine

**Henry's RADIO LIMITED**  
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
354-356 High Fidelity and Tape Equipment 01-402 5854 / 4736  
309 PA-Disco-Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW

Open 9am-6pm  
6 days a week  
All stores open all day Saturday

