

PRACTICAL WIRELESS

APRIL
1974

25p

Special offer



PLUS:

'QUICK-WIPE'
WINDSCREEN
WIPER DELAY
UNIT



the
'SLIMLINE'
5-Band
Receiver



Australia 50c
New Zealand 50c
South Africa 45c
Rhodesia 45c
Nigeria K40
Malaysia \$1.80
Sweden Kr 3.50
Malta 22c5
Norway Kr 5.10


ALSO:

Guide to the Multi-range Testmeter

look! electronics really mastered

... practical
... visual
... exciting!

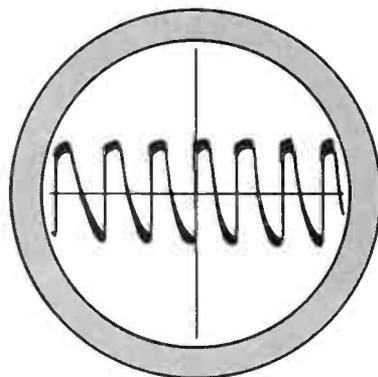no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

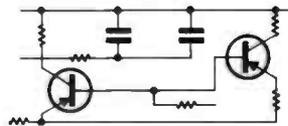2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL44

special free gift also to all our students

PRACTICAL WIRELESS

VOL. 49 NO. 12

ISSUE 806

APRIL 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR Morris A. Colwell

ASSISTANT EDITOR
Lionel E. Howes, G3AYA

ART EDITOR Peter Metalli

TECHNICAL EDITOR
Eric Dowdeswell, G4AR

**PRODUCTION & NEWS
EDITOR** Colin R. Riches

PROJECTS SUB-EDITOR
Geoffrey C. Arnold

TECHNICAL ARTIST
Alan Martin

SECRETARIAL Jenny Maunder
01-634 4292 Susan Corne

ADVERTS. MANAGER
01-634 4293 Roy Smith

CLASSIFIED ADVERTS.
01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £3.50 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". Binders (£1.34) and indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of *Practical Wireless* and *Television* only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

1142 SAFETY FIRST—Leader article and May preview

1143 NEWS . . . NEWS . . . NEWS . . .

1146 TELEVISION—Coming in the April issue

1167 NEXT MONTH IN PRACTICAL WIRELESS

1195 ON THE AIR

1195 Broadcast Short Wave—*Malcolm Connah*

1196 Medium Wave—*Charles Molloy*

1196 VHF/FM—*Simon David*

● CONSTRUCTIONAL

1144 THE "QUICKWIPE" variable time sweep windscreen wiper—
P. S. Collins

1154 EXPERIMENTAL WORKSHOP. Grounded Emitter Amplifiers—
M. J. Hughes, M.A.

1165 BATTERY CHARGER—AUTOMATIC 12V CAR BATTERY
CHARGER—*Richard Collin*

1168 'SLIMLINE' 5-band portable receiver—*F. G. Rayer*

1174 "P.W. CRATA" Cassette Recorder and Tuner Amplifier Part 2—
Richard Collin

● OTHER FEATURES

1146 TECHNICROSS No. 3—Solution

1147 GUIDE TO MULTI-RANGE TEST METERS—*H. Leeming, G3LLL*

1161 IMPEDANCE MATCHING—*C. Budd*

1180 OSCILLOSCOPE TECHNIQUES Part 2—*Alan C. Ainslie*

1191 SAFETY IN DOMESTIC ELECTRONICS

1192 OFF THE RECORD

● SPECIAL OFFER

1179 PRACTICAL WIRELESS TOOL KIT

HUGE DISCOUNTS

ON LEADING BRAND HI-FI

ALL R.S.C. PRICES INC VAT

★ FULL LABOUR AND MATERIAL GUARANTEES FOR 12 MONTHS

LOW DEPOSIT TERMS OVER 8 MONTHS

	List Price	RSC Price
WHARFEDALE DENTON	£39.93pr	£29.95
WHARFEDALE LINTON	£48.69pr	£35.95
LEAK 150	£46.82pr	£37.50

Prices shown correct at time of going to press 12.2.74

AKAI GXC 36D Tape Unit	£76.95 (Rec. Price £109.50)	Carr. £1
AKAI 4000DS Tape Unit	£76.95 (Rec. Price £109.50)	Carr. £1
AKAI 1721L Tape Unit	£79.95 (Rec. Price £114.50)	Carr. £1
AKAI GXC46D Tape Unit	£104.75 (Rec. Price £149.50)	Carr. £1
GOLDRING GL72 T/Table & P.U.	£29.95 (Rec. Price £37.29)	Carr. 75p
with Free Goldring G800 Cartridge worth over £10 fitted to above unit.		
GOLDRING GL75 T/Table & P.U.	£34.95 (Rec. Price £47.19)	Carr. 85p.
with Free Goldring G800 Cartridge worth over £10 fitted to above unit.		
BSR MP60 T/Table & P.U.	£9.95 (Rec. Price £14.95)	Carr. 40p
T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER		
GARRARD SP25 with G850	£16.95 SPECIAL PRICE	(Carr. £1)
MacDonald MP60 with G800	£17.95 SPECIAL PRICE	(Carr. £1)
GARRARD AP76 with G800	£28.95 SPECIAL PRICE	(Carr. £1)



A HIGH FIDELITY 30 + 30W STEREO SYSTEM

AUDIO FIDELITY MODEL 60 AMPLIFIER. PAIR AUDIO FIDELITY MARQUESS 30 SPKRS. McDONALD MP60 with G800 Cartridge. Total Value over £165 Ready wired on Plinth with Cover. Cabinet finished in Teak Veneer. Send S.A.E. for leaflet. Carr. £3

£99.95

HI-FI 10 + 10W STEREO SYSTEM


AUDIOTRINE STEREO 20 AMPLIFIER. GARRARD TURNTABLE with Sonotone Carr. ridge wired on Plinth with cover. PAIR DIPLOMAT 10W SPEAKERS. Teak Veneer finish.

£55

SPECIAL PURCHASE Wert


HI-FI SPEAKER ENCLOSURES

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 45p per enc.
 JE8 Size 16" x 11" x 9". Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. £5.50
 SE8 For optimum performance with any 8in. Hi-Fi speaker. £6.50
 Size 19 x 10 1/2 x 9in.
 SE10 For outstanding results with 10in. Hi-Fi speaker. Size 25 1/2 x 16 x 9in. Ported. £6.75
 SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter. £7.95
 Size 25 1/2 x 16 x 9in.

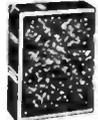

RSC G66 MkII 6.6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequencies range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250V. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS. OR FACTORY BUILT IN TEAK VENEER CABINET as illustrated £12.60 or dep. £2.12 and 8 monthly payments £2.12 (Total £19.98).

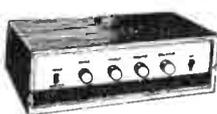

AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 16,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.
 Exceptional performance at low cost.
 HF808T 8" 10W £2.98 HF120D 12" 15W £5.50
 HF102D 10" 10W £3.30 HF126 12" 15W £6.85
 HF120 12" 15W £4.95 HF126D 12" 15W £6.85



FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is tilted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. £3.99
 PLEASE STATE IMPEDANCE REQUIRED List £4.99
 MODEL 803T 8" 10W with parasitic Tweeter. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15 Ω. £5.50 List £6.00



R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET. Only high grade components by leading manufacturers.
 • Push Button Selector Switching
 • Jack Socket for Headphones
 • Neon Indicator
 • Satin Silver Finish Metal Fascia
 • Solid State Circuitry
 • Twenty Silicon Transistors
 • Four Diodes, Four Rectifiers
 • Send S.A.E. for full descriptive leaflet.
 For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8 Ω. Frequency Response 7 Hz to 70 KHz ± 1 dB.



COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £22.50
 £5 extra. £42.50

R.S.C. STEREO FM III TUNER.

in cabinet. Visually matches Super 30 Mk. III £37.50

FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 8 monthly payments £5.17 (Total £48.36).

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED.

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in. 250v., 60mA, 6.3v. 2a. £1.10
 250v.-0-250v., 60mA 6.3v. 2a. £1.16

TOP SHROUDED DROP-THERO TYPE
 250-0-250v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.40
 250-0-250v. 100mA, 6.3v. 3.5a. £1.71
 250-0-250v. 100mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.75
 300-0-300v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.81
 250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.45
 300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.45
 300-0-300v. 130mA, 6.3v. 4a., c.t. 6.3v. 1a. £2.45
 Suitable for Mullard 510 Amplifier. £2.85
 350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.45
 300-0-300v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.85

FILAMENT or TRANSISTOR POWER PACK
 Types 6.3v. 1.5a. 55p; 6.3v. 2a. 60p; 6.3v. 3a. 85p; 6.3v. 6a. £1.45; 12v. 1a. 61p; 12v. 3a. or 24v. 1.5a. £1.50; 0.9-18v 1 1/2a. £1.25; 0.12-25-42v 2a. £1.95.

SELENIUM RECTIFIERS F.W. (Bridged) All 6/12. D.C. output. Max. A.C. Input 15v. 1a, 28p, 2a, 39p, 3a, 55p, 4a, 72p, 6a, 88p.
 CHARGER TRANSFORMERS 0.9-15v. 1 1/2a. £1.10, 2 1/2a. £1.25; 3a. £1.40; 5a. £1.60; 6a. £1.85; 8a. £2.20
 AUTO (Step UP/step DOWN) TRANSFORMERS 0.110/120v. 200-230-250v. 50-80 watts £1.25, 150 watts, £2.10 250 watts £3.00; 500 watts £6.40

OUTPUT TRANSFORMERS
 Push-Pull 8 watts EL84 to 3 Ω or 15 Ω. 95p
 Push-Pull 10 watts 6V6, ECL86 to 3-5-8-15 Ω. £1.55
 Push-Pull EL34 to 3 or 15 Ω 10-12 watts. £1.50
 Push-Pull Ultra Linear for Mullard 510, etc. £2.45
 Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω. £2.20
 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω. £3.65

SMOOTHING CHOKES
 150mA, 7-10H, 250 Ω 77p; 100mA, 10H, 200 Ω 66p; 80mA, 10H, 350 Ω 55p; 60mA, 10H, 400 Ω 28p.

RSC

DISCO SYSTEM


50 WATT SPEAKER

100 WATT AMPLIFIER

50 WATT SPEAKER



HEADPHONES MICROPHONE

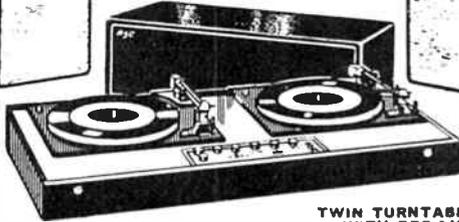

TWIN TURNTABLE WITH PRE-AMP

- Units listed below
- (a) 100w POWER AMPLIFIER
- (b) PAIR OF HI-FI HEADPHONES
- (c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
- (d) PAIR 50 WATT SPEAKERS
- (e) RSC TDI DISCO CONSOLE

RSC TDI DISCO CONSOLE

£149.95

Carr. £3-00

Terms Deposit £50 and 18 monthly payments of £7-06 (Total £177-08).

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonotone or Acos Cartridges with diamond stylus. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid. See illustration on left. Or Dep. £22.50 and 12 mthly pymts £4.50 (Total £277-98) Carr. £1-50

£69.95

R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

- All types 16 Ohms covered in Rexine and Vynair TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN
- TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback horn characteristic high flux 13" x 8" 20 watt £21.95
 - TERMS: Dep. £3-95 and 8 mthly payments £2-67 (Total £25-81) Carr. 65p
 - TYPE C818 60 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 34" x 14" x 11". Dep. £4-72 & 8 mthly pymts £32.72
 - TERMS: Dep. £4-15 (Total £37-92) Carr. 85p
 - TYPE C4100 100 WATTS Inc. four 12" 50 watt speakers for conservative ratings. Extra heavy construction. Size approx. 58" x 16" x 10". Acoustically filled and pressurised. Terms: Dep. £22-00 & 12 mthly. pytd. £4-29 (Total £78-48) Carr. £1-50

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.



- | 'POP' 100 | 'POP' 60 | 'POP' 50 |
|--|---|--|
| 18" 100Watt
14,000 gauss
8/15Ω | 15" 60 Watt
14,000 gauss
8/15Ω | 12" 50 Watt
13,000 gauss
15Ω |
| £27-50 | £15-75 | £12-75 |
| Dep. £3-50 and 8 mthly payments £3-50 (Total £31-50) | Dep. £2 and 8 mthly payments £2 (Total £18) | Dep. £1-71 and 8 mthly payments £1-71 (Total £15-29) |
- FOR BASS GUITAR, ELECT. ORGAN, ETC. PAIR SUITABLE ALL PURPOSES

'POP' 55 12" 60W £15.95

Gauss 15,000 Imp 8/15 Or Dep £2-45 and 8 monthly payments £2 (Total £18-45) Carr. Free

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT £8.75

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free or Dep. £1-15 and 8 mthly payments £1-15 (Total £10-35)

GROUP EQUIPMENT PACKAGE OFFERS

- | | | |
|---|--------|---------------|
| F.A.L. PHASE 60 MK.III AMPLIFIER | £89-98 | PACKAGE PRICE |
| PR. FANE POP 60 L/8 SPEAKERS | £17-50 | |
| TERMS: Deposit £17-32 and 12 monthly payments of £2-38 (Total £57-88) | £67-43 | £51-95 |
| F.A.L. PHASE 50 MK.III AMPLIFIER | £89-98 | PACKAGE PRICE |
| PR. FANE POP 60 L/8 SPEAKERS | £25-50 | |
| TERMS: Deposit £20 and 12 monthly payments of £3-90 (Total £66-80) | £65-43 | £59-99 |
| F.A.L. PHASE 50 AMPLIFIER | £39-93 | PACKAGE PRICE |
| PAIR L12/20 8PKRS (in Cabinets) | £26-30 | |
| TERMS: Deposit £20-00 and 12 monthly payments £3-90 (Total £66-80) | £66-23 | £59-99 |

ALL RSC PRICES INCLUDE VAT

INTEREST CHARGES REFUNDED on Credit Purchases settled in 3 months

FANE CRESCENDO SPEAKERS

Full range available at ALL BRANCHES

MINSTREL 8W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Main Volume Control: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: Deposit £3-95 and 8 monthly payments £2-39 (Total £23-07). Carr. free

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £9-93 & 8 monthly payments £4-31. Total £44-41. £39-93



RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.

For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £20-00 and 12 monthly payments £3-90 (Total £66-80). Carr. £1-50 SAE for leaflet [UK Mainland] ONLY £59-95



HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50 Or deposit £5-95 and 8 monthly payments of £4-72. Total £43-71 L12/20 12" 25 WATT 13,000 Gauss 8/15 ohms L12/10 10-15 Watt veneer finish cabinet 12" unit 8-15 ohm. Size approx. 14" x 14" x 9". Carr. 65p. Dep. £2-25 & 8 mthly pymts £1-04 (Total £10-67) £8-25

REGENT 50 AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating Loudspeaker unit either horizontal or vertical mounting. ★ Two extra heavy duty 12in. 50w Loudspeakers. ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or 'mikes'. Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £24-50 & 12 monthly payments of £4-68. (Total £68-68.) Carr. £2-50 £72-50



GP30 AMPLIFIER For Guitar, Vocal or Instrumental Group

A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £14-40 and 8 monthly payments of £3-09 (Total £29-12). Carr. 75p £25-85

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BMI. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces battery supplying 1.5v and 90v, to battery radio where A.C. mains 200/250v. 50c/s is available. Carr. 30p. £4-15

NOW SEVEN NEW BRANCHES BOLTON, COVENTRY, DONCASTER, STOCKPORT, SUNDERLAND, PRESTON and NOTTINGHAM



NEW LARGER PREMISES AT HULL, DARLINGTON, NEWCASTLE & DERBY

All items subject to availability. Prices correct at 12.2.74 E. & O.E.

HI-FI CENTRES LTD.

R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

- BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
- BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
- BIRMINGHAM 30/31, Great Western Arcade. Tel. 921-236 1279 (Closed Wed.)
- COVENTRY 17 Shelton Square, The Precinct. Derby 97 St. Peter's Street. (Closed Wed.). Tel. 41381
- DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

- DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.)
- EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
- GLASGOW 328 Argyle St. (Closed Tues.). Tel. 248 4158
- HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
- LEICESTER 32 High Street (Closed Thurs.). Tel. 58420
- LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252
- LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
- LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1829

- MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 238 2778
- MIDDLESBROUGH 106 Newport Rd. (Closed Wed.)
- NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21489
- NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48668
- PRESTON 41 Friargate Walk, St. Georges Shopp Prec SHEFFIELD 13 Exchange Street (Castle Mkt. Blds. (Closed Thurs.). Tel. 20716
- STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777
- SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone 6743

0A3	.40	81K7	.60	6L129	.55	12N37	.44	85A3	.60	ZAF42	.50	EP85	.34	HABC80.44	PENDD-	UF41	.70	AC107	.17	BA153	.17	OA73	.17	
0B2	.40	81B6	.60	6S7GT	.60	14N47	.65	85A3	1.00	ZAF801	.50	EP86	.30	H123DD.75	4020	UF42	.70	AC113	.28	BC107	.14	OA79	.10	
0Z4	.47	81H16	.70	6Q7G	.50	14H7	.55	90C1	.75	EB34	.25	EP89	.27	H14DD	PI.33	UF80	.50	AC126	.14	BC108	.14	OA81	.10	
1A3	.52	81J6	.50	6Q7GT	.50	19A05	.42	90C2	2.40	EB91	.15	EP91	.30	H14DD	PI.36	UF86	.55	AC127	.19	BC113	.28	OA85	.09	
1A6GT	.50	81K7A	.50	6Q7G(M)	.55	19G6	.50	150R2	.75	EB92	.50	EP92	.30	HN309	1.40	PI.81	.44	AC128	.22	BC116	.28	OA90	.14	
1A7GT	.65	81K7	.95	6R7G	.60	20D4	.70	2158C	.50	EB93	.50	EP97	.70	HVR2	.58	PL81A	.55	UF89	.38	AC132	.22	BC116	.28	
1B30T	.52	81R8	.85	6R7M	.75	20P2	.75	20T	.80	EB98	.30	EP98	.80	HVR2A	.58	PI.82	.37	UL41	.65	AC154	.28	BC118	.25	
1H6GT	.65	81B7	1.40	68A7	.44	20L1	.88	5702	.80	EB99	.50	EP18	.29	KT2	.50	PI.83	.39	UL44	.38	AC156	.22	BC110	.60	
1N4	.14	68B7C	.65	687GT	.33	25Z3	.30	5763	2.00	EBF89	.30	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
1R4	.38	68Z6	.49	68H17	.44	20P5	1.30	AC/PEN	.98	EC86	.59	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
1R6	.38	68C6A	.40	68K7C	.44	25A6G	.38	AC/PEN	.98	EC88	.59	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
1U4	.65	6C4	.28	68Q7GT	.38	25L6G	.50	DD	.98	EC92	.45	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
1U6	.90	6C9	1.25	6V6G	.17	25Y6G	.70	AC6PRN	.38	EC93	1.50	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
2B21	.48	6C106G	.80	6V6GT	.38	25Z4A	.38	ACTH1	.81	EC95	1.20	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
20K6	.53	6C10A	.75	6X4	.30	25Z3	.30	AL60	1.00	EC94	1.00	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
BA4	.42	6C116	.60	6X3GT	.28	25Z4A	.70	AT1	1.40	EC95	1.20	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
BD6	.19	6C16	.55	7B6	.75	20D7	1.00	AZ1	.60	EC98	.28	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
3Q4	.49	6C17	.75	7B7	.50	30A5	.65	AZ31	.60	EC98	.28	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
3Q5GT	.55	6C17G	.75	7B7	.75	30C16	.75	AZ41	.65	EC98	.28	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
3R4	.33	6C17A	.70	7B7	1.50	30C17	.90	CL33	1.50	EC98	.28	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
40R6	.55	6D7	.75	7Y4	.65	30C18	.73	CY1C	1.00	EC98	.28	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
40R8	.60	6D7A	.75	7Z4	.80	30P5	.33	CY31	.45	EM10A	.42	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
5R4G	.70	6E16	.75	9D7	.65	30P1	.75	DAF91	.30	EC189	.55	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
5U40	.30	6E5	1.00	10C2	.65	30F12	.75	DAF96	.44	EC80A	.60	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
5V40	.54	6F1	.70	10DE7	.55	30F12.10	.60	DF91	.30	EC804	.60	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
6Y30T	.38	6F61	.50	10F1	.50	30F13	.55	DF96	.44	ECF80	.34	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
5Z3	.53	6F13	.55	10F9	.65	30F14	.85	DH63	.50	ECF82	.34	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
6Z40	.35	6F14	.75	10F18	.55	30L15	.75	DH76	.45	ECF86	.75	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
6Z40T	.35	6F18	.55	10F11	.70	30L17	.70	DH40	.70	ECF80	.60	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55	
6Z80L2	.60	6F23	.85	10P13	.70	30P4MR	.80	DR92	.70	2.10	EZ40	.55	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55
6AR0	1.25	6P24	.85	10P14	2.00	1.00	DK96	.55	ECH21	1.50	EZ41	.50	EP184	.32	KT41	.98	PI.84	.38	UM80	.44	AC157	.28	BC112	.55
6AC7	.49	6P22	1.00	12AG	1.00	30P12	.80	DL92	.33	ECH35	.65	EZ80	.24	.55	UCC86	.75	2N3709	.22	BA130	.11	OA70	.17		
6AG5	.27	6P28	.70	12AG	.60	30P19	.75	DL96	.44	ECH42	.70	EZ81	.25	.65	PCL96	1.47	UCF80	.65	2N3988	.55				
6AH6	.50	6F32	.65	12AD6	.65	30P14	.75	DM70	.44	ECH81	.30	GY501	.75	.25	PI800	1.44	UCF21	.65	2N323	.55				
6AJ3	.75	6H19A	.75	12AE6	.65	30P11	.88	DM71	2.00	ECH83	.44	GZ32	.54	.65	PN445	.80	UCH43	.65	AA119	.17				
6AK5	.34	6H26	.65	12AF6	.35	30P17	.75	DY87	.20	EC26	.44	GZ33	1.00	.65	PN446	.30	UCH81	.35	AA130	.17				
6AL6	.60	6H17	.75	12AG	.45	30P14	.80	DY82	.33	ECH80	.40	GZ34	.57	.65	PN453DD	UCF82	.88	AA129	.17					
6AM8A	.65	6H6GT	.18	12AV6	.40	30P15	.85	EB00C1	1.65	ECL82	.34	GZ37	.67	2.00	UC183	.60	AAZ13	.20						
6AN8	.49	6J5GT	.32	12BAG	.30	35A3	.85	EB00P	1.20	ECL83	.57													
6AQ6	.40	6J6	.25	12BEG	.38	35C5	.75	EB3F	1.20	ECL84	.60													
6AR5	.55	6J7	.30	12BH7	.27	35L6G	.55	EB80C	.80	ECL85	.60													
6AN7	1.00	6J7A	.75	12E1	3.00	35W4	.33	EB92C	1.00	ECL86	.40													
6AT6	.35	6K7G	.19	12JGT	.55	35Z4T	.45	EB10V	1.00	EP22	1.50													
6AU6	.30	6K8	.85	12K5	.65	35Z54T1	.60	EB2CC1	.60	EF40	.40													
6AV6	.33	6L1	2.00	12K7GT	.38	50B5	.85	EB148	.53	EF41	.70													
6AW8A	.65	6L8GT	.58	12Q7GT	.45	50C5	.45	EA50	.27	EF42	.55													
6AX4	.55	6L7	2.00	12MGT	.50	50C16D	1.25	E476	1.00	EP73	1.50													
6BR0	.30	6L18	.49	12MGT	.38	60E16	.55	E4HC00	.30	EP80	.28													
6HA6	.28	6L19	2.00	12H17	.35	60L6GT	.65	E4C91	.75	EP93	.40													

VALVES ALSO REQUIRED FOR CASH. LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.
All goods are untested and subject to the standard 90 day guarantee. Cash or cheque with order only. Despatch charges: Orders below £5, add 10p per order up to three items, each additional item 3p extra. Orders between £5 and £20 add 25p total. Orders over £20 are post free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p order extra. Terms of business free on request.
Business hours Mon.-Fri. 9-5.30 p.m. Closed 1-2 p.m. and Sat. We do not handle seconds or rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply. ALL PRICES VALID UNTIL 5.4.74.



ERNIE



MINICOMP 100



MINICOMP 1000

LEARN THE DIGITAL COMPUTER LOGIC TECHNIQUES

NEW! SUPERBLY IMPROVED

Build something completely out of the ordinary: Build the fascinating MINICOMP the miniaturised ERNIE.

The MINICOMP employs sophisticated LOGIC techniques and brilliant NIXIE tubes to display truly RANDOM NUMBERS. At the mere touch of a button the neon numbers "WHIP" round spectacularly at high speed, before a random number within a pre-set range is selected and displayed.

MINICOMP 100
Includes four range selections within 00-99.
* DICE: 1-6 * ROULETTE: 00-36 * POOLS: 00-99 * BINGO: 00-99
Kit includes 7 latest LOGIC I.C.'s, 3 transistors, 2 NIXIES, fibreglass P.C. board, the power supply and various other components.

MINICOMP 1000
After tremendous popularity of MINICOMP 100 we are now pleased to introduce MINICOMP 1000, which has all the original features of MINICOMP 100 but in addition it provides two higher ranges:
* QUARTO: 000-399 * KILO: 000-999
Kit includes 9 latest LOGIC I.C.'s, 3 transistors, 3 NIXIES, 2 P.C. boards, the power supply and various other components.

The MINICOMP is extremely easy to build as the P.C. boards are supplied with I.C.'s fully assembled and tested. The illustrated instructions include an introduction to the LOGIC techniques employed in the MINICOMP. Attractive blue or red NYLON coated and elegantly sized case, approx. 7", 4", 3" and silk aluminium panel.

APPLICATIONS: The MINICOMP simulates electronically all phenomena in nature or activity in daily life with random occurrence. RANDOM PULSE TRAINS are found useful in medical and statistical research. Digital LOGIC makes possible a modern and exciting means of playing any number of NUMBER GAMES the human mind can conjure up.
A PROFOUND ATTRACTION FOR PARTY GAMES, FETES, RAFFLE AND POOLS DRAWS. A purely random selection of the draws could well contribute to your winning combination.

U.K. PRICES: Overseas and quantity prices on request.
240V, 50 HZ. OR 110V, 60 HZ. mains operated
MINICOMP100, KIT: £39.50 Built & Guaranteed Units: £42.50 | All prices in-
MINICOMP1000, KIT: £49.50 : £53.50 | clude V.A.T.
TERMS: C.W.O. or C.O.D., MAIL ORDER ONLY. : and P&P.
* Patent applied for.

MICROELECTRONICS MICRO
51 Mexfield Road, London SW15 2RG. Tel: 01-870 2368

Why pay more - look at our Fantastic Bargain Offer!

THE AVON AUDIO SYSTEM



The uncabineted system is ideal as an economical replacement for an outdated chassis. Stereo Amplifier for Stereo/Mono record reproduction. Tuner with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

LATEST BSR STEREO/MONO RECORD CHANGER plays all types of 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKERS These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £35.00. Credit Terms £3.50 deposit plus £2 Post & Packing followed by 9 payments of £4.10 (Total Credit Terms £44.40) Don't miss this bargain.

SEND £5.50 TODAY

ALL EQUIPMENT COVERED BY OUR 12 MONTHS FULL GUARANTEE


CALLERS WELCOME

LEWIS radio PW 4/74
100 Chase Side, Southgate, London N14 5PL
Tel: 01-886 3733/9666



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

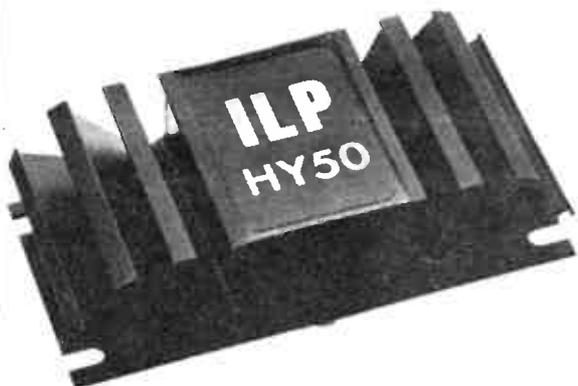

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy, sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of 'King-size' cigarettes.


Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

OUTPUT POWER:	SPEC.
LOAD IMPEDANCE:	25 watts RMS, 50 watts peak music power
INPUT SENSITIVITY:	4-16 Ω into 8 Ω
INPUT IMPEDANCE:	0db (0-775 volts RMS)
TOTAL HARMONIC DISTORTION:	47K Ω
SIGNAL/NOISE RATIO:	Less than 0-1% at 25 watts typically 0-05 better than 75db
FREQUENCY RESPONSE:	10Hz-50KHz \pm 1db
SUPPLY VOLTAGE:	\pm 25 volts
SIZE:	105 x 50 x 25 mm

Price £5-80 mono, £11-60 stereo

Price inclusive of VAT & P & P

NEW HY5 PRE-AMPLIFIER

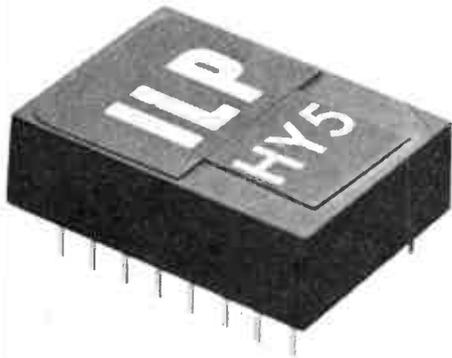

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids. Like the HY50, the new HY5 has no external components & has been redesigned to run off a split power-line with improvements in signal/noise, overload, capability & reduced distortion. The output has been increased to match the power module (Odb), and to share the same power supply. Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 & power supply only potentiometers are required to complete a simple mono amplifier with input & output facilities expected to be found on HI-FI amplifiers. The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

INPUTS	SPEC.
Magnetic Pick-up 3mV (within 1db RIAA curve)	
Ceramic Pick-up up to 3mV	
Microphone 10mV	
Tuner 250mV	
Auxiliary 3-100mV	
Input impedance 47k Ω 1kHz	

OUTPUTS
Tape 100mV.
Main output, 0db (0-775volts)

ACTIVE TONE CONTROLS

Treble \pm 12db at 10kHz

Bass \pm 12db at 100Hz

OVERLOAD CAPABILITY (equalization stage) 40db on most sensitive input

OUTPUT NOISE LEVEL (below 10mV magnetic input) 68db


DISTORTION 0-05% at 1kHz

SUPPLY VOLTAGE \pm 16-25 volts

SUPPLY CURRENT 15mA

Price £4-85 mono, £9-70 stereo

Price inclusive of VAT & P & P

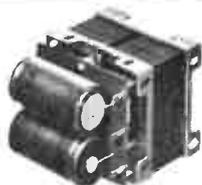

POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 2½ inches high and can be used for either mono or stereo systems.

SPEC.
OUTPUT VOLTAGE \pm 25 volts
INPUT VOLTAGE 210-240 volts
SIZE L. 70, D. 90, H. 60 mm

Price £5-23

Price inclusive of VAT & P & P

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS
 IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS
 You need a catalogue! 55p post paid complete with Discount Vouchers



UK's
**LARGEST RANGE
 OF KITS &
 GADGETS**



TEST EQUIPMENT

MULTIMETERS

- (carr. etc. 30p)
- M210 (Case £1.25) 20K/Volt Slimline 6 75
 - TLH33D 2K/Volt Robust 7 50
 - U437 10K/Volt Steel case. AC up to 40 KHz 4 95
 - U4324 20K/Volt with AC current ranges 8 90
 - AF105 (Case £1.90) 50K/Volt 11 95
 - U4313 20K/Volt AC current. Steel case 10 50
 - U4341 Plus Built in translator tester 10 50
 - Model 500 (Case £1.95) 30K/Volt 9 95

OTHER EQUIPMENT

- SE250B Pocket Signal Injector 2-10 carr. 15p
- SE500 Pocket Signal Tracer 1 70 carr. 15p
- TE15 Grid Dip meter 440kHz-280MHz 15-00 carr. 30p
- TE40 AC Millivoltmeter 1-2mHz 19 75 carr. 35p
- TE65 28 Range valve voltmeter 22 50 carr. 40p
- TE20D 120kHz-500mHz RF Generator 18 95 carr. 40p
- TE22D 20Hz-200kHz Audio Generator 19 95 carr. 40p
- SE350A Deluxe Signal Tracer 12 50 carr. 20p
- SE400 Volts/ohms/R-C aub./RF field/RF gen. 14 75 carr. 20p

New Revolutionary Supertester 680R

- | 680R Multi-Tester | Accessories |
|-------------------|----------------------------|
| £18 50 | Transistor tester 11 00 |
| | Electronic voltmeter 18 00 |
| | Amp clamp 11 95 |
| | Temperature probe 11 95 |
| | Gauss meter 11 95 |
| | Signal Injector 5 95 |
| | Phase Sequence 5 95 |
| | EHT Probe 3 95 |
| | Shunts 25/50/100A 4 50 |

A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester 8 50 p & p 15p
- C4002 Photoelectric System 13 70
- E1310 Stereo mag. cart. preamp. 4 80 p & p 25p
- Eaaphone D1201 telephone amplifier 7 50 p & p 25p
- D1203 Tcleamp. with PU coil 4 95 p & p 20p
- LL1 Door Intercomm. and chima 8 40 p & p 25p
- 1 Kw Dimmer/controller 3 00 p & p 10p
- 9" Twin spring unit For 3 30 p & p 15p
- 15" Twin spring unit Reverb 8 85 p & p 25p
- US50 Ultrasonic Switch Transmitter/Receiver 312 75
- C3041 1-250 MHz 42 25
- C3043 5CH 1-300 MHz 43 75
- VHF 105 Aircraft Band Converter 4 50 p & p 15p
- B2005 4 Ch. mic. mixer 4 20 p & p 15p
- B2004 2 ch. Stereo mixer 8 75 p & p 15p
- PK3 Kit. Etch your own printed circuits 41 95 p & p 20p

EXCLUSIVE: SPECIAL OFFERS

- MW/LW CAR RADIO AKAI GX40 + or - Earth with speaker Stereo cassette recorder, and fixings. £8 50 carr./pack, 50p. Pair Akai ADM microphones. £8 95 carr./pack, 20p.
- 8 TRACK CAR STEREO (- Earth) with speakers in Pods & fixings. £12 50 carr./pack, 40p.
- Portable Battery Cassette Tape Player £7 25.
- Car Lighter Plug and adaptor for all cassette and radio 6 7 1/2 volt output (state width) £1 95 each
- Rotel Stereophones RM630 £4 50 RM700 £8 75 RM430 £3 30
- Rotel RA310 15+15 watt Stereo Amplifier (List £52 00) £34 52.
- Weln W500 Battery/Mainst Cassette Recorder £12 75
- AKAI GX40 Stereo cassette recorder. £58 95 carr./pack, 50p.
- Pair Akai ADM microphones. £8 95 carr./pack, 20p.
- PORTABLE CASSETTE TAPE PLAYER— for car or carry around. £7 25 carr./pack, 20p.
- HANIMAX BC808 POCKET CALCULATOR WITH % KEY. £28 95.
- HANIMAX BC811M MEMORY VERSION £37 50
- MAINS UNIT for BC808, BC811M £2 85 (state model)
- HANIMAX H101 STEREO COMPACT RECORD PLAYER 2 x 7 watts Complete with Speakers (List £54 50) Price £39 95 Plus free pair of stereo phones.

SPECIAL PURCHASES


UHF TV TUNERS CHANNELS 21 TO 64

Brand new transistorised geared tuners for 625 Line Receiver IF output. £2 50. Post 20p.



EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

- | Model No. | Description | Price |
|-----------|---|-------|
| 310 | Radio control receiver | 2 98 |
| 300 | 4-channel R/C transmitter | 5 95 |
| 345 | Superhet R/C receiver | 5 95 |
| 455 | AM signal generator | 12 33 |
| 65 | Simple transistor tester | 1 40 |
| 115 | 8 watt Amplifier | 3 90 |
| 120 | 12 watt amplifier | 4 70 |
| 125 | Stereo control unit | 5 70 |
| 130 | Mono control unit | 3 60 |
| 605 | Power supply for 115 | 4 55 |
| 610 | Power supply for 120 | 4 55 |
| 615 | Power supply for 2 x 120 | 5 73 |
| 230 | AM/FM aerial amplifier | 2 83 |
| 240 | Auto packing light | 5 90 |
| 275 | Mic. preamplifier | 6 08 |
| 575 | LF generator 10Hz-1mHz | 15 80 |
| 575 | Sq. wave generator 20Hz-20KHz | 14 50 |
| 590 | SWR meter | 12 85 |
| 620 | NI-CAD Charger 1-2-12v | 8 00 |
| 630 | STAB Power supply 6-12v 0 25-0 1A | 8 15 |
| 690 | DC motor speed Gov. | 2 87 |
| 700 | Electronic Chaffinch | 7 00 |
| 705 | Windscreen wiper timer | 10 75 |
| 760 | Acoustic switch | 10 75 |
| 780 | Metal Detector (electronics only) | 9 65 |
| 790 | Capacitive Burglar alarm | 6 85 |
| 835 | Guitar preamp. | 4 25 |
| 840 | Delay car alarm | 6 15 |
| 875 | C.A.P. Discharge ignition for car engine (-V Earth) | 13 15 |
| 80 | Scope Calibrator | 2 25 |
| 255 | Level Indicator | 6 15 |
| 525 | 120-180mHz VHF timer | 11 30 |
| 715 | Photo cell switch | 7 70 |
| 795 | Electronic continuity tester | 4 30 |
| 860 | Photo timer | 7 15 |
| 871 | Slide projector auto feed control | 13 25 |
| 235 | Acoustic Alarm for driver | 14 60 |
| 465 | Quartz XTAL checker | 8 75 |
| 220 | Signal injector | 2 30 |
| 390 | VOX | 15 50 |
| 432 | Teatalk | 18 30 |
| 670 | Buffer Battery Charger | 6 55 |
| 885 | Capacitive Contact Alarm | 6 55 |
| 850 | Electronic Keyar | 18 75 |
| 820 | Electronic Digital Clock | 58 50 |

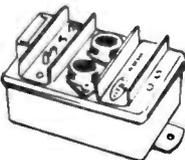

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY

Prices correct at time of preparation. Subject to change without notice.

BUILD THIS TUNER

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrita aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4 85. carr. 15p.

MULTI-USE & RADIONIC KITS

- | | | |
|-------|------------------------|-------|
| 10-1 | 10 Projects | 3 90 |
| 50-1 | 10 Projects | 6 00 |
| 150-1 | 150 Projects | 13 20 |
| | Telephone Communicator | 7 28 |
| X20 | 20 (Etc.) Projects | 4 95 |
| X40 | 40 (radio) Projects | 8 45 |
- (carr./packing 40p)

BUILD THIS RADIO

Portable MW / LW radio kit using Mullard RF/IF module. Features MW — bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7 99 (battery 22p). carr. etc. 32p.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/Eraser heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9 50 carr. 30p

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post. etc. 15p any quantity).

Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K. 1 Meg. 45p each.

Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 500K each. (Quantity discounts available)

Complete with knobs.

MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO '17' High Impedance £2 00

'18' Med. Impedance £2 00

R730/E73 2 track mono Record/Eraser low imp. 75p pair.

Eraser Heads for '17' and '18' 75p

'63' 2 track mono. HI Imp. £1 75


'43' Eraser Head for '63' 75p

(Post. etc. 15p any quantity).

SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

- AMPLIFIERS (carr., etc. 20p)
- 4-300, 0-3 watt 9 volt 1 75
 - 104, 1 watt 9 volt 3 10
 - 304, 3 watt 9 volt 3 95
 - 555, 3 watt 12 volt 4 10
 - E1208, 5 watt 12 volt 5 10
 - 608, 10 watt 24 volt 4 95
 - 410, 10 watt 28 volt 4 95
 - E1206, 30 watt 45 volt 9 95
 - E1210, 2 1/2 + 2 1/2 watts 12 volt 7 75
 - RE500, 5 watt IC mains operated Amplifier with controls 6 30
 - SAC14, 7 + 7 watt 11 75
 - SAC14 with controls 11 75
 - SAC13, 15 + 15 watt Stereo with controls 14 95
 - SP405 2Z40/Stereo 80/PZ6 30 45
 - SP406 2Z60/Stereo 80/PZ8 30 45
 - Transformer PZ8 3 95
- New SINCLAIR PROJECT 80
- Stereo Preamp. 11 95
 - Audio Filter Unit 6 95
 - Z40 15 Watt Amp. 3 45
 - Z60 25 Watt Amp. 6 95
 - PZ5 Mod. for 1 on 2 Z40 4 98
 - PZ6 Mod. (S Tab) 7 98
 - 1 on 2 Z40 (S Tab) 7 98
 - 1 on 2 Z60 (S Tab) 7 98
 - TRANSFORMER FOR PZ8 3 95
 - Project 605 Kit 18 95
 - Project 805 28 95

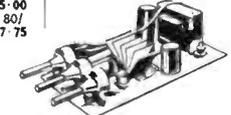- SP405 2Z40/Stereo 80/PZ5 25 00
- SP406 2Z40/Stereo 80/PZ6 27 75



POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
- 470C 6 7 1/2 volt 300 mA (Includes Multi-Adaptor for Tape Recorders, etc.) 2 15 post 20p
 - Car Lighter Voltage Adaptors 300mA (State voltage 8v, 7 1/2v, 9v) 1 95 ea. post 25p
 - SC202 3/6 7 1/2 volt 400mA 3 35 carr. 30p
 - HC244R Stabilised version 4 35 carr. 30p
 - P500 9 volt 500mA 2 90 post 20p
 - P11 24 volt 500mA (chassis) 2 90 post 20p
 - P15 26/28 volt 1 amp (chassis) 2 90 post 20p
 - P1080 12v 1 amp (chassis) 4 50 post 20p
 - P1081 45v 0 9 amp (chassis) 7 15 post 20p
 - P12 44-12 volt 0 4-1 amp 7 15 post 30p
 - SE101 A 3 1/6/12 volt 1 amp (Stab.) 10 30 post 25p
 - RP164 8 1/2/12 1 amp (Stab.) 12 95 post 30p

FIBRE OPTICS

- 0 01 Diam. Mono Filament £3 00 per 50 metre reel
- 0 13 Diam. 64 Fibres Sheathed. £1 00 per metre
- SPRAYS 15mm Diam. (Mares Tall Spray £10 50 7mm. Diam. £5 00)



All types offered subject to availability. Prices correct at time of press E & OF 10% VAT to be ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.

Henry's

RADIO LIMITED

SEE FACING PAGE FOR ADDRESSES

EDGWARE ROAD, W2

FREE BOOKLET

All types of
TRANSISTORS — RECTIFIERS
BRIDGES—SCR'S—TRIACS
INTEGRATED CIRCUITS
F.E.T.—LIGHT DEVICES

OVER 1500 DIFFERENT DEVICES
ENTIRELY NEW EDITION
SEND FOR YOUR FREE COPY TODAY



More Devices
New Prices
New Ranges

This is a must for all

Semi-conductor Users
(ask for booklet No. 36)

INTEGRATED CIRCUITS VERY IMPORTANT. ONLY branded I.C.'s

ALL others are not. Henry's sell only branded Integrated Circuits... From TEXAS... I.T.T. ... FAIRCHILD ... SIGNETICS. So why buy alternatives or under spec. devices when you can purchase the genuine article from us—ex stock... need we say more!



Type	1/11	12/29	30/99	Type	1/11	12/29	30/99	Type	1/11	12/29	30/99
8N7400N	0.20	0.18	0.16	8N7448N	1.50	1.27	1.13	8N74142N	2.85	2.88	2.82
8N7401N	0.20	0.18	0.16	8N7450N	0.20	0.18	0.16	8N74145N	1.44	1.44	1.26
8N7401AN	0.38	0.38	0.33	8N7451N	0.20	0.18	0.16	8N74147N	2.30	2.30	1.83
8N7402N	0.20	0.18	0.16	8N7453N	0.20	0.18	0.16	8N74148N	2.01	2.01	1.83
8N7403N	0.20	0.18	0.16	8N7454N	0.20	0.18	0.16	8N74150N	2.30	2.30	2.01
8N7403AN	0.38	0.38	0.33	8N7460N	0.20	0.18	0.16	8N74151N	1.15	1.15	1.00
8N7404N	0.24	0.21	0.18	8N7470N	0.25	0.20	0.27	8N74153N	1.09	1.09	0.92
8N7405N	0.20	0.18	0.16	8N7472N	0.38	0.38	0.34	8N74164N	2.30	2.30	2.01
8N7405AN	0.44	0.44	0.38	8N7473N	0.44	0.41	0.37	8N74165N	1.15	1.15	1.00
8N7406N	0.40	0.38	0.35	8N7474N	0.48	0.48	0.42	8N74156N	1.09	1.09	1.00
8N7407N	0.40	0.38	0.35	8N7475N	0.59	0.55	0.51	8N74157N	1.09	1.09	0.95
8N7408N	0.25	0.22	0.19	8N7476N	0.45	0.38	0.32	8N74159N	2.44	2.44	2.14
8N7409N	0.32	0.32	0.28	8N7480N	0.80	0.70	0.60	8N74160N	1.58	1.58	1.38
8N7409AN	0.44	0.41	0.35	8N7482N	0.87	0.80	0.72	8N74162N	1.58	1.58	1.38
8N7410N	0.20	0.18	0.16	8N7483N	1.20	1.10	1.00	8N74163N	1.68	1.68	1.38
8N7411N	0.25	0.23	0.21	8N7485N	1.87	1.87	1.63	8N74164N	2.01	2.01	1.76
8N7412N	0.28	0.28	0.25	8N7486N	0.50	0.50	0.44	8N74165N	2.01	2.01	1.76
8N7412AN	0.38	0.38	0.33	8N7489N	4.32	4.32	3.78	8N74166N	2.16	2.16	1.89
8N7413N	0.30	0.27	0.25	8N7490N	0.75	0.70	0.63	8N74167N	4.10	4.10	3.59
8N7414N	0.72	0.72	0.63	8N7493N	0.75	0.70	0.63	8N74170N	2.35	2.35	2.32
8N7415N	0.30	0.27	0.25	8N7492N	0.75	0.70	0.63	8N74172N	5.76	5.76	5.04
8N7417N	0.30	0.27	0.25	8N7493N	0.75	0.70	0.63	8N74173N	1.68	1.68	1.45
8N7422N	0.28	0.28	0.25	8N7494N	0.85	0.80	0.75	8N74174N	1.80	1.80	1.57
8N7422AN	0.38	0.38	0.33	8N7495N	0.85	0.80	0.75	8N74176N	1.29	1.29	1.13
8N7423N	0.37	0.34	0.32	8N7496N	1.00	0.90	0.83	8N74177N	1.44	1.44	1.26
8N7425N	0.37	0.37	0.32	8N74100N	0.16	0.16	0.16	8N74177N	1.44	1.44	1.26
8N7427N	0.37	0.37	0.32	8N74104N	0.60	0.53	0.45	8N74180N	1.58	1.58	1.38
8N7428N	0.43	0.43	0.37	8N74105N	0.60	0.53	0.45	8N74181N	5.18	5.18	4.53
8N7430N	0.20	0.18	0.16	8N74107N	0.51	0.51	0.45	8N74182N	1.44	1.44	1.26
8N7432N	0.37	0.37	0.32	8N74110N	0.57	0.57	0.50	8N74184N	2.16	2.16	1.89
8N7433N	0.43	0.43	0.38	8N74111N	0.86	0.86	0.75	8N74185AN			
8N7433AN	0.57	0.57	0.50	8N74116N	2.16	2.16	1.89				
8N7437N	0.43	0.42	0.37	8N74188N	1.00	0.90	0.83	8N74188N	4.48	4.48	3.87
8N7438N	0.43	0.43	0.37	8N74192N	0.30	0.30	0.21	8N74190N	2.30	2.30	2.01
8N7438AN	0.57	0.57	0.50	8N74192N	1.05	1.05	0.92	8N74191N	2.30	2.30	2.01
8N7440N	0.20	0.18	0.16	8N74121N	0.57	0.57	0.50	8N74192N	2.30	2.30	2.01
8N7441AN	0.85	0.79	0.73	8N74122N	0.80	0.80	0.70	8N74193N	2.30	2.30	2.01
8N7442N	0.85	0.79	0.73	8N74123N	1.44	1.44	1.26	8N74194N	1.72	1.72	1.51
8N7443N	1.50	1.27	1.13	8N74125N	0.60	0.60	0.60	8N74195N	1.44	1.44	1.26
8N7444AN	1.50	1.27	1.13	8N74126N	0.60	0.60	0.60	8N74196N	1.58	1.58	1.38
8N7445N	2.16	2.16	1.89	8N74132N	0.72	0.72	0.63	8N74197N	1.58	1.58	1.38
8N7446N	2.16	2.16	1.89	8N74136N	0.83	0.83	0.55	8N74198N	3.16	3.16	2.77
8N7447AN	1.80	1.80	1.57	8N74141N	1.00	0.90	0.80	8N74199N	2.88	2.88	2.82

LARGER QUANTITY AND O.E.M. PRICES PHONE (01) 723 3646. PRICING OF 8N7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX. 8N74... HIGH POWER... 8N74... LOW POWER SERIES IN STOCK... SEND FOR LIST 36, FREE ON REQUEST. LOW PROFILE SOCKETS 14 PIN... 15p 16 PIN... 17p 8 PIN... 14p

TRANSISTORS 16 SELECTION FOR FULL LIST SEND FOR BOOKLET 36 TODAY

AAZ13 10p	BC182 12p	BYZ13 35p	OC36 85p	ZTX108 10p	2N3714 1.60
AC107 35p	BCY32 85p	CI06D 55p	OC44 18p	ZTX300 14p	2N3771 1.75
AC128 20p	BCY39 1.00	GET111	OC45 18p	ZTX302 18p	2N3773 2.25
AC137 20p	BCY65 2.50		OC71 15p	ZTX500 15p	2N3790 2.25
ACY17 35p	BCY70 15p	GET115 75p	OC72 25p	2N391 40p	2N3819 3.50
ACY39 85p	BCV71 20p	GET880 55p	OC77 55p	2N807 15p	2N3827 1.50
AD149 50p	BCY72 13p	LM309K	OC81 28p	2N706 10p	2N3903 75p
AD161 39p	BD124 80p		OC83 25p	2N930 20p	2N4002 14p
AD162 39p	BD131 45p	MAT121 25p	OC140 85p	2N987 45p	2N4126 15p
AF117 20p	BF115 22p	MJE340 50p	OC170 25p	2N1132 25p	2N4871 35p
AF118 50p	BF164 25p	MJE520 65p	OC200 55p	2N1304 22p	2N5457 36p
AF139 35p	BF194 13p	MJE305 20p	OC202 90p	2N161 20p	2N5686 8.00
AF186 40p	BFX13 25p		OC217 1.00	2N1671 1.00	2N8206 9.00
AF239 44p	BFX34 55p	MFF105 46p	ORF12 55p	2N2147 75p	2N8303 70p
AFY27 30p	BFX88 22p	NKT217 45p	ORP60 45p	2N2160 69p	40250 45p
BA115 10p	BFY50 20p	NKT404 60p	P346A 20p	2N2926 10p	40361 45p
BAX13 5p	BFY51 20p	OAK3 60p	TIL209 25p	2N3053 20p	40362 40p
BC105 15p	BFY64 45p	OAK1 10p	TIP29 40p	2N3054 45p	40408 50p
BC108 15p	BFY90 75p	OA200 85p	TIP30A 55p	2N3055 45p	40468 75p
BC109 15p	BLY36 62p	OA202 10p	TIP31A 61p	2N3440 90p	40636 1.00
BC109C 14p	BSX20 15p	OC16 85p	TIP41A 74p	2N3442 1.10	40430 85p
BC113 16p	BU105 2.20	OC20 1.25	TIP42A 90p	2N3525 80p	
BC147 12p	BY100 15p	OC28 85p	TIS43 28p	2N3614 59p	
BC169C 14p	BY127 15p	OC35 55p	V405A 25p	2N3702 11p	

All types offered subject to availability. Prices correct at time of press E. & O. E. 10% VAT to be added to all orders. UK post, etc, 15p. per order.

Henry's RADIO LIMITED

EDGWARE ROAD, LONDON W2

404.406 Electronic Components and Equipment 01-402 8381
309 PA Disco Lighting High Power Sound 01-723 6963
303 Bargains Store Callers only
Also used Car Electronic parts, radios, Lamps and batteries, new ones
120 Shaftesbury Avenue, London W1 01 437 9692
104 Burnt Oak Roadway, Burnt Oak, Edgware 01 952 7402
190-194 Station Road, Harrow, Middlesex 01 663 7788 9
354-356 Edgware Road, London W2 01 402 5854 4736

All mail to
303 Edgware Road,
London W2 1BW

All orders must be sent by
post unless a note
is made otherwise
M.F. Take Equipment
Delivery Stock List
Free on all orders

TBA305 5 WATT I.C.
Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output.
With circuits and data £1-50



Sinclair IC12
with circuits and data. 6 watt IC with printed circuit board
28 volt operated £2-00



ZN414 IC
Integrated circuit radio as featured by many magazines (PW Jan. 73 Reprint Ref. No. 19 for 10p) £1-20



STROBE TUBE
ZF74A/XTF2. Suitable for Dec. '73 Pract. Electronics £2-50



ST2 (D32) DIAC 25p
CRS1/40 SCR 45p

Ultrasonic Transducers
Operate at 40Khz up to 100 yds. Ideal remote switching and signalling. Complete with data transmitter and receiver new I.C. circuits.
Per pair £5-90
TA960 IC with socket £1-80

101F5 7 SEG.
I.C. size complete with data price £1-70 each (digital clock circuits ref. No. 31, 15p)



TRANSISTORS SPECIAL OFFER

2N3055
25 47p ea
100 42p
500 39p
1000 34p

BY127
25 12p ea
100 10p
500 8p
1000 8p

ZENER DIODES
400 m/w BZY88/BZK83. From 3-3 volt - 33 volts 10p each

LINEAR I.C.
702C (T05) 75p
709C (T05) 39p
709C (D.L.L.) 39p
723C (T099) 90p
723C (D.L.L.) 90p
728C (D.L.L.) 45p
728C (T099) 45p
741C (T05) 50p
741C (D.L.L.) 50p
747C (T099) £1-00
748C (D.L.L.) 81p

SILICON RECTIFIERS
1 amp series IN4001 to IN4007
From 6p ea
1-5 amp PL4001 to PL4007
From 6p ea
3 amp PL7001/IN5400
From 14p ea
Send for full list 36

MORE OF EVERYTHING AT HENRY'S
See pages 1126 & 1127, and Outside Back Cover of this magazine.
BEST VALUE

Semi-Conductor QUANTITY DISCOUNTS
10% 12+, 15% 25+, 20% 100+

Any one type except where quantity discounts shown.
Min. order £1-00 please.

TRIACS - Std. mounting with accessories
3 AMP RANGE
Type P.I.V. Price ea.
SC35A 100v 80p
SC35B 200v 85p
SC35D 400v 90p
SC35E 500v £1-20

6 AMP RANGE
SC40A 100v 90p
SC40B 200v 95p
SC40D 400v £1-20
SC40E 500v £1-50

10 AMP RANGE
SC45A 100v £1-05
SC45B 200v £1-15
SC45D 400v £1-45
SC45E 500v £1-85

15 AMP RANGE
SC50A 100v £1-45
SC50B 200v £1-65
SC50D 400v £1-95
SC50E 500v £2-25

TRIACS - Additional Types
40430 TRIAC (T066) 85p
40669 TRIAC (Plastic) 90p
40486 TRIAC (T05) 75p

NEW RANGES BRIDGE RECTIFIERS
FEATURES SMALL SIZE AND LOW COST Sizes approx. 250MVA QUARTER AMP
B025/05 50 PIV 16p
B025/10 100 PIV 18p
± x ± x ± dia.


1 AMP P.I.V.
B1/05 50v 25p
B1/10 100v 25p
B1/20 200v 28p
B1/60 600v 30p
± x ± x ± dia.

1 AMP P.I.V.
W005 50v 29p
W01 100v 30p
W02 200v 32p
W06 600v 35p
± x ± Tubular

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.00 a.m.-6.00 p.m.



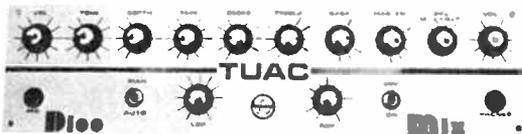TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD.
DEPT. W
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137/9080



TUAC DISCOTHEQUE MIXER WITH AUTO FADE

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions.

£25.50

Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw, Tape Vol, L&R Deck Faders, Deck Volume, Treb. & Bass, H. Phon Vol, Selector, Master Vol, on/off sw. Max. output 1V RMS.

PANEL SIZE 18" x 4 1/2" DEPTH 3"

POWER SUPPLY £3.50p

NEW!
3 CHANNEL LIGHT MODULATOR

- ★ 1,000 watts per channel
- ★ Operates from 1/4th watt to 100 watts
- ★ Full wave control
- ★ Fully fused and suppressed
- ★ 12 easy connections

£17.25

Single channel version **£6.50p**



ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS

ALL PRICES INCLUDE VAT

BARGAIN PARCELS 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 37p p.p.; 56lb at £4.95 plus £1.37 1/2 p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B.16 4VH, medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £1.55 post paid.

NEW HEAVY COAX CABLE dia. 1/4" 70 ohms approx. 50ft. lengths £1.55, p. & p. 32 1/2p. 100 ft. lengths £2.97, p. & p. 55p.

AERIALS. New Condition Whip Type, 4ft. 22p; 11ft. 82 1/2p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 67 1/2p. p. & p. 27 1/2p.

CRYSTALS AS NEW, Hc 6u; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,295 Kc/s. 55p each plus 8p p.p.

TRANSISTOR BOARDS—consisting of transistors, diodes and resistors etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 25p. Quotations for quantity.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 27 1/2p. minimum order of six.

AERIAL POLES 4ft high 2" in diameter push-in type as new 75p each p. & p. 25p each minimum four.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1.10 each section. Carriage 37 1/2p each section. 1/4" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1.10 + 32 1/2p p.p.

AS NEW 500ua PENNY SIZE METERS complete with jack plug price £1.10 each, p. & p. 10p.

COMMUNICATION RECEIVER PCRS price £10. post paid. PCR No. 2 6 to 22 Mexs.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

NEW

ALL SILICON!



PRACTICAL WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, supplied with de-luxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit£7.97 U.K. Post Free
 De-Luxe Kit£9.62 U.K. Post Free

Quantity Discounts:
 Trade and Overseas 1-5 Nett 6-9 Less 10%
 Enquiries Invited 10-49 Less 15% 50-99 Less 20%
 Mail Order Only 100-999 Less 25% 1000 up Less 30%

ALL PRICES INCLUDE VAT

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.


DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
 WALSALL, STAFFS. WS1 1UZ
 Tel. Walsall 34365

**MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.00 a.m.-6.00 p.m.**



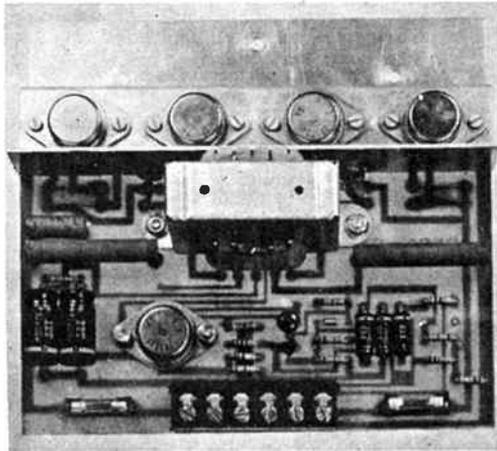**TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD.
DEPT. W
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137/9080**




NEW TUAC POWER MODULES

- | | |
|---------------------------------------|---|
| TP125
illustrated
£15-25 | <ul style="list-style-type: none"> ★ 125 Watts RMS continuous sine wave output ★ 4 RCA 150 Watt 15 Amp output transistors ★ Special layer wound driver transformer ★ Short, open, and thermal overload protection ★ Compact size: 7 x 6½ x 3 in. |
| TL100
£11-50 | <ul style="list-style-type: none"> ★ 100 Watts RMS sine wave ★ 2 RCA 15 Amp output transistors ★ Rugged transformer driver ★ Full thermal overload protection ★ Compact size: 5 x 5 x 3in. |
| TL60
£9-75 | <ul style="list-style-type: none"> ★ 60 Watts RMS sine wave ★ RCA 115 Watt output transistors ★ Only six connections to make ★ Same size as TL100 |
| TL30
£7-50 | <ul style="list-style-type: none"> ★ 30 watts RMS sine wave ★ Rugged transformer driver ★ 2 RCA output transistors ★ Full thermal overload protection |

Power supplies vacuum impregnated Transformers with supply board incorporating stabilised pre-amp supply:
 PS 125 + 50 volts for one TP125 **£8-75**
 PS 100 + 45 volts for one TL100 **£8-00**
 PS 60 + 40 volts for one TL60 **£8-75**
 PS 30 + 30 volts for one TL30 **£4-50**
 PSU 2 for supplying disco mixer **£3-50**

Specification on all three power modules:
 All output power ratings + 1dB. Output impedance 8-15 Ohms. THD at full power 1% typically 0-5%. Input sensitivity 60mV into 10k. Frequency response 10Hz-25kHz +2dB. Hum and noise better than -75dB.

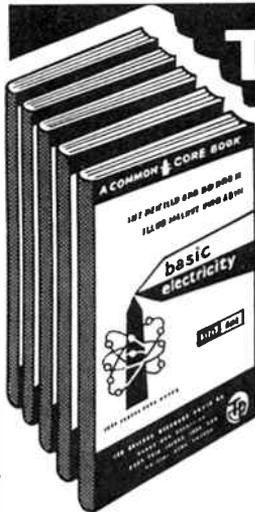**ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING
ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER
H.P. ARRANGED THROUGH PAYBONS**



The Pictorial Method

BASIC ELECTRICITY (5vols) BASIC ELECTRONICS (6vols) BASIC TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR
100%
GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

- I am well pleased with this pictorial system. Everything is clearly set out in diagrams.
L. P. Antrim
- I was very pleased with the set of Basic Electronics. Please send me Basic Electricity.
D. W. Ramsgate
- I am very pleased with the books for they are of great assistance to me in my employment.
S. A. K. Luton
- These books are, without a doubt, the best explanatory books that I have ever possessed.
M. J. Sunderland

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....
 BASIC ELECTRICITY 5 parts £5-30
 BASIC ELECTRONICS 6 parts £6-40
 BASIC TELEVISION 3 parts £3-60

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
 BLOCK LETTERS
 FULL POSTAL.....
 ADDRESS

POST NOW FOR THIS OFFER!

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.60. 3 for ONLY 55p + p & p 30p

SPECIAL ONE. As above PLUS Power Transistors ONLY 55p each + p & p 15p

STABILISED POWER MODULES
Complete with circuit diagrams, etc. 99p each + p & p 15p

PAXOLINE BOARDS 7½" x 9" approx. 4 for 30p + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½" x 4" approx. 2 for 55p

DECON-DALO 33PC Marker

Eich resistant printed circuit marker pen 90p each

VEROBOARDS

Packs containing approx., 50sq. ins. various sizes, all 1 matric 55p

REPANCO CHOKES & COILS

RF Chokes
CH1. 2.5mH 25p CH2. 5.0mH 25p
CH3. 7.5mH 25p CH4. 10mH 25p
CH5. 1.5mH 25p

COILS

DRX1 Crystal set £1p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 7p
1" Cores & Formers 8p

SWITCHES

DP/DT Toggle 25p 8P/8T Toggle 18p

FUSES

1" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A
QUICK-BLOW 4p ea. ANTI-SURGE 6p ea.

EARPHONES

Crystal 2.5mm plug 33p
Crystal 3.5mm plug 33p
8 ohms 2.5mm plug 22p
8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.60

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB @ 21.2K

CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS
Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	5½"	2"	90p
BV2	11"	6"	3"	£1.20

ALUMINIUM BOXES

BA1	5½"	4"	1½"	42p
BA2	4"	4"	1½"	41p
BA3	4"	2½"	1½"	41p
BA4	5½"	4"	1½"	47p
BA5	4"	2½"	1"	41p
BA6	3"	2"	1"	34p
BA7	7"	6"	2½"	84p
BA8	8"	6"	3"	84p
BA9	6"	4"	2"	54p

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)


Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri. Tel. 61593

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.84

Chrome Finish Model 60 £1.50

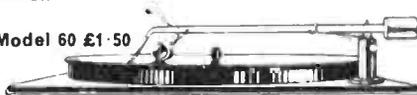

Ref. 36A. Record/Styleus Cleaning Kit 25p
Ref. 43. Record Care Kit £2.35
Ref. 31. Cassette Head Cleaner 54p
Ref. 32. Tape editing Kit £1.54
Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 31p
Ref. 32A. Styleus Balance £1.36
Ref. J. Tape Head Cleaning Kit 51p
Ref. 34. Cassette Case £1.27
Ref. 56. Hi-Fi Stereo Hints & Tips 32p

ANTEX SOLDERING IRONS

X25. 25 watt £1.93
CCN 240. 15 watt £2.15
Model G. 18 watt £2.15
8K2. Soldering Kit £2.86
STANDS: 8T1 £1.21. 8T2 77p
SOLDER: 18SWG Multicores 7oz 82p
22SWG 7oz 82p. 18SWG 22ft 28p
22SWG Tube 22p

ANTEX BITS and ELEMENTS

Bits No.
102 For model CN240 3/32" 38p
104 For model CN240 3/16" 38p
1100 For model CCN240 3/32" 38p
1101 For model CCN240 3/8" 38p
1102 For model CCN240 1" 38p
1020 For model G240 3/32" 38p
1021 For model G240 1/8" 38p
1022 For model G240 3/16" 38p
50 For model X25 3/32" 38p
51 For model X25 1/8" 38p
52 For model X25 3/16" 38p

ELEMENTS

ECN 240 £1.16 ECCN 240 £1.32
EG 240 £1.16 EX 25 £1.16

ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C1	250	Resistors mixed values approx. count by weight	0.55
C2	200	Capacitors mixed values approx. count by weight	0.55
C3	50	Precision Resistors 1%, 2% mixed values	0.55
C4	75	1/4 W Resistors mixed preferred values	0.55
C5	5	Pieces assorted Ferrite Rods	0.55
C6	2	Tuning Gangs, MW/LW VHF	0.55
C7	1	Pack Wire 50 metres assorted colours	0.55
C 8	10	Reed Switches	0.55
C 9	3	Micro Switches	0.55
C10	15	Assorted Pots & Pre-Sets	0.55
C11	5	Jack Sockets 3 x 3.5m 2 x Standard Switch Type	0.55
C12	40	Paper Condensers preferred types mixed values	0.55
C13	20	Electrolytics Trans. types	0.55
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets etc.	0.55
C15	4	Mains Side Switches	0.55
C16	20	Assorted Tag strips & Panels	0.55
C17	10	Assorted Control Knobs	0.55
C18	4	Rotary Wave Change Switches	0.55
C19	3	Relays 6—24V Operating	0.55
C20	4	Sheets Copper Laminate approx. 10" x 7"	0.55

PLUGS AND SOCKETS

SOCKETS
PB 35 DIN 2 Pin (Speaker) 0-06
PB 36 DIN 3 Pin 0-10
PS 37 DIN 5 Pin 180° 0-10
PS 38 DIN 5 Pin 240° 0-10
PS 39 Jack 2.5mm Switched 0-09
PS 40 Jack 3.5mm Switched 0-10
PS 41 Jack 1" Switched 0-17
PS 42 Jack Stereo Switched 0-28
PS 43 Phono Single 0-06
PS 44 Phono Double 0-10
PS 45 Car Aerial 0-09
PS 46 Co-Axial Surface 0-09
PS 47 Co-Axial Flush 0-14

INLINE SOCKETS

PB 21 D.I.N. 2 Pin (Speaker) 0-13
PB 22 D.I.N. 3 Pin 0-17
PB 23 D.I.N. 5 Pin 180° 0-17
PB 24 D.I.N. 5 Pin 240° 0-17
PS 25 Jack 2.5mm Plastic 0-10
PS 26 Jack 3.5mm Plastic 0-12
PS 27 Jack 1" Plastic 0-24
PS 28 Jack 1" Screened 0-28
PS 29 Jack Stereo Plastic 0-22
PS 30 Jack Stereo Screened 0-28
PS 31 Phono Screened 0-14
PS 32 Car Aerial 0-16
PS 33 Co-Axial 0-17

PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0-11
PS 2 D.I.N. 3 Pin 0-12
PS 3 D.I.N. 4 Pin 0-15
PS 4 D.I.N. 5 Pin 180° 0-14
PS 5 D.I.N. 5 Pin 240° 0-15
PS 6 D.I.N. 6 Pin 0-15
PS 7 S.I.N. 7 Pin 0-15
PS 8 Jack 2.5mm Screened 0-10
PS 9 Jack 3.5mm Plastic 0-09
PS 10 Jack 3.5mm Screened 0-12
PS 11 Jack 1" Plastic 0-13
PS 12 Jack 1" Screened 0-18
PS 13 Jack Stereo Screened 0-29
PS 14 Phono 0-06
PS 15 Car Aerial 0-15
PS 16 Co-Axial 0-10

CABLES

CP 1 Single Lapped Screen 0-06
CP 2 T.W in Common Screen 0-08
CP 3 Stereo Screened 0-08
CP 4 Four Core Common Screen 0-23
CP 5 Four Core Individually Screened 0-30
CP 6 Microphone Fully Braided Cable 0-10
CP 7 Three Core Mains Cable 0-07
CP 8 Twin Oval Mains Cable 0-08
CP 9 Speaker Cable 0-04
CP 10 Low Loss Co-Axial 0-10

CARBON POTENTIOMETERS

Log and Lin
47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M
VC 1 Single Less Switch 0-14
VC 2 Single D.P. Switch 0-26
VC 3 Tandem Less Switch 0-44
VC 4 1K Lin Less Switch 0-14
VC 5 100K Log anti-Log 0-44

HORIZONTAL CARBON PRESETS

0-1 watt 0-06 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

WORLD SCOOP

JUMBO SEMICONDUCTOR PACK

Transistors—Germ. and Silicon Rectifiers—Diodes—Triacs—Thyristors—ICs and Zeners ALL NEW AND CODED.

APPROX 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

EX-COMPUTER BOARDS BY THE BOXFULL!

20 Boards packed with Semiconductors and other Electronic Components. Each board approx. size 8" x 7". All known type no's and easily recognisable.

FANTASTIC VALUE AT £2.20 per BOX p. & p. 52p

SPECIAL PURCHASE

2N3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one abel 115w. T03. Metal Case.

OUR SPECIAL PRICE 8 for £1

LOW COST CAPACITORS

01UF 400v. 3p. each
500UF 50v. Elect. 10p each

RECORD STORAGE/CARRY CASES

7" EP. 18½" x 7" x 8". (50 records) £2.10
12" LP. 13½" x 7½" x 12½". (50 records) £2.95

CASSETTE CASES

Holds 12. 10" x 2½" x 5". Lock & Handle. £1.90

8-TRACK CARTRIDGE CASES

Holds 14. 13" x 5" x 6". Lock & Handle £1.95
Holds 24. 13½" x 8" x 5½". Lock & Handle £2.70

COLOURS: Red, Black and Tan—Please state preference.

REPANCO TRANSFORMERS

240v. Primary. Secondary voltages available from selected tappings 4v, 7v, 8v, 10v, 14v, 16v, 17v, 19v, 21v, 25v, 31v, 33v, 40, 60 and 25v-0-25v.

Type	Amps.	Price	P & P
MT50/1	1	£1.98	30p
MT50/1	1	£2.42	35p
MT50/2	2	£3.30	40p

CARTRIDGES

ACOS GP91-18C. 200mV at 1-2cm/sec £1.16
ACOS GP93-1. 280mV at 1cm/sec £1.85
ACOS GP96-1. 100mV at 1cm/sec £2.65
TTC J-2005. Crystal/Hi Output 95p
TTC J-20 10C Crystal/Hi Output Compatible £1.10
TTC J-200 CS Stereo/Hi Output £1.60
TTC J-2105 Ceramic/Med. Output £1.84

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 1/8th watt available in PAKS of 50 pieces, assorted into the following groups:—

R1	50	Mixed 100 ohms-820 ohms	40p
R2	50	Mixed 1K ohms-8.2K ohms	40p
R3	50	Mixed 10K ohms-82K ohms	40p
R4	50	Mixed 100K ohms-1 Meg. ohms	40p

THESE ARE UNREPEATABLE PRICES—LESS THAN 1p EACH INCL. V.A.T.


BI-PAK SUPERIOR QUALITY LOW-NOISE CASSETTES

C60, 32p C90, 41p C120, 52p

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

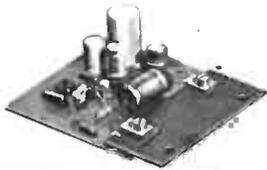

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.
The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0.25%
LOAD IMPEDANCE	—	8 - 16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE @ 3dB	Po = 2 WATTS	50 Hz - 25KHz
SENSITIVITY FOR RATED O/P	Vs = 25V, RI = 8 Ω f = 1KHz	75mV, RMS
DIMENSIONS		3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. (RL = 8 Ω f = 1 KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL10. 3 watts RMS £2 19
AL20. 5 watts RMS £2 59
AL30. 10 watts RMS £3 01

POWER SUPPLIES

PS 12. (Use with AL10 & AL20) 89p
SPM 80. (Use with also AL30 & AL50) £3 25
FRONT PANELS SP 12 with Knobs £1 10

PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20) £4 35
PA 100. (Use with AL30 & AL50) £13 15

TRANSFORMERS

T461 (Use with AL10) £1 38 P & P 15p
T538 (Use with AL20) £1 93 P & P 15p
BMT80 (Use with AL30 & AL50) £2 15 P & P 25p

PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response—
20Hz - 50KHz (± 3dB)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
†Input 2. Impedance
30 K ohms
Sensitivity 4mV


Look for our
SEMICONDUCTOR ADVERTISEMENTS in

Practical Wireless
Wireless World
Radio Constructor

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch, volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion—Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz

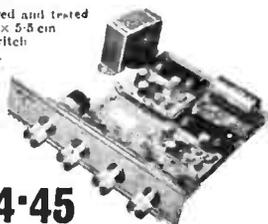

£14.45

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER


THE AL50

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than 0.1% at 1 KHz.

★ Signal to noise ratio 80dB.

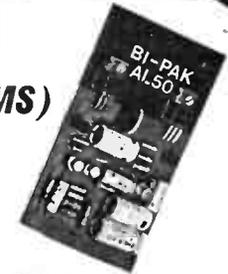

ONLY
£3.58 each

★ Supply voltage 10-35 Volts.

★ Overall size 63mm 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT TESTED GUARANTEED.



STABILISED POWER MODULE SPM80

SPM80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest component and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.2 amps at 35 volts. Size: 63mm x 105mm x 30mm.
These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disc Systems, Public Address-Intercom Units, etc. Handbook available 10p PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market the PA100 stereo pre-amplifier has been conceived from the latest circuit technique. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.
Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION

Frequency Response 20Hz - 20KHz ± 1dB
Harmonic Distortion better than 0.1%
Inputs: 1. Tape Head 1.25 mV into 50K Ω
2. Radio, Tuner 35 mV into 50K Ω
3. Magnetic P.U. 1.5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. input equalised to RIAA curve within ± 1dB, from 20Hz to 20KHz.
Bass Control ± 15dB at 20Hz
Treble Control ± 15dB at 20 KHz
Filters: Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than -65dB
Input overload ± 26dB
Supply ± 35 volts at 20mA
Dimension 292mm x 82mm x 35mm

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

120 240 V Sec. 120 240 V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	£	P & P
07	20	1 8	7.0 x 6.0 x 6.0	2.32	30
149	60	3 12	9.9 x 7.7 x 8.6	3.45	36
150	100	5 8	9.9 x 8.9 x 8.6	3.79	52
151	200	8 0	12.1 x 9.3 x 10.2	6.45	52
152	250	13 2	12.1 x 11.9 x 10.2	8.41	67
153	350	15 0	14.0 x 10.8 x 11.8	11.22	82
154	500	19 8	14.0 x 13.4 x 11.8	16.25	—
155	750	29 0	17.2 x 14.0 x 14.0	22.10	—
156	1000	38 0	17.2 x 16.6 x 14.0	29.87	—
158	2000	60 0	21.6 x 15.3 x 18.1	49.25	—

PLEASE NOTE
NEW ADDRESS
AS BEFORE

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	£	P & P
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.22	22
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.40	30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.89	36
66	300	6 4	9.9 x 9.6 x 8.6	5.63	52
67	500	12 8	12.1 x 11.2 x 10.2	8.36	67
84	1000	19 8	14.0 x 13.4 x 14.3	15.19	82
93	1500	30 4	14.0 x 15.9 x 14.3	21.99	—
95	2000	32 0	17.2 x 16.6 x 14.0	28.70	—
73	3000	40 0	21.6 x 13.4 x 18.1	39.17	—

CASED AUTO TRANSFORMERS

115V 500W enclosed transformer, with mains lead and two 115V outlet sockets. £9.49, P & P 67p. 20 Watt version £2.02 P & P 7p

TRANSFORMERS

PRIMARY 240 250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	12V 24V	Amps.	Weight lb oz	Size cm.	Secondary Windings	£	P & P
111	0.5	0.25	1 4	4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.22	22
213	1.0	0.5	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.44	22
71	2	1	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	1.90	22
18	4	2	2 12	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.68	30
70	6	3	3 8	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.20	42
108	8	4	5 8	9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.60	52
72	10	5	6 4	9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.25	52
112	12	6	6 12	12.1 x 10.2 x 9.6	0-12V at 6A x 2	5.10	52
17	0	0	8 12	12.1 x 9.9 x 10.2	0-12V at 8A x 2	6.56	52
115	20	10	11 8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	8.36	67
187	30	15	15 8	14.0 x 12.1 x 11.8	0-12V at 15A x 2	15.40	82
226	60	30	32 0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	28.44	*

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.42	22
79	1.0	2 4	7.0 x 6.7 x 6.1	1.92	36
3	2.0	3 4	8.9 x 7.7 x 7.7	2.90	36
20	3.0	4 8	9.9 x 8.3 x 8.6	3.58	42
21	4.0	6 4	9.9 x 9.6 x 8.6	4.25	52
51	5.0	6 12	12.1 x 8.6 x 10.2	5.30	52
117	6.0	8 0	12.1 x 9.3 x 10.2	6.31	52
88	8.0	12 0	12.1 x 11.8 x 10.2	8.18	67
89	19.0	13 12	14.0 x 10.2 x 11.8	10.33	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	1.90	30
103	1.0	2 12	8.3 x 7.4 x 7.0	2.80	36
104	2.0	5 8	9.9 x 8.9 x 8.6	3.87	42
105	3.0	6 12	9.9 x 10.2 x 8.6	5.26	52
106	4.0	10 0	12.1 x 10.5 x 10.2	6.99	52
107	6.0	18 0	12.1 x 10.2 x 11.8	10.35	67
118	8.0	18 0	14.0 x 12.7 x 11.8	12.51	97
119	10.0	25 0	17.2 x 12.7 x 14.0	16.93	*

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-428-69C	1.93	36
126	1.0	3 4	8.9 x 7.7 x 7.7	2.70	36
127	2.0	6 4	9.9 x 9.6 x 8.6	4.25	42
125	3.0	8 12	12.1 x 9.9 x 10.2	6.46	52
123	0	13 12	12.1 x 11.8 x 10.2	8.36	67
40	5.0	12 00	14.0 x 10.2 x 11.8	9.85	87
120	6.0	15 8	14.0 x 12.1 x 11.8	12.14	82
121	8.0	25 00	14.0 x 14.7 x 11.8	13.65	*
122	10.0	25 0	17.2 x 12.7 x 14.0	20.09	*
189	12.0	29 00	17.2 x 14.0 x 14.0	22.49	*

MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA.	Weight lb oz	Size cm.	VOLTS	£	P & P
238	200	1 4	2.8 x 2.6 x 2.0	3-0-3	1.31	10
212	1A, 1A	1 4	6.1 x 5.8 x 4.8	0-6-0-6	1.52	22
13	100	1 4	3.9 x 2.6 x 2.9	0-9-0	1.12	10
235	330, 330	4 4	4.8 x 2.9 x 3.5	0-9, 0-9	1.52	10
207	500, 500	1 00	6.1 x 5.4 x 4.8	0-8.9-0-8.9	2.03	22
208	1A, 1A	1 12	7.0 x 6.4 x 6.1	0-8.9-0-8.9	2.73	30
226	200, 200	4 4	4.8 x 2.9 x 3.5	0-15, 0-15	1.52	10
214	300, 300	1 4	6.1 x 5.8 x 4.8	0-20-0-20	1.60	22
231	700 (D.C.)	1 8	7.0 x 6.1 x 6.1	20-15-0-12-20	1.41	30
206	1A, 1A	2 12	8.3 x 7.7 x 7.0	0-15-20, 0-15-20	3.08	36
203	500, 500	2 4	8.3 x 7.0 x 7.0	0-15-27, 0-15-27	2.82	38
204	1A, 1A	3 4	8.9 x 7.7 x 7.7	0-15-27, 0-15-27	2.86	38

PLEASE ADD 10% FOR V.A.T.
INCLUDING P. & P.

BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.



for fast, easy reliable soldering
Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS

Size 5
Savbit alloy
18 swg, 24p (illustrated).
Size 19A
60/40 alloy
18 swg, 25p
Size 15
60/40 alloy
22 swg, 28p

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 36p

Size 12 REEL for Service Engineers and Electricians.
18 swg
Savbit alloy. £1-16

BIB WIRE STRIPPER AND CUTTER

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to: Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

This 76 page FREE book shows how!

Do you want promotion, a better job, a better pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Practical Radio & Electronics (Technatron) Electronic Engineering TV Maintenance & Servicing (General Radio & TV Engineering Radio Servicing, Maintenance & Repairs City & Guilds Radio, TV Electronics Mechanics	<input type="checkbox"/> Radio Amateurs Practical TV Colour Television Computer Electronics C & G LI Radio TV Servicing Cert. Post Master General 1st & 2nd Class Certs. C & G Electrical Engineering Practise C & G LI Installations and Wiring	<input type="checkbox"/> General Electrical Engineering Society of Engineers (Electrical Eng.) Electrical Installations and Wiring C & G Electrical Technicians (Primary) C & G Telecommunication
--	--	---

To B.I.E.T. BPW 01 Aldermaston Court, Reading RG7 4PF QK **BPW 01**

NAME (Block Capitals Please) _____
ADDRESS _____
Other subjects _____ Age _____

Accredited by C.A.C.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteryless Crystal Radio.
- ★ 1 Transistor Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 2 Transistor Regenerative Radio.
- ★ Signal Injector.
- ★ 5 Transistor Short Wave Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP.
- ★ Electronic Metronome.
- ★ Audible Continuity Tester.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator.
- ★ Sensitive Pre-Amplifier.

Total Building Costs
£7-23 P P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 72p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors, 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9" x 7" x 2 1/2" approx. Parts Price List and Plans 30p (FREE with parts).

Total Building Costs **£6-95** P P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 69p)

POCKET FIVE



3 Tunable wavebands, M.W., L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List 15p (Free with parts).

Total Building Costs **£2-28** P P & Ins. 26p
(+ 10% VAT 22p)
(Overseas P & P £1-25)



TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts).

Total Building Costs **£2-50** P P & Ins. 26p
(+ 10% VAT 25p)
(Overseas P & P £1-35)

TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

Total building costs **£4-48** P P & Ins. 33p
(+ 10% VAT 44p)
(Overseas P & P £1-25)

ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Total building costs **£3-98** P P & Ins. 31p
(+ 10% VAT 39p)
(Overseas P & P £1-85)

NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes, MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£2-73** P P & Ins. 30p
(+ 10% VAT 27p)
(Overseas P & P £1-25)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£3-60** P P & Ins. 30p
(+ 10% VAT 36p)
(Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 20p. Free with parts. Overseas P & P £1-05.


Total Building Costs **£4-08** P P & Ins. 31p
(+ 10% VAT 40p)
(Overseas P & P £1-85)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced gauged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

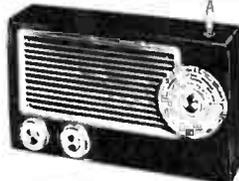Total building costs **£6-98** P P & Ins. 47p
(+ 10% VAT 69p)
(Overseas P & P £1-85)



ROAMER TEN

WITH VHF INCLUDING AIRCRAFT




10 Transistors. Latest 4 1/2 watt Ferrite Magnet Loudspeakers. 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Gauged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off, Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

Total building costs **£8-50** P P & Ins. 52p
(+ 10% VAT 85p)

"EDU-KIT"

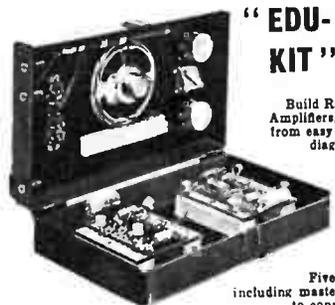

Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include:
Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine Tone 3" Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; 2 Plugs and Sockets; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.
Parts price list and plans 25p (FREE with parts).

Total building costs **£5-50** P P & Ins. 33p
(+ 10% VAT 55p)
(Overseas P & P £1-85)

RADIO EXCHANGE LTD

★ Callers side entrance. Lavelle's shop
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel.: 0234 52367. Box. No. 788372.

I enclose £..... for

Name

Address
(Dept. PW25.)

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

THE PAIR. Post 25p. (Available separately. Woofer £4.25. Tweeter £1.90)

Comprising a fine example of a Woofer 10 1/2 x 8 1/2 in. with a massive Ceramic Magnet. 440z. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 25 to 18,000 cps
Bass Resonance 45 cps



£9.90 Post 25p

SUITABLE ENCLOSURE 20 x 13 x 8 in. MODERN DESIGN. TEAK WOOD FINISH.

8in. or 10in. ELAC HI-FI SPEAKER



Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts

£3.75

TEAK VENEER HI-FI SPEAKER CABINETS

Fluted Wood Fronts

MODEL "A". 20 13 9 in. For 12in. dia. or 10in. speaker. £9.90 Post 25p

MODEL "B". 18 x 10 9 in. For 13 x 8 in. or 8 in. speaker. £6.60 Post 25p

MODEL "B2" ditto. Triangular corner version.

MODEL "C". 18 x 8 4 in. For 8 x 5 in. speaker. £4.40 Post 25p




LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft.

BARGAIN AM TUNER.

Medium Wave. Transistor Superhet Ferrite aerial. 9 volt. £4.95

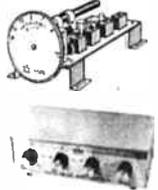BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will accept Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. £3.95



STEREO VERSION OF ABOVE £5.95

BARGAIN FM TUNER.

88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. £12.85



BARGAIN FM TUNER. £8.85

As above less cabinet. BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. £4.50



THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETIZER.

Suitable for cassette and all sizes of tape reels. A.C. mains 200/250V. Leadset S.A.E. £3.50 Post 20p



WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handmen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails - Ideal for airing cupboard. Ideal for anti-frost device for the garage - preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1.50) ALL POST PAID - Discounts for quantity.

BAKER MAJOR 12" £9.90



Post Free 30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50

Please state 3 or 8 or 15 ohms. Post Free

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 65 cps.

GROUP "25" 12in. 25 watt £8.80 Post Free

GROUP "35" 12in. 35 watt £9.90 Post Free

GROUP "50" 15in. 50 watt £22.00 Post Free

NEW 12" VERSION 50 watt 8 or 15 ohms £17.60



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. £49 Carr. £1.00



CALLERS ONLY! DE LUXE 100 WATT AMPLIFIER CHASSIS

7 valve version, 4 input 10 wide range controls. For mikes, Discos, Organs, Guitars, etc. 4, 8 & 15 ohm loudspeakers matching £89.00.

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

8" Sizes	74p	1 1/2" Key 'B' for above 10p	£1.70
9" Key 'T' for above 6p	83p	2" Key 'B' for above 10p	£2.25
10" Key 'T' for above 6p	90p	2 1/2" Key 'B' for above 10p	£2.50
11" Key 'T' for above 6p	92p	3" Key 'B' for above 10p	£3.30
12" Key 'T' for above 6p	99p	Key 'C' for above	13p
13" Key 'T' for above 6p	£1.00	2 1/2" Key 'C' for above	£4.50
14" Key 'T' for above 6p	£1.15	3" Key 'C' for above	£5.75
15" Key 'T' for above 6p	£1.20	Key 'E' for above 20p	£9.00
16" Key 'T' for above 6p	£1.35	1" Square, with key	£2.10
17" Key 'T' for above 6p	£1.70		

SPECIAL OFFER 100 Ohm 20 watt Rheostat

2 1/2 in diam. Ceramic Former. Screw Terminals (in. diam. spindle. 95p. Post 25p.

SPECIAL OFFER 3 inch Panel Meter 50 Microamp.

unusual scale require recalibrating. £1.75 post 25p.

REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt. £1.95 Post 25p
spindle 1 1/2" x 7/32", size 3 1/2" x 3".
As illustrated, 240V. AC mains.

E.M.I. GRAM MOTOR

120v. or 240V. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2" x 2 1/2". £1.00 Post 25p.

BAKER HI-FI SPEAKERS HIGH QUALITY - BRITISH MADE

REGENT 12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps 3 or 8 or 15 ohm models.



£8.80 Post Free

DE-LUXE Mk II 12in 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-18,000cps 8 or 15 ohm models.



£11 Post Free

SUPERB 12in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 18,500gauss
Useful response 20-17,000cps 8 or 15 ohm models.




£16.50 Post Free

AUDITORIUM 12in. 25 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Disco-theques.

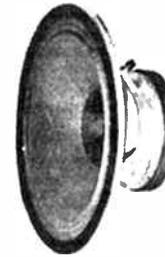Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 25-16,000cps 8 or 15 ohm models.



£15.40 Post Free

AUDITORIUM 15in. 35 watts

A high wattage loudspeaker of exceptional quality with a large response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic Instruments and the home.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps 8 or 15 ohm models.



£22 Post Free

Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free.

CUSTOMERS FREE CAR PARK
SPECIALISTS
(Exports Remit cash and extra postage.)
OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-2-30
337 WHITEHORSE ROAD CROYDON
Telephone 01-684-1665
Buses 50, 68, 159. Rail Selhurst

ESSENTIAL BOOKS FOR RADIO AMATEURS

RADIO AMATEURS' EXAMINATION MANUAL

by G. L. Benbow, G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. Success in the RAE should be assured if all that it contains is understood and remembered.
84 pages

Price 90p post paid

TELEPRINTER HANDBOOK

by D. J. Goacher, G3LLZ, and
J. G. Denny, G3NTT

A brand new book covering all aspects of modern teleprinter techniques. Full descriptions and maintenance data for all widely-used machines, together with design and use of ancillary equipment. Definitely a book for the teleprinter enthusiast's work bench.
376 pages

£5.35 post paid

A GUIDE TO AMATEUR RADIO

by Pat Hawker, G3VA

This extensively revised 15th edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby, it covers technical, operating and licensing matters.
96 pages

Price 90p post paid

AMATEUR RADIO TECHNIQUES

by Pat Hawker, G3VA

(4th Edition)

A source book for many useful circuits and aeriels. An *Ideas* book aimed at extending the reader's awareness of new devices and techniques.
256 pages

£1.80 post paid

These are just four of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.



RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688

STILL at £42.50
Solartron CD 71S.2 Double Beam Oscilloscope DC-9 mc/s; 3 mv/cm; trigger delay; crystal calibrator; 4; flat faced tube, in good working condition. Carr. £1.50.

12" LONG PERSISTANCE CRT, Full spec. Price £7.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5.50, P. & P. 25p. (Not cased, not calibrated.)

NEW WIDE RANGE WOBBULATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for ONLY £5.75, P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB. SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7.85 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each, P. & P. 5p. £1 worth of 'UFS'. Six Brand New capacitors all between 15V and 100V. Total capacitance not less than 7,000µfd. P. & P. 45p.

PHOTOMULTIPLIER type 931A £3.25 ea. P. & P. 25p.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 2 off 4pole 2 way etc.). 50p P & P 20p.

PLEASE ADD 10% V.A.T.

CHILTMead LTD

7/9 ARTHUR ROAD, READING, BERKS.
(near Tech. College) Tel.: Reading 582605/65916

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors ½ and ¼ watt, many high stabs, etc. Fine value at 50p, P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

Fabric Chloride Resistance Pen FREE (whilst stock lasts) on all purchases of our £1 Fibre Glass pack. 5 CRYSTALS 70 to 90kHz. Our choice. 25p, P. & P. 15p.

5 MOVING COIL METERS. Various. £2, P. & P. 37p.

CAPACITOR PACK—50 Brand new components, only 50p, P. & P. 17p.

POTS—10 different values. Brand new. 50p, P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic; 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 520pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 10p.

FLAT FACED 4" TWIN BEAM TUBE type CV2193, Green trace. Brand new £4 each, P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New. 3p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each. **CLARE RESISTOR** type Clare 703. Two for 50p.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. Two-tone green £3.75 each. Black £2.75 each. P. & P. 25p ea. Also **TOPAZ YELLOW** £4.50 each, P. & P. 25p.

Ideal EXTENSION TELEPHONES with standard GPO type dial, bell and lead coding. £1.75 each P. & P. 25p.

DELIVERED TO YOUR DOOR
1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

Open 9 a.m. to 6.30 p.m. anyday.

SPARKRITE MK II

ELECTRONIC IGNITION KIT



COMPRISES

Everything:—
Ready Drilled Case and Metalwork, Cables, Coil Connectors, Silicon Grease, Printed Circuit Board, 5 year guaranteed components and a full 8 page instruction leaflet.

WHEN COMPLETE THE UNIT CAN BE FITTED TO YOUR CAR IN ONLY 15 MINUTES USING THE STANDARD COIL AND CONTACT BREAKER POINTS: TO GIVE YOU:—

Instant all weather starting. Up to 20% fuel saving. Longer battery life. Higher top speed. Faster acceleration. Spark plugs last about five times longer. Misfire due to contact breaker, bounce electronically eliminated. Purer exhaust emission resulting in less air pollution. Contact breaker burn eliminated.

Suitable for all petrol engines up to 8 cylinders

PRICE ONLY £12.65

Ready Built Unit £14.85

Unit for Motor

Cycles with twin coils

and twin C.B. Points £19.80

(prices include VAT and post

& packing)

(NOT AVAILABLE IN KIT FORM)

Please state whether Positive

or negative earth units are

required when ordering.

SEND FOR YOUR UNIT OR FULL BROCHURE NOW

FROM
ICE ELECTRONIC SYSTEMS DEPT P.W.
114 PARK FARM ROAD
BIRMINGHAM B43 7QH



**INCORPORATING LASKYS RADIO
AND G. W. SMITH & CO. (RADIO).**

LB3 TRANSISTOR TESTER
Tests ICO and B. PNP/NPN. Operates from 9V battery. Instructions supplied.
OUR PRICE
£3.95 P&P 20p



KAMODEN HM350 TRANSISTOR TESTER
High quality instrument to test reverse leak current and DC current. Amplification factor of PNP, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.
OUR PRICE £12.50 P&P 30p



S100TR MULTIMETER TRANSISTOR TESTER
100,000 opv. Mirror scale. Overload protection. 0/12/ 0.6/3/12/30/120/ 600V DC. 0/5/10/50/100/200/300/3000 ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.
OUR PRICE £15.00 P&P 20p



Model HT100B4 MULTIMETER
Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/1.5/50/500/1000V DC. 0.25/ 0.5/1/5/10/50/100/175A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.
OUR PRICE £15.00 P&P 20p



TE16A TRANSISTORISED SIGNAL GENERATOR
5 ranges, 400kHz to 30 MHz. An indispensable instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 145 x 149 x 82mm. Complete with instructions and leads.
OUR PRICE £8.97 P&P 25p



MODEL TE20 RF SIGNAL GENERATOR
Six bands. 120kHz-250MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 105-125V 220-240V AC. Size: 193 x 95 x 150mm. Complete with test leads etc.
OUR PRICE £17.50 P&P 40p



ARF 300 AF/RF SIGNAL GENERATOR
All transistorised. Complete with fully portable AF sine-wave 18Hz to 200 kHz. AF square wave 18Hz to 100 kHz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.
OUR PRICE £29.95 P&P 50p



AT201 Decade ATTENUATOR
Frequency range 0-200kHz. Attenuator 0-111dB. 0.1dB steps. Impedance 600 ohms input power maximum 30dBm. Size: 180 x 90 x 65mm.
OUR PRICE £12.50 P&P 37p



MCA220 Automatic Voltage Stabiliser
Input 88-125V AC. Output 120V AC or 240V AC 200V/A rating. P&P 50p.
OUR PRICE £11.97



PS100B Regulated POWER SUPPLY UNIT
Solid state. Output 6, 9 or 12V DC up to 3 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x 159mm.
OUR PRICE £11.97 P&P 25p



PS200 Regulated POWER SUPPLY UNIT
Solid state. Variable output 5-20V DC up to 2 Amp. Indes pendant meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.
OUR PRICE £19.95 P&P 25p



AUDIOTRONIC Model ATM1
Top value 1,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0-1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.
OUR PRICE £2.95 P&P 15p



AUDIOTRONIC Model ATM5
Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0-31/15/50/300/1200V AC. (2500 opv). 0-6/30/300/600V DC. (5000 opv). 0-300 uA/0-300mA DC. Resistance: x 10 & x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 28mm.
OUR PRICE £3.75 P&P 15p




MODEL C1092 MULTIMETER
Features 5,000 opv jewel movement and a good selection of range functions. Edgewise ohms adjustment. Ranges: 0-3/15/50/300/1,200V AC (2,500 opv). 0-6/30/300/600V DC (5,000 opv). DC current: 0-30kA/300mA. Resistance: R x 10, R x 1,000. -10 to +16dB. Complete with battery, test leads and data booklet. Size: 120 x 73 x 28mm.
OUR PRICE £3.75 P&P 35p



MODEL U437 MULTIMETER
10,000 opv. A first class instrument manufactured in USSR to the highest standards. Ranges: 2.5/10/50/250/500/1000V DC. 2.5/10/50/250/500/1000V AC. DC current 100uA/1/10/100mA/1A. Resistance 300 ohms/3/30/300k/3 Meg. ohms. Complete with batteries, test leads, instructions and a sturdy steel carrying case.
OUR PRICE £4.95 P&P 25p



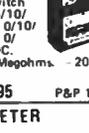MODEL TH12
20,000 opv. Overload protection. Slide switch selector. 0/0.25/1.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/50uA/0.25/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.
OUR PRICE £5.95 P&P 15p



U4233 MULTIMETER
20,000 opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 0.5/2.5/10/50/250/500/1000V AC. DC Resistance 5/10/100k ohms/1Meg. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.
OUR PRICE £7.00 P&P 20p



MODEL TE300
30,000 opv. Mirror scale. Overload protection. 0/0.5/1.5/10/50/300/1200V DC. 0/6/30/120/600/1200V AC. 0/30uA. 6mA/60mA/300mA. 600mA. 0/8k/80k/800k/8 Meg ohms -20 to +63dB.
OUR PRICE £7.50 P&P 15p




HIOKI Model 720X VOM
A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50uA/250mA. 0-20k/2 Megohms.
OUR PRICE £5.97 P&P 20p



U4324 MULTIMETER
High sensitivity, overload protected. 20,000 opv. Ranges: 0.5/1.5/10/50/100/200V DC. 3/6/15/50/150/300/600/900V AC. Current: 0.05/0.5/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.
OUR PRICE £8.00 P&P 20p



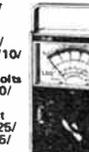TMK MODEL TW50K
40k ranges, mirror scale. 50kV DC. 50kV/AC. DC Volts: 0.125/ 0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts 1.5/3/15/125/250/500/1000. Resistance: 10k/100k/1 Meg/10 Meg ohms. -20 to +81.5dB.
OUR PRICE £8.50 P&P 17p



U435 MULTIMETER
20,000 opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/2.5 A DC. 5/25/100mA. 0.5/2.5 A AC. Resistance: 0.3/3/30k/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and test carrying case.
OUR PRICE £8.75 P&P 20p



U4312 MULTIMETER
20,000 opv. Handy instrument for general electrical use. 667 opv. Ranges: 0/0.3/1.5/5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300mA/1/1.5/6A DC. 0/1.5/15/150/300/600mA/1/1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with test leads, carrying case, leads and instructions.
OUR PRICE £9.75 P&P 25p



KAMODEN 360 MULTIMETER
High sensitivity. DC 10k ohm/V. AC 10k ohm/V. 5" mirror scale, overload protected. Ranges: 0.5/ 2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms. 0/100k ohms. 0/100M ohms. Decibels: -20 to +62dB. Battery operated. Size 180 x 140 x 80mm. Supplied complete with test leads etc.
OUR PRICE £13.95 P&P 25p



U91 Clamp VOLT AMMETER
For measuring AC voltage and current without break circuit. Ranges: 300/800V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 28 x 94 x 38mm. Complete with carrying case, leads and fuses.
OUR PRICE £10.50 P&P 20p



MODEL 500
30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA. 12A DC. 0/6k/60 meg/10k megohms.
OUR PRICE £10.95 Carr. paid Leather case for above £1.75



HIOKI 750X VOLT-Ohm-MILLIAMMETER
43 ranges: 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1200V DC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/60uA/1.5/3/15/30/150/300 mA/8/12A. Resistance: 0-3/30k/3/30k ohms. Decibels: -10 to +17dB. Output -0.3/6/15/30/60/120/300V. Accuracy ± 2%. DC, 4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 5 inch meter. Built in protection. Size: 57 x 102 x 153mm.
OUR PRICE £11.95 P&P 40p



KAMODEN HM720B FET VOM
Input impedance 10 Megohms. Ranges: 0/0.25/1.25/10/50/100V DC. 0/2.5/10/50/100V AC. Resistance: 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 50k Megohms.
OUR PRICE £14.95 P&P 30p



370WTR MULTIMETER
Features AC current ranges, 20,000 opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/0.75/150/300/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.
OUR PRICE £17.50 P&P 25p



TE40 HIGH SENSITIVITY AC VOLT METER
10 ranges: 0.001/ 0.010/ 0.1/ 0.3/ 1/ 3/ 10/ 30/ 100/ 300V RMS. 5cps. ± 2MHz. -40 to +50dB. Supplied complete with leads and instructions.
OUR PRICE £17.50 P&P 25p



MODEL U4311 Sub-standard Multi-range Volt-Ammeter
Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750uA. 1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5 A DC. 0/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5 A AC. 0/0.75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V DC. 0/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.
OUR PRICE £49.00 P&P 50p



U4317 MULTIMETER
High sensitivity instrument for field and laboratory work. Knife edge pointer, 86mm. mirror scale. Ranges: 100V/V. 0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/175A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.
OUR PRICE £15.00 P&P 20p



Model HT100B4 MULTIMETER
Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/1.5/50/500/1000V DC. 0.25/ 0.5/1/5/10/50/100/175A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.
OUR PRICE £17.50 P&P 40p



TE85 VALVE VOLTMETER
28 ranges. DC volts 1.5-1500V. AC volts 1.5-1500V. Resistance up to 1000 Megohms. 200/240V AC operation. Complete with probe and instructions.
OUR PRICE £17.50 P&P 30p



C15 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25. HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-3000usc. Free running 20-200 kHz in nine ranges. Calibrator pips. 220 x 380 x 430mm. 115-230V AC.
OUR PRICE £39.00 Carr. paid



RUSSIAN C116 Double Beam OSCILLOSCOPE
5 MHz case band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2usc to 100 milli-sec/cm. Free running time base. 50Hz-1MHz. Build time base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.
OUR PRICE £87.00 Carr. paid



LB4 TRANSISTOR TESTER
Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.
OUR PRICE £4.50 P&P 20p



U4341 Multimeter & Transistor Tester
27 ranges. 16,700 opv. Overload protected. Ranges: 0.3/1.5/3/30/60/150/300/900V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.05/0.5/5/6/6/60/800mA DC. 0.3/30/300mA AC. Resistance: 0/0.8/8/20/60/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.
OUR PRICE £10.50 P&P 20p



ALL PRICES EXCLUDE VAT
Also see following pages



CLEAR PLASTIC PANEL METERS


USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL S0640

Size: 85 x 64mm

50uA	£3.35
100uA	£3.30
200uA	£3.30
500uA	£3.25
50-0-500uA	£3.35
100-0-1000uA	£3.30
1mA	£3.20
5mA	£3.20
10mA	£3.20
50mA	£3.20
100mA	£3.20
500mA	£3.20
1A DC	£3.20
5A DC	£3.20
10A DC	£3.20
5V DC	£3.20

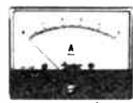

20V DC .. £3.20
50V DC .. £3.20
100V DC .. £3.20
15V AC .. £3.30
300V AC .. £3.30
VU Meter .. £3.45

CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.55
100uA	£4.35
500uA	£4.10
50-0-500uA	£4.35
100-0-1000uA	£4.30
1mA	£3.95
1A DC	£3.95
5A DC	£3.95
20V DC	£3.95
50V DC	£3.95
300V DC	£3.95



CLEAR PLASTIC MODEL 45P

Size: 50 x 50mm

50uA	£3.00
100uA	£2.85
200uA	£2.75
500uA	£2.70
50-0-500uA	£2.75
100-0-1000uA	£2.90
1mA	£2.65
5mA	£2.65
10mA	£2.65
50mA	£2.65
100mA	£2.65
500mA	£2.65
1A DC	£2.65
5A DC	£2.65
10V DC	£2.65
20V DC	£2.65
50V DC	£2.65
300V DC	£2.65
15V AC	£2.70




300V AC .. £2.70
S Meter 1mA .. £2.75
VU Meter .. £3.00
1A AC .. £2.65
5A AC .. £2.65
10A AC .. £2.65
20A AC .. £2.65
30A AC .. £2.65

EDGEWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.15
100uA	£3.95
200uA	£3.75
500uA	£3.50
50-0-500uA	£3.95
100-0-1000uA	£3.85
1mA	£3.50
300V AC	£3.50
VU Meter	£4.25

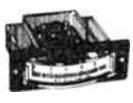

MODEL E0107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



50uA	£7.60
100uA	£7.05
50-0-500uA	£7.70
1A DC	£6.55
5A DC	£6.55
10V DC	£6.55
15V DC	£6.55
20V DC	£6.55
50V DC	£6.55

300V DC ..	£6.55
500mA/5A DC	£6.55
5V/50V DC ..	£7.70
5V/15V DC ..	£7.70
1A/15A DC ..	£7.70

CLEAR PLASTIC MODEL 85P

Size: 120 x 110mm


50uA	£4.85
100uA	£4.70
200uA	£4.45
500uA	£4.30
50-0-500uA	£4.70
100-0-1000uA	£4.65
500-0-5000uA	£4.30
1mA	£4.30
1-0-1mA	£4.30
10mA	£4.30
50mA	£4.30
100mA	£4.30
500mA	£4.30
1A DC	£4.30
5A DC	£4.30
15A DC	£4.30
30A DC	£4.30
10V DC	£4.30
20V DC	£4.30
50V DC	£4.30



CLEAR PLASTIC MODEL S0460

Size: 59 x 46mm

50uA	£3.10
100uA	£3.05
200uA	£3.00
500uA	£2.80
50-0-500uA	£3.10
100-0-1000uA	£3.05
1mA	£2.85
5mA	£2.85
10mA	£2.85
50mA	£2.85
100mA	£2.85
500mA	£2.85
1A DC	£2.85
5A DC	£2.85
10A DC	£2.85
15A DC	£2.85
20A DC	£2.85
3V DC	£2.85
10V DC	£2.85

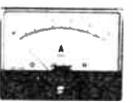

15V DC .. £2.50
20V DC .. £2.50
50V DC .. £2.50
100V DC .. £2.50
300V DC .. £2.50
300V AC .. £2.55
S Meter 1mA .. £2.55
VU Meter .. £2.90

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heat duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. X" diameter shafts. Bulk quantities available.



25 WATT	10/25/50/100/250/500/1000 Ohms	£1.15	P&P 10p
50 WATT	10/25/50/100/250/500/1000/2500/5000 Ohms.	£1.62	P&P 10p
100 WATT	15/10/25/50/100/250/500/1000/2500 Ohms	£2.34	P&P 15p

AUTO TRANSFORMERS

0/115/250V. Step up or step down.

80 WATTS	£2.75	P&P 18p
150 WATTS	£3.50	P&P 18p
300 WATTS	£4.50	P&P 23p
500 WATTS	£6.95	P&P 33p
1000 WATTS	£9.50	P&P 38p
1500 WATTS	£12.50	P&P 43p
2250 WATTS	£20.95	P&P 50p
5000 WATTS	£44.95	P&P £1

CP110 CHASSIS PUNCH SET



Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.

OUR PRICE £3.00 P&P 20p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V. MODEL S260 BENCH MOUNTING

1A	£10.50	30p
2.5A	£12.00	35p
5A	£17.50	37p
8A	£30.35	50p
10A	£37.75	75p
12A	£42.50	75p
20A	£85.00	125p
25A	£95.00	130p
40A	£120.00	150p

MODEL S260B PANEL MOUNTING

1A	£10.00	30p
2.5A	£12.00	35p

BVD5 Vernier TUNING DIAL

App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Size 128 x 76mm. Overall size 190 x 117 x 41mm. Deep including knob and coupling. K" diam. shaft

OUR PRICE £1.62 P&P 15p

2 TRANSISTOR RADIO KIT



No Soldering required. All connect-made with spring clips. Kit includes all parts and wire including ear-piece. Will receive all normal broadcasts on Medium Wave 535-1805kHz. Operates from standard 9V battery or Solar Cell included.

OUR PRICE £1.30 P&P 30p


SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedance 52 Ohm. 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.

OUR PRICE £4.25 P&P 25p

SUPER VALUE TOP QUALITY TRIO equipment

TRIO JR590 RECEIVER

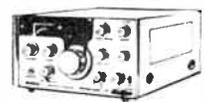

Nine wave-bands covering 1.8-29.7 MHz. 140-146MHz and 10MHz WWV SSB, CW, AM and FM. AF output is more than 1 watt. S Meter. Squelch control. BFO. Variable AF and RF controls. 4-16 ohm output and jack for phono. Power requirement 100/240V AC, 12/14V DC. Size: 270 x 140 x 310mm.

Our Price £132.50 CARR. PAIO

TRIO 9R500S RECEIVER



Four bands covering 550kHz to 30 MHz continuous and electrical band spread on 10, 15, 20, 40, and 80 mtrs. 8 valve plus 7 diode circuit. 4 to 8 ohm output and phone jack. SSB-CW, ANL, variable BFO. S Meter and separate band spread dial. IF frequency 445kHz, audio output 1 1/2 watt. Variable RF and AF gain controls. 115/250V AC, with instructions.


Our Price £42.50 CARR. PAIO

TRIO TR2200 TRANSCEIVER

Fully transistorised portable VHF transceiver. Will transmit and receive on six channels between 144-146MHz. 1 watt transmitter. 12V DC internal or external supply. Built-in charger for Ni-Cad cells. Power/volume switch, squelch control, channel selector, mic, socket, earphone/external speaker socket. Complete with microphone and 144.48, 144.72 & 145.32 crystals. Size: 134 x 58 x 180mm.

OUR PRICE £79.50 Carr.paid

BELTEK W5400 CAR TRANSCEIVER

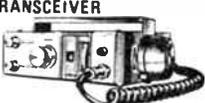

Solid state mobile transceiver for 12 volt DC car. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: On/off/volume, squelch and channel selector. Internal 3" speaker. Complete with dynamic mic. P.T.T switch, three sets crystals for 144.48, 144.6, 144.6 and 145MHz, mounting bracket and instructions. Size: 150 x 70 x 220mm.

OUR PRICE £75.00 P&P 50p

WALKIE TALKIES



SK YFON 100mw
OUR PRICE £24.95 per pair
P302 Two Channel 300mW
OUR PRICE £52.50 per pair
P1003 Three Channel 1 Watt
OUR PRICE £71.25 per pair
P&P 50p per pair
NB. Licence required for use in UK

KE630 3 Station INTERCOM



Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries

OUR PRICE £5.25 P&P 50p



**INCORPORATING LASKYS RADIO
AND G. W. SMITH & CO. (RADIO).**

**CALL INTO YOUR
NEAREST BRANCH
OR ORDER WITH
CONFIDENCE BY
MAIL ORDER**

CENTRAL LONDON

- 10 TOTTENHAM CT. RD. 01-637 2232
- 27 TOTTENHAM CT. RD. 01-636 3715
- 33 TOTTENHAM CT. RD. 01-636 2605
- 42/45 TOTTENHAM CT. RD. 01-636 0845
- 87 TOTTENHAM CT. RD. 01-580 3739
- 257/8 TOTTENHAM CT. RD. 01-580 0670
- 21 OLD COMPTON ST. 01-437 9369
- 109 FLEET ST. EC4 01-437 6204
- 34 LILLE ST. WC2 01-437 9155
- 118 EDGWARE RD. W2 01-723 9789
- 193 EDGWARE RD. W2 01-723 6211
- 207 EDGWARE RD. W2 01-723 3271
- 311 EDGWARE RD. W2 01-262 0387
- 346 EDGWARE RD. W2 01-723 4453
- 382 EDGWARE RD. W2 01-723 4194
- 152/3 FLEET ST. EC4 01-353 5812
- 738 HARROW RD. W9 01-286 9530

ESSEX

- 86 SOUTH ST. ROMFORD 70-20218

SURREY

- 1046 WHITGIFT CENTRE, CROYDON 01-681 3027
- 27 EDEN ST. KINGSTON 01-546 7845
- 32 MILL ST. RICHMOND 01-948 1441

KENT

- 53/57 CAMDEN RD., TUNBRIDGE WELLS 0892-23242

LEICESTERSHIRE

- 45 MARKET PLACE, LEICESTER 0533-537678

**ALL BRANCHES OPEN FROM
9am to 6pm MON. TO SAT.**

**HEAD OFFICE AND MAIL
ORDER DEPARTMENT**

**AUDIOTRONIC HOUSE,
THE HYDE INDUSTRIAL ESTATE,
THE HYDE, LONDON NW9 6JJ.
TELEPHONE: 01-205 3735 & 5651.**

MAIL ORDER SPECIALISTS
We offer a speedy and efficient service by mail order. Remember to add 10% VAT to total value of goods including carriage and packing and send cash with order to head office. **TO AVOID DELAYS PLEASE PRINT NAME AND ADDRESS CLEARLY IN CAPITALS.**

BARCLAYCARD & ACCESS
Holders welcome call into any branch or telephone your order to head office. **CREDIT TERMS available for Personal Shoppers on sales of £50 and over.**

BARGAIN CENTRE
Many special clearance offers and end of stock lines at **87 TOTTENHAM COURT RD. FOR PERSONAL SHOPPERS.**

EXPORT Personal exports arranged for overseas visitors at all our branches. Goods despatched to all parts of the world through our Export Mail Order Department. Immediate attention given to orders.

CHEQUES ACCEPTED FROM PERSONAL SHOPPERS ONLY WITH BANKERS CARD.

All prices correct at 12-2-74 but subject to change.

LHO2S STEREO HEADPHONES

Light weight head-phones with padded ear pieces. 4/16 ohms 200-20,000Hz. Complete with 6' lead and plug.
OUR PRICE £1.97



TE1018 Deluxe Mono High Impedance Headset.

Sensitive magnetic headset with soft ear pads. Impedance 2,500 ohms (600 ohms DC) Frequency response 200-4,000Hz.
OUR PRICE £2.25




HO2S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable head band. Impedance 8 ohms 20-12,000Hz. Complete with lead and plug.
OUR PRICE £2.25



TE1035 Stereo HEADPHONES

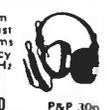Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and stereo jack plug.
OUR PRICE £2.60



SH80V MONO/STEREO HEADPHONES

Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.
OUR PRICE £4.97




BH001 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.
OUR PRICE £5.95



SPECIAL BARGAIN!! PHONIC 10 Two Way Speakers

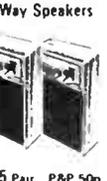Matched pair of compact bookshelf speakers of unique design incorporating a 2" high frequency unit & 6" woofer. 8 ohms impedance. Size: 348 x 228 x 110mm.
OUR PRICE £8.85 pair



SPECIAL BARGAIN !! STEREO SOUND SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size: 368 x 228 x 190mm. 8 ohms. 8 watts RMS. 16 watts peak. Complete with Din lead.
OUR PRICE £12.95



AUDIOTRONIC CRITERION SPEAKERS

High quality three way speaker system offering a performance better than more expensive units. Teak finished with dark fronts. Frequency response: 40Hz-20kHz. 8 ohms impedance. Maximum power 20 watts. Size: 476 x 232 x 232mm.
OUR PRICE £27.50 Pr.



HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Packing 15p per kit.

- AE1 100mW output stage..... £1.65
- AE2 Pre-amplifier..... £1.26
- AE3 Diode receiver..... £2.00
- AE4 Flasher..... £1.09
- AE5 Astable multi-vibrator..... £1.05
- AE6 Monostable multi-vibrator..... £1.02
- AE7 RC generator..... £1.06
- AE8 Bass filter..... 99p
- AE9 Treble filter..... 99p
- AE10 CCR filter..... 99p
- AF20 Mono amplifier..... £3.60
- AF25 Mixer..... £3.60
- AF30 Mono pre-amplifier..... £2.61
- AF35 Emitter amplifier..... £2.27
- AF300 0.5W mic. amp..... £4.22
- AF305 Intercom..... £9.52
- AF310 Mono amplifier..... £5.91
- AT5 Automatic light control..... £2.58
- AT25 Window wiper robot..... £5.82
- AT30 Photo cell switch unit..... £5.70
- AT50 400V triac light dimmer/speed control..... £4.80
- AT55 2.200V triac light dimmer/speed control..... £6.90
- AT60 1 channel light control..... £7.80
- AT65 3 channel light control..... £14.55
- GF304 Circuit board..... £4.80
- GP310 Stereo pre-amplifier for use with 2 x AF310..... £21.27
- GP312 Circuit board..... £11.45
- GU330 Tremolo unit..... £7.45
- HF61 Diode detector..... £3.32
- HF65 FM transmitter..... £2.70
- HF75 FM receiver..... £2.87
- HF310 FM tuner..... £15.81
- HF325 Deluxe FM tuner..... £24.12
- HF330 Decoder (HF310/325)..... £9.96
- HF380 lw/hf aerial amplifier..... £4.94
- HF395 broadband serial amp..... £1.77
- LF380 Quadraphonic device..... £11.36
- M160 Multi-vibrator..... £1.71
- M191 VU Meter..... £4.55
- M192 Stereo balance meter..... £4.97
- NT00 Transistor tester..... £8.45
- NT10 Stabilised power supply 100mA 9V..... £5.15
- NT300 Stabilised p. supply..... £12.51
- NT305 Voltage converter..... £4.50
- NT315 Power supply 240V AC to 4.5/15V DC, 500mA..... £9.57

Amateur Electronics by Josty-Kit, the professional book for the amateur - covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10 above.
OUR PRICE £3.30 (No VAT)
P&P 25p plus VAT.

OT55G DIGITAL CLOCK MECHANISM

Features 24 hour alarm setting on/off Transistor tester and auto alarm 'sleep switch illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V-3 Amp.
OUR PRICE £5.95

SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS

High quality 2 way speaker systems. 25 Watts. 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 255mm. approx. Wood grain finish with black fronts.
OUR PRICE £26.95 PR. P&P £1

RUH6 Reflex Horn Speaker

Built-in driver unit. Impedance 16 ohms. Power rating 10W. Response 380-7000Hz. Size approx. 6" x 6" x 5". Weather and UV shock protected.
OUR PRICE £4.97



RECORD DECKS

- B5R McDONALD £3.95
- C125 Min. £5.50
- C137 £7.00
- S10/TPD..... £12.55
- H10/TPD..... £11.35
- 610/TPD..... £16.65
- 710..... £22.70
- 810..... £28.30
- MP60..... £9.90
- MP60/ADC K8..... £11.50
- MP60/TPD..... £14.20
- H770..... £12.50
- H770/ADC K7E..... £15.95
- H770/TPD..... £17.80
- CDDNOISE..... £10.20
- BD1 Kit..... £10.20
- BD1 Chassis..... £12.50
- BD2/SAU/2/Chassis..... £25.50
- BD2/SAU/2/Print/Cover..... £32.25
- GARRARD £4.95
- 1025T Stereo..... £6.35
- 2025T L3 Cartridge..... £6.35
- MP20/M44..... £9.25
- SP25 Mk3/G800..... £10.95
- SP25 Mk4..... £10.90
- SP25 Mk4/M75-8..... £12.90
- B65B..... £7.00
- LS65B..... £11.15
- SL72B..... £17.75
- GL95B..... £28.00
- GL10 Mk2/P/C..... £22.50
- GL72..... £25.45
- GL72P..... £33.75
- GL70..... £32.90
- GL75P..... £41.65
- GL78..... £34.60
- GL78/P/C..... £56.25
- GL85/P/C..... £72.00

RECORD DECK PACKAGES

- B5R McDONALD P&P 75p
- C125/CM..... £9.50
- MP60/G800..... £19.50
- MP60/TPD/ADC K8..... £16.80
- MP60/M44..... £17.55
- H770/TPD/ADC K7E..... £21.25
- 610/TPD/ADC K8..... £19.25
- GARRARD £11.35
- 2025TC/9TA-HC/D..... £19.45
- SP25 Mk3/G800..... £18.25
- SP25 Mk3/M44-7..... £17.80
- SP25 Mk3/M55E..... £18.80
- SP25 Mk3/Module/M75-8..... £19.45
- SP25 Mk4/G800..... £19.95
- SP25 Mk4/AMC50E (M55E)..... £21.30
- AP76/G800..... £26.75
- AP76/G800E..... £28.95
- AP76/M44..... £28.00
- AP76/M55E..... £28.60
- AP76/M75E..... £35.20
- GL75/G800..... £31.25
- GLD LR..... £31.60
- GL72/G800..... £36.65
- GL75/G800..... £40.90
- GL75/G800E..... £43.90
- GL78/G800..... £45.65
- GL78/G800E..... £48.15
- G101/P/C/G800..... £23.70
- RANK DOMUS £43.60
- BD4000..... £53.95
- BA4000..... £67.50
- WHARFEDALE £23.90
- Linton W30 Teak..... £25.10
- Linton W30 White..... £25.10

AUDIOTRONIC LOW NOISE CASSETTES

- TYPE 5 10 25
- C60 £1.27 £3.00 £7.08
- C90 £2.24 £4.25 £10.00
- C120 £2.73 £5.17 £12.24

AUDIOTRONIC CrO2 CASSETTES

- TYPE 5 10 25
- CR90 £5.32 £10.46 £25.22

AUDIOTRONIC 8 TRACK CARTRIDGES

- TYPE Each 5 10
- 40M 85p £4.00 £7.50
- 80M £1.15 £5.40 £10.25

P&P Cassettes 3p. Cartridges 5p each OVER 10 of either POST FREE!

EMI LOUOSPEAKERS

Model 350 13 x 8" with single tweeter/crossover 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.
OUR PRICE £7.25 each P&P 37p
Model 450 13 x 8" with twin tweeters/crossover 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms.
OUR PRICE £3.62 each P&P 25p

SINCLAIR CAMBRIDGE CALCULATOR

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator.



OUR PRICE £24.95 P&P free
ALSO AVAILABLE READY BUILT Recommended Price £29.95

OUR PRICE £27.20 P&P 25p

Also available - **SINCLAIR EXECUTIVE** Recommended Price £39.00

OUR PRICE £35.45 P&P 25p

SINCLAIR EXECUTIVE with MEMORY Recommended Price £49.00

OUR PRICE £41.50 P&P 25p

SINCLAIR Project 80 Modules

- Z40 Power Amplifier..... £5.45
- Z60 Power Amplifier..... £6.95
- Stereo 80 Pre-Amplifier..... £11.95
- Active Filter Unit..... £6.95
- Project 80S..... £26.95
- P25 Power Supply..... £4.98
- P26 Power Supply..... £7.98
- P28 Power Supply..... £7.98
- P29 Power Supply..... £7.98


SINCLAIR Project 80 Packages

- 2 x Z40/Stereo 80/P25..... £25.00
- 2 x Z40/Stereo 80/P26..... £27.75
- 2 x Z60/Stereo 80/P28..... £30.45

POST & PACKING 35p each.

AUDIOTRONIC AH401 Stereo Headphone Amplifier

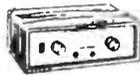All silicon. transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.
OUR PRICE £8.50 P&P 20p



1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. Two gain controls. On-off slide switch, stereo headphone socket.
OUR PRICE £2.25 P&P 15p



MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated Size 235 x 127 x 26mm. Inputs: Mic. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 4mV 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k.
OUR PRICE £8.97 P&P 20p



EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, extra etc. and output to your amplifier. Volume control and depth of reverb control. Beau-walnut cabinet, 184 x 77 x 108mm.
OUR PRICE £7.50 P&P 20p



Model A1018 FM TUNER

6 transistor high quality unit - 3IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.
OUR PRICE £9.65 P&P 30p
Stereo multiplex adapter £4.97 extra.



ALL PRICES EXCLUDE VAT

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit-£24.95! (PLUS VAT)

The Cambridge – new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

Total cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 – so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge

- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{1}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents :

1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no : 699483 England
VAT Reg. no : 213 8170 88

Why only Sinclair can make you this offer

The reason's simple : only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)

Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)

PW 4/74

To : Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me

a Sinclair Cambridge calculator kit at
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready
built at £29.95 + £3.00 VAT
(Total: £32.95)

*I enclose cheque for £ _____, made
out to Sinclair Radionics Ltd, and
crossed.

*Please debit my *Barclaycard/Access
account. Account number _____

*Delete as required.

Name _____

Address _____

PLEASE PRINT

SAFETY FIRST

TO encourage safety in the mere presence of electrical, electronic, radio or television apparatus, let alone during their operation, is not only laudable but vital. Hence the British Electrotechnical Approvals Board for Household Equipment (now affectionately BEAB) is extending the BEAB Approval Scheme to include audio and radio products including record players, radios, radiograms, mains/battery portable receivers with (curiously) "continuously rated audio outputs up to 6 + 6 watts stereo or 10 watts mono". Manufactured equipment that is licensed to bear the BEAB approval marking has to be first subjected to some detailed and stringent tests at the BSI laboratory.

The specification for the tests, detailed in BS 415: 1972 (with amendments), highlights for the more casual of the manufacturers, and probably some of the amateur constructor fraternity, areas of potential risk in mains driven equipment that all too often are taken for granted. There are, of course, extreme cases like the ladies' dangling necklace test and the test which inserts artificial fingers into apertures almost in determination to find live contact.

Generally the scheme is an excellent one. In most British equipment, that is designed and manufactured by responsible people, it is unlikely that no thought will be given to hazards such as shock, fire risk, ionised radiation, implosion and the like.

What has been needed is some form of yardstick by which a known hazard can be measured. Let us not be carried away by any thought that this standard is for manufacturers only. There are frequent cases where more strict attention to detail is needed by everyone who has mains driven appliances or electronic equipment.

We have only one serious complaint: that is the use of graphical symbols to indicate the nature of the supply (a.c. or d.c.) and to indicate live terminals. To the uninitiated layman, technical symbols mean nothing and he will not be inclined to buy BS3939 to find out before operating his new purchase.

Elsewhere in this issue we have highlighted only a few of the points in BS415 that we feel the general public need to know about. It is stressed that the detailed specification is designed to cover most contingencies of normal operation; we recommend manufacturers, suppliers and users to refer to this for more information.

M. A. COLWELL—*Editor*.

The May issue of *Practical Wireless* will include a special pull-out feature to make a handy booklet "Guide to Long Distance Reception of Radio and TV", (useful for locals, too!). Also appearing will be constructional projects: the medium wave "Mini-Pop" (goes in a jacket pocket); an audio booster and power supply to enable you to hear cassette recordings in the car; a trace doubler to enable you to convert a single-beam oscilloscope for four displays. We shall also be giving first details of a super new project that we know will appeal to sports fans all over the world. Don't miss out—order your copy regularly NOW.

(All advanced details are subject to the current national industrial situation).

Further details on page 1167

NEWS...

Export sales of British made Dolby

IN a recent statement Phoenix Videosonic Ltd., of Braintree, Essex, Europe's only manufacturer of Dolby Noise Reduction Units announced significant export sales to Europe, North America and Japan.

A Videosonic spokesman stated: "Videosonic leads the world in the technical specification of its equipment: in the PD4 we have introduced a new high level Dolby 'B' circuit providing a unique range of over 95dB between noise and 0.1% distortion. At this time the PD4 represents the ultimate way to take the PSSST! out of tape.

To further extend our lead in the World Hi-Fi market, the PD2b has been introduced as the world's first battery operated Dolby Unit, allowing 'field' use in the most rigorous conditions. The integral microphone pre-amplifier makes this an ideal unit for reporter or similar usage.

World recognition of Videosonic technical manufacturing competence has been most encouraging, and we can only take pride in our immediate penetration of the Japanese market in the face of very strong local competition. We are advised that our range of Dolby products will be displayed and demonstrated in the top 850 Hi-Fi Retail Shops in Japan, and that local response to date has been very positive. Our first shipment to Japan leaves this week.

Portable Fluorescent Lamp (March P.W.)

WILL readers please note, that the transformer specified is now no longer available. An improved transformer is available from Messrs G. F. Milward at 77p plus 20p p & p. This includes full modification details and uses fewer components. A 21 in. 13W tube is available at 50p + 20p p & p, and it is claimed that this tube gives a greater light output than the 15W tube. S.A.E. to G. F. Milward for further details.

Bargains galore

IF you are in the "Ally Pally" area on March 24th, pay a visit to the Collector's Bazaar which is being held in the Palm Court.

This is a five-bazaar event which includes militaria, vintage post cards, vintage toys, transport relics and, of most interest to our readers, vintage records, horn gramophones, phonographs and probably some items of vintage radio equipment.

Practical Wireless visited one of these bazaars held at St. Johns Wood a few months ago, and it was there that Colin Riches purchased an Edison "Gem" phonograph to be featured in a future "Going Back."

If any readers want to find out the details of hiring a stall at the bazaar (£3.50 for the day) contact the organiser John Carter, Smewins, Shottesbrooke, nr. Maidenhead, Berks, SL6 3SR (Tel. Shurlock Row 539).

Otherwise, put on your cycle clips and pedal along to Alexandra Palace, Wood Green, London N.22, on March 24th. They'll let you in at 1 p.m. but be sure to have your entrance fee of 30p at the ready.

Hi-Fidelity 74

HI-FIDELITY 74 is a rival exhibition to the Sonex show. It will be run at the same time and held at the Heathrow Hotel, Bath Road. It's the idea of Malcolm Blockley who is the Hi-Fi Division Sales Manager of Pyser-Britex Ltd.—the sole UK distributor of Marantz, Teledyne and Kenosonic equipment.

The organiser states that this show has been arranged because many manufacturers are fed-up with trying to demonstrate their products in small, cramped hotel bedrooms.

Hi-Fidelity 74 will run from March 27th to 31st inclusive but the first two days will be for the trade and press only.

Blast them out!

IN order to reduce the effects of interference from an East German station at night, the BBC has increased the transmitting power of the Radio 4 Moor-side Edge transmitter to 300kW.

R and TV Components Ltd.

IN their March advertisement, the price of postage and packing for the "Stereo 21" should have read £1.60. Apologies to R and TV Ltd.

Public Address Exhibition

Readers who have an interest in outdoor activities, such as rallies, will be planning events for the coming season. To get up to date on public address installations, it would be worthwhile to visit Sound '74, the international exhibition of the Association of Public Address Engineers. A lecture programme will be held concurrently on p.a. design, building acoustics, microphones, and the financial side of public address work from the practical point of view.

The A.P.A.E. has received more stand space bookings than previously, but there are still a few left for those who wish to come in at a late stage, including suppliers of disco equipment.

Admission is free to all in-

terested persons: tradesmen, manufacturers, buyers, and users of public address and allied equipment in the entertainments business. Tickets can be obtained from exhibitors or from the A.P.A.E. Secretariat, 6 Conduit Street, London W1R 9TG.

The scope of activities covered is extended to include audio-visual effects.

Overseas readers will be interested to learn that the A.P.A.E. are exhibiting in Hall 9A at the Hanover Fair from 25th April to 3rd May 1974 and at the I.C.E.T.I.A. exhibition at Melbourne, Australia from 7th to 11th October

Practical Wireless will be on show at the Hanover Fair.

UK wavebands and frequencies

THE BBC Engineering Department have issued a useful data sheet which shows the frequencies and wavebands allocated to broadcasting in the United Kingdom. Below we give the details from that sheet:

Band	Frequencies	Service
Low frequency (l.f.) (long waves)	160-255kHz (1875-1176m)	} a.m. radio
Medium frequency (m.f.) (medium waves)	525-1605kHz (571-187m)	
High frequency (h.f.) (short waves)	3950-4000kHz (75-m band)	
	5950-6200kHz (49-m band)	
	7100-7300kHz (41-m band)	
	9500-9775kHz (31-m band)	
	11700-11975kHz (25-m band)	
	15100-15450kHz (19-m band)	
	17700-17900kHz (16-m band)	
	21450-21750kHz (13-m band)	
	25600-26100kHz (11-m band)	
Band I	(v.h.f.) 41-68MHz (channels 1 to 5)	405-line television
Band II	(v.h.f.) 88-97.6MHz	f.m. radio
Band III	(v.h.f.) 174-216MHz (channels 6 to 13)	405-line television
Band IV	(u.h.f.) 470-582MHz (channels 21 to 34)	625-line television
Band V	(u.h.f.) 614-854MHz (channels 39 to 68)	625-line television
Band VI	(s.h.f.) 11700-12500MHz (11.7-12.5GHz)	Not yet in use for broadcasting



A VARIABLE TIME SWEEP WINDSCREEN WIPER

P. S. COLLINS

IMAGINE the situation: you are driving your car in drizzly rain, you put on the windscreen wiper. One sweep is sufficient, so you switch it off. Five, ten or fifteen seconds later the windscreen needs another wipe, so you switch on the wiper again for another single stroke. This could go on for some time and tends to be wearisome.

The circuit here described saves this tiresome routine and allows you to relax in the automation of a variable time-sweep wiper. Although the circuit is designed for wiper motors with automatic parking facility, there is some information at the end of the article which will be helpful to those who have wiper motors without this facility.


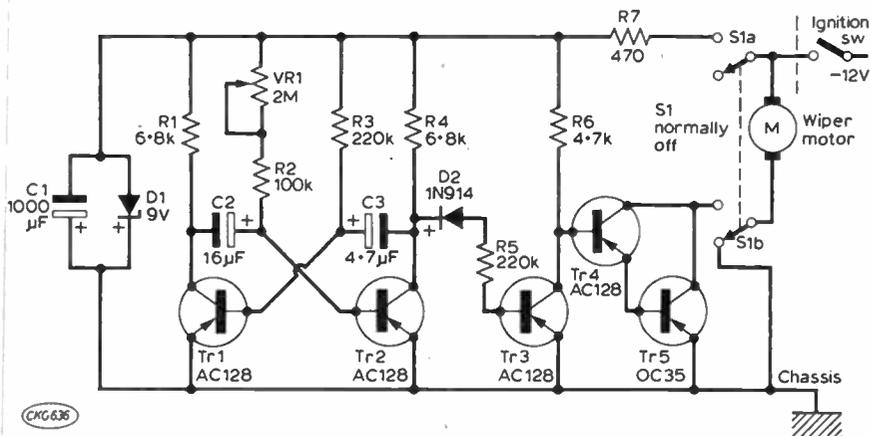
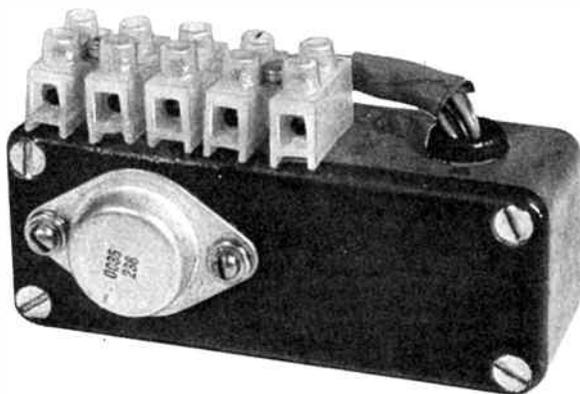


Fig. 1. Circuit of the Quickwipe for a vehicle with a **POSITIVE** earth system. It is essential to be quite sure which side of the battery is connected to chassis.

CMG636

Fig. 2. In this circuit for a **NEGATIVE** earth system, different transistors are used and capacitors and diodes are reversed compared to those in Fig. 1.

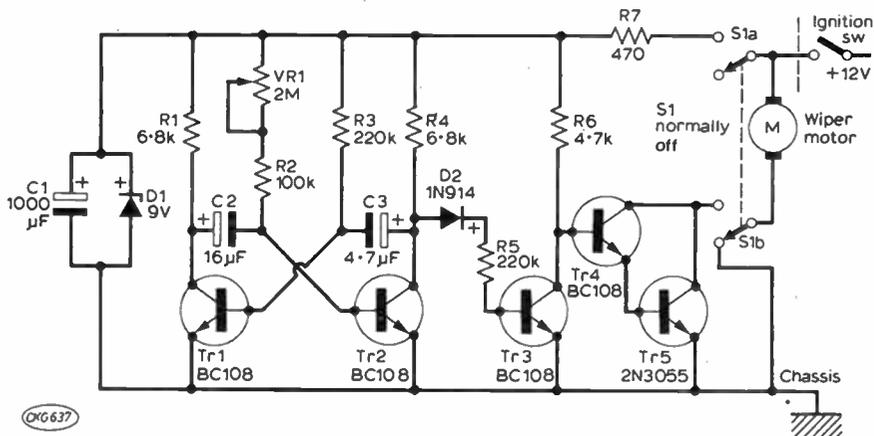

CMG637


Figures 1 and 2 are the circuits for positive and negative earthed vehicles; the difference lies only with the active components and reverse connection of the polarised ones. The circuit action remains the same. Tr1 and Tr2 form a multivibrator generating a pulse of fixed length with a variable repetition rate. VR1 allows this rate to be varied between approximately 3 and 30 seconds. Tr3, 4 and 5 form a pulse amplifier to drive the wiper motor.

The fixed pulse length is $\frac{3}{4}$ second which is sufficient time to drive the motor long enough for its internal switches to take over the drive and thus return it to the park position. Switch S1 is centre off. One switch, S1b, switches for continuous operation, earth being directly applied to the motor.

In the other position, S1a, applies 12 volts to the circuit and S1b connects the motor as the load for the pulse amplifier. The vehicle wiper switch may now be regarded as redundant, or left in the circuit, as desired.

CONSTRUCTION

The whole unit can be comfortably housed in a die-cast box measuring $3\frac{1}{2} \times 1\frac{3}{8} \times 1\frac{1}{8}$ in. Figure 3

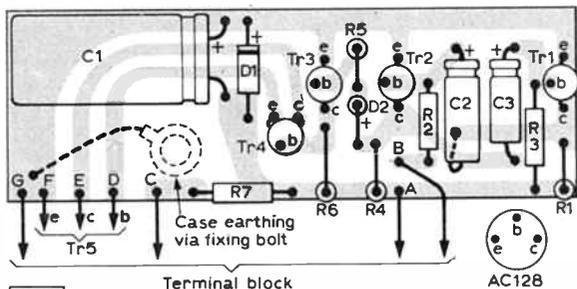

AM 0158


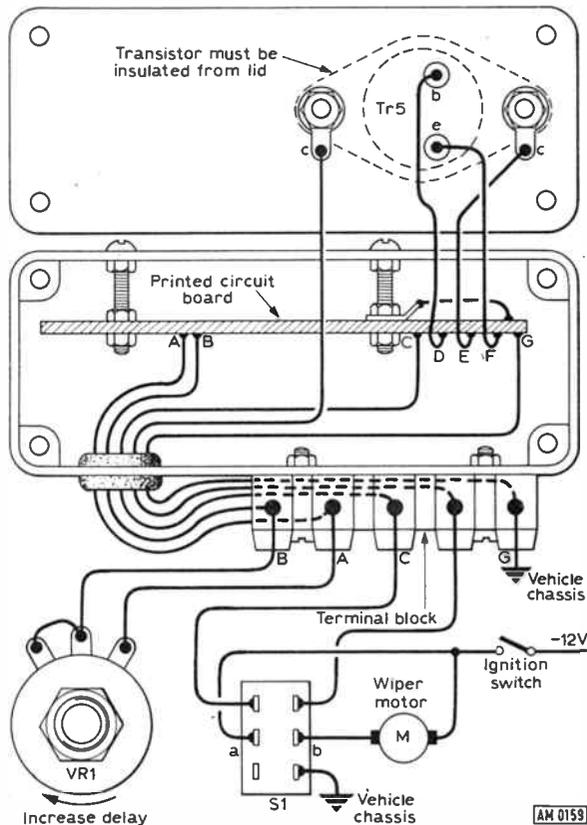
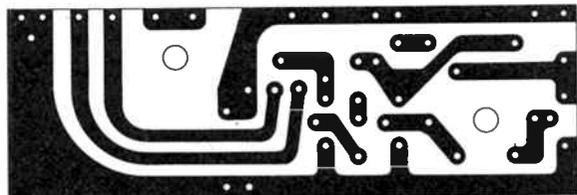


Fig. 3, left, shows PCB actual size and component layout for POSITIVE earth unit. Fig. 4, above, illustrates external wiring of Quickwipe.

shows the printed circuit board. Tr5 is mounted on the lid with insulating washer and bushes. All leads from the circuit board and Tr5 are connected to a five-way terminal strip fixed to the side of the box. This enables easy connection to the vehicle's wiring, as shown in Fig. 4.

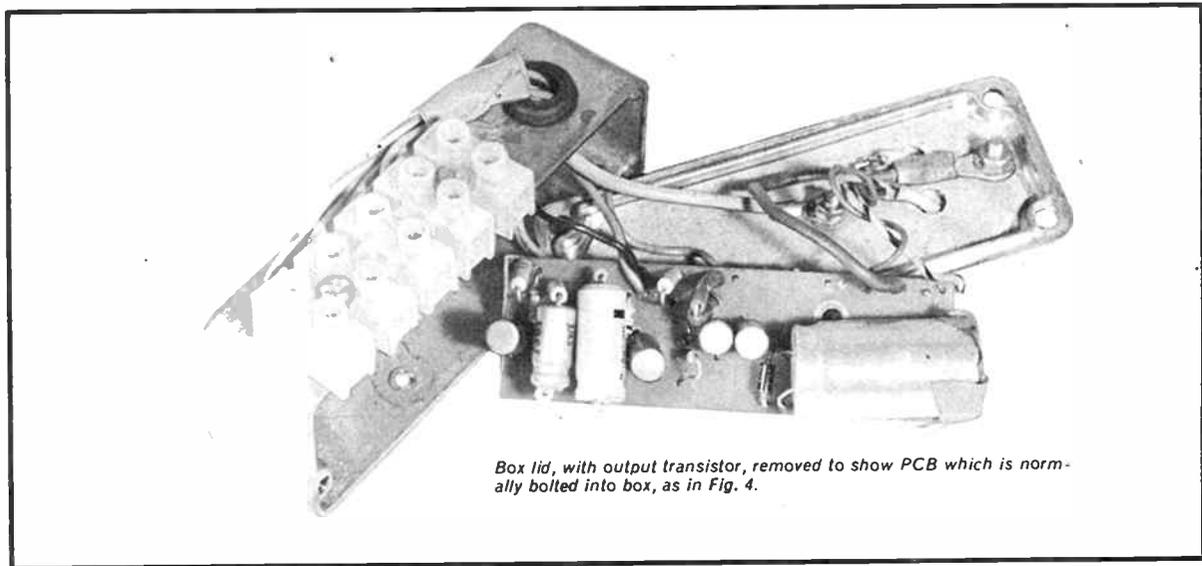Confirm the chassis polarity of the vehicle before constructing the unit, then use Fig. 1 OR Fig. 2 as appropriate.



Box lid, with output transistor, removed to show PCB which is normally bolted into box, as in Fig. 4.

★ components list

Resistors

R1	6.8k Ω	R5	220k Ω
R2	100k Ω	R6	4.7k Ω
R3	220k Ω	R7	470 Ω
R4	6.8k Ω	VR1	2M Ω linear

Resistors 10% $\frac{1}{2}$ W except R7 $\frac{1}{4}$ W

Capacitors

C1 1000 μ F 25V C2 16 μ F 16V C3 4.7 μ F 16V

Semiconductors

D1 9V zener 400mW D2 1N914

Positive Earth Tr1—4 AC128 Tr5 OC35

Negative Earth Tr1—4 BC108 Tr5 2N3055

Miscellaneous

S1, Double pole—double throw switch, centre off. Diecast box (RS Comps.—"Box 992"). Printed circuit board. Insulation kit for Tr5. Five way terminal block.

NOTE: It may be possible to arrange the fixed pulse length to correspond with the time taken for the wipers to travel one complete sweep, in the case of wipers without the self-park facility. This could be achieved by altering the values of R3 and C3.

These points are offered only as helpful guides. The author has conducted no tests in this regard and cannot therefore give any facts regarding accuracy or success. ■

Pw TECHNICAL CROSS PUZZLE No. 3 Solution



TELEVISION

IN THE APRIL ISSUE

CLOSED-CIRCUIT TV

Next month we start a new series aimed at giving an essentially practical account of closed-circuit TV equipment, its use and the servicing techniques required. To start with, the basic element in CCTV work, the vidicon camera tube, is explained along with its basic circuitry.

TRANSISTOR FIELD TIMEBASES

Fully transistorised field timebases have been around for some time now, particularly in colour receivers, and have proved to be generally very reliable. Nevertheless it is time we took a look at common faults and their causes, also at the operation of the class A output stage generally used.

THE DIODE DROPPER

The use of a diode dropper in the heater circuit reduces heat dissipation and is also cheaper than using a completely resistive dropper. The action of the diode dropper circuit is often misunderstood however, which can lead to the use of an incorrect accompanying resistor value and damage to the valves in the chain. The circuit action will be explained and the procedure for determining the value of the accompanying resistor given, either for designing a new circuit or for working out a diode dropper substitution for an existing set.

SERVICING TELEVISION RECEIVERS

The next chassis to be dealt with by Les Lawry-Johns is the Pye 169 single-standard monochrome chassis and its derivatives, the 569, 769 and 173.

PLUS ALL THE REGULAR FEATURES

Details of the April issue are subject to the current national situation at the time of going to press.

TO
(Name of Newsagent)

Please reserve/deliver the APRIL issue of TELEVISION (25p) and continue every month until further notice.

NAME

ADDRESS

GUIDE TO multi-range test meters

H. LEEMING G3LLL

IT does not seem many years since test meters were so expensive that, in the radio and TV trade, at least, one was shared between several engineers, the losers having to make do with wet fingers and neon screwdrivers! Test meters are now relatively cheap so that no enthusiast or handyman can really afford to be without one; whether it be for attending to the Hi-Fi system, fixing the car, or even sorting out a fault on the front door bell. Despite their simplicity in operation these meters can deceive the unwary and so it is hoped that a little basic theory will be of practical assistance.

The multi-range test meter commonly contains ranges such as AC and DC voltage, DC current and at least one resistance range. Other functions may be included on the more elaborate instruments but all use the basic meter movement plus the switching of various internal components in or out of circuit.

The DC Voltmeter

The meter movement fitted to most modern test instruments needs a current of something in the range of 1 to 1/100 of a milliamp to move a pointer across the full extent of the scale. The theoretical circuit of the basic meter movement is shown in Fig. 1. The "internal resistance" is not an actual resistor, but is the resistance of the coil of wire in the meter movement. From Ohm's Law, (voltage = current \times resistance) this 1mA meter movement shown will require a voltage of 0.1 volt for full scale deflection, ($1/1,000 \times 100/1 = 0.1$ volt). This basic meter could therefore be used to measure voltages of up to 0.1 volt or currents of up to 1 milliamp—not very useful!

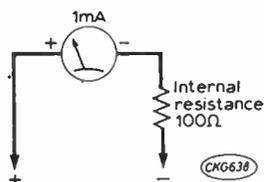


Fig. 1: Representation of meter movement must include resistance of moving coil.

The meter movement is basically a current operated device, but it can be made to read various quantities. A little thought will show that a 1mA meter movement will read full scale if 1 volt is

applied to it through a series resistance which, including internal resistance, totals 1,000 ohms. From Ohm's Law, 1 volt across 1,000 ohms causes a current of 1mA to pass. A voltmeter using a 1mA meter movement is said to have a sensitivity of 1000 ohms per volt.

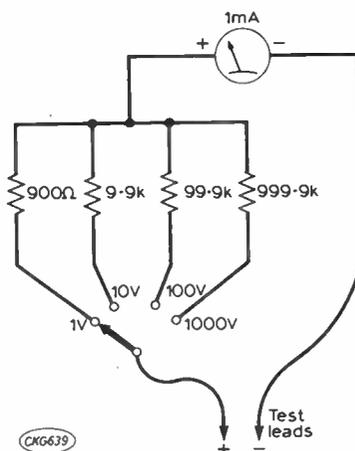


Fig. 2: Series resistors for voltmeter allow for coil resistance. Only of importance on lower ranges.

Fig. 2 shows the meter wired to read four ranges of voltage and it will be seen that the total resistance of the meter is 1,000 ohms for every volt of the range in question. For this reason it is referred to as 1,000 OPV and this would usually be marked on the meter scale.

Such a meter does have its disadvantages and its relatively low resistance can greatly affect circuit voltages as will be shown. In Fig. 3a two 1 ohm resistors are connected across the supply and the voltage between X and Y is measured. If the meter is switched to the 1 volt range it has a total resistance of 1,000 ohms (remember 1,000 OPV) this resistance being shunted across R2. As the meter resistance is very high, compared to R1 and R2, its effect is negligible and the reading is given accurately as 0.5 volts. If, however, the meter is transferred to the circuit in Fig. 3b and another reading is taken the resulting accuracy is quite different. Once again, the reading should be 0.5 volts, but note what happens when the meter is

connected across R2. R2 is shunted by the meter's resistance of 1,000 ohms and the resistance of the bottom half of the circuit drops to around 900 ohms. The voltage divides itself according to the ratio of the resistors and the meter reads just below 0.1 volts.

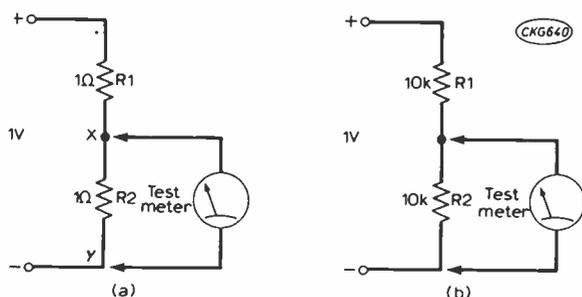


Fig. 3 (a) and (b) : to demonstrate effect of meter resistance on high and low resistance circuits.

The meter is not really wrong, it simply reads the voltage that is present when it is connected. Using the same meter a more accurate reading could be taken by switching to the 10 volt range when the test meter's resistance would rise to 10,000 ohms; the meter's resistance in parallel with R2 would then total 5,000 ohms and whilst the voltage reading would still be low at 0.33 instead of 0.5, it would be a little more realistic. Could we take the same argument further and switch to the 100 volt range with a meter resistance totalling 100,000 ohms, and obtain an accurate result? Unfortunately, no, since when the meter was switched to this range the pointer would move so little that we would not be able to take an accurate reading from it.

If we want a more accurate reading in a high resistance circuit the answer is a more sensitive meter movement that will allow us to insert larger values of voltage multiplier resistors. If for instance, we substitute a meter with a 50 micro-amp movement, (0.05mA), we will obtain a sensitivity of 20,000 OPV. Using circuit Fig. 3b we would then obtain, on the 1 volt range, a reading that was almost correct, (20,000 ohms being shunted across R2), or by switching to the 10 volt range using this higher sensitivity meter we would obtain a reading that was accurate to within all normal requirements.

As has been illustrated, the DC voltmeter can only read the voltage which is present when it is connected. It cannot guess at the voltage which appears when it is disconnected. When using a voltmeter one should get into the habit of comparing the resistance of the range being used with the resistance of the circuit being measured.

In many cases when operating in a high resistance circuit a more accurate reading will be obtained if a higher voltage range is used. If in doubt a reading should be taken on two adjacent ranges of the test meter. With any good quality instrument these readings should be about the same, but if they are not it implies that the meter is loading the circuit on the lower voltage range.

Valved or Transistorised Voltmeters

To obtain higher sensitivities using normal techniques requires very expensive and delicate meter movements. It is not common practice, therefore, to make multi-range test meters with a sensitivity


of much over 50,000 OPV. In some circumstances an even higher sensitivity is required, so that test meters of as high a sensitivity as this would be of little use at measuring, say, 0.1 volts in a circuit with resistance of several megohms. To enable higher sensitivities to be obtained, the valve and then the transistorised voltmeter were introduced. In these devices amplification is used so that an input resistance of 10 megohms or more is presented, even on the lowest voltage ranges. Such instruments are essential if tests are to be made in some high impedance transistorised circuits where very small voltages are present.

Frequency Response

Most test meters are basically intended for making tests at the mains frequency and their accuracy often falls off at frequencies in the audio range. One should check the frequency response of a test meter before relying upon it to check audio or bias frequency voltages. In the latter case it should be remembered that high frequency bias voltages can damage the rectifier in some test meters, and also that even if the meter's frequency response is adequate that its loading (possibly only a few hundred OPV) can, in many circuits, much reduce any voltage present. If it is desired to accurately measure voltages at high audio or radio frequencies the valve or transistorised voltmeter is again essential.

The AC Voltmeter

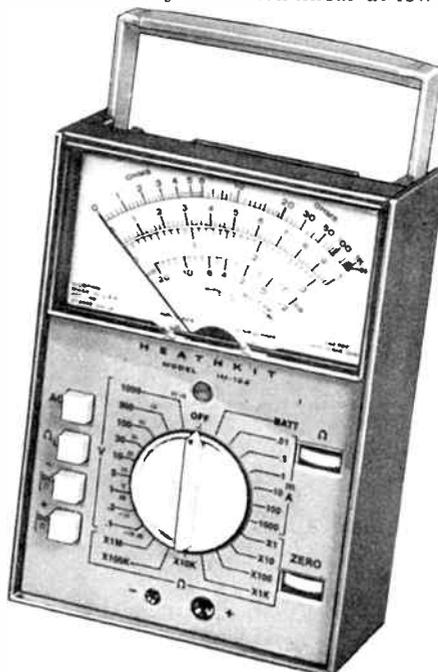The AC ranges of multi-range test meter function in very much the same way as the DC ranges except that a rectifier is incorporated to enable the basic DC meter movement to function, see Fig. 4. As with the DC voltage section of the meter, the amount of loading on the circuit being tested is indicated by the sensitivity in ohms-per-volt. Rectifiers have a tendency to be non-linear at low current



The Heathkit IM-104 multimeter, a modern design providing 53 ranges on four scales. Frequency response up to 50kHz on AC voltage ranges. Input resistance of 10 MΩ on DC voltage ranges.

(Courtesy Heath (Glos.) Ltd.)

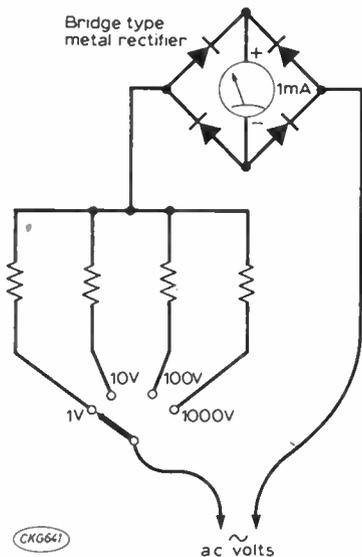


Fig. 4: Incorporation of meter bridge rectifier on AC voltage ranges.

levels and so, in the interest of accuracy, it is common to reduce the sensitivity of the test meter when switched to the AC ranges. The popular Avo Model 8, for instance, has a sensitivity of 20,000 OPV on the DC ranges but only 1,000 OPV on the AC ranges.

The Direct Current Ranges

The basic DC meter movement, as we have seen, will reach full scale when a small current is passed through it. The example shown in Fig. 1 needed 1mA for full scale deflection. If it is desired to measure a larger current, some of the current must be by-passed. The circuit with various resistors which are known as "shunts" is shown in Fig. 5. The value of shunt resistor R3, for instance, is calculated so that when the test meter is measuring 1A, 999 millicamps go via R3 and 1mA passes through the meter.

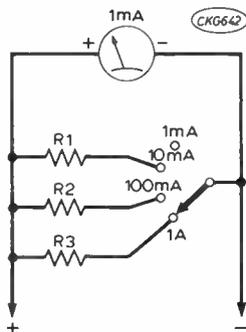


Fig. 5: Switchable shunts to increase current range of basic meter.

It is important to note that when measuring current, some voltage is required to operate the meter, as was shown earlier, when dealing with the DC voltmeter. In this case 0.1 volts will be dropped across the meter terminals. In most cases when making measurements, as in Fig. 6a, this small voltage drop will make negligible difference, being small in relation to the voltages in the circuit. If we try to make a test as shown in Fig. 6b however,

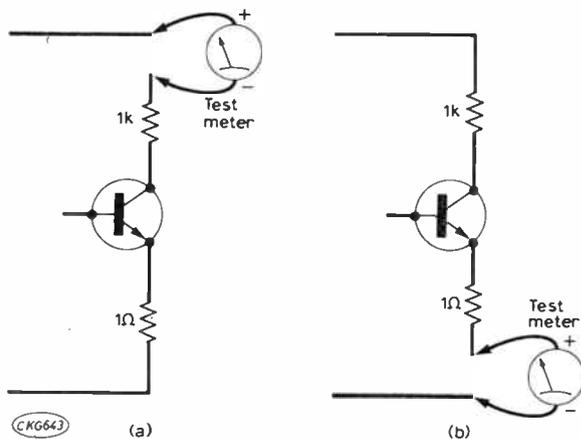



Fig. 6 (a) Correct and (b) incorrect method of inserting meter in transistor circuit.

this is not the case. Here the effect of adding the meter in series with the circuit is to considerably increase the value of the emitter resistor. Increasing this effective value would mean that the current which flowed with the test meter connected would be much less than the current which normally flowed in the circuit.

When checking current flow in low impedance circuits, it is better to measure the voltage across a known resistor and then to calculate the current.

The Resistance Ranges

Figure 7 shows a basic method of resistance measurement. If the test prods are touched together R2 can be adjusted until the meter reads full scale, the current being provided by the battery. As we have seen a 1mA meter when used as a voltmeter

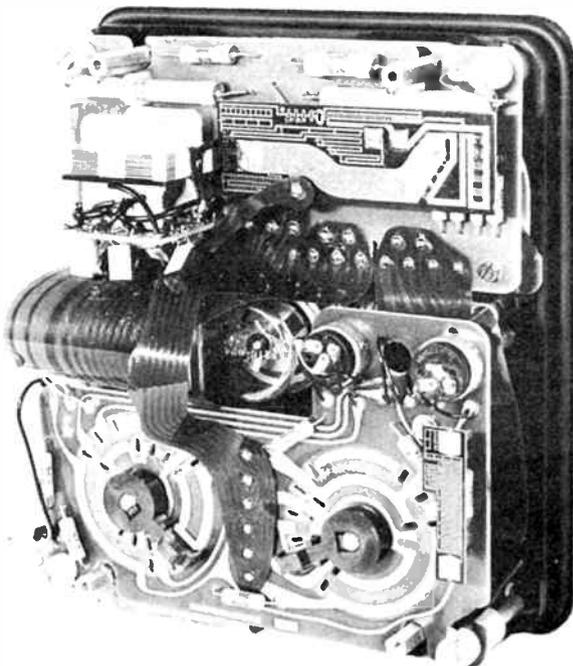

An excellent view of the latest AVO Model 8. It uses printed circuit techniques for shunts and switchboards. (Courtesy AVO Ltd. Dover)

has a sensitivity of 1,000 OPV and here, if the battery is exactly 1.5V, R1 plus R2, plus internal resistance must equal 1,500 ohms, when R2 is set to provide full scale deflection with the test prods touching. If now, instead of touching the test prods together, we connect them to a resistor being tested, of 1,500 ohms, the meter will then read half-scale as an external resistor of the same value as the built-in resistance has been added to the circuit. The centre of the scale would be marked 1,500 ohms and with suitable calibration resistors of between, say, 50 and 50,000 ohms, resistors could be checked using this set-up, with reasonable accuracy.

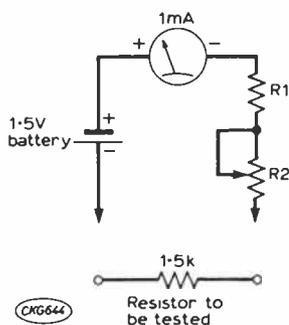


Fig. 7: Basic circuit for measuring resistance.

To divide the range by 10 we can shunt the meter as was done on the current ranges so that the sensitivity of the circuit becomes 100 OPV, enabling R1 and R2 to be reduced to 1/10 of their previous value. Alternatively, we can multiply the range by 10 by fitting a 15V battery and increasing R1 and R2 tenfold. In this way we obtain a meter with a centre scale range of 150, 1,500 and 15,000 ohms on three ranges enabling resistors from below 10 to above 500,000 ohms to be checked with good accuracy.



A large, clear scale with an anti-parallax mirror is the highlight of the latest AVO.

Use of Ohms Range

From the above discussion it will be seen that a current is passed through the component to be tested and that a voltage is also applied across it. In most cases this will do no harm, but it is wise to be aware that voltages of up to 25 or so are possible on the high resistance ranges and that currents in the order of 100mA or more may be found on the low ohms ranges of some test meters. When checking circuits where there is the slightest risk of damage being caused, it is wise to avoid using the highest or lowest ohms range on the test meter and to concentrate tests on the range which applies low voltage and low current. If magnetic devices, such as tape heads, are tested, note that they will be magnetised by the meter current. These tests should not be made, therefore, unless a de-fluxer is available to remove the residual magnetism.

It should be noted that no checks of resistance can be made unless the circuit which is being tested,

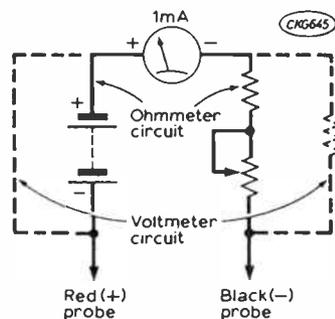


Fig. 8: Illustration of reverse polarity of probes in an ohmmeter circuit.

is completely dead. All voltage sources should therefore be disconnected before tests take place, as, quite apart from giving the wrong results, severe damage can be caused to the test meter and equipment if resistance tests are attempted on live circuits. Devices such as transistors, diodes and electrolytic capacitors are inherently polarity sensitive so the polarity of the voltage output of the test meter should be noted whilst making tests on these devices. As will be seen from Fig. 8 using normal circuit arrangements the polarity of the test prods is normally opposite to the ohms range to that marked on the meter for the voltage and current ranges.

Decibels

Many test meters have a scale marked in decibels marked in + and - values over a total of 15dB's or so. It must be clearly understood that the decibel is not an absolute value, such as the ohm or volt, but, as will be seen from the shape of the dB scale, is a logarithmically based system of comparison. Whilst many test meters are calibrated so that 0dB=0.775V this is just an arbitrary figure. In practical use, such as measuring the frequency response of an amplifier, the signal level is adjusted so that the output when measured with the test meter set to a suitable range, reads 0dB. If the input frequency is then varied the output variation, and hence the frequency response of the equipment being tested, can be read off directly in decibels.

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

5p for 1 Valve.
Each additional Valve add 2p.

DM70	0.83	EF80	0.46	PC86	0.75	PL84	0.88	30C15/	
DY51	0.85	EF83	1.03	PC88	0.75	PL504	0.88	PCF801	1.05
DY86/7	0.42	EF85	0.43	PC97	0.45	PL508	1.05	30C17	1.00
DY802	0.45	EF86	0.60	PC900	0.56	PL509	1.55	30C18/	
EABC80	1.00	EF89	0.91	PC984	0.52	PL802	0.98	PCF805	0.90
EB91	0.38	EF91	1.20	PC988	0.80	PY33	0.66	30F3/PF818	
EB81	0.75	EF92	1.40	PC989	0.65	PY81/800	0.50		1.10
EBF80	0.60	EF95	1.35	PC989	0.65	PY82	0.55	30FL1/	
EBF83	0.62	EF183	0.60	PC989	0.65	PY88	0.60	PCE800	0.75
EBF89	0.58	EF184	0.60	PC989	0.65	PY800A	1.05	30FL2	0.75
EC86	0.75	EF190	0.58	PC989	0.65	PY800	0.50	30FL12	1.05
EC88	0.77	EL34	0.95	PCF200	0.85	PY801	0.50	30FL14	0.85
EC81	0.48	EL36	1.05	PCF201	0.87	U25	1.00	30LI/PCC84	
EC82	0.48	EL81	0.90	PCF802	0.71	U191	1.00		0.52
EC83	0.45	EL84	0.47	PCF802	0.71	U193	0.50	30L15/PCC85	
EC84	0.65	EL85	0.55	PCF806	0.66	UABC80	0.98	U191	1.05
EC85	0.58	EL86	0.95	PCH200	0.88	UABC81	0.70	30L17	0.90
EC88	0.75	EL96	0.70	PCH200	0.88	UBF89	0.90	30P4MR	1.30
EC8189	0.71	EL91	1.81	PCL82	0.64	UCB81	1.00	30P12/PC801	
ECF80	0.55	ELK60	1.30	PCL83	0.66	UCB85	0.80		1.05
ECF82	0.78	EM84	1.18	PCL84	0.63	UCL84	0.70	30P19/PC802	
ECF86	0.71	EM87	1.18	PCL85/85		UFB8	0.90		1.00
ECF81	1.00	EY51	0.88	PD500	1.55	UL84	0.85	30P14/PC801	
ECF83	1.00	EY86/87	0.42	PFL200	0.80	U785	0.50		0.95
ECH84	0.78	EY86	0.64	PFL200	0.80	U786	0.50	30P12/	
ECL80	0.85	EZ80	0.51	PL81	0.75	6P23J/	1.00	PCF800	1.20
ECL82	0.61	EZ81	0.40	PL81A	0.88	6P23J/EF812		30P14/	
ECL83	0.68	GY501	0.90	PL82	0.50			PCL88	1.25
ECL86	0.63	GZ34	0.78	PL83	0.98	30C1/PCF80		30P16	1.05

BP41	3.00	6J6	0.30
8P61	0.75	6J7M	0.45
T41	1.00	6J7GT	0.40
U14	1.00	6K6GT	0.75
U25	0.58	6K7M	0.45
U26	0.85	6K7G	0.30
U191	0.75	6K8M	0.70
UABC80	0.40	6K8G	0.45
UAC42	0.78	6K25	0.78
U6A1	0.75	6L5G	0.55
UBC81	0.45	6Q7M	0.50
UBF80	0.40	6Q7G	0.50
UBF89	0.40	6SL7GT	0.48
UCC85	0.45	6SN7GT	0.48
UCH42	0.75	68Q7GT	0.48
UCH81	0.40	6U5G	0.75
CL82	0.35	6V6G	0.40
UC83	0.70	6V6GT	0.48
UF41	0.75	6X4	0.40
UF89	0.40	6X5G	0.40
UL41	0.85	6X5GT	0.45
UL84	0.48	7B6	0.75
U141	0.48	7B7	0.70
U785	0.40	7C9	1.30
VR105-30	0.40	7C6	0.75
VR150-30	0.40	7H7	0.70
OA2	0.40	7R7	0.75
OB2	0.40	787	2.25
1R5	0.45	7F4	0.75
1R5	0.40	12A7A	0.40
1T4	0.30	12A7T	0.40
384	0.40	12A06	0.45
3V4	0.70	12A07	0.38
5R4GY	0.80	12A X7	0.38
5U4G	0.40	12B A8	0.45
5V4G	0.50	12B B5	0.50
5Y3GT	0.45	30C1	0.80
5Z4G	0.45	30C15	1.05
6J30L2	0.90	30C17	1.10
6A K5	0.40	30C18	0.90
6A M5	0.90	30F6	1.10
6A Q5	0.45	30FL1	0.80
6A S7G	0.85	30FL2	0.75
6A T6	0.45	30FL14	0.90
6A U6	0.80	30LI6	1.05
6B A6	0.28	30LI7	0.95
6B E6	0.35	30P4MR	1.30
6B H6	0.75	30P12	1.05
6B J6	0.55	30P19	1.00
6B R7	1.00	30P1L	0.95
6B S7	1.35	30PL13	1.20
6B W6	0.90	30PL14	1.25
6B X7	0.90	30PL15	1.20
6C4	0.35	35W4	0.50
6C3DG	1.30	35Z4GT	0.70
6C H6	1.40	50C6DG	1.20
6C W4	1.00	807	0.50
6E23	1.05	813	ITT 213
6E25	1.00	813	ITT 213
6E28	0.70	813	ITT 213
6E35	0.65	865A	45.75
6E35	0.45	865A	1.00

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0.60	EF90	0.25	PC86	0.60
AZ31	0.55	EF85	0.35	PC88	0.60
CHL31	1.20	EF86	0.30	PC97	0.50
CL33	1.50	EF89	0.28	PC900	0.48
CY31	0.50	EF91	0.37	PC984	0.40
DAF91	0.30	EF92	0.50	PC885	0.55
DAF96	0.50	EF95	0.40	PC989	0.50
DCC90	1.35	EF98	0.75	PC189	0.60
DF91	0.30	EF183	0.30	PCF80	0.30
DF96	0.50	EF184	0.35	PCF82	0.35
DK91	0.45	EL32	0.60	PCF86	0.60
DK92	0.70	EL33	1.75	PCF801	0.50
DK96	0.60	EL34	0.50	PCF802	0.50
DL92	0.40	EL36	0.60	PCF805	0.90
DL94	0.48	EL37	2.50	PCF806	0.75
DL96	0.55	EL41	0.90	PCF808	0.90
DY86/7	0.35	EL42	0.90	PCF82	0.35
DY802	0.37	EL84	0.28	PCL83	0.66
EABC80	0.88	EL95	0.40	PCL84	0.45
EAF42	0.75	EL80	1.00	PCL85	0.50
EB91	0.22	EM80	0.45	PCL86	0.45
EB33	1.00	EM81	0.60	PCL805/85	
EB41	0.75	EM84	0.35		
EB81	0.38	EM85	1.00	PD500	1.50
EBF80	0.40	EY51	0.40	PEN45	0.75
EBF83	0.40	EY86	0.40	PL36	0.55
EBF89	0.32	EZ40	0.75	PL81	0.50
EHL31	1.50	EZ41	0.75	PL82	0.45
EC81	0.40	EZ80	0.28	PL83	0.45
EC82	0.38	EZ81	0.26	PL84	0.40
EC83	0.35	GY501	0.80	PL500	0.75
EC84	0.30	GZ30	0.45	PL504	0.75
EC85	0.40	GZ32	0.50	PL508	0.90
EC88	0.40	GZ34	0.85	PL509	1.55
ECH36	1.25	GZ37	1.25	PL802	0.95
ECH42	0.30	HN209	1.50	PL84	0.40
ECH81	0.20	KT451	0.75	PLX4	3.50
ECH83	0.45	KT66	2.50	PX25	0.50
ECL80	0.55	KT81 (7C5)		PY81	0.30
ECL82	0.35			PY82	0.35
ECL83	0.70	KT81	1.75	PY83	0.38
ECL86	0.40	KT88	2.90	PY88	0.40
ECL880	3.00	KT451	1.00	PY900	1.00
EF7A	1.20	MU14	1.00	PY81/800	0.50
EF39	1.20	N74	2.75	PY901	0.50

TRANSISTORS-INTEGRATED CIRCUITS

EXPRESS POSTAGE

3p for first Transistor, for each additional add 1p.

AA119	0.7	BD132	0.50
AAZ13	0.10	BF115	0.22
AAZ15	0.10	BF167	0.25
AC107	0.35	BF173	0.28
AC126	0.25	BF179	0.33
AC127	0.25	BF180	0.35
AC128	0.20	BF181	0.35
AC176	0.25	BF194	0.13
AC187	0.20	BF195	0.13
AC188	0.20	BF197	0.15
ACY21	0.22	BF200	0.32
ACY39	0.65	BF861	0.25
AD140	0.50	BF898	0.25
AD149	0.50	BFX29	0.28
AD161	0.38	BFX28	0.22
AD182	0.39	BFY50	0.20
AF115	0.25	BFY51	0.20
AF116	0.25	BFY52	0.20
AF117	0.20	BFW10	0.81
AF186	0.40	BI100	0.15
AF239	0.44	BY128	0.14
ABY27	0.30	BY127	0.15
ABY28	0.25	BXZ61 series	
BA102	0.25		0.20
BA115	0.10	BZY88 series	
BC107	0.12		0.10
BC108	0.12	CR81-05	0.30
BC109	0.12	CR81-40	0.45
BC113	0.16	CR83-05	0.40
BC117	0.21	CR83-40	0.55
BC143	0.30	MJE340	0.50
BC147	0.12	MJE370	0.68
BC148	0.14	MJE320	0.65
BC190C	0.14	MJE2855	1.10
BC182	0.12	MJE3055	0.75
BC182L	0.12	MFP102	0.40
BC184L	0.13	MFP103	0.38
BCY32	1.20	MFP104	0.35
BCY33	0.38	MFP105	0.48
BCY34	0.45	MK7404	0.60
BCY70	0.15	OA5	0.60
BCY71	0.20	OA10	0.40
BCY72	0.15	OA79	0.10
BCZ11	0.65	OA81	0.10
BD121	1.00	OA91	0.10
BD124	0.30	OA90	0.08
HD131	0.45	OA202	0.10

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

OC16	1.00	ZTX500	0.15	2N2646	0.50
OC20	2.00	ZTX501	0.15	2N2904	0.20
OC23	1.25	ZTX503	0.16	2N2904A	0.25
OC25	0.40	ZTX531	0.25	2N2906	0.32
OC28	0.70	ZTX550	0.18	2N2905A	0.25
OC32	0.55	1N3014	0.06	2N2906	0.20
OC35	0.65	1N4001	0.8	2N2926	0.10
OC42	0.40	1N4002	0.7	2N3053	0.20
OC44	0.18	1N4003	0.8	2N3055	0.60
OC45	0.18	1N4004	0.8	2N3255	0.80
OC71	0.15	1N4005	0.10	2N3614	0.59
OC72	0.25	1N4006	0.12	2N3615	0.65
OC76	0.30	1N4007	0.12	2N3792	0.11
OC77	0.55	1N4009	0.08	2N3703	0.12
OC81	0.28	1N4148	0.06	2N3704	0.14
OC81D	0.28	18921	0.07	2N3705	0.12
OC81Z	0.45	18Z033	0.20	2N3706	0.10
OC83	0.25	18Z051A	0.10	2N3707	0.13
OC84	0.65	18Z00A	0.20	2N3708	0.07
OC170	0.25	18Z010	0.25	2N3709	0.10
OC171	0.20	2N696	0.16	2N3710	0.11
OC200	0.55	2N697	0.15	2N3711	0.11
OC201	0.80	2N706	0.10	2N3819	0.85
OC202	0.90	2N706A	0.12	2N3820	0.80
OC203	0.55	2N1305	0.25	2N3923	0.50
OC210	0.25	2N1301	0.25	2N3933	0.15
OC211	0.20	2N1302	0.25	2N3933	0.15
OC212	0.55	2N1302	0.18	2N3904	0.20
OC213	0.45	2N1303	0.18	2N3905	0.25
OC214	0.20	2N1304	0.22	2N3906	0.16
OC215	0.29	2N1305	0.22	2N4058	0.15
OC216	0.25	2N1306	0.25	2N4059	0.10



WILMSLOW AUDIO

THE Firm for speakers!


SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£6.60
Baker Group 35, 3, 8 or 15 ohm	£7.50
Baker Group 50/12, 8 or 15 ohm	£12.50
Baker Deluxe	£9.75
Baker Major	£7.50
Baker Superb	£12.00
Baker Regent	£7.00
Celestion P578 (for Unilex)	£2.55
Celestion MF1000, 8 or 15 ohm	£10.45
Celestion HF1300, Mk II	£6.16
Celestion G12M, 8 or 15 ohm	£12.00
Celestion G12H, 8 or 15 ohm	£15.00
Celestion G15C, 8 or 15 ohm	£24.00
Celestion G18C, 8 or 15 ohm	£33.00
EMI 13 x 8, 3, 8 or 15 ohm	£2.15
EMI 13 x 8 d/c, 3, 8 or 15 ohm	£2.35
EMI 13 x 8 t/w, 3, 8 or 15 ohm	£3.60
EMI 13 x 8 type 350, 8 ohm	£8.25
EMI 8 x 5, cer. mag., 8 ohm	£1.65
EMI 8 x 5, 10 watt d/c roll surr., 8 ohm	£2.50
EMI 6 1/2" 93850, 4 or 8 ohm	£2.80
EMI 5" 98132CP, 8 ohm	£2.30
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2.65
Elac 6 1/2" d/c roll surr., 8 ohm	£3.35
Elac 6 1/2" d/c cone, 8 ohm	£2.65
Elac Tweeter TW4 4"	£1.21
Elac 10" 8 ohm	£2.65
Fane Pop 100 watt 18"	£22.50
Fane Pop 60 watt 15"	£13.00
Fane Pop 50 watt 12"	£11.00
Fane Pop 25/2 12"	£6.40
Fane Pop 15 watt 12"	£4.40
Fane Crescendo 12A or 12B	£29.00
Fane Crescendo 15	£36.00
Fane Crescendo 18	£47.50
Fane 807T 8" d/c roll surr. 8 or 15 ohm	£3.85
Fane 808T 8" d/c 8 or 15 ohm	£2.75
Goodmans 8P 8 or 15 ohm	£4.49
Goodmans 10P 8 or 15 ohm	£4.70
Goodmans 12P 8 or 15 ohm	£11.65
Goodmans 15P 8 or 15 ohm	£18.00
Goodmans 18P 8 or 15 ohm	£31.00
Goodmans 12P-D 8 or 15 ohm	£15.25
Goodmans 12P-G 8 or 15 ohm	£14.50
Goodmans 12AX Audiomax 8 or 15 ohm	£39.65
Goodmans Audiom 100	£9.50
Goodmans Axent 100	£6.60
Goodmans Axiom 401	£15.10
Goodmans Twinaxiom 8, 8 or 15 ohm	£6.79
Goodmans Twinaxiom 10, 8 or 15 ohm	£7.61
Kef T27	£4.75
Kef T15	£5.75
Kef B110	£6.75
Kef B200	£7.50
Kef B139	£11.75
Kef DN8	£1.92
Kef DN12	£4.12
Kef DN13	£2.75
Richard Allan 12" d/c 3 or 15 ohm	£2.50
Richard Allan CG8T 8" d/c 8 ohm	£6.35
WMT1 speaker match. trans. 3-15 ohm	£1.10
Wharfedale Super 10 RS/DD	£9.80
2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm	£5.65
7" x 4" 3, 8 or 15 ohm	£1.38
8" x 5" 3, 8 or 15 ohm	£1.38
10" x 6" 3, 8 or 15 ohm	£1.92

SPEAKER KITS

Wharfedale Linton 2 (pair)	£19.25
Wharfedale Glendale 3 (pair)	£34.50
Wharfedale Dovedale 3 (pair)	£52.00
Richard Allan Twinkit (each)	£8.25
Richard Allan Triple 8 (each)	£13.00
Richard Allan Triple (each)	£18.00
Richard Allan Super Triple (each)	£21.50
Goodmans DIN 20 (each)	£8.75
Fane Mode 1 (each)	£9.90
Peerless 20-2 (each)	£10.41
Kefkit 2 (each)	£23.50
Kefkit 3 (each)	£34.00
Helme XLK25 (pair)	£18.17
Helme XLK50 (pair)	£37.18
Baker Major Module	£9.50

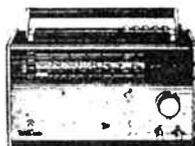P.A. and Hi-Fi Speaker Cabinets.
Send for Free booklet "Choosing a Speaker".
Carr. and Insurance 75p per kit (£1.50 pair).



PA/DISCO AMPLIFIERS

Carriage and Insurance £1.00	
Baker Major 100 watt	£46.00
Linear 30/40	£25.00
Linear 40/60	£30.00
Linear 80/100	£55.00

RADIOS/CASSETTES

Grundig Solo Boy	£16.00
Grundig Top Boy	£17.75
Grundig Party Boy 500	£22.75
Grundig Melody Boy 500	£26.75
Grundig Elite Boy 500	£26.75
Grundig Signal 500	£26.50
Grundig Yacht Boy 210	£34.00
Grundig Melody Boy 1000	£38.75
Grundig Satellit 2000	£121.00
Grundig C410 Cassette	£28.50
Grundig RF430 mains radio	£26.75
Grundig RF310 mains radio	£22.00
Tandberg TP41	£43.00
ITT Weekend Auto	£18.00
ITT Golf Preset	£24.50
ITT Colt	£11.50
ITT Europa	£20.50
ITT SL53 Cassette	£25.75
ITT Studio 60M Cassette	£32.75
ITT Studio 73 Cassette	£48.00
Bush VTR178 5 band (inc. air)	£29.00
Koyo KTR1770 11 band	£58.95
Koyo KTR1663 or 1664 8 band	£42.00
Koyo KTR1883 5 band	£22.00
Murphy BA209 Radio/Cassette	£32.75

Carriage and Insurance 75p.
FREE with each radio—World radio stations book.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 35p per speaker (tweeters and crossovers 20p)

ALL PRICES QUOTED INCLUDE V.A.T.

WILMSLOW AUDIO Dept. P.W.

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

SINCLAIR CALCULATORS

Cambridge Kit £23.95 (£2.80)
Cambridge Assembled £25.95 (£3.00)
Executive £32.95 (£3.70)
Executive Memory £39.95 (£4.40)

FERRANTI ZN414

IC radio chip with data £1.20 (23p). Also available kit of parts to build a MW/LW radio £2.39 (35p). Send sae for free leaflet.

SINCLAIR PROJECT 80

AFU £5.95 (80p)	
Z40 £4.65 (67p)	
Z50 £5.95 (80p)	
O18 £6.70 (87p)	
PZ5 £4.28 (55p)	
PZ6 £6.95 (92p)	
PZ8 £6.95 (92p)	
Decoder £6.45 (85p)	Trans for PZ8 £2.95 (50p)
Tuner £9.95 (£1.20)	Stereo 80 £9.95 (£1.20)



SINCLAIR SUPER IC12

6W rms power with 44 page booklet and printed circuit £2.10 (43p)



SWANLEY IC TOMORROW

The world's most powerful IC amplifier. Similar to the IC12 but rated at 10W rms power. Supplied with data but no printed circuit £2.60 (47p)

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.55 (26p). Stereo model with balance control £3.50 (46p).

IC12 POWER KIT

Supplies 28V 0.5 Amps £2.47 (50p)

LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1.10 (27p). 5" x 8" 8 ohm £1.55 (37p).

PREAMPLIFIER KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1.30 (24p). Stereo model £2.30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1.20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR

BARGAIN

£3.75 (60p)
The most versatile battery eliminator ever offered. Switched output of 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500mA.



Other eliminators stocked 50 mA unless stated:—
4 1/2V £1.50 (30p); 6V £1.50 (30p); 9V £1.50 (30p);
7 1/2V cassette type £2.25 (30p); Double 4 1/2V + 4 1/2V £2.50 (35p); 6V + 6V £2.50 (35p); 9V + 9V £2.50 (35p).

IC RADIO CHIP TBA851

The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1.75 (29p).

S-DECS AND T-DECS

S-DEC £1.98 (31p)

T-DEC £3.83 (47p)

µ-DEC A £3.99 (51p)

µ-DEC B £6.99 (81p)

IC carriers:—

16 dill £1.77 (25p)

10 TOS £1.68 (24p)



ZIPPY CABINETS

Attractive plastic instrument cases in 4 sizes. P1 80 x 50 x 30mm 60p (25p). P2 115 x 65 x 40mm 87p (30p). P3 155 x 90 x 50mm £1.20 (35p). P4 210 x 125 x 70mm £1.80 (45p).

ECONOMICAL QUADRAPHONICS

£9.95 (£1.30)
Complete self contained matrix quadrasonic synthesizer in attractive cabinet. Just feed output of ordinary stereo hi-fi into it and hook up to 4 speakers to obtain the latest experience in sound.

SWANLEY ELECTRONICS

PO BOX 68, SWANLEY, KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome.

No vat on overseas orders which are most welcome.

EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

LEARNING BY PRACTICAL PROJECT STEPS

PART 6—GROUNDED EMITTER AMPLIFIERS

LAST month's emitter followers were all types of current amplifiers. In every case the output voltage was the same, or slightly less than the input voltage. Many applications require voltage amplification—e.g. raising the output level of a microphone to an extent that when current amplification is applied the resultant signal could drive a loudspeaker. The grounded emitter amplifier will provide a reasonable degree of voltage and current amplification and is, perhaps, the most used type of amplifier stage in the whole of electronics. Because both voltage and current is amplified we call the grounded emitter stage a *power amplifier* but not necessarily in the sense that you can expect several watts of useful output; specialised power stages are better equipped for the latter purpose and these will be covered later in the series.

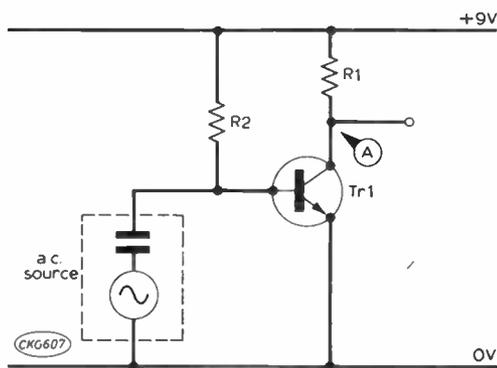


Fig. 42: It is difficult to predict a value for R2 to set the potential at A to mid-rail unless the h_{FE} for Tr1 is accurately known.

Referring to Fig. 42, we know that we can make the voltage at point A go to +9V by ensuring that the transistor is cut off (i.e. by passing zero base current) and conversely we can make it fall to zero volts by passing a certain amount of base current through R2. By knowing an accurate value of h_{FE} for the transistor we could calculate a value for R2 that will cause just sufficient collector current to flow that the voltage drop across R1 will be 4.5V. Theoretically we could hold the voltage at A exactly

mid-way between the two supply rails. At the same time we could connect a source of voltage through a capacitor to the base of the same transistor and (assuming the source voltage was zero at the time) this would not affect our bias condition. However, as soon as we begin to generate a voltage from the source this would cause current to be added or subtracted from the bias current (depending on the polarity of the a.c. signal) and would cause the voltage at A to rise and fall in exact relation—except for the 180° change of phase. Having point A biased “mid rail” allows maximum peak swings of voltage without the transistor clipping (going totally out of conduction) or bottoming (going into saturated conduction) unsymmetrically. In the ideal amplifier the voltage seen at A should faithfully represent that from the source.

In practice the method of obtaining this mid-rail bias shown in Fig. 42 is not very satisfactory because the h_{FE} for the transistor must be accurately known and this can vary widely from one device to another (even though they may be of the same type number).

Base current

A simple way of compensating for this device variation is to use the potential at A as the voltage source for providing the base current—shown in Fig. 43. If the potential at A is too high the base current will be increased, hence the collector potential falls; conversely if A tends to be too low the base current decreases and the potential at A is forced to rise. By careful selection of component values this feedback bias circuit caters well for quite wide variations in the gains of transistors. It is not perfect by any means but is an improved way of getting a mid rail voltage reliably. You can make up the circuit of Fig. 43 on T Dec and try different BC108 devices. The voltage you measure should not fall outside the range of +3.5 to +5.5V. For those interested it is quite easy to arrive at the component values. First of all assume that the collector load is to be 1k Ω . For the potential at A to be +4.5V (assuming a 9V supply) the drop of 4.5V across R1 will be caused by a collector current of

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1-05p** P & P 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **27 1/2p** POST & PACKING 16p

Tested and Guaranteed Paks



- | | | | |
|-----|-----|--|---------------|
| B79 | 4 | IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic | 55p |
| B81 | 10 | Reed Switches, 1" long. 1/8" dia. High Speed P.O. type | 55p |
| B99 | 200 | Mixed Capacitors. Approx. quantity, counted by weight | 55p P & P 15p |
| H4 | 250 | Mixed Resistors. Approx. quantity counted by weight | 55p P & P 15p |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked. | 55p |
| H38 | 30 | Short lead Transistors, NPN Silicon Planar types | 55p |
| H39 | 6 | Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945 | 55p |
| H41 | 2 | Sil Power transistors comp pair BD151/132 | 55p |



Unmarked Untested Paks

- | | | | |
|-----|-----|---|-----|
| B1 | 50 | Germanium Transistors PNP, AF and RF | 55p |
| B66 | 150 | Germanium Diodes Min. glass type | 55p |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202 | 55p |
| B86 | 100 | Sil. Diodes sub. min. IN914 and IN916 types | 55p |
| H16 | 15 | Experimenters' Pak of Integrated Circuits, Data supplied | 55p |
| H20 | 20 | BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts. | 55p |
| H34 | 15 | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can. | 55p |

Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

£2.75 p.p. 38 1/2p Per instrument

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73p.
Extension Telephones. 71p each. p.p 27 1/2p. £1.37 1/2 for 2. P.&P. 55p.
These phones are extensions and do not contain belts.

A Cross Hatch Generator £3-85 post paid

A complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. A project in the Sept. '72 edition of Television.

New Paks

TESTED & GUARANTEED

- | | | | |
|-----|---|---|-----|
| H63 | 4 | 2N3055 type NPN Sil. power transistors. Below spec. devices | 55p |
| H64 | 4 | 3819 N Channel FETs | 55p |
| H65 | 4 | 40361 Type NPN Sil. transistors TO-5 can comp to H66 | 55p |
| H66 | 4 | 40362 Type PNP Sil. transistors TO-5 can comp to H65 | 55p |

UNTESTED, UNMARKED

- | | | | |
|-----|----|--------------------------------------|-----|
| H67 | 10 | 3819N Channel FETs plastic case type | 55p |
|-----|----|--------------------------------------|-----|

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can
TYPE "B" PNP Silicon, plastic encapsulation
TYPE "E" PNP Germanium AF or RF
TYPE "F" NPN Silicon plastic encapsulation
TYPE "G" NPN silicon similar ZTX 300 range
TYPE "H" PNP silicon similar ZTX 500 range

8 RELAYS FOR VARIOUS TYPES P & P 27 1/2p £1-10p

High Speed Magnetic Counter



4 digit (non-reset) 24V or 48V (state which)
4 x 1 x 1 in. 33p. P.&P. 5p.

Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shattering low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min. 15. HFE Min. 15.
40 Watt 1-12 13-25 26-50
22p 20p 18p
90 Watt 26p 24p 22p
Range 2. VCE. Min. 40. HFE Min. 40.
40 Watt 1-12 13-25 26-50
33p 31p 29p
90 Watt 38p 36p 33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in *Practical Wireless* Dec. issue, complete with application data £1-10p.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 15p Wall Chart 18p

LOW COST DUEL IN LINE I.C. SOCKETS

14 pin type at 16 1/2p each } Now new low profile
16 pin type at 18p each } type

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak.

Please ask for Pak P.1. only 55p

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME
ADDRESS

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co. Reg. No B20919

Dept. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.


TELEPHONE: SOUTHEND (0702) 46344.

TUNERS TRANSMITTERS AMPLIFIERS...

NEW FROM WOLFFERS ELECTRONICS

INEXPENSIVE BUT RELIABLE EQUIPMENT—
IDEAL FOR THE YOUNGER RADIO ENTHUSIAST

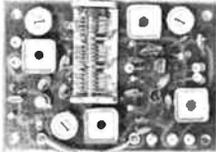W.T.7 AIRCRAFT BAND TUNER
From 110 Mhz—130 Mhz
I.F. 1.5 Khz 12 volt supply
£14.45



Not Illustrated

W.T.9. V.H.F. TUNER
142 Mhz—162 Mhz
I.F. 1.5 Khz 12 volt supply
£14.45


W.T.15
TWO METRE
VARICAP TUNER
144 Mhz—146 Mhz
I.F. 1.5 Khz
12 volt supply
£14.08



Not Illustrated

W.A.7 V.H.F. ANTENNA AMPLIFIER 60 Mhz—
150 Mhz. 15 d.b. gain at 100 Mhz
9—15 volt supply. 6 M/Amps £2.97

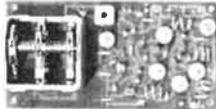W.Z.9 TWO METRE
F.M. Transmitter
V.F.O. Control
Output:
200 M/Watts
Frequency 144—146 12 volt supply £18.63



Also Available:

CRYSTAL SET KIT which comes complete
with all components and earphone £1.99

*All Prices shown are recommended retail
and include VAT.

Available through leading Radio and Hi-Fi
Dealers or direct from:—

TRADER IMPORTS

4 & 7 CASTLE STREET · HASTINGS · SUSSEX
Telephone Hastings 2875
Sole Distributors for the United Kingdom
Trade Enquiries Welcome.

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 405285

SPECIAL OFFER

Used 19" TV Tubes. Type AW 47-91. Perfect condition. 6 months
guarantee. £3 carr. paid.

Complete untested TV Sets 19" 405-line Types £3.50 carr. and
ins. paid.

19" 625-line types untested. Complete with UHF Tuner £5.50
carr. and ins. Paid.

One Students and One Instructors Wireless Procedure Training
Set, each unit housed in a small wood box and comprises Mike,
Single L.R. Phone and connectors. Requiring Bell Battery (not
supplied) to make intercom. £1.30 post paid.

Small Clock Type Sangamo Weston 200—250v 200 r.p.m. mains
motor with Gear train (ex slot machine) Fair condition 60p
post paid.

½ cwt. of ex Government Scrap Resistors, Panels, Gears, etc
30p carr. 80p.

Speakers removed from TV sets. All 3 ohm, 2½ watts 7 x 4, 6 x 4,
8 x 2½. All at 27p. Post and packing 12p.

Top Quality Tape, Reel to Reel 5" LP 55p. 5½" LP 60p. 7" ST 66p.
7" LP 80p. Cassette Types C60 35p, C90 45p. Post on any tape 12p.

Tap Earpiece, 8 ohm, magnetic, 3-S 12p post paid.

Ex Equipment Valves all Tested before despatched. 3 months
guarantee on all valves. Single valves post 3p, over post paid.

ARP12	6p	EF184	20p	PY801	17p
DY86	20p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	15p	UI91	20p
EBF89	15p	PCL84	15p	6BV7	12p
ECC81	12p	PCL85	20p	6F23	15p
ECC82	12p	PL36	17p	30F5	12p
EY86	20p	PY81	10p	30FL1	20p
EF183	20p	PY800	17p	30P19	10p

ABOVE PRICES INCLUDE V.A.T.

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man
in every field of Electronics today—both in the U.K. and
throughout the world. We offer the finest home study
training for all subjects in radio, television, etc., especially
for the CITY & GUILDS EXAMS (Technicians' Certifi-
cates); the Grad. Brit. I.E.R. Exam.; the RADIO
AMATEUR'S LICENCE; P.M.G. Certificates; the
R.T.E.B. Servicing Certificates; etc. Also courses in Tele-
vision; Transistors; Radar; Computers; Servo-mech-
anisms; Mathematics and Practical Transistor Radio course
with equipment. We have OVER 20 YEARS' experience
in teaching radio subjects and an unbroken record of
exam. successes. We are the only privately run British
home study College specialising in electronics subjects only.
Fullest details will be gladly sent without any obligation.

To: British National Radio & Electronics School, P.O. Box 156,
Jersey, C.I.

Please send FREE BROCHURE to

NAME Block

ADDRESS Caps.

..... Please

..... W.C. 44

BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL

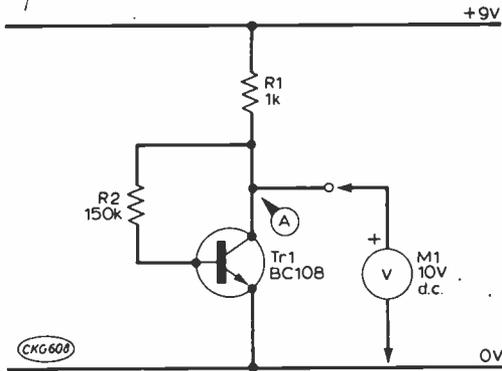


Fig. 43: Using the potential at A as the driving source for base current helps compensate for variations in h_{FE} .

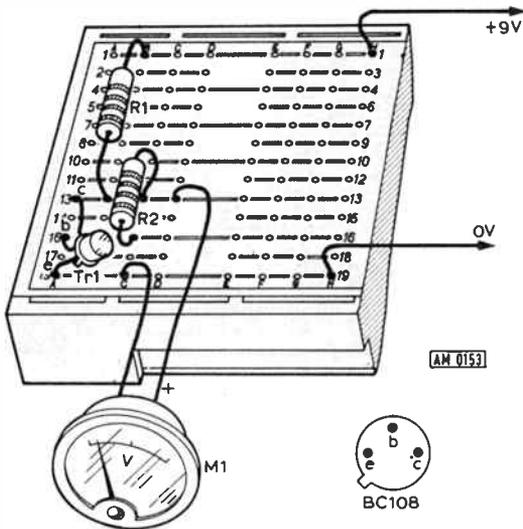


Fig. 44: Component layout for Fig. 43.

4.5mA. If we expect an h_{FE} of around 200 for the BC108 this means that the base current needed to cause 4.5mA collector current is $4.5/200 = 0.0225\text{mA}$. The value of R2, to give this current is calculated from the potential difference across it (potential at A minus the 0.6V base emitter drop) divided by the base current $3.9/0.0225\text{k}\Omega = 170\text{k}\Omega$. The small base current drawn will theoretically modify our original assumption of the potential at A but is so small that it can be ignored. Strictly speaking we should have shown R2 as having a value of 170k Ω but because of other experiments to follow we have made it 150k Ω . The effect of this is to cause the quiescent voltage to be slightly less than mid-rail—but near enough for the experiment.

A crystal microphone is a very easily obtainable source of a.c. voltage that is of a capacitive nature and this can be connected straight across the base of Tr1 and ground of our circuit without affecting the bias conditions (see Fig. 45). Note that we have split the value of our original R2 between two resistors (R2 and R3) in series. Initially leave out the capacitor C1 and connect a meter set to a low a.c. range through a capacitor to point A. Most modern

test meters have this capacitor built into them if you use the input socket marked "Output". The capacitor is there so that the meter only responds to a.c. components on top of the d.c. quiescent voltage at A. Whistle loudly into the microphone and you should see a slight movement of the meter (probably 1V maximum).

Remember, though, that the output from the microphone is unlikely to be greater than a few tens of millivolts. Clearly there is some form of voltage amplification. If you think about it, though, the a.c. fluctuations at A are being fed back, out of phase, to the base through resistors R2 and R3. This will negate the input signal and the overall gain of the amplifier is going to be considerably impaired. We can, however prevent the a.c. component of the feedback signal reaching the base by connecting a capacitor from the junction of R2 and R3 to ground. Do this while whistling into the microphone and you should see at least a two to one improvement in amplification. We call C1 a decoupling capacitor and it should be of a high enough capacitance to shunt even the lowest frequencies to ground.

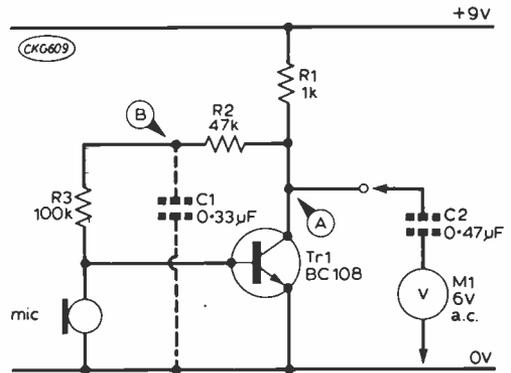


Fig. 45: A signal from a crystal microphone can be superimposed on the bias current but the components have to be slightly modified. Use a meter with an "Output" connection switched to a.c. or alternatively insert C2 when using an a.c. voltmeter.



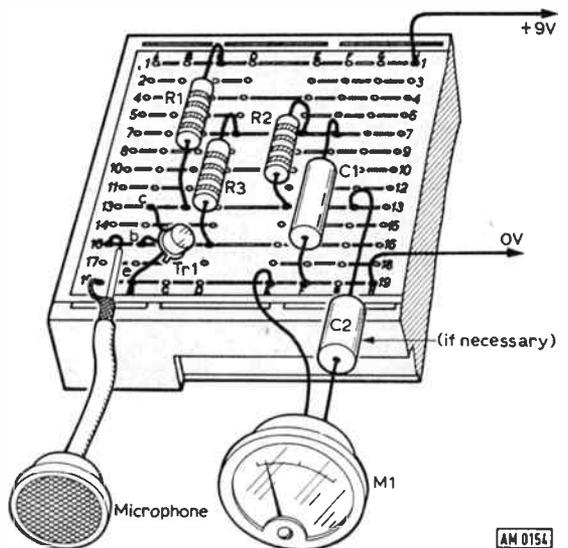


Fig. 46: Component layout for Fig. 45.

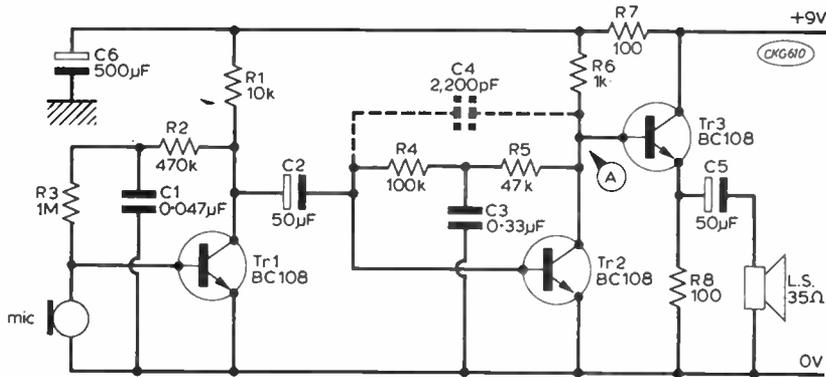

◀ Fig. 47: A basic amplifier capable of driving a small loudspeaker from a crystal microphone and suitable for an intercom or baby alarm.

Fig. 48: Component layout for Fig. 47.

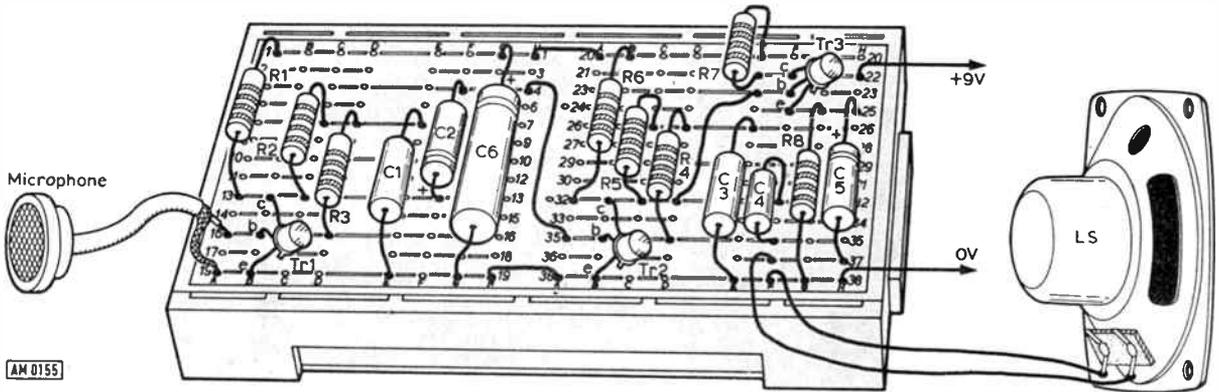

AM 0155

The output current from a crystal microphone is very small—because of its high impedance—particularly at low frequencies but there must be quite a reasonable current generated between collector and emitter of the transistor to give rise to the voltage swings we can see at point A. Thus the transistor can be seen to give both current and voltage amplification. The component values in Fig. 45 are not really ideal for coupling from a crystal microphone because we require a fair amount of a.c. base current from the source, and as mentioned earlier, there is not much of this available at low frequencies. The low frequency response of this amplifier would therefore be pretty poor. We can, however, use exactly the same approach to make a stage that needs only one tenth of the input current by increasing all our resistance values by factors of ten (the first stage of Fig. 47. The output from the collector of Tr1 is now coupled as an a.c. signal source to the base of Tr2 which, excluding C4, is identical to the stage we have just described. Before connecting C4 or Tr3 measure the a.c. signal at point A exactly as before; you should see a really high voltage swing (getting on for three or four volts) and more than that, you can get a useful reading for ordinary speech a few inches away from the microphone.

The circuit is clearly providing more voltage gain and has a more useful response at the lower frequency of the human voice. Obviously by increasing the gain at low frequencies we must be overdoing it at high frequencies therefore we insert capacitor C4 which is used, deliberately, to feedback signal from the collector of Tr2 to its base. Because it has a low value it will provide more negative feedback


at high frequencies than at low frequencies and hence helps to linearise the frequency response of the two stage amplifier. Use the "whistle and speech" test to see that the amplitude for the whistle is reduced but the level for normal speech has not been appreciably affected. Because we now have a useful voltage swing at A for speech we can use a current amplifier (an emitter follower) to give sufficient current at that voltage to drive a loudspeaker. This is provided by Tr3.

Note that it is necessary to decouple the power rail between the output stage and the amplifiers by means of R7 and C6. Without these components the current drawn by the output transistor could cause voltage variations on the line which are then seen as a form of signal by the preceding stages and amplified. This leads to instability and the whole circuit would oscillate wildly.

The amplifier of Fig. 47 does not have a particularly good frequency response but is quite adequate for intercom or baby alarm applications. No volume control is provided and in some circumstances you might encounter acoustic feedback (howl-round). This can be prevented by keeping the microphone and the loudspeaker well apart.

A problem with the circuits we have covered, so far, is that the voltage gain is very much dependent on the h_{FE} of the transistor in question. There are other circuits which—at the expense of a little gain—enable us to get what there is under reasonably accurate control.

To be continued

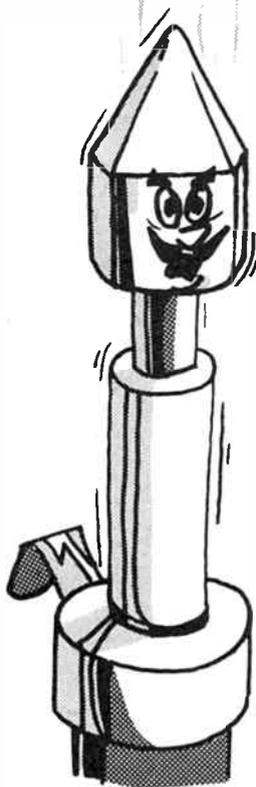

The Hot-Head

You know his type...always blowing hot and cold... getting overheated just when you need him to be controlled and efficient. It's the same with some people's soldering irons.

Hopelessly inefficient heat control can make soldering operations a nightmare; if this is what soldering means to you it's time you woke up to Antex.

Choose a new model from the comprehensive Antex range of soldering instruments, with low-leakage characteristics, unique construction advantages and really precise heat control.

Choose ANTEX—the warm hearted iron

(and keep your cool)

MODEL X25 ▶

220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed. **PRICE £2.05** (rec. retail) P & P 10p. Suitable for production work and as a general purpose iron.

MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet. **PRICE £3.48** (rec. retail) P & P 12p.



MODEL G ▶

18 watt miniature iron, fitted with long-life iron-coated bit 3/32" Voltage 240, 220 or 110 2 other spare bits available 1/8" and 3/16" **PRICE £2.26** (rec. retail) P & P 10p.

MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64" including Heat Shield. **PRICE £2.48** (rec. retail) P & P 10p.

MODEL MLX KIT

Battery operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder". **PRICE £2.54** (rec. retail) P & P 12p.



MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, and "How to Solder" booklet. **PRICE £3.25** (rec. retail) P & P 10p.



MODEL C

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE £2.05** (rec. retail) P & P 10p.

ST3 Stand — This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration.



PRICE: £1.00 (rec. retail) P & P 10p.

ALL PRICES include VAT at 10%



Please send the following:


Please send the ANTEX colour catalogue.

I enclose cheque/P.O./Cash (Giro No. 258 1000) PW4

NAME _____

ADDRESS _____

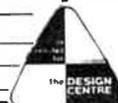From radio or electrical dealers, car accessory shops or in case of difficulty direct from:
ANTEX LTD. FREEPOST PLYMOUTH PL1 1BR
(no-stamp required) Tel 0752 67377



Fully guaranteed Individually packed VALVES

B12H	£3.00	ECL86	40p	N78	£2.75
CY31	45p	EF36	60p	OA2	40p
DAP96	45p	EF37A	1.00	OB2	40p
DK96	60p	EF40	62p	PABCO	35p
DL92	45p	EF41	65p	PC90	48p
DL94	45p	EF83	1.10	PC84	36p
DL96	55p	EF85	31p	PC85	40p
DM70	60p	EF86	27p	PC88	55p
DY86	35p	EF89	25p	PC89	45p
DY87	30p	EF92	40p	PC169	50p
DY802	30p	EF92	40p	PC82	35p
E88CC/01	£1.08	EF95	35p	PC82	35p
E180CC	65p	EF184	31p	PC84	54p
E182CC	£1.15	EF1200	60p	PC86	54p
EAS0	21p	EL34	50p	PC200	75p
EAB30B	35p	EL36	47p	PC201	75p
EAF42	55p	EL41	55p	PC201	75p
EB91	20p	EL81	55p	PC805	90p
EBC33	60p	EL82	52p	PC806	65p
EBC41	65p	EL94	21p	PC808	85p
EBF60	40p	EL85	44p	PC1200	70p
EBF80	40p	EL86	35p	PC181	50p
EBF83	40p	EL90	60p	PC182	45p
EBF89	27p	EL95	36p	PC183	35p
ECC41	35p	EL96	38p	PC184	35p
ECC42	25p	EL504	70p	PC186	45p
ECC83	35p	EM31	60p	PC1805	50p
ECC84	27p	EM80	45p	PD500	1.30
ECC85	35p	EM84	35p	PL200	65p
ECC86	40p	EM87	70p	PL202	75p
ECC88	35p	EY51	40p	PL28	65p
ECC89	65p	EY81	40p	PL41	40p
ECP80	31p	EY86	40p	PL82	40p
ECP82	35p	EY88	40p	PL83	45p
ECP83	67p	EZ40	50p	PL84	30p
ECP801	40p	EZ41	75p	PL500	75p
ECH49	70p	EZ90	23p	PL504	75p
ECH81	30p	EZ81	27p	PL508	90p
ECH83	40p	EY601	70p	PL509	1.10
ECH84	40p	EZ34	60p	PL802	95p
ECL80	40p	EZ37	63p	PY33	65p
ECL82	31p	KT56	£2.30	PY80	33p
ECL83	70p	KT88	£2.80		

V.A.T.

Please add 10% to all orders

METERS

Full List of our very large stock of meters on request.

TRANSISTORS, ZENER DIODES etc.

AC 07	35p	BC118	20p	NKT222	30p	OC75	25p	ORP61	45p	2N2411	55p
AC113	15p	BC12A	11p	OA5	60p	OC76	25p	ORP90	95p	2N2646	40p
AC126	20p	BC212A	18p	OA10	40p	OC77	45p	OR183	£1.10	2N2904	20p
AC 37	20p	BCY72	15p	OA70	10p	OC78	25p	RAE31JAF		2N2989	£4.00
AC128	20p	BD136	45p	OA71	10p	OC78D	25p			2N3053	20p
AC132	25p	BF115	25p	OA72	15p	OC81	20p	SD94	35p	2N3054	45p
AC176	20p	BF167	25p	OA74	15p	OC81D	20p	V405A	25p	2N3055	55p
AC187	25p	BF173	25p	OA79	10p	OC81DM	20p	ZR11	50p	2N3646	60p
AC188	25p	BF173	25p	OA81	08p	OC82	25p	ZR21	30p	2N3730	65p
AC192	25p	BF177	20p	OA91	07p	OC82DM	30p	ZR22	25p	2N3731	70p
ACY28	35p	BF180	35p	OA200	07p	OC83	25p	ZT20	£1.00	2N3819	25p
AD149	40p	BF200	30p	OA202	10p	OC84	25p	ZT83	60p	2N3803	70p
AD149	40p	BFY51	20p	OA2200	50p	OC122	£1.00	ZT84	£1.00	2N3804	80p
AD161	35p	BFY52	40p	OA2201	45p	OC139	25p	ZT91	£2.00	2N3807	£1.60
AD162	35p	BFY90	75p	OC116	40p	OC140	65p	ZT202	50p	2P703	75p
AF118	25p	B8Y29	30p	OC22	£1.00	OC141	60p	ZT203	50p	40S94	65p
AF127	30p	BYZ13	35p	OC25	40p	OC170	25p	ZTX302	80p	40S95	75p
AF139	30p	BYZ16	60p	OC28	35p	OC171	30p	1N823A	65p	40S96	£1.00
AF178	45p	CRS110	30p	OC28	65p	OC200	40p	1N4785	60p	40S97	45p
AF180	45p	CRS120	40p	OC29	65p	OC201	75p	2N1918	37p	68Y7	25p
AF181	45p	CRS140	48p	OC35	50p	OC202	80p	2N1987	45p	68Y7GT	25p
AF186	40p	CRS33/40A/P	OC36	65p	OC203	55p	2N1304	22p	68Y7GT	25p	
AFZ12	£1.00	CRS25/025	OC44	17p	OC204	65p	2N1305	22p	68Y7GT	25p	
ABY28	25p	GET115	75p	OC70	12p	OC205	£1.00	2N1306	25p	68Y7GT	25p
AC107	10p	GET116	85p	OC71	12p	OC206	£1.10	2N1307	25p	68Y7GT	25p
BC128	10p	GET116	85p	OC72	20p	OC207	£1.10	2N1308	27p	68Y7GT	25p
BC113	16p	GEX66	£1.50	OC73	20p	OC208	£1.10	2N1309	28p	68Y7GT	25p
						OC209	£1.10	2N1310	28p	68Y7GT	25p
						OC210	£1.10	2N1311	28p	68Y7GT	25p
						OC211	£1.10	2N1312	28p	68Y7GT	25p
						OC287	£1.10	2N1388	28p	68Y7GT	25p
						OC288	£1.10	2N1389	28p	6	

IMPEDANCE MATCHING



THE WHYS AND WHEREFORES

C. BUDD

THE concepts of input impedance and output impedance are not really difficult to understand although there is no single rule to cover every situation. What is correct practice depends almost entirely on the individual design requirements.

The most important rule of impedance matching is derived from the maximum power transfer theorem.

The maximum power transfer theorem

If a signal source with a purely resistive output source is required to drive a purely resistive load, maximum power will be transferred from source to load when the load resistance is equal to the output impedance of the source. It should be noted that the theorem assumes that the input and output impedances to be purely resistive, which will rarely be the case in practice, and that to deliver maximum power to the load is the sole requirement.

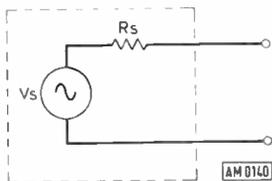


Fig. 1: Equivalent circuit of signal source with resistive output impedance.

Fig. 2: Equivalent circuit of resistive load.

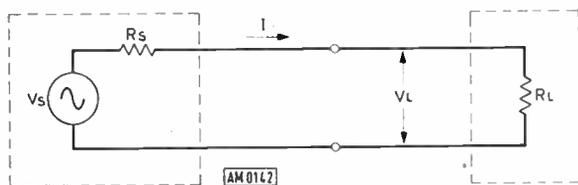
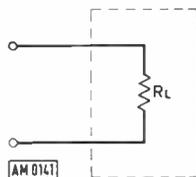


Fig. 3: Equivalent circuit of the source of Fig. 1 driving the load of Fig. 2.

Assuming that our signal source may be represented by an a.c. voltage source in series with a resistance (Fig. 1) and that our load may be represented by a pure resistance (Fig. 2), we can combine the two (Fig. 3) and write some pertinent equations as follows.

Calling the power delivered to the load P

$$V_L = \frac{V_S R_L}{R_L + R_S} \text{ by potential divider action}$$

and $I = \frac{V_S}{R_L + R_S}$ where I is the a.c. current flowing

$$P = IV_L$$

$$\therefore P = \frac{V_S^2 R_L}{(R_L + R_S)^2}$$

where V_L = load voltage, V_S = source voltage, R_L = load resistance, and R_S = source resistance.

Given the source voltage and the source and load resistances we can, with this formula, calculate the power delivered to the load. But we can do more than that. If we assume arbitrary values for V_S and R_S we can plot a graph of R_L against P. The curve obtained will be similar to that in Fig. 4. From the graph it may be seen that the power transferred is at maximum at approximately the point where R_L equals R_S . It may be shown that P reaches a maximum when R_L is exactly equal to R_S .

Maximum power transfer between source and load occurs when the source resistance is equal to the load resistance.

Other considerations

In practice, however, it is not as straightforward as this because maximum power transfer may not be our only concern. Consider the simple audio output stage shown in Fig. 5. The purpose if T1 is to match the speaker impedance to the output impedance presented by the transistor.

From the maximum power transfer theorem, one could reasonably assume the the "correct" load resistance would be the output resistance of the transistor, but this is not so. In this case maximum

efficiency (i.e. power transfer from amplifier to load) is not our main concern.

Of greater importance is the maximum power that the stage will deliver without distortion due to bottoming (the transistor being turned off by the input signal) or saturation. In fact the load resistance into which the stage will deliver the maximum power without distortion, known as the optimum load, is equal to the supply voltage divided by the quiescent collector current and has nothing to do with the actual output resistance of the stage.

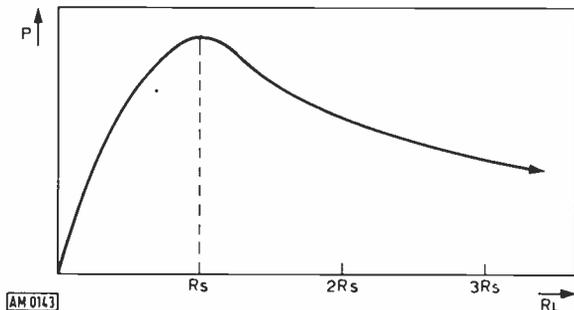


Fig. 4: Sketch graph showing that the power delivered to the load is at a maximum when $R_L = R_s$.

In a practical case the optimum load will generally be higher than the output resistance for an audio power amplifier, and this is the reason that commercial audio power amplifiers, intended to drive load impedances of 3, 8 or 16 ohms, often have output impedances of a fraction of an ohm.

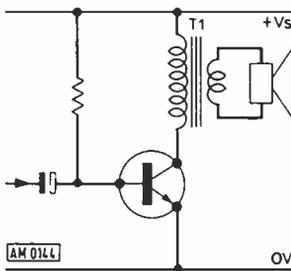


Fig. 5: Simple audio output stage.

Reactive components

An input or output impedance will have reactive components as well as a resistive one. If possible, the reactive element of the source impedance should be cancelled by those of the load impedance. In other words, a source with an equivalent series capacitance should "see" a load with an equivalent series inductance, the reactance being equal, but opposite, to that of the source capacitance.

In this way, the source capacitance and the load inductance form a series-tuned circuit which, ideally, has zero dynamic impedance (zero resistance). Any net reactance in the source-load circuit is undesirable since it reduces the maximum power that can be delivered to the load by the source. Such "reactance balancing" is only possible at a single frequency and in a system of large relative bandwidth (e.g. an audio preamplifier) it is of no use.

At r.f. however, the relative bandwidth will generally be much less and it is usually easy to make the reactive elements of source and load cancel out in the frequency band in use. As an example, one of the functions of the aerial tuning unit in a transmitting system is to cancel out the reactive elements of the aerial impedance.

Equal load and source resistance

Now let us consider another situation in which it would be better to deviate from the rule of making the load resistance equal to the source resistance because maximum power transfer is not our only concern. Fig. 6 shows the equivalent circuit diagram of a typical crystal microphone or ceramic pick-up. The output impedance of such a device consists of a fairly large resistance (typically a few megohms) in series with a small capacitance of perhaps two or three hundred picofarads. If the capacitive element was absent, the transducer drives a pre-amp with an input resistance equal to R_s and all would be well.

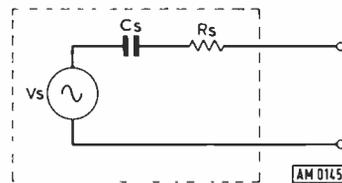


Fig. 6: Equivalent circuit of typical crystal microphone or ceramic pick-up.

However, at the lower audio frequencies, the reactance of C_s in a practical transducer becomes large enough to be significant in comparison to R_s and attenuation of the bass frequencies would result if the input impedance of the pre-amp were equal to R_s .

Since an inductance in series with the transducer would only cancel the capacitance at a single frequency and would, in any case be ridiculously large, the simplest solution to the problem is to make the input impedance of the pre-amp very large compared to R_s . The reactance of C_s at bass frequencies would then be insignificant compared to the total resistance in circuit and no significant attenuation of the bass frequencies would occur.


High impedance input

The circuit diagram of a crystal microphone driving a pre-amp with an ample input resistance of $10M\Omega$ is shown in Fig. 7. One could reasonably think, from the maximum power transfer theorem, that the large ratio between the resistive component of the source impedance and the load resistance would result in a large loss of available power.

This is the case, but it may be shown that the power gain of a common source f.e.t. stage (and that of a common cathode valve stage) is proportional to the value of the resistor (R_1 in Fig. 7) shunting the input, which is roughly equal to the

—continued on page 1166


SUPERSOUND 13 HI-FI MONO AMPLIFIER

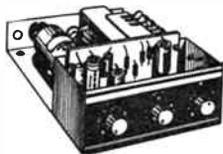

A superb solid state audio amplifier. Brand new components throughout. Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts into 8 ohms. Frequency response 12Hz-30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £11.00. P. & P. 50p.

F.H.S. into 8 ohms. Frequency response 12Hz-30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £11.00. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

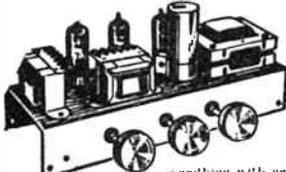

A.C. mains 200-240 v. Input v. heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2 x ECC83 Triodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono). Into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £9.90. P. & P. 50p.

Valve line up: 2 x ECC83 Triodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono). Into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £9.90. P. & P. 50p.

POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7.5v. and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5.00 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 28p pair. P. & P. 6p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.81 P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 600 ma. £1.10. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.81. P. & P. 26p. Pri. 200/240v. Sec. 10-0-10 at 1 amp. £1.82. P. & P. 35p.

For personal callers only! Limited number of stereo radiogram chassis, covering LW/IFM bands. Mono radio and stereo gram. Overall size approx. 16 1/2" W, 6 1/2" H, 8" Depth. 4 watts per channel output. only £16.50.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price £1.00. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents 80p
Transistor Equivalents 90p
Transistor Characteristics £1.15
POST FREE
All three together £2.80

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias 95p, Post Free
8 pole 3 way 2 bank low loss Yaxley type switches 1 1/2" sections. Standard spindle. 2 switches 66p + 10p P. & P.

Open 9-5.30 Monday to Friday, 9-5 Saturday
Early closing Wed.

A few minutes from South Wimbledon Tube Station.

RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
LATEST B.S.R. C109/C129 AUTOCHANGER UNITS with latest stereo/mono compatible cartridge £7.60 + 50p P. & P.

SPECIAL BARGAIN OFFER!
Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £8.00 + p. & p. 60p.

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025, 2500, 3000, 2500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover).
NOW ONLY £4.95. P. & P. 70p.

LATEST ACOS GP11/15C mono compatible cartridge with 1/2 stylus for LP/EP/78. Universal mounting bracket. £1.60. P. & P. 15p.

SOMOTONE STACH COMPATIBLE STEREO CARTRIDGE
T/O stylus Diamond Stereo. P. & P. Sapphire 78.
ONLY £2.40 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.80. P. & P. 15p.
LATEST ROSETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. £1.63 P. & P. 15p.
LATEST ROSETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.60. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £4.40. P. & P. 50p.
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £2.85. P. & P. 60p.

SPECIAL OFFER! HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 8" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £9.25 Carr. 75p
Cabinet Available Separately £4.95, Carr. 65p.
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £7.15, Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.
P. & P. 40p BARGAIN PRICE £3.30

LOUDSPEAKER BARGAINS

5in. 3 ohm £1.95, P. & P. 15p. 7" x 4in. 3 ohm £1.40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 6in. 3 ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £2.50. P. & P. 30p. E.M.I. 13" x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4.95. P. & P. 30p. E.M.I. Ceramic magnet heavy duty tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. £1.25 + 20p. P. & P. **BRAND NEW.** 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly £7.50. Guitar models: 25w. £7.60, 35w. £9.85, P. & P. 45p.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CORE LOUSPEAKERS
With large ceramic magnet and plasticised cone surround.
8 ohm impedance. £3.70. P. & P. 35p.

Also available specification as above but size 10" x 6" £2.70 and size 8" round £2.80. P. & P. 35p.


LIMITED NUMBER EMI 2 1/2" 8 ohm Tweeters. Mounted on flat bracket size 2 1/2" wide x 7 1/2" long. Ex. equipment but new and tested 70p per pair plus 15p P. & P.

12in. "RA" TWIN CORE LOUSPEAKER. 10 watts peak handling, 3, 8 or 15 ohm £2.45. P. & P. 36p. 35 ohm SPEAKERS 3in. only 70p P. & P. 25p.

"POLY PLANAR" WAFER-TYPE. WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 1 1/2" x 1 1/2" x 1 1/2". Weight 18oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £8.55 each. P. & P. 34p.

VYNAIR & BEXINS SPEAKERS & CABINET FABRICS
app. 54 in. wide. Our price £1.10 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

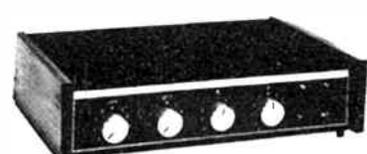HARVERSONIC SUPER SOUND 10 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH OUTRAGE OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response ±3dB 12-30,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth: ±3dB 12-15,000 Hz. Bass boost approx. to ±12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. **AMPLIFIER KIT £11.65 P. & P. 25p** (Magnetic input components 33p extra) **POWER PACK KIT £3.30 P. & P. 35p** **CABINET £3.30 P. & P. 35p** (Post Free if all units purchased at same time) Full after sales service

Also available ready built and tested £23.10. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discoteque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" x 1 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5.50. P. & P. 45p. **ESL "TUB" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4.50. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished transistor amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.

Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP86 and E280 rectifier. Simple instruction booklet 15p + S.A.E. (Free with parts) All parts sold separately. ONLY £8.50 P. & P. 60p. Also available ready built and tested £12.10 P. & P. 70p.

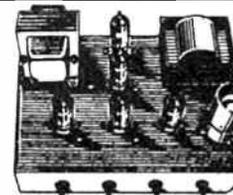

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable Bexiform earmuffs. Wired and fitted with standard stereo 3/4" jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.30. P. & P. 25p.

PRICES INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 9385

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Out now!

Free



Get the Heathkit Catalogue..and save

Handcrafted electronics with built-in quality and kit form savings.
 Hundreds of models to choose from.
 Heath offer you outstanding specifications and plus values that will impress you, your family and friends. Want to know more? Send for your personal introduction to the international world of Heathkit electronics... the Free Heathkit Catalogue.

Free

Please send me the FREE Heathkit Catalogue & details of Monthly budget plans

NAME _____

ADDRESS _____

HEATH
Schlumberger

HEATH (GLOS) LTD DEPT PW/4/74
Bristol Road,
Gloucester GL2-6EE



TO SPARK YOUR IMAGINATION!

the **SPARKRITE** Mk II
Electronic Ignition Kit
 only £11-62

Kit comprises EVERYTHING
 Case, cables, coil connectors,
 Silicon grease
 8 page instruction leaflet.

Fascinating to build Fantastic improvement to your car's performance Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed Printed circuit design All metalwork drilled ready Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition Price £11-62 inc V A T and postage. (12 volt only State Pos or Neg earth). Ready built unit also available £14-85 inc V A T and postage GUARANTEED 5 YEARS

ORDER NOW—send P.O./Cheque direct to:
ELECTRONICS DESIGN ASSOCIATES, Dept. PW4
 82 Bath St., Walsall WS1 3DE. Phone: 33652

ELECTRONIC & AUDIO BARGAINS

HILLS HEADPHONE JUNCTION BOX MODEL JB3
 For connecting headphones to amplifiers.
 OUR PRICE £1-37



AUDIO EXTENSION CABLES
 15ft. straight headphone cables £1-10
 20ft. single screened coiled cable 88p
 6 metres twin screened coiled cable 94p
 5 pin-5 pin record lead 68p
 5 pin-4RCA phono plugs 75p

VYNIAR SPEAKER CLOTH
 Black or Black and Silver.
 Sizes: 18in. x 25in. 66p
 36in. x 25in. £1-10
 36in. x 50in. £2-20

Send 7p stamp for our samples of Vyniar and Audio Components Catalogue.

SOLDERING IRONS
 CCN240 15 Watt £1-99
 X25 25 Watts £1-65
 Replacement Elements £1-10
 Replacement Bits 38p
 ST3 Stand 96p

SWITCHES
 Small Slide Switch 10p
 Large Slide Switch 10p
 SPST Toggle Switch 16p
 DPDT Toggle Switch 20p
 Small (Biased) Push to Test Switch 10p

VEROBOARD

Plain	0-1	0-15	0-15
2-5in. x 3-75in.	21p	17p	11p
2-5in. x 5in.	25p	24p	12p
3-75in. x 3-75in.	26p	24p	—
3-75in. x 5in.	29p	28p	19p
Spot Face Cutter	39p	39p	—
Pin Insertion Tool	50p	50p	—

HILLS DYNAMIC HEADPHONES MODEL H10VSM

Extremely high quality with padded headband & earcups with volume controls & mono stereo switching.

OUR PRICE £4-50 P & P 30p
"HOMMER" INTERCOM
 2 Station Inc. Volume Control On-Off Switch. Batteries & 66ft of Cable. OUR PRICE £3-70

CARTRIDGES
 Acos GP91-3SC Mono Crystal

GP93-1 Stereo Crystal £1-15
 GP96-1 Stereo Ceramic £1-85
 Sonitone 9TAHC Diam. £1-80

SPEAKERS
 6 x 4 Std. Magnet 8Ω £1-10
 7 x 4 Std. Magnet 3Ω £1-10
 8 x 5 Std. Magnet 8Ω & 3Ω £1-26

ALUMINIUM BOXES

HB1	5 1/2" x 2 1/2" x 1 1/2"	42p
HB2	4" x 4" x 1 1/2"	41p
HB3	4" x 2 1/2" x 1 1/2"	41p
HB4	5 1/2" x 4" x 1 1/2"	47p
HB5	4" x 2 1/2" x 2"	41p
HB6	3" x 2" x 1 1/2"	34p
HB7	7" x 5" x 2"	66p
HB8	8" x 6" x 3"	84p
HB9	6" x 4" x 2"	54p

CASSETTE TAPE RECORDER DYNAMIC MICROPHONE with Remote Control On-Off Switch.
 OUR PRICE £1-80

TELEPHONE PICKUP COIL for Amplifiers or Tape Recorders.
 OUR PRICE 40p

VISIT OUR TRADE COUNTER
 ALL CALLERS WELCOME
 MON.—SAT. 9 a.m. till 5.30 p.m.

HILLS COMPONENTS LTD. ALL PRICES INCLUDE V.A.T.
 DEPT. (PW3) UNIT NO. 6, MELINITE INDUSTRIAL ESTATE, BRIXTON ROAD, WATFORD, HERTS. WD2 5SL. Tel. Watford 27711
 Please add 10% for P.P.
 Min. Order £1-00

AUTOMATIC 12V CAR BATTERY CHARGER

Richard Collin

THIS simple automatic battery charger was originally designed for use with the very popular battery operated fluorescent lamp described in the December issue of *Practical Wireless*. Its purpose was to keep the battery in a fully charged state, restoring energy used when mains power is available.

The circuit is of course suitable for charging any 12 volt car battery at a maximum rate of 2.25A. When the battery reaches full charge (13.5 volts) a "crowbar" circuit operates and shuts off the charge current. Interruption of the mains supply restores the crowbar to its off state.

Circuit description

The circuit diagram is shown in Fig. 1. A mains isolation transformer with a 30V centre-tapped secondary winding feeds a full-wave thyristor circuit to provide the charging current. The thyristors are triggered by the d.c. potential applied to the gate electrodes via diodes D1 and D2 and the associated smoothing capacitor C1.

Resistors R1, R2 and R3 limit the gate current together with the indicator lamp LP2. Resistor R1 and lamp LP2 also limit the current through the crowbar thyristor CSR3 when it is 'on'. Resistors

R4 and R5 are connected in parallel. They limit the charge current to 2.25A to protect the transformer, CSR1 and CSR2. Diode D3 is included to stop current flowing back from the fully charged battery into the crowbar circuit once it has triggered.

The crowbar trigger potential is set by the 6.8V zener diode D4 in the gate circuit of CSR3. By using the potentiometer across the circuit output it is possible to adjust the voltage of the output to a pre-determined level at which the crowbar circuit 'fires'. The crowbar thyristor 'shorts' the main gates to earth and stops them from receiving gate pulses, so stopping conduction.

★ components list

R1	68Ω 5W wirewound resistor
R2, R3	270Ω ½W
R4, R5	1Ω 10W wirewound
R6	1.2kΩ ½W
R7	330Ω ½W
VR1	2.2k potentiometer (miniature preset)
C1	640μF 25V
LP1	Mains neon indicator
LP2	6.3V 0.2A lamp
S1	Single pole, single throw toggle
FS1	3A fuse
T1	Mains transformer, secondary 30V centre tapped, 3A
CSR1	2N3228 TO-66 or any 50V 5A thyristor, and mounting hardware
CSR2	2N3228 TO-66 or any 50V 5A thyristor, and mounting hardware
CSR3	TIC44
D1	1N4001
D2	1N4001
D3	1N1612R or any 50V 5A stud type (stud is anode) and mounting hardware
D4	6.8V 1 watt zener diode

Lamp holder (m.e.s.), connecting wire, mains lead, fuseholder, nuts, bolts, etc. Heatsinks (see Fig. 3.)

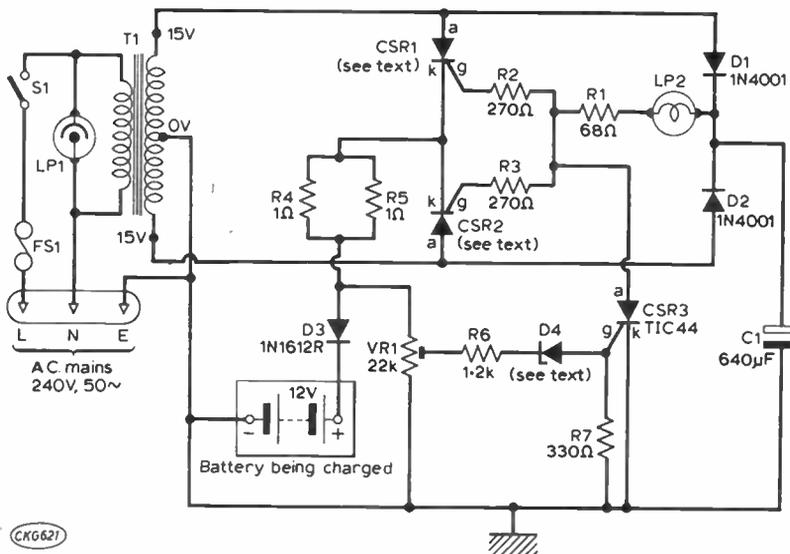


Fig. 1: Schematic circuit of the automatic battery charger.

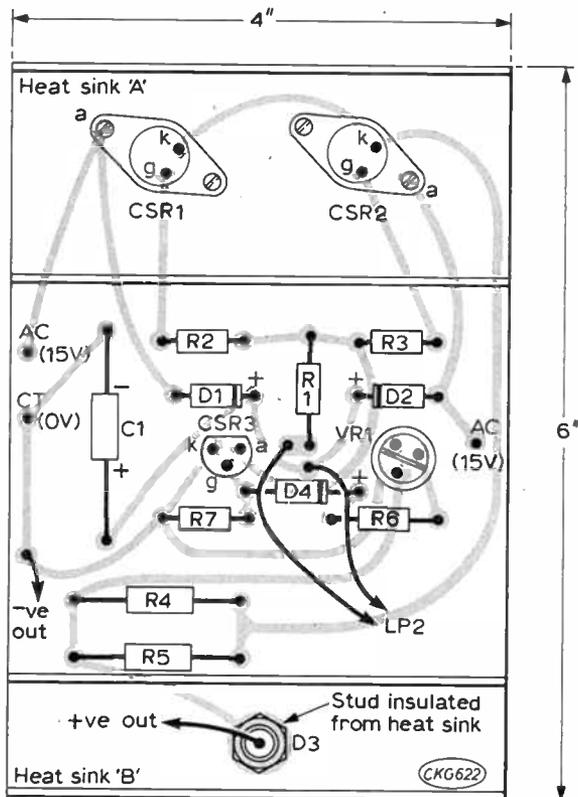


Fig. 2: Printed circuit board and component layout.

The circuit board layout is shown in Fig. 2. All components should be mounted onto the board and soldered up. Ensure that electrolytic C1 is connected correctly and check also the polarity of the thyristor and diode connections. The main thyristors, CSR1 and CSR2 and diode D3 must be mounted with insulators on their respective heatsinks. A smear of silicon grease should be applied to each side of the mica washers to ensure good thermal contact. Resistors R4 and R5 should be spaced clear of the board as they will run quite warm.

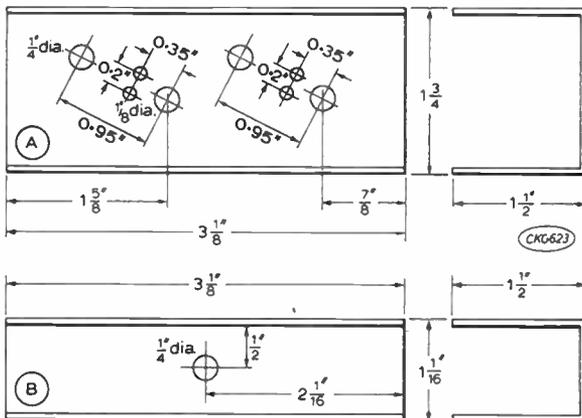


Fig. 3: Heat sink details, in 16 s.w.g. aluminium.

When the board is complete and all wires to the transformer are connected make a final wiring check. Then set VR1 fully anticlockwise, and switch on the mains. Measure the voltage across C1; it should be approximately 20V.

Then connect a fully charged 12V battery (about 13.4V off load) across the output terminals. Advance VR1 slowly until the crowbar circuit just operates (lamp LP2 comes 'on'). The voltage measured between earth and R4, R5 and D3 junction should then be about 14V. Do not move the setting of VR1 again—sealing with a dab of glue is a good safeguard. Switch off the unit and disconnect the battery.

Connect a discharged battery to the unit and switch on. If an ammeter is available check the charge rate—about 2.25A. Alternatively measure the voltage across R4, R5; this should be about 1.1V. The crowbar circuit should not operate until the battery is fully charged and reaches 13.4V. Once operated the crowbar cannot be reset unless the mains supply is interrupted.

During power cuts this will be "automatically" accomplished. ■

IMPEDANCE MATCHING—continued from page 1162

input impedance of the stage. Thus, a high input impedance makes for higher power gain and, hence, greater output power from the stage as well as improving the bass response, as it does in this particular application.

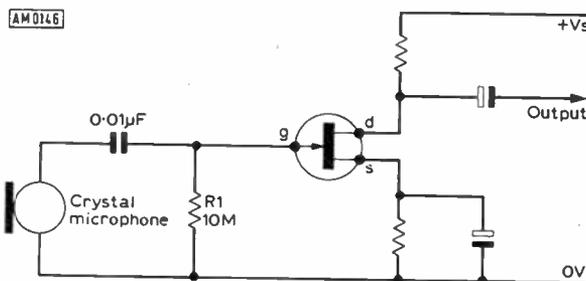


Fig. 7: A crystal microphone driving an audio preamp with a high input impedance.

Power fall-off


There are many such situations in which maximum transfer of power from source to load is not our only concern and load resistance should not be made equal to source output resistance. But the basic principles should be borne in mind. The maximum possible power will be delivered to the load when the input resistance of the load is equal to the output resistance of the source and any reactive components in the source impedance should be cancelled out by equal but opposite reactive elements in the load impedance.

In many practical cases exact equality of source and load resistances is not easy to achieve. It may be seen from Fig. 1 that the power transfer falls off more rapidly with decreasing load resistance than it does with increasing load resistance. Therefore, if it is necessary for a mismatch to occur, it is clearly much better to make the load resistance greater than the source resistance. ■

IN NEXT MONTH'S


PRACTICAL WIRELESS

'MINI-POP' RADIO

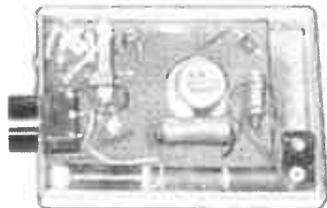


This is the miniature radio you can hold in one fist. Brings in the popular radio stations on the medium waves. Construction details provided—it's easy to make!

OSCILLOSCOPE TRACE DOUBLER

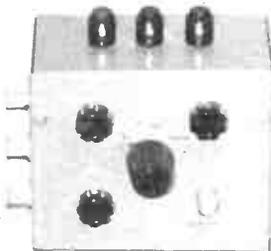


In conjunction with our current series, aimed to help you get the best out of oscilloscopes, this simple i.c. add-on unit can convert a single beam oscilloscope to double-beam. With twin units, a double-beam oscilloscope can be converted to show four waveforms simultaneously.

CAR CASSETTE AUDIO BOOSTER

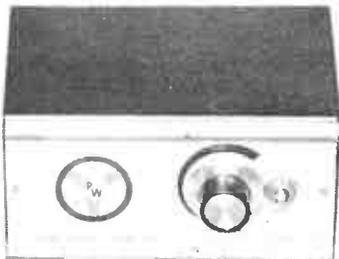

All ready for the new fair-weather motoring season or that long trip on holiday. Relax with music in your ears—don't let the car noise drown your enjoyment. Useful for car radios, too!

SPECIAL PULL-OUT FEATURE

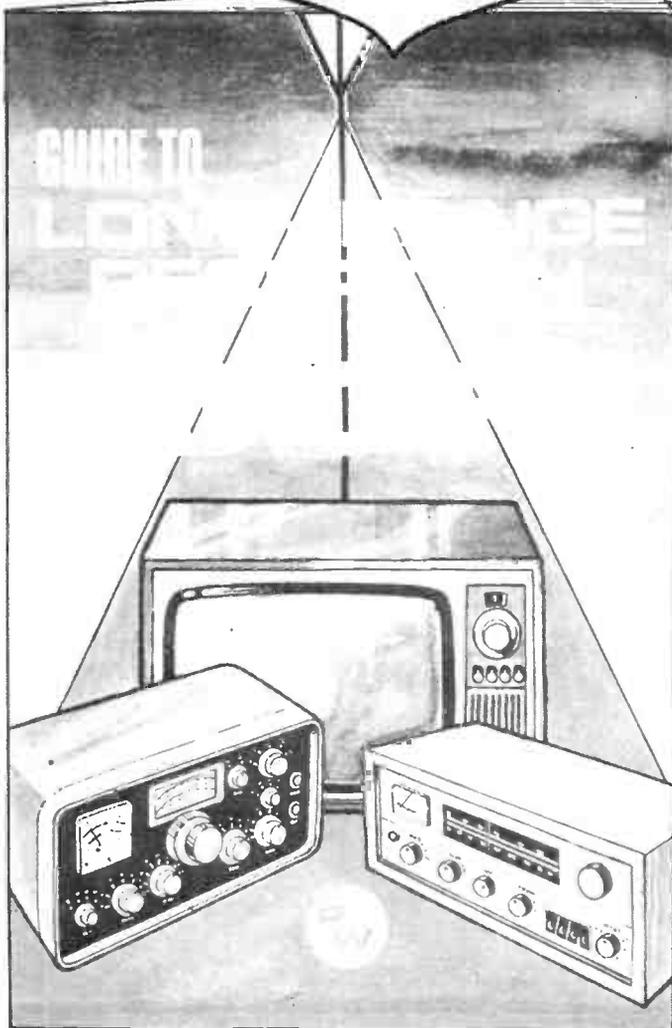

The reception of stations far away is a fascinating hobby. When it can be done on a domestic receiver it becomes even more exciting. Read how radio signals are propagated over thousands of miles, how to choose a short wave receiver, how to select a suitable aerial and how to get FM stereo and TV pictures from the Continent.

**ORDER YOUR COPY NOW!
MAY ISSUE ON SALE APRIL 5th**

**PRACTICAL WIRELESS—THE MAGAZINE WITH THE
BEST CONSTRUCTIONAL ARTICLES EACH MONTH**

THE 'SLIMLINE'

5-Band

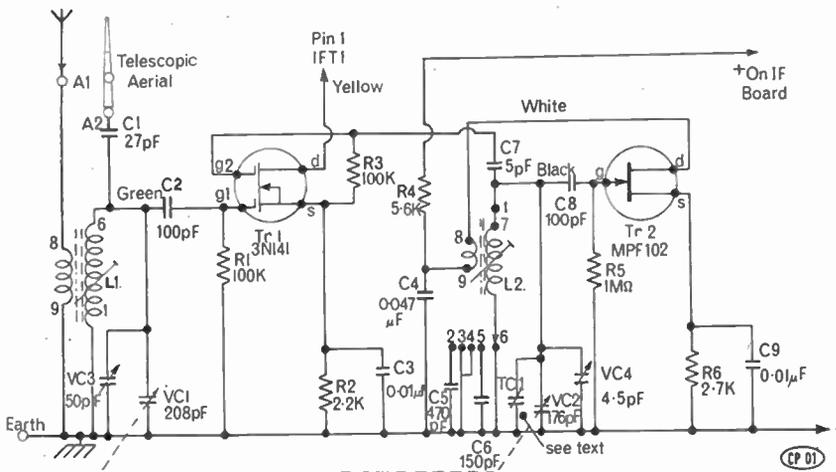


Fig. 1. First part of the circuit of the Slimline receiver. This contains the mixer stage Tr1 and the oscillator Tr2. Padders C5 and C6 are automatically connected into circuit when the appropriate coil L2 is inserted.

Fig. 2. The output from the mixer stage feeds into the first IF transformer IFT1 and amplified by Tr3 and Tr4. The capacitors across the windings are part of the IFT assemblies.

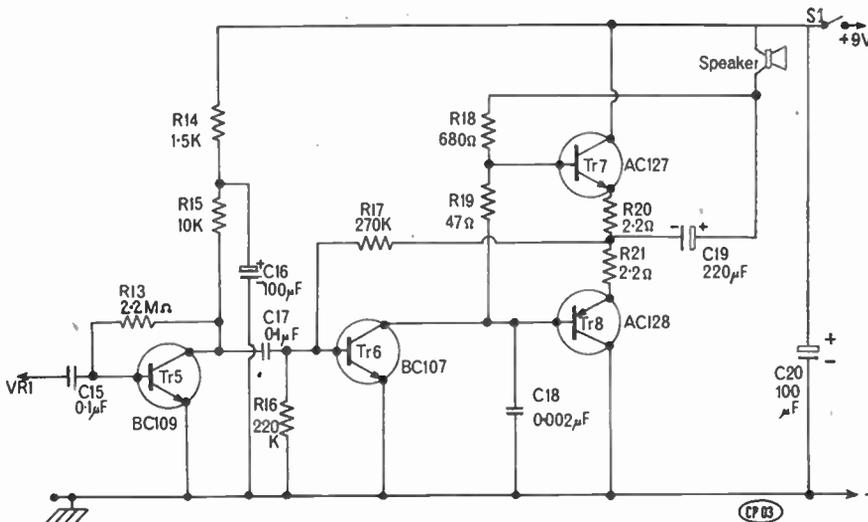
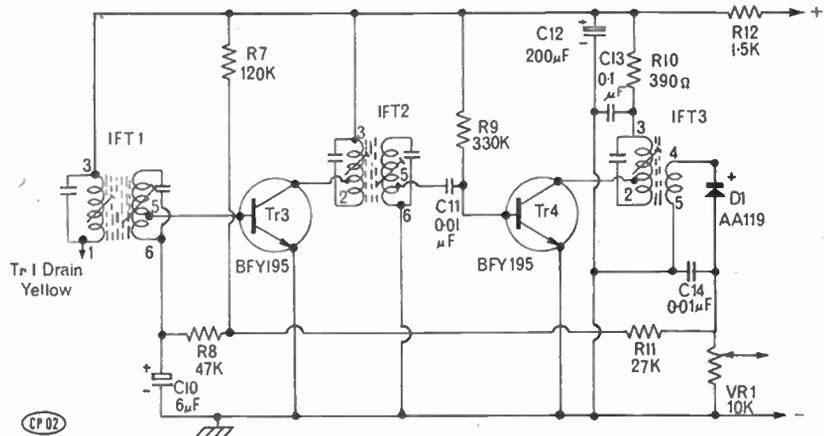


Fig. 3. The audio signal from the detector diode D1 in Fig. 2 is fed via the volume control to Tr5 and further amplified by Tr6, 7 and 8 and thence to the speaker.

Portable Receiver

THIS portable receiver is in a 7×5in. case only 1in. deep, though to these dimensions must be added those of the Trimmer, Fine Tuning and Volume/On-Off controls at one end, and the Band-setting dial on the front. These do not however increase the size very much. The receiver may be operated with its own telescopic rod aerial, with an improved aerial such as a few yards of thin insulated flexible wire or with a conventional aerial.

The coverage of the five bands is approximately as follows:—

Band 1	160—350kHz
„ 2	580—1500kHz
„ 3	1.75—4.0MHz
„ 4	5.9—11.5MHz
„ 5	13—27MHz

The receiver thus has a wide general utility, tuning medium and long waves, if required, in addition to the most popular short wave bands.

Eight transistors and one diode are employed and the receiver is wired and assembled in separate units. A dual-gate 3N141 mixer is used with an MPF102 FET oscillator, followed by two BFY195's and AA119 diode for IF amplification, demodulation and AGC. The audio section has a BC109 pre-amplifier and BC107 driving an AC127 and AC128 complementary output stage, which provides adequate power for the internal speaker.

CIRCUIT DETAILS

The telescopic aerial, or a short wire aerial, is connected to socket A2 Fig. 1, but longer indoor or outdoor aerials are plugged into socket A1, using



F. G. RAYER

the primary coupling winding of the aerial coil L1. This circuit is tuned by VC1 and the panel trimmer VC3 is provided so that this can be peaked for maximum efficiency with any aerial. Signals are taken to gate 1 of Tr1 and gate 2 is coupled by C7 to the oscillator Tr2. The oscillator coil L2 is tuned by the second section of the ganged capacitor VC1/VC2. VC4 is a bandspread tuning control to allow easy tuning on the short wave bands.

L1 and L2 are plug-in coils so there is no need to obtain coils for those bands which are not required. Band 1 is for long wave coverage and may not be wanted in some areas. The extreme high frequency end of this band is not used (above about 350kHz) as instability arises when this stage is tuned near the intermediate frequency, as would be expected.

Band 2 is for medium wave coverage while Band 3 includes shipping and other transmissions, as well as the 160m and 80m amateur bands. Most general short wave broadcasts come in Band 4 and also Band 5.

Capacitors C5 and C6 in Fig. 1 are padders and the correct value is brought into circuit for each coil when it is inserted, by wiring to the appropriate socket pins. TC1 is an integral trimmer on VC2. If VC1/2 is a type without trimmers a separate 30pF or similar small pre-set must be connected here.

Fig. 2 is the circuit of the IF amplifier. IFT1 and IFT2 are double tuned and IFT3 single tuned and these, with the two BFY195's, result in good selectivity and gain. The demodulator diode D1 provides audio signals for the volume control VR1, and automatic gain control bias for the first IF stage. Current for the IF stages is taken from the 9V supply, through R12, the mixer drain circuit being supplied through the primary of IFT1. The on-off switch S1 is incorporated with the volume control VR1.

The circuit of the audio stages is shown in Fig. 3. Tr5 is a low level high gain amplifier with output to the driver Tr6 which drives the NPN/PNP pair Tr7 and Tr8, R17 providing stabilisation of the DC operating conditions. The circuit is intended for an 18 ohm speaker but it will be found that good results are obtained with a 25 ohm or 35 ohm unit.

CONSTRUCTION

Both sides of the mixer/oscillator board are shown in Fig. 4. Plain perforated Veroboard is most suitable, with 0.15in matrix. The resistors and capacitors are inserted as shown and the board turned over and leads soldered underneath. In most places the wire ends of the components are long enough to reach other points. Soldered joints should be small and leads kept near the board, with sleeving on leads which may touch each other. The tag MC is later secured with a 6BA or 8BA bolt, to hold the board clear of the panel and to form a negative or earth return.

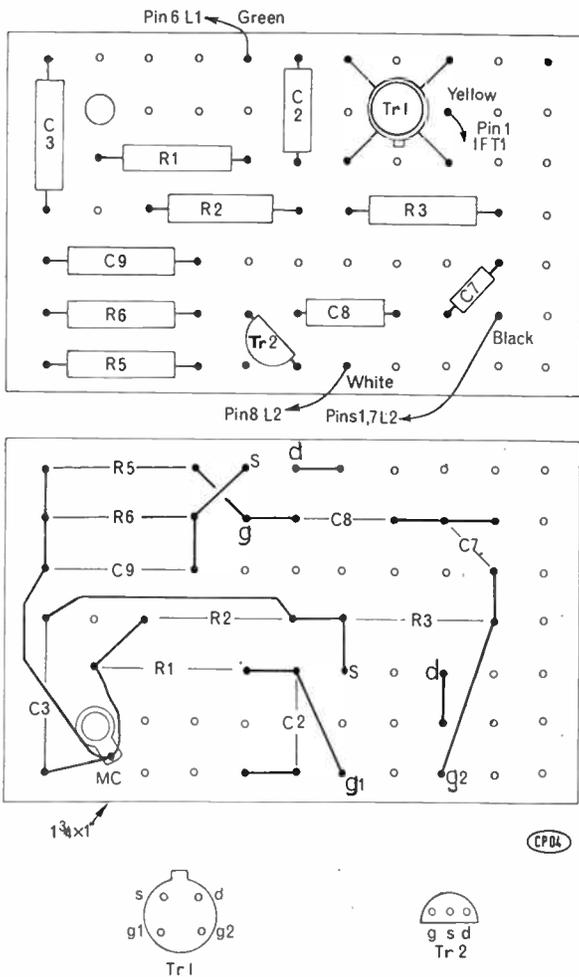


Fig. 4. Layout of the mixer/oscillator board. Veroboard pins can be used where necessary, if component leads are too short.

Important. An insulated gate transistor of the 3N141 type has an extremely high gate internal resistance and it can be destroyed by the static charge of metal or plastic tools, or by touching its leads with the fingers. Despite this, there is virtually no danger to the transistor if it is installed correctly and once R1, R2 and R3 are connected to it, these protect the gate circuits from static charges.

Leave Tr1 until other wiring on this board is finished. Tr1, as supplied, should have a thin spring or loop which short circuits its four leads, to protect it. This is not removed until the transistor is soldered in place. If it has to be unsoldered for any reason, a length of thin, clean wire should be wound round the four leads, under the transistor, before this is done. Spread the leads with a matchstick so that they come through the holes shown in Fig. 4, bend over the wires from R1, R2 and R3, and solder them to the transistor leads.

It is convenient to use colour coded leads for the external connections. These may be green from C2 for VC1 and pin 6 of L1, yellow for the drain circuit, white from Tr2 drain to pin 8 of L2 and black for VC2 and pins 1 and 7 of the holder for L2.

The IF board is shown in Fig. 5. Holes for the IFT pins and screening can tags should be drilled first. The pins are identified by their spacing, and should be arranged as in Fig. 5. A very small round file may

be useful in adjusting the positions of holes, if drilling is not quite correct, so that the IFTs fit without strain on their pins. Holes should also be drilled so that the cores can be reached. Two small tags are secured with the bolts MC, which also fix two angle brackets in place. These brackets allow the board to be fixed to the receiver panel.

Note the polarity of C10, C12 and D1. Proceed with the wiring as for the mixer-oscillator board, with insulated sleeving where required. The wire ends of R12 and C14 can be left projecting, so that other connections can be soldered on later.

The AF amplifier board is built in a similar manner, components being positioned as in Fig. 6. As it is rather difficult to see the transistor lead positions when these are in place, short pieces of coloured sleeving may be put on these wires first, to identify them—green for emitter, blue for base and orange for collector.

Capacitors C16 and C20 are arranged vertically. Bolts secure the tags MC and small brackets, as with the IF board. If necessary, these brackets can be cut from a small spare section of flanged universal

★ components list

Resistors

R1 100kΩ	R8 47kΩ	R15 10kΩ
R2 2.2kΩ	R9 330kΩ	R16 220kΩ
R3 100kΩ	R10 390Ω	R17 270kΩ
R4 5.6kΩ	R11 27kΩ	R18 680Ω
R5 1MΩ	R12 1.5kΩ	R19 47Ω
R6 2.7kΩ	R13 2.2MΩ	R20 2.2Ω
R7 120kΩ	R14 1.5kΩ	R21 2.2Ω

All resistors 5% $\frac{1}{4}$ watt

VR1 10kΩ log. pot. with switch S1

Capacitors

C1 27pF	C8 100pF	C15 0.1μF
C2 100pF	C9 0.01μF	C16 100μF 10V
C3 0.01μF	C10 6μF 4V	C17 0.1μF
C4 0.047μF	C11 0.01μF	C18 0.002μF
C5 470pF	C12 200μF 10V	C19 220μF 6.4V
C6 150pF	C13 0.1μF	C20 100μF 10V
C7 5pF	C14 0.01μF	

VC1/2 208—176pF gang (Jackson 00)

VC3 50pF (Jackson C804)

VC4 4.5pF (Jackson C804)

TC1 30pF trimmer, see text

Semiconductors

Tr1 3N141	Tr4 BFY195	Tr7 AC127
Tr2 MPF102	Tr5 BC109	Tr8 AC128
Tr3 BFY195	Tr6 BC107	D1 AA119

Inductors

IFT1/2 IF Transformer (Denco IFT18/465)

IFT3 IF Transformer (Denco IFT14)

L1/2 Plug-in coils, 9 pin miniature valve type for ranges required (Denco—'Blue' for aerial coils and 'Red' for oscillator coils)

Miscellaneous


Speaker, about 2½in dia., 18 to 35 ohms. Telescopic aerial. Small sockets (2). B9A valveholders, plain (2). Perforated veroboard 0.15in matrix, 1½ x 1in, 3½ x ¾in and 2½ x ¾in. Knobs (4). Perspex for dial.

Casework Plates 7 x 5in (2) (CU168)

Flanged members 7 x 1in (2) (CU54A)

Flanged members 5 x 1in (2) (CU52A)

All from Home Radio.

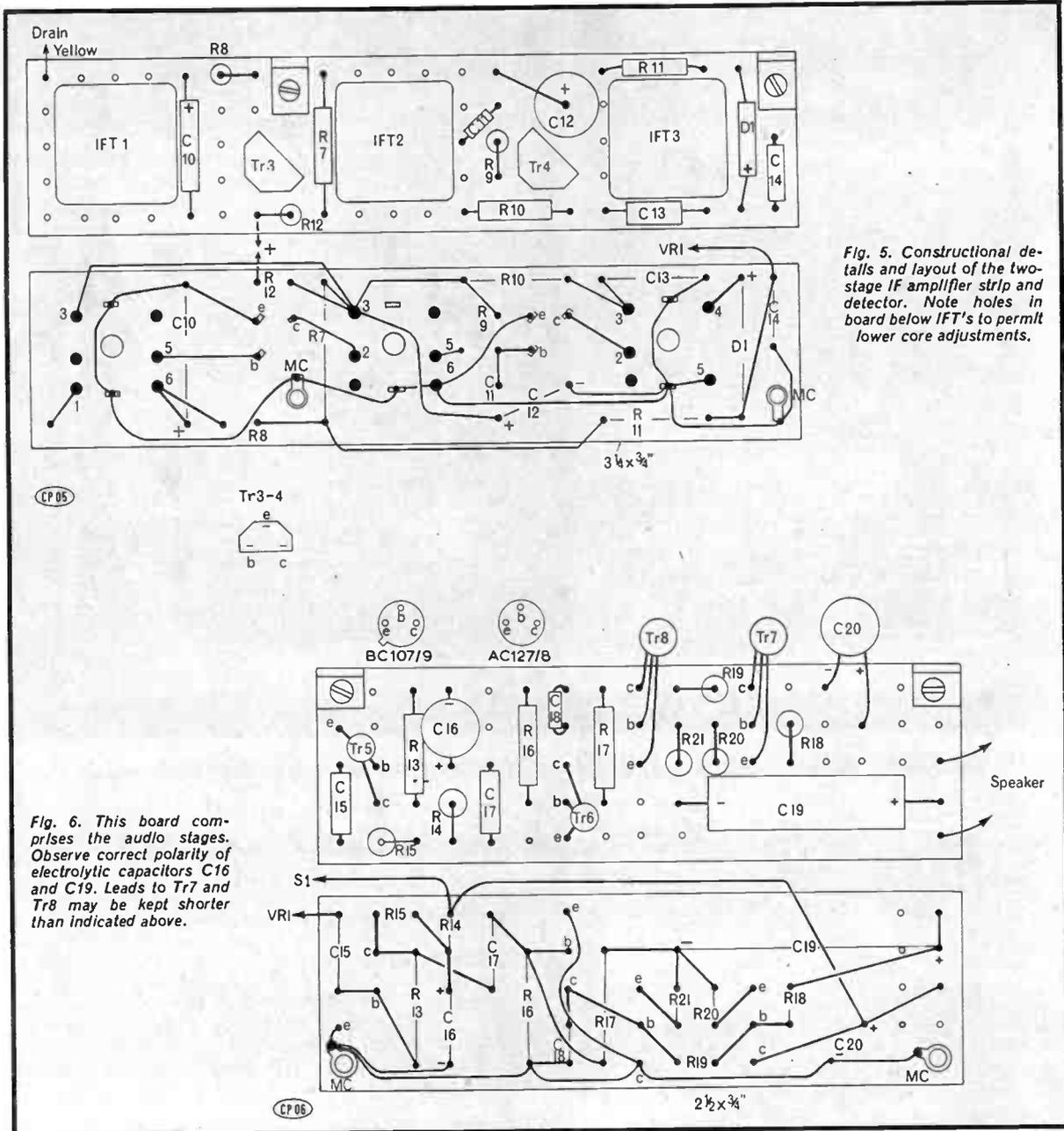

chassis, as used later for the coil holders. Both brackets and insulated board are drilled for 8BA bolts.


A piece of metal with a flange, for mounting the coil holders, is cut $2\frac{3}{4} \times 1$ in so that the holders can be fitted as in Fig. 7. A small section is cut away near L2 as shown, to allow the speaker to fit.

The flange is bolted 1 in. from the edge of the panel, as in Fig. 8. There is little free space so items should be positioned carefully. The flange is held with 6BA countersunk bolts and nuts. The ganged capacitor is held with three 4BA bolts, which must be cut or filed short so that they do not project beyond the thickness of the capacitor's front plate.

Wiring can then be completed as in the diagrams. The IF, AF and mixer-oscillator boards are held

with 8BA countersunk bolts. The one 5×1 in flanged runner is fixed with bolts or self-tapping screws so that VC3, VC4 and VR1 can be mounted, but the other flanged members are left off until later. Leads between units are run against the metal. The speaker is cemented over a $1\frac{3}{4}$ in diameter hole and the leads soldered to it. Other connections will be seen in Figs. 7 and 8.

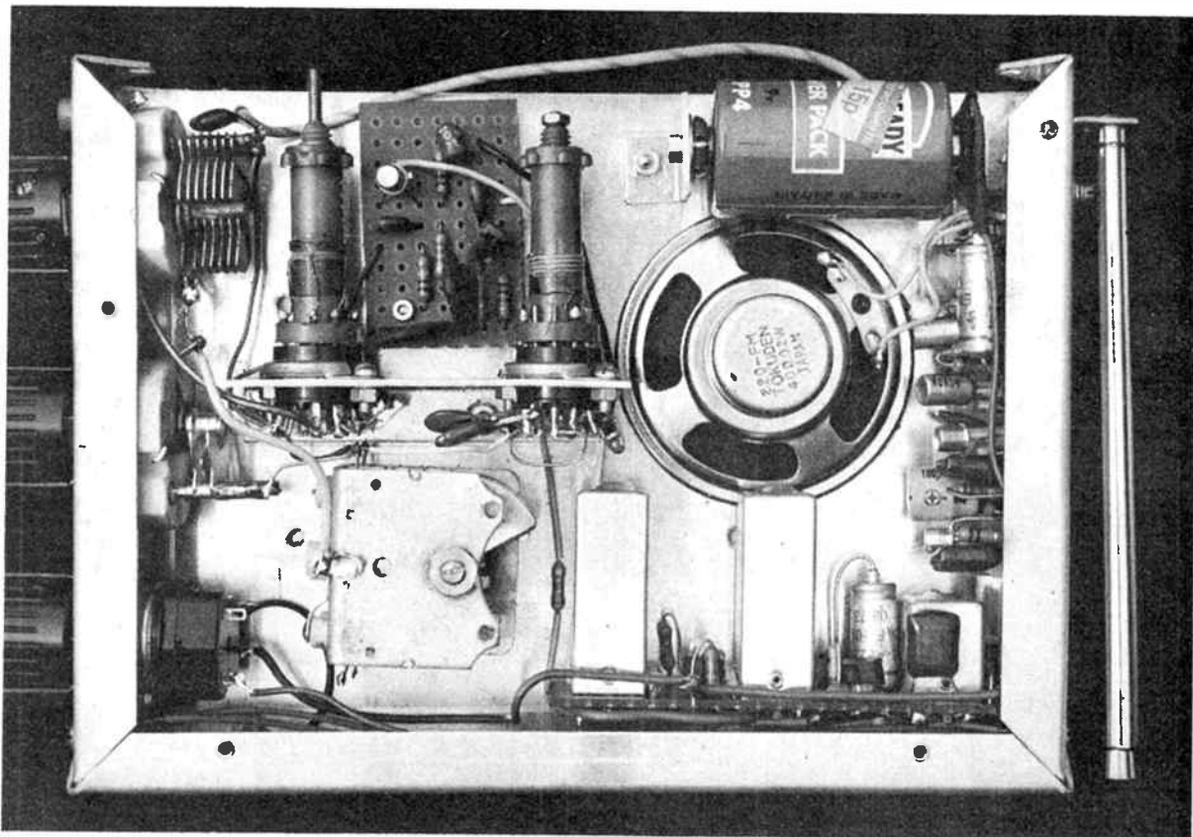The battery is mounted by a bracket, to which a negative snap connector is bolted. This both holds the battery and provides the negative connection. Two small sockets provide A1 and Earth connections. When all wiring is finished, except for the telescopic aerial, the receiver can be aligned. Do not forget to remove the shorting collar or wire from the mixer transistor.



Inside the Slimline receiver. Main components may be identified from Fig. 8.

IF ALIGNMENT

As the IFT's are supplied pre-aligned, the cores should not be touched until reasonable results are being obtained. A properly fitting tool must be used, such as that available from the IFT maker, as a wedge-shaped blade may easily break the cores so that they cannot be rotated. Where a signal


generator is available, place the output lead of this near the yellow lead (mixer drain) and adjust the cores for best output.

If no generator is available turn the audio gain control to near maximum and tune in a weak but stable signal, such as that obtained from a local BBC transmitter, with no aerial at all in use. With this tuned in correctly, adjust the five cores slightly, as may prove to be necessary, for best volume. An alternative is to connect a high resistance test meter across VR1 (positive to chassis) and use a somewhat stronger signal, so that cores can be peaked for the best reading. When these cores have been adjusted, they should be left alone since their settings are not changed when dealing with the mixer and oscillator circuits.

MIXER/OSCILLATOR ALIGNMENT

If VC1/2 has trimmers, open fully the trimmer on VC1 and screw down the trimmer on VC2 and set VC3 and VC4 about half open. Each range is dealt with separately. Suppose that Range 3 is aligned first. Adjust the core of L2 (Red coil) so that band coverage is approximately correct. Then tune in a signal around 3.5 to 4.0MHz and adjust VC3 for best volume. Leave VC3 at this setting and tune to a signal around 1.9MHz. The core of L1 is then adjusted for best results, after which there is little need for much adjustment of VC3, throughout the band. When VC3 is peaked for best results, it should be neither fully closed nor fully open.

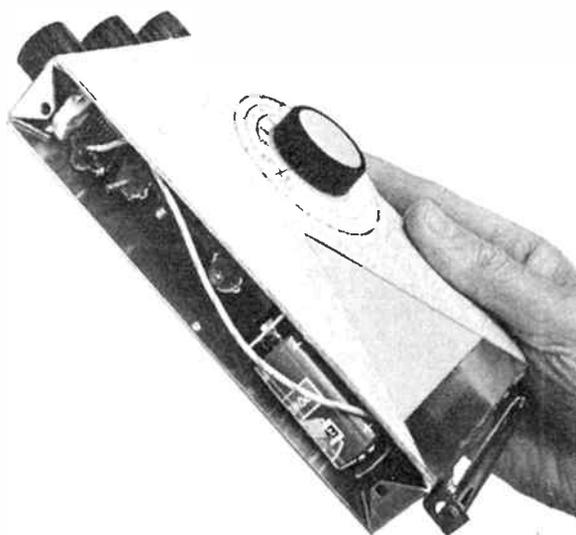The other ranges are dealt with in the same manner. The cores of L2 are adjusted in that



Removal of edge panel permits easy coil changing or replacement of battery.

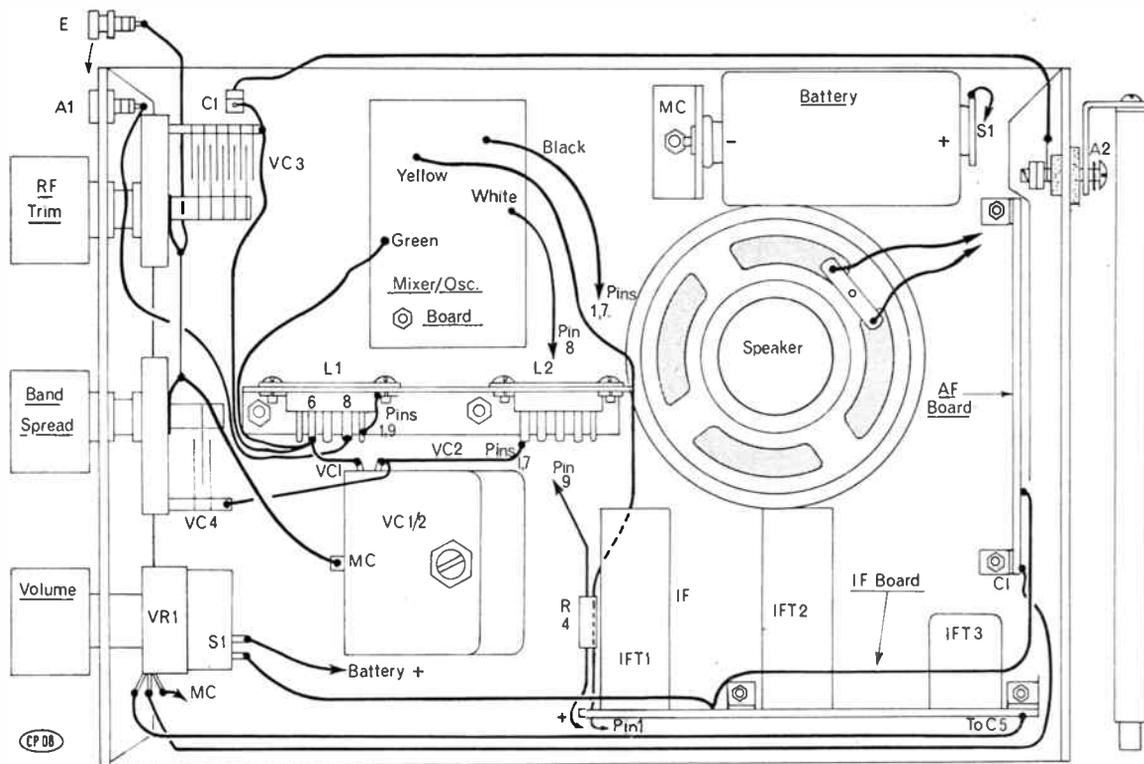


Fig. 8 Location of the three boards and major components. The battery is held in position by the bracket holding the negative clip.

direction which takes them away from the smaller winding for Ranges 1 and 3, otherwise continuous oscillation may prove troublesome at the high frequency end of these bands. This arises from the degree of coupling between L2 and its feedback winding. Should excess oscillation or "squegging" of the oscillator be troublesome, R4 could be increased in value. On the other hand, if Tr2 has somewhat reduced gain the value of R4 could be reduced. However, with the value shown, several MPF102 transistors proved satisfactory, so this should not be necessary.

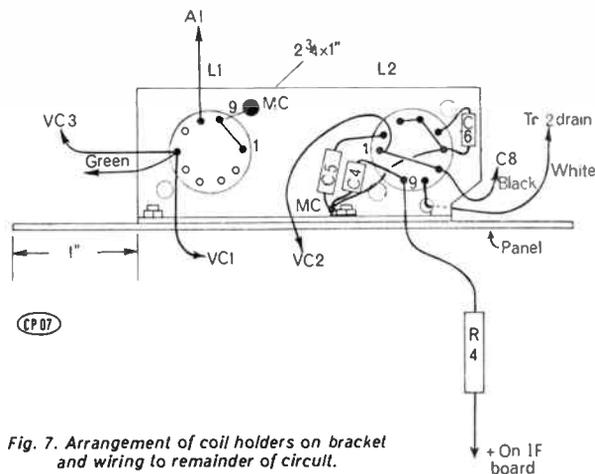


Fig. 7. Arrangement of coil holders on bracket and wiring to remainder of circuit.

FINISHING OFF

The aerial is fixed to a small right angle bracket which is pivoted on a 6BA bolt passing through the side of the case. The hole is drilled to take an insulated bush and an insulated washer rests between the bracket and case. A spring washer is placed under the screw head and the nuts locked together so that the aerial can be extended vertically with the case flat or standing upright. A flexible lead runs from the aerial to C1.

The dial is marked on card and is about 2 3/4 in. in diameter. The control knob is a shallow type to which is attached a 2 3/4 in. diameter disc of 1/16 in. thick Perspex. This can be fixed with adhesive or self-tapping screws. A line is marked across the Perspex. A disc can be easily cut with an adjustable tank or washer cutter, but if this is not available a pointer knob could be substituted for the disc.

The case is completed by screwing on one 7 x 1 in member and the remaining 5 x 1 in member. The 5 x 1 in members fit inside the 7 x 1 in members so that the top 7 x 1 in flanged member can be taken off to change the battery or coils. The back, a 7 x 5 in flat plate, is permanently attached with self-tapping screws, but only one screw is run into the top member flanges.

There is some opportunity for individual choice in the way in which the case is finished. If left bare or painted, gauze or perforated metal should be fitted over the speaker aperture inside. The case shown was covered at the front with fabric and self-adhesive material as used for shelves, boxes, etc.

CASSETTE RECORDER AND TUNER AMPLIFIER



Mount the strip of four output devices onto the circuit board and solder up the connections. Then mount the two driver transistors in a similar fashion. Once soldered ensure that the power transistors are not bent back and forth on their leads—plastic packaged devices can be easily damaged by stressing the lead outs. Once complete the power board should be put away safely until needed later on.

TUNER AND IF CIRCUIT (UNIT 3)

The AM section utilises the Ferranti ZN414 integrated circuit IC1 and a single transistor amplifier Tr1. A small ferrite rod aerial forms part of a double-tuned aerial circuit which is used to eliminate swamping effects of strong local transmissions by improving the selectivity. The circuit and printed board illustrated are for the single-station version. Further channels may be added by inserting a suitable two-pole rotary switch at the points marked "X" and "Y" in Fig. 10 to select additional pairs of trimmer capacitors for each station required.

The ferrite aerial may be insufficient in some areas of poor signal strength. The AM aerial socket, which is loosely coupled to the ferrite rod by two turns of insulated wire, allows adequate reception under such conditions by connection of an external aerial.

In the FM section, a Mullard varicap tuned module type LP1186 feeds an RCA IF amplifier integrated circuit IC2 through a ceramic filter tuned to 10.7 MHz. This integrated circuit requires only one IF coil to provide the audio output for the decoder and also an AFC control voltage.


PART 2

RICHARD COLLIN

POWER AMPLIFIER ASSEMBLY

The first stage in assembly is to mount all components except the plastic power transistors onto the board, ensuring correct polarity of electrolytic capacitors. Solder each joint carefully—do not overheat the components, but make sure joints are properly made. Check that all parts are in the correct position and then cut off all excess lead wires. Note that R13 and C9 are mounted on the speaker sockets, not on the printed board.

Next fit the output and driver transistors onto their respective heat sinks ensuring that the mica washers and nylon bushes are correctly located. Check that each device is isolated from the heatsink after assembly. Then form the leads for insertion into the printed board. **Do not** bend the leads less than $\frac{1}{8}$ in from the transistor body. **Do** support the leads near the body with long-nose pliers whilst forming. **Do not** radius the bends tighter than $\frac{1}{16}$ in.

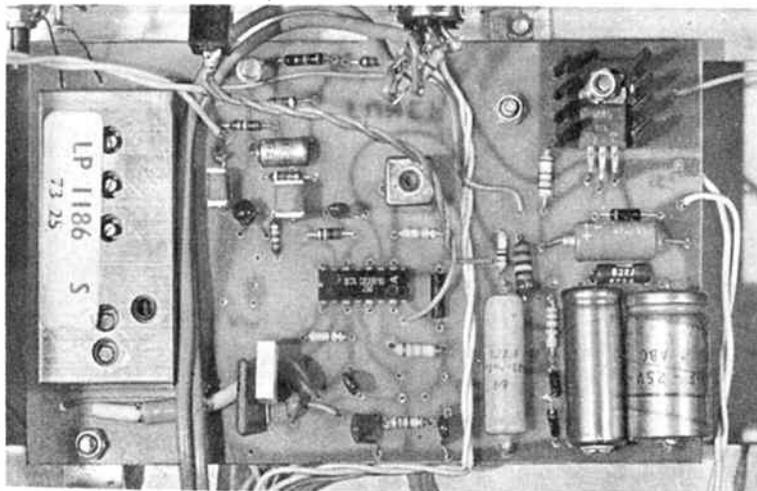

The prototype Tuner and IF board shown here has some variations in layout from the final version given in Fig. 12

Trannies

All orders to be sent to our new retail shop at:-

4 Bush House, Bush Fair, HARLOW, ESSEX.

Telephone: 37739 — P. & P. 10p. — Catalogue 10p.

74 Series TTL

(National Semiconductors and I.T.T.)
LOW PRICES, HIGH QUALITY

* 100 plus less 10% on the 25+ column

No's	1+	25+	No's	1+	25+
7400	20p	18p	7412	20p	18p
7401	20p	18p	7413	31p	29p
7402	20p	18p	7414	49p	47p
7403	20p	18p	7415	57p	55p
7404	21p	19p	7416	20p	18p
7405	21p	19p	7417	77p	74p
7406	54p	49p	7418	20p	18p
7407	54p	48p	7419	81p	78p
7408	20p	18p	7420	20p	18p
7409	28p	24p	7421	22p	19p
7410	20p	18p	7422	60p	58p
7411	23p	21p	7423	60p	58p
7412	40p	35p	7424	50p	48p
7413	31p	29p	7425	35p	31p
7414	49p	47p	7426	35p	31p
7415	57p	55p	7427	55p	51p
7416	20p	18p	7428	55p	51p
7417	77p	74p	7429	20p	18p
7418	20p	18p	7430	20p	18p
7419	81p	78p	7431	42p	39p
7420	20p	18p	7432	42p	39p
7421	22p	19p	7433	97p	91p
7422	60p	58p	7434	77p	74p
7423	60p	58p	7435	77p	74p
7424	50p	48p	7436	20p	18p
7425	35p	31p	7437	81p	78p
7426	35p	31p	7438	81p	78p
7427	55p	51p	7439	11p	10p
7428	55p	51p	7440	11p	10p
7429	20p	18p	7441	11p	10p
7430	20p	18p	7442	11p	10p
7431	42p	39p	7443	11p	10p
7432	42p	39p	7444	11p	10p
7433	97p	91p	7445	22p	19p
7434	77p	74p	7446	22p	19p
7435	77p	74p	7447	22p	19p
7436	20p	18p	7448	22p	19p
7437	81p	78p	7449	22p	19p
7438	81p	78p	7450	22p	19p
7439	11p	10p	7451	22p	19p
7440	11p	10p	7452	22p	19p
7441	11p	10p	7453	22p	19p
7442	11p	10p	7454	22p	19p
7443	11p	10p	7455	22p	19p
7444	11p	10p	7456	22p	19p
7445	22p	19p	7457	22p	19p
7446	22p	19p	7458	22p	19p

All Prices FULLY INCLUSIVE of VAT



AMTRON KITS

We have been appointed stockist of Amtron high quality construction kits. (20p P/P on all kits)

UK65 Transistor tester	£2.80
UK120 Hi-Fi Amplifier 12w	£5.20
UK110 Stereo Amp 4+4w	£11.97
UK115 Hi-Fi Amp 8w	£4.31
UK220 Signal Injector	£2.57
UK300 Four Channel Radio Control Transmitter	£6.55
UK310 Radio Control Receiver	£3.28
UK325 'GX2' Channel Splitting Unit. 1000 & 2000 Hz	£7.85
UK330 'GX2' Channel Splitting Unit. 1500 & 2500 Hz	£7.86
UK415 Resistor Box	£8.69
UK425 Capacitor Box	£8.39
UK515 MW Radio Receiver	£7.86
UK790 Capacitive Burglar Alarm	£7.57

Many other kits available. Send for the free Amtron Catalogue.

★ These Kit Prices include VAT ★

OUR NEW RETAIL SHOP IS NOW OPEN

Monday to Saturday 9-5.30
Friday late opening 6 o'clock

VEROBOARD		
2 1/2 x 3 1/2	0.1	0.15
2 1/2 x 5	27p	25p
3 1/2 x 5	31p	31p
17 x 2 1/2	82p	83p
17 x 3 1/2	£1.10	87p
17 x 5 (Plain)	80p	83p
Pin insertion tool	57p	57p
Spot face cutter	48p	46p
1k 36 Pins	20p	20p

Resistors

1 watt 5% carbon	1p
1 watt 5% carbon	1p
1 watt 10% carbon	21p
range 10 ohms to 4.7 megohms	
1 watt m/o 2	4p
range 10 ohms to 1 megohms	

MINIATOR DIGITAL INDICATOR TYPE 3015F

Read 0-9 and decimals. ONLY £1.65


PE RONDO

KIT AVAILABLE
SAE for List

Transistors/ Diodes	BC109 11p	BC303 50p	MP121 33p	TIP32A 73p	Diodes & Rectifiers
	BC113 151p	BC304 40p	MP122 44p	TIP33 £1.05	
	BC125 16p	BCY70 17p	MP123 50p	TIP34A	
	BC126 25p	BCY71 37p	NKT211 28p	£1.54	1N814 8p
	BC127 15p	BD131 65p	NKT212 28p	£2.53	1N896 8p
	BC128 15p	BD132 90p	NKT213 28p		1N918 8p
	BC130 16p	BD133 42p	NKT214 28p		1N940 22p
	BC131 16p	BD134 50p	NKT215 28p		1N941 17p
	BC132 16p	BD135 42p	NKT216 28p		1N942 22p
	BC133 16p	BD136 50p	NKT217 28p		1N943 17p
	BC134 16p	BD137 42p	NKT218 28p		1N944 22p
	BC135 16p	BD138 42p	NKT219 28p		1N945 22p
	BC136 16p	BD139 42p	NKT220 28p		1N946 22p
	BC137 16p	BD140 42p	NKT221 28p		1N947 22p
	BC138 16p	BD141 42p	NKT222 28p		1N948 22p
	BC139 16p	BD142 42p	NKT223 28p		1N949 22p
	BC140 16p	BD143 42p	NKT224 28p		1N950 22p
	BC141 16p	BD144 42p	NKT225 28p		1N951 22p
	BC142 16p	BD145 42p	NKT226 28p		1N952 22p
	BC143 16p	BD146 42p	NKT227 28p		1N953 22p
	BC144 16p	BD147 42p	NKT228 28p		1N954 22p
	BC145 16p	BD148 42p	NKT229 28p		1N955 22p
	BC146 16p	BD149 42p	NKT230 28p		1N956 22p
	BC147 16p	BD150 42p	NKT231 28p		1N957 22p
	BC148 16p	BD151 42p	NKT232 28p		1N958 22p
	BC149 16p	BD152 42p	NKT233 28p		1N959 22p
	BC150 16p	BD153 42p	NKT234 28p		1N960 22p
	BC151 16p	BD154 42p	NKT235 28p		1N961 22p
	BC152 16p	BD155 42p	NKT236 28p		1N962 22p
	BC153 16p	BD156 42p	NKT237 28p		1N963 22p
	BC154 16p	BD157 42p	NKT238 28p		1N964 22p
	BC155 16p	BD158 42p	NKT239 28p		1N965 22p
	BC156 16p	BD159 42p	NKT240 28p		1N966 22p
	BC157 16p	BD160 42p	NKT241 28p		1N967 22p
	BC158 16p	BD161 42p	NKT242 28p		1N968 22p
	BC159 16p	BD162 42p	NKT243 28p		1N969 22p
	BC160 16p	BD163 42p	NKT244 28p		1N970 22p
	BC161 16p	BD164 42p	NKT245 28p		1N971 22p
	BC162 16p	BD165 42p	NKT246 28p		1N972 22p
	BC163 16p	BD166 42p	NKT247 28p		1N973 22p
	BC164 16p	BD167 42p	NKT248 28p		1N974 22p
	BC165 16p	BD168 42p	NKT249 28p		1N975 22p
	BC166 16p	BD169 42p	NKT250 28p		1N976 22p
	BC167 16p	BD170 42p	NKT251 28p		1N977 22p
	BC168 16p	BD171 42p	NKT252 28p		1N978 22p
	BC169 16p	BD172 42p	NKT253 28p		1N979 22p
	BC170 16p	BD173 42p	NKT254 28p		1N980 22p
	BC171 16p	BD174 42p	NKT255 28p		1N981 22p
	BC172 16p	BD175 42p	NKT256 28p		1N982 22p
	BC173 16p	BD176 42p	NKT257 28p		1N983 22p
	BC174 16p	BD177 42p	NKT258 28p		1N984 22p
	BC175 16p	BD178 42p	NKT259 28p		1N985 22p
	BC176 16p	BD179 42p	NKT260 28p		1N986 22p
	BC177 16p	BD180 42p	NKT261 28p		1N987 22p
	BC178 16p	BD181 42p	NKT262 28p		1N988 22p
	BC179 16p	BD182 42p	NKT263 28p		1N989 22p
	BC180 16p	BD183 42p	NKT264 28p		1N990 22p
	BC181 16p	BD184 42p	NKT265 28p		1N991 22p
	BC182 16p	BD185 42p	NKT266 28p		1N992 22p
	BC183 16p	BD186 42p	NKT267 28p		1N993 22p
	BC184 16p	BD187 42p	NKT268 28p		1N994 22p
	BC185 16p	BD188 42p	NKT269 28p		1N995 22p
	BC186 16p	BD189 42p	NKT270 28p		1N996 22p
	BC187 16p	BD190 42p	NKT271 28p		1N997 22p
	BC188 16p	BD191 42p	NKT272 28p		1N998 22p
	BC189 16p	BD192 42p	NKT273 28p		1N999 22p
	BC190 16p	BD193 42p	NKT274 28p		1N1000 22p
	BC191 16p	BD194 42p	NKT275 28p		
	BC192 16p	BD195 42p	NKT276 28p		
	BC193 16p	BD196 42p	NKT277 28p		
	BC194 16p	BD197 42p	NKT278 28p		
	BC195 16p	BD198 42p	NKT279 28p		
	BC196 16p	BD199 42p	NKT280 28p		
	BC197 16p	BD200 42p	NKT281 28p		
	BC198 16p	BD201 42p	NKT282 28p		
	BC199 16p	BD202 42p	NKT283 28p		
	BC200 16p	BD203 42p	NKT284 28p		
	BC201 16p	BD204 42p	NKT285 28p		
	BC202 16p	BD205 42p	NKT286 28p		
	BC203 16p	BD206 42p	NKT287 28p		
	BC204 16p	BD207 42p	NKT288 28p		
	BC205 16p	BD208 42p	NKT289 28p		
	BC206 16p	BD209 42p	NKT290 28p		
	BC207 16p	BD210 42p	NKT291 28p		
	BC208 16p	BD211 42p	NKT292 28p		
	BC209 16p	BD212 42p	NKT293 28p		
	BC210 16p	BD213 42p	NKT294 28p		
	BC211 16p	BD214 42p	NKT295 28p		
	BC212 16p	BD215 42p	NKT296 28p		
	BC213 16p	BD216 42p	NKT297 28p		
	BC214 16p	BD217 42p	NKT298 28p		
	BC215 16p	BD218 42p	NKT299 28p		
	BC216 16p	BD219 42p	NKT300 28p		

Linear Integrated Circuits


301 DIL	50p	723c DIL	89p
301 TO99	55p	723c TO99	95p
301 8 PIN DIL	46p	741c 8 PIN DIL	38p
301A DIL	69p	741c 14 PIN DIL	41p
301A TO99	69p	741c TO99	41p
301A 8 PIN DIL	69p	747c DIL	46p
307 DIL	69p	748c DIL	39p
307 TO99	69p	748c TO99	41p
307 8 PIN DIL			

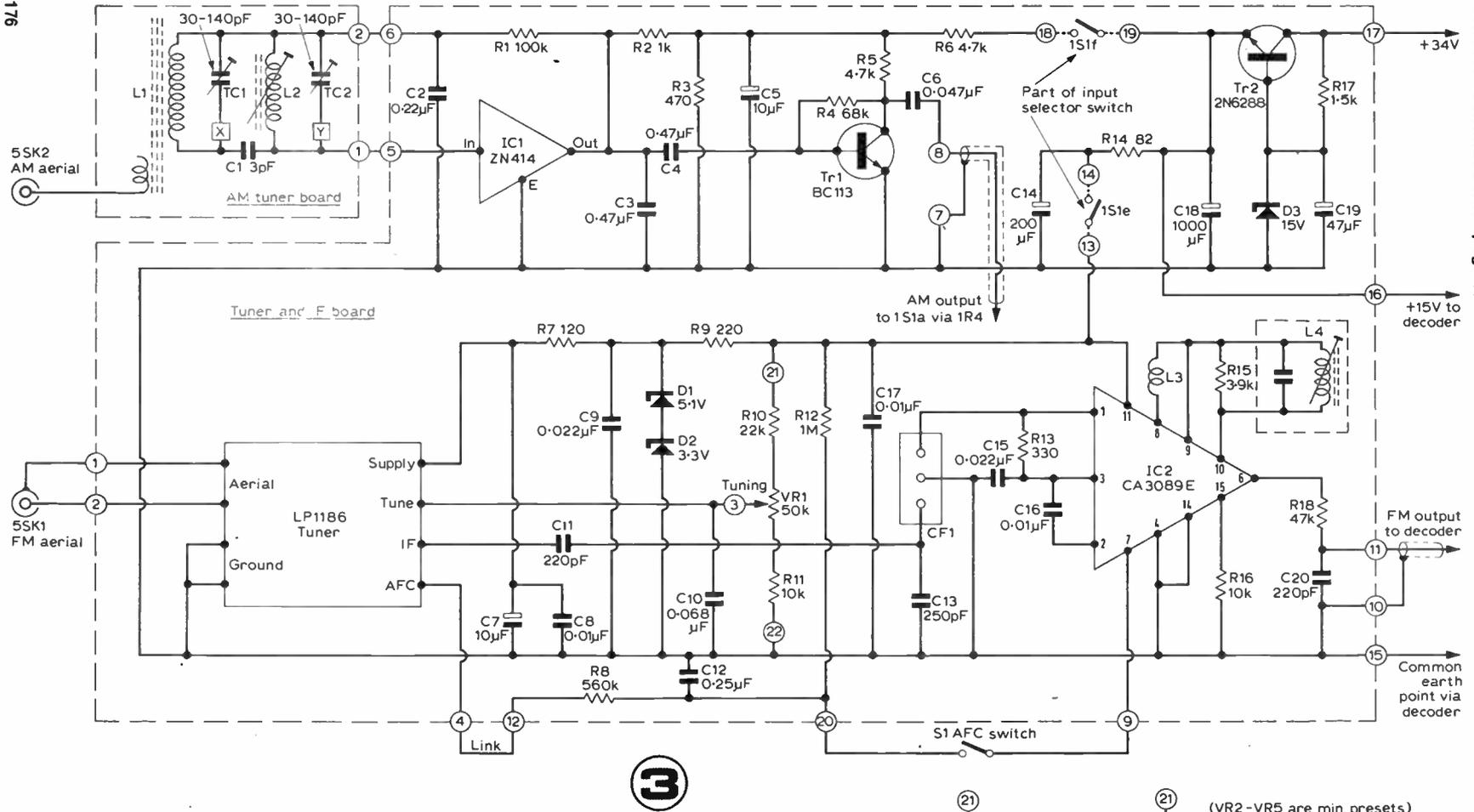

CRATA—continued from page 1174

Fig. 10: Circuit of the Tuner and IF section, including the separate AM Tuner Board.

Fig. 11: Circuits of the alternative VHF tuning control arrangements described in the text:—
 (a) Full Band II coverage
 (b) Four-station preselected tuning.

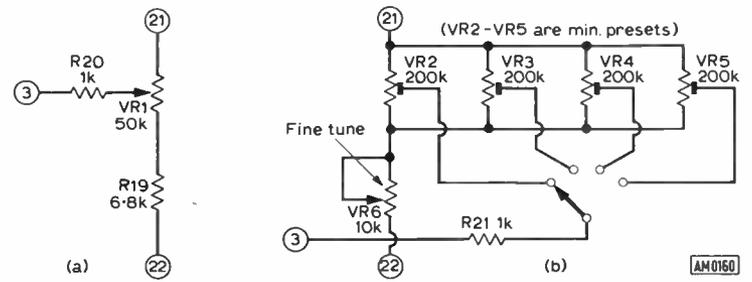

AM0160

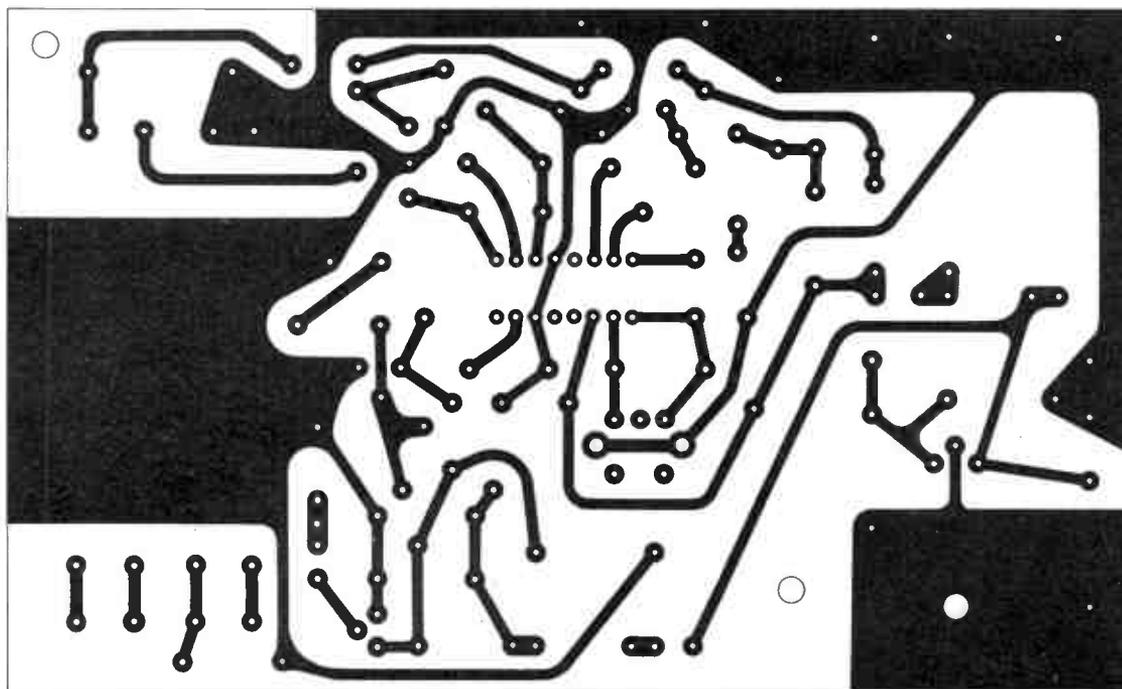
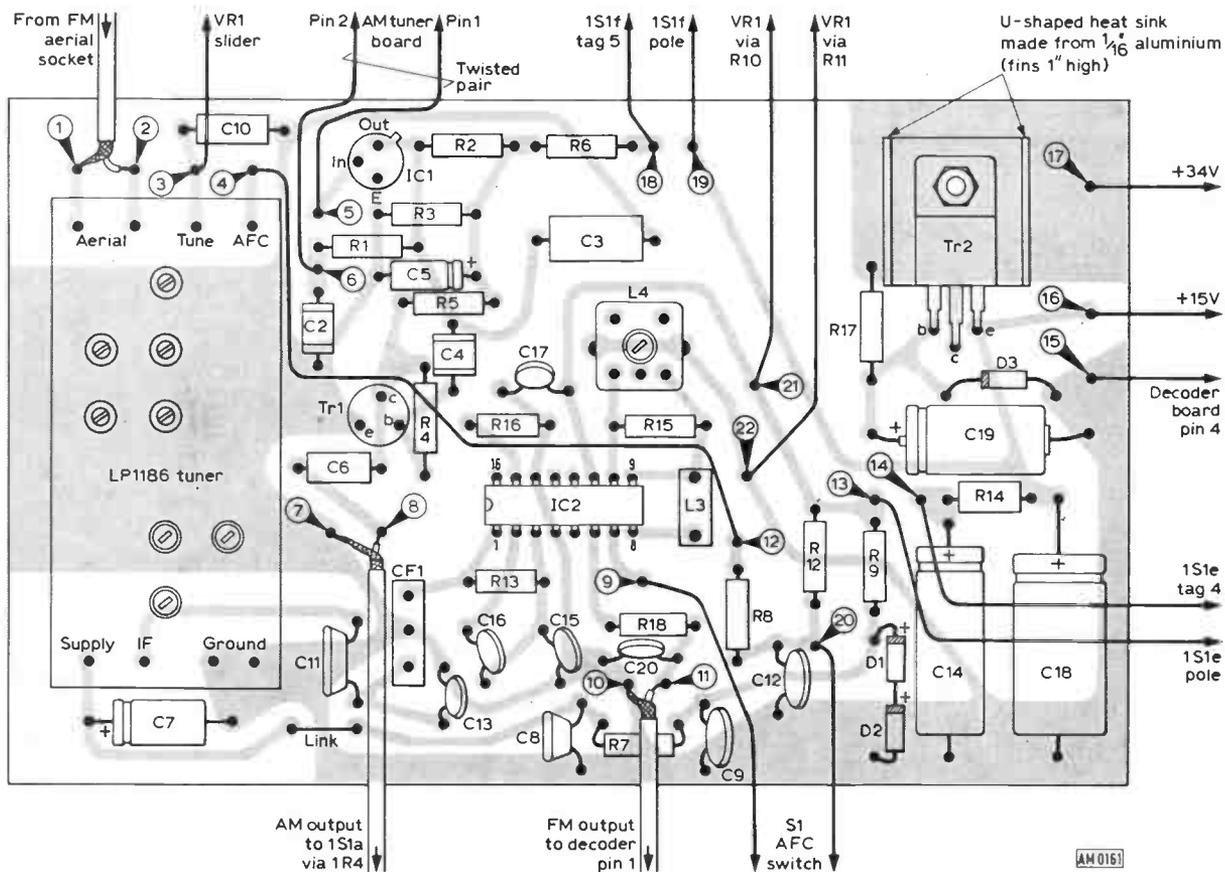


Fig. 12: Component location and printed circuit layout for the main Tuner and IF board. Both drawings are actual size.

★ components list

TUNER & IF BOARDS

Resistors

R1 100kΩ	R11 10kΩ
R2 1kΩ	R12 1MΩ
R3 470Ω	R13 330Ω
R4 68kΩ	R14 82Ω
R5 4.7kΩ	R15 3.9kΩ
R6 4.7kΩ	R16 10kΩ
R7 120Ω	R17 1.5kΩ
R8 560kΩ	R18 47kΩ
R9 220Ω	
R10 22kΩ	VR1 50kΩ lin

Note—The alternative VHF tuning arrangements require the following changes in components.

(1) Full range continuous tuning (Fig. 11a)

Delete R10 and R11 above and add
R19 6.8kΩ R20 1kΩ

(2) Preselected tuning (Fig. 11b)

Delete R10, R11 and VR1 above and add
R21 1kΩ VR2–VR5 each 200kΩ min. preset
VR6 10kΩ lin
All fixed resistors ¼W 5% carbon film

Capacitors

C1 3pF ceramic	C11 220pF ceramic
C2 0.22μF ceramic	C12 0.25μF ceramic
C3 0.47μF polyester	C13 250pF ceramic
C4 0.47μF polyester	C14 200μF 25V
C5 10μF 16V	C15 0.022μF polyester
C6 0.047μF polyester	C16 0.01μF polyester
C7 10μF 16V	C17 0.01μF polyester
C8 0.01μF polyester	C18 1000μF 16V
C9 0.022μF polyester	C19 47μF 16V
C10 0.068μF polyester	C20 220pF ceramic
TC1 30–140pF compression trimmer	
TC2 30–140pF compression trimmer	

Semiconductors

Tr1 BC113	IC1 ZN414 (Ferranti)
Tr2 2N6288 (RCA)	IC2 CA3089 E (RCA)
D1 BZY88 C5V1	D2 BZY88 C3V3
D3 BZY88 C15	

Miscellaneous

- L1 55 turns of 30swg enamelled copper wire on 2¼" x ⅜" dia. ferrite rod
- L2 Single-tuned Medium Wave coil
- L3 RF Choke 15μH Toko 7BA 150J
- L4 Toko KACS-K586-HM
- CF1 Crystal filter Vernitron FM4 or Toko CFS10-7
- S1 SPST min. toggle switch
- FM tuning head Mullard LP1186
- Tuning drive drum 1¼" dia.
- Slow-motion cord drive spindle
- Cord tension spring ¼"
- 3 small nylon pulleys
- Printed circuit boards

Notes

1. RCA semiconductors are available from E.C.S. (Windsor) Ltd. (see Part 1 of this project).
2. Toko components are available from Ambit International.

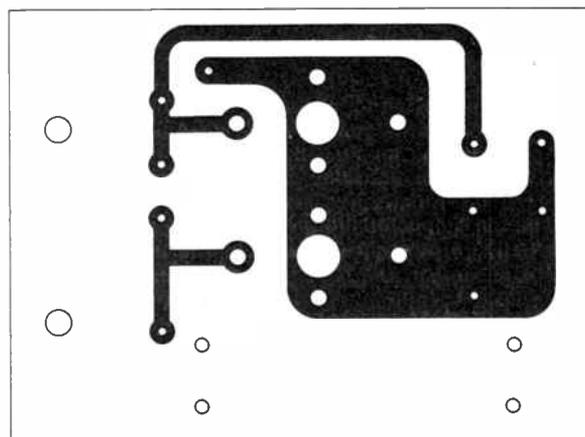
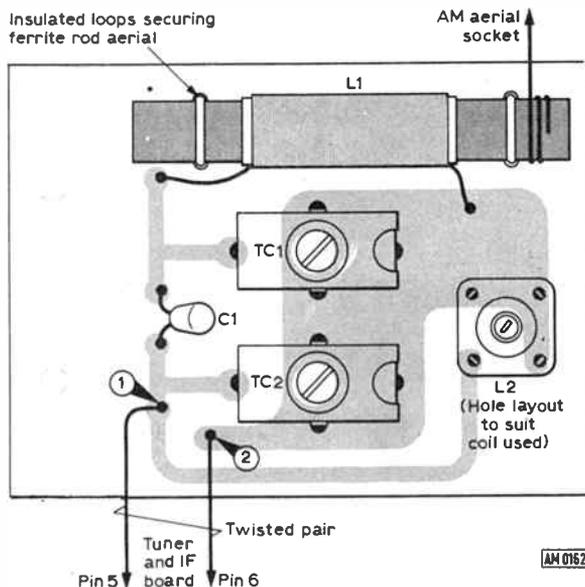


Fig. 13: Location of components and actual size layout for the AM Tuner Board.

Four power supplies are derived from the main 34V rail through a series stabiliser transistor Tr2 and various filter networks.

1. The decoder 15V supply is taken direct from the stabiliser and decoupled via C18.
2. The AM tuner 1.5V supply is provided by a resistive potential divider across the 15V supply R3/R6. Decoupling is provided by capacitor C5.
3. The FM IF and tuner varicap supply is taken from the 15V supply via R14 and decoupled by C14/C17. This supply is 12V.
4. The FM tuner 8V supply is provided from the 12V supply by R9, D1/D2 and R7. Decoupling is provided by C7, C8 and C9.

When assembling the printed board care must be taken not to overheat the integrated circuit pins and also not to short-circuit the adjacent connections as they are fairly close together. Ensure that all electrolytics and diodes are polarised correctly and that the ZN414 leads are correctly positioned. The ceramic filter CF1 may be mounted any way round—the centre pin is earthed and either of the other two pins may be input or output. The series stabiliser transistor Tr2 does not require isolation from either its heatsink or the copper print on the board.

The values given for the tuning control circuit allow coverage of 88–100 MHz. A restricted coverage has the advantage of making the tuning finer and spaces the stations farther apart. The alternative circuit of Fig. 11a provides coverage of the full band 88–104 MHz whilst a four-station preselected tuning arrangement is given in Fig. 11b.

Special Offer tool kit



BE HONEST WITH YOURSELF!

HAVE YOU SEEN YOUR TOOLS LATELY?

DOES YOUR SON BORROW THEM?

DO YOU HAVE ALL THE TOOLS YOU NEED FOR MAKING P.W. PROJECTS?

ARE THEY STILL AS GOOD AS NEW?

DO YOU HAVE NO TOOLS AT ALL?

P.W. READERS CAN BECOME P.W. CONSTRUCTORS FOR as little as £3.70*

Good tools are expensive to buy and it is seldom worth paying for low grade tools because they rarely do a good job for very long.

If you add up how much it can cost to invest in the very best of all the tools you need, it would very likely come to about £12 or more. That's a lot of money in these credit-squeeze days so how can you get good value for money?

Practical Wireless has gone to a great deal of trouble to help you solve the problem; all you need is the equivalent of a small H.P. deposit and nothing more to pay (except postage and packing). Add to this the advantage of good quality tools at realistic retail prices, the backing of our experts who have already tried them out, and you are bound to want our recommended tool kit. The kit does not contain high priced items that you rarely need to use and yet it is not devised for all your jobs in the home.

This kit comprises the tools for doing most of the constructional projects that we publish and others too! In it you will find:

- Wire cutters with insulated handles;
- Long-nose wiring pliers with stripping and cutting blades and insulated handles;
- Small insulated handle screwdriver with neon mains tester;
- Large insulated handle screwdriver;
- Soldering iron kit containing 15 watt soldering iron with $\frac{1}{8}$ " bit, two spare bits $\frac{3}{32}$ " and $\frac{1}{4}$ ", heat shunt clip, stand, solder and instruction booklet "How To Solder".

The normal total recommended retail value of these tools is £6. This kit is supplied to readers of Practical Wireless at the special price of £3.70 (inc. V.A.T.).

*To get your special offer P.W. Tool Kit complete the attached coupon in ink and send with your remittance of £3.70 plus 50p for carriage and packing made payable to Stewart Chance & Co.

Remember, strictly one tool kit per coupon only! Please allow 14 days for delivery in U.K. only.

This offer is limited and subject to stocks still being available.

PRACTICAL WIRELESS TOOL KIT OFFER—

APRIL 1974

To Stewart Chance & Co.,
Wilburn House, London Road,
Sunningdale, Berkshire, SL5 0DJ

Please send to me ONE PRACTICAL WIRELESS TOOL KIT. I enclose *Cheque/Postal Order No.

..... to the value of to cover the cost. I understand that you can supply only one Practical Wireless Tool Kit per coupon. (Block letters please)

NAME

ADDRESS

.....

..... (postal code)

This offer is subject to stocks remaining available at the date of receipt of this coupon.

CRATA—continued

The AFC switch is mounted on the tuner back panel near the aerial sockets—it may be sited on the front panel if required, but do not locate it near to the mains neon and switch.

The AM aerial board, Fig. 13, on which the ferrite rod is mounted should ideally be mounted such that it can be rotated through 90° for maximum signal pickup. Alternatively it may be rigidly mounted in the correct position if the tuner will always be sited in one particular place. The leads between the printed board and the rotary switch in the multi-station version should be kept very short. A suitable position for the switch is immediately above the Input Selector.

Due to pressure on editorial space, details of the Stereo Decoder have been held over until our May issue which will also describe the Power Unit and Chassis.

oscilloscope

PART 2

techniques ALAN AINSLIE

OSCILLOSCOPE DISPLAYS

The very heart of any oscilloscope is the cathode ray display tube. After all the electronic functions have been executed the ultimate result is displayed, visibly, on the face of the tube. We shall take a look at a few types of CRT and their associated circuitry as applied to oscilloscopes.

The electron beam, produced by an electron gun, passes through a deflecting mechanism and arrives at the screen where it causes the screen material to fluoresce. The whole mechanism is housed in an evacuated glass container and, in an oscilloscope, only the front face is visible. Fig. 1 shows the general arrangement. For oscillographic use we require a bright spot of light, intense but very small.

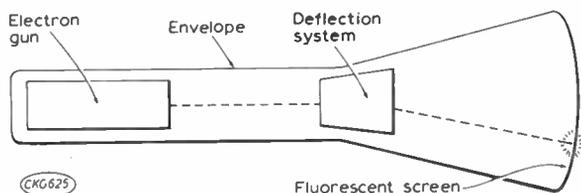


Fig. 1: Main elements in a CRT intended for use in an oscilloscope.

It is the purpose of the electron gun to produce the narrow stream of electrons of high energy to cause local luminescence of the screen. When the beam hits the phosphor screen it causes fluorescence. However, if the beam is cut off suddenly the screen continues to glow with phosphorescent light. It is this phosphorescent light that determines the after-glow of the tube.

ELECTRON GUN

A hot cathode on the axis of the tube produces electrons by thermionic emission, as in a conventional electronic valve. By a suitable arrangement of anodes an electric field distribution inside the tube is created focusing the electrons into a high velocity pencil, arranged to converge on to the screen. A simple gun arrangement is shown in Fig. 2. This type of arrangement is often used and is known as a pentode or five electrode gun.

The cathode is heated to emissive temperature and is surrounded by the grid, in this case shaped like a top hat with a hole in it, known as a Wehnelt cylinder. The grid is maintained slightly negative with respect to the cathode and focuses the space charge around the cathode along the axis of the gun.

The first anode (A1) is positive with respect to the cathode by perhaps a couple of hundred volts. Fig. 3 shows how the electrons are accelerated out of the grid area towards the first anode, and in so doing are focused at Z by the equipotential lines, shown dotted. The diameter at Z is used as an "image" and consequently should be as small as possible for a small spot on the screen. The electron beam enters the first anode diverging and a number of stops are added to keep the beam width small and keep out fringe electrons which impair definition. The diverging electron beam emerging from the first anode now needs to be focused on to the screen, or put another way, an image of Z is projected on to the screen.

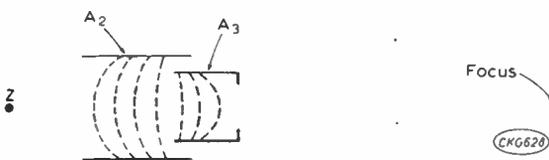
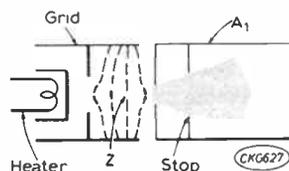
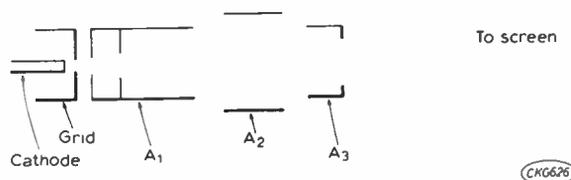


Fig. 2: top, arrangement of electrodes used in a pentode gun. Fig. 3, centre, shows the beam focusing action of the grid and A1. Fig. 4, bottom, the effect of the remaining anodes A2 and A3 in focusing the beam on to the screen.

Fig. 4 shows how the second (A2) and third (A3) anodes accomplish this focusing. The second anode is at a higher potential than A1, and A3, the final anode, is at a still higher potential. Thus the equipotential lines are as shown dotted. The beam of electrons now converges as it crosses the A2-A3 fields and by adjustment of the voltage between A2 and A3 the beam can be focused on the screen of the CRT.

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m. 5 p.m.

PLEASE ADD 10% VAT

RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.
1/2W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.
1/2W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	Price
1	5%	4.7Ω-2.2MΩ	E24	1p 0.8p
1	10%	3.3MΩ-10MΩ	E12	1p 0.8p
1	2%	10Ω-1MΩ	E24	3.5p 3p
1	10%	1Ω-3.9Ω	E12	1p 0.8p
1	5%	4.7Ω-1MΩ	E12	1p 0.8p
4	10%	1Ω-10Ω	E12	6p 5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107	15p	AF126	20p	BF115	25p	OC42	12p	2N3707	12p
AC126	12p	AF139	32p	BF173	20p	OC44	12p	2N3708	10p
AC127	15p	AF178	32p	BF177	28p	OC45	12p	2N3709	11p
AC128	15p	AF180	40p	BF178	32p	OC70	12p	2N3710	11p
AC131	12p	AF181	40p	BF179	32p	OC71	12p	2N3711	11p
AC132	12p	BC107	12p	BF180	32p	OC72	12p	2N3819	32p
AC176	15p	BC108	12p	BF181	32p	OC81	12p	2N4062	12p
AC187	22p	BC109	12p	BF194	14p	OC82D	12p	2N4286	20p
AC188	22p	BC147	12p	BF195	14p	2N2646	60p	2N4289	20p
AD140	50p	BC148	12p	BF197	15p	2N2904	20p	40360	35p
AD149	45p	BC149	12p	BF200	32p	2N2926	10p	40361	35p
AD161	33p	BC157	14p	BFY50	20p	2N3054	50p	40362	40p
AD162	36p	BC158	14p	BFY51	20p	2N3055	60p	40408	40p
AF114	20p	BC159	14p	BFY52	20p	2N3702	12p	ZTX108	15p
AF115	20p	BC187	22p	BUY105	225p	2N3703	12p	ZTX300	15p
AF116	20p	BD131	75p	OC26	45p	2N3704	12p	ZTX302	20p
AF117	20p	BD132	75p	OC28	50p	2N3705	12p	ZTX500	15p
AF118	38p	BD133	75p	OC35	50p	2N3706	11p	ZXT503	20p

ZENER DIODES

400mW 5%, 3.3V to 30V, 12p.

WIRE WOUND POTS, 3W, 10, 25,

50Ω and decades to 100kΩ, 35p.

DIODES

DIODES	RECTIFIER	1250V	1A	12p	SIGNAL	7p
BY127	1250V	1A	12p	OA85	7p	
IN4001	50V	1A	7p	OA90	5p	
IN4002	100V	1A	8p	OA91	5p	
IN4004	400V	1A	8p	OA202	7p	
IN4006	800V	1A	10p	IN4148	8p	
IN4007	1000V	1A	10p	BA114	8p	

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K log. or lin. 40p.

DUAL GANG, 10K + 10K etc. log. or lin. 60p.

KNOB FOR ABOVE, 12p.

FRONT PANEL, 65p.

18 Gauge panel 12in x 4in with slots cut for use
with slider pots. Grey or matt black finish complete
with fixings for 4 pots.

BRUSHED ALUMINIUM PANELS

12in x 6in, 25p

12in x 2in, 10p

9in x 2in, 7p

THYRISTORS

2N5060	50V 0.8A	30p
2N5064	200V 0.8A	40p
106F	50V 4A	40p
106D	400V 4A	55p

ALUMINIUM BOXES

AB7	2 1/2" x 5 1/2" x 1 1/2"	50p	AB14	7" x 5" x 2 1/2"	84p
AB8	4" x 4" x 1 1/2"	50p	AB15	8" x 6" x 3"	108p
AB9	4" x 2 1/2" x 1 1/2"	50p	AB16	10" x 7" x 3"	122p
AB10	4" x 5 1/2" x 1 1/2"	50p	AB17	10" x 4 1/2" x 3"	108p
AB11	4" x 2 1/2" x 2 1/2"	60p	AB18	12" x 5" x 3"	120p
AB12	3" x 2" x 1"	44p	AB19	12" x 8" x 3"	160p

HEATSINKS—REDPOINT

2W	24p	4W	45p	TO5 Clip	5p	TO1 Single	5p
3W	36p	6W	60p	TO18 Clip	5p	TO1 Double	8p

TRANSFORMERS All have 240V primary

MT30/2	0-12-15-20-24-30V	2A	£2.85
MT50/1	0-19-25-33-40-50V	1A	£1.90
MT50/1	0-19-25-33-40-50V	1A	£1.55
MT50/2	0-19-25-33-40-50V	2A	£3.50
MT60/1	0-24-30-40-48-60V	1A	£2.10
MT60/1	0-24-30-40-48-60V	1A	£2.80
MT60/2	0-24-30-40-48-60V	2A	£3.80

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 0.1μF, 0.15μF, 0.22μF, 0.33μF, 0.47μF, 0.68μF, 1μF, 1.5μF, 2.2μF, 3.3μF, 4.7μF, 6.8μF, 10μF, 15μF, 22μF, 33μF, 47μF, 68μF, 100μF, 150μF, 220μF, 330μF, 470μF, 680μF, 1000μF, 1500μF, 2200μF, 3300μF, 4700μF, 6800μF, 10000μF, 15000μF, 22000μF, 33000μF, 47000μF, 68000μF, 100000μF, 150000μF, 220000μF, 330000μF, 470000μF, 680000μF, 1000000μF, 1500000μF, 2200000μF, 3300000μF, 4700000μF, 6800000μF, 10000000μF, 15000000μF, 22000000μF, 33000000μF, 47000000μF, 68000000μF, 100000000μF, 150000000μF, 220000000μF, 330000000μF, 470000000μF, 680000000μF, 1000000000μF, 1500000000μF, 2200000000μF, 3300000000μF, 4700000000μF, 6800000000μF, 10000000000μF, 15000000000μF, 22000000000μF, 33000000000μF, 47000000000μF, 68000000000μF, 100000000000μF, 150000000000μF, 220000000000μF, 330000000000μF, 470000000000μF, 680000000000μF, 1000000000000μF, 1500000000000μF, 2200000000000μF, 3300000000000μF, 4700000000000μF, 6800000000000μF, 10000000000000μF, 15000000000000μF, 22000000000000μF, 33000000000000μF, 47000000000000μF, 68000000000000μF, 100000000000000μF, 150000000000000μF, 220000000000000μF, 330000000000000μF, 470000000000000μF, 680000000000000μF, 1000000000000000μF, 1500000000000000μF, 2200000000000000μF, 3300000000000000μF, 4700000000000000μF, 6800000000000000μF, 10000000000000000μF, 15000000000000000μF, 22000000000000000μF, 33000000000000000μF, 47000000000000000μF, 68000000000000000μF, 100000000000000000μF, 150000000000000000μF, 220000000000000000μF, 330000000000000000μF, 470000000000000000μF, 680000000000000000μF, 1000000000000000000μF, 1500000000000000000μF, 2200000000000000000μF, 3300000000000000000μF, 4700000000000000000μF, 6800000000000000000μF, 10000000000000000000μF, 15000000000000000000μF, 22000000000000000000μF, 33000000000000000000μF, 47000000000000000000μF, 68000000000000000000μF, 100000000000000000000μF, 150000000000000000000μF, 220000000000000000000μF, 330000000000000000000μF, 470000000000000000000μF, 680000000000000000000μF, 1000000000000000000000μF, 1500000000000000000000μF, 2200000000000000000000μF, 3300000000000000000000μF, 4700000000000000000000μF, 6800000000000000000000μF, 10000000000000000000000μF, 15000000000000000000000μF, 22000000000000000000000μF, 33000000000000000000000μF, 47000000000000000000000μF, 68000000000000000000000μF, 100000000000000000000000μF, 150000000000000000000000μF, 220000000000000000000000μF, 330000000000000000000000μF, 470000000000000000000000μF, 680000000000000000000000μF, 1000000000000000000000000μF, 1500000000000000000000000μF, 2200000000000000000000000μF, 3300000000000000000000000μF, 4700000000000000000000000μF, 6800000000000000000000000μF, 10000000000000000000000000μF, 15000000000000000000000000μF, 22000000000000000000000000μF, 33000000000000000000000000μF, 47000000000000000000000000μF, 68000000000000000000000000μF, 100000000000000000000000000μF, 150000000000000000000000000μF, 220000000000000000000000000μF, 330000000000000000000000000μF, 470000000000000000000000000μF, 680000000000000000000000000μF, 1000000000000000000000000000μF, 1500000000000000000000000000μF, 2200000000000000000000000000μF, 3300000000000000000000000000μF, 4700000000000000000000000000μF, 6800000000000000000000000000μF, 10000000000000000000000000000μF, 15000000000000000000000000000μF, 22000000000000000000000000000μF, 33000000000000000000000000000μF, 47000000000000000000000000000μF, 68000000000000000000000000000μF, 100000000000000000000000000000μF, 150000000000000000000000000000μF, 220000000000000000000000000000μF, 330000000000000000000000000000μF, 470000000000000000000000000000μF, 680000000000000000000000000000μF, 1000000000000000000000000000000μF, 1500000000000000000000000000000μF, 2200000000000000000000000000000μF, 3300000000000000000000000000000μF, 4700000000000000000000000000000μF, 6800000000000000000000000000000μF, 10000000000000000000000000000000μF, 15000000000000000000000000000000μF, 22000000000000000000000000000000μF, 33000000000000000000000000000000μF, 47000000000000000000000000000000μF, 68000000000000000000000000000000μF, 100000000000000000000000000000000μF, 150000000000000000000000000000000μF, 220000000000000000000000000000000μF, 330000000000000000000000000000000μF, 470000000000000000000000000000000μF, 680000000000000000000000000000000μF, 1000000000000000000000000000000000μF, 1500000000000000000000000000000000μF, 2200000000000000000000000000000000μF, 3300000000000000000000000000000000μF, 4700000000000000000000000000000000μF, 6800000000000000000000000000000000μF, 10000000000000000000000000000000000μF, 15000000000000000000000000000000000μF, 22000000000000000000000000000000000μF, 33000000000000000000000000000000000μF, 47000000000000000000000000000000000μF, 68000000000000000000000000000000000μF, 100000000000000000000000000000000000μF, 150000000000000000000000000000000000μF, 220000000000000000000000000000000000μF, 330000000000000000000000000000000000μF, 470000000000000000000000000000000000μF, 680000000000000000000000000000000000μF, 1000000000000000000000000000000000000μF, 1500000000000000000000000000000000000μF, 2200000000000000000000000000000000000μF, 3300000000000000000000000000000000000μF, 4700000000000000000000000000000000000μF, 6800000000000000000000000000000000000μF, 10000000000000000000000000000000000000μF, 15000000000000000000000000000000000000μF, 22000000000000000000000000000000000000μF, 33000000000000000000000000000000000000μF, 47000000000000000000000000000000000000μF, 68000000000000000000000000000000000000μF, 100000000000000000000000000000000000000μF, 150000000000000000000000000000000000000μF, 220000000000000000000000000000000000000μF, 330000000000000000000000000000000000000μF, 470000000000000000000000000000000000000μF, 680000000000000000000000000000000000000μF, 1000000000000000000000000000000000000000μF, 1500000000000000000000000000000000000000μF, 2200000000000000000000000000000000000000μF, 3300000000000000000000000000000000000000μF, 470

Ambit International

We are not just another component retailer—but a complete semiconductor service. We can either supply or tell you where to get any 'hard to find' I.C.'s, and can now provide data on most devices you can think of. See our latest datalogue issue for full information.

15p—no S.A.E. required

For those of you who already have an AMBIT datalogue, send us an A5 S.A.E. plus 10p, stating the date of your datalogue—and we will send you all the latest update releases (to page 29).

AMBIT—the linear microcircuit specialists—for Phase Locked Loops

- NE561B AM/FM coil-less radio receiver or IF strip £3-19
- AM/FM demodulator kits with mechanical filter—see October's PW £5-00
- NE562B Similar to the 561, but without AM facility. The VCO output is separately available for synthesizer applications £3-15
- NE565 High stability-low frequency telemetry demodulator and NBFM demodulator £2-55

- 567 A P.L.L. for tone, NBFM and AM decoding (5-9V) working £2-75
- 555 Versatile timing IC, use as 'one-shot' or multi-vibrator £0-78
- LS8038 A unique triangle/square/sine wave function generator up to 1MHz—complete signal generator in a chip. A data sheet is included with each device on request £2-70

for Audio

- LM380N Simple, safe and versatile 2W RMS at 12V: 4W RMS at 18V £1-38
- (14 DIL) Stereo AMP P.C.B. for 2 x LM380N £1-85

for Radio

- TBA910S 7W RMS 14V £1-85 (see last month's advertisement for our radio IC features)
- TBA851 1 μ V sensitivity AM/FM/SSB with RF mixer and IF low external parts count (16 DIL) £1-82
- TBA120 FM IF strip and detector £1-00 (14 DIL)
- CA3089E FM IF system AFC-AGC-SQUELCH-TUNING-METER OUTPUT—the very best FM IC £1-95
- MC1310P P.L.L. Stereo decoder IC with layout spec. £2-85
- (14 DIL) FULL kit with P.C.B. £4-00

- for TOKO filters at 455KHz and 10-7MHz Ceramic
- CFT455B 8KHz bandwidth £0-45
- CFT455C 6KHz bandwidth £0-45
- CFU455C 4-8KHz bandwidth £0-50
- CF510-7 Wide band FM (2 required per set) £0-37
- 455KHz MFH-T 4, 5 or 7KHz versions £1-35
- Mech-LPF2016 A stereo pilot tone notch filter (19 and 38KHz) for HiFi, recording, etc. Both channels £2-20

Plus LED displays, 250MHz decade counters, voltage regulators kits for tone coders, Ni Cads—in fact everything to lead you through the microcircuit maze.

ULTRASONIC REMOTE CONTROL PROJECT, S.A.E. for details of kits and availability.

PW FERRET KIT, Electronics only £9-50

LARSOLT VHF FM TUNERSSETS

1 μ V input for 26dB S/N. INCLUDES SQUELCH, TUNING METER DRIVE BAND SCAN FACILITY, 4 VARICAP CONTROL £16-00

S.A.E. for specification details

FOR ELECTRONIC SUB ASSEMBLIES

Audio SINE/SQUARE/TRIANGLE generator with sweep facility—001Hz-1MHz.

Full kit of components and instructions £11-50

STOP PRESS

Mk. II Ferret: Phase Locked Loop IC metal detector (BFO type)

- Features: *Audible/meter/LED indication of presence of metal
- *Varicap control of search oscillator
- *Phase locked harmonic selection
- *FET reference and search oscillator for extra stability
- *Speaker output

Electronics only kit—P.C.B.—components—instructions £14-50

Please send a S.A.E. for details.

Positively the most technological BFO metal detector at the price!

Ready built and tested—guaranteed 12 months £37-50

PLEASE NOTE ALL PRICES NOW EXCLUDE VAT

37A HIGH STREET, BRENTWOOD, ESSEX CM14 4RH Tel: (0277) 216029

Terms: C.W.O. All prices EXCLUDE VAT. Handling charge 10p per order. FIRST CLASS POSTAGE on all items under 8oz.

TRANSFORMERS

DOUGLAS GUARANTEED
Prices include P. & P. and 10% VAT
12 or 24 Volts

Output V. & Amps.	Ref. No.	Price
12V x 2 250mA x 2	MT111CS**	£1-55
12V x 2 500mA x 2	MT213**	£1-99
12V x 2 1A x 2	MT71CT*	£2-45
12V x 2 2A x 2	MT18CT	£3-08
12V x 2 3A x 2	MT70AT	£3-95
12V x 2 4A x 2	MT108AT	£4-49
12V x 2 5A x 2	MT72AT	£5-28

60 Volts. All tapped at 0-12-15-20-30V.

Output Amps.	Ref. No.	Price	Output Amps.	Ref. No.	Price
500mA	MT112CT* £1-81		4A	MT21AT	£5-22
1A	MT79CT* £2-77		5A	MT31AT	£6-10
2A	MT3AT £3-77		5A	MT88AT	£9-88
3A	MT20AT £4-81		10A	MT89AT	£11-97

400V. Output at 50Hz.

Power Winding	Winding tapped at	Ref. No.	Price
20VA	0-115-210-240	MT113CT	£1-48
75VA	..	MT64AT	£2-95
150VA	0-115-220-240	MT4AT	£3-81
200VA	..	MT85AT	£4-81

C-D Ignition System by R. M. Marston, Esq., Wireless World.

Reference 173AT

EQUIPMENT RANGE

Sec. Output (r.m.s.)	Ref. No.	Price
3-0-3V	200mA MT288CS**	£1-89
0-0-9	100mA MT13CS**	£1-39
12-0-12	50mA MT239CS**	£1-39
20-0-20	30mA MT241CS**	£1-89
0-20-20	300mA x 2 MT214CT**	£2-13
0-8-9 x 2	300mA x 2 MT207CT**	£2-58
0-15-20 x 2	500mA x 2 MT205AT**	£3-89
0-15-27 x 2	500mA x 2 MT203AT*	£3-78
0-15-27 x 2	1A x 2 MT204AT*	£3-78
20-12-0-12-20	700mA (d.c.) MT221AT*	£1-96

AT indicates open universal fixing with tague; CT is open U-clamp fixing with tague; CS is open U-clamp fixing with P.C. spalls; * with interwinding screen; † untapped 240 primary; ‡ tapped at 210-240V.; other primaries tapped at 200-220-240V.

OVER 200 TYPES IN STOCK through Agents or Direct. Please send for lists.

DOUGLAS ELECTRONIC INDUSTRIES LTD.

Direct Sales Dept. P.W., Thames Street, LOUGH, Lincs. LN11 7AD

A DEXTER DIMMASWITCH

ALLOWS COMPLETE LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete 'ready to install' unit or 'simple to assemble' kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescent, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42

All plus 12p post and packing
Prices include VAT. Please send c.w.o. to

DEXTER & COMPANY

5 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO H.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

TIME SWITCH

Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bill, etc. £1-95.

RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are: 2 track record playback heads 50p each; 4 track record playback heads 75p each. Erase heads are also available separately—2 track 35p, 4 track 55p. Metal mounting shields 80p each, 2 track-heads already fixed on heavy mounting plate with shield £1-22.

RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio Kit amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal carpiece. £2-20—twin stethoscopes instead of carpiece 83p. extra—post and ins. 20p.

SLIMLINE FIVE BAND RADIO

As featured this issue! Our 1974 catalogue lists hundreds of bargains and probably many of the parts needed for this project. 66p brings the catalogue and the next 6 monthly supplements.

TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless, August issue. £3-80 plus 20p post and insurance.

MAINS TRANSISTOR P.P.

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1-10.

SLIDE SWITCHES

Slide Switch, 2-pole changeover panel mounting by two 6B.A. screws. Size approx. 1in x 1/2in rated 250v lamp 8p each, 10 for 75p. Ditto as above but for printed circuit 6p each, 10 for 63p. Sub Miniature Slide-Switch, DPDT19mm (1in approx.) between fixing centres. 20p each or 10 for £1-80 8P Change over spring return 250v 1 amp 11p.

THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2-95 plus 20p post and insurance. Industrial model 3A £3-30. (Not on plate).

U.V. LIGHTING

Useful for flaw detection in metals and for looking for water marks, etc. also for fitting over tropical fish tanks, African violets and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 8" U.V. tube—choke—starter holder and tube ends. Price £2-20 plus 20p post.

MULLARD UNILEX 4 WATT HI-FI AMPLIFIER FOR ONLY £1.60

Sensational "once in a lifetime offer" because Mullard over-produced—definitely not repeatable—once our stocks (now over half sold) are cleared. Hi-Fi 4 transistor amplifier, complete in case ready to use. Batt., car or mains operated—freq. range 50Hz-16KHz—distortion better than .2%. Comes complete with guarantee and data FREE to purchasers. Great handbook published by Mullard "tells all you need to know" to build your own stereo. Complete Unilex Stereo System £11.80, pair of speakers for same £8.80.

ADD 10% VAT AND 25p POST AND SERVICE CHARGE IF ORDER UNDER £5

J. BULL (ELECTRICAL) LTD.

(Dept. PW), 7 Park St., Croydon CR0 1YD
Callers to: 102/3 Tamworth Rd., CROYDON

In simpler types of CRT A2 is omitted giving a tetrode electron gun. The final focusing takes place between A1 and the final anode and geometrically is suitable for a fine spot. However, if focusing is achieved by varying A1 (the final anode potential is fixed as we shall see later) this affects the velocity of the beam because A1 is the primary accelerating anode. The change in velocity changes the position of the point Z and the range of focus is restricted for a good spot size. This situation in practice means that when the grid potential (brightness) or the A1 potential (focus) is altered the other potential must be changed as well, giving restricted focus and brightness range. It is for this reason that the pentode type of tube is almost universally used.

BEAM DEFLECTION

An electron has a negative charge of 1.6×10^{-19} coulombs. This is a very small charge, and conversely any electric field acting on the electron will produce only a very small force. However the mass of the electron is very small and so large accelerations can be produced with only moderate potentials.

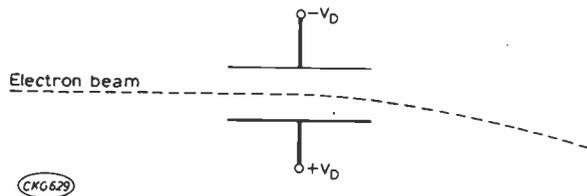


Fig. 5: Effect of the deflecting plates on the electron beam.

If a beam of electrons, focused into a fine pencil, is allowed to pass between two parallel plates as in Fig. 5, the electrons will experience a force towards the positive plate and it can be shown that the deflection is proportional to the deflecting voltage (V_d) and inversely proportional to the accelerating voltage (V_a). A purely mathematical outlook shows that electrostatic deflection produces a (theoretically) linear deflection mechanism.

DEFLECTION PLATES

In order to keep the sensitivity as high as possible the tube is physically large and the deflector plates are placed as close together as possible, usually of the form shown in Fig. 6 to permit high deflection sensitivity to be achieved without the beam catching the actual deflector plates. If this occurs (for example if the timebase is overdriven to give X expansion) secondary emission occurs at the surface of the plates, and the low energy secondary electrons can be accelerated towards the screen causing flare and high background illumination. This undesirable


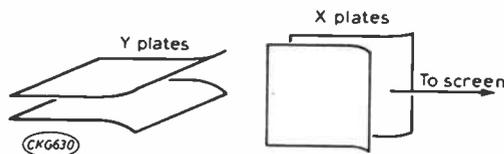


Fig. 6: Arrangement of the X and Y plates, the Y plates being nearer to the gun system.

effect can be avoided by coating the plates with a material of low secondary emission, or providing "beam catchers," small cups that accept the beam when driven off the screen. The X plates are usually mounted nearer to the tube face so that the Y plates have the maximum sensitivity.

To ensure that the electron beam does not become distorted in any way by extra acceleration due to the deflector plates they are arranged to be at the same potential as the final anode. Of course this is only true when the beam is travelling along the axis, but to prevent any gross errors on deflection it is common to provide symmetrical or push-pull deflection. This ensures that the mean electric field is not altered by deflection.

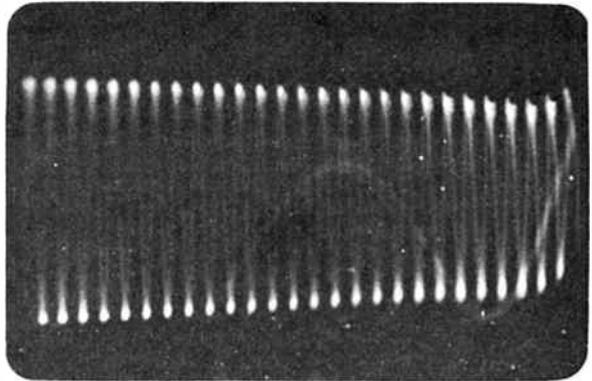

Trapezium distortion on a simple CRT operating with asymmetrical deflection on both axes. The focus and definition make this scope useful only for the simplest applications.

If the plates and final anode were at differing potentials then there would be a deformation of the circular cross-section of the beam (remember it is NOT in focus at this point, only at the screen where the cross-section area should be almost zero) by the plates attracting, or repelling, the outer electrons at opposite sides of the beam. This gives a sausage-shaped spot and the remedy is to make the final anode potential variable so that it may be matched to the Y plates. The X plates are then adjusted to be equal to the Y plate potential (as we shall see in a later section, it would be difficult to alter the Y plate potential). The control for setting the final anode volts is known as the "Astigmatism" potentiometer and is usually a front panel control.



The same CRT displaying a 1kHz square wave. Astigmatism is most noticeable as is the lack of HF response due to the simple deflection amplifier.

Another cause of incorrect spot size and shape is due to the pencil of electrons tending to spread, all being negatively charged. However, in high voltage tubes the velocity of the beam is high enough to keep the electrons in line by the magnetic field that they produce. The mechanism of electrostatic deflection relies on the electron beam being in the field of the deflector plates for a finite time. This means that when a very high frequency, say above 100MHz, signal is applied to the plates the signal may have changed before the electrons have emerged.

If, for example, a beam of electrons takes 10ns to travel through the plates a 100MHz signal will have completed one cycle and the deflection will be zero. In modern high velocity tubes the effect only occurs over 150 or 200MHz and the remedy is to arrange a series of deflectors, linked so that the velocity of the signal down the plates is the same as the velocity of the electron beam. However there are few uses for deflection amplifiers that can produce 200MHz output so this is of academic interest only.

THE FINAL ANODE

In order to produce the high velocity beams that are required to display fast transients, a high accelerating voltage is required. As we have seen, if this is applied to the final anode deflection sensitivity will be reduced so we apply the accelerating potential after deflection, called post deflection acceleration or PDA. Several methods of applying the PDA potential are used but they all aim at not reducing the deflection sensitivity, most important when the deflection amplifiers use transistors having only a limited output voltage swing.

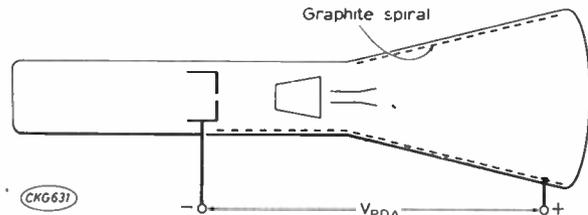


Fig. 7: Location of post deflection acceleration electrode in CRT.

The most popular form of PDA until a few years ago was the form shown in Fig. 7 and used in a lot of Cossor CRT's. The electron gun and tube are as they have been described so far and the beam is accelerated and deflected and focused normally. Around the inner wall of the tube is wound a resistive graphite spiral, connected to the final anode, and at the other end to a few kV positive. The beam is thus accelerated through this field to arrive at the screen with high velocity.

The screen tends to charge negatively at these high energies because more electrons are being gained than lost by secondary emission from the screen. The back of the phosphor is therefore given a very thin coating of aluminium and this conducts the charge to positive PDA, eliminating "screen sticking". This occurs where a local area of screen acquires a negative charge and tends to repel the beam, giving low light output. The aluminium also produces a more axial accelerating field giving better geometry and increased light output by reflecting the light forwards.

The field of the PDA is such as to produce a slightly convergent lens giving a smaller image and also, if it penetrates into the deflector plate region, causes acceleration before and during deflection, decreasing the scan even further. But in spite of this the PDA system offers a distinct advantage of increased trace brightness.

A fine wire mesh can be placed in the path of the beam just after deflection and if connected to the final anode acts as a screen to keep any PDA fields out of the deflection system. This arrangement gives rise to a PDA field that acts as a diverging lens, magnifying the deflection considerably, but also the spot size. Alternatively this mesh can be placed near the screen and PDA applied between the mesh and the screen. This gives very good results without affecting geometry but such tubes are prone to internal flashover.

SCREEN PHOSPHORS

The screen material or phosphor is arranged to give the highest possible light output of the correct colour and persistence. The table shows the range of phosphors used in cathode ray tubes, the most usual being P1 or P5, whilst P7 is sometimes used for medical applications.

Phosphor	Persistence	Fluorescence	Phosphorescence (Afterglow)	Uses
P1	Medium	Green	Green	Scopes (Visual)
P2	Long or Short	Blue/Green	Yellow/Green	Scopes (Visual)
P3	Medium	Yellow	Yellow	Television
P4	Medium	White	White	Scopes (Photography)
P5	Short	Blue	Blue	Television
P6	Medium	White	White	Radar
P7	Long	Blue/White	Yellow	Storage Tube
P8	Short	Blue/White	Yellow	Scopes (Photography)
P9	Long	White	White	Scopes (Photography)
P10	Permanent	Magenta	Magenta	Radar
P11	Short	Blue	Blue/Green	Storage Tube
P12	Long	Orange	Orange	Scopes (Photography)
P14	Long	White	Orange	Radar
P15	Short	Blue/Green	Orange/Green	Radar
P19	Long	Orange	Orange	Flying Spot Scanners Radar

Table of phosphor types and principal applications.


Although the trace produced on a tube can be intensely bright, even with only a couple of kV, the contrast between the trace and the background (grey/white) is usually quite small. A filter of about 65% transmission, of the colour of the trace, placed in front of the tube can increase the contrast by a large amount despite a decrease in light output.

GRATICULES

The graticule or measuring scale can be engraved on the filter or a better idea is to cut the graticule into a piece of 1/8in. perspex. If the markings are on the front, the observer can move so that the reflection of the line from the back surface of the graticule are in line with the actual lines. This ensures zero parallax when making measurements. The perspex can be lit from the side by a red bulb causing the cuts in the perspex to light up red, although white light is better for photography due to the uneven spectral response of films. Constructors making their own graticules out of perspex must bear in mind that the clearest line, especially with side illumination, is produced by cutting the perspex with a sharp knife and not by scratching.

ELECTROVALUE

CATALOGUE 7

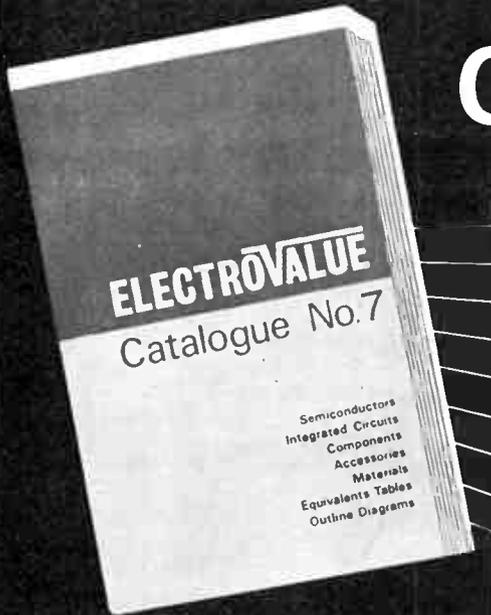

An A to Z guide to component buying

On the index page of Catalogue 7, between "Aluminium Boxes" and "Zener Diodes" are over 200 references to contents amounting in all to thousands of items, classified, described, often illustrated, and priced. There is a wealth of technical diagrams and data. At 25p, Catalogue 7 is excellent value by any standard. With the 25p Refund Voucher it costs you virtually nothing when you order £5-worth or more.

25p INCLUDING 25p REFUND VOUCHER ALLOWABLE ON ORDERS £5 OR MORE LIST VALUE

★ A SELECTION FROM EV CATALOGUE 7

TRANSISTORS

and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc. etc.

MINITRON DIGITAL INDICATORS

3015F Seven segment filament, compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL (some alphabetical symbols available) £1.20
Suitable BCD decoder driver £1.15
3015G showing + or - & 1 & dec. pt. £1.20

DALY ELECTROLYTIC CAPACITORS

In cans, plastic sleeved
1000mF/25V 28p 1000/50 41p
5000/100 £2.91 2000/50 57p
5000mF/25V 62p 5000/50 £1.18

POLYESTER CAPACITORS TYPE C.280

Radial leads for P.C.B. mounting. Working voltage 250V d.c.
0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p
0-068, 0-1, 0-15 ea. 4p
0-22, 5p; 0-33 7p; 0-47 8p; 0-68 11p; 1 0 14p;
1-5 21p; 2-2 24p

SILVERED MICA CAPACITORS

Working voltage 500V d.c.
Values in pFs—2 to 820 In 32 stages ea. 6p
1000, 1500 7p; 1800 8p; 2200 10p; 2700, 3600 12p;
4700, 5000 15p; 6800 20p; 8200, 10,000 25p

POTENTIOMETERS

ROTARY CARBON TRACK. Double wipers for good contact and long working life.

P.20 SINGLE linear 100ohms to 2-2megohms, ea. 14p
P.20 SINGLE log. 4-7Kohms to 2-2megohms, ea. 14p
JP.20 DUAL GANG lin. 4-7Kohms to 2-2megohms, ea. 48p

JP.20 DUAL GANG log. 4-7Kohms to 2-2megohms, ea. 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only ea. 48p

JP.20 DUAL GANG antilog 10K only 48p

2A DP mains switch for any of above 14p extra.
Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets Type PR, horizontal or vertical 6p each.

SLIDER POTENTIOMETERS

Linear or log. 10K to 1 meg. In all popular values. ea. 30p

Escutcheon plates, black, white or light grey, ea. 10p
Control knobs, blk/wht/red/yel/grn/blue/dk. grey/lt. grey ea. 7p

ZENER DIODES

Full range E24 values: 400mW: 2-7V to 36V, 14p each;
1W: 6-8V to 82V, 21p each; 1-5W: 4-7V to 75V, 48p each. Clip to increase 1-5W rating to 3 watts (type 266F), 5p.

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/20	82-220K	9	8	7-5
CC	1/3	4-7-470K	1-3	1-1	0-9 nett
CC	1/2	4-7-10M	1-3	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-9 nett
C	1	4-7-10M	3-2	2-5	1-9 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-3-9	9	9	8
WW	3	1-10K	7	7	6
WW	7	1-10K	9	9	8 nett

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide, Ektrosil TR5, ultra low noise.
WW = wire wound, Plessey.

Values: All E12 except C 1/2W, C 1/2W, and MO 1/2W. E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.

E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% ±0.05Ω and MO 1/2W 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

VEROBOARD

Copper clad 0-1 matrix—2-5 x 3-75 ins. 24p: 3-75 x 3-75 ins.—27p; 2-5 x 5 ins.—27p; 3-75 x 5 ins.—30p.

Copper clad 0-15 in. matrix 2-5 x 3-75 ins.—18p; 3-75 x 3-75 ins.—27p; 2-5 x 5 ins.—27p; 3-75 x 5 ins.—33p.

Vero spot face cutter (any matrix) 43p.

0-040 pins (for 0-1 matrix) per 100—30p.

0-052 pins (for 0-15 matrix) per 100—30p.

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-90.

The size and weight of this product obliges us to charge 70p part cost of carr. in U.K.

Equaliser Assembly, £2-30.

Loudspeaker Unit 59RM109, £2-45.

Cabinet Kit (to Baxandall design), £10-45.

Cross-over choke included in full kit above, £1 30.

This is EV Service

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14-99. 15% on orders £15 and over.

PACKING AND POSTAGE FREE

in U.K. For mail orders for £2 list value and under there is an additional handling charge of 10p.

GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale.

Prices quoted do not include V.A.T., for which 10% must be added to total net value of order. Prices subject to alteration without notice.

GIRO ACCOUNT No. 38/671/4002

All postal communications, mail orders etc. to Head Office at Egham address. S.A.E. with enquiries requiring answers.

ELECTROVALUE LTD


28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily Sat 9-1 p.m.

Hours of business (both addresses) 9-5.30 p.m., 9-1.30 Saturdays.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

NELSON-JONES FM TUNER KIT

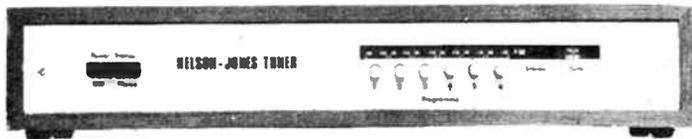

VARICAP TUNING

as in 'W.W.' June '73

Now available to readers of 'Practical Wireless'. The Nelson-Jones tuner uses dual gate MOSFET's in the RF stages, integrated circuits and ceramic filters in the IF stages, for very high performance and quick assembly. Do not confuse with tuners using only bipolar transistors and IF coils!

Tuning is accomplished by variable capacitance diodes and a Push Button Unit with 6 positions. AFC disable is incorporated as well as a pointer for each button showing tuning position in the range 87.5-108MHz, i.e. each 'button' is fully tuneable simply by turning.

Our complete metalwork system is supplied with nuts, bolts, board standoffs, push button mains on/off and stereo mute assembly, sockets, fuse and holder. Printed and Anodised Front Panel and Veneered Teak case. Power supply kits are supplied with complete kits of parts, or separately. LED tuning ind. is also supplied.

Prices for complete kits start at £23.95 + 50p pp. + VAT for mono tuners, (phase locked decoders are also available to fit in the cabinet). Please send large SAE for complete details of special offers and our complete lists.

GREEN LED's—the latest for 'stereo' lamps. 1-9 69p, 10+ 59p.


TEXAN AMPLIFIER

The Cabinet of the Nelson-Jones Tuner is specially designed to match the Texan amplifier cabinet, see photographs, so that owners of Texan's are assured of compatibility, both in superb performance and appearance.

Texan amplifier kits are available at £28.50 + 50 ppp. + VAT.

Worried about tuner alignment? then let our alignment service take over.

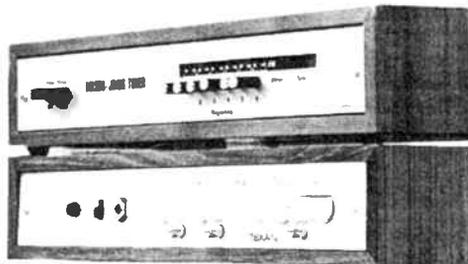Telephone queries. We have REAL ENGINEERS, not salesmen, to answer queries.



INTEGREX LIMITED, Dept. P.W., P.O. Box 45, Derby, DE1 1TW. Tel. Repton (028389) 3580

Train for television

Course commences 4th September, 1974

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____


THE PEMBRIIDGE COLLEGE OF ELECTRONICS
 (Dept. PW1) 34a Hereford Rd., London W2 5AJ

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D, 2D have removable space dividers. Build up any size cabinet for wall, bench or table top

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HARDY!
TIDY!

DISCOUNT PRICES

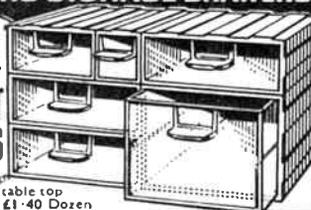

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.40 Dozen
DOUBLE UNITS £2.30 Dozen
TREBLE (3D) £2.50 for 8
DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.60 for 8
EXTRA LARGESIZE (6D1) £3.40 for 8. Carriage 35p
 Orders over £10 post free. **QUANTITY DISCOUNTS!** 5% in £1 for orders over £10, 7 1/2% over £20, 10% over £50. Quotations for large quantities.
PLEASE ADD 10% VAT TO TOTAL REMITTANCE.
 (Dept. PW4), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

FELSTEAD ELECTRONICS (PW78), LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

STYL1 Replacements for virtually all ACOS, BSR, COLLARO, GARRARD, PHILIPS, RONETTE, SONOTONE. Single Tip: Sapphire 18p. Diamond 35p. Double Tip: Can be Stereo/LP + 78 or ST/LP + 8T/LP Sapphire 32p. Double Tip: Diamond ST/LP + Sapphire 78 65p. Diamond ST/LP + Diamond ST/LP £1.20. For GOLDRING Diamond 0800, G800H, and G850 at £1.90 each. G800E at £3.75. (SHURE, PICKERING, are in List.) PIN DOUBT SEND YOUR OLD ONE. IMMEDIATE RETURN GUARANTEED. Charges 8p any quantity.
CARTRIDGES. All with styl1 and fittings. Replacements for ACOS GP/918C (Mono-Stereo compat. + 78) series at 89p. GP93 Stereo + 78. £1.35. GP94 Ceramic Stereo + 78 at £1.75. For RONETTE DC400/SCM (speed change switch at front for GP67, TC8 &c.) £1.15. SONOTONE 9TAHC (dia. stylus) £1.98. 9TAHC6 (slimmer for many Garrard pick-ups) £2.18. For BSR X3H, X5H, X3M at £1.25 ea. SX5H, and SX3M at £1.60 ea. TC8H at £1.40. TC8 Stereo (3 pins) £2.00. Charges 8p any quantity.
RECORDING TAPE. 5" 600 ft. 40p. 5 1/2" 900 ft. 55p. 7" 1200 ft. 62p. 5" 900 ft. 57p. 5 1/2" 1200 ft. 65p. 7" 1800 £1.05. ALL FINEST BRITISH MYLAR. Charges: 5" and 5 1/2" one to 4, 8p each; 5 and over 33p the lot. Charges for 7" 1-3, 11p each. 4 & 5, 33p the lot 6 and over 39p the lot.
PICK-UP WIRE. Super thin, flex acrd. 2-core 8p yd. 4-core 14p yd. Charges up to 10 yds. 8p lot. Over 10 yds. no charge.
SPEAKERS. 2 1/2", 3", 8" or 64 ohms (state which) 55p. Charges 8p ea. 12" Round, fitted cone tweeter, 6 watts undistorted, 3, 8 or 15 ohms (state which) £2.20 (charges 30p). OR. PAIR FOR STEREO, £4.75 charges paid.
CONNECTING WIRE. Pkt. of 5 coils, avtl. coils, ea. 5 yds. Solki core 17p (8p charges). Flexible 19p (+ 10p).
EARPIECES. Magnetic, 2-5 or 3-5mm plug, (state which) 13p. CRYSTAL (3-5mm only) 30p (all 8p up to 6).
VIBRATORS. 7-pin SYNCH. (12SR7 type) 72p. 4-pin NON-synch. (121HD4) 40p (all 8p ea.)
SEND SAE NOW FOR FREE COMPONENTS LIST.

PHOTOGRAPHY

Photographic film (even so called panchromatic) is most sensitive in the blue region and for this reason blue tubes are best suited to making photographic records. However, fast film (400ASA) together with a wide aperture, f2.8 or better, can give reasonably short exposures from a green tube.

When using single lens reflex cameras, best suited to this type of work, it is important to remember that the image on the film is scanned from right to left (lens inversion) and the direction of motion of the blind could well be from left to right, giving a small vertical exposure if the scope sweep speed is slow. The average shutter takes 1/30 or 1/60 of a second to scan the film and so one must be aware of these difficulties when dealing with fairly slow sweep speeds at fast shutter speeds. For single shot photography it is best to have the shutter completely open before the appearance of the trace.

ABERRATIONS

The ideal characteristics of a cathode ray tube are not always realised in practice due to assumptions in the theory, or plain constructional error (anodes off axis, etc.). One of the most important flaws or "aberrations" is that known as "Astigmatism" and this has already been dealt with, together with its cure.

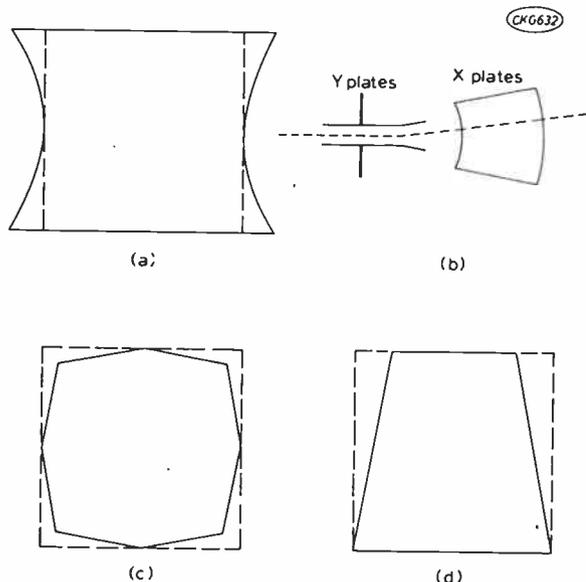


Fig. 8: Pin cushion distortion (a) can be corrected by shaping the plates as in (b). (c) illustrates barrel distortion and (d) trapezium distortion.

Most of the other aberrations are most apparent when the tube is displaying a raster. Ideally such a raster should be capable of being focused into a perfect square of scan lines, all in focus. Some defocusing occurs in deflections due to lens action between the final anode and plates, and between the plates. The effect between the plates is reduced by placing an "interplate shield" between the two sets of plates with a hole for the beam to pass through. This shield is at final anode potential and reduces the defocusing effects.

If the raster takes on the shape of Fig. 8a the distortion is known as pin-cushion distortion and is

caused by the deflected beam travelling through a greater distance between the second set of plates thus arriving at an oblique angle. This can be reduced by making the second pair of plates as in Fig. 8b. Fig. 8c shows barrel distortion caused by loss of extreme scanning sensitivity due to the PDA fields. This can only be reduced by careful design of the PDA spiral. Fig. 8d shows trapezium distortion. This is caused by asymmetrical Y deflection accelerating the beam as the driven Y plate goes positive and decreasing the X sensitivity accordingly. Specially designed plates are available for asymmetrical deflection only.

CRT DEFECTS

Other defects occur in specific tubes and it must be realised that any CRT is a compromise between conflicting factors. Consequently the best instrument tubes as fitted in laboratory scopes can cost several hundreds of pounds, but the home constructor can purchase surplus tubes for just a few pounds and many quite good home-made scopes have been built using these tubes.

With age or abuse cathode ray tubes tend to develop faults the most serious of which is likely to occur at virtually any time, is when the mechanical structure of the electron gun fails. The gun is constructed with tiny spot welds and severe shock or vibration can cause an element to be dislodged. If this happens the tube is almost surely destined for scrap.

Also linked to the mechanical structure of the tube is a fault producing what is known as a "soft" tube. This occurs when a small amount of air leaks into the bulb through an imperfect glass-to-metal seal. This may become evident only after many hours of operation and the symptoms are a diffuse display and a blue glow in the gun assembly. As the pressure inside the tube rises further, tracking occurs in the gun and external circuits can be damaged. In order to avoid this fault occurring it is necessary to take great care when handling the tube and making connections to it. Connections should never be soldered directly on to the tube pins as this is almost certain to break a seal or even crack the envelope, with glass flying everywhere at high velocity.

Perhaps the most common fault, linked directly to old age, is low cathode emission. The cathode surface loses emissivity either by the emissive layer evaporating or becoming poisoned by the remaining gas in the tube. The effect is that in order to see a trace at all the brightness control has to be advanced so far that the beam spot goes out of focus and silvery. The silvery effect is due to the cathode emitting in patches and on some scopes, if the focus control has sufficient range (making focus anode nearly the same potential as final anode), it is possible to produce an image of the cathode on the screen. The image looks a little like the full moon, the dark patches representing areas of low emission.

Sometimes a low emission tube can be improved by deflecting the spot off screen and turning brightness full up for a couple of hours. If this does not work a small transformer supplying 6.3V + 10% can be used to supply the heater (common practice in TV's). However the insulation of such transformers is doubtful over 1kV and a breakdown would make the tube heater/cathode short or damage it in an even worse manner. A small auto transformer is

perhaps the best idea, fed from the normal tube heater supply with a boost of about 10%.

Really bad tubes (that would be thrown out anyway) can sometimes be restored by the circuit in Fig. 9. The heater of the CRT is supplied with 6, 8 or 10V from T1. When the HT switch is closed a small current will flow due to cathode emission. This current strips the top coating off the cathode and if the emissive layer beneath is better then the current will rise. 10 or 15mA is typical of the current to be expected from a good tube if R1 is made 12kΩ.

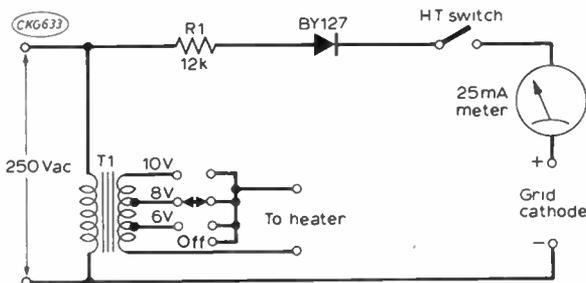


Fig. 9: Circuit of arrangement to restore the cathode emission of a CRT.

The pulse nature of the HT helps the stripping, but if nothing happens then 8 volts can be tried on the heater, 10V is for a real emergency! In many cases switching the heater off with HT still applied, at low cathode temperature, quite vigorous stripping can occur. This is shown by rapid kicks of the meter and small flashes in the gun. In this way really bad tubes can be recovered but it is also possible to weld the grid and cathode together or strip the cathode completely so it should be saved as a last resort.

A3 +150V, Y plates and X plates (depending on external deflection circuits) +150V, PDA anode +1kV. Springs on A3 contact the graphite coating leading to the PDA spiral.

R1, C2 and C3 smooth the -EHT line and R4, C5, and C6 smooth the PDA line. In simple scopes with PDA tubes the PDA is sometimes connected to the highest HT line. C1 couples pulses to the grid to bias the gun off during timebase flyback and R2 is merely to isolate the grid from the EHT line.

When the PDA potential required is only low the EHT is derived from a mains transformer, but when 10kV or so is required, together with high beam currents, use is made of an RF EHT supply. This generates AC at about 30kHz and is fairly safe. We shall consider this in greater detail in a later section on power supplies, but one important advantage must be mentioned here.

Because the RF EHT supply is self generating, involving usually an oscillator and a power output stage driving a transformer, the supply is easily stabilised against variations by sampling the output and applying feedback and, because of the high frequency, smoothing is relatively simple.

SPECIAL TUBES

Often it is necessary to present two traces simultaneously on one tube, scanned by a common X timebase. Although successful electronic methods are available to enable two traces to be presented apparently simultaneously a double beam tube is favoured for some applications.

The simplest approach is to construct two guns in one envelope, each with a set of Y plates and common X plates. This method is expensive, however, and the principle usually adopted is to split

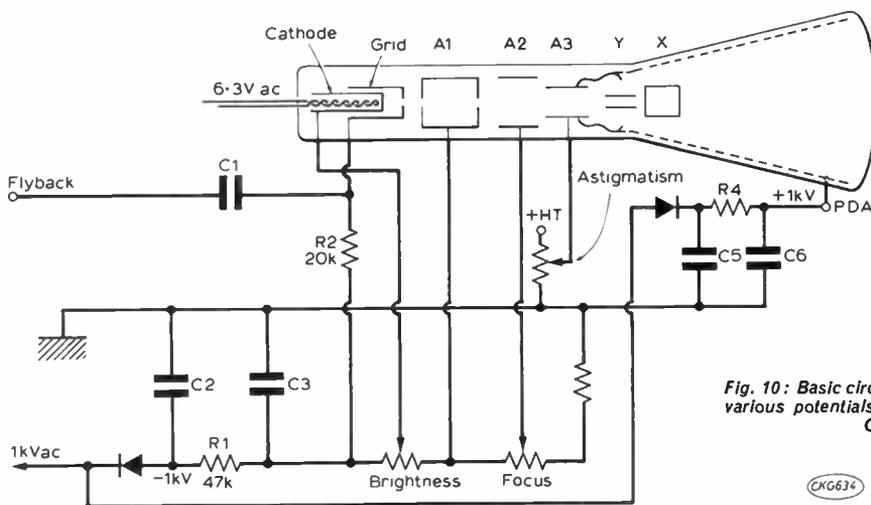


Fig. 10: Basic circuit for supplying the various potentials required by a PDA CRT.

CRT POTENTIALS

We are now in a position to consider the arrangement of the potentials on the tube to provide the necessary electric fields. Fig. 10 shows a typical arrangement. As we saw earlier A3 must be the same potential as Y plates and so the potentials are decided around this. Typical potentials might be grid -1000V, cathode -995V, A1 -850V, A2 -150V,

the beam. Usually the splitting is done by a splitter plate connected to the final anode. A snag with this method is that secondary electrons produced at the plate cause high background illumination of the screen. Sometimes this is prevented by performing the splitting between A1 and A2.

To be continued

C. T. ELECTRONICS

267 ACTON LANE, LONDON
W4 5DG 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

SEMICONDUCTORS

AC107	35p	BCY31	55p	MJ2801	£1.25	OC36	65p	TIP36C	£4.10	2N2398	70p
AC125	25p	BCY32	95p	MJ2901	£2.20	OC42	40p	TIP41C	95p	2N2646	50p
AC126	25p	BCY33	45p	MJE340	50p	OC44	20p	TIP42C	£1.10	2N2846	£1.50
AC127	27p	BCY34	60p	MJE370	75p	OC45	20p	T1550	40p	2N2904	25p
AC128	28p	BCY38	85p	MJE371	90p	OC70	15p	ZTX107	15p	2N2905	25p
AC176	27p	BCY39	£1.00	MJE390	85p	OC71	15p	ZTX300	15p	2N2906	25p
AC177	25p	BCY55	£1.60	MJE2955	£1.95	OC72	20p	ZTX500	10p	2N2907	25p
ACY18	30p	BCY70	22p	MJE3055	85p	OC75	25p	ZTX501	20p	2N2926	12p
ACY19	30p	BCY71	22p	MM1613	43p	OC76	25p	ZTX504	50p	2N3053	25p
ACY20	25p	BCY72	25p	MM1712	60p	OC77	40p	ZTX531	30p	2N3054	85p
ACY39	55p	BDX21	75p	MPF102	45p	OC81	25p	ZTX550	25p	2N3055	50p
AD140	60p	BD123	75p	MPF103	50p	OC83	25p	1N659	8p	2N3232	70p
AD149	65p	BD124	80p	(2N5457)	35p	OC84	25p	1N914	4p	2N3255	95p
AD161	40p	BD131	75p	MPF104	40p	OC139	30p	1N916	6p	2N3702	14p
AD162	40p	BD132	75p	(2N5458)	35p	OC140	30p	1N4001	8p	2N3703	12p
AF114	25p	BD153	75p	MPF105	40p	OC170	25p	1N4002	9p	2N3704	12p
AF115	25p	BD156	75p	(2N5459)	35p	OC171	30p	1N4003	9p	2N3705	12p
AF116	25p	BDY11	£1.40	MPS A06	35p	OC200	50p	1N4004	10p	2N3706	12p
AF117	25p	BDY12	£1.60	MPS A07	35p	OC201	60p	1N4005	12p	2N3707	12p
AF118	60p	BDY19	£1.95	MPS A56	35p	OC202	75p	1N4006	15p	2N3708	12p
AF172	30p	BF152	20p	MPS U06	75p	TIP29A	49p	1N4007	10p	2N3709	12p
ASY28	30p	BF194	14p	MPS U66	75p	TIP30A	58p	1N4148	7p	2N3771	£2.70
ASZ21	60p	BF195	15p	NKT135	35p	TIP31A	62p	2N696	25p	2N3772	£2.75
BA102	33p	BFX29	30p	NKT222	25p	TIP32A	74p	2N697	20p	2N3773	£2.95
BA112	16p	BFX24	30p	NKT401	85p	TIP33A	£1.05	2N698	25p	2N3819	35p
BA114	16p	BFX85	30p	NKT404	80p	TIP34A	£1.35	2N706	15p	2N3820	35p
BA156	15p	BFX86	30p	NKT773	30p	TIP35A	£3.35	2N708A	15p	2N3825	95p
BC107	12p	BFX88	30p	NKT774	25p	TIP36A	£2.65	2N708	15p	2N3904	22p
BC108	12p	BFY10	35p	OA5	20p	TIP41A	75p	2N930	20p	2N3905	25p
BC109	14p	BFY44	50p	OA10	20p	TIP42A	90p	2N1132	25p	2N4058	12p
BC147	12p	BFY50	25p	OA47	10p	TIP29B	58p	2N1302	16p	2N4059	12p
BC148	12p	BFY51	25p	OA70	12p	TIP30B	60p	2N1303	16p	2N4060	12p
BC149	12p	BFY52	25p	OA79	12p	TIP31B	70p	2N1304	25p	2N4061	12p
BC153	15p	BFY53	25p	OA81	10p	TIP32B	82p	2N1305	25p	2N4126	17p
BC157	14p	BFY90	60p	OA90	10p	TIP33B	£1.12	2N1306	25p	2N4286	15p
BC158	15p	BSW63	65p	OA91	10p	TIP34B	£1.68	2N1307	25p	2N4287	15p
BC159	15p	BSW68	80p	OA200	10p	TIP35B	£2.81	2N1308	25p	2N4288	15p
BC160C	14p	BSY95A	12p	OA201	10p	TIP36B	£3.64	2N1309	25p	2N4289	15p
BC182	14p	BY100	15p	OA210	15p	TIP41B	83p	2N1513	25p	2N4290	15p
BC183	14p	BY122	65p	OA221S	35p	TIP42B	85p	2N1711	25p	2N4444	£1.90
BC184	14p	BY126	20p	OC16	90p	TIP29C	71p	2N1247	70p	2N4871	35p
BC212	14p	BY127	20p	OC19	85p	TIP30C	70p	2N1260	65p	2N4920	60p
BC213	14p	BY164	65p	OC22	55p	TIP31C	85p	2N2217	25p	2N5191	90p
BC214	14p	IS100	15p	OC26	65p	TIP32C	£1.95	2N2218	25p	2N5194	£1.10
BC238	12p	IS103	15p	OC28	65p	TIP33C	£1.30	2N2219	25p	40360	50p
BC239	12p	ML340	55p	OC28	65p	TIP34C	£1.90	2N2220	20p	40361	50p
BCY30	40p	MJ481	95p	OC35	60p	TIP35C	£3.20	2N2222A	25p	40362	55p

DIGITAL	INTEGRATED CIRCUITS	SNT491AN	SNT4145E1-50	SNT4176E1-60					
SNT400	24p	SNT422	48p	SNT450	25p	£1.00	SNT4150E3-35	SNT4177E1-60	
SNT401	24p	SNT423	48p	SNT451	30p	SNT492	75p	SNT4180E1-55	
SNT402	24p	SNT425	48p	SNT453	30p	SNT495	75p	SNT4153E1-35	SNT4181E7-00
SNT403	24p	SNT427	42p	SNT454	30p	SNT494	80p	SNT4154E2-00	SNT4182E2-00
SNT404	24p	SNT428	50p	SNT460	30p	SNT495	80p	SNT4155E1-55	SNT4184E2-45
SNT405	24p	SNT430	29p	SNT470	30p	SNT496	£1.00	SNT4156E1-55	SNT4185A
SNT406	24p	SNT432	42p	SNT472	30p	SNT497	£2.25	SNT4157E1-80	£2.40
SNT407	34p	SNT433	70p	SNT473	40p	SNT4100E2-50	SNT4160E2-00	SNT4190E1-85	
SNT408	26p	SNT437	65p	SNT474	40p	SNT4104E1-45	SNT4161E2-00	SNT4191E1-95	
SNT409	45p	SNT438	65p	SNT475	55p	SNT4105E1-45	SNT4162E3-40	SNT4192E2-00	
SNT410	26p	SNT440	20p	SNT476	45p	SNT4107	50p	SNT4163E3-40	SNT4193E2-90
SNT411	26p	SNT441AN75	SNT480	80p	SNT4110	80p	SNT4164E2-75	SNT4194E2-50	
SNT412	42p	SNT443	75p	SNT481	£1.25	SNT4118E1-00	SNT4165E4-00	SNT4195E1-85	
SNT413	30p	SNT443	£1.90	SNT482	37p	SNT4166E1-90	SNT4166E1-90	SNT4196E1-50	
SNT416	30p	SNT445	£2.00	SNT483	£1.00	SNT4121	95p	SNT4167E8-20	
SNT417	30p	SNT446	£2.00	SNT484	90p	SNT4122E1-35	SNT4170E4-10	SNT4197E1-50	
SNT419	30p	SNT447	£1.75	SNT486	45p	SNT4123E2-70	SNT4174E2-00	SNT4198E8-60	
SNT420	24p	SNT448	£1.75	SNT490	75p	SNT4141E1-00	SNT4175E1-35	SNT4199E8-60	

S.C.R.	TRIACS
BTY79/400R	75p
CRS 1/05	25p
CRS 1/10	30p
CRS1/20	30p
CRS1/40	45p
CRS 3/035	30p
CRS 3/10	30p
CRS3/40	50p
CRS 3/60	70p
CRS 7/400	70p
CRS 7/600	86p
CRS 16/100	85p
CRS 16/200	72p
CRS16/600	£1.05
CI08B	70p
CI10D	85p
TIC 44	35p
16RC/20	70p
2N3525	£1.05

BRIDGE RECTIFIERS	LINEAR OP. AMPS	
BY122 1.5A 40V	709C TO99/DIL	40p
BY164 1.4A 200V	723C TO99/DIL	£1.05
CIC2-100 2A 100V 39p	741C DIL	50p
6A 100V 65p	747Z TO99/DIL	£1.10
	72748P DIL	85p
	723C TO99	£1.05
	CA3014	£1.55
	CA3018	£1.00
	CA3028	£1.20
	CA3036	£1.00
	CA3046	£0.95
	CA3048	£2.54
	CA3075	£1.60
	CA3090Q	£4.85
	MCI3003L	£1.85
	MFC4000B	60p
	SL403D	£1.80
	ZN414	£1.25
	LM309K	£1.90
	TAD 100	£1.90
	TOKO FILTER	45p
	TAD 110	£2.00

LOW COST OSCILLOSCOPES

Coscor Solartron
1035 D.B. CD643.1
1049 Mk.3A. CD711S.2
D.B.
1049 Mk.4. EM1
D.B. WM2

Solartron
WM3B
AD557 WM7
CD513.2 WM8
CD523 S.2 WM16
CD643 WM18
WM26

All prices and details on application, phone 01-994 6275. Inspection welcome—call at warehouse.

V.A.T.

Unless otherwise stated all prices are EXCLUSIVE OF V.A.T. Please add 10% to all orders. Carriage extra, under £5 + 20p. Over £5 post free.

WAREHOUSE

28-24 BEAUMONT ROAD, W.4.
SURPLUS COMPONENTS, TEST EQUIPMENT, etc. etc.

THOUSANDS OF BARGAINS

Test Equipment ★ Oscilloscopes ★ Signal Generators ★ Counters
Cabinets ★ Bridges ★ Meters ★ Transmitters ★ Receivers ★ Power
Supplies ★ Laboratory Equipment ★ Galvanometers ★ Audio Equipment
★ Video Equipment ★ Meters ★ Battery Chargers ★ Motors ★ Etc. ★ Etc.

20 TONS OF ELECTRONIC EQUIPMENT

Resistors ★ Relays ★ Capacitors ★ Switches ★ Transformers ★ Meters
★ Potentiometers ★ Component Panels ★ Semiconductors ★ Cable ★
Values ★ Etc. ★ Etc. ★ Etc.

Regret no lists available. Personal callers only. Cash and Carry only.

AUDIO ACCESSORY SHOP

17, TURNHAM GREEN, TERRACE,
CHISWICK W4.

VALVE AMPLIFIERS

5 Watt £12.50	50 Watt £36.25
15 Watt £24.50	150 Watt £75.00
30 Watt £29.50	500 Watt £124.50

TRANSISTOR AMPLIFIERS

FAL Phase 50W £39.93 | FAL Phase 100W £69.95

DISCO CONSOLES

FAL Disco Mk 2 £82.99 | FAL Power Disco £123.75
(with 70W RMS Amp)

HEAVY DUTY LOUDSPEAKERS

★ SPECIAL OFFER PRICE ★
Decca 8in 10 watt Hi-Fi speaker, plus matching tweeter £7.50 complete
Suitable 2 way Xover £1.21
15in. 70W E.M.I. 8 ohm £19.50

DISCO LIGHTING

Sound-lighting module £7.90
3 channel sound-light £22.50
Oihwhite 6in dia. £5.25
Suitable 1/8m motor £1.90
Strobe 4 Joule £25.00
Single flash box (100W Red, Blue, Gn. Yel.)
Triple flash box £16.25
Suitable for any 12in. speaker
150W Projector and Wheel £25.00
Size: 18in x 18in x 8in approx. £9.90

TEAK VENEERED SPEAKER CABINETS

For 8 x 5in speaker £3.50 each
For 8in. + Tweeter £5.00 each
For 13 x 8in. £8.50 each
For 12in. + Tweeter £9.90 each

ALSO: Audio Connecting Leads, Tape, Cassettes, Stereo Systems, Mixers, M.C. Stands, Speaker Cloth, Turntables, Plyths, Covers, etc., etc.

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

SGS EA1000
Pack No.
1 500 Carbon resistors, 1/4, 1/2, 1 watt
100 Electrolytic Condensers
3 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers
4 250 Polyester, Polycarbonate, Paper, etc., Condensers
5 25 Potentiometers, assorted
6 250 High-stab, 1%, 2%, 5% resistors.
7 50 Assorted Tagstrips
8 1lb Assorted nuts, bolts, washers, spacers, etc.
9 25 Assorted switches, rotary, lever, micro, toggle, etc.
10 50 Preset Potentiometers.
13 30 Unmarked OC71 Transistors.
14 25 Unmarked 250mW Zenerdiodes, 4.7V, 5.1V, 6.2V, 7.5V, 9.1V, 10V. Measured and tested. Please state voltages required.
15 50 GE Diode OA47 equivalent.

ALL COMPONENTS NEW AND UNUSED
£1 + 25p p.p. per pack, £3 for 5 packs p/fee.

★ ★ SPECIAL OFFERS ★ ★

MINIATURE MAINS TRANSFORMER PRI. 240V, SEC. 12V. 100MA
Manuf.: Hinchley
Size: 36 x 45 x 40mm.
F.C. 53mm.

Price 1-65p. 100-60p ea. 1000-50p ea. 10,000-40p ea.

3 CORE PVC INSULATED MAINS CABLE, GREY ML6650, 3 x 7/0-2mm
Price 100m-£4.50, 1000m-£35, 10,000m-£330.

8-47mfd. 50V. MYLAR FILM CAPACITOR. Size 1" x 0.35" x 0.65" P.C. Mount.
Price 100-6-8p ea. 1000-5p ea. 10,000-4-3p ea.

DISCOUNTS UP TO

60%

FULL 12 MONTH AFTER SALES SERVICE
with probably the best discounts offered in the U.K.

ALL PRICES ARE INCLUSIVE OF V.A.T.

FANTASTIC OFFER GARRARD SP25 MK IV.

Goldring G800. Teak finish, plinth and tinted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1.75 for P. & P. and ins. **£17.85**

TURNTABLES

Please add 95p P & P and ins.
BSR MP60 £9.75
Garrard SP 25 Mk IV (CHA) £11.50
Garrard SP25 Mk III £10.50
Garrard 5L65B £13.95
Garrard AP76 £17.50
Garrard 401 £29.50
Garrard Zero 10 (sge) £31.95
Garrard Zero 100 (Auto) £35.95
Goldring GL85/P, P & C £65.95
Goldring G101/P P & C £21.75
Goldring GL72 £24.90
Goldring GL72/P £31.90
Goldring GL75 £43.95
Goldring GL75/P £38.95
Goldring GL75/L £4.25
Thorens TD125 Mk II £98.95
Thorens TD125 AB Mk II £54.95
Thorens TD160 AB & C £47.95
Thorens TD165 AB & C £47.95
Condor Auto Cleaner (Star Value) £1.40 P & P 15p

TUNERS

Please add 55p P & P and ins.
Alpha Highgate FF150 £32.95
Amstrad Multiplex 3000 £37.90
Metrosound FMS 40 £37.90
Metrosound FMS 20 Mk II £37.90
Philips RH 621 £72.95
Rogers R/brook FET 4 (Cha) £32.95
Rogers R/brook FET 4 (Cased) £36.95
Sinclair 2000 tuner £26.90
Sinclair 4000 tuner £27.95
Teleton GT202 (N/P) £29.95

SPEAKERS

£1.65 for P & P (Per Pair)
Amstrad Acoustra 1500 £26.25
Amstrad Acoustra 2500 £30.25
Celestion Ditton 15 £51.95
Celestion Ditton 44 £82.95
Goodmans D/Maxim £40.95
Goodmans Mezzo 3 £56.95
Goodmans Havant £37.95
Keletron K54 £14.95
Keletron K58 £23.25
Rank-Domus 150 £27.60
Rank-Domus 175 £34.25
Sinclair Q16 £12.05
Sinclair Q30 £30.50
Wharfedale Denton II £27.40

SPEAKER KITS

Wharfedale Linton Kit £16.75
Wharfedale Glendale Kit £29.40
Wharfedale Dovedale Kit £44.95

All prices correct at time of press (E. & O. E.) and are subject to alterations

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept PW4, 174 Pentonville Road, London, M1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.


MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

PRINTED CIRCUIT KIT

BUILD 60 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2in x 2 1/2in. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist. Solvent. (6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet Printed Circuits for Amateurs. (9) 2 Miniature Radio Dials 8W/MW/LW. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 60 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements.

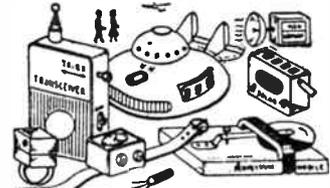

EXPERIMENTER'S PRINTED CIRCUIT KIT

70p

Postage & Pack. 10p (UK)
Commonwealth:
SURFACE MAIL 15p
AIR MAIL 60p
Australia, New Zealand,
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or PhotoCell Radio. (8) "TRI-PLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62in x 0.95in x 0.25in. (11) Wristwatch Radio 1.15in x 0.80in x 0.55in. (12) Ring Radio 0.70in x 0.70in x 0.55in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. (41) Light Dimmer. (42) I.C. Pre-amplifier. (43) I.C. Amplifier. (44) I.C. Intercom. (45) I.C. Radio. (46) Raudive Voices Receiver. (47) Biofeedback Amplifier. (48) Brainwave Detector. (49) Proximity Switch. (50) Laser Projector.
Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector, etc.

YORK ELECTRICS, Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details and a brief description of all kits and Projects.

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary, Slide, Key Switches, I.F.'s, Tag Strips, Drive Drums, Springs, Handles, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels, etc., etc.

Save yourself £'s on these well selected parcels 6lbs net weight £1.00, p. & p. 40p.

Brand new Wire-wound Resistors 1-7 Watts. Good selection, 100 for £1, p. & p. 15p.

Assorted Computer Panels. These panels are exceptionally good value and contain a minimum of 75 transistors, stacks of diodes plus Trim Pots, Polyester Capacitors, and include a few I.C.s. 10 panels for £1.00 p. & p. 27p.

Mullard Ferrite Cores LA3 59p, LA4 75p, LA2100 50p.

BSR Record Player Motors, 9 volts. £1.00 + V.A.T.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection. 300 for £1, p. & p. 20p.

Please include 10% V.A.T. to total cost of goods.

MAIL ORDER ONLY XEROZA RADIO

1, EAST STREET, BISHOPS TAWTON, DEVON

PW Q4 PROJECT


UNIT "A" (Rs, Cs, S/c's) £1.20
UNIT "B" (Rs, Cs, S/c's) £3.88
MULTI-SYSTEM DECODER ADDITIONAL
ALL THESE PARTS ARE FOR THE SAME Q4 PROJECT
PARTS (Rs, Cs, Pots, Switch) £4.91
POWER SUPPLY (R, Cs, S/c's, Transformer) £2.52
PRINTED CIRCUIT BOARDS (set of 5) £2.25
(Fibreglass, drilled, tinned)

ADD 10p P & P ADD 10% V.A.T.

S.A.E. for free list of Q4 and other kits and PCB's for P.W. and P.E. Projects, list with all other enquiries.

PHONOSONICS

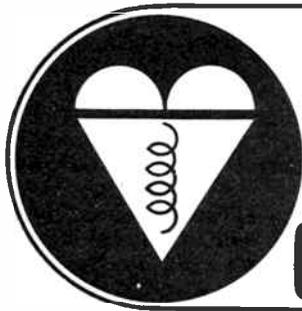Dept PW4, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
MAIL ORDER ONLY



SAFETY IN DOMESTIC ELECTRONICS

THE British Electrotechnical Approvals Board for Household Equipment was set up by the British Standards Institution to promote the widespread practice of standard safety rules in domestic electrical and electronic apparatus. The scheme is now being extended to include audio and radio products, within the first group, i.e. record players, record players with radio, radiograms and mains/battery portable radio receivers with rated audio outputs up to 6+6 watts stereo and 10 watts mono, both continuous sine wave ratings.

The scheme applies the specifications and testing procedures as detailed in BS415: 1972 (with amendments). This short article has been prepared to assist constructors and users of related equipment, since some of the specifications in BS415 are of particular interest to constructors.

The specification states the scope of the safety requirements, the definition of terms used in context, the general requirements, conditions of test, marking and instructions, ionizing radiation, heating, electric shock, insulation, fault conditions, mechanical strength, components, terminal devices, flexible cables, connections, television and other picture tubes and mechanical stability. The notes that follow are for guidance only, in the interest of practising safety considerations.

GENERAL REQUIREMENTS

Under the terms of BS415 adopted for the scheme, the apparatus is expected to be designed and constructed to present no danger and in particular provide for personal protection against electric shock, and the effects of excessive temperature, ionizing radiation, implosion, fire, mechanical instability and moving parts.

MARKING

The equipment should have indelible markings, that cannot be removed by rubbing with cloth soaked in petrol or water, on the exterior (but not on the bottom) or inside a removable lid. The information to be marked should include the following:

1. The nature of the supply, a.c. or d.c. using symbols according to BS3939.
2. The rated supply voltage or range of voltages. In the latter case the indicated voltage setting being used must be clearly shown.
3. The rated mains frequency in hertz if a.c.
4. The voltage and current or power which may be drawn from the main unit to supply other units.
5. Warning of live parts made accessible by removing or opening a cover.
6. Mains flexible leads should have a label attached if permanently connected to the equipment, or a marking should be close to the mains connector on the equipment, giving the following information (for U.K.): "Warning: this apparatus must be earthed".
7. Mains flexible leads should be connected in accordance with the British Standard colour code: Brown to "live", L, or red painted terminal; Blue to "neutral", N, or Black painted terminal; Green and Yellow to "earth", E, green painted or earth symbol terminal.
8. Fuses should be used to protect equipment and the ratings marked close to the fuse (if mounted on equipment) or by labelling the mains supply lead. (As a guide, for equipment of power consumption rated at less than 500W use a 3A fuse, or to withstand switch-on surges, a 5A fuse; for power consumption rated at less than

800W use a 5A fuse; for less than 3kW use a 13A fuse. It is seldom wise to use a 13A fuse to protect small equipment of less than 500W.) The power consumption should be indicated and not exceeded by more than 10%.

TERMINALS

1. Where a separate safety earth terminal is fitted the standard symbol (BS3939) should be visibly marked adjacent to it.
2. Where terminals are live under normal operating conditions a symbol should be marked adjacent to it to indicate this fact. This should include the output terminals of high power amplifiers and transmitters.
3. The outputs of "battery eliminator" units should clearly indicate by marking near the terminals the load power and voltage that can be handled.
4. Terminals used for inter-connecting one or more units to a "master" power supply source should indicate ratings as in number 3 above.

SHOCK PROTECTION

Inaccessible live terminals used for providing connections to other units should be protected by an insulated and captive cover. Live terminals should not be easily accessible during normal operation.

Accessibility is determined by BSI as being touchable by inserting through apertures, or otherwise easily applying, a "standard test finger". For test purposes, this finger is approximately equivalent in size to an average adult index finger 80mm long by 12mm across its narrowest thickness. Also used is a "standard test pin" 25mm long by 6mm diameter, being near the size of a pencil.

Live operating shafts and aper-

tures should be adequately protected so that a free hanging endless metal test chain of 2mm diameter (approximating to a lady's metal necklace chain of small links) cannot make electrical contact through any aperture.

Knobs, levers, push-buttons and similar manually operated devices should be fastened so that their operation will not impair the protection against shock. When removed by detaching the fixing screw, pin, or clip, there should be no exposed live parts.

A metal pin 100mm long and 4mm diameter should not be capable of being brought into contact with any live part, through any aperture, when held by the fingers.

Access holes for setting up of preset controls by means of a screwdriver or hexagonal key wrench should not introduce a risk of the tool touching live parts with a risk of shock. Any other hole within 25mm of this hole should not involve the risk of a shock.

OTHER POINTS

Accessible metal parts should be connected to the earth wire of a 3-core mains cable and effectively earthed through the mains wiring system.

Resistors should not present unstable overload conditions in the event of a short-circuit or disconnection through fault conditions, presenting a hazard under any of the safety require-

ments. Similarly, with the breakdown of capacitors, normally having adequate dielectric strength for the voltage rating quoted by the maker, such a hazard should not result.

High voltage components and assemblies (above 5kV) should not give rise to risks of fire to surrounding apparatus or give rise to any other hazard.

For equipment provided with a connector socket for the mains supply, the safety earth terminal should be an integral part of this socket.

Terminations (including screw soldered or crimped) should be so located or shielded that even one strand of the conductor, that may escape the termination, does not present a risk of accidental contact with another live part or metal accessible part.

Screw terminals should be fixed so that they will not work loose when the nut or screw is tightened or loosened during normal fixing or detachment of connections. Screw terminals should not cause damage to the wire when tightened, thus risking a subsequent fracture.

Flexible mains leads should comply with BS6500.

FINALLY

These are just some of the points worth noting. We would add here that small children are at particular risk unless special care is exercised regarding accessibility to equipment and, of course, hot soldering irons. If

you have small children please do not leave your workbench unattended without first making sure that they cannot gain access to your work. Best to lock the door and/or switch everything off. Large electrolytics hold their charge for some time; it is wise to tape the terminals to insulate against accident touching.

Always use a protective guard for your soldering iron and never leave an exposed hot iron hanging by a hook. Splashes of hot solder and flux can ruin your clothes; wear an overall or old working trousers.

It is always a wise move to have a first aid kit for cuts and shock. Minor burns can be best treated by running cold water on the affected area immediately for at least three minutes. More serious burns should be seen by a doctor. Never apply ointments or creams to a burn without first seeing your doctor.

British Standard specifications can be inspected free of charge at the BSI library in London, W.1. Purchases should be addressed to BSI Sales Dept., Newton House, 101 Pentonville Road, London N1 9ND.

Manufacturers and vendors wishing to be considered for application of BEAB approval to their products are invited to apply to BEAB, Mark House, 153 London Road, Kingston-upon-Thames, Surrey KT2 6NX with full details of their products. All applications within these categories should be received by 8th March, 1974. ■

off the record

AS this is the last issue of *Practical Wireless* in Volume 49, we thought that readers would be interested in a few details before we launch into the 50th volume next month.

Volume 49 carried the most number of pages (1,232 plus covers) in the 33½ years history of monthly *Practical Wireless*. The previous best was 1,184 in volume 37, 1961-62, for 12 monthly issues. Pre-September 1940 issues were weekly. Of these (taken over a six-month period) Volume 1 1932-33 carried 1,256 pages and Volume 3 1933-34 carried 1,184 pages.

There were 89 constructional articles and serial parts, 46 features and serial parts, 8 Datacards, 3 Crosswords, 2 Supplements, 1 competition, 1 special offer, plus the usual regular News and Comment items, all in Volume 49.

We have not counted the number of components that have been listed for our projects, but would make an estimate of several thousands. This may explain the reason why we have broken records with advertisements too, more than 760 pages in Volume 49. There were more than 500 pages of editorial material. What a bargain for £2.50!

The official ABC (Audit Bureau of Circulations) figure for the circulation of *Practical Wireless* for the six-month period July to December 1973 showed a 0.37% increase over the same period of 1972. This was greater than its nearest rivals in a similar field in the U.K., and it still represents the highest ABC figure of all U.K. do-it-yourself radio and electronics journals.

It does show that the magazine's strength is in the active participation of you, the readers, buying components and making them into working projects. Our records of response to advertisements endorse this statement. There must be many of you who are equally content to read about other constructors' activities. For these readers and those of you who are just starting to follow our projects, why not have-a-go now? What's that—you have no good tools? Then you simply must invest in our Special Offer Tool Kit!

COMING SOON

We have some unusual ideas coming in our summer issues, details of which will be given next month. If you can't afford a holiday this year, you can afford 25p for *Practical Wireless* each month. If you can afford a holiday, take P.W. with you. Thousands do!

MAPLIN ELECTRONIC SUPPLIES

*** SAME DAY SERVICE**



Model 120

LARGE or SMALL

PROJECTS DESERVE A CENTURION PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white.



Model 320

Model	W	H	D	Price
120	8	2 1/2	6	£1-85
220	8	6	3 1/2	£2-85
221	8	6	6	£2-90
320	12	8	12	£5-75

Chassis for model 320 £1-75 extra. Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

- ★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator.
- ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra.
- ★ Gold-plated plug-in edge connection. ★ Complete fibre glass board (including tremulant if required) ONLY 3-7in. x 4-5in. ★ Very low power consumption.
- ★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

★ S.a.e. please for full technical details. Trade enquiries welcome.

DMO2T (with tremulant) ONLY £14-25. SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2-83 each OR special price for pack of 12: £25 00. S.a.e. please for data sheet.

MAPLIN: Projected site of London's third airport.

TRANSISTORS, DIODES & IC's.

AC127	25p	BF194	15p	OA90	7p
AC128	20p	BFY51	18p	OA91	6p
AC176	17p	MPF102	36p	1N914	4p
AD149	47p	OC44	20p	1N4148	4p
AD161/2	69p	OC71	20p	1N4001	6p
BC107	10p	T1843	28p	1N4002	81p
BC108	10p	2N1711	24p	1N4003	7p
BC109	10p	2N2919	25p	1N4004	71p
BC147	10p	2N2646	45p	1N4005	8p
BC148	10p	2N2905	33p	1N4006	81p
BC149	12p	2N2907	25p	1N4007	9p
BC168	13p	2N2926D	10p	W005	30p
BC169C	12p	2N2926Y	10p	W04	33p
BC1821	10p	2N2926J	10p	741C 8-pin	
BC204	14p	2N3053	18p	D.I.L.	36p
BC209A	14p	2N3055	49p	741C 14-pin	
BD131	45p	2N3819	30p	D.I.L.	45p
BD132	54p	AA119	7p	D.I.L. Sockets	
BD131/2	£1-20	BY127	16p	8-pin	20p
BD135	36p	BY164	49p	14-pin	15p

See our catalogue for our full range of transistors. 74 series I.C.'s bridges etc.

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price	
1.63	6p	68	6.3 6p	
1.5	63	6p	68	16 6p
2.2	63	6p	68	63 10p
3.3	63	6p	100	4 6p
4.7	63	6p	100	10 6p
6.8	63	6p	100	25 6p
10	25	6p	100	63 12p
10	63	6p	150	5.3 6p
15	16	6p	150	16 6p
15	40	6p	150	25 6p
15	63	6p	150	40 10p
22	10	6p	150	63 12p
22	25	6p	220	4 6p
22	63	6p	220	10 6p
33	6.3 6p	220	16 6p	1000 25 22p
33	16 6p	220	25 10p	1500 6.3 12p
33	40 6p	220	40 12p	1500 10 18p
47	4 6p	220	63 18p	1500 16 22p
47	10 6p	330	4 6p	2200 6.3 18p
47	25 6p	330	10 6p	2200 10 22p
47	40 6p	330	16 10p	3300 6.3 22p
47	63 6p	330	63 22p	4700 4 22p

OMNIUM GATHERUM

- PP3, 6 etc. battery clip dual min. 9p
- PP1, 9 etc. battery clip separate per pair 6p
- Pair crocodile clips 1 red, 1 black insulated sleeve. 7p
- Solder Multicore 22awg 10 metres 20p
- Silicone grease in special dispenser 20ml. 43p
- Red neon 240V panel mounting 25p
- Lacing Cord Strong rayon core 250m. 43p
- Panel fuse holders 20mm 20p; 1 1/2" 35p
- Transformers
 - LT700 min. output transformer Pri. 1-2k Ω Sec. 5 Ω 200mW 37p
 - Sub-min. Mains Transformer 6.0-6V 100mA 95p
 - 12-0-12V 50mA Size: Both approx. 30 x 27 x 25mm. 95p
 - Min. Mains Transformer (Size: 46 x 31 x 38mm) 0-12V 250mA, 0-12V 250mA £1-38
 - Mains transformer MT3AT Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A £3-05
 - Mains Transformer MT206AT Pri. 200-220-240V, Sec. 0-15-20V 1A. 0-15-20V 1A £3-68
- Also in stock: Wide range of brass and nylon nuts, bolts and washers + solder tags, shakproof washers etc.

PLUGS AND SOCKETS



- DIN PLUGS**
 - 2 pin (1 flat) 8p
 - 3 pin, 5 pin A line socket. Per pair 28p
 - (180°), 6 pin B SA 2190 3 pin SA chassis plug 80p
 - SA 1862 Line socket for above 23p
- MAINS**
 - P360 3 pin 1.5A chassis plug with line socket. Per pair 28p
 - SA 2190 3 pin SA chassis plug 80p
 - SA 1862 Line socket for above 23p
- DIN Sockets**
 - 2 pin 6p
 - 3 pin, 4 pin, 5 pin 6p
 - A (180°), 6 pin B plug 7p
- McMURDO**
 - R18 8 way chassis socket 62p
 - 8 way chassis plug with line socket. Per pair 28p
- PHONO**
 - Plug plastic 5p
 - Plug screened 9p
 - Chassis socket 4p
- JACK**
 - Std. 1/4" mono plug Plastic 13p
 - Screened 17p
- Std. 1/4" stereo plug**
 - Plastic 18p
 - Screened 25p
 - Open mono socket 1/4" 10p; Moulded mono socket 1/4" with 2 break contacts 13p; Moulded stereo socket 1/4" with 3 break contacts 18p; 3.5mm. plug plastic 8p; screened 11p; open socket 8p.

WE KNOW YOU NEED IT!



The MES 1974 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! SEND ONLY 25p for our beautifully produced catalogue and leave the rest to us!

POTENTIOMETERS

- Rotary miniature carbon track 1" spindle
 - Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p
- Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 38p.
- Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 23p
- PRESETS
 - Sub-miniature 0-1W Vert or Horiz 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p
- Wirewound 10% 1W 1/2" spindle 10, 50, 100R 34p; 250, 500, 1k, 5k 33p; 10k, 37p; 25k 40p; 50k 44p.

KNOBS

- All 1/4" shaft. Grub screw fixing
- Diameter shown in brackets
 - K30/1 (13mm) 29p
 - K30/3 (17mm) 23p
 - K30/2 (13mm) 26p
 - BK12 32mm long, black pointer with white stripe 61p
 - F12 (33mm) 23p
 - MK50 (34mm) 28p
 - CK4 (36mm) 15p
 - K30/6 (32mm) 42p
- F18 (26mm) with numbered skirt 23p

SWITCHES

- Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p. Mains rotary DPDT 250V 2A 20p.
- Push to make non-locking 13p
- Slide Miniature DPDT 9p
- Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl. toggle) 250V 3A 66p
- Toggle 250V 1.5A with ON/OFF plate 25p.

RESISTORS

- Carbon Film 1/4W 5% 1 Ω to 1M; 10% 1/2M to 10M E12 1p
- Carbon Film 1/4W 5% 1 Ω to 10 Ω; 10% 1/2M to 10M E12 1p
- Carbon Film 1/4W 5% 11 Ω to 910k E12 & E24 1p
- Carbon Film 1W 5% 10 Ω to 10M E12 3p
- Metal Oxide 1W 2% 10 Ω to 1M E12 & E24 4p
- Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms E12 10p
- Wirewound 2 1/2W 5% 1ohm to 270ohms E12 10p
- E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
- E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

VAT Please add 10% to the final total.

Post & packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues for MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. PHONE SOUTHBEND (0702) 4101

"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC... to winding for a maximum holding torque of 3000oz.in with 35v at 0.35 amps through winding. For AC (synchronous) operation at 120r., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz.in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 1/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price.

OUR PRICE ONLY £15

MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/4" x 1 1/2". Pull is approximately 2lbs., plunger travel 1 1/2". Fixing eye takes up to 1/2" bolt, plunger non-captive. NEW in original maker's boxes. £1.20. P. & P. 20p. Large number available, special price for quantity.



SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1/4"; (80 DB) 1/2" x 5/32" x 1/4". Equipment, all tested. £1.20 each. P. & P. FREE.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinge of "to 1 lb. or w". Bracket incorporates 2 fixing screws. Length of arm. 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1 FREE P. & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

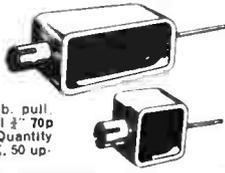240AC type MM6 3lb. pull, 2 1/2" x 1 1/2" x 1 1/2", Travel 1". 90p. each. P. & P. 10p.
240AC type MM4, 2lb. pull 1 1/2" x 1 1/2" x 1". Travel 3/4" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12", 24" x 12", 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32", £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

SILVANIA MAGNETIC SWITCH


Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1 1/2amp at 240v. Size: (approx.) 1 1/4" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8; 100 for £16.50. FREE P. & P. over 10.



AMPEX 7.5v. D.C. MOTOR

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 6000rpm ± speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available 75p each. FREE P. & P.

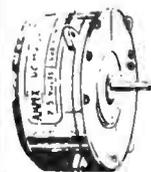

ALL PRICES NOW INCLUDE V.A.T. UNLESS OTHERWISE STATED

All items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50 C.W.O., please. Company orders under £2.50, surcharge 60p unless C.W.O.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

WB44
BLOCK CAPS please

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. £2.30p.

P-C BOARDS (not computer panels)

- 1 off 6 transistors single wave band
- 1 off 4 transistor audio
- 1 off 3 transistor £1.60 the three.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 30p each, 4 for £1.00.

All Transistor STEREOGRAM CHASSIS. Medium, Long and VHF/FM. 3 Watts per channel S/M rating. With circuit service manual. Less tuning scale which can be obtained from well known British manufacturer . . . £20.

Colour Translator panels, as used on well known British E.V.R. Teleplayer. All new panels and components. Type and contents of transistors listed below. Each panel £3.50 each.

X605 .12 off BC148. 2 RCA ca3054(ic). 1 crystal 4.433618MHz. Z607 .12 off BC148. 1 BC158. 1 BC108. 1 RCA ca3046. 1 RCA ca3045(ic).

Z608 .23 off BC148. 2 BC158.

Z612 .12 off ME4102. 2 BC251B. 1 BFY50.

CRYSTAL CALIBRATOR (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz—10MHz (harmonics up to 30MHz) power required 300V DC 15mA. 12V 0.3A DC. Test equipment for 62T M/RC. £2.50 each.

WIRE-WOUND RESISTORS. Our selection of mixed Ohms and Watts. 25 for £1.50, 50 for £2.50, parcel of 1,000 £30.00.

CONDENSER-ELECTRET MIC INSERT incorporating FET Preamp 1 1/2 volt Supply. Details of connections included £1.75.

AUDIO AMPLIFIER MODULE. Due to bulk purchase we can now offer the Audio Amplifier Module (Mullard LP1173) output power, nominal 10 watt. Supply voltage +24 volt, with reference data for £2.50.

ALL ITEMS INCLUDE VAT

All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.



BROADCAST BANDS

SHORT WAVE DX by MALCOLM CONNAH

ONE of the most frequent questions asked by those of you who have written to me recently has been about the modification of the CR100 receiver mentioned in an earlier article. These modifications were described in detail by C. Molloy in the April 1968 issue of *Practical Wireless*.

I appreciate that an issue of this age is rather difficult to come by, but I feel sure that anyone who is really interested should be able to obtain one. (Out of print—Ed.) Perhaps the best way of tackling the problem of finding a copy is to use the CQ column of this magazine.

Two months ago I mentioned that Radio New Zealand should soon be audible again. News has just reached me, via DX Corner Belgium, that the station has recently been heard in the U.S.A. Radio New Zealand was heard on 9540kHz at 0600 and again on 11780 at 0700. Reception was better on the latter frequency.

I know that it means getting up early in the morning, or alternatively staying awake all night; but how about one (or more) of our readers trying to receive this fairly rare station.

Radio Clube de Mozambique is reported to be using 120kW on 7210 from 0700 to 1400 and on 11820 from 0350 to 1500. Tests are also being carried out on 15293kHz.

Readers' Logs

By way of coincidence the first log this month comes from New Zealand. Ian Cook of Nelson has a Stewart-Warner R-146X, 7-valve receiver and a 120ft end-fed aerial which extracted the following signals from the Antipodean ether:

- 3995 *Solomon Islands BS*, in English at 0945.
- 5960 *R. Canada Int.*, in French at 0610.
- 9009 *Kol Israel* in English at 0510.
- 9520 *RNE, Spain* in Spanish at 0310.
- 9625 *R. Canada*, in English at 0830.
- 10135 *Voice of Vietnam, Hanoi* at 1030.
- 11745 *HCJB, Quito, Ecuador* in English at 0530.
- 11875 *Radio Japan*, in English at 0930.
- 11890 *FEBC, Manila* in English at 0935.

Simon Wormleighton and "J. P." Fletcher have returned to school in Cirencester and send the following log using an impressive line-up of equipment (Heathkit SW717 with 35ft wire; Astrad-Altair with 150ft wire and HRO with 8 metre folded dipole):

- 6090 *R. Luxembourg* in German at 1130.
- 7095 *R. Pakistan* in English at 1820.
- 9770 *ORF, Vienna* in German at 1200.
- 11705 *Kol Israel* in English at 2000.
- 15012 *Voice of Vietnam, Hanoi* at 1800.
- 15155 *RSA, South Africa*, in Dutch at 1700.
- 15185 *R. Finland* in English at 1820.
- 17920 *R. Cairo, U.A.R.* in English at 1405.

A gentleman from Northville Road, Bristol who remains anonymous as there is no name on his letter used his CR100 (Modified) and 150ft long-wire to hear:

- 5930 *R. Prague, Czechoslovakia* at 1930.
- 5995 *VOA, Tangier* noted at 2130.
- 6005 *R. Berlin Int.* in English at 1735.
- 6155 *ORF, Vienna* in English at 1830.
- 6190 *Vatican Radio* noted at 2000.
- 7065 *R. Tirana, Albania* at 2210.
- 7110 *VOA, Rhodes* noted at 2125.
- 7275 *RAI, Rome* in English at 1920.
- 9735 *TWR, Monte Carlo* noted at 0915.

Paul Broadhurst from Clevedon in Somerset obtained a Trio 9R59-DS three weeks before sending in this report which is the result of those three weeks of listening. The antenna was a 150ft long wire.

- 5930 *R. Prague, Czechoslovakia* at 1915.
- 6020 *R. Kiev* in English at 1932.
- 6025 *R. Portugal* noted at 2105.
- 6050 *RAI, Rome* in English at 1930.
- 6065 *R. Sweden* in English, at 1600.
- 6070 *R. Sofia, Bulgaria* noted at 1930.
- 6150 *R. Belgrade, Yugoslavia* at 2010.
- 6165 *Swiss Broadcasting Co.*, English at 1330.
- 6190 *Vatican Radio* in English at 2050.
- 7220 *R. Budapest, Hungary* noted at 1630.

Richard Starkey of Southampton is another reader with a new receiver, this time a Vega VEF 206. Using only the built-in telescopic aerial Richard heard the following stations:

- 5930 *R. Prague, Czechoslovakia* at 1900.
- 6025 *R. Budapest, Hungary* in English at 2300.
- 6065 *R. Sweden* in English at 2100.
- 6100 *R. Belgrade, Yugoslavia* at 2000.
- 9625 *R. Canada Int.* in English at 2100.
- 11740 *AFRTS, U.S.A.* in English at 1900.
- 11970 *RSA, South Africa* in English at 1900.

MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

FROM Orkney, G. M. Christie reports hearing BBC Radio London on 1457kHz and IBA Radio Clyde 1151kHz at good strength but subject to fading. He remarks how surprising it is to hear local stations at such a distance. This of course highlights the attraction of medium wave DXing. The majority of medium wave stations serve areas limited by the ground wave (daylight range) but after dark signals can be propagated by skywave far beyond the service area to be picked-up, when conditions are favourable, by 'eavesdroppers' thousands of miles away.

F. F. Wildman (Bournemouth) has been listening to the "As it Happens" programme broadcast by CBA Moncton N.B. in Canada on 1070kHz between 2300hrs and midnight GMT. Using his Codar CR70A receiver with the *Practical Wireless* Medium Wave loop antenna he has logged WNEW 1130kHz in New York City; CHER in Sydney, Nova Scotia on 950kHz and WCBS also in NYC on 880kHz.

W. Pennington (Grimethorpe, Yorks) sent in an excellent log of North American DX using his Trio 9R59DS receiver and 25ft outdoor aerial. Canadians heard include CKCM Grand Falls, Newfoundland on 620kHz; CBN St John's Nfld on 640kHz; CJOX Grand Bank, Nfld 710kHz; CJON St John's on 930kHz; CHNS Halifax N.S. on 960kHz; CFRB Toronto on 1010kHz; CBA Moncton N.B. on 1070kHz. From the United States WHDH Boston on 850kHz; WCBS 880kHz; WINS 1010kHz; WHN 1050kHz and WNEW 1130kHz, the last four being in New York City. Reception was between 2300hrs and midnight in January but it is possible to hear these stations

in March and April from approx. 0100hrs GMT until sunrise.

Ed Baker brought along his Eddystone EB35 when he went on holiday to Majorca and he hooked onto the hotel heating pipes for an aerial. On the Long Waves Azilal, Morocco 209kHz and Tipaza, Algeria 251kHz were heard during daylight together with medium wave outlets in Algeria on 548kHz, 890kHz, 980kHz and 1421kHz. After dark, Caltanissetta, Sicily was heard on 566kHz; Cagliari, Sardinia on 1061kHz; Libya on 1124kHz and 1250kHz. Ed has been interested in MW DXing since 1962 and has received verifications from MW stations in 136 countries.

Simon Hockenhall (Helston, Cornwall) has an HMV 4-band receiver and a 60ft longwire antenna. He reports afternoon reception on the long waves of Motala, Sweden on 191kHz and Azilal, Morocco on 209kHz. On the medium waves Oviedo, Spain 548kHz; Cork, Eire 1250kHz and Nice, France 1554kHz were heard. John Thorburn (Glasgow) used a Vasco Radio with internal ferrite aerial to log BBC R. Merseyside 1484kHz; R. Bristol and R. Teesside on 1546kHz; Tunis on 629kHz; Cairo, Egypt 773kHz; Lisbon, Portugal 755kHz. Philip Allott (Knaresborough, Yorks) has an HRO receiver with vertical antenna and has picked-up BBC local stations at Blackburn 854kHz; Sheffield 1034kHz; Leeds 1106kHz; Stoke 1502kHz; Nottingham 1520kHz; Teesside 1546kHz.

Richard Buckby of BBC Radio Derby sends details of the transmitter operating on 1115kHz (269m). The temporary caravan transmitter is situated at the village of Burnaston, between Derby and Burton and runs 500W into a 110ft vertical mast. Reception reports are welcome and should be sent to Richard at BBC Radio Derby, St Helen's Street, Derby, DE1 3HY.

VHF/FM DXING

by SIMON DAVID

MUCH as I dislike saying this, some of you really are not trying hard enough. Often the cry comes up that you can get BBC programmes but no continentals and, in the south not a good IBA station. This is incredible for the Greater London area and home counties readers who write to me.

Success depends on a combination of factors including tuner sensitivity, aerial used, the nature of the terrain between aerial and transmitter, the rotational direction that achieves maximum pick-up by the aerial, atmospheric conditions. *Practical Wireless* has published considerable information recently to help which I recommend to all DXers of FM.

In the February issue, my article mentioned details of an aerial I have tried. One important aspect in its characteristics was uniformity of loading impedance over a broad band of the FM scale involving broadcast programmes. Without this inbuilt factor in the aerial design, the aerial is usually designed to tune at one frequency, the response tailing off slightly on either side.

This is usually the cause of noisy reception and lower levels at extreme ends, i.e. the 89MHz and 97MHz extremes. Since BBC Radio 2 and the L.B.C. programmes are near these frequencies their signal strength and/or noise will be inferior unless a broad-band near perfect match aerial is employed, such as the Antiference FM263T, 264T and 266T or the equivalents by other manufacturers.

Having fitted such an aerial, then you stand a

better chance of picking up the French stations I mentioned, although weak stations may still be subject to fading and drifting.

Many of you in Northern districts and in Scotland have some difficulty because of the hilly country but it should be possible to receive something, if your aerial is aimed in the right direction with reflector behind the dipole. You could try picking up Irish stations (in the north-west and Wales) and local BBC radio stations up to about 200 miles away. For those of you near the east coast from Aberdeen right down to Kent, you could try for stations in Scandinavia, Holland and Belgium.

Here are some stations to aim at: Oslo 88.65MHz, Bokn 93.5MHz (both Norway); Roermond 88.2MHz(s), 90.9MHz(s), 94.5MHz, all Netherlands; Aalter (Belgium) 90.4MHz, broadcasting the Dutch Network. Mild weather conditions and high humidity should help you.

Let me know how you get on and I will include your results in my article. In the meantime my thanks to the following readers, among others, who have written to me on subjects related to this article. H. Lincoln of Enfield also comments on the effects of mains voltage reductions; S. A. Logier of Belfast has just taken up DXing on retirement; N. S. Gonzales of Chiswick, London, wants less noise, particularly from disc jockeys.

Finally, some details on IBA developments; the following commercial stations are expected to go on the air in 1974, most frequencies to be announced: Birmingham (Feb.), Manchester (March/April), Swansea (summer), Tyneside Wearside (summer), Edinburgh and Liverpool in late '74.

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

**Better built
Better performance
Better value**

SAXON HI-FI POWER AMPS FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.



To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.

SA35 35 watts RMS. Uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

SA50 50 watts RMS. 7 transistors, 7 diodes. Carr. paid. **£5.65**

SA100 makes an ideal unit in disco assemblies. A real glutton for work. Reliable, tough and compact, 11 transistors, 6 diodes. Carr. paid. **£10.90**

BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA.100.

Freq. response	15-40,000 Hz \pm 1dB
Distortion	0.2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75dB
Supply voltage	SA35 45 volts SA50 45-85 volts SA100 40-70 volts

Size	4 1/2" x 4" x 1" (SA 100) 4" x 3" x 1" (SA35/SA50)
------	---

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES

FOR THE SA35, SA50 AND SA100 POWER AMPS. ABOVE

PU.45 Unstabilised supply for 2 SA35's **£4.90**

PU.70 Unstabilised supply for one or two SA50 or SA100 Carr. 40p **£7.75**

PS.45 Stabilised module for two SA35's or one SA50 Carr. free **£3.50**

MT.45 Transformer for above, heavy duty Carr. 20p **£2.85**

MT.30 Transformer for unstabilised supply complete with rectifier diodes mounted Carr. 20p **£3.50**

PS.70 Stabilised supply module for one or two SA100's Carr. free **£4.90**

MT.70 Transformer for PS70 Carr. 40p **£4.90**

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

Orders and personal shoppers to

SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.

Telephone 01-684 6385

Hours 9.30 a.m. - 5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED

SAXON P/A MIXER CONTROL UNITS

In extra slimline easy-fit case

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos etc. Standard jack sockets. Compact design. In strong metal cases. All units guaranteed for 3 years.

● **HIGH AND LOW IMPEDANCE INPUTS**

● **BASS/TREBLE/VOLUME ON EACH PAIR**

● **MASTER CONTROL ON OUTPUT**



● **M4H** 4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" x 2 1/2". Carr. paid. + V.A.T. **£18.50**

● **M6HL** Case 18" x 8" x 2 1/2" 12 inputs (6 high Z, 6 low Z). Carr. paid. + V.A.T. **£27.50**

Channel section modules, for building your own: gain-16 x (24dB). Tone controls-13dB swing. Carr. paid. + V.A.T. **£3.50**

CONTROL UNITS — Unbeatable for quality & value

EXCITING NEW STEREO VERSION. MK. II With Mic. over-ride and case (carr. 30p) **£19.75**



Mono (as shown) For 9v battery operation. As stereo mode less mic. input Carr. 20p **£6.50**

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume. Microphone volume, bass, treble, mains on/off. **COMPARABLE TO UNITS AT OVERTWICE THE PRICE.**

AKG MICROPHONES

World famous D.190C—the one the professionals use—at special bargain price of

£19.50 + V.A.T.

GENERAL PURPOSE DYNAMIC MIC. Professional quality. Special offer carr. paid **£9.90**

120 WATT HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 TO3 can (115 watt) output transistors.

SPECIFICATION

Power output 120 watts into 8 ohms
Freq. response 20-20,000 Hz \pm 2dB
Input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)
Low distortion parallel push-pull output stage.

Module & power supply (Carr. 40p) **£18.95**

● 160 watt version with power supply **£27.90** (Carr. 50p)



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. Carr. 30p. **£19.75**

SOUND AND LIGHT UNITS


Our popular 3 channel model handles up to 3kW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.

SINGLE CHANNEL UNIT

Operates from 5 to 100 watt amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£7.50**

COMPLETE AMPLIFIERS CSE 100

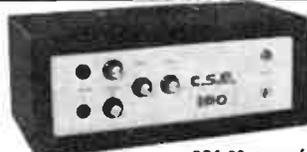The versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. **£34.90 carr. free**



SAXON 100 **£48.50 carr. free**
With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms **£6.95** carr. 30p 15" 50 watt 8/15 ohm **£14.50** carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm **£11.50** carr. 40p.

Prices subject to alteration without notice. E. & O.E.

V.A.T. Please add 10% to total value of order (inc. carr.) for Value Added Tax.

Please include S.A.E. with written enquiries.

TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by road letter please

R T V C

COMPLETE* STEREO SYSTEM



£51.00

40 Watt Amplifier.
Viscount III - R102 now 20 watts per channel. System I includes.
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.
Specification
20 watts per channel into 8 ohms.
Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power).
Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: -12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble -12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.
Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13½" x 9" x 3½".
Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.
Two Duo Type II matched speakers - Enclosure size approx. 17" x 10½" x 6½" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. **Complete System £51.00**

£69.00

System II
Viscount III amplifier (As System I)
Garrard SP. 25 (As System I)
Two Duo Type IIIA matched speakers - Enclosure size approx. 31" x 13" x 11½". Finished in teak veneer. Drive units approx. 13½" x 8½" with 3½" HF speaker. Max. power 20 watts. 8 ohms. Freq. range 20Hz to 20kHz.
Complete System £69.00

PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24.20	£1 p & p
2 Duo Type II speakers	£14.00	£2.20 p & p
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover	£21.00	£1.75 p & p.
	total £59.20	


Available complete for only **£51.00 + £3.50 p. & p.**

PRICES: SYSTEM 2

Viscount R 102 amplifier	£24.20	+ £1 p & p
2 Duo Type IIIA speakers	£39.00	+ £4.00 p & p
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover	£21.00	£1.75 p & p.
	total £84.20	

Available complete for only **£69.00 + £4 p & p.**

STEREO 21

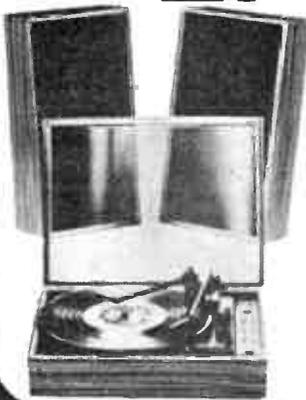

QUALITY SOUND* FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit. - no soldering required. Includes:-
BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.
Two 8" x 5" speakers with cabinets.
Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.
For the technically minded:-
Specifications:
Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for tapping discs. **Overall Dimensions.** Speakers approx. 15½" x 8" x 4". Complete deck and cover in closed position approx. 15½" x 12" x 6". Complete only **£18.95**
Extras if required.
Optional Diamond Stylus **£1.37** - £1.60 p & p.
Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.
Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).
Inputs *5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs.
*Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.
INPUT SENSITIVITIES
1) Crystal Mic or Guitar 9mV. 2) Moving coil Mic or Guitar 8mV. 3), 4), 5) Medium output equipment (Gram. Tuner, Monitor, Organ, etc.) - all 250mV sensitivity.
AC Mains 240V. operation.
Size approx. 12½" ins x 6 ins x 3½" ins
£13.50 + 60p.
postage & packing.



8 TRACK CARTRIDGE PLAYER*

Elegant self selector push button player for use with your own stereo system. Compatible with Viscount III system, the Stereo 21 and the Unisound module.
Technical specification.
Mains input, 240V. Output sensitivity 125mV
Comparable unit sold elsewhere at £24.00 approx.
Yours for only £10.95 + 90p. p & p



BUILD YOUR OWN STEREO AMPLIFIER*

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.
240V. AC only. **£7.64 + 55p. p & p**

PETAPE LINK CONSTRUCTORS



A suitable 3 speed tape deck, less heads. Caters up to 5½ ins. spools. 240V AC mains. Unused but store soiled hence no warranty. **£4.00 + £1.00 p & p**



BUILD YOUR OWN TOURIST PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
- 2.) Integrated circuit output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.

Size Chassis 7 ins. wide, 2 ins. high and 4 1/8 ins. deep approx.

Remember! one of the Top Ten Accessory Awards from Motor magazine PUSH BUTTON* CAR RADIO KIT

NOTE: The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p. free with kit.

Car Radio Kit

£6.60 + 55p. postage & packing.


Speaker including baffle and fixing strips

£1.65 + 23p. postage & packing.

Recommended Car Aerial - fully retractable and locking.

£1.35 post paid.

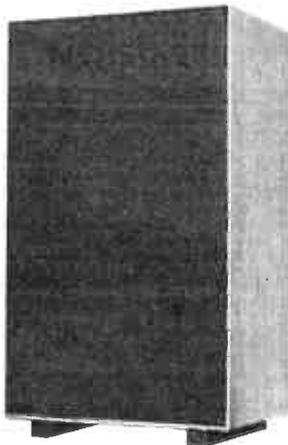THE ULTIMATE COMPLETE SPEAKER SYSTEM EMI LE 315



Recommended retail selling price, £86.00.

Our price £45.00 +
£3.50 postage & packing.

A professional standard five way speaker system with enclosure giving top quality performance.

Enclosure Dimensions approx. (3ft. x 2ft. x 1ft.).

Drive Units

Hand built - 15" diameter bass with 3" voice coil, - two 5" diameter Mid Range units,

- two 3 1/4" HF. units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.

Powder Handling

Continuous rating 35 W rms., Peak power rating 70 W.

Frequency Response 20 Hz 20,000 Hz.

EMI SPEAKERS FANTASTIC REDUCTION



15" 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70 +
£1.50 p & p



950 Kit - Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 1/4" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00.

OUR PRICE £25.00 +
£1.50 p & p
Special Offer.



Just write your order giving your credit card number

DO NOT SEND YOUR CARD

- Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.

- Leaflets available for all items listed. Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.
21 High Street, Acton, London W3 6NG (C)
323 Edgware Road, London W2

Edgware: 9 a.m.-5.30 p.m. Half day Thurs.

Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

POP 40 10" 40 Watt

Impedance 8-15 ohms
Gauss 14,000
Voice Coil Diam. 1 1/2 in
Fitted Tweeter Cone
Range 50-15,000 Hz
Rec. Retail Price



£10.95

Also for those who can afford the very best For Bass Instrument Reproduction

BASS CRESCENDO '12'

12" 100 Watt 3" Pole Diam.

BASS CRESCENDO '15'

15" 100 Watt 3" Pole Diam.



Rec. Retail Price CRESCENDO '12'

£39.95

Rec. Retail Price CRESCENDO '15'

£48.83

Please send S.A.E. for leaflet on 'POP' or 'CRESCENDO' Range Speakers

POP 55 12" 60 Watt

Impedance 8-15 ohms
Gauss 15,000
Voice Coil Diam. 2 in
Range 50-9,000 Hz
AN ALL PURPOSE UNIT OF HIGH sensitivity
Rec. Retail Price



£15.95

There is also a 12" Crescendo Speaker for General Purpose Public Address, and another one for Lead or Rhythm Guitar

PRICES QUOTED INCLUDE VAT

Prices correct at 11.2.74

Brief details of other 'POP' Speakers Rec. Retail

POP '15' 12" 15 Watt **£5.75**

1" Voice Coil

POP '25/2' 12" 30 Watt **£8.75**

2" Voice Coil

POP '50' 12" 50 Watt **£12.75**

2" Voice Coil

POP '60' 15" 60 Watt **£15.75**

2" Voice Coil

POP '100' 18" 100 Watt **£27.50**

3" Voice Coil

Distributors to Wholesale and Retail Traders—LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.
Manufacturers enquiries to—FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS

New Product CASED AUTO TRANSFORMERS

240 Volt Mains to 115 Volt, smart steel-cased units coated in tough resin, fitted with power lead, fuse and 115 Volt American type socket up to 500VA. above 500VA Cable entry.

VA (Watts)	Price	Post
200	£5.20	£0.38
500	£9.50	£0.67
1000	£14.70	£0.82
2000	£27.40	£1.50

20VA version uncoated, no fuse **£2.40** £0.30

MAINS KEYNECTOR

The safe, quick, connector for electrical appliances, 13 Amp rating, fused, will connect a number of appliance-quickly and safely to the mains, ideal for testing, demonstrating, window displays, etc. Warning Light. Interlocked to prevent connecting when live.



POWER UNIT Type PI076



Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500mA D.C. Operates from 240 V. mains, suitable for Radios, Tape Recorders, Record Players, etc. Size 7-5 x 5-0 x 1-4 cm Price **£3.95**. Post 25p.

TRANSFORMERS

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen.		Price		P & P
VA (watts)	Ref.	Cased	Open	£
60	149	—	£ 8.40	0.38
100	150	—	8.80	0.52
200	151	£ 9.20	8.80	0.52
250	152	11.18	8.70	0.65
350	153	13.00	10.40	0.82
500	154	14.83	12.00	1.00
1000	156	28.22	24.97	1.20
2000	158	55.90	50.40	—
3000	159	78.00	65.90	—

12 & 24 Volts Prim. 200-240V.

Amps	Type	No.	Price	P & P
0.3	0.15	242	1.22	0.22
0.5	0.25	111	1.22	0.22
1	0.5	213	1.45	0.22
2	1	71	1.90	0.22
4	2	18	2.50	0.38
6	3	70	3.24	0.42
8	4	108	3.60	0.52
10	5	72	4.25	0.52
12	6	116	5.18	0.52
16	8	17	6.04	0.52
20	10	115	9.30	0.69
30	15	187	15.50	0.97
40	20	252	18.60	1.00
60	30	226	20.50	1.10

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.		Price		P & P
Amps	Type	£	£	£
0.5	112	£1.44	£0.22	0.38
1	79	2.00	0.38	
2	3	2.90	0.38	
3	20	3.60	0.42	
4	21	4.25	0.52	
5	51	5.28	0.52	
6	117	6.30	0.52	
8	88	8.18	0.67	
10	89	10.00	0.67	

50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.		Price		P & P
Amps	Type	£	£	£
0.5	102	£1.92	£0.30	0.38
1	103	2.80	0.38	
2	104	3.90	0.42	
3	105	5.25	0.52	
4	106	6.80	0.52	
8	107	10.00	0.67	
8	118	12.90	0.97	
10	119	16.00	0.97	

60 Volts

Prim. 200-240V. Sec. 24, 30, 40, 45, 60V.		Price		P & P
Amps	Type	£	£	£
0.5	124	£1.92	£0.38	0.38
1	126	2.70	0.38	
2	127	4.25	0.42	
3	125	6.50	0.52	
4	123	8.50	0.67	
5	40	10.50	0.67	
6	120	12.34	0.82	
8	121	14.58	1.00	
8	122	17.65	1.00	
12	189	19.68	1.10	

MINIATURE AND EQUIPMENT

Prim. 240V with screen.		Miliamps		Type	Price	P & P
Volts		Sec. 1	Sec. 2	No.	£	£
Sec. 1	Sec. 2	200	—	238	1.12	0.10
0-0.3	0-6	500	500	234	1.30	0.10
0-6	0-6	1000	1000	212	1.58	0.22
9-0 1/2	—	100	—	13	1.12	0.10
0-9	0-9	330	330	235	1.30	0.22
0-8-0	0-8-9	500	500	207	2.04	0.30
0-5-0	0-8-9	1000	1000	208	2.76	0.40
15-0-15	—	40	—	240	1.12	0.10
0-15	0-15	200	200	236	1.80	0.10
20-0-20	—	30	—	241	1.12	0.10
0-20	0-20	150	150	237	1.30	0.10
0-15-20	0-15-20	500	500	205	2.70	0.38
0-20	0-20	300	300	214	1.60	0.22
0-20	—	3500	—	1116	3.00	0.40
20-12-0-12-20	—	700 (D/C)	—	221	1.41	0.30
0-15-20	0-15-20	1000	1000	206	8.80	0.38
0-15-27	0-15-27	500	500	203	2.80	0.38
0-15-27	0-15-27	1000	1000	204	2.85	0.38

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 Volt 25p	50 Volt 35p	100 Volt 55p	50 Volt 65p
100 Volt 25p	100 Volt 40p	200 Volt 59p	100 Volt 70p
200 Volt 28p	200 Volt 45p	400 Volt 85p	200 Volt 80p
600 Volt 30p	400 Volt 50p	600 Volt 75p	400 Volt 80p



PLEASE ADD 10% FOR V.A.T.

ADD 10p P & P PER ORDER

A.S.P. LTD.

BYRE HOUSE · No. 2 UNIT · SIMMONDS RD · WINCHEAP
CANTERBURY · KENT · CT1 3RW Canterbury (0227) 52436

BLOWER MOTORS double ended type for use on 6 to 28v DC size overhaul 6 x 3 1/2" new £1-90. **HEAD & MIKESET** for 19 set M.C. type low res. new £1-84. **JOY STICK CONTROLLER** gives control in 4 directions with 1p c/o micro swt. £1-35. **HEADPHONE LEAD & MATCH TRANS** high to low imp. with 5ft cord & standard jack plug, new. 65p. **CRYSTAL OVEN** with 12 type Hc6/u crystal holders can be removed. 76p. **TRIMMERS** 20pf air spaced ceramic 10 for 60p. **METERS** 500 Ua scale 0 to 5 1/4" OSD on panel with 2 swts. £1-25, also 1 Ma FSD special scale marks 2 1/2" 85p, also 1 Ma FSD scale 0 to 1 & 0 to 180 2 1/2 Sq. 88p, also 270' scale FSD 1 Ma size 3 1/2 x 3 1/2 also as 100-0-100 Ua in same case. £3. C.R.T. type 78P7A 7" flat face emag. def. & focus. Blue/Yell-phosfor 6-3 heater new with base conn. £1-83. **JUNCTION BOXES** contain 22 screw terminals, etc. £1-55. **MORSE KEYS** with send Rx swt fully enclosed with adjustor' £1-10. R4187 Rx units Crystal cont. HF Rx 2-8 to 18 Mc/s provision for 24 chan-with circ. £9-90. **SUB CHASSIS** with 3 min valves' pot core 1 1/2 x 3/4" cond. luf 1% etc. new. £1-15. **NEONS** wire ended type NE.2 new 10 for 60p. **DIODES** 200 PIV 8 amps 4 for 60p also 800 PIV 750 Ma 15 for £1-10. **YAXLEY SWTS** 4p 1 l w 4b 76p, 4p 4w 2b 40p 3p 6w 3b 40p. **SWT BANK** push button type, 8 buttons latch in type ea 1 c/o & 3 N.O. 85p. **INST SWT** 2p 23w 2b with knob 76p

All above prices inc. post & Vat.

SAE for list or enquiry.

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD. S9 5HL
444278 (0742)

look what's 'in store'
for you... at **IMHOFS**



SONY



HACKER



VAN DER MOLEN



DYNATRON

IMHOFS

Eight magnificent showrooms—each one entirely devoted to one of the world's leading manufacturers—plus our own hi-fi demonstration rooms and superb record departments.

Whatever your requirements, be it IM styli or other accessories; a transistor or short wave radio; cassette player or colour television; a single piece of equipment or a complete audio system, you are sure to find just what you want at Imhofs. And remember, all new equipment bought from us is covered by the Imhofs Sales Charter which includes 12 months' service completely free of charge.

So, if you are in town—pop into Imhofs.

112-116 New Oxford Street
London WC1A 1HJ
Telephone 01-636 7878



ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£			£
EMI 13" x 8" 3, 8 or 15 ohm	Plain	2-05	ELAC 8" 8ohm Dualcone	..	2-10
With Co-Axial Tweeter	..	2-20	FANE 7" x 4" 3 or 8 ohm	..	1-00
Twin Tweeter	..	3-55	8" Dualcone 8 ohm	..	2-40
Type 350 8 ohm, 20 watt	0-00		CELESTION 8" 15 ohm	..	1-55
6 1/2" 8 ohm, 10 watt	2-70		ADAstra 10" 8 or 15 ohm,	..	3-05
8" 8 ohm, 10 watt	3-75		10 watt	..	
12" 8 ohm, 20 watt	5-50		BAKER GROUP 25 12" 8 or	..	6-45
6" x 5" C/Mag. 5 watt	1-20		15 ohm, 25 watt	..	
6" x 5" Dualcone	2-45		P. & P.	..	25
8 ohm, 10 watt	2-45		5" 8 ohm, 5 watt C/Mag.	..	85
GOODMANS 6 1/2" 8 ohm	1-60		2 1/2" 8 ohm or 64 ohm	..	50
Dualcone	..	1-60	P. & P.	..	10

TWEETER & CROSSOVER		£			£
EMI 3 1/2" 3 or 8 ohm C/Mag	..	1-00	Dome Tweeter 8 ohm, 30 watt	..	4-85
Cone Tweeter 8 or 15 ohm,	..	2-40	Crossovers CN23 (3 ohm),	..	1-05
10 watt	..	2-40	CN28 (8 ohm), CN216 (16	..	1-10
Cone Tweeter 8 ohm, 3 watt	1-40		ohm)	..	1-05
Horn Tweeter 8 ohm, 20 watt	5-85		P. & P.	..	10

KIT FORM CABINETS TEAK VENEER		£			£
12 x 12 x 8 with 8" 8" x 5" or	6 1/2" and 3 1/2" cut.out	2-45	18 x 11 x 9 with 13" x 8" cutout	for EMI 350	4-25
17 x 10 x 9 with 8" or 13" x 8"	cut.out	3-50	P. & P. ea.	..	35

MICROPHONES		£			£
CM20 Crystal Hand	..	50	TW200	..	5-75
CM70 Planet stick metal,	..	1-55	CONDENSER MIKE 600 ohm,	..	7-90
switch crystal	..	3-85	Cassette Stick Mike with R.	..	1-35
DM160 Dynamic uni-dir, ball	..	5-50	Control on/off switch	..	15
metal	..		(2-5 & 3-5mm J/Ply)	..	
UD130 50K/600 ohm, uni-dir	..		P. & P.	..	
ball metal	

SOLDERING IRONS		£			£
ANTEX CN240 15 watt	..	1-60	X25 25 watt (low	..	1-00
SK 1 Kit (15 watt iron	..	2-65	leakage)	..	10
2 spare B1b etc.)	..		P. & P.	..	

CARTRIDGES		£			£
ACOS GP91/25C or GP91/35C	..	1-00	19-T1 Stereo crystal	..	1-00
Stereo comp.	..	1-35	BSR SX5M Stereo ceramic	..	2-25
GP93/1 Stereo crys.	..	1-75	SX5M Stereo crystal	..	1-00
GP94/1 Stereo crys.	..	1-35	X5H Mono/atero	..	1-25
GP95/1	..	1-75	X5M Mono/atero	..	1-25
GP96/1	..	1-75	GOLDRING G900 G850 £3-85 £2-95	..	
GP101	..	1-75	5"TVLI for above cartridges	..	1-25
SONOTONE	..	1-80	Sapphire -35 D Diamond	..	1-00
9THAC Stereo cer. diam.	..	1-80	GOLDRING G800 G850	..	1-00
			P. & P.	..	85

BATTERY ELIMINATORS		£			£
240v Input 6, 7-5 or 9 300mA	..	2-20	lighter socket) 6, 7-5 or 9	..	2-20
12v d.c. Input (fits in car	..	1-10	d.c. output at 300mA	..	1-30p
			P. & P.	..	10

TAPES		£			£
Stnd. LP DP	..	7"	Stnd. LP DP	..	7"
45p 55p 65p	..	70p 95p	1-00p 1-30p	..	1-30p
31"	..	95p	P. & P. 1-3, 9p ea. 4 or more, lot 30p	..	

LOW NOISE CASSETTES		£			£
1-5 6-10 11-20	..	35p 33p 43p 52p	Cassette Head Cleaner	..	35p
C80 C90 C120	..		P. & P. 1-5, 3p ea. 6-10, 15p tot.	..	
			11-20, Post Free.	..	

PLASTIC LIBRARY CASES		£			£
For 5" Reels	..	18p	CASSETTE CASES	..	10p
5 1/2" Reels	..	22p	P. & P. 1-3, 5p ea. 4 or more, 20p	..	
7" Reels	..	25p		..	

BIB ACCESSORIES		Ref.	£	BUDGET SPEAKER SYSTEMS	
Tape Editing Kit	..	23	1-30	1. Pr. of 10watt 8ohm 2 speaker system in deluxe teak veneer cabinet 18" x 11" x 8" wired, inc. plugs. £25-00 per pair.	
Recording Tape	..	20	1-15	2. Pr. of 20watt 8ohm 2 speaker system, freq. response 50 c.p.s. to 17,000 c.p.s. Teak veneer cab. 21 1/2" x 12" x 9" with 12ft. cable and plugs. £29-95 per pair.	
Cassette Tape, editing	..	24	1-40		
Cassette Salvage Kit	..	29	40p		
12" Cassette Case	..	34	£1-00		
Stylus Balance	..	32A	1-15		
Spirit Lever	..	46	50p		
Hi-Fi Stereo Test Cassette	..		1-90		
Groove-Kleen Record Cleaner	..		1-90		
P. & P.	..		10		

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED.

Riversdale Electronics
Mail Order Department P.W.4
P.O. Box 470, Manchester M60 4BU.

NEW VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH.

74 Series TTL

INTERNATIONALLY KNOWN BRANDS
1st GRADE DEVICES AT NEW
ROCK BOTTOM PRICES

SN7400	18p	SN7447	£1-10
SN7401	18p	SN7473	41p
SN7402	18p	SN7474	41p
SN7404	18p	SN7475	50p
SN7408	20p	SN7476	44p
SN7410	18p	SN7490	82p
SN7413	31p	SN7492	84p
SN7420	18p	SN7493	82p
SN7430	18p	SN74100	£2-37
SN7441	81p	SN74121	50p
SN7442	81p	SN74141	£1-10
		SN74192	£2-15

PRICE BARRIER SLASHED

LED LITRONIX DL707
READOUTS SERIES

0.3in high characters
14pin Oil



ALSO +1 REF. LED1A

Ref LED1

£1.99 + 20p VAT = £2.19

Veroboard



Copperclad		Plain Extra	
0 1in 0	15in 0	15in P & P	
2 1/2in x 1in	7p	7p	—
2 1/2in x 3 1/2in	24p	18p	12p
2 1/2in x 5in	26p	23p	19p
3 1/2in x 3 1/2in	26p	23p	—
3 1/2in x 5in	30p	30p	22p
17in x 2 1/2in	82p	63p	45p
17in x 3 1/2in	£1-10	86p	60p
17in x 5in	—	90p	10p

Dip Veroboard 115p
Veroboard 28p
Spot: Face Cutter 44p
Pin Insertion tool 55p
Terminal Pins (packs of 50) state size 55p


I.C. SOCKETS



DUAL IN LINE 8 pin 13p, 14 pin 15p, 16 pin 17p, 24 pin 26p, 1 28 pin 39p, 36 pin 41p, 40 pin 44p.
ZIG ZAG 14 pin 18p, 16 pin 21p.

HEAT SINKS

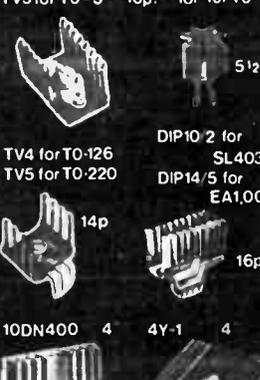TV2 for TO-66 15p, 5F for TO-5 15p
TV3 for TO-3 16p, 18F for TO-18 18p



TV4 for TO-126 5 1/2p
TV5 for TO-220 5 1/2p

DIP10/2 for SL403D
DIP14/5 for EA1,000

10DN400 4 46p, 4Y-1 4 35p

BRIDGE RECTIFIERS



P I V	1 amp	R M S	2 amp
100V	20p	50V	35p
200V	22p	100V	40p
600V	25p	200V	45p
1000V	38p	400V	50p

RECTIFIERS

P I V	1 amp	3 amp
50	1N4001 6p	1N5400 15p
100	1N4002 7p	1N5401 16p
200	1N4003 9p	1N5402 17p
400	1N4004 9p	1N5404 22p
600	1N4005 11p	1N5406 26p
800	1N4006 13p	1N5407 30p
1000	1N4007 16p	1N5408 33p
BY100	16p	BY133 23p
BY103	22p	BY164 55p
BY105	16p	BY176 £1-65
BY126	16p	BY182 £1-65
BY129	16p	BY250 25p

OR FILAMENT INDICATOR

MINITRON 3015F & G



16pin Oil

at **BREAKTHROUGH**

Cheapest Opto yet

GaAsp LED's



LED 2 0.125 26p
LED 3 0.175 17p
LED 4 0.125 69p
LED 5 0.175 75p

Remember **Vat Inclusive Prices**

DIGITAL CLOCK

on a chip



just imagine one MOS LSI I.C. eliminating 15 MSI I.C.s and numerous other components Either

12 or 24 hour, 4 or 6 digit
50 or 60Hz operation
leading zero suppression
single voltage supply
similar to DIGITRONIC in P.W. March 1973.

Only **£7 99**

With 4 LED's £16-59
With 6 LED's £20-75

CHROMASONIC electronics

RESISTORS

Rating	Type	Tolerance	Range	Price Each	
1/2 watt	Carbon Film	± 5%	E12 Series	5Ω to 330KΩ	1p
1 watt	Metal Oxide Film	± 2%	E12 Series	10Ω to 1MΩ	4p
1/2 watt	Cormet Thick Film	± 2%	E12 Series	56Ω to 150KΩ	8p
1/2 watt	Carbon Film	± 5%	E24 Series	10Ω to 10MΩ	1p
1/2 watt	Carbon Composition	± 0.5Ω	(2 2Ω) 2 7Ω 3 3Ω 3 9Ω 4 7Ω	4p	
1 watt	Carbon Composition	± 10%	(5 6Ω) 6 8Ω 8 2Ω	5p	
1 watt	Carbon Film	± 5%	E12 Series	10Ω to 10MΩ	3p
2 watt	Carbon Film	± 5%	E12 Series	10Ω to 10MΩ	6p
2 1/2 watt	Wire Wound	± 10%	E12 Series	0.22Ω to 0.47Ω	10p
2 1/2 watt	Wire Wound	± 5%	E12 Series	1Ω to 270Ω	10p
5 watt	Wire Wound	± 5%	~E12 Series	0.5Ω to 8.2KΩ	10p
10 watt	Wire Wound	± 5%	10KΩ 15KΩ 20KΩ 25KΩ	11p	
10 watt	Wire Wound	± 5%	10KΩ 15KΩ 20KΩ 25KΩ	17p	
15 watt	Wire Wound	± 5%	10KΩ to 16.8KΩ	13p	

DISCOUNTS 10% on any 100 or more mixed value or wattage. 25% on any 100 or more same value and same wattage

TRANSISTORS and DIODES

AC10*	18p	ASY25	33p	BC328	24p	BF180	33p	BSY95A	14p	T1P41A	8p
AC125	13p	BC17	11p	BCV70	17p	BF181	33p	BU105	£1-75	T1P42A	8p
AC128	13p	BC108	11p	BCV72	17p	BF184	28p	BU105.02	£1-92	T1S43	32p
AC129	13p	BC109	11p	BC210	28p	BF185	28p	D13V	35p	T1S43	36p
AC175	15p	BC114	15p	BC211	28p	BF194	15p	MJ4000	£1-49	T1S91	31p
AC187	22p	BC147	22p	BD115	74p	BF195	17p	MJ4010	£1-49	2N3055	18p
AC187K	22p	BC147	20p	BD124	82p	BF196	37p	MJE340	52p	2N706	13p
AC188	22p	BC148	10p	BD131	55p	BF197	18p	MJE2955	£1-82	2N708	18p
AC188K	22p	BC149	10p	BD132	46p	BF200	32p	MJE3055	92p	2N914	24p
ACV19	25p	BC157	15p	BD131.2	£1-18	BF200	27p	MPF102	27p	2N1302	22p
ACV20	25p	BC158	12p	BD133	72p	BF214.9	27p	MPF103	41p	2N1303	25p
AD140	48p	BC159	14p	BD135	42p	BF262	25p	MPF104	45p	2N1305	24p
AD149	48p	BC168B	11p	BD136	44p	BF263	25p	MPF105	45p	2N3705	24p
AD161	29p	BC169	12p	BD137	50p	BF272	£1-21	MPF106	49p	2N3706	24p
AD162	29p	BC170	20p	BD138	52p	BF272	£1-21	MPF106	49p	2N3707	24p
AF124 2PR	17p	BC172	17p	BD139	81p	BF274	£1-21	OC28	50p	2N3707	24p
AF114	17p	BC174B	30p	BD140	86p	BF274	£1-21	OC28	50p	2N3707	24p
AF115	17p	BC177	22p	BD201	£1-55	BF279	87p	OC44	14p	2N4163	22p
AF116	17p	BC178	22p	BD202	£1-57	BF287	87p	OC45	14p	2N4171	22p
AF117	17p	BC179	24p	BD203	£1-55	BF291	87p	OC71	14p	2N4189	52p
AF118	92p	BC182L	11p	BD204	£1-37	BF293	37p	OC72	14p	2N4190	52p
AF124	27p	BC183L	12p	BF109	75p	BF298	86p	OC75	15p	2N4219	51p
AF125	27p	BC184L	12p	BF115	75p	BF299	50p	OC81	14p	2N4246	55p
AF126	27p	BC187	27p	BF160	25p	BFY51	22p	OC83	25p	2N4295	46p
AF127	27p	BC212L	12p	BF167	24p	BFY52	22p	OC140	22p	2N4294	46p
AF130	25p	BC213L	13p	BF173	24p	BR100	43p	OC170	28p	2N4295	18p
AF172	25p	BC214A	11p	BF177	28p	BR139	44p	OC171	28p	2N4295	18p
AF176	41p	BC258	15p	BF178	28p	BK320	11p	TIC44	46p	2N4308	25p
AF235	41p	BC327	24p	BF179	33p	BK321	22p	TIC22D	£1-97	2N4353	18p

CAPACITORS

MULLARD C333, 629 and 630 series
—Ceramic Plate E12 series from 1.8pF to 0.002µF. 51p.

CERAMIC DISC—LOW VOLTAGE—
0.01µF. 0.022µF. 0.047µF. 51p.
0.1µF. 0.22µF. 61p.

POLYSTYRENE (160V)—From 10pF to 0.01µF in multiples of 10pF 15pF 22pF 33pF 47pF and 68pF 41p.

MYLAR PLATE (100V)—1000 Pf. 2000Pf. 5000Pf. 21p. 0.01µF. 0.02µF. 0.04µF. 0.05µF. 31p. 0.068µF. 0.1µF. 5p. 0.2µF. 61p.

MULLARD C280 (250V POLYESTER)
—0.01µF. 0.015µF. 0.022µF. 0.033µF. 0.047µF. 31p. 0.068µF. 4p. 0.1µF. 0.15µF. 41p. 0.22µF. 51p. 0.33µF. 7p. 0.47µF. 9p. 0.68µF. 12p. 1.0µF. 14p. 1.5µF. 17p. 2.2µF. 26p.

NEW

stabilised

POWER PACK CONVERTER

Switched 3, 6, 7, or 9 volts
Up to 400mA Output



Max Output Load with 3mm plug plus FREE multi Pin and socket adaptor

Main Lead (over 4ft)

Power Output Transistor

Transistor and Zener Stabiliser Circuit

On/Off Switch

Rubber Feet

Voltage Selector

Polarity Reversal Switch

Metal Case

Our Price £3.99 + P. & . 16p.
Unstabilised Version (if above £2.99
Other Eliminators (unstabilised)*

6 volts at up to 50mA	£1-65
9 volts at up to 50mA	£1-65
9 volts (miniature) up to 50mA	£2-09
6 - 6 volts at up to 50mA	£2-75
9 - 9 volts at up to 50mA	£2-75
7 1/2 volts for Cassette Players (small)	£2-20
3, 4, 6, 7, 9, 12 volts up to 1A	£3-75
Fully Stabilised* Car Battery Converter, giving switched outputs of 6, 7, or 9 volts	£5-49

P & P. on all models 16p


ZENERS

All 5% tolerance

BZY88. 400mW. 3.3V to 33V	11p
1ZS. 1W. 3.3V to 100V	18p
BZX70. 2.5W. 7.5V to 75V	27p

VAT INVOICES ON REQUEST

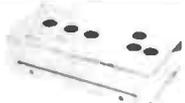UNLESS SHOWN OTHERWISE P&P ON U.K. ORDERS IS 8p. OVERSEAS ORDERS AT COST



Mullard LP1186
Varactor diode tuned F.M. tuning heart. £4-15, as described in P.E. May 1973 LP1185 matching I.F. strip. £4-85.



TEC TEXAN
20 - 20 Watt Integrated Stereo Amplifier Kit Superb state-of-the-art design by engineers of Texas Instruments £31-35 - P & P 49p



SGS EA1000
3 watt amplifier module Price including handbook and FREE heatsink and Our price £2-49. Quantity discounts



A10055
F.M. tuner chassis fully transistorised 9 Volt positive earth operation Our Price £6-35.



A1018
F.M. tuner, similar to A10055 but in oiled walnut cabinet, etc. Our Price £9-38.



A1005MS
Multiplex Stereo Decoder, fully built and aligned, to match A10055. Our Price £5-95.

AUDIO I.C.'S

Audio I.C. Leaflet No. 12 FREE (only with I.C. s—10p separately)

Pre-Amplifiers
Dual MC1303L £1-89
Low Noise Dual MC1339P £1-29




Amplifiers

250mw. MFC4000A 49p
1 watt. TAA300 £1-79
2 watt. LM380 £1-40
3 watt. SL414 £1-76
5 watt. TBA800 £1-59
7 watt. TBA805 £1-70
15 watt. BHA0002 £3-95
35 watt driver. NE540L £1-32



NEW SL414 pin for pin = SL403D 3 watt £1-76

3 1/2 decade DVM

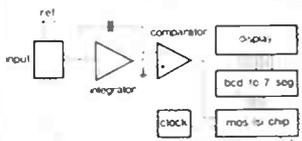

- Maximum Display - or 1 999V
- Minimum Display - or 1mV
- Can be scaled up to read 1 999V
- Automatic Polarity Detection
- Dual Ramp Integration
- Automatic Overrange Indication
- Up to 50 readings per second
- Chopper Output provided

Supplied with complete data All this on a single 16 pin DIL packed MOS LSI Integrated Circuit

A State-of-the-Art Digital Voltmeter I.C. for only £7-79

Coil-less Phase-Locked Loop I.C. Stereo Decoder

Motorola MC1312, supplied complete with our leaflet No. 11 Our Price £3.05

MC1312 decodes CBS SO. Free leaflet No. 11 gives full circuit and details. Our Price £6-49

QUADRISONICS

inc. all parts for decoder, inc. Veroboard, V.A.T., P & P. (Leaflet alone 10p.)

Linears



Part No.	Price	Part No.	Price
CA3046	85p	MVR5V(L005)	£1-85
CA3075	£1-85	MVR12V(L005)	£1-85
CA3082	£1-85	MVR15V(L037)	£1-85
LM101H	£1-85	NE555	85p
LM201H	£1-15	NE560B	£4-92
LM301	£1-85	NE581B	£4-92
LM307H	£1-85	NE582B	£4-92
LM309N	£1-45	NE585	£2-80
LM309K	£2-80	NE586	£2-75
LM3900	77p	NE587	£2-80
MC1330	84p	SO3302N	£3-08
MC1350	83p	SL440	£2-89
MC1351	£1-10	TA5323	99p
MC1352	£1-10	TAA293	99p
MC1357	£1-50	TAA310	£1-37
MC1358	£1-85	TAA320	99p
MC1458G	£1-75	TAA350	£2-54
MC1458CP	£2-42	TAA370	£5-15
MC1459	£1-85	TAA380	99p
MC1496A	£1-49	TAA370	£1-85
MC3401	77p	TAA720	£4-49
MFC4019A	81p	TAD100	£1-55
MFC4060	78p	TAD110	£1-85
MFC603CA	83p	TBA511	£2-80
NE540L	13p	TA911	£3-89

the component people

Dept 1, 56, Fortis Green Road, London. N10 3HN. telephone: 883 3705

INDUCTORS

MULLARD block filter LP1175 as used with TAD100 now only £1-49

R.F. CHOKES, 0.1µH to 19mH. For full details ask for List No. 5. P & P 5p.

DENCO COILS



Transistor Range: Series 1T to 5T inclusive Blue, Yellow, Red and White all 44p each. I.F. Transformers: IFT13, 14, 16 and 17, 55p each. IFT 15, 76p; IFT18, 73p.

Dual Purpose Range: Series 1 to 7 inc. Blue, Yellow, Red and White, 44p each.

1 to 5 Green. List No. 5 gives full details. Ferrite Aerials: Medium and Long—state 300pF or 500pF tuning, 87p each.

Tuning Gangs



Type C804 5pF 61p 50pF 66p 100pF 61p 60pF 79p 150pF 61p 75pF 79p 20pF 66p 100pF 75p 25pF 61p
Type 0 365pF 80p 365 - 365pF 96p Type 00 208 - 176pF with screen and trimmers 99p
P & P all types 10p

NEW FERRANTI RANGE

ZN414

The Radio Inc. in a TO18 can. Supplied with our data leaflet No. 10. Giving circuit and component information. (Leaflet alone 10p.)

Part No.	Price	Part No.	Price
BF559	15p	ZTX302	17p
BF560	20p	ZTX303	14p
BF561	20p	ZTX304	21p
BF596	15p	ZTX310	9p
BF597	23p	ZTX311	10p
BF598	20p	ZTX312	10p
ZTX107	10p	ZTX313	11p
ZTX108	10p	ZTX314	15p
ZTX109	15p	ZTX320	31p
ZTX212	14p	ZTX330	21p
ZTX213	14p	ZTX331	16p
ZTX214	15p	ZTX341	22p
ZTX300	12p	ZTX550	17p
ZTX301	13p	ZTX551	17p
		ZTX502	17p
		ZTX503	14p
		ZTX504	43p
		ZTX510	17p
		ZTX511	13p
		ZTX512	16p
		ZTX517	17p
		ZTX516	23p
		ZTX578	37p
		ZTX577	37p
		ZTX576	37p
		ZTX575	37p

Our Price £1.32

KSO30A Zener Series BZY88 Series 11p each.

ELECTROLYTICS

µF	4V	6.3V	10V	16V	25V	40V	63V	100V	160V	450V
1							61p	61p	61p	15p
1.5							61p	61p	61p	
2							61p	61p	61p	
2.2							61p	61p	61p	
3							61p	61p	61p	
3.3							61p	61p	61p	
4							61p	61p	61p	
6							61p	61p	61p	
6.8							61p	61p	61p	
8							61p	61p	61p	
10							61p	61p	61p	
15							61p	61p	61p	
22							61p	61p	11p	24p (16µF)
33		61p	61p	61p	61p	61p	61p	61p	33p (32µF)	
47		61p	61p	61p	61p	61p	61p	61p	25p (30µF)	
68		61p	61p	61p	61p	61p	61p	61p	25p	
100		61p	61p	61p	61p	61p	61p	61p	25p	
150		61p	61p	61p	61p	61p	61p	61p	25p	
220		61p	61p	61p	61p	61p	61p	61p	31p	
330		61p	61p	61p	61p	61p	61p	61p	47p	
470		61p	61p	61p	61p	61p	61p	61p	47p	
680		8p	10p	11p	14p	20p	25p	47p	59p	
1000		13p	14p	14p	19p	22p	25p	44p	79p	
1500			18p	19p	25p	39p	44p	79p	149p	
2200			18p	24p	24p	39p	44p	79p	149p	
3300			26p	26p	26p	39p	44p	79p	149p	
4700			25p			44p	64p	79p	149p	252p
6800						75p				

Potentiometers



5kΩ 250kΩ 10kΩ 500kΩ 25kΩ 1MΩ 50kΩ 2MΩ 100kΩ
Log or lin less switch (and 1kΩ lin) 13p
Log or lin with switch 26p
Dual less switch 44p
Dual with switch 10kΩ 100kΩ and 1MΩ log only 57p
10kΩ log - 10kΩ antilog less switch 44p



10kΩ Single 25kΩ 40p 50kΩ Dual 100kΩ 60p
New Silver and Black Knob 16p

Presets

Vertical or Horizontal 0.1 watt 51p 0.25 watt 7p
100Ω 1kΩ 10kΩ 100kΩ 1MΩ 250Ω 2.5kΩ 25kΩ 250kΩ 2.5MΩ 500Ω 5kΩ 50kΩ 500kΩ 5MΩ
Cermet Type to 1MΩ only 41p.

VDR's & Thermistors

Part No.	Price	Part No.	Price
A15B	46p	GL23	£1-21
CZ1	181p	R53	£1-49
CZ4	18p	R54	£1-61
CZ13A	18p	VA1005	16p
CZ19	18p	VA1026	16p
E298CD A258	13p	VA1033	16p
E298ED A256	13p	VA1034	16p
E298ED A260	13p	VA1039	16p
E298E D A262	13p	VA1040	16p
E298ED A265	13p	VA1053	16p
E298ED P268	13p	VA1055S	16p
E298Z D5	13p	VA1056S	16p
E298Z D5	13p	VA1056S	16p
E298Z D5	13p	VA1066S	17p
E299DD P336	14p	VA1067S	16p
E299DD P338	14p	VA1077	19p
E299DD P342	14p	VA1098	21p
E299DD P348	14p	VA1104	31p
GL16	£1-21	VA1107	29p

Other types obtainable upon application

CASED AMPLIFIERS

Polished wooden cabinet 14 x 13 x 9in containing a sensitive (20µV) 4 valve amplifier with tone and volume controls. 3W output to 7 x 4in 30 speaker. Also included is a non-standard tape deck. Supplied in good working condition complete with circuit. Mains operated. £3 (£1 up to 200 miles, £1.25 over). Suitable cassette £1 (30p). Spare Head 30p. TAPE (ex-computer) 68p (20p). Amplifier Chassis, complete and tested (2 x ECC83, ELL84, EZ80) + Speaker £2 (45p). Motors. 35p (30p).

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, pots, switches, + PC Boards with transistors and diodes, also crystals and loads of odds and ends. Amazing value at £1.65 (40p).

COMPUTER PANELS

31b assorted panels £1 (30p); 71b £2 (40p); 12 high quality boards with IC's, power transistors, trim pots etc. £2 (30p); 100 ditto £12 (£1); Pack of boards containing at least 500 components with at least 50 transistors, 60p (20p); Panel with 20 2N 29 26 type transistors + other parts 20p (10p); pack with 25 flat pack I.C.'s (No info) 30p (10p).

AMPLIFIER UNIT

In fully screened case 5 1/2 x 5 x 3 1/2. 2 GET 116 on heat sink, 2 zeners, 3 pot cores, 4 transformers, 1" R's and C's, 40 way tag-board and fuse with circuit 65p (30p); 4 for £2 (65p). Qty. discount.

ADD 10% TO TOTAL FOR VAT

Carr. in brackets; small parts 3p
S.A.E. LISTS

GREENWELD (PW11)

24 Goodhart Way, West Wickham, Kent. SHOPS AT: 21 Deptford Broadway SE8. (Tel. 01-692 2009) and 38 Lower Addiscombe Road, Croydon.

NEW COMPONENTS

400V SA SCR. 60p; 200V, 40p; OC16, 20p; OC45 8p; OC71, 9p; OC171, 15p; BFY18, 12p; BCY72, 8p; 741C, 32p Trendata keyboard. Cometer: data input terminal with display. Converts to IFO code. Erase, new and boxed less than 2 years old and cost £650. No data available. So only £80 (£2). Send 10p for photo. 80 + 80 + 20µF, 350V, 10p; 10, 75p (30p); 8µF, 2,500V, £2 (50p); 4µF, 2000, £1 (40p); 10µF 236V 40p 15p; 1Ω resistor 2W 4p; 10Ω 2W 10; 25p; 100K 1W 30p/100 (10p); 4 pole, 8 way Yaxley Switch 30p (8p); Crystal + Cats whisker 15p; 20K 10 turn Colvorn wire wound pot 75p (10p); miniature 50v ceramic plate 22pF-1000pF 2p; Heavy duty heat sink 6 x 5 x 3 inches with 2 power transistors 80p (30p); 230v fans 2800r.p.m. 6 1/2" dia. blades, complete with grill and mounting plate £2 50 (40p); Scopes in stock for callers, ring for details.

COMPONENT PACKS

500 assorted resistors £1 (20p); 2,500 £4 (40p); 10,000 £12 (£1); 100,000 £80 + carr. 150 poly, mica, ceramic, caps, 60p (10p); 25 ICX crystals £1 (30p).

FERRIC CHLORIDE

Anyhdrous to mil-spec in 1lb sealed packs. 1lb 50p (20p); 3lbs £1 20 (30p); 10lbs £3 50 (60p).

VERSATILE POWER UNIT

Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1-7v-10 5v output with 2 extra capacitors. Ideal for Nickel-cad battery chargers. 5v TTL supply, cassette or radio, etc. Brand new. British made, complete with information. ONLY 75p (20p).

TRAMPUS

MONEY BACK IF NOT SATISFIED

All brand new, full spec. Top grade.
FREE fabulous NEW catalogue. Send S.A.E.



Red + data, 1/8" pin source LED's 17p; TIL 209 and clip 22p
BIG 1/2" panel clip and RED LED 28p. Green and clip 59p.
INFRA RED LED £1. IC photo amp 44p and amp/switch 85p.

DIGITAL DISPLAY. LEO 1/3" 0-9 DP. DIL. £1.69. Mintron type 0-9 DP DIL £1.19. SOCKETS 13p. Calculator batt/mains 1 from £19.

IC DIGITAL CLOCK CHIPS. Texas etc. with 4 displays £12 6 displays

and chip £14. Mostok data and alarm chips with 5 displays £19. pcb £1.49.
KIT: All parts and case. National chip, 4 digit £20. 6 x £23.
GAS sensor TGS 398 £2. KIT £4.69. Fully built £8.

With data INTEGRATED CIRCUITS 741: 8 pin 29p. to 99 and 14 pin 27p.
748 33p. 709 21p. 710 35p. 723 55p. 555 timer 79p. ZN414 rx. £1.10. 703 rf if 28p.
mc 1310 and led £2.76, mc 1339 £1.20. TAD 100 and if £2

1 AMP + REGULATOR 7805, 5 (& 7-20) V. also 12 & 15V £1.49.

AUDIO AMPS: mc 4000 50p; 1 and 2W £1.19; 3V/ £1.29.

74N TTL low prices



Gates 7400, etc. 16p. 7413 32p. 7447 £1.25. 7470/72 32p. 7474/76 39p. 7490 63p.

7492 69p. 74121 49p and all others in cat.

NEW 16 pin counter/driver 90/47 £2.25. DALO p.c.b. PEN 69p,

DIL SOCKETS: Professional/gold P. Pins hi or lo Profile 8, 14, 16 Pin 13p.

2N3055 33p four £1. BC107, BC108, BC109 all 7p each.

IN914 3p. ZENERS BZY88 8p, 1A RECTS 50V 3p, 400V 5p. BRIDGE 20p,

FETS: 2N3819 19p, 2N3823 20p, 4416E 25p, BC182/3/4 10p, BC212/3/4 11p,

BCY70 13p, BD131/2 35p ea., BFY51/2/3 15p, TIS43 25p, 2N2926 Oy 7p, 2N3053 15p,

2N3702/3/4/5/6/7/8/9/10/11 all 9p ea., 2N3904/6 14p. HEATSINKS 5I/T05, 18I/T018

5p. T03: 4YL 29p. TV3 14p

CAPACITORS: 25V 10, 50, 100 of 5p. DISCS 4p. PRESETS 5p. CARBON-

PTS 11p. Switch + 11p. Dual 55p. ULTRASONIC TRANSDUCERS £2 ea.

FLUORESCENT LIGHTS, 8W 13" 12 VOLT £2.59.

Trampus electronics

ADD 10% VAT TO PRICE.

P. & P. 10p C.WO.

P.O. BOX 29, BRACKNELL, BERKS.

A SELECTION of the more unusual items from the famous HOME RADIO (Components) CATALOGUE...

LIGHT SENSITIVE DEVICES **SILICON PHOTO-VOLTAIC CELL**

Maker: FERRANTI

These cells were developed for the space programme. They may be used to power transistorised radios, small electric motors or operate light meters. For example, they will generate enough current to operate our SD104, SD105 and SD106 motors when exposed to 100 watt lamp. Although we give an output current and voltage these are nominal and taken in strong sunlight. The voltage will vary with the amount of current being consumed.

Cat No	Maker's No.	Maker	Volts	mA	Size
SD103	FRB150	Ferranti	1.1v	100	1 x 1 x .012 in (19 x 19 x 3 mm)

PRICE (Including VAT and Postage) £1.89

SMALL ELECTRIC MOTORS

Cat. No.	Maker's No.	Size	1 volt
SD106	M5	33 x 28 mm.	6 V

Note: The SD106 will run off 2 of our SD103 Photo Voltaic silicon cells connected in series if illuminated by sunshine or 100 watt lamp at 1 ft

PRICE (Including VAT and Postage) £2.84

SILICON GLASS TUBING

This tubing will withstand temperatures up to 250 C

Cat. No	Maker's No.	Length	Outside Dia
8Z274	LTG54	6 in (152 mm)	2 in (51 mm)

PRICE (Including VAT and Postage) £2.54

When purchasing any of the above items, please state "As per your advertisement"

It goes without saying that our catalogue lists run-of-the-mill goods like Resistors, Capacitors, Pots and Coils, so we bring to your notice here one or two of the more exotic items. Take the SD103 cell. Apart from its rarity, it's very useful. Recently we built a 3-transistor radio with loudspeakers, and found that three of these cells would operate it. Regarding the mini motor and silicon glass tubing, your ingenuity will suggest ways in which you can make good use of them. These are but 3 of *thousands* of exciting components in our catalogue. By now you are reaching for your pen and cheque book, but don't just buy the items shown here; get the catalogue and feast your eyes on all 240 pages. At 77 pence it's almost a gift—especially as by using the vouchers as directed you can reclaim 50p. Post the Coupon now with your cheque or P.O. for 77p.

Please write your Name and Address in block capitals

Name _____

Address _____

Home Radio (Components) Ltd. Regd No 912966, London
Dept. PW, 234-240 London Road, Mitcham, CR4 3HD.

NO EXTRAS
ALL PRICES INC. VAT
FREE! P. & P.

AMPLIFIERS

Kelton KSA 700 7-7 watt	25.00
MK II KSA 1500 15-15 watt	32.50
Tripletone MKII H-F1777-7 watt	27.50
MK II H-F1818 18-18 watt	35.00
Kelton MKII SAQ3078 8 watt	27.00
EMI 1515 15-15 watt	37.00
RA210	32.00
Rotel RA210	44.00
Rotel Tuner/Ampl. RX150A	51.00
SANSUI models in stock.	

RECORD DECKS

Garrard 2025TU/9TAH/6	11.00
SP25 Mk III	11.00
BSR MP60/SX5H	11.00
Connoisseur H14 Kit	11.00
H12 Chassis	29.50
SAV2 Pick-up Arm	12.25
SCU1 Cartridge	4.95

RECORD DECK PACKAGES

SP25 Mk.II, in Plinth & Cover	218.95
wired	19.50
Garrard SP25 Mk.III/10800 C. & P.	30.00
AP76/1800 C. & P.	30.00
Plinth & Cover for Garrard	
SP25/2025TU	3.95

SPEAKER BARGAINS

EMI 15" x 8" 3, 8 or 15 ohm	
Plain	2.35
With Co-Axial Tweeter	2.50
Twin Tweeter	3.95
Type 350 8 ohm, 20 watt	8.50
6 1/2" 8 ohm, 10 watt	2.65
8" 8 ohm, 10 watt	3.90
12" 8 ohm, 20 watt	5.75
12" 8 ohm, 20 watt	1.40
12" 8 ohm, 20 watt	1.40

8" x 5" Dualcone 8 ohm	2.70
10 watt	
FANE 7" x 4" 3 or 8 ohm	1.15
8" Dualcone 8 ohm	2.50
15 ohm	1.75
ADASTRA 10" 8 or 15 ohm,	
10 watt	3.25
BAKER GROUP 25	
12" 8 or 15 ohm, 25 watt	6.50
5" 8 ohm, 5 watt 4/3Mag.	.95
2 1/2" 8 ohm or 64 ohm	.80
CELESTION 8" 15 ohm	
WHARFEDALE SPEAKERS ALSO	
AVAILABLE.	

KIT FORM CABINETS-TEAK VENEER

12" x 12" x 6 with 8", 8" x 5",	
or 6 1/2" and 3 1/2" cutout	2.75
17" x 10" x 9 with 8" or 13" x 8"	
cutout	3.95
18" x 11" x 9 with 13" x 8" cut	
out for EMI 350	4.80

TWEETER & CROSSOVER

EMI 3 1/2" 3 or 8 ohm 4/3Mag.	1.10
Cone Tweeter 8 or 15 ohm, 10 watt	2.50
Cone Tweeter 8 ohm, 3 watt	1.50
Horn Tweeter 8 ohm, 20 watt	5.95
Home Tweeter 8 ohm, 30 watt	4.95
Crossovers CN23 (3 ohm), CN28	
(4 ohm), CN216 (16 ohm)	1.15

CARTRIDGES

ACORN 4/P1/25C or GP91/25C	
Stereo comp.	1.05
GP92/1 Stereo crys.	1.35
GP94/1 Stereo crys.	1.75
GP95/1	1.35
GP96/1	1.75
GP101	.75

SONOTONE

9TAHC Stereo ceramic, diam.	1.80
9TAHC/S 8mm ft, stereo cer.	
diam.	1.80
19-T1 Stereo crystal	.85
BSR 805M Stereo ceramic	2.25

SX5H Stereo crystal	1.65
SX5M Stereo crystal	1.65
X5H Mono/stereo	1.30
X5M Mono/stereo	1.30
GOLDRING G800	3.85
G850	2.95

STYLII For Above Cartridges

Stylus	.30
D. Diamond	1.25
GOLDRING G800 G850	1.95

MICROPHONES

CM20 Crystal Hand	.60
CM70 Magnet stick metal, switch	
crystal	1.70
DM100 Dynamic uni-dir. ball	
metal	4.00
UD10 50K/600 ohm, uni-dir.	
ball metal	4.65
TW206	6.90
CONDENSER MIKE 600 ohm,	
uni-dir.	7.90

Cassette STICK MIKE with R

Control on/off switch (2.5 &	
3.5 mm J/P/C)	1.45
MIKE MIXERS Mono	4.10
Mono/stereo de luxe	5.50

CASSETTES

Type	Low noise	Pin-nucle	Philips	Memorex	Amperex
C45	35p	40p	50p	55p	45p
C90	45p	55p	69p	75p	55p
C120	55p	75p	105p	110p	75p
Cassette Head Cleaner					.45
BIB Stereo Test Cassette					1.85
AMPEX Head Cleaner De-					
magnetiser					1.65
PLASTIC LIBRARY CASES for 5"					
Reels 20p, 5 1/2" Reels 25p, 7"					30p
CASSETTE CASES					12p
TAPES 8mm, L.P., D.P.					
5" 55p					80p
5 1/2" 65p					75p
7" 80p					£1.05
					£1.40



Credit Terms for Callers

BUDGET SPEAKER SYSTEMS

- Pr. of 10watt 8ohm 2 speaker system in deluxe teak veneer cabinet 18" x 11" x 9" wired, inc. plugs. £25.00 per pair.
- Pr. of 20watt 8ohm 2 speaker system freq. response 50c.p.s. to 17,000p.s. Teak veneer cab. 21 1/2" x 12" x 9" with 120W cable and plugs. £29.95 per pair.

AKAI TAPE DECK

4000DS Tape	75.50
GXC40D Cassette	64.85

HEADPHONES

AMSTRAD H185A	4.95
ROTEL 430	4.90
630	6.20
700	6.20
AKAI ASE 115	8.95
ASE 20	6.75
ASE 22	9.25
KOSS K711 (Black or Red)	9.95
K8	11.95
KMAC (with Vol. control)	13.25
K0727B	15.75
K0747	19.50
HVI	19.50
PRO4AA	26.95
PHOSLAC	28.75
250P	42.75
LEERSON ELECTRONATIC Mono/stereo super de luxe 8-16Ω	19.50
Headphone Adaptor	2.75
Curly Ex, Lead 20ft.	2.50
	1-10

IN-CAR ENTERTAINMENT SECTION

Car Cassette Stereo Player and Two Speakers	20.95
Car 8-track Stereo Player and Two Speakers	16.50
Pair of Car Stereo Speakers	3.85
Pair of Car Stereo Speakers (Door Mounting)	3.95

NEWMART ELECTRONICS

ALL MERCHANDISE FULLY GUARANTEED

MAIL ORDER DEPT. (PW/4)

BELMONT STREET MONTON, ECCLES MANCHESTER

Tel. 061-789 5268

CALLERS WELCOME AT OUR BRANCHES

Manchester	Liverpool
30-32 Shudehill	15 Whitechapel
061-832 7710	051-236 0738
Leeds	
4 New Market St.	
0532 42708	

EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data. 10 boards 50p (12p) 25 boards for £1 (30p)

Panels with 4 Power transistors sim OC28 50p (10p) Dural extruded heatsinks outline 10D black anodised. Drilled for 4 x TO3 transistors. 5 x 4 x 1 1/2" 40p (14p) Similar to above but 5 x 8 x 1 1/2" drilled for 8 x TO3 70p (26p)

COMPUTER GRADE ELECTROLYTICS

12,000µ 100v, 5 x 2 1/2 dia	75p (25p)
30,000µ 25v	65p (20p)

ELECTROLYTICS

4,000µ 70v, 3,600µ 40v, 10,000µ 50v,	
4 1/2 x 2 in dia	55p (14p)
10,000µ 35v, 5,000µ 35v, 4 1/2 x 2 in	
	40p (12p)

2,000µ 30v, 400µ 40v, wire ends	15p (6p)
100 piv 20A, Si diodes	4 for £1 (10p)
100 piv 3A, Si diodes	4 for 50p (7p)
250 mixed resistors	60p (9 1/2p)
250 mixed capacitors	60p (9 1/2p)
200 Si planar diodes	50p (7p)
Min. glass neons	12 for 50p (7p)
Reed relays mixed	10 for 50p (7p)
Micro switches	8 for 50p (9p)
Assorted relays	8 for £1 (18p)
Papst extractor/blower fans	
100 c.f.m. 4 1/2 x 4 1/2 x 2in	£3.50 (28p)
QH bulbs 12v 55w	50p (6p)

Postage and package shown in brackets. Please add 10% VAT to prices.
KEYTRONICS
(Mail Order only)
44 EARLS COURT ROAD LONDON W8. 01-478 8499

BETTER GET 'SET'

FAMOUS NO. 19 SET TRANS RECEIVER

TR50/51 2-8 MHZ in 2 bands. 11 valve. 80T PA Power reqs 12VLT 275-VHT REC 500VTM. Rebuilt £12-50, Carr. £1. Complete station 12 VOC PSU, Mic. Cables £23-50, Carr. £2-50.

TR55 VHF 60-90 LHZS XTALSINC 3

3 channel 12 valve super Het. 12 VDC Sync Internal Supply. size 14" x 12" x 7" as new £16-50 Carr £1-25.

TE76/CT52
A superb Miniature Oscilloscope £25, Carr. £1-50.


RE102 42/MAST
12-3/6" x 2" sections WIRE GUYS STRAINERS in carry holdall £23-50 Carr. £2.

AERIAL RODS
3" x 1" screwed M & F ends 10 £2 Post 75p, 25 £5 c.p.
AE101. Telescopic mast antenna £3-75, Carr. £1-25 List 25p refundable with purchase.

XTAL CALIBRATOR
No. 10
1/2 10MHZ Harmonics 30 MHZ £3 Post 50p.

Surplus Electronic Trading
P.O. BOX No. 19, HITCHIN, HERTS. SG4 8TN

VEROBOARD

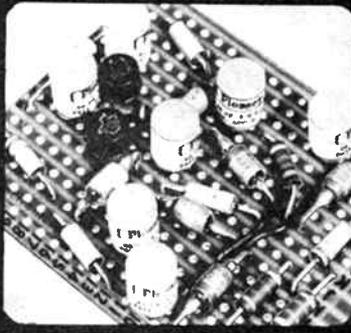

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper clad universal circuit boards. AVAILABLE FROM YOUR LOCAL RETAILER. TRADE DISTRIBUTOR: N. Rose Electrical Ltd. London, W.C.1



VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, SO5 3ER Tel: Chandler's Ford 7413

YOU AIN'T HEARD NOTHIN' YET !!

... until you tune in to stereo
perfection with 'Varicap'



'p.e.' f.m.
varicap stereo tuner

Size approx.
8 1/2" x 2 1/2" x 6 1/2"

This elegant and practical stereo tuner features push button 'spot-on' tuning with up to five simple pre-set stations (no difficult tuning dial and drive cord). It's easy 'no problem' construction requires only a few simple setting adjustments with a D.C. Voltmeter. It incorporates NEW pre-set modules for R.F. and I.F. circuits, this eliminates the need for the usually difficult circuit alignment.

All this, coupled with the latest Motorola high efficiency, Integrated Circuit 'phase lock loop' stereo decoder and automatic stereo lamp indicator, ensures perfect stereo reception.

The 'Varicap' is, in our opinion, THE most easily constructed stereo tuner available which will achieve professional results. The kit comprises Fibre glass P.C. board, elegant slimline teak veneer cabinet, brushed aluminium front panel, push buttons, instructions, in fact everything you need.

We also supply any of these kit components as separate items.

Total kit price ONLY £28 50 (inclusive of VAT and postage).

IDEAL FOR USE WITH THE 'TEXAN', 'GEMINI' OR ANY OTHER GOOD QUALITY STEREO AMPLIFIER.

PARTS FOR PRACTICAL WIRELESS PROJECTS:

After many requests, Electro Spares are supplying lists of components for ALL projects featured in 'Practical Wireless' from July 1973 issue onwards. We regret that we cannot supply lists for projects published before this date.

All you have to do is send us a stamped addressed envelope, not less than 9" x 4", stating which project is of interest to you. We will then forward you an individually priced list of the components required, there is, of course, no necessity to purchase a full kit, you may purchase only the parts you require at any one given time. We believe this method of 'one source' buying can save you time and postage—AND THAT MEANS MONEY !!

ALL COMPONENTS SUPPLIED BY ELECTRO SPARES ARE NEW, BRANDED PRODUCTS OF REPUTABLE MANUFACTURERS AND THEREFORE CARRY THE MAKERS FULL GUARANTEE.

'P.E.' 'GEMINI' STEREO AMPLIFIER

The 'Gemini' is a quality hi-fi stereo amplifier for the home constructor, featuring a genuine 30 watt R.M.S. per channel output into 8 ohms. Total harmonic distortion of 0.02% and a frequency response (-3dB) 20Hz - 100kHz, at all power levels. We are continuing to supply components for this fabulous amplifier, which is now recognised as practically THE ultimate in High-Fidelity.

We know no better unit for the home constructor—hundreds have been supplied throughout the world.

Electro Spares have available a booklet containing full specification, complete constructional information, wiring diagrams and fault finding guide etc.

The price is 55p + 4p postage, along with which we will send you our new LOW PRICE LIST. Price list available separately on receipt of a large S.A.E.

Our new Mail Order department address is set below. We aim for quick, efficient service—or why not pay us a call, we make all enthusiasts welcome and there are no parking problems.

ELECTRO SPARES

288 ECCLESALL ROAD
SHEFFIELD S11 8PE
Tel. (0742) 668888

'The Component Centre of the North'

EEMI ELECTRONIC ORGAN KITS



There are four
excellent quality
Models for the
do it yourself
enthusiast

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2x5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55.

V.A.T. please add 10%—show separately on order.

All components can be bought separately. Send 50p for 24-page catalogue which includes details of specialised components plus free vouchers worth 50p.

Also available—WIRELESS WORLD SOUND SYNTHESIZER KITS complete with reprinted instructions.

Elvins Electronic Musical Instruments SUPPLIERS OF COMPONENTS TO THE MUSICAL INDUSTRY

12 Brett Road, Hackney, London, E.8. Tel: 01 986 8455
8 Putney Bridge Rd., London, SW18 1HU. Tel: 01 870 4949

KEEP WARM AT A COOL PRICE.

Slash central heating costs with AMKIT.

If you can put in electric wiring, you can install Amkit. The unique nylon 'pipe' hot water central heating system, that you install yourself in hours.

Look at these advantages:

- No soldering
- No 'T' junctions
- No special equipment
- No leaks, no lagging, no corrosion
- No structural upheaval

Just reliable, effective central heating (Guaranteed 25 years) at a saving of between £150 & £250. This famous system has been successfully marketed since 1968.

Clip the coupon, and we'll tell you more.

To Autocon Manufacturing Co.

Spring House, 10, Spring Place, London, NW5, 3BH
Please send your brochure telling me all about Amkit.

Name

Address

PW4




or see for yourself at: THE AMKIT D.I.Y. CENTRE,
15, Procter St., London, W.C.1. (opp Holborn Undgnd).
Open Mon-Fri 9.30 am-5.30 pm. Sat 9 am-1 p.m.

Project 80

the slimmest, most elegant hi-fi modules ever made

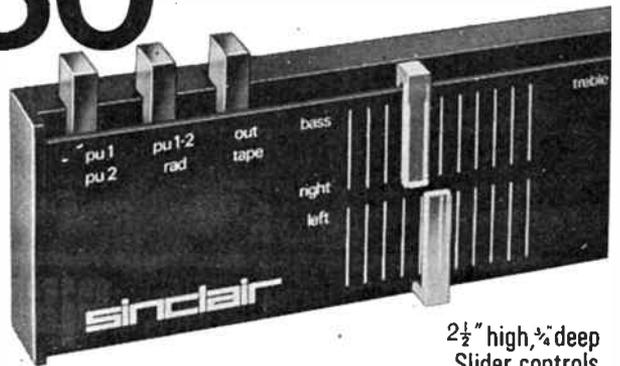
Living with hi-fi takes on new meaning with Project 80 modules. They can be assembled virtually anywhere, creating opportunities to install systems hitherto only dreamed about and never before made practical. Quality and reliability are everything you could wish for. Units are mounted by 6BA bolts at rear passing through drilled holes, cases are in black with white embellishment.



2½" high, ¾" deep
Slider controls
New circuitry

Stereo 80 pre-amplifier and control unit

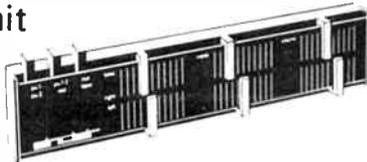Each channel has independent tone and volume slider controls enabling exceptionally good environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry which includes generous overload margins. Clear instructions with template are supplied.




Size - 260 · 50 · 20mm (10½ · 2 × ¾ ins)
Inputs - Mag. P.U. 3mV RIAA corrected, Ceramic P.U., Radio, Tape
S/N ratio - 60dB
Frequency range - 10Hz to 25KHz - 3dB
Power requirements - 20 to 35 volts
Outputs - 100mV + AB monitoring for tape
Controls - Press button for tape, radio and P.U. Sliders for Volume, Bass and Treble

R.R.P. £11.95 +£1.19 V.A.T.

Project 80 FM-tuner and stereo decoder

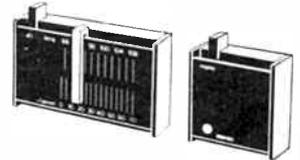FM Tuner
Size - 85 × 50 × 20mm
Tuning range - 87.5 to 108 MHz
Detector - I.C. balanced coincidence
AFC - Switchable
One 26 transistor I.C.
Twin dual varicap tuning
Distortion 0.2% at 1 KHz for 30% modulation
4 pole ceramic filter in I.F. section
Sensitivity - 4 microvolts for 30dB quieting
Output - 300mV for 75 KH deviation




Decoder -
With gallium arsenide tuning beacon and 19-transistor I.C.
Size - 47 × 50 · 20mm

FM tuner R.R.P. £11.95 +£1.19 V.A.T.

Decoder R.R.P. £7.45 +0.45p V.A.T.

Project 80 active filter unit

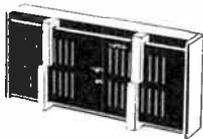

Size - 108 · 50 · 20mm (4¼ · 2 · ¾ ins)
Voltage gain - minus 0.2dB
Frequency response - 36Hz to 27KHz, controls minimum
Distortion - at 1KHz 0.03% using 30V
HF cut off (scratch) 22KHz to 5.5KHz, 12dB/oct slope
L.F. cut off (rumble) - 78dB at 20Hz, 9dB/oct slope

R.R.P. £6.95 +0.69p V.A.T.

Z.40 & Z.60 power amplifiers



Z.40
Size - 55 · 80 · 20mm
Input sensitivity - 100mV
Output - 15W RMS continuous 8 Ω (35V).
Frequency response - 10Hz 100KHz ± 1dB
Signal to noise ratio - 64dB
Distortion - less than 0.1% at 10W into 8 Ω
Power requirements - 12-35 volts

R.R.P. £5.45 +0.54p V.A.T.

Z.60
Size - 55 × 98 × 20mm
Input sensitivity - 100-250mV
Output - 25W RMS 8 Ω (45V).
Distortion - typically 0.03%
Frequency response - 10Hz to more than 200KHz ± 1dB
S/N ratio - better than 70dB

R.R.P. £6.95 +0.69p V.A.T.

Sinclair power supply units



PZ.8

The worlds most advanced unit in its class. It is a stabilised unit. Re-entrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V.
R.R.P. £7.98 · 0.79p V.A.T.
Without mains transformer
PZ.5 30V un-stabilised
R.R.P. £4.98 · 0.49p V.A.T.
PZ.6 35V stabilised
R.R.P. £7.98 · 0.79p V.A.T.

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

Should any defect arise in normal use, we will service it without charge. For damage arising from mis use a small charge (typically £1.00) will be made.

sinclair

R.O. London Road, St Ives, Huntingdon, PE17 4HJ Phone St. Ives (0480) 64311 Reg. No. 699483 England

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

BLOCK LETTERS

FEB. 74

SPECIAL OFFER !!!

SMALL ELECTROLYTICS

Ref. No.	Capacity	Voltage	Price	Ref. No.	Capacity	Voltage	Price
H8/1	1µF	150V	4p	H7/4A	64µF	35V	5p
H8/1A	2µF	150V	2p	H7/5	80µF	16V	4p
H8/2	2.2µF	25V	4p	H7/6	100µF	25V	5p
H8/2A	3.3µF	25V	4p	H7/7	100µF	25V	4p
H8/3	3µF	50V	4p	H7/8	125µF	16V	5p
H8/3A	4µF	50V	4p	H7/8A	100µF	35V	6p
H8/4	4.7µF	25V	4p	H7/9	100µF	63V	6p
H8/4A	5µF	64V	4p	H7/9A	125µF	4V	4p
H8/5	5µF	10V	4p	H7/10	125µF	25V	6p
H8/5A	5µF	150V	4p	H7/10A	160µF	2.5V	3p
H8/6A	10µF	10V	4p	H7/11	160µF	25V	6p
H8/7	10µF	70V	4p	H7/11A	150µF	16V	5p.
H8/8	16µF	35V	4p	H7/13A	200µF	25V	8p
H8/8A	16µF	16V	4p	H7/14	220µF	50V	10p
H8/9	20µF	6V	2p	H7/14A	220µF	16V	6p
H8/9A	20µF	70V	4p	H7/15	220µF	25V	5p
H8/10	22µF	50V	4p	H7/15A	220µF	35V	16p
H8/10A	22µF	100V	4p	H6/1A	250µF	4V	3p
H8/11	25µF	12V	4p	H6/2	250µF	25V	3p
H8/11A	24µF	275V	4p	H5/3A	320µF	2.5V	3p
H8/12	32µF	1.5V	4p	H6/4	320µF	16V	4p
H8/12A	30µF	10V	4p	H6/4A	330µF	18V	5p
H8/13A	32µF	50V	4p	H6/5	330µF	25V	10p
H8/14	40µF	25V	5p	H6/5A	350µF	35V	15p
H8/14A	40µF	16V	4p	H6/8	470µF	25V	10p
H8/15	47µF	50V	4p	H6/8A	470µF	35V	20p
H8/15A	40µF	35V	4p	H6/9A	400µF	40V	20p
H7/1	50µF	6V	3p	H6/13A	1000µF	25V	16p
H7/1A	50µF	10V	4p				
H7/2A	84µF	2.5V	2p				
H7/3A	84µF	25V	4p				
H7/4	64µF	15V	4p				

POSTAGE: 15p PER ORDER

ALL GOODS PLUS 10% V.A.T.

MULLARD ELECTROLYTIC CAPACITORS

Type No.	Working Voltage Vdc.	Capacitance µF	Max. Ripple Current at 50°C	Weight	Price
071 15332	16	3300	2.4 amps	1oz	15p
071 15472	16	4700	3.9 amps	1oz	17p
071 15682	16	6800	5.8 amps	1½oz	22p
072 15752	16	7500 + 7500	10.5 amps	3oz	37p
072 15113	16	11000 + 11000	13.8 amps	4½oz	48p
071 16472	25	4700	5.4 amps	1½oz	22p
072 16502	25	5000 + 5000	9.6 amps	3½oz	37p
072 16752	25	7500 + 7500	12.6 amps	4½oz	48p
071 18681	63	680	2.1 amps	1oz	15p

Type No.	Voltage	Capacitance	Weight	Price
106 16223	25	22000	17 amps	10oz £1.12
106 17103	40	10000	12 amps	7½oz 94p
107 10222	100	2200	10 amps	5½oz 74p

Type No.	Voltage	Capacitance	Weight	Price
102 15163	16	16000	8oz	20p
104 90003	20	39000	16oz	38p
102 16802	25	8000	7oz	25p
104 90001	45	20000	16oz	50p

A further 10% discount on lots of 100 of any one type.

Please calculate the weight of your order and include appropriate postage.

Not over	Ordinary Parcels	Not over	Ordinary Parcels
1½lb	16p	10lb	37p
2½lb	21p	14lb	47p
4lb	25p	18lb	57p
6lb	29p	22lb	67p

UNIUNCTION TRANSISTORS SIMILAR TO 2N 2646 25p

£1 100 1-1 WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 20p | PACK No. 1

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

POSTAGE 20p | PACK No. 2

£1 1 VERO-BOARD CUTTER
5 2½ in. x 1 in. x 15 BOARDS
50 SQ. INS. "OOO PIECES" VERO

POSTAGE 20p | PACK No. 3

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

POSTAGE 20p | PACK No. 4

£1 20 ASSORTEED UNUSED MARKED, TESTED TRANSISTORS BC108 ETC.

POSTAGE 20p | PACK No. 5

£1 1 TRANSISTORISED SIGNAL TRACER KIT
1 TRANSISTORISED SIGNAL INJECTOR KIT

POSTAGE 20p | PACK No. 6

£1 4 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS & CAPACITORS

POSTAGE 27p | PACK No. 7

£1 100 RESISTORS
100 CAPACITORS (ASSORTEO TYPES)

POSTAGE 20p | PACK No. 8

WORK WITH ADCOLA AND YOU KNOW YOU ARE USING THE BEST ELECTRICAL SOLDERING EQUIPMENT!

When you buy ADCOLA equipment you are purchasing the best soldering merchandise. These instruments identical to those used in industry world wide. The electronics industry use ADCOLA for our reliability, efficiency, precision and high safety standards. ADCOLA must be right for you!

Treat yourself to the BEST! Order on your coupon NOW

Please send me the following items

- A L706 INVADER Soldering instrument £2.42
- B L646 INVADER Soldering instrument £2.66
- C L1676 INVADER Soldering instrument £2.73
- D BL646 INVADER 12v Battery model £3.35
- E BL1076 INVADER 12v Battery model £3.50
- F INVADER Soldering Kit £4.73
- G R500 ELECTRIC Desoldering tool £9.79
- H REEL Desoldering Braid £0.75
- I L686 SOLDERING stand £1.97
- J L68 PROTECTIVE stand £1.31
- K ½ KILO SOLDER REEL £1.74
- L 3oz SOLDER REEL £0.52
- M SOLDER PACK £0.10

New Catalogue
All prices include 10% VAT

Please tick items required


PRINT NAME _____

PRINT ADDRESS _____

the economy hi-fi pack



complete down to measured leads-requires no soldering-ready to assemble

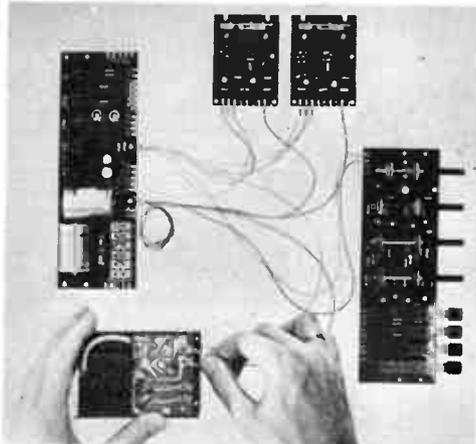

Project 605

No other firm has the same experience and manufacturing facilities as Sinclair for the design and production of modules for audio systems. That is why they were able to introduce Project 605 a complete pack produced specially for those wishing to assemble a true high fidelity stereo system at an attractively economical price. In the Project 605 you will find two Sinclair power amplifier modules capable of delivering together 30 watts RMS into 4 ohm loudspeakers, a combined control/pre-amp unit, an A.C. mains power supply unit and the Masterlink unit to which inward and outward connections are made. Wires, colour-coded and tagged with press-on clips make soldering unnecessary. Assembly is straightforward and very easy when you follow the carefully prepared instructions manual. Provision is made for connecting a stereo or mono radio tuner.

FROM DEALERS EVERYWHERE

sinclair

Sinclair Radionics Ltd, London Rd, St Ives.
Huntingdon PE17 4HJ. St Ives (048 0)6 4311

Specifications

Output - 30 watts music power (10 watts per channel R.M.S. into 3 Ω).
Inputs - Mag. P.U. - 3mV. R.I.A.A. correct. Ceramic pick-up, 50mV. Radio - 50 to 150mV. Aux. adjustable between 3mV. and 3V.
Signal to noise ratio - Better than 70dB.
Distortion - Better than 0.2% under all conditions.
Controls - Press buttons for on-off, P.U., radio and aux; Rotary Treble, Bass, Volume and Stereo Balance.
Channel matching within 1dB.
Front panel - brushed aluminium with black knobs.
Project 605 comprises pre-amp/control unit, two power amplifiers, power supply unit. Masterlink, leads and instructions manual complete in one pack. Post free

R.R.P. **£29.95** + £2.99
V.A.T.

Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Aerials

**GENUINE FULL SIZE
18 element TV aerial**
as used by leading
TV companies



IMPERIAL TRADING (AERIALS) LTD.
The quality Aerial Specialists.

BAINES for High Frequency Aerials

Full range of J Beam Aerials available
Parabeam UHF PBM 12 £2.35 PBM 18 £4.30
Multibeam UHF MBM 30 £4.40, MBM 40 £6.90, MBM 70 £12.10 MBM 70 £28.40
Stereobeams VHF/FM SBM 22 £2.95, SBM 4 £4.80, SBM 6 £7.25, 75/300 Balun £1.60
Aerial Rotators £31.50
Marthead VHF and UHF amplifiers £8.95, Petback £4.50.
Accessories: 9 x 4 RA6 please. Co-ax 5p and 10p a meter.
Postage is paid on all aerial orders. NO VAT to be added.
11 Dale Cres., Tupton, Chesterfield S42 6DR. Tel: 663755

VHF/F.M. Aerials. Loft Type, Ten for £6. Roof Type, Ten for £15. Samples each type £3. J. E. Cook, 90 Ewhurst Road, Crawley, 23895 Sussex.

Ladders

LADDERS, 'Special Offer' Unvarnished triples. 9ft 7in closed—23ft lin. extended. £18.90 delivered. Home Sales Ladder Centre (WLS2) Haldane (North) Halesfield (1) Telford, Shropshire. Tel: 0952 586644.

Service Sheets

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,
RECORD PLAYERS, TRANSISTORS,
STEREOGRAMS, RADIOGRAMS,
CAR RADIOS)
ALL AT 48p EACH

**" PLEASE ENCLOSE LARGE S.A.E
WITH ALL ENQUIRIES & ORDERS "**
Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

Educational

CITY & GUILDS EXAMINATIONS

Make sure you succeed with an ICS home study course for C & G Electrical Installations, Telecommunications Technicians and Radio Amateurs. Free details from: International Correspondence Schools, Dept. 732E, Intertext House, London, SW8 4UJ.

COLOUR TV SERVICING

Make the most of the current boom. Learn the techniques of servicing Colour & Mono TV sets through new home study courses, approved by leading manufacturers. Also radio and audio courses. Free details from: International Correspondence Schools, Dept. 732E2, Intertext House, London, SW8 4UJ.

TECHNICAL TRAINING

Get the qualifications you need to succeed. Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering & Programming. Also self build radio kits. Free details from: International Correspondence Schools, Dept. 732E3, Intertext House, London, SW8 4UJ.

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, T.V. Computers, Draughtsmanship, Building, etc. FREE book form: BIET (Dept. BPW.4 Aldermaston Court, Reading, RG7 4PF. Accredited by CACC. Member A.B.C.C.

AMIMI, MAA/LMI DIPLOMA, City & Guilds, etc. Thousands of passes. For details of postal courses in all branches of Engineering and illustrated book—FREE—BIET (Dept. BPW.3) Aldermaston Court, Reading RG7 4PF. Accredited to CACC. Member A.B.C.C.

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course (including Mono revision) for men with a good electronics background.

Next session commences on April 16th.

Prospectus from: London Electronics College, Department A4, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 25p

OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

NEW BOOKS & PUBLICATIONS (Please add 10% P.&P. on all books)	PRICE
SECOND BOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES by B.B. Babani...	£0.95
HANDBOOK OF INTEGRATED CIRCUITS (ICs) EQUIVALENTS & SUBSTITUTES...	£0.75
RAPID SERVICING OF TRANSISTOR EQUIPMENT 2nd, Edition by G.J. King. 184pp.	£1.90
SIMPLE SINGLE CHANNEL RADIO CONTROL by R.H. Warring. 144pp.	£1.50
RADIO CONTROL ANNUAL. Contains model plans on recent designs. 146pp.	£1.25
CONTROL LINE MANUAL 4th Edition, by R. Moulton. Aeromodelling using line. 216pp	£1.50
IMPROVING YOUR HI-FI by John Earl. 202pp	£3.00
QUESTIONS & ANSWERS ON INTEGRATED CIRCUITS by R.G. Hibberd. 96pp.	£0.75
BEGINNERS GUIDE TO ELECTRONICS 3rd, Edition, by T.L. Squires. 240pp.	£1.90
110 THYRISTOR PROJECTS USING SCRs AND TRIACS by R.M. MARSTON. 146pp.	£1.40
COMPREHENSIVE COLOUR TV MANUAL. Pinpoints faults with cures on Colour TVs.	£2.25
MAZDA BOOK OF PAL RECEIVER SERVICING by D.J. Seal. 288pp.	£3.80
TELEVISION ENGINEERS POCKET BOOK by P.J. McGoldrick. 6th Edition. 400pp	£2.50
AUDIO TECHNICIANS BENCH MANUAL by John Earl. 182pp.	£3.00
RADIO TECHNICIANS BENCH MANUAL by H.W. Hellyer. 215pp.	£3.00
TV TECHNICIANS BENCH MANUAL by G.R. Wilding. 187pp	£2.50
THE HI-FI AND TAPE RECORDER HANDBOOK by G.J. King. 304pp.	£2.00
TRANSISTOR AUDIO & RADIO CIRCUITS by Mullard Ltd. 230pp. 2nd Edition.	£1.80
BASIC ELECTRICITY by The Technical Press Ltd. In 5 parts (£1. per part) or 5 parts	£4.25
BASIC ELECTRONICS by The Technical Press Ltd. In 6 parts (£1. per part) or 6 parts	£5.10
BASIC SYNCHROS & SERVOMECHANISMS by The Technical Press Ltd.	£2.25
BASIC ELECTRONIC CIRCUITS by The Technical Press Ltd.	£2.25
BASIC TELEVISION by The Technical Press Ltd. In 3 parts (£1.10p each) or combined	£3.50

★ A LARGE SELECTION OF OTHER TITLES AVAILABLE AT OUR NEW SHOP PREMISES ★
OPEN UNTIL 8pm, MONDAY TO SATURDAY. CALLERS WELCOME TO COME AND BROWSE
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) good prices paid

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, YORKSHIRE. Telephone (0423) 55885

Situations Vacant

MEN!
£70p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators Training Centre

T65, Oxford House
9-15, Oxford Street, W.1.
Telephone: 01-734 2874

OPPORTUNITIES IN AUSTRALIA for Video/CTV/CCTV Technicians. Progressive company, member of major Australian Group expanding rapidly in Video field requires experienced technicians in colour TV, Video system, closed circuit TV systems including cameras. Top salary car supplied, assistance in travelling and housing. Location—Hobart, Melbourne, Sydney. Telephone Anne Graham, London 636-0541 for further details.

Books and Publications

Technical Books — Radio & Electronics

Handbook of Tested Transistor Circuits.....	£0-40
Radio Servicing for Amateurs.....	£0-20
Practical Radio Inside Out.....	£0-40
Coil Design and Construction Manual.....	£0-30
Boys Bk of Crystal Sets and Simple Circuits.....	£0-18
Transistor Circuits Manual No. 1.....	£0-15
Transistor Circuits Manual No. 2.....	£0-15
Transistor Circuits Manual No. 4.....	£0-15
Transis Circuits for Radio Controlled Models.....	£0-40
Rad & Electr Colour Codes and Data Charts.....	£0-15
Handbk of Transistor Equip. and Substitutes.....	£0-40
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0-75
High Fidelity Loudspeaker Enclosures.....	£0-40
Transistor Test Equip. and Servicing Manual.....	£0-25
Handbook of Simple Transistor Circuits.....	£0-35
Modern Transistor Circuits for Beginners.....	£0-40
Sound and Loudspeaker Manual.....	£0-50
Practical Car Radio Handbook.....	£0-30
Radio TV and Industrial Tube & Valve Equip.....	£0-40
Know Your Oscilloscope.....	£1-70
Television Servicing Vol. No. 1.....	£0-85
Television Servicing Vol. No. 3.....	£0-60
Television Servicing Vol. No. 4.....	£0-85
Using an Oscilloscope.....	£0-70
Servicing Transistor Radios for Beginners.....	£0-75
Television Timebase Circuits.....	£1-00
Jack Daws Service Clinic.....	£1-35

NEW TITLES NOW AVAILABLE

Manual of Electronic Circuits for the Home.....	£0-50
Modern Crystal Set Circuits for Beginners.....	£0-35
Electronic Novelties for the Motorist.....	£0-50
2nd Book of Transistor Equip. & Substitutes.....	£0-95
Handbook of Electronic Musical Novelties.....	£0-50
Transistorised Novelties for Hi Fi Enthusiast.....	£0-35
Fault Location Exercises in Rad. & TV Vol.1.....	£0-80
Fault Location Exercises in Rad. & TV Vol.2.....	£1-35
Colour TV Picture Faults.....	£2-50
99 Ways to Improve your Sh. Wave Listening.....	£1-90
Semi-conductors from A—Z.....	£1-50
Modern Electronic Troubleshooting.....	£1-30
104 Ham Rad. Proj. for Novice & Technician.....	£1-25
How to Solve Solid State Circuit Troubles.....	£1-75
Integrated Circuits Equip. & Substitutes Hbk.....	£0-75

PLEASE ADD 10% FOR POSTAGE & PACKING
FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

WORLD RADIO TV HANDBOOK 1974, £3.15. How to Listen to the World, £2.00. Postage and VAT included. David McGarva, PO Box 114, Edinburgh EH1 1HP.

DIRECT FROM MANUFACTURER—a comprehensive catalogue of UHF & VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (PW), 261 Hardest Street, London S.E.24.

"FROM SEMAPHORE TO SATELITE", a 300-page hardcoverd history of communications with 1000 illustrations, is sent from Geneva to readers who send £1.99 to David McGarva, PO Box 114, Edinburgh EH1 1HP. We sell books, publish World Radio Bulletin and print monitors' reporting forms.

"SHORTWAVE VOICES OF THE WORLD", £1.70, postage and VAT 11p. "SWL Address Book," £1.55+11p. "Confidential Frequency List," £1.70+11p. Books and full details from any bookshop, or in difficulty write to: David McGarva, PO Box 114, Edinburgh EH1 1HP.

For Sale

MORSE MADE EASY!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only £3-80, Complete Course £4-60 P.F.I. etc. plus 10%. (Overseas £1-00 extra) details only, 4p stamp. 01-660 2896 GSHSC (Box 11), 45 GREEN LANE, PURLEY, SURREY

TV LINE OUTPUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe Rd., Richmond, Surrey. TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

FOR SALE. P.W. August 1947-February 1974, less November 1956. P.T. Vol. 1 No. 1. April 1950-July 1965. Framfield (Sussex) 308.

LIGHTSHOW PROJECTORS from only £17, effect wheels from only £4. Many lightshow bargains at ROGER SQUIRE'S (Disco Centre), 176 Junction Road, London N19. Tel. 01-272 7474.

Wanted

TOP PRICES PAID for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),

367 Kensington Street, Bradford 8, Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

EARLY WIRELESS LITERATURE before 1934. Johnson Raffles, Haverbreaks, Lancaster. Telephone 67770 evenings.

WANTED. Early G.E.C. alldry portable BC4141. Condition immaterial, but must be complete. Box 110.

Receivers and Components

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. Extremely low leakage. All 63v D.C. Plus or minus 1% tolerance: 0.47µF—56p; 1.0µF—66p; 2.2µF—80p; 4.7µF—£1.30; 6.8µF—£1.64; 10.0µF—£2.00; 15µF—£2.75. Also available ±2% and ±5%, ex. Stock.

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15v/25v or 35v; 10.0µF at 60v/20v or 25v; 22.0µF at 61v/10v; 33.0µF at 162v/10v; 47.0µF at 3v or 6v; 100µF at 3v. All at 10p each; 10 for 95p; 50 for £4.00.

TRANSISTORS: BC107, BC108, BC109; All at 9p each; 6 for 51p; 12 for 96p. May be mixed for quantity price. BC182 and BC212 at 10p each; AF179 at 30p each. All brand new and marked. Full spec devices.

POPULAR DIODES: IN914, 6p each; 8 for 45p; 18 for 90p IN916, 8p each; 6 for 45p; 14 for 90p; IS44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13, 15, 15V. Tol. ±5% at 5 mA. All new and marked. Price 7p each; 6 for 39p; 11 for 84p. Special offer 6 off each voltage (66 zeners) £3-65.

RESISTORS. Carbon film 5%. ½W at 40°C ¼W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440v A.C. CAPACITORS: 0.1µF, size 1½in x ½in—40p; 0.25µF (1½" x 1½")—55p; 0.47 and 0.5µF (1½" x 2")—66p; 1.0µF (2" x 2")—85p; 2.0µF (2" x 2")—1.15.

SILICON PLASTIC RECTIFIERS 1-5 amp. Brand new wire-ended D027, 100 P.I.V. at 7p each; 4 for 26p. 400 P.I.V. at 8p each; 4 for 30p; 800 P.I.V. at 11p each; 4 for 42p.

7p Post and Packing on all orders below £5.00. Export orders—please add cost of air/sea mail.

PLEASE ADD 10% V.A.T.

TO ALL ORDERS

Send S.A.E. for lists of other ex-stock items, L.E.D.'s, disc capacitors, electrolytics etc.

Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. W4, The Maltings, Station Road, WEM, Salop. Tel: NANTWICH (Cheshire) 63291.

TAPE HEADS

Send stamp for lists.
R.D.I. Ltd.
Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

For valve and transistorized recorders from £2 ea.

**GUARANTEED SEMICONDUCTORS
FAST SERVICE . LOW PRICES**

AC107 10p	2N706 10p	ZENER DIODES
AC126 18p	2N930 20p	400mW 5%
AC127 18p	2N1131 22p	3-3 to 33 volts
AC128 18p	2N1132 22p	10p each
BC107 9p	2N1711 20p	1 watt 5%
BC108 9p	2N2904 22p	6-8 to 200 volts
AF114 14p	2N2904A 25p	20p each
AF115 14p	2N2905 25p	
AF116 14p	2N3053 15p	
AF117 14p	2N3054 50p	
BCY70 15p	2N3055 80p	RECTIFIERS
BCY71 25p	2N3702 11p	P.I.V. 1 AMP
BCY72 15p	2N3703 11p	50 IN4001 4½p
BFX84 24p	2N3704 11p	100 IN4002 4½p
BFX85 25p	2N3705 11p	200 IN4003 5p
BFX86 21p	2N3706 11p	400 IN4004 6p
BFX87 24p	2N3707 11p	600 IN4005 7p
BFX88 25p	2N3708 11p	800 IN4006 8p
BFX20 15p	2N3709 11p	1000 IN4007 8p

**CASH W.O. PLUS P.P. 10p to
ROSSLER SERVICES
PARNDON HALL . HAMSTEL ROAD
HARLOW . ESSEX**

INTEGRATED CIRCUIT and FET modules for construction of low-cost receivers, converters, pre-selectors, etc. SAE details,—P. R. Gollidge, Glen Tor, Torrington, Devon.

AMTRON KITS. Your Devon Stockist. E. Wenmouth, 50 South Street, Exeter 76058.

NEW MODEL V.H.F. KIT MK2

Our latest kit, improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.


Only £3.50 + p.4p 15p U.K. only.

Illustrated catalogue of selected kits and components. 20p inc. VAT. P&P free.

ALL PRICES PLUS 10% VAT

Galleon Trading Co.,
12, Burns Way,
Corringham,
Stanford-Le-Hope,
Essex. SS17 9DE

TEXAN AMPLIFIER

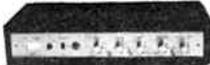

Pack

1. Resistors, 80p, post 15p
 2. Small Caps, 1.50, post 15p
 3. Large caps, 1.40, post 15p
 4. Sundries, 2.50, post 15p
 5. Switches, 1.00, post 15p
 6. Potentiometers, 1.45, post 15p
 7. Semi Conductors, 8.25, p. 15p
 8. Transformer, 5.95, post 25p
 9. Printed Circuit, 2.50, post 15p
 10. Chassis, 3.00, post 25p
 - 10a. Front Panel, 1.50, post 15p
 11. Preformed Cables, 40p, p. 15p
 12. Handbook, 30p, post 6p
 13. Teak Veneer Case, 2.75, p. 30p
- Complete Kit £29.50
Add 10% V.A.T.

TELERADIO ELECTRONICS
325 Fore St., LONDON, N.9
Tel. 01.807.3719. 4p will bring full lists of available kits.

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfd.—4p, 22, 47—41.2p. (50V—5p.) 100—51.2p. (50V—7p.) 220—6p. (50V—9p.). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p. 0.04, 0.05—3p. 0.068, 0.1—31.2p. Polystyrene 63V, E12 series 10 pf.—1,000 pf.—2p. 1,200 pf.—10,000 pf.—3p. Miniature Highstab resistors, 5%, E12 series—Carbon Film 1/4W 10—10MΩ (10% over 1 Meg.) Metal Film 1/4W 10Ω—2.2MΩ and 1W, 27Ω—10MΩ all 1/4p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

TRANSISTOR AMPLIFIERS 50p Vol/Tone Pre-Amps 30p. LW-MW Mixer-osc panels 50p all with circuits. Record player cabinets £3. Radio cabinets, suitable ext speakers, colours blue, brown, yellow. 50p Mains droppers 76Ω + 66Ω + 66Ω + 25Ω + 24Ω + 26Ω 30p. Archer, 9 Pine Grove, Maidstone, Kent.

V.H.F. & SHORT WAVE KITS

Precision standard, low cost valve and transistor Kits 10-350 m. V.H.F. 80-180 MHz. "Easy-Build" diagrams and simplified instructions. For free literature send S.A.E. to sole manufacturers. (Overseas: Int. Reply Coupon).

JOHNSONS (RADIO) Est. 1943
Shaw St, Worcester, WRI 3QQ
Tel. 24864 A JOHN BANNER CO.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

MINIATURE CERAMIC CAPACITORS 50V 25 each E6 value 22pf to 1000pf, Total 275. £3.75. NEK ELECTRONICS (W3) 28, Carnegie Road, St. Albans, Herts.

5-N CHANNEL FETS TYPE 3819E—£1 (incl VAT). Full spec devices complete with circuit details for building volt-meter, timer, etc. For full list of fets and other transistors available, send 10p. Redhawk Sales Ltd, 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

TUNBRIDGE WELLS, Components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

Miscellaneous

Darned Electronic Wizardry

by Dewtron (VAT extra.)

Famous kits, e.g. waa-waa complete kit £2.95; Fuzz kit £5.50 auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

UNIQUE HI-FI SPEAKER SYSTEM

24 WATTS PEAK!

Beautiful bookshelf units in mahogany type finish. Employs infinite baffle enclosure with dual cone 8 ohm drive unit. Brand new with 6' leads.

£9.80 Per Pair P&P 60p

GREGG Electronics
PW3, 24 Cranbourn Street
Leicester Sq. London WC2

HARDWARE SUPPLIES. Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. Ramar Constructors Services, 29 Shelbourne Road, Stratford on Avon. Warwks. CV37 9JP.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big 1/2 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g) send £1.35 for your Maxi-Volt now!
 - ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5.90 for yours now!
 - ★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £2.20 now!
- (all prices include V.A.T., packing & postage.)

Send remittance to:

BOFFIN PROJECTS,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY
(Mail order only)
Or for more details, send 15p for lists plus free design project sheet.

MORE RANGES FOR LESS MONEY!



MULTIMETER AC-DC Type U-437

10kOhms/V 2.5% Precision
A-DC 0.1-1A - 5 Ranges.
V-OC/AC 2.5 to 1000 V - 6 Ranges.
Ohms-100 to 1 MegOhm - 4 Ranges.
Frequency: 45-40kHz - 2 Ranges.
TAUT SUSPENSIONS
MOVEMENT.
Complete with steel case.
Dimensions without case:
212 x 118 x 75mm

£4.95

AC/DC Multimeter type U4324

A-DC 0.06-3A - 6 Ranges.
A-AC 0.3-3A - 5 Ranges.
V-DC 0.6-1200 V - 9 Ranges.
V-AC 3-900 V - 8 Ranges.
Frequency: 45 to 20kHz-2 Ranges.
Resistance: 500 Ohm to 5 MOhm-5 Ranges. Decibel: -10 to +12dB - 2 Ranges. Accuracy ± 2.5%.
Dimensions: 167 x 98 x 63 mm.

Only £8.00

SUPERTESTER 680 R ICE

10 Fields - 80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC - Temperature -50C to +200C - Magnetic fields up to 15 KGauss-Phase indicator- EHT 25kV Electronic Volt Ohm- meter Transistor Diode Tester etc.

£18.50

AC-CLAMP Type U-91

7 ranges 10-500 A.
Dimensions: 283 x 94 x 38mm, 680 grams with case.

£10.50

Add 10% VAT to all items + 35p P&P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB Tel: 837 7781

PRINTED CIRCUIT BOARDS. Any P.C.B. Published in **PRACTICAL WIRELESS/ELECTRONICS**, E.T.I. etc. etc. Any month any year. 5p/sq in. Postage Free. (Min. 50p). Also Artwork and/or photography undertaken. Return of post service. P. Lancaster, 11 Chesterton Road, Cambridge. CB4 3AD.

Personal

S.I.M. COMPUTER DATING. The most exciting way to make friends. Write, S.I.M. (E/17) 109 Queens Road, Reading.

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45—UHF 625, B12—VHF 405, B11—VHF RADIO

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30:—
ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY88, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF85, PCF80B, PCL82, PCL83, PCL84, PCL85, PFL200, PL38, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, PC86, PC88.

19" UHF/VHF (BBC2) £6.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—65p

± to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Ceramic Capacitors from 1PF to 8200PF (our choice) 65p.

BARGAINS PARTS

Transistor UHF Tuners—£2.00, 500k-ohms V/C with Switch—25p. 50 mixed Tuner Valves—£2.25. Brand New Transistors BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order Money back guarantee. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

M & B COMPONENTS (Leeds) LTD.

86 BISHOPGATE STREET, LEEDS 1. Phone 35649

SPECIAL OFFER

MOTOROLA CAR RADIO CHASSIS. (Not complete) Chassis—1.P. Transformers—Trimmers—Res/Caps Transistors 25B RP/Atmp. M25A Mix. M540/M241 AP *Transistor may vary slightly. Complete with Circuit 60p each, 15p P. & P LIMITED STOCK.

Few only as above, complete with P.A. Transistors 90p each, 15p P. & P.

STOCK CLEARANCE LINE

Small 12 Volt Model Makers Motor. New. 50p each, 10p P. & P. Also available 6 Volt (few only). Size approx. 1½" x 1¼".

ERNEST TURNER 1mA METERS. New Boxed. Scaled in Watts, 4" diameter, 2" deep, £1.25 each, P. & P. 25p. NOT TO BE MISSED AT THIS PRICE.

BULK PURCHASE

GREEN TRACE/MAGNETIC SQUARE FACED TUBES. Ideal Monitor/T.V. Size approx. 5" x 3" face, 12" neck. New boxed. £1.00 each, P. & P. 40p each.

E.M.I. EMPTY TAPE SPOOLS. 7" standard. New boxed. 24 for £2, P. & P. 30p.

BALANCED ARMATURE EARPIECES. Ideal for Hi-Fi Tweeters/Speaker/Microphone. Many uses. 25p each, 10p P. & P.

BUILD THE TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knock down to only 17in.
- Probuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete Kit Post 35p **£9-80** Built, tested and guaranteed Post 35p **£13-75**

MINKITS ELECTRONICS, 35a LANGLEY DRIVE, WANSTEAD LONDON, E11 2LN (Mail order only)

Versatile
10 in ONE



MIN-LAB

Comprising:

- AC and DC Voltmeter
- Audio Generator
- Ohm Meter
- Resistance Substitution
- Capacitance Substitution
- DC Ammeter
- Battery Supply
- RF Signal Generator
- RF Field Strength Indicator.

This new, unique instrument combines all you need for testing. Money back if not satisfied.

£11-95

includes VAT & p. & p.

Cash with order or send s.a.e. for illustrated data sheet to:

J. H. ASSOCIATES LTD. (DEPT. PW) Cricketfield Lane, Bishop's Stortford, Herts.

Build your next project in a BEC (Book end chassis)



New Improved with alloy trim on bottom of all cabinets. Now in easy to assemble kits.

GB3 (illustrated) . . . 14" x 9" x 4". £4-99 P & P 45p. Other sizes, SAE with enquiries. Callers welcome after 10 a.m.

H. M. ELECTRONICS 275a, Fulwood Rd, Sheffield S10 3BD (Behind Broomhill P.O.)

STABILISED 6.7.5 & 9V from 12V BATTERY



In-Car Entertainment and many other uses. Battery operated cassette recorders, radios etc., powered by 12V car battery by means of ingenious electronic of ingenious electronic.

AUTO ADAPTOR adaptor—at virtually no cost. One lead included. Only £3.75 + V.A.T. + 12p (p.p.). Also Mains Battery Eliminator £3.00. Lead (optional) 60p. State type of plug. Partics.:—

OMNIA PRODUCTS, 25 Wilbury Gdns., Hove, Sussex.

BA NUTS, BOLTS AND WASHERS per 100 Size Nuts Bolts W/ra 4 44p 55p 35p 8 35p 44p 35p	BA SPANNER SET 29p Each	CORED SOLDER ½lb. reel 62p Each
SELF TAPPING SCREWS Box of 100 Assrt. 36p	FASTENERS Box of 100 Assrt. 55p	PVC 100 GROMMETS 1", 9/32" or 1" hole State Size 44p
Toggle Switches SP/ST 26p SP/DT 37p	Continuity Probe 25p Each	5" PLIERS OR SIDE CUTTERS Insulated Handles 99p Each

*while stocks Post free Orders under £2 All prices over £2 add p&p 15p inc. VAT.

SILHILL PRODUCTS, Dept. PW4, 226 Mary St., BIRMINGHAM B13 9RJ (021-440 3600)

AERIAL WIRE. PVC covered multi-strand tinned copper. 25ft-23p. 50ft-45p. 75ft-67p. 100ft-89p. 150ft-£1.32p. 200ft-£1.76p. Including VAT. All plus 12p P&P. Al Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

VALVES Large Stock 1930 to 1973. S.A.E. for quotation. Cox Radio, The Parade, East Wittering, Sussex.

LOW COST I.C. Mounting. I.C. pin sockets in lengths of 100 for 60p (p&p 5p). Quantity rates. S.A.E. details and sample. GASKELL, Oak Lodge, Tansley, Derbyshire.

BUILD OR BUY a MINIATURE TRANSMITTER



A precision piece of equipment that has been designed and produced after 2 years research and development. The smallest transmitter available in the UK. 2" x 1" approx. Fits in the palm of your hand. Can pick up and transmit voices and minute sounds, excellent range. Can be worn round the neck, held in the hand or placed on a shelf. Receive on a VHF radio. Universal battery connections enable use of PP3 battery operates 0-15 volts, no other connections (completely self contain) to operate. simply switch on. Used the world over, many applications. Fully transistorised printed circuit. Guaranteed for 12 months.

Assembled unit ready to use £15.50
Kit with step-by-step assembly instructions . . . £11.50
If required, suitable radio for receiving transmitter £13.50

Inc. P. & P. 45p

MULHALL ELECTRONICS (PW)
Ardglass, Co. Down, U.K. BT30 7SP.
(Exporters to 14 countries)
R.A.E. licence required.

WIRE. H.C. Copper, P.V.C. Insulated 24 A.W.G. (0.2 mm.²) in P.V.C. Colours Black, Yellow, Blue or White. Reels 8ozs £0.95; 1lb £1.80; 2lbs £3.50; 4lbs £6.75 including VAT and postage larger Reels available C.W.O.

H. A. WAINWRIGHT & CO. LTD.
9A Farncombe Street, Farncombe, Godalming, Surrey.
Tel. Godalming 23545

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

FIBRE OPTICS DPTIKIT 103 contains 2 m. Crofon 1610, 64 Strand Light Conduit plus 5 metres each FP20, FP40, FP60 Plastic Monofibre (diameter 0.5, 1.0, 1.5mm). Price £4.84 inc. booklet, pp., VAT.

2N577 SILICON PHOTODARLINGTON AMPLIFIER sensitive light detector, supercedes CdS cell. Price 1 off 55p, 5 off £2.53 inc. pp and data.

RED LIGHT EMITTING DIODES MLED 500 in TO92 case, MV54 miniature (2mm). Price (both types) £1-10 for 5 inc. pp and data.

40 kHz ULTRASONIC TRANSDUCER T/R PAIR Type S05B. £3.85 per pair.

C.W.O. please to **FIBRE OPTIC SUPPLIERS (PW)**, P.O. BOX 702, LONDON, W10 6SL

FREE

Headphones or Speakers; Suitably Terminated Connectors; Handbooks; Carriage; Insurance. In addition a JOYSTICK V.F.A.; JOYMATCH A.T.U.; feeder external mounting insulators are supplied FREE or greatly reduced when you buy a PARTRIDGE PACKAGE plus DX-CRYSTAL SET.

A PARTRIDGE PACKAGE constitutes a COMPLETE RADIO STATION—ready to use however confined your domestic space. The World renowned TRIO range of Communications Receivers and Transceivers, the WORLD RECORD, internationally patented JOYSTICK V.F.A. (all band aerial) only 7' 6" long (assembled) and a JOYMATCH aerial tuning unit, a pair of matching headphones or internal speaker, plus accessories, go to complete your READY TO USE RADIO STATION at a price that truly represents VALUE FOR MONEY! H.P. FACILITIES WHERE POSSIBLE—24 HOUR DELIVERY (MON-FRI.) ADD £3.00—OUR RISK!

PARTRIDGE PACKAGE — MORE PARTRIDGE PACKAGES — HUGE SAVINGS — WRITE FOR DETAILS! PACKAGE PRICE
 No. 1 with Gen. Coverage AM/CW/SSB (MW/SW) 9R59DS Receiver (£46-75) £64-52 (Save £14-28)
 No. 3 with Amateur Bands 160 thru 10m plus 2m AM/CW/SSB JR599 (£145-75) £159-07 (Save £19-86)
 No. 4 with Amateur Bands 80 thru 10m TS/PS 515 Transceiver, 180w (£231-00) £231-00 (Save £39-50)

NOTHING MORE TO PAY! OUR RISK Access/Barclaycard orders accepted by phone
 JOYSTICK V.F.A. £13-75; JOYMATCH TX/RX A.T.U. 111A 1-6-32mHz £13-75; JOYMATCH A.T.U. 111 RX only 500kHz-32mHz £13-75; JOYMATCH A.T.U. LO-Z500 TX/RX 500w SSB (PA input), Built-in RF meter £19-91; Communications 8Ω head-phones (suitable TRIO, EC10 etc.) £3-14; Matching Speaker (with instructions for internal fitting in 9R59DS & JR310) £2-00; TRIO: Linear Amplifier TL911 £172-15; TR2200 2m personal transceiver £87-45; TR7200 2m car transceiver £142-45; Spare set valves for 9R59DS £2-35; OA2 Mains Stabiliser 74p.

Amazing "DX-CRYSTAL SET" £2-42 incl. unique aerial. Free with your Partridge Package.
NEW: AMTRON QUALITY KITS—send for brochure and prices.

PARTRIDGE BUDGET LINE

Artificial Earth—solves receive and transmit earth problems (as used on North Sea Oil Rigs!) £5-80; Aerial Bandwidth—tuned aerial for domestic receivers £5-80; A.T.U. KIT—for use with transmitters and Communications Receivers £5-80; (assembled £7-01); Mini SWR Bridge—1-8 to 180mHz, 2kw P.E.P., 75 or 50Ω, SO239 sockets; 1:1 to 1:3 ratio, 80 x 30 x 30mm £5-60. (All prices quoted INCLUDE V.A.T., CARRIAGE, PACKING, INSURANCE.)

Send 3½p stamp for full illustrated details. Special TRIO brochures (state which) 3½p stamp extra.
 Carriage and insurance extra overseas orders
NO V.A.T. ON OVERSEAS ORDERS!



G3CED — G3VFA
 FOR EXPERT ADVICE AND INFORMATION
 Tel: 0843 62535 or 62839 evenings and weekends



GIRO NO. 331 7056
 C.W.O. only. P. & P. 10p on orders below £5
 Discount: £10-10%, £20-15% (except net items)
 Export Order enquiries welcome (VAT free)
 Official Orders accepted from
 Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS

10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 610 (CARBON FILM 5%), £3-10 net
 10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 610 (CARBON FILM 5%), £3-20 net
 25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1525 (CARBON FILM 5%), £7-20 net
 25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1525 (CARBON FILM 5%), £7-35 net
 20E12 1W KIT: 20 of each E12 value, 10 ohms—1M, a total of 1220 (METAL FILM 5%), £7-30 net
 15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £8-15 net
 10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £12-65 net

RESISTORS

W. Type Range	1-9	10-49	50-99	100-249	250-499	500-999	1000+	Size mm
CF	22-1M	1	0-8	0-65	0-62	0-55	0-5	0-45
CF	22-2M2	1	0-8	0-65	0-62	0-55	0-5	0-45
CF	22-1M	1	0-8	0-65	0-62	0-55	0-5	0-45
MF	10-2M7	1	0-9	0-8	0-7	0-65	0-65	0-6
MF	10-2M2	1	0-9	0-8	0-7	0-65	0-65	0-6
MF	10-10M	1	5	1-25	1-25	1	0-95	0-98
MF	10-10M	3	2-5	2-5	2	1	1-75	1-6

For value mixing prices, please refer to our catalogue. (price in pence each)
VALUES AVAILABLE—E12 Series only.

PRESET SKELETON POTENTIOMETERS

MINIATURE 0-25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc.
 UP TO 1M Ω
 SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 5p each

MULLARD POLYESTER CAPACITORS C280 SERIES	
250V P.C. Mounting:	0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 3½p, 0-068µF, 0-1µF, 4½p, 0-15µF, 4½p, 0-22µF, 5½p, 0-33µF, 8p, 0-47µF, 9p, 0-68µF, 11p, 1µF, 15p, 1-5µF, 22p, 2-2µF, 25p.
MULLARD POLYESTER CAPACITORS C296 SERIES	
400V:	0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 2½p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3½p, 0-047µF, 0-068µF, 0-1µF, 4½p, 0-15µF, 6½p, 0-22µF, 8½p, 0-33µF, 12p, 0-47µF, 14p, 0-68µF, 18p, 0-1µF, 0-15µF, 4½p, 0-22µF, 0-01µF, 0-015µF, 0-022µF, 2½p, 0-047µF, 0-068µF, 3½p, 0-1µF, 0-15µF, 4½p, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 7½p, 0-68µF, 11p, 1µF, 12p.
MINIATURE CERAMIC FILM CAPACITORS	
50V:	(pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0-01, 0-015, 0-022, 0-033, 0-047, 2½p, each, 0-1, 30V, 4½p, 0-1; 100V, 5½p.
POLYSTYRENE CAPACITORS 160V 5%	
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p, 6p, 2200, 10,000, 4½p.	

B. H. COMPONENT FACTORS LTD.

(P.W.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ
 Tel: Cheddington 668446 (Std. Code 0296)
 PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electrolytics	
1-0µF 63V	6p
1-5µF 63V	6p
2-2µF 63V	6p
3-3µF 63V	6p
4-0µF 40V	6p
4-7µF 63V	6p
6-8µF 63V	6p
8-0µF 40V	6p
10µF 16V	6p
10µF 25V	6p
10µF 63V	6p
15µF 16V	6p
15µF 63V	6p
16µF 40V	6p
22µF 25V	6p
22µF 63V	6p
32µF 10V	6p
33µF 16V	6p
33µF 63V	6p
47µF 10V	6p
47µF 25V	6p
47µF 63V	8p

VEROBOARD 0-1 0-15	
2½ x 5"	28p 28p
2½ x 3½"	26p 19p
3½ x 5"	32p 33p
3½ x 3½"	28p 28p
2½ x 5" (Plain)	7p 7p
2½ x 3½" (Plain)	— 12p
5 x 3½" (Plain)	— 22p
Insertion tool	59p 59p
Track Cutter	44p 44p
Plugs, Pkt. 25	10p 10p
TRANSISTORS	
AC127 16½p	BC212L 12p
AC128 22p	BC213L 12p
BC107 11p	BC214L 17p
BC108 12p	OC44 18p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	Y1543 33p
BC183L 12p	2N2926 11p
BC184L 13p	2N3702 11p

POTENTIOMETERS	
Carbon Track 5K Ω to 2M Ω, log or lin. Single, 16½p Dual Gang 46p. Log Single with switch 26p	
Slider Pots. 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 55p.	
DIODES	
IN4001 6½p	DIN 2 Pin 12p
IN4002 7½p	3 Pin 13p
IN4003 9p	5 Pin 180° 15p
IN4004 9½p	Std. Jack 14p
IN4005 12p	2.5mm Jack 1p
IN4006 14p	Phono 5½p
IN914 7p	
IN916 7p	
BA100 8p	
OA5 42p	
OA47 9p	
OA81 11p	
OA200 8p	
PLUGS	
DIN 2 Pin 12p	
3 Pin 13p	
5 Pin 180° 15p	
Std. Jack 14p	
2.5mm Jack 1p	
Phono 5½p	
ELECTROLYTIC CAPACITORS. Tubular & Large Cans	
(µF/V): 2-2/25, 2-2/63, 4-7/10, 4-7/25, 4-7/63, 22/10, 22/25, 22/63, 5p, 2/10, 10/10, 50/10, 100/10, 50/25, 10/50, 100/50, 200/10, 100/25, 50/50, 64p, 500/10, 200/25, 100/50, 9p, 1000/10, 500/25, 200/50, 11p, 2000/10, 1000/25, 500/50, 164p, 1000/50, 500/25, 200/50, 11p, 2000/10, 1000/25, 500/50, 164p, 1000/50, 33p, 1000/100, 66p, 2000/25, 27p, 2500/12, 17p, 2500/25, 33p, 2500/50, 62p, 3000/50, 72p, 5000/25, 66p, 5000/50, 94p, 7000/50, 60p, 25,000/25, 74p, HI-VOLT: 8/350, 14p, 16/350, 19p, 32/350, 25p, 50/250, 18p 100/500, 33p.	
METALLISED PAPER CAPACITORS	
250V: 0-05µF, 0-1µF 4½p, 0-25µF, 5½p, 0-5µF, 6½p, 1µF, 9p.	
500V: 0-025µF, 0-05µF, 4½p, 0-1µF, 5½p, 0-25µF, 6½p, 0-5µF, 9p.	
1000V: 0-01µF, 10p, 0-022µF, 12p, 0-047µF, 0-1µF, 16p, 0-22µF, 31p, 0-47µF, 39p.	
SOCKETS	
DIN 2 Pin 10p	
3 Pin 10p	
5 Pin 180° 12p	
Std. Jack 14p	
2.5mm Jack 1p	
Phono 5½p	
QUANTITY DISCOUNT	
SPECIAL BULK BUY PRICES ARE AVAILABLE BY QUOTATION FOR LARGE PROJECTS AND TRADE	

WEYRAD

IMPORTANT ANNOUNCEMENT

IT IS WITH GREAT REGRET THAT WE HAVE TO STATE THAT OWING TO REVISED COMPANY POLICY WE SHALL NO LONGER BE PRODUCING COMPONENTS FOR AMATEUR CONSTRUCTORS OR SMALL QUANTITY USERS.

THIS CHANGE WILL COME INTO EFFECT IMMEDIATELY AND WE ARE UNABLE TO ACCEPT FURTHER ORDERS FROM THE TRADE OR INDIVIDUAL CUSTOMERS. EXISTING ORDERS WILL BE COMPLETED WITH A MINIMUM OF DELAY.

WE ARE SORRY TO HAVE TO TAKE THIS STEP WHICH HAS BEEN FORCED UPON US BY INCREASES IN THE COST OF LABOUR AND MATERIALS WHICH NOW MAKE ANY FORM OF SMALL SCALE PRODUCTION HOPELESSLY UNECONOMIC. IN CLOSING THIS PARTICULAR FACET OF OUR BUSINESS WE SHOULD LIKE TO THANK ALL OUR PAST AND PRESENT CUSTOMERS FOR THEIR VALUED SUPPORT OVER MANY YEARS.

WEYRAD (ELECTRONICS) LIMITED



BAKER 12' MAJOR £11.55
30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £14.85
30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W £10.45	Superb 12 in. 20W £18.70	New Group 60/12
Major 12 in. 20W £11.55	Group 25 12 in. 25W £10.45	12 in. 50W £17.60
Deluxe 12 in. 15W £13.20	Group 35 12 in. 35W £11.55	

BAKER LOUDSPEAKER CO., BENSHAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684 1665
ALL PRICES INCLUDE V.A.T. HI-FI ENCLOSURE PLANS 42p

If you have difficulty in obtaining

PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£3.25) to:—

Subscription Department,
Practical Wireless,
Tower House, Southampton Street,
London, WC2E 9XQ

PLUGS & LEADS

Plugs	
Pack 107 5 pin Din	22p
Pack 108 3 pin Din	20p
Pack 135 1/4" Jack	27p
Pack 130 1/4" Jack Stereo	50p
Pack 103 Loudspeaker Plug	17p
Pack 100 Phono Plug	7p
Pack 230 3 pin Socket	25p
Pack 236 5 pin Socket	33p
Pack 234 Loudspeaker Socket	33p

RECORD CARE

Cecil Watts Dust Bug	£1.20
Parastatic Disc Preener	45p
Antistatic Fluid	20p
Dust Bug Spares (Brush & Roller)	15p

CASSETTE TAPES

Audio-Magnetic C60	
Qty 3 6 10 20	
Price [£1.00 £1.90 £3.20 £6.30	
Cassette Caddy £1.20	
Cassette Head Cleaner 35p	

ZONAL ILFORD TAPE

5" Standard 600ft	25p
5 1/2" Standard 900ft	50p
7" (Plain boxed) 1200ft	60p
7" (Westminster Boxed) 1800ft	£1.25
7" Reel of Leader Tape (Blue or green)	75p

HEADPHONES

Sennheisser HD414	£12.50
AKG K50	£6.50
Beyer DT48S	£35.00

MICROPHONES

AKG D109	£11.50
AKG D202E1	£39.50
AKG D190C	£17.00
AKG D190E	£18.20
AKG D224	£50.00
Sennheisser MD211N	£45.00
Sennheisser MD413N	£27.00
Sony ECM50	£85.00
Audio RMS7F Radio Mike	£210.00

SPEAKERS

E.M.I. 350 Kit Bohms	£8.20
E.M.I. 450 Kit Bohms	£4.50

DIAMOND STYLI

8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8. All at 80p each.
Double Diamond £1.25
Diamond suitable for Orbit NM22; G800; M3D £2.25 each

CARTRIDGES

Goldring G800	£6.00
Orbit NM22	£4.00
Shure 75/6	£6.00
Sonotone 9TAHC (Dia)	£2.00
Sonotone 8TA4 (Dia)	£1.50
Ronnette 105 (Dia)	£1.25

All prices include VAT and postage

J. J. Francis (Wood Green) Ltd

MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS
Telephone: Matching 476

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 0-15 in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

THE MANAGEMENT ADVISES WITH REGRET THAT DUE TO RISING COSTS AND STAFF SHORTAGE THE MAIL ORDER SERVICE HAS TO BE CURTAILED. FROM 1ST JANUARY 1974 ALL MAIL ORDERS ACCOMPANIED BY REMITTANCE WILL BE SUBJECT TO A MINIMUM CHARGE OF £5.00 EXCLUDING V.A.T., I.E. £5.50 INCLUDING V.A.T. GOODS OF VALUE UNDER £5.00 WILL BE AVAILABLE ONLY TO PERSONAL CALLERS, EITHER AT OUR RETAIL BRANCH, 85, TOTTENHAM COURT ROAD, W.1, OR TRADE COUNTER AT 44A WESTBOURNE GROVE, LONDON W2. MINIMUM ORDER CHARGE FOR APPROVED ACCOUNT CUSTOMERS IS £10.00 EXCLUSIVE OF V.A.T.

TAUT SUSPENSION MULTIMETERS MADE IN USSR



8 models of multimeters from simple 22-range instrument priced at £4.95 to sophisticated 43-range instrument with full transistorised safety trip circuit, priced at £17.00. Models available with transistor testing facilities (U4341) and built-in audio/i.f. oscillator (U4323).

All the above instruments and full range of other test equipment are included in our new 1973/74 combined catalogue/price list which covers valves, semi-conductors and passive components, basic specifications of semiconductors, cathode ray tubes, Klystrons and magnetrons, as well as transistor substitution list.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER. CALLERS SATURDAYS

C.W.D. Please, P. & P. add 10p to orders under £2. Prices exclusive of VAT
PLEASE ADD 10% TD FINAL TOTAL
Send 10p Postage for our comprehensive catalogue.

TRANSISTORS

AC125 12p	AF126 19p	BF195 15p	OC81 13p	OA85 7p
AC126 12p	AF127 20p	BFY50 22p	TIS43 30p	OA90 5p
AC127 12p	BC107 10p	BFY51 22p	2N1306 23p	OA91 5p
AC128 12p	BC108 10p	MJE370 57p	2N1307 23p	OA200 8p
AC176 14p	BC109 11p	MJE520 52p	2N2926 9p	OA202 8p
AC187 12p	BC147 12p	OC26 40p	2N3014 10p	1N914 5p
AC188 12p	BC148 12p	OC28 40p	2N3053 20p	1N4001/2 6p
AD161 30p	BC149 12p	OC35 40p	2N3054 43p	1N4003/4 7p
AD162 30p	BC177 14p	OC42 10p	2N3055 55p	1N4005 7p
AF114 12p	BC178 14p	OC44 10p	2N3704 12p	1N4006/7 8p
AF115 12p	BC179 14p	OC45 10p	2N3705 11p	1N4145 8p
AF116 12p	BD131 49p	OC70 10p	2N3706 11p	BYZ11 18p
AF117 12p	BD132 49p	OC71 10p	2N3707 11p	W01 30p
AF118 10p	BF194 15p	OC72 10p	2N3819 25p	W06 34p

DIODES

THYRISTORS

CRS 1/05 50V 1A	20p
CRS 1/60 600V 1A	38p
CRS 3/60 600V 3A	48p
C107B 200V 4A	52p

SWITCHES

Toggle SPST	18p
Standard DPDT	22p
Slide 1 amp DP	10p
Wafer 1/12, 2/6, 3/4, 4/324p	

ZENER DIODES

BZY88 Series 400mW	
3-3V-33V	
Price 10p each	

VEROBOARDS

PITCH	0-1	0-15	0-15
	plain		
2 1/2 x 3 1/2	22p	16p	12p
2 1/2 x 5	24p	24p	12p
3 1/2 x 3 1/2	24p	24p	
3 1/2 x 5	28p	27p	21p
2 1/2 x 17	80p	60p	45p
3 1/2 x 17	105p	84p	63p
5 x 17	141p		89p
Pkt. of 50 pins			20p
Spot face cutter			42p
Pin Insertion tool			52p

JACK PLUGS (CHROME)

Standard Screened	12p	SOCKETS	12p
Stereo Screened	30p	Stereo	15p
2-5mm Screened	8p	2-5mm	7p
3-5mm Screened	10p	3-5mm	7p

DIN PLUGS, SOCKETS AND COUPLERS

Plugs: 2, 3, 4, 5 (180°, 240°), 6, 7
PLUGS: 12p, SOCKETS: 8p, COUPLERS: 10p

PHONO PLUGS, SOCKETS AND COUPLERS

Assorted Coloured Plugs: 5p, COUPLERS: 8p
SOCKETS single: 5p, Double: 7p, Triple: 10p

POLYESTER CAPACITORS. Axial lead type.
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 2µp, 0.01µF, 0.015µF, 0.022µF, 3µp, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 4µp, 0.22µF, 7p, 0.33µF, 10p, 0.47µF, 13p, 160V: 0.1µF, 0.15µF, 4µp, 0.22µF, 5p, 0.33µF, 6p, 0.47µF, 7p, 0.68µF, 10p, 1µF, 13p.

ELECTROLYTIC CAPACITORS. Miniature axial lead type.
50V d.c. Plaque type 25mm leads
Track 0-25W, log and linear values.
0.33V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 8.2µF, 10µF, 15µF, 22µF, 47µF, 68µF, 6p each.
40V: 100µF, 6p; 150µF, 25V, 6p; 25V: 220µF, 11p; 470µF, 13p; 1,000µF, 25p.
16V: 1000µF, 1500µF 18p

CERAMIC CAPACITORS:
50V d.c. Plaque type 25mm leads
Range: 22pF-10,000pF. Price 2p each.
0.015µF, 0.022µF, 0.033µF, 0.047µF 3p.

MYLAR FILM CAPACITORS
100V: 0.001µF, 0.002µF, 0.005µF, 0.01µF, 0.02µF, 0.04µF, 0.05µF 3p
100V: 0.1µF, 0.2µF, 50V: 0.47µF 6p.

POTENTIOMETERS: Carbon
Track 0-25W, log and linear values.
1kΩ-2MΩ Single gang 12p
5kΩ-2MΩ s/gang w/switch 24p
2kΩ-2MΩ Dual gang 37p

PRESET POTENTIOMETERS
0-25W 1kΩ-1MΩ Hor. and Vert. 6p
0-1W 100Ω-220kΩ Vert. only 3p

SLIDER POTENTIOMETERS
0-25W log and linear values
10kΩ-100kΩ Single gang 40p
10kΩ-100kΩ Dual gang 55p

KNOBBS
To fit 1/8" shaft unless specified.
Black Pointer type 6p
Sliver Silvered 10p
Slider 1" with chrome rim 15p
Slider Pot knob (Black) 10p
Slider Pot knob (Silvered) 10p

RESISTORS

±W	Tol	Range	Values	1-9	10-99
1/2W	5%	2R-10M	E12	1p	0-8p
1/2W	5%	2R-10M	E12	1p	0-8p
1W	5%	2R-10M	E12	2p	1-5p
4W	10%	1-10 ohm	E12	6p	

LINEAR IC's

LM300	TO99	£1 70
LM304	TO99	£1 70
709C	TO99	30p
709C	8pin DIL	32p
709C	14pin DIL	32p
741C	8pin DIL	36p
741C	14pin DIL	36p
723C	14pin DIL	80p
TBA 800 5 Watt IC		£1 35

ZN414 Radio IC £1 15
TBA800 5 Watt IC £1 35
TGS Gas Sensing Semiconductor £1 85

TTL 74 SERIES

7400	17p	7407	39p	7416	48p	7433	88p	7451	17p
7401	17p	7408	20p	7420	17p	7440	17p	7460	17p
7402	17p	7409	20p	7425	55p	7441	74p	7476	44p
7403	17p	7410	17p	7426	50p	7442	74p	7490	74p
7404	17p	7411	28p	7427	50p	7447	99p	7495	90p
7405	17p	7412	39p	7430	17p	7448	£1-08	74141	98p
7406	39p	7413	32p	7432	50p	7450	17p	74180	£2-00

BARGAIN OFFER OF THE MONTH
ELECTROLYTIC CAPACITORS
Axial Lead: 4µF/10V 33µF/16V, 40µF/16V, 80µF/16V-4V, 100µF/16V, 125µF/16V
4p each. 250µF/15V, 640µF/10V, 1000µF/10V 8p each.

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained thousands of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold!"—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW51 Aldermaston Court, Reading RG7 4PF.

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Faringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Publisher's subscription rate (including postage) for one year UK £3-25, Overseas £3-50. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

World Radio History

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers—A.M.S.E. (Mech.) Institute of Engineers & Technicians (M.I.E.) CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work Eng. Inspection Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineers Designers (A.M.I.E.D.) General Draughtsmanship Elec. Draughtsmanship Architectural Draughtsmanship Technical Drawing	<input type="checkbox"/> A.B.T. Clerk of Works Construction Surveyors Institute—L.C.S.I. CITY & GUILDS General Building (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities, Estimates Hydraulics Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers—A.M.S.E. (Elec.) CITY & GUILDS Gen. Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng. Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS Radio, TV, Electronics CITY & GUILDS Telecoms. Gen. Radio & TV Eng. Radio Amateurs Exam Radio Servicing TV Servicing Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Acctnts. Computer Programming Works M'tment. Work Study Gen. Production Eng. Estimating & Planning Storekeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I. M.A.A. I.M.I. CITY & GUILDS Auto Eng. Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage M'tment ARB Aero Engineering Certs. Gen. Aero Eng.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers—A.M.S.E. (Civ.) Institute of Building—L.I.O.B.		<input type="checkbox"/> G.C.E. — choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW51 Aldermaston Court, Reading RG7 4PF

NAME _____ QN _____ BPW51

Block Capitals Please

ADDRESS _____

OTHER SUBJECTS _____

AGE _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

**DONT RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Order your latest Henry's Catalogue Price 55p post paid
complete with Discount Vouchers



You pay less
VAT with Henry's
Low Prices

BUILD THE TEXAN

**20 + 20 WATT IC
STEREO AMPLIFIER**

As featured by
Practical Wireless
1972




Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6 IC's, 10 transistors, stabilisers Gainers low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** — DEVELOPED BY **RISCAO ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES.** On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner. Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21 30p. Distributed by Henry's throughout UK. **FREE**—Teak cabinet with complete kit.

Kit price **£28.50** (+VAT +50p carr/packing) or built and tested **£35.00** (+VAT +50p carr/packing) as illustrated.

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98.50**
100 watt amplifier for above **£118.50**
As above but with Slider Controls **£49.50**
SDLS 100 watt mixer/amplifier with slider controls **£69.00**
R50 50 watt mixer/amplifier **£49.50**
R100 100 watt mixer/amplifier **£57.50**
DISCO AMP 100 watt mixer/amplifier **£73.00**
Northcourt:
400 40 watt mixer/amp **£37.50**
800 80 watt mixer/amp **£45.00**
DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers) **£49.50**
SDLI (rotary controls) **£58.50**
SDLI (slider controls) **£58.50**
DISCO VOK (slider controls) the complete disco preamp **£72.00**
DJ100 100 watt power amplifier for above **£49.50**
DJ30L Mk II 3 channel 3kw sound to light **£41.25**
DJ30L Mk III slider controls **£45.50**
DJ DISC LITE as 30L-2 plus variable speed flashes **£54.00**
DIMAMATIC 1 kW adjustable speed auto dimmer **£25.00**
Carlsboro Reverberation Unit **£44.00**
Disco anti-feedback microphone **£11.95**
Cote 150 watt liquid wheel projector **£23.50**
150 watt QI liquid wheel projector **£50.00**
150 watt QI cassette wheel projector **£50.00**
Spare Effects and liquid cassettes large range of patterns **£6.00**
6 inch Liquid wheels, various cassettes **£6.00**
Mini spot bank fitted 3 lamps **£12.95**
Auto Trilite (mini with flashers) **£17.00**
Bubblemaker with liquid **£22.50**
Mixers/Mics/Speakers/Lighting
U.K.'s largest range of Disco Lighting. **FREE STOCK LIST REF. NO. 18 ON REQUEST**
AKG / RESLO / DJ / CARLSBORO / EAGLE MICS., STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURNTABLES, PUBLIC ADDRESS COMPONENTS.

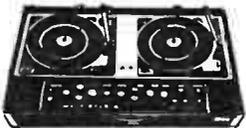

All prices carr. paid (UK) (VAT EXTRA)
Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter systems, 8" Bass/Midbass and Melinex Domed HF radiator plus crossover **£12.50** per pair of systems (carr./packg. 40p) or built into veneered cabinets, size 18 x 12 x 6 1/2" **£19.50** pair (carr. £1).

HI-FI TAPE EQUIPMENT



U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17). Phone 01-402-4736 for Barclay/Access Card. Direct orders and latest prices

TRANSISTORS/SEMI-CONDUCTORS

U.K.'s largest range for every application. Small quantity discounts. Also Trade, Export and Industrial enquiries invited. Latest stock list (Ref. No. 36) including valves on request.

ELECTRONICS SUPPLIES

Specialists in electronics for more than 30 years. Trade and industry supplies—every type of component and equipment.



NEW SINCLAIR PROJECT 80

Stereo Pre-Amplifier **£11.95**
Audio Filter Unit **£6.95**
Z40 15 Watt Amplifier **£5.45**
Z60 25 Watt Amplifier **£6.95**
PZ5 Mod. for 1 or 2 Z40 **£4.95**
PZ6 Mod. (S Tab) 1 or 2 Z40 **£7.98**
PZ8 Mod. (S Tab) 1 or 2 Z60 **£7.98**
TRANSFORMER FOR PZ8 **£3.95**

NEW FM TUNER **£11.95**
STEREO DECODER **£7.45**

All items post paid.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe.



KIT PRICE £21.00 (+ VAT)
or built and tested **£24.95 (+ VAT)**

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN 1/2 REC. PRICES COMPLETE WITH LIBRARY CASES

	3 for	6 for	10 for	25 for
C 60	£1.10	£1.98	£3.00	£7.40
C 90	£1.46	£2.80	£4.60	£11.25
C 120	£1.80	£3.45	£5.50	£13.45



Quantity and trade enquiries, invited
LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian **£1.36** per course. **£5** for any 4.

LOW COST HI-FI SPEAKERS

SPECIAL OFFERS
EMI 13" x 8"—full range speakers (post 20p each or 30p pair)
*150TC—8 ohms Twin Cone 10 watt **£2.20** each or **£4.00** pair.
*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms **£3.85** each
EW 15 watt 8 ohms C/o Tweeter **£5.25** each or **£7.90** pair.
350 20 watt C/o Tweeters 8 or 15 ohms **£7.80** each
* Polished wood cabinet **£4.80** post 35p.



8 ohms full range (post 20p)			
FR4	4"	5 watt	£4.75
FR65	6 1/2"	10 watt	£6.30
FR8	8"	15 watt	£8.50
FR23	9 x 6"	15 watt	£8.90
BASS & MID RANGE—8 ohms (post 20p)			
AA12	5"	15 watt	£3.75
B110	5 1/2"	15 watt	£7.20
B200	5 1/2"	15 watt	£8.50
B139/2	13" x 8"	30 watt LF	£13.75
TWEETERS AND CROSSOVERS (post 20p)			
K2006	10 watt	8 or 15 ohms	£2.10
FHT6	15 watt	8 ohms	£3.35
K2011	30 watt	8 ohms	£4.80
T27	KEF		£5.52
Accent 100	30 watt	8 ohms	£2.70
K4009	1kHz/5kHz C/o		£2.70
SN75	3kHz var. C/o		£3.10
SPEAKER KITS (carr. etc. 35p)			
20-2	8"	30 watt	£24.50 pair
20-3	8"	40 watt	£35.95 pair
LINTON 2		20 watt	£18.30 pair
GLENDALE 3		30 watt	£32.95 pair
DOVEDALE 3		50 watt	£51.50 pair
KEF KK2			£55.00 pair
KEF KK3			£78.00 pair

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble— that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2 1/2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs. Tangents. Sines etc.



£24.95 Also available assembled **£27.20**
+ VAT. ready to use. + VAT.

10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E & O E. Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402-8791. See pages 1126 & 1127 of this magazine

Henry's RADIO LIMITED

EDGWARE ROAD, LONDON W2

404 406 Electronic Components and Equipment 01 402 8381
309 PA Disco Lighting High Power Sound 01 723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres London and branches now open
120 Shaftesbury Avenue, London W1 01 437 9692
104 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
130-134 Station Road, Harrow, Middlesex 01 663 7788/9
354-356 Edgware Road, London W2 01 402 5854/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to
6 pm six days a week
Hi-Fi — Tape Equipment
Discount Stock List
Free at all stores