

PRACTICAL WIRELESS

JANUARY
1975

25p

P
W

MODEL CONTROL by RADIO

PART 1



ALSO:

LOW FREQUENCY AND MARINE RECEIVER

PRE-PUBLICATION BOOK OFFER: details inside

CONCLUDING SECTION of PW BUYERS' GUIDE 74/5

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder


- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator.
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

Total Building Costs
£7.23 P P & Ins. 44p
(Overseas P & P £1.85)
(+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/4" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

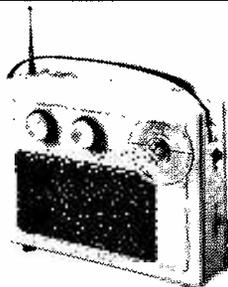


Nine Transistors, 9 Tuneable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors, 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/4" x 7" x 2 1/2" approx. Parts Price List and Plans 40p (Free with parts).

Total Building Costs **£6.95** P P & Ins. 44p
(Overseas P & P £1.85)
(+ 8% VAT 55p)


POCKET FIVE

NOW WITH 3" LOUD-SPEAKER

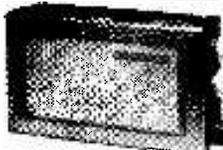

3 Tuneable wavebands, M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/4" x 1 3/4" x 3 1/4" approx. Plans and Parts Price List 20p (Free with parts).

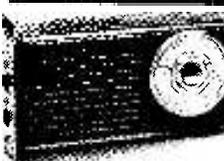Total Building Costs **£2.50** P P & Ins. 26p
(Overseas P & P £1.25)
(+8% VAT 20p)



TRANSONA FIVE NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 20p (Free with parts).


Total Building Costs **£2.75** P P & Ins. 26p
(Overseas P & P £1.25)
(+8% VAT 21p)

TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tuneable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/4 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 35p (FREE with parts).

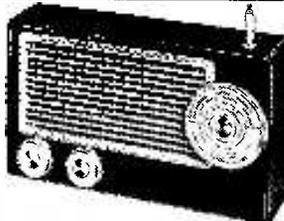Total building costs **£4.48** P P & Ins. 33p
(Overseas P & P £1.25)
(+ 8% VAT 36p)



ROAMER SIX


CASE AND LOOKS AS TRANS-EIGHT

6 Tuneable Wavebands: MW, LW, SW1, SW2, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/4 x 2 1/2 in. approx. Plans and parts price list 35p (FREE with parts).

Total building costs **£3.98** P P & Ins. 31p
(Overseas P & P £1.85)
(+ 8% VAT 32p)

NEW Everyday Series

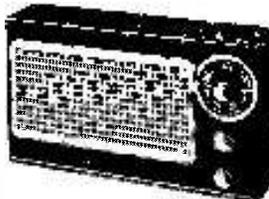Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/4" x 2 1/2" approx. Parts Price List and Plans 20p. Free with parts.

Total Building Costs **£2.95** P P & Ins. 30p
(Overseas P & P £1.25)
(+ 8% VAT 23p)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans 30p. Free with parts.

Total Building Costs **£3.60** P P & Ins. 30p
(Overseas P & P £1.25)
(+ 8% VAT 29p)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 35p. Free with parts. Overseas P & P £1.05.

Total Building Costs **£4.08** P P & Ins. 31p
(Overseas P & P £1.85)
(+ 8% VAT 32p)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL




7 Tuneable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4 in. approx. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

Total building costs **£6.98** P P & Ins. 47p
(Overseas P & P £1.85)
(+ 8% VAT 56p)

ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

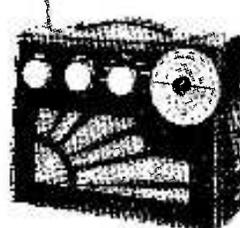

10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers. 9 Tuneable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

Total building costs **£8.50** P P & Ins. 52p
(Overseas P & P £1.85)
(+ 8% VAT 68p)

"EDU-KIT"



Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches; Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors; 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

Parts price list and plans 40p (FREE with parts).
Total building costs **£5.50** P P & Ins. 33p
(Overseas P & P £1.85)
(+ 8% VAT 44p)

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelis" shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel.: 0234 52887. Reg. No. 788372.

I enclose £..... for

Name

Address

(Dept. PW1.)

PRACTICAL WIRELESS

VOL. 50 NO. 9

ISSUE 815

JANUARY 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalli

PRODUCTION & NEWS

EDITOR Colin R. Riches

PROJECTS SUB-EDITOR

Geoffrey C. Arnold

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder

01-634 4292

Susan King

ADVERTS. MANAGER

01-634 4293

Roy Smith

CLASSIFIED ADVERTS.

01-634 4301

Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £4.35 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.34) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974/5. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 798 THINGS TO COME—Leader article
- 799 NEWS ... NEWS ... NEWS ...
- 805 P.W. AT THE AUDIO FAIR—Pictures
- 806 NEXT MONTH IN PRACTICAL WIRELESS
- 808 PRODUCTION LINES Products reviewed by *Colin Riches*
- 821 ARRA EXHIBITION at Leicester
- 828 ON THE AIR
- 828 Amateur Bands—*Eric Dowdeswell, G4AR*
- 829 Broadcast Bands—Medium Wave—*Charles Molloy*
- 830 —Short Wave—*Derek Bell*
- 835 Tele-Tennis reprint
- 836 HOTLINES on recent developments by *Ginsberg*

● CONSTRUCTIONAL

- 800 LOW FREQUENCY AND MARINE RECEIVER—Part 1—*Charles Heath*
- 810 AN ACTIVE AERIAL—*Charles Heath*
- 817 P.W. 'KEMPTON' CAR STEREO CASSETTE PLAYER—Part 2—*Keith Cummins & Tony Francis*
- 822 MODEL CONTROL BY RADIO—Part 1—Receiver—*F. G. Rayer, G3OGR*
- 831 TAKE 20, No. 67, BASIC WOBBLATOR—*David Andrews*
- 839 EXPERIMENTAL WORKSHOP Phase Shift Circuits (contd)—*M. J. Hughes, M.A., C. Eng., MIERE*

● OTHER FEATURES

- 830 POINTS ARISING ...
- 835 TECHNICROSS No. 8
- 847 GOING BACK—Equipment of yesteryear—*Colin Riches*

SPECIAL PRE-PUBLICATION BOOK OFFER—Page 832
BUYERS' GUIDE to Radio and Electronic Components—FINAL PART

HUGE DISCOUNTS

ON LEADING BRAND HI-FI ALL RSC PRICES INCLUDE VAT LOW DEPOSIT CREDIT TERMS

Full labour and material guarantees for 12 months

	List Price	RSC Price
WHARFEDALE DENTON	£42.31 Pr.	£29.95
WHARFEDALE LINTON	£52.39 Pr.	£38.95
LEAK 250 SPEAKERS	£65.48 Pr.	£42.00
LINEAR 202 AMPLIFIER	£39.23	£24.95
ROTEL RT222 AM/FM Tuner	£50.57	£38.95
ROTEL RT322	£73.16	£53.50
ROTEL RX150 A Tuner/Amp	£77.09	£54.95
LEAK 2000 Tuner/Amp	£165.70	£134.95
Wharfedale Denton Tun/Amp	£93.28	£59.95
RANK 150a Stereo System	£137.35	£79.95

Also Shure Cartridges, Basf Tape, Koss H/Phones, etc.
Prices of above correct at Nov 12 1974

AKAI TAPE UNITS

Model	Rec. Price	£
GXC 36D	£110.72	£72.50
GXC 38	£147.19	£105.95
GXC 38D	£137.38	£97.95
GXC 46D	£157.59	£109.95
GXC 40T	£186.09	£135.95
GXC 75D	£199.90	£142.95

GXC 510D Rec. price £189.90 £135.95

Model	Price	£
GXR 82D	£122.65	£89.95
4000 DS	£130.12	£94.95
4000 DB (Dolby)	£196.27	£139.95
1721 L	£118.58	£84.95
CR 81D	£98.10	£69.95
CS33D	£105.81	£75.95

GOLDRING GL72 T/Table & G800 £29.95 (Approx. value £46) Carr. 75p
GOLDRING GL75 T/Table & G800 £34.95 (Approx. value £65) Carr. 85p
PIONEER PL12D T/Table on plinth & cover £41.75 List £61.90
BSR TD8S 8 track player. Special price £14.95
T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER
GARRARD SP25 MK IV with G850 Special Price £19.95 (Carr. £1)
McDONALD MP60 with G800 or G850 ,, ,, £19.95 (Carr. £1)
RANK BD2000 Rec. Price £67.27 £48.95 (Carr. £1)

FANE HI-FI LOUDSPEAKERS AT APPROXIMATELY HALF-PRICE

UNREPEATABLE OFFER BRAND NEW BOXED FULLY GUARANTEED for High-Fidelity NOT Group Disco use
 Available by Mail Order only due to small quantities of some models. SAE for leaflets. Please state impedance required where not ind.

Model	Price	Model	Price	Model	Price	Model	Price	Model	Price	Model	Price	Model	Price
505	£2.78	807T 3Ω	£2.25	121/10	£3.17	138/10LR	£2.50	138/15TLR	£4.96	122/10TLR	£6.36	122/14ALR	£9.52
506	£2.61	1001	£4.37	121/10T	£3.37	138/10TLR	£2.63	101/10A	£4.27	122/12	£6.75	122/17	£10.26
507	£1.08	1002	£4.19	121/11	£3.58	138/11	£3.55	101/14	£6.04	122/12A	£7.08	122/17A	£10.59
801	£3.93	1005	£3.85	121/11T	£3.78	138/11LR	£3.87	101/14A	£6.74	122/12D	£6.88	122/17T	£10.50
802T	£3.89	1008	£3.50	121/15	£4.61	138/13	£3.88	122/10	£5.16	122/12T	£7.08	122/17LE	£10.98
802T	£3.82	1008	£2.93	121/16LR	£5.33	138/13LR	£4.15	122/10A	£5.49	122/14	£8.47	122/17ALR	£11.31
805	£3.25	1001LR	£5.09	138/10	£2.18	138/15	£4.51	122/10LR	£6.08	122/14A	£8.80	152/10	£9.26
806	£2.56	1005LR	£4.37	138/10T	£2.81	138/15LR	£4.83	122/10T	£5.49	122/14LR	£9.19	152/12	£10.84

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 - 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12.95 Carr. Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.95 or dep. £2.12 and 8 monthly payments £2.12 (Total £19.08).



HI-FI SPEAKER ENCLOSURES

Teak veneer Carr. 50p. Sizes approx. per enc.
MEB 13 x 9 1/2 x 6 1/2 in. £3.95
JEB 16 x 11 x 9 in. £5.95 } Both cut for 8in. speaker
SE10 25 x 16 x 9 in. Cut for 10in. and Tweeter £8.95
SE12 25 x 16 x 9 in. Cut for 12in. and Tweeter £8.95



AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 Gauss 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. £6.95 Carr. 45p
 OR SENIOR 15 WATT INCLUDING £8.95 Carr. 50p
HF123 13,000 GAUSS SPEAKER

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Response 30-20,000 c.p.s. -2dB. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm spkrs. Max. sensitivity 5mV. O/P rating I.H.F.M. Enclosed enamelled case 9 1/2 x 2 1/2 x 5 1/2 in. Silver finish fascia 10 1/2 x 3 1/2 in. Complete kit, wiring diagrams and instructions. £7.95 Carr. 40p. FACTORY BUILT £10.95



R.S.C. TA12 MKIII 6.5+6.5 WATT STEREO AMPLIFIER

Fully Transistorised. Hi-Fi/O/P of 6.5 watts per channel. Optimum performance with any crystal or ceramic P.U. Cartridge, Radio Tuner, Tape Rec. etc. Input Sel. Switch, Bass, Treble, Vol. & Bal. Controls. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS £12.95 Carr. 40p. Or in Teak Dep. £2.50 & 8 mthly pymts 12 mths guarantee £16.61 Veneer housing £19.55 £2.50 (Total £22.50)



AUDIO FIDELITY FRI SPEAKER KIT

Response 30Hz-15KHz. Rating 15 watts in sealed cabinet. Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material, Screws, Terminal Panels. £10.95

SPECIAL OFFER £14.99 Pair Carr. 50p each. Carr. Free.

AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE. Exceptional performance at low cost.

HF80ST 8" 10W	£3.55	HF180D 12" 15W	£6.50
HF102D 10" 10W	£3.50	HF180 12" 15W	£7.95
HF120 12" 15W	£5.95	HF180D 12" 15W	£8.50

AUDIO FIDELITY MODEL 80 HI-FI SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high tone response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 8-15Ω. £4.50 ea. £7.98 pr.

MODEL 83 8" 15w. with Parasitic Tweeter. £5.99 ea. £10.95 pr. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 8-15Ω.



HI-FI 8" x 5" 7 watt LOUDSPEAKERS

with parasitic Tweeter 8 ohm imp. Post and Packing 20p

£1.25

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET Only high grade components by leading manufacturers

- * Push Button Selector Switching
 - * Jack Socket for Headphones
 - * Neon Indicator
 - * Satin Silver Finish Metal Fascia
 - * Solid State Circuitry
 - * Twenty Silicon Transistors
 - * Four Diodes, Four Rectifiers
- Send S.A.E. for full descriptive leaflet.

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ± 1 1/2 dB.



COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £4.90 extra. Assembled unit in cabinet £42.50

£22.50

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms
 Performance comparable with COMPLETE KIT units at twice the cost

£25.95 Carr. 75p

Deposit £4.71 and 8 monthly payments £2.12 (Total £29.87) Consists of (1) 12in. 15w Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) Dome Pressure Tweeter. (5) Quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions.



R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

Model	Price
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.	
250v., 60mA, 6.3v. 2a	£1.50
250-0-250v., 60mA 6.3v 2a	£1.60
FULLY SHROUDED UPRIGHT MOUNTING	
250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a.	£2.25
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£3.75
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£3.75
300-0-300v. 130mA, 6.3v. 4a. c.t., 6.3v. 1a.	£4.50
For Mullard 510 Amplifier	£4.50
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£3.75
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	£4.50
425-0-425v. 200mA, 6.3v. 4a., c.t., 5v. 3a.	£8.50
425-0-425v. 200mA, 6.3v. 4a., twice 5v. 3a.	£8.70
450-0-450v. 250mA, 6.3v. 4a., c.t., 5v. 3a.	£9.00

FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50/s. Screened

Model	Price
CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. £1.75, 2 1/2a. £1.95, 3a. £2.00, 4a. £2.45, 5a. £2.75, 6a. £3.00	
AUTO (Step Up/Step Down) TRANSFORMERS 0-110/120v. 200-250v. 50-80 watts £2.50, 150 watts, £4.50 250 watts £5.50; 500 watts £8.50	
OUTPUT TRANSFORMERS	
Std. Pentode 5000-3Ω or 7000-3Ω	88p
Push-Full 8 watts EL84 to 3Ω or 15Ω	£1.45
Push-Full 10 watts 6V6, 3-5-8-15Ω	£2.25
Push-Full EL84 to 3 or 15Ω 10-12 watts	£2.25
Push-Full Ultra Linear for Mullard 510, etc.	£3.75
Push-Full 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15Ω	£3.20
Push-Full 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15Ω	£5.50

SELENIUM RECTIFIERS

F. W. (Bridged) All 6/12v. D.C. output. Max. A.C. input 18v.
 1a, 38p. 2a, 49p.
 3a, 65p. 4a, 81p.
 6a, 97p.
 L.F. CHOKES
 150mA, 7-10H, 250
 10H, 200 Ω 95p;
 60mA, 10H, 400
 Ω 95p.

RSC 100watt DISCO SYSTEM

50 WATT SPEAKER **50 WATT SPEAKER**

TWIN TURNTABLE WITH PRE-AMP and POWER AMPLIFIER

HEADPHONES MICROPHONE

Complete with lid

AT FANTASTIC LOW PRICES!

Units listed below
 (a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier
 (b) PAIR OF HI-FI HEADPHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
 (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"

£149-95

(a) (b) (c) & (d) Carr. £3-00

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP80 type turntables and Sonotone or Acoac Cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid, see illustration on left. Or Dep. £9-00 and 18 fortnightly pymts. £4-22 (Total £34-98) Carr. £1-50

£75-00

STEREO VERSION OF ABOVE SYSTEM Carr. £3-50 Or DEP £29-95 and 18 fortnightly pymts. £11-11 (Total £229-98) **£199-95**

TD2S STEREO VERSION of above Car. £1-80 Terms. Dep. £15-00 and 18 fortnightly payments £6-51 (Total £132-18) **£115-00**

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £99-95 Carr. £2-50

Garrard SP25 or McDonald MP60 turntables. Sonotone or Acoac cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £11-48 and 18 fortnightly payments £5-74 (Total £114-80)

STEREO DISCOMASTER **£145** or DEP. £20 and 18 fortnightly pymts £8-15 (Total £166-70). Carr. £3

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair

TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback howl characteristic high flux 13" x 8" x 20 watt speakers. Terms: Dep. £8-95 and 8 m'thly payments £2-67 (Total £25-31) Carr. 65p. **£19-95**

TYPE C3/70 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5-11 & 8 m'thly pymts. £5-11 **£39-95** (Total £45-99) Carr. 85p

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 Gauss 8/15Ω £29-95 Dep: £3-80 and 8 m'thly payments £3-80 (Total £34-20)	15" 60 Watt 14,000 Gauss 8/15Ω £16-95 Dep. £2-17 and 8 m'thly payments £2-17 (Total £19-53)	12" 50 Watt 13,000 Gauss 15Ω £12-95 Terms for pairs Dep £3-90 & 8 m'thly pymts £3-16 Total £29-18 PAIR SUITABLE ALL PURPOSES

FOR BASS GUITAR, ELECT. ORGAN, ETC.

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

MINSTREL 8W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: Deposit £4-40 and 8 monthly payments £2-67 (Total £25-78) Carr. free **£19-95**

FANE CRESCENDO SPEAKERS FULL RANGE AVAILABLE AT ALL BRANCHES



'POP' 25/2 12" 30W. Dual cone. 15 ohm Imp. (Not for Bass Guitar use) **£8-95**

PH50 HIGH POWER TWEETER Rating 50 Watt with 4 to 6 mtd filter. Imp 8 Ω **£5-95**

GROUP EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK. III AMPLIFIER PR. FANE POP 25/2 30W L/SPEAKERS Terms: Deposit £7-35 and 8 monthly payments of £7-35 (Total £66-15)	£43-95 £17-90 £61-85	PACKAGE PRICE £56-95 carr. £1-10
F.A.L. PHASE 50 MK. III AMPLIFIER PR. FANE POP 50 L/SPEAKERS Terms: Deposit £22-00 and 12 monthly payments of £4-20 (Total £72-40)	£43-95 £25-80 £68-85	PACKAGE PRICE £63-95 carr. £1-10
F.A.L. PHASE 50 AMPLIFIER PAIR L12/25G SPKRS (in Cabinets) Terms: Deposit £22-00 and 12 monthly payments £4-20 (Total £72-40)	£43-95 £25-90 £69-85	PACKAGE PRICE £63-95 carr. £2-00

FAL MAESTRO COMBINED 30W AMP. AND 12" SPEAKER £43-74 Carr. Free

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size Fitted carrying handle. Deposit £5-59 and 8 m'thly payments £5-59 (Total £50-31)

RSC 'PHANTOM 50' Rating 50 watts. 3 inputs, 2 vol. controls. Bass, Treble, Presence **£49-95** Carr. £1-50
Terms: Deposit £6-39 & 8 m'thly. pymts. £6-39 (Total £57-51).

FAL PHASE 50 Mk. III AMPLIFIER 50 WATT £43-95 Carr. Free

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speaker/s 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £5-75 & 8 monthly payments £5-75. Total £51-75. Carr. Free **£43-95**

REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P rating. Not for Bass Guitar. ★ Two Fane heavy duty high flux 12in. spkrs. ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £27-98, & 18 fortnightly payments of £3-99 (Total £79-80). Carr. £2-50 **£69-95**

REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-18 & 18 fortnightly payments £4-59. (Total £91-80). Carr. £2-50 **£79-95**

GP30 AMPLIFIER £29-95 Carr. 75p

For Guitar, Vocal or Instr. Group, Gram, Radio or Tape. 4 inputs. 2 Vol. Controls. Current Valves. Peak o/p rating. Strong Vynide covered cabinet with carrying handles. Black/Silver Fascia. Neon Indicator. For 200-250v A.C. For 3 or 15 Ω **£29-95** Carr. 75p
speakers. Send SAE for leaflet. Terms: Dep £5-58 & 8 m'thly pymts £3-58 (Total £34-22)

REGENT '50' AMPLIFIER £36-95 Carr. £1

As supplied with Regent 50x or 59B. Terms: Dep. £4-72 & 8 m'thly pymts £4-72 (Total £42-48) **£36-95** Carr. £1

COMPLETE PULSAR £99-95 'SOUND TO LIFE' SYSTEM

AT A WORTHWHILE SAVING ON individual units purchased separately. Terms: Deposit £11-48 and 18 fortnightly payments £5-74. (Total Credit Price £114-80). Super SL Unit. 1000 watt per channel. Manual override buttons, 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd and 10 yd leads, fitted plugs. Units sold sep.

TITAN 18" 100W SPEAKERS £25-95

15 ohms impedance List £35 Carr 75p

FAL DISCO PRE-AMPLIFIER £18-50

Monitoring, Mic, Jack & Tape inputs. Independent Vol. Control. Std. 200-250v A.C. Mains operation

NEW BRANCHES AT
**BOLTON, COVENTRY
 DONCASTER, PRESTON
 and STOCKPORT**
 OPEN ALL DAY SATURDAYS (5 Day Week)



Barclaycard and Access accepted
 All items subject to availability. Prices correct at 23.10.74 E. & O.E.

HI-FI CENTRES LTD.

- DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.) Tel. 63069
- EDINBURGH 101 Lothian Rd. (Closed Wed.) Tel. 229 9501
- GLASGOW 326 Argyll St. (Closed Tues.) Tel. 248 4158
- HULL 7 Whitefriargate (Closed Thurs.) Tel. 20505
- LEICESTER 32 High Street (Closed Thurs.) Tel. 56420
- LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.) Tel. 28252
- LIVERPOOL 73 Dale St. (Closed Wed.) Tel. 236 3573
- LONDON 238 Edgware Road, W.2. (Closed Thurs.) Tel. 723 1629

- MAIL ORDERS & EXPORT ENQUIRIES TO: AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: Pudsey (09785) 77681.
 MAIL ORDER MUST NOT BE SENT TO SHOPS TERMS C.W.O. or C.O.D. or C.O.D. under #1. POSTAGE 40p PER ORDER OR AS QUOTED. TRADE SUPPLIED.
 S.A.E. PLEASE WITH ENQUIRIES.
- MANCHESTER 60A Oldham Street (Closed Wed.) Tel. 236 2776
 - MIDDLESBROUGH 106 Newport Road (Closed Wed.) Tel. 47098
 - NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.) Tel. 21469
 - NOTTINGHAM 19/19A Market Street (Closed Thurs.) Tel. 48088
 - PRESTON 41 Friargate Walk, St. Georges Shoppg Prec. Tel. 51979
 - SHEFFIELD 13 Exchange Street (Castle Mkt. Blds.) (Closed Thurs.) Tel. 20716
 - STOCKPORT 8 Little Underbank (Closed Thurs.) Tel. 480-0777
 - SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 70573

- BRADFORD 10 North Parade (Closed Wed.) Tel. 25349
- BOLTON 23 Deansgate. (Closed Wed.) Tel. 33512
- BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)
- COVENTRY 17 Shelton Square, The Precinct. Tel. 25983
- DERBY 97 St. Peter's Street. (Closed Wed.) Tel. 41361
- DARLINGTON 19 Northgate (Closed Wed.) Tel. 68043



Newnes - Butterworths

Books on Radio, TV, Electronics etc . . .

- BEGINNER'S GUIDE TO ELECTRONICS—3rd Edn. Squires and Deason £1.90
- BEGINNER'S GUIDE TO RADIO—7th Edn. King. £1.00
- BEGINNER'S GUIDE TO TELEVISION—5th Edn. King. £1.60
- BEGINNER'S GUIDE TO TRANSISTORS. Reddihough. £1.00
- FM RADIO SERVICING HANDBOOK—2nd Edn. King. £3.00
- FOUNDATIONS OF WIRELESS AND ELECTRONICS—8th Edn. Scroggie. £3.00, limp £1.80
- 110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR. Marston. Cased £1.80, limp £1.20
- 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR. Marston. Cased £1.80, limp £1.20
- 110 THYRISTOR PROJECTS USING SCRs AND TRIACS. Marston. Cased £2.40, limp £1.40
- PRACTICAL WIRELESS CIRCUITS—18th edn. The Technical Staff of 'Practical Wireless'. £1.20
- PRINCIPLES OF TRANSISTOR CIRCUITS—4th edn. Amos. Cased £3.00, limp £1.50
- QUESTIONS AND ANSWERS ON ELECTRONICS. Brown. £0.75
- QUESTIONS AND ANSWERS ON INTEGRATED CIRCUITS. Hibberd. £0.75
- QUESTIONS AND ANSWERS ON RADIO AND TELEVISION—3rd Edn. Hellyer. £0.75
- QUESTIONS AND ANSWERS ON TRANSISTORS—3rd Edn. Brown. £0.75
- RADIO AND ELECTRONIC HANDBOOK. Wilding. £1.20
- RADIO VALVE AND TRANSISTOR DATA—9th Edn. Ball. £0.75
- RAPID SERVICING OF TRANSISTOR EQUIPMENT—2nd Edn. King. £1.90
- TRANSISTOR POCKET BOOK. Hibberd. £1.40
- 20 SOLID STATE PROJECTS FOR THE CAR AND GARAGE. Marston. Cased £1.80, limp £1.20
- 20 SOLID STATE PROJECTS FOR THE HOME. Marston. Cased £1.60, limp £1.00
- WIRELESS SERVICING MANUAL—10th Edn. Cocking. £1.50

All these books, and many more, are available from

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, YORKSHIRE. Telephone: 0423-55885

Please add 10% for Postage and Packing on all books. Send large S.A.E. for FREE booklists. Open until 6 pm Daily and 8 pm Saturday

THIS CHRISTMAS

have a TV Tennis game exactly like the pub. Plug into your own TV aerial socket. Special features inc. score shown on screen, sound when ball hits bat etc.

11

7

Ball serves and speeds up automatically, bats will deflect the ball in five different directions, picture fully interlaced. Absolute game of skill for all the family, the TV game you'll never get tired of. This is the ultimate in TV games.

No other company can offer so many features, complete in Cabinet, tested and ready for use, normal price £199.00, special Christmas price £120.00. For the do-it-yourself enthusiasts logic card with vision modulator and sound amplifier assembled and tested £85.00 in Kit form Printed circuit board and Instructions £14.50. All prices inclusive of VAT and delivery.

Send cheques and postal orders to
LOGIC LEISURE LTD.

Kingfisher House, 68 Park Road,
New Barnet, Herts. Tel: 01-440 9173/4

Please send s.a.e. for further details. Callers welcome for demonstration. Trade enquiries welcome. Export can be arranged.

NEW

ALL
SILICON!



PRACTICAL
WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was described in *Practical Wireless*, and has proved extremely popular.

The kit is supplied with a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with AMP Electrical Spade Connector Block together with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE OFFER SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components are available separately. Case size 4 3/4" x 3 3/4" x 2". Complete assembly and construction manual free with kit, available separately 25p.

SUITABLE FOR 12V SYSTEMS WITH NEG. OR POS. EARTH.

PRICE: **£9.50** U.K. ORDERS PLEASE ADD VAT


Quantity Discounts:

Trade and Overseas	1-5 Nett	6-9 less 10%
Enquiries Invited	10-49 less 15%	50-99 less 20%
Mail Order Only.	100-999 less 25%	1000 up less 30%

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING

DABAR ELECTRONIC PRODUCTS

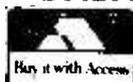98 LICHFIELD STREET
WALSALL, Staffs WSI 1UZ



MAPLIN ELECTRONIC SUPPLIES

★ SAME DAY SERVICE

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3-7in. x 4-5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2T (with tremulant) ONLY £14.95.

DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.

Keyboards: High quality adjustable type.

Sloping front 61-note C to C £18.50

Sloping front 48-note C to C £14.85

Flat front 48-note F to E £14.85

Contact Blocks GB2 (2 make contacts) 19p

Palladium earth bar per octave length 15p

Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch 49p

Swell pedal 10k log pot fitted £5.98

REVERBERATION UNIT

Enhances the sound of any electronic musical instrument.

Ready built spring line driver module suitable for use with almost any spring line £5.34

Two types of spring line available:

Short line £3.05

Long line £7.59

S.a.e. please for details. leaflet MES 24

BASIC ORGAN CIRCUIT

Leaflet MES 51 shows complete circuit for a basic fully polyphonic organ. Send only 15p for leaflet and start building now! REMEMBER—when you have built this organ you will later be able to use the same top quality component parts as the basis of a large sophisticated instrument with all the facilities you want. Watch our ads for details.

Leaflet MES 52 shows how to extend your MES 51 basic organ to two keyboards with lots more stops. Just send 5p (stamp) with an s.a.e. and we will send you a copy.

DISCOUNTS! DISCOUNTS!

Every time you spend over £2 (excluding VAT) you will receive some MES Discount Vouchers, one for each full pound spent on goods. Two for each full pound if you spend over £6 on goods. When you've collected over 25 vouchers send them to us with an order and we'll give you FREE GOODS TO THE VALUE OF £1.

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price	Mfd V	Price
1.63	6p	68	6-3	6p	
1.5	63	6p	68	16	6p
2.2	63	6p	68	63	14p
3.3	63	6p	100	4	6p
4.7	63	6p	100	10	6p
6.8	40	6p	100	25	6p
6.8	63	6p	100	40	6p
10	25	6p	100	63	16p
10	63	6p	150	6-3	6p
15	16	6p	150	16	6p
15	40	6p	150	25	6p
15	63	6p	150	40	14p
22	10	6p	150	63	16p
22	25	6p	220	4	6p
22	63	6p	220	10	6p
33	6-3	6p	220	16	6p
33	16	6p	220	25	14p
33	40	6p	220	40	16p
47	4	6p	220	63	25p
47	10	6p	220	100	25p
47	25	6p	330	10	6p
47	40	6p	330	16	14p
47	63	6p	330	25	16p
			4700	4	28p

OMNIUM GATHERUM

PP3, 6 etc. battery clip dual min.	9p
PP1, 9 etc. battery clip separate per pair	6p
Pair crocodile clips 1 red, 1 black insulated sleeve.	10p
Solder Multicores 22swg 10 metres	25p
Silicone grease in special dispenser 20ml.	54p
Red neon 240V panel mounting	23p
Lacing Cord Strong rayon cored PVC 25m.	51p
Panel fuse holders 20mm 20p; 1 1/2"	41p
Transformers	
LT700 min. output transformer Pri. 1-2k Ω Sec. 5 Ω 200mW	50p
Sub-min. Mains Transformer 6-0-6V 100mA	95p
12-0-12V 50mA	95p
Size: Both approx. 30 x 27 x 25mm.	
Min. Mains Transformer (Size: 46 x 31 x 38mm) 0-12V 250mA, 0-12V 250mA	£1.38
Mains transformer MT3AT Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A	£3.60
Mains Transformer MT206AT Pri. 200-220-240V, Sec. 0-15-20V 1A, 0-15-20V 1A	£3.98

MES CATALOGUE 25p

Our 80 page catalogue has over 20 pages showing connexion details and data for our complete range of transistors, diodes, I.C.'s etc. + Over 100 Photographs + Over 100 line drawings. Seeing exactly what you're buying makes ordering so easy!

PLUGS AND SOCKETS



DIN PLUGS

2 pin (1 flat) 8p
3 pin 9p
4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 10p

DIN Sockets

2 pin 6p
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 7p, 6 pin 9p

MAINS

P360 3 pin 1-5A chassis plug with line socket. Per pair 30p
SA 2190 3 pin 5A chassis plug 22p
SA 1882 Line socket for above 25p

McMURDO

RP8 8 way chassis plug 52p

RSS 8 way chassis socket

88p

PHONO

Plug plastic 5p
Plug screened 12p
Chassis socket 4p

JACK

Std. 1/2" mono plug Plastic 13p
Screened 21p

Std. 1/2" stereo plug


Plastic 18p
Screened 20p

Open mono socket

2" 10p; Moulded mono socket 1/4" with 2 break contacts 14p; Moulded stereo socket 1/4" with 3 break contacts 15p; 3.5mm. plug plastic 9p; screened 15p; open socket 9p.

POTENTIOMETERS

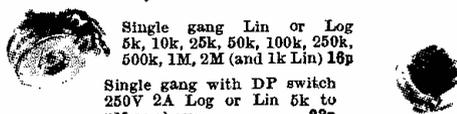Rotary miniature carbon track 1/2" spindle.



Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 18p

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 33p

Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 49p.

PRESETS

Sub-miniature 0-1W Vert or Horiz. 100, 250, 500, 1k, 2-5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 7p

NE555V 8-pin DIL 69p

RESISTORS

Carbon Film 1/4W 5% 1Ω to 1M; 10%; 1-2M to 10M E12	1p
Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1-2M to 10M E12	1p
Carbon Film 1/4W 5% 1Ω to 910k E12 & E24	1p
Carbon Film 1/4W 5% 10Ω to 10M E12	31p
Metal Oxide 1/4W 2% 10Ω to 1M E12 & E24	4p
Wirewound 2 1/2W 10% 0-22ohms to 0-47ohms E12	14p
Wirewound 2 1/2W 5% 1ohm to 270ohms E12	12p
E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades	
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades	

WE KNOW YOU NEED IT!



The MES 1974 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY.

You'll be IMPRESSED with our POST FREE ordering system, EXCITED by our BIG VALUE discount vouchers, STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

LINEARS

CA3046	69p
LH0042C. TO99 (TO5). FET i/p Op Amp	£4.25p
LM301A. 8-pin DIL. Op Amp	39p
MC1303L. 14-pin DIL. Stereo Preamplifier	£1.39p
MC1310P. 14-pin DIL. FM Stereo Decoder (no coils needed)	£3.15p
MFC6040. electronic attenuator	86p
MFC8010. 8-pin base, 1W Audio Power Amp	£1.37p
MFC4000B 1 watt Audio Amp	38p
NE555V. 8-pin DIL. Precision Timer	69p
NE561B. 16-pin DIL. Phase Locked Loop	£4.48p
SG3402N Amplifier/Multiplier	£1.69p
SG1495D. 14-pin DIL. Four Quadrant Analogue Multiplier	£2.70p
UA723C. TO99 (TO5), 2 to 37V Voltage Regulator	75p
UA723C. 14-pin DIL, 2 to 37V Voltage Regulator	75p
UA741C. 8-pin DIL. Op Amp	36p
UA741C. 14-pin DIL. Op Amp	45p
UA747C. 14-pin DIL. Dual Op Amp	£1.05p
UA748C. 8-pin DIL. Op Amp	39p
ZN414. TO5. TRF Radio	£1.20p

Full data, pin connexions, etc., on nearly all types listed in our catalogue. Price 25p

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way. each 88p. Mains rotary DPST 250V 2A 20p

Push to make non-locking 14p	
Toggle 250V 1-5A with ON/OFF plate 25p.	
Slide Sub-miniature DPDT 9p	
High quality "sub-miniature" toggle switches	
SPDT 1-5A 204V AC	56p
DPDT 1-5A 240V AC	75p
DPDT 3A 240 AC	77p
Four Pole DT 3A 240V AC	£1.37

VAT Please add 8% to the final total.

Post & packing FREE in U.K. (15p handling charge on orders under £1.) First class post pre-paid envelope supplied free with every order.

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. PHONE SOUTHEND (0702) 44101

Radio Operators. How to see more of your wife without losing sight of the sea.



Join the Post Office Maritime Service. We have openings for Radio Operators at several of our coastal stations. The work is just as interesting, just as rewarding as aboard ship, but you get home to see your wife and family more often. You need a United Kingdom General or First Class Certificate in Radiocommunications, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting pay for a man of 25 or over is £2,270, plus cost of living allowance with further

annual increases after that. Though we're happy to take people from 19 up. In addition to your basic salary, you'll get an average allowance of £450 a year for shift duties and there are opportunities for overtime.


Other benefits include a good pension scheme, sick pay and prospects of promotion to Senior Management.

For more information, write to: ETE Maritime Radio Services Division (RC12), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London, EC1A 1AS.

**Post Office
Telecommunications**

QUALITY STEREO SOUND

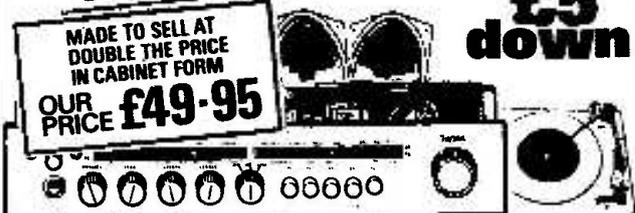ALMOST **1/2 PRICE OFFER!** SOLENT AUDIO SYSTEM



MADE TO SELL AT
DOUBLE THE PRICE
IN CABINET FORM
OUR PRICE **£49.95**

**£5
down**

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £2.50. Send £7.50 today.

Chassis only available for cash at £35.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every order.

LEWIS radio

WS 1/75 100 CHASE SIDE SOUTHGATE
LONDON N14 5PL. Telephones: 01-882-1644

16 CHERRY LANE
BRISTOL BS1 3NG

THE RADIO SHOP

TELEPHONE
0272-421196



TRIACS



1.6 AMP PLASTIC TAB		6.5 AMP ISOLATED TAB		10 AMP ISOLATED TAB	
NAS0161W 100V	.27	NAS0651W 100V	.46	NAS1001W 100V	.63
NAS0161X 100V	.26	NAS0651X 100V	.44	NAS1001X 100V	.60
NAS0162W 200V	.30	NAS0652W 200V	.58	NAS1002W 200V	.78
NAS0162X 200V	.28	NAS0652X 200V	.56	NAS1002X 200V	.74
NAS0164W 400V	.40	NAS0654W 400V	.84	NAS1004W 400V	1.09
NAS0164X 400V	.38	NAS0654X 400V	.80	NAS1004X 400V	1.04
NAS0166W 600V	.55	NAS0656W 600V	1.05	NAS1006W 600V	1.34
NAS0166X 600V	.52	NAS0656X 600V	1.00	NAS1006X 600V	1.28
3 AMP "CLIPPED TAB"		8.5 AMP ISOLATED TAB		16 AMP ISOLATED METAL	
NAS0301W 100V	.30	NAS0851W 100V	.50	NAS1601W 100V	.90
NAS0301X 100V	.28	NAS0851X 100V	.52	NAS1601X 100V	.82
NAS0302W 200V	.36	NAS0852W 200V	.67	NAS1602W 200V	.95
NAS0302X 200V	.34	NAS0852X 200V	.64	NAS1602X 200V	.88
NAS0304W 400V	.52	NAS0854W 400V	.97	NAS1604W 400V	1.40
NAS0304X 400V	.50	NAS0854X 400V	.92	NAS1604X 400V	1.32
NAS0306W 600V	.70	NAS0856W 600V	1.20	NAS1606W 600V	1.85
NAS0306X 600V	.66	NAS0856X 600V	1.14	NAS1606X 600V	1.75

Devices with Internal Trigger have "W" suffix. "X" denotes Standard Triac.



THYRISTORS



1.6 AMP MIN. T05		4 AMP ISOLATED TAB		6 AMP ISOLATED TAB	
NAS006P 50PIV	.25	NAS106P 50PIV	.26	NAS206P 50PIV	.37
NAS006Q 100PIV	.28	NAS106Q 100PIV	.30	NAS206Q 100PIV	.42
NAS006R 200PIV	.31	NAS106R 200PIV	.36	NAS206R 100PIV	.50
NAS006S 400PIV	.40	NAS106S 400PIV	.57	NAS206S 100PIV	.77
NAS006T 600PIV	.52	NAS106S 400PIV	.57	NAS206S 100PIV	.77
8 AMP ISOLATED TAB		16 AMP ISOLATED TAB			
NAS306P 50PIV	.41	NAS806P 50PIV	.50		
NAS306Q 100PIV	.47	NAS806Q 100PIV	.58		
NAS306R 200PIV	.59	NAS806R 200PIV	.73		
NAS306S 400PIV	.85	NAS806S 400PIV	1.15		

Quantity prices on application, S.A.E.

ME 55 Integrated circuit timer 8 pin dill only 62p.
MULTITURN POTENTIOMETERS EX. EQUIPMENT RELCON 1k + or - % good condition 25p.
2 1/2 in 75 ohms or 40 ohm miniature speaker 45p each.

Please add 8% VAT to all listed prices. Postage & packing 15p per order. Send 13p for latest catalogue. Callers welcome.

Crescent Quality Components

BARGAIN CAPACITOR 2,200MFD at 63v. DC w/kg.
Size = 2" x 1 1/2" diameter. Tag ended. All new and unused. Our price 35p.

STEREO/MONO HEADPHONE VOLUME CONTROL BOX



Plug stereo phones into this control box and you then incorporate a right and left hand volume control and a stereo/monoswitch. Complete with stereo jack plug and 2m cable. A bargain at £1.

TWO WAY STEREO ADAPTOR

Stereo Jack plug to two stereo free sockets, complete with 110mm cable. For connecting two stereo inputs into one.

A bargain at 65p.



LIGHT EMITTING DIODES

Til 209 (Red) With Clip 22p each
Til 209 (Green) With Clip 35p each
Til 209 (Yellow) With Clip 90p each
Med 500 T092 Type 16p each

LED READOUTS

Litronix
DL707 3 Character 14 Pin Dtl. £2.00
DL701 as above but ± 1 £2.00
DL747 6 Character £2.62

Minitron

3015 7 Segment 16 Pin Dtl £1.18
3015G as above but ± 1 £1.18

Clock Chip

CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet £8.95
Circuits and Information Sheet 15p
Lit 704 Led Display for above £1.35
Or 4 for £5.25

WAFER SWITCHES

1 Pole 12 Way
2 Pole 2 Way
2 Pole 3 Way
2 Pole 4 Way
2 Pole 6 Way
2 Pole 4 Way
4 Pole 3 Way
22p each



POTENTIOMETERS

All types 1" and less diameter
Singles
5K Log or 5K
10K Lin Less 10K
25K Switch 25K
50K 15p each 50K
100K 100K
250K Double 250K
500K Pole 500K
1M Switch 1M
2M 30p each 2M

PRE SETS

Sub Miniature Skeleton Type 0-1 Watt Horizontal Mounting 100, 250 and 500 ohm, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, and 1M ohm 6p each

MAINS TRANSFORMERS

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high
Fixing centres: 2 5/32"
TR1 20-0-20v 100 m/a
TR2 12-0-12 v 100 m/a All
TR3 9-0-9 v 100 m/a 240 Volt
TR4 6-0-6 v 100 m/a Primary
TR5 3-0-3 v 100 m/a
Our Price £1.23 each

200/250v MAINS RELAY

Heavy duty contacts 2-500 ohm coil. All new and unused D.P.D.T. mains relays 50p, Carr. Free. Special quantity £40 per 100 off.

MINIATURE RELAYS

Brand new range of British made Relays. Size 1 1/2" x 1" x 1/2". All two changeovers with 250v 1.5A contacts and suitable for fitting on 1m Veroboard.

Type	Volts	Current	Ohms	All
27/A	12v	17M/A	700	
21/A	12v	28M/A	430	£1.30
12/A	6v	33M/A	185	each

DOUGLAS TRANSFORMERS

All types are standard 240 volt primary. MT 102 ct. 0 = 19 = 25 = 33 = 40 = 50 at 500M/A

Model	Price
MT237cs 20-0-20 at 150M/A	£2.00 each
MT241cs 20-0-20 at 30M/A	£1.25
MT240cs 15-0-15 at 30M/A	£1.05
MT239cs 12-0-12 at 50M/A	£1.05
MT238cs 3-0-3 at 200M/A	£1.05

POWER PACKS

PP1 Switched 3 - 6 - 7 1/2 - 9 volt 400M/A Transistor and Zener Stabilised On/Off Switch and Polarity Reversal Switch, in a black metal case £5.25 each.
PP2 Switched 6 - 7 1/2 - 9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders £2.75 each (philips type £3.00).
PP3 Car converter. From 12v Pos. or Neg. to = 6 - 7 1/2 - 9 volt. Easy to fit and transistor regulated £2.50 each



VEROBOARD

Size	Price	Plain	Price
2 1/2" x 3 1/2"	32p	15	15p
2 1/2" x 5"	34p	34p	18p
3 1/2" x 3 1/2"	34p	34p	
3 1/2" x 5"	39p	45p	
17" x 2 1/2"	1.06p	77p	60p
17" x 3 1/2"	1.45p	1.16p	75p
17" x 5"	1.85p		1.10p

Pin insertion tool 72p
Spot face cutter 52p
Pkt. 36 pins (state 1 or 15) 25p

LOUDSPEAKERS

Model	Price
2 1/2" 8 ohm	50p
2 1/2" 40 ohm	50p
2 1/2" 80 ohm	50p
5" 8 ohm ceramic	£1.25
6 1/2" 8 ohm dual cone ceramic	£2.50
10" 8 ohm dual cone ceramic	£3.75
7" x 4" 8 ohm ceramic	£1.60
8" x 5" 8 ohm Permanent Magnet	£1.60



***EMI 13" x 8" 450 Kit**

3 - 8 - 15 ohm £4.10

*EMI 13" x 8" 350 Kit 8 ohm £7.50


FANE ULTRA HIGH POWER LOUDSPEAKERS

Model	Price
*Pop 25/2 30 watt 150 ohm 12"	£8.29
*Pop 55 60 watt 8/15 ohm 12"	£14.50
*Pop 50 50 watt 15 ohm 12"	£11.99
*Pop 60 60 watt 8/15 ohm 15"	£15.70
*Pop 100 100 watt 8/15 ohm 18"	£28.70

* Carr. on L/S over 13 x 8 and 12" 50p per L/S.

MAINS KEYNECTOR

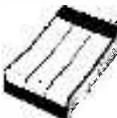Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for beach, garage demonstrations, etc. Multi connections can be made (max. load 13A fused). £3.25p.



ALUMINIUM BOXES

Metal project boxes give your work a professional finish

Model	L	W	H	Price
AB7	2 1/2"	5 1/2"	1 1/2"	54p
AB8	4"	4"	1 1/2"	63p
AB9	4"	2 1/2"	1 1/2"	54p
AB10	4"	5 1/2"	1 1/2"	63p
AB11	4"	2 1/2"	2"	54p
AB12	3"	2"	1"	45p
AB13	6"	4"	2"	69p
AB14	7"	5"	2 1/2"	84p
AB15	8"	6"	3"	99p
AB16	10"	7"	3"	£1.35
AB17	10"	4 1/2"	3"	£1.02
AB18	12"	5"	3"	£1.20
AB19	12"	8"	3"	£1.50

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1005 = 105mm x 73mm x 45mm = 51p
1006 = 150mm x 75mm x 47mm = 66p
1007 = 184mm x 124mm x 60mm = 96p
1021 = 106mm x 74mm x 45mm (sloping front) = 50p


BARGAIN BOARDS

Components galore for the experimenter Ex Computer boards with Resistors, Capacitors and useful Transistors—at least 4 transistors per board. Five boards £1.00.

CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.

ME6	= 0 to 50 micro amp Full Scale
ME7	= 0 to 100 micro amp Full Scale
ME8	= 0 to 500 micro amp Full Scale
ME9	= 0 to 1 m/a Full Scale
ME10	= 0 to 5 m/a Full Scale
ME11	= 0 to 10 m/a Full Scale
ME12	= 0 to 50 m/a Full Scale
ME13	= 0 to 100 m/a Full Scale
ME14	= 0 to 500 m/a Full Scale
ME15	= 0 to 1 amp Full Scale
ME16	= 0 to 50 volts A.C. Scale
ME17	= 0 to 300 volts A.C. Full Scale
ME18	= "S" Meter
ME19	= "VU" Meter

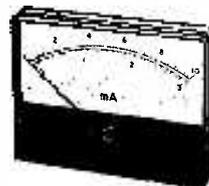

OUR PRICE £3.00

Q-MAX SHEET METAL PUNCHES

The easiest and quickest way of punching holes in sheet metal (up to 1.625mm Mild Steel)

Model	Price	Key
DECON DALO 38PC	68p	"T" 6p
ETCH RESIST PEN	75p	
The Decon Dalco 33PC is a unique instrument for the professional and amateur electronics engineer, enabling him to prepare in minutes a perfect printed circuit board	83p	"A" 6p
OUR PRICE 80p	83p	
ADD LUXURY TO YOUR CAR with a motor driven car aerial	83p	
SPEC: ★ 5 section	88p	
★ extended length 100cm	88p	
★ Length under fender 40cm	90p	"B" 10p
★ Cable length 120cm	90p	
Supplied complete with fixing bracket and control switch	98p	"C" 13p
OUR PRICE 80p	98p	
1 1/2" SQUARE PUNCH complete with key	£1.03	
1 1/2" SQUARE PUNCH complete with key	£1.05	"B" 10p
1 1/2" SQUARE PUNCH complete with key	£1.10	
1 1/2" SQUARE PUNCH complete with key	£1.25	"B" 10p
1 1/2" SQUARE PUNCH complete with key	£1.43	
1 1/2" SQUARE PUNCH complete with key	£1.50	"B" 10p
1 1/2" SQUARE PUNCH complete with key	£2.05	
1 1/2" SQUARE PUNCH complete with key	£2.30	"B" 10p
1 1/2" SQUARE PUNCH complete with key	£4.10	
1 1/2" SQUARE PUNCH complete with key	£5.25	"B" 10p
1 1/2" SQUARE PUNCH complete with key	£8.10	

1" SQUARE PUNCH complete with key £2.10

STOP PRESS

BHA0002	15 watt Amp Module	£2.50
NE555	Timer I.C.	78p
MC1310P	Stereo Decoder I.C.	£2.00
7805	Regulator	£1.49
TIP 29A		55p
TIP 30A		63p
BC107		10p
BC 108		10p
BC109		10p



I.C. SOCKETS

D.L.L.	
8 pin	
14 pin	14p
16 pin	

BARGAIN TRANSFORMERS

12-0-12 volt 500m/a
240 volt primary transformer bargain. approx size = 60mm x 40mm x 50mm fixing centres = 75mm
Our Price = £1.20.

18 volt 500m/a
240 volt tapped 120 volt with screen. approx size = 60mm x 40mm x 50mm fixing centres = 75mm
Our Price = £1.00.

BARGAIN BOX

Loud buzzer mounted in a metal box complete with two U2 battery size holder. Designed and can be used as a fire alarm but is ideal as a door or Morse code practice buzzer. Approx. size = 2 1/2" x 6 1/2" x 1 1/2".
OUR PRICE—50p.

U.K. POSTAGE 15p UNLESS OTHERWISE STATED

V.A.T. Please add 8% to all Totals

CRESCENT RADIO LTD.

All mail to 11 MAYES ROAD, WOOD GREEN, LONDON N22 6TL
Phone: 01-888 3206

Callers Welcome at 15 Mayes Road & 13 South Mall, Edmonton N9.


If you construct You should own one.

CRESCENT CATALOGUE
Price 20p.

R T V C

FOR AUDIO AT A BUDGET

COMPLETE STEREO SYSTEM System 1. £51-00

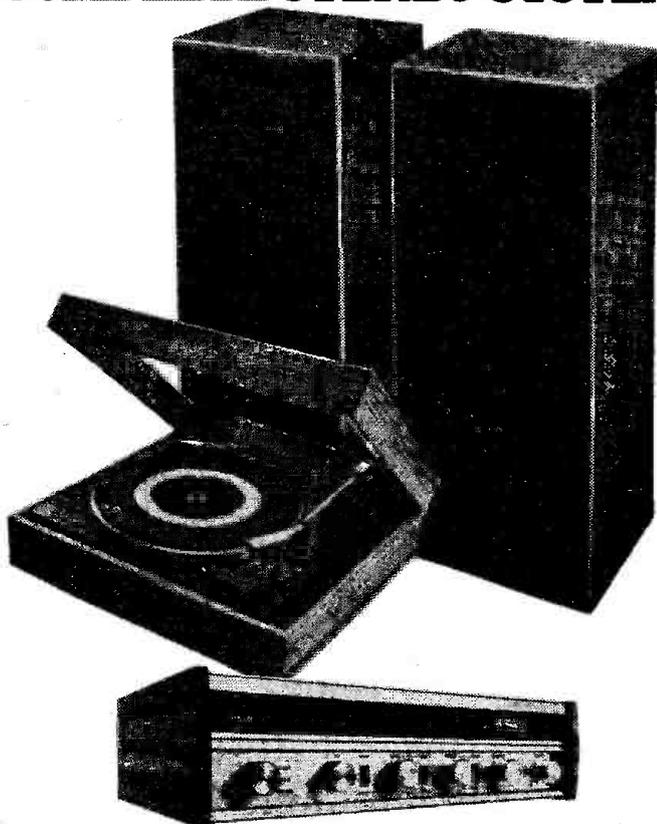

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.
System 1 includes:
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.
Specification
 20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within ± 1 dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics:* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".
Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.
Two Duo Type II matched speakers - Enclosure size approx. 17 $\frac{1}{2}$ " x 10 $\frac{3}{4}$ " x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter, 10 watts handling.

Complete System £51-00

System 2. £69-00

Viscount III amplifier (As System 1)
Garrard SP 25 Mk III deck (As System 1)
Two Duo Type III matched speakers - Enclosure size approx. 127" x 13" x 11 $\frac{1}{2}$ "
 Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £69-00

PRICES: SYSTEM 1


Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£59.20

Available complete for only: **£51-00**
 + £3.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£84.20

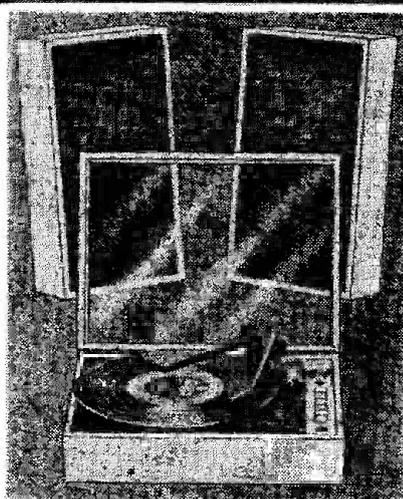Available complete for only: **£69-00**
 + £4.00 p & p



STEREO 21 * QUALITY SOUND FOR LESS THAN £20-00

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes: - BSR 3 speed deck, automatic, manual facilities together with stereo cartridge, Two speakers with cabinets.
Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.
Specifications: For the technically minded: -
 Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. 15 $\frac{1}{2}$ " x 8" x 4". Complete deck and cover in closed position approx. 15 $\frac{1}{2}$ " x 12" x 6".
Complete only £19.55 + £1.60 p & p. Extras if required. Optional Diamond Stylus £1.37.
 Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance, **£3.85.**



BUILD YOUR OWN * STEREO AMPLIFIER



For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only. **£7-64 + 55p. p & p**

8 TRACK HOME CARTRIDGE PLAYER *



Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. **Yours for only £11.95 + 90p p & p.**

PORTABLE DISCO CONSOLE

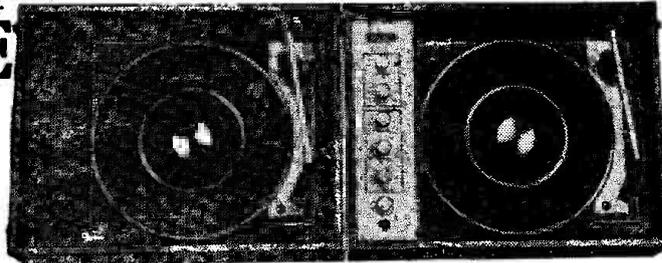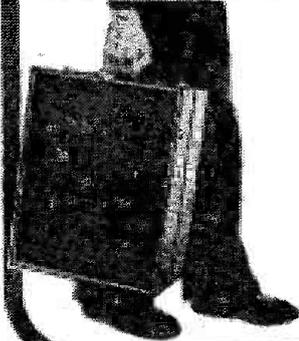

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges. The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record. The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

TECHNICAL SPECIFICATION:

Pre-amp - Output - 200mV.
 Auxiliary inputs - 200mV and 750mV into 1 meg.
 Mic input - 6mV into 100K. 240 volt operation.
Turntables capacity - 7", 10" or 12" records.
Rumble, wow and flutter -
 Rumble Better than -35dB. Wow Better than 0.2%.
 Flutter Better than 0.06% (Gaumont kalee meter).
Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.
Console size -
 Unit Closed - 17 3/4" x 13 3/4" x 8 3/4" (approx.)
 Unit Open - 35 3/4" x 13 3/4" x 4 3/4" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging diamond spun control knobs with matching control panel.

Yours for only £45.00 + £3.50 P. & P.

EMI SPEAKERS AT FANTASTIC REDUCTIONS



20 WATT SPEAKER SYSTEM *
 System consists of a 13" x 8" (approx) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components.


Technical Specification:
Bass Unit
 Flux density-100 K. speech coil-1 1/2", Cone. Triple laminated paper with P.V.C. surround.
Mid Range Unit
 Flux density-33K. speech coil-1" with parasitic tweeter.
Power Handling
 20 watts R.M.S., impedance - 8 ohms, frequency response - 20 Hz to 18,000 Hz.

OUR PRICE
£6.60. Complete
 + 90p p & p.



15" 14A/780 BASS UNIT
 Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 39 Hz. Flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

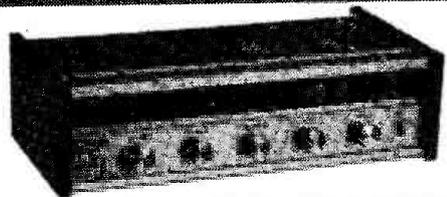Recommended retail price £40.80.
OUR PRICE £18.70
 + £1.50 p & p.




DISCO AMPLIFIER *

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.
Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).
Inputs *4 electrically mixed inputs. *3 individual mixing controls.
 *Separate bass and treble controls common to all 4 inputs.
 *Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry.
 *Attractive styling.

INPUT SENSITIVITIES -Input - 1.) Crystal mic, guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).
 -Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2". **£15.00 + 60p. p & p**

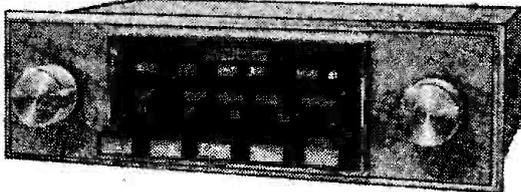PUSH BUTTON CAR RADIO KIT * The Tourist II



NO SOLDERING REQUIRED!

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board. **£7.70 + 55p p & p**

Technical specification: (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth. (2) **Integrated circuit** output stage, pre-built three stage IF Module. **Controls** volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.
 Size chassis 7" wide, 2" high and 4 3/4" deep approx

Speaker including baffle and fixing strip **£1.65+23p.p&p.**


Car Aerial Recommended - fully retractable **£1.37+20p.p & p**

The Tourist I Kit For the experienced constructor If you can solder on a printed circuit board you can build this model.

Same technical specification as Tourist II **Price £6.60 + 55p p & p.**



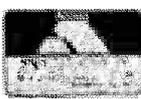DO NOT SEND CARD
 Just write your order giving your credit card number



Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Nov. 1974 and subject to change without notice. All prices include V.A.T. at 8% rate.

Personal Shoppers **Edgware Road:** 9a.m.-5.30p.m. Half day Thurs. **Acton:** 9.30a.m.-5p.m. Closed all day Wed.



Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG
323 Edgware Road, London W2

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

5p for 1 Valve.
Each additional Valve add 2p.

DM70	0-61	ECL83	0-66	GY501	1-18	PL82	0-48	30C1/PCF80	0-54
DY51	0-80	ECL86	0-64	GZ34	0-80	PL83	1-04	30C15/	
DY86/7	0-41	EF80	0-42	PC88	0-95	PL84	0-68	PCF800	1-01
DY802	0-46	EF83	0-88	PC97	0-42	PL50	0-90	80C17	1-01
EABCS0	1-08	EF84	0-42	PC900	0-57	PL508	1-24	30C18/	
EB91	0-64	EF86	1-16	PC884	0-54	PL509	1-56	PCF805	1-00
EB91	0-64	EF86	1-16	PC885	0-80	PL802	1-40	30F6/FF818	
EB91	0-64	EF86	1-16	PC888	0-66	PL802	1-40		1-08
EB91	0-64	EF86	1-16	PC889	0-64	PL802	1-40		
EB91	0-64	EF86	1-16	PC890	0-64	PL802	1-40		
EB91	0-64	EF86	1-16	PC891	0-64	PL802	1-40		
EB91	0-64	EF86	1-16	PC1000	0-64	PL802	1-40		

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.


AZ1	0-75	EF39	1-25	N78	3-50	PY500	1-10	6F28	0-75
AZ31	0-80	EF80	0-85	OA2	0-45	6J5M	0-50	6J5M	0-65
CBL31	1-40	EF85	0-45	OB2	0-45	6J5G	0-55	6J5G	0-80
CL33	1-50	EF86	0-45	OC3	0-65	6J6	0-55	6J6	0-85
CY31	0-60	EF89	0-35	PC88	0-65	6J7G	0-85	6J7G	0-80
DAF91	0-40	EF91	0-40	PC97	0-55	6J7M	0-85	6J7M	0-85
DAF96	0-60	EF92	0-50	PC900	0-55	6K6GT	0-80	6K6GT	0-80
DCC90	1-35	EF95	0-45	PC884	0-45	6K7G	0-85	6K7G	0-85
DF91	0-40	EF98	0-80	PC888	0-62	6K7M	0-85	6K7M	0-85
DF96	0-60	EF183	0-40	PC889	0-55	6K8G	0-45	6K8G	0-45
DK91	0-50	EF184	0-40	PC890	0-55	6K8M	0-70	6K8M	0-70
DK92	1-00	EL32	0-60	PC891	0-40	6K9S	1-00	6K9S	1-00
DK96	0-75	EL33	2-00	PC892	0-42	6L6G	0-55	6L6G	0-55
DL92	0-50	EL34	0-70	PC893	0-65	6Q7G	0-40	6Q7G	0-40
DL94	0-48	EL36	0-60	PC894	0-60	6Q7M	0-60	6Q7M	0-60
DL96	0-55	EL37	2-50	PC895	0-55	6R7G	0-80	6R7G	0-80
DY86	0-42	EL41	0-90	PC896	0-80	6S7G	1-30		



for fast easy reliable soldering
EASY TO USE DISPENSERS AND REELS
IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive P.B.S. instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser

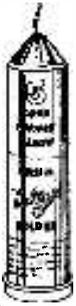

A coil of Ersin Multicore Savbit Solder in a dispenser 7ft 6 in of 18 s.w.g. (2.2mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy, 63ft of 18 s.w.g. (19.2 metres of 1.22mm)



Size 12 £1.72

ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.



Size 4 £2.32

Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.



Size 10 £1.44

For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.



Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER



Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B, 70p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited, Prices shown are recommended retail excluding V.A.T.
 Sole U.K. Sales Concessaires P.O. Box 78, 100, Hamstead, Essex, SS2 7EP. From Electrical and Hardware Stores. A multi-branch, send 10p P&P. Prices and specifications subject to change without notice.

TECHNOMATIC LTD. 54 SANDHURST ROAD, LONDON NW7

AC128 11p	BFY52 15p	Rectifiers 5p	BRIDGE RECTIFIERS
AC127 11p	MPP103 81p	IN4001 6p	50v 100v 400v 600v
AC128 11p	MPP104 81p	IN4004 7p	1A 20p 21p 24p 25p
AC174 11p	MPP105 81p	IN4007 7p	2A 30p 35p 45p 45p
AC187 12p	OC26 47p	BY127 12p	4A 45p 45p 60p 70p
AC188 11p	OC28 48p	Signal Diodes	6A — 55p 75p 100p
AC145 4p	OC35 48p	IN914 3p	
AC151 3p	OC44 11p	IN4148 3p	SCR-THYRISTORS
AD103 3p	OC71 11p	OA91 8p	50v 100v 400v 600v
AF115 13p	TIP2955 70p	OA200 8p	1A 42p 48p 60p 78p
AF117 13p	TIS43 25p	OA200 8p	2A 48p 48p 78p 86p
BC107 8p	4706 18p	OA202 8p	4A — 60p 84p 114p
BC108 8p	4N780 18p	Zeners	1A — 78p 96p 120p
BC109 10p	2N3645 32p	400MW 8p	
BC169 11p	2N2905 18p	1.3W 13p	
BC172 10p	2N2938 8p	1.5W 25p	TRIACS
BU190 10p	2N3053 18p	Other Diodes Tun'1 3A — 50v 400v 500v	85p 99p 120p
BU192 11p	2N3068 40p	ABY11 50p	— 88p 120p 150p
BU212 11p	2N3702 11p	LED 10A — 109p 154p 165p	— 145p 180p 200p
BU213 10p	2N3703 11p	TIL209 18p	
BU214 12p	2N3704 11p	DIL SOCKETS	
BU215 4p	2N3705 10p	8 pin 18p; 14 pin 18p; 16 pin 15p	
BU216 4p	2N3706 10p	Mica Washers + 2 Bushes (TO3 or TO66) 6p	
BU217 15p	2N3707 11p		
BU218 15p	2N3819 20p		

LINEAR ICs	TTL SERIES	MOSFETS
555 55p 536 22-25	7400 14p 7449 9p	2N140 85p
556 120p 8038 23-00	7401 18p 7473 36p	2N141 90p
567 290p CA3046 55p	7402 18p 7474 34p	40603 58p
709 28p MC1310 22-40	7404 18p 7475 35p	
723 55p MC1312 22-20	7408 20p 7476 37p	
741 28p MFC4000 40p	7410 15p 7489 380p	
747 70p TBA800 21-00	7413 90p 7490 25p	C-MOS
748 38p TBA810 21-25	7420 15p 7493 55p	CD4001AE 50p
7805 21-40 TBA820 80p	7430 15p 7497 45p	CD4016AE 21-20
7812 21-40 ZN414 21-10	7441 75p 7498 34p	CD4017AE 23-00
Data sheets on above ICs 10p ea.	7447 95p 7499 85p	CD4047AE 21-85

FOR MORE SELECTION PLEASE REFER TO OUR ADVERTISEMENT IN P.E. & WW

Complete Semiconductor Kits (inc. DIL Sockets for various projects available e.g. Tele-tennis Tri-colour Unit PE Minisonic Miniature battery-operated Sound Synthesiser Rhythm Generator Novel Transistor Tester For data sheets & prices, please send S.A.E. +25p.	SPECIAL PRICES
	555 55p
	723 55p
	741 28p
	CA3046 55p
	MC1310P 2-40
	MC1312P 2-20

Minimum Order £2. All prices exclusive of VAT. P. & P. 10p orders below £5. Trade, Colleges enquiries welcome.

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept W.C. 15 P.O. Box 156, Jersey, C.I.
 Please send FREE BROCHURE to

NAME Block
 ADDRESS Caps.
 Please

BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL



TRAMPUS ELECTRONICS LTD

58-60 GROVE ROAD,
WINDSOR, BERKS.

FAST SERVICE SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.

CATALOGUE/LIST FREE SEND S.A.E.

Digital Displays



MINITRON 3015F
0-9DP £1.15 ea
LED 0.3" digit
0-9DP £1.49 ea
JUMBO LED 0.6"
0-9DP £2.25 ea
LIQUID CRYSTAL
6 digit £18

LEDS 14p.

MINI PIN SOURCE OR RED DIFFUSE
LEDS.209 STYLE.NO CLIP. 14p ea
TIL209 RED LED & CLIP 17p ea
BIG 1" RED LED & CLIP 18p ea
ORANGE & GREEN LEADS:
MINI 25P ea.BIG & CLIP 33P ea
INFRA RED LED £1.2NS777 33p.
PS12 PHOTO IC/amp/switch £1.

DIGITAL CLOCK

MOS INTEGRATED CIRCUITS.
AY51224 4 DIGIT CLOCK supplied
with 14pin socket & data £4.25
MMS311/14 6 DIGIT CLOCK with
28 pin socket & data £7.50
3DIGIT DVM AY53500 £7.50
4DIGIT COUNTER/DRIVER £7.50

CASSETTE mechanics £12.50

STEREO CASSETTE MECHANISM.
As used in imported types
costing £100.Only requires a
case & electronics.Heads
supplied.Send for data 15p.

IC's & Semiconductors

722 OPA £8
703 RF/IF £5
709 TO99 £2
729 DIL 14 £2
710 DIL 14 £2
720 Radio £1.39
723 Regulator £2
741 TO99 29p
741 DIL8 31p
741 DIL14 31p
747 Dual 741 89p
748 DIL 8 36p
1505 IC A/D
Converter £7

7805 IA5V £1.59
7808 IA8V £1.69
7812 IA12V £1.69
7815 IA15V £1.69
76009 IW AF 75p
76013 6W AF £1.39
8038 Sig Gen £3

CA3046 69p
LM301 OPA 49p
LM307 OPA 49p
LM308 HiBoPa 95p
LM309K Reg. £2.29
LM371 RF/IF £2
LM372N AF/IF £2
LM373 £3
LM377 2x2W £2.69
LM380 2W AF 99p
LM381 2xpre. £2
LM382 amp £2
LM3900 4xOPA 69p

MC1303 £1.20
MC1306 49p
MC1310 & LED £2.69
MC1312 Sqamp £2.50
MC1330 69p
MC1339 £1
MC1350 55p
MC1351 71p
MC1352 71p
MC1357 £1
MC1358 £1
MC1375 £1.25

MFC4020 IW AF 35p
MFC4060 54p
MFC6030 52p
MFC6040 30p
MFC8010 £1.10
MFC8040 £1
NE531 35V/us £2
NE536 FET OPA £2
NE540 Driver £1
NE546 AM Rxl.50
NE550 2v ref 79p

NE555 TIMER 67p
NE556 Dual £1.30
NE560 PLL £3.15
NE561 PLL £3.15
NE562 PLL £3.19
NE565 PLL £2.69
NE566 Gen £2.49
NE567 code £2.69
SN72709 709 29p
SN72741 741 31p
SN72748 748 36p
SN76131 £1.20
SN76660 FMIF £1
SN76611 IF £1.25
TAD 100 & IF £2
ZN400E £3
ZN402T £1.75
ZN403 Servo £2.50
ZN414 AM Rxl.09

7400 etc gates 16p
7413 schmitt 31p
7447 driver £1.09
7470/72 32p
7475/74/76 39p
7475 48p
7490 Counter 63p
7492 Counter 69p
74121 mono 45p
74141 range 83p
Full range in Cat..

SPECIAL OFFERS

741 29p MFC4000 35p
555 67p ZN414 £1.09
BC107,BC108,BC109 9p ea
2N3055 39p Three fo. £1
115W/TO3 or 90W plastic
2N3819E 16p 2N3053 17p
BFY50/51/52/53 all 18p
1A50Vrect 4p ea IN914 4p

Price each:-

AC127/128 16p TIP2955 90p
AC187/188 19p TIP3055 55p
AD161/162 35p TIS43 UJT 25p
BC107/8/9 9p IN4001 4p
BC132/4/7 18p IN4004 6p
BC147/8/9 10p IN4148/914 4p
BC157/8/9 12p 2N697 13p
BC167/8/9 12p 2N706/8 10p
BC177/8/9 18p 2N2646 49p
BC182/3/4*11p 2N2904/5 20p
BC212/3/4*12p 2N2926royg 9p
*A or L 2N3053 17p
BCY70/1/2 15p 2N3055 39p
BD151/2 39p 2N3614 49p
BFY50/1/2 18p 2N3702/3 9p
BFY53 17p 2N3704/5 10p
BSX20 12p 2N3706/7 9p
MJE2955 95p 2N3708/9 8p
MJE3055 62p 2N3710/11 9p
MPU131put 49p 2N3563/64 16p
OAP1 8p 2N3566/67 16p
TIP29A 48p 2N3638 16p
TIP30A 57p 2N3641/2 16p
TIP31A 61p 2N3819E 16p
TIP32A 73p 2N3832E 17p
TIP41A 78p 2N3904/6 14p
TIP42A 89p 2N4249 16p

BZY88 400mW TAG 1/400 55p
ZENERs 9p C107D1 SCR 55p
BRIDGE RECT 4A/400V
1A 50V 20p
GAS SENSOR £2 SC146D TRIAC
GAS KIT £5 10A 400V 75p

vero



VERO PINSx36 25p
COPPER CLAD VEROBOARD 0.1"
2 1/2x5" 27p. 2 1/2x3 1/2" 24p. 3 1/2x3 1/2" 27p.
3 1/2x5" 29p. 3 1/2x1 7" £1.50
DIL IC's BOARDS 6x4 1/2" £1.50
24 way edge connector 60p
36way 90p. PLAIN 3 1/2"x1 7" £1
FACE CUTTER 45p. FEC ETCHANT

DAlopen69p

PRINTED CIRCUIT BOARD KIT £1.69
COPPER BOARD 6x4" 40p.
DESOLDER BRAID reel 59p
HEAT SINKS
5E/TO5 & 18E/TO18 5p ea.
TV4 12p. TV3/TO3 16p. 4YI/TO3 29p.

CAPACITORS

22pf to 0.1uf 4p ea. ELECTROLYTIC
25V 2/10/50/100uf 6p. 1000uf 20p
PRESETS VERT: 5p. RESISTORS 5% 12p

POTS AB or EGIN

ROTARY: 12p. SWITCH 13p. DUAL 38p.
SLIDERS: SINGLE 26p. DOUBLE 48p.
SWITCHES: SPST 18p. DPDT 25p.
MINI 1": SPST 39p. PUSH 39p.

BENCH POWER SUPPLY 3-12V 15p.
DIN PLUGS all 13p ea. Sockets 9p
TRANSFORMERS 1A 6/12V £1.34
BHA 0002 MODULE 15WATT AMP £5
EA1000 4W AF MODULE £2.49
8W/12V FLUORESCENT LIGHT £3.

Oil sockets


PROFESSIONAL
GOLD PLATED
& GREY NYLON.
8, 14 or 16 PIN
ONLY 15p each.

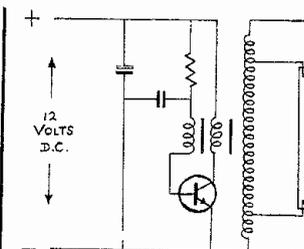G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

12 VOLT FLUORESCENT LIGHTING



INVERTER TRANSFORMERS 13/15 WATT 70p
(CIRCUIT INCLUDED)
"CURRENT ECONOMY" TRANSISTOR (600 ma.) 50p
"MAXIMUM LIGHT" TRANSISTOR (1.3A) 50p
RESISTORS/CAPACITORS TO SUIT 15p
LAMP HOLDERS (LONG LEAD) 30p PAIR
(SHORT LEAD) 20p PAIR
WHITE ENAMEL CASE, 18" or 21" (Postage 30p) 70p
TUBE, 18"-15 WATT or 21"-13 WATT 45p
(NOTE:- TUBE ONLY SUPPLIED IF CASE ORDERED,
TO PREVENT POSTAL DAMAGE)
13 WATT FITTING READY BUILT AND TESTED—
INCLUDING TUBE (Postage 30p) £3.75
Post/Packing 25p per order except where shown



NEW IMPROVED CIRCUIT!

Drives 21" 13 watt
18" 15 watt
or adaptable for
2 x 12" 8 watt

BRAN TUB !!!

- ★ Resistors, Wire-wound and Carbon
- ★ Capacitors, Silver-mica, Paper, Ceramic, Polyester and Electrolytic
- ★ Controls, Volume, Pre-set, Carbon, Wire
- ★ Diodes, Silicon, Germanium, Zenér
- ★ Transistors, Silicon, Germanium

All the above are new and unused stock.

We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic, unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!

To make things even more interesting—TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!

And the price that we are asking? Only £1.50 including both postage and VAT!

Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat!

£1 100 +- WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 25p PACK No. 1

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

POSTAGE 25p PACK No. 2

£1 1 VERO-BOARD CUTTER
5 1/2 in. x 1 in. x 15 BOARDS
50 SQ. INS. "ODD PIECES"
VERO

POSTAGE 25p PACK No. 3

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

POSTAGE 25p PACK No. 4

£1 20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108 ETC.

POSTAGE 25p PACK No. 5

£1 1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT

POSTAGE 25p PACK No. 6

£1 6 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS
& CAPACITORS

POSTAGE 30p PACK No. 7

£1 100 RESISTORS
100 CAPACITORS
(ASSORTED TYPES)

POSTAGE 25p PACK No. 8

NOTE:- ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)

SAXON

Money saving high performance audio equipment DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £5.45 Carriage free

35W RMS 25-50V
7 transistors, 7 diodes


SA50 £6.90 Carriage free

50W RMS 25-65V
7 transistors, 7 diodes

SA100 £12.50 Carriage free

100W RMS 45-70V
10 transistors, 7 diodes

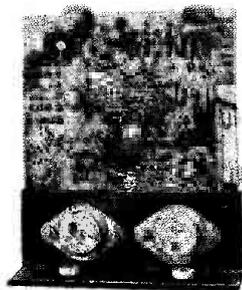- ★ 25Hz-25kHz
- ★ 0.2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4-16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components



THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED

PU45 Suits 2 SA35 or 1 SA50 (4 ohm) **£5.45** Carriage 30p

PU70 Suits 2 SA50 (8 ohm) or 2 SA100 **£8.45** Carriage 40p

STABILISED

PS45 Suits 2 SA35 or 2 SA50 (4 ohm) **£4.45** Carriage free

MT45 Transformer for above **£3.50** Carriage 30p

PS70 Suits 2 SA100 **£5.45** Carriage free

MT70 Transformer for above **£4.90** Carriage 40p


N.B. PS70 is not suitable for the SA50

120 watt module complete with built-in supply—extra heavy duty £22.50 Carr. 60p

Mk II STEREO DISCO MIXER £22.50

Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, h/phone select. vol, Mains. Size 17½in x 3in x 4in deep.

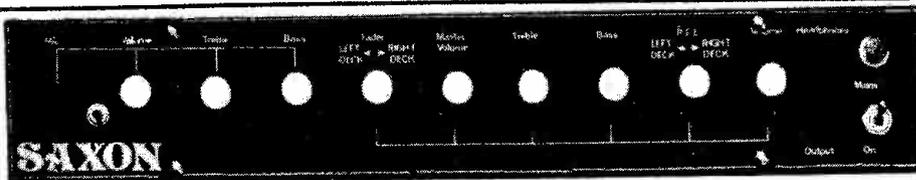

DISCO MODULE £9.50

Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50

Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.50 Carr. free

Recently reduced in price due to increasing sales, handles 1kW. Full wave operation.

ADD 8% VAT TO ALL ORDERS

MULTI-PURPOSE MIXERS


M4HL

£19.50 Carr. 50p

M6HL

£29.50 Carr. 50p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

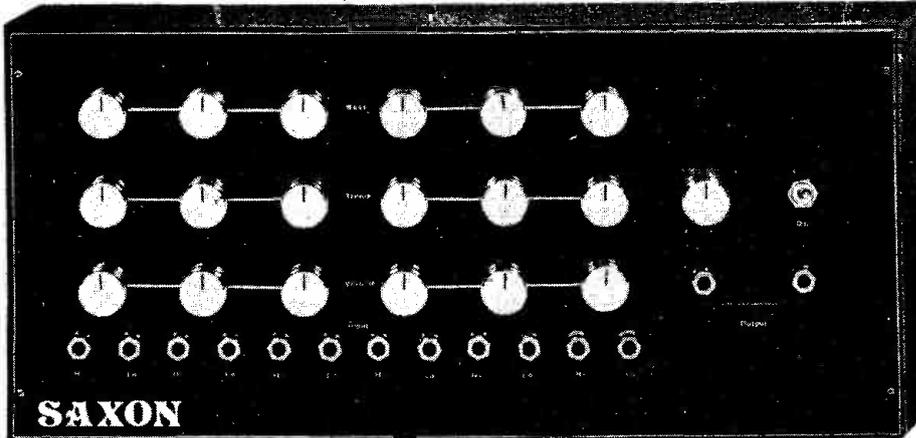

VA30 CHANNEL MODULE £3.50 Carr. free

This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)


SAXON CSE 100

COMPLETE AMPLIFIER


£34.90

Carr. free

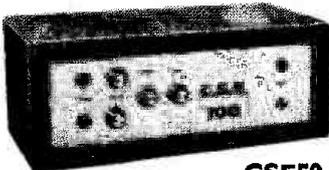100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE50 £29.50 Carr. free

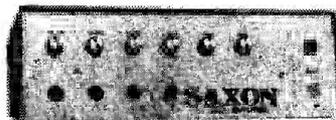

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output from twin, loudspeaker sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

SAXON 100 COMPLETE AMPLIFIER

£53.00

Carr. free

SAXON 50

£37.50

Carr. free

CALLERS AND MAIL ORDER

SAXON ENTERTAINMENTS LIMITED

327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)


SHOP HOURS: 9 a.m.—5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m. 24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 10p FOR OUR 26 PAGE MANUAL—full circuits & details.


TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.

Please send S.A.E. with all enquiries.

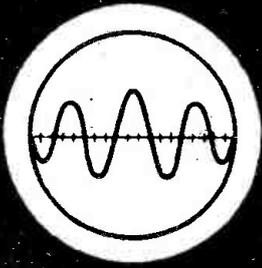VAT @ 8% must be added to all orders including carr. charges.




TUAC

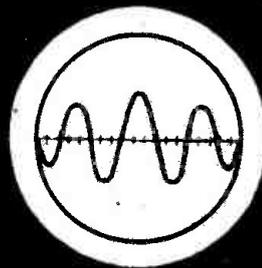

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD · LONDON SW17 9PG 01-672 3137/9080

TUAC DISCOTHEQUE MIXER WITH AUTO FADE

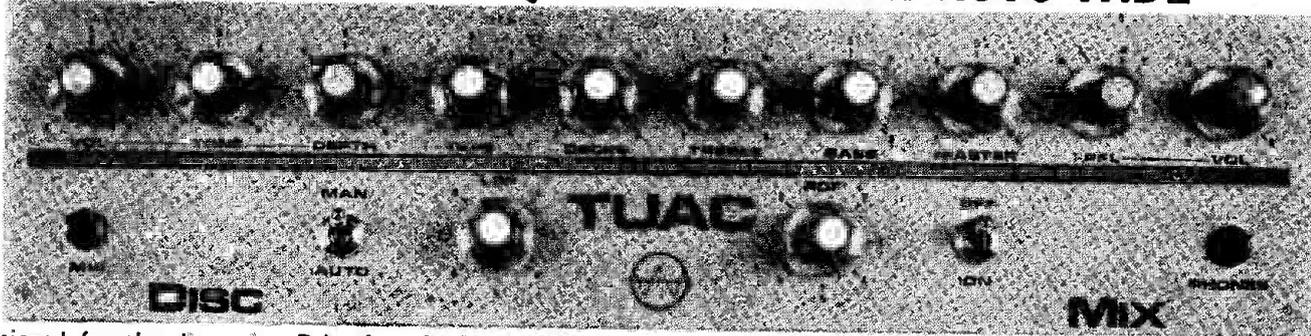

Designed for the discerning D.J. of professional standard Offering a vast variety of functions. Controls; Mic Vol; Tone, over-ride depth; auto/ Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1m Ω ; Deck Tone Controls—Treble +20 - 10dB at 12kHz. Bass +22 - 15dB at 40Hz; Mic input—200 ohms upwards. 2mV into 10k Ω ; Mic Tone Control—Total Variation Treble 15dB. Total Variation Bass 10dB; Tape input —30mV into 47k Ω ; Power Requirements—30-45 volts at 100mA.

£26.50

PANEL SIZE
18 x 4½ in.
DEPTH 3in.

HOW TO ORDER BY POST

Make cheques/P.O.'s payable to TUAC LTD (P.W.). OR QUOTE ACCESS/BARCLAYCARD No. and post to TUAC LTD (P.W.), 163, MITCHAM ROAD, LONDON S.W.17 9PG.


We accept Phone orders against ACCESS/Barclay Card Holders. Phone. 672-3137.

Stockists—Callers only

A.I Music Centre, 88 Oxford St., Manchester 1. Tel. 061-236-0340.
Bristol Disco Centre, 86, Stokes Croft, Bristol 1. Tel. Bristol 41666. Calbarrie Audio, 88, Wellington St., Luton, Beds. Tel. Luton 411733. Mitchell Electronics, 64, Winchester St., Salisbury. Tel. Salisbury 23689. Socodi, 9, The Friars, Canterbury, Kent. Tel. Canterbury 60948. Wee Lighting, 35, Northam Road, Southampton, Hants. Tel. Southampton 28102.

NEW! 3 CHANNEL LIGHT MODULATOR

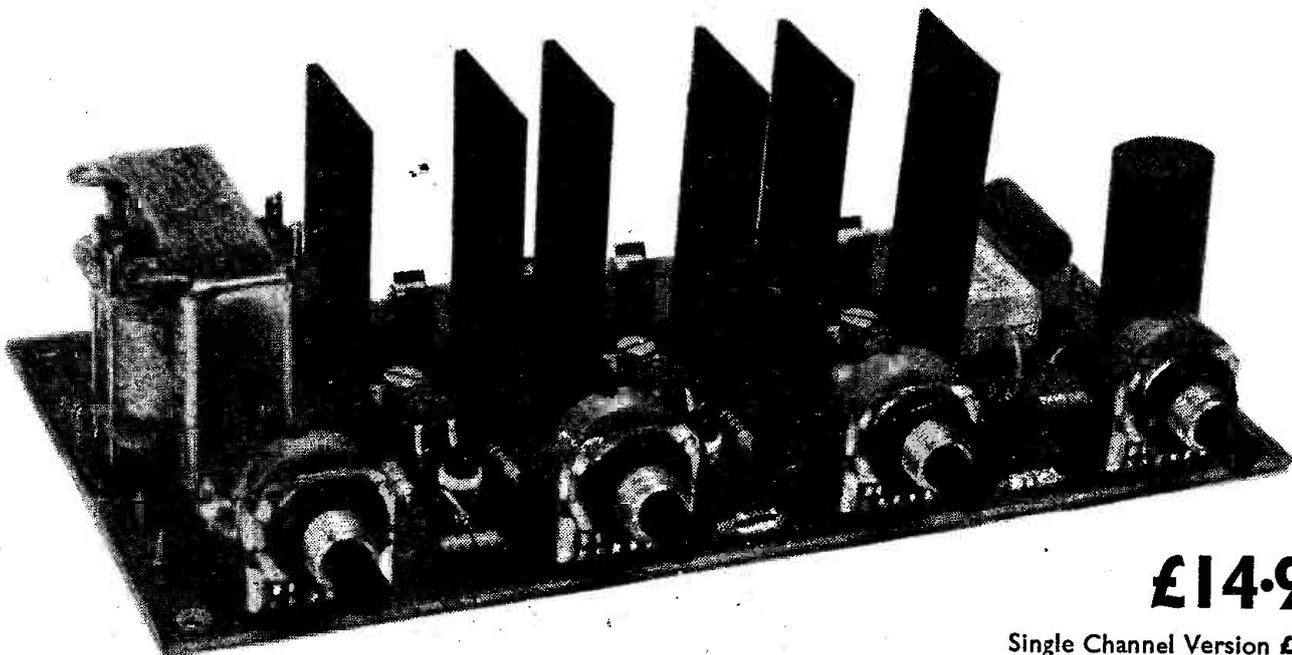- R.C.A. 8 Amp Triacs ● 1000W per channel ● Each channel fully suppressed and fused
- Master control to operate from 1W to 100W ● Full wave control—12 easy connections




£14.90

Single Channel Version £6.60

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT · OPEN 6 DAYS A WEEK 9.30am-6.00pm

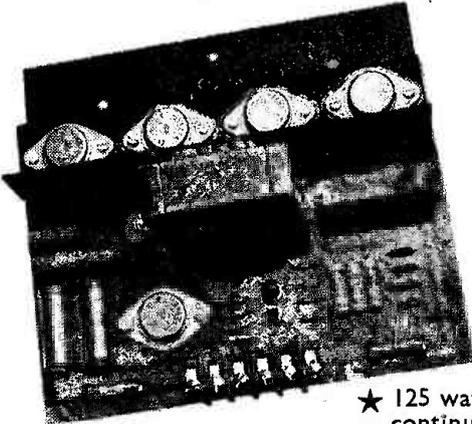NEW TUAC POWER MODULES offering more power and quality than ever before.



Specification on all power modules:
All output power ratings ± 0.5 dB;
Output impedance 8-15 ohms; THD at full power 2% typically 1%;
Input sensitivity 60mV into 10k Ω ;
Frequency response 20Hz-20kHz ± 2 dB; Hum and noise better than -70dB.


TP125

7 x 6 $\frac{1}{2}$ x 3in

£17.00

- ★ 125 watts RMS continuous sine wave output

- ★ 4 R.C.A. 150 watt 15 amp output transistors

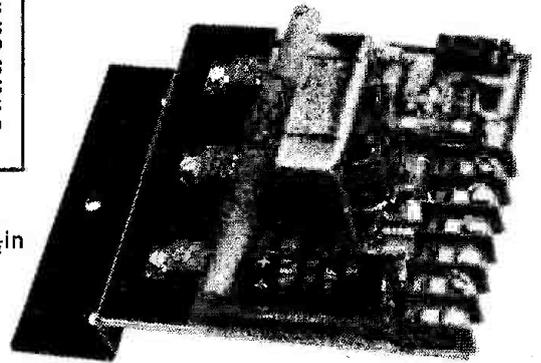


TL30

4 x 5 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in

£9.30

- ★ 30 watts RMS continuous sine wave output
- ★ 2 R.C.A. 40 watt output transistor

- ★ Rugged layer wound driver transformer.
- ★ Short—Open—and Thermal overload protection
- ★ Only 6 connections

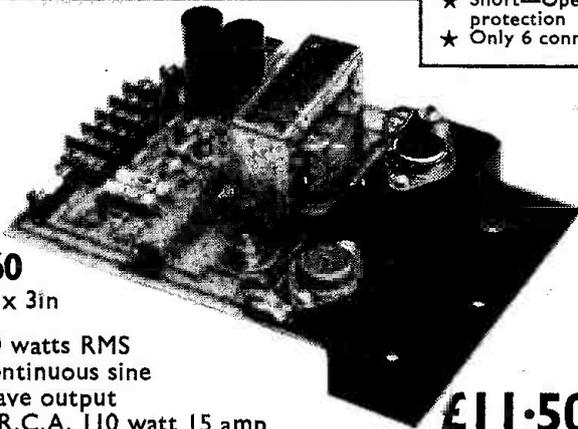

TL60

5 x 5 x 3in

- ★ 60 watts RMS continuous sine wave output
- ★ 2 R.C.A. 110 watt 15 amp transistors


£11.50

TL100

5 x 5 x 3in

- ★ 100 watts R.M.S. continuous sine wave output
- ★ 2 R.C.A. 150 watt 15 amp transistors

£13.20

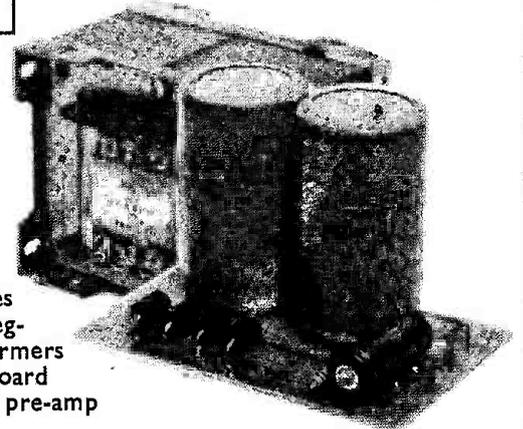

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 \pm 50 volts for one TP125	£11.50
PS 100 \pm 45 volts for one TL100	£10.50
PS 60 \pm 40 volts for one TL60	£9.30
PS 30 \pm 50 volts for one TL30	£6.85
PSU 2 for supplying disco mixer	£4.65


TUAC HIGH POWER AMPLIFICATION—ALL PURPOSE AMPLIFIER

built to high standards, and built to last
Suitable for Disco, PA, Guitar, 4 inputs, 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leathercloth covered case, short and open circuit protection. Tone control specification as VAO8 pre-amp. **FULLY FUSED**

50	RMS SINE WAVE
WATT	£43.00
100	RMS SINE WAVE
WATT	£64.50

Also available

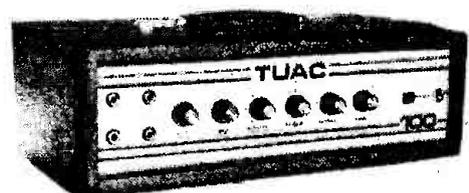100 WATT SLAVE AMPLIFIER
Spec as above. **£48.50.**



ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED · Just Send or Phone us Your Number · H.P. ARRANGED THROUGH PAYBONDS

How to order the cassette unit for your Kempton or Ascot player.

As a reader of Practical Wireless, you can get the cassette mechanism for your car stereo player direct from Goldring.

The units for both the PW Kempton and Ascot are made by Lenco and based on the famous STARR design, with wow and flutter reduced to 0.3% max.


All you have to do is send the coupon to us, with a cheque or PO made out to Goldring Ltd. Be sure to state which unit you need. For the Kempton, it's Lenco FFR at £18.90; for the Ascot, it's Lenco CRV at £19.98. Prices include packing, carriage and VAT.

The units are also available from selected distributors.



Lenco FFR for the Kempton. Robust and precision engineered, it's widely used in industry and by Europe's largest car stereo manufacturer.

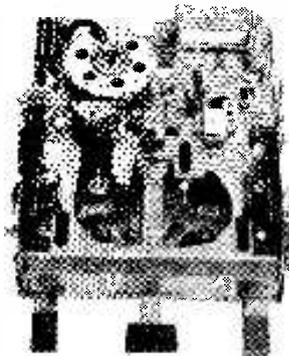Lenco CRV for the Ascot. A record/replay unit made to hi-fi standards. Features include dynamic noise limiting, auto-stop and cassette ejection.



To: Goldring Ltd, 10 Bayford Street, Hackney, London E8 3SE.

Please send me: Lenco FFR at £18.90

Lenco CRV at £19.98

I enclose PO, cheque for £ _____

NAME _____

ADDRESS _____

Goldring

PC ETCHING KIT

Contains 100 sq ins copper laminate board DALO etch resist pen, 1lb Ferric Chloride, etching dish, abrasive cleaner, and instructions, all for only £3.30.

RESISTORS & CAPACITORS

500 assorted resistors £1.35, 2500 £5.200 poly, mica, ceramic capacitors £1.250 Hi-Stab resistors, 1, 2 & 5% £1.20 15 different atspaced & compression trimmers up to 1250pF £1.

VEROBOARD

Polished wooden cabinet 14 x 13 x 9" containing a sensitive (20uV) 4 valve amplifier with tone and volume controls, 3 watts output to the 7 x 4" 3Ω loudspeaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation £4.50. Suitable cassette £1.10. Spare head 33p. Tape (ex-computer) 57p. Amplifier Chassis only, complete & tested (2x ECC83, EL84, EZ80) and speaker £3. With circuit.

3W TAPE AMPLIFIERS

Polished wooden cabinet 14 x 13 x 9" containing a sensitive (20uV) 4 valve amplifier with tone and volume controls, 3 watts output to the 7 x 4" 3Ω loudspeaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation £4.50. Suitable cassette £1.10. Spare head 33p. Tape (ex-computer) 57p. Amplifier Chassis only, complete & tested (2x ECC83, EL84, EZ80) and speaker £3. With circuit.

VERSATILE POWER SUPPLY

Contains mains transformer, 2 amp thermal cut-out and bridge rectifier in neat plastic case. Will give 1.7-10.5V output with 2 extra capacitors (provided). Supplied complete with data sheet. Only £1.20.

STABILIZED POWER UNITS

Made by WEIR Electronics. Mains input, output +26, +15, +6, 0, -6V. All fully stabilized. (Uses 8 2N3055, and 20 other transistors. £16.

UNISELECTORS

4 Bank (1 continuous) 25 way, 100Ω coil. Ex-equipment in good condition £2.50.

FERRIC CHLORIDE

Anhydrous technical quality to Mill-Spec in 1lb double sealed packs. 1lb 80p, 3lb £1.60, 10lb £4.45, 100lb £33

PO AMPLIFIER UNIT

Contained in steel case 5 1/2 x 5 x 3 1/2" are: 2 GET116 transistors on heat sinks, 3 pot cores, 2 30V zeners, 4 audio transformers, 1 1/2 R's & C's. With circuit diagram £1.

7 lb BARGAIN PARCELS

Hundreds of new components—Pots, resistors, capacitors, switches + PC boards with transistors & diodes. Also loads of odds & ends. Contents always changing as new stocks arrive. Amazing value at £2.30.

COMPUTER PANELS

3lbs assorted £1.40, 7lbs £2.65, 56 lbs £15. Pack containing 500 components, including at least 50 transistors. 90p. 12 high quality panels with power transistors, trim pots IC's etc. £2.50. Pack with 20 trim pots + other parts £1. Pack with 24 FCH181 or MC1818 DTL IC's £1. Panels with 12 2N3053, 12 2N706 + 69 other parts £1. Export Pack—special selection of Panels, delivered anywhere in the World for £8.

MISCELLANEOUS

Transformers: (All mains Pri.) 16-0-16V with 9V tap @ 1 1/2A £2; 6-0-6V @ 100mA 85p; 9-0-9V @ 100mA 90p; 12-0-12V... 100mA 95p. Balanced armature earpiece, use as mic or spkr, 20Ω 30p. Silicon grease 2oz tube 60p. IN4001 10/50p; IN4004 10/80p; IN4007 10/£1; SC40D Triac £1; 2200uF 25V 26p; AC127-128-151-176-187-188 All 20p; BC107-8-9 10p; 2N3055 38p, 741C 35p.

Good range of Multimeters in stock from £3.50. Surplus components & equipment wanted for cash.

All prices shown include 8% VAT and postage (mainland only) SAE list, enquiries.

GREENWELD ELECTRONICS (PW10)

Mail order dept., wholesale/retail shop 51 SHIRLEY PARK ROAD, SOUTH-AMPTON. Tel 0703 772501. Other retail shops at 21 Deptford Broadway SE8, Tel 01-692 2009 and 38 Lower Addiscombe Road, Croydon. Callers Welcome.

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit) <input type="checkbox"/>	Electronic Engineering <input type="checkbox"/>	CITY AND GUILDS Installations and Wiring <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Computer Electronics <input type="checkbox"/>	CITY AND GUILDS Electrical Technicians <input type="checkbox"/>
Electrical Installations and wiring <input type="checkbox"/>	Computer Programming <input type="checkbox"/>	CITY AND GUILDS Telecommunications <input type="checkbox"/>
Electrical Draughtsmanship <input type="checkbox"/>	General Radio and TV Engineering <input type="checkbox"/>	Radio Amateurs' Exam etc. etc. <input type="checkbox"/>
Electrical Mathematics <input type="checkbox"/>	Radio Servicing, Maintenance and Repairs <input type="checkbox"/>	
	Transistor Technology <input type="checkbox"/>	

To ALDERMASTON COLLEGE Dept. BPW95, Reading RG7 4PF **BPW 95**

NAME (Block Capitals Please) _____

ADDRESS _____

Other subjects _____ Age _____

Accredited by C.A.C.C. Member of A.B.C.C.


BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £13.50. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

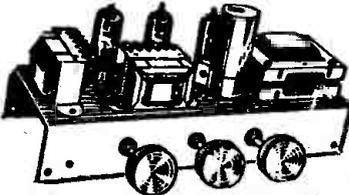

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. £10.75. P.&P. 50p.

POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7.5v. and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Metal Rectifiers, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5.20 P. & P. 35p.

VYNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1.20 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. £4.20 P. & P. 40p BARGAIN PRICE

FEW ONLY!

High grade mains transformer with grain orientated lamination. Primary 200/240 Secondary 18.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2" h x 2 3/4" w x 2" d overall. £1.35 plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.60 P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. £1.20. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.40. P. & P. 26p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £2.00. P. & P. 35p.

HI-GRADE COPPER LAMINATE BOARDS 8" x 6", Five for 70p plus 30p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price 1.20p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.


3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents, 80p; Transistor Equivalents, 90p; Transistor Characteristics, £1.15; POST FREE All three together, £2.60

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias 95p, Post Free 8 pole 3 way 2 bank low loss Yaxley type switches 1 1/2" sections. Standard spindle. 2 switches 64p + 10p P. & P.

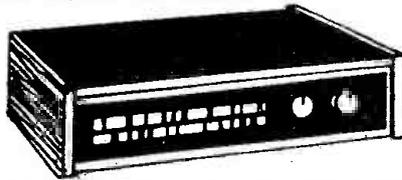HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £23.00 Post and Packing 50p.

STEREO-DECODER

SIZE 2" x 3" x 1 1/2" ready built. Pre-aligned and tested. Sens. 20-560 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5.00 plus 10p. P. & P. Stereo beacon light if required 40p extra.



SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £8.00 + p. & P. 60p.

LATEST Hi Sensitivity Uni-directional slim-line condenser microphone as used by many professionals. Very low acoustic feedback. Available hi impedance or low impedance. State which required. £13.50 plus 25p P. & P

LATEST ACOS GP91/LSC mono compatible cartridge with 1/0 stylus for LP/EP/78. Universal mounting bracket. £1.46. P. & P. 15p.

SONOTONE STAHC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.27 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.76. P. & P. 15p.

LATEST T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. £1.60 P. & P. 15p. **LATEST T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £5.50. P. & P. 50p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6.70. P. & P. 60p.

HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £9.50 Carr. 90p
Cabinet Available Separately £5.00, Carr. 90p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.00, Carr. 90p.

LOUSPEAKER BARGAINS

5in. 3 ohm £1.25. P. & P. 15p. 7 x 4in. 3 ohm £1.40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3.50; P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4.65. P. & P. 30p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £1.25 + 20p. p. & p.


BRAND NEW Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiFiux ceramic ferrobar magnet assembly £7.50. Guitar models: 26w £7.50. 35w, £7.50. P.&P. 45p.

12in. "RA" TWIN CONE LOUSPEAKER. 10 watts peak handling. 3 or 8 or 15 ohm (state which) £3.00. P. & P. 30p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6.80 each. P. & P. 34p.

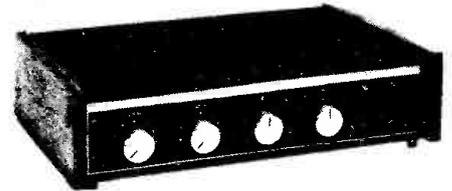HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.


AMPLIFIER KIT £12.96 P. & P. 30p
(Magnetic input components 33p extra)
POWER PACK KIT £4.32 P. & P. 40p
CABINET £4.32 P. & P. 40p

(Post Free if all units purchased at same time)

Full after sales service

Also available ready built and tested £28.08. Post Free.

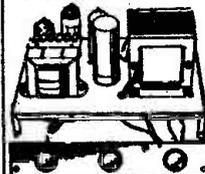Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc. and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £8.50. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc £5.50 P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 8-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 15p + SAE (Free with parts) All parts sold separately. ONLY £10.25 P. & P. 60p. Also available ready built and tested £14.00 P. & P. 70p.

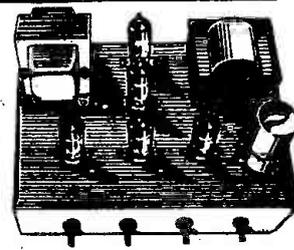

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable Hexifoam ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.50. P. & P. 25p.

PRICES INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday

Closed Wednesday.

A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES



GIRO NO. 331 7056
C.W.O. only, P. & P. 10p on orders below £5
Discount: £10-10%, £20-15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.58 net
10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.77 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.19 net
25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.28 net
5E12 1/2W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £2.80 net
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3 1/2p, 0.068µF, 0.1µF, 4 1/2p, 0.15µF, 4 1/2p, 0.22µF, 5 1/2p, 0.33µF, 8p, 0.47µF, 9p, 0.68µF, 12p 1µF, 15p, 1.5µF, 23p, 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2 1/2p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3 1/2p, 0.047µF, 0.068µF, 0.1µF, 4 1/2p, 0.15µF, 6 1/2p, 0.22µF, 8p, 0.33µF, 12p, 0.47µF, 14p.

160V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 3 1/2p, 0.1µF, 4 1/2p, 0.15µF, 5p, 0.22µF, 5 1/2p, 0.33µF, 6 1/2p, 0.47µF, 8p, 0.68µF, 12p, 1µF, 14p.

MINIATURE CERAMIC FLAT CAPACITORS

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2 1/2p, each, 0.1-30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%

(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 4 1/2p.

RESISTORS

CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%.

W. Type	Range	1-99	100-499	500-999	1000+	Size mm
CF	22-1M	1	0.75	0.60	0.55	2.4x7.5
CF	22-2M2	1	0.75	0.60	0.55	3.9x10.5
CF	22-1M	1	0.75	0.60	0.55	5.5x16
MF	10-2M7	2	1.54	1.32	1.1	3x7
MF	10-2M2	2	1.43	1.21	0.99	4.2x10.8
1 MF	10-10M	3	1.98	1.81	1.65	6.6x13
2 MF	10-10M	4.5	3.52	3.08	2.75	8x17.5

For value mixing prices, please refer to our catalogue. (price in pence each).
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 5p each.

B. H. COMPONENT FACTORS LTD.

(P.W.) 61 CHEDDINGTON ROAD, PITSTONE
NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ
Tel.: Cheddington 668446 (Std. Code 0296)
CATALOGUE No. 3 20p

Miniature Mullard Electrolytics

1.0µF 63V	6 1/2p	68µF 16V	6 1/2p
1.5µF 63V	6 1/2p	68µF 63V	12p
2.2µF 63V	6 1/2p	100µF 10V	6 1/2p
3.3µF 63V	6 1/2p	100µF 25V	6 1/2p
4.0µF 40V	6 1/2p	100µF 63V	14p
4.7µF 63V	6 1/2p	150µF 16V	6 1/2p
6.8µF 63V	6 1/2p	150µF 63V	15p
8.0µF 40V	6 1/2p	220µF 6.4V	6 1/2p
10µF 16V	6 1/2p	220µF 10V	6 1/2p
10µF 25V	6 1/2p	220µF 16V	8p
10µF 63V	6 1/2p	220µF 63V	21p
15µF 16V	6 1/2p	330µF 16V	12p
15µF 63V	6 1/2p	330µF 63V	25p
15µF 40V	6 1/2p	470µF 6.4V	9p
22µF 25V	6 1/2p	470µF 40V	20p
22µF 63V	6 1/2p	680µF 16V	15p
33µF 10V	6 1/2p	680µF 40V	25p
33µF 16V	6 1/2p	1000µF 16V	20p
33µF 40V	6 1/2p	1000µF 25V	25p
33µF 63V	6 1/2p	1500µF 4V	15p
47µF 10V	6 1/2p	1500µF 16V	25p
47µF 25V	6 1/2p	2200µF 10V	25p
47µF 63V	8p	3300µF 6.4V	26p

VEROBOARD 0.1 0.15

2 1/2 x 5"	36p	36p
2 1/2 x 3 1/2"	33p	25p
3 1/2 x 5"	42p	46p
3 1/2 x 3 1/2"	36p	36p
2 1/2 x 1"	9p	9p
2 1/2 x 5" (Plain)	—	19p
2 1/2 x 3 1/2" (Plain)	—	16p
5 x 3 1/2" (Plain)	—	29p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 25	22p	22p

TRANSISTORS

AC127	16 1/2p	BC212L	12p
AC128	22p	BC213L	12p
BC107	11p	BC214L	18p
BC108	12p	OC44	18p
BC109	13p	OC71	13p
BC148	12p	OC81	16p
BC149	12p	OC170	23p
BC182L	12p	TIS43	33p
BC183L	12p	2N2926	11p
BC184L	13p	2N3702	11p

POTENTIOMETERS

Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 16 1/2p Dual Gang 46p. Log single with switch 26p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001	6 1/2p	DIN 2 Pin	12p
IN4002	7 1/2p	3 Pin	13p
IN4003	9p	5 Pin 180°	16p
IN4004	90p	Std. Jack	20p
IN4005	12p	2.5mm jack	13p
IN4006	14p	Phono	6p
IN914	7p	SOCKETS	
IN916	7p	DIN 2 Pin	10p
BA100	10p	3 Pin	10p
OA5	42p	5 Pin 180°	12p
OA47	9p	Std. Jack	15p
OA81	11p	2.5mm Jack	13p
OA200	8p	Phono	6p

Integrated Circuits

µA709C	49p
µA741C	50p
µA723C	98p
ZN414	£1.30

PLUGS

DIN 2 Pin	12p
3 Pin	13p
5 Pin 180°	16p
Std. Jack	20p
2.5mm jack	13p
Phono	6p

SOCKETS

DIN 2 Pin	10p
3 Pin	10p
5 Pin 180°	12p
Std. Jack	15p
2.5mm Jack	13p
Phono	6p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans

(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 6 1/2p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 88p, 2000/25, 30p, 2000/100, 93p, 2500/25, 38p, 2500/50, 61p, 5000/25, 65p, 5000/50, £1.08.

HI-VOLT: 4/350, 14p, 8/350, 19p, 100/100 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/250, 30p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7 1/2p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7 1/2p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 34p.

Screened Wire, Metre

Twin Screened Wire, Metre	12p
Stereo Screened Wire, Metre	12p
Connecting Wire, All colours, Metre	21p
Neon Bulb, 90V Wire Ended	5 for 24p
Panel Neon, 240V Red, Amber, Clear	20p

ZENER DIODES

Low cost 400mW Tol ±7%
All values E24 series 3V-30V
1-24 25-99 100-499 1000—
9p 7 1/2p 6 1/2p 5 1/2p

MULTIMETER U4323

22 Ranges plus AF/IF Oscillator 20,000Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—5Ω—1MΩ in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465 KHz (A, M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8.30 net p & p 25p.

MULTIMETER U4341

27 Ranges plus Transistor Tester, 16,700Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 6 ranges.
Idc—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2KΩ—2MΩ in 4 ranges.
Accuracy—dc—2 1/2%, ac—4% of F.S.D.
hfe—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.30 net p & p 30p.

MULTIMETER U4324

34 Ranges. High sensitivity, 20,000Ω/Volt. Overload protected.
Vdc—0.6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25Ω—5MΩ in 5 ranges.
Accuracy—dc and R—2 1/2% of F.S.D. ac and db—1% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £9.95 net p & p 25p.

MULTIMETER U4313

33 ranges. Knife edge with mirror scale, 20,000Ω/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ranges.
Iac—0.6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1 1/2%, ac—2 1/2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £13.40 net p & p 30p.

NEW CAPACITOR KITS

C280 Kit—PC Mounting polyester 250V, 5 of each value: 0.01 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47, 1µF. £1.30 net.
C296 Kit—Tubular polyester, 400V, 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47µF. £1.30 net.
Ceramic Kit—square planquette 50V, 5 each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0.01µF. £1.30 net.
250V Paper kit—Tubular metal case. 3 of each value: 0.05, 0.1, 0.25, 0.5, 1µF. 90p net.
500V Paper Kit—Tubular metal case. 3 of each value: 0.025, 0.05, 0.1, 0.25, 0.5µF. 90p net.
1000V Paper Kit—Tubular metal case. 3 each value: 0.01, 0.025, 0.05, 0.1µF. £1.10 net.

S-DeC

T-DeC	£2.14
S-DeC	£3.92
µDeC "A"	£4.30
µDeC "B"	£7.53

ANTEX

CCN240	£2.43
CN240	£2.01
X25	£2.01

PANEL METERS

2" scale	
100µA	
500µA	
1mA All	
5mA at	
10mA	£3.75
50mA	
100mA	
500mA	
1A	

Dalo Pen "expert" solder gun £6.56
Wire pack 5 x 5mtrs. 27p
Diode pack (Ge) 50 for 25p
Jackson "00" 365pF 98p
C804, 5pF, 10pF, 15pF 83p
20pF, 25pF, 50pF 89p
60pF, 75pF, 100pF 98p
Dilecon 100, 300, 500pF
LED, TIL 209 5 for £1
Panel I/holder 4 colours 22p
R'y Sw'chs: IP12W, 2P6W, 3P4W, 4P3V 6P2W 30p

INTER-LOCKING PLASTIC STORAGE DRAWERS

Nearest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D have space dividers. Build up any size cabinet for wall, bench or table top.

NEAR HANDY TIDY!

DISCOUNT PRICES

SIZES ALL INTERLOCK

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £2.00 Dozen
DOUBLE UNITS £3.50 Dozen. **TREBLE (3D)** £3.50 for 8
DOUBLE TREBLE £4.90 for 8.
EXTRA LARGE SIZE (6D1) £4.50 for 8.
Carriage 40p. Orders over £10 post free.

QUANTITY DISCOUNTS! 5% in £1 for orders over £15
7 1/2% for orders over £30. Quotations for large quantities.
PLEASE ADD 8% VAT TO TOTAL REMITTANCE.

FLAIRLINE SUPPLIES (Dept. PW1), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary and Slide Switches, IF's, Tag Strips, Drive Drums, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels, etc. Save yourself £'s on these well selected parcels, 6lb net weight £1.00, p.p. 50p.

Brand New Wire-wound Resistors 1-7 watts, mostly Plessey GWS-1-3-5-7. Good selection. 100 for £1.00, p.p. 20p.

Mullard Ferrite Cores LA3 50p, LA4 75p, LA2100 50p.

SPECIAL OFFER. Metallised Polyester Capacitors by Erie, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160, .033/160, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £1.50, p.p. 20p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene, Tremendously good selection. 300 for £1, p.p. 20p. Please add 8% V.A.T.


Mail Order Only.

XEROZA RADIO,
1, EAST STREET, BISHOPS TAWTON, DEVON.





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

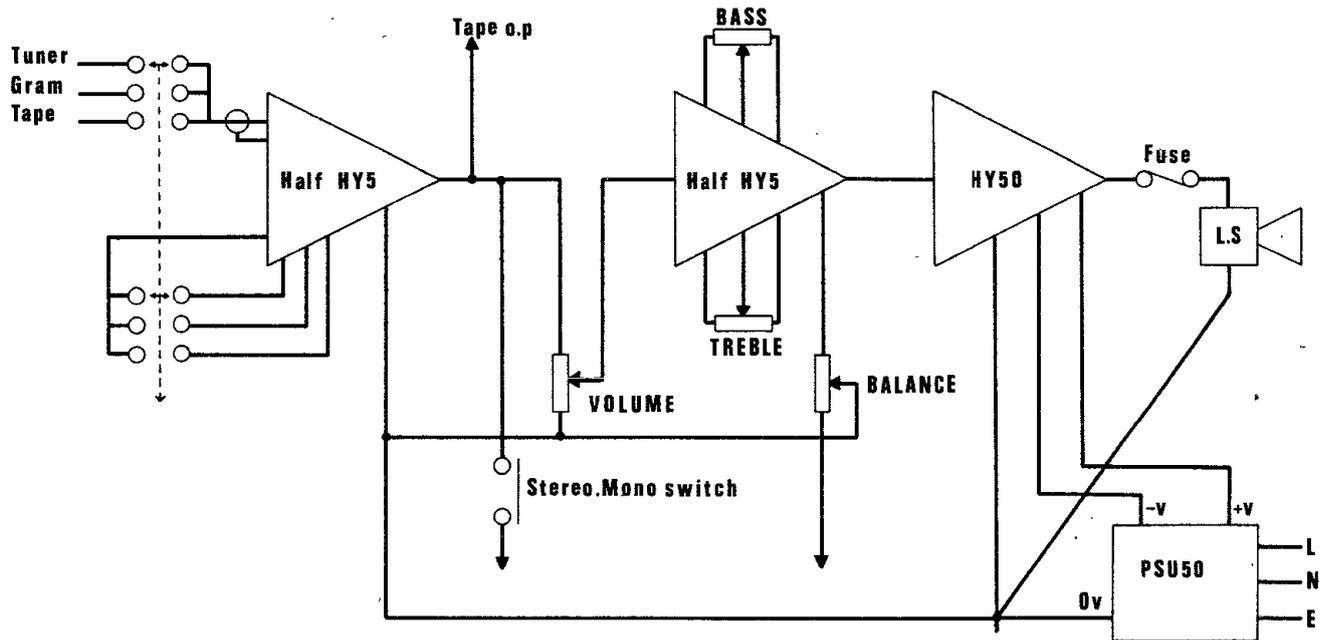

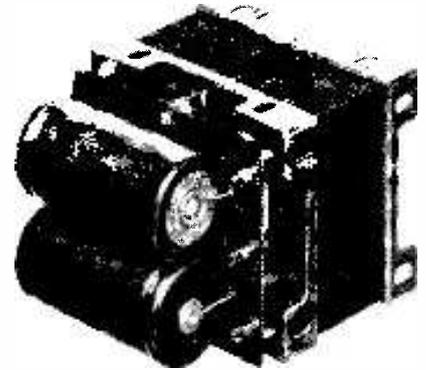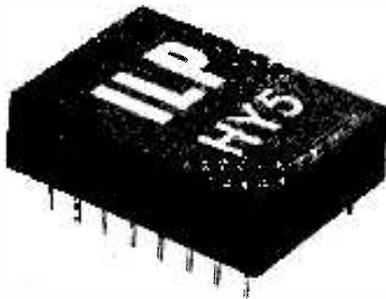MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxillary 3-100mV; input/impedance 47kΩ at 1kHz. **Outputs:** Tape 100mV; Main output 0db (0.775V RMS). **Active Tone Controls:** Treble ± 12db at 10kHz; Bass ± 12db at 10kHz; Bass ± 12db at 100Hz. **Distortion:** 0.5% at 1kHz. **Signal/Noise Ratio:** 68db. **Overload Capability:** 40db on most sensitive input. **Supply Voltage:** ± 16-25V.

PRICE £4.50 + 36p VAT
P. & P. free

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8kΩ. **Load Impedance:** 4-16Ω. **Input Sensitivity** 0db (0.775V RMS). **Input Impedance:** 47kΩ. **Distortion:** Less than 0.1% at 25W typically 0.05%. **Signal/Noise Ratio:** Better than 75db. **Frequency Response:** 10Hz-50kHz ± 3db. **Supply Voltage:** ± 25V. **Size:** 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT
P. & P. free

The PSU50 can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: 50V (25-0-25V). **Input Voltage:** 210-240V. **Size:** L.70. D.90. H.60mm.

PRICE £5 + 40p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD

Tel (0227) 63218

Please supply,
Total Purchase price
I Enclose, Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name & Address
.....
Signature

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	0.22	AD162	0.39	BC149	0.13	BD124	0.76	BF181	0.33	MAT121	0.22	2G306	0.44	2N2160	0.66	2N2055	0.55	2N4059	0.11
AC113	0.20	AD161 &		BC150	0.20	BD131	0.55	BF182	0.44	MJE2955	0.95	2G308	0.39	2N2192	0.39	2N3391	0.16	2N1060	0.13
AC115	0.22	AD162(MP)	75	BC151	0.22	BD132	0.66	BF183	0.44	MJE3055	0.62	2G309	0.39	2N2193	0.39	2N3391A	0.18	2N4061	0.13
AC117K	0.22	ADT140		BC152	0.19	BD133	0.72	BF184	0.28	MJE3440	0.55	2G339	0.22	2N2194	0.39	2N3392	0.16	2N4062	0.13
AC122	0.18	AF114	0.27	BC153	0.31	BD135	0.44	BF185	0.33	MPP102	0.46	2G339A	0.18	2N2217	0.24	2N3393	0.16	2N4284	0.10
AC125	0.19	AF115	0.27	BC154	0.33	BD136	0.44	BF187	0.30	MPP104	0.41	2G344	0.20	2N2218	0.22	2N3394	0.16	2N4285	0.10
AC126	0.19	AF116	0.27	BC157	0.20	BD137	0.50	BF188	0.44	OC19	0.39	2G345	0.18	2N2219	0.22	2N3395	0.19	2N4286	0.10
AC127	0.20	AF117	0.27	BC158	0.13	BD138	0.55	BF194	0.13	OC20	0.70	2G371	0.18	2N2220	0.22	2N3402	0.28	2N4287	0.19
AC128	0.20	AF118	0.27	BC159	0.13	BD139	0.61	BF195	0.13	OC21	0.54	2G371B	0.13	2N2221	0.22	2N3403	0.23	2N4288	0.10
AC132	0.16	AF124	0.33	BC160	0.50	BD140	0.66	BF196	0.16	OC22	0.52	2G373	0.19	2N2222	0.22	2N3404	0.21	2N4289	0.19
AC134	0.16	AF125	0.33	BC161	0.55	BD155	0.88	BF197	0.16	OC23	0.54	2G374	0.19	2N2368	0.19	2N3405	0.46	2N4290	0.19
AC137	0.16	AF126	0.31	BC167	0.13	BD175	0.66	BF200	0.50	OC24	0.62	2G377	0.33	2N2369	0.16	2N3414	0.17	2N4291	0.10
AC141	0.20	AF127	0.31	BC168	0.13	BD176	0.66	BF222	£1.05	OC25	0.42	2G378	0.18	2N2369A	0.16	2N3415	0.17	2N4292	0.19
AC141K	0.32	AF129	0.33	BC169	0.13	BD177	0.72	BF257	0.50	OC26	0.32	2G381	0.18	2N2411	0.27	2N3416	0.21	2N4293	0.19
AC142	0.20	AF178	0.55	BC170	0.13	BD178	0.72	BF258	0.66	OC28	0.55	2G382	0.18	2N2412	0.27	2N3417	0.21	2N4294	0.19
AC142K	0.20	AF179	0.55	BC171	0.16	BD179	0.77	BF259	0.94	OC29	0.55	2G401	0.33	2N2646	0.52	2N3525	0.83	2N5294	0.60
AC151	0.17	AF180	0.55	BC172	0.16	BD180	0.77	BF262	0.61	OC35	0.46	2G414	0.33	2N2711	0.23	2N3614	0.74	2N5457	0.35
AC154	0.22	AF181	0.55	BC173	0.16	BD185	0.72	BF263	0.61	OC36	0.55	2G417	0.33	2N2712	0.23	2N3615	0.82	2N5458	0.35
AC155	0.22	AF186	0.55	BC174	0.16	BD186	0.72	BF270	0.39	OC41	0.22	2N388	0.39	2N2714	0.23	2N3616	0.82	2N5459	0.44
AC156	0.22	AF239	0.41	BC175	0.24	BD187	0.77	BF271	0.39	OC42	0.27	2N388A	0.61	2N2904	0.19	2N3646	0.62	2N6221	0.75
AC157	0.27	AL102	0.72	BC177	0.21	BD188	0.77	BF272	0.88	OC44	0.17	2N404	0.22	2N2904A	0.23	2N3702	0.13	28301	0.55
AC165	0.22	AL103	0.72	BC178	0.21	BD189	0.83	BF273	0.39	OC45	0.14	2N404A	0.31	2N2905	0.23	2N3703	0.13	28302A	0.46
AC166	0.22	ASY26	0.28	BC179	0.21	BD190	0.83	BF274	0.39	OC70	0.11	2N524	0.46	2N2905A	0.23	2N3704	0.14	28302	0.46
AC167	0.22	ASY27	0.28	BC180	0.27	BD195	0.94	BF275	0.39	OC71	0.11	2N527	0.46	2N2906	0.17	2N3705	0.13	28303	0.61
AC168	0.27	ASY28	0.28	BC181	0.27	BD198	0.94	BF276	0.39	OC72	0.16	2N598	0.46	2N2906A	0.20	2N3706	0.13	28304	0.77
AC169	0.16	ASY29	0.28	BC182	0.16	BD197	0.99	BF284	0.34	OC74	0.16	2N599	0.50	2N2907	0.22	2N3707	0.14	28305	0.86
AC176	0.22	ASY50	0.28	BC182L	0.16	BD198	0.99	BF285	0.33	OC75	9.17	2N696	0.14	2N2907A	0.24	2N3708	0.09	28306	0.86
AC177	0.27	ASY51	0.28	BC183	0.16	BD199	£1.05	BF286	0.24	OC76	0.17	2N697	0.15	2N2923	0.16	2N3709	0.10	28307	0.86
AC178	0.31	ASY52	0.28	BC183L	0.16	BD200	£1.05	BF287	0.27	OC77	0.28	2N698	0.27	2N2924	0.16	2N3710	0.10	28321	0.62
AC179	0.31	ASY54	0.28	BC184	0.22	BD205	0.88	BF288	0.24	OC81	0.17	2N699	0.39	2N2925	0.16	2N3711	0.10	28322	0.46
AC180	0.22	ASY56	0.28	BC184L	0.22	BD206	0.88	BF289	0.24	OC81D	0.17	2N706	0.09	2N2926(G)	14	2N3819	0.31	28322A	0.46
AC180K	0.32	ASY56	0.28	BC186	0.31	BD207	£1.05	BF290	0.22	OC82	0.17	2N706A	0.10	2N2926(Y)	12	2N3820	0.55	28325	0.62
AC181	0.22	ASY57	0.28	BC187	0.31	BD208	£1.05	BF291	0.22	OC82D	0.17	2N708	0.13	2N2926(O)	11	2N3821	0.39	28324	0.77
AC181K	0.32	ASY58	0.28	BC207	0.12	BDY20	£1.10	BFY53	0.19	OC83	0.22	2N711	0.33	2N2926(R)	11	2N3823	0.31	28325	0.77
AC187	0.24	ASY73	0.28	BC208	0.12	BF115	0.27	BSX19	0.17	OC139	0.22	2N717	0.39	2N2926(B)	11	2N3903	0.31	28326	0.77
AC187K	0.24	ASZ21	0.44	BC209	0.13	BF117	0.50	BSX20	0.17	OC140	0.22	2N718	0.27	2N3010	0.77	2N3904	0.33	28327	0.77
AC188	0.24	BC107	0.14	BC212L	0.14	BF118	0.77	BSY25	0.17	OC169	0.25	2N718A	0.55	2N3011	0.16	2N3905	0.31	28701	0.44
AC188K	0.25	BC108	0.15	BC213L	0.14	BF119	0.77	BSY26	0.17	OC170	0.25	2N726	0.31	2N3063	0.19	2N3906	0.30	40361	0.46
AOY17	0.28	BC109	0.14	BC214L	0.18	BF121	0.50	BSY27	0.17	OC171	0.28	2N727	0.31	2N3064	0.51	2N4058	0.13	40362	0.50
ACY18	0.22	BC113	0.11	BC225	0.28	BF123	0.55	BSY28	0.17	OC200	0.28	2N743	0.22						
ACY19	0.22	BC114	0.17	BC226	0.28	BF125	0.55	BSY29	0.17	OC201	0.31	2N744	0.22						
ACY20	0.22	BC115	0.17	BC301	0.30	BF127	0.55	BSY30	0.20	OC202	0.31	2N914	0.16						
ACY21	0.22	BC116	0.17	BC302	0.27	BF152	0.61	BSY39	0.20	OC203	0.28	2N918	0.33	AA119	0.09	BY128	0.17	OA10	0.15
ACY22	0.18	BC117	0.20	BC303	0.35	BF153	0.50	BSY40	0.31	OC204	0.28	2N929	0.23	AA120	0.09	BY130	0.16	OA47	0.08
ACY27	0.20	BC118	0.11	BC304	0.40	BF154	0.50	BSY41	0.31	OC205	0.39	2N930	0.23	AA129	0.09	BY133	0.23	OA70	0.08
ACY28	0.21	BC119	0.33	BC440	0.34	BF155	0.77	BSY95	0.14	OC309	0.44	2N1131	0.22	AA130	0.10	BY164	0.55	OA79	0.08
ACY29	0.39	BC120	0.88	BC460	0.40	BF156	0.53	BSY95A	0.14	OC309	0.44	2N1132	0.24	AAZ13	0.11	BYX38/300-46	0A81	0.08	
ACY30	0.31	BC125	0.13	BCY30	0.27	BF157	0.61	Bu105	£2.20	ORP12	0.48	2N1302	0.16	BA100	0.11	BYZ10	0.39	OA85	0.10
ACY31	0.31	BC126	0.20	BCY31	0.29	BF158	0.61	C111E	0.55	ORP60	0.44	2N1303	0.16	BA116	0.23	BYZ11	0.33	OA90	0.07
ACY34	0.23	BC132	0.13	BCY32	0.23	BF159	0.66	C400	0.55	ORP61	0.44	2N1304	0.19	BA126	0.24	BYZ12	0.33	OA91	0.07
ACY35	0.23	BC134	0.20	BCY33	0.24	BF160	0.44	C407	0.28	P20	0.55	2N1305	0.19	BA148	0.16	BYZ13	0.23	OA95	0.08
ACY36	0.19	BC136	0.13	BCY34	0.24	BF162	0.44	C424	0.28	P346A	0.28	2N1306	0.23	BA154	0.13	BYZ16	0.44	OA200	0.07
ACY40	0.19	BC138	0.17	BCY70	0.16	BF163	0.44	C425	0.55	P397	0.46	2N1307	0.23	BA155	0.16	BYZ17	0.39	OA202	0.08
ACY41	0.20	BC137	0.17	BCY71	0.22	BF164	0.44	C426	0.39	RT140	0.14	2N1308	0.26	BA156	0.15	BYZ18	0.39	SD10	0.06
ACY44	0.39	BC139	0.44	BCY72	0.16	BF165	0.44	C428	0.22	RT141	0.19	2N1309	0.26	BA173	0.16	BYZ19	0.31	SD19	0.06
AD130	0.42	BC140	0.33	BCZ10	0.22	BF167	0.24	C441	0.83	TIS43	0.34	2N1613	0.22	BY100	0.17	CG62	1N34	0.08	
AD140	0.53	BC141	0.33	BCZ11	0.23	BF173	0.24	C442	0.39	UT46	0.30	2N1711	0.23	BY101	0.13	(OA91 Eq)-0.06	1N34A	0.08	
AD142	0.53	BC142	0.33	BCZ12	0.23	BF176	0.39	C444	0.38	ZN414	£1.20	2N1889	0.35	BY105	0.19	CG651-	1N914	0.08	
AD143	0.42	BC143	0.33	BD115	0.68	BF177	0.39	C450	0.24			2N1890	0.50	BY114	0.13	(OA70-79)-0.07	1N916	0.06	
AD149	0.55	BC145	0.50	BD116	0.68	BF178	0.33	CAT100	0.21			2G3802	0.21	BY124	0.18	OA5	0.39	1N4148	0.06
AD161	0.39	BC147	0.11	BD121	0.66	BF179	0.33	CAT101	0.22			2G3803	0.21	BY126	0.16	OA5 short	18021	0.11	
		BC148	0.11	BD123	0.72	BF180	0.33	MAT120	0.22			2G3804	0.27	BY127	0.17	leads	0.23	18951	0.07

DIODES AND RECTIFIERS

Type	Price	Type	Price	Type	Price	Type	Price
AA119	0.09	BY128	0.17	OA10	0.15		
AA120	0.09	BY130	0.16	OA47	0.08		
AA129	0.09	BY133	0.23	OA70	0.08		
AA130	0.10	BY164	0.55	OA79	0.08		
AAZ13	0.11	BYX38/300-46	0A81	0.08			
BA100	0.11	BYZ10	0.39	OA85	0.10		
BA116	0.23	BYZ11	0.33	OA90	0.07		
BA126	0.24	BYZ12					

-the lowest prices!

P.W. TELE-TENNIS KIT OF PARTS

Including all resistors, capacitors,
semi-conductors, I.C. sockets, switches
and transformer

Our Usual Price £27.50

SPECIAL OFFER

£23.50 incl. V.A.T. and P. & P.

We regret free pack not applicable to this offer

ND 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for
BSX 21, O 407, 2N 1893
120veb.

1	25	100+
0.19	0.17	0.16

Sil. trans. suitable for
P.E. Organ. Metal TO-18
Eqvt. ZTX300 6p each.
Any Qty.

GP 100 TO3 METAL CASE GERMANIUM

Vebo=80V. Vceo=60V.
I.C.=10 amps. Ptot=
30W. hfe=30-170.
Replaces the majority of
Germanium power transistors
in the OC, AD
and NKT range.

1	25	100+
0.47	0.44	0.40

GP 300 TO3 METAL CASE SILICON

Vebo=100V. Vceo=60V.
I.C.=15 amps. Ptot=
115W. hfe=20. 100fT.=
1MHz. Suitable replacement
for 2N 3055,
BDY 11 or BDY 20.

1	25	100+
0.55	0.53	0.51

NEW 8th EDITION 250 pages

TRANSISTOR EQUIVA-
LENTS BOOK. A com-
plete cross reference and
equivalents book for
European, American and
Japanese Transistors.
Exclusive to BI-PAK.
£1.85 each.

A LARGE RANGE OF
TECHNICAL AND DATA
BOOKS ARE NOW
AVAILABLE EX STOCK.
SEND FOR FREE LIST.

SIL. G.P. DIODES 2p

300mW 30 0.55
40PIV(Min.) 100 1.85
Sub-Min. 500 5.50
Fully Tested 1,000 9.90
Ideal for Organ Builders.

ADI61/162

M/P COMP PNP
TRANS. OUR LOW-
EST PRICE OF 75p
PER PAIR.

LOOK FOR OUR
**AUDIO &
ELECTRONIC
COMPONENTS
ADVERTISEMENTS**
PRACTICAL WIRELESS
EVERYDAY
ELECTRONICS AND
RADIO CONSTRUCTOR

FULL RANGE OF
ZENER DIODES
VOLTAGE RANGE
2-33V. 400mV (DO-7
Case) 12p ea. 1½W (Top-
Hat) 18p ea. 10W (SO-10
Stud) 32p ea.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 2p
Q1	20 Red spot transistors PNP	0.55
Q2	16 White spot R.F. transistors PNP	0.55
Q3	4 OC 77 type transistors	0.55
Q4	6 Matched transistors OC44/45/81/81D	0.55
Q5	4 OC 75 transistors	0.55
Q6	5 OC 72 transistors	0.55
Q7	4 AC 128 transistors PNP high gain	0.55
Q8	4 AC 126 transistors PNP	0.55
Q9	7 OC 81 type transistors	0.55
Q10	7 OC 71 type transistors	0.55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0.55
Q12	3 AF 116 type transistors	0.55
Q13	3 AF 117 type transistors	0.55
Q14	3 OC 171 H.F. type transistors	0.55
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0.55
Q17	5 NPN 2 x ST.141 & 3 x ST.140	0.55
Q18	4 MADD'S 2 x MAT 100 & 2 x MAT 120	0.55
Q19	3 MADD'S 2 x MAT 101 & 1 x MAT 121	0.55
Q20	4 OC 44 Germanium transistors A.F.	0.55
Q21	4 AC 127 NPN Germanium transistors	0.55
Q22	20 NKT transistors A.F. R.F. coded	0.55
Q23	10 OA 202 Silicon diodes sub-min.	0.55
Q24	8 OA 81 diodes	0.55
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.55
Q26	8 OA95 Germanium diodes sub-min IN69	0.55
Q27	2 10A PIV Silicon rectifiers 18425E	0.55
Q28	2 Silicon power rectifiers BYZ 13	0.55
Q29	4 Silicon transistors 2 x 2N698, 1 x 2N697, 1 x 2N698	0.55
Q30	7 Silicon switch transistors 2N706 NPN	0.55
Q31	6 Silicon switch transistors 2N708 NPN	0.55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.55
Q33	3 Silicon NPN transistors 2N1711	0.55
Q34	7 Silicon NPN transistors 2N2369, 500MHz (code P397)	0.55
Q35	3 Silicon PNP TO-5. 2 x 2N2904 & 1 x 2N2905	0.55
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0.55
Q37	3 2N3053 NPN Silicon transistors	0.55
Q38	7 NPN transistors 3 x 2N3703, 2 x 2N3702	0.55

555 I.C. 65p each

MAMMOTH I.C. PACK

APPROXIMATELY 200 PIECES ASSORTED
MANUFACTURERS FALL-OUT INTE-
GRATED CIRCUITS INCLUDING LOGIC
74 SERIES LINEAR and AUDIO AMPLIFIERS

MANY CODED also SOME UNKNOWN
TYPES — YOU TO IDENTIFY

PAK NO. M.I.C. 200

PRICE £1.25 per PAK including p & p & V.A.T.

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units.
These are classed as "out-of-spec" from the maker's very rigid specifications, but
are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	=12 x 7400	0.55	UIC46	=5 x 7446	0.55	UIC90	=5 x 7490	0.55
UIC01	=12 x 7401	0.55	UIC48	=5 x 7448	0.55	UIC91	=5 x 7491	0.55
UIC02	=12 x 7402	0.55	UIC60	=12 x 7450	0.55	UIC92	=5 x 7492	0.55
UIC03	=12 x 7403	0.55	UIC61	=12 x 7451	0.55	UIC93	=5 x 7493	0.55
UIC04	=12 x 7404	0.55	UIC63	=12 x 7453	0.55	UIC94	=5 x 7494	0.55
UIC05	=12 x 7405	0.55	UIC64	=12 x 7454	0.55	UIC95	=5 x 7495	0.55
UIC06	=8 x 7406	0.55	UIC60	=12 x 7460	0.55	UIC96	=5 x 7496	0.55
UIC07	=8 x 7407	0.55	UIC70	=8 x 7470	0.55	UIC100	=5 x 74100	0.55
UIC10	=12 x 7410	0.55	UIC72	=8 x 7472	0.55	UIC121	=5 x 74121	0.55
UIC20	=12 x 7420	0.55	UIC73	=8 x 7473	0.55	UIC141	=5 x 74141	0.55
UIC30	=12 x 7430	0.55	UIC74	=8 x 7474	0.55	UIC151	=5 x 74151	0.55
UIC40	=12 x 7440	0.55	UIC76	=8 x 7476	0.55	UIC154	=5 x 74154	0.55
UIC41	=5 x 7441	0.55	UIC80	=8 x 7480	0.55	UIC193	=5 x 74193	0.55
UIC42	=5 x 7442	0.55	UIC81	=5 x 7481	0.55	UIC199	=5 x 74199	0.55
UIC43	=5 x 7443	0.55	UIC82	=5 x 7482	0.55			
UIC44	=5 x 7444	0.55	UIC83	=5 x 7483	0.55			
UIC45	=5 x 7445	0.55	UIC86	=5 x 7486	0.55			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

2 Amp. BRIDGE RECTS.
50 v RMS 35p each
100 v RMS 40p ..
200 v RMS 45p ..
400 v RMS 50p ..
1,000 v RMS 55p ..
Size 16 mm x 16 mm.

D1699 NPN SILICON
DUAL TRANSISTOR
(Similar to 2N2050)
1 25 100+
0.28 0.26 0.28

LINEAR INTEGRATED CIRCUIT PAKS
ULIC709 10 x 709 .. 0.55
ULIC710 7 x 710 .. 0.55
ULIC741 7 x 741 .. 0.55
ULIC747 5 x 747 .. 0.55
ULIC748 7 x 748 .. 0.55

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price 2p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.55
U 2	Mixed Germanium Transistors AF/RF	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA6, OA47	0.55
U 4	Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0.55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0.55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.55
U10	20 BA750 charge storage Diodes DO-7 Glass	0.55
U11	PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.55
U13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0.55
U14	150 Mixed Silicon and Germanium Diodes	0.55
U15	NPN Sil. Planar Trans. TO-5 like BFY61, 2N697	0.55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.55
U19	Silicon NPN Transistors like BC108	0.55
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0.55
U23	MADT's like MHz Series PNP Transistors	0.55
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.55
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0.55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1.10
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0.55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.55
U36	Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.55
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 2S322	0.55
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.55
U39	30 R.F. Germ. PNP Transistors 2N1303/5 TO-5	0.55
U40	10 Dual Transistors 5 lead TO-5 2N2060	0.55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.55
U44	20 Sil. Trans. Plastic TO-5 BC115/116	0.55
U45	7 3A SCR. TO86 up to 600PIV	1.10
U46	20 Unijunction transistors similar to TIS43	0.55
U47	10 TO220AB plastic triacs 50V 5A	£1.10
U48	9 NPN Sil. power transistors like 2N3055	£1.10
U49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	£1.10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE
One 55p Pak of your
own choice free with
orders valued £4 or over

CADMIUM CELLS
ORP12 48p

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A	
50	0-05	0-06	1N4001	0-05	0-08	0-15	0-21	0-60
100	0-05	0-07	1N4002	0-06	0-10	0-17	0-23	0-75
200	0-06	0-10	1N4003	0-07	0-12	0-22	0-25	1-00
400	0-08	0-15	1N4004	0-08	0-15	0-20	0-28	1-25
600	0-09	0-17	1N4005	0-10	0-18	0-26	0-35	1-90
800	0-12	0-19	1N4006	0-11	0-20	0-28	0-35	2-10
1000	0-14	0-20	1N4007	0-12	0-25	0-48	0-65	2-50
1200	—	0-25	—	0-30	0-58	0-75	3-00	—

NEW LOW PRICED TESTED S.C.R.'s

PIV	1A	3A	5A	5A	7A	10A	16A	30A
50	0-26	0-28	0-39	0-39	0-52	0-55	0-64	1-27
100	0-28	0-37	0-52	0-52	0-55	0-64	0-70	1-84
200	0-39	0-41	0-64	0-64	0-83	0-83	1-76	—
400	0-48	0-52	0-82	0-82	0-74	0-83	1-03	1-93
600	0-59	0-63	0-75	0-75	0-85	1-07	1-38	—
800	0-70	0-77	0-88	0-88	0-99	1-32	1-65	4-40

DIACS
FOR USE WITH
TRIACS.
BR100 (D32) 25p each

TRIACS
VBOM 2A 6A 10A
TO-5 TO-66 TO-48

	P	P	2p
100	33	55	83
200	55	86	99
400	77	83	1-21

10 amp POTTED
BRIDGE RECTIFIER
on heat sink.
100PIV. 99p each

2N3055
115 WATT SIL
POWER NPN
55p EACH

Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS
Postage and packing add 15p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.
Guaranteed Satisfaction or Money Back

THINGS TO COME

WITH the year of 1974 almost behind us—what of 1975? During 1974 Practical Wireless introduced to the constructor the first build-it-yourself TV tennis game and now it is universally known as P.W. Tele-Tennnis.

The popularity of this design has been immense, and to those readers who visited our stand at the recent International Audio Festival & Fair especially to see P.W. Tele-Tennis in operation, we trust that you all got your chance to have a go—despite the queues. Interest was high, especially with regard to our new range of constructional projects that were on display and that we have especially commissioned for the New Year. To start 1975 off, we are featuring in the January issue of Practical Wireless Part 1 of a constructional series on model control by radio. A radio controlled boat—using the system to be described—was on display on our stand at the Audio Fair.

A new version of the popular Texan Amplifier was also on display. This was of Swedish origin and the manufacturers expect to introduce the kit to the U.K. market during 1975. Known as the Texan U66, it had in addition to numerous extra features, a push button FM tuner! We shall be giving brief details of this interesting design in our February issue.

Author, Richard Mann of Texas Instruments Limited, designer of the original P.W. Texan amplifier is currently engaged in updating and uprating the original design. This amplifier was especially designed for Practical Wireless magazine by Richard Mann in 1972. Full constructional details on this Mk II version will be published in Practical Wireless during 1975.

The February issue of Practical Wireless features the P.W. Ascot Stereo Cassette Deck. Especially designed for home hi-fi systems, it utilises a Goldring tape transport mechanism and also includes dynamic noise reduction. Start building the P.W. Ascot with the February issue.

Our March issue will feature Part 1 of the P.W. Easy-Build Electronic Organ—for use with home hi-fi systems. For those readers who require further details of these unique P.W. constructional projects and do not want to miss other new and exciting P.W. constructional designs that will be appearing in 1975 we recommend that you order P.W. on a regular basis.

To our many readers
wherever you may be—
the Editor and staff of
PRACTICAL WIRELESS
wish you all
seasonal greetings
and a prosperous 1975.

Do not miss out—place a regular order with your local newsagent or alternatively write to our Subscription department, details are given on page 777.

LIONEL E. HOWES—Editor.

NEWS...

'Look ahead' Radar

LARGE modern tankers may have little time to spare for manoeuvre in a potentially dangerous situation. A fully automatic radar system can speed up the work of the watch officer and provide those extra vital seconds. With this in mind, four new Shell tankers are getting the Predictor system of anti-collision radar. Predictor was developed by Marconi Marine with co-operation from Shell International Marine.

When the equipment is fitted to the new tankers Limnea, Liparus and Lancella (all 300,000 tonners) and the liquified natural gas carrier Genota, 15 Shell tankers will be carrying Predictor radar.

Predictor was the first commercial radar system which released the navigating officer from the task of manually assessing other ships' movements. As its name implies, it enabled him to 'see ahead'. Predictor gives the navigating officer an accurate prediction of the effect a contemplated change of course or speed by his ship would have on the entire radar scene, before he actually takes any such action.

Predictor was also the first system to provide fully automatic plotting of all targets visible on the radar screen. It shows up all above-surface objects—ships, coastlines or buoys—in its area. Simply by pressing a switch, and without the need for any prior action or calculation, the tracks of all fixed and moving objects are plotted continuously. The Predictor presents them either in relative motion—relative, that is, to the radar-carrying ship in its present position—or true motion. The plot is updated every 10 seconds, but situations up to 18 minutes previously can be shown.

When the Predictor system was originally being developed, Marconi approached members of Marine Operational Services division in Shell International Marine. They were sufficiently impressed with the Predictor approach to suggest that when a prototype model was available it should be tested on a Shell tanker.

Practical Wireless Tele-Tennis on BBC's "Nationwide" programme



MIKE HUGHES, the author of *P.W. Tele-Tennis*, was recently interviewed on BBC's "Nationwide" programme.

It was suggested by the interviewer, pretty Suzanne Hall, that all the equipment one required for playing our armchair tennis game was a soldering iron and a pair of slippers!

It was stated on the programme that most of the 12,000 television tennis games are situated in pubs and clubs but the *Practical Wireless* design was the only do-it-yourself game available for the home constructor.

Mike Hughes explained to viewers that the *P.W. Tele-Tennis* had been designed with the home constructor in mind and that it employed integrated circuits and printed circuit boards. The aver-

age constructor could build it providing he had some ability to carry out the soldering and follow a circuit layout.

When asked how the Tele-Tennis worked in relation to an ordinary television set, Mike Hughes explained that at the back of the Tele-Tennis case, there was a socket, just like the aerial socket on the back of a TV receiver. All that was needed was a length of cable like TV aerial downlead cable with a standard co-axial plug each end. One end plugged into the game and the other end plugged into the TV aerial socket. The game was then connected to the mains and switched on. The next move was then to tune the TV to a spare channel just as if one were tuning in a normal television programme.

Suzanne Hall asked if the unit could be adapted to play other games and Mike Hughes replied, "Yes, in fact the basic game we are looking at here is very fundamental. It can be turned into a football or basket-ball game but I must admit some of them stretch the imagination a little."

Mike then played a few games of Tele-Tennis with Suzanne Hall and explained to viewers that he was not the real expert. The Tele-Tennis 'champ' was his seven-year-old son, Andrew.

Admitting defeat, Suzanne concluded the interview and admitted she was not quite quick enough on the trigger. She told Mike Hughes that she would have to have a lot more practice before she could win a game of Tele-Tennis.

Mullard Data Book

A NEW feature of the 1974/75 edition of the Mullard Data Book is brief data on radio, audio and TV modules and TV assemblies.

The traditional formula has been changed slightly to show ICs separately. The full ranges of valves, TV picture tubes, semiconductors, capacitors, resistors and other components for entertainment applications are fully covered.

As before, different coloured papers are used for each of the main products sections, i.e. blue for semiconductors and ICs;

orange for valves and TV picture tubes; green for capacitors, resistors, modules and assemblies.

Copies may be obtained from local booksellers or *Technical Press Limited, Freeland, Oxford OX7 2AP.* for 40p.

IBA Journal

THE Independent Broadcasting Authority has launched a new quarterly journal of opinion with the object, as the foreword describes, "Of presenting the opportunity to provide frank accounts of the problems the Authority must face and the

elements which go into deciding its policies and plans".

The journal is also to give a wide range of people, as well as those engaged in broadcasting, a chance to present their own views about the many opinions expressed in it or to raise any fresh issues for examination in future editions.

The first issue contains articles on "Impartiality in Broadcasting", "Future pattern of the ILR", "Television Coverage", "Role of Television in Science Education."

For further information, contact the *Editor, Independent Broadcasting, IBA, 70 Brompton Road, London, SW3 1EY.*

low frequency & marine receiver

PART
1

CHARLES HEATH

MANY receivers provide no tuning coverage over the frequency range of about 300kHz to 550kHz, this being the "gap" between the long wave band of approximately 150-300kHz, and the medium wave band extending from about 550kHz to 1,500kHz. Such receivers usually have an intermediate frequency of around 470kHz, which lies between these LW and MW bands.

By adopting an IF of 1.6MHz it is possible to arrange tuning to give continuous coverage, thereby including the 600m or 500kHz shipping band, as well as other signals using adjacent frequencies. The receiver described here does in fact have three bands, with continuous coverage from 150kHz to 5MHz (except for a small gap at the 1.6MHz IF). These ranges therefore include ship and shore; 1.8-2.0MHz and 3.5-3.8MHz amateur bands; 2.5MHz standard frequency transmissions; other signals in these ranges, as well as the usual medium and long wave bands.

Ranges are selected with a bandswitch, and are approximately as follows:

Range 1.	150-470kHz.	2000-640m.
Range 2.	470-1500kHz.	640-200m.
Range 3.	1.55-5.0MHz.	190-60m.

The receiver will operate with AM (amplitude modulation), CW (Morse) and SSB (single sideband) signals, which will be found in the broadcast, amateur, and other bands covered.


Circuitry is confined to three boards; mixer, oscillator and IF sections, BFO unit, and 3-stage audio amplifier.

MIXER AND OSCILLATOR

Fig. 1 shows this part of the circuit. S1 and S2 select the aerial coils L1, L2 or L3 as required. S3 and S4 are the remaining sections of the 3-way switch, and select oscillator coils L4, L5 or L6, each with its own padder capacitor, C7, C8 or C9.

The $2 \times 500\text{pF}$ tuning capacitor VC1/2 is operated by a dual ratio ball drive. As a panel trimmer TC1 is provided, with a fixed capacitor, C10, in the oscillator section, individual trimmers for each coil are not necessary. Even if individual trimmers were fitted for each range, changes to the aerial might upset alignment, while the use of TC1 does make sure this circuit can be peaked up at any frequency.

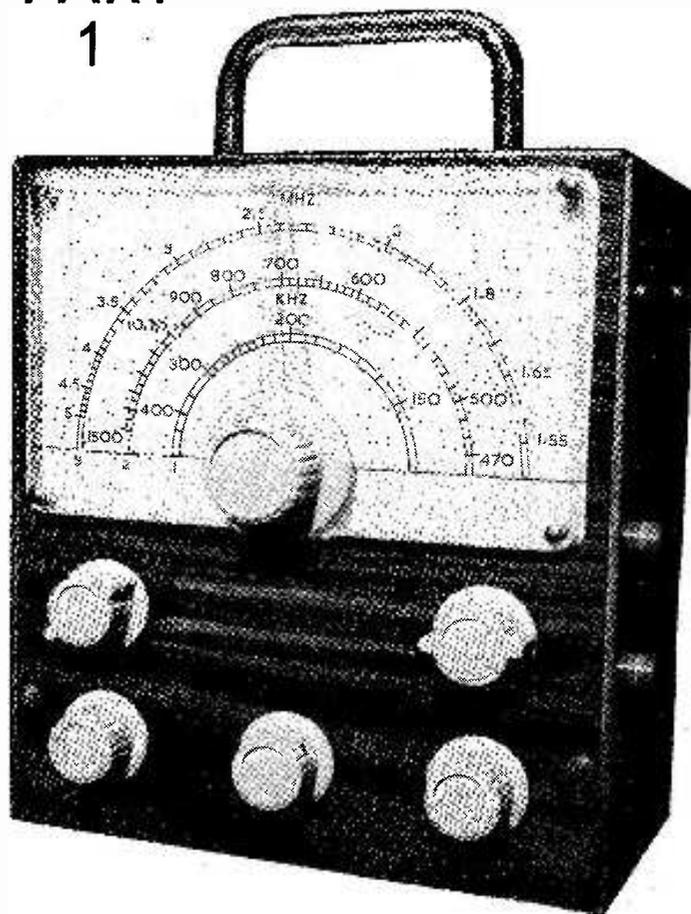Tr1 is gate-protected, with signals at gate 1, oscillator injection at gate 2, and the drain circuit running to the first IF transformer.



IF AMPLIFIER

This is on the same board, using the circuit in Fig. 2, and operates at 1.6MHz. IFT1 and IFT2 are double tuned, and IFT3 is single tuned. These IFT's are pre-set by the manufacturer, the cores of which should not be adjusted except for final alignment after construction is completed.

Automatic gain control is applied to Tr3 through R12 and R7 in the usual way, while VR1 constitutes the audio gain or volume control.

R9 can be 560 ohms. However, the actual gain of Tr3 and Tr4 may vary quite widely. If gain is high, instability arises, and whistles accompany all signals. It is then necessary to increase R9 in value. On the other hand, where gain is low, R9 can be of lower value, or might in some cases be omitted completely. R9 therefore is not critical, but efficiency is at a maximum when the value here is the lowest which prevents instability. There is probably no point in having available more than three or four possible values, such as 100, 330, 560 ohm, and perhaps 1k Ω .

BFO UNIT

The beat frequency oscillator is constructed on a separate board, using the circuit in Fig. 3. (If this section is omitted, the receiver is suitable for reception of AM only, from 150kHz to 5MHz.)

The BFO operates at 1.6MHz, and is set to this frequency by rotating the core of L7, with VC4 half

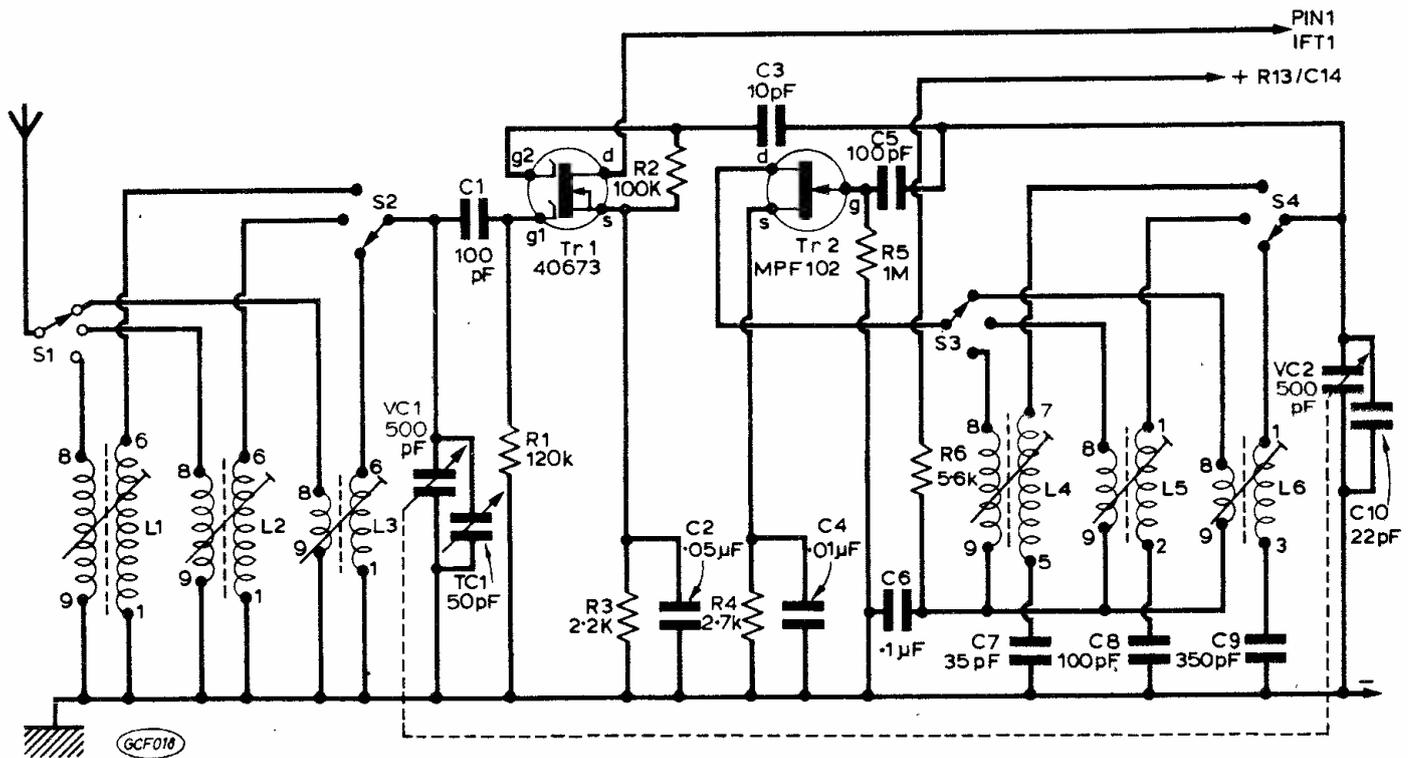


Fig. 1: Circuit of the mixer and oscillator stages of the Marine receiver. For simplicity the remaining stages are shown as separate diagrams. Band switches S1 to S4 are ganged.

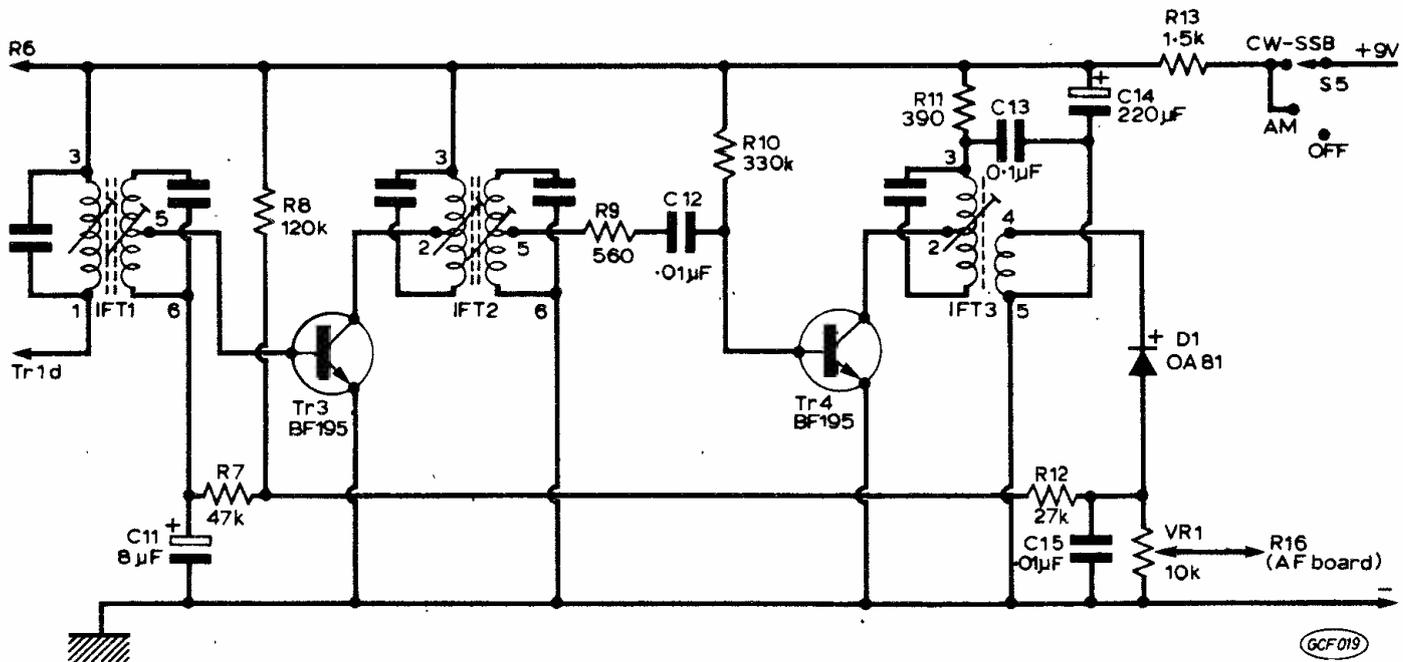


Fig. 2: The IF amplifier, circuit shown here, is built on a common circuit board with the mixer/oscillator.

closed. The frequency can then be shifted either side the IF by turning VC4. This allows an audible beat frequency to be obtained for CW reception, or allows the reception of SSB signals by adjusting the oscillator to the frequency of the suppressed carrier.

S5 (Fig. 4) and S6 has three positions, these being "Off," "AM" and "CW-SSB" reception. Tr5 operates in the last position only. The large capacitor C19 prevents frequency modulation at voice frequency by smoothing out the fluctuating current demand on the battery made by the output stage, at other than

low-volume levels.

AUDIO AMPLIFIER

This has three stages and is constructed on its own board (Figs. 4 and 9). Tr6 is a pre-amplifier, followed by the driver Tr7, and push-pull output stage Tr8/9. Quiescent current is pre-set by the adjustable resistor VR2, which gives good gain and volume, depending upon operating conditions and transistors used. It is preferable that Tr8/9 are a matched pair. Many other transistors of comparable type will be suitable as driver and for output purposes.

★ components list

Resistors

R1 120k Ω
 R2 100k Ω
 R3 2.2k Ω
 R4 2.7k Ω
 R5 1M Ω
 R6 5.6k Ω
 R7 47k Ω
 R8 120k Ω
 R9 560 Ω
 R10 330k Ω
 R11 390 Ω
 R12 27k Ω
 R13 1.5k Ω
 VR1 10k Ω log potentiometer

Capacitors

C1 100pF
 C2 0.05 μ F
 C3 10pF
 C4 0.01 μ F
 C5 100pF Silver Mica
 C6 0.1 μ F
 C7 35pF 1% Silver Mica
 C8 100pF 1% Silver Mica
 C9 350pF 1% Silver Mica
 C10 22pF SM
 C11 8 μ F 6.4V electrolytic
 C12 0.01 μ F
 C13 0.1 μ F
 C14 220 μ F 10V electrolytic
 C15 0.01 μ F
 VC1/VC2 Polar 2 x 500pF gang with feet. (Home Radio)
 TC1 50pF Jackson C804

Inductors

L1 Blue, Range 1
 L2 Blue, Range 2
 L3 Blue, Range 3
 L4 White, Range 1
 L5 White, Range 2
 L6 White, Range 3
 All miniature, valve type (Denco)

Semiconductors

Tr1 40673
 Tr2 MPF102
 Tr3 BF195
 Tr4 BF195
 D1 OA90

Miscellaneous

IFT1/2 (Denco IFT18/1-6), IFT3 (Denco IFT17),
 Veroboard (0.15in. matrix,) 3½ x 4in., Switch (S1-S4)
 4-pole 3-way rotary.

BFO BOARD

Resistors

R14 270k Ω
 R15 5.6k Ω

Capacitors

C16 180pF
 C17 330pF Silver Mica
 C18 5000pF
 C19 220 μ F 10V electrolytic
 VC4 15pF Jackson C804

Inductors

L7 55 turns 32swg enamelled wire on 7/16 in.
 diameter cored former.

Semiconductors

Tr5 BC107

Miscellaneous

Veroboard (0.15in matrix) 2½ x 2½in., Switch (S5-S6)
 2-pole 3-way rotary.

AUDIO BOARD

Resistors

R16 1k Ω
 R17 2.2M Ω
 R18 10k Ω
 R19 2.2k Ω
 R20 12k Ω
 R21 47k Ω
 R22 680 Ω
 R23 10k Ω
 R24 10k Ω
 R25 4.7 Ω
 All resistors 5% ¼W
 VR2 250 Ω miniature pre-set potentiometer

Capacitors

C20 0.5 μ F
 C21 100 μ F 10V electrolytic
 C22 8 μ F 6.4V electrolytic
 C23 100 μ F 10V electrolytic
 C24 100 μ F 6.4V electrolytic

Semiconductors

Tr6 BC107
 Tr7 AC128
 Tr8 AC128 } matched pair
 Tr9 AC128 }

Miscellaneous

T1 (Home Radio TR64), T2 (Home Radio TR65A),
 Veroboard (0.15in. matrix) 4½ x 2in.

CABINET ETC.

8 x 7 x 4in. universal chassis box with extra 7 x 4in.
 flanged side and 7 x 8in. flat plate.
 DL6 dual-ratio drive (Home Radio, Mitcham). Knobs,
 rubber or plastic feet, insulated sockets, bolts and
 tags etc. Battery PP9, with terminal clips.

MIXER/OSC./IF BOARD

These stages are assembled on plain Veroboard, approximately 3½ x 4in in size, and perforated with holes on a 0.15in matrix. It would be possible to use plain unperforated 1/16in thick paxolin sheet, drilling this in advance for resistors and other items.


Holes are drilled so that the IFT pins come as in Fig. 6. Central holes to reach the cores are necessary under IFT1 and IFT2.

A metal bracket approximately 3 x 1¼in with a 5/8in flange is drilled for the switch and TC1 (Fig. 5), and bolted to the insulated board. (A piece cut from a flanged universal chassis member is ideal here.) Components can then be fitted as in Fig. 5, taking care to observe the polarity of C11, C14 and D1.

When starting the construction, it will be found that the easiest method is to fit a few items at a time, then turn the board over, and solder connections as in Fig. 6. In some places 24swg or similar connecting

wire will be necessary. Place sleeving on any leads which may touch other wires or joints.

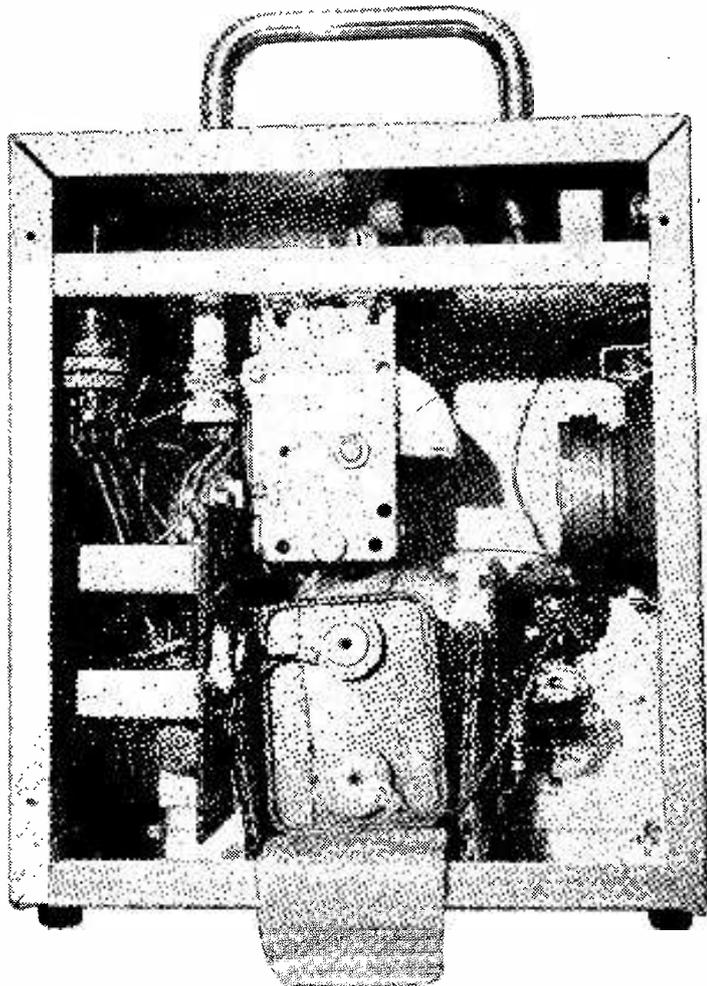It can be a little confusing to check the leads of Tr1 and Tr2 when these are fitted. This can be overcome by using short pieces of coloured sleeving and referring to Fig. 6. For example Tr1, blue can be used for g1, green for g2, orange for d, and s can be left bare. Tr2 on the other hand can have blue for g, orange for d, and leave s bare.



Inside the Marine receiver with the audio board across the top, the mixer/oscillator board at the left and BFO board to the right.

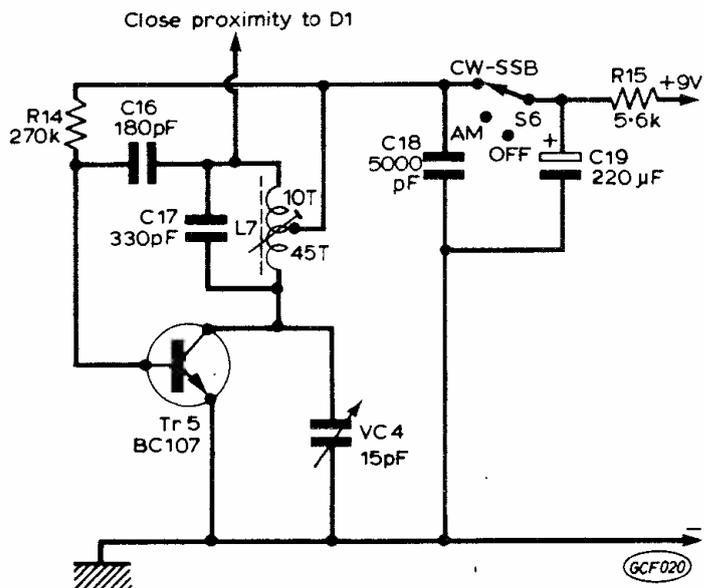


Fig. 3: Circuit of the BFO unit. Below, view of the receiver with casework removed.


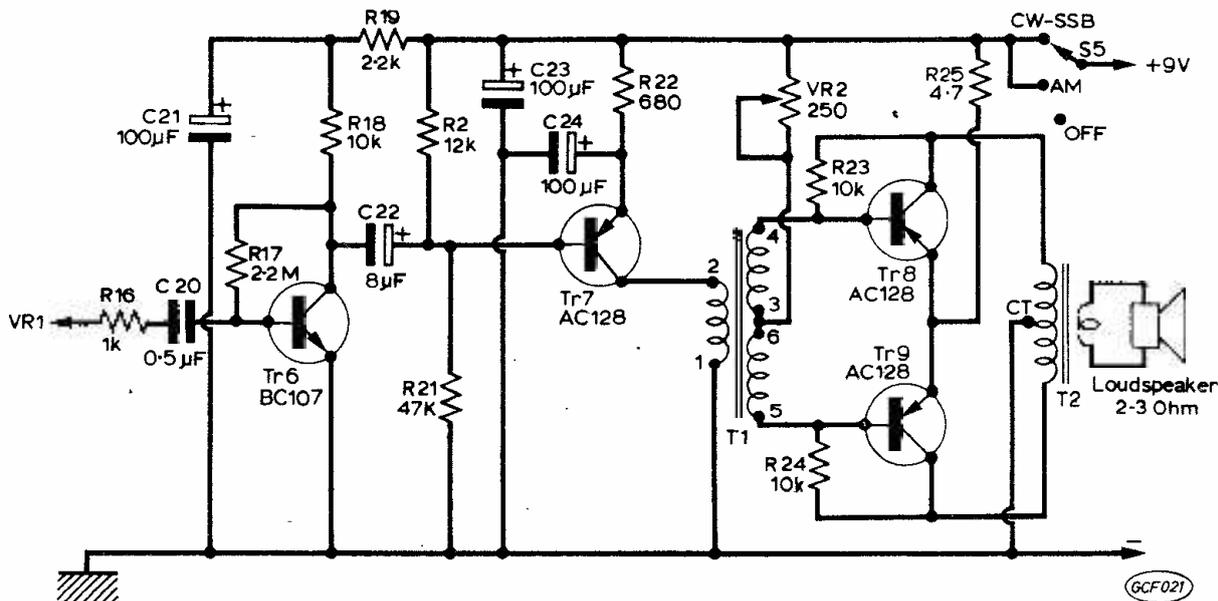
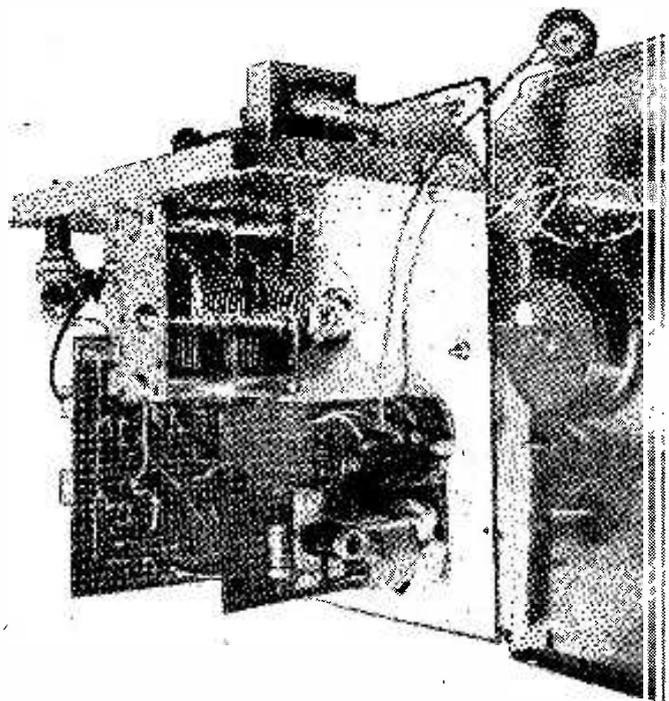
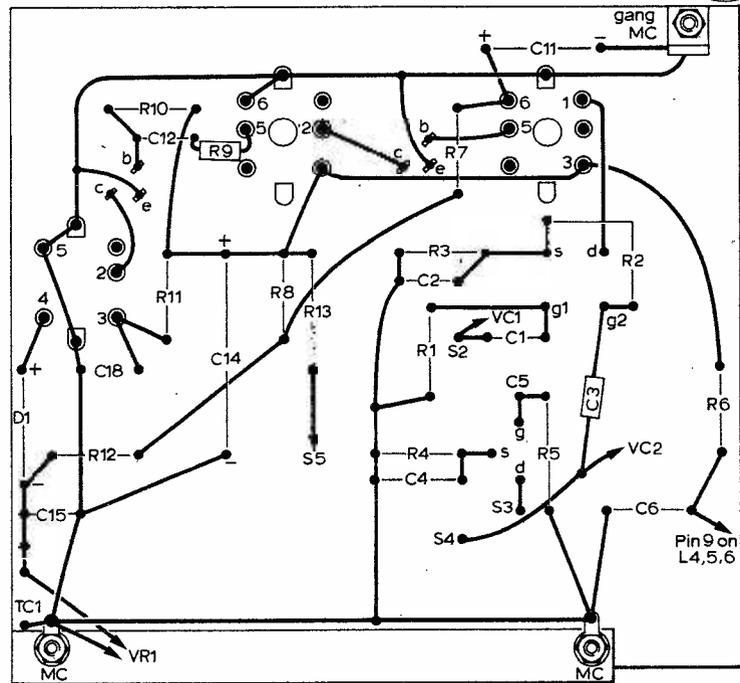


Fig. 4: The final circuit is of the audio amplifier. The speaker is fitted over a suitable aperture in the side of the case.

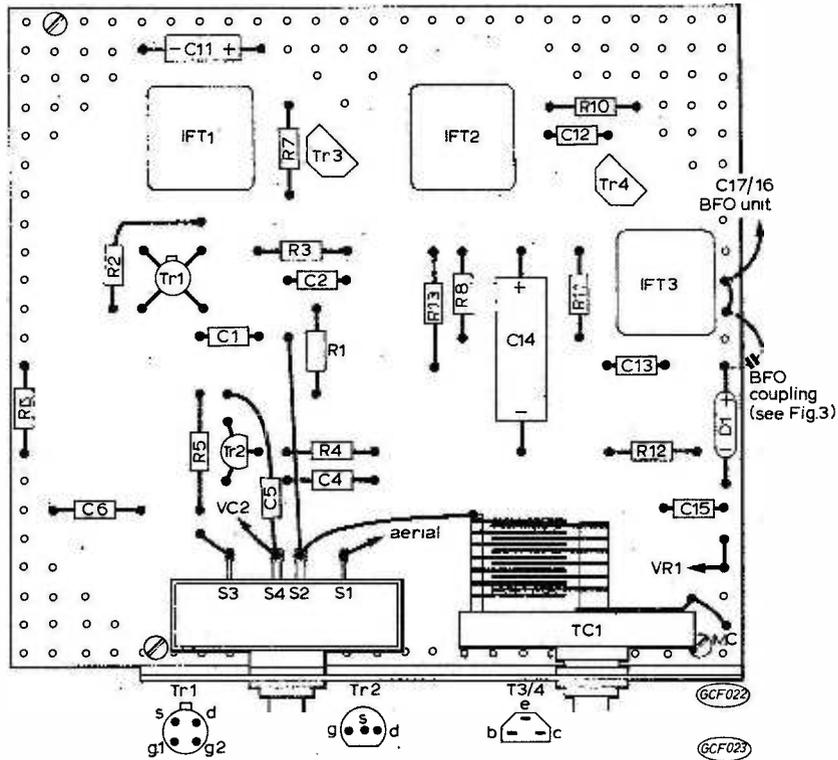

Figs. 5 and 6: Component layout and wiring of the combined mixer/oscillator and IF amplifier board.

R9 is soldered directly to pin 5 of IFT2, enabling it to be changed easily if this proves necessary. Flying leads are provided from D1 and C15 to go to the volume control and chassis return (Fig. 6). Connections also rundown through the board to go to VC1 and VC2 and to L4, L5 and L6. The switch and TC1 are now fitted, but the bush nuts of these are later used to hold the assembly to the front of the case.

BFO UNIT

Prepare another metal bracket as already described, and bolt Veroboard approximately $2\frac{3}{4} \times 2\frac{3}{4}$ in to this, as in Fig. 7. The nuts holding VC4 and the switch will eventually secure this unit to the panel, as with the earlier board.

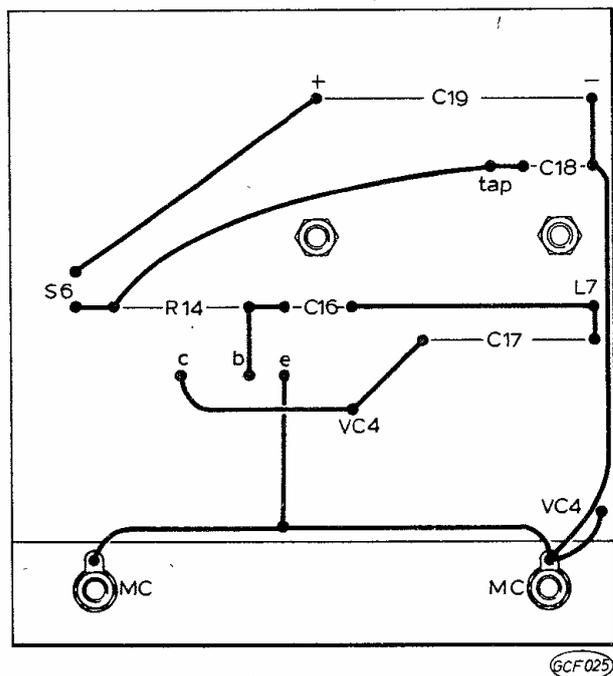
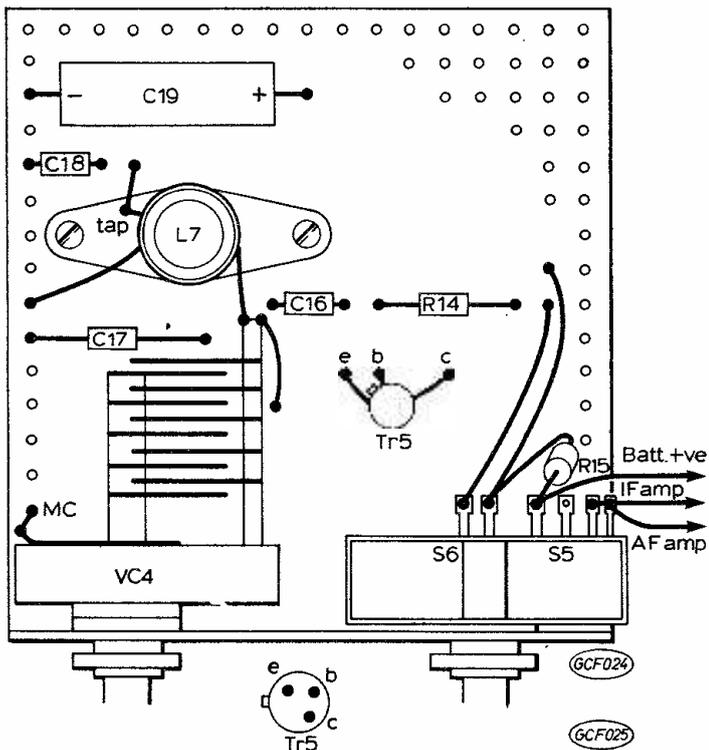


Fig. 7: above and Fig. 8, right, show both sides of the circuit board for the BFO unit.

L7 has 55 turns of 32swg enamelled wire, close wound on a 7/16in diameter former with adjustable core. Begin at the bottom of the former, leaving an end to reach to VC4 as in Fig. 7. Wind 45 turns, scrape the wire, and form a loop or tapping. Continue winding for another 10 turns, and take the wire down through the board to C17.

Wire switch S5/S6 as follows:

- (1) Off.
- (2) Battery positive to IF and AF amplifiers.
- (3) Battery positive to IF and AF amplifiers, and BFO Unit via R15 and C19 and S6.

Fig. 8 shows the underside of the BFO unit board. As mentioned, normal AM reception is obtained without this in use, so it can be built and added later if preferred.

PART 2 NEXT MONTH ON ALIGNMENT AND TESTING

Pw at the audio fair

In the picture below, visitors to the Audio Fair gather round our stand to watch Tele-Tennis on the JVC "Videosphere".

The Top-right photograph shows a typical crowd round the stand. It was like this every day of the exhibition.

(Bottom right) Two visitors play Tele-Tennis while two pretty P.W. readers study some Data Cards.



**complete
your HI-FI
system...
with our**


**IN NEXT MONTH'S
PRACTICAL
WIRELESS**

**P^W
'ASCOT' STEREO
CASSETTE DECK**

A stereo cassette deck designed especially for the home constructor, using the Goldring-Lenco CRV front-loading tape transport mechanism. Features include dynamic noise reduction circuitry, inputs for microphones and radio, and a pre-monitor facility which allows the sound levels to be set before recording commences. Separate record and replay amplifiers and electronic switching greatly reduce mechanical complexity.



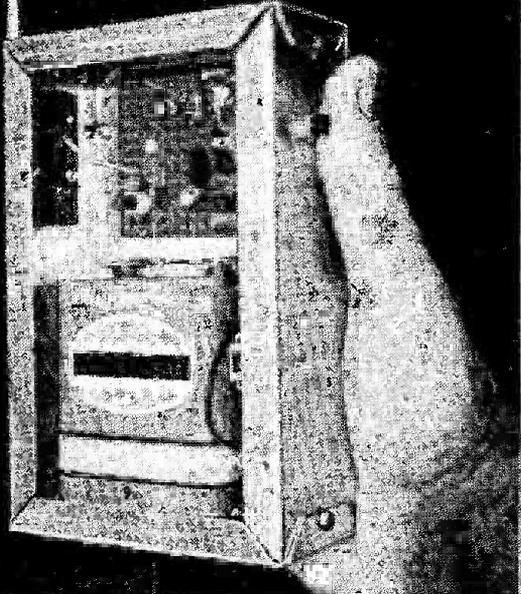
**RADIO CONTROL
SERIES—PART 2
The TRANSMITTER**



**HOME
TELEPHONE
EXCHANGE**

**ON
SALE IN
JANUARY**

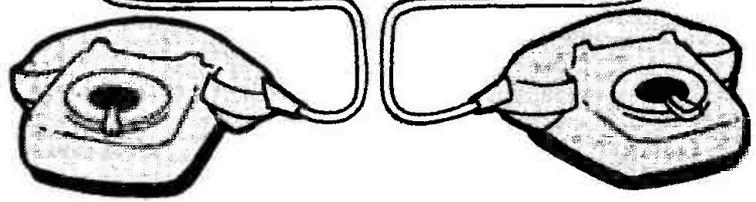Completely silent . . . except for the bell!
A single PCB provides facilities for up to
nine subscribers. Solid state switching
using reed relays. Mains operation,
taking just three watts. Overall size an
unbelievable 5" x 5" x 8" long.





With the Doram catalogue, even the guarantee is guaranteed.

Doram is an entirely new way of buying electronic components.

So, to succeed, it's got to have something going for it, right?

We agree with you. And where Doram scores is in the security it gives the amateur buyer.

We'll give you peace of mind three ways.

No-quibble guarantee.

Firstly, we guarantee to replace any component which arrives faulty. Absolutely free of charge.

And secondly, our guarantee is backed by the biggest electronics distribution Group in Britain.

7-day service.

Thirdly, we guarantee you'll have your components within 7 days from our receipt of your orders.

We're so confident of our service that if we can't supply

the part you want within 7 days we'll give you an immediate refund.

So you'll never get a tedious wait.

You know just where you stand with Doram.

All branded goods.

All goods supplied by Doram are made by big-name manufacturers. And they're all to manufacturer's specifications. They're the best money can buy.

In fact, Doram gives the amateur the sort of service only professionals have enjoyed before.

Millions of components.

All in all, we're big enough to offer you stocks of millions of components, on over 4,000 product lines.

All you do is buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint of lager) and then take your pick from it.

Use the coupon now. Send today for the first-ever Doram catalogue. It can take a lot of worry out of amateur components buying.

And for 25p that's not bad, is it?

I ENCLOSE 25p* PLEASE SEND ME THE NEW DORAM CATALOGUE.

Name.....

Address.....

Doram Electronics Limited,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

DORAM

PW/1175

PRODUCTION LINES

colin riches

EMITAPE X1000

EMITAPE X1000 a new ultra dynamic ferric oxide cassette—has been introduced by EMI Tape Ltd., at the recommended retail price of 99p for a C.60 (excluding VAT).

Having satisfied itself of the tape's characteristics under laboratory conditions EMI Tape adopted the move of proving the tape in the way that hi-fi enthusiasts will judge it—by its sound reproduction qualities under user conditions.

To this end a programme of comparative listening tests was mounted over a three-month period. Under the adjudication of Mr. Denys Killick, who is publisher and editor of Hi-Fi Trade Journal as well as being audio editor of Cassettes and Cartridges, these tests set out to determine whether leading musicians and others representing the many sectors of music today—from the classics to pop—could discriminate in 'blind' tests between X1000 and expensive chrome formulations.


To ensure absolute impartiality in the tests, the performance of the Tandberg cassette decks used was checked to specification by Tandberg engineers and the recorders sealed by Denys Killick.

Music was recorded onto standard production cassettes—both X1000 and chrome—from EMI master tapes at Abbey Road under the scrutiny of Denys Killick and two senior audio engineers from AIR London, the biggest independent studios in London.

Later, at a series of listening tests the cassettes were played back—under supervision—to the musicians who made the original recordings ranging from the L.S.O. to the Spinners folk group.

In every case the participants were asked to record their opinions on a questionnaire and subsequent analysis of these shows clearly that even the trained ear has difficulty in discerning any difference between X1000 and the expensive chrome cassettes used in the tests.

Mr. Ted Naef, managing director

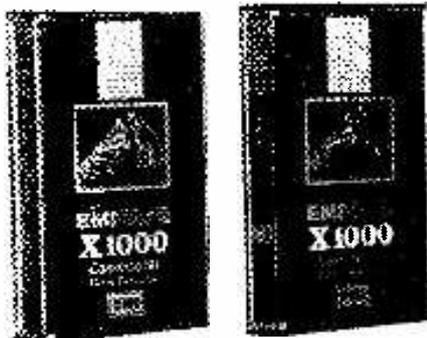

of EMI Tape Ltd., commented "We began our research from the belief that what really matters to an audio enthusiast is the quality of sound he gets from his chosen medium, related to the cost of the product. Our new cassette which gives as pleasing a reproduction as expensive chrome dioxide cassettes is considerably cheaper to buy. In addition X1000 is a much less abrasive tape, and there is no need for a special bias switch on the recording machine. It will without doubt improve the performance of many cassette tape recorders."

The main technical improvements in X1000 are:

- 1) An increase of 3-4dB in the 8-15kHz frequency range, compared to low noise tapes such as EMITAPE Hi-dynamic, giving a more realistic treble resulting in a brighter, more sharply defined sound.
- 2) Superior overload characteristics ensuring low distortion at high recording levels.
- 3) A wider dynamic range is obtained due to the tape's increased magnetic remanence, which results in less tape hiss.
- 4) When used with comparably high quality audio equipment, the tape exhibits a usable frequency response extending from 25Hz to 15kHz, giving a smooth clear bass coupled with crisp treble performance.
- 5) The improved high frequency response ensures a low level of intermodulation distortion providing a cleaner recording.

Further details may be obtained from EMI Electronics and Industrial, Blyth Road, Hayes, Middlesex.

PEAK READING V.U. METER.

Partridge Electronics announce the release of a special V.U. meter system which registers true peak programme levels. This is achieved by the use of a professional grade Bach-Simpson meter with special electronic circuitry, which responds to both positive and negative peaks. It also has an attack and decay time normally only associated with PPMs; and does not suffer from zero drift; is independent of normal voltage fluctuations and therefore requires no setting up. 0dB reading is equivalent to 6 on a standard PPM meter. Operates from a 24 volt positive supply, and only consumes 4mA. This unit fills the gap left between the shortcomings of the conventional V.U. system and high cost PPM units. It will market at £8.32 plus VAT. Partridge Electronics, 21-25, Hart Road, Benfleet, Essex, England. SS7 3PB.

BEYER PHONES

Beyer Dynamic, the West Germany based manufacturer of microphones, headsets and audio equipment, has produced a new headphone, type DT 302.

The DT 302 is a very lightweight headset. This is achieved by the design of the headband, which allows simple adjustment of the ear pieces up or down. These are protected by foam plastic pads eliminating any interference from "local noise", at the same time being exceptionally comfortable to the wearer. Three metres of lightweight cable complete the DT 302

Frequency response is quoted as 20-20,000Hz. Impedance: 2×600 ohms (can be connected directly to either high or low impedance outputs). Rated Power is approx. $7mW=7, IV$ for 600 ohms. The price of this headset is £7.83 plus V.A.T. Beyer Dynamic (GB) Limited, 1 Clair Road, Haywards Heath Sussex.



IN CIRCUIT TESTER

Daystrom-Schlumberger have just released an in-circuit tester designated Type 670. It is aimed at those engineers and constructors who need to take voltage, current and resistance measurements in solid-state circuitry.

With the 670, it is simply a question of connecting the two probes across the current carrying conductor then reading off the value of the current.


To provide this measurement facility—claimed by the manufacturers to be unique for an instrument in its price range—the 670 uses a pair of two-terminal concentric probes. Capable of contacting circuit board rails 0.015in. apart, these specially-designed probes can be snapped together for fixed spacing, or detached for separate use.

One contact in each probe senses the voltage drop across the current-carrying conductor under test. A differential amplifier senses this and generates a bucking current until the voltage drop is balanced. The bucking current is therefore proportional to the circuit current, which is read directly on the meter.

In addition to the "in-circuit" current measuring capability, the FET multi-meter offers eight voltage ranges and fourteen resistance ranges. Seven of the resistance ranges use low-power techniques—max 85mV—for testing semiconductors. Conventional current measurements can

be made with the standard probes also supplied with the "670".

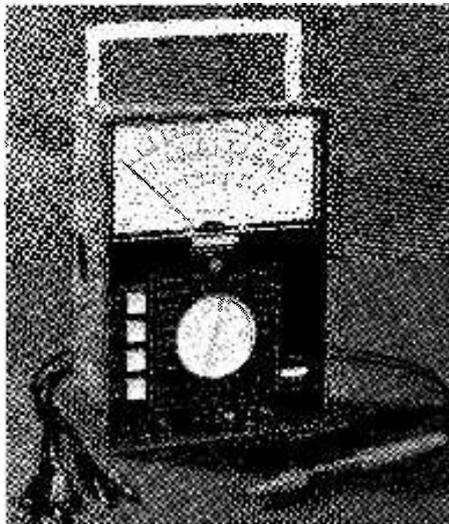The 670 is priced at £132. The kelvin clip probes for "in-circuit" current measurements in solid wire conductors are an optional extra. *Daystrom Schlumberger, Gloucester.*



VIDOR POWER PLUS

Vidor have introduced the Power Plus line of batteries to extend their range.


The Power Plus line comprises six alkaline manganese and five mercury types.

A four-page colour leaflet describing the new batteries is available from: *Crompton—Parkinson Ltd., Vidor Division, 50-52 Marefair, Northampton, NNI 1NY.*

PRINTED CIRCUIT KIT

This printed circuit kit from Eagle International of Wembley, Middlesex contains all the items necessary to reproduce a printed circuit to exact individual requirements. Designated the PK3 it is supplied in a durable case complete with comprehensive instructions.

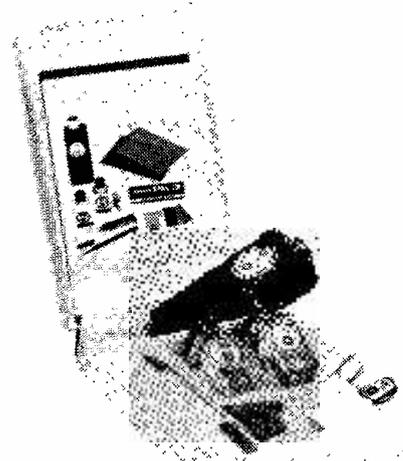The contents of the kit include: polishing powder, etch resist, etching liquid, resist remover, flux, copper clad phenolic circuit boards, stencil knife, spatula and etching tray. Recommended retail price of the PK3 is £2.86 excluding VAT. *Eagle International, Precision Centre, Heather Park Drive, Wembley HA0 1SU.*



BATTERY FLUORESCENT

The Electronics Design Associates' 12V fluorescent lighting kit comes complete with printed circuit board, transformer, ready-drilled metalwork, tube end-caps, components, 8W tube, nuts, bolts etc.


The unit, which only takes about half-an-hour to build up, draws about 0.6A from the battery.

Full instructions for building are supplied with every kit and construction is simplicity itself—all you need to know is how to wield a soldering iron!

At the price of £3.19, which includes post and packing, this kit represents very good value for money and would make a good investment particularly at the time of the year we are often threatened with power cuts.


If you want to order a diffuser to give a really professional finish, there is an extra charge of 59p including VAT (12p post and packing if ordered separately).

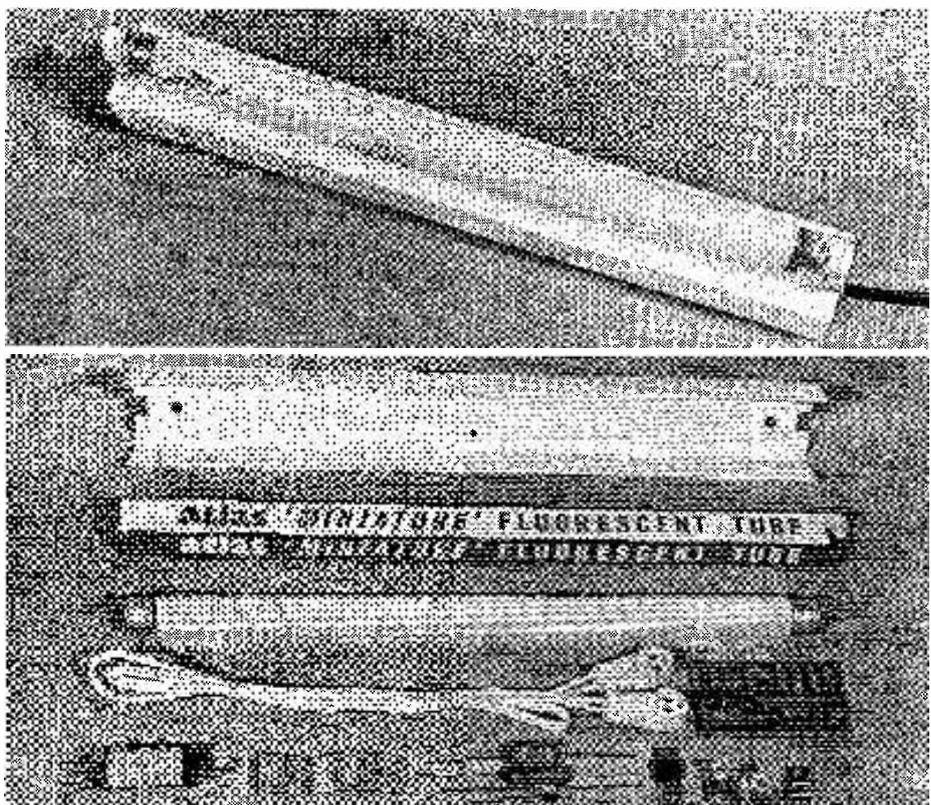The kit is available from *Electronics Design Associates, 82 Bath Street, Walsall, WS1 3DE.*



The built unit and a kit of parts.

An Active Aerial

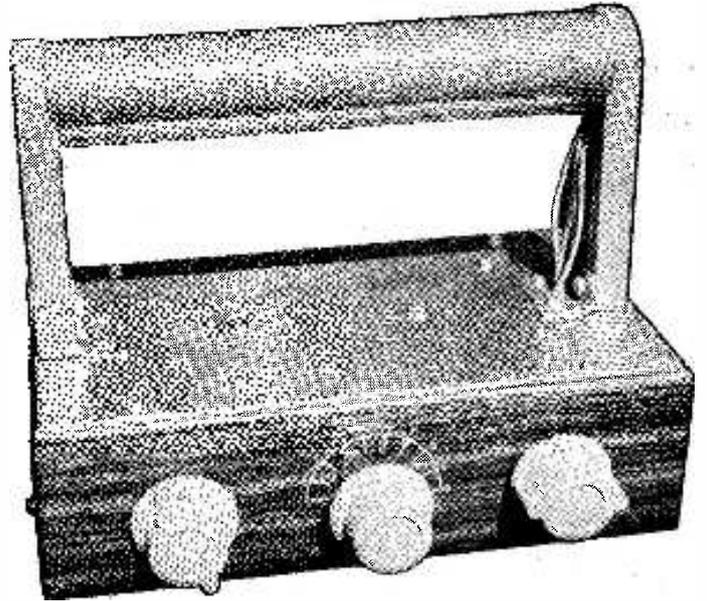

THOUGH this unit is particularly intended for use with the Low Frequency & Marine 3-Band receiver described elsewhere in this issue, it can be employed with other receivers of suitable type, covering tuning long, medium and short wave bands up to 5MHz. It allows such a receiver to be operated without the use of an outdoor or extended wire aerial. The additional tuned circuit also considerably reduces second channel interference.

CIRCUIT

This is shown in Fig. 1, and uses a 3-band ferrite aerial. For LW coverage, S1, is at L, and L1, L2 and L3 are in series, tuned by VC1. L4 and L5 are the base coupling windings for Tr1. For MW reception, S1b shorts the LW coil L3. With the specified ferrite aerial, no switching of the base circuit is necessary for the change to this band. For SW reception, L2, L3 and L5 are shorted, leaving L1 and L4 in use. L6 wound on L1, and L7 situated between L2 and L3 allow an external aerial to be coupled, if wanted.

Transistor Tr1 provides RF amplification; its gain is controlled by VR1. This is necessary to avoid overloading the receiver input. The transistor can be adjusted to be nearly regenerative, giving best sensitivity.

In the 3-band receiver mentioned, the bandwidth selects one of the three aerial coil primaries. This winding is present from Aerial to Earth sockets of the receiver, as in Fig. 1, and forms the collector load for Tr1, and also provides its DC return.

The active aerial unit is constructed in a screened box, except for the ferrite aerial, which is protected by an external insulated tube. The receiver described is also screened, and this prevents unwanted coupling between aerial and Tr1 collector inductors, which would cause feedback.

CIRCUIT BOARD

This is approximately 2½ x 1½in, Fig. 2. Two tags are first secured with ½in 6BA bolts, for the points MC. The resistors and capacitors can then be inserted, and connected as shown, keeping the leads against the board. R3 must be mounted close to the base of Tr1. If wished, R5 can be modified to suit the actual gain of Tr1, though 1.2kΩ is generally satisfactory.

continued on page 813


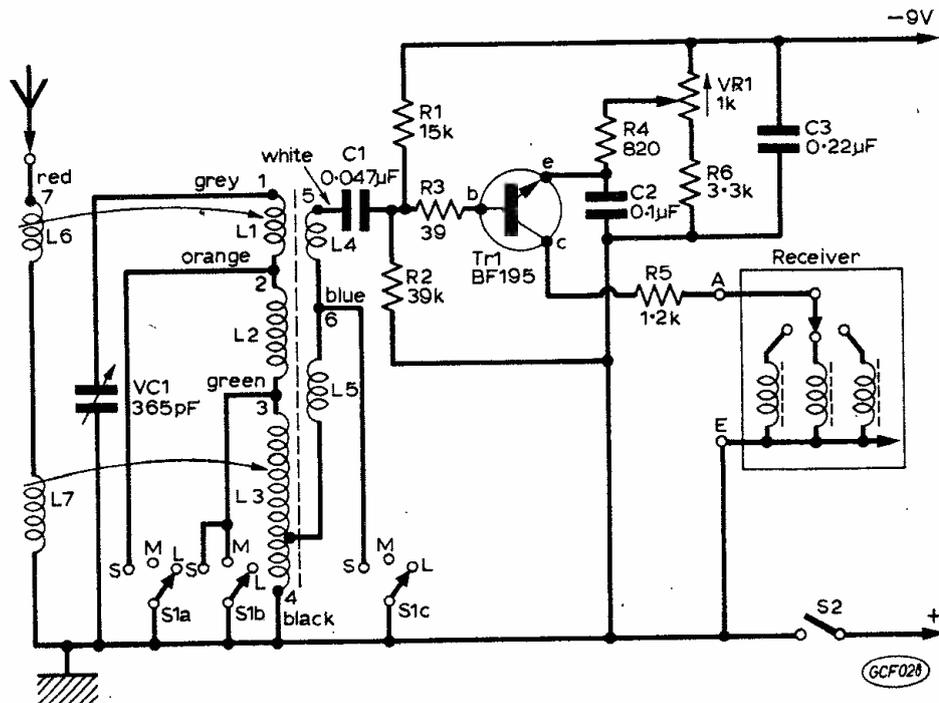
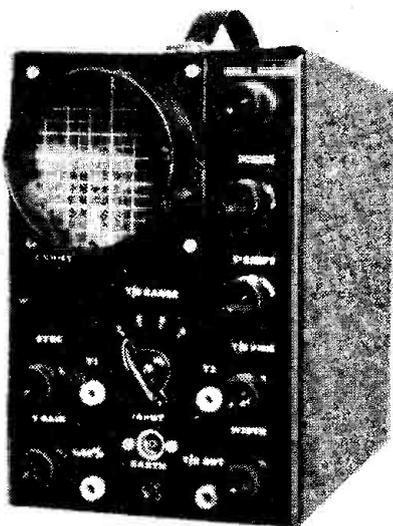


Fig. 1: Circuit of the Active Aerial. It is essential that there is a DC path between the aerial and earth terminals on the receiver being fed by the Active Aerial.

look! electronics really mastered

... practical
... visual
... exciting!

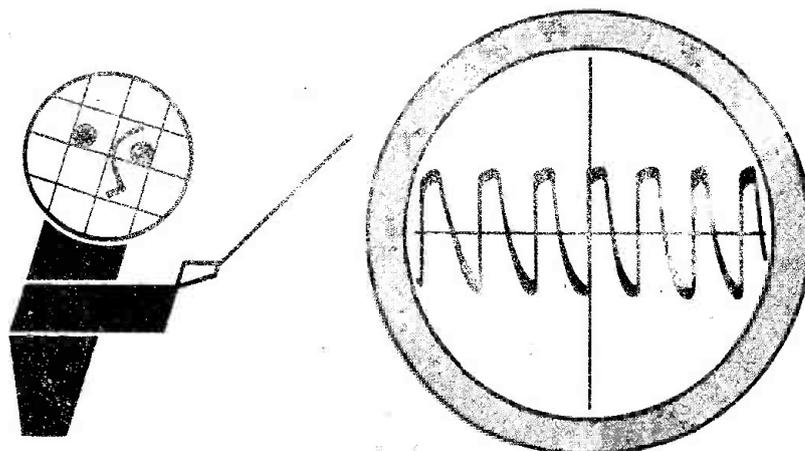no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

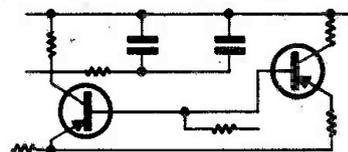2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept., WL15**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives


NAME

BLOCK CAPS

ADDRESS

PLEASE

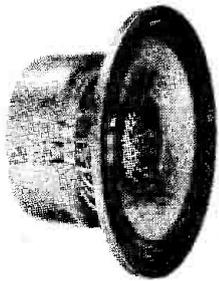special free gift also to all our students



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7-75
Baker Group 35 3, 8 or 15 ohm	£8-50
Baker Group 50/12 8 or 15 ohm	£12-50
Baker Deluxe 12" d/cone	£10-75
Baker Major	£8-50
Baker Regent	£7-75
Baker Superb	£14-50
Baker Auditorium 12	£12-50
Celestion MH1000 horn	£10-95
Celestion PST8 for Unilix	£2-55
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00
Coral 6 1/2" d/cone roll surr. 8 ohm	£2-50
Coral 8" d/cone roll surr. 8 ohm	£3-25
EMI 13 x 8 3, 8 or 15 ohm	£2-25
EMI 13 x 8 150 d/c 3, 8 or 15 ohm	£2-50
EMI 13 x 8 450 t/tw 3, 8 or 15 ohm	£3-75
EMI 13 x 8 type 350 8 or 15 ohm	£8-25
EMI 13 x 8 20 watt base	£6-00
EMI 6 1/2" 93850 4 or 8 ohm	£3-00
EMI 5" 98132CP 8 ohm	£2-50
EMI 8 x 5 d/cone, roll surr 10 watt	£2-50
EMI 2 1/2" tweeter 97492AT	£5-00
Eagle DT33 30 watt tweeter	£5-45
Eagle HT15 horn tweeter	£3-80
Eagle CT5 cone tweeter	£1-75
Eagle CT10 tweeter 8 or 16 ohm	£2-55
Eagle MHT10 horn tweeter	£3-80
Eagle crossover CN23, CN28, CN216	£1-50
Eagle FR4	£5-30
Eagle FR65	£8-35
Eagle FR8	£10-65
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2-80
Elac 6 1/2" 6RM171 d/c roll surr.	£3-50
Elac 6 1/2" 6RM220 d/cone	£2-65
Elac 4" tweeter TW4	£1-21
Elac 10" d/cone 10RM239 8 ohm	£2-85
Elac 8" 8CS175 3 ohm	£2-50
Fane Pop 15 watt 12"	£4-80
Fane Pop 25/2 25 watt 12"	£6-95
Fane Pop 40 watt 10"	£8-50
Fane Pop 50 watt 12"	£11-00
Fane Pop 55 12" 60 watt	£12-50
Fane Pop 60 watt 15"	£13-00
Fane Pop 100 watt 18"	£22-50
Fane Crescendo 12A 100 watt 12"	£29-00
Fane Crescendo 12B bass	£29-00
Fane Crescendo 15" 100 watt	£36-00
Fane Crescendo 18" 150 watt	£49-50
Fane 801T 8" d/c roll surr.	£7-00
Fane 807T 8" d/c roll surr.	£3-85
Fane 808T 8" d/c	£2-75
Fane 701 twin ribbon horn	£35-00
Fane 910 horn	£12-75
Fane 920 horn	£33-00

Goodmans 8P 8 or 15 ohm	£5-00
Goodmans 10P 8 or 15 ohm	£5-30
Goodmans 12P 8 or 15 ohm	£12-95
Goodmans 12P-D 8 or 15 ohm	£16-75
Goodmans 12P-G 8 or 15 ohm	£15-75
Goodmans Audiomax 12AX 100 watt	£37-50
Goodmans Audiomax 15AX	£40-00
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Midax 750	£18-00
Goodmans Axent 100 tweeter	£7-25
Goodmans Audlom 100 12"	£12-00
Goodmans Axlom 401 12"	£17-25
Goodmans Twinaxlom 8	£8-25
Goodmans Twinaxlom 10	£9-00
Kef T27	£5-25
Kef T15	£6-00
Kef B110	£7-25
Kef B200	£8-25
Kef B139	£14-25
Kef DN8	£2-00
Kef DN12	£4-95
Kef DN13	£3-30
STC4001G super tweeter	£6-18
Richard Allan CGBT 8" d/c r/surr.	£8-35
Wharfedale Super 10RS/DD	£9-00
2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm	£5-00
2 1/2" 75 ohm	£5-00
7" x 4" 3 or 8 ohm	£1-40
8" x 5" 3 or 8 ohm	£1-50
10" x 6" 3, 8 or 15 ohm	£2-30

SPEAKER KITS

Baker Major Module	each £10-75
Fane Model One	each £9-80
Goodmans DIN 20	each £9-75
Helme XLK 25	pair £22-00
Helme XLK 30	pair £14-95
Helme XLK 50	pair £39-95
Keffit 2	each £24-75
Keffit 3	each £36-75
Richard Allan Twinkit	each £8-85
Richard Allan Triple 8	each £13-75
Richard Allan Triple	each £19-95
Richard Allan Super Triple	each £23-75
Wharfedale Linton 2 kit	pair £19-25
Wharfedale Glendale 3 kit	pair £34-50
Wharfedale Dovedale 3 kit	pair £52-50

PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£49-75
Linear 30/40	£30-00
Linear 40/60	£35-00
Linear 80/100	£58-95
Linear 100 watt slave	£44-00
Eagle PA range in stock—ask for catalogue.	

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, speaker kits 75p each (£1.50 pair) tweeters and crossovers 20p.

ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
Discount Radio, PA, Hi-Fi: 10 Swan St. Wilmslow
Send stamp for free booklet "Choosing a Speaker"



Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!

	1	5	10
C60	37p	£1-80	£3-50
C90	50p	£2-48	£4-95
C120	63p	£3-10	£6-20

AGFA HIGH DYNAMIC SUPER

	1	5	10
C60+6	50p	£2-40	£4-70
C90+6	68p	£3-35	£6-60
C120	99p	£4-90	£9-80

AGFA STEREO-CHROM CHROMIUM DIOXIDE

	1	5	10
C60	85p	£4-20	£8-30
C90	£1-08	£5-35	£10-60

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO (DEPT. PW)

10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

Wire Wound Resistors. Our selection of mixed values. 30 for £1.50, 100 for £4.00.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.50.

Ferguson Stereogram chassis Model 3357, all transistor, medium long, VHF/FM. 3 watts per channel S/M. with connection data, less tuning scale, £20.

Crystals HC6U: 52-03333 MHz: 52-02500: 52-01667: 51-56667: 51-58330: 37-76250: 37-75000: 12-895-8: 12-891-6: 12-700-0: 9-458-33: 9-456-25: 9-455-55: 9-533-33: 9-531-94: 9-530-55: 9-090-62: 9-087-5: 9-096-87: 50p each.

Electrolytics. 32/32/32µF, 325v, 2" x 1 1/2" 35p: 2000µF 30v, 2" x 1 1/2" 25p: 2000µF 35v 3" x 1" 30p: 470µF 100v 3" x 1 1/2" 25p: 2000/2000µF 25v 2" x 1 1/2" 35p: 30,000µF 25v 4 1/2" x 2 1/2" 50p: 700µF 200v 3 1/2" x 1 1/2" 30p: 16 16µF 275v 1 1/2" x 1" 20p: 40/40/20µF 275v 3" x 1" 20p: 4500/900/900µF 30v 2 1/2" x 1 1/2" 50p: 4000µF 35v 3" x 1 1/2" 40p: 200/100/50/100µF 325v 3" x 1 1/2" 50p: 4000µF 18v 2" x 1" 20p: 470µF 25v 1 1/2" x 1 1/2" 15p.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5", 8 x 5 8" ohms ceramic, 5 watts RMS. Complete with din leads. £11.00 pair.

Thorn TV IF chassis, 950 series (less valves), £1.75.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, £3.25.

Light Dependent Resistors (RCA sq3536) 30p each, 4 for £1.00.

P-C Boards (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1-60, three boards.

Rank EVR Teleplayer colour trans- lator panels, type and components on new panels listed as follows, £2-50, each panel. Z605—14 off BC148: 2 RCA ca3054 (ic): 1 crystal 4-433618 MHz—Z607—12 off BC148: 1 BC108: 1 BC158: 1 RCA ca3046 (ic), 1 RCA ca3045 (ic): Z608—23 off BC148: 2 BC158—Z612—12 off ME4103: 2 BC-251B: 1 BFY50.

Mains Droppers, 10 mixed values, £1.00.

Edgewise Level meters, 200µA, size 1/2" overall, 50p.

Chrome Plastic knobs, 3 types, 4 off each with spring clip, £1.25.

Die Cast Boxes, 4 1/2" x 3 1/2" x 3" 95p: 8 1/2" x 5 1/2" x 2" £1-20. 8 1/2" x 5 1/2" x 4" £1-70.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 70p: 10" x 7 1/2" x 2 1/2" 85p. 11" x 7 1/2" x 2 1/2" 95p.

BSR P128, similar to HT70 single play, with heavy die cast turntable, less cartridge, £11.00.

Transistorised FM tuner head, with A.M. gang, slow motion drive 88-108 Mcs, with circuit diagram, £2-30.



Mono Amp Transistorised (Mains) Ideal for record player 8 ohms 2 watts. £3-50.

Ferguson Stereogram Chassis. MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £28.50.

Goods not despatched outside UK (Post and packing free in UK) 15p handling charge on orders under £1.00. All items include VAT

SURPLECTRONICS


216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

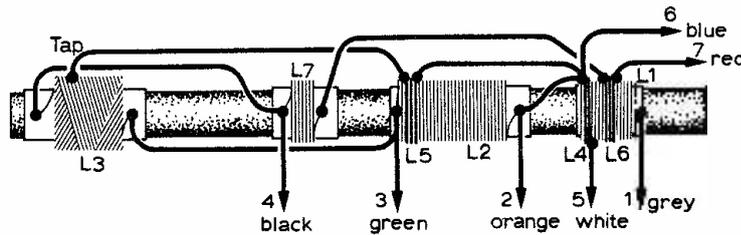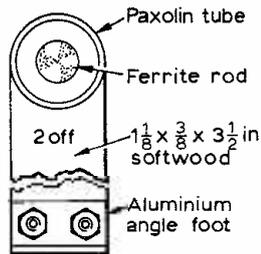

L2, L3, L5 see component list
 L1 28t
 L4 2t
 L6 3t
 L7 25t
 All 32 s.w.g. enamelled

GCF030

Fig. 3: above, gives details of the additional windings required on the ferrite rod aerial.
 Fig. 2: below, shows the component layout of the small circuit board.

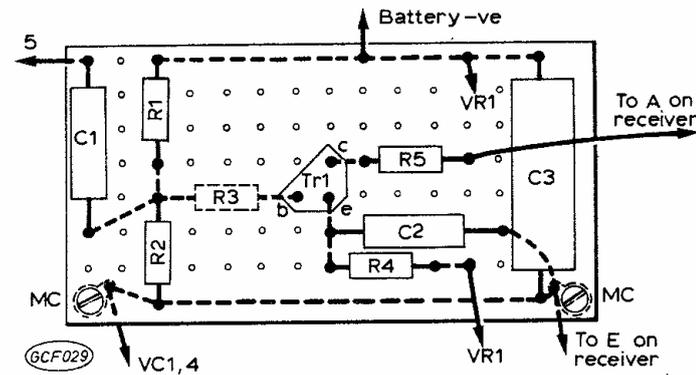

AN ACTIVE AERIAL—continued from page 810

Flying leads are left from the MC line for 4 and VC1. Battery positive and R6 circuits are connected to the chassis. R4 is connected to VR1 wiper, and VR1 outer tag to negative. The board is mounted as in Fig. 4, with extra nuts on each bolt to give a 3/8in space between board and metal chassis.

FERRITE AERIAL

The rod may be either 5in or 6in long, and is 3/8in in diameter. The 1in paxolin tube should be the same length as the rod.

Two supports are made, each of 3/8in wood, about 1 1/8in wide and 3 1/2in high overall. First drill a 3/8in diameter hole to a depth of about 1/8in, as in Fig. 3, to support the end of the rod. A 1in diameter channel is then cut to the same depth, to take the paxolin tube. This is most easily done with an adjustable tank cutter.

Two brackets are cut from aluminium angle and drilled to allow the supports to be mounted vertically, at such a distance apart as to take the rod and tube.

All leads will pass down the right hand support, and a hole is drilled through chassis and bracket here. The wooden support (or one end of the paxolin

tube) is notched to leave space for the leads. The whole aerial is wired and tested before the tube is placed over it. This can be done by loosening the left hand support.

A tag strip which will provide seven connecting points for the leads (including MC) is bolted under the chassis, as in Fig. 4. These can also be identified by using thin coloured sleeving, as shown.

Details of the aerial, which is a standard component with four additional windings, can be seen from Figs. 1 and 3. Connections must be so made that all turns are in the same direction, beginning at 1, going to junction of L1 and L2 at 2, and on through L3 to point 4. L4, L5 and L3 are also in the same phase, as are L6 and L7.

This is most easily arranged by fitting L2 first, with the base winding L5 towards the centre of the rod. Now identify the ends of L3, either by examination, or by testing with a meter—the resistance from 3 to the tapping will be much higher than the resistance from 4 to the tapping. Place L3 as shown in Fig. 3.

Wind L7—25 turns of 32swg enamelled wire—on a strip of paper or thin card. L5 can then be connected to the tap on L3. L2 and L3 can also be connected together, and a green lead taken down to tag 3 on the strip. L7 and L3 are also joined, and a black lead is taken down to tag 4.

Next wind L1 in the same direction as L2. L1 has 28 turns of 32swg enamelled wire, side by side on thin card. Cover L1 with paper or tape, and wind on L4, comprising two turns, as in Fig. 3. Note that L4,

★ components list

Resistors All resistors 1/4W ± 5%


R1 15kΩ
 R2 39kΩ
 R3 39Ω
 R4 820Ω
 R5 1.2kΩ
 R6 3.3kΩ
 VR1 1kΩ linear pot with switch

Capacitors

C1 0.047μF
 C2 0.1μF
 C3 0.22μF
 VC1 Jackson 365pF single, reduction drive optional

Miscellaneous

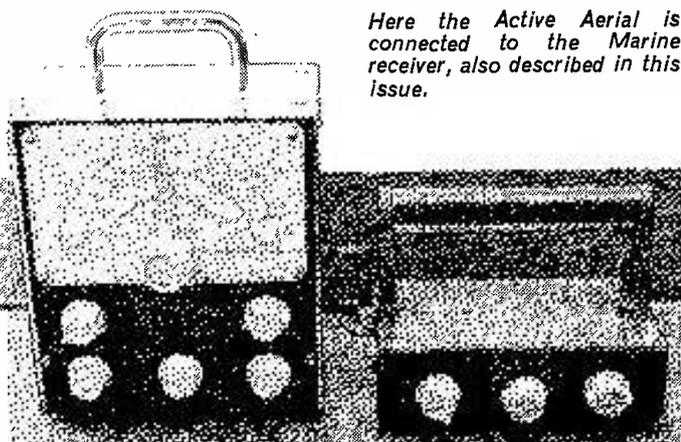L2, L3, L5, Denco MW/LW ferrite rod aerial
 L1, L4, L6, L7, see text
 Tr1 BF195
 S1, 3-pole 3-way rotary switch. S2 ganged with VR1.
 1in. dia. paxolin tube (see text).
 Universal chassis 7 x 4 x 2in. and extra 7 x 4in. flat plate. Plain Veroboard, 0.15 matrix. Rubber feet, Tag strip, Knobs, battery clips, insulated sockets.



Here the Active Aerial is connected to the Marine receiver, also described in this issue.


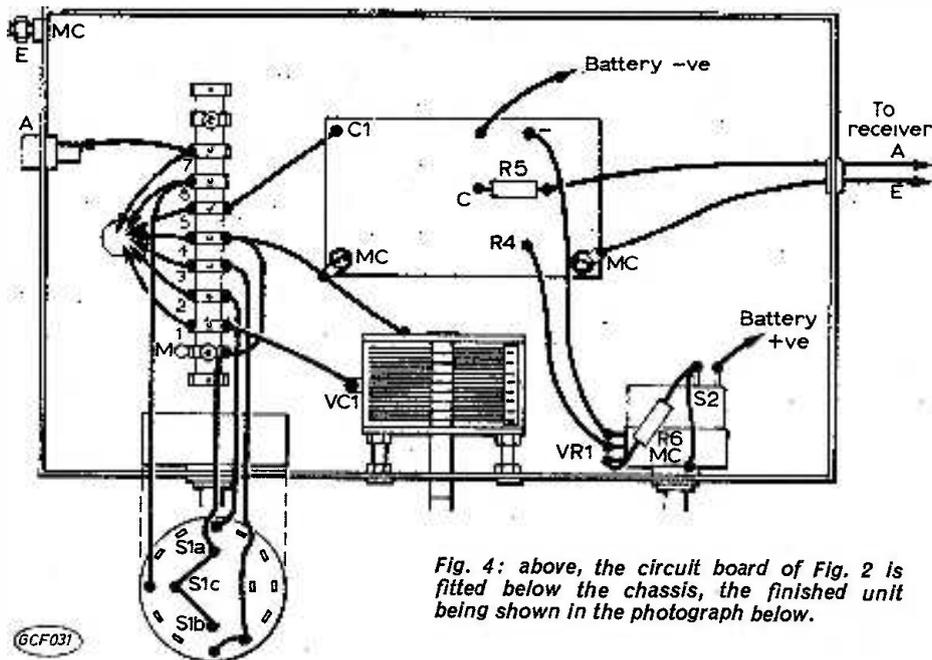


Fig. 4: above, the circuit board of Fig. 2 is fitted below the chassis, the finished unit being shown in the photograph below.

GCF031

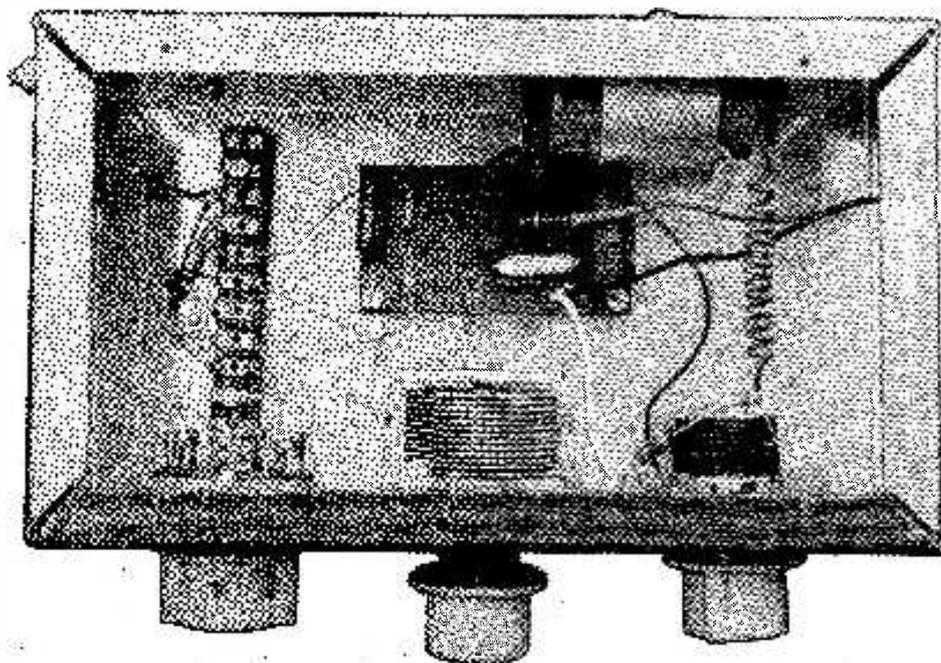

is in the same direction as L5. Add three turns for L6, as in Fig. 3, in the same sense as L7. Thin insulated wires may be soldered on for connections or the leads themselves may be run through sleeving, and taken to the appropriate tags.

It is possible to modify band coverage in the usual way, by sliding the windings on the rod. However, as this circuit is individually tuned by VC1, and does not have to gang with another tuned circuit, this is not essential.

If the wires are kept against the support, and run down to the tags as the aerial is prepared, the paxolin tube can be fitted over the finished aerial with little disturbance.

ASSEMBLY

This can be seen in Fig. 4. VC1 is secured with three 4BA bolts, which may have washers, spacers or extra nuts, as they must not project inside the capacitor. A reduction drive is not essential, but eases tuning.

The battery is held with a clip inside the case. No external connections are required except to plug the output and chassis return leads into the Aerial and Earth sockets of the receiver. The active aerial unit is placed to the right of the receiver mentioned, and a short output (Aerial) lead is possible, so that no screening is necessary for this connection. Tuning scale markings are not essential, as tuning is readily peaked for best reception.

USE WITH RECEIVER

In most cases VR1 is not advanced for maximum gain, as this is likely to cause overloading. When receiving SSB or CW signals it is generally essential to turn the RF gain VR1 back, while advancing the receiver AF gain control, in order that the relative strengths of the received signal and BFO will allow proper resolution. If not, SSB cannot be received, or will sound like severely over-modulated AM.

The receiver aerial trimmer is peaked for best reception for each band, as with an extended aerial in use. The ferrite rod aerial and additional tuned circuit will considerably reduce second channel signal interference.

At some time of day and in some conditions a receiver with a high, extended outdoor aerial will pick up untunable noise at a high level. A similar pick-up of external noise can be encountered with the active aerial unit, and in these circumstances does not indicate any fault in the latter.

If the unit is to be employed with any receiver other than that described, the receiver must have an aerial coupling winding, as in Fig. 1, for Tr1 collector circuit. A receiver with a low impedance input such as 75Ω is not very suitable.

Due to the addition of L1, MW coverage is changed from that obtained by L2 alone. With L2 unmodified, and the coils situated approximately as in Fig. 3, coverage is 140-360kHz, 300-1150kHz, and 1.65-5.0MHz for the three bands. If it is wished to modify this, 22 turns can be removed from the outer end of L2 (junction with L1). Coverage is then 140-350kHz, 350-1500kHz, and 1.2-5.0MHz, which is convenient for the 3-Band receiver mentioned.

Signal pick-up is influenced to some extent by the bearing of the ferrite rod, and by the proximity of large areas of metal, as with a portable receiver. With construction and values as shown, regeneration to the point where oscillation arises is not obtained on all frequencies, but interference-free reception of many signals should be obtained.



Well here's a fine how d'y do! Santa himself caught in the act of 'borrowing' a few of our catalogues . . . and Rudolph laughing his silly head off! We can't see the old chap getting away with it, but we did warn him to lay in a large stock of catalogues. Well, let's hope he gets bailed out in time to deliver one to you. The demand for this famous components catalogue grows by leaps and bounds each year. We at Home Radio Components work hard on it to make sure it more than comes up to everybody's expectations. If you haven't seen one you really should treat yourself for Christmas. It costs 65 pence plus 33p packing and postage, but with it we give you 14 vouchers, each worth 5p when used as directed. That means you can get 70 pence back. In which case this magnificent publication will have cost you only 28 pence! It can be bought over our counter at Mitcham for only 65p . . . or send the coupon below with a cheque or postal order today for 98 pence. If by any chance Santa Claus is still 'detained for questioning' we'll send your catalogue round by postman!

The price of 98p applies only to customers in the U.K. and to B.F.P.O. addresses.



**A Happy
Christmas
to all our
readers.**

Name _____
Address _____



**HOME RADIO (Components) LTD. (Regn. No. London 912966)
Dept. PW, 234-240 London Road, Mitcham CR4 3HD**

HOME RADIO (Components) LTD. Dept. PW, 234-240 London Road, Mitcham CR4 3HD Phone 01-648 8422

TRANSFORMERS

POWER UNIT Type A125

Supplying 6 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5A mains plug.

2 metre output lead with 4-way multiplug giving 2.1 and 2.5 mm sockets and 3.5 mm plugs.

Price £2.25. Post 10p.



2" and 4" PANEL METERS

2"

4"

SIZE: 60mm Wide x 45mm High x 40mm Deep.

SIZE: 110mm Wide x 82mm High x 43mm Deep.

Movement	I.R. Ohms	0-50 micro A.	0-100 micro A.	0-500 micro A.	0-1 mA	0-5 mA	0-10 mA	0-50 mA	0-100 mA	0-500 mA	0-1 AMP	0-2 AMP	0-25 Volt	0-50 Volt	0-300 Volt	"g" Meter	VU Meter
1250	1250	0-50 micro A.	0-100 micro A.	0-500 micro A.	0-1 mA	0-5 mA	0-10 mA	0-50 mA	0-100 mA	0-500 mA	0-1 AMP	0-2 AMP	0-25 Volt	0-50 Volt	0-300 Volt	"g" Meter	VU Meter
1400	730	200	200	200	200	200	6	0.5	0.5	0.5	0.5	0.5	15K	50K	300K	200	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.15 Post 10p. Price 4" £4.15 Post 10p. Lamps 75p per set.

1/2 watt CARBON FILM RESISTORS
1/2 watt at 70°C E 12 range 10Ω—1MΩ 5% tol above 470 KΩ 10% tol at 95p per 100.


ELECTRONIC MAINS TIMER

A reliable unit ideal for timing Bathroom/Toilet Ventilators Stairway/Cloakroom Lighting etc. Gives up to 30 mins delay before switching off. Delay 1-30 mins. adjustable. Max Load 400VA or 1000 watts resistive. White Case 3 1/2" x 3 1/2" x 2". Fitting instructions included. Trade Price £5.80. Post 20p.



MAINS KEYNECTOR

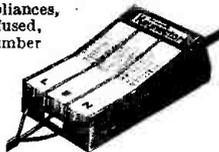The safe, quick, connector for electrical appliances, 13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains, ideal for testing, demonstrating, window displays, etc. Warning Light, interlocked to prevent connecting when live. Trade Price: £3.25. Post 25p.



SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA (watts)	Ref. No.	Price Cased £	Price Plugs 2 Pin + 1 Earth	Price Open £	Post £
60	149	7.85	0.80	4.00	0.38
100	150	8.22	0.80	4.80	0.52
200	151	10.20	0.80	7.40	0.52
250	152	11.68	0.80	8.88	0.65
350	153	14.10	0.80	10.80	0.80
500	154	15.68	0.80	12.38	1.00
750	155	24.63	1.00	18.72	1.20
1000	156	32.19	1.00	26.50	1.20
1500	157	38.18	1.00	30.34	O.A.
2000	158	45.20	2.40	34.68	O.A.
3000	159	66.50	2.40	53.35	O.A.

12 & 24 Volts Prim. 200-240V.

Amps	Ref. No.	Price £	Post £
0.3	0-15	2.42	1.34
0.5	0-25	1.11	1.38
1	0-5	2.13	1.58
2	1	7.1	2.09
4	2	18	2.58
6	3	70	3.80
8	4	108	4.20
10	5	72	4.80
12	6	116	5.01
16	8	17	6.22
20	10	115	9.47
30	15	187	11.95
40	20	232	13.28
50	30	226	15.30

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.

Amps	Ref. No.	Price £	Post £
0.5	112	1.72	0.22
1	79	2.21	0.38
2	3	3.25	0.38
3	20	4.10	0.42
4	21	4.69	0.52
5	51	5.80	0.52
6	117	6.50	0.52
8	88	8.50	0.67
10	89	8.97	0.67

AUTO TRANSFORMERS

Cased versions are 240 Volt Mains to 115 Volts, smart steel cased units coated in tough resin with power lead, fuse and 115 Volt American type socket up to 500VA, above 500VA cable entry.

VA Watts	Ref. No.	Price Cased £	Price Plugs 2 & 3 pin	Price Open £	Post £
20	113	8.00	0.15	1.55	0.30
150	4	5.80	0.15	3.98	0.39
200	65	6.40	0.15	4.50	0.40
300	66	7.27	0.15	5.28	0.52
500	67	9.99	0.15	8.29	0.67
750	83	12.58	0.75	9.78	0.82
1000	84	15.70	0.75	12.40	0.82
1500	93	19.88	0.75	16.58	1.50
2000	95	30.10	1.44	22.05	1.50
3000	73	43.58	1.90	32.00	1.90

PLEASE ADD 8% FOR V.A.T.

50 Volts

Prim. 200-240V. Sec. 19, 25, 38, 40, 50V.

Amps	Ref. No.	Price £	Post £
0.5	102	2.33	0.30
1	103	3.00	0.38
2	104	4.57	0.42
3	105	5.20	0.52
4	106	6.89	0.52
6	107	11.17	0.67
8	118	14.19	0.97
10	119	15.47	0.97

60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 48, 60V.

Amps	Ref. No.	Price £	Post £
0.5	124	2.08	0.38
1	126	2.96	0.38
2	127	4.63	0.42
3	125	6.84	0.52
4	123	7.94	0.67
5	40	8.88	0.67
6	120	10.15	0.82
8	121	13.58	1.00
10	122	18.15	1.00
12	189	16.00	1.10

MINIATURE AND EQUIPMENT

Prim. 240V with screen.

Sec. 1 Volts	Sec. 2 Volts	Milliamps	Ref. No.	Price £	Post £
3-0-3	—	200	238	1.22	0.10
0-6	0-6	500	234	1.30	0.10
0-6	0-6	1000	1000	1.93	0.22
0-9	—	100	12	1.23	0.10
0-9	0-9	330	235	1.43	0.10
0-9	0-9	500	207	1.75	0.22
0-9	0-9	1000	208	2.80	0.30
15-0-15	—	40	240	1.23	0.10
0-15	0-15	200	236	1.30	0.10
20-0-20	—	30	241	1.23	0.10
0-20	0-20	150	150	2.37	0.10
0-15-20	0-15-20	500	500	2.47	0.38
0-20	0-20	300	300	2.14	0.22
0-20	—	3500	NO SCREEN	1116	3.00
0-12-0-12-20	—	700 (D/C)	—	221	2.31
0-15-20	0-15-20	1000	1000	2.06	0.38
0-15-27	0-15-27	500	500	2.73	0.38
0-15-27	0-15-27	1000	1000	2.04	3.52

PLASTIC CASED SILICON BRIDGE RECTIFIERS


One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 59p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p

ADD 10p P & P PER ORDER



POWER UNIT Type CC 12-05

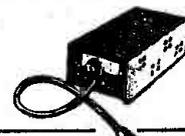Output switched 3, 4.5, 6, 7.5 9 and 12 volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc Size 7.5 x 5.0 x 14.0cm. Price £3.85. Post 25p.



MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation. Price: Packet of 10 for 50p. Postage 10p.

A.S.P. LTD.

DEPT PW12, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker Super-thin construction permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 1-3/4" x 14-11/16". Weight: 19 ounces.

£7.50 each Stereo pair £14.50

INCLUSIVE OF VAT AND POSTAGE

web europa

P.O. Box 162, Watford WD1 1AA



AERIAL BOOSTERS £3.30

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF, RADIO

VALVE BARGAINS

Any 5-50p, 10-75p, 50-£3.30:-
ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, EH90, PC88, PC86.

TV COLOUR VALVES

PL508, PL509, PY5001A, 25p EACH.

Press Button U.H.F. Tuners—£2.50.

Rotary U.H.F. Tuners—£2.00.

PLUGS SOCKETS (Price per item, in brackets for ten)

CO-AX PLUGS 6p (50p) Socket surface 7p (60), Connectors

4p (35p).

D.I.N. PLUGS. 2 pin, 3 pin and 5 pin 20p (£1.65).

JACK PLUGS. Standard 18p (£1.50), 3.5 mm 10p (80p), 2.5 mm

10p (80p).

All prices include V.A.T. P. and p. 10p per order. Money back refund. S.A.E. for leaflet.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge Street, Ramsbottom, Bury, Lancs.

Tel: Rams. 3036

PW
KEMPTON

CAR STEREO CASSETTE PLAYER

PART TWO

KEITH CUMMINS & TONY FRANCIS*

MOTOR CONTROL

The motor control board contains circuits for two basic functions, motor speed regulation and automatic stopping of the machine at the end of a cassette.

We shall deal first with the motor speed control. It will be seen from the circuit diagram (Fig. 2) that the motor is fed from the nominal 12V supply line via transistor Tr52 and resistors R55, R56 and R58. The base current for Tr52 is formed by the collector current of Tr51, the sensing transistor.

When power is supplied to the system, by inserting a cassette, a potential of just under two volts appears at the junction of resistors R53 and R54. This potential is applied, via diode D51, to the base of Tr51, so turning this transistor on. Collector current flowing in Tr51 provides the base current to turn Tr52 on and the resultant current flows into the motor via R55 and R56 in parallel. The motor starts to turn and diodes D52 and D53 conduct, so clamping the emitter of Tr51 at a fixed voltage negative with respect to the positive side of the motor.

This action results in the emitter of Tr51 moving positive, but the base also moves positive since the

collector of Tr52 is connected to Tr51 base via network R51, VR51 and R52. As a consequence, D51 becomes reverse-biased, so disconnecting the starting circuit, R53, R54 from Tr51 base. The emitter-base bias on Tr51 is now a function of the voltage developed across R55 and R56, since the top end of these resistors feeds the base circuit, while the bottom end is clamped to the emitter of Tr51 via D52 and D53.

If the motor load increases, so does its current drain. As a result, the voltage drop across R55 and R56 increases, so increasing the forward bias on Tr51. The increase in Tr51 collector current increases the flow of current in Tr52, so applying more power to the motor to compensate for its increase in load. If the load decreases, the process operates in reverse. Likewise, changes in the supply voltage are accommodated since the only reference required is the measure of current through the resistors in series with the motor, and the apparent DC resistance of Tr52 is adjusted accordingly.

The running speed of the motor is set by VR51 which varies the preset forward bias applied to Tr51. R58 provides a bleed current through the motor in the starting condition and also shunts Tr52, reducing its dissipation.

* Hamilton Electronics Ltd.


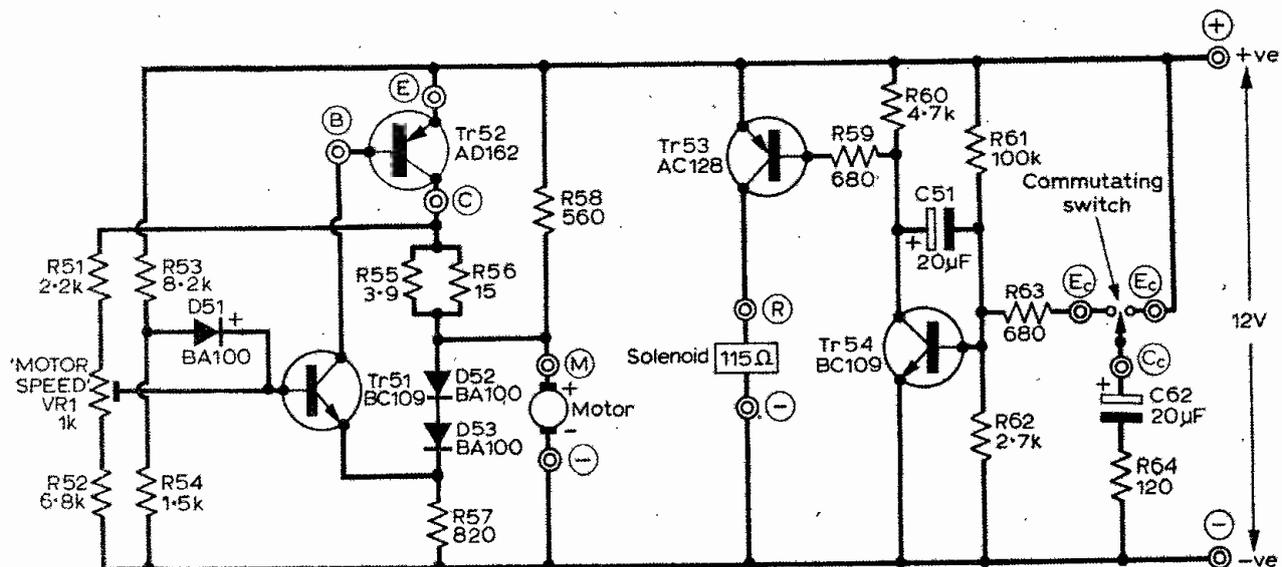


Fig. 2: Circuit of the motor control board. The motor, solenoid and commutating switch are part of the cassette mechanism.


NOTES:

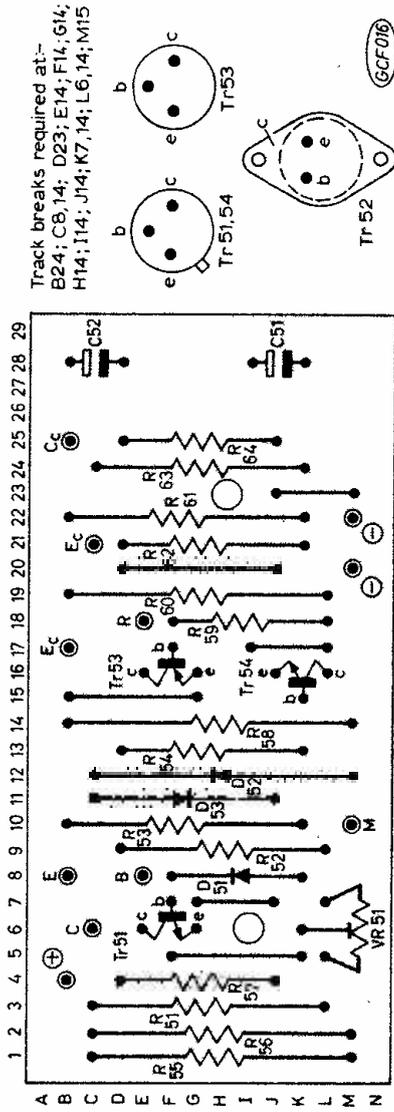1. The Motor Speed control should be labelled VR51.
2. Capacitor C62 should be labelled C52.

88 **Fig. 3: Layout for the motor control board, using 0.1 in pitch Veroboard**
3 x 1.4 in.




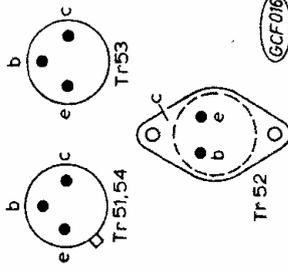Track breaks required at:-
B24; C8,14; D23; E14; F14; G14;
H14; I14; J14; K7,14; L6,14; M15



Both these boards are viewed from the component side.


Fig. 4: Layout for the amplifier board built on 0.1 in. pitch Veroboard
6.75 x 2.5 in. The lower half of the board (Right channel) is a mirror image of the upper half except for the transistors shown, which are reversed for ease of assembly.

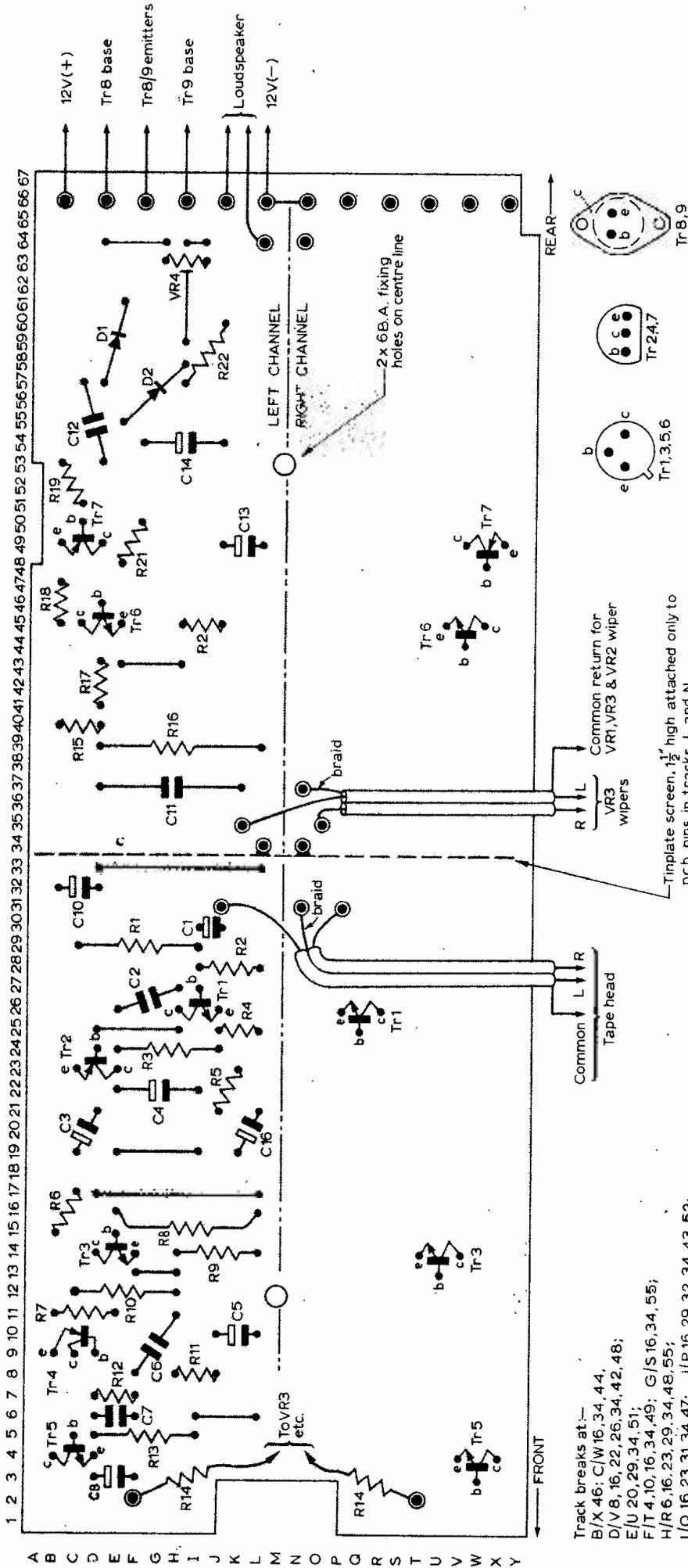

Track breaks at:-
B/X 46; C/W 16, 34, 44,
D/V 8, 16, 22, 26, 34, 42, 48;
E/U 20, 29, 34, 51;
F/T 4, 10, 16, 34, 49; G/S 16, 34, 55;
H/R 6, 16, 23, 29, 34, 48, 55;
I/Q 16, 23, 31, 34, 47; J/P 16, 29, 32, 34, 43, 52;
K/O 7, 16, 25, 34, 38;

Henry's

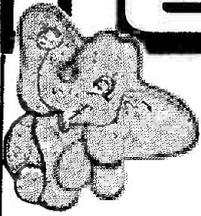
UK'S LARGEST RANGE OF TRANSISTORS, IC'S
RECTIFIERS, ALL SEMICONDUCTOR DEVICES
BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL



INTEGRATED CIRCUITS

EXTRA DISCOUNTS

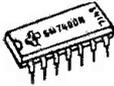Semi-conductors
Any one type or mixed
SN 74 Series 'IC'
12 EXTRA 10%
25 EXTRA 15%
100 EXTRA 20%



74 Series	£ p	£ p	£ p
SN7400N	0.16	SN7485N	1.63
SN7401N	0.16	SN7486N	0.47
SN7402N	0.16	SN7489N	3.87
SN7403N	0.16	SN7490N	0.55
SN7404N	0.16	SN7491AN	1.00
SN7405N	0.16	SN7492N	0.70
SN7406N	0.42	SN7493N	0.70
SN7407N	0.42	SN7494N	0.80
SN7408N	0.28	SN7495N	0.80
SN7409N	0.28	SN7496N	0.95
SN7410N	0.16	SN7497N	3.87
SN7411N	0.25	SN74100N	1.89
SN7412N	0.30	SN74104N	0.58
SN7413N	0.36	SN74105N	0.53
SN7414N	0.72	SN74107N	0.45
SN7416N	0.36	SN74110N	0.58
SN7417N	0.36	SN74111N	0.88
SN7420N	0.16	SN74116N	1.89
SN7421N	0.33	SN74118N	0.90
SN7422N	0.25	SN74119N	1.68
SN7423N	0.37	SN74120N	0.95
SN7425N	0.37	SN74121N	0.50
SN7426N	0.32	SN74122N	1.00
SN7427N	0.37	SN74123N	1.00
SN7428N	0.40	SN74125N	0.65
SN7430N	0.16	SN74132N	0.72
SN7432N	0.37	SN74141N	0.90
SN7433N	0.37	SN74145N	1.28
SN7437N	0.37	SN74150N	1.75
SN7438N	0.37	SN74151N	1.00
SN7440N	0.22	SN74153N	0.95
SN7441AN	0.92	SN74154N	2.00
SN7442N	0.79	SN74155N	1.00
SN7443N	1.20	SN74156N	1.00
SN7444N	1.27	SN74157N	0.95
SN7445N	1.60	SN74160N	1.38
SN7446N	1.35	SN74161N	1.38
SN7447AN	1.60	SN74162N	1.38
SN7448N	1.27	SN74163N	1.38
SN7450N	0.16	SN74164N	1.76
SN7451N	0.16	SN74165N	1.76
SN7453N	0.16	SN74166N	1.60
SN7454N	0.16	SN74167N	3.00
SN7460N	0.16	SN74170N	2.52
SN7470N	0.38	SN74173N	1.66
SN7472N	0.38	SN74174N	1.57
SN7473N	0.41	SN74175N	1.10
SN7474N	0.42	SN74176N	1.26
SN7475N	0.59	SN74177N	1.26
SN7476N	0.45	SN74180N	1.26
SN7480N	0.60	SN74181N	3.95
SN7481N	1.10	SN74182N	1.26
SN7482N	0.87	SN74184N	1.80
SN7483N	1.10	SN74185N	1.80
SN7484N	1.00	SN74190N	2.00
		SN74191N	2.00
		SN74192N	2.00
		SN74193N	2.00
		SN74194N	1.30
		SN74195N	1.10
		SN74196N	1.20
		SN74197N	1.20
		SN74198N	2.77
		SN74199N	2.52

COSMOS INTEGRATED CIRCUITS — FULL RANGE IN STOCK

AAZ13	£ p	BLY36-	£ p	TIP42A	£ p
AC107	0.51	BSX20	0.13	TIS43	0.26
AC128	0.15	BU105	2.20	V405A	0.22
AC187	0.21	BY100	0.27	ZTX108	0.08
ACY17	0.40	BY127	0.12	ZTX300	0.13
ACY39	0.78	BZ13	0.42	ZTX302	0.18
AD149	0.58	CI06D	0.54	ZTX500	0.13
AD161	0.44	GET111	0.72	2N697	0.16
AD162	0.44	GET115	0.90	2N706	0.12
AF117	0.24	GET880	0.60	2N930	0.18
AF118	0.57	LM309K	2.00	2N987	0.42
AF139	0.41	MAT121	0.25	2N1132	0.24
AF186	0.48	MJE340	0.47	2N1304	0.28
AF239	0.44	MJE520	0.63	2N1613	0.21
ASY27	0.33	MJE3055	0.77	2N1671	1.20
BA115	0.10	MJE2955	1.27	2N2147	0.78
BAX13	0.05	MPF105	0.36	2N2160	0.78
BC107	0.14	NKT404	0.66	2N2926	0.12
BC108	0.13	OA5	0.72	2N3053	0.18
BC109	0.14	OA81	0.18	2N3054	0.48
BC109C	0.16	OA200	0.08	2N3055	0.45
BC113	0.15	OA202	0.06	2N3440	0.58
BC147	0.10	OC28	0.66	2N3442	1.39
BC148	0.08	OC35	0.55	2N3525	0.91
BC149	0.10	OC36	0.60	2N3614	0.65
BC169C	0.15	OC44	0.20	2N3702	1.11
BC182	0.12	OC45	0.20	2N3714	1.41
BCY32	0.85	OC71	0.18	2N3771	1.77
BCT39	1.50	OC72	0.28	2N3773	2.40
BCY55	2.64	OC77	0.54	2N3790	2.10
BCY70	0.18	OC81	0.29	2N3819	0.38
BCY71	0.22	OC83	0.27	2N3886	0.72
BCY72	0.12	OC140	1.14	2N3903	0.15
BD124	0.65	OC170	0.30	2N4002	0.15
BD131	0.42	OC200	0.54	2N4126	0.15
BF115	0.20	OC202	0.90	2N4871	0.34
BF180	0.36	OCPT71	1.20	2N5457	0.30
BF194	0.10	ORP12	0.60	2S303	0.60
BFX13	0.26	ORP60	0.55	40550	0.54
BFX34	0.70	P346A	0.18	40361	0.45
BFX88	0.24	TIL209	0.20	40362	0.40
BFX50	0.21	TIP29A	0.49	40408	0.50
BFX51	0.20	TIP30A	0.57	40486	0.85
BFX64	0.36	TIP31A	0.61	40636	1.00
BFX90	0.31	TIP41A	0.74	40430	0.85

SILICON CONTROLLED RECTIFIERS

TO5 1 Amp	£ p
CRS1/05AF	0.42
CRS1/10AF	0.48
CRS1/20AF	0.52
CRS1/40AF	0.60
CRS1/60AF	0.78

TRIACS


3 Amp	£ p
SC35A	0.85
SC35B	0.91
SC35D	0.99
SC35E	1.30

BRIDGE SILICON RECTIFIERS

1/2 Amp	£ p
B025/025	0.14
B025/05	0.16

1 Amp	£ p
B1/05	0.20
B1/10	0.21
B1/20	0.24
B1/60	0.25
B1/100	0.30

ELECTRONIC COMPONENTS

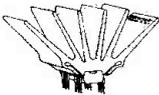

Strobe Tubes
ZFT8A (similar to 4A) £4.00.
ZFT12A £5.00.
7 segment indicators 3015F with data £1.70 ea
Spring delay units
Ultrasonic transducers with data/circuits £5.90 pr



Ceramic Filters
Miniature 10-7 MHz filters 40p pair.
ZN414 Radio IC with circuit £1.20

SPECIAL OFFER CASSETTE STORAGE



Rotating unit up to 32 cassettes stackable £3.60 pp 15p
Car unit with bracket for 10 cassettes £2.80 pp 10p

ELECTRONIC COMPONENTS & EQUIPMENT

More selection — bigger stocks of electronic components and equipment for supply purpose. Let us quote for your requirements.
(Please enclose large SAE with all enquiries).

TEST EQUIPMENT MULTI- METERS




(carr./packing 35p)
U4324, 20k/V with case £9.25
U435, 20k/V with steel case £8.75
U4313, 20k/V with steel case £12.50
U4317, 20k/V with case £16.50
U4341, 33k/V + transistor tester steel case £10.50
U4323, 20k/V plus 1KHZ OSC with case £7.70
ITI-2, 20k/V slim type £5.95
THL33D (L33DX) 2k/V Robust £7.50
TP53N, 20k/V (Case £2.00) £8.25
TP105 2k/V £6.25
TW205 20k/V £10.00
TW50K 50K/V £11.25
EPI0KN 10K/V £9.95
AF105 50k/V, Deluxe (case £1.90) £12.50
S100TR 100k/V Plus trans. tester £22.50

GENERAL TEST EQUIPMENT

(+ carr/pack 50p. *c/p 30p unless stated)
New Revolutionary Super tester 680R 680R Multi-tester £18.50
Accessories
Transistor tester £11.00
Electronic volt. £18.00
Amp clamp £11.95
Temp. probe £11.95
Gauss meter £11.95
Signal injector £5.95
Phase Sequence £5.95
EHT Probe £5.95
Shunts 25/50/10A £4.50
+13100 IMA Stripchart recorder £44.00
+TE40 AC Multi voltmeter £19.75
+TE15 Grid dip meter 440KHZ-28MHZ £19.95
+TE65 28 Range valve voltmeter £22.50
+TK20D RF Generator 120-KHZ 500MHZ £18.95
+TK22D AF Gen 20HZ-200KHZ £19.95
+HM350 In circuit transistor tester £19.50
*C3025 Deluxe meter 1-300 MHz £4.95
*TT145 Compact transistor tester £14.75
+G3-36 R/C osc. 20HZ-200KHZ £19.75
+C3042 SVR Meter £5.75
*SE350A Deluxe signal tracer £12.95
*SE400 Mini-lab all in one tester £15.50
C1-5 Scope 500,000KHZ (carr. £1) £43.00
*C30435 CH F/A meter 1-300MHZ £5.75
Resistance sub box } Post, etc. £2.10
Capacitor } 20p
2 amp var. transformers (carr. £1) £6.55
Radio activity counter 0-10 (carr. £1) £9.97

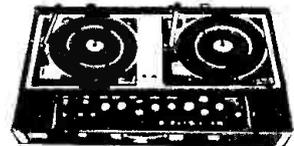Mains unit for above (carr. 50p) £3.75
PA-DISCO-LIGHTING Equipment



Without doubt UK's best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc. FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF AT HENRY'S DISCO CENTRE 309 EDGWARE ROAD 01-723 6963.

QUALITY CASSETTE TAPES

"Living Sound" made specially for Henry's by EMI Tapes Ltd.
5 screw type with library case
Post paid (GB)
3 for 6 for 10 for 25 for
C60 £1.10 £2.00 £3.15 £7.50
C90 £1.47 £2.85 £4.65 £11.37
C120 £1.83 £3.54 £5.60 £14.00

8% VAT TO BE ADDED
TO ALL ORDERS
(EXPORT VAT FREE)

Henry's RADIO


EDGWARE ROAD, W2

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Hi Fi and
Electronics
Centres Open
9 am - 6 pm

Prices correct at time of preparation. Subject to change without notice. E. & O. E.

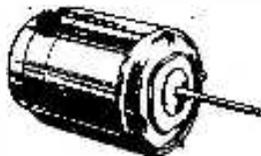"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC. (synchronous) operation at 120v., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 100 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 3/4", spindle length 2 1/2" x 1/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. **OUR PRICE ONLY £15**

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant, ideal for P.C.'s. Sizes: 12" x 12", 24" x 12", 24" x 24"; FULL SHEET 43" x 37" (11 sq ft.) Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.



SMITHS RINGER-TIMER


Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 3/16"; (80 DB) 3/8" x 5/32" x 3/16". Equipment, all tested. £1.20 each. P. & P. FREE.

Ultra PRECISION CENTRIFUGAL BLOWER

by Air Control Ltd.

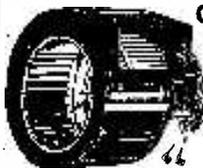

30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 A.C. Very powerful and silent running. 5 1/2" dia. 3" inlet dia. Outlet flange 3" x 2 1/2". LIMITED NUMBER ONLY £8.95. P & P 40p.

MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "e l b o w". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 3/4" x 1" x 1 1/2". Travel 1", 90p each. P. & P. 10p. 240AC type MM4. 2lb. pull, 1 1/2" x 1 1/2" x 1". Travel 3/4" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 A.C., 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v., 1amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8.80; 100 for £15.50. FREE P. & P. over 10.



AMPEX 7.5v. D.C. MOTOR

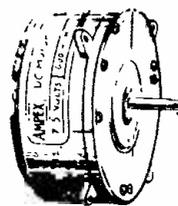

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500rpm. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. 1" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. **OUR PRICE £3.30. P. & P. 25p.** Quantity available. Mu-metal enclosure available 75p each. FREE P. & P.

ALL PRICES INCLUDE V.A.T.

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580

TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

POP 70 10" 70 Watt

Impedance 8 ohms or 15 ohms
Gauss 17,000
Voice Coil Diam. 2"
70 watt RMS
Range 45-8,000 Hz



£19.95 Rec. Retail Price inc. VAT

BRIEF DETAILS OF 'POP' RANGE NOW AVAILABLE IN 8 ohms or 15 ohms

POP '15'	12"	15 Watt	£6.30
	1" Voice Coil		inc. VAT
POP '25T'	12"	25 Watt	£8.99
	1" Voice Coil		inc. VAT
POP '50'	12"	50 Watt	£12.95
	2" Voice Coil		inc. VAT
POP '60'	15"	60 Watt	£16.95
	2" Voice Coil		inc. VAT
POP '100'	18"	100 Watt	£31.00
	3" Voice Coil		inc. VAT

Also for those who can afford the very best For Instrument Reproduction

Two Super Sensitive Models
CRESCENDO '12' B
Ideal for Lead Guitar etc.
12" 75 Watt 2" Pole Diam. Gauss 20,000
CRESCENDO '15/100A'
General Purpose
15" 100 Watt 2" Pole Diam. Gauss 20,000



Rec. Retail Price
£39.96 **£46.59**
CRESCENDO '12' B CRESCENDO '15/100A'

There is also a 12" Crescendo Speaker for General Purpose Public Address, and a 12" and 15" for Bass Guitar etc.

Please send S.A.E. for leaflet on HORN UNITS & 'POP' or 'CRESCENDO' Range of Loudspeakers

POP 55 12" 60 Watt

Impedance 8-15 ohms
Gauss 15,000
Voice Coil Diam. 2"
Range 50-9,000 Hz
AN ALL PURPOSE UNIT OF HIGH SENSITIVITY
Rec. Retail Price inc. VAT



£15.99

HIGH FREQUENCY HORN UNITS

MODEL 910
Rating 50 watts with recommended filter

£15.96 inc. VAT
MODEL 920 Mk II (as illust)
SIGNIFICANTLY INCREASED SENSITIVITY. UNCHANGED PRICE. Rating with recommended filter **£39.23** inc. VAT
Filters for either model available if required



Distributors to Wholesale and Retail Traders—LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.
Manufacturers enquiries to—FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS

Prices shown correct at Nov 7, 1974

AUTO STOP

Now we come to the autostop mechanism. When the cassette is pushed in, it will only hold in provided the solenoid is energised, to operate the latch. The solenoid is controlled by transistor Tr53. Attached to the cassette feed-spool hub is a commutating switch, below the deck, which constantly switches a common contact between the others provided the hub is rotating.

When power is applied to the circuit by inserting a cassette, capacitor C51 charges via R60, R59 and the base circuits of both Tr53 and Tr54. The resultant collector current in Tr53 energises the solenoid to hold the latch. The flow of collector current in Tr54 reduces the charging voltage applied to C51, so forming a "Miller integrator" circuit linearising the charging of the capacitor. Under these circumstances C51 would eventually become fully charged, and the current would stop flowing, so de-energising the solenoid and releasing the latch. However, this process is not allowed to complete.

LATCHING

As soon as the cassette is inserted, the motor starts to move the tape, and the commutating switch commences operation. C52 is alternately charged from the 12V supply, and discharged via R63 into the base of Tr54. The process is integrated by C51 so that a constant hold-in current flows through the solenoid. R64 is included to prevent excessive charging current in C52, with the attendant risk of contact wear and electrical interference.

When the cassette comes to the end, the feed hub stops rotating, and with it the commutating switch. As a result, no current pulses are fed into the base of Tr54, and C51 reaches its point of maximum charge. Current flow in the transistors then ceases, so de-energising the solenoid. The latch drops out releasing the deck mechanism and the cassette is ejected.

Obviously, any attempt to re-insert the cassette without turning it over will be fruitless, since the commutating switch will be inoperative and the cassette will be promptly ejected again.

CONSTRUCTION

Construction can commence with the two circuit boards. The motor control board, Fig 3, is quite straightforward but take care to cut the tracks in the correct places. When completed, the board is mounted on the rear panel of the cassette mechanism in the position shown in the photographs. Nylon nuts and bolts should be used to avoid shorting or earthing any of the tracks.

The rear panel also acts as the heatsink for Tr52 and is supplied already punched with the necessary pattern of holes. An insulating mounting kit must be used for this transistor.

The amplifier board carries the two channels side by side, one being a mirror image of the other apart from five of the transistors. These are turned around to make mounting easier. See Fig. 4.

Note that the amplifier starts in the middle of the panel and moves towards the controls. The signal is then conveyed via screened cables to the other half of the board, where it progresses towards the output transistors at the rear of the unit. Because of this layout it is essential, if feedback is to be avoided, to place a screen across the middle of the board, as shown in the diagram. This screen is a piece of thin tinfoil, soldered to two tags in the negative rails at the centre of the board. It should not touch any other metalwork.

The main earthing is via the deck mechanism; nylon fixing bolts are used to secure the amplifier board to the case. This method of earthing at one point avoids feedback loops which can affect both the stability of the equipment and its immunity to interference. It also eases the conversion to positive earth working.

When constructing the boards, it is wisest to cut the tracks in the appropriate places first, using the lists provided. Then, as you fit the components, check against the circuit diagram that the actual circuit you are making follows it precisely. Any apparent deviations should be checked, and will probably reveal incorrect positioning of components or incorrect cutting of the copper strips.

Next month we will conclude with details of the metalwork required plus final assembly and testing.

THE THIRD MIDLAND Amateur Radio & Electronics Exhibition

THE Third Midland Amateur Radio and Electronics Exhibition was held at the Granby Halls, Leicester on October 31st and November 1st and 2nd 1974. It was organised for the Amateur Radio Retailers' Association by T. Darn, G3FGY and L. J. Hellier, G3TED.

The following manufacturers, retailers and organisations were represented: Radio Society of Great Britain; D. P. Hobbs, Luton; Amateur Radio Bulk Buying Group; J. & A. Tweedy, Chesterfield; Home Office (Posts & Telegraphs); Homer & Whitbread, Crayford; Taurus Electrical, Loughborough; British Amateur Teleprinter Group; Stephen James, Liverpool; LMB Speakers, Loughborough; M & B Components, Leeds; Eley Electronics; International Short Wave League; Baginton Electronics; Datong Electronics; Doram, Leeds; Burns Electronics; Garex Electronics; Radio Shack Ltd.; Lowe Electronics; John Birkett; Amateur Radio Shop; Bamber Electronics; Western Electronics; RAIBC; D. Tilcock; Richard White; Bennison, Kings Lynn; Amateur Electronics; Microwave Modules; Isherwood Electronic; Telford Communication; Heath, Gloucester.

The "DX" station and talk-in station were operating under the call GB3ARE.

During the Exhibition hours the following programmes were scheduled for showing in the film theatre: Cough and You'll Deafen thousands; The History of the B.B.C.; Television Camera Tube; The Electroners; Semi-Conductor Physics; Television Carrier Wave; Its The Tube that makes the Colour; Something Big in Micro-Circuits; A Planned Environment.

From all reports, the exhibition was a huge success—it was very well organised!



MODEL CON

PART 1-THE R

This receiver is intended for use with the 27MHz model control transmitter to be described next month, but it may also be used in conjunction with any transmitter giving a tone modulated carrier. Though a superhet receiver has a less simple circuit than the super-regenerative receivers which are often used for model control, it does have some advantages. One of these is the additional selectivity obtained so that, if more than one model is in use, it is unlikely that control will be taken over accidentally by another person whose transmitter is near, as may happen with an unselective receiver.

The crystal controlled oscillator of the receiver also gives a high degree of reliability and frequency stability so that the receiver is unlikely to need regular adjustment. The receiver operation is not influenced by changes to the aerial, which can be critical with super-regenerative circuits.

RECEIVER CIRCUIT

The circuit shown in Fig. 1 employs five transistors and one IC. The aerial tuned circuit L1C2 is coupled through C1. The length of aerial used naturally influences the maximum range obtainable and can generally be some 12in. to 18in. or so. There is no critical or exact length which must be fitted.

Coil L2 couples signals to the base of the mixer Tr1 while Tr2 is the crystal controlled oscillator, coupled to Tr1 by C4. There is a difference of 455kHz between this oscillator and the frequency of the transmitter. Mixing in Tr1 thus provides a 455kHz output feeding the intermediate frequency transformer IFT1. IFT1 and IFT2 form a compact but quite selective IF filter and signals pass to pin 2 of IC1 providing IF amplification, automatic gain control and demodulation, the resultant audio tone being obtained at pin 1. Tr3 an audio amplifier after which the audio tone is coupled to Tr4 by the driver transformer T1.

When no tone is present Tr5 base is negative via R10 and no collector current passes. When the tone

TAKE NOTE!

The use of radio for controlling a model is permitted only under the authority of a licence issued by the Home Office. This authorises the use of A1, A2, F1 and F2 emissions in the frequency band 26.96 to 27.28 MHz with a maximum effective radiated power of 1.5 watts and in the band 458.5 to 459.5 MHz with a maximum effective radiated power of 0.5 watt. The licence authorises the use of the apparatus anywhere in the UK and is valid for five years. Applications for the licence should be sent to:—Home Office (Radio Regulatory Division), Waterloo Bridge House, Waterloo Road, London SE1 8UA together with the fee of £1.50 **NO EXAMINATION IS REQUIRED.**

CONTROL BY RADIO

RECEIVER

F. G. RAYER

G3OGR

present Tr4 conducts when its base is driven positive by T1 and these pulses are smoothed by C12. Tr5 base bias now results in collector current which operates the relay. The relay switches the circuit to magnetic or similar devices which in turn control steering or other functions in the model.


Current drain of the whole circuit is small and it is intended for use with any 4.5 volt or 3-cell battery.

CRYSTAL FREQUENCY

With a 27.005MHz crystal in the transmitter the receiver crystal is 27.460kHz, giving a difference, or IF, of 455kHz. There is no need to use these specific frequencies which are quoted as an example. Model control crystals are available for various channels, some being colour coded. If the equipment is being used by itself, remote from other model control transmitters, any channel may be used. But if other persons are operating model control equipment nearby each transmitter should use a separate channel to avoid interference. If a change in frequency is ever found necessary both transmitter and receiver crystals have to be pulled out and replaced by a pair for the new working frequency.


CIRCUIT BOARD

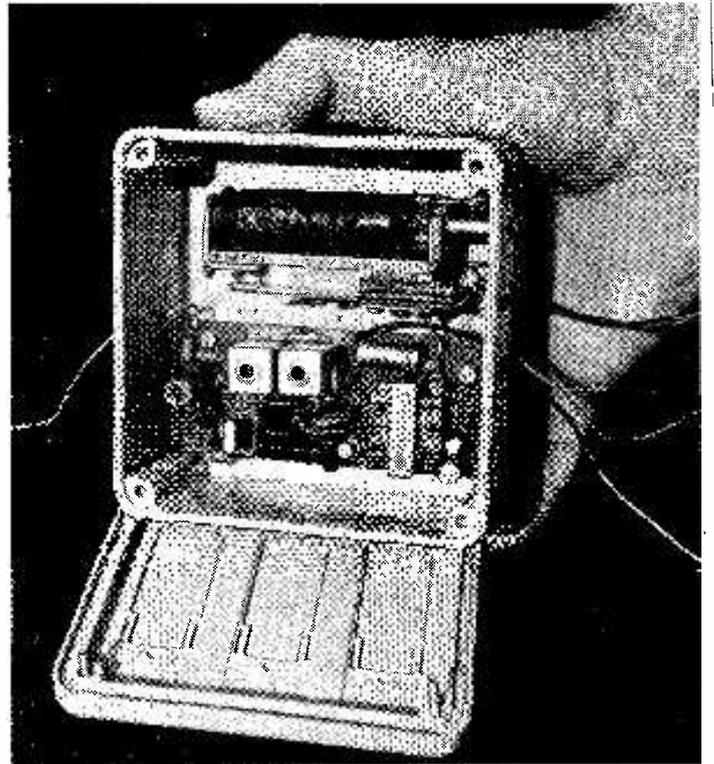This board measures about 3⁵/₈ x 1⁵/₈in. without the relay but may be extended to permit a small relay to be mounted on it near Tr5, but the relay can just



▲ The finished receiver board mounted in a protective plastic box together with the relay. The battery switch and battery are mounted externally.

▼ Fig. 1: Circuit diagram of the crystal controlled receiver.

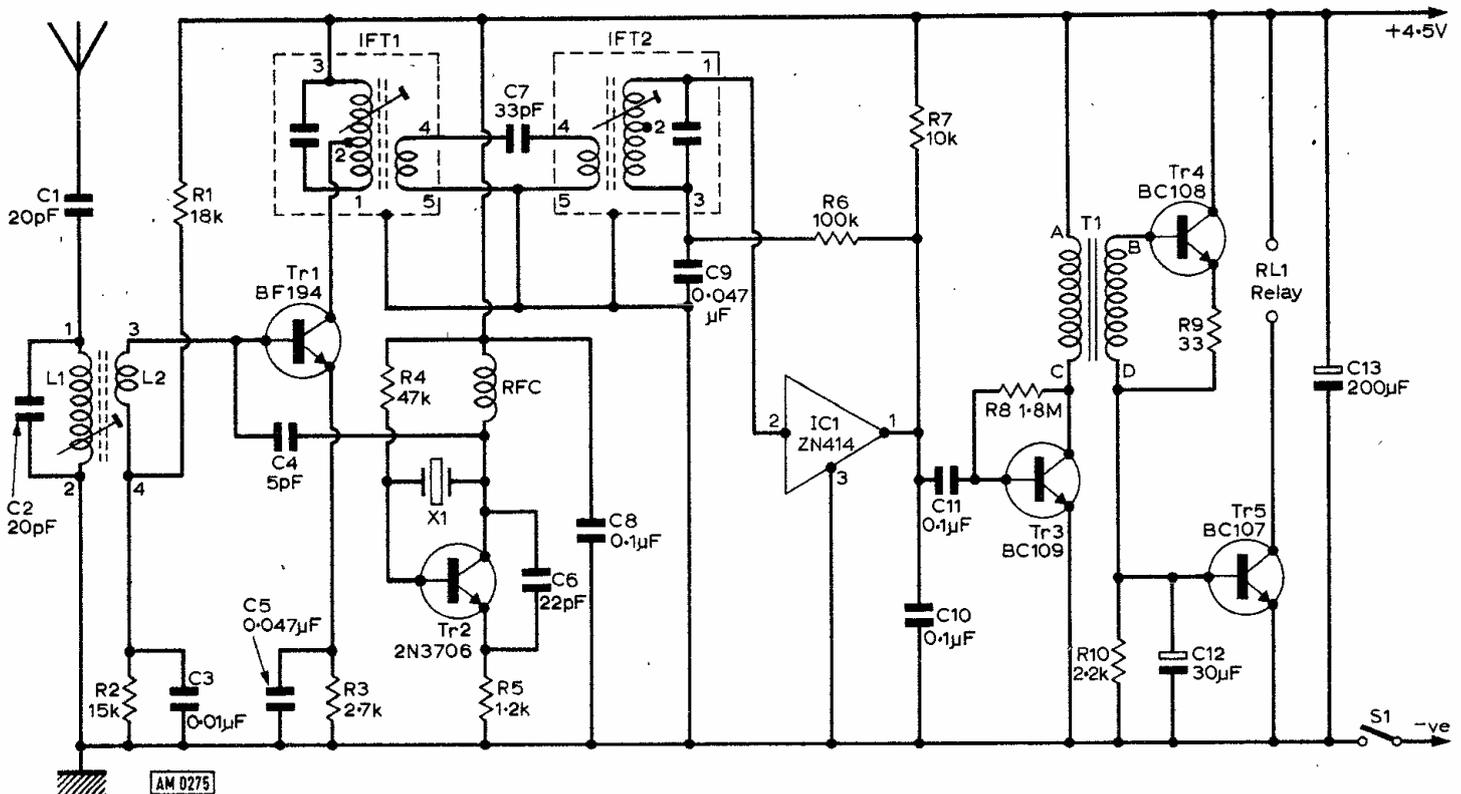

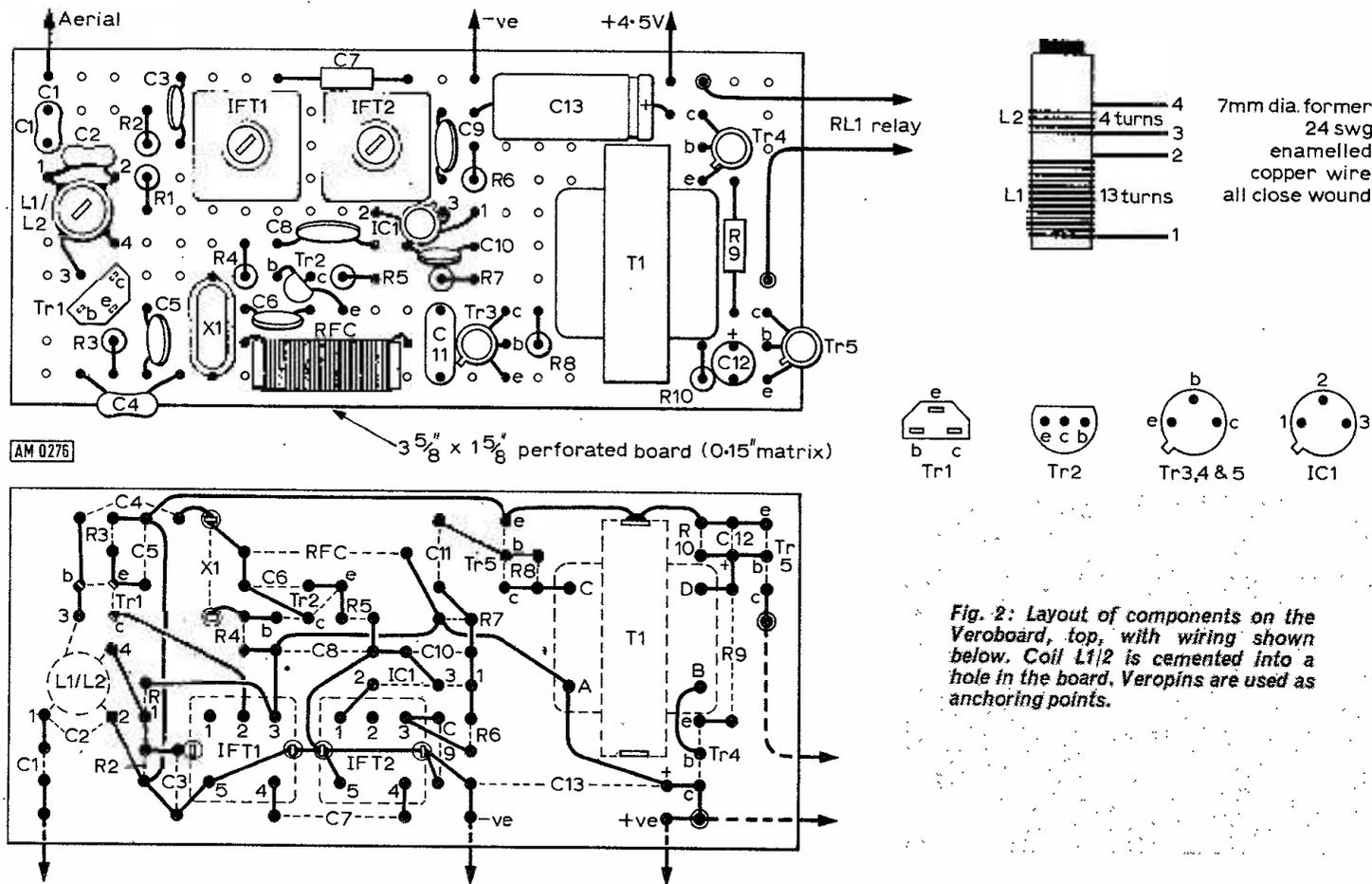


Fig. 2: Layout of components on the Veroboard, top, with wiring shown below. Coil L1/2 is cemented into a hole in the board. Veropins are used as anchoring points.

as well be separated from the receiver. Both sides of the circuit board are shown in Fig. 2. Holes are drilled for the pins and screening can tags of IFT1 and IFT2, for T1 and the crystal holder before fitting any items. The coil L1/L2 is a push fit in a hole and is cemented in place. A flying lead is left for the aerial connection and leads for battery positive and battery negative. The on-off switch S1 is placed in an easily reached position on the model. Two leads are soldered to Veropins which run to the relay.

The RF choke has 46 turns of 32SWG enamelled copper wire, close wound on a 1/4in diameter former about 3/4in long cut from insulated rod (some potentiometers have an insulated shaft which is suitable). A small hole is drilled near each end of the rod, the wire is taken through one hole and the choke wound then the wire is cut and passed through the other hole. Adhesive at the ends holds the choke to the board. The whole winding should not be covered with adhesive or any other protection.

In most places the wire ends of components are long enough to reach connecting points. Elsewhere, 22SWG wire can be used. Sleeving is necessary on leads which cross other wires or run near joints. Tr1 has tags which pass directly through the circuit board holes. The leads of the other transistors and IC1 are arranged as shown. Leads 1 and 2 of IC1 must be well separated as in Fig. 2.

The can tags of the IFT's are connected to the negative line as is the core of T1. The secondary centre tap of T1 is not used.

TESTING

The receiver is adjusted by setting the cores of L1, IFT1 and IFT2 and is best done with the aid of a multi-range meter. Set the meter to 100mA range

and clip it to the relay pins, with a resistor of about 100 ohms or so in series with one lead (the resistor is essential). Meter positive is taken to the positive pin. With the receiver switched on, current should be almost zero.


The transmitter (Part 2) is then switched on and the cores of IFT1 and IFT2 are rotated for maximum meter reading. To avoid overloading the transmitter aerial should not be extended and no aerial need be present on the receiver. A correctly shaped tool, such as that available from the IFT makers, should be used to adjust the cores, as a steel blade is unsuitable and wedge-shaped tools may split the cores so that they cannot be rotated. It may be helpful to have someone take the transmitter a short distance away so that the relay current shown by the meter only rises to 15 to 20mA or so. The core of L1 is also peaked for best results. In the absence of a transmitter a signal generator will suffice.

When the IFT's have been set they need no further adjustment. But when changing or connecting the aerial some small re-adjustment of L1 core may be needed.

AERIALS

A vertical or slightly sloping aerial will not appear out of place on many models. It can be the small telescopic receiver-type of aerial or a rod or stout wire which can be inserted in an insulated socket. A self-supporting vertical wire should have a loop formed on the top so that it is not a hazard to face or eyes. The length of the aerial will depend on the size of the model and the maximum range wanted. For close ranges the aerial can be short which would be useful for a small model boat controlled over a limited distance.

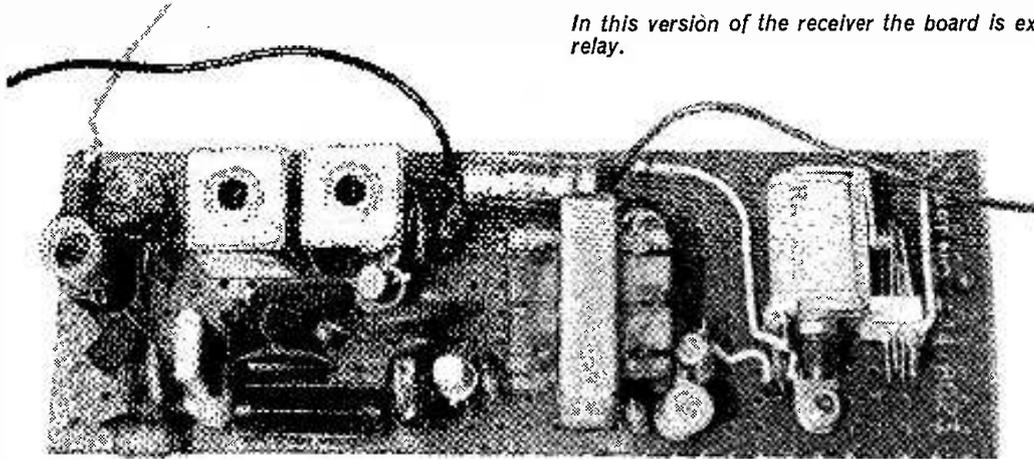In this version of the receiver the board is extended to take a small relay.



RECEIVER PROTECTION

In a model boat there may well be moisture, spray or oil so the receiver can be protected by fitting it into an insulated box with a tight lid, with aerial, relay and battery leads emerging through small holes.

A check on operation and range should always be made after any changes to the equipment. If loss of control may result in the model not being recovered, a careful watch should be kept on the condition of all batteries. These may appear adequate after an interval of rest, but may soon lose voltage when delivering current, if in poor condition.

RELAY

Provided the relay opens and closes reliably when the transmitter is keyed, at the range wanted, it will probably need no further attention. However, as range is increased, the rise in current decreases. The maximum range which can be obtained thus depends on the relay sensitivity, as well as other adjustments. For example, if the relay requires

35mA to close, operation will be satisfactory where this or a higher current is obtained, but will become unreliable and cease when current falls below 35mA. So if the relay were set to close at 25mA instead, control would still be obtained at an increased range.

The simplest way to check the operation of the relay, if necessary, is to connect the relay, a 2k Ω or similar wire-wound potentiometer and a 9V battery in series, with the meter on 100mA range also in circuit. Begin with the full resistance and on reducing this note at what current the relay closes. Some relays have an adjusting spring and can be set to very close limits. With others, careful bending of the contact springs or a flat spring will be needed.

Both a miniature model control relay, with a coil having a resistance of 35 ohms and a larger surplus type relay were found suitable. The small relay originally required 60mA but was re-adjusted to pull in at 25mA and this easily gave control at 100 yards. The larger relay was capable of more sensitive adjustment. A miniature relay is more appropriate for a model having limited space. In general, a relay of moderately high resistance, such as 100 to 250 ohms, will be more sensitive than relays of under 100 ohms but the greater coil resistance naturally reduces maximum current. If wanted, an extra battery could be added in series with the relay so that the additional voltage is available for Tr5 only, but this was not needed with relays of the type mentioned.

Where the relay may switch circuits carrying appreciable power it is necessary to watch that the relay contacts are suitable or they will rapidly deteriorate and become pitted or stick together. A small relay can control the circuit to a small actuator or motor but it is not suitable for controlling directly speed models where a propulsion motor may consume several amperes. Where the receiver relay is unsuitable for the current required, it should control a relieving relay of more robust type, which will in turn switch the circuit required.

With a 100 ohm relay and 4.5V battery supply, current through the relay cannot exceed 45mA. Using this receiver at ground level, with a 20in aerial and the hand-held 5-transistor tone transmitter described in Part 2 a current change of about 40mA was maintained up to a distance of 100 yards. This easily gives strong, reliable operation of the relay. With no tone radiated, the receiver draws approximately 3mA which is a very light load for even small cells.

PART 2 NEXT MONTH DEALS WITH THE TRANSMITTER CONTROL UNIT.

★ components list

Resistors

R1	18k Ω	R6	100k Ω
R2	15k Ω	R7	10k Ω
R3	2.7k Ω	R8	1.8M Ω
R4	47k Ω	R9	33 Ω
R5	1.2k Ω	R10	2.2k Ω

All $\frac{1}{2}$ or $\frac{1}{4}$ W 5%

Capacitors

C1	20pF SM	C8	0.1 μ F
C2	20pF SM	C9	0.047 μ F
C3	0.01 μ F	C10	0.1 μ F
C4	5pF SM	C11	0.1 μ F
C5	0.047 μ F	C12	30 μ F 6V
C6	22pF SM	C13	200 μ F 6V
C7	33pF SM		

Semiconductors

Tr1	BF194	Tr4	BC108
Tr2	2N3706	Tr5	BC107
Tr3	BC109	IC1	ZN414

Miscellaneous

IFT1/2 (Denco IFT13). Pair of crystals, Type HC6U, see text (Henry's) and crystal holders. Transformer T1 (Home Radio TR64). S1, slide switch, on-off. Waterproof box to suit. Plain Veroboard $3\frac{5}{8}$ x $1\frac{5}{8}$ in. 0.15in matrix. Former 7mm dia. and core.

Now two fascinating ways to enjoy saving money!

NEW! Sinclair Scientific kit **£19.95** (INC. VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range — features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £32.35 (including VAT).

And as a kit it costs under £20!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle *directly*

- sin and arcsin,
- cos and arccos,
- tan and arctan,
- automatic squaring and doubling,
- \log_{10} , antilog_{10} , giving quick access to x^Y (including square and other roots),
- plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied — all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer — they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

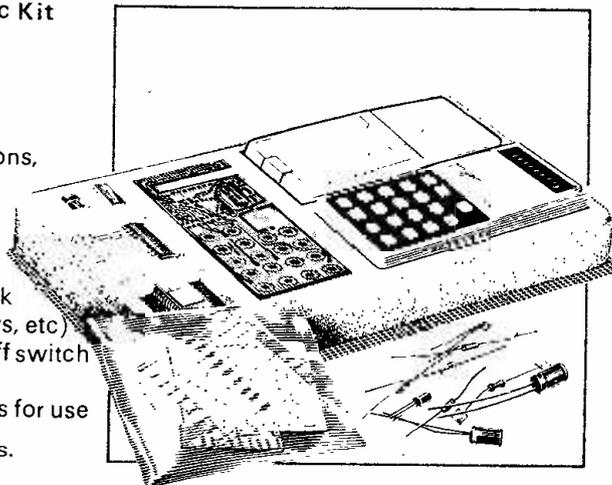

Features of the Sinclair Scientific

- **12 functions on simple keyboard**
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.

- **Scientific notation**
Display shows 5-digit mantissa, 2-digit exponent, both signable.

- **200-decade range**
 10^{-99} to 10^{+99} .

- **Reverse Polish logic**
Post-fixed operators allow chain calculations of unlimited length — eliminate need for an = button.

- **25-hour battery life**
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.

- **Genuinely pocketable**
 $4\frac{1}{3}'' \times 2'' \times 1\frac{1}{16}''$. Weight 4 oz. Attractively styled in grey, blue and white.



Sinclair Cambridge kit

Now only
£14.95
 (INC. VAT)

At its new low price, the original Sinclair Cambridge kit remains unbeatable value.

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below – then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

Take advantage of this money-back, no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

Scientific

Price in kit form £19.95 inc. VAT.


Price built £32.35 inc. VAT.

Cambridge

Price in kit form £14.95 inc. VAT.

Price built £21.55 inc. VAT.

Features of the Sinclair Cambridge

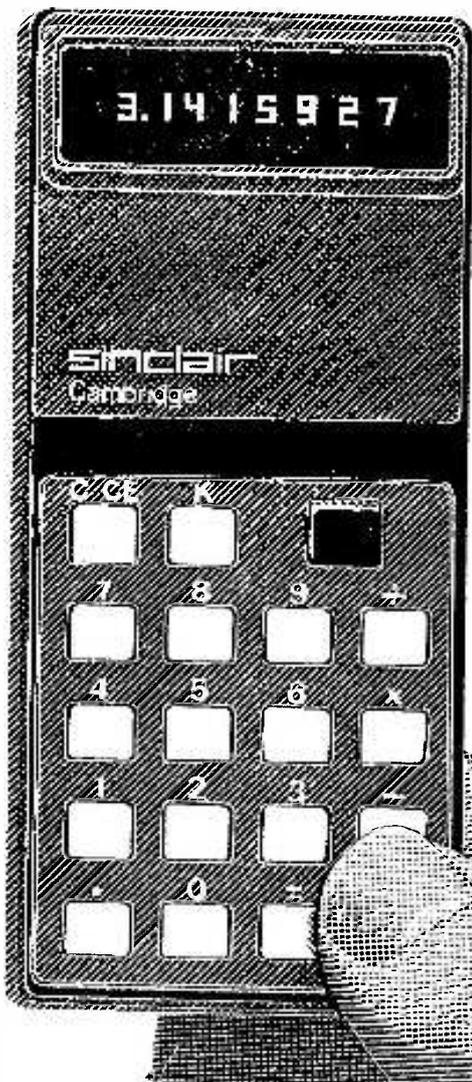

- Uniquely handy package. 4 1/3" x 2" x 11/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, -, ×, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £15.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,
 FREEPOST St Ives,
 Huntingdon, Cambs. PE17 4BR

Please send me

- Sinclair Scientific kit at £19.95
- Sinclair Scientific built at £32.35
- Sinclair Cambridge kit at £14.95
- Sinclair Cambridge built at £21.55

All prices include 8% VAT.

*I enclose a cheque for £....., made out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/ Access account. Account number

--	--	--	--	--	--	--	--	--	--	--	--

*Delete as required.

Signed _____

Name _____


Address _____

Please print. FREEPOST – no stamp needed.

PW/1/75

sinclair
 Sinclair Radionics Ltd,
 FREEPOST St. Ives,
 Huntingdon, Cambs. PE17 4BR.

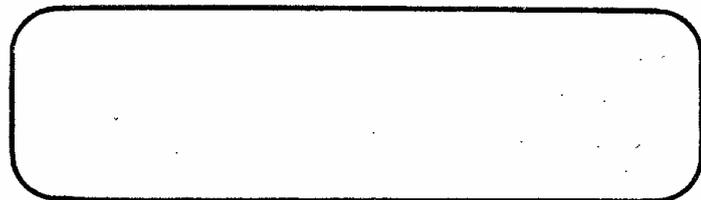Reg. No: 699483 England. VAT Reg. No: 213 8170 88.



by **Eric Dowdeswell G4AR**

JUST back from a couple of weeks of sunshine in SV-land, to be greeted by a nice pile-up of logs. Personally, I prefer a pile-up on 20m, especially if I am the focal point! All letters and logs will have been answered by the time this appears in print. I normally try to answer mail within a day or so of receipt but I have to have a break some time!

Eric Carling (Lymington, Hants) expresses surprise at the lack of logs for 10m especially since his Yaesu FR50B has rounded up 113 countries for him on that band this year. All round signals from a quarter wave vertical feed a Hamgear PMIA pre-selector. **Andrew Darragh** (Nr. Wetherby, Yorks) apologises for the absence of a log this month. He's been busy rewiring his AR88 and promises better things henceforth. Just so long as you haven't deserted us OM!

Paul Barker BRS 34898 (Sunderland) volunteered to provide some photos taken off his SSTV monitor but until I can persuade the Editor to give me some more space I am afraid it is not possible to include photographs. But, I can promise that there will not be any pics of any Fred Bloggs and a desk full of commercial equipment! Paul will be glad to assist those interested in SSTV. Also had a very interesting letter from MK Products, 5 Lancashire Drive, Belmont, Durham (alias G3LIV and G3RDI) who can provide PC boards for homebrew SSTV equipment, such as used by Paul Barker, and promise info and help to interested readers.

Lately 15m has been a happy hunting ground for **Bernard Hughes** BRS 25901 and his FR500SDX, logging 36 JA's in a couple of days. His comprehensive logging system shows a band/countries total of 533 countries on SSB from 10 to 160m so far this year with an all-time total of 1,048. Not to be outdone by Paul Barker and his SSTV antics, **Peter Roughley** (Warrington, Lancs) weighs in with a long list of RTTY call signs copied on 14.1 MHz in just a couple of days. His modest gear, fed from a 60ft wire or 21ft whip aerial is a BC312 with a Racal IF unit "grafted on as a Q5-er" feeding a homebrew terminal unit and 7B printer.

Michael Green A8088 (Northwich, Cheshire) bemoans his folk's colour TV timebase QRM and appeals for suggestions on suppressing same. Try shorting the aerial input to the chassis and see

how much is coming through the mains OM. Fit a mains suppressor if necessary, or try earthing your gear to a separate point such as an earth rod, after disconnecting the mains earth. All my own gear is earthed to an extensive buried radial system, used for 160m, and I get no QRM from a colour set situated about 15ft away. **Max France** (Warrington, Lancs) found that a 20ft vertical plus ATU produced better signals from the DX than separate dipoles for 10, 15 and 20m. Generally will OM, if one can tolerate the lack of horizontal discrimination such as a dipole will provide when placed end-on to the Euro QRM! **Tim Charles** (Colchester, Essex) has been braving our English summer and getting up at 0400 to check on 80m, usually finding ZL's at the top end. He is not too happy at a certain G-net station relaying VK and ZL's from 20 or 40m on to 80m giving the impression of a two-way QSO on 80m!

Kind letters from **Leonard Page** (Kilmarnock), **Malcolm Nesland** (Blyth) and **Bill Major** (Keighley) with hints on curing the hum on Yaesu 9R59 series of receivers, mentioned recently in this column. All amount to fitting an attenuator to the output and then turning up the audio gain. Try 100 and 10 ohm resistors in series across the output, the 100 ohm going to the live side and connect the phones to the junction of the resistors and earth. **Bill Urquhart** (Sutherland) repositioned the output transformer but got more joy replacing the 2kΩ resistor in the power supply circuit with a 10H choke. **Len Allard** (Leigh-on-Sea) wrote direct to Japan, to the makers, who suggested additional smoothing capacitors but again little improvement resulted. On my own 9R59DS I spent a week-end making some 25 mods to improve the overall performance, some taken from past articles in Radio Constructor, so it looks as if a separate article on the subject is now called for!

Alan Rae (Glasgow) has also taken the advice of your OT and provided himself with a 60ft vertical plus ATU for his CR100 and "it proved very effective especially on 80m" enabling Alan to log his first ZL's on the band.

Log extracts

Alan Rae:—80m VK2VQ VK4NE ZL2AR ZL3ACW ZL4BX 20m EA8TR TU2EF 3A2CP VE6JL/P.

Tim Charles:—80m VK2ALK ZL2BFT ZL3GX ZL4AA ZL4FB 40m BU3OS ST2RE ZL1AOP 20m AP9VHE XE6OMB YS2RL.

Max France:—80m FL8DJ ZD3R 6W8FP 9M2CJ 20m VK9YV VP8NS XP1AA 7P8AQ 15m KX6NQ 5N2ESH 10m CR6UE ZE4JW 3B8CV.

Michael Green:—40m HK4DHR 20m 7SL2AO



TU2DO.


Peter Roughly:—20m ALL RTTY DAILS DJ0CP DL2BR EA3OT EA8FF F5WG F9IB G3AWA G8FC HA5KDQ HZ1SH IIPXC I3BA IC8SMY SM0ASW TF3IRA VE7BDQ VK3KF W3KV 3A2GX.

Bernard Hughes:—20m KL7HRP VK5YH ZLIPZ ZD3R 3D2AZ (Fiji) 15m A35AF JG1MVA JR1YFD JE1MLK.

Paul Barker:—20m DUINRS FM7AQ TJ1AF TU2DO ZB2CJ (QSL G3ATU) KL7GDX JR1VMC 15m VQ9BP/D 7P8AY 10m A4XFE (Oman) HZ1KE 3B8CV.

Eric Carling:—10m VU2DK EA9FA VQ9BP/D (Desroches Is) 9Y4SH HC1CW FY7YM 5U7BA FH8CJ 7Q7DW CT2AK ZS3AW KC4AAC 9J2DT PAOIWH/S21 (Bangladesh) JY9GR VP8HZ.

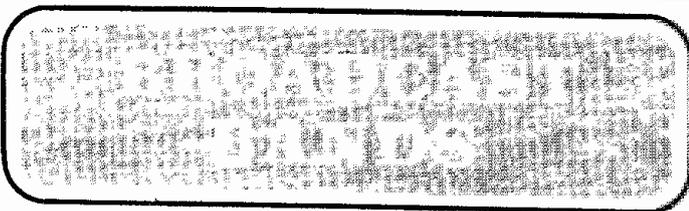CW stations in bold, remainder SSB. Please note that logs should be in alphabetical order for every band.



MEDIUM WAVE BROADCASTS

by Charles Molloy

RODNEY ARMSTRONG who lives at Ashby-Cum-Fenby, near Grimsby refers to the October issue of PW and the reception of the Yorkshire TV sound on the medium waves by **E. Jenkinson** of Sheffield. Rodney has had similar reception which he has traced to re-radiation from his domestic TV receiver. He can also receive BBC1 sound on the 49m band when his TV is switched to that programme. Reception was on a Sony 7R33L portable connected to a 50ft longwire antenna.

Timothy James reports again from Southampton. With his Fidelity RAD 16 he has pulled-in BBC local stations at Medway on 1034kHz (290m); London on 1457kHz (206m); Brighton on 1484kHz (202m); Oxford, also on 1484kHz; Bristol on 1546kHz (194m) and the BBC1 relay at Bournemouth on 1484kHz; the IBA outlets, Capital Radio on 557kHz and London Broadcasting on 719kHz. Europeans heard include AFN Frankfurt on 872kHz; Cluj, Romania on 1151kHz; Radio Sweden 1178kHz; Radio Prague 1268kHz and Radio Norway 1578kHz (this station has an English programme at midnight on a Sunday and there is a DX programme on the first Sunday/Monday of the month at 0020hrs GMT).

Paul Slinger refers to Radio City, the new Independent Local Radio outlet in Liverpool which is now on the air for twenty-four hours a day. The frequency is 1546kHz (194m) and the transmitter has a power of 1200 watts.

Brendon McNamee (Portrush, N. Ireland) reports that the low power relays at Dublin and Cork, both

of which transmit on 1250kHz have been experimenting recently with individual local programmes during the daytime.

Long distance reception on the medium waves is at its best during the winter months when a path of darkness exists for part of the day between the UK and the American continent to the west and to large parts of Asia to the east. Ideally, a communications receiver and medium wave loop aerial are the tools used by the MW DXer, but complicated equipment is unnecessary on this band. A domestic radio connected to an outdoor aerial will pull-in some DX and when conditions are favourable for reception of this area, will certainly receive a few of the stronger North American outlets.

DX from the west begins about 2330hrs when the path starts to open and a number of Europeans have closed down for the night. Canadians appear first. Listen for CJON in St. John's, Newfoundland on 930kHz; CBN also in St. John's on 640kHz; CHER in Sydney, Nova Scotia on 950kHz and CBA in Moncton, New Brunswick on 1070kHz. High power outlets on the east coast of the United States appear by midnight. Search for WNBC in New York City on 660kHz; WOR also in NYC in 710kHz; WINS in NYC on 1010kHz; WBZ in Boston on 1030kHz and WNEW in NYC on 1030kHz. Latin Americans to look for are Radio Jornal, Rio de Janeiro on 940kHz; Radio Belgrano, Buenos Aires on 950kHz; Radio Margarita, Venezuela on 1020kHz; Radio el Mundo, Buenos Aires on 1070kHz and Radio Tupi, Rio de Janeiro on 1280kHz. DX from North and South America reaches a peak between 0100hrs and 0200hrs GMT but it continues throughout the night until it gradually becomes swamped by Europeans opening up again for the next days broadcasting.

SHORT WAVE BROADCASTS

by Derek Bell

THE main topic of conversation among the short wave enthusiasts over the past few weeks has been the heavy storms that have reached us from the sun, dosing the ionosphere with radiation. This spectacular solar hiccup produced very far reaching effects that ruined many an evening's listening on the short wave frequencies.

The main disturbance was centered round the 14, 15, 16, of September with a visible aurora in Finland on the evening of the 15th. The outbreak started to bite on the Sunday the 15th at 1430, and by nightfall the 80 metre band went out completely. The BBC North Atlantic path also went out, along with most of the hope of amateurs engaged in contests. On Thursday, September 19th, another smaller disturbance was registered, and between them these two sent the sound of frying bacon and assorted grunts and groans down the spectrum to remarkably low frequencies, still it's an ill wind, I suppose our VHF colleagues enjoyed the fun.

To move on to the latest QSL news, Radio Canada is sending out a multi-coloured card depicting the world cycling championships 1974. This is a nice example of the graphic designer's skill, a pity it is unsigned and thus robs the artist of his due credit. Meanwhile, "Down Under" Radio Australia is accepting reports that are sent to its London office at **54 Portland Place, London W1**, they are still "clocking" between 60 and 90 days for a reply though. One of the most original "QSLs" that I have heard of comes



from Radio Baghdad, I have it on good authority that a certain collector received through the post (would you believe) two pounds of Dates!! Another QSLer has had the three volume biography of Kim Il Sung, from the Lebanon, he thinks that it came via the Radio Fyongyang mailing list.

While on the subject of the broadcasting stations, we must welcome Radio Israel to the ranks of those that put out a DX show, they have one due to start shortly hosted by one **Ben Dolphin** who I am told is an amateur and who hopes that his listeners will send him technical questions. Radio Israel also announce that they are to start a transmission to Australia and South East Asia at 1030 on their usual frequencies these are on the air with short gaps for twenty four hours a day, and the tuning signal is a national hymn on trumpets and drums with the spoken announcement "Kanshidurei Yisrael Mi-Yerusalayim" in Hebrew.

One final station to look at is Radio Finland who recently resumed their English Transmissions to North America at 0300-0330 with a 100kW on 9585 dropping their 2300 to 2330 transmission.

Turning now to postbag, letters are sparse this month due to the changeover. However, I have beside me a missive from **Trevor Bland** who resides at Lea in Lincolnshire. He operates a Teleton TF182 FB and the pick of his loggings are as follows:—

- 9545 Radio Ghana at 2115 in English
 - 11880 Voice of Turkey at 0005 in English
 - 15265 Radio Afghanistan at 1145 in English
- His aerial is a built-in telescopic five feet long assisted by a seventy-five foot-long external wire.

Mr. J. A. Martin (sorry about the formality but I have no more information) of Staines in Middlesex also tells us of his catches on his Codar CR70A, he runs a hundred foot aerial in the loft among the spiders and this picks out of the ether such goodies as:—

- 15270 Voice of Nigeria at 0600 in English
 - 15012 Radio Hanoi at 1800 in English
- To be awake at 0600 and DXing show that we have a dedication to our hobby equalled only by such people as fisherman, mountain climbers, or ardent PW readers!

Well folks that brings this month to a close so it only remains for me to wish you all good DX and long may your long-wires prove truly fruitful!

BROADCAST BANDS

Short Wave and VHF reports by the 15th of the month to **Derek Bell** c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to **Charles Molloy**, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/ alphabetical order by the middle of the month to **Eric Dowdeswell G4AR**, Silver Firs, Leatherhead Road, Ashted, Surrey, KT21 2TW.

points arising...

'TELE-TENNIS'

We have heard from several readers of problems in setting up Board A. Symptoms are the display of two or more "courts" side by side on the television screen.

A cure may generally be effected by increasing the value of R4 to 2.7k Ω , though it may be necessary to change VR2 to 25k Ω to be sure of coping with timing spreads in IC2.

'EPSOM' SHORT WAVE RECEIVER

The following points should be noted in conjunction with Fig. 13 in the October, 1974 issue.

1. The various coils and IF transformers are all wound with 28swg enamelled copper wire.
2. Winding L9 is a straight 40 turns—no centre tap.

'SANDOWN' F.M. TUNER

From experience gained in constructing several more tuners to this design, the authors have recommended a number of minor modifications to ensure consistent performance.

1. With certain samples of Tr102 and Tr103, spurious oscillations occur in the mixer stage at about 400MHz. These may be cured by inserting a ferrite bead between C110 and the junction of R107, R108, and Tr102 g2. If C110 is stood on end, the bead can be threaded onto the longer lead.
2. To reduce the effect of hum pickup in the oscillator tuned circuit, increase C118 to 0.1 μ F and insert a 100k Ω resistor, R118, between the junction of R111 and C118 and the tuning line (H). No modification to the pcb is necessary as R118 can replace the wire link beside C118.
3. The decoupling capacitor C227 on pin 11 of IC202 should be changed to a 22 μ F tantalum bead type.
4. If stronger a.f.c. action is required, R217 may be increased in value up to a maximum of 47k Ω .
5. Some mains transformers, although of the rating specified in the components list, may be incapable of driving scale lamps as shown in Fig. 3.

If the resistance of the secondary winding is too high, the voltage drop due to the lamp load will cause the supply to IC301 to fall below the level required for satisfactory operation. The ripple on the stabilised 13V line will increase and cause hum on the audio output.

For those constructors requiring the dial lamps, the solution is to use a transformer of a higher current rating or a slightly higher secondary voltage. If the voltage at pins 11 and 12 of IC301 exceeds 19V, a resistor of about 10 Ω should be inserted in the line to these pins to restore it to that level.

TAKE 20

DAVID ANDREWS

No. 67 BASIC WOBBULATOR

A series of simple transistor projects, using not more than twenty components.

ALTHOUGH we call this month's project a Wobbulator it is in fact a voltage controlled r.f. oscillator and as such might prove a valuable experimental circuit for many applications. Its most obvious application is as an aid to circuit alignment and we have designed it to operate from about 400kHz to just over 1MHz. Basically it consists of a conventional Hartley oscillator centred around Tr2, Fig. 1.

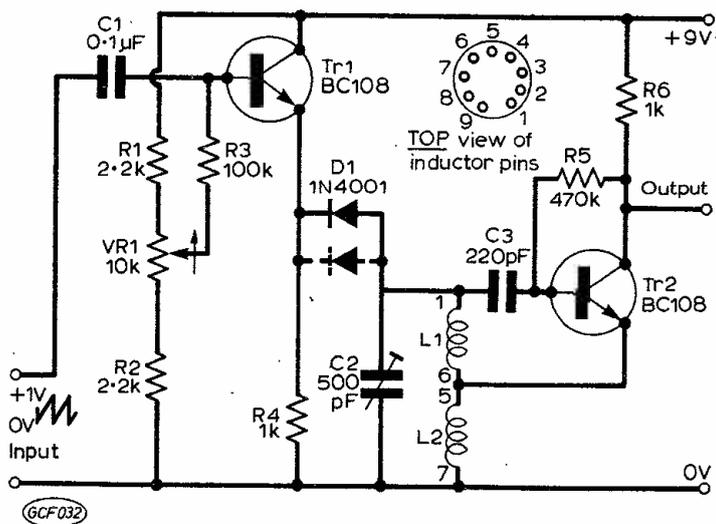


Fig. 1: Circuit for the Basic Wobbulator.

The coil used was one of the Denco Maxi-Q transistor aerial coils (Blue type) range 2T to give the desired frequency range. This is tuned by means of C2 and gives good coverage of the medium wave band as well as conventional intermediate frequencies. A high level is available at the output at quite a low impedance, nevertheless the oscillator is liable to "pulling" if too high a capacitive load is applied to the output. In most applications it will be found desirable to attenuate the signal by means of a suitable RC network—alternatively the output can be very loosely coupled to receivers under test (the output being taken "close" to the circuit in question without physical connection).

Higher frequencies

The prototype has only been tried with the above coil in the frequency range mentioned but there is no reason why it should not work at higher frequencies with different coils—provided the transistor has sufficient gain and circuit parasitics do not present problems. Should the gain of the transistor fall off at higher frequencies feedback coupling can be increased by increasing the value for C3. Excessive feedback will distort the output waveform as clipping sets in so do not make C3 larger than necessary for satisfactory oscillation.

"Wobbling"

To obtain "Wobbling" control of the frequency we must arrange to frequency modulate the oscillator with a control signal. In most applications this signal will be a sawtooth waveform extracted from the time base circuits of the test oscilloscope. The voltage control part of the circuit is around Tr1. The d.c. level at Tr1 emitter is set by VR1 and the sawtooth sweep is superimposed upon this. The voltage from Tr1 is used to control the shunt capacitance in the tuned circuit of the r.f. oscillator stage by means of D1. This diode is acting as a cheap substitute for a varactor diode and works extremely well. The principle of operation depends on the parasitic capacitance of the diode's depletion layer. When a diode is reverse biased very little current flows through it because of the layer between the p and n regions—known as the depletion layer—which is temporarily devoid of charge carriers. The depletion layer thus acts as a dielectric and the junction acts as a capacitor the value of which depends on the area of the junction and the width of this depletion layer. To get significant capacity we are using a large area junction—as found in a power rectifier—this gives capacity in the order of tens of picofarads.

★ components list

R1	2.2kΩ	} ¼W ± 10%	VR1	10kΩ linear
R2	2.2kΩ		C1	0.1µF (polyester)
R3	100kΩ		C2	500pF trimmer
R4	1kΩ		C3	220pF (see text)
R5	470kΩ		D1	1N4001
R6	1kΩ		Tr1 and Tr2	BC108

L1 and L2 Denco Maxi-Q aerial coil (Blue) range 2T B9A valve base (pc mounting).

The diode's capacity is varied by altering the width of the depletion layer. The greater the reverse bias on a diode the wider the depletion layer and hence the lower the junction capacity. Conversely as the bias on the diode is shifted in a forward direction the capacitance increases as the depletion layer gets narrower up to the point when the depletion layer disappears altogether and the diode is then said to be conducting in the forward direction.

Our circuit shows this diode as D1 and, of course, its polarity is very important. The polarity is such that it is always reverse biased by signal levels at the emitter of Tr1 and if these voltages vary, the internal capacity of the diode will change. The higher the voltage from Tr1 (in a positive direction) the more the diode is reverse biased and hence the

lower its capacitance and vice versa. Although it is not obvious from the diagram, this variable capacitance diode is acting in parallel with the main tuning capacitor C2 and hence input signal voltages will alter the frequency of the r.f. oscillator. For a wider range of control (together with a general increase in shunt capacity) you can put two or more similar diodes in parallel—this is shown by the dotted lines in both the schematic drawing and the layout.

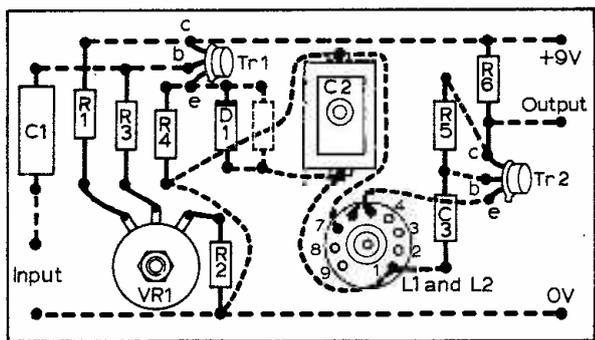


Fig. 2: Layout of Wobblator on plain Veroboard with components mounted on pins or tags. Dotted lines indicate wiring below the board. A B9A valve-holder may be used to take L1/L2, especially if different bands are contemplated.

The basic frequency of oscillation is set by C2 and this can be modified by the d.c. level at Tr1 emitter which is itself set by VR1. The degree of voltage control (as a percentage of the basic frequency) depends on the relative values of D1 and C2. At high frequencies (when C2 is at a low value) there will be a wider range of control than at low frequencies. In extreme cases the percentage variation is from about 100% to almost zero so some experimentation is needed. Of course, the voltage control is NOT linear with the output frequency over wide ranges—nevertheless it can be considered linear for a few percent modulation. R1 and R2 are present to prevent Tr1 being biased in extreme directions so that the input signal will always have some effect but it should be remembered that an excessive input signal could push Tr1 into an extreme conduction state if VR1 is set at either extreme.

As the title implies, this is a very basic circuit and although we cannot guarantee its quantitative accuracy it could prove very useful as a simple qualitative aid. Other applications could include experimental circuits involving phase locked loops and possibly self-tracking local oscillators for constant frequency reception of c.w. morse signals. **PW**

**DID YOU MISS THE
PW TELE-TENNIS
SERIES?**

**THIS TIME YOU ARE
LUCKY!**

For reprint information see page 835

Ensure you do not miss PW by taking out a subscription.

*SPECIAL PRE-PUBLICATION BOOK OFFER

RADIO SERVICING POCKET BOOK

3rd Edition

by Vivian Capel

- Completely rewritten to include developments and trends since the 1962 edition . . . including Stereo Radio and Car radios with more on various forms of interference.
- Gives basic theory on modern radio circuitry and design . . . plus useful information on older equipment.
- Emphasis has been placed on the practical aspect with chapters on Planning the Workshop, Test Equipment, Fault Finding and Alignment.
- Workshop routine and servicing techniques are prominently featured with a view to cutting labour costs.
- Incorporates a useful data section designed to reduce superfluous information, concentrating on the important facts.
- Incorporates for the first time in book form, a Makers' and Service Depots Directory that will prove invaluable for obtaining spare parts and service data for particular models.

NOT TO BE MISSED by

Radio Hobbyists

Radio Service Trade

Students working for RTEB examination

CONTENTS

Modern Radio Components. Valve Receivers. Modern Transistor Radios. FM Receivers. Stereo Broadcasting. Car Radios. Radio Aerials. Interference. Setting up the Workshop. Workshop Equipment. Workshop Techniques. Fault Diagnosis. Receiver Alignment. Useful Data. Directory of Radio Manufacturers and Service Depots.

256 pages 7½ x 5 ins. Illustrated, available at the end of December

Cover Price £1.95 (£2.10 inc. p/p)


**SPECIAL PRE-PUBLICATION
OFFER** only to readers of PW

SEND just **£1.60** to:-

**NEWNES-BUTTERWORTH (Dept PW)
BOROUGH GREEN, SEVENOAKS,
KENT TN15 8PH**

Do not send money or correspondence on this offer to Practical Wireless.

BIG Discounts

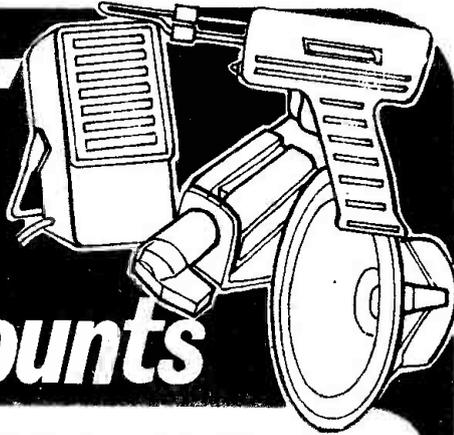

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£	£	
EMI 13" x 8" 3, 8 or 15 ohm	Plain	2-05	GOODMANS 6 1/2" 8 ohm Dualcone	2-15
With Co-Axial Tweeter 8 ohms only	Twln Tweeter	3-70	ELAC 8" 8 ohm Dualcone	2-25
Type 350 8 or 15 ohm, 20 watt		7-50	ELAC 8 ohm Dualcone 10 watt	3-50
6 1/2" 8 ohm, 10 watt		2-40	FANE 7" x 4" 3 or 8 ohm	1-00
8" 8 ohm, 10 watt		3-75	ADAstra 10" 8 or 15 ohm, 10 watt	3-45
12" 8 ohm, 20 watt		6-70	BAKER GROUP 25 12" 8 or 15 ohm, 25 watt	7-95
8" x 5" C/Mag. 5 watt		1-25	P. & P.	3-30
8" x 5" Dualcone		2-45	5" 8 ohm, C/Mag.	85
8 ohm, 10 watt		2-45	2 1/2" 8 ohm or 64 ohm	50
			P. & P.	15

TWEETER & CROSSOVER		£	£	
EMI 3 1/2" 3 or 8 ohm C/Mag	Cone Tweeter 8 or 15 ohm, 10 watt	1-20	Dome Tweeter 8 ohm, 30 watt	5-40
Cone Tweeter 8 ohm, 3 watt	Horn Tweeter 8 ohm, 20 watt	1-45	Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-20
		6-40	P. & P.	10

KIT FORM CABINETS TEAK VENEER		£	£	
12 x 12 x 6 with 8" 8" x 5" or 6 1/2" and 3 1/2" cut out	17 x 10 x 9 with 8" or 13" x 8" cutout	2-45	18 x 11 x 9 with 13" x 8" cutout for EMI 350	4-25
		3-50	P. & P. ea.	45

MICROPHONES		£	£	
CM70 Planet stick metal, switch crystal	DM160 Dynamic omni-dir. ball metal	1-55	UD130 50K/600 ohm, uni-dir ball metal	5-95
		3-85		
		5-95		

SOLDERING IRONS		£	£	
ANTEX CN240 15 watt	SK1 Kit (15 watt Iron 2 spare Bib etc.)	1-90	X25 25 watt (low leakage)	1-90
		3-30	P. & P.	10

CARTRIDGES & STYLII		£	£	
ACOS GP91/2SC or 3SC ster. comp.	GP93/1 or 95/1 ster. cryst.	1-00	GP94/1 or 96/1 ster. ceram.	1-75
		1-35	GP101 cryst. comp.	0-80
			GP104 ster. ceram.	1-65
			BSR X5M or X5H cryst. comp.	1-70
			SX6M or SX6H cryst. comp.	1-90
			SC5M ster. ceram.	2-60

CALCULATORS SINCLAIR		£	£
Cambridge	Scientific	19-00	

BATTERY ELIMINATORS		£	£	
240v Input 6, 7.5 or 9 300mA	12v d.c. Input (specify output)	2-95	6, 7.5 or 9 d.c. output at 300mA	2-30
			P. & P.	15

TAPES		£	£
5" 50p	LP 65p	1-00p	DP 1-00p
5 1/2" 85p	1-80p	1-40p	1-80p
7" 85p	1-10p	1-80p	1-80p

LOW NOISE CASSETTES		£	£
C60	35p	33p	30p
C90	45p	43p	40p
C120	55p	52p	50p

BIB ACCESSORIES		£	£
Tape Editing Kit	Ref. 23	1-35	
Recording Tape Splicer	Ref. 20	1-15	
Cassette Tape, editing	Ref. 24	1-50	
Cassette Salvage Kit	Ref. 29	45	
12's Cassette Case	Ref. 34	£1-50	
Stylus Balance	Ref. 32A	1-20	
Spirit Lever	Ref. 46	50	
Hi-Fi Stereo Test Cassette		2-10	
Groove-Kleen Record Cleaner		1-90	
	P. & P.	10	

PLASTIC LIBRARY CASES		£	£
For 5" Reels		18p	
5 1/2" Reels		22p	
7" Reels		25p	
	P. & P. 1-3, 9p ea. 4 or more, lot 30p		

WHARFEDALE SPEAKER BARGAINS		£	P&P
Linton 2 Kit (pr)		19-00	1-00
Glendale 3 Kit (pr)		33-50	1-50
Dovedale 3 Kit (pr)		52-00	1-50
Danton 2 Speaker (pr)		30-00	2-00
Linton 2 Speaker (pr)		39-50	2-00
Dovedale 3 Speaker (each)		42-00	2-00
Glendale 3 Speaker (pr)		57-00	3-00
Kingsdale 3 Speaker (each)		59-95	3-00

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

Riversdale Electronics

Mail Order Department **PWI**

P.O. Box 470, Manchester M60 4BU.



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: **ALDERMASTON COLLEGE**
DEPT. BPW 85
READING RG7 4PF

BPW85

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Trannies LTD.

4 BUSH HOUSE, HARLOW, ESSEX

Retail shop open
9.30 to 5.30 Monday to Saturday
Closed all day Wednesday

ALL PRICES FULLY INCLUSIVE OF VAT

SEMICONDUCTORS

TRANSISTORS—DIODES—RECTIFIERS—THYRISTORS—TRIACS—74 SERIES—IC's—THERMISTORS

Transistors	BA145 24p	BCY30 58p	ME04075 34p	NKT713 34p	2N930 22p	Ther-	IN5407 28p	7437 77p	74154 22.90
AA119 7p	BA154 14p	BCY31 68p	ME0491 23p	NKT773 30p	2N1131 26p	mistors	IN5408 34p	7738 77p	74155 21.95
AC107 25p	BA156 18p	BCY70 17p	ME0492 23p	OAS(GH5001) 19p	2N3132 26p	VA10668 15p	400mW Zener	7440 20p	74156 21.64
AC126 22p	BAX16 8p	BCY71 27p	ME0493 21p	OA10 24p	2N302 30p	VA10658 15p	Diodes	7441 81p	74157 21.81
AC127 18p	BC107 14p	BCY72 14p	ME1001 16p	OA47 9p	2N1803 30p	VA1066 15p	3-3v to 33v 12p	7442 81p	74160 22.18
AC128 18p	BC108 14p	BD124 1-30	ME1002 17p	OA90 6p	2N1804 38p	VA1067 15p		7443 7443	74161 22.44
AC141 25p	BC109 14p	BD131 52p	ME1075 19p	OA95 6p	2N1805 38p	VA1069 14p	Thyristors	7444 7444	74162 22.61
AC141k 29p	BC113 18p	BD132 57p	ME1100 20p	OA91 6p	2N1806 47p	VA1040 14p	1 amp	7445 7445	74163 22.84
AC142 22p	BC114 18p	BD131 } M/F	ME1120 20p	OA95 6p	2N1807 47p	VA1077 15p	50v 30p	7446 7446	74164 23.08
AC142k 29p	BC115 18p	BD132 } \$1.18	ME2001 15p	(HG1005, 7p	2N1808 58p	VA1100 14p	100v 32p	7447 7447	74165 23.38
AC151 23p	BC117 26p	BDY20 91p	ME2002 18p	OA900 9p	2N1809 56p		200v 37	7448 7448	74166 23.68
AC152 23p	BC126 17p	BF167 25p	ME3001 21p	OA920 9p	2N1813 24p		400v 46p	7450 7450	74174 23.78
AC153k 39p	BC126 17p	BF173 23p	ME3002 25p	OA919 55p	2N1711 25p	Bridge	3 amp	7451 7451	74175 23.94
AC153k } M/P	BC136 19p	BF177 27p	ME3011 21p	OC25 45p	2N2218 35p	Rectifiers	50v 36p	7453 7453	74177 23.95
AC170k } 8p	BC137 19p	BF178 34p	ME4001 18p	OC28 65p	2N2218a 45p	1 amp	100v 40p	7454 7454	74180 22.70
AC170k } 42p	BC140 35p	BF179 33p	ME4002 17p	OC29 69p	2N2219 42p	1 amp	200v 44p	7454 7454	74181 26.49
AC176 24p	BC147 12p	BF194 16p	ME4003 19p	OC35 59p	2N2219a 55p	2 amp	400v 46p	7454 7454	74182 22.16
AC187 22p	BC148 11p	BF195 16p	ME4101 18p	OC36 65p	2N2484 46p	5 amp	100v 54p	7472 7472	74184 23.69
AC187k 23p	BC149 13p	BF244 27p	ME4102 17p	OC41 20p	2N2646 51p	1 amp	50v 48p	7473 7473	74190 23.08
AC188 22p	BC157 17p	BF254 16p	ME4103 16p	OC44 20p	2N2904 25p	2 amp	100v 58p	7474 7474	74191 22.80
AC188k 23p	BC158 16p	BFX29 34p	ME4104 16p	OC45 20p	2N2904a 38p	5 amp	400v 67p	7475 7475	74192 22.53
ACY17 22p	BC159 16p	BFX84 25p	ME6001 18p	OC70 28p	2N2905a 38p	1 amp	50v \$1.89	7476 7476	74193 22.53
ACY18 22p	BC167 13p	BFX85 32p	ME6002 19p	OC71 18p	2N3053 23p	2 amp	200v \$1.98	7481 7481	74195 22.42
ACY19 22p	BC168 13p	BFX86 25p	ME6003 17p	OC72 18p	2N3055 45p	5 amp	400v \$2.25	7482 7482	74196 22.78
ACY20 23p	BC169 13p	BFX87 27p	ME6101 19p	OC75 24p	2N3702 18p	10 amp	400v \$2.45	7483 7483	74197 22.78
ACY21 24p	BC177 23p	BFX88 25p	ME6102 20p	OC81 28p	2N3703 11p	10 amp	100v \$2.51	7484 7484	74198 22.65
ACY22 19p	BC178 21p	BFY50 23p	ME8001 18p	OC81D 25p	2N3704 12p	10 amp	400v \$2.95	7485 7485	74199 26.65
AD140 67p	BC179 24p	BFY51 19p	ME8002 21p	OC83 24p	2N3705 11p		7400 20p	7486 7486	
AD142 59p	BC182 12p	BFY52 23p	ME8003 23p	OC84 28p	2N3706 11p		7401 20p	7489 7489	
AD143 52p	BC183 11p	BFY64 39p	ME9001 17p	TIP29a 54p	2N3707 11p		7402 20p	7490 7490	
AD149 65p	BC184 12p	BFY90 \$1.15	ME9002 18p	TIP30a 64p	2N3707 11p		7403 20p	7492 7492	
AD161 46p	BC212 13p	BY100 17p	ME9003 16p	TIP31a 77p	2N3708 10p	Silicon	7404 21p	7493 7493	
AD162 44p	BC213 15p	BY127 17p	ME9002 19p	TIP32a 88p	2N3709 11p	Rectifiers	7405 21p	7494 7494	
AD161 } M/P	BC214 15p	BFZ10 39p	ME9002 18p	TIP33a \$1.13	2N3710 11p	IN4001 7p	7406 21p	7495 7495	
AD162 } 95p	BC257 15p	BFZ11 38p	ME9002 18p	TIP34a \$1.86p	2N3711 11p	IN4002 7p	7407 21p	7496 7496	
AF114 20p	BC258 13p	BFZ12 38p	ME8112 38p	TIP35a \$2.19p	2N3712 11p	IN4003 8p	7408 26p	7497 7497	
AF115 20p	BC259 15p	BY213 28p	MP8113 49p	TIP36a \$4.07p	2N3719 20p	IN4004 9p	7409 26p	7498 7498	
AF116 20p	BC267 14p	C407 19p	MP8113 49p	TIP41a 88p	2N3819 27p	IN4005 10p	7410 26p	7499 7499	
AF117 20p	BC268 13p	MA8001 30p	NKT211 29p	TIP42a \$1.10p	2N2926 11p	IN4006 11p	7411 26p	7500 7500	
AF124 29p	BC269 14p	MA8002 40p	NKT212 29p	TIP2955 \$1.05p	2N3904 17p	IN4007 13p	7412 40p	7501 7501	
AF125 29p	BC270 15p	MA8003 40p	NKT213 29p	TIP3054 55p	2N3906 17p	PL4001 8p	7413 38p	7502 7502	
AF126 29p	BC271 15p	MA8003 40p	NKT214 27p	TIP3055 66p	2N4036 57p	PL4002 10p	7414 44p	7503 7503	
AF127 29p	BC272 25p	ME0402 24p	NKT217 58p	TIS43 27p	2N4058 13p	PL4003 11p	7415 44p	7504 7504	
AF139 62p	BC297 26p	ME0404 19p	NKT261 25p	V763 38p	2N4059 13p	PL4004 12p	7416 44p	7505 7505	
AF239 66p	BC298 24p	ME0404/1 19p	NKT271 21p	IN33a 11p	2N4060 13p	PL4005 14p	7417 44p	7506 7506	
AFY79 73p	BC300 41p	ME0404/2 19p	NKT274 21p	IN914 8p	2N4061 13p	PL4006 17p	7418 44p	7507 7507	
ASY26 39p	BC301 40p	ME0411 22p	NKT405 75p	IN916 9p	2N4062 12p	PL4007 22p	7419 44p	7508 7508	
ASY27 50p	BC302 36p	ME0412 21p	NKT405 75p	IN4148 5p	2N5172 11p	IN5400 18p	7420 45p	7509 7509	
ASY28 39p	BC303 48p	ME0413 18p	NKT603F 41p	IN4149 5p	4N5192 85p	IN5401 20p	7421 45p	7510 7510	
ASY29 42p	BC304 39p	ME0414 19p	NKT613F 38p	1544 5p	40361 45p	IN5402 21p	7422 60p	7511 7511	
BA111 32p	BC41 89p	ME0462 23p	NKT674F 33p	2N696 23p	40362 45p	IN5403 23p	7423 60p	7512 7512	
BA115 10p	BC461 45p	ME0463 23p	NKT677 30p	2N706 12p	40363 45p	IN5405 28p	7424 60p	7513 7513	
					40364 45p	IN5406 26p	7425 60p	7514 7514	
					40365 45p		7426 60p	7515 7515	
					40366 45p		7427 45p	7516 7516	
					40367 45p		7428 79p	7517 7517	
					40368 45p		7429 20p	7518 7518	
					40369 45p		7430 20p	7519 7519	
					40370 45p		7431 45p	7520 7520	
					40371 45p		7432 45p	7521 7521	
					40372 45p		7433 79p	7522 7522	

Resistors

1/2 watt 5% carbon 3-9 ohms to 10 meg	1p
1/2 watt 5% carbon " " " "	1p
1/2 watt 2% m/o 10 ohms to 1 meg	41p
1 watt 5% carbon 5-6 ohms to 10 meg	3p
3 watt wirewound 1 ohm to 6K8 ohms	10p
5 watt wirewound " " " "	12p
10 watt wirewound " " " "	18p

Volume Controls

Potentiometers
Carbon track 1k to 2meg
Log or Linear

Single	141p
Dual Gang Stereo	45p
Single type with D.P. Switch	32p

Miniature Presets

Carbon Skeleton type
All values 100 ohms to 5 meg ohms

1 watt	6p each
2.5 watt	7p each

Neons

8mm neon indicators
Red or Amber
at 6v, 12v, 28v, 110v or 230 volt.

26p each

miniature neon lamps
240v or 110v

6p each

Silver Mics 350v DC, ±1%

Values in pF's 2-2 to 220pF, 11p; 250 to 820pF, (12p; 1000 to 1800pF, 17p; 2200pF, 18p; 2700, 3600-F, 24p; 4700, 5000pF, 33p; 6800pF, 44p; 8200, 10,000pF, 55p.

Tantalum Bead

Solid tantalum capacitors Tol ±20%.

All values 20p each.

MF/voltage: -1/35, -22/35, -33/35, -47/35, 1/35, 2-2/35, 4-7/35, 10/6-3, 10/16, 10/25, 22/16, 47/6-3, 100/3.

Mullards Polyester Capacitors

C280 SERIES
250V P.C. mounting: 0-1µF, 0-015, 0-022 81p. 0-033, 0-047, 0-068 4p. 0-1 41p. 0-15, 0-22 51p. 0-33 7p. 0-47 91p. 0-68 12p. 1µF 14p. 1-5µF 22p. 2-2µF 27p.

C290 SERIES
400V: 0-001µF, 0-0015, 0-0022, 0-0033, 0-0047 3p. 0-0068, 0-01, 0-015, 0-022, 0-033 31p. 0-047, 0-068, 0-1 41p. 0.15 61p. 0.22 81p. 0-33 12p. 0p47 141p.

180V: 0-01µF, 0-015, 0-022, 0-033, 0-047, 0-068 31p. 0-1 41p. 0-15 4p. 0-1 41p. 0-15, 0-22 51p. 0-33 7p. 0-47 91p. 0-68 12p. 1µF 141p. 1-5µF 22p. 2-2µF 24p.

Veroboard

24 x 31	26p	15	Pin insertion tool	68p
24 x 5	31p	31p	Spot face cutter	57p
34 x 31	31p	31p	Pkt 50 Pins	22p
34 x 5	35p	35p		
17 x 31	24p	74p		
17 x 31	41-32	41-13		
17 x 5 Plain	41-10			

Electrolytic Capacitors

4 VOLT	10 VOLT	25 VOLT	40 VOLT
47µF 61p	220µF 8p	47µF 61p	470µF 18p
100µF 61p	330µF 10p	100µF 8p	680µF 25p
200µF 61p	470µF 10p	150µF 8p	1000µF 25p
320µF 61p	1000µF 11p	220µF 10p	2200µF 44p
1000µF 18p	1500µF 20p	470µF 13p	
4700µF 23p	2200µF 24p	680µF 20p	
		1000µF 22p	
		2200µF 35p	
		5000µF 68p	
6.3 VOLT	16 VOLT		63 VOLT
33µF 61p	15µF 61p		1µF 61p
68µF 61p	33µF 61p		2-2µF 61p
150µF 61p	150µF 61p		4-7µF 61p
470µF 11p	150µF 8p		6-8µF 61p
680µF 18p	220µF 9p		10µF 61p
1500µF 18p	680µF 17p		22µF 61p
2200µF 18p	1000µF 17p		68µF 10p
3300µF 26p	1500µF 25p		100µF 11p
	2000µF 43p		150µF 18p
10 VOLT	25 VOLT		220µF
22µF 61p	10µF 61p		470µF 26p
47µF 61p	22µF 61p		1000µF 44p


Ceramics

Miniature Ceramics 50v DC.

All values 1-8pF of 10,000pF 3p each.

- £1 BARGAIN PACKS**
- 10 Silicon npn power transistors (2N3055), tested/unmarked.
 - 30 Plastic FET's unmarked/untested. Similar to 2N3819.
 - 20 TO5 transistors npn 2 to 5A, untested/unmarked.
 - 20 TO18 transistors npn like BC178, BC179, etc., untested/unmarked.
 - 30 Plastic 2N3055, unmarked/untested. TO220 case.
 - 10 General purpose, fully tested FET's.

You've asked for it — here it is!

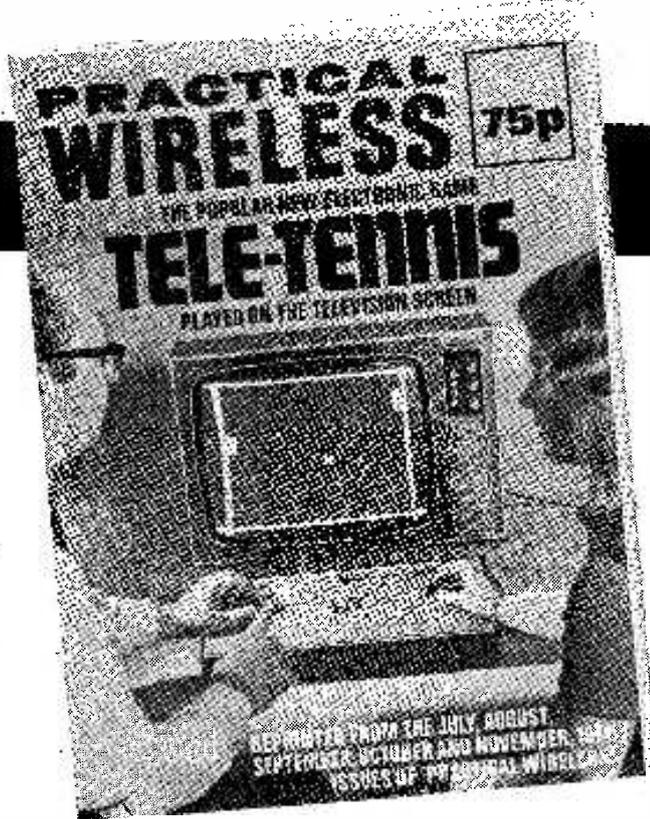


AVAILABLE NOW

Reprint of PW's TELE-TENNIS

SERIES JULY TO NOVEMBER '74

Send 75p + 5p (post & packing) to :-
Chief Cashier (PW Tele-Tennis),
I.P.C. Magazines,
Tower House, Southampton St.,
London, WC2E 9QX

PW TECHNICAL PUZZLE No.8

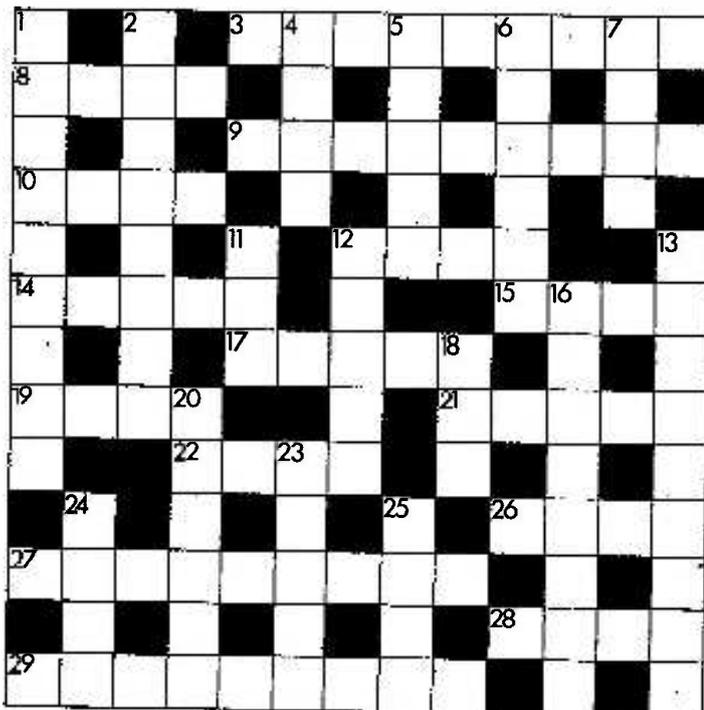

ACROSS

- 3 It shows the power of a circuit! (9)
- 8 Call-sign of an outside broadcaster (4)
- 9 Record twister in sound reproduction! (9)
- 10 Need a rectifier for perfect garden reception?(4)
- 12 If re-echoing within, it's unstable (4)
- 14 Sound level in a sporting arena (5)
- 15 Press-button control of breeding (4)
- 17 A call for cats-whisker enthusiasts? (5)
- 19 The heart of electro-magnetism (4)
- 21 Decay in earthing technique (5)
- 22 Circuitous safety device (4)
- 26 Scots resort to bandwidth induction (4)
- 27 Electrical manufacturer may be dynamic (9)
- 28 An insulator from the mainland (4)
- 29 The frequency with which it transposes! (9)

DOWN

- 1 It starts strongly but weakens (5, 4)
- 2 It reveals current pressure in receiver design (8)
- 4 A strange connection made by Lily! (4)
- 5 A fine selector of wavelengths! (5)
- 6 Uses the by-pass technique (6)
- 7 Girl central to model laser design? (4)
- 11 Electrical unit from the old German (3)
- 12 Picturesque type of aerial (5)
- 13 I nosed about around Meg for an early phonograph(6, 3)
- 16 Aim be set to adapt oscilloscope system? (8)
- 18 Low howls with someone unknown inside? (3)
- 20 Result of cultivated distortion is a fact! (6)
- 23 Band that's not cold-shouldered (5)
- 24 Ferrite terminals cause a celebration (4)
- 25 Eastern European electrode? (4)

FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH

HOTLINES

ON RECENT DEVELOPMENTS

TV WALLPAPER

Printed circuit boards are all very well in saving the amount of wiring which needs to be done by hand, but the idea has now been taken a step further. A laminate company is offering for sale printed circuit boards which have a resistive layer beneath the copper layer. The idea is that one first etches away all the copper not required leaving only the desired connection pattern on the board surfaces. This exposes the layer of resistive material which the copper etchant does not affect. The required resistor pattern is then selected by printing using a negative and photoresist just as in normal PCB processing. The board is then etched in a solution which dissolves the unwanted resistive layer and bingo, resistive networks etc can be printed down and connected via the copper connection pattern. One company recently exhibited some tiny resistive patterns connected in this way. The patterns had small holes drilled through the PCB. The idea was that one simply pushed a transistor into the holes and the active device, together with the resistors already connected up, formed the well-known Schmitt trigger circuit. I wonder what else can be printed down onto the PCB? Perhaps in the end, the circuitry for television sets will be printed rather like wallpaper.

MEDICAL HELP

One of the most distressing ailments of our time is cancer. A British doctor, with the aid of electronics, is trying to do something about it. One way to check for cancer is to "tag" tumor antibodies in the patient and then measure the quantity. The "tagged" antibodies react with the patient's cells and give an indication of any cancer which might be lurking. Trouble is that all this takes time. The new method employs a mini-computer and allows some seven times the amount of samples per day to be processed when compared to other methods less automated. There's even a print out system which keeps the physician informed as to just how the test is going.

DEATH RAY

Readers may remember my commenting on a cigar-sized laser which was capable of putting out some very high power. I hear now that a nuclear-pumped laser has just arrived on the scene which would appear (at least in theory) to be capable of arc welding a missile to the nearest cloud. Experiments so far have been confined to using a helium-xenon gas laser which is excited by a neutron pulse from a reactor. Because of the military applications possible with this device, information is sketchy. However, it seems that the "death ray" is here and that metal could be melted and destroyed at quite vast distances.

MAGNETIC BUBBLES

Magnetic bubbles are back in the news. These are tiny bubbles which can be magnetised and passed along a chain thus forming a kind of memory which could be used in computer applications. These bubbles are only tiny—around 5 micrometers. "Too big," say Bell Laboratories who aren't known for telling fibs. Bell think that a single solitary micrometer is quite big enough. The effect will be to give greater packing density and lower power consumption. Well worth watching, these bubbles. Bell produced a bubble device about 12 to 14 months ago which took the form of a 100-bit shift register. Now they have succeeded in building an 8,000 bit array onto a 40 × 40 mil chip. How's that for progress in just over a year! If you really want to get technical about it, the film which contains these tiny bubbles in the latest device is composed of a gadolinium-cobalt-molybdenum alloy which in turn has been sputtered onto a glass substrate. Looks like future electronics engineers will need a degree in chemistry too.

Before you get all excited about the bubbles for memories, don't forget that charge coupled devices are bubbling along; an 8 million-bit memory was the highest count I last heard of—but then that was a month or two ago! Another interesting comparative newcomer is the

Josephson effect device. These are almost unbelievable if all the tales are true. To date they are claiming switching speeds in million-millionths of a second and power consumptions of meagre microwatts. Already these devices have been mentioned in applications for amplifications at 300GHz.

WELL 'ORGANISED'

Electronic organ enthusiasts will be pleased at the sound of the new SAH 200. It's an integrated circuit which can produce the top 13 notes of an electronic organ. Previously this task took three of the company's ICs. The device needs a single supply of 22V and is based on MOS technology. It comes in a 16-pin dual in-line package.

I.C. A CAR!

Motoring enthusiasts may like to know of a different IC; this time it's designated SAK 140 and it is intended for engine rev counters. It converts input pulses from the engine contact breaker into output current pulses of constant width and amplitude. I hope to give greater details next month if the circuitry (which is extremely simple) arrives in time.

DIGITAL TUNING

A parting thought. Your hi fi amplifier may be digitally tuned and controlled in future. Some ICs on the market require only a variable d.c. applied to be able to control such things as frequency response. One application given by the manufacturers shows an active bandpass filter whose response is controlled by a simple d.c. signal. Other examples include channel selection from a number of separate inputs. One advantage is that the d.c. control signal is not prone to interference in the same way that an a.c. control signal would be.

Ginsberg

no extras
all prices inc VAT
FREE delivery



ALL ITEMS SUBJECT TO
MANUFACTURERS INCREASE
AND AVAILABILITY
**Personal
Callers are
Welcome!**

**High Quality
Construction
Kits, stocked
at all branches
Send for
catalogue!**

AMPLIFIERS
Teleton SAQ3078 + 8 watt £27.00
Rotel RA211 £43.95
RA311 £54.95
RA611 £86.95
Leak Delta 30 £54.75
Samsui AU101 £48.25
AU505 £74.95
Sinclair 2000 £34.95
Sinclair 4000 £45.95

Adastra 'Hi-Ten' 10in
10 watt 8 or 15 ohm £3.60
Also 5in 8 ohm speaker £0.99
2 1/2in 8 or 64 ohm
speaker £0.50

G800 3.95 1.95
G800H 3.95 1.95
G800E 6.99 3.95
SHURE
M44G 4.95 3.95
M55E 6.25 4.95
M75ED Type 2 11.75 8.25
MJ5EJ Type 2 9.75 6.25
VIS Type 3 32.25 —

CALCULATORS
Sinclair Cambridge Build £19.95
Scientific £29.95

SINCLAIR PROJECT 80
Stereo Pre-amp. £11.95
Active Filter Unit £6.95
Z40 15 watt Amp £5.45
Z60 25 watt Amp £6.95
P25 Power Supply for 240 £4.98
P26 Power Supply for 240 £7.98
P28 Power Supply for 260 £7.98
FM Tuner £11.95
Stereo Decoder £7.45
Q16 Speaker £7.10

TUNERS & RECEIVERS
Leak Delta AM/FM £58.75
Sinclair 2000/4000 Tuner £34.95
Rotel RT222 £42.75
Rotel RX150A Tuner/
Amp. £59.95
Rotel 152A £69.95
Sansui
210 AM/FM/MPX £84.25
310 AM/FM/MPX £99.50
350A AM/FM/MPX £106.95

**WHARFEDALE SPEAKER
BARGAINS**
Denton 1 pr. £26.75
Denton 2 pr. £32.00
Linton 2 pr. £40.75
Glendale 3 pr. £60.95
Kingsdale 3 ea. £64.95
Dovedale 3 ea. £44.95

MICROPHONES
UD130 50K/600 ohm
uni-dir. ball metal £5.95
UD147 £9.25
Condenser Mic. 600 ohm
uni-dir £9.50
Cassette Stick Mic. with
R/Control £1.60
Mic-Mixers Mono/stereo £5.50
AKAI ADM14 £5.95

PORTABLE RADIOS
Vega Jade £5.75
Vega Zircon £8.25
Vega Sapphire £7.25
Vega VEF206 £13.95
Micado LM/MW/FM/5SW £18.95
Murphy
8833 MW/VHF £9.95
BA838 LW/MW/VHF
M/Batt £18.50
MA5003 Head Set
Radio LW £7.95

RECORD DECKS
SP25 Mk III £11.00
Garrard SP25 MkIV £12.95
BSR MP60 £11.95
BSR Invicta P & C/SC7M £9.95
Garrard
SP25 MkIV P & C G/800 £21.00
AP76 Module £30.00
Goldring GL78 P & C/
G800E £59.95
Connoisseur
BDI Kit £13.50
BD2 Chassis/SAU2 £32.50
SAU2 £14.25
SCUI £5.95

KITS
Linton 2 pr. £20.95
Glendale 3 pr. £35.95
Dovedale £55.50

HEADPHONES
Rotel
RH430 £4.75
RH 630 £7.75
RH 700 £11.50
Koss
K711 £10.95
KRO711 £10.95
K6 £11.50
K6LC £14.00
K0727B £16.00
K0747 £20.75
HV1 £21.95
PRO4AA £26.95
PRO54 £29.95
K6LCQ £26.00
Sansui SS10 £14.20
*Headphone adaptor
(Junction box) £2.50
extension lead 2ft curly £1.35

BUSH
VTRI65 LW/MW/VHF £22.00
VTRI27 LW/MW/VHF £15.50
VTRI78 VHF/MW/2SW/
AIR M/Batt £27.50
VTR 175 LW/MW/VHF £13.95
VTRI88 LW/MW/VHF/
2SW M/Batt £31.95
BY5661 LW/MW/VHF £14.95

TAPE DECKS (Insurance 2.00)
Akai
4000DS Reel to Reel £93.95
4000DB Reel to Reel
Dolby £149.50
1721L Special Offer £77.95
GXC36D £82.00
GXC38D £103.95
CS33D £79.95
Akai CR81D 8-track Rec.
player £73.95

**SPEAKER CABINETS IN
KIT FORM (Teak Veneer)**
12in x 8in x 6in
(8 x 5 or 7 x 4 cutout) £2.50
14in x 12in x 9in
(10", 8 x 5, 8", 6 1/2" & 3 1/2") £3.75
18in x 11in x 9in
(8" x 2" or 13 x 8) £4.95
22in x 14in x 9in
(12" & 3" or 13 x 8) £6.25

CASSETTES
C40 C60 C90 C120
Low Noise — 35p 45p 55p
Philips — 55p 75p 110p
Memorex 65p 79p 110p 155p
Ampex (360) 45p 55p 70p 99p
Ampex
(20-20+) 59p 65p 99p 135p
Chromium
Dioxide — 99p 140p —
Cassette Head Cleaner 45p
Ampex Head Cleaner/Demag £1.65
BIB Stereo Test Cassette £2.15
Cassette Racks (hold 6) £0.45
Cassette Rotating Racks
(hold 20) £3.50
Cassette Carrying Case
(BIB) (hold 12) £1.60

CLOCK RADIOS
Bush CR128 LW/MW £13.60
Bush CR232 MW/VHF £24.95
Murphy MV5600
MW/VHF £22.95

SPEAKERS
Chassis Speakers
EMI (Plain) 13in x 8in,
3, 8 or 15 ohm Bass unit £2.30
with Single Tweeter
(only 8ohm) £2.45
with Twin Tweeter £3.95
Type 350 Kit 15 watt 8 ohm £8.25
13in x 8in Bass unit
15 watt 8 ohm £4.95
8in x 5in 5 watt 3, 8 or
15 ohm £1.50
8in x 5in 10 watt
Dualcone 8 ohm £2.50
6 1/2" 10 watt 8 ohm £2.65
8in 10 watt 8 ohm £3.90
12in 20 watt 8 ohm £6.95
Fane 8in 4 or 15 ohm £2.25
Fane 7in x 4in 3 or 8 ohm £1.20
Elac 8in 8 ohm Dualcone £2.50
Elac 10in 8 ohm Dualcone £3.75
Goodman 6 1/2in 8 ohm
Dualcone £2.40
Baker Group 25 12in 8 or
15 ohm £7.95
Adastra 'Top 20' 12in
25 watt 8 or 15 ohm £8.25

TWEETERS & CROSSOVERS
EMI 3 1/4" c/magnet in 3 or
8 ohm £1.25
Cone Tweeter 10 watt
8 or 15 ohm (K2006) £2.70
Cone Tweeter 3 watt
8 ohm (K2003) £1.55
Horn Tweeter 8 ohm
(K2007) £6.50
Dome Tweeter 8 ohm
(K2011) £5.50
2-way Crossovers (CN23,
CN28, CN216) £1.30
3-way Crossover (CN38) £2.75

8-Track Cartridge Blanks
C40 C64 C80
80p 95p £1.10
Ampex
8-track H/Cleaner
Demagnetiser £1.90
8-track Carrying Cases
(BIB) £1.65

CASSETTE RECORDERS
Murphy BA206 £16.95
Bush TP66 M/Batt £25.75
Murphy BA200 M/Batt £22.75
Bush BT8504 (miniature) £25.50

CARTRIDGES & STYLI
D/D
Styli
ACOS
GP91/2SC or 3CS
(ster. comp) 1.10 1.25
GP93/1 or 95/1
ster. cryst. 1.35 1.25
GP94/1 or 96/1
ster. ceram. 1.75 1.25
GP101 cryst.
comp. 90 —
GP104 ster.
ceram. 1.75 1.25
BSR
X5M or X5H
cryst. comp. 1.75 1.25
SX6M or SX6H
cryst. ster. 2.00 1.25
SCSM ster. ceram. 2.75 1.25
SONOTONE
9TAHC or
9TAHC/G
(Diam.) 1.85 1.25
3509 Magnetic
AUDIO TECNICA
AT55 1.95 —
EMPIRE 999 REX 3.95 —
GOLDRING
G850 2.95 1.95

TAPES & CASSETTES
Std LP DP Cases
5" 55p 65p 1.00 20p
5 1/2" 65p 86p 1.35 25p
7" 80p 110p 1.85 30p
High frequency Ampex
5" — 1.40p 1.55p
7" — 1.90p 2.95p
AKAI Metal Reel 7" £1.99

**RADIO CASSETTES
(Mains/Batt.)**
Micado 8155 AM/FM £25.95
Murphy BA209 MW/VHF £33.50

**STEREO RECORD PLAYER
& SYSTEMS**
Bush SPR58 £29.50
Bush SPR59 £31.50
Bush A1005 £56.50
Hanimec H101 £39.95
Hanimec HRC5060 8-track
AM/FM/MPX + Speaker £116.95

CAR AUDIO
Bush Car Cassette BT8501 £36.75
Hitachi Car Radio
WM702R LW/MW £16.50
KM1510 LW/MW/VHF £32.50
Hitachi Car Cassette
CS114 £45.00

ALL MERCHANDISE FULLY GUARANTEED

ALL ITEMS SUBJECT TO
MANUFACTURERS INCREASE
AND AVAILABILITY

**PERSONAL CALLERS
WELCOME**

**NEWMART
ELECTRONICS**

Mail Order Dept PW/I
Belmont St, Monton,
Eccles, Manchester.
Tel: 061-789 5268

Manchester
30-32 Shudehill. tel 061.832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738

4-STATION INTERCOM



£15.05

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 50p

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £23.75 per pair P. & P. 60p

INTERCOM/BABY ALARM



OUR PRICE ONLY **£6.50**

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire and Battery. P. & P. 40p

TELEPHONE AMPLIFIER



£6.45

Why not boost business efficiency with this incredible Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 30p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.9)
169 KENSINGTON HIGH STREET, LONDON. W.8.

TRANSISTORS (p. & p. 10p.)

All new and full spec.

BC107/8/9, BC147/8/9, BC157/8/9 all 9p
BF180 25p, BF182/3 40p, BF184 17p,
BF187 13p, BFW10 55p, 741 8DIL 34p,
BF336 35p, 2N3771 £1.10, 2N3441 50p,
BD131 40p.

EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards £1 (30p)

DURAL EXTRUDED HEATSINKS, 10D outline, black anodised, drilled for 4 x TO3 transistors 5 x 4 x 1 1/4 40p (15p)
Sim. to above but for 8 x TO3 5 x 8 x 1 1/4 70p (27p)

ELECTROLYTICS

15,000µ 30v, 68,000µ 16v 65p (22p)
30,000µ 25v 65p (22p)
4,000µ 70v, 3,600µ 40v 4 x 2" 55p (15p)
5,000µ 35v 40p (12p)
20A 100 piv Si recs. 4 for £1 (12p)
3A 100 piv Si recs 4 for 50p (8p)
250 mixed resistors 60p (13p)
250 mixed capacitors 60p (11p)
150 mixed HI-STABS 60p (11p)
200 Si planar diodes 60p (8p)
QH bulbs 12v 55w 50p (7p)
2N3055 EQUIV 4 fo £1 (10p)

Postage and packing shown in brackets
ADD 8% VAT TO TOTAL

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8. 01-478 8499

AMBIT INTERNATIONAL

'74 Datologue issue:

The latest datologue has more data, more new devices than ever. Linear, Digital, Discrete, LEDS. now 20p

New trade and professional price structure for quantity buyers.

NE561B AM/FM PLL **£3.19**
NE 562B FM (synth) **£3.19**
NE565A FM/FSK **£2.55**
NE567V AM/FM tone **£2.75**
NE555V Timer **77p**
CA3089E FM IF **£1.95**
CA3090Q Stereo dec. **£3.55**
SN76660N FM IF **£1.00**
µA753 FM gain **£0.99**
MC1310P Stereo dec **£2.85**
TBA651 AM/FM/SSB **£1.81**
TAD 100 AM **£1.47**
LM309K 5v 1amp **£1.90**
NE550/µA723 reg. IC **£0.85**
710 comparator **£0.47**
741 op amp **£0.38**
3900 quad amp in 14 DIL. really versatile **£0.68**
1496 bal mix. (SSB) **£1.02**
LM380 audio power amp **£1.00**
TBA810S 7w rms AF **£1.50**

8038 sine : square : triangle generator. 1000 : 1 sweep complete audio generator—including 12 pages of data **£3.10 each**

See the datologue for more details of more devices.

TOKO INDUCTORS AND FILTERS. Only from AMBIT

CFS 10.7 FM ceramic **£0.40**
CFT 455 ceramic **£0.45**
CFU 455 ceramic **£0.50**
MFH *T mechanical **£1.35**
KACS 586 HM (CA3089) 30p
150J now 220K " 15p
CA3090Q 2mH coil " 30p
MW & IF coils (10mm) 30p
BLR2011N 19 & 38kHz filter for stereo **£1.80**
TOKO inductors and filters—only from Ambit.

DFM & TIMER constructors:
FND70 7 seg. LED display with 7490 & 9368 on a DS FG PCB **£5.00 ea. £4.50 ea 4 off**
1 MHz TTL Clock—Divided down to 1 Hz **£9.50 inc. xtal.**


AMBIT INTERNATIONAL (PW7)

37a High Street, Brentwood, Essex CM14 4RH. (216029)

New devices + data
PLEASE ADD 8% VAT. P.P. 10p.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

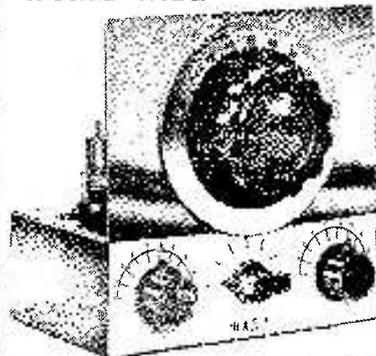

Famous for over 25 years for Short-Wave equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public School, R.A.F., Army, Hams, etc.

1974 "DX" RECEIVER

Complete kit—Price £4.60 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver."


This kit contains all genuine short-wave components, drilled chassis, Valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits and components. Test Report available. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX No. 16, EAST GRINSTEAD, SUSSEX RH19 3SN

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

RUN YOUR TRANSISTOR RADIO OR CASSETTE RECORDER FROM YOUR CAR BATTERY (Similar to illustration)

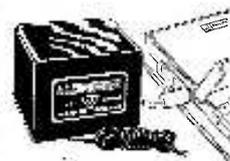This unit enables you to run your cassette tape recorder from the car whilst travelling. It is easily fitted and comes complete with fitting instructions. Please state make of cassette, voltage and type of plug required



ONLY £2.86

RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, make and type of plug required, if in doubt send diagram of recorder socket.)



ONLY £3.40

MAINS UNIT FOR TRANSISTOR RADIO ONLY



For single outputs, 6v, 9v **£2.86**

For two separate outputs, 6v + 6v, 9v + 9v **£3.52** per unit. (Please state outputs required.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety. All British Made. All Prices inc. V.A.T. and P. & P. R.C.S. PRODUCTS (RADIO) LTD. (Dept. P.W.J.)

31 Oliver Road, Walthamstow, London, E17
Full refund if not completely satisfied.

EXPERIMENTAL WORKSHOP

M. J. HUGHES
M.A., C.Eng., MIERE.

LEARNING BY PRACTICAL PROJECT STEPS

PART 14—PHASE SHIFT CIRCUITS (cont)

THERE are innumerable applications of positive feedback and it would be impossible to give examples of all of them. Nevertheless following on from last month's experiments we felt it would be logical to continue with two other types of circuit which rely on phase shift and can be used in conjunction with feedback to make oscillators. At the same time we hope to show that positive feedback, alone, is not sufficient for oscillation to take place—there must always be a loop gain greater than unity.

We have selected two important circuits to describe this month; the **Wien Bridge** and the **Twin-T** or **Bridged-T network**.

Fig. 99 shows the basic circuit of a **Wien Bridge**. Basically it is a top cut and bottom cut filter rolled into one. Although it needs a lot of mathematics to prove it one can consider it as a circuit that will attenuate low frequencies and high frequencies to a great extent but will not have such a dramatic attenuation effect on middle frequencies. The response curve showing what the output voltage would be for different frequencies of input voltage is shown in Fig. 100.

The frequency of maximum output is called the *resonant frequency* and if the values of components in the bridge circuit follow the rule that $R_1=R_2$ and $C_1=C_2$ the output voltage at the resonant frequency is always one third of the input voltage

$$V_{out} = \frac{V_{in}}{3}$$

For all other frequencies the output voltage is considerably lower than the input.

Provided the two resistors and capacitors are of equal value there is a simple formula that relates the resonant frequency to these components

$$f(\text{resonance}) = \frac{1}{2\pi \times R \times C}$$

where R is in ohms, C in farads and f is in hertz.

Clearly, one could use this circuit as a passive filter of the "band pass" variety by inserting it between two stages of an amplifier—rather like the simple top and bottom cut filters described in an earlier part.

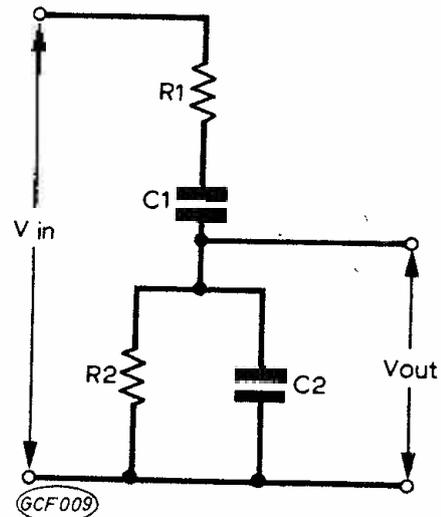


Fig. 99: Basic circuit of a Wien Bridge. Usually $R_1=R_2$ and $C_1=C_2$.

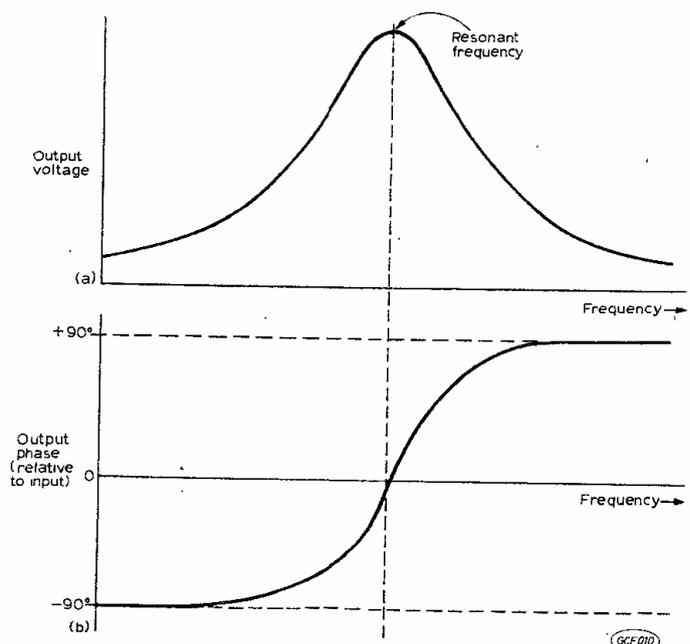


Fig. 100: top, shows that the output from a Wien Bridge is maximum at a particular frequency (resonance), below, indicates that there is no difference in phase between input and output at the resonant frequency.

The Q , or *quality factor* of such a filter is not very great so consequently it could not be used for accurate frequency selection.

When dealing with complex filters of this type one must not overlook what happens to the *phase* of the signal as it is processed by the circuit. In practice one can draw two curves to describe a filter's characteristics; the amplitude/passband characteristic that we have just described, also the relative phase of the output signal with respect to the phase of the input at different frequencies. Such a phase plot is shown in Fig. 100.

It should be noticed that for all frequencies below the resonant frequency the output lags behind the input by up to 90° in the extreme case, but above the resonant frequency the output has changed through zero phase to a leading condition and in the extreme this can be $+90^\circ$. This means that at resonance the output signal is *exactly* in phase with the input—in other words the network offers zero phase shift at resonance.

We can make use of this effect to produce a very versatile oscillator, the basic block diagram of which is shown in Fig. 101. We have already established


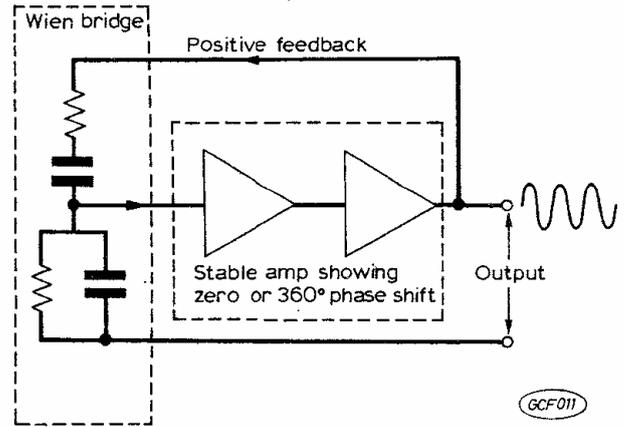


Fig. 101 : When connected into the feedback path of an amplifier having zero overall phase shift the Wien Bridge offers a simple way of making a sine wave oscillator.

that a two stage grounded emitter amplifier has an overall phase shift of 360° (which is the same as zero). Thus, if the output was connected back to the input we would have a condition for positive feedback.

continued on page 843

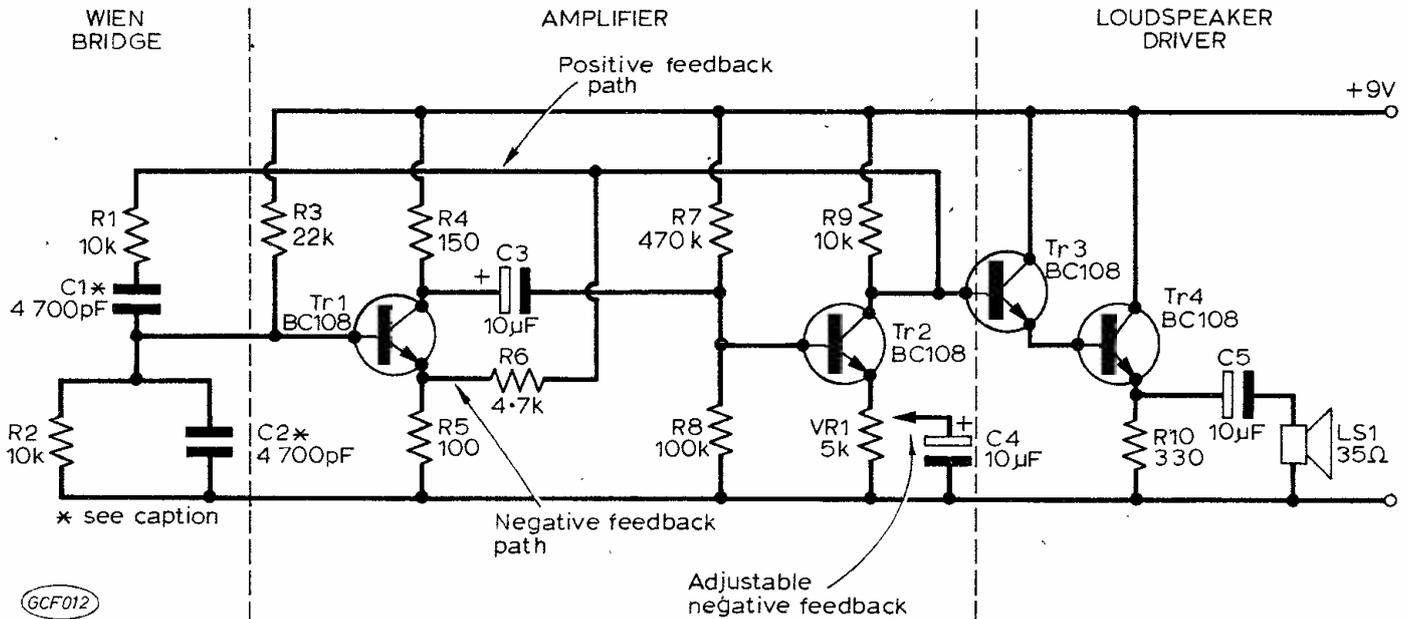

GCF012

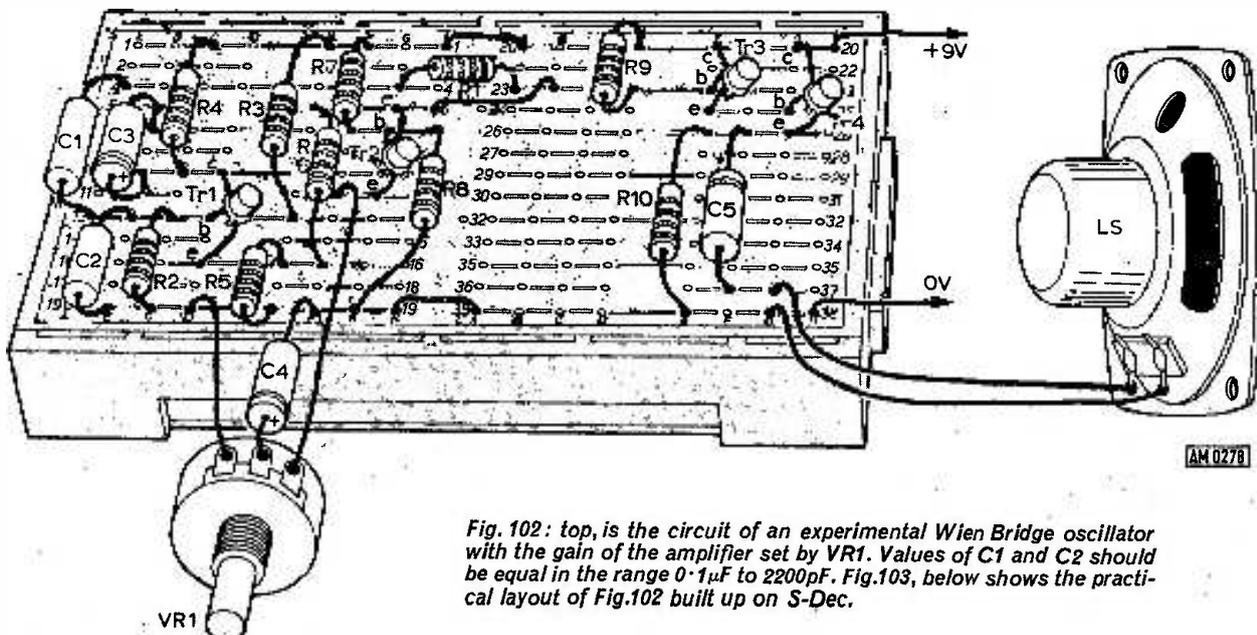


Fig. 102: top, is the circuit of an experimental Wien Bridge oscillator with the gain of the amplifier set by VR1. Values of C1 and C2 should be equal in the range $0.1\mu\text{F}$ to $2200\mu\text{F}$. Fig.103, below shows the practical layout of Fig.102 built up on S-Dec.

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prr. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 8	7.0 x 6.0 x 6.0	2.55 38
149	60	3 12	9.9 x 7.7 x 8.6	3.98 45
150	100	5 8	9.9 x 8.9 x 8.6	4.45 45
151	200	8 0	12.1 x 9.3 x 10.2	7.39 53
152	250	13 12	12.1 x 11.8 x 10.2	8.93 73
153	350	15 0	14.0 x 10.8 x 11.8	10.80 73
154	500	19 8	14.0 x 13.4 x 11.8	12.41 91
155	750	29 0	17.2 x 14.0 x 14.0	18.65 *
156	1000	38 0	17.2 x 16.6 x 14.0	26.50 *
157	1500	46 0	21.6 x 13.4 x 18.1	30.23 *
158	2000	60 0	21.6 x 15.3 x 18.1	33.70 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.52 30
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.64 38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	3.75 45
66	300	6 4	9.9 x 9.6 x 8.6	"	5.29 53
67	500	12 8	12.1 x 11.2 x 10.2	"	8.02 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	12.44 91
93	1500	30 4	14.0 x 15.9 x 14.3	"	16.65 *
95	2000	42 0	17.2 x 16.6 x 14.0	"	22.00 *
73	3000	60 0	21.6 x 13.4 x 18.1	"	31.90 *

CASED AUTO TRANSFORMERS
115V mains lead input and U.S.A. 2-pin outlets. 20VA £2.85 pp 38p
500VA £9.50 pp 80p 1000VA £15.92 via B.R.S.

TRANSFORMERS

PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	Amps. 12V 24V	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5 0.25	8	4.8 x 2.9 x 3.5	0-12V at 0.25A x2	1.34 23
213	1.0 0.5	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x2	1.58 30
71	2 1	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x2	2.09 38
18	4 2	2 12	8.3 x 7.7 x 7.0	0-12V at 2A x2	2.60 38
70	6 3	3 8	8.9 x 8.0 x 7.7	0-12V at 3A x2	3.75 45
108	8 4	5 8	9.9 x 8.9 x 8.6	0-12V at 4A x2	4.15 45
72	10 5	6 4	9.9 x 9.6 x 8.6	0-12V at 5A x2	4.67 53
116	12 6	6 12	9.9 x 10.2 x 8.6	0-12V at 5A x2	5.02 53
17	16 8	8 12	12.1 x 9.9 x 10.2	0-12V at 8A x2	6.62 60
115	20 10	11 8	14.0 x 9.6 x 11.8	0-12V at 10A x2	9.45 73
187	30 15	15 8	14.0 x 12.1 x 11.8	0-12V at 15A x2	12.29 85
226	60 30	32 0	17.2 x 15.3 x 14.0	0-12V at 30A x2	15.30 *

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.65 30
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.18 38
3	2.0	3 4	8.9 x 7.7 x 7.7	"	3.18 38
20	3.0	4 8	9.9 x 8.3 x 8.6	"	4.12 45
21	4.0	6 4	9.9 x 9.6 x 8.6	"	4.67 53
51	5.0	6 12	12.1 x 8.6 x 10.2	"	5.83 53
117	6.0	8 0	12.1 x 9.3 x 10.2	"	6.51 60
88	8.0	12 0	12.1 x 11.8 x 10.2	"	9.00 67
89	10.0	13 12	14.0 x 10.2 x 11.8	"	8.97 73

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.35 30
103	1.0	2 12	8.3 x 7.4 x 7.0	"	3.08 38
104	2.0	5 8	9.9 x 8.9 x 8.6	"	4.26 45
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.28 53
106	4.0	10 0	12.1 x 10.5 x 10.2	"	6.91 67
107	6.0	12 0	14.0 x 10.2 x 11.8	"	11.00 67
118	8.0	18 0	14.0 x 12.7 x 11.8	"	11.80 85
119	10.0	25 0	17.2 x 12.7 x 14.0	"	15.45 *

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.12 38
126	1.0	3 4	8.9 x 7.7 x 7.7	"	3.10 38
127	2.0	6 4	9.9 x 9.6 x 8.6	"	4.62 45
125	3.0	8 12	12.1 x 9.9 x 10.2	"	6.84 60
123	4.0	13 12	12.1 x 11.8 x 10.2	"	7.96 67
40	5.0	12 00	14.0 x 10.2 x 11.8	"	8.87 73
120	6.0	15 8	14.0 x 12.1 x 11.8	"	10.27 85
121	8.0	25 00	14.0 x 14.7 x 11.8	"	13.64 *
122	10.0	25 0	17.2 x 12.7 x 14.0	"	15.93 *
189	12.0	29 00	17.2 x 14.0 x 14.0	"	18.16 *


MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA.	Weight lb oz	Size cm.	VOLTS	P & P £ p
238	200	2	2.8x2.6x2.0	3-0-3	1.40 10
212	1A 1A	1 4	6.1x5.8x4.8	0-6-0-6	1.67 30
13	100	4	3.9x2.6x2.9	9-0-9	1.28 13
235	330,330	4	4.8x2.9x3.5	0.9-0-9	1.42 19
207	500, 500	1 00	6.1x5.4x4.8	0-8.9-0-8.9	1.75 30
208	1A, 1A	1 12	7.0x6.4x6.1	0-8.9-0-8.9	3.00 38
236	200, 200	4	4.8x2.9x3.5	0-15-0-15	1.30 19
214	300, 300	1 4	6.1x5.8x4.8	0-20-0-20	1.76 30
221	700 (D.C.)	1 8	7.0x6.1x6.1	20-12-0-12-20	1.98 38
206	1A, 1A	2 12	8.3x7.7x7.0	0-15-20, 0-15-20	3.15 38
203	500, 500	2 4	8.3x7.0x7.0	0-15-27, 0-15-27	2.73 38
204	1A, 1A	3 4	8.9x7.7x7.7	0-15-27, 0-15-27	3.50 38

* Carriage via BRS

PLEASE ADD 8% FOR V.A.T. INCLUDING P. & P.

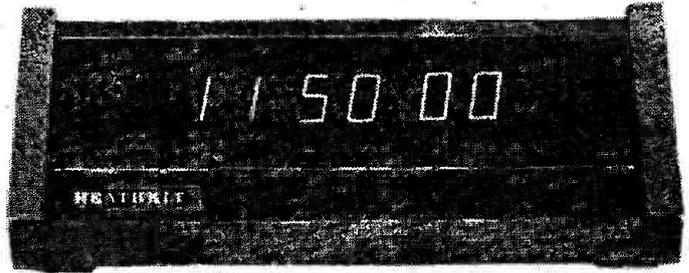With a kit as complete as this, all you need add is a little time.



You may have found, from past experience, that your definition of 'complete' is not quite the same as other people's. And your so called complete kit comes minus a cabinet, or knobs, or a multitude of other bits and pieces.



That won't happen with a Heathkit.

Take our very popular digital alarm clock kit. Every part you need will be there, right down to the solder. And you'll also receive a very easy to understand instruction manual that makes light work of assembly.



In fact all you need are a few basic tools and a few enjoyable hours of your time.

After which you may like to try your hand at

our AR-1214 stereo receiver. Or even a TV. And how about an ultrasonic burglar alarm disguised as a book?


Or, for a bookful of other ideas, just clip the coupon and we'll send you the Heathkit catalogue.

Otherwise call in and see us at the London Heathkit Centre, 233 Tottenham Court Road.

Or at our showroom in Bristol Road, Gloucester.

You'll find it well worth your time.

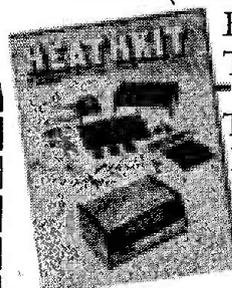Heath (Gloucester) Limited, Dept. PW-15, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.



To: Heath (Gloucester) Limited, Dept. PW-15, Gloucester, GL2 6EE. My free Heathkit catalogue, please.

Name _____
Address _____

Postcode _____

Remember easy terms are available with the Heathkit Monthly Budget Plan.



BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/3

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

ELECTROVALUE

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

Present

top quality electronic components for price-minded buyers

112 p. CATALOGUE · FREE POSTAGE (U.K.) · ATTRACTIVE DISCOUNTS · SPECS. GUARANTEED

A 100 OF THE BEST

From our transistor stock

2N1307	47p	BC149C	14p
2N2646	51p	BC158B	15p
2N3053	26p	BC159	15p
2N3054	60p	BC167B	13p
2N3055	70p	BC168B	12p
2N3702	11p	BC169B	12p
2N3703	10p	BC169C	13p
2N3704	11p	BC179B	26p
2N3705	10p	BC182L	26p
2N3794	18p	BC184L	26p
2N3819	25p	BC212L	12p
2N4082	11p	BC214L	14p
2N4443	93p	BC257A	14p
2N5062	42p	BC259B	14p
2N5163	20p	BCY58	30p
2N5459	32p	BD130	90p
40361	48p	BD131	48p
40382	44p	BD132	48p
40602	46p	BD135	52p
40636	£1.36	BD136	37p
40689	£1.10	BDY20	39p
AC128	17p	BF194	83p
AC151R	23p	BFR39	15p
AC153	27p	BFR79	23p
AC153K	27p	BFX29	33p
AC176	24p	BFX84	27p
AC176K	38p	BFY51	23p
AC187K	31p	BRY39	45p
AC189K	29p	BY164	51p
AD133	£1.32	C108B1	42p
AD136	£1.41	C108D1	62p
AD149	65p	C1406	78p
AD161	42p	MJ481	£1.20
AD162	40p	MJ491	£1.35
AF200U	40p	MJ2955	80p
A F29	60p	MJE571	81p
E106	36p	MJE581	81p
BA138	31p	MJE2955	£1.12
BB103	24p	MJE3055	62p
BB105	34p	OA91	6p
BB109	48p	SD4	8p
BC107A	15p	TIP31A	70p
BC107B	15p	TIP32A	80p
BC108	14p	TIP41A	80p
BC108C	14p	TIP42A	£1.00
BC109B	18p	W02	30p
BC109C	18p	ZTX300	14p
BC147A	12p	ZTX304	23p
BC147B	13p	ZTX500	14p
BC148B	12p	ZTX504	45p

100s MORE IN CATALOGUE 7

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 13in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90.

The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2.30.

Loudspeaker Unit 59RM109, £2.45. Cabinet Kit (to Baxandall design), £10.45. Cross-over choke for additional woofer to above, £1.50.

DISCOUNTS

Available on all items except those shown with NETT PRICES 10% on orders from £5 to £14.99, 15% on orders £15 and over.

FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders - carriage charged at cost. Giro A/C No. 38/671/4002

RESISTORS

Code	Watts	Ohms	1 to 9	19 to 99	100 up
(see note below)					
C	1/3	4.7-470K	1.3	1.1	0.9 nett
C	1/2	4.7-10M	1.3	1.1	0.9 nett
C	3/4	4.7-10M	1.5	1.2	0.97 nett
C	1	4.7-10M	3.2	2.5	1.92 nett
MO	1/2	10-1M	4	3.3	2.3 nett
WW	1	0.22-3.9Ω	11	10	8 nett
WW	3	1-10K	9	8	6 nett
WW	7	1-10K	11	10	8 nett

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide, Electrofil TR5 ultra low noise.
WW = wire wound, Plessey.

Values: All E12 except C 1/3W, C 1/2W and MO 1/2W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% ± 0.05Ω below 10Ω and 1/2W MO 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only

POTENTIOMETERS

ROTARY, CARBON TRACK.

Double wipers for good contact and long working life

P.20 SINGLE linear 100 ohms to 4.7 megohms, each 14p

P.20 SINGLE log. 4.7 Kohms to 2.2 megohms, each 14p

JP.20 DUAL GANG 1in. 4.7 Kohms to 2.2 megohms, each 48p

JP.20 DUAL GANG log, 4.7 Kohms to 2.2 megohms, each 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only, each 48p

JP.20 DUAL GANG antilog 10K only 48p

2A DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets, Type PR, horizontal or vertical 6p each.

SLIDER

Linear or log mono 4.7K to 1 meg. In all popular values each 30p

STEREO, matched tracks, lin. or log in all popular values from 4.7K to 1 meg. 60p

Escutcheon plates, mono, black, white or light grey, each 10p

Control knobs, blk/wht/red/yel/grn/blue/dk. grey/lt. grey, each 7p

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6.3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	11p	11p	8p
1.0	—	—	—	—	11p	—	8p	8p
2.2	—	—	—	—	—	8p	8p	8p
4.7	—	—	—	11p	—	8p	8p	8p
10	—	—	—	—	8p	8p	8p	10p
22	—	—	8p	—	8p	8p	10p	13p
47	8p	—	8p	8p	8p	10p	12p	19p
100	9p	8p	8p	8p	10p	11p	17p	28p
220	8p	8p	8p	10p	10p	11p	17p	24p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	10p	17p	20p	25p	41p	—
2,200	15p	18p	13p	23p	26p	37p	—	—
4,700	26p	30p	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point: 9mm characters in 16 lead DIL £1.20
Suitable BCD decoder driver 7447 £1.15
3015G showing + or - & 1 & dec. pt. £1.20

LEDs (Light Emitting Diodes)

Photo Cells Cadmium Sulphide, each 25p

ANTEX Soldering Irons

CN240 £2.15 Spare bits 32p
CCN240 £2.76 Spare bits 40p

DESOLDER BRAID

6 ft strip 66p

WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 6 way
3 pole 4 way; 4 pole 3 way each 29p
TAG STRIP 28 way 11p

NUTS, SCREWS, etc.

In lots of 100 each
4BA NUTS 28p; 6BA NUTS 28p
1/4" 4B Screws 28p; 1/4" 6BA Screws 24p
Threaded pillars 6BA, 1/2" hexagonal £2.10

Plain spacers 1/2" round £1.40

Other sizes available

ENAMEL COPPER

WIRE IN 2 ounce reels

16, 18, 20, 22 SWG 34p
24, 26, 28, 30 SWG 40p
32, 34 46p; 36, 38, 40 54p

DIN CONNECTORS

1 way loudspeaker	10p	Socket	12p
3 way audio	10p	Plug	12p
5 way audio 180	12p		15p
5 way audio 240	12p		15p
6 way audio	13p		15p

EV CATALOGUE 7

2nd printing—Green and yellow Cover

112 pages, thousands of items; illustrations; diagrams; much useful technical information. The 2nd printing has been updated as much as possible on prices. It costs only 25p post free including refund voucher for 25p for spending when ordering goods list value £5 or more.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale. Prices quoted do not include V.A.T. for which 8% must be added to total net value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.

ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PW.12. S.A.E. with enquiries requiring answers.

EXPERIMENTAL WORKSHOP—contd. from page 840

If we insert our Wien Bridge network in this feedback loop the bridge will alter the phase relationship of all frequencies *except* for the resonant frequency of the bridge in question; thus we would only obtain positive feedback at the resonant frequency.

The feedback signal is attenuated to one third of the output level, as we have just explained hence to obtain oscillation the gain of the two stage amplifier should be three. Although there is no problem in obtaining a low gain like this there are problems in maintaining its stability particularly as we are forced into using two stages to get the necessary phase response. Consequently our experimental circuit shown in Fig. 102 looks a little complex as we have built in two stages of *negative feedback* to fix and adjust the gain at this low level.

R6 in conjunction with R5 provide one negative feedback path which is fixed and VR1 allows a variable degree of feedback for experimental purposes. In practical production circuits a thermistor might be used instead of R6 to control the overall gain automatically.

If the gain diverges considerably from the desired value two things can happen. If it is too low the circuit will not oscillate, and if too high the output waveform at the collector of Tr2 might suffer from clipping. You should be able to experience this effect with the following experiment.

Make up the circuit of Fig. 102 complete with loudspeaker driver stage. Set the wiper of VR1 to the bottom end of its track. Depending on the components you have used the chances are that the circuit will not oscillate because we have excessive negative feedback around Tr2.

Increase the gain of the amplifier by reducing this negative feedback (advance the wiper of VR1) and the circuit should oscillate nicely. If you increase the gain too much you should hear the onset of clipping by a sudden change in tone of the signal from the loudspeaker.

You will find that there is a certain degree of sluggishness in getting oscillations started and they might build up in amplitude over a second or two which is caused by the high degree of negative feedback.

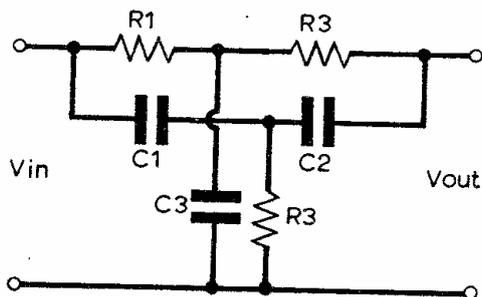


Fig. 104: Basic circuit of a 'Twin-T' or 'Bridged-T' filter. Normally the circuit is symmetrical with $R1=R2$ and $C1=C2$. $R3$ should equal $\frac{1}{2}R1$ and $C3$ should be $2 \times C1$.

A big advantage of this type of oscillator (compared with the phase shift type described last month) is that you only need change the values of two components in the frequency determining network (the bridge) to alter frequency and the range of adjustment is very large. In theory one can change the values of $C1$ and $C2$ or $R1$ and $R2$. However, in our experimental circuit you are limited to playing with different values for the capacitors only because $R2$ forms part of the potential divider biasing for Tr3

and changing its value would modify the gain levels of the amplifier. Nevertheless try substituting different pairs of values for $C1$ and $C2$ in the range $2,200\text{pF}$ to $0.1\mu\text{F}$.

This circuit is widely used by audio oscillator manufacturers for test instruments; for what it does it is a very simple circuit and is often used in amateur projects.

Whereas the Wein Bridge is a pass filter at resonance the **Bridge-T filter**, shown in Fig. 104 gives a high degree of attenuation at its resonant frequency. The onset of resonance is very sharp and this circuit is often used as a *notch* filter when a particular frequency needs to be removed from a series without significant influence on the amplitudes of neighbouring frequencies.

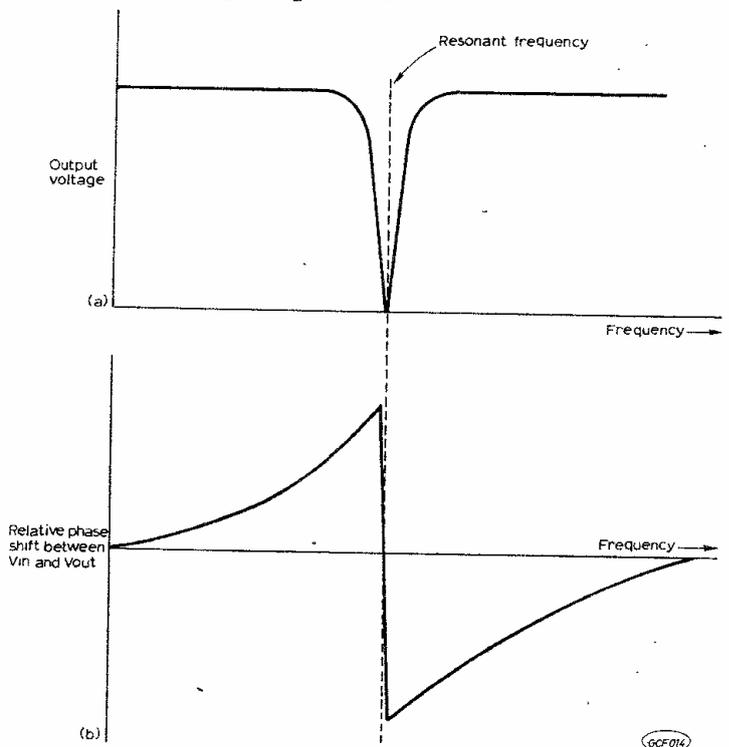


Fig. 105: top, output voltage at different frequencies for a fixed amplitude input signal. Below, at the resonant frequency 180° phase shift occurs.

The relationship between the component values is slightly more complex than the previous filter and although there is an unlimited variety of values one can use the Bridged-T is usually represented in its symmetrical form. This means that $R1$ should equal $R2$ and $R3$ should be half the value of $R1$. At the same time $C1$ should equal $C2$ and $C3$ should be twice the value of $C1$. Provided this relationship is maintained the resonant frequency is given by

$$f = \frac{1}{2\pi \times C_1 \times R_1}$$

where C_1 is in farads, R_1 in ohms and f in hertz.

The *phase* response of the filter is somewhat more complex. At the resonant frequency there is a sudden 180° phase shift between input and output. Depending on which side of the resonance frequency one looks one can say that the output is 180° out of phase with the input or it is in phase with the input. However, at the resonant frequency the theoretical output from the filter is zero, Fig. 105.

We can use this filter in the *negative* feedback loop of an amplifier (Tr1 of Fig. 106). Because of the rather strange phase response we shall get negative

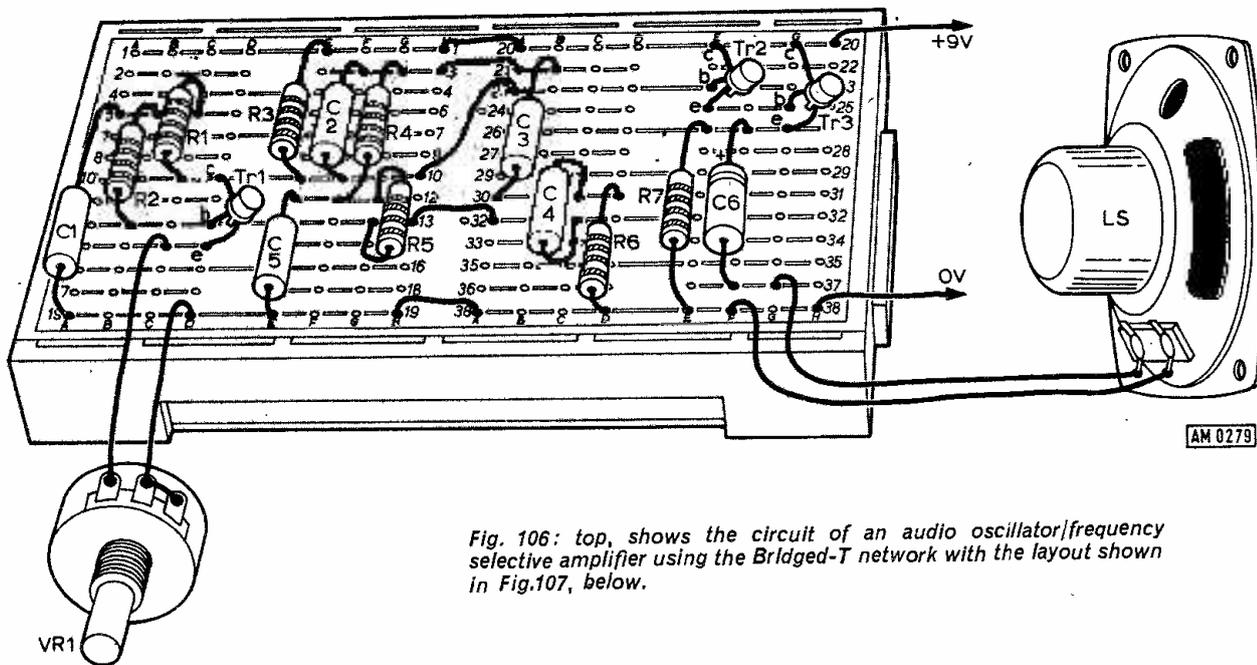
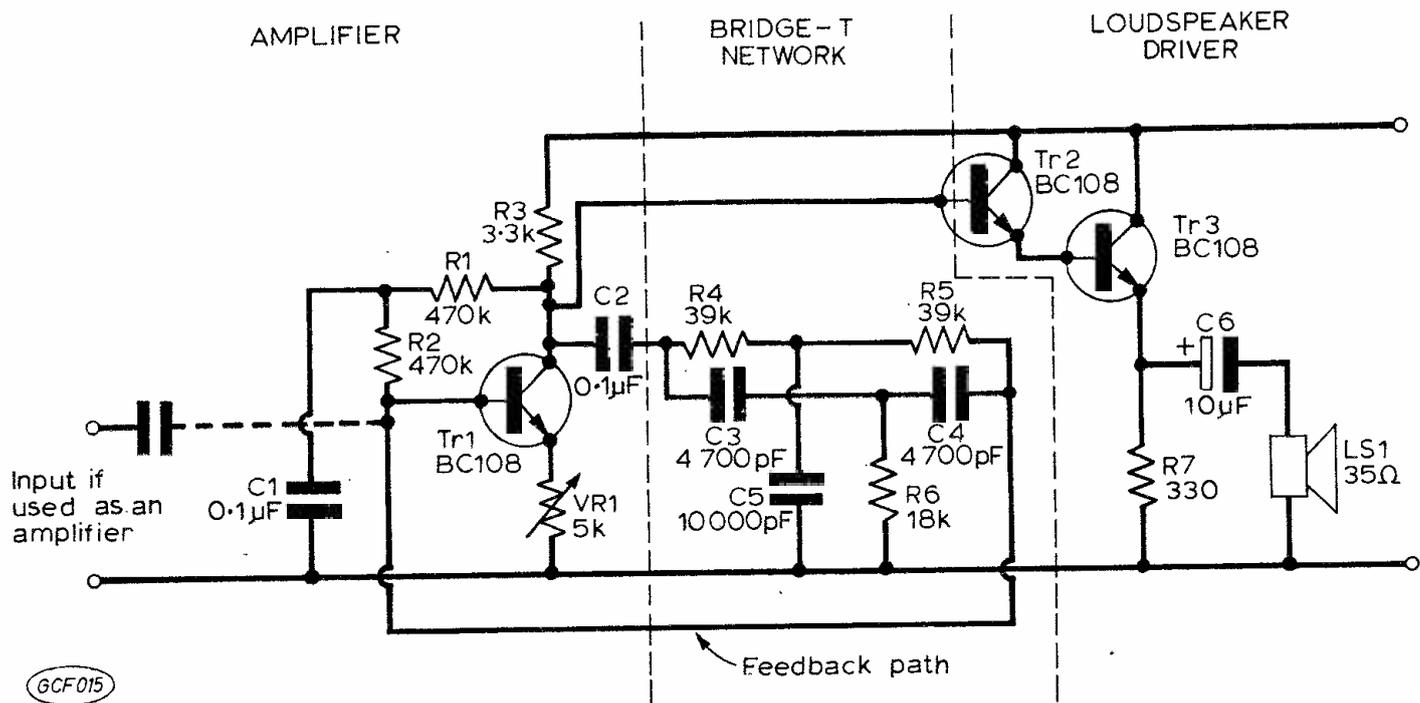


Fig. 106: top, shows the circuit of an audio oscillator/frequency selective amplifier using the Bridged-T network with the layout shown in Fig.107, below.

feedback on one side of resonance and positive feedback on the other side. By careful adjustment of the amplifier's gain we can get the circuit to oscillate at a frequency just slightly one side of resonance, by reducing the gain a little we have a complex balance between negative feedback on the one hand and positive feedback on the other. Thus it is possible to make a frequency selective amplifier that has a maximum gain (because of the zero negative feedback signal at resonance) at the resonant "notch".

This is very useful in many special applications and is frequently used by amateurs to make Waa-Waa effects with guitars and organs particularly if it is possible to sweep the resonant frequency by adjusting one of the components in the feedback circuit (usually R6).

You can experiment with the circuit as an oscillator or a frequency selective amplifier by suitable adjustment of VR1. Notice (as for the Wien Bridge)

that reducing VR1 too much (increasing gain) causes *clipping* and, in this case shifts the frequency further away from the notch.

As an amplifier connect the output of a crystal cartridge (through an attenuator if necessary) to the base of Tr1 through a 0.1µF capacitor and substitute a variable 50Ω potentiometer for R6.

By advancing the gain of the amplifier to just below the oscillating point you can deliberately make a *ringing amplifier*; i.e. a circuit that will respond to a pulse input and give a decaying train of sinewaves out. This effect is commonly used to produce electronic percussion effects to simulate drums or bells. You can stimulate such a ring by momentarily shorting the junction of R1 and R2 to the +9V rail. Altering the values of R4, R5, R6, C3, C4 and C5 will produce different sound effects.

Next month: Radio frequency oscillators.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O.

only **99p** P & P 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

only **25p** POST & PACKING 11p

Tested and Guaranteed Paks



- B79 4 IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic 50p
- B81 10 Reed Switches, 1" long, 1/4" dia. High Speed P.O. type 50p
- H35 100 Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked. 50p
- H38 30 Short lead Transistors, NPN Silicon Planar types 50p
- H39 6 Integrated Circuits. 4 Gates BMC 982, 2 Flip-Flops BMC 945 50p
- H41 2 Sil Power transistors comp pair BD131/132 50p
- H63 4 2N3055 type NPN Sil. power transistors. Below spec. devices 50p
- H64 4 3B19 N Channel FETs 2N3819 in plastic case 50p



Unmarked Untested Paks

- B1 50 Germanium Transistors PNP, AF and RF 50p
- B66 150 Germanium Diodes Min. glass type 50p
- B83 200 Transistors, manufacturers rejects, AF, RF, Sil. and Germs. 50p
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202 50p
- B86 100 Sil. Diodes sub. min. IN914 and IN916 types 50p
- H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can. 50p
- H67 10 3B19N Channel FETs plastic case type 50p

Lenco cassette tape recorder mechanisms

Type FFR for the P.W. Kempton car stereo cassette player

£21.50 30p p&p

Electronic Transistor Ignition £6.00

Complete kit p. & p. 11p

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

Extension Telephones

Ideal for childrens toys **70p** each P. & P. 25p.

New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available

Will align the colour guns on a colour T.V. receiver

Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3" x 5 1/2" x 3".

Ready built unit only **£9.95** Complete kit **£7.95**

(includes p. & p. but no batteries)



LM380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL60745.

This fantastic little 3watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00** ea complete with data and projects book

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can
TYPE "B" PNP Silicon, plastic encapsulation
TYPE "E" PNP Germanium AF or RF
TYPE "F" NPN Silicon plastic encapsulation
TYPE "G" NPN silicon similar ZTX 300 range

8 RELAYS FOR various types p & p 27p **£1.00p**

UHF TV Tuner Units

Brand new by a famous manufacturer

Data supplied **£2.50**

Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.		1-12 13-25 26-50	
40 Watt	20p	18p	16p
90 Watt	24p	22p	20p
Range 2. VCE. Min. 40. HFE Min 40		1-12 13-25 26-50	
40 Watt	30p	28p	26p
90 Watt	35p	33p	30p

Please state NPN or PNP on order.

HIGH SPEED MAGNETIC COUNTERS

4 Digit (non-reset) 4 x 1 x 1 in ex G.P.O. 30p

INTEGRATED CIRCUITS

We stock a large range of I.Cs at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 12p Wall Chart 18p

LOW COST DUEL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile 16 pin type at 17p each / type

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me the FREE Bi-Pre-Pak Catalogue I enclose large SAE with 5p stamp

NAME
ADDRESS

Please add VAT at current rate
MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 15p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
TELEPHONE: SOUTHEND (0702) 46344.

DISCOUNTS UP TO 60%

FANTASTIC OFFER



GARRARD SP25 MkIV
Plinth & Cover
Garrard SP25 MkIV deck, Goldring
G800 Cartridge, Teak finished Plinth/
Cover (Non Hinged) All Leads.
GLOBAL'S PRICE £19.80
Carr. & Ins. £1.93

TURNTABLES

Please add £1.05 for p & p & Ins.
Garrard SP25 Mk IV Chassis £12.95
Garrard 86SB P/C Cart (Mod.) £47.50
Garrard 86SB Chassis £22.49
Garrard 401 Chassis £22.99
Goldring 101 Mk II P/C G800 £29.95
Goldring GL78 P/C G800 £29.95
Goldring GL78 P/C G800 £44.40
Goldring PL85 P/C £56.95
Pioneer PL 12D P.O.A.
Sansul SR 212 P.O.A.
Thorens TD125 MkII £72.25
Thorens TD125AB Mk II £111.95
Thorens TD160 ABC £59.95
Thorens TD165 ABC £52.95

Transcriptor Saturn With Vestigial Arm .. £63.95

AMPLIFIERS

Please add £1.05 for p & p & Ins.
Amstrad Integra 4000 Mk II .. £25.75
Amstrad IC2000 MkII .. £31.95
Amstrad 8000 MkIII .. £18.50
Eagle AA2 .. £31.98
Eagle AA4 .. £43.18
Eagle AA4 .. £26.15
Metro-Sound ST20E MkII .. £26.15
Metro-Sound ST40 .. £33.25
Metro-Sound ST60 .. £46.75
Sansul AU101 .. P.O.A.
Sinclair 2000 .. £29.95
Sinclair 4000 .. £44.95
Sinclair 4000 .. £30.50
Teleton GA202 .. £23.95
Teleton SAQ208B .. £22.95
Teleton SAQ307D .. £27.20

COMBINATION UNITS

Please add £1.10 for p & p & Ins.
Goodmans Compact 80 (Teak) £131.15
Goodmans Compact 90 .. £169.99
Goodmans Compact 1-10 (Teak) .. £191.00

TUNERS

Please add £1.05 for p & p & Ins.
Amstrad MLX 3000 .. £26.25
Eagle AA8 .. £45.95
Eagle TST 152 .. £32.95
Metro-Sound FMS 20 Mk II .. £33.35
Teleton T300 .. P.O.A.

Teleton ST202 .. £36.00
Sinclair 2000 Mk III .. £29.95
Sinclair 4000 .. £37.45

TUNER/AMPLIFIERS

Please add £1.21 for p & p & Ins.
Amstrad 5000 .. £56.95
Goodmans Module 90 .. £92.99
Goodmans 1-10 Module .. £108.50
Goodmans 120 .. £113.95

SPEAKERS


Add £1.82 for p & p & Ins per Pair.
Amstrad 1500 .. £25.65
Amstrad 2500 .. £29.95
Amstrad 2500 .. £45.25
Celestion County .. £42.65
Celestion Ditton 10 MkII .. £65.50
Celestion Ditton 15 .. £129.95
Celestion Ditton 25 .. £108.45
Celestion Ditton 44 .. £198.95
Celestion Ditton 66 .. £39.25
Celestion Hadleigh .. £127.95
Goodmans Dimension 8 .. £44.50
Goodmans Havant SL .. £107.75
Goodmans Magisters .. £24.85
Goodmans Magnum K2 SL .. £38.00
Goodmans Minister .. £37.35
Goodmans Mezo 3SL .. £31.95
Marsden Hall 110P/C .. £36.25
Marsden Hall 150P/C .. £44.95
Marsden Hall 200P/C .. £37.50
Marsden Hall 300P/C .. £32.25
Wharfedale Denton 2 .. £35.25
Wharfedale Dovedale .. £59.25

CARTRIDGES

Please add 12p for p & p & Ins.
Goldring G800H .. £3.87
Goldring G800E .. £6.20
Goldring G800 .. £3.49
Shure V15 Type 3 .. £28.40
Shure M75EJ Type 2 .. £7.99

Shure M75ED Type 2 .. £9.10
Shure 91ED .. £8.29
Shure M3D .. £3.10
Sonotone 9 TACHD .. £1.30

FABULOUS OFFER

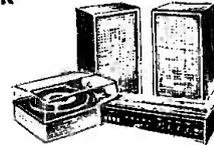

AMSTRAD IC2000 MkII STEREO SYSTEM
Amstrad IC2000 MkII with increased power 25+25 watts amplifier. Complete with a pair of Amstrad Acoustara 2500 speakers, Garrard SP25 MkIV deck, G800 Cart, Plinth/Cover (Non Hinged) all leads.
GLOBAL'S PRICE £80.75
Carr. & Ins. £3.30

STEREO HEADPHONES

Please add 42p for p & p & Ins.
Koss ESP 6 .. £47.85
Koss ESP 9 .. £44.15
Koss K7/11 Red Devil .. £6.99
Koss K6 .. £11.70
Koss K6/LC .. £12.25
Koss KD727E .. £14.90
Koss 747 .. £18.35
Koss HV1/A N/P .. £29.95
Koss HV1/LC/A N/P .. £24.99
Koss PRO 5/LC .. £27.15
Koss K7/11 Black .. £8.99
Sennheiser HD414 .. £18.75
Sennheiser HD 424 .. £15.35

GLOBAL AUDIO

Please Note Every effort is made to ensure prices listed are correct at time of going to press, but are subject to alteration without prior notice. (E&OE)

FULL 12 MONTH AFTER SALES SERVICE

We give a **FULL 12 MONTH GUARANTEE** on all products purchased at any branch parts and labour absolutely **FREE**

BIRMINGHAM

Tivoli Shopping Centre, 1536 Coventry Road, Yardley
Tel: 021-706 9949

ESSEX

4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford.
Tel: 01-550 1086

LONDON

328 Edgware Road, W2.
Tel: 01-262 3847

246 Pentonville Road, N1.
Tel: 01-837 3535
120 Notting Hill Gate, W11
Tel: 01-229 1437
50 Stamford Hill, N16.
Tel: 01-806 4699

PORTSMOUTH

12 London Road, North End
Tel: 0705 68321

READING

46 Market Place.
Tel: 0734 595331

WATFORD

105 St Albans Rd. Tel: 39832

H.P. FACILITIES AVAILABLE FOR PERSONAL CALLERS ONLY

MAIL ORDERS
TO: 174 PENTONVILLE ROAD, LONDON, N1.
Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Reg. Mail.

NO HIDDEN PRICES AT GLOBAL AUDIO - ALL OUR PRICES ARE SHOWN WITH VAT INCLUDED

PERSONAL CALLERS VERY WELCOME!
COMPARE OUR PRICES WITH ANY IN THE BOOK!
OPEN MONDAY TO SATURDAY 9.30 am - 5 pm
LATE NIGHT FRIDAY OPEN UNTIL 7 pm.

PLEASE NOTE All Cheques, Money Orders, Postal Orders, Bank Draft, or Giro to be made payable to **MAUTOHEAD LTD.**

SPARKRITE Mk II

Electronic Ignition... Better on all points

Because you keep your points!


The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly - with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of norm, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Instant all weather starting. ● Cleaner plugs - they last 5 times longer without attention. ● Faster acceleration. ● Faster top speeds. ● Coil and battery last longer. ● Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

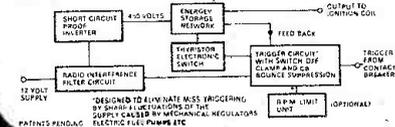WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!



Sparkrite MK II - full capacitive discharge electronic system - not just a transistorised inductive discharge booster.

PRICES

D.I.Y. Kit only £10.93 incl. VAT and P & P
Ready Built Unit £13.86 incl. VAT and P & P
(Both to fit all cars with coil/distributor ignition up to 8 cylinders).

We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition. Details on request. Call in and see us for a demonstration.

ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES
(Dept PW 11) 82 Bath Street, Walsall WS1 3DE Phone 33652

Please supply Sparkrite Mk 2 D.I.Y. Kit(s) at £10.93 each incl. VAT and P & P (Will make pos. or neg. earth).

Sparkrite Ready Built Neg. Earth Unit(s) at £13.86 each incl. VAT and P & P


Sparkrite Ready Built Positive Earth Unit(s) at £13.86 each incl. VAT and P & P

NAME _____

ADDRESS _____

I enclose cheque/P.O. for £ _____
Send SAE for brochure.

GOING BACK...

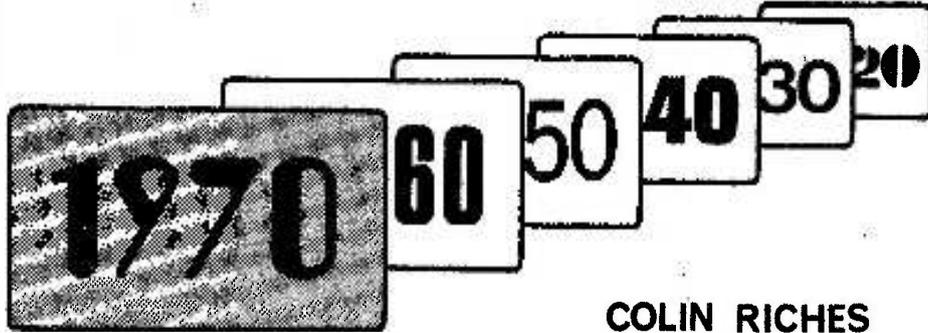

COLIN RICHES

MR. A. Midgley from Northwood Middlesex has been kind enough to let me have some information on an Ediswan "One-Der" receiver his father once owned.

This set employed an ES 220 valve which was described as the "outcome of prolonged research and experiment". In 1925 it cost 22s. 6d.

Hints for obtaining maximum efficiency from the "One-Der" were as follows:

The "ONE-DER" Receiver, owing to the system of amplification employed, is capable of giving the purest reception at present obtainable, and in order

that this may not be marred by any faults, in or about the installation, the following hints are given:—

AERIAL.—Upon the efficiency of the aerial and earth system depends the amount of energy collected and supplied to the set, and every effort should be made to see that the aerial is as good as it is possible to obtain under the circumstances.

The aerial should be as large and as high as possible, and the lead-in wire from the aerial to the point of entry into the house should be clear of walls or buildings. If it must run parallel or side by side with a wall or any other obstruction, it should be kept at least two feet away, this may be achieved by propping it out. Good insulation of the aerial is absolutely essential, and where bare wire is employed the porcelain or other insulators used for its suspension should be periodically cleaned, particularly in large towns where smoke is prevalent. The aerial wire itself should be of the stranded variety known as 7/22, and each strand should be insulated from the other by a coating of enamel. This type of wire can be obtained at most dealers. This insulation, however, is not good enough to render the use of porcelain insulators unnecessary. This wire is usually sold in lengths of 100 feet, and where possible, erection should commence at the free end and the wire should be brought right to the AERIAL terminal on the set without being broken, so as to avoid making a joint.

EARTH.—Too much attention cannot be paid to the earth connection. The lead from the Receiver to earth should be as short as possible, and the cable should be at least as heavy as that employed for the aerial, or preferably heavier.




The Ediswan "One-Der" speaker (£2.10s in 1925).


There is nothing better than what is known as cab tyre, which is insulated with a thick external sheath of rubber.

In most cases we expect that the connection will be made to the water system, and this is quite good provided connection can be made to a "rising main." On no account should connection be made to the hot water system as the joints which are inevitable in all such systems are usually packed with non-conducting material, and the fact that such pipes are usually made of iron, makes this method most unsatisfactory. Always endeavour to connect to a lead pipe. First scrape the lead perfectly clean and screw on the clean place some clip arrangement, many satisfactory types of which are obtainable at wireless dealers, and when this is clipped in position, it is a good plan to cover the joint made with tallow or Vaseline as this to some extent, will prevent the oxidation of the newly-cleaned lead and will ensure a good electrical joint.

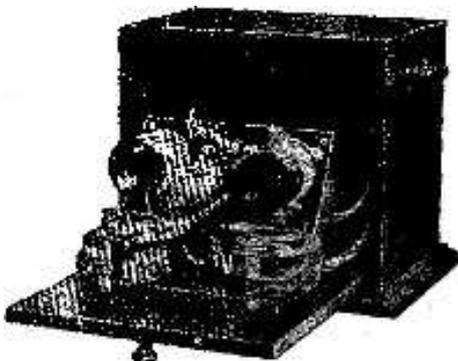LOW TENSION ACCUMULATOR—The L.T. accumulator which is the source from which the current for heating the filament is drawn, as a rule gives very little trouble beyond the need for re-charging when it is run down. It does, however, require careful charging, and the owner is advised to take the accumulator for re-charging to a reliable electrician who will



Interior view of the "One-Der."

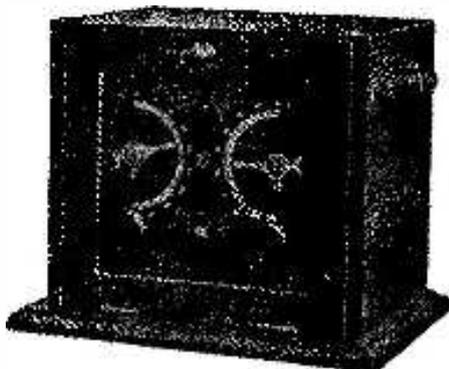

Front panel of the receiver.

not overcharge it and so shorten its life. Accumulators which have glass for their outer container are always to be preferred before those in celluloid containers. The terminals of the accumulator should be kept clean and occasionally covered with Vaseline, and any connection made to the terminals of the accumulator should be screwed down tightly.

HIGH TENSION SUPPLY—The high-tension supply to most wireless sets is probably obtained from dry batteries, and it is essential that these should be of reliable make, otherwise the discharge may be somewhat intermittent, or noisy. Batteries of inferior manufacture often give rise to noises not unlike atmospherics, and for this reason high-tension batteries bearing a reputable name should always be purchased. As the "ONE-DER" Valve requires only a very small anode current, even when working a loudspeaker at full strength (it takes only 1-1½ milliamperes, which is probably less than any other valve available), a very small high-tension battery therefore is all that is needed, but it must consist of sufficient units to give 120 volts.

GRID BIAS.—It will be noted that the high-tension batteries

used include tapplings for Grid Bias at the negative (−) end, so that if this type of battery is used there is no need to employ a separate Grid Bias battery.

Place valve in holder, the two legs which are close together being put to the sockets which are similarly spaced. The others will be found to fit.

The coils are placed so that the one having the most winding and which has four inside tapplings is put on the left-hand side, while the one with the lesser winding and only two connections is placed on the right-hand side. Both coils have four pins, but in the case of one coil there are only two of these pins which have wire connections, the other two being left blank—this is visible on looking down inside the coil. The coil is placed on the right hand side working from the front of the set. To switch "on" or "off" pull out, or push in respectively, the small knob on lower front of set. The filament voltage required by this valve being 2 volts no filament rheostat is needed, as the filament is correctly dimensioned for this voltage.

Tuning is effected by means of the two larger knobs. As a general rule start with both

pointers at zero and advance each equally. It will be found that the two indicators will be at approximately the same positions on the scales. If any difference it will be found that the right-hand one is slightly higher up the scale than the one on the left-hand. Tuning is rather critical and this is purposely made so in order that powerful nearby stations can be eliminated without the use of a wave-trap. Continue to turn until the station wave or "mush" is heard, when a forward and backward final adjustment of both condensers will enable the station to be tuned in correctly. Should the set be inclined to oscillate even when the right-hand pointer is at zero, a reduction of voltage on the Green wire will always prevent this."

When new, the Ediswan "ONE-DER" Single Valve Receiver complete with valve, one pair of coils, H.T. and L.T. leads, and including all royalties, cost £5 10s. Daventry Coils were 10s. 6d. per pair. The Ediswan "ONE-DER" Loudspeaker (full size model) cost £2 10s., the Ediswan "Loten" Accumulator, XLG 282 was 10s. 6d. Ediswan 60 volt. High-tension Dry Batteries (two required), with tapplings for Grid Bias, were 10s.

ESSENTIAL BOOKS FOR RADIO AMATEURS

New book from RSGB

NBFM MANUAL
by
R. S. Hewes, G3TDR
and
G. R. Jessop, G6JP

The use of frequency modulation by radio amateurs as a communication system has generally been confined to the vhf and uhf bands. When used for this purpose it is essentially a narrow band mode radically different from that used for high fidelity broadcasting. Until now references to narrow band frequency modulation equipment have been confined to articles appearing in various journals, but this manual is intended to present complete coverage of the subject from one source.

It is hoped that it will encourage the home construction of equipment which is truly narrow band, using the frequency or phase methods of modulation and taking full advantage of the mode by the use of the correct demodulator.

The relative freedom from interference to television, radio and audio equipment, and the excellent rejection of impulse noise, makes the mode attractive and economic for both fixed and mobile operation.

60 pages

Price: £1 inc p & p

New Editions Just Published

AMATEUR RADIO TECHNIQUES
(5th edition)

by **Pat Hawker, G3VA**

Basically an ideas and source book, this ever-popular work brings together a large selection of new circuits and devices and many constructional and fault-finding hints.

In this new edition some 50 pages of new material have been included and other sections have been revised and expanded.

304 pages Price £2.25 inc p & p Over 700 diagrams

**RSGB AMATEUR RADIO
CALL BOOK 1975**

Incorporates new call signs and amendments notified between August 1973, when the previous edition closed, and August 1974.

Also includes valuable operating data such as band plans, beacons, amateur radio prefixes in country order, ITU zone list, beam headings and QSL Bureau sub-managers, and a list of RSGB affiliated societies, clubs and groups.

160 pages

Price £1.20 inc. p & p

These are just three of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 3688



C. T. ELECTRONICS

NOW AT 267 & 270 ACTON LANE, LONDON W4 5DG

Now open—our new components shop. These premises are very much larger and will enable us to have greater stocks than we already have. Having all the components under one roof will now guarantee you specialist service on the counter, and on the mail order side. We have an enormous range of components to choose from. If you are having problems getting your components then come along. We are open from 9.30 a.m. through till 6.0 p.m. Monday to Saturday. The nearest underground is Chiswick Park, and there are no parking restrictions.


SEMICONDUCTORS

AC107	35p	BCY30	40p	MJ340	55p	OC36	85p	TIP41C	95p	2N2846	£1-10	2N2846	£1-10	2N2846	£1-10
AC125	25p	BCY31	55p	MJ481	95p	OC42	40p	TIP42C	£1-10	2N2904	£1-10	2N2904	£1-10	2N2904	£1-10
AC126	25p	BCY32	95p	MJ2801	£2-20	OC45	20p	T1550	40p	2N2905	25p	2N2905	25p	2N2905	25p
AC127	27p	BCY33	45p	MJ2901	£2-20	OC45	20p	ZTX107	15p	2N2906	25p	2N2906	25p	2N2906	25p
AC128	27p	BCY34	65p	MJ340	50p	OC70	15p	ZTX300	15p	2N2907	25p	2N2907	25p	2N2907	25p
AC176	27p	BCY38	65p	MJE370	75p	OC71	17p	ZTX500	15p	2N2926	12p	2N2926	12p	2N2926	12p
ACY17	25p	BCY39	£1-00	MJE371	90p	OC72	20p	ZTX501	20p	2N3053	25p	2N3053	25p	2N3053	25p
ACY18	30p	BCY50	£1-00	MJE520	65p	OC75	25p	ZTX504	50p	2N3054	65p	2N3054	65p	2N3054	65p
ACY19	30p	BCY70	22p	MJE2955	£1-95	OC76	25p	ZTX531	30p	2N3055	65p	2N3055	65p	2N3055	65p
ACY20	25p	BCY71	22p	MJE505	85p	OC77	40p	ZTX550	25p	2N3232	75p	2N3232	75p	2N3232	75p
ACY29	55p	BCY72	25p	MM1613	43p	OC81	25p	IN659	8p	2N3525	95p	2N3525	95p	2N3525	95p
AD140	60p	BD121	75p	MM1712	60p	OC83	25p	IN914	8p	2N3702	14p	2N3702	14p	2N3702	14p
AD149	60p	BD123	75p	MJE3055	85p	OC84	25p	IN916	8p	2N3703	12p	2N3703	12p	2N3703	12p
AD161	40p	BD131	75p	MPF102	45p	OC198	30p	IN4001	8p	2N3704	12p	2N3704	12p	2N3704	12p
AD162	40p	BD132	75p	MPF104	35p	OC199	30p	IN4002	8p	2N3705	12p	2N3705	12p	2N3705	12p
AF114	25p	BD153	75p	(2N5457)	35p	OC190	30p	IN4003	8p	2N3706	12p	2N3706	12p	2N3706	12p
AF115	25p	BD156	75p	MPF105	35p	OC171	30p	IN4004	10p	2N3707	12p	2N3707	12p	2N3707	12p
AF116	25p	BDY17	£1-00	(2N5459)	40p	OC200	50p	IN4005	12p	2N3708	12p	2N3708	12p	2N3708	12p
AF117	25p	BDY11	£1-00	MPSA06	35p	OC201	60p	IN4006	15p	2N3709	12p	2N3709	12p	2N3709	12p
AF118	25p	BDY17	£1-00	MPSA06	35p	OC202	75p	IN4007	18p	2N3771	£2-70	2N3771	£2-70	2N3771	£2-70
AF172	30p	BDY19	£1-95	MPSA16	30p	TIP29A	49p	IN1448	7p	2N3772	£2-75	2N3772	£2-75	2N3772	£2-75
AS278	30p	BF152	20p	MPSA56	35p	TIP30A	58p	2N696	25p	2N3773	£2-95	2N3773	£2-95	2N3773	£2-95
AS281	30p	BF154	14p	MPSU08	75p	TIP31A	62p	2N697	20p	2N3819	35p	2N3819	35p	2N3819	35p
AS221	30p	BF195	15p	MPSU56	70p	TIP32A	62p	2N698	25p	2N3820	55p	2N3820	55p	2N3820	55p
BA102	60p	BFX29	30p	NKT135	35p	TIP33A	£1-05	2N706	15p	2N3868	85p	2N3868	85p	2N3868	85p
BA112	50p	BFX84	30p	NKT222	25p	TIP34A	£1-55	2N705A	15p	2N3904	22p	2N3904	22p	2N3904	22p
BA114	16p	BFX85	30p	NKT401	85p	TIP35A	£3-35	2N708	15p	2N3905	25p	2N3905	25p	2N3905	25p
BA135	15p	BFX86	30p	NKT404	80p	TIP36A	£2-65	2N930	20p	2N4058	12p	2N4058	12p	2N4058	12p
BC107	14p	BFX88	30p	NKT773	30p	TIP41A	75p	2N1132	25p	2N4059	12p	2N4059	12p	2N4059	12p
BC109	15p	BFY10	35p	NKT774	25p	TIP42A	90p	2N1302	16p	2N4060	12p	2N4060	12p	2N4060	12p
BC147	12p	BFY44	50p	OA5	20p	TIP29B	58p	2N1303	16p	2N4061	12p	2N4061	12p	2N4061	12p
BC148	12p	BFY51	25p	OA7	10p	TIP30B	66p	2N1304	25p	2N4126	17p	2N4126	17p	2N4126	17p
BC149	12p	BFY52	25p	OA70	12p	TIP31B	70p	2N1305	25p	2N4286	15p	2N4286	15p	2N4286	15p
BC153	15p	BFY53	25p	OA79	12p	TIP32B	70p	2N1306	25p	2N4287	15p	2N4287	15p	2N4287	15p
BC157	14p	BFY90	68p	OA81	10p	TIP33B	£1-12	2N1307	25p	2N4288	15p	2N4288	15p	2N4288	15p
BC158	15p	BSW63	65p	OA90	10p	TIP34B	£1-68	2N1308	25p	2N4289	15p	2N4289	15p	2N4289	15p
BC159	15p	BSW68	80p	OA91	10p	TIP35B	£2-61	2N1309	25p	2N4290	15p	2N4290	15p	2N4290	15p
BC182	14p	BSY95A	12p	OA200	10p	TIP36B	£3-64	2N1813	25p	2N4444	£1-90	2N4444	£1-90	2N4444	£1-90
BC183	14p	C111	50p	OA202	10p	TIP41B	83p	2N1711	25p	2N4871	95p	2N4871	95p	2N4871	95p
BC184	14p	BY126	40p	OA210	10p	TIP42B	98p	2N2147	70p	2N4920	60p	2N4920	60p	2N4920	60p
BC212	14p	BY128	40p	OA211	10p	TIP29C	71p	2N2160	65p	2N5191	95p	2N5191	95p	2N5191	95p
BC213	14p	BY129	40p	OA212	10p	TIP30C	78p	2N2217	25p	2N5194	£1-10	2N5194	£1-10	2N5194	£1-10
BC214	14p	BY164	65p	OC16	35p	TIP31C	85p	2N2218	25p	40360	50p	40360	50p	40360	50p
BC238	12p	IS100	15p	OC22	55p	TIP32C	£1-05	2N2219	25p	40361	50p	40361	50p	40361	50p
BC239	12p	IS103	20p	OC25	65p	TIP33C	£1-30	2N2220	25p	40362	55p	40362	55p	40362	55p
				OC28	85p	TIP34C	£1-90	2N2222A	25p						
				OC30	80p	TIP35C	£3-20	2N2398	70p						
				OC30	80p	TIP36C	£4-10	2N2646	50p						

S.C.R.s

CRS1/05	40p	TR1A1	40p	TR1A2	40p	TR1A3	40p	TR1A262	40p	TR1A263
---------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	--------	-----	--------	-----	--------	-----	--------	-----	---------	-----	---------	-----	---------	-----	---------	-----	---------

Forward with Project 80 into

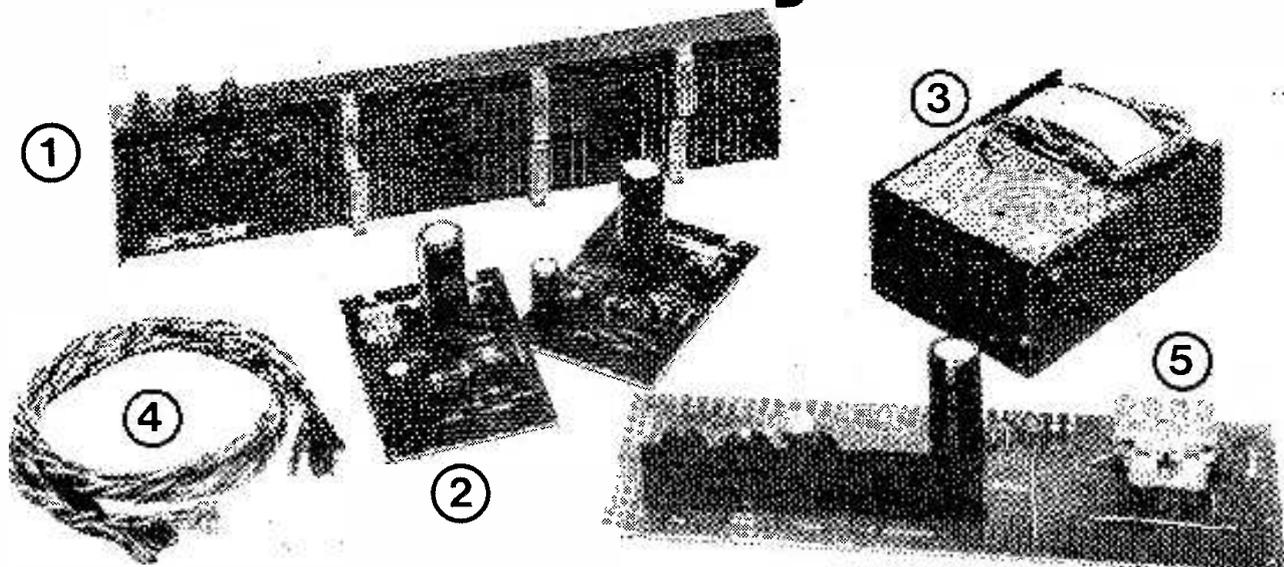

Everything you want in one pack to build the world's most advanced modular hi-fi WITHOUT SOLDERING

- 1 Stereo 80 Control Unit
For mag. and ceramic cartridges, radio and tape.
- 2 Project 80 power amplifiers
Two Z.40s to give 8/8 watts R.M.S. output per channel.
- 3 Power supply unit
One PZ.5.
- 4 Connecting wires
All wires plus nuts, bolts, screws etc.
- 5 Project 805 Masterlink
For input and output connections.
- 6 Mains switch block and instructions manual (not illustrated).

This is Project 80 made even easier to build

You have seen how the marvellously compact Project 80 modules (only 2" high x 3" deep) are so adaptable and easy to install. Now, with Project 805, this wonderful system is made easier still to put together. In this, you have not only all the Project 80 modules in one pack for building an 8/8 watt R.M.S. hi-fi amplifier — there is also a loom of colour coded wires cut to length and tagged for clipping on so that you don't even have to solder! Input and output connections go via the 805 Masterlink panel. With the explicit stage-by-stage large 32 page instructions manual included, it becomes easy for anyone, no matter how inexperienced to install an ultra-modern assembly so advanced in appearance and design that it sets brand new concepts in domestic hi-fi — and of course, you can convert to quadraphony just whenever you wish by adding 805SQ. Only Sinclair know-how and manufacturing facilities could hope to bring you such quality and versatility.

TAGGED WIRES CUT TO LENGTH · NO SOLDERING

Project 805

the complete ready-to-build hi-fi
STEREO AMPLIFIER

Project 805 comprises a Stereo 80 Pre-amp/Control Unit with input for both magnetic and ceramic cartridges, radio, tape; separate bass and treble cut/lift, and volume controls 2 x Z.40 power amplifiers, PZ.5 power unit, 805 Masterlink, wire loom, instructions manual, etc down to nuts, bolts and washers.

£39.95


+£3.20 VAT (R.R.P.)



SINCLAIR RADIONICS LTD
London Rd, St Ives, Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64646


sinclair

true quadraphonics... *NOW!*

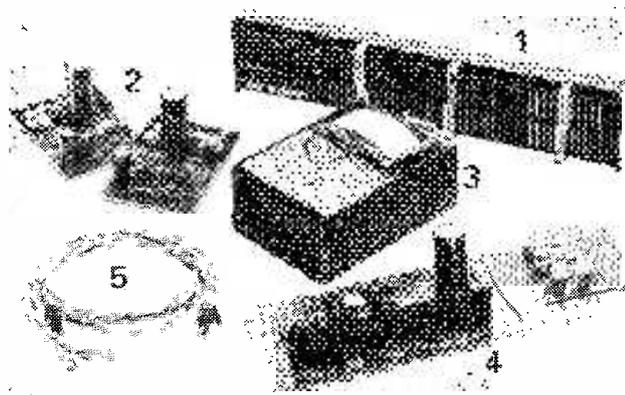

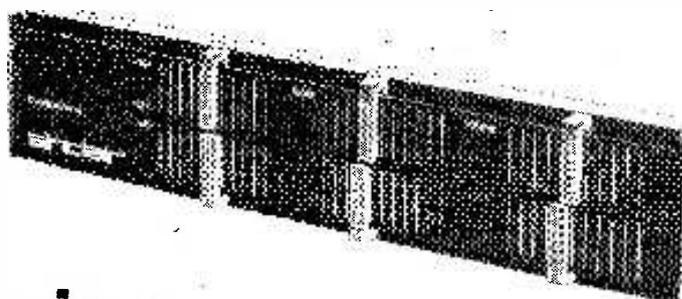1. Project 80SQ decoder with controls.
2. Two Z 40 power amplifiers.
3. PZ.5 power pack
4. Project 80Q Masterlink unit.
5. Wire loom, with clip-on tags – NO SOLDERING!
6. (Not illustrated) Instructions manual, nuts bolts, washers, etc.

The most effective and economical way to enjoy this spectacular breakthrough in hi-fi listening




Project 80SQ Decoder
(available separately)
£18.95 + £1.52 VAT


Add a fourth dimension to your stereo sound

It's so simple to convert to quadraphonics when you already have Project 80, or are about to start with Project 805. Project 805SQ is a complete add-on system at the heart of which is the Project 80SQ decoder. It uses the CBS.SQ matrix principle, by now the widest used method of containing four sound channels within the groove of the record. Project 805SQ includes two power amplifiers, power supply unit, connecting wire loom, 805Q Masterlink, switch block and instructions manual. The 80SQ decoder (also obtainable separately) has independent tone and volume slider controls on the two rear channels for matching true four channel sound to domestic environment. Project 805SQ is money saving too since you do not have to scrap existing Project 80 equipment to enjoy the newest and most exciting form of home listening in the entire history of sound, and your Project 80 quadraphonic assembly is compatible with stereo and mono records.

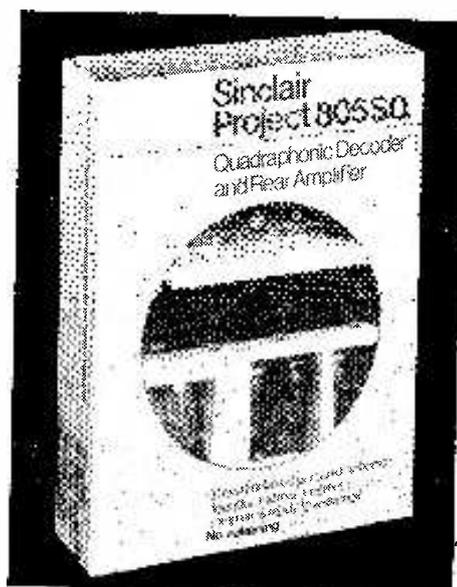- Frequency response · 3db 15 Hz-25kHz
- Rated output 100mV
- S/N ratio 58dB
- Distortion 0.1%
- Power requirements 22-35 volts
- Phase shift network 90° ± 10°, 100 Hz-10kHz
- Adaptable to discrete (CD4) use



Project 805SQ

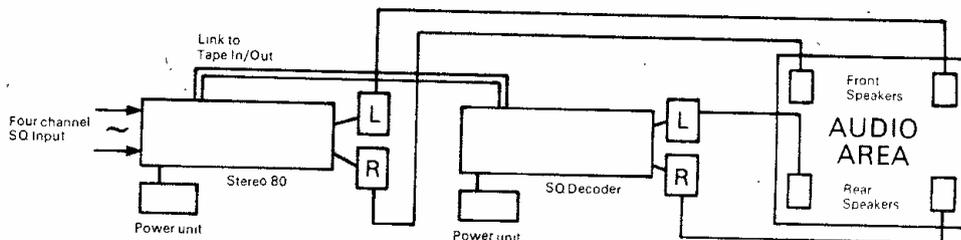

The output from any good stereo cartridge feeds into Stereo 80 and passes via the tape outlet to the 80SQ decoder. Here the signal is separated into its constituent 4 channels, those for the front being accepted by the Stereo 80, those for the rear going from the decoder to the two additional power amplifiers and speakers.


£44.95

+£3.60 VAT (R.R.P.)

Guarantee If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair Appointed Stockists also offer this guarantee. Should any defect arise in normal use within 2 years, we will service it without charge. For damage arising from mis-use a nominal charge will be made.

All Project 50 modules, Project 805 and Project 805SQ are obtainable from your local Sinclair stockist or direct, post free, in case of difficulty

BI-PRE-PAK Audio Bargains

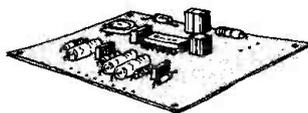


**STEREO
DECODER
£4.50**

incl. P. & P.

Ready-built unit, ready for connection to the IF stages of existing FM Radio or Tuner. The very latest 2nd Generation coil less integrated circuit design, operating on this phase locked loop system, offering even better stereo separation. Only owing to our bulk buying capacity are we able to offer this at the old price. LED stereo indicator lights available. **RED** at 25p. **GREEN** at 40p.

3 W.R.M.S. I.C. AMP
only **£1.50**

Incl. P. & P.
Order Code I.C.A.1

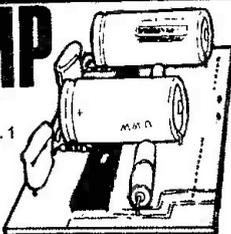


on P.C. Board with all components
or 2 on one board for £2.60

Order Code I.C.A.1/S

These amps. are supplied with a free booklet
on connecting up, specifications and easy to
build projects using the I.C.A.1

5W & 10W AMPS

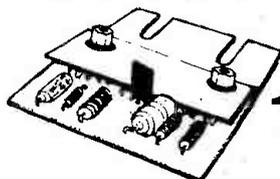

5W ONLY £1.80
10W ONLY £2.26

inc. P. & P.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2½" x 1½". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. **Cheapest in the UK. Built and tested.**

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit 15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain crystal or ceramic pick-up cartridges. **£1.10**

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. **£1.55**

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.10**

Instruction leaflet supplied with all units. Post and packing included in prices. Add VAT at current rate.

I enclose £..... for..... Decoders/.....
3W Amps/..... 5W Amps/..... 10W Amps/.....
Stereo Pre-Amps 1 Stereo Pre-Amps 2
Stereo Tone Controls
(Please insert quantities and delete those not applicable)
Name
Address


BI-PRE-PAK

Dept. D, 222/224 West Road,
Westcliffe-on-Sea, Essex SS0 9DF
Telephone: Southend (0702) 46344

Co. Regn. No. 820919

Guest Speaker

The Castle 8. RS. DD.

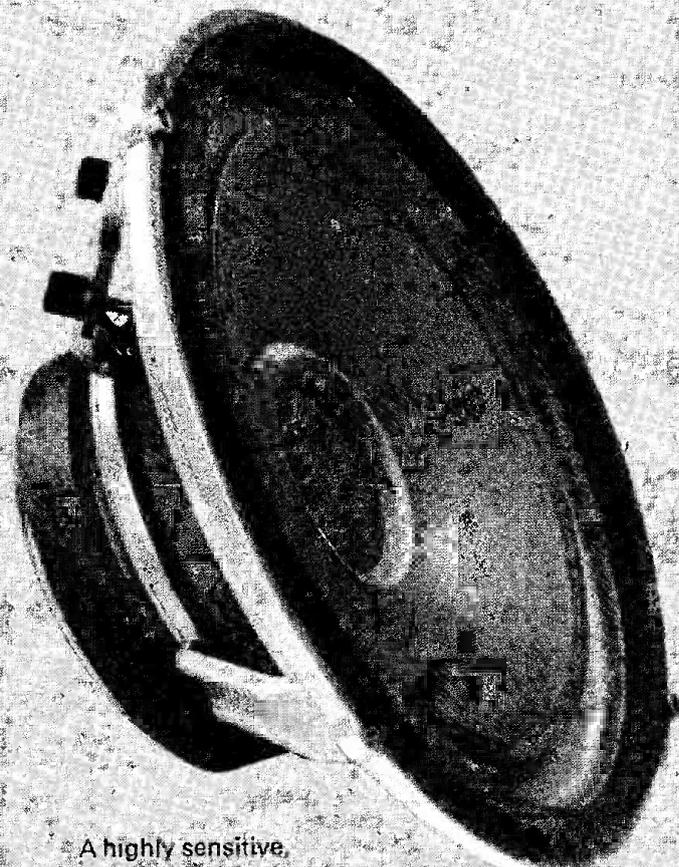

A highly sensitive, full range eight inch unit designed for use in the recommended cabinet, or one of similar dimension.

Suitable for use with good quality stereo installations, tape recorders, car radios, public address and background music systems, it has a frequency range of 50 to 20,000kHz - the lower limit variable with increases in cabinet volume. Recommended retail price is £9.00 excluding VAT

Aluminium Voice Coil

High-Flux 14,000 Oersteds Ceramic Magnet


Roll Surround

Double-Diaphragm

8" Die-Cast Chassis

8 ohms Impedance

15 Watt DIN Power Handling

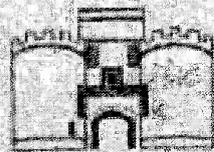

**Castle
Acoustics Limited**

Park Mill, Shortbank Road,
Skipton, Yorks. Tel: Skipton 5333.

CHROMASONIC electronics

Dept. 1
56, Fortis Green Road, London, N10 3HN.
telephone: 01-883 3705

RESISTORS

The standard ranges of Resistors stocked are either E12 or E24 and the values are all in multiples of ten times the decade shown below. The E12 items are only those in bold type. The E24 items are both those in bold and light type.

10	18	33	56
11	20	36	62
12	22	39	68
13	24	43	75
15	27	47	82
16	30	51	91

CARBON FILM $\frac{1}{4}$ watt $\pm 5\%$ tol. 2p ea.
E12 Series 10 Ω to 330K Ω

CARBON FILM $\frac{1}{2}$ watt $\pm 5\%$ tol. 13p ea.
E24 Series 10 Ω to 10M Ω

'CERMET' THICK FILM $\frac{1}{2}$ watt $\pm 2\%$ tol. 8p ea.
E12 series 56 Ω to 150K Ω

METAL OXIDE FILM $\frac{1}{2}$ watt $\pm 2\%$ tol. 43p ea.
E12 series 10 Ω to 1M Ω

CARBON COMPOSITION $\frac{1}{2}$ watt 43p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; ± 0.5 tol.
5.6 ; 6.8 ; 8.2 $\pm 10\%$ tol.

CARBON COMPOSITION 1 watt 53p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; ± 0.5 tol.
5.6 ; 6.8 ; 8.2 $\pm 10\%$ tol.

CARBON FILM 1 watt $\pm 5\%$ tol. 33p ea.
E12 series 10 Ω to 10M Ω

CARBON FILM 2 watt $\pm 5\%$ tol. 63p ea.
E12 series 10 Ω to 10M Ω

WIREWOUND 2 $\frac{1}{2}$ watt $\pm 5\%$ tol. 0.22 to 0.47 Ω 153p
E12 series $\pm 10\%$ 1 to 270 Ω 13p

WIRE WOUND 5 WATT 13p ea.

1	25	250	1.5K
1	30	270	1.8K
1	39	300	2K
2	50	330	2.2K
2	60	350	2.5K
3	68	400	2.7K
3	75	470	3K
4	82	500	3.3K
5	100	560	3.5K
5	125	600	3.9K
6	133	680	4.7K
8	150	750	5K
10	180	820	5.6K
15	200	1K	6.8K
21	220	1.2K	8.2K

WIRE WOUND 10 watt 14p ea.
All the values shown in bold in the 5 watt range

WIRE WOUND 10 watt $\pm 5\%$ tol. 20p ea.
10K ; 15K ; 20K ; 25K

WIRE WOUND 15 watt 133p ea.
All the values from 10 Ω upward shown in bold in the 5 watt range.

POTENTIOMETERS



5K 250K Log or Lin Less Switch (and 1K Lin) 14p
10K 500K Log or Lin with Switch 26p
25K 1 Meg Dual Less Switch 46p
50K 2 Meg Log only 57p
100K 10K Log + 10K Antilog Less Switch

Sliders

10K Single 33p
25K
50K DUAL 55p
100K

Presets

Vertical or Horizontal

1 Watt 53p .25 Watt 7p

100 1K 10K 100K 1Meg
250 2.5 25K 250K 2.5 Meg
500 5K 50K 500K 5Meg

Cermets

100 2.5K 25K 250K
500 5K 50K 500K
1K 10K 100K 1Meg

CAPACITORS

Ceramic Plate
Mullard C333 Series 63 Volts Wkg.

all at 53p each

+0.25pf	1.8 pf	$\pm 2\%$ 12 pf	$\pm 2\%$ 68 pf
2.2 pf	15 pf	82 pf	
3.3 pf	18 pf	100 pf	
3.9 pf	22 pf	120 pf	
4.7 pf	27 pf	150 pf	
5.6 pf	33 pf	180 pf	
6.8 pf	39 pf	220 pf	
8.2 pf	47 pf	270 pf	
10 pf	56 pf	330 pf	

Mullard 630 series 40 volts $\pm 10\%$ tol.
629 series 100 volts

all at 53p each

390 pf	1000 pf	3300 pf
470 pf	1200 pf	3900 pf
560 pf	1500 pf	4700 pf
680 pf	1800 pf	* 10 nf
820 pf	2200 pf	* 22 nf
	2700 pf	

Erie Monolithic Ceramic 30 Volts Wkg.

27 nf 11p; 47 nf 13p; 100 nf 17p

Low Voltage Disc Ceramics

all at 53p each

0.01 uF	18v	0.1 uF	30v
0.022 uF	18v	0.22 uF	6v
0.047 uF	18v	0.47 uF	3v

Mylar Film 100 Volts Wkg.

1000 pf	23p	0.05 uF	33p
2000 pf	23p	0.068uF	5p
5000 pf	23p	0.1 uF	5p
0.01 uF	33p	0.2 uF	63p
0.02 uF	33p	0.47 uF	7p
0.04 uF	33p		


VDR's &

Thermistors



CZ1 17p
CZ4 18p
CZ13A 18p
CZ19 18p
E298CDA258 13p
E298EDA258 13p
E298EDA260 13p
E298EDA262 13p
E298EDA265 13p
E298EDP268 13p
E298Z205 13p
E298Z206 13p
E299DDP336 14p
E299DDP338 14p
E299DDP342 14p
E299DDP348 14p
G116 E1.21
G123 E1.21
R53 E1.49
R54 E1.61
VA1005 16p
VA1026 16p
VA1033 16p
VA1034 16p
VA1039 16p
VA1040 16p
VA1053 16p
VA1055S 16p
VA1056S 16p
VA1066S 17p
VA1057S 19p
VA1067S 19p
VA1077 21p
VA1098 31p
VA1104 31p
VA1107 29p

CAPACITORS

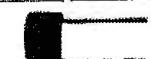

Silvered Mica 350V.
Tol. $\pm 0.5\%$ 11p each
2.2 pf 18pf 30pf
3.3 pf 20pf 33pf
5 pf 22pf 39pf
10 pf 25pf 47pf
Tol. $\pm 1\%$ 11p each
50pf 82pf 150pf
56pf 100pf 180pf
66pf 120pf 220pf
73pf
250pf 330pf 560pf
270pf 390pf 680pf
300pf 470pf 820pf
300pf
1000 pf 1500pf 220p
1800pf
2700pf 3600pf 5000pf
4700pf
6800pf 8200pf 10000pf

Mixed Dielectric 600 Volts Wkg.
0.01 uF 8p ; 0.1 uF 9 p
0.022 uF 8p ; 0.22 uF 173p
0.033 uF 8p ; 0.47 uF 263p
0.047 uF 8p ; 1 uF 363p
0.068 uF 9p ;

Mixed Dielectric 1000 Volts Wkg.
1000 pf 63p ; 0.022 uF 11p
2200 pf 63p ; 0.047 uF 13p
3300 pf 7p ; 0.1 uF 13p
4700 pf 7p ; 0.22 uF 243p
0.01 uF 10p ; 0.47 33p

Solid Tantalum Beads
all at 163p
0.1 uF 35v ; 10 uF 6.3v
0.22 uF 35v ; 10 uF 16v
0.47 uF 35v ; 10 uF 25v
1.0 uF 35v ; 22 uF 16v
2.2 uF 35v ; 47 uF 6.3v
4.7 uF 35v ; 100 uF 3v

Feed-through Ceramics
1000 pf 350v 6p

Disc Ceramics 750 Volts Wkg.
all at 53p each
470 pf; 1000 pf; 5000 pf; 0.01 uF

Tubular H1-K Ceramics 750 Volts Wkg.
1000 pf 53p ; 3000 pf 53p
1500 pf 53p ; 5000 pf 53p
2000 pf 53p ; 0.01 uF 53p

Pulse Ceramics all at 10p each
12 kv D.C. Wkg 8kv D.C.
10pf 120pf 200pf
22pf 140pf 220pf
68pf 150pf 250pf
82pf 100pf 270pf
100pf 200pf 300pf

VAT INCLUSIVE PRICES AT 8% OVERSEAS CUSTOMERS DEDUCT $\frac{2}{27}$ VAT INVOICES ON REQUEST P&P On U.K. Orders 15p. Overseas Orders at Cost


CHROMASONIC electronics

Dept. 1
56, Fortis Green Road, London, N10 3HN.
telephone: 01-883 3705

INDUCTORS

Denco Maxi-Q Coils

Ferrite Rod Aerials

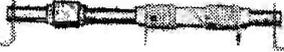

FRA1 Long & Medium Wave band (300pf) 80p
FRA2 Long & Medium " (500pf) 80p

Tuning Coils in two series:

Range

1	150 khz	to	400 khz
2	515 khz	to	1.545 Mhz
3	1.67 Mhz	to	5.3 Mhz
4	5 Mhz	to	15 Mhz
5	10.5 Mhz	to	31.5 Mhz
6	30 Mhz	to	50 Mhz *
7	45 Mhz	to	78 Mhz *

* 50 pf tuning, all others based on 300 pf.

Series A Transistor - 48p each

Only available in ranges 1 to 5 inc.
4 Coils complete each range:

Blue	-	Aerial Coil
Yellow	-	R.F. Interstage
Red	-	Osc. Coil for 465 khz I.F.
White	-	Osc. Coil for 1.6 Mhz I.F.

give range number, letter 'T' and colour.

Series B Dual Purpose Coils 48p each

For FET or Valve Circuits
All ranges available
5 Coils complete each range:

Blue	-	Aerial
Yellow	-	Interstage R.F.
Green	-	R.F. plus reaction
Red	-	Osc. Coil for 465 khz I.F.
White	-	Osc. Coil for 1.6 Mhz I.F.


(Note use Red instead of White for ranges 6 & 7).

Chokes



We stock from 1 μH to 19 mH
Check levels & prices when ordering

TUNING CONDENSERS

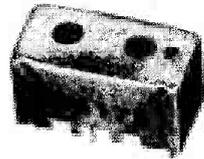


Tuned Block Filter incorporating a Ceramic element. Pre-aligned to 470 Khz. 3db bandwidth 5KHz. Zin 100K. Zout 100K.

LP1175 £1.46

I.F. Transformers

I.F.T 13	465 khz 1st & 2nd d/tuned	65p
I.F.T 14	465 khz final single tuned	65p
I.F.T 15	10.7 Mhz d/tuned	65p
I.F.T 16	1.6 Mhz 1st & 2nd d/tuned	65p
I.F.T 17	1.6 Mhz Final d/tuned	65p
I.F.T 18	465 khz or 1.6 Mhz d/tuned	75p

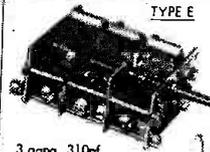

3 gang 310pf

£3.99

TYPE CB04



5pf 80p

10pf 80p

15pf 80p

25pf 80p

50pf 80p

60pf 94p

75pf 94p

100pf 99p



TYPE OO



208 + 176 pf with screen & trimmers

£1.48

DILECON



100pf 69p

300pf 69p


500pf 69p



365 pf 83p

365 x 365 pf £1.30

VEROBOARD

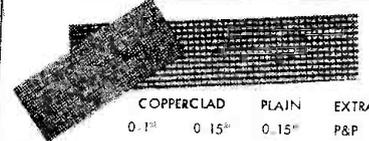

	COPPERCLAD	PLAIN	EXTRA
0.1"	0.15"	0.15"	P&P
21" x 11"	7p	7p	-
21" x 31"	26p	21p	12p
21" x 5"	30p	25p	13p
31" x 31"	30p	25p	-
31" x 5"	34p	34p	25p
17" x 21"	90p	69p	45p
17" x 31"	£1.21	75p	57p
17" x 5"	-	-	99p

D.I.P. Breadboard 4.15" x 6.15" £1.40
VEROSTRIP (State .1" or .15") 30p
Pin Insertion Tool (State .1" or .15") 63p
Spot Face Cutter 51p
Terminal Pins in Pkts. of 50 (State .1" or .15") 22p

Details of I.C.'s; Rectifiers; Diodes; Bridges; Passive Components; LED's; Clocks; Triacs etc. can be seen on other pages and/or issues of Wireless World; Practical Wireless; and Practical Electronics.

Electrolytics

UF	4V	6.3V	10V	16V	25V	40V	63V	100V	160V	450V
1										
1.5							63p		83p	15p
2.2							63p		83p	
3.3							63p		83p	
4.7							63p		83p	17p(40F)
6.8							63p	63p	83p	
8							63p	63p	83p	21p
10							63p	63p	83p	
15							63p	63p	83p	
22							63p	63p	83p	24p(160F)
33							63p	63p	83p	
47							63p	63p	83p	
68							63p	63p	83p	
100							63p	63p	83p	
150							63p	63p	83p	
220							63p	63p	83p	
330							63p	63p	83p	
470							63p	63p	83p	
680							63p	63p	83p	
1000							63p	63p	83p	
1500							63p	63p	83p	
2200							63p	63p	83p	
3300							63p	63p	83p	
4700							63p	63p	83p	
6800							63p	63p	83p	

DIODES

AA119	10p	BY103	22p	0A91	8p
AA120	10p	BY105	16p	0A200	11p
AA129	10p	BY126	16p	0A202	12p
BA100	10p	BY127	16p	ZS120	8p
BA102	27p	BY133	23p	ZS140	8p
BA110	44p	BY164	54p	ZS141	25p
BA115	19p	BY176	£1.62	ZS142	42p
BA144	20p	BY182	£1.62	ZS170	32p
BA145	22p	BY250	25p	ZS270	11p
BA148	22p	BZX70	27p	ZS271	16p
BA154	20p	Series		ZS278	36p
BA155	15p	BZY88	11p	IN914	8p
BA156	16p	Series		IN916	10p
BAX16	10p	0A47	11p	IN4009	7p
BB104	45p	0A79	10p	IN4148	5p
BB1CSB	41p	0A81	8p	IN4448	9p
BY100	16p	0A85	10p	IZS Series	18p
		0A90	8p		

TRANSISTORS

AC107	16p	BC213L	13p	D13V	52p	ZTX301	13p	2N3707	12p
AC126	13p	BC214L	13p	D40N3	59p	ZTX302	17p	2N3708	10p
AC127	13p	BC268	15p	MJ480	93p	ZTX303	14p	2N3709	10p
AC128	13p	BC407	16p	MJ481	£1.18	ZTX304	21p	2N3710	11p
AC176	15p	BCY70	17p	MJ490	£1.01	ZTX311	10p	2N3711	11p
AC187	22p	BCY71	22p	MJ491	£1.42	ZTX312	22p	2N3791	£2.55
AC187K	20p	BCY72	17p	MJ900	£1.42	ZTX341	22p	2N3792	£2.00
AC188	22p	BD115	73p	MJ1000	£1.22	ZTX384	18p	2N3791	£2.55
AC188K	25p	BD123	89p	MJ2955	£1.88	ZTX500	12p	2N3819	27p
ACY17	39p	BD124	80p	MJ3055	£1.21	ZTX501	13p	2N3821	81p
ACY17	38p	BD131	44p	MJ4000	£1.46	ZTX502	17p	2N3823	99p
ACY20	22p	BD132	52p	MJ4010	£1.95	ZTX503	14p	2N3903	15p
AD140	48p	BD131ZPR	£1.17	MJE340	45p	ZTX504	42p	2N3904	19p
AD149	48p	BD135	41p	MJE350	97p	ZTX531	22p	2N3905	25p
AD161	37p	BD136	43p	MJE2955	£1.20	ZTX550	17p	2N4056	13p
AD162	38p	BD201	£1.95	MPE102	72p	2N697	16p	2N4059	19p
AD161/62MP	74p	BD202	£1.46	MPE103	27p	2N706	13p	2N4062	16p
AF114	17p	BF109	74p	MPE104	40p	2N708	16p	2N4289	19p
AF115	17p	BF115	25p	MPE105	44p	2N914	24p	2N4441	85p
AF116	17p	BF160	25p	MPE106	49p	2N930	23p	2N4442	£1.04
AF117	17p	BF167	24p	MPE111	22p	2N1303	20p	2N4443	£1.42
AF118	54p	BF173	24p	MPSU06	63p	2N1304	20p	2N4444	£2.06
AF124	32p	BF178	28p	MPSU06	77p	2N1305	24p	2N4871	59p
AF139	34p	BF179	32p	MPSU56	77p	2N1305	24p	2N4901	£1.41
AF172	25p	BF180	32p	OC28	49p	2N1306	24p	2N5067	£1.07
AF239	40p	BF181	32p	OC35	49p	2N1307	27p	2N5129	16p
ASV26	32p	BF184	27p	OC36	49p	2N1308	34p	2N5172	11p
BC107	11p	BF185	27p	OC44	14p	2N1309	34p	2N5171	77p
BC108	11p	BF194	15p	OC45	14p	2N1711	20p	2N5194	91p
BC109	12p	BF195	17p	OC72	14p	2N1718	£4.37	2N5295	52p
BC117	22p	BF196	16p	OC72	14p	2N1893	52p	2N5447	16p
BC147	10p	BF197	16p	OC75	15p	2N2218	22p	2N5449	16p
BC148	10p	BF200	31p	OC76	27p	2N2219	38p	2N5457	46p
BC149	10p	BF244B	27p	OC81	14p	2N2646	54p	2N5458	43p
BC157	13p	BF262	25p	OC83	25p	2N2894	97p	2N5459	43p
BC158	12p	BF263	25p	OC170	27p	2N2904	32p	2N5485	52p
BC159	14p	BF272	£1.19	OC171	32p	2N2905	30p	2N5777	48p
BC167	17p			OC P71	£1.54	2N2924	16p	2N6068	44p
BC168B	11p	BF597	23p	ORP12	65p	2N2925	18p	2N6069	51p
CC169	12p	BF598	20p	TIP29	53p	2N2926G	10p	2N6070	57p
BC171	20p	BFW10	65p	TIP31	67p	2N3053	51p	2N6071	62p
BC172	17p	BFX 29	41p	TIP31A	67p	2N3054	50p	2N6072	67p
BC177	22p	BFX88	26p	TIP32A	79p	2N3055	51p	2N6075	£1.46
BC178	22p	BFY50	22p	TIP41A	36p	2N3375	£3.56	2N6076	16p
BC179	24p	BFY51	22p	TIP42A	36p	2N3442	£1.19	2N6111	54p
BC182L	11p	BFY90	£1.09	TIS43	37p	2N3442	18p	2N6288	60p
BC183L	12p	BR100	42p	TIS88A	36p	2N3638	20p	2N6420	99p
BC184L	12p	BRY39	43p	TIS91	32p	2N3702	13p	3N141	87p
BC187	27p	BSX20	18p	ZTX107	10p	2N3703	12p	3N153	87p
BC204	14p	BSX21	22p	ZTX108	10p	2N3704	13p	40321	54p
BC209	14p	BSY95A	14p	ZTX109	15p	2N3705	12p	40330	£1.39
BC212L	12p	BU105/02	£1.95	ZTX300	12p	2N3706	14p	40673	55p

REGULATORS

	100mA (TO-39)	500mA (TO-3)	500mA (SOT-32)	1A (TO-220)
5V	TBA625A £1.03	100ST1 (MVR5V) £1.45	L129 £1.39	TDA1405 97p
12V	TBA625B £1.03	1036T1 (MVR12V) £1.45	L130 £1.39	TDA1412 97p
15V	TBA625C £1.03	1037T1 (MVR15V) £1.45	L131 £1.39	TDA1415 97p

12" LONG PERSISTENCE CRT.
Full spec. Price £6.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for **ONLY £6.25, P. & P. 25p.** (Not cased, not calibrated.)

WIDE RANGE WOBBLATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls. preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6 3V A.C. and use within minutes of receiving. All this for **ONLY £5.75, P. & P. 25p.** (Not cased, not calibrated.)
20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. **£8.85 each, P. & P. 25p.** (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic **15p each, P. & P. 5p.**

Large quantity of good quality components — **NO PASSING TRADE** — so we offer 3lbs of **ELECTRONIC GOODIES** for **£1.50, Post paid.**

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 1 off 4pole 2 way etc.). **50p, P. & P. 20p.**

P.C.B. PACKS S. & D. Quantity 2 sq ft—no tiny pieces. **50p each, P. & P. 20p.**

CAPACITOR PACK—50 Brand new components, only **50p, P. & P. 20p.**

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. **ALL BRAND NEW.** 25p the lot. **P. & P. 10p.**

PHOTOCELL equ. OCP71, **13p each.**
MULLARD OCP70—**10p each.**

DELIVERED TO YOUR DOOR
1 cwt of Electronic Scrap chassis, boards, etc. No rubbish. **FOR ONLY £4.00.**

MODERN TELEPHONES type 706. Two-tone grey, **£3.75 each.** Two-tone green **£3.75 each.** Black **£3.75 each.** **P. & P. 35p.**

Ideal **EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding. **£1.75 each, P. & P. 35p.**

HANDSETS — complete with 2 inserts and lead **75p each, P. & P. 37p.**
DIALS ONLY 75p each, P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—no 2 boards the same—no short leaded transistor computer boards **£1.75 post paid.**

Beehive Trimmer 3/30 pf Brand new. Qty. 1—**9.13p ea, P. & P. 15p.** 10—**99 10p ea, P. & P. 25p;** 100—**999 7p ea, P. & P. free.**

HF Crystal Drive Unit. 19in. rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) **£5 ea. Carr. £2.00**

1000pf FEED THRU CAPACITORS only sold in packs of 10, **30p, P. & P. 10p.**

ALWAYS some CHEAP SCOPES AVAILABLE—or build your own—send for our tube list with a S.A.E.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTMead LTD

7/9 ARTHUR ROAD, READING, BERKS.

(near Tech. College)

Tel.: Reading 582605/65916



Tele-Tennis

As described in Practical Wireless

Play the game that's sweeping the nation. You've seen it in pubs, clubs and arcades—now you can play it in the comfort of your own home.


Plugs into the aerial of your U.H.F. 625 Black & White or Colour television. No internal connections to your T.V. set. Does not interfere with other T.V. programmes. Built from 6 neat sub-sections, purchase a complete kit or sub-section at a time.

All parts available separately including P. C. boards, case and ready punched and slotted fascia panel.

S.A.E. for full details.

DABAR ELECTRONIC PRODUCTS

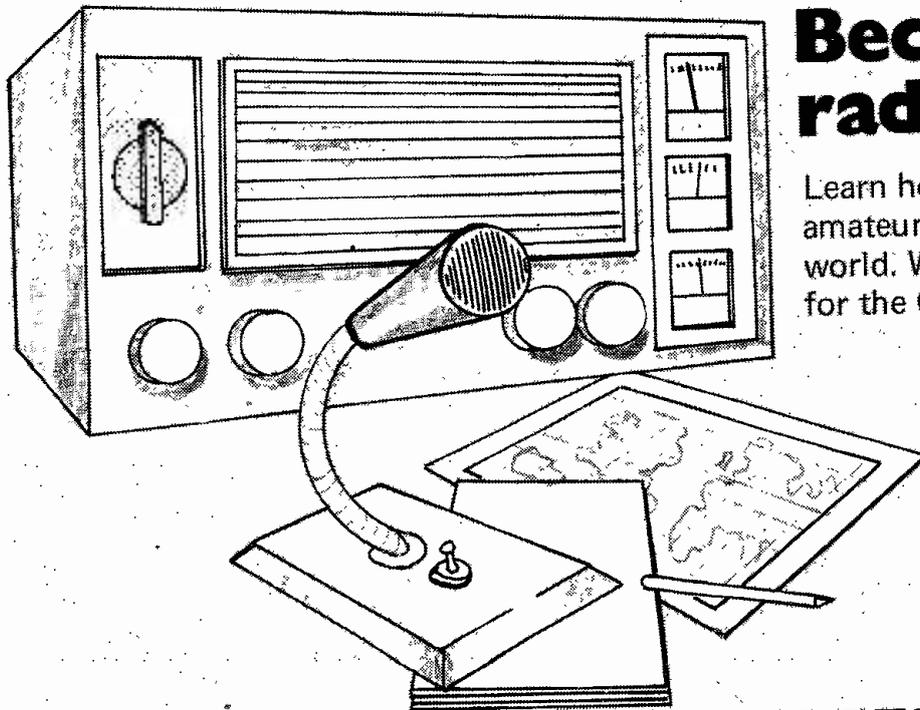98 LICHFIELD STREET
WALSALL, Staffs WSI 1UZ



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept., W.B. 15
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

ALL OUR PRICES INCLUDE V.A.T.

£5.50 Post 25p



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop. Acos stereo/mono cartridge. Base-plate. Size 11in x 8in. Turntable. Size 7in. diameter. A/C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2 x 10 x 8in. 3 watts per channel, plays all records 33 rpm, 45 rpm. Separate volume & tone controls. 240V AC mains.



Attractive Teak finish Weight 13lbs. Bargain Price £25 85p carriage

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob Turn on or off at full or intermediate settings. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated. **OUR PRICE £1.95 Post 25p**



WEYRAD P50—TRANSISTOR COILS

RA2W Ferrite Aerial .85p Printed Circuit, PCA1 .85p
I.F. P50/200 470 kc/s .40p J.B. Tuning Gang .£1.20
3rd I.F. P50/300 .40p Weyrad Booklet .10p
Spare Cores .3p OPT1 .65p
P50/IAC .60p Driver Trans. LFDT4 .65p
Ferrite Rod 8 x 1in. 20p 6 x 1/2in. 20p 3 x 1/2in. 10p

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. Edge 5K.S.P. Transistor 25p

80 Ohm Coax 5p. rd. BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £2. 60 yd. £3. FRINGE LOW LOSS Ideal 625 & colour 10p rd.

8in & 10 x 6in ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm 10 watt.



£3.75 Each Post 52p

10 inch 12 watt Twin Cone, 8 ohm £4.50

E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) **£4.50** Post 25p



With flared tweeter cone and ceramic magnet. 10 watt. Base res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p. **£2.75**

BOOKSHELF CABINET

Size 16 x 10 x 9in. teak finish **£6.60** Post 25p

E.M.I. 13 x 8in. BASS WOOFER. 20 WATTS 15Ω RUBBER CONE SURROUND. £5.50 Post 25p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides 6 x 4in. 45p; 8 x 6in. 53p; 10 x 7in. 65p; 12 x 8in. 85p; 14 x 9in. 90p; 16 x 10in. 90p; 18 x 11in. 90p; 20 x 12in. 90p. £1. ALUMINIUM BOXES 3 x 4 x 3in. 60p; 4 x 4 x 4in. 70p; 6 x 4 x 4in. 80p; 8 x 4 x 4in. 81p; 12 x 4 x 4in. 81p. ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 12p; 8 x 5in. 19p; 14 x 8in. 20p; 10 x 7in. 24p; 12 x 8in. 25p; 12 x 8in. 34p; 16 x 6in. 34p; 14 x 9in. 40p; 12 x 12in. 47p; 12 x 10in. 60p FAXIOL PANEL 10 x 8in. 30p.

SPECIAL OFFER

100 ohm 20W Rheostat 2 1/2in. diam. Ceramic Former, screw terminals, 2in. diam. spindle. 95p, post 25p.

ANOTHER RCS BARGAIN!

ELAC 9 x 5in. HI-FI SPEAKER. TYPE 69RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE **£2.95** 10 WATT, 8 OHM. CERAMIC MAGNET.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. **£2.20** Post Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. d.c. operation. Size 1 1/2" x 1 1/2" x 1". Response 25 c/s. to 25 Kc/s, 26 dB gain. For use with valve or transistor equipment. **99p** Post Full instructions supplied. Details S.A.E. 20p

TEAKWOOD LOUDSPEAKER GRILLS. Will easily fit to baffle board. Size 18 1/2 x 10 1/2in—75p. 10 1/2 x 7in—45p.

E.M.I. WOOFER AND TWEETER KIT

Woofer 10 1/2 x 8in. Ceramic Magnet, 44oz. 13,000 lines. Tweeter 8in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms. Power 12 watts. **£5.75** Post 45p.

BRITISH FM/VHF TUNING HEART

88 to 108 M/CS British made. 2 Transistors ready aligned requires 10-7 M/CS I.F. Complete with tuning gans. Connections supplied but some technical experience essential **Our price £3.95** 10-7 M/CS IF Strip 24-95 Post 20p.

MAINS TRANSFORMERS

250-0-250 8mA. 6-3V 2amp All post 25p each
250-0-250 80 mA. 6-3V 8-5A. 6-3V 1A or 6V 2A... £2.00
350-0-350 80 mA. 6-3V 8-5A. 6-3V 1A or 6V 2A... £3.00
300-0-300V 120mA. 6-3V 4A C.T. 6-3V 2A... £4.25
MINIATURE 200V 20mA. 6-3V 1A... £1
MIDGET 220V 45mA. 6-3V 2A... £1.10
HEATER TRANS. 6-3V 1 amp 85p, 3 amp £1.20
GENERAL PURPOSE LOW VOLTAGE. Trapped outputs at 2 amp, 3, 4, 5, 6, 8, 10, 12, 15, 18, 24 and 30V 25-00 1 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 25-00 2 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 24-00 3 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 26-00 5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 29-75 3, 5, 6, 10, 12V or 15-0-15V 3 amp. £1.50; 6-0-6-0V 500mA 90p 9V 1 amp 95p 2V 300mA 75p 12V 500mA 85p 12V 750mA 95p 12, 36, 48V 2 amp £2. 20V 3 amp £2.
AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W £2.95; 500W £7.50; 750W £10; 1000W £15
CHARGER TRANSFORMERS. Input 200/250V. For 6 or 12V, 1 1/2 amp £1.50; 2 amp £1.80; 4 amp £3.50
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 8 amp. £4.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS; 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **OUR PRICE £12** Carr. Famous make. (Value £19) 95p Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V .. 14p	100/25V .. 10p	50+50/300V .. 50p
4/350V .. 14p	250/25V .. 14p	350+50/325 .. 85p
8/350V .. 22p	500/25V .. 20p	32+32/350V .. 40p
16/450V 25p	1000/25V .. 25p	32+32/450V .. 60p
32/450V 35p	1000/50V .. 47p	32+32+32/350V 65p
32/500V 50p	8+8/450V .. 22p	32+32+32/450V 85p
25/25V .. 10p	8+16/450V 25p	900/350V .. 95p
50/50V .. 10p	16+16/450V 40p	4700/83V .. 95p

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p. 500mF. 12V. 15p; 25V. 20p; 50V. 30p. 1000mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p. 2000mF. 6V. 25p; 25V. 42p; 50V. 57p. 2500mF. 50V. 62p; 8000mF. 25V. 47p; 50V. 65p. 5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 85V. 85p; 50V. 95p.

MICRO SWITCH. Single Pole Change Over. 20p. Sub Min 25p.

CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p, 0.5 15p; 1mF 15p; 2mF 150V 15p. 500V-0.01 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. TWIN GANG. "0.0" 208pF + 176pF, £1.20; 500pF standard 75p; 368+865 with 25+25pF slow motion drive 50p. SLOTTED WAVE, SINGLE. 10pF 80p; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS. 250V AC/DC Amber 25p. RESISTORS. 1W 1/2W, 20% 1p; 2W, 5p. 10Ω to 10M. HIGH STABILITY. 1W, 2% 10 ohms to 8 meg., 10p. Ditto 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each. TAPE OSCILLATOR COIL. Valve Type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 12in. 50 watt GROUP 50/12 8 or 15 ohm high power full range. Professional quality. £12.95

BAKER MAJOR 12" £8.50



30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10.95** Post free Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS Post free
'Group 25' 12 inch 25 watt 3 or 8 or 15 ohm **£7.75**
'Group 35' 12 inch 35 watt 3 or 8 or 15 ohm **£8.50**
'Group 50' 15 inch 50 watt 3 or 8 or 15 ohm **£17.80**

TEAK VENEERED HI-FI SPEAKER CABINETS
For 12in. or 10in. dia. speaker 20x13x9" £10.50 Post 75p
For 13x8in. or 8in. speaker 16x10x9" £8.50 Post 45p
For 8 x 5in. speaker 16 x 8 x 6" £4.95 Post 35p
For 6in. and tweeter 12 x 8 x 6" £4.00 Post 25p
LOUDSPEAKER CABINET WADDING 18in. wide, 20p ft

EMI 6 1/2in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns, HI-FI Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2in. £4.00. Suitable Tweeter 22.00.



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total responses from 1,000 c/s to 18,000 c/s. Size 8 1/2 x 3 1/2in. deep. Rating 10 watt, 8 ohm Suitable Crossover £1.30 **£1.90** Post 20p

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1.95 CROSSOVERS TWO-WAY 3000cps 3 or 8 or 15 ohm £1.30 LOUDSPEAKERS 3 OHMS. 7 x 4in. £1.25; 6in. £1.50. 8 x 5in. £1.60 8in. £1.75; 10 x 6in. £1.90; 10in. £2.00. SPECIAL OFFER: 80 ohm, 2 1/2in.; 2 1/2in. 35 ohm, 2in., 3in., 25 ohm, 2 1/2in. dia., 5in. dia., 6" x 4" **£1 EACH** 15 ohm, 3 1/2in. dia.; 6 x 4in.; 7 x 4in.; 8 x 5in. TYPE 3 ohm, 2 1/2in.; 2 1/2in.; 3 1/2in.; 5in. dia. (6 x 4in. 8 ohm £1.50) RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. diameter 4 watt £2.50. 10in. diameter 5 watt £2.50; 12in. diameter, 8 watt £2.95. VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50:1 40p. Mike trans. mu metal 100:1 £1.25.

MAJOR 100 WATT ALL PURPOSE GROUP OR DISCO AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. MAJOR 50 WATT 4 INPUTS. 2-WAY MIXING £39.95 IDEAL FOR DISCO.



£49 Carr. £1.00

3-WAY CROSSOVER 950 CPS and 3000 CPS with leads ready assembled £1.95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **£4.50**

TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, treble and bass controls 18v. DC operation. **£3.95**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p COAXIAL OUTLET BOXES, surface, 85p.

BALANCED TWIN FEEDER 300 ohms 7p yard. JACK SOCKET Std. open-circuit 15p, closed-circuit 23p. Chrome Lead Socket 45p. Phono Plug 8p. Phono Socket 8p. JACK PLUGS Std. Chrome 20p; 3-6mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 10p; CANS 5p.

REVERSIBLE 4 POLE MOTOR £2.25
1,400 r.p.m. Reversible 42 Watt. Post 25p spindle 1 1/2" x 7/8", size 3 1/2" x 3". As illustrated. With Cooling Fan 240V A.C.

E.M.I. GRAM MOTOR £1.00
120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. Post 25p.

RADIO COMPONENT SPECIALISTS

Minimum post 20p.

Illustrated Brochure, Radio Books & Components Lists 10p.

337 WHITEHORSE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1663

SAVE OVER £36 NOW!

FIRST TIME EVER! A Genuine 'MEMORY' POCKET CALCULATOR
 *YOURS FOR UNDER 1/3RD OF IMPORTERS RECOMMENDED SELLING PRICE!

THE INCREDIBLE NEW WORLD SHATTERING
004 MEMORY POCKET SIZE ELECTRONIC CALCULATOR
ONLY £15.47 (POST ETC 50p) (INCLUDES V.A.T. NO MONEY TO PAY!)

Full Business, Scientific & All Basic Mathematical Functions
 Basic Arithmetic, Chain Calculations, Percentages, V.A.T. Calculations, Net Values, Interest simple and compound, Depreciation, Mortgages and hire purchase interest and payments, Counting for stock-taking, Currency conversion Taxation calculations, Statistics, Electronics, etc., etc., Squares, Powers of Numbers, Square Root, Reciprocals, Logarithms, Hyperbolic Functions, Equations, Physics Calculations, Sum of Product, Polynomials, Computer Maths, nTH Roots, Trigonometric and Inverse Trigonometry Functions, Exponential Functions, etc., etc.



- Amazing "Brain Button" allows random MEMORY Access
- MASSIVE entry and recall capacity
- Never overflows or loses information
- Problems entered as they are spoken
- Large eight digit display
- Fully floating decimal point
- Automatic minus sign
- Automatic true credit balance plus or minus
- Percentages with automatic net value, plus or minus
- K Constant on all four functions
- Correction of entry & function entry errors
- Correction of decimal point position
- Last answer can be recalled even after clearing

The incredible new 004 "MEMORY" Calculator heralds the beginning of a new era in pocket-size electronics! And, thanks to a special arrangement we have made with the suppliers, you can be among the first in this country to own one AND SAVE OVER £36 INTO THE BARGAIN! Brilliantly designed! Manufactured to the highest standards! So much is incorporated into this incredibly compact product of advanced modern science it's almost unbelievable! Only 2 1/2 x 4 1/2 x 3/16 overall approx. So small & light-weight you can slip it into your pocket or handbag & not know it's there at all! Yet wonderful also on Desk Top, in the office, shop or home. Extremely reliable & robust. Designed to give years of perfect service. Bold, clear visual display reading. Large, well-spaced keys for fast accurate use with utmost ease. The most incredibly complicated calculations completed in a wink with miraculous "space-age" electronic accuracy! Everything worked out with utter simplicity! Accountant, schoolboy or professor, the 004 "Memory" Calculator has a virtually limitless capacity to solve your every mathematical problem! Works off standard batteries (obtainable everywhere) also works off 220/250v. A.C. Mains using mains battery eliminator (available as optional extra). Brand spanking new. Complete with Owner's Manual, Quick Reference Guide, simple instructions with working examples, and WRITTEN GUARANTEE, ONLY £15.47, post etc. 50p. Standard battery & special protective carry case 50p extra. Mains battery eliminator £2.50 extra, if required. Buy one, or buy as many as you like! What an investment! At this incredible price you just can't lose. You save £££'s & £££'s! Send quickly, test on 7 days Mail Order approval from receipt of goods. Refund if not delighted. Or call at either store.

Order by post to Uxbridge Road or call at either store.
Callers: ACCESS & BARCLAY CARDS ACCEPTED
 Bargains galore at both stores—(COMMERCIAL TRAVELLERS NOTE: Merchandising office at Holborn)

Dept WP/40, 164 UXBRIDGE ROAD, (facing Shepherds Bush Green), LONDON W12 8AG. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thur. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

SHOPERTUNITIES LTD.

BENTLEY ACOUSTIC CORPORATION LTD.																									
7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX					Telephone 6743																				
All prices inclusive of V.A.T.																									
OB2	.40	6BA6	.28	6L7	.50	12Q7GT	.45	35Z4GT	.70	DY87/6	.35	ECL82	.34	HY88	.40	PCH200	.80	UBF80	.40	Transistors	AF117	.21	BYZ13	.28	
OZ4	.47	6BC8	.60	6L18	.55	12SC7	.50	35Z5GT	.75	DY802	.35	ECL83	.70	HY91	.58	PCL82	.38	UBF89	.40	& Diodes	AF121	.33	FSY11A	.25	
1A3	.45	6BE6	.35	6L19	2.00	12BG7	.40	42	-.50	E800C	2.20	ECL84	.60	RZ40	.50	PCL83	.50	UBL21	.77	AF124	-.28	FSY41A	-.25		
1A8GT	.50	6BH6	.60	6LD20	.75	12BH7	.35	43	1.00	E80F	1.40	ECL85	.60	RZ41	.55	PCL84	.45	UC92	.45	2N404	-.20	AF125	-.19	OA9	-.14
1A9GT	.65	6B16	.55	6N7GT	.60	12BJ7	.44	50B5	-.85	E83F	1.30	ECL86	.40	RZ80	.28	PCL86	.47	UCC84	.75	2N966	-.58	AF126	-.20	OA10	-.47
1H6GT	.60	6BQ7A	.55	6Q7G	.50	128Q7	-.68	50C5	-.60	E88CC	.75	ECL87	.50	RZ81	.29	PCL805	.55	UCC85	-.45	2N1756	-.55	AF180	-.53	OA47	-.11
1L4	.28	6BR8	1.50	6Q7(M)	.55	14H7	-.55	50EH5	-.75	E180F	1.00	ECL88	.40	RZ82	.30	PEN45	.80	UCF80	.70	2N2147	-.94	AF186	-.61	OA70	-.17
1N6GT	.65	6BT7	1.40	6R7G	.60	14S7	-.80	50L6GT	.65	E182CC1	.25	ECL89	.40	RZ83	.25	PEN45DD	-.80	UGH21	2.00	2N2297	-.25	BA115	-.15	OA73	-.17
1R5	.45	6BW6	.70	6R7M	.75	19AQ5	.50	58A2	-.60	E1145	.52	ECL90	.40	RZ84	.20	PEN46	.50	UGH81	.40	2N3053	-.36	BA129	-.14	OA81	-.10
1S4	.83	6BW7	.70	6R7A	.44	19G8	6.00	58A3	-.60	EA50	.27	ECL91	.40	RZ85	.20	PEN45DD	2.00	UCL82	.38	2N3121	2.75	BA180	-.11	OA85	-.09
1U4	.60	6BZ6	.48	6SC7GT	.33	20D4	2.00	90AG	2.50	EA76	1.00	ECL92	.40	RZ86	.20	HABC80	.60	UCL83	.55	2N3703	-.21	BA163	-.17	OA90	-.14
1U5	.75	6C4	.35	6SG7	.44	20P2	.75	90C1	.75	EABC80	.38	ECL93	1.00	RZ87	.60	H123	.60	UF41	.70	2N3709	-.22	BC107	-.14	OA91	-.10
2D21	.45	6C5A	.50	6SH7	.44	20L1	1.10	90C2	2.40	EAC91	.75	ECL94	.40	RZ88	.60	H123DD	.75	UF42	.70	AA119	-.17	BC108	-.14	OA95	-.10
2KX	.55	6C6	.40	6SJ7	.55	20P3	-.80	150B2	.75	EAF42	.75	ECL95	.40	RZ89	.60	H220	.60	UF80	.35	AA120	-.17	BC109	-.11	OA200	-.10
2X2	.60	6C9	1.00	6SK7GT	.44	20P4	1.00	215SG	.50	EAF801	.75	ECL96	.40	RZ90	.60	H220DD	.75	UF85	.44	AA129	-.17	BC113	-.28	OA202	-.11
3A4	.50	6CD8G	1.25	6TK7GT	.45	20P5	1.30	807	.59	EA50	.25	ECL97	.40	RZ91	.60	H220DD	.75	UF86	1.00	AAZ13	-.20	BC115	-.17	OC44	-.11
3D6	.40	6CG8A	.75	6TV8G	.17	25A6G	.60	4032X	6.00	EB91	-.20	ECL98	.40	RZ92	.60	H220DD	.75	UF87	.44	AA129	-.17	BC116	-.28	OC45	-.18
3Q4	.40	6CL6	.65	6V6GT	.45	25Y6G	.70	8057	1.00	EBB31	.25	ECL99	.40	RZ93	.60	H220DD	.75	UF88	.44	AA129	-.17	BC117	-.28	OC46	-.17
3Q5GT	.55	6CL8A	.80	6X4	.40	25Y6G	.70	8060	1.00	EBF80	.29	ECL100	.40	RZ94	.60	H220DD	.75	UF89	.40	AC107	-.17	BC118	-.28	OC46	-.17
3S4	.40	6CM7	.75	6XBGT	.45	25Z6G	.70	7193	-.58	EBF89	.32	ECL101	.40	RZ95	.60	H220DD	.75	UF90	.40	AC113	-.28	BC118	-.28	OC46	-.17
3V4	.70	6CU5	.75	7B6	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL102	.40	RZ96	.60	H220DD	.75	UF91	.40	AC126	-.14	BCY10	-.50	OC70	-.14
4CB6	.55	6CW4	1.00	7B7	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL103	.40	RZ97	.60	H220DD	.75	UF92	.40	AC127	-.19	BCY12	-.55	OC71	-.18
5CG8	.55	6DE7	.75	7H7	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL104	.40	RZ98	.60	H220DD	.75	UF93	.40	AC128	-.22	BCY33	-.22	OC72	-.19
5R4GY	.80	6DE6A	.75	7H7	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL105	.40	RZ99	.60	H220DD	.75	UF94	.40	AC129	-.22	BCY34	-.22	OC74	-.25
5U4G	.40	6EW6	.75	7Y4	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL106	.40	RZ100	.60	H220DD	.75	UF95	.40	AC132	-.22	BCY38	-.25	OC75	-.12
5V4G	.50	6E5	1.00	7Z4	.80	25Z6G	.70	7193	-.58	EBF89	.32	ECL107	.40	RZ101	.60	H220DD	.75	UF96	.40	AC132	-.22	BCY38	-.25	OC76	-.17
5Y3GT	.45	6F1	.75	9D7	.85	25Z6G	.70	7193	-.58	EBF89	.32	ECL108	.40	RZ102	.60	H220DD	.75	UF97	.40	AC132	-.22	BCY38	-.25	OC77	-.80
5Z3	.75	6F6G	.50	10C2	.85	25Z6G	.70	7193	-.58	EBF89	.32	ECL109	.40	RZ103	.60	H220DD	.75	UF98	.40	AC132	-.22	BCY38	-.25	OC78	-.17
5Z4G	.45	6F13	.70	10D87	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL110	.40	RZ104	.60	H220DD	.75	UF99	.40	AC132	-.22	BCY38	-.25	OC78	-.17
5Z4GT	.45	6F14	.75	10F1	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL111	.40	RZ105	.60	H220DD	.75	UF100	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6J30L2	.80	6F18	.55	10F18	.85	25Z6G	.70	7193	-.58	EBF89	.32	ECL112	.40	RZ106	.60	H220DD	.75	UF101	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6A8G	1.25	6F23	.85	10D118	.70	25Z6G	.70	7193	-.58	EBF89	.32	ECL113	.40	RZ107	.60	H220DD	.75	UF102	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6A07	.49	6F24	.85	10D117	.70	25Z6G	.70	7193	-.58	EBF89	.32	ECL114	.40	RZ108	.60	H220DD	.75	UF103	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6A65	.87	6F25	1.00	10P13	.75	25Z6G	.70	7193	-.58	EBF89	.32	ECL115	.40	RZ109	.60	H220DD	.75	UF104	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6A86	.60	6F28	.87	10P14	2.00	25Z6G	.70	7193	-.58	EBF89	.32	ECL116	.40	RZ110	.60	H220DD	.75	UF105	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AJ5	.65	6F32	.50	12A6	1.00	25Z6G	.70	7193	-.58	EBF89	.32	ECL117	.40	RZ111	.60	H220DD	.75	UF106	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AK5	.40	6G6G	.60	12AC6	.70	25Z6G	.70	7193	-.58	EBF89	.32	ECL118	.40	RZ112	.60	H220DD	.75	UF107	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AK6	.60	6GH8A	.75	12AD6	.65	25Z6G	.70	7193	-.58	EBF89	.32	ECL119	.40	RZ113	.60	H220DD	.75	UF108	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AM8A	.55	6GK5	.65	12AE6	.65	25Z6G	.70	7193	-.58	EBF89	.32	ECL120	.40	RZ114	.60	H220DD	.75	UF109	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AN8	.70	6GU7	.75	12AT6	.40	25Z6G	.70	7193	-.58	EBF89	.32	ECL121	.40	RZ115	.60	H220DD	.75	UF110	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AQ5	.45	6H6GT	.25	12AU6	.45	25Z6G	.70	7193	-.58	EBF89	.32	ECL122	.40	RZ116	.60	H220DD	.75	UF111	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AR5	.60	6J5GT	.45	12AV6	.50	25Z6G	.70	7193	-.58	EBF89	.32	ECL123	.40	RZ117	.60	H220DD	.75	UF112	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6A87	1.00	6J6	.30	12BA6	.45	25Z6G	.70	7193	-.58	EBF89	.32	ECL124	.40	RZ118	.60	H220DD	.75	UF113	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AT6	.45	6J7G	.30	12BB6	.50	25Z6G	.70	7193	-.58	EBF89	.32	ECL125	.40	RZ119	.60	H220DD	.75	UF114	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AU6	.80	6J8A	.75	12BH7	.50	25Z6G	.70	7193	-.58	EBF89	.32	ECL126	.40	RZ120	.60	H220DD	.75	UF115	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AV6	.45	6K7G	.30	12E1	8.00	25Z6G	.70	7193	-.58	EBF89	.32	ECL127	.40	RZ121	.60	H220DD	.75	UF116	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AW8A	.95	6K8G	.45	12J7GT	.60	25Z6G	.70	7193	-.58	EBF89	.32	ECL128	.40	RZ122	.60	H220DD	.75	UF117	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6AXA	.75	6L1	2.00	12K5	1.00	25Z6G	.70	7193	-.58	EBF89	.32	ECL129	.40	RZ123	.60	H220DD	.75	UF118	.40	AC132	-.22	BCY38	-.25	OC78	-.17
6B8G	.80	6L6GT	.58	12K7GT	.50	25Z6G	.70	7193	-.58	EBF89	.32	ECL130	.40	RZ124	.60	H220DD	.75	UF119	.40	AC132	-.22	BCY38	-.25	OC78	-.17

RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are:
2 track record playback heads 55p each.
4 track record playback heads 80p each.
Erase heads are also available separately—
2 track 40p—4 track 65p.

NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts. 9p each, 10 for 74p. Plastic pushrod suitable for operating. 7p each, 10 for 68p.

1 R.P.M. MOTOR+GEAR BOX

Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit. Price £1.25 each.

AUTO-ELECTRICAL CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £6.95 plus 25p post and insurance.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.50.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—
3 pole, 3 way—4 pole, 3 way—2
pole, 4 way—3 pole, 4 way—2 pole
6 way—1 pole, 12 way. All at 30p
each.

MULTI-SPEED MOTOR.

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,500 r.p.m. Shaft is 1/4 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price £1.00 plus 25p postage and insurance.

SLIDE SWITCHES

Slide switch. 2-pole changeover panel mounting by two 6B.A. screws. Size approx. 1in x 1/4in rated 250V lamp. 10p each. 10 for 90p. Ditto as above but for printed circuit 8p each 10 for 72p. Sub Miniature Slide Switch. DPDT 19mm (1in approx.) between fixing centres. 20p each or 10 for £1.80. SP Change over spring return 250V 1 amp. 15p.

ISA ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.30 + 20p p. & p. or with glass front, chrome bezel, £1.00 extra.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, 37p each.

12 VOLT 1 1/2 AMP. POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2.50 plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6.95 plus £1.00 post.


PC BOARD MARKER

Valve action fibre tipped marking pen filled with black etch resist—It's easy with this to make a perfect PC board, just draw straight on to the copper—allow 15 minutes to dry, then immerse in ferric chloride or other etchant on removal the circuit stands in high relief, 99p.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs. per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £20 each. Special snip price £7.50 plus 25p post and insurance. Don't miss this terrific bargain.


TANGENTIAL HEATER UNIT

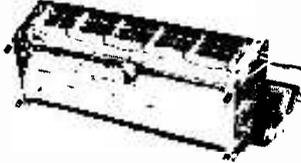

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters. Comprises motor, impeller, 2kW, element allowing switching 1, 2kW, and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch, £2.75. Don't miss this. Control Switch, 44p. P. & P. 40p.

STEREO RADIO CABINET

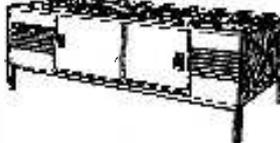Long, Low and Modern. Teak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 4ft. 2in x 15in x 15in. Probably cost over £20 to make. Our Price £8.10 each.




TWENTYLITE

Fluorescent lighting units with polyester choke and finished white enamel, 40 ins. model. Ideal kitchen, bedroom, hallway, porch, lift, etc., with tube. Assembled ready to install. Price £2.20 + 40p p. & p.



—THIS MONTH'S SNIP— SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w) Unit in Box all ready to work. £7.95 plus 95p VAT and postage.

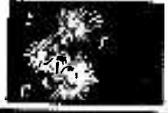

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows—

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated. Size 3in. x 3in. x 2in. deep. Price £4.35 as illustrated but less case.



SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25-31.39 & 49 metre bands—Kit contains chassis front panel and all the parts. £1.25—crystal earphone 50p.




MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this—

1 Unilex Amplifier	Ref. EP.9000	£1.60
1 Unilex Amplifier	Ref. EP.9000	£1.60
1 Unilex Pre-Amp	Ref. EP.9001	£1.98
1 Unilex Power Unit	Ref. EP.9002	£2.53
1 Control panel kit with spun aluminium faced knobs		£3.30

Or the complete outfit—£11.30 post paid. Pair of 15 ohm speakers made by Goodmans are also available if required, price £3.80 the pair. No extra postage if ordered with the above, otherwise add 25p.

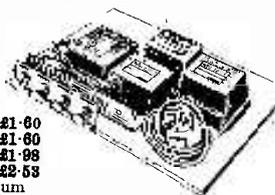SPECIAL PRICES TO COLLEGES AND INSTITUTION ENGINEERING: THIS KIT IN THEIR CURRICULUM.



SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc.
24in x 18in £1.90
13in x 0in £1.50



HORSTMANN "TIME AND SET" SWITCH

(A 30 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Two models 15 amp £2.18, 30 amp £3.35. P. & P. 25p each.



TERMS:—

ADD 8% V.A.T.

Send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 30p.

AM/FM TUNER

Unit made by the American GEC company, 8 transistor, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tunes AM range 540 to 1620 KHz, FM range 88 to 108 MHz. Switches for on-off and AFC. Output for MXP or direct. Special snip price £5 plus 30p post. Three or more post free.

7 WATT STEREO AMPLIFIER

Again by the American GEC company. This has exceptionally good tone quality. Is complete with pre-amp and treble base, volume and balance controls. Also has mains smoothing circuit and rectifiers so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner, pick-up, mike, etc. Special snip price £6 plus 30p post. Three or more post free.

COMPLETE SYSTEM

AM/FM and MPX Tuner
Decoder and stereo amplifier. Specifications of tuner and amplifier are approximately as given above. This is ready built and tested system complete with scale and pointer, ready to install into suitable cabinet. (Our big stereo cabinet should be ideal for this.) Limited quantity, £15 each.

AMPLIFIER PANELS



Very nice looking, polished black pressspan with firing holes, 6 phono sockets and changeover slide switch and is printed as sketch. Price is 30p.

BATTERY CHARGERS

Famous Atlas in metal case with meter, output leads terminated by crocodile clips. For 6 or 12v charging simply by changing plug on front panel. Ready built new and still in maker's original packing. Two models: 1 1/2 amp £1.99 and 3-4 amp £2.95. Please add 40p postage for one and 75p postage for two.



ELECTRIC MOTORS

7 powerful battery motors as used in racing cars and power models. Output and types vary to make them suitable for hundreds of different projects—tools, toys, models, etc. All brand new reversible and for 10 to 12v. Bats., wiring diagrams included. Post and VAT 30p.

FREE Details of how to make miniature power station.

NEW ITEMS THIS MONTH

Car Cassette Power Kit. With a stabilised output of 6v, 9v or 12v. The kit comprises transistors, zener diode, resistors and condensers. Price £2.10. Suitable plastic case 40p extra.

Black Light as used in discotheques and for stage effects, etc. Virtually no white light appears until the rays impinge on luminous paint or white shirts, etc. We offer 12" 8w tubes complete with starter, choke, lamp holders and starter holder. Price £2.75 + 30p post. Tubes only £2 + 30p post. **3 KV Rectifiers.** For replacements in colour TVs or for experimenting with really high voltage for doublers and triplers, etc. Famous maker. 45p each. Quantity prices available.

Meters. All flush mounting with chrome-plated surround. 0-2 amp 40p. 0-3 amp 45p. 0-4 amp 55p. 0-10 amp 95p.

Rectifiers. All 24v full wave (bridge) with cooling fins. 1 1/2 amp 25p. 3-4 amp 85p. 5-7 amp £1.25. **15 way Screen Cable.** Suitable for equipment wiring, multi-way telephone installations, etc. Each core has seven strands copper, PVC insulated and colour coded differently from every other core. These are then laid together encased first by a metal screen and then grey PVC. Price 30p metre or 10 metres £2.50.

Touch Switch. This switch suitable for up to 10 amps mains voltage. Stands up approximately 1/2" rather like a joy stick and no matter which direction it is pushed, it makes contact. Base size approximately 2 1/4" x 2". Price 25p each.

Light Switch. Automatically switches on lights at dusk and off at dawn. Can also be used where light and dark is a convenient way to stop and start an operation. Requires only a pair of wires to the normal switch. In bakelite box normal switch plate size. 1 amp model £2.95.

J. BULL (ELECTRICAL) LTD.

(Dept. PW), 102/3 Tamworth Road, CROYDON CRO IXX

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System—with a big plus over all the other kits—the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well. Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car. When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages.

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES

The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (C)
Tel: Sheffield (0742) 668888

Marshall's

A. Marshall & Son (London) Limited Dept. PW
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161
& 85 West Regent Street Glasgow G22 QD Tel: 041-332 4133

Everything you need is in our new catalogue available now price 20p

Trade and export enquiries welcome

PW TELE TENNIS

As featured in PRACTICAL WIRELESS July - November 1974.
Also on BBC Nationwide and in the Daily Mail October 2nd 1974.

This exciting new game is now available in kit form. Due to popular demand we are now able to offer a fantastic saving on list prices. Ideal game for whole family. No need to modify your TV set, just plugs in to aerial socket. Parts list as follows:

A Resistor Pack	£1.00	p.p.	20p
B Potentiometer Pack	£1.25	p.p.	20p
C Capacitor Pack	£3.10	p.p.	20p
D Semiconductor Pack	£14.50	p.p.	20p
E IC Sockets	£4.00	p.p.	20p
F Transformer	£1.15	p.p.	25p
G PCB's	£7.50	p.p.	20p
H Switches	£4.50	p.p.	20p
I UHF Modulator Kit...	£7.20	p.p.	20p

Special Prices—complete kit (excluding case) £42.00 p.p. 50p Sections A-F incl. £23.50 plus 30p. Assembly instructions with complete kit or 75p on request.

SN7400	16p	SN7420	16p	SN7453	16p	SN7491	£1.10
SN7401	16p	SN7423	37p	SN7454	16p	SN7492	75p
SN7401A	38p	SN7425	37p	SN7460	16p	SN7493	65p
SN7402	16p	SN7427	45p	SN7470	30p	SN7494	85p
SN7403	16p	SN7430	16p	SN7472	38p	SN7495	80p
SN7404	24p	SN7432	45p	SN7473	44p	SN7496	£1.00
SN7405	24p	SN7437	35p	SN7474	48p	SN74100	£2.16
SN7406	45p	SN7438	35p	SN7475	59p	SN74107	43p
SN7407	45p	SN7440	16p	SN7476	45p	SN74118	£1.00
SN7408	25p	SN7441	85p	SN7480	75p	SN74119	£1.92
SN7409	33p	SN7442	85p	SN7481	£1.25	SN74121	57p
SN7410	16p	SN7445	£1.59	SN7482	87p	SN74122	80p
SN7411	25p	SN7446	£2.00	SN7483	£1.20	SN74123	72p
SN7412	28p	SN7447	£1.30	SN7484	95p	SN74141	£1.00
SN7413	50p	SN7448	£1.50	SN7485	£1.58	SN74150	£1.44
SN7416	45p	SN7450	16p	SN7486	45p	SN74190	£1.95
SN7417	30p	SN7451	16p	SN7490	65p		

OUR NEW GLASGOW SHOP IS NOW OPEN

Prices correct at August 1974, but all exclusive of V.A.T.
Post and Package 20p postage and package charges

Popular Semi-conductors

2N696	22p	2N3707	13p	AD142	59p	BC309	10p	LM709	
2N697	16p	2N3708	70p	AD143	45p	BC237	21p	TO 99	48p
2N698	40p	2N3715	£1.50	AD161	45p	BC238	17p	8DIL	38p
2N699	45p	2N3716	£1.80	AD162	45p	BCY70	19p	14DIL	40p
2N1302	19p	2N3771	£2.20	AD161	pr	BCY71	22p	LM723C	90p
2N1303	19p	2N3772	£1.80	AD162	£1.05	BCY72	13p	LM741	
2N1304	24p	2N3773	£2.65	AF109R	40p	BD123	32p	TO 99	40p
2N1305	24p	2N3819	37p	AF115	24p	BD131	40p	8DIL	40p
2N1306	24p	2N3820	38p	AF124	30p	BD132	50p	14DIL	38p
2N1307	22p	2N3823	£1.42	AF125	30p	BD135	42p	LM747	£1.00
2N1308	25p	2N3904	27p	AF126	28p	BD136	49p	LM7805	£2.00
2N1309	36p	2N3905	24p	AF127	28p	BD137	55p	MC1310	£2.92
2N1671	£1.44	2N4036	63p	AF139	39p	BD138	63p	MJ480	90p
2N1671A	£1.54	2N4037	42p	AF178	55p	BD139	71p	MJ481	£1.14
2N1671B	£1.72	2N4126	20p	AF179	65p	BD140	87p	MJ490	98p
2N1671C	£4.32	2N4289	34p	AF180	58p	BF115	25p	MJ491	£1.38
2N2102	50p	2N4921	73p	AF239	51p	BF116	23p	MJE340	45p
2N2147	78p	2N4922	84p	AF240	72p	BF117	43p	MJE2955	£1.12
2N2148	94p	2N4923	83p	AF279	54p	BF154	16p	MJE3055	68p
2N2160	60p	2N5190	92p	AF280	54p	BF163	32p	NE555V	70p
2N2218A	22p	2N5191	95p	BC107	16p	BF180	35p	OC28	76p
2N2219	24p	2N5192	£1.24	BC108	15p	BF181	34p	OC71	20p
2N2219A	26p	2N5195	£1.46	BC109	19p	BF184	30p	OC72	25p
2N2221	18p	2N5245	43p	BC147	12p	BF194	12p	SC35D	£1.68
2N2221A	21p	2N5457	49p	BC148	13p	BF195	12p	SC36D	£1.46
2N2222	20p	2N5458	45p	BC149	12p	BF196	13p	SC40D	£1.89
2N2222A	25p	2N5459	49p	BC167B	13p	BF197	15p	SC41D	£1.32
2N2646	55p	40361	48p	BC168B	13p	BF198	15p	SC45D	£1.89
2N2904	22p	40362	50p	BC168C	11p	BF200	40p	SC46D	£1.96
2N2904A	24p	40363	88p	BC169B	13p	BF237	22p	SC50D	£2.60
2N2905	24p	40406	44p	BC169C	13p	BF238	22p	SC51D	£2.39
2N2905A	26p	40407	33p	BC182	12p	BFX29	30p	SL414A	£1.80
2N2906	19p	40408	50p	BC182L	12p	BFX30	27p	TAA263	£1.00
2N2906A	21p	40409	52p	BC183	09p	BFX84	24p	TBA800	£1.50
2N2907	22p	40410	52p	BC183L	09p	BFX85	30p	TBA810	£1.50
2N2907A	24p	40411	£2.25	BC184	11p	BFX87	28p	TP29A	49p
2N2926	11p	40602	46p	BC184L	11p	BFX88	25p	TP30A	58p
2N3053	25p	40604	56p	BC212K	10p	BFX89	45p	TP31A	62p
2N3054	60p	40669	£1.00	BC212L	16p	BFY19	62p	TP328	74p
2N3055	75p	AC117	20p	BC214L	21p	BFY51	23p	TP33A	£1.01
2N3441	97p	AC126	20p	BC237	09p	BFY52	21p	TP34A	£1.51
2N3442	£1.69	AC127	20p	BC238	09p	BFY90	75p	TP35A	£2.90
2N3415	10p	AC128	20p	BC239	09p	BRY39	48p	TP36A	£3.70
2N3416	15p	AC151V	25p	BC257	09p	CI060	65p	TP41A	79p
2N3417	21p	AC152V	17p	BC258	09p	CA3020A	1.80	TP42A	90p
2N3702	11p	AC153K	25p	BC259	13p	CA3046	70p	TP2995	93p
2N3703	12p	AC176	18p	BC300	£2.12	CA3048	£2.11	TP3055	60p
2N3704	14p	AC176K	25p	BC301	34p	CA3089E	1.96	ZTX300	13p
2N3705	12p	AC187K	23p	BC307	10p	CA3090E	£4.23	ZTX302	20p
2N3706	9p	AC188K	34p	BC308	09p	LM301A	46p	ZTX500	15p

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119 7p	BD131/132 56p	MJ802/MJ4502 £7-65	ZTX302 24p	2N6027 (D13T1) 58p
AC107 68p	BDY20 96p	MJ900 £1-88	ZTX303 15p	3N128 74p
AC126 25p	BF115 30p	MJ1000 £1-50	ZTX304 30p	3N140 92p
AC128 22p	BF167 25p	MJ4502 £4-00	ZTX314 18p	3N141 82p
AC128/AC176 51p	BF180 50p	MLM309K £2-08	ZTX320 40p	3N152 92p
AC151 26p	BF194 18p	MPP102 49p	ZTX500 20p	741/T05 50p
AC152 40p	BF195 18p	MPP103 (2N5457) 45p	ZTX501 22p	741/18DIL 34p
AC153 42p	BF196 18p	MPP104 (2N5458) 61p	ZTX502 25p	747/14DIL 85p
AC176 29p	BF200 46p	MPP105 (2N5459) 78p	ZTX503 20p	748/T05 41p
AC153/176K 71p	BF254 17p	NE555V 45p	ZTX504 60p	3015F £1-40
AC187K 40p	BF255 17p	NKT0033 92p	1N914 4p	3015G £2-00
AC188K 36p	BF259 39p	NKT211 32p	1N4001 4p	7400 24p
AC187/188K 76p	BFX84 34p	NKT212 32p	1N4002 4p	7401 24p
ACY17 41p	BFX85 41p	NKT271 22p	1N4003 5p	7402 24p
ACY18 28p	BFX86 35p	NKT272 22p	1N4004 7p	7403 24p
ACY19 32p	BFX87 33p	NKT273 22p	1N4005 8p	7404 30p
ACY20 26p	BFX88 30p	NKT274 22p	1N4006 8p	7405 30p
ACY21 30p	BFY50 33p	NKT275 29p	1N4007 9p	7408 30p
ACY22 10p	BFY51 30p	NKT279A 36p	1N4148 4p	7409 30p
AD140 80p	BFY52 31p	NKT281 22p	1N5400 16p	7410 24p
AD149 70p	BFY53 28p	NKT282 22p	1N5404 22p	7413 36p
AD161 64p	BFY90 £1-35	NKT401 88p	1N5408 33p	7420 24p
AD162 64p	BPX29 £1-62	NKT402 96p	1S44 4p	7425 36p
AD161/162 £1-28	BR100 22p	NKT403 82p	1S920 10p	7430 24p
AF106 40p	BRV39 66p	NKT404 78p	2N404 58p	7440 29p
AF114 46p	BSX19 26p	NKT405 £1-00	2N697 26p	7442 24p
AF115 40p	BSX20 25p	NKT406 79p	2N706 25p	7443 £1-39
AF118 40p	BSY27 27p	NTGD10 50p	2N706A 27p	7444 £1-74
AF117 58p	BSY95A 12p	OA10 (NTGD10) 50p	2N708 20p	7445 £2-47
AF124 40p	BT106 £1-26	OA47 10p	2N914 25p	7446 £1-74
AF125 38p	BY100 22p	OA79 6p	2N918 54p	7447 £1-50
AF126 39p	BY127 12p	OA90 6p	2N930 25p	7450 24p
AF139 64p	BZY88C3V3 to 10p	OA91 6p	2N1303 61p	7451 24p
AF168 30p	BZY88C30V 10p	OA95 9p	2N1305 65p	7453 24p
AF239 69p	BZX61C7V5 to 28p	OA200 8p	2N1307 69p	7454 24p
AF279 74p	BZY93C9V1 80p	OA202 8p	2N1309 73p	7460 24p
ASY26 70p	BZY93C12V 80p	OC25 72p	2N1613 26p	7470 54p
ASY27 72p	BZY93C15V 80p	OC28 87p	2N1711 30p	7472 36p
BA138 35p	BZY93C18V 80p	OC29 88p	2N1893 46p	7473 54p
BB103 27p	CA3005 £1-35	OC35 78p	2N2218 34p	7474 55p
BB104 50p	CA3011 83p	OC36 78p	2N218A 48p	7475 54p
BB105 37p	CA3013 £1-17	OC41 57p	2N2219 43p	7476 54p
BC107 16p	CA3014 £1-37	OC44 20p	2N2218A 50p	7480 80p
BC107/BC177 46p	CA3018 72p	OC45 20p	2N2368 26p	7482 £1-04
BC108 14p	CA3018A 63p	OC71 20p	2N2369 23p	7483 £1-58
BC108/BC178 49p	CA3020 £1-39	OC72 20p	2N2389A 25p	7486 39p
BC109 18p	CA3028A 79p	OC75 20p	2N2484 48p	7490 84p
BC109/BC179 44p	CA3035 £1-37	OC76 46p	2N2646 52p	7491 A £1-54
BC109C 18p	CA3043 £1-57	OC77 62p	2N2904 38p	7492 £1-02
BC140 52p	CA3046 70p	OC81 32p	2N2904A 35p	7493 90p
BC147 16p	CA3048 £2-11	OC83 32p	2N2905 38p	7494 £1-36
BC148 16p	CA3052 £1-82	OC84 32p	2N2905A 40p	7496 £1-78
BC149 16p	CA3053 47p	OC170 44p	2N2924 23p	7499 96p
BC157 17p	CA3065 £1-28	OC171 47p	2N2925 27p	74100 £1-97
BC158 15p	CA3088E £1-24	OC172 47p	2N2926 10p	74107 62p
BC159 17p	CA3089E £1-94	ORP12 50p	2N3053 30p	74121 51p
BC147/157 33p	CA3123E £4-20	PM7A2 £1-98	2N3054 60p	74141 £1-20
BC148/158 31p	CA3130P £1-40	PM7A6 £2-82	2N3055 65p	74151 £1-32
BC149/159 33p	CR1/051C 65p	PN70 13p	2N3228 88p	74153 £1-62
BC167 15p	CR1401C 86p	PN71 13p	2N3391 A 40p	74154 £2-40
BC168 14p	CZ6 17p	PN107 9p	2N3525 £1-04	74155 £1-86
BC169 14p	D10 (NTGD10) 50p	PN108 9p	2N3702 14p	74156 £1-86
BC169C 15p	IR2160 82p	PN109 9p	2N3703 14p	74190 £2-16
BC177 30p	IR220 60p	PN3819 (2N3819) 24p	2N3704 14p	74191 £2-16
BC178 35p	JA424 £2-08	SL103A 54p	2N3705 14p	74192 £2-09
BC179 28p	LD30A 29p	SL403A 54p	2N3706 14p	74193 £2-09
BC182 15p	MC1303L £1-59	(Rectifier) 71p	2N3707 14p	74196 £1-80
BC182L 15p	MC1305P £1-99	SL803A 94p	2N3708 14p	74197 £1-80
BC183 14p	MC1307P £1-38	ST2 22p	2N3709 14p	40250 58p
BC183L 14p	MC1310P £2-80	T2700D £1-01	2N3710 14p	40310 56p
BC184 16p	MC1330P 88p	T2800D 90p	2N3711 14p	40312 56p
BC184L 13p	MC1352P 90p	T2800M £1-33	2N3773 £3-20	40360 40p
BC212 19p	MC1468L £3-50	TAD100 £1-97	2N3819 35p	40361 38p
BC212L 19p	MC1468L £2-41	TAD110 £1-97	2N3866 82p	40362 40p
BC238 15p	MC4024P £1-84	TBA810S £1-32	2N3904 20p	40406 44p
BC238/308 28p	MC4044P £1-84	TIL112 £2-00	2N3906 24p	40407 34p
BC257 16p	MFC4000B 50p	TIL209 30p	2N4058 15p	40408 50p
BC258 15p	MFC6030 £1-21	TIS43 36p	2N4060 16p	40409 52p
BC259 16p	MFC6040 £1-15	TR1 22p	2N4061 16p	40410 52p
BC307 17p	MFC8010 £1-44	VA1039 15p	2N4062 16p	40430 51p
BC308 14p	MFC8040 £1-24	VA1040 15p	2N4441 70p	40468A 44p
BCY70 22p	MFC9020 £1-56	VA1066s 15p	2N4444 £2-20	40575 41p
BCY71 33p	MJE371 94p	VA1077 17p	2N4871 48p	40576 46p
BCY72 19p	MJE520 70p	W005 25p	2N4990 54p	40602 46p
BD241 A 54p	MJE521 82p	W01 26p	2N4991 46p	40673 52p
BD242 A 60p	MJE2955 £1-49	W02 26p	2N5245 68p	
BD243 A 72p	MJE3055 87p	W04 27p	2N5457 (MPF103) 45p	
BD244 A 78p	MJ480 £1-15	W06 32p	2N5458 (MPF104) 61p	
BD124 £1-00	MJ481 £1-45	W08 32p	2N5459 (MPF105) 45p	
BD131 24p	MJ491 £1-84	ZTX107 14p	2N5756 £1-00	
BD132 32p	MJ802 £3-65	ZTX108 11p	2N5777 54p	

COSMOS LOGIC

CD4000AE 46p	CD4017AE £2-27	CD4030AE 89p
CD4001AE 46p	CD4018AE £2-27	CD4035A £2-23
CD4002AE 46p	CD4019AE £1-04	CD4040A £2-70
CD4007AE 46p	CD4020AE £2-53	CD4042A £1-80
CD4009AE 91p	CD4022AE £2-23	CD4043A £2-02
CD4010AE 91p	CD4023AE 46p	CD4044A £2-02
CD4011AE 46p	CD4024AE £1-62	CD4049A 72p
CD4012AE 46p	CD4025AE 46p	CD4050A 72p
CD4013AE 83p	CD4026AE £3-04	CD4051A £2-36
CD4014AE £2-27	CD4027AE £1-35	CD4056A £1-80
CD4015AE £2-27	CD4028AE £1-97	CD4060A £3-56
CD4016AE 86p	CD4029AE £3-06	CD4069A 46p

MULLARD MODULES

LP1185 FM IF Module £4-69
 LP1186 FM Tuner Module with Diode Tuning £6-00
 LP1400 High performance stereo decoder module using frequency multiplex system £6-08
ORDER AS TYPE NO. 1 "MULLARD MODULES" DATA & APPLICATION CIRCUIT FREE WITH MODULE UPON REQUEST
 N.B. SEE BELOW FOR SPECIAL DISCOUNT ALLOWANCE

INTEGRATED CIRCUIT TEST CLIP

Indispensable aid to the engineer working with DIL IC's. For use with both 14 & 16 lead packages. Clips on to device under test. Can be used as a removal tool. Accidental shorting of IC leads eliminated & Capacitance effects at HF are negligible.
£1-95 each

INTEGRATED CIRCUIT PINS

The lowest priced IC mounting available. Pin Sockets come in a reel, just drill your board at required centres, drop in pins and solder, break off frame holders—your DIL mounting is complete!!

Pin Sockets	1,000 pieces	£7-00
Pin Sockets	100 pieces	£1-00

NE555V TIMER I.C.

As used in magazine articles including July Practical Wireless.
DATA AND CIRCUITS 78p 15p

CA3123E Superhet System with RF Amp. IF Amp, Mixer, OSC. I.C. g.c. Detector and Voltage Regulator. Ideal for car radio applications.
APPLICATION SHEET & DATA 15p

SEVEN WATT AUDIO AMP. I.C.

TBA810S £1-32
 Featuring thermal protection. Ideal for car radio applications.
APPLICATION SHEET & DATA 15p

PACKAGED CIRCUITS

The complete range of Newmarket modules currently being featured in magazine articles. See catalogue for details.

ANTEX SOLDERING EQUIPMENT

X25/240v 25w Iron. £2-25 SK2/240v 15w kit £3-60
 MLX 12v 25w kit, essential for car tool kit £2-85
 X50TC 240v 50w temperature controlled £8-50

ARROW SPECIALISE IN EDUCATIONAL AND GOVERNMENT ORDERS
 —See catalogue for further details.

ARROW SERVICE PLUS

10% DISCOUNT OVER £4. NO POSTAGE AND PACKING. TOP QUALITY PRODUCTS ALWAYS BY RETURN
COMPREHENSIVE CAT.

Important Notice "All prices are exclusive of V.A.T. Please add V.A.T. to the final total of your order after deducting any discount which may be due" VAT. REG. 246602672

ARROW ELECTRONICS LTD.

DEPT. PW 14, 7 COPTFOLD ROAD
 BRENTWOOD
 ESSEX CM14 4BN

I enclose PO/Cheque for 10p
 Name _____
 Address _____
Arrow Electronics Limited
 Dept. PW 12
 7 Coptfold Road
 Brentwood,
 Ch14 4BN

REGISTRATION No. 1062424

Practical Wireless Classified Advertisements

Classified advertisements 12p per word (minimum 12 words). Box No. 30p. Semi-display setting £10 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Receivers and Components



CRATA F.M. TUNER

- | | |
|------------------------|-------|
| Pack 1. Resistors | 36p |
| 2. Capacitors | £1.70 |
| 3. Semi Conductors | £5.85 |
| 4. Inductors & filters | £7.00 |
| 5. Chassis & hardware | £5.00 |
| 6/7. A.M. Parts | £3.65 |

TEXAN 20 + 20W AMP.

- | | |
|--------------------|-------|
| Pack 1. Resistors | 80p |
| 2/3. Capacitors | £3.65 |
| 5. Switches | £1.00 |
| 6. Potentiometers | £1.45 |
| 7. Semi Conductors | £8.25 |
| 8. Transformer | £6.95 |
| 9. Printed Circuit | £2.50 |
| 10. Chassis | £3.00 |
| 11. Cables | 40p |

V.A.T. EXTRA
add 20p p/p etc. except transformer (35p)

S.A.E. for lists
TELERADIO ELECTRONICS,
325-7 Fore Street, Edmonton,
London N9 0PE 01-807-3719
Closed Thursdays

ALLARD ELECTRONICS

Branded Components—Full Specification

TRANSISTORS	SCR's	Price ea.	DIODES	Price ea.
AC125/6/7/8	CRS1/05	0.30	LN914	0.05
AD140/149	CRS1/10	0.58	LN4001/2/3/4/0-08	0.04
AD161/162	CRS1/20	0.60	LN4005/6/7/8/0-08	0.04
AF114/5/6/7	CRS1/40	0.45		
AF118	CRS3/40	0.55		
BC107/8/9	CRS7/400	0.98		
BC147/8/9	CRS16/100	0.85		
BC182/3/4	CRS16/200	0.88		
BC212/3/4	CRS16/600	1.50		
BCY70/71/72/0-15	I.C.'s			
BD131/132	TBA800	1.35		
BF194/5/6	free data			
BFY50/51/52/53				
BY127				
MJE370				
MJE371				
OC28				
OC35				
OC83				
TIL209				
2N2218				
2N2906				
2N2928 all				
2N3053				
2N3054				
2N3055				
2N3702/3/4				
2N3705/6				
2N3707/8/9				
2N3819				

Price ea.	Price each
CRS1/05	0.30
CRS1/10	0.58
CRS1/20	0.60
CRS1/40	0.45
CRS3/40	0.55
CRS7/400	0.98
CRS16/100	0.85
CRS16/200	0.88
CRS16/600	1.50
TBA800	1.35
2N414	
RADIO I/C	
£1 Free Circuit	
ZENERS	
BZY88	0.10
All voltages	
BZX61 series	
1-3 watt	0.17

BRIDGE RECTIFIERS—	Price each		
p.i.v. 1A	2A	4A	6A
50v 0.24	0.34	—	0.64
100v 0.24	0.39	0.54	0.69
200v 0.27	0.44	0.58	0.79
400v —	0.49	0.64	0.89
600v 0.29	—	0.74	—

299/301 BALLARDS LANE
LONDON N12 8NP
MAIL ORDER ONLY Telephone enquiries:
01-445 5188 Cash with order. Add V.A.T.
Orders under £2 plus 12p P. & P.

MULLARD 10W RMS AMPLIFIER MODULES. Absolutely complete. £2.65 inclusive. LTE, 46 Minehead Road, South Harrow, Middx.

BETA DEVICES

FOR BETTER PRICES

TRANSISTORS	10W	DIODES & RECT.
AC187/188	709C TO.99 0.30	LN914 0.04
PR.	709C D.I.L. 0.30	LN4148 0.04
BC107/	741C TO.99 0.36	BY127 0.14
BC108	741C D.I.L. 0.38	LN4001/2 0.05
BC109C	723C D.I.L. 0.80	LN4003/4/5 0.08
BC147/8/9	747C D.I.L. 0.85	LN4006/7 0.08
BCY70/71/72/0-13	748C D.I.L. 0.38	
BFX86/87/88		
BFY50	5 Watt Audio I.C.	WO1 1A 0.20
BFY61/52	TBA 800 £1.50.	WO6 1A 0.80
OC28	Data free with every order.	
OC35		
2N2646	D.I.L. SOCKETS	BZY88 3-3 0.09
2N3053	8-Pin 0.12	33V 5% 0.09
2N3055	14-Pin 0.12	1 Watt 6-8 0.15
2N3442	18-Pin 0.14	200V 5% 0.15
2N3773		
TIP41A		
40636		

C.W.O. PLUS P.P. 10p TO BETA DEVICES,
263 THE RIDGEWAY, ENFIELD, MIDDX.

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £4.00 + p&p 20p U.K. only.

Illustrated catalogue of selected kits and components, 20p inc. VAT. P&P free.

ALL PRICES PLUS 8% VAT

Galleon Trading Co.,
12, Burrs Way,
Corringham,
Stanford-Le-Hope,
Essex. SS17 9DE

250mA. Cartridge Fuses 1 1/2" 90p per 100.
Unused Carbon Resistors. 100 different 45p.
Unused W/W Resistors. 100 assorted £1.10.
100 Capacitor Mixture, 85p.
1/2b. 8 to 2BA. Nut & Bolt mixture 28p. Brass 32p.
20 Assorted Potentiometers Unused £1.15.
Ex Government Standard Jack Plugs 4 for 50p
6 volt 36 or 18 watt Bulbs. SBC, 70p per doz.
Earphones Ex Govt. 70p per pair.
New Meter or Cassette Cases, stiff imitation leather 6 1/2" x 3 1/2" x 4". Only 55p.
Ex T.V. Speakers. Perfect. 352 elliptical 55p.
0-300mA Meters New. £1.75p.
7" Tape Spools 16p each.
All postage included in price
SOUND SYSTEMS OF SUFFOLK
676 Foxhall Rd., Ipswich, Suffolk IP3 8NQ

BRAND NEW COMPONENTS by return. Electrolytics, 15V, 25V, 50V 0.47, 1, 2.2, 4.7, 10 Mfds.—4p, 22, 47—4 1/2 p (50V—5p). 100—5 1/2 p (50V—7p). 220—6p (50V—9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V—9p. Mylar Film 100V 0.001, 0.002, 0.005, 0.01, 0.02—2 1/2 p. 0.04, 0.05—3p. Mullard Tubular Polyester 400V E6 series, 0.001-0.022—3p. 0.033-0.1—4p. Mullard miniature C333 ceramics E.12 series 2% 1.8pf.-47pf.—2 1/2 p. 56pf.-330pf.—3p. Polystyrene 63V, E12 series 10pf.-1,000pf.—2 1/2 p. 1,200pf.-10,000pf.—3 1/2 p. Miniature Highstab Carbon Film Resistors 1/3W E12 series 5% 10-10MΩ (10% over 1 Megohm)—1p. Postage 8p. Prices VAT inclusive. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

NEW COMPONENTS Post Free, 8% VAT included. 2N3702, 2N3704, 12p. Guest UPM 050 1/2 W Carbon Film resistors 1p each. Seven segment common anode LED displays, 0.3in DL707 £2.19, 0.6in DL747 £2.89. Siemens B32540 250V Polycarbonate 0.01, 0.015, 0.022, 0.033, 0.047, 4p; 0.068, 0.1µF, 5p. Triac TAG 250 400V/8A, 75p. D32 diac 25p. 300W Light Dimmer, £2.75. Delivery from stock or your money returned. GREENBANK ELECTRONICS, 94 New Chester Road, Wirral, Merseyside L62 5AG.

Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

440V AC (±10%)	63V Range	±1%	±2%	±5%	
0.1µF (1 1/2" x 1 1/2")	50p	0.47µF	56p	46p	36p
0.22µF (1 1/2" x 1 1/2")	59p	1.0µF	66p	56p	46p
0.25µF (1 1/2" x 1 1/2")	62p	2.2µF	80p	65p	55p
0.47µF (1 1/2" x 1 1/2")	71p	4.7µF	£1.30	£1.05	85p
0.5µF (1 1/2" x 1 1/2")	75p	6.8µF	£1.64	£1.29	£1.09
0.68µF (2" x 1 1/2")	80p	10.0µF	£2.00	£1.60	£1.40
1.0µF (2" x 1 1/2")	81p	15.0µF	£2.75	£2.15	£1.90
2.0µF (2" x 1 1/2")	£1.22				

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 85p, 50 for £4.

TRANSISTORS: BC183/183L 11p BFY50 20p
BC107/8/9 9p BC184/184L 12p BFY51 30p
BC114 12p BC212/212L 14p BFY52 20p
BC147/8/9 10p BC547/558A 12p AF178 30p
BC153/7/8 12p BF194 12p OC71 15p
BC182/182L 11p BF197 13p 2N3055 50p

POPULAR DIODES—LN914 6p, 8 for 45p, 18 for 80p; LN916 8p, 6 for 45p, 14 for 80p; 1844 5p, 11 for 50p, 24 for £1.00, LN4148 5p, 6 for 27p, 12 for 48p; LN4001 5p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p.
LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each, 6 for 39p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.50.

RESISTORS—High stability, low noise carbon film 5%, 1/4W at 40°C, 1/4W at 70°C. E12 series only—From 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 45p.
SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended OD27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p); 800 P.I.V. 11p (4 for 42p).
BRIDGE RECTIFIERS—2 1/2 amp: 22p 40p; 350v 45p; 600v 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 6p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 2.5m, 5m, 1kΩ, 2.2kΩ, 4.7kΩ, 8.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ.
PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 8% V.A.T. TO ORDERS.
Send S.A.E. for lists of additional ex-stock items.
Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. W1)

The Old School, Edstaston, Nr. Wem, Shropshire.
Tel: Whixall 464/465 (STD 094 8792)
(Proprs.: Mintcost Trading Ltd.)

INCOMPARABLE V.H.F. KIT

CV2—unique triple-purpose (Converter, Receiver, Tuner-Feeder) kit for the amateur enthusiast. Fantastic transistorised performance, World Wide Sales. Complete kit of top grade parts covers 80-180 MHz with easy build diagrams only £5 direct from makers or S.A.E. for free literature.

JOHNSONS (RADIO) Est. 1943
SHAW ST., WORCESTER WR13QQ.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

MULLARD UNIVERSAL AUDIO PRE-AMPLIFIER ready built and tested, £9.70. For complete data send SAE to Quantec, Mile Road, Widdrington, Morpeth, Northumberland.

Service Sheets

SERVICE SHEETS for over 6,000 models of Televisions, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only 30p plus SAE with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. SAE enquiries. Catalogue 20p plus SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 20p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

BELL'S TELEVISION SERVICES for Service Sheets, Manuals, Books on Radios, TVs, etc. Service Sheets 40p plus s.a.e. Free booklists on request. Back issues of PW, PE, EE, TV available 25p plus 7p post. S.a.e. with enquiries.—B.T.S. (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

For Sale

NELSON-JONES Stereo Tuner built from Integrex kit. Push button varicap tuning, Portus and Haywood decoder. Performs to specification. £44. I. G. Bowman, 35 Park Hill Road, Torquay, S. Devon.

MICROPHONES: AKG D109, £12-65; AKG D202EI, £43-45; AKG D190C, £18-70; AKG D190E, £20; AKG D224 £55; Sennheiser MD211N, £49-50; Sennheiser MD413N, £29-70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

SOUND TO LIGHT CONVERTORS 3-channel, 1.5 kw £18, 3 kw £25, single channel £9; Sequencer £93; Strobes from £19; Projectors from £24; etc. Call or mail Aarvak Electronics, 98A West Green Road (Side Door), London N15 5NS. 01-800 8656.

VALVES, VALVES & MORE VALVES. Large stocks 1930-1974, many obsolete. Also available many types of transistors and styli. Price lists available, 15p. Cox Radio, The Parade, East Wittering, Sussex. West Wittering 2023.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

Wanted

TOP PRICES PAID for NEW VALVES and TRANSISTORS popular T.V. and Radio types. **KENSINGTON SUPPLIES (C)**, 367 Kensington Street, Bradford 8, Yorkshire.

EARLY WIRELESS receivers, components and magazines, details to Johnson Raffles, Haverbreaks, Lancaster.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

EARLY WIRELESS components, valves, magazines, please contact C. Sawyer, 210 Gordon Avenue, Camberley, Telephone 0276 29460.

WANTED. Valve preamplifier (Williamson or Mullard 512 type). Details to Hughes, "Brooklands", Hall Bank Drive, Bingley, West Yorks. BD16 4BZ.

AVO. 7 & 8 any condition. Any quantity. Huggett's, 2 Pawsons Road, W.

SONY TR8460 or Heathkit GR98, also Standard SR4555F. In good working order. Box No. 120.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Aerials

GENUINE FULL SIZE 18 element TV aerial as used by leading TV companies

ITV, BBC1 & 2B/W & Colour Guaranteed Perfect Pictures. Save ££s. We supply this genuine U.H.F. aerial for only £2.20, can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting complete with clamp instructions. Money Back Refund. Wall/Varavan Bracket 25p. Best Cable 12P per yard. Plug 10P & FREE with outer maps & channel reference of Radio & TV Transmitters. SEND DIRECT TO DEPT. PW10 219 Mansfield Rd. Nottingham.

FOR ONLY £2.20

IMPERIAL TRADING AERIAL LTD.

J. & A. TWEEDY LTD. Incorporating R. Baines
Prices include VAT and Postage
Multibeams: MBM 30 £25-20, MBM 46 £28-35, MBM 70 £14-25.
Parabeams: PBM 12 £4-05, PBM 18 £5-15, Log-periodic £7-20.
Stereobeams: SBM 1 £2-65, SBM 2 £3-66, SBM 3 £5-30, SBM 4 £5-80, SBM 6 £8-75.
Masthead Amplifiers UHF or FM VHF £10-00, Setback £5-50.
We are stockists of AMTRON KITS and BIB ACCESSORIES.
VHF Co-ax 8p/m, Low Loss 12p/m.
Open Tuesday to Saturday 0900-1730.
79 Chatsworth Road, Chesterfield S40 2AP.

Situations Vacant

MEN! £70p.w. can be yours

Jobs galore? Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 + p.a.

You know you can rely on us as we are the only computer school recognised by the Government backed National Computing Centre.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators Training Centre

Y19, Oxford Hse.,

9-15 Oxford St. W1. Tel: 01-734 2874

Ladders

LADDERS, timber and aluminium. Tel: Telford 586644 for brochure.

Books and Publications

UFO CHARTS: Wave Prediction 54p; Daily Flight Pattern, 50p; Map, 50p; TV UFO Detection, 2 Optical Circuits, 63p; Propulsion Theory, 55p; "Anti-Gravity", 55p. Circuits: Transistor Optical Detector, 66p; Radiation/Optical, 44p; Microdetectors, memory, auto-record, 80p. Sighting Recorder, 55p. R. & E. Highlands, Needham, Suffolk.

Technical Books - Radio & Electronics

Handbook of Tested Transistor Circuits. £0-40
Audio Amplifiers £0-53
Boys Book of Crystal Sets & Simple Circuits £0-25
Television Timebase Circuits. £1-00
How to Solve Solid State Circuit Troubles. £1-75
How to get the best out of your Tape Recorder £1-50
Modern Electronic Troubleshooting £1-30
Jack Darr's Service Clinic. £1-35
Transistor Circuits for Modern Test Equipment. £0-60
Rad & Electr Colour Codes and Data Chart. £0-15
Handbk of Transistor Equiv. and Substitutes. £0-40
Hi Fi, PA & Disco Amplifier Design Handbk. £0-75
Radio Servicing Problems £0-60
Electronic Circuits for the Amat Photographer £0-60
Handbook of Simple Transistor Circuits £0-35
How to build Solid State Audio Circuits £1-75
Sound and Loudspeaker Manual £0-50
TV Technicians Bench Manual £2-50
Radio Amateur Operator's Handbook £0-70
Television Servicing Vol. No. 1. £0-85
Television Servicing Vol. No. 2. £1-10
Television Servicing Vol. No. 3. £0-60
Television Servicing Vol. No. 4. £0-85
Radio Technicians Bench Manual £3-00
Servicing Transistor Radio Receivers. £0-75
1st Book of Hi Fi Loudspeaker Enclosures £0-60
2nd Book of Hi Fi Loudspeaker Enclosures £0-60
Manual of Electronic Circuits for the Home. £0-50
Modern Crystal Set Circuits for Beginners. £0-35
Electronic Novelties for the Motorist. £0-50
2nd Book of Transistor Equiv. & Substitutes. £0-95
Handbook of Electronic Musical Novelties. £0-50
Transistorised Novelties for Hi Fi Enthusiast. £0-35
Fault Location Exercises in Rad. & TV Vol.1. £0-80
Fault Location Exercises in Rad. & TV Vol.2. £1-35
Colour TV Picture Faults. £2-50
Practical Transistor Novelty Circuits £0-40
Boys Book of Practical Radio & Electronics £0-60
Radio Receiver Construction using ICs & Transis. £0-60
ICs & Transistor Gadgets Construction Handbk. £0-60
Integrated Circuits Equiv. & Substitutes Hbk. £0-75

FREE! *****
* A Resistor Colour Code Calculator *
* (Invaluable to the keen radio constructor) *
* OFFERED FREE ON REQUEST FOR ORDERS £3 AND OVER *
* PLEASE ADD 10% FOR POSTAGE & PACKING *

RADIO BOOK SERVICE
40 Edwill Way, Beckenham BR3 2RZ

Miscellaneous

MINI ACCUMULATORS

2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.
Size L450-1.4" x 1.1" x .44". 3 for £1.50 inc. P. & P.
Size GA2-1.7" x 1.3" x .5". 3 for £1.95 inc. P. & P.
GARFIELDS, 269 Rye Lane, London, S.E.15

NEW YEAR BONANZA!

B.B. SUPPLIES offer:—
LEVER key switch, 4-pole, lock-off-lock, in black plastic stackable case app. 120mm x 120mm x 25mm. Brand new **75p**
PUSH button switching unit, 3 two-pole c/o units, one cancels others, room for one more unit. App. 75mm x 60mm x 35mm. Brand new (wired and numbered) **50p**
RELAY, 24 volt, 3600 ohms, 4 c/o contacts. Size: 40mm x 33mm x 15mm (wired and covered). Brand new **50p**
LAMP fitting, 6 volt—contained in hammer finished, grey steel box on wood plinth. Ideal case for small projects. Size app. 75mm x 75mm x 70mm. Brand new **50p**
SPECIAL price until 31-3-75 for all 4 above items + useful accessory. **£2-00**
4T S/energising earpieces (salvaged) **20p**
All prices include VAT and p. & p. Many other Govt. surplus, new and s/hand items at bargain prices, S.A.E. for New Year Catalogue of teletronic parts to:
38 HEATHWOOD GARDENS, SWANLEY, KENT BR8 7HN

LOW COST I.C. MOUNTING. Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each. (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

HEADPHONES: 8 ohms. Suitable communications receivers, £3-39. Partridge Electronics Ltd., Broadstairs, Kent.

BUILD THE TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete Kit £9.80 P & P 45p + 78p VAT

Built, tested and guaranteed £13.75 P & P 45p + £1.10 VAT

MINIKITS ELECTRONICS, 35a LANGLEY DRIVE, LONDON E11 2LN (Mail Order Only)

FLUORESCENT LIGHT KIT

12 v 8 w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied: the tube, white enamelled metalwork, first quality components, P.C.B., instructions, etc.

Price only £3-19 Inc VAT post & packing
 Ready built £3-78
 Diffuser only 59p extra

ALUMINIUM BOXES

Prices include lid, screws, and V.A.T. Post and packing 10p extra on all orders.

7	5 1/2"	by	2 1/2"	by	1 1/2"	high	39p
8	8	by	4"	by	1 1/2"	"	39p
9	4"	by	2 1/2"	by	1 1/2"	"	39p
10	5 1/2"	by	4"	by	1 1/2"	"	43p
11	4"	by	2 1/2"	by	2"	"	39p
12	3"	by	4"	by	1"	"	29p
13	6"	by	4"	by	2"	"	59p
14	7"	by	5"	by	2 1/2"	"	65p
15	8"	by	6"	by	3"	"	82p
16	10"	by	7"	by	3"	"	99p

Order now to—

ELECTRONICS DESIGN ASSOCIATES
 DEPT. PW
 82 Bath St., Walsall, WS1 3DE. Phone 33652

Hi-Fi Console

JUST SEND YOUR ADDRESS TO

Widens your STEREO S-P-A
 takes AUDIO UNITS Range of £8.95
 BOOKS & RECORDS Units

FREE COLOUR BROCHURE

Elegant **WHITE/TEAK MELAMINE**
 70 pounds of SOLID VALUE


WHITE illustr. £29.50 carr. 1.90

LEISURE TIME Dept. V, CROZIER Rd PLYMOUTH

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

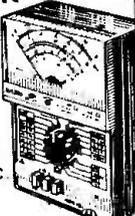A-DC 0-06-3A - 6 Ranges.
 A-AC 0-3-3A - 5 Ranges.
 V-DC 0-6-1200 V - 9 Ranges.
 V-AC 3-900 V - 8 Ranges.
 Freq.: In the range of 45 to 20kHz.
 Resistance: 500 Ohm to 5 MOhm - 5 Ranges, Decibel: -10 to +12dB.
 Accuracy: ± 2.5% DC, ± 4% AC.
 Dimensions: 167 x 98 x 63 mm.



Only **£8.85**

SUPERTESTER 680 R ICE

20,000 Ohm per Volt/sensitivity ● Fully screened against external magnetic fields ● Scale width and small case dimensions (128 x 95 x 32mm) ● Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading ● Simplicity and ease of use and readability ● Full ranges of accessories ● 1000 times overload ● Printed circuit board is removable without de-soldering ● More ranges than any other meter. Ask for free catalogue


£18.50

Accessories Extra

Accessories available to convert Supertester 680R into following: SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLTMETER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR - Send for details.

ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including ● 17v-21mA ● All d.c. operation ● Uniform, continuous line characters of equal height ● Memory with simple solid state drive circuits ● Readability in high ambient light... 200 footcandle brightness ● Long life with no loss of brightness ● Character height 2 1/2 in.

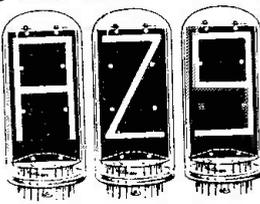

Price only **99p** each plus 16p P/P.
 Bases for above 50p each.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

ultra-long life, high quality, 0-9 & 2 independent decimal points. Supply voltage 200V D.C. Current 14mA, Pulse duration 100µs. Character height 0-51, overall size 1-4. Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853st

1-25 £1.00 25+ 90p 100+ 80p

1000+ price on application

Add 8% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.
 49-53 Pancras Road, London NW1 2QB
 Tel: 01-837 7781

ANTIQUÉ WIRELESS ENTHUSIASTS.

For all your requirements in radio, pre-1945, contact Tudor Rees's Antique Wireless Service. Retail shop now open at 64 Broad Street, Staple Hill, Bristol. Tel: 0272 565472.

BUILD THE STEREO FM TUNER

P.W. SANDOWN LOOK

- PCB & Cmpnts Inc. TR & BOX - £ 26.32
- Push Button Unit. 6 Position - £ 2.97
- METERS, Tuning & Level - each £ 1.50
- Subminiature Switches - set of 4 £ 2.62
- Cabinets & Front Panels - to order
- VAT INCLUSIVE PRICES P & P 25p

S.A.E. for further details

FW ELECTRONICS, 40 TUDENHAM RD, IPSWICH, SUFFOLK IP4 2SL Mail Order only

P.W. TENNIS KITS. All semiconductors (61 pieces) £13.50. Socket set (30 pieces) £3.50. Post free inclusive prices. **ISLAND DEVICES, PO BOX 11, Margate, Kent.**

GADGETS GALORE!!

Alarms - Test Gear - Musical Instruments
 Timers - Audio - Disco - Sound Effects

*** READY BUILT + TESTED ***

Sample prices: Signal Injector £1.95
 Signal Tracer £2.95

Prices include U.K. Postage and Batteries
 -Mail Order Only- S.A.E. list to:

G.K. SERVICES,
 83 Westdale Road, London SE18 3BQ

Synthesiser "Sounds Supreme" by Dewtron (VA extra.

Famous kits, e.g. waa-waa complete kit £3.50; Fuzz kit £5.50. P & P 25p under £10. Ring Modulator modules £9. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

PSYCHEDELICATESSEN

Is the only way to describe the *paradise* of Freaky gear now available from Boffin. Look!

KITS

No Licence Exam Transmitter/Receiver £6.90
 Variable-rate, Bright-Flash, Pocket Mini-Strobe £2.90

READY-MADE EXPERIMENTAL MODULES

Maxi-Volt Spark Generator (1/2 inch spark), 15,000 Volts! £1.90
 Mini Dream-Laboratory £3.20
 Sensitive non-anatomical electronic Stethoscope £3.20
 Electronic 'Voice-Thrower' £3.20
 Ghost-Hunting Aid £3.20
 People Detector £3.20
 Speak-Thru-Water-Fone £6.40
 Psychedelic Meditation Aid £3.20
 Bird-Watchers' Remote Monitor £3.20
 Psychological Cross-Eyed Ears Device £6.40
 'Big Ear' Sound-Catcher £3.20

(All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS
 4 Cunliffe Road, Stoneleigh Ewell, Surrey
 (Mail order U.K. only)

Or for more details, send 20p for lists, plus free design project sheet

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4 1/2 p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

12 VOLT 21" 13 Watt Fluorescent Lighting (by Thorn/AEI) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT

SALOP ELECTRONICS 23 Wyle Cop, Shrewsbury, Shropshire Tel. 53296

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronics and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Fast despatch! Free literature, Bazelli, Department No. 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

LOWEST COST IC SOCKETS. Use Soldercon IC socket pins for 8 to 40 pin DILs. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price). In strips of 100 pins: 100+ pins 70p, 300+ 50p, 1,000+ 40p. Instructions supplied. 10p p&p for orders under £2. Add 8% VAT. SINTEL, 53n Aston Street, Oxford.

PRINTED CIRCUIT MANUFACTURERS offer P.W. Project P.C.B.'s, 70p each. Also, Production, Design, Artwork, Photography, Electroplating, Screen-printing, Tinning. Undertaken. Estimates by return or phone W.K.F. Electronics, Welbeck St., Whitwell, Worksop, Notts. Tel. 695.

AERIAL WIRE. High quality PVC covered multi-strand copper, 50ft 60p (10p), 75ft 86p (13p), 100ft £1.19 (15p), 150ft £1.77 (24p), 200ft £2.36 (26p), 250ft £2.95 (28p), 300ft £3.54 (31p). Egg insulators 12p pair (6p). P&P in brackets. S.A.E. all enquiries. A.I. Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

AUDIOSCAN, the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send 7p in stamps for bargain list to: Audioscan, Dept. PW-8, 4 Princes Square, Harrogate, Yorks.

PRINTED CIRCUIT BOARDS. PCB from your patterns £1 plus 5p per square inch. From published patterns in this magazine 50p per board. Add VAT, 5p p&p per PCB. Mail order only. T.E.C. 241 Burnt-oak Broadway, Middlesex.

HAVE YOU HAD YOUR CHIPS? AY-5-1224 Digital Clock chip now £3.95 inc. VAT, post free. Circuit and details s.a.e. GREENBANK ELECTRONICS (Dept. 322), 94 New Chester Road, Wirral, Merseyside L62 5AG.

ALL PRICES INCLUDE VAT

AERIAL MAST POLES. Approx. 5ft. 2in. high, 2in. dia. Interlocking ends. Minimum order 3. As new £1.25 (each) P. & P. 40p each.

AERIALS. As new. Whip Type 11ft. £1 each Collapsible type. P. & P. 20p. New Bases. for the above 75p. P. & P. 30p.

PAIR OF 4 x 150A VALVES complete with bases ex-equip not tested. Good condition £3. P. & P. 30p.

BARGAIN PARCELS 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57p p.p.; 56lb at £4.95 plus £1.37½ p.p. Contains pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £2 post paid.

TRANSISTOR BOARDS—consisting of transistors, diodes and resistors, etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 30p. Quotations for quantity.

OUR SELECTION OF 6-EX. Equ. METERS consisting of 3in., 2½in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 30p. minimum order of six.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft £1, p. & p. 25p.

AERIAL POLES 4ft high 2in. in diameter push-in type as new £1 each p. & p. 25p each minimum four.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY.

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.
Radio Dept. High Street, Cheslyn Hay, Nr Walsall, Staffs.

SINCLAIR CALCULATORS



Cambridge Memory £20.95 (£1.95)
Cambridge Assembled £15.95 (£1.55)
Sinclair Scientific £22.45 (£2.05)
Executive with Memory £25.95 (£2.49)
Executive £22.75 (£2.25)

FERRANTI ZN414

IC radio chip with data £1.20 (22p). Also available kit of extra parts to complete a radio £2.45 (42p). Send sae for free leaflet.

SINCLAIR PROJECT 80

AFU £6.38 (73p)
Z40 £5.12 (63p)
Z60 £6.38 (73p)
Q16 £7.21 (80p)
PZ5 £5.11 (63p)
PZ6 £7.79 (84p)
PZ8 £7.36 (80p)
Decoder £7.75 (84p). Trans for PZ8 £3.85 (50p).
Tuner £11.62 (£1.37). Stereo 80 £11.62 (£1.37).
Project 805 £29.95 (£2.80).
Project 805SQ £33.95 (£3.10).




ECONOMICAL QUADRAPHONICS

Introducing the Napolex QA10 self contained matrix quadraphonic synthesizer. Just feed the output of any stereo system (including Project 80 or 80) into it and hook on 4 speakers to obtain the latest experience in sound. Send sae for free leaflet. Only £10.15 (£1.10).



SINCLAIR SUPER IC12

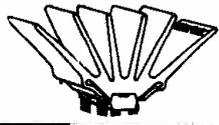6W rms power. With 44 page booklet and printed circuit £1.80 (40p).



NEW SINCLAIR IC20

High power IC audio amplifier £8.45 (£1.05).

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.70 (20p). Stereo model with balance control £3.70 (43p).

IC12 POWER KIT

Supplies 28V 0.5 Amps £2.97 (52p).

LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1.30 (29p). 5" x 8" 8 ohm £1.65 (37p).

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1.40 (25p). Stereo model £2.50 (33p). Type 2 for ceramic or crystal pickups. Mono 70p (19p). Stereo £1.40 (24p).

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAINS

The most versatile battery eliminator ever offered. Switched output of 3, 4½, 6, 7½, 9 and 12V at 500 mA £3.90 (70p).



Other eliminators stocked:—


250mA:—3 way switched model giving 6, 7½ and 9V £2.25 (55p).

50mA:— 4½V £1.95 (40p), 6V £1.95 (40p), 9V £1.95 (40p), 7½V cassette type £2.50 (40p), Double 4½V + 4½V £2.75 (43p), 6V + 6V £2.75 (43p), 9V + 9V £2.75 (43p).

500mA:— Heavy duty deluxe models 6V £2.78 (55p), 7½V £2.78 (55p), 9V £2.78 (55p).

S-DECS AND T-DECS

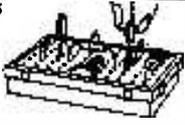S-DeC £1.98 (31p)
T-DeC £3.63 (47p)
U-DeC A £3.99 (51p)
U-DeC B £6.99 (81p)



IC carriers:—
16 dil: Plain 81p (15p) with socket £1.77 (25p)
10 TO5: plain 78p (15p). With socket £1.68 (24p).
Experiment guides:—A £1.50 (26p), B £1.77 (29p), C 90p (18p), D £2.40 (35p), E £4.20 (53p).

SWANLEY ELECTRONICS
PO BOX 68, SWANLEY,
KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and new VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back up service to ensure your success. VHF and UHF Modulator Kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes, special mains transformers and focus/scan coil assemblies, ready built cameras also available. Complete kits also available P.W. tele-tennis game. Send 5" x 7" S.A.E. for full details or come along for a demonstration and a chat with our technical staff.

GROFTON ELECTRONICS

124 Colne Road, Twickenham, Middlesex, TW2 6QS

Tel: 01-898-1569

Telex 934642 Cadanac LDN

BRIARWOOD TRADING CO.

161 Brownroyd Hill Road, Wibsey, Bradford.

Tel. Bradford (0274) 671960

Offer the following list of T.V. spares—

- Push button transistorised tuners**
- Philips UHF/VHF 210 series £7
- Philips single standard £7
- Philips G6 dual standard and single standard colour £7
- Pye/Echo, UHF/VHF £6
- Decca MS 1700 & DR 21, MS 2000 and MS 2400 £5
- GEC 4 & 6 button £4
- Bush D/S 6 button £6

ROTARY TRANSISTORISED TUNERS

- Pye/Echo D/S (as used in olympic and Europa chassis) £3.50
- (State whether cable or micro switch optional S/S)
- GEC 2010 series £3.50
- Decca DRI £3

Colour Panels for Spares & Parts

- Convergence S/S £2 & D/S £4
- TIB boards £1.75
- RGB boards £2
- LOPT boards £1
- S/F boards £1.45
- Pye 36 & Olympic I.F. panels £4

Trade sets available for personal callers. All prices include P. & P. and VAT.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER. CALLERS SATURDAYS ONLY

C.W.O. Please. P. & P. add 15p to orders under £3. Prices exclusive of VAT

All components brand new and fully guaranteed
(less 10% for 25+ of one type)

TRANSISTORS			TTL 74 SERIES		
AC107 16p	BCY42 28p	OC82 15p	2N1306 24p	7400 15p	7480 80p
AC125 13p	BCY43 25p	OC83 20p	2N1307 26p	7401 16p	7481 110p
AC126 13p	BCY58 18p	OC140 100p	2N1893 30p	7402 16p	7482 86p
AC127 13p	BCY59 18p	OC201 70p	2N1890 45p	7403 16p	7483 110p
AC128 14p	BCY70 15p	OC202 80p	2N2217 23p	7404 19p	7484 95p
AC176 14p	BCY71 18p	TIP29 43p	2N2303 25p	7405 19p	7485 187p
AC187 13p	BCY72 12p	TIP29A 45p	2N2483 30p	7406 39p	7486 36p
AC188 13p	BD131 40p	TIP30 48p	2N2894 30p	7407 39p	7487 155p
ACY17 35p	BD132 40p	TIP30A 54p	2N2906 15p	7408 21p	7489 360p
ACY19 25p	BD137 45p	TIP31 54p	2N2907 18p	7409 24p	7490 62p
ACY20 24p	BD145 55p	TIP32 64p	2N2926 .9p	7410 16p	7491 99p
ACY21 29p	BDY11 115p	TIP33 95p	2N3053 18p	7411 22p	7492 69p
ACY22 16p	BDY17 135p	TIP34 130p	2N3054 42p	7412 28p	7493 69p
AD140 48p	BDY18 125p	TIP41 65p	2N3055 45p	7413 28p	7494 90p
AD149 48p	BDY60 52p	TIP41A 68p	2N3614 59p	7414 60p	7495 80p
AD161 35p	BDY61 50p	TIP42 70p	2N3615 65p	7415 35p	7496 95p
AD162 35p	BF194 10p	TIP42A 74p	2N3702 12p	7417 35p	74104 53p
AF114 14p	BF195 10p	TIS43 26p	2N3703 12p	7420 16p	74105 53p
AF115 14p	BF196 12p	TIS44 17p	2N3704 12p	7422 24p	74107 43p
AF116 14p	BF197 15p	TIS45 50p	2N3705 12p	7423 38p	74110 56p
AF117 14p	BFX84 22p	TIS46 26p	2N3706 10p	7425 38p	74111 85p
AF118 40p	BFX86 21p	TIS60 16p	2N3707 10p	7426 28p	74118 90p
BC107 9p	BFX88 22p	TIS61 19p	2N3708 8p	7427 37p	74121 50p
BC108 9p	BFY50 16p	TIS62 28p	2N3709 8p	7428 39p	74122 50p
BC109 10p	BFY51 16p	TIS91 28p	2N3713 12p	7430 16p	74123 99p
BC147 10p	BFY52 16p	ZTX107 10p	2N3715 150p	7432 37p	74141 90p
BC148 10p	BFY53 17p	ZTX108 10p	2N3716 150p	7433 36p	74150 145p
BC149 10p	BFY55 35p	ZTX109 12p	2N3771 140p	7437 36p	74151 100p
BC157 13p	MJE370 63p	ZTX300 12p	2N3772 160p	7438 43p	74153 99p
BC158 11p	MJE371 78p	ZTX301 14p	2N3773 240p	7440 16p	74154 166p
BC159 13p	MJE520 62p	ZTX302 18p	2N3819 28p	7441 75p	74155 105p
BC167 12p	MPF102 30p	ZTX304 22p	2N3820 38p	7442 75p	74156 100p
BC168 12p	MPF103 30p	ZTX311 10p	2N3823 60p	7443 120p	74160 135p
BC169 12p	MPF104 28p	ZTX341 19p	2N3903 15p	7444 120p	74168 160p
BC170 11p	MPF105 36p	ZTX500 15p	2N3904 15p	7445 160p	74167 300p
BC171 11p	OC26 40p	ZTX502 18p	2N3905 17p	7446 189p	74174 160p
BC172 11p	OC28 58p	ZTX504 42p	2N3906 17p	7447 105p	74176 126p
BC177 16p	OC35 48p	ZTX531 23p	2N4037 35p	7448 118p	74180 126p
BC178 16p	OC36 52p	ZTX550 18p	2N4062 12p	7450 16p	74182 126p
BC179 18p	OC41 35p	2N706 11p	40311 34p	7451 16p	74184 180p
BC182 11p	OC42 35p	2N708 16p	40323 32p	7453 16p	74185 180p
BC183 11p	OC44 12p	2N1131 20p	40324 47p	7454 16p	74190 195p
BC184 11p	OC45 12p	2N1132 20p	40326 35p	7460 16p	74191 195p
BC212 13p	OC70 12p	2N1301 20p	40360 40p	7470 28p	74192 200p
BC213 13p	OC71 12p	2N1302 20p	40361 45p	7472 28p	74193 200p
BC214 13p	OC72 12p	2N1303 20p	40362 39p	7473 37p	74194 139p
BCY39 99p	OC74 28p	2N1304 24p	40407 32p	7474 37p	74198 270p
BCY40 80p	OC81 12p	2N1305 24p		7475 35p	74198 270p
				7476 37p	74199 270p

LINEAR IC'S	DIODES	BRIDGE RECTIFIERS	TRIACS
MC1304P 169p	AA120 10p	400V 3A 85p	400V 3A 120p
MC1310P 275p	BY100 18p	(Plastic Case)	500V 6A 120p
MC1710CG 60p	BY164 35p	1A 50V 20p	500V 6A 150p
729C DIL/TO99 35p	BY211 25p	1A 400V 23p	400V 10A 145p
742C DIL/TO99 75p	NE562 FM Syn 35p	1A 600V 25p	500V 10A 180p
741C 8pin DIL 32p	PA263 150p	OA5 39p	
" 14pin DIL/TO99 38p	PA263 445p	OA9 9p	
747C 14pin DIL 80p	SL403D 150p	OA79 10p	
748C 8pin DIL 40p	SL414A 165p	OA81 8p	
ML91 1p	TAD100 AM 150p	OA85 10p	
7805 (TO3) 1.60	TBA800 5W AUD. 135p	OA90 6p	
CA3018 72p	ZN414 115p	OA91 6p	
CA3020 140p		OA200 6p	
CA3035 135p		OA201 6p	
CA3036 90p		PL4001 6p	
CA3046 70p		PL4004 8p	
CA3048 210p		PL4007 12p	
CA3050 135p		IN914 5p	
CA3075 150p		1N4001/2 5p	
CA3081 150p		1N4003 6p	
CA3089E 195p		1N4004/5 6p	
CA3099Q 345p		1N4006/7 7p	
LM300 TO99 170p		1N4148 5p	
LM304 TO99 170p			
LM305 TO99 170p			
MC724P 50p			
MC1303L 130p			

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F).
400V: 0.001, 0.0012, 0.0015, 0.0018, 0.0022, 0.0033, 0.0047, 0.0068, 0.01, 0.015, 0.022, 3p; 0.047, 0.068, 0.1, 4p; 0.15, 0.22, 7p; 0.33, 10p; 0.47, 13p; 100V: 0.1, 0.15, 4p; 0.22, 5p; 0.33, 6p; 0.47, 9p; 0.68, 10p; 1.0, 13p. 250V: 0.22, 6p; 0.33, 8p; 0.47, 9p; 0.68, 12p; 0.47, 9p; 2.2, 18p.
RADIAL LEAD P.C. TYPE (Values are in μ F).
250V: 0.01, 0.015, 0.022, 3p; 0.033, 0.047, 0.068, 3.3p; 0.1, 4p; 0.15, 4p; 0.22, 0.33, 5p; 0.47, 7p; 0.68, 10p; 1.0, 11p; 1.8, 20p; 2.2, 22p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F).
63V: 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 20, 22, 47, 68, 8p each, 100, 12p. 40V: 100, 6p. 30V: 350, 35p. 25V: 68, 6p; 150, 6p; 220, 11p; 470, 13p. 25V: 680, 18p; 1000, 24p; 2200, 34p; 3000, 39p. 16V: 40, 125, 250, 6p. 10V: 1000, 1500, 16p. 10V: 4, 100, 5p; 640, 10p; 1000, 14p; 2200, 18p.

CERAMIC CAPACITORS
50V d.c. Plaquette body 25mm leads.
Range: 5pf-10,000pf price 2p each.
0.015 μ F, 0.022 μ F, 0.033 μ F, 0.047 μ F 3p

MYLAR FILM CAPACITORS
100V: 0.001 μ F, 0.002 μ F, 0.005 μ F, 0.01 μ F
0.02 μ F, 0.04 μ F, 0.05 μ F 3p. 0.1 μ F, 0.2 μ F.
50V, 0.47 μ F 6p.

POTENTIOMETERS (AB) Carbon
Track, 0.25W Log & 0.5W Linear values
1K Ω -2M Ω single gang 14p
5K Ω -2M Ω single gang D/P switch 28p
2K Ω -2M Ω dual gang stereo 42p

PRESET POTENTIOMETERS
0.25V: 100 Ω -1M Ω Horizontal 6p
1K-1M Ω Vertical 6p
0.1W: 50 Ω -1M Ω Vertical 4p

SLIDER POTENTIOMETERS
0.25W log and linear values
5K Ω -500K Ω single gang 35p
10K-500Kohm Dual gang 50p
KNOBs for above Black or Silvered 8p

RESISTORS High Stability Low noise
Pr. Type Tol. Range Val. 1-49 50+
1W C 5% 2.2 Ω -10M E24 1p 8p
1W C 5% 2.2 Ω -10M E12 1p 8p
1W C 5% 2.2 Ω -10M E12 2.5p 2p
4W WW 10% 1 Ω -100 Ω E12 8p —

	JACK PLUGS & SOCKETS			
	Screened chrome	Plastic Body	Open metal	Moulded with break contacts
2.5mm	10p	8p	8p	
3.5mm	14p	8p	8p	
Standard mono	17p	13p	13p	17p
Standard stereo	30p	18p	15p	2.5

	PLUGS	SKCTS.	CPLRS.	DIL SOCKETS
DIN	12p	8p	15p	8 Pin 14p
2 Pin-6 Pin				14 Pin 15p
				16 Pin 16p
CO-AXIAL (TV)	10p	8p	15p (f.f.)	CAR AERIAL PLUGS 10p
PHONO assorted colours	6p	5p (sgl.) 7p (dbl.) 10p (trpl.)	8p	CHOKES (RFC) 15p each
BANANA	6p	5p		

SWITCHES
TOGGLE: SPST 18p
DPDT 22p
SLIDE: 1A DP 250V 19p
1/2A DP 250V 9p
PUSH BUTTON: Miniature push to make or break nonlocking 15p
ROCKER (white): 5A 250V SP changeover 25p
centre off
ROTARY WAFER: 1 pole/12 way, 2p/6w, 2p/2w, 2p/4w, 3p/3w, 3p/4w, 4p/2w, 4p/3w, 24p

TRANSFORMERS
Primary 220V-240V
6.0-6 (miniature) 100mA 90p
9.0-9 " 100mA 90p
12.0-12 " 100mA 90p
18.0-18 also 24V 100mA 90p
24.0-24 " 500mA 220p
30-24-20-15-12-0 1A 230p
9-0 2A 110p
8-0 2A 110p
5-0 2A 110p

LAMP HOLDERS/LAMPS
LES HOLDERS Dome top, Red, Blue, Green/Yellow/White, 3/4" hole 14p
Les Bulbs 6v and 12v 6p
MES Holder, Heavy duty, round top Red, requires 3/4" hole 25p
NEON, 240V RES round top 3/4" hole 25p
NEON, As above but with 1/2" square RED top 25p
NEON, As above but with 1/2" square green top 25p

ALUM. BOXES
2.2x5.4x1.1" 45p
4x4x1.1" 45p
4x2.2x1.1" 45p
4x2.2x2.2" 48p
3x2x1" 38p
7x5x2.2" 78p
3x1x1" 8p
10x7x3" 99p
10x4x3" 118p
10x4x3" 99p
12x5x3" 120p
12x8x3" 150p

VEROBOARD
Pitch 0.1 0.15 0.15 (copper clad) (plain)
2.2x3.3" 30p 32p 32p
2.2x5" 32p 32p 32p
3.2x5" 38p 38p 38p
2.2x1.7" 98p 75p 55p
3.2x1.7" 130p 105p 78p
4.2x1.7" 173p 105p 105p
Pkt of 36 pins 20p
Spot face cutter 49p
Pin Insertion tool 68p

FELSTEAD

HAVE REDUCED ALL PRICES FOR THE XMAS SEASON TO HELP FIGHT INFLATION!

ALL prices in our current list (sent immediately for S.A.E.) and advertised in this magazine's December issue reduced by 10% FROM NOW UNTIL JANUARY 11th ONLY

Orders received by us on and after JAN. 13th must revert to our very reasonable prices as per our NOV. 1974 and/or FEB. 1975 advertisements in this journal, and our current list. (This special offer cannot cover charges which are not under our control.) Regret not applicable overseas.

MAKE SURE YOUR PLAYER HAS A NEW CARTRIDGE and/or STYLUS (our offer includes All Diamond and Sapphire Styli, English, Continental and JAP. Offer also includes RECORDING TAPE, SPEAKERS, HEADPHONES, MIKES, CASSETTES, PLUGS, SOCKETS, LEADS, MAINS UNITS, TRANSISTORS, SWITCHES, VOL. CONTROLS, CON. WIRE, etc., and many other Hi-Fi components and accessories.

Send S.A.E. NOW for free, up-to-date LIST by return to—

FELSTEAD ELECTRONICS (PW87), LONGLEY LAKE, GATLEY, CHEADLE, CHESHIRE SK8 4EE

PUBLISHER'S ANNOUNCEMENT


Due to production difficulties existing at the time this issue went to press, we strongly advise readers to check with advertisers the prices shown, and availability of goods, before purchasing.

LISTEN TO

CODAR®

THE WORLD!

★ **CR70A**

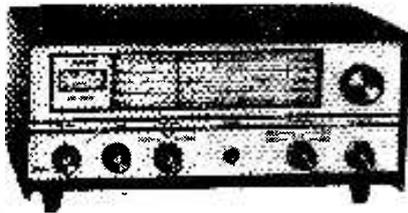

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning. Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your order receipt, sent by return.



ON THE DESIGN STAFF—
G3SZM G3IRE


CODAR®

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

THE WORLD!

★ **P.R.40** ★

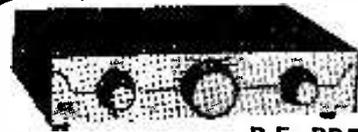

£10-93!
VAT PAID
CARR. 32p
R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee . . .



★ **MULTIBAND-6** ★
SHORT WAVE RECEIVER KIT
£16-90! CARR. 43p

All transistor T.L.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual. Fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST

TELECOMMUNICATIONS AND ELECTRONIC
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS
GOVERNMENTS

BN15 - 8TZ

INDEX TO ADVERTISERS

Allard Electronics	862
Ambit International	838
Arrow Electronics	861
A.S.P. Ltd.	816
B.B. Supplies	863
Barrie Electronics	841
Bentley Acoustics	858
Beta Devices	862
B.H. Component Factors Ltd.	794
Bib Hi-Fi Accessories Ltd.	787
Bi-Pak Semiconductors	796-797
Bi-Pre Pak Ltd.	845, 852
Boffin Projects	864
Briarwood Trading	865
British Institute of Engineering Technology	792, 833, cover iii
British National Radio & Electronics School	787, 811, 856
Bull, J. (Electrical) Ltd.	859
Castle Acoustics Ltd.	852
Chiltmead Ltd.	856
Chromasonics Electronics	854-855
Codar	867
Colomol (Electronics) Ltd.	868
Crescent Radio Ltd.	783
Crofton Electronics	865
C.T. Electronics	849
Dabar Electronic Products	780, 856
D.E.W. Ltd.	864
Doram Electronics Ltd.	807
Electronics Brokers Ltd.	864
Electronic Design Assoc.	846, 868
Electronic Mail Order Ltd.	816
Electrospares	860
Electro-Tech	820
Electrovalue Ltd.	842
E.T.E.H.	782

Felstead Electronics	866
Flairline Supplies	794
F.V. Electronics	864
Galleon Trading Co.	862
Garfields	863
G.K. Electronics	864
Global Audio	846
Goldring	792
Greenweld Electronics	792
H.A.C. (Shortwave) Products	838
Harverson Surplus Co. Ltd.	793
Heath (Gloucester) Ltd.	841
Henry's Radio Ltd.	819, cover iv
Home Radio Components	815
I.L.P. (Electronics) Ltd.	795
Imperial Trading (Aerials) Ltd.	863
Johnsons (Radio)	862
Kensington Supplies	863
Keytronics	838
Leisure Time Ltd.	864
Lewis Radio	782
Linear Products Ltd.	820
Logic Leisure Ltd.	780
London Computer Operators Training Centre	863
Maplin Electronic Supplies	781
Marco Trading	862
Marshall, A.	860
Milward, G. F.	788
Minikits Electronics	864

Newmart Electronics	837
Newnes-Butterworth	780
Partridge Electronics Ltd.	853
Radio Book Services	863
Radio Component Specialists	857
Radio Exchange Ltd.	cover ii
Radio Shop, The	782
Radio Society of Great Britain	848
R.C.S. Products Ltd.	838
RSC (Hi-Fi) Centre Ltd.	778-779
RST Valve Mail Order Co.	786
R & TV Components Ltd.	784-785
Riversdale Electronics	833
Salop Electronics	864
Saxon Entertainments Ltd.	789
Shoptunities Ltd.	858
Sinclair (Cambridge) Ltd.	826-827
Sinclair Radionics Ltd.	850-851
Sound Systems of Suffolk	862
Surpletronics	812
Swanley Electronics	865
Technomatic Ltd.	787
Teleradio Electronics	862
Thacker, A. H.	865
Trampus Electronics Ltd.	788
Trannies Ltd.	834
Tuac Ltd.	790-791
Tweedy, Ltd. (J. A.)	863
Watford Electronics	866
West London Direct Supplies	838
Web Europa Ltd.	816
Wilmslow Audio	812
Xeroza Radio	794
Z & I Aero Services	868


Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 0.15 in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

AC/DC MULTIMETER TYPE U4324

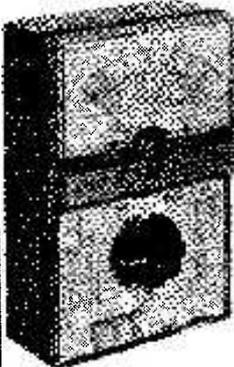

33 ranges up to
3 Amps AC/DC;
1200V DC, 900V
AC, 500kΩ, +12
db.

Sensitivity:
20kΩ/V DC;
4kΩ/V AC

Accuracy:
±2.5% DC;
±4% AC

Movement is protected by silicon diodes.

Dimensions 167×98×63 mm. Weight: 1.5lb.

PRICE: complete with test leads, instruction manual and fibre-board storage case £9.25. Packing & carr. £0.50.

MULTIMETER TYPE U4323

Sensitivity: 20,000Ω/V.




7 D.C. Voltage ranges 0.5-1000V
6 A.C. Voltage ranges 2.5-1000V
5 D.C. Current ranges 0.05-500mA

4 Resistance ranges 1kΩ-1mΩ
Built-in oscillator providing AF output of 1kHz and I.F. output of 465kHz with an amplitude of 1 volt minimum.

Dimensions: 140×87×40 mm. Weight 0.5kg

PRICE complete with leads and plastic storage case £7.70. Packing & postage £0.50

AC/DC MULTIMETER TYPE U4313

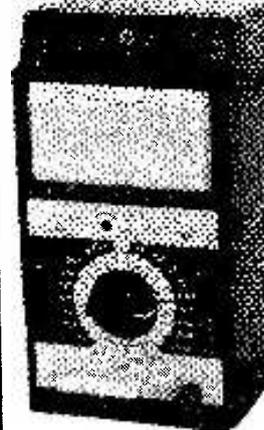

39 ranges:
600μA to 1.5A
AC
60μA to 1.5A DC
75mV to 600V
DC

1.5V to 600V AC
1MΩ, 0.5μF, 12db

Accuracy: 1.5%
DC; 2.5% AC

Sensitivity: 20k
Ω/V DC; 2kΩ/V
AC

Mirror scale 86mm long.

Dimensions: 115×215×90 mm, Weight 3.3lb.

PRICE, complete with test leads, service manual and steel carrying case £12.50. Packing & carriage £0.50.

ALL THE ABOVE INSTRUMENTS FEATURE TAUT SUSPENSION MOVEMENTS
PRICES ARE EXCLUSIVE OF V.A.T.

Fully guaranteed Individually packed VALVES

A1065	£1.25	ECL80	55p	GZ34	70p	PY80	40p
ARS	55p	ECL82	35p	GZ37	£1.00	PY81	40p
ATP4	50p	ECL83	70p	KT66	£2.50	PY82	40p
B12H	£3.00	ECL86	45p	KT88	£3.00	PY83	40p
CY31	50p	EF36	65p	MH4	75p	PY88	45p
DAF96	50p	EF37A		ML6	65p	PY500	£1.00
DF96	50p		£1.20	OA2	45p	PY800	45p
DK96	70p	EF40	75p	OB2	45p	PY801	50p
DL92	40p	EF41	65p	PABC80	40p	QQV03-10	
DL96	60p	EF80	30p	PC97	50p	QQV06-40A	£1.40
DY86/87		EF83	£1.25	PC900	50p	QQV08-12	£8.00
DY802	40p	EF86	35p	PC884	40p	QV08-12	£1.10
E88CC/01		EF89	30p	PC885	40p	R19	60p
	£1.80	EF91	45p	PC889	50p	SCI/400	£3.00
E180CC	70p	EF92	50p	PC189	60p	SCI/600	£5.00
E182CC		EF95	40p	PC878	40p	SP61	75p
EA50	£1.95	EF183	35p	PCF82	40p	TT21	£5.00
EABC90	40p	EF184	35p	PCF84	60p	U25	85p
EAF42	70p	EFL200	75p	PCF86	60p	U26	75p
EB91	25p	EFL32	£2.50	PCF200	75p	U27	65p
EBC33	£1.00	EL34	70p	PCP201	75p	U191	75p
EBC41	70p	EL36	60p	PCP801	55p	U801	75p
EBF80	40p	EL37	£1.80	PCF802	50p	UABC80	
EBF83	50p	EL41	30p	PCF805	90p	UAF42	40p
EBF89	35p	EL82	55p	PCF806	75p	UBC41	60p
EC52	35p	EL84	30p	PCF808	90p	UBF80	40p
ECC81	40p	EL85	60p	PCF808	90p	UBF89	40p
ECC82	35p	EL86	45p	PCF82	40p	UBL1	£1.00
ECC83	35p	EL90	45p	PCL83	65p	UBL21	70p
ECC84	35p	EL504	80p	PCL84	45p	UCB85	45p
ECC85	40p	EM301	60p	PCL86	50p	UCH42	75p
ECC86	90p	EM80	55p	PCF805	60p	UCH81	45p
ECC87	50p	EM84	70p	PFL200	70p	UCL82	45p
EC0189	70p	EMS7	£1.00	PL36	60p	UCL83	65p
ECF80	40p	EV51	45p	PL81	50p	UF41	75p
ECF82	40p	EV781	45p	PL82	45p	UF80	30p
ECF801	75p	EV786	40p	PL84	45p		
ECH35		EV788	50p	PL85	45p		
	£1.40	EZ40	70p	PL504	80p		
ECH42	80p	EZ41	75p	PL608	£1.00		
ECH81	35p	EZ80	30p	PL509	£1.85		
ECH83	45p	EZ81	30p	PL802	85p		
ECH84	45p	GY501	75p	PY33	60p		

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

TRANSISTORS, DIODES etc.

AC 113	AF 139	BSY 27	OA 202	OC 200	2N 3053
AC 126	AF 178	BSY 38	OA 200	OC 206	2N 3054
AC 127	AF 186	BSY 90A	OC 22	OC 25	2N 3055
AC 128	AFZ 12	BYZ 16	OC 25	OC 25	2N 3390
AC 176	ASY 26	CRS 1/10	OC 26	OC 26	ZR 21
AC 18	ASY 27	CRS 1/20	OC 28	1N 23A	2N 3391
AC 19	ASY 28	CRS 1/30	OC 29	1N 25	2N 3730
AC 20	BC 108	CRS 1/40	OC 35	1N 32A	2N 3731
AC 28	BC 118	CRS 3/10	OC 36	1N 38A	2N 3819
AC 39	BC 119	CRS 3/20	OC 42	1N 43	2N 4038
AC 40	BC 136	CRS 3/30	OC 44	1N 70	2N 4058
AD 149	BC 137	CRS 3/40	OC 45	1N 877	2N 4061
AD 161	BC 148A	CRS 25/C25	OC 70	1N 415C	2N 4785
AD 162	BC 172	GET 115	OC 78	1N 4148	2N 5285
ADZ 11	BC 172A	GET 116	OC 78	3N 128	3N 128
ADZ 12	BC 212A	GEX 46	OC 78D	3N 154	3N 154
AF 114	BCY 31	NKT 222	OC 81	3N 159	3N 159
AF 115	BCY 33	OA 5	OC 82	2N 918	2S 803
AF 116	BCY 72	OA 7	OC 82D	2N 1304	404
AF 117	BF 115	OA 70	OC 82DM	2N 1305	2082
AF 118	BF 167	OA 71	OC 83	2N 1307	40250
AF 124	BF 185	OA 73	OC 139	2N 1309	40251
AF 125	BFY 51	OA 79	OC 140	2N 2062	0668
AF 126	BFY 52	OA 91	OC 170	2N 2147	
AF 127	BFY 90	OA 200	OC 172	2N 2411	
				2N 2989	

—V.A.T.—
Please add 8%
to all orders

UF85	45p	1R5	40p	6BG6G	90p	6H6	35p
UF89	50p	1S4	30p	6B76	65p	6J4WA	
UL41	70p	1T4	30p	6BQ7A	60p		£1.25
UL84	40p	1X2A	60p	6BR7	£1.20	6J5	85p
UY41	45p	1X28	75p	6BW6	£1.00	6J5GT	50p
UY85	40p	2D21	50p	6BW7	£1.00	6J6	30p
VR105/30	45p	3A4	60p	6C4	40p	6J7	80p
VR150/30	45p	3D6	40p	6C6	50p	6J7G	40p
X61M	£1.40	3V4	85p	6CB6	50p	6K6GT	30p
X66	65p	58/254M	£4.00	6CCL6	£1.45	6K7	50p
Z800V	£2.70	5B255M	£8.50	6D6	55p	6K7G	30p
Z801U	£2.70	5R4GY	90p	6EA8	85p	6K8GT	50p
Z900T	£1.20	5U4G	45p	6EAS	75p	6K25	£1.00
LA3	55p	5V4G	55p	6F7	£1.10	6L6	£1.25
LL4	25p	6A8	45p	6F8G	75p	6L6G	40p
		6AK5	25p	6F23	90p	6L7G	40p
		6AL5W	55p	6F32	75p	6SA7	50p
		6AM6	45p	6EA6	30p	6SA7	50p
		6AN8	45p	6BE6	35p	6SA7GT	40p

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME.
OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K.
Postage Up to £2 12p. £2-£3 22p. Over £3 post free. C.O.D. 25p extra.

29/41FT. AERIALS each consisting of ten 3ft., 7in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag. £7.50 new £4.50 slightly used. Carriage £1.50.



ALL valves
guaranteed

68C7GT	40p	20P4	£1.10	6060	70p	
68G7	50p	25L6GT	70p	6064	60p	
68J7	55p	30C15	£1.00	6065	£1.00	
68J7GT	35p	30C17	£1.00	6067	70p	
68K7	55p	30C18	90p	6080	£2.30	
68L7GT	50p	30P5	£1.00	6146	£2.25	
68N7GT	50p	30P11	£1.00	6146B	£3.25	
68Q7	55p	30P12	80p	6220	£5.00	
6V6G	15p	30P14	90p	9001	£5.00	
6V8GT	50p	30FL14	90p	9002	50p	
6X4	40p	30L15	95p	9003	70p	
6X5G	40p	30L17	95p	9004	35p	
6X5GT	50p	30P19	£1.00	9006	£3.50	
6Y8G	90p	30P19	£1.00			
6Z4	65p	30PL1	95p			
6-30L2	90p	30PL13				
7B7	80p	30P14	£1.10	DG7-5		
7Y4	80p	30P14	£1.10	DG13-2		
9D8	40p	35L6GT	75p	DG13-2		
11E2	£6.00	35W4	50p	MW13-35		
12A6	55p	35Z4GT	70p	50C15-60		
12A7	45p	50C25	60p	VCR139A		
12A7T	40p	50C26G				
12A7U	85p					
12AV6	50p	75	£1.00	3EP1	£4.50	
12AX7	35p	75C1	75p	88D	£9.00	
12BA6	45p	76	75p	88J	£8.00	
12BE6	50p	78	70p	88L	£9.00	
12BH7	50p	80	75p			
12C8	55p	85A2	75p	Special		
12E1	£3.80	733a/b	£8.00	Valves		
12K5	£1.10	803	£8.00	CV239		
12K7GT	50p	805	£14.00			
12K8GT	70p	807	65p			
12Q7GT	70p	813	£6.50	M503-2742	£45.00	
12SA7GT	80p	836A	£1.20		£42.00	
		70P	931A	£6.00	K301	£7.00
		75P	931A	£6.00	KRN2A	
		55P	954	50p		£6.00
		55P	955	50p		
		40P	956	50p	OY4-250	
		£1.00	957	50p		£19.00
		65p	1305	20p	TY4-500	
		£8.00	1629	70p		£30.00
		£6.00	2051	£1.00	725A	£23.00
		£14.00	5933	£8.00	2J/192	
		60p	6057	75p		£140.00

VALVES AND TRANSISTORS
Telephone enquiries for valves,
transistors, etc. retail 749 3934;
trade and export 743 0899.

Colomar (Electronics) Ltd.
170 GOLDHAWK ROAD, LONDON W12.
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

FREE!

Over 150 ways to engineer a better future



HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course".
Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.

"My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to

ALDERMASTON COLLEGE

Dept. TPW01, Reading RG7 4PF.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

MECHANICAL

- Society of Engineers—
- A.M.S.E. (Mech)
- Institute of Engineer & Technicians (A.M.I.E.)
- CITY & GUILDS**
- Gen. Mech. Eng.
- Maintenance Eng.
- Welding
- Gen. Diesel Eng.
- Sheet Metal Work
- Eng. Inspection
- Eng. Metallurgy

ELECTRICAL & ELECTRONIC CITY & GUILDS

- Gen. Electrical Engineering
- Electrical Installations
- Electrical Maths
- Computer Electronics
- Electronic Eng.
- Practical Radio & Electronics (with kit)

MANAGEMENT & PRODUCTION

- Institute of Cost & Management Acctns.
- Computer Programming
- Works M'tment
- Work Study
- Gen. Production Eng.
- Estimating & Planning
- Storekeeping Management
- Skills
- Quality Control

DRAUGHTSMANSHIP

- Institute of Engineering Designers (A.M.I.E.D.)
- General Draughtsmanship
- Elec. Draughtsmanship
- Architectural Draughtsmanship
- Technical Drawing

RADIO & TELECOMMUNICATIONS

- City & Guilds Telecoms.
- Gen. Radio & TV Eng.
- Radio Amateurs Exam
- Radio Servicing

AUTOMOBILE & AERONAUTICAL

- Institute of the Motor Industry
- A.M.I.I.
- MAA/IMI
- City & Guilds Auto Eng.
- Gen. Auto Eng.
- Motor Mechanics
- Auto Diesel Eng.
- Garage M'tment
- AEC Aero
- Engineering Exams
- Gen. Aero Eng.

CONSTRUCTIONAL

- Institute of Building L.I.O.B.
- A.B.T. Clerk of Works

- Construction Surveyors Institute L.C.S.I.
- City & Guilds General Building (all branches)
- Heating & Vent.
- Inst. Clerk of Works
- Site Surveying
- Health Engineering
- Road Construction
- Quantities
- Estimates
- Hydraulics
- Structural Eng.

GENERAL

- Agricultural Eng.
- Council of Eng. Institutions
- Farm Science
- Plastics
- Supplementary courses for Nat. Certificates.

G.C.E.
—choose from 58 'O' & 'A' level subjects

Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To **Aldermaston College,**
Dept. TPW01, Reading RG7 4PF.

NAME.....
Block capitals please
ADDRESS.....
.....
..... POSTCODE.....
OTHER SUBJECTS.....
..... AGE.....

Accredited by C.A.C.C.

Member of A.B.C.C.


Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Publisher's subscription rate (including postage): for one year UK £3.25, Overseas \$4.35. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's SO MUCH MORE - AND YOU PAY LESS VAT WITH HENRY'S LOW PRICES

FREE STOCK LISTS
 No. 36 Transistors /valves/ semi-conductors
 No. 18 Disco-lighting-high power sound
 No. 17 Hi-Fi TV-Tape Equipment
 Send large stamped addressed envelope with all enquiries.

You can build the Texan and Stereo FM Tuner TEKAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardners low field transformer, 6-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and, P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2" x 2 3/4" x 6 3/8" mains operated. Free teak sleeve with every kit. **£31.00 (GB post paid).** (also built and tested £37.50)

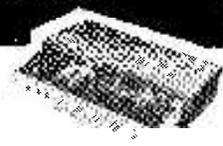

STEREO FM TUNER Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 2 3/4" x 6 3/8". Complete kit with teak sleeve **£21.00 (GB post paid).** (also built and tested £24.95)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

POWER SUPPLIES MAINS INPUT (* chassis-rest cased)

470C 6/7 1/2 9V 300 MA with ad'rs	2.25	*PI081 45V 0.9A	7.80
P500 9 volt 500 MA	3.20	PI2 4 1/2 12V. 0.4-1 amp	7.15
HC244R 3/6/7 1/2 9V. 400 MA		SE101A 3/6/9/12V. 1 amp stabilised	
stabilised	5.50	PI076 3/4 3/6/7 1/2 9/12V. 1/2 amp	4.20
*PI1 24v. 1/2 amp. 3.30	3.30	SE800A 1-15 VOLT 0.2A stabilised	17.50
*PI5 28V. 1/2 amp	3.30		
*PI080 12V 1A 4.70	7.80		

SINCLAIR MODULES & KITS

SINCLAIR PROJECT 80			
ST80 Stereo preamplifier	11.95	FM TUNER	11.95
Audio Filter Unit	6.95	STEREO DECODER	7.95
Z40 15 Watt Amplifier	5.45	IC20 power amp kit	7.95
Z60 25 Watt Amplifier	6.95	PZ20 power supply for 1 or 2 IC20	5.45
PZ5 Power Supplies	4.98	PACKAGE DEALS (carr./packg 35p)	
PZ6 Power Supplies (S Ta3) for 1 or 2 Z40	7.98	2 x Z40 ST80 PZ5	25.00
PZ8 Power Supplies (S Ta3) for 1 or 2 Z60	7.98	2 x Z60 ST80 PZ6	27.75
TRANSFORMER FOR PZ8	3.95	2 x Z60 ST80 PZ8-trans	34.40

SINCLAIR SPECIAL PURCHASES

*Project 60 stereo preamp	£6.75 (post 20p)
*Project 605 Kit	£19.95 (post 25p)
IC 12.6W amp	£12.10 (post 15p)
Cambridge Calculator kit	£13.50 (post 15p)
Sinclair Cambridge Memory	£22.50
Cambridge Calculator built	£17.50 (post 15p)
Cambridge Scientific built	£26.95 (post 15p)

FM MODULES

Mullard LP 1186 FM tuner (front end) with data 10.7 MHZ O/P	4.85
Mullard LP 1185 10.7 MHZ IF unit with data	4.50
Gorler Permability FM tuner (front end) 10.7 MHZ O/P	4.20

FM AND AM TUNERS AND DECODERS

FM5231 (tu 2) 6 volt fm tuner	7.95	All models fitted dials supplied with instructions
TU3 12 volt version (FM use with Decoder)	7.95	
SD4912 Stereo Decoder for Tu 3.12 volt	7.95	
	11.95	
SP62h 6 volt stereo FM tuner	4.80	
A1007 9 volt MW-AM tuner	11.95	
Sinclair 12/45 volt FM tuner stereo recorder for above	7.45	
A1018 9 volt FM tuner in cabinet	13.95	
A1005M (S) 9-12 volt Stereo decoder FM for above	6.50	
106Z 12 volt Stereo decoder general purpose	7.50	

PREAMPLIFIERS

Sinclair Stereo 60 Preamplifier with controls	6.75
E1300 Cart/Tape/Mic inputs 9 volt Module	2.85
E1310 Stereo 3-30 mV mal cart 9 volt	4.75
FF3 Stereo 3 mV tape head 9 volt	4.95
3042 Stereo 5-20 mV Mag. cart. mains	5.95
EQ25 Mono 3-250 mV Tape/Cart/Play 9 volt	5.95

TRANSISTORISED MODULES

Tuners - Power Suppliers - Amplifiers	
AMPLIFIERS (All single channel unless stated)	£ p
4-300 9 volt 300 MW O/P 3-8 OHM, 1-10 MV I/P Special Offer	1.75
2004 9 volt 250 MW O/P 3-8 OHM, 10-100MV I/P	2.70
104 9 volt 1 watt O/P 8-16 OHM, 10 MV I/P	3.10
304 9 volt 3 watt O/P 4-8 OHM, 10 MV I/P	3.95
555 12 volt 3 watt O/P 8-16 OHM, 150 MV I/P	4.10
555ST 12 volt 1 1/2 + 1 1/2 watt O/P 8 OHM, 150 MV I/P Stereo module	5.95
E1208 12 volt 5 watt O/P 4-16 OHM, 25-60 MV I/P	5.10
608 24 volt 10 watt O/P 4-8 OHM, 30-50 MV I/P	4.95
410 28 volt 10 watt O/P 8 OHM, 160 MV I/P	4.95
620 45 volt 30 watt O/P 4-8 OHM, 150 MV I/P	9.95
Z40 30/35 volt 15 watt O/P 4-8 OHM, 100 MV I/P	5.45
Z60 45/50 volt 25 watt O/P 4-8 OHM, 100-250 MV I/P	6.95
SA6817 24 volt 6 + 6 O/P 8 OHM 100 MV I/P Stereo module	10.20

EMI SPEAKERS SPECIAL PURCHASE

13 in x 8 in chassis speakers (Carr./packing 30p each or 50p pr.)
 *150 TC 10 watts 8 ohms twin cone £2.20
 *450 10 watts 4, 8, 15 ohm with twin tweeters and crossover £3.85 each
 EW 15 watt 8 ohm with tweeter £5.25
 350 20 watt 8, 15 ohm with tweeter £7.80 ea.
 * Polished wood cabinet £4.80 carr., etc.
 35p each or 50p pair.



EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max. DC operation, complete with data. Price £1.50 each or 2 for £2.85 Printed Circuit Panels. 50p

UHF TV TUNERS

625 line receiver UHF transistorised tuners FM UK operation. Brand new. (Post/packing 25p each).
 TYPE C variable tuning £2.50
 TYPE B 4-button push-button (adjustable) £3.50

TAPE HEADS

Marriot XRSP/17 1/2 Track High	£2.50
Marriot XRSP/18 1/2 Track Med.	£3.50
Marriot XRSP/36 1/2 Track Med.	£5.00
Marriot XRSP/63 1/2 Track High	£1.75
Marriot Erase Heads for XRSP 17/18/36	
XES11 7	75p
Marriot BX1ZE 343	75p
R/RPI Record/Play 1/2 Track	45p
H/RP Single Track Rec/Play	35p
Bogen Type UL290 Erase	£1.50
Miniature Stereo Cassette Rec/Play	£2.25

CALCULATORS

Sinclair Cambridge Kit	£13.50
Sinclair Cambridge (Built)	£17.50
Sinclair Memory	£22.50
Sinclair Scientific	£26.95

DOSIEMETERS

0-5R	62p	} EACH PER DOZEN
0-50R	62p	
0-150R	62p	

HENRY'S HOME ENTERTAINMENT CENTRES

London
 354/6 Edgware Rd. W2 01-402 5854
 376/8 Edgware Rd. W2 01-723 2564
 372 Edgware Rd. W2 01-402 8140
 120 Shaftesbury Ave. W1 01-437 9692
 230 Tottenham Court Rd. W1 01-580 1785
 144 Burnt Oak B'way, Burnt Oak, Edgware 01-952 7402
 190/4 Station Rd., Harrow, Middlesex 01-863 7788
Out of Town
 256 Banbury Rd., Summertown, Oxford (0865) 53072
 55 Gloucester Rd., Bristol 7 (0272) 45791

PORTABLE RADIO Activity Counter Complete with Power Pack £9.97 pp £1

GRAVINER INFRA RED DETECTOR DESIGNED FOR HEAT OR LIGHT DETECTOR. CONTAINING 931A PHOTO MULTIPLIER & GK45 & NETWORK £3.50

AMTRON KITS AVAILABLE EX-STOCK SEND FOR FREE LISTS

JOSTY KITS AVAILABLE EX-STOCK SEND FOR FREE LISTS

INVERTOR KITS 15 WATT £5.20 pp 30p 40 WATT £6.80 pp 40p

P.P.9 BATTERY ELIMINATOR COMPLETE KITS OR PARTS INCLUDING P/C BOARDS £1.95 COMPLETE KIT

HENRY'S UK'S No. 1 FOR ELECTRONICS AND HI-FI

8% VAT TO BE ADDED TO ALL ORDERS VAT-UK ONLY

SUPPLIERS OF ELECTRONICS FOR OVER 30 YEARS

Henry's RADIO
 EDGWARE ROAD, W2

Electronic Centras
 404-406 Electronic Components & Equipment 01-402 8381
 309 PA-Disco-Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 303 Edgware Road, London W2 1BW

Hi-Fi and Electronics Centras Open 3 am - 6 pm

Prices correct at time of preparation. Subject to change without notice. + H.O.E